

OCTOBER  
1947  
35c

# RADIO NEWS

FORMERS CONDENSERS




RN-57-J60789-48  
LAURENCE THORSON  
DALLAS WIS

ELECTRONIC PARTS MERCHANDISED IN MODERN MODE
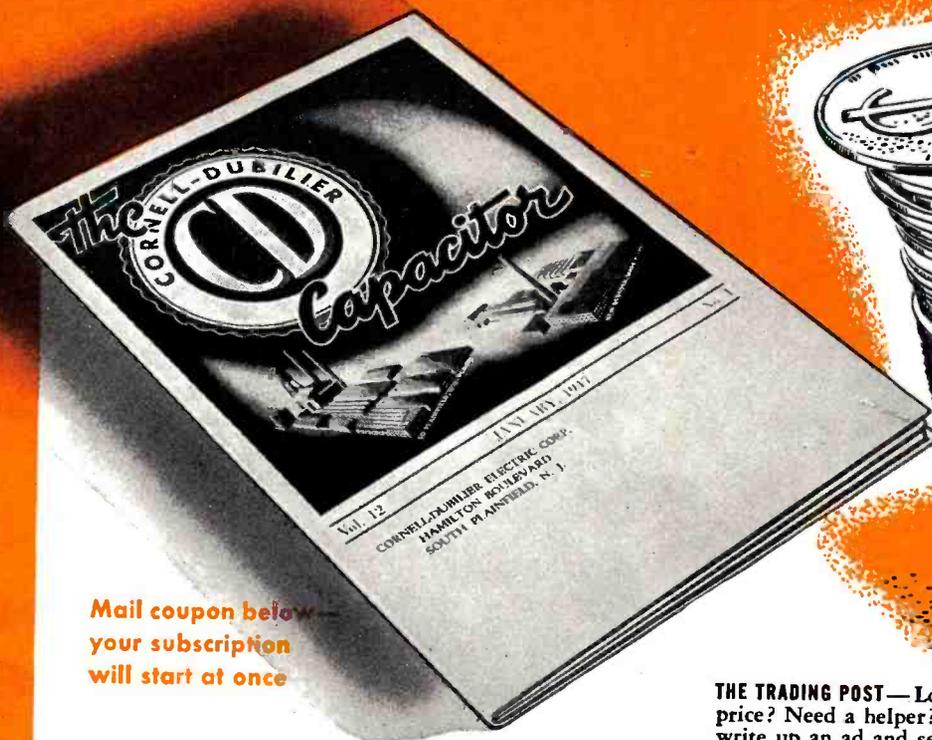
# Free to Servicemen...

this great source  
of money-making ideas



Mail coupon below—  
your subscription  
will start at once

Meet "The Capacitor"—the magazine that's published by Cornell-Dubilier solely to help servicemen speed up their work—build up their business.

It has no frills—it isn't cluttered up with complicated mathematics—and you could read it for years without learning how to build a crystal set. Instead its articles are meaty, down-to-earth—practical discussions of the problems every serviceman meets every day. Never before has there been such a great demand for helpful servicing ideas—and "The Capacitor" is C-D's answer to this demand.

Use "The Capacitor" to help build up your service business—as it has for thousands of other successful servicemen. *Don't wait—mail coupon NOW and your FREE subscription will start immediately.*

**THE TRADING POST**—Looking for a new 'scope at a bargain price? Need a helper? Have you anything to sell? If so, write up an ad and send it in to "The Trading Post"—the serviceman's clearing house—which appears every month in "The Capacitor." This feature alone may make "The Capacitor" worth many dollars to you.

**LATEST FM CIRCUITS**—"It works all right on AM but when I try to use FM all I get is a lot of noise." You'll be hearing that story more and more as the new FM jobs come on the market. Get set for them now by keeping up with the new FM circuits as they appear in "The Capacitor."

**"THE CAPACITOR IS EXCELLENT"**—"I received my first copy of 'The Capacitor' the other day and I want to tell you that I think it is excellent. The articles are very interesting and clearly written. You have my congratulations on a very fine magazine." Culled from the hundreds of letters received every week.

1910 1947



**CORNELL-DUBILIER**  
WORLD'S LARGEST MANUFACTURER OF  
**CAPACITORS**

MICA • DYKANOL  
PAPER • ELECTROLYTIC

CLIP COUPON—MAIL NOW


Cornell-Dubilier Electric Corporation Dept. RN-10  
South Plainfield, New Jersey

Please start my FREE subscription to "The Capacitor"  
at once.

Name.....

Address.....

City.....Zone.....State.....

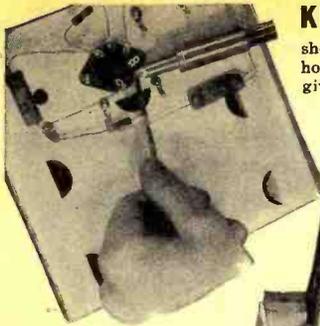

**KIT 1** (left) I send you Soldering Equipment and Radio Parts; show you how to do Radio Soldering; how to mount and connect Radio parts; give you practical experience.

**KIT 2** (left) Early in my course I show you how to build this N. R. I. Tester with parts I send. It soon helps you fix neighborhood Radios and earn EXTRA money in spare time.





**VETERANS**

You can get this training in your own home under G. I. Bill. Mail coupon for full details.

**Be a RADIO Technician**  
Learn by **PRACTICING** in Spare Time


with **BIG KITS** of **RADIO PARTS** I send you

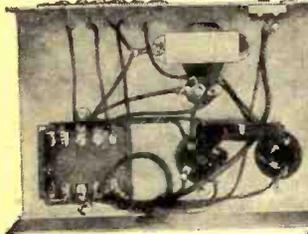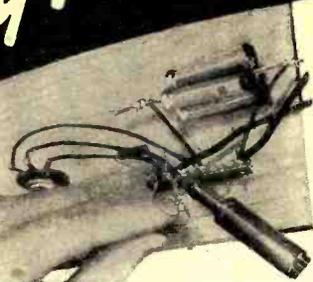**KIT 3** You get parts to build Radio Circuits; then test them; see how they work, learn how to design special circuits; how to locate and repair circuit defects.




**KIT 4** You get parts to build this Vacuum Tube Power Pack; make changes which give you experience with packs of many kinds; learn to correct power pack troubles.

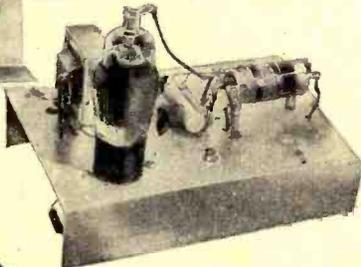**KIT 5** Building this A. M. Signal Generator gives you more valuable experience. It provides amplitude-modulated signals for many tests and experiments.



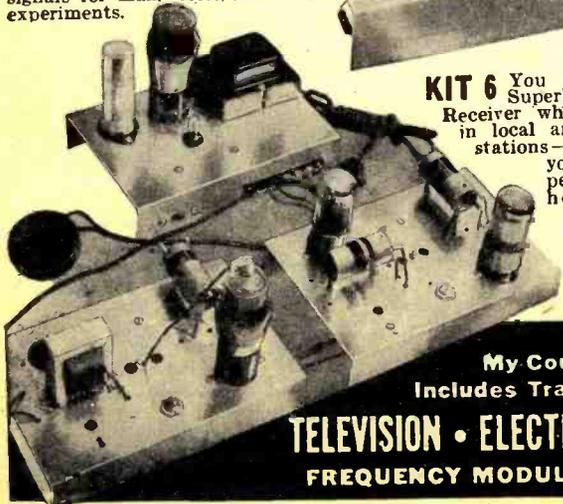**KIT 6** You build this Superheterodyne Receiver which brings in local and distant stations—and gives you more experience to help you win success in Radio.



My Course Includes Training in **TELEVISION • ELECTRONICS** FREQUENCY MODULATION

Do you want a good-pay job in the fast-growing Radio Industry—or your own Radio Shop? Mail the Coupon for a Sample Lesson and my 64-page book, "How to Be a Success in Radio-Television-Electronics," both FREE. See how I will train you at home—how you get practical Radio experience building, testing Radio circuits with **BIG KITS OF PARTS** I send!

**Many Beginners Soon Make Extra Money in Spare Time While Learning**

The day you enroll I start sending EXTRA MONEY manuals that show how to make EXTRA money fixing neighbors' Radios in spare time while still learning! It's probably easier to get started now than ever before, because the Radio Repair Business is booming. Trained Radio Technicians also find profitable opportunities in Police, Aviation, Marine Radio, Broadcasting, Radio Manufacturing, Public Address work. Think of even greater opportunities as Television, FM and Electronic devices become available to the public! Send for FREE books now!



**Find Out What NRI Can Do For You**

Mail Coupon for Sample Lesson and my FREE 64-page book. Read the details about my Course; letters from men I trained; see how quickly, easily you can get started. No obligation! Just MAIL COUPON NOW in envelope or paste on penny postal. J. E. SMITH, President, Dept. 7KR, National Radio Institute, Pioneer Home Study Radio School, Washington 9, D. C.

Our 33rd Year of Training Men for Success in Radio

Sample Lesson **FREE**  
64 Page Book


Mr. J. E. SMITH, President, Dept. 7KR  
National Radio Institute, Washington 9, D. C.

Mail me FREE, Sample Lesson and 64-page book about how to win success in Radio and Television—Electronics. (No salesman will call. Please write plainly.)

Name ..... Age.....

Address .....

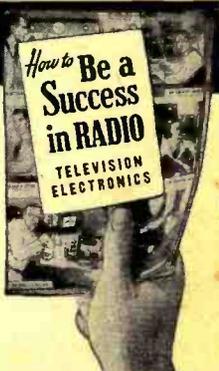
City ..... State.....  
(Please include Post Office zone number)



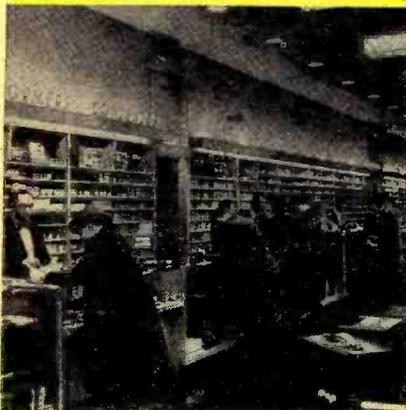**Approved for Training under GI Bill**

*Editor*  
**OLIVER READ, W9ETI**  
*Managing Editor*  
**WM. A. STOCKLIN**  
*Technical Editor*  
**H. S. RENNE, EX-W8PTS**  
*Associate Editors*  
**RAY FRANK, W9JU**  
**PAUL WENDEL**  
**FRED HAMLIN**  
**GAITHER LITRELL**  
**P. B. HOEFER**  
**C. M. SULLIVAN**  
*Staff Photographers*  
**ARTHUR E. HAUG**  
**WALTER STEINHARD**  
*Staff Artist*  
**R. S. KUPJACK**

*Advertising Manager*  
**L. L. OSTEN**  
*Midwestern Advertising Manager*  
**JOHN A. RONAN, JR.**  
*Art Director*  
**HERMAN R. BOLLIN**



COVER PHOTO: A section of Concord Radio Corporation's new sales room in Chicago. Complete stocks of radio parts, well displayed, are the secret of this distributor's merchandising success. Photo by Arthur E. Haug

*Chairman of the Board and Publisher*  
**WILLIAM B. ZIFF**  
*President*  
**B. G. DAVIS**  
*Secretary-Treasurer*  
**ARTHUR T. PULLEN**  
*Vice-Presidents*  
**GEORGE BERNER**  
*Advertising and Sales Director*  
**MICHAEL H. FROELICH**  
*Editorial Director*  
**H. J. MORGANROTH**  
*Production Director*  
**H. G. STRONG**  
*Circulation Director*

**BRANCH OFFICES**  
**NEW YORK (1)**  
 Empire State Bldg., WI 7-0400  
*Manager, Eastern Division*  
**CHARLES R. TIGHE**  
**LOS ANGELES (14)**  
 815 S. Hill St., TUcker 9213  
*Manager, Western Division*  
**WILLIAM L. PINNEY**  
**WASHINGTON (4)**  
 International Bldg., EXecutive 2502  
**TORONTO**  
 21 King Street, East  
**ASSOCIATED COMPANIES**  
 Ziff Davis, Ltd., Grampians Bldg.  
 Western Gate, London, England  
 Ziff-Davis-Patel, Ltd.  
 190 Hornby Road, Bombay, India

# RADIO NEWS

*First in radio-electronics*

Average Paid Circulation over 135,000

Reg. U. S. Pat. Off.

OCTOBER, 1947

## FOR THE SERVICEMAN-DEALER

A Simplified Signal Generator.....	H. G. Pratt, W8SEA	42
All-Wave Television-FM Antenna.....		49
Television Installation (Part 2).....	W. W. Waye	54
A Serviceman's Tube Tester.....	Fred J. Lingel	57
FM Receiver Alignment.....	Irving Abend	66
Practical Radio Course.....	Alfred A. Ghirardi	70
Increase Your Sales with Contests!.....	Zenn Kaufman	92

## FOR THE AMATEUR

Adapting the TBY-7 for Amateur Use.....	W. B. Ford, W6YT	39
10-Meter Mobile FM Transmitter.....	Ray Frank, W9JU	44
Easy-to-Build Modulation Monitor.....	C. M. Dibrell, W5BLW	50
A 600-watt Phone Transmitter.....	Rufus P. Turner, W1AY	61
Utility Locker Makes Deluxe Cabinet.....	Charles H. Welch, W5MHK	69

## OF GENERAL INTEREST

Television Camera Tubes.....	Henry J. Seitz	46
The Recording and Reproduction of Sound (Part 8).....	Oliver Read	51
Timing Chart for 78.26 R.P.M. Phonograph Records.....		60
Wireless Pre-Amp.....	Richard L. Parmenter	64

## DEPARTMENTS

For the Record.....	The Editor	8	RN Circuit Page.....	80
Spot Radio News.....	Fred Hamlin	16	What's New in Radio.....	84
Within the Industry.....		28	Technical Books.....	136
Short-Wave.....	K. R. Boord	68	Manufacturers' Literature.....	164
New Receivers for Fall Market....				192



COPYRIGHT 1947  
 ZIFF-DAVIS PUBLISHING COMPANY  
 185 North Wabash Ave., Chicago 1, Ill.  
 VOLUME 38 • NUMBER 4



Member  
 Audit Bureau of  
 Circulations

RADIO NEWS is published monthly by the Ziff-Davis Publishing Company, 185 N. Wabash Ave., Chicago 1, Ill. Subscription Rates: in U. S. and Canada \$4.00 (12 issues), single copies 35 cents; in Mexico, South and Central America, and U. S. Possessions, \$4.00 (12 issues); in British Empire, \$5.00 (12 issues)—all other foreign countries \$5.00 (12 issues). Subscribers should allow at least 2 weeks for change of address. All communications about subscriptions should be addressed to: Director of Circulation, 185 N. Wabash Ave., Chicago 1, Ill. Entered as second class matter March 9, 1938, at the Post Office, Chicago, Illinois, under the Act of March 3, 1879. Entered as second class matter at the Post Office Dept., Ottawa, Canada. Contributors should retain a copy of contributions and include return postage. Contributions will be handled with reasonable care but this magazine assumes no responsibility for their safety. Accepted material is subject to whatever revisions and by-line changes that are necessary. Payment made at our current rates, covers all authors', contributors' or contestants' rights, title, and interest in and to accepted material, including photos and drawings.

RADIO NEWS

"THE hottest ham performance ever at this price . . ." That's the verdict of amateurs who have had a chance to try Hallicrafters new Model SX-43.

This new member of the Hallicrafters line offers continuous coverage from 540 kilocycles to 55 megacycles and has an additional band from 88 to 108 megacycles. AM reception is provided on all bands, except band 6, CW on the four lower bands and FM on frequencies above 44 megacycles. In the band of 44 to 55 Mc., wide band FM or narrow band AM just right for narrow band FM reception is provided.

One stage of high gain tuned RF and a type 7F8 dual triode converter assure an exceptionally good signal-to-noise ratio. Image ratio on the AM channel on band 5 (44 to 55 Mc.) is excellent as the receiver is used as a double superheterodyne. The new Hallicrafters dual IF transformers provide a 455 kilocycle IF channel for operating frequencies below 44 megacycles and a 10.7 megacycle IF channel for the VHF bands. Two IF stages are used on the four lower bands and a third stage is added above 44 megacycles. Switching of IF frequencies is automatic. The separate electrical bandspread dial is calibrated for the amateur 3.5, 7, 14, and 28 megacycle bands.

Every important feature for excellent communications receiver performance is included.


## Model SX-43


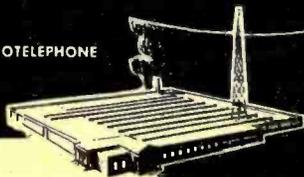
### FEATURES FOUND IN NO OTHER RECEIVER AT THIS PRICE

- ALL ESSENTIAL AMATEUR FREQUENCIES FROM 540 kc to 108 MC
- AM - FM - CW RECEPTION
- IN BAND OF 44 TO 55 MC: WIDE BAND FM OR NARROW BAND AM . . . JUST RIGHT FOR NARROW BAND FM RECEPTION
- CRYSTAL FILTER AND EXPANDING IF CHANNEL PROVIDE 4 VARIATIONS OF SELECTIVITY ON LOWER BANDS
- SERIES TYPE NOISE LIMITER
- TEMPERATURE COMPENSATION FOR FREEDOM FROM DRIFT
- PERMEABILITY ADJUSTED "MICROSET" INDUCTANCES IN THE RF CIRCUITS
- SEPARATE RF AND AF GAIN CONTROLS
- EXCEPTIONALLY GOOD SIGNAL-TO-NOISE RATIO
- SEPARATE ELECTRICAL BANDSPREAD CALIBRATED FOR THE AMATEUR 3.5, 7, 14 AND 28 Mc BANDS



BUILDERS OF *Skyphone* AVIATION RADIOTELEPHONE


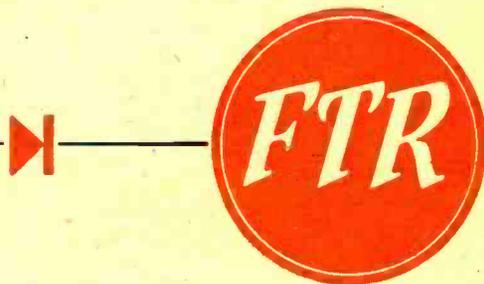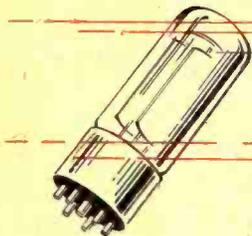
## hallicrafters RADIO

THE HALLICRAFTERS CO., MANUFACTURERS OF RADIO AND ELECTRONIC EQUIPMENT, CHICAGO 16, U. S. A.

Sole Hallicrafters Representatives in Canada: Rogers Majestic Limited, Toronto-Montreal



## STORY WITHOUT WORDS


...here's how it can boost *your* profits

AS SURELY AS the "gasoline buggy" replaced the horse-drawn carriage, the Miniature Selenium Rectifier—an original Federal development—is destined to take the place of the rectifier tube in AC-DC receivers. Already, more and more manufacturers are building it into their radio sets—and more and more maintenance shops are installing it in the sets they service.

What about *you*? Here is really a big chance for you to

make *extra money*—by *modernizing* AC-DC sets now using a rectifier tube—giving them faster starting, better all-around performance. And as new sets using the Miniature Rectifier as original equipment come to you for servicing, you'll want to be ready with replacements. It's your opportunity to be a *leader* by introducing this improvement *now*—by installing Federal's Miniature Selenium Rectifier in every AC-DC receiver you service.

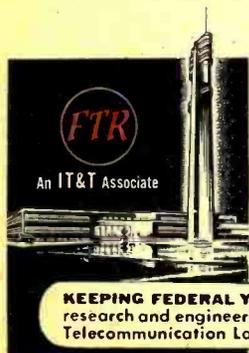Available through major jobbers from coast to coast—complete with detailed instructions.



KEEPING FEDERAL YEARS AHEAD... is IT&T's world-wide research and engineering organization, of which the Federal Telecommunication Laboratories, Nutley, N. J., is a unit.

### Federal Telephone and Radio Corporation

SELENIUM and INTELIN DIVISION, 1000 Passaic Ave., East Newark, New Jersey

In Canada: — Federal Electric Manufacturing Company, Ltd., Montreal.

Export Distributors: — International Standard Electric Corp., 67 Broad St., N.Y. C.



**I Put You to Work with Your Hands to LEARN RADIO!  
You Build Receivers! You Make Typical Defects Occur  
and Make Tests to Prove the Theory!**

**YOU GET  
8 BIG KITS OF RADIO  
PARTS & EQUIPMENT  
including  
2-BAND SUPER  
RECEIVER!  
and 16 RANGE METER  
FOR TESTING**

F. L. SPRAYBERRY, PRES-  
IDENT of the SPRAYBERRY  
ACADEMY OF RADIO. This  
is the man who directs  
your study. His years of  
experience and Radio  
"know-how" assure you of  
the finest in home Radio  
Training!

**LEARN RADIO  
to MAKE MONEY!**

**LOW COST TRAINING — EASY PAYMENT PLAN!**

**You Learn at Home How to  
Build and Test Dozens and  
Dozens of Circuits — Simple  
and Complex!**


**YOU DO  
OVER 175  
INSTRUCTIVE  
EXPERIMENTS**




**YOU BUILD  
ALL THESE TESTERS  
..... AND MORE!**



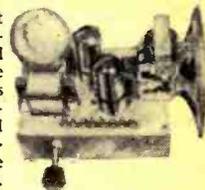
I give you a fine,  
moving-coil type  
Meter Instrument  
on Jewel Bearings  
— with parts for a  
complete Analyzer  
Circuit Continuity  
Tester. You learn  
how to check and  
correct Receiver  
defects with professional speed and  
accuracy.



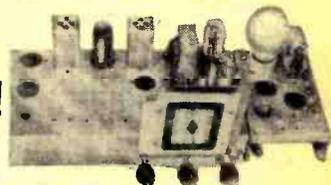You'll get  
valuable expe-  
rience and  
practice  
building this  
Signal Gen-  
erator and  
multi-  
purpose  
Tester. Makes a  
breeze out of fixing Radios and you  
don't have to spend money on ready-  
made Equipment.



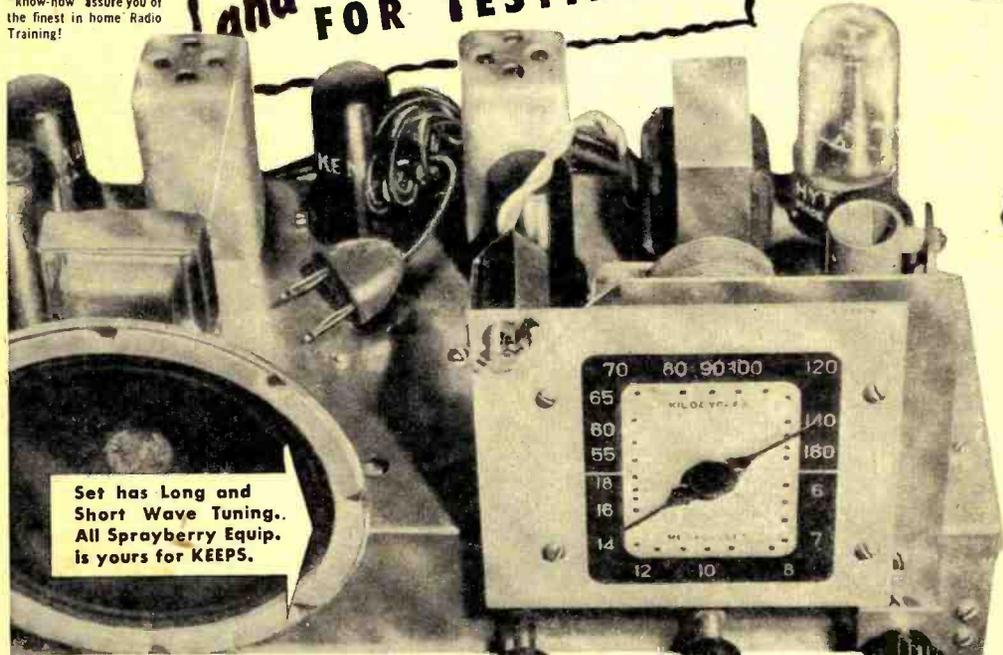Soldering, wiring, connecting Radio  
parts . . . building circuits with your  
own hands — you can't beat this  
method of learning. When you con-  
struct this Rectifier and Filter, Res-  
istor and Condenser Tester, etc., you  
get a really practical slant on Radio  
that leads to a money-making future.



**Set has Long and  
Short Wave Tuning.  
All Sprayberry Equip.  
is yours for KEEPS.**

**SPRAYBERRY HOME TRAINING is PLANNED to MAKE MONEY for you FAST!**

I train you with regular professional Radio Equip-  
ment. I tell you exactly what to do . . . how to do  
it. You handle Radio Parts, see them operate,  
learn what they're for. With the fine Kits I supply,  
you learn how to build Radio Circuits, construct  
your own Test Equipment. I'll show you how to  
cause typical Radio defects so you can watch and  
see how they act. You learn the latest methods for  
trouble-shooting and repair. All this adds up to

the finest kind of "bench" experience. And you get  
it right in your own home. In no time at all, you'll  
be ready for a business of your own or a good job  
in Radio, FM, Television,  
Radar, Industrial Elec-  
tronics, etc. Now's  
the time to get  
started!

**VETERANS!**

You Can Get  
Sprayberry  
Training  
At Home  
Under G.I. Bill.  
Mail Coupon  
For Full  
Details.

**SEND FOR MY  
VALUABLE  
FREE BOOKS!**

**"How To Read Radio Diagrams and Symbols"**

A wonderfully complete new book, which ex-  
plains in simple English how to read and  
understand any Radio Set Diagram. Includes  
translation of all Radio symbols. Send for this  
volume at once! It's free! With it I'll send  
you another Big Free Book, describing in  
detail my Radio Electronic Training!

**SPRAYBERRY ACADEMY OF RADIO**

F. L. Sprayberry, President  
Room 25107, Pueblo, Colorado

Please rush my FREE copies of "How to MAKE MONEY in RADIO, ELEC-  
TRONICS and TELEVISION" and "How to READ RADIO DIAGRAMS and  
SYMBOLS."

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

(Mail in envelope or paste on penny postcard)

# TRANSVISION

Scores Another  
**Great Scoop!**

The DeLuxe  
**7" TELEVISION  
KIT with a  
Complete FM RADIO**  
covering the entire FM Band  
(88 to 108 MC)



Now . . . build yourself a magnificent two-in-one receiver—**Television and FM Radio**—and save more than 50% on the comparative cost of a completed set.

Wire up the DeLuxe 7" Transvision Kit, install the FM Radio which comes with it and requires no assembly, and you have a receiver worth over \$400.00.

### Note These Outstanding Features:—

- You get the famous 7" Transvision Television Kit, plus—
- A superb high quality, high fidelity FM Radio which covers the entire FM Band, from 88 to 108 MC. Radio comes assembled ready to install.
- FM front end as well as the television front end are completely wired and tuned.
- You get ALL the parts, including front panel, specially designed FOLDED DIPOLE ANTENNA and 60 ft. of low-loss lead in cable.
- **NO TECHNICAL KNOWLEDGE REQUIRED** for assembly. No instruments required.
- As easy to assemble as the standard 7" Transvision Television Kit.
- DeLuxe 7" TRANSVISION TELEVISION KIT with FM RADIO RECEIVER. LIST \$199.00

**BEAUTIFUL FURNITURE FINISH  
CABINET LIST \$32.50**

### FM CONVERSION KIT

You can incorporate a complete FM radio into your present television receiver by means of the Transvision FM conversion kit . . . . . LIST **\$29.95**

If your kit already has FM sound, a conversion to FM radio will cost even less. Ask your distributor.

See your local distributor, or for further information write to:

**TRANSVISION, INC.** Dept.  
R. N.  
385 North Ave., New Rochelle, N. Y.

## For the RECORD.

BY THE EDITOR

**R**ADIOS for Everyone . . . Everywhere" is the dominant theme as the Third Annual National Radio Week (October 26-November 1) gets under way. Marking the 27th anniversary of radio broadcasting, the Third Annual observance of National Radio Week will be carried out under the joint sponsorship of the Radio Manufacturers Association (RMA) and the National Association of Broadcasters (NAB).

Of particular interest to our many thousands of radio servicemen readers, National Radio Week is a three-way cooperative combination designed to keep retail sales volume high, to increase radio listening audiences, and to maintain steady and full employment in the radio industry. National Radio Week will also climax the year-round "Radio-in-Every Room" campaign sponsored by RMA and endorsed by NAB, the object of which is to increase radio set ownership and radio listening by encouraging families to have radios available throughout the house and for each member of the family.

This important week will be observed by all branches of the radio industry as well as allied groups interested in increasing the listening audience. Radio dealers, broadcasters, and radio advertisers have the greatest stake in its success but many other groups will benefit from the national recognition accorded to radio broadcasting on its 27th birthday.

Dealers will be provided with promotion material, posters, streamers, etc., and will have ample stocks to display the newest radio receivers. Broadcasters will be given similar promotion materials plus special aids and suggestions for broadcasting during Radio Week. The networks and national radio sponsors are being asked to devise their own programs for Radio Week, using spot announcements, program tie-ins where practical, special programs, and other devices to point up radio's development during the past 27 years, its stature today, and its future potentialities.

A number of special events are being developed by the RMA-NAB Joint Committee which will include a nationwide contest for high school students in which "The Voice of Democracy" will be chosen competitively in local, regional, and national contests. Another contest for women listeners will be conducted by the Association

of Women Broadcasters with the cooperation of RMA whose members will donate the prizes. Other special events, such as local and national forums, may be included.

Promotion material soon to be available to broadcasters, radio dealers, and others interested in actively supporting National Radio Week includes a 32-page, two-color workbook giving background and suggestions for cooperative observances, posters, window streamers, radio scripts, advertising copy, etc. A special 8-page folder, which forms a part of the workbook, will be made available separately to retail organizations for distribution to their members.

Radio servicemen have at their fingertips a golden opportunity to cash in on National Radio Week. Shop work should be kept at a minimum in order that time will be available to make calls on as many customers as possible. When you do drop by for a visit, don't stress any particular sales campaign, rather inquire as to the performance of all sets in the household. Take advantage of this opportunity to personally tune in several stations on each set and point out salient features of the new FM-AM television sets. And be sure to leave your business card.

**T**HE radio amateurs, particularly the "oldtimers," who have seen radio grow from a mediocre beginning into one of the foremost industries of our day, can well remember the early days of broadcasting when Doc Conrad and Doc De Forest gave birth to this "electronic era." No one has contributed more than the American amateur to the rapid growth of AM, FM, TV, and electronics. As we celebrate National Radio Week, we should not forget the contributions made by these men. As in the past, the future holds equal opportunity for today's amateur. From his attic and basement will come many more new ideas and developments.

**R**ADIO NEWS is proud of its long association with radio broadcasting and we point with pardonable pride to the fact that we have already passed our 27th anniversary of service to radio servicemen, amateurs, and the industry itself.

We welcome this opportunity to join in the celebration of National Radio Week. . . . .O.R.

**RADIO NEWS**

# There's Only One Complete Radio Buying Guide!

It's **ALLIED'S 164-PAGE**  
**RADIO CATALOG** — *Get It!*

**FREE**




## Everything in Radio at Lowest Prices!

Get your copy of this big COMPLETE book NOW! It shows everything you need and want in radio and electronic equipment—over 10,000 items—and all at real money-saving prices. You'll find new, ultra-modern radios, phonos, recorders—high quality test equipment of all types—complete PA and Sound Equipment—new, powerful Communications

Receivers—plus thousands of parts, tubes, tools, books, diagrams, kits . . . everything for the experimenter, builder, serviceman, ham and short-wave listener. Send today for your copy of Radio's biggest and best Buying Guide. Make ALLIED your Radio Headquarters—it's the established, dependable supply source for America's radio men.
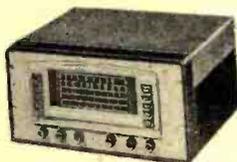
### New Communications Receivers—Earliest Delivery from ALLIED



**HALLICRAFTERS S-47**

New FM-AM receiver. AM reception 535-1720 Kc. and 5.9-18.2 Mc.; FM reception 88-108 Mc. 14 tubes plus rectifier. Bandsread from 9-12 Mc. and 15-18 Mc. Calibrated slide-rule dials; dual tone controls. 500 ohm output. Phono input socket; push-button channel selection; response essentially flat from 30-7500 cps AM; 30-15,000 cps FM. 110 v. AC. 12 watts power output. In cabinet, **NET... \$200.00**  
Chassis only, **NET... \$189.50**



**NATIONAL HRO-7**

Newest model in the world-famous, dependable HRO line—a remarkable performer under any receiving conditions. Features modern styling, voltage regulated 6C4 oscillator, double-action type variable noise limiter, tone control, accessory power take-off, separate power supply for 110-220 v. AC operation. Complete with tubes and power supply. **NET... \$299.36**



**HALLICRAFTERS SX-43**

The new SX-43 gives you more value—greater performance, broader frequency coverage (550 Kc. to 55 Mc. and 88-108 Mc.)—a fine investment in the medium price range. AM-FM-CW reception, Crystal filter, calibrated main and bandsread dials, variable tone control, precision engineered for custom-built performance! This is a real, big-league, all-around Communications Receiver for Ham or Short Wave Listener. **NET... \$169.50**

#### Other Communications Receivers

National NC-173 & Spkr. \$189.50	Hammarlund HQ-129X & Speaker..... \$173.25
National NC-2-40D..... 225.00	RME-84..... 98.70
National NC-46 & Spkr.. 107.40	RME-45 & Speaker..... 198.70
Hallicrafters SX-42..... 275.00	RME VHF-152 Converter. 86.60
Hallicrafters S-38..... 47.50	RME DB-22 Preselector... 60.00
Hallicrafters S-40A..... 89.50	
Hammarlund SPC-400X & Speaker..... 347.25	

Net FOB Chicago. Prices subject to change without notice

#### TIME PAYMENTS Trade-Ins Accepted

#### RADIO'S LEADING BUYING GUIDE

**FREE**



**ALLIED RADIO CORP.**  
833 W. Jackson Blvd., Dept. 1-KK-7  
Chicago 7, Illinois

- Send FREE 164-Page ALLIED CATALOG
- Enter order for.....
- Enclosed \$.....  Full Payment  
 Part Payment (Balance C.O.D.)

Send full information on Communications Receivers and Time Payment Plan, without obligation.

Name.....

Address.....

City..... Zone..... State.....

**ALLIED RADIO**  
Everything in Radio and Electronics



**5 WORDS** that assure **ACCURACY, DEPENDABILITY** and **VALUE**  
in all **SILVER** test instruments

You . . . and every serious service technician . . . have long dreamed of your shop equipped with the same caliber of laboratory instruments found in the factories making the radios you must service. Today's complex AM, FM and Television receivers can't be efficiently serviced by anything less.

Under war pressure McMurdo Silver devised new techniques to lift the manufacture of laboratory-type instruments out of the costly model-shop. He discovered how to put them on the low-cost, high-volume production line. The result is instruments of laboratory precision, accuracy, dependability . . . at prices far below what you'd expect to pay. These are the same identical **Laboratory Caliber Electronic Test Instruments** the big manufacturers, universities and the government select.

Can you afford less than the best — when the best costs you less?

**MODEL 906 FM/AM SIGNAL GENERATOR:** 8 ranges calibrated  $\pm 1\%$  accurate, 90 kc. thru 210 mc. 0-100% variable 400V<sub>AM</sub>; 0-500 kc. variable FM sweep built-in. Metered microvolts; variable 0-1 volt. Strays lower than \$500 laboratory generators. Only \$99.50 net.

**"VOMAX" UNIVERSAL V.T.V.M.:** The overwhelming choice of experts. 51 ranges, d.c., a.c., a.f., i.f., r.f., current, db., and resistance. Visual signal tracing to 500 mc. New 5" pencil-thin flexible r.f. probe. Only \$59.85 net.

**MODEL 904 CONDENSER/RESISTANCE TESTER:** Measures accurately  $\frac{1}{4}$  mmfd. thru 1,000 mfd.;  $\frac{1}{4}$  thru 1,000 meg $\Omega$ . Internal 0-500 V. variable d.c. polarizing voltage. Measures condensers with rated d.c. volts applied. Only \$49.90 net.

**MODEL 905 "SPARX" SIGNAL TRACER:** Visual and audible tracing; also tests phono pickups, microphones, speakers, PA amplifiers. Is your shop test-speaker, too. 20V thru 200 mc.; PM speaker; mains-insulated transformer power supply. Only \$39.90 net.

OVER 36 YEARS OF RADIO ENGINEERING ACHIEVEMENT

*McMurdo Silver Co., Inc.*

1249 MAIN ST., HARTFORD 3 CONNECTICUT

SEND FOR COMPLETE CATALOG. See these and Silver communication transmitters, receivers, "Micro-match", Xtal-controlled VFO, pre-tuned freq. multiplier at your jobber.

**NEW! A complete  
portable recording console  
THE PRESTO 90-A**

Here in one easily portable unit is complete amplifier equipment to produce recordings on remote assignments that equal the best recordings in permanent installations.

Presto 90-A has 3 low-level input channels with mixers, master gain control and variable high and low frequency equalizers.



It has four fixed characteristics: flat between 30 and 15,000 CPS... NAB recording... 78 r. p. m. recording... playback complimenting NAB recording.

Other features include: line input and output, V. U. meter, switching for one or two recorders, over-all gain—115 db, power—10 watts undistorted.

In quality of parts and workmanship and in flexibility of operation, the Presto 90-A is the equal of the finest studio equipment.

Presto engineers are proud to present this new recording console as a forward step in recording equipment.

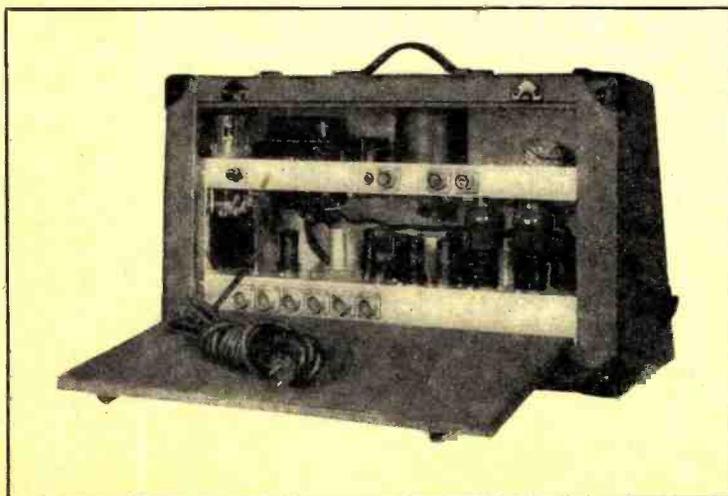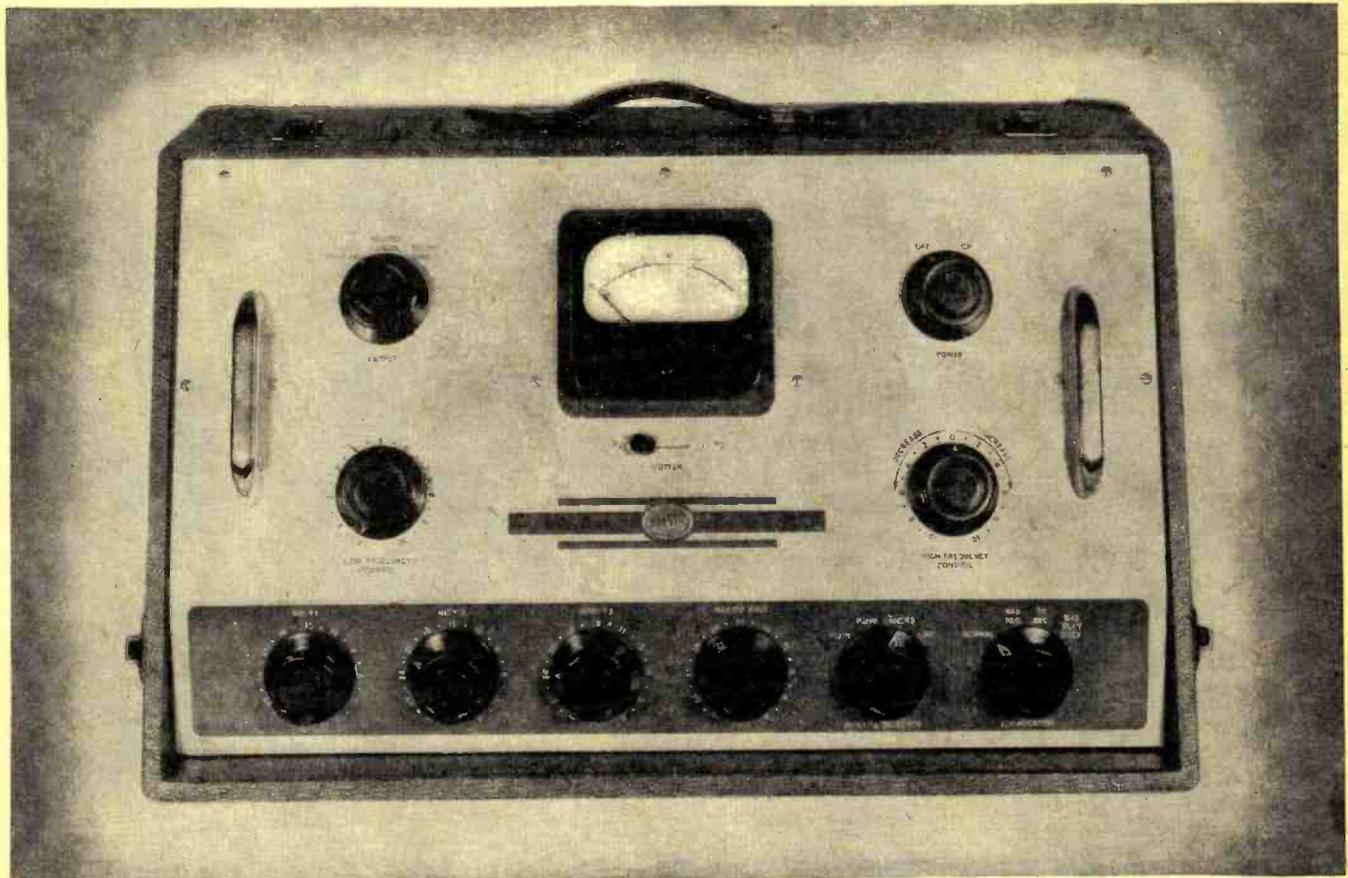*Immediate delivery can be made from stock.*



**PRESTO**


**RECORDING CORPORATION**

244 WEST 55TH STREET, NEW YORK 19, N. Y.

Walter P. Downs, Ltd., in Canada

**FREE!** Presto will send you free of charge a complete bibliography and digest of all technical and engineering articles on disc recording published since 1921. Send us a post card today.

# A Sign of Successful Servicing

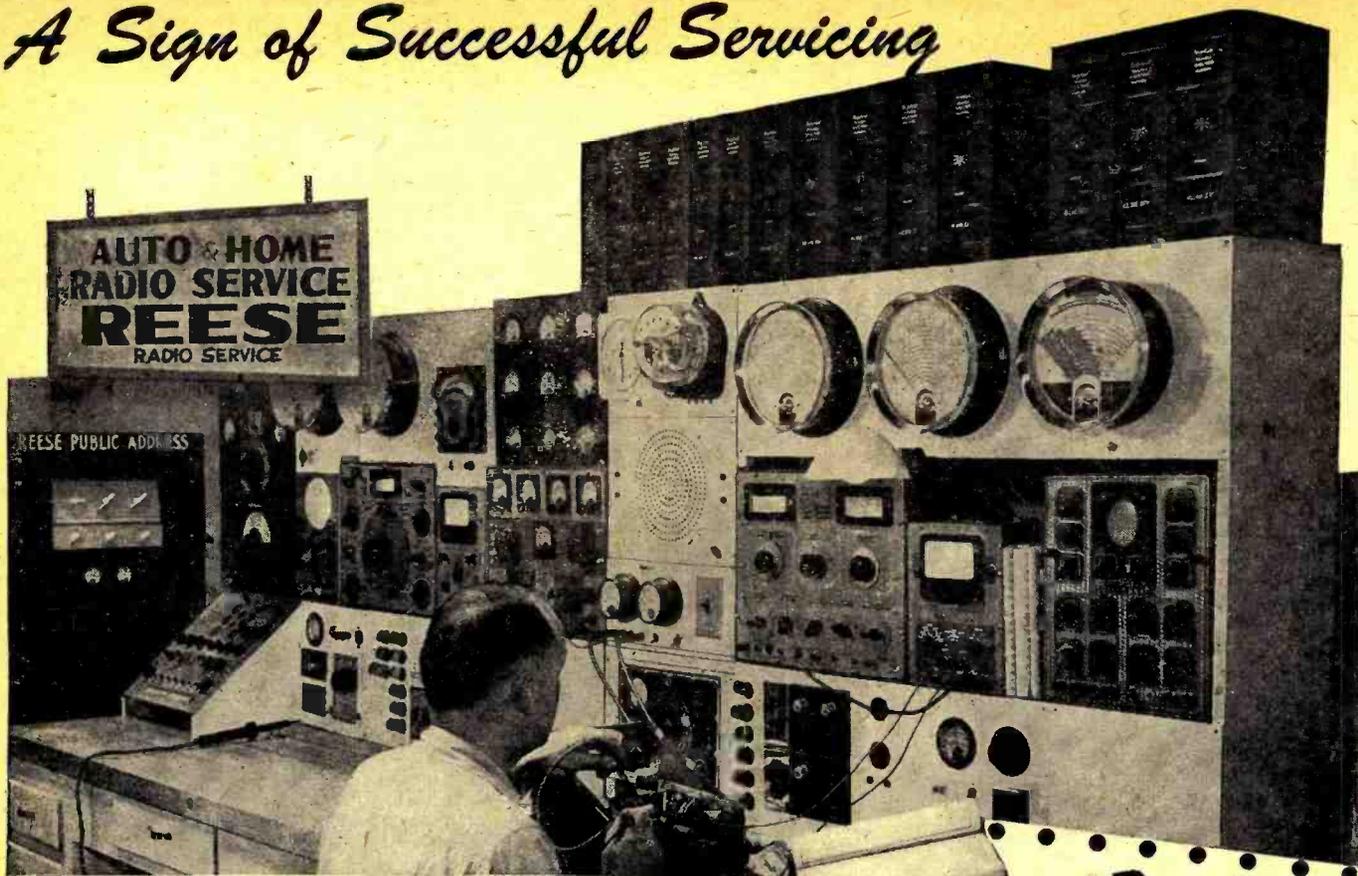

## Reese has all Fifteen RIDER MANUALS (and Volume XVI on order)

THE servicing shop of Francis Reese in Olean, N. Y. has been the subject of several success stories recently published in radio magazines. Shops so featured are significantly distinguished by a better-than-average profit and a complete set of Rider Manuals. Thus, at Reese you will find all volumes, kept conveniently handy for ready reference. For, no other single source of information supplies the essential data contained in Rider Manuals and nowhere but in the first fourteen volumes can you find the material you must have to service 80% of the receivers now in American homes. (Those issued from 1920 to 1942.)

To those shops repairing any and all makes of receivers, sets of all ages, this pre-war data is absolutely essential for profitable operation.

—And, Rider Manual data is reliable, the OFFICIAL AUTHORIZED servicing data right from the service departments of the companies that make the sets. No one knows better than the

manufacturer what procedures are best for his products. This is the basis for the authority and success of Rider Manuals.

Volume XVI will be at your jobbers in October; order it today. Remember, Rider Manuals are investments; they keep pouring out profits for you. Copies of Volume I, bought over seventeen years ago, are still benefiting their owners. So, be sure your shop has the sign of successful servicing—be sure it has all sixteen Rider Manuals.


### RIDER MANUALS—16 VOLUMES

Volume XVI.....	\$ 6.60
Volume XV.....	18.00
Volumes XIV to VII (ea. vol.)	15.00
Volume VI.....	11.00
Abridged Manuals I to V (one volume).....	17.50
MASTER INDEX, covering all Rider Manuals except Vol. XVI, which has its own index	1.50
Record Changers and Recorders (a manual).....	9.00

JOHN F. RIDER, PUBLISHER, Inc., 404 Fourth Avenue, New York 16  
Export Agent: Rocke International Corp. 13 E. 40th St., N.Y.C. Cable ARLAB

## RIDER MANUALS MEAN SUCCESSFUL SERVICING

*Just Out!*  
**VOL. XVI**

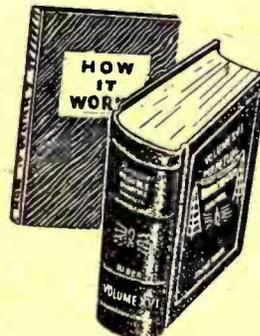

**RIDER  
MANUAL**  
*At your jobbers  
in October*  
**768 Pages**  
**PLUS SEPARATE  
'HOW IT WORKS'  
BOOK**  
**\$6.60**

During "Seventeen Years of Continuing Service to the Servicing Industry" we have been anticipating its needs. So, because of the present high rate of receiver production, Rider Manuals are being issued three times a year, to give you complete, authoritative servicing data at the earliest necessary date. And, at the minimum investment; Vol. XVI is less than a cent a page. The binding is the same sturdy, custom-made, loose-leaf binder that matches your present Rider Manuals. And, the contents are the usual high standard, supplemented with "clarified-schematics" on multi-wave band sets and a separate "How It Works" book explaining the kinks of the newer receivers. We are proud to publish Vol. XVI, you will find it profitable to possess.

**PLACE YOUR ORDER TODAY**



In the ST-202-A, STANCOR engineers have pooled valuable ideas gleaned from years of pre-war amateur kit design as well as war-time transmitter production to create a versatile combination of features which every amateur desires.

Integrated in a compact unit of pleasing appearance, a transmitter has evolved incorporating substantial power output, separate high and low voltage power supplies, a highly novel, but simple, exciter band switching arrangement and extreme ease of adjustment and operation.

Every consideration was given to the ultimate user of this piece of equipment . . . the amateur; that is why a choice is given of several different R. F. output tubes . . . that is why the circuit design is straightforward and reliable . . . that is why the ST-202-A is properly priced.

See your STANCOR dealer for the ST-202-A descriptive bulletin.

Amateur net price of ST-202-A transmitter, less accessories . . . . . \$92<sup>80</sup>

- 100-125 WATTS INPUT TO FINAL AMPLIFIER.
- COVERS ALL AMATEUR BANDS BETWEEN 3.5 AND 30 MCS.
- THREE STAGE R. F. CIRCUIT.
- BAND SWITCHING OF EXCITER STAGES.
- ONLY TWO TUNING CONTROLS (EXCITER AND AMPLIFIER).
- SELECTION OF SIX CRYSTAL POSITIONS.
- ADJUSTABLE LINK OUTPUT CIRCUIT.
- TWO SEPARATE POWER SUPPLIES INCLUDED.
- EASE OF CONSTRUCTION (CABLED WIRING HARNESS SUPPLIED)
- SMALL SIZE—APPROXIMATELY 14" x 13" x 9".
- PROVISIONS FOR USE WITH AM OR FM MODULATOR.
- PRICED RIGHT.

SEE YOUR AUTHORIZED STANCOR DEALER FOR DISCRIPTIVE BULLETIN



**STANDARD TRANSFORMER CORPORATION**  
ELSTON, KEDZIE AND ADDISON • CHICAGO 18, ILLINOIS, U. S. A.

Meets **EVERY** Testing Requirement **BETTER**

# NEW model 3413 ...LEVER SWITCHING... tube tester



**THIS INGENUOUS  
LEVER SWITCHING**

*"Pictures your circuit"*

**FAST • SIMPLE • FLEXIBLE**

Provides individual  
control of each  
tube element


With the new Model 3413 you can make your settings instantly—just snap the switch up or down. You actually "picture" the circuit. Usually not more than five of the ten lever switches need be set, yet you have individual control of each tube element. Many other convenient features make Model 3413 the buy of its field—such as the handy, built-in SPEED-ROLL tube chart, the larger easy-reading meter, the handsome new case with streamlined design. For either counter or portable use you will find Model 3413 a quality-packed tester that you'll be proud to own. Write today. Address Dept. N107.


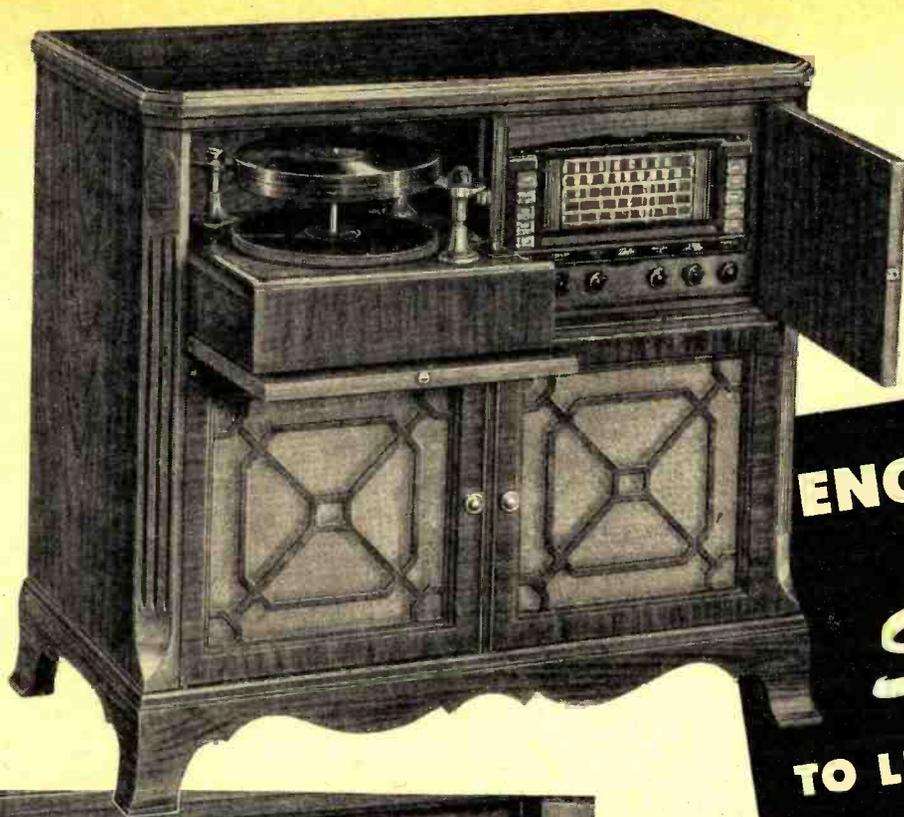
# Triplet



**ELECTRICAL INSTRUMENT CO. BLUFFTON, OHIO  
RADIO NEWS**



**ENGINEERED**  
AND  
*Styled*  
**TO LEAD THE FIELD!**



**PUSH-BUTTON TUNING ON BOTH AM AND FM!**  
This is only one of the many features that put the new Delco Combination ahead of the field. With 14 tubes, plus rectifier, this Combination also provides three short-wave bands and a record player that handles fourteen 10-inch or ten 12-inch records, with automatic shut-off.

## **DELCO RADIO** **A GENERAL MOTORS PRODUCT**

*Delco radios are distributed nationally by United Motors Service. See your United Motors distributor about the Delcoradio line.*



October, 1947

# *The New* **DELCO RADIO** *Combination*

**STYLE-WISE** and performance-wise, the new Delco Combination sets entirely new standards of radio value!

Its advanced engineering is apparent in such features as the 15-inch speaker for finer reproduction . . . the 24 different base and treble combinations . . . the ball-bearing roller mechanism for the phonograph . . . the precision-designed selector blades that prevent record-chipping . . . the lightweight tone arm with *jeweled-point* pick-up . . . and many more.

Its superb styling is evident in the graceful lines and exquisite workmanship of the 18th-Century cabinets. Two models are available—R-1251 in walnut, and R-1252 in mahogany—both furniture pieces of authentic distinction.

To see and hear *the best of all that's new in radio*, ask your United Motors Service distributor to demonstrate the new Delco Radio Combination and other popular models.

All the Science of  
**BASIC RADIO-  
ELECTRONICS**  
in one 3½ lb. book

**ONLY  
\$5**

Complete

**RADIO  
PHYSICS  
COURSE**

ALFRED A. GHIRARDI

**WRITTEN FOR  
BEGINNERS**



**36 COURSES IN ONE**

If this big 972-page Book were broken into monthly lessons and sold as a "course" you'd regard it as a bargain at \$50 or more!



A. A. Ghirardi's famous 972-page, 3½ lb. **RADIO PHYSICS COURSE** book with its 500 illustrations and 856 Self-Test Review Questions can teach you basic Radio-Electronics quicker, easier and at far less cost

**START NOW!**

than you may have thought possible! It has given more people their start in Radio than any other! It is used more for home study and was more widely used in U. S. Army Signal Corps and Navy war-time training programs than any other book of its type!

**LEARN IN A FEW WEEKS!**

**RADIO PHYSICS COURSE** is written for beginners who want to learn at home in spare time. Many who never even studied a circuit diagram before have completed it in a few weeks. Every basic subject is fully covered. Nothing is omitted. You'll be pleased how quickly it has you understanding subjects that other books and courses make seem too complicated. Send coupon today! Our **5-DAY MONEY-BACK GUARANTEE** protects you absolutely.

**"Better than a \$150 Course!"**

"I had already taken a \$150 radio course," writes Gerard Champagne of Montreal, "but since reading **RADIO PHYSICS COURSE**, I put the other one away. Ghirardi's is the book I need because it teaches so clearly!"

**NO RISK COUPON mail today**

Dept. RN-107, Murray Hill Books, Inc.  
232 Madison Ave., New York 16, N. Y.

Enclosed find \$5 (\$5.50 foreign) for a copy of Ghirardi's 972-page **RADIO PHYSICS COURSE** book; or  send C.O.D. for \$5 plus postage (no foreign C.O.D.'s). In either event, if not satisfied, it is understood I may return book in 5 days for complete refund of my money.

Name .....

Address .....

City & Dist. No. .... State .....

**YOU'LL NEVER GO WRONG  
on a GHIRARDI BOOK!**

*Spot Radio News*

★ Presenting latest information on the Radio Industry.

By **FRED HAMLIN**

Washington Editor, RADIO NEWS

**SCHOOL BELLS** are ringing over the air this year more numerous and frequently than ever before, according to a survey made as this went to press. And on the heels of this comes word of a survey into the future by the FCC indicating that radio in education is to stay. Twenty-three states reported active interest in establishing state-wide FM educational networks. Plans have already reached the legislative stage in California, Pennsylvania, South Carolina, Virginia, and Wisconsin, and planning committees are active in Georgia, Illinois, Kentucky, Louisiana, Michigan, and Texas. Planning is also under way in Indiana, Maryland, Montana, and New Jersey. A score of other commonwealths have expressed active interest.

**FCC IS HAPPY** about the whole thing, which culminates their encouragement of educational radio begun in 1938. First FM "school" station went on the air as early as May, 1939, run by the New York City Board of Education. War knocked out further progress in the field. Comeback was slow, but as of this summer, six educational FM's held regular licenses, 32 building permits were outstanding, and eight applications were pending. . . . Radio education is not, however, brand new—there were 171 licenses in the field as early as 1925 and within ten years after that, more than a hundred others were added. Most of these were universities, all standard AM's. They're also still going strong.

**SPEAKING OF** radio education and history, we're tempted to turn the column this time into a book review on what will probably be the best buy in radio literature during the fall season. It's called "Radio—A Public Primer" and was written by George O. Gillingham, public relations head of FCC. Lest anybody think we are splitting royalties with Mr. G. on his tome, it should be added that no royalties are due the author. He wrote it for the government, and the Government Printing Office, Washington, D. C., will send you a copy on request after the publication date—sometime before Nov. 1—for the handsome sum of (about) ten cents. Final price had not been set as this went to press. . . . The FCC pamphlet is actually a new edition of the same thing, written by Gillingham when he came to FCC in

1939 from TVA, where he was a Washington press man. Subsequently he went to war for five years, winding up as a lieutenant colonel in the chemical warfare service. Returning, he found his 1939 version of the "Primer" dated, and, between answering phones, he has revised it.

**BEST THINGS** about the primer are that it is singularly free of gobbletygook, a language designed to be so filled with long words that even the guy who wrote it can't make out the meaning; and that it swings clear around the radio circuit, giving brief, clear glimpses of what the other half of the radio industry is doing. We found it full of tasty morsels of radio history, news, and believe-it-or-nots, some of which you may have forgotten or (like us) never knew. For instance: "Radio" in its present-day sense is an American word, introduced by the Navy in 1912 as "radiotelegraphy." The long end of it was later dropped by the Americans, although the British still frown on the contraction.

First radio crooner was Enrico Caruso. De Forest had him on the air in 1910.

Attempts were made to organize a fully-authorized Federal radio bureau as early as 1911, but radio was a governmental stepchild until the Communications Act of 1934, which created the FCC.

The AM broadcast band is only one/thirty-thousandth of the entire known radio spectrum, which extends from 10 to 30 million kc.

It took nearly ten years for F(requency) M(odulation) to get to first base. A healthy experiment in the early 1930's, it didn't get an okay for commercial operation from FCC until 1941.

Is there such a thing as a radio station operating in the U. S. without a license? Yup. Matter of fact, all government radio stations are exempt from licensing.

The largest single radio group today licensed by the Commission is hams. Aviation is second, with some 17,000 airborne stations and 1100 on the ground.


**THE LAW**, according to the FCC Primer, has pioneered in radio. In 1916, New York City had a station, KUVS, to communicate with police boats in the harbor. Pennsylvania

**RADIO NEWS**

Now IN YOUR OWN HOME Learn
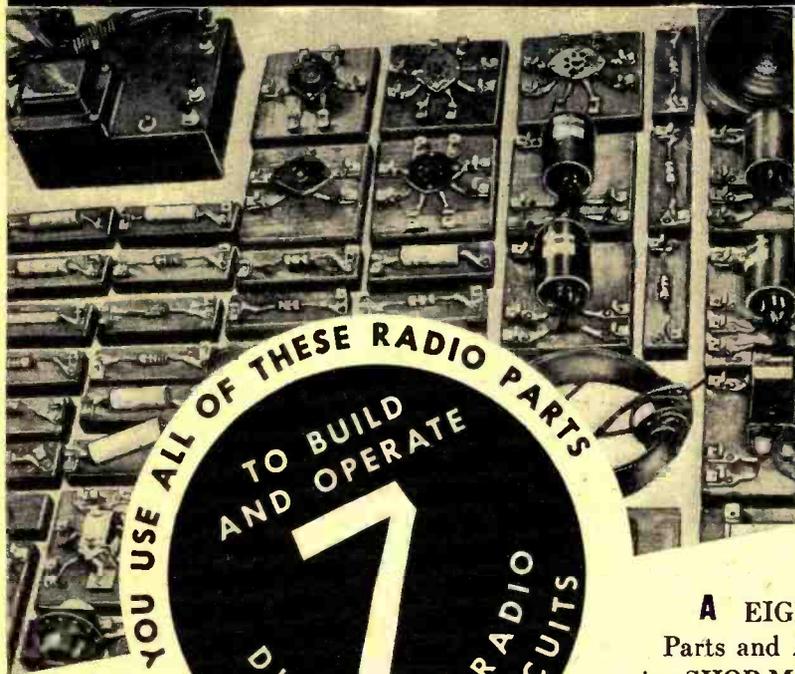
# RADIO ELECTRONICS

The Practical  
"HOME-TESTED"  
Modern "A-B-C" Way



YOU USE ALL OF THESE RADIO PARTS  
TO BUILD AND OPERATE  
**7**  
DIFFERENT RADIO RECEIVING CIRCUITS

WITH THE HELP OF

**A** EIGHT Big Kits of Actual "Learn-by-Doing" Radio Parts and Assemblies with which you make 133 fascinating SHOP METHOD EXPERIMENTS in your own home! Imagine building 7 different Radio Receivers that operate!

**B** A 16 mm Home Movie Projector and Twelve Reels of "Learn-by-Seeing" Home Movie Films . . . for picture-clear, fast understanding of Radio Fundamentals!

**C** Modern, well-illustrated, Loose-leaf Lessons, prepared in clear, simple, understandable language . . . to guide you throughout your training!

## NO PREVIOUS RADIO OR ELECTRICAL EXPERIENCE NECESSARY

DeForest's Training, Inc. provides every major home study aid to help you learn Radio-Electronics rapidly and thoroughly . . . to give you the experience and confidence needed for a responsible, Good-Pay Job, or to Start a Business of Your Own! Here is a REAL opportunity field for YOU . . . when you are a trained Radio-Electronics man! Just think of the tremendously exciting future ahead of FM Radio, Aviation and Broadcast Radio, Sound Motion Picture Equipment, Servicing and Sales of Radio Equipment, etc. Put yourself in this picture . . . See how you can benefit from a PRACTICAL training in this fascinating work! Think, too, of the coming possibilities ahead of Radar, Facsimile and Television. Send TODAY for the interesting, opportunity-revealing book, "Victory for You!" See how others probably no more talented or ambitious than you, have advanced in earning power after this training . . . how YOU can do it too! Mail the coupon NOW!

INCLUDING:

1. Simple Receiver
2. Two Tube Receiver
3. Tuned Radio-Frequency Receiver
4. Short Wave Receiver
5. Aviation Band Receiver
6. 4-Tube Superheterodyne
7. 5-Tube Superheterodyne with Magic Tuning Eye

... PLUS SCORES OF OTHER FASCINATING, INSTRUCTIVE RADIO-ELECTRONIC EXPERIMENTS

THEN GET THE HELP OF OUR EFFECTIVE EMPLOYMENT SERVICE

16 MM MOVIE PROJECTOR




YOU USE "LEARN-BY-SEEING" MOVIES

DEFOREST'S TRAINING, INC. INCLUDES INSTRUCTION IN MOTION PICTURE SOUND EQUIPMENT, FM RADIO AND TELEVISION . . . RESIDENTIAL TRAINING IN OUR MODERN CHICAGO LABORATORIES ALSO AVAILABLE—ASK US FOR INFORMATION!
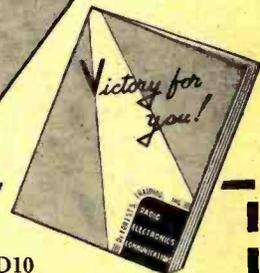
### VETERANS!

Big things are happening at DeForest's Training, Inc. for veterans! See how you can prepare yourself WITHOUT COST for a GOOD JOB or a BUSINESS OF YOUR OWN in the vast Radio-Electronic opportunity field.



E. B. DEVRY, President  
DEFOREST'S TRAINING, INC.  
2535-41 North Ashland Ave., Dept. RN-D10  
Chicago 14, Illinois, U.S.A.

Send FREE "VICTORY FOR YOU!" BOOK, showing how I may make my start in Radio Electronics.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

If under 16, check here for special information.

If a discharged Veteran of World War II, check here.

**DeFOREST'S TRAINING, INC.**  
CHICAGO 14, ILLINOIS

October, 1947

17



**LABOR has a holiday from transformer service, when the installations are Merit-Made. The Merit "know how" in design and construction is summed up in MERIT QUALITY.**

**EXPORT DEPARTMENT:**  
 1607 Howard Street, CHICAGO 26, U. S. A.  
 Cable Address: MERIT

**MERIT COIL & TRANSFORMER CORP.**

TELEPHONE  
 4427 North Clark St. Long Beach 6311 CHICAGO 40, ILL.

**SPOT RADIO NEWS**

was the first to have a state police radio system, in 1923. Michigan had the first radio patrol automobiles. Detroit, incidentally, was responsible for a fad in early broadcasting, when its police asked for a station designation KOP. Other nifties: WGN for "World's Greatest Newspaper," Chicago Tribune tower; WACO for guess-where in Texas, and Miami Beach's WIOD for "Wonderful Isle of Dreams." . . . But FCC is careful to add that special designations cannot be handed out these days. You take what's on the top of the list. You can't even take over a designation from a pal or your father, because under present rules a vacated call must be kept inactive for five years to avoid confusion. . . . Hams, FCC adds, have done an outstanding job of cherishing call letters—"gravestones even bear beloved call signals." They add that "perhaps the outstanding example of a deceased's call being perpetuated is the case of WIAW. For many years it was held by Hiram Percy Maxim, the inventor, and remains as a memorial in identifying the West Hartford, Conn., headquarters station of the great amateur station which he founded—The American Radio Relay League."

**RADIO BEING WHAT IT IS,** FCC is busy as ever, latest policing activities involving so-called "ambulance chasers"—legal and other characters who run after police and fire calls in an effort to pick up some business. "From time to time," the Commission reports, "complaints are received that certain repair men, ambulance operators, and other unauthorized persons intercept such calls to capitalize on fires, accidents, crimes, etc. This is contrary to the Communications Act, which protects intrastate as well as interstate and foreign communications from interception or divulgence for private benefit."

**THAT TELEVISION HOOK-UPS** will continue to figure in radio debates both in Washington and elsewhere during the winter, was indicated with the recent *American Telephone and Telegraph* announcement that it had requested FCC to withdraw tariffs previously filed "covering rates for intercity television transmission." These rates were due to become effective late in summer. Withdrawing them would mean an eventual cut in rates, Washington concensus agrees, but *AT&T* begged to dissent. "No change is contemplated in the basis of charges for pickup and other wire and radio facilities provided by *Bell System* telephone companies for special point-to-point transmission of television programs," officials stated, adding: "Present experimental television service over the New York-Washington coaxial cable which has been given without charge to the television industry will be continued (Continued on page 167)"

**RADIO NEWS**

# Radio Service Engineers

Build a Laboratory that will  
serve your needs for years!

Here it is!—The Industry's most modern Test Equipment,  
designed for tomorrow's needs as well as for today's. New  
circuits, new styling, new ruggedness, new accuracy. Equip  
yourself to do a bigger, better, *more profitable* service business  
—with Philco Test Equipment.



## PHILCO TEST EQUIPMENT

- ★ **PHILCO SIGNAL GENERATOR, MODEL 7070.** Range from 100 kc to 110 mc—all fundamentals! No switching trouble at any frequency. Residual output less than 5 microvolts! High output—over 1 volt at 100 mc. Coaxial output cable.
- ★ **PHILCO CIRCUIT MASTER, MODEL 7001.** Uses exclusive vacuum tube voltmeter and electronic bridge circuit. All ranges and functions including 10,000 volts AC or DC. Probe available for RF measurements to over 200 mc.
- ★ **PHILCO DYNAMIC TESTER, MODEL 7030.** Searchlighted probe head has lucite lens and four switch positions giving wide choice of input impedances. Covers RF and IF circuits, with DC position for microphone and amplifier testing.
- ★ **PHILCO JUNIOR SCOPE, MODEL 7019.** Small, lightweight, rugged portable. New C-R tube, vertical and horizontal amplifiers, self contained sweep circuit and synchronization, complete power supply.
- ★ **PHILCO TUBE TESTER, MODEL 7050.** Can never become obsolete with changes in tube types, thanks to exclusive Philco Element Switching system. Built-in loose leaf chart.

See your Philco Distributor about these modern instruments—today.

# SPECIAL OFFER DURING

## Testing & Aligning TELEVISION RECEIVERS

By **Maxon Schreap**

## Part I: The Oscilloscope... how to use it.

by **Karl E. Albert**

This is the concluding article of a series on the use of the oscilloscope. It covers the alignment of receivers, using the oscilloscope and a frequency sweep generator.

**The Oscilloscope... How to use it**

A series wave series that is produced here before proceeding with the last article on the use of the oscilloscope. The last article dealt with the use of the oscilloscope in the alignment of receivers. This article deals with the use of the oscilloscope in the alignment of receivers. It covers the alignment of receivers, using the oscilloscope and a frequency sweep generator.

## The Oscilloscope... How to use it

## servicing FM receivers

101 FM Stations Are Now On The Air!

Two Million F.W. Sets Will Be Produced In 1947!

This is the first of several articles designed to expedite the servicing, repairing, and aligning FM receivers which are now rolling off the production lines.

By **Walter Kaufman**

Adjusting the television receiver... This is the concluding article of a series on the use of the oscilloscope. It covers the alignment of receivers, using the oscilloscope and a frequency sweep generator.

# 16

# ISSUES OF FOR ONLY

## Modern Bench Construction


by **Joseph J. Moore**

## servicing by EAR

Troubleshooting by half analysis

By **John T. Frye**

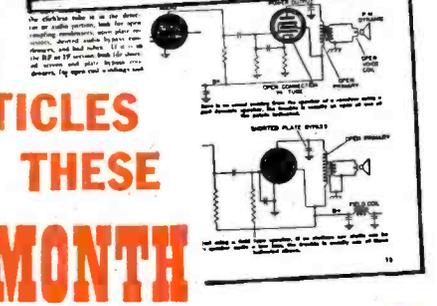to use the alignment and phase... This is the concluding article of a series on the use of the oscilloscope. It covers the alignment of receivers, using the oscilloscope and a frequency sweep generator.



## GET ARTICLES SUCH AS THESE EVERY MONTH

Our readers have given the articles illustrated here unprecedented acclaim. They are unanimous in their indorsement of RADIO MAINTENANCE as an aid in their work—a reference in their libraries—and a vital tool in their shops!

Radio Maintenance has filled a breach that has existed in the radio field for a long time. Already 30,000 servicemen read Radio Maintenance every month because it is devoted entirely to the radio service-technician. The Radio Maintenance staff specializes in the preparation of articles on every phase of radio maintenance in series form which may be filed and used for reference. The leading articles cover everything for the radio serviceman on Television, FM and AM; Test Equipment; Electronic Appliances; Tools; Antennas; Alignment;





# Compare "Hi-Kaps"

See why Centralab's ceramic by-pass and coupling capacitors are your best buy for **QUALITY!**

"HI-KAP" FEATURES	DESCRIPTION	ADVANTAGES
1. Impervious to moisture	Ceramic-X is non-hygroscopic. Moisture absorption is .007% or less.	No deterioration, no shorting. Longer life even under the most adverse conditions.
2. Low mass weight	Av. Wt. Dimensions Values .029 oz. D—.315" .00005— L—.540" .00025 mfd.	For unit size and weight, Centralab BC "Hi-Kaps", made with Ceramic-X, are the only capacitors on the market which provide these voltage ratings.
3. Small size	.044 oz. D—.315" .0005 mfd. L—.830"	
4. High capacity	.050 oz. D—.340" .000750— L—1" .005 mfd.	
	.082 oz. D—.400" .01 mfd. L—1.305"	
	Rating: 600 WVDC — 1000 VDC flash test.	
5. Special insulation	Wax impregnated, lacquered, dipped in special phenolic resin, cured and wax impregnated.	Prevents any possibility of shorting to adjacent leads, chassis or components.
6. Convenient side leads	Heavy #22 gauge tinned copper.	Permit rapid, close-coupled connections. No tricky bending or fitting required.
7. Low power factor	Initial — .6%. After 100 hours, 95% humidity test — 3.0%.	More efficient circuit operation, fewer failures.
8. High leakage resistance	Initial — 5000 megohms. After humidity — 500 megohms.	Long life, more efficient performance.
9. Maximum dependability	One-piece construction. Leads soldered directly to electrodes.	Will not short or become intermittent.
10. Factory tested	For your protection, all units 100% factory tested before packaging and shipping.	Your guarantee to your customers of reliable service and performance.



See why Centralab's ceramic by-pass and coupling capacitors are your best buy for **PRICE!**

NEVER BEFORE has the dependability, permanence and convenience of ceramic by-pass and coupling capacitors been offered to Radio Service Dealers at a favorable price! As more and more manufacturers turn to BC "Hi-Kaps" for longer life and better set performance, Centralab now offers you this opportunity to give yourself and your service customers the newest and finest in capacitor components! Made with high dielectric constant Ceramic-X, BC "Hi-Kaps" are rated at 600 WVDC — 1000 V. flash tested. Values from .000050 to .010000 mfd., list priced from \$1.25 to \$1.50 per envelope of five.

Look for large counter display at your Centralab Distributor. Write today for new free booklet, "Why Ceramic Capacitors", containing complete history of origin and development of ceramic capacitors!


**Centralab**  
Division of GLOBE-UNION INC., Milwaukee

DESIGNED FOR THE BETTER SERVICE SHOP . . .



**RCA'S NEW TEST OSCILLATOR**  
 . . . second unit of a  
 revolutionary new line

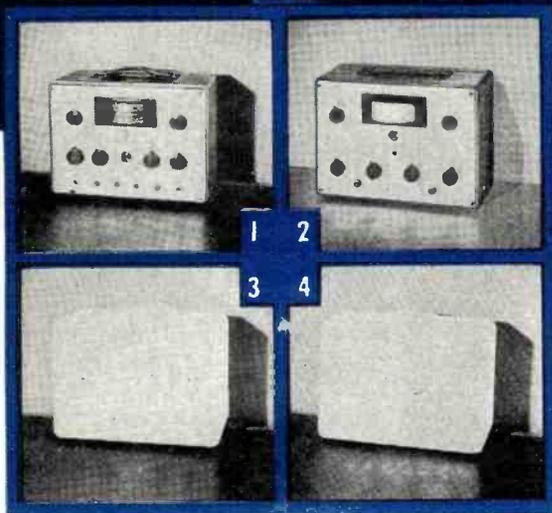**Reduces testing and alignment time  
 by as much as 50 per cent**



**ON THE WAY**—a superior line of test equipment that puts time-consuming service jobs on a profitable, production-line basis . . . that anticipates all FM and television needs. Matched styling of all instruments permits attractive, convenient grouping. Watch for announcements of the other units in this new line.

● The WR-67A is a time-saver that adds *profitable* hours to your service day . . . puts you dollars ahead.

When aligning a receiver, for example, you can switch from a pre-tuned i-f signal to pre-tuned broadcast-band signals without dialing or retuning. The range switch gives you three fixed frequencies: 1500, 600, and 455 kc. It also permits instant switching to any other frequency you select between 100 kc and 30 mc by presetting the smoothly variable tuning control.

Other outstanding features include: a signal injection probe for high-speed servicing . . . a four-step attenuator with fine control . . . double

shielding . . . miniature-type tubes throughout . . . a six-band drum dial with an easy-to-read, four-foot scale spread . . . adjustable modulation level for internal and external modulation . . . a two-stage power-line filter to minimize leakage, and a 400-cycle *audio* signal source.

Every RCA WR-67A is factory-tested with the finest precision measuring equipment. Heavy-duty components—plus the WR-67A's ability to withstand rigorous "drop," "shake," and humidity tests—add up to real on-the-job reliability. A new bulletin is yours for the asking. *Keep in touch with your RCA Test Equipment Distributor.*



**TEST AND MEASURING EQUIPMENT**  
**RADIO CORPORATION of AMERICA**  
**ENGINEERING PRODUCTS DEPARTMENT, CAMDEN, N.J.**

In Canada: RCA VICTOR Company Limited, Montreal

# TELEVISION-

## America's Next Giant Industry?



Billboard Announcing Telecasts of Ball Games in Chicago

Today, RIGHT NOW, clear and bright pictures of great sports events, as well as other equally interesting programs, are being telecast for the enjoyment of thousands. Television stations in New York, Chicago, Philadelphia, Washington, Detroit, St. Louis and Los Angeles are already operating on regular schedules. Construction has started in several other centers and it is believed that practically every major city in the country will have this wonderful service before the end of 1948.

Who will build, maintain, and operate the new telecast stations? Who will design, produce, install and service the receivers?

### Men Must Be Trained for These New Professions

Alert young men with an ambition to grow with television are training now in the greatly enlarged instruction laboratories of American Television, Inc. A wide choice of courses available. Advanced methods and latest obtainable equipment used.

One of Our New Buildings.  
Air Conditioned the Year Round.



U. A. Sanabria

Dr. Lee deForest

### The Men Who Direct American Television

The instructional quality of training is under the constant personal supervision of two internationally known engineers, Mr. U. A. Sanabria, President and Founder of American Television, Inc. and Dr. Lee deForest, the famed inventor of the radio tube.



### FREE PRE-ENTRANCE COURSE

A Short Home Study Television Course is available to qualified war veterans who are considering residence training. This course is free of any charge or obligation. Your success with it will help you to learn your own abilities in television. It will also aid us greatly in qualifying you for residence training. Your acceptance of the Home Study course in no way obligates you to enter our residence school. So we urge you to take advantage at once of the very unusual opportunity it offers.



Approved for Veteran Training Under G. I. Bill of Rights

## American Television, Inc.

5050 BROADWAY

CHICAGO 40, ILLINOIS

### REQUEST FOR FREE INFORMATION

American Television, Inc., Dept. of Information  
5050 Broadway, Chicago 40, Illinois

Please send details of your Television Training.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

ZONE \_\_\_\_\_ STATE \_\_\_\_\_

I am a veteran



**Snap-on**  
**Vacuum Grip**  
REG. U. S. PAT. OFF.  
**Pliers**

A complete line . . . engineered for performance


Pliers are basic tools in an extremely wide and varied range of operations. The *right pliers for the job* can make a tremendous difference in speed and workmanship. The Snap-on pliers illustrated are typical of the many types of Vacuum Grip pliers . . . each type *job-engineered* for peak performance on the work for which it is designed.

Snap-on builds Vacuum Grip pliers in a modern plant devoted exclusively to the production of the finest, most efficient pliers that can be produced. Vacuum Grip pliers are hammer forged from special high car-

bon chrome-silico-manganese alloy tool steel, hardened and tempered through and through. Light in weight, perfectly balanced. Smooth, easy riding joints, sharp, deeply milled teeth. Hand filed, perfectly aligned cutters. Spring-tempered, "Vacuum Grip", non-slip handles.

A famed name in Snap-on's complete line of more than 4,000 tools for production and service, Vacuum Grip pliers are available everywhere through Snap-on's nation-wide direct-to-user tool service.

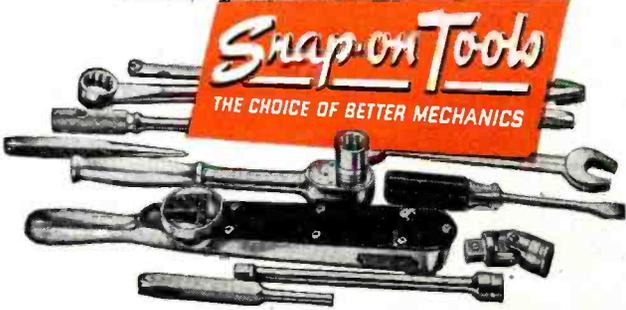**SNAP-ON TOOLS CORPORATION**  
 8120-J 28th AVENUE KENOSHA, WISCONSIN  
 International Division: Kenosha Wis. U. S. A.




# Don't Miss PHOTOFAC Set No. 23!

## WITH EXCLUSIVE NEW "Standard Notation" SCHEMATICS

### The Greatest Service Data Development in 20 Years!

I am proud to announce to my Servicemen friends the successful development of a new system of "Standardized Schematics" that is now yours exclusively in PHOTOFAC Folders. We have worked on this project for over one year, because we knew that uniform, standardized schematics would save you hours of time and countless headaches—would help you earn more. NOW—we have developed uniform, standardized diagrams on all sets. Now—you can save time—go from diagram to diagram and see the same, easy-to-understand symbols and designations. You no longer have to puzzle out the differences in schematic notations or bang your head against queer-looking diagrams. You'll recognize instantly the functions of all parts in any circuit. The standards used in our new diagrams are yours—the result of the PHOTOFAC "Standards Poll" and thousands of interviews with Servicemen. I wish space would permit me to tell you more—but PHOTOFAC Set No. 23 speaks for itself. You owe it to yourself to see the new diagrams. Use them—learn what a difference they'll make in faster, more profitable servicing.

*Howard W. Sams*

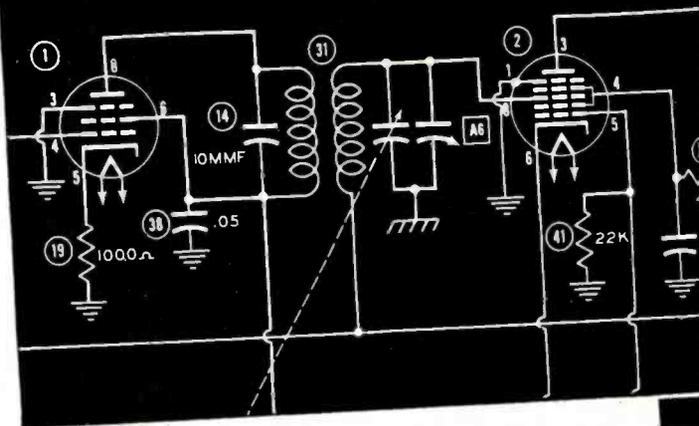

### NOW! UNIFORM SCHEMATICS FOR FASTER, MORE PROFITABLE WORK!

Beginning with Set No. 23, and thereafter, all PHOTO-FACT Folders will feature the new, uniform "Standard Notation" schematics. Each and every diagram is drawn to the same basic set of clear, uniform, easy-to-understand standards. Here's what the new "Standard Notation" Schematics mean to you: Makes circuit analysis simple, quicker, fool-proof, more accurate! No more time wasted puzzling over odd-looking diagrams! No more trouble with varying symbols and confusing styles! Just ONE CLEAR STANDARDIZED STYLE FOR ALL CIRCUITS—SAVES YOU TIME—HELPS YOU EARN MORE. Only PHOTOFAC offers you the "Standard Notation" Schematics!

### TWO IMPORTANT NEW HOWARD W. SAMS PUBLICATIONS



#### DIAL CORD STRINGING GUIDE

There's only one *right* way to string a dial cord. And there's only one book that shows you how. It's the Howard W. Sams DIAL CORD STRINGING GUIDE. Here, for the first time, in one handy pocket-sized book, are all available dial cord diagrams and data covering 1938 through 1946 receivers. Licks the knottiest dial cord problem in a matter of minutes. This low-cost book is a "must" for servicing. You'll want two copies—one for your tool kit and one for your shop bench. Order them today. **75c ONLY**



#### 1947 AUTOMATIC RECORD CHANGER MANUAL

Nothing like it! COVERS MORE THAN 40 DIFFERENT POST-WAR MODELS. Absolutely accurate, complete, authoritative—based on actual study of the equipment. Shows exclusive "exploded" views, photos from all angles. Gives full change cycle data, information on adjustments; service hints and kinks, complete parts lists. Shows you how to overcome any kind of changer trouble. PLUS—for the first time—complete, accurate data on leading WIRE, RIBBON, TAPE, and PAPER DISC RECORDERS! Over 400 pages; hard cover; opens flat. No modern service shop can afford to be without this manual. **\$4.95 ONLY**

**HOWARD W. SAMS & CO., INC.**  
INDIANAPOLIS 6, INDIANA

Export—Ad. Auriema—89 Broad St., New York 4, N. Y.—U. S. of America  
Canada—A. C. Simmonds & Sons, 301 King St., East—Toronto, Ontario

## PHOTOFAC SERVICE

"The Service that pays for itself over and over again"

### FREE PHOTOFAC AIDS!

**FREE. PHOTOFAC CUMULATIVE INDEX**  
—Your guide to more than 1800 receiver models and chassis (1946 and 1947 models covered in PHOTOFAC Folder Sets 1 through 20).

**FREE. HOW TO FILE FOLDER**—Shows 5 good ways to file PHOTOFAC Folders, including new "30-Second" filing method.

Ask your parts jobber for FREE copies of these PHOTOFAC aids, or write us direct.

### RESERVE SET NO. 23 TODAY

MAIL THIS ORDER FORM TO YOUR PARTS JOBBER TODAY—or send directly to HOWARD W. SAMS & CO., INC., 2924 E. Washington Street, Indianapolis 6, Indiana.

My (check) (money order) for \$..... enclosed.


- Send PHOTOFAC Set No. 23 (at \$1.50).
- Send . . . SAMS' DIAL CORD STRINGING GUIDE(S), at \$0.75 per copy.
- Send . . . SAMS' 1947 AUTOMATIC RECORD CHANGER MANUAL(S) at \$4.95 per copy.
- Send PHOTOFAC Volume No. 1 (including Sets Nos. 1 through 10) with DeLuxe Binder, \$18.39.
- Send PHOTOFAC Volume No. 2 (including Sets Nos. 11 through 20) in DeLuxe Binder, \$18.39.
- Send FREE PHOTOFAC Aids.

Name.....

Address.....

City..... State.....
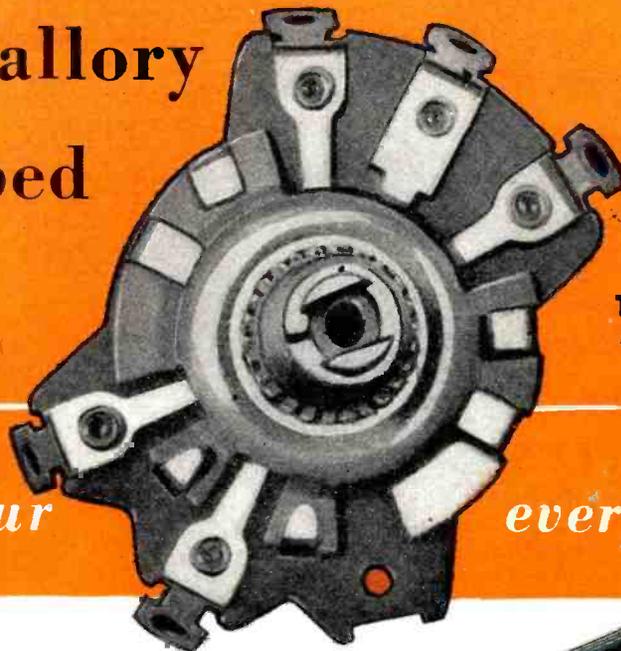
# 10 Resistance Values in Mallory Double-Tapped Controls...



**TYPE DTM  
(DOUBLE TAP)**

*To supply your every need*

**M**ALLORY is pretty fussy about the taper and resistance values of the controls it makes. That's because it has a thorough knowledge of controls in all original receiving sets... conscientiously duplicates these controls with a streamlined, but *complete* line of replacements.

Mallory Double Tapped Midget Controls are a case in point. They come in ten resistance values—to supply every need! By merely combining them with the right Mallory Plug-In Shaft, you can duplicate most double tapped original controls in the "special" category.

Furthermore, Mallory provides *large* double tapped controls in four resistance values. These are to replace originals with fixed shafts of 3 inches or less.

See the Mallory Catalog for the complete story. Or contact your Mallory distributor.

*You Expect More—and Get More—from Mallory*



## **INSIST ON MALLORY— THE COMPLETE CONTROL LINE**

*Mallory is the manufacturer  
that offers:*

- 33 Correctly Tapered Wire-Wound Controls
- 31 Values in Single Tapped Controls
- 10 Values in Double Tapped Controls
- 12 Clutch Type Controls
- 10 Universal Dual Controls
- 92 Popular Special Controls

**P. R. MALLORY & CO. Inc.**  
**MALLORY**

VIBRATORS... VIBRAPACKS\*... CAPACITORS... VOLUME  
CONTROLS... SWITCHES... RESISTORS... FILTERS  
... RECTIFIERS... POWER SUPPLIES.

\*Reg. U. S. Pat. Off.

**APPROVED PRECISION PRODUCTS**

*National Radio Week  
Oct. 26—Nov. 1*

**P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA**

**October, 1947**

27




## "SPINTITES"

One of the surest ways of sustaining assembly line speed is to standardize on Spintite wrenches. Made to meet the particular problems of radio and electrical assembly and repair, they're designed for precision performance, volume production, durability and ease of operation with a minimum of skill.

Built like a screwdriver, the Spintite shaft readily reaches difficult assembly spots, and it is partly hollowed to permit tightening of nuts through which the bolt protrudes.

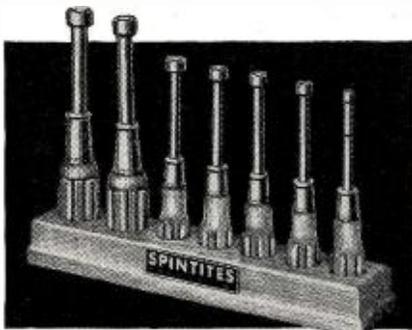Available with either fixed or chuck-type handle, Spintites can be had to fit square, knurled or hex nuts in sizes from 3/16" to 5/8". For the radio and electrical industry's three requisites in tools, speed, accessibility and quantity — specify Spintites.



T-73 SET, has 7 sizes of hex heads. Shock-proof handles, and cold forged sockets assure safety and strength. OVER 40 YEARS OF MASTER TOOLMAKING



**STEVENS-WALDEN, INC.**  
Worcester • Massachusetts

# Within the INDUSTRY

**KENNETH W. SICKINGER**, formerly a department manager with *Oakes & Company* of Chicago, has been placed in charge of advertising for the Radio Division of *Stewart-Warner Corporation*.



Prior to his connection with *Oakes & Company*, Mr. Sickinger was assistant general sales and advertising manager of the *Belmont Radio Corporation* of Chicago. He has also been associated with *Rainfair, Inc.*, *Western Advertising Agency* and the *Racine Journal-Times*. Mr. Sickinger will maintain offices in Chicago.

\* \* \*

**FARNSWORTH TELEVISION & RADIO CORPORATION** has announced the appointment of the *J. N. Ceazan Company* of San Francisco as distributors of *Farnsworth* products in 47 counties in northern California and 10 counties in western Nevada.

One of the oldest wholesale distributing organizations in the West, the *Ceazan Company* was founded in 1919. Julius N. Ceazan, founder of the company, serves as president.

The firm's warehouse and offices are located at 1547 Mission Street in San Francisco. In addition, the company maintains permanent display space at the Western Merchandise Mart.

\* \* \*

**JOSEPH W. WHITESIDE**, a *General Electric Company* employee since 1929, has been named sales manager of the company's new tube parts and equipment sales section.



The new section, which is part of the Tube Division, has been set up to sell electronic tube parts and tube-making equipment to manufacturers. In addition to his new duties, Mr. Whiteside will continue to be responsible for all purchases, including subcontracting, for the Tube Division. He will maintain headquarters at the company's plant in Schenectady.

\* \* \*

**HARVEY W. HARPER**, Chairman of the Board of *Tung-Sol Lamp Works Inc.*, has just issued a statement refuting the rumors of a possible merger between *Tung-Sol* and *National Union Radio Corporation*.

According to Mr. Harper, "There is no basis whatsoever to the rumor that this company will merge with the

*National Union Radio Corporation*. In fact no such proposal has ever been made or considered by the present management of *Tung-Sol Lamp Works Inc.*, and so far as this management is concerned, there is no intention of proposing such a merger."

\* \* \*

**ORRIN E. DUNLAP, JR.**, has been elected to the post of Vice-President in Charge of Advertising and Publicity for *Radio Corporation of America*.

Mr. Dunlap became Director of Advertising and Publicity of *RCA* on January 1, 1944, after serving four years as Manager of the Information Department.

Before joining the company in 1940, Mr. Dunlap was Radio Editor of *The New York Times* for eighteen years. He is a member of the ARRL, a life member of the Veteran Wireless Operators' Association and a senior member of the I.R.E.

He is the author of ten books on radio, including two volumes on the subject of radio as an advertising medium.

\* \* \*

**EDWARD A. MILLER** has been named Vice-President in charge of Engineering by the Board of Directors of the *Acme Electric Corporation* of Cuba, New York.



After joining the company in 1930, Mr. Miller devoted his time to improving the design and performance of the company's line of luminous tube transformers. He was also active in the development of various equipment used by the communication and radio industries.

He is an active member of the I.R.E. and the A. I. E. E.

\* \* \*

**STANLEY H. MANSON**, public relations manager of *Stromberg-Carlson Company*, has been appointed chairman of the Radio Manufacturers Association Advertising Committee, succeeding John S. Garceau, advertising manager of *Farnsworth Television & Radio Corporation*, who resigned after seven years' service in the post.

As chairman of the subcommittee in charge of the RMA "Radio-in-Every-Room" campaign, Mr. Manson has been active in the committee's sales promotion activities.

The RMA Advertising Committee has been enlarged because of the expanding activities of the committee. Victor A. Irvine, advertising manager of *Motorola, Inc.*, has been named vice-chairman of the committee.

*Opportunity now FOR YOU!*

**NATIONAL SCHOOLS SHOP METHOD**

**HOME TRAINING in RADIO**


**TELEVISION and ELECTRONICS**



RADIO SHOP AT NATIONAL



BROADCAST STUDIO AT NATIONAL

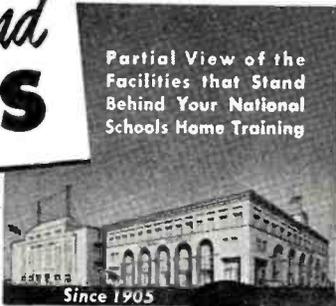

Partial View of the Facilities that Stand Behind Your National Schools Home Training

Since 1905



TELEVISION STUDIO AT NATIONAL

**We Bring NATIONAL SCHOOLS to You**

**A PRACTICAL RESIDENT TRADE SCHOOL**

*With Its Own Shops and Laboratories*

**FOR OVER 40 YEARS**

**TODAY, OPPORTUNITIES IN THE RADIO, ELECTRONICS AND TELEVISION INDUSTRY ARE TAKEN FOR GRANTED**

We see them everywhere: The Home Radio Service Field continues to grow. Television is here . . . Television Broadcasting facilities are being rapidly expanded. Television sales, service, installation and maintenance requirements are more and more important from day to day. Electronics is an important factor in many applications for utility, safety, accuracy and convenience. Airlines are finding new uses for Radio bringing new benefits to air transportation. Ships at sea are employing Radar together with other conventional Radio apparatus for ship-to-shore communications and safety. Frequency Modulation is modernizing Radio Broadcasting, offering static-and-interference-free reception in the home. The list of Radio applications is almost endless, and every one represents increasing opportunities in our modern world for the **RADIO, TELEVISION AND ELECTRONICS TECHNICIAN WITH A SOLID TECHNICAL BACKGROUND.**

**NOT JUST ANY TRAINING WILL DO**

It is not a question of opportunity but rather how to take advantage of existing opportunity. Only proper training can make these opportunities a reality. National Schools of Los Angeles, one of the oldest and largest technical trade schools in the United States, offers you **Shop Method Home Training, a proved method that builds qualified technicians.** Here is Home Training that **BRINGS RESULTS.**

Behind all training from National Schools stands a permanent faculty of experienced instructors and engineers. These men are daily teaching resident students right in our own Shops and Laboratories. From first hand experience with students here at school, our instructors understand the needs and ambitions of men like you. All of our instructors, both Home Study and Resident, have ideal facilities to make your training practical, up-to-the-minute, interesting. It takes years of experience to know how to train men, especially in the practical technical trades. Established almost 50 years ago, National Schools has a rich background of experience to help you to take full advantage of the opportunities in the Radio, Television and Electronics Industry

**HERE'S JUST A FEW OF THE INTERESTING FACTS YOU LEARN WITH THE FREE MANUAL**

1. Routine for Diagnosing Radio Troubles.
2. Preliminary Inspection of Receivers.
3. How to Check Power Supply.
4. How to Identify Various Stages of Receivers.
5. How to Trace the Circuit and Prepare Skeleton Diagram.
6. How to Test and Measure Voltages.
7. How to Test Speaker in Audio Stages.
8. How to Test Detector, I.F., R.F., and Mixer Stages.
9. Complete Reference Table for Quickly Locating Receiver Troubles.

**VETERANS**

During the war, National trained enlisted men under contract with the War Department. Both the Armed Forces Institute and Marine Corps Institute used our lesson texts on a wide scale. Now, we are training veterans, both resident and home study, through the Veterans Administration. If you are a veteran of World War II—and qualified for training under the G.I. Bill o. Rights, check the coupon for special information.



**GET THESE 2 BIG BOOKS FREE!**



**Begin Training at Home Later Come to Our Shops and Laboratories in Los Angeles —If You Prefer**

National's Master Shop Method Home Training in Radio, Electronics and Television is COMPLETE in itself. No other training is necessary; but, some men do prefer to take a short experience course here in our resident shops and laboratories, at the end of their Home Study training. They find it helpful to spend a short period of time in our modern Broadcasting Station, or our New Television Laboratories and Studios, or our Extensive Radio Servicing Shops—as well as other departments covering every specialized phase of the Radio Industry.

You are welcome to take advantage of this additional instruction if you wish. If you are interested, check the coupon below. Full details will be sent you by return mail. National Schools' **OUTSTANDING FACILITIES MAKE IT POSSIBLE TO OFFER THE FINEST POSSIBLE TECHNICAL TRADE TRAINING IN RADIO, TELEVISION AND ELECTRONICS.**

**You Get All This Radio Experimental Equipment to Use and Keep at Home!**

**LEARN BY DOING** is the basic principle of National's Shop Method Home Training. We send you standard Radio parts for an interesting series of experiments which demonstrate the fundamentals of Radio, Television and Electronics. The very essence of this training is **EXPERIENCE**—you get actual experience by building many different types of circuits. You build a fine, long distance **MODERN SUPERHETERODYNE RECEIVER**, signal generator, low-power Radio transmitter, audio oscillator, etc. This **practical work** develops your knowledge of Radio step by step, makes you a practical Radio Technician.

G. I. APPROVED

**NATIONAL SCHOOLS**

LOS ANGELES 37, CALIFORNIA EST. 1905



**MAIL OPPORTUNITY COUPON FOR QUICK ACTION**

NATIONAL SCHOOLS, Dept. 10-RN  
4000 South Figueroa Street, Los Angeles 37, California

Mail me FREE the two books mentioned in your ad, including a sample lesson of your course. I understand no salesman will call on me. I have checked below the plan which interests me.

NAME..... AGE.....

ADDRESS.....

CITY..... STATE.....

(Include your zone number)


- I am interested in home study only.
- Send information on your Combined Home-Study and Modern Resident Shop Training.
- Veteran of World War II.

# the Crescent C-250 Record Changer

does these  
3 jobs  
better



## THE CRESCENT Speakers

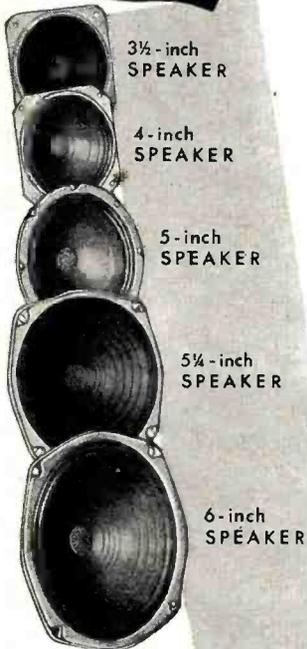

Crescent Speakers, designed and engineered to the most exacting standards, deliver the finest in tonal performance.

## performs • endures • attracts

The most attractive and well designed changer in the popular priced field. Equipped with dependable cushion mounted motor — "Barry" mounts to eliminate vibrations and fool-proof in operation. Hammertone finished with smart plastic trim. Has both reject button and control knob for convenient on-off-manual and automatic operation. Plays 10" or 12" records automatically.

CONTACT YOUR CLOSEST  
CRESCENT SALES REPRESENTATIVE  
WM. RUTT, c/o CRESCENT ELECTRONICS CO.  
401 Broadway, New York 13, N. Y.  
MILLER-JOYCE CO.  
609 S. Vermont Ave., Los Angeles 5, Calif.  
LES LOGAN CO.  
530 Gough St., San Francisco, Calif.  
HARRISON-REYNOLDS CO.  
419 Commonwealth Ave., Boston 15, Mass.



**CRESCENT INDUSTRIES INC.**  
4132-54 W. BELMONT AVENUE  
CHICAGO 41, ILLINOIS

Plans are now being completed for observance of National Radio Week, October 26-November 1, an annual event inaugurated in 1945 by the National Association of Broadcasters. The RMA "Radio-in-Every-Room" campaign will reach its climax coincident with the National Radio Week observance.

**SAM NORRIS**, Sales Manager for *Ampex Electronic Corporation* since 1942, has been named Executive Vice-President of the company.



Well-known in the industry for his activities in the Radio Manufacturers Association and the National Electrical Manufacturers Association, Mr. Norris has announced the establishment of an independent development group of engineers to work closely with customers on application problems. He will also visit South America to renew prewar trade contacts and to expand the firm's export business.

**RADIO MANUFACTURERS ASSOCIATION'S** Parts and Transmitter Divisions have named new section chairmen for the 1947-48 fiscal year.

Chairman J. J. Kahn, President of the *Standard Transformer Corp.*, announced the appointment of 20 section chairmen for the Parts Division: Coil Section, Edwin I. Guthman, *Edwin I. Guthman & Company, Inc.*; Fixed Capacitor Section, W. Myron Owen, *Aerovox Corporation*; Fixed Resistor Section, J. Hall Stackpole, *Stackpole Carbon Company*; Instrument & Test Equipment Section, R. L. Triplett, *The Triplett Electrical Instrument Co.*; Insulations Section, John W. Apgar, *Irrington Varnish & Insulator Co.*; Metal Stampings and Metal Specialties Section, S. L. Gabel, *Superior Tube Company*; Phonograph Cartridges and Pickups Section, George B. Fraser, *The Astatic Corporation*; Plastics and Molded Parts Section, John J. Bachner, *Chicago Molded Products Corporation*; Record Changer and Phono Motor Section, Allan W. Fritzsche, *The General Industries Company*; Socket Section, Frank Holmstrom, *Hugh W. Eby, Inc.*; Speaker Section, Laurence A. King, *The Rola Company, Inc.*; Speaker Parts Section, A. D. Plamondon, Jr., *The Indiana Steel Products Company*; Special Products Section, William R. MacLeod, *King Laboratories, Inc.*; Switch Section, William S. Parsons, *Centralab*; Transformer Section, R. A. Hoagland, *Jefferson Electric Company*; Variable Condenser Section, G. F. Behringer, *The American Steel Package Co.*; Variable Resistor Section, D. S. W. Kelly, *Allen-Bradley Company*; Vibrator Section, Ray F. Sparrow, *P. R. Mallory & Co., Inc.*; Wire Section, R. G. Zender, *Lenz Electric Mfg. Co.*; and Wire Wound Resistor Section, D. T.

(Continued on page 120)

**RADIO NEWS**

**READY**  
For immediate delivery

# AIR KING WIRE RECORDER

and RADIO-PHONO COMBINATION

**AIR KING OPENS AN EXCITING NEW FIELD IN HOME ENTERTAINMENT.**


Air King was the first radio manufacturer to successfully combine the Wire Recorder, Radio and Phonograph into a smooth functioning, foolproof, home entertainment unit that even a child can operate. Another out-growth of Air King's Engineering "Know-How".

Consumer acceptance of the Wire Recorder, in combination with a radio phonograph at no extra cost has been sensational! It has proven itself in thousands of American homes and is considered by top merchandisers to be the hottest item of the year.

Smart dealers will insist upon the Wire Recorder in all future radio-phonograph combinations.

Air King believes that progress makes sense and dollars too. Here is your opportunity to get on the Air King bandwagon and be the first to sell the Air King Wire Recorder Radio-Phono Combination in your community.

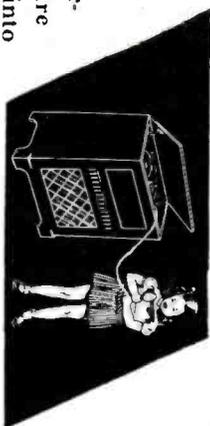★ WE HAVE A LIMITED NUMBER OF DISTRIBUTOR AND DEALER TERRITORIES OPEN. Write or wire (new Address): Air King Products Co., Inc., 170 53rd Street, Brooklyn 52, N. Y. Export Address: Air King International, 75 West Street, New York 6, N. Y.




Records your voice, Disc Records or Radio Programs, simple, finger-tip controls.



The music lovers' dream comes true. Amazing high fidelity noise free recordings.

It's a Radio, Phonograph and Wire Recorder all in one!

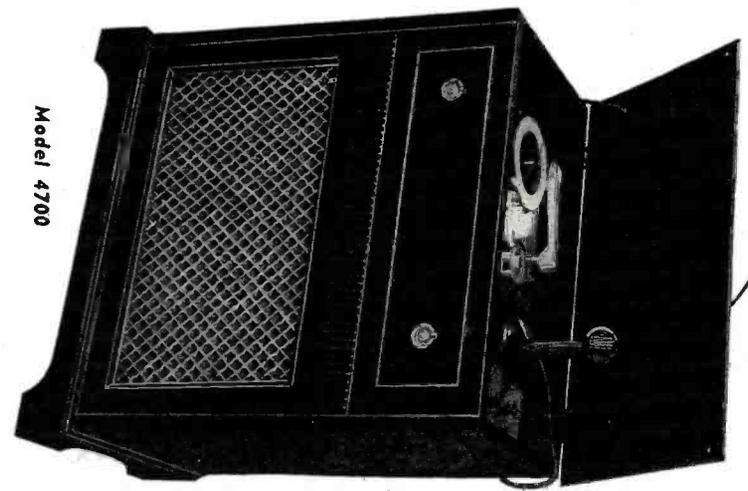


Model 4700

**FEATURES YOU CAN SELL!**

- Records Voice on Wire, through Microphone.
- Records Phonograph Records on Wire.
- Records Radio Broadcasts on Wire.
- Powerful Super-Sensitive Radio.
- High Quality Phonograph.
- Amazing Air King "Wiretone" Reproduction.

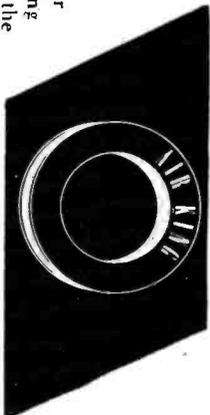**FIRST AID PROGRAM for HEALTHY BUSINESS**

Air King places its Advertising and Sales Promotion Department at your disposal. Write today, for information on our First Aid Program to help you promote the Air King line in your community. A new idea in manufacturer dealer cooperation.



One hour of recording on a small spool of wire. Replay or erase for new recording.

The Heritage of Radio Since 1920

## AIR KING RADIO

Division of HYTRON RADIO & ELECTRONICS CORP.

**KEN-RAD TUBES  
BUILD BUSINESS FOR MY  
RADIO REPAIR SHOP!**



You hear that statement from service-men who've learned that at all times they can count on Ken-Rad tube quality, stamina, and long playing life.

**Ken-Rad double acceptance—by dealers and users  
—means a doubled sales-and-profit potential!**

As a radio-repair specialist or tube dealer you can "cash in" on the twofold popularity of Ken-Rad tubes—their acceptance by service experts because they're *good tubes*, and the favor they enjoy with radio owners based on their fine performance and long life.

Profits can come not alone from your growing volume of Ken-Rad tube business, but by selling more parts and repair time to owners who seek the superior service you offer your clients. *For Ken-Rad tubes are your*

*most effective advertisement of this service.*


Here is a splendidly engineered *modern* line of receiving tubes, backed by great facilities in research and manufacture, with a brand name deservedly popular and growing more so daily. Here too is OPPORTUNITY to increase your sales, boost your income, underscore with the Ken-Rad good name your own fine local reputation.

Put Ken-Rad double acceptance to work for you . . . profitably!

**SPEAKING FOR APPRECIATIVE  
OWNERS, KEN-RAD TUBES  
BUILD GOODWILL!**



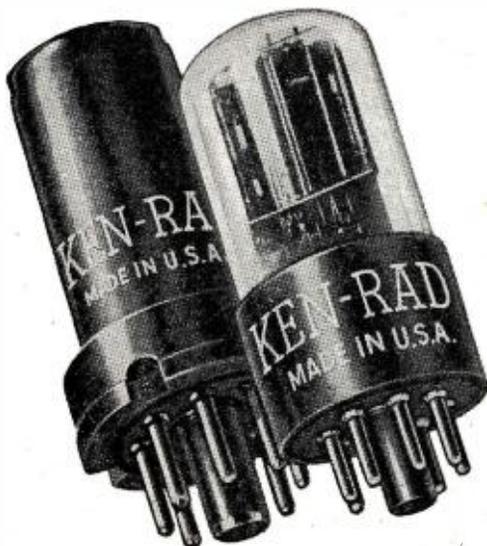Customers soon discover that Ken-Rad tubes give a "lift" to radio performance. Advanced tube design and precision manufacture are responsible.



Write for Ken-Rad Booklet ETR-16, "Essential Characteristics". This well-known publication contains the technical data you need to select Ken-Rad tube types for sets being repaired. The three "C"s apply throughout: Convenient, Concise, Comprehensive. Just one of many Ken-Rad helps—including the trade's *finest display, advertising, and promotion material*—available to radio service-men and tube dealers!

178-FD-8880



# Announcing

## SCOTCH *Sound Recording* TAPE


BRAND

OFFERING HOME AND PROFESSIONAL RECORDERS A NEW STANDARD OF TONE FIDELITY AND EASE OF HANDLING



Developed in the research laboratories of the 3M Company . . . the world's largest manufacturers of pressure-sensitive adhesive tapes . . . "SCOTCH" Sound Recording TAPE is now available in quantity for immediate delivery. No other magnetic recording medium can offer all these advantages:

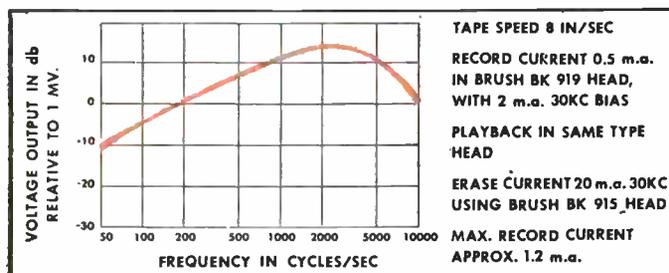1. Better frequency response at slow recording speeds—due to "SCOTCH" Sound Recording Tape's extremely thin, uniform magnetic coating.
2. Low noise level because of uniform dispersion of particles and mirror-like surface.
3. Higher Coercive Force—350 oersteds—insures higher frequency response and greater signal strength.
4. Flat surface and large area provide positive contact with the pick-up and give greater dynamic range.
5. Uniform width control in manufacture insures even, constant tracking.
6. Adequate space on 1/4 inch width for multiple sound tracks.
7. The non-magnetic tape backing between the layers of magnetic coatings in the roll prevents "cross-talk."
8. Easy to handle. No snarls, backlashes, or kinks.
9. Freedom from breakage. Resin treated backing provides a tensile strength of 8 to 10 pounds.
10. Can be marked on back to indicate start and stop of different sound sequences in the same roll.
11. Easily edited by snipping out unwanted portions and then taping together with "SCOTCH" transparent Tape.
12. Perfect reproduction for several thousand playbacks. Erases clean with low power—no special erase head required.



*Licensee of Armour  
 Research Foundation*

Made in U. S. A. by **MINNESOTA MINING & MFG. CO.** Saint Paul 6, Minn.

THE **3M** COMPANY

**DON'T LET OTHERS PUT YOU  
OUT OF THE PICTURE!**



## Here's How CREI Home Study Training Prepares You NOW for a BETTER Job and a SECURE Career in Radio-Electronics and Television

**CREI Courses for Every Radioman Keep You Ahead of Competition—Earn You More!** Never before have so many men like you had the opportunity to step ahead into better-paying jobs and enjoy lasting success. Men with up-to-date technical training are needed in every branch of radio-electronics. That's because radio's *manpower* has not kept pace with radio's *technical* developments.

What are you doing to meet this need for highly trained, expert technicians and engineers? You must improve your technical knowledge not only to qualify for the better job you want, but to *hold* the job you now occupy. CREI offers you a proved program of technical self improvement that you can study in your spare time, at home. The same type of practical, down-to-earth training for which thousands have enrolled since 1927.

Remember, too, there's a CREI course for *you*. No matter what your radio experience—CREI offers complete training in radio-electronics for *any* man who wants to improve his ability and his chances for advancement. You can "go all the way with CREI" from introductory basic principles to advanced training and on to specialized engineering subjects.

Read our 24-page booklet and a free sample CREI lesson . . . then judge for yourself. There is no obligation. You are already started in this field. Find out how you can rapidly prepare to advance beyond your present level. Send the coupon NOW!

**VETERANS! CREI TRAINING AVAILABLE UNDER THE "G. I." BILL!**

### Capitol Radio Engineering Institute *An Accredited Technical Institute*

DEPT. RN-10, 16TH AND PARK ROAD, N. W., WASHINGTON 10, D. C.

Branch Offices: New York (7): 170 Broadway • San Francisco (2): 760 Market St.


## SAMPLE LESSON **FREE**

Now, see for yourself! Mail the coupon for free sample lesson and see how simple it is to study at home and improve your ability the CREI way.

**"ELECTRON PHYSICS AND ELECTRON THEORY"**—This interesting lesson from the Radio-Electronics course discusses modern theories of the composition of matter, including *atomic energy*, and their relation to present-day radio and electronics.

**"PICK-UP TUBES—ICONOSCOPE AND IMAGE DISSECTOR TUBES"**—An informative lesson from the Television course. These are the fundamental pick-up tubes of the television camera. It precedes the study of the Orthicon and the Image Orthicon.
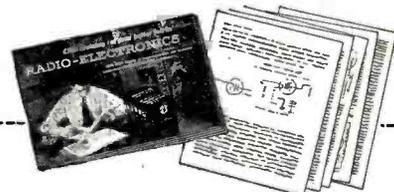
### MAIL COUPON FOR FREE BOOKLET & SAMPLE LESSON



#### CAPITOL RADIO ENGINEERING INSTITUTE

16th & Park Rd., N.W., Dept. RN-10, Washington 10, D. C.

Mail me ONE FREE sample lesson and your 24-page booklet, "CREI Training for Your Better Job in Radio Electronics". I am attaching a brief resume of my radio experience, education and present position.

Check One  PRACTICAL RADIO-ELECTRONICS  
Course:  PRACTICAL TELEVISION

NAME \_\_\_\_\_

STREET \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

I am entitled to training under the "G. I." Bill.



Courtesy of Science Illustrated

Captain Bjorn Arnold Rorholt,  
c/o Norwegian Embassy  
Washington, D. C.

Los Angeles, Calif.

Dear OM,

I have the answers to the questions regarding the radio equipment on the Kan-Tiki; I will first put the question as sent to them and then their reply

- 1 - Q, Have you tried generator GN58 for receiver?  
A, No.
- 2 - Q, How many batteries did you take?  
A, All 41 six volts and 30 forty-five volts.
- 3 - Q, Is there any difference in output between generator and battery operation?  
A, Not tried yet.
- 4 - Q, Are you using 6995 KC crystal from the ten meter rig?  
A, Yes, but ten meter rig in use too.
- 5 - Q, Have you removed last audio valve in 173 Receiver?  
A, Tried, but receiver then too weak.
- 6 - Q, What kind of antenna do you normally use?  
A, L antenna
- 7 - Q, Have you tried balloon or kite supported antennas?  
A, Both tried.
- 8 - Q, Have you tried voice modulation since shortly after leaving Peru?  
A, Yes, results not good.
- 9 - Q, Do you use mark two transmitter?  
A, Yes, and then very good.
- 10 - Q, How does the NC-173 stand up under conditions on board?  
A, Excellent.
- 11 - Q, How many hours can you operate the transmitter on one set of batteries?  
A, High tension batteries very long life but long articles kill our heater batteries.

In case you did not hear me yesterday their heater batteries are used but Raaby tells me that they make 1½ volt units from their 45 volt batteries and then use four of these for six volts and thus get about four days service from each set. They have about five sets left so are O.K. for sometime yet.

"Pen" sends his vy 73 to you as do I and I hope to work you again soon. I am anxious to meet the boys but I am also going to miss these daily contacts with the raft.

I hope Knut, and Torstein keep up their radio and get on the air when they get back to Norway for I would enjoy very much keeping up our friendship via amateur radio.

Again VY73 to you Pronto and hope to cul.

Very Sincerely,

HAL -W6EVM



**NC-173**

Frequency coverage from 540 KC to 31 mc plus the 48-56 mc range. Calibrated amateur band spread on 6, 10-11, 20, 40 and 80 meter bands.

Amateur Net...NC-173 (with speaker) \$189.50



The press of the entire country has carried stories concerning the day-to-day activities of the 6 young Norwegian scientists, members of the Kon-Tiki Expedition, who set out on a raft to drift more than 5000 miles across the Pacific Ocean.

Very little mention has been made, however, of the battery-powered transmitter and model NC-173 receiver which allowed the Expedition to dispatch over 500 messages and 30,000 words.

These figures furnish one more proof that a National receiver in the hands of a good operator makes an unbeatable combination.

**National  
Company, Inc.**

**Dept. No. 15**


**Malden, Mass.**

**U. S. A.**

MAKERS OF LIFETIME RADIO EQUIPMENT
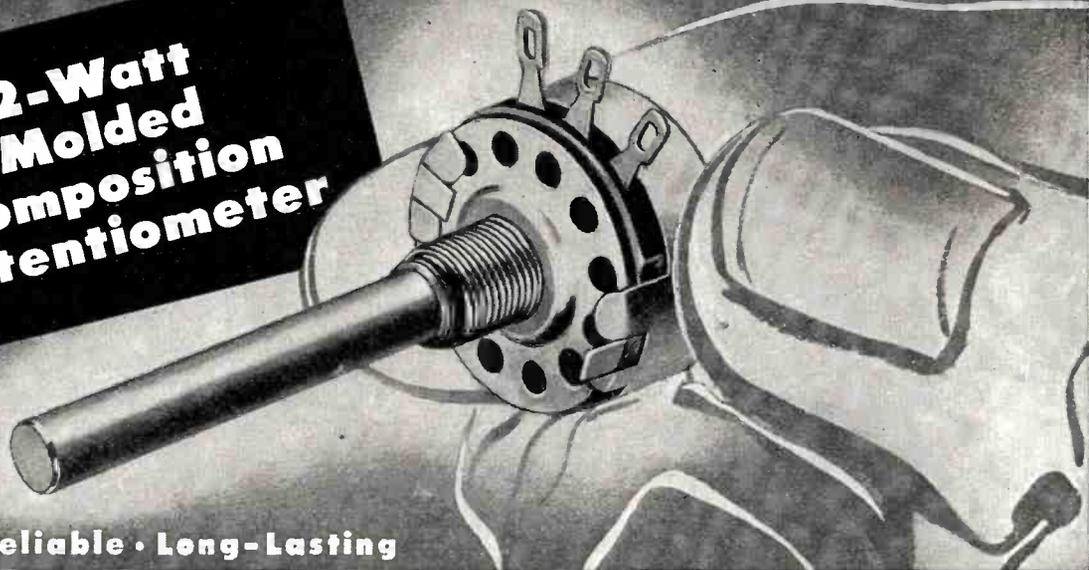
# New OHMITE

**2-Watt  
Molded  
Composition  
Potentiometer**



**Rugged • Reliable • Long-Lasting**

*A high quality unit...* **withstands  
heat, cold, moisture and severe service**

• Nothing like this potentiometer has ever been offered to the industrial market through the radio parts distributor. It is primarily a high quality unit—built to last. The resistor material is not of the paint or film type, but is solid molded. Heat, cold, or moisture cannot affect it. Wear does not change its contact resistance, hence the control retains its very low noise characteristic. Furthermore, it has a 2-watt rating with a good safety factor.

**Sold only through Ohmite distributors**

### Specifications



Terminals are imbedded in solid molded resistor element.

**RESISTANCE:** Max resistance values, 50 ohms to 5 megohms in linear taper. Also logarithmic tapers in limited ranges.

**POWER:** Max continuous rating at 100% rotation —2.25; 50%—2.0; 25%—1.3.

**VOLTAGE:** Max cont. across entire resistor, 500 volts provided wattage rating is met.

**AMBIENT TEMP:** From —60 C to + 100 C.

*...another NEW  
Ohmite item*



**± 5% TOLERANCE  
LITTLE DEVIL  
COMPOSITION RESISTORS**

• These popular resistors are now available in ½- and 1-watt sizes in tolerances of ±5%—in addition to the standard ±10% units. The resistance and wattage are clearly marked on every unit. *Sold only through Ohmite Jobbers.*

**OHMITE MANUFACTURING CO.**

4884 Flournoy Street, Chicago 44, Illinois



*Be Right with*

# OHMITE

**RHEOSTATS • RESISTORS • TAP SWITCHES • CHOKES • ATTENUATORS**



# Use my 19 years of Radio Experience To Double Your Earning Cut Servicing Time in 1/2

**30 LECTURES COMPLETE \$3.00 ONLY**

Get ahead in radio servicing by using ideas and tricks of an expert. Add years of valuable experience to your present radio knowledge. Improve your servicing ability double-quick; avoid costly mistakes. Use this new giant 3-in-1

lecture-manual of practical facts, time-saving hints, hundreds of circuits, suggestions, "know-how" tips, and explanations. Lick the hard cases in a jiffy. Find the cause of every puzzling radio defect. Use M. N. Beitman's 19 years of successful radio experience to your own advantage.

## SOLVES ALL ADVANCED SERVICING PROBLEMS

Let these lectures show you how to improve your store or shop, how to obtain free advertising for your business, what to charge, and how to keep records. Down-to-earth practical help on the business side of radio. Many lectures describing circuits, operation, and application of modern radio test equipment of every type. Meters, volt-ohmmeters, vacuum tube voltmeters, tube testers, analyzers, signal generators, oscilloscopes, signal tracers, condenser testers, Q-Meters. Units of RCA, Weston, Precision, Supreme, Superior, Meissner, Feiler, Biley, and others completely described. Also fourteen lectures on radio circuits and advanced trouble-shooting. See list of topics at left. Material on television. Frequency modulation lecture originally delivered by Westinghouse engineers.

## KNOWLEDGE TO PUT YOU ABOVE COMPETITION

Complex and unusual radio faults may waste hours of your valuable time. The author has foreseen all possible problems (above the elementary level) and provided explanations and practical solutions in this unique on-the-job manual. Keep it on your work bench to aid and guide you on tough repairs. Use the thousands of advanced hints and servicing suggestions to speed up routine jobs. No other training book or course can compare to this new manual. Published in September 1947. Be first to use it and forge ahead of others. Learn to do complicated repairs in minutes instead of hours.

## LECTURE-COURSE WORTH \$60 YOURS FOR ONLY \$3

Think what it would have cost you to attend in person the 30 lectures completely printed in *Advanced Radio Servicing* manual. Perhaps \$60, maybe even more figuring carfare. But in this giant volume you have every word of all the lectures, plus illustrations of every slide used, and many additional photographs and charts. And the special bargain price for the complete 30 lectures in the giant manual, as shown at the top of page, is only \$3.00, full price. Take advantage of this remarkable bargain and secure on "no-risk" trial this practical radio training that will add years to your own experience. Send coupon today. Examine and use material for 10 days under our "money-back" guarantee.

**Guarantee**  
We guarantee you complete satisfaction or will refund your total remittance.  
**SUPREME PUBLICATIONS**

**BOOK ONE**  
**BUSINESS SIDE OF RADIO SERVICING**  
Four complete lectures by M. N. Beitman. Discussion of radio service problems. Opening and operating a radio store and shop. Selecting the right location. Store arrangement. Tested advertising ideas that cost little — bring big results. Window display suggestions. Service department. Model shop. What to charge. Bookkeeping and records.

**BOOK TWO**  
**EQUIPMENT USED FOR LOCATING FAULTS**  
Visual and aural time-saving methods. Meters, volt-ohm-milliameters, related circuits. Vacuum tube voltmeters. Voltage and resistance point-to-point servicing. Tube testers (emission, leakage, dynamic, and mutual conductance types). Using a signal generator. Cathode ray oscilloscope as a servicing tool. Tuned signal tracers. Simplified signal tracing technique. Condenser testers. Bridges. Advanced test equipment. 12 illustrated lectures.

**BOOK THREE**  
**RADIO CIRCUITS AND TROUBLE-SHOOTING INCLUDING TELEVISION AND F.M.**  
Fourteen easy-to-follow lectures on radio testing and making repairs. Tests for audio voltage and power amplifiers. Audio corrective circuits. Inverse feed-back. Phase inverters. Understanding impedance. Loud-speakers and output transformer matching. Function and adjustment of tuned circuits (a non-mathematical treatment for servicemen). Detector and AVC circuits. Troubles in R.F. and I.F. stages. Superhet converters and alignment hints. Power supplies; A.C., AC-DC, and doubler types. Television facts. F.M. fundamentals and receiver description. Trouble-shooting and alignment in F.M. receivers. All 30 lectures of all 3 books, only \$3.00; see next column for more details; and send coupon today.

**RADIO SERVICING COURSE-BOOK**  
A Companion Manual for Those Needing More Help  
Here is your fundamental radio training and review course. 22 lessons on radio servicing essentials. Covers every radio topic, just like a \$150.00 correspondence course. Pictures, drawings make text simple to follow and easy to apply. With self-testing questions plus index. Large size: 8 1/2 x 11 in., 224 pages. 6th edition. Complete 22 lessons, only..... **\$2.50**

**Supreme Publications**  
PUBLISHERS OF RADIO BOOKS, MANUALS, AND DIAGRAMS

## NO RISK TRIAL ORDER COUPON

**SUPREME PUBLICATIONS, 9 S. Kedzie Ave., Chicago 12, ILL.**  
Please send manual checked. You guarantee satisfaction or will refund my total remittance.  
 **Advanced Radio Servicing, \$3.00**  **Radio Servicing Course, \$2.50**  
30 Lectures, as described. Elementary companion volume.  
 I am enclosing \$....., send postpaid.  
 Send C.O.D. I am enclosing \$..... deposit.

Name: .....  
Address: .....

**See Your Radio Jobber or Send Coupon —**  
October, 1947

# You're Looking at the Finest—



## —a complete Hammarlund station

An HQ-129-X receiver, the choice of thousands of well-satisfied owners. And a Four-20 Transmitter with its companion Four-11 Modulator, a combination that is getting out all over the world. R9+ reports from China, Argen-

ina, Hawaii, Australia . . . coming in to the many amateurs now using the Four-20 on the air.

You, too, can be in this picture . . . Equip yourself with a complete Hammarlund station.

*There will be no new Hammarlund receiver in the price range of the HQ-129-X until the spring of 1948 at the earliest.*



# HAMMARLUND

THE HAMMARLUND MFG. CO., INC., 460 W. 34TH ST., NEW YORK 1, N. Y.  
MANUFACTURERS OF PRECISION COMMUNICATIONS EQUIPMENT




Write for Descriptive Booklet

# ADAPTING the TBY-7 for Amateur Use

*This easily converted war surplus item covers the 28 and 50 mc. amateur bands.*

By  
W. B. Ford, W6YT

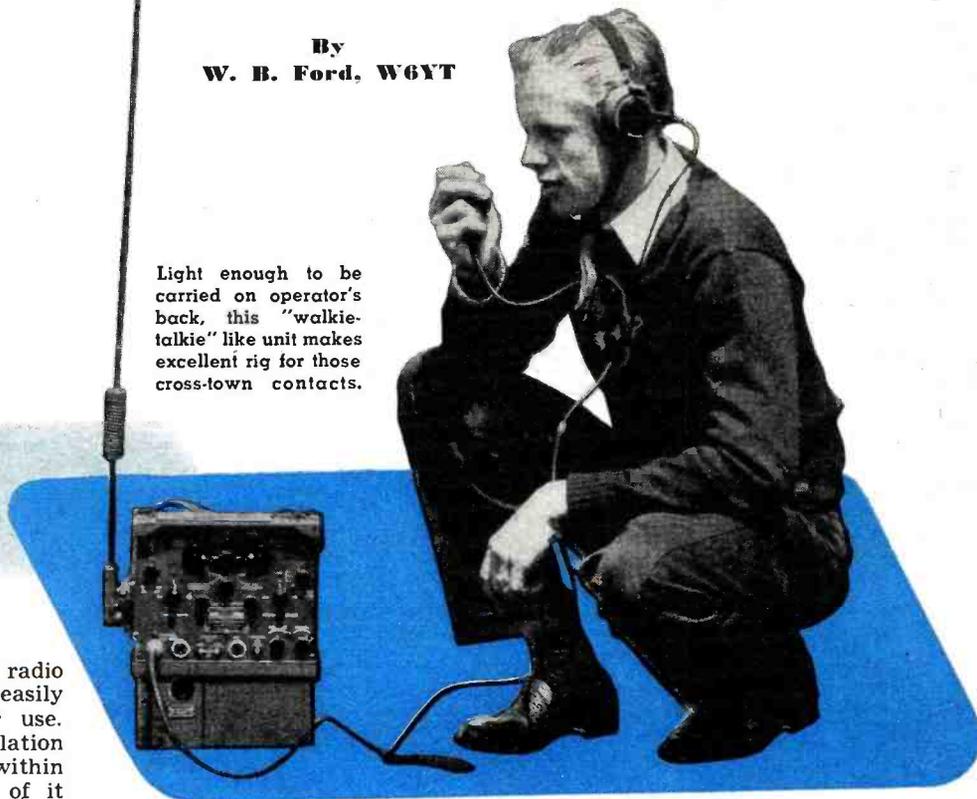Light enough to be carried on operator's back, this "walkie-talkie" like unit makes excellent rig for those cross-town contacts.



**N**OT all of the surplus radio gear now available is easily adapted for amateur use. Some of it requires the installation of new tuning units to bring it within licensed bands, and nearly all of it requires the rewiring of the filament circuits if the equipment is to operate from conventional power supplies. Many of the units were built so compactly that a major operation is necessary before any part of the circuit can be altered, and often the work becomes so involved that the builder begins to wonder if the time could not have been spent more profitably in building new equipment. A notable exception to the above is the little TBY-7 transmitter-receiver, which was used in Navy landing operations.


When the writer first saw the TBY-7 he was impressed with the possibilities it offered as a portable unit for field trips, a mobile rig for the car, or as a supplementary set to the home transmitter when low-powered contacts are desired. Weighing less than 50 pounds, complete with storage battery and vibrator power supply, it is equipped with a canvas carrying case that may be strapped to the operator's back when desired. The battery provides a minimum of 15 hours' continuous operation when the transmitting and receiving peri-

ods are of approximately the same length. When the battery is discharged it may be recharged from the car battery or a convenient six-volt charger. Finally, the transmitting section may be adapted to meet existing regulations with a minimum of circuit changes.


The r.f. section of the transmitter, in its original state, consists of a self-excited oscillator using two 958-A tubes in push-pull. The tuning circuit consists of a split-stator condenser, 22  $\mu\text{fd.}$  per section, and four inductances mounted on a rotating turret assembly, which is controlled by a four-band switch on the front panel. The tuning range is continuous from 28 to 80 mc. The oscillator is inductively coupled to the antenna coil which is, in turn, connected through a send-receive relay switch to a sectional whip antenna mounted on the side of the metal case. An additional terminal is provided to connect the unit to other types of antennas. The antenna circuit is tuned by means of

a 100  $\mu\text{fd.}$  variable condenser mounted on the front panel. The oscillator may be either voice modulated or tone modulated by using the type 30 audio tube as a tone generator. A 5000 kc. crystal is provided for checking the transmitter over its tunable range. A 1E7 twin pentode tube in push-pull serves as a modulator. A push switch on the microphone operates the send-receive relay.

The receiver section consists of an r.f. amplifier using a 959 tube, followed by a superregenerative detector with a 958-A tube. The r.f. and detector stages are tuned over the 28-80 mc. range by means of ganged 14  $\mu\text{fd.}$  condensers and turret coils, similar to those used in the transmitter. The first audio stage uses a type 30 tube, which also serves as a tone generator when m.c.w. is being used. The second audio stage is a push-pull arrangement using the same 1E7 that serves as the voice modulator for the transmitter. Vol-

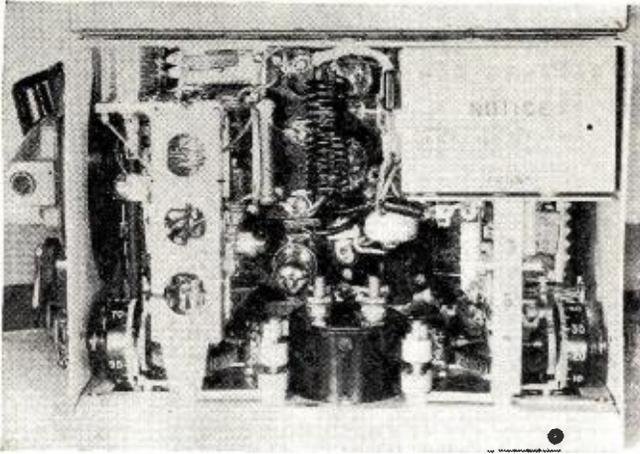

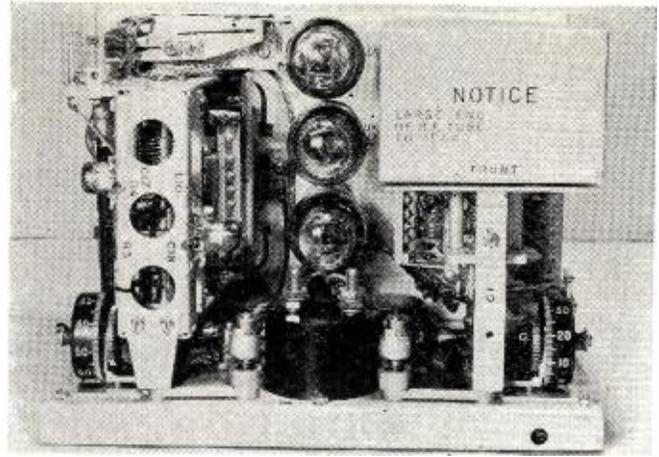Interior view of the TBY-7 after unit has been converted to crystal control. Note crystal oscillator mounted to meter studs.



The TBY-7 before conversion. Tube directly behind meter is removed to provide space for installing the new oscillator unit.

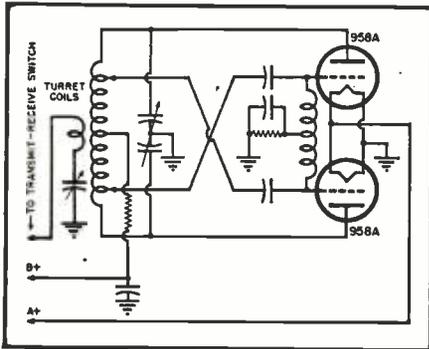


Fig. 1. Schematic diagram of the original wiring for transmitter section of the unit.

ume and regeneration controls are provided on the front panel. Correct filament voltages are maintained through rheostats and a voltmeter mounted on the front panel. The voltmeter also serves as a milliammeter to determine the plate load of the transmitting tubes. The 5000 kc. crystal oscillator used for checking the transmitter also provides checking points for receiver calibration.

The TBY-7 was intended to be used


with a specially built dry-battery pack, which supplies "A," "B," and "C" voltages, or a combination vibrator-storage battery pack with similar outputs. Either of the power supplies may be securely attached to the bottom of the unit. Since both types of power supplies were made solely for use of the Armed Forces, it is very unlikely that any dry battery packs with fresh batteries may be obtained today. The purchaser of a TBY-7 may either make up his own dry-battery pack, or obtain one of the vibrator-storage battery packs generally listed as TBY-7 accessories. From the viewpoint of economy, the vibrator unit is strongly recommended over the dry battery pack, since the present price of the former is little more than cost of one set of batteries. Then, too, there is the matter of easy recharging, which is of no minor importance when one considers the many uses to which the little set may be put.

The vibrator-storage battery combination consists of a four-volt, leak-proof storage battery and a vibrator unit which supplies voltages of 2.35,

3.3, 4.2, 8.6, and 158 volts. The storage battery may be separated from the vibrator for charging, or it may be charged while attached to the vibrator. Only in the former case does the charging polarity have to be observed. When the vibrator and battery are attached together and connected to a six volt storage battery or other charging source, a dry rectifier and relay within the vibrator section case automatically connects the charging source to the four-volt battery at the correct polarity. Floating indicators visible through the side of the battery case permit the condition of the battery to be determined at all times.

In analyzing the original circuit of the TBY-7, it was readily seen that stabilized frequency control would be necessary if it were to comply with present day requirements. Furthermore, since both the transmitting and receiving sections covered two of the licensed bands, namely the 28 and 50 mc. bands, it seemed desirable to include those bands when designing the oscillator for frequency stability. Several possible combinations were

Fig. 2. TBY-7 transmitter after unit was rewired and crystal control added. Balance of the transmitter-receiver remains unchanged.

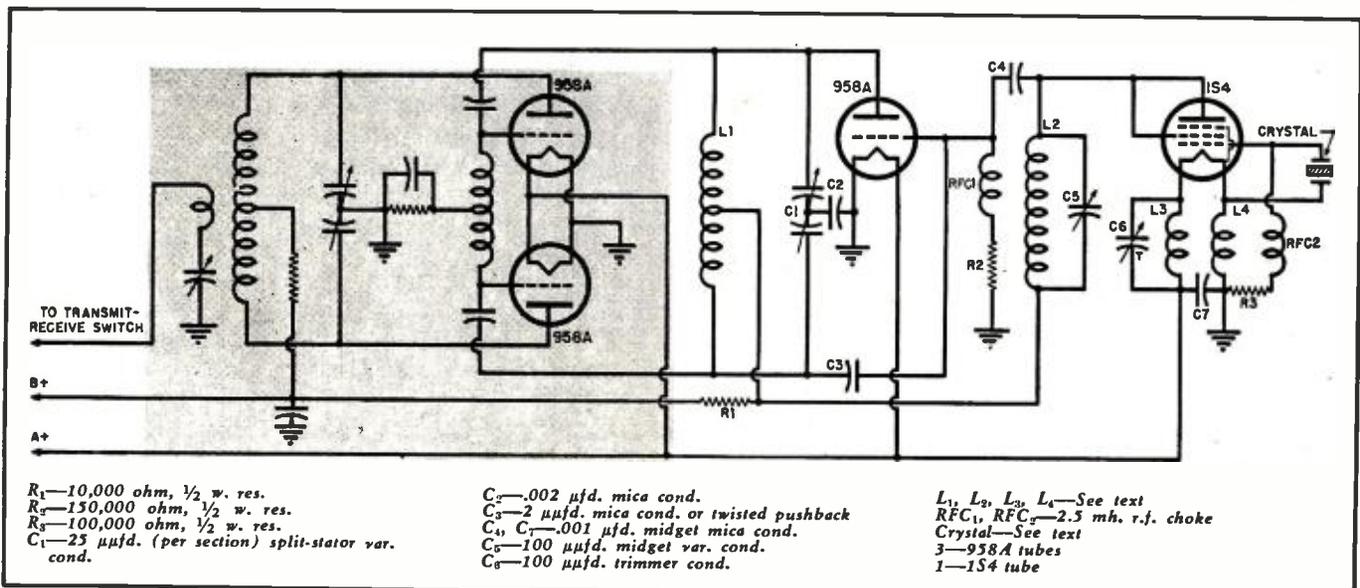

tried on paper and the one finally chosen was one that would require the least changes in the original circuit, that change being the switching of the grid leads in the self-excited oscillator from the turret coil to the buffer-doubler or buffer-tripler coil, depending upon the frequency of the final stage. Like most of the radio equipment designed for the Armed Forces, there is little wasted space in the TBY-7, hence the matter of finding space for the two stages necessary to cover the frequency ranges desired presented a real problem. Space was finally provided by removing the type 30 tube (directly back of the voltmeter) which served as a crystal calibrator for checking the transmitter and receiver. The small space occupied by the 5000 kc. calibration crystal was not needed, but since the crystal was no longer required for its original purpose, it was removed and set aside for some future use.

A crystal oscillator stage was mounted on a piece of  $\frac{3}{8}$  inch bakelite as shown in Fig. 3. Two strips of 20 gauge sheet steel, drilled and shaped as shown, serve as brackets to mount the oscillator stage on the meter terminals. The ends of the mounting brackets are bent in opposite directions, so that they can be mounted on the bakelite strip at the proper angle. Since the brackets will be "hot" whenever the voltmeter is in use, care should be taken that they do not make contact with any other metal parts of the oscillator stage. A 1S4 tube connected as a triode serves as the oscillator. This tube was preferred to an acorn type, due to its smaller socket requirements. The 1S4 is connected in parallel with the 958-A filaments (Fig. 2) in the transmitter, so that its filament voltage is slightly below the specified 1.4 volts. This, however, seems to have no effect upon the operating efficiency of the tube. The oscillator tube doubles in its plate circuit for both operating frequencies and uses a 7194 kc. crystal for the 28 mc. band, and an 8650 kc. crystal for the 50 mc. band.

The inductances  $L_2$  and  $L_1$  consist of eight turns each of No. 20 d.c.c wire, wound side by side on a 1 inch form.  $L_2$  is tuned with a 100  $\mu$ fd. trimmer and once adjusted needs no further attention. The inductance  $L_1$  consists of 14 turns of No. 16 enameled wire, closewound on a 1 inch form, and is tuned with a 100  $\mu$ fd. midget variable condenser. This combination tunes both doubled frequencies and provides ample excitation to the following buffer stage. Single tip jacks are used for the crystal holder.  $RFC_1$ ,  $RFC_2$  and  $R_3$  are mounted on the under side of the bakelite strip. The positive filament lead from the 1S4 tube is connected to the filament terminal of the 958-A transmitting tube, directly above the transmitter turret coils.

The buffer stage consisting of a 958-A tube is mounted on the side of the

detector shield can and its associated tuning unit,  $L_1$  and  $C_1$ . The tuning unit consists of a split-stator condenser, 25  $\mu$ fd. per section, and air-wound coils for the particular frequency being used. By using a condenser of larger capacity, one coil could have been made to cover both frequencies, but to provide a satisfactory  $L/C$  ratio, it was deemed advisable to provide two coils. The occasion is rare when it is desired to change from the 28 mc. to the 50 mc. band, or vice versa, instantly, but even when the time element does enter, the coils may be changed in a matter of a few seconds. The variable condenser is mounted on the back of the metal cabinet. Mounting holes may vary with different makes of condensers. The condenser is adjusted by means of a screwdriver and is of the locking type. The buffer stage coil mount consists of a  $\frac{1}{8}$  inch piece of bakelite, properly drilled and tapped. This strip is mounted directly upon what would be the bottom of the condenser, the condenser being mounted on the cabinet with the bottom side up. Clip for securing the coils to the bakelite strip consists of pieces of No. 26 gauge spring brass. The inductance  $L_1$  consists of 14 turns

No. 16 enameled wire,  $\frac{5}{8}$  inch i.d., air wound,  $1\frac{1}{4}$  inch long, for the 28 mc. band, and 6 turns No. 16 enameled wire,  $\frac{5}{8}$  inch i.d., air wound, 1 inch long, for the 50 mc. band. The resistor  $R_3$  is mounted on terminal strips soldered to the metal frame directly above the end of transmitter turret coils. Before the lid of the metal cabinet could be closed it was necessary to remove the metal frame that held the spare acorn tubes, which was riveted to the lid.


Tuning the transmitter is done in the conventional manner. Since two additional tubes will register current beyond the original center mark of the milliammeter, that marking should be disregarded. With proper antenna loading the meter needle will swing to about three-fourths full scale, dipping in the usual manner when resonance is reached.

Even with the low power output of this transmitter, many satisfactory DX contacts may be made on either 28 or 50 mc. when conditions are right. There is a particular thrill in a good contact made with this extremely low power.

During the few months the author has owned the converted TBY-7 it has

(Continued on page 201)

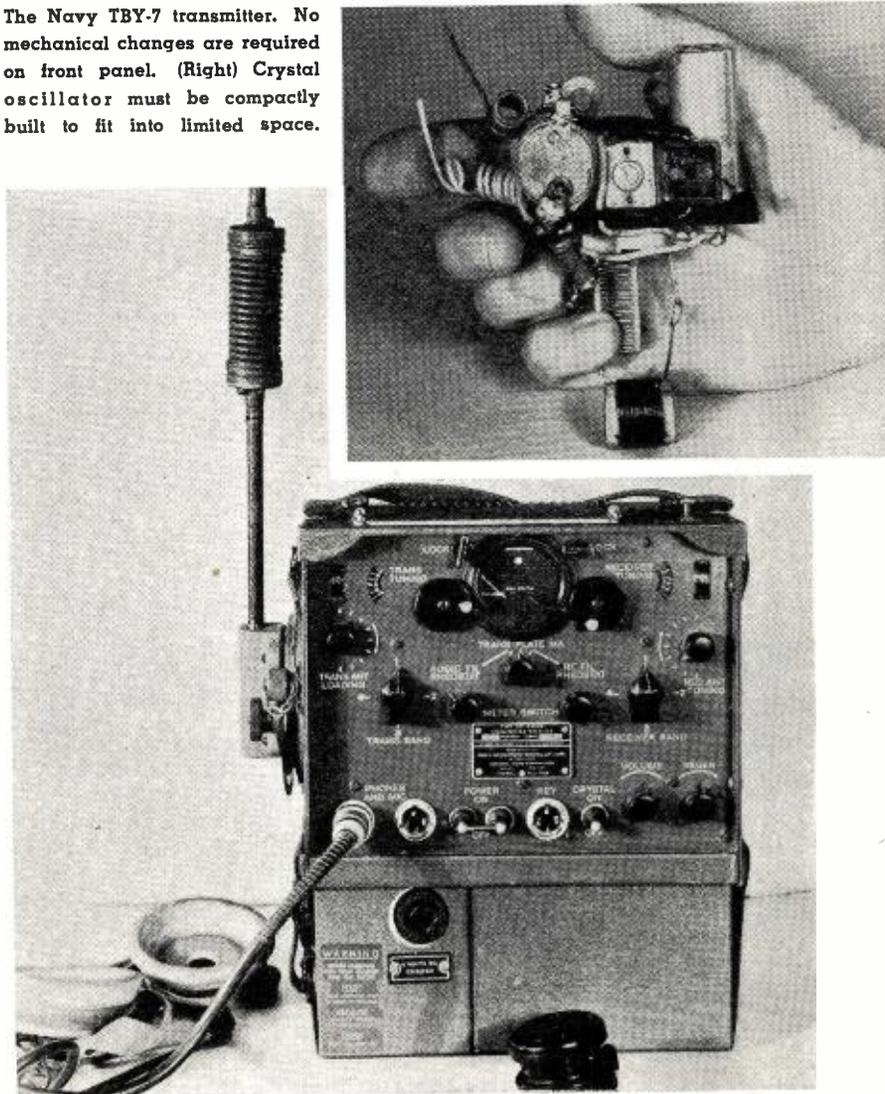The Navy TBY-7 transmitter. No mechanical changes are required on front panel. (Right) Crystal oscillator must be compactly built to fit into limited space.



# A SIMPLIFIED SIGNAL GENERATOR

By  
**H. G. PRATT, WBSEA**

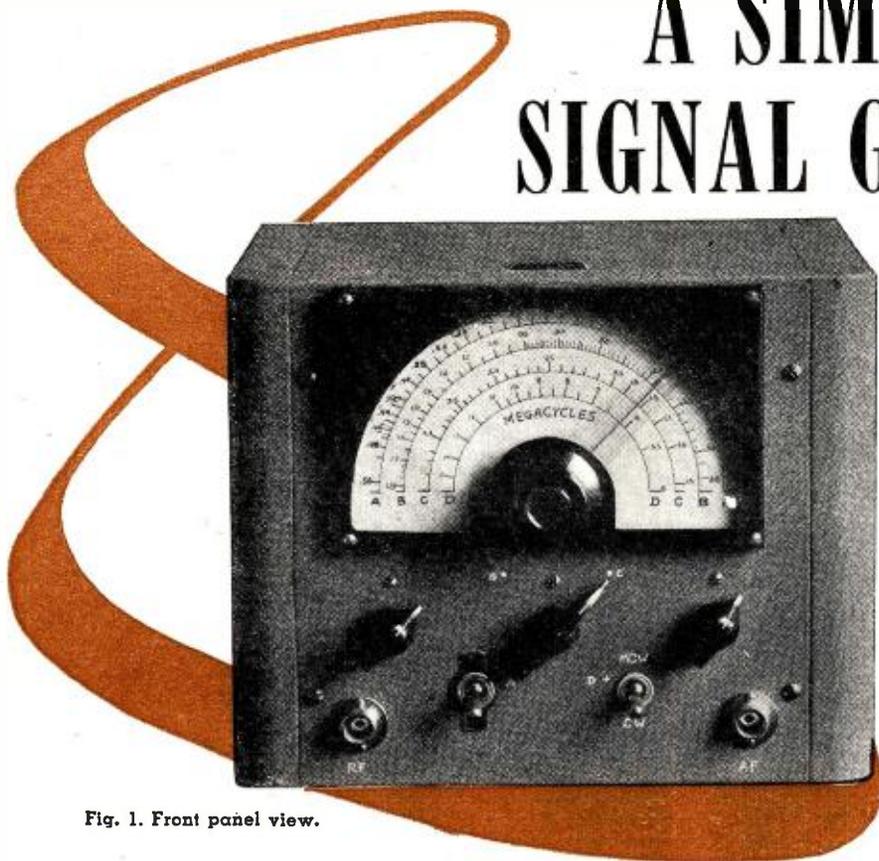



Fig. 1. Front panel view.

**A low-cost signal generator that covers 170 kc. to 15 mc. in four bands. Separate audio signal is also available.**

**I**N VIEW of the general scarcity of new test equipment, it is felt that many amateurs and servicemen will be interested in a description of a simple and economical signal generator.

As can be seen from the schematic (Fig. 3), the design is straightforward, including only the features that are essential to the average job of alignment and troubleshooting by the signal injection method.

Fig. 2. Top view shows parts layout.

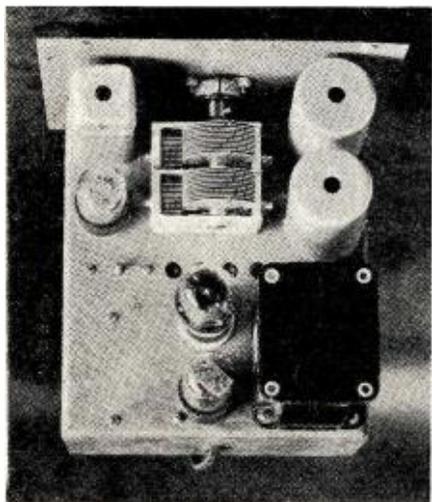

One half of a 6SN7 tube serves as the r.f. oscillator in the conventional tuned grid oscillator circuit. Four coils, in conjunction with the two-gang variable condenser, are used to cover the range from 170 kc. to 15 mc. A three-gang rotary switch is used to select the desired coil. All coils are equipped with permeability tuning slugs and trimmer condensers. Determination of the frequency range for each coil resulted from the following reasoning. Band A should cover all intermediate frequencies commonly used in the average receiver. Recalling that several old sets using 175 kc. i.f. amplifiers are still in circulation, (those 1928 models that just won't give up) this coil is adjusted for a lower limit of 170 kc. With the tuning condenser specified, the high frequency end can be trimmed down to 500 kc., just to keep it in round numbers.

The second coil, for Band B, should cover the entire broadcast band for convenience in aligning the front end of broadcast receivers. As a single 240  $\mu\text{f}$ d. variable condenser will not cover this range easily, the second section of the dual condenser is connected in parallel on this band only. A single 365  $\mu\text{f}$ d. condenser could have been used instead, but would have reduced the bandspread on the higher frequency bands.

The third coil, used on Band C, is adjusted for a low frequency limit of 1500 kc., which allowed the high frequency end to be rounded off at 5 mc.

The fourth coil, designated Band D, is then adjusted for a low frequency limit of 5 mc. and the upper limit is about 15 mc.

Output from the oscillator is taken from the plate through an attenuator network and coupling condenser to the front panel "R.F. Output" jack.  $C_{10}$  at the output jack allows the generator to be connected to the plate of a receiver tube without using an external blocking condenser.

## Audio Frequency Section

The second half of the 6SN7 is used as the audio oscillator and modulator. An audio transformer serves as a tuned grid circuit and feedback coil for this oscillator. Plate voltage for the r.f. oscillator is taken from the audio oscillator plate to produce a modulated output.  $S_2$  opens the cathode circuit of the audio oscillator for unmodulated r.f. output. An audio coupling network and attenuator is incorporated to provide a variable a.f. signal at the front panel jack.

## Power Supply

A transformer type power supply is used to avoid unhappy entanglements with a.c.-d.c. sets. As the current drain is low, a resistance-capacity filter is used. A VR150/30 tube is connected across the output, and greatly improves the oscillator stability.

## Construction

\* Figs. 2 and 4 show the general location of component parts on the 7 x 7 inch chassis. The tuning condenser is mounted in the center, on top of the chassis, with the bandswitch directly below. The coils are mounted on either side of the tuning condenser, allowing easy wiring of the r.f. circuits. Four trimmer condensers, one for each coil, can be seen directly behind the tuning condenser. The 6SN7 tube is located near the tuning condenser, with the audio transformer on one side and the power supply on the other side. A fair degree of isolation is obtained by the location of parts, and by placing shields over the coils. The entire unit is housed in a metal cabinet to provide further shielding.

The oscillator coils are the only components that require special comment.  $L_1$  and  $L_2$  are both replacement windings for 455 kc. i.f. transformers, mounted on a polystyrene coil form, fitted with an adjustable powdered iron slug. The use of a tuning slug allows the inductance to be adjusted to the desired value without resorting to the tedious process of removing or adding turns to the coil. When first assembled,  $L_1$  is cemented in place with coil dope, while  $L_2$  is left free to slide on the form until the proper location is determined (as described under "Adjustments").

$L_3$  and  $L_4$  make up the coil for Band B, and is one of the "universal replacement" broadcast band r.f. coils which comes equipped with a tuning slug. No modification need be made on this coil.

$L_5$  and  $L_6$  are used on Band C. The grid coil ( $L_5$ ) is wound with 85 turns of #28 enameled wire, closewound on a half inch form. The plate coil ( $L_6$ ) consists of 60 turns of the same wire, jumble wound as shown in Fig. 5.

$L_7$  and  $L_8$  are grid and plate coils for Band D. The grid coil is wound with 13 turns of #28 enameled wire, spaced one diameter between turns, on a half inch form.  $L_8$  is separated  $\frac{1}{8}$ " from the grid coil, and consists of 13 turns of #28 wire, closewound. This coil is also provided with a tuning slug for final adjustment.

The location of parts is such that short, direct leads may be used in the r.f. wiring, and shielded leads are not required. However, all leads in these circuits should be of solid wire which will not be easily jarred around, as any movement would otherwise cause an unstable signal and errors in calibration.

The dial used is one having a blank scale, upon which the final calibration may be marked with drawing ink.

#### Initial Adjustments

After wiring has been completed and checked, a few adjustments will be necessary before calibration is started. First remove the 6SN7 tube and connect a milliammeter in series with the VR tube (point "X," Fig. 3). As soon as the rectifier has warmed up,  $R_7$  may be adjusted until the meter reads 25 to 30 ma. This adjustment is not critical, and is only to insure that the VR tube is operating within its ratings.

The next step is to check the r.f. oscillator on all four bands. With the 6SN7 in place, remove the shield from Coil A, and connect a milliammeter in the grid return of the r.f. oscillator (point "Y," Fig. 3). With the band-switch on Band A, and the power turned on, oscillation will be indicated by a deflection of the meter. The position of  $L_2$  may now be adjusted until grid current of about one ma. is obtained. Now rotate the tuning condenser from maximum to minimum while observing the grid current. If the current should drop to zero, coupling must be increased by moving  $L_2$  closer to  $L_1$ . If the grid

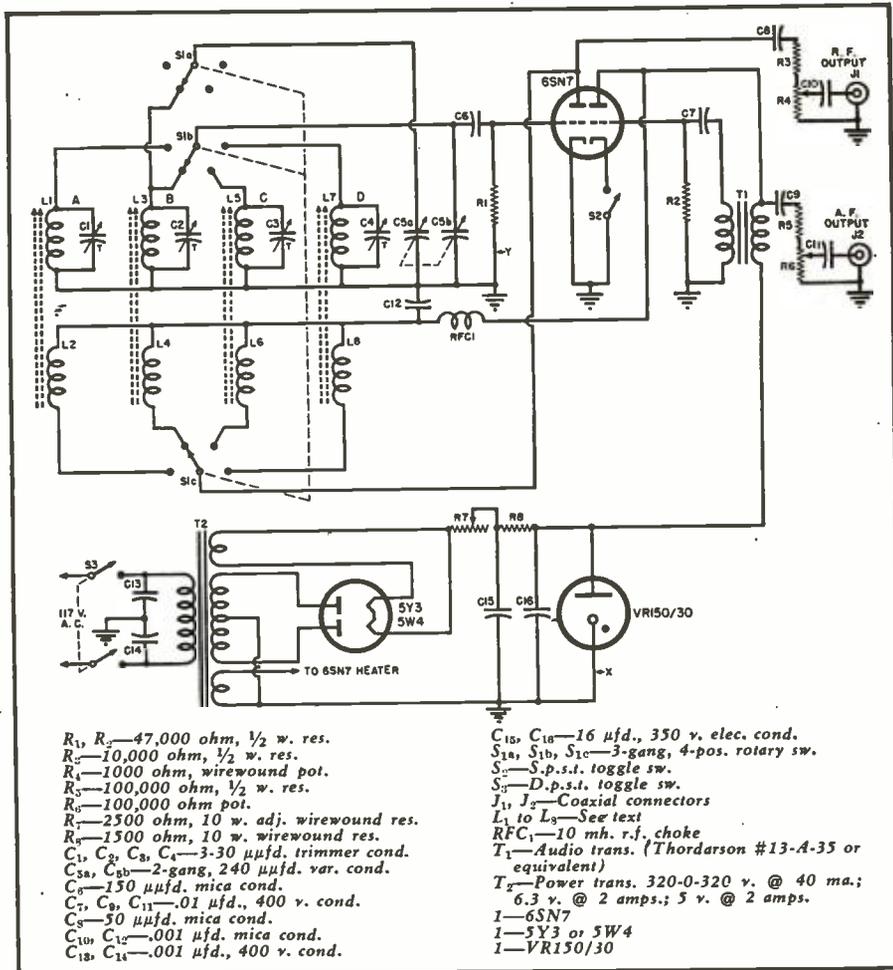


Fig. 3. Schematic diagram of a.c. operated signal generator.

current tends to jump or become unstable (caused by the oscillator blocking or motorboating), coupling must be reduced by increasing the spacing between  $L_1$  and  $L_2$ . It is to be expected that the grid current will change somewhat across the band due to the changing LC ratio, however, the fluctuations should be smooth and gradual. Abrupt changes, caused by overcoupling, indicate a change in mode of operation and must be avoided. Likewise, too little coupling will result in oscillation failing or becoming unstable over a portion of the band. After the proper location for  $L_2$  is determined, it is cemented in place with coil dope and the shield replaced.

With the meter still in the grid circuit, check the operation of the remaining three bands by observing grid current as in the case of Band A. With the coils specified, no difficulty should be experienced. However, should there be an indication of improper coupling it may be corrected by either of the two general methods listed below.

To increase coupling: Move the grid and plate coils closer together or increase the number of turns on the plate coil.

To reduce coupling: Move the coils farther apart, or decrease the number of turns in the plate coil.


Should one coil completely fail to

oscillate at any point, it is advisable to check the wiring first, as no amount of coupling will cause oscillation if one of the coil connections is reversed.

Like most adjustments, these are easier to make than to describe, and actually not too critical. Any value of grid current from about  $\frac{1}{2}$  to a maximum of 5 mils will give satisfactory results.

The audio oscillator may be (Continued on page 176)

Fig. 4. Under chassis view.

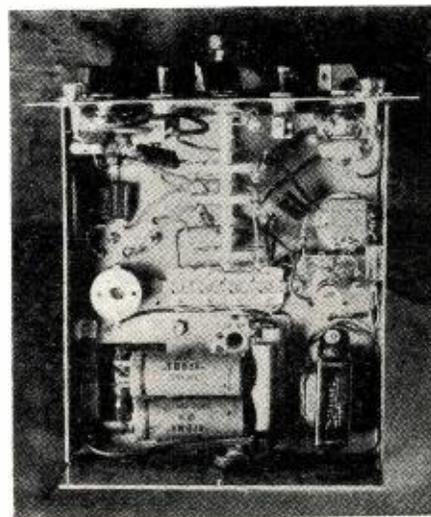

# 10-METER MOBILE FM TRANSMITTER

By  
**RAY FRANK, W9JU**  
Associate Editor, RADIO NEWS

**Construction details for a compact narrow-band FM rig with filament type tubes and stable oscillator.**

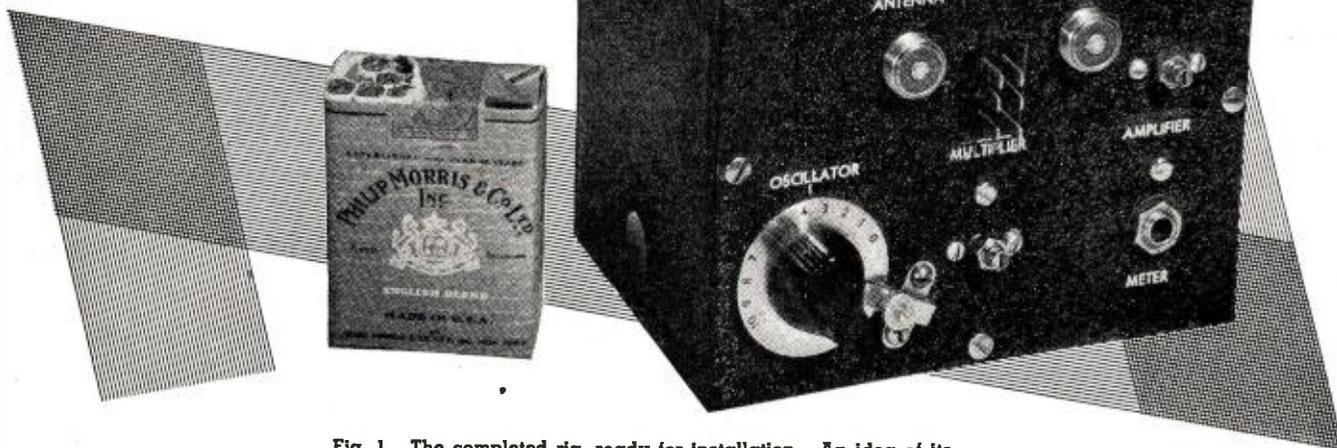


Fig. 1. The completed rig, ready for installation. An idea of its size may be gained by comparison with a package of cigarettes.

**T**HE use of amateur narrow-band FM has up until the present time generally been confined to fixed stations. Inasmuch as police and other emergency services have been using narrow-band FM with great success for several years, it was decided to try this type of modulation for amateur mobile work. The transmitter to be described is giving an excellent account of itself on 10-11 meters, in W9ETI's NBFM mobile installation.

There have been many different types of FM transmitters described in the various publications in the past few years. Some have used crystal control, while others have resorted to the v.f.o., modulated by a reactance tube. It was felt that the use of a v.f.o.-reactance tube type would offer greater versatility for mobile work as it is easily possible to QSY to get away from interference.

One of the difficulties of the v.f.o. type is the attainment of the necessary stability of the oscillator, under the extreme vibration encountered in this type of service. In addition, to keep the rig simple, the output of the oscillator must be relatively high to keep the number of stages to a minimum.

The completed rig, exclusive of the power supply, is illustrated in Fig. 1. The case used is a standard 4 by 5 by 6 inch box. The small size is deliber-

ate to allow the placing of the rig in almost any location in the car. Components used, however, are all standard, and there is no noticeable loss of efficiency, or undue crowding.

The lineup consists of a 2E30, used as an oscillator, a 2E30 tripler, and a 5516 final amplifier. An 0A2 voltage regulator is used to hold the voltage constant on the oscillator and reactance tube. Modulation is supplied by a 9001 used as a reactance tube.

There is no battery drain, except that of the 9001 heater, until the microphone switch is closed. This results in a great saving of power during listening periods.

A 2E30 was tried in place of the 9001 reactance tube, in an effort to reduce the battery drain to zero during standby periods, but the characteristics of this tube are such that satisfactory performance could not be obtained. Unfortunately, none of the filament type tubes available in miniature sizes have characteristics suitable for this application.

A chassis measuring  $3\frac{3}{4}$  inches wide, 5 inches long, and 2 inches deep is formed from scrap aluminum. The microphone transformer  $T_1$  is mounted in the right center, with the four miniature tubes grouped about it. The top view of the chassis, Fig. 4, clearly shows this placement. The

9001 reactance tube is mounted at the right lower corner, with the 2E30 oscillator near the front panel. The oscillator coil,  $L_1$ ,  $L_2$ , is mounted below the chassis between these two tubes.

To the left of the transformer are mounted the 0A2 regulator tube along the rear edge, and the 2E30 tripler in the front center. The final tank coil  $L_4$ ,  $L_5$  and the final tuning condenser  $C_{21}$  are mounted to the left of the doubler. The final tube is located at the left center, with the antenna relay  $RL_1$  in the lower left corner.

In the under chassis view, Fig. 3, parts are shown located to afford the shortest leads. The bandset condenser  $C_9$  is mounted along the left edge of the chassis by means of a small bracket, and once set, need not be touched again. A plug button on the side of the case allows this condenser to be adjusted after the transmitter is placed in the case, if necessary.

No audio stage is used, the microphone transformer feeding directly into the grid of the reactance tube. Deviation is controlled by means of a one megohm potentiometer  $R_2$ . As this control need not be changed once set, it is mounted along the rear edge of the chassis and a screwdriver slot is cut in the end of the shaft.

The tuning condenser for the oscil-

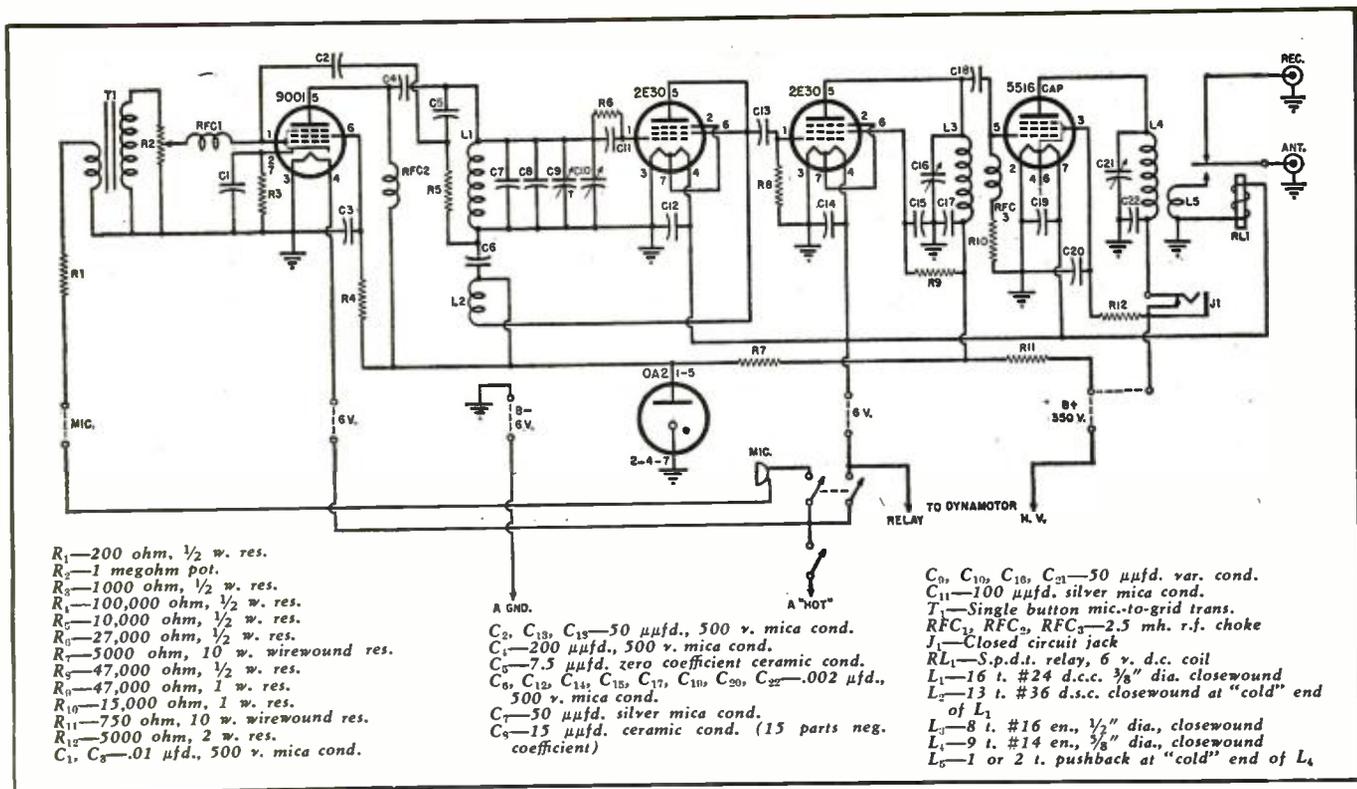



Fig. 2. Schematic diagram of the complete rig. A suggested control system is shown.

lator  $C_{10}$  and the tripler plate condenser  $C_{16}$  are mounted at the left side and center respectively, of the chassis. A closed circuit jack  $J_1$  is mounted at the right hand side to permit measuring the final plate current.

The oscillator coil is wound on a  $\frac{3}{8}$  inch diameter ceramic form, salvaged from a piece of surplus equipment. It is desirable to use a ceramic form in this position as the change in dimensions with temperature change is negligible. This results in much better frequency stability. A pillar type standoff insulator may be used if a coil form is not available.

The tripler tank coil,  $L_3$ , is wound on a piece of  $\frac{1}{2}$  inch diameter polystyrene rod and is located just to the right of the tripler plate condenser.

Fig. 3. Bottom view of the chassis. The bandset condenser is located at the left hand side and mounted by a small bracket.

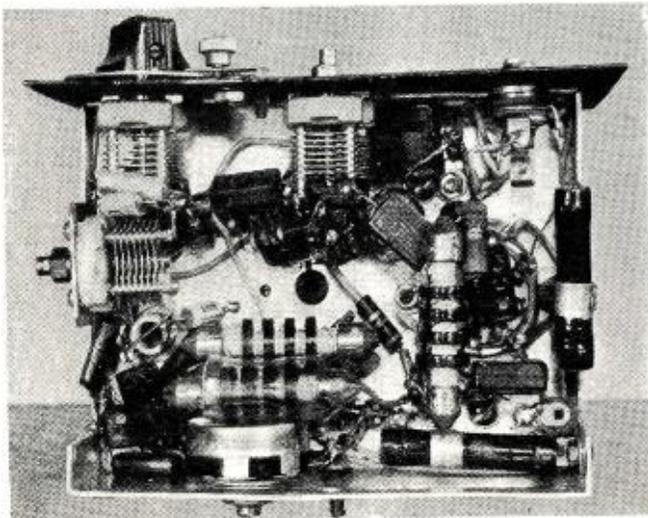

To allow the shafts of the tuning condensers to be at ground potential the "cold" ends of the tripler and final tank coils are connected to the condensers by means of bypass condensers, rather than direct. It is desirable to use mica condensers in these positions to keep the losses low.

All variable condensers used were of the APC type. The particular ones used are equipped with locking nuts, although this is not necessary. The condenser used for oscillator tuning,  $C_{10}$ , has a  $\frac{1}{4}$  inch shaft, which permits the attachment of a small dial. This dial is equipped with a lock to insure against accidental movement.

The two voltage dropping resistors  $R_7$  and  $R_{11}$  are mounted under the chassis as far from the oscillator com-


ponents as possible. It would probably be preferable to mount these units above the chassis to eliminate as much heat as possible from under the chassis.

Wiring of all components associated with the oscillator section should be very rigid. Any mechanical movement of parts in this section of the transmitter will have a serious effect on the frequency.

It was decided at the outset, that inasmuch as FM is also allowed on the 11 meter band, that the transmitter should be capable of operation on this band as well as ten meters. The oscillator works on one third the output frequency, so, in order to cover the range of 27,160 kc. to 29,700 kc., a

(Continued on page 124)

Fig. 4. The four miniature tubes are grouped around transformer, T1, with antenna relay mounted below the final.

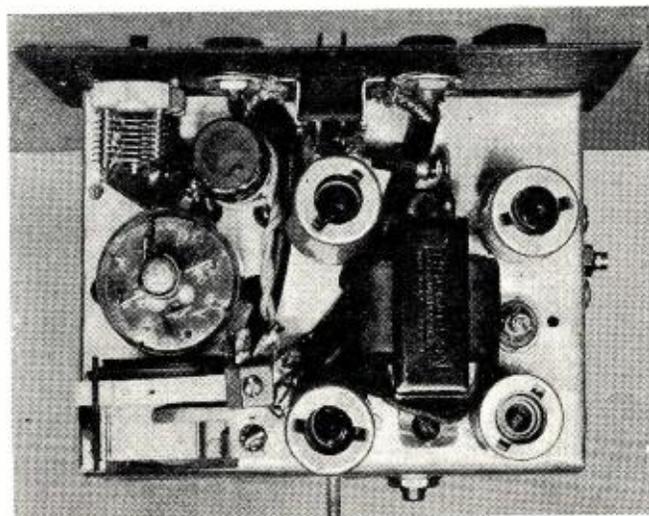

# Television

## CAMERA TUBES

By  
**HENRY J. SEITZ**

**M**ANY interesting principles, scientific as well as electronic, are embodied in the action of an ordinary television camera tube. Physicists, chemists, and electronic engineers have combined both their talents and skills in the production of this most marvelous device.

Heinrich Hertz, the German physicist, in experiments conducted about 1880 first demonstrated what is today known as the photoelectric effect. He found that an electric spark could be made to jump more rapidly between spark-gap electrodes if one of them was more brightly illuminated than the other.

Max Planck, whose name is synonymous with the well-known mathematical constant, developed the idea that the energy inherent in light is accumulated into small bundles or quanta. Einstein, in 1905, gave increased credibility to the photoelectric theory by further elaboration upon the above concept.

The amount of energy required to tear an electron away from its parent atom is dependent not only upon certain characteristics of the atom in question but also upon the quanta of applied light. The energy contained within a quantum of light or *photon*, as it is more commonly called, is proportional to its frequency and is expressed by the equation  $E=hf$ , Planck's constant  $h$  being equal to  $6.55 \times 10^{-34}$  joule-second, and  $f$  the frequency.

Sir J. J. Thompson, a British physicist whose research into the nature and qualities of electron particles has immeasurably enriched both the knowledge and practical application of television, proved conclusively by means of electrostatic and magnetic fields that electrons are negative particles and can therefore be influenced or deflected.

A fundamental rule of electron physics states that a magnetic field



The RCA image orthicon shown makes possible round-the-clock television coverage of news and special events. It picks up scenes in candlelight and semi-darkness and paves the way for practical outdoor TV programming.

### *A review of the many basic principles that are applied in the design of camera tubes.*

has the same effect upon a stream of electrons in free space as it has upon a wire or line carrying the equivalent of current. Another and quite important principle to bear in mind is that while an electrostatic field will deflect electrons along its lines of force, a magnetic field will deflect them perpendicularly to its lines of force.

Speeding electrons, when under the influence of a magnetic field, will proceed towards their destination in a somewhat spiral or corkscrew fashion. (See Fig. 1.) In the basic image dissector, for instance, it has been possible through the use of advanced mathematics to prove that the electrons comprising the image do rotate through a certain angle. This, however, does not cause distortion inasmuch as the entire electron image


is rotated as a whole. For the purposes of future discussion we shall therefore assume that electrons in motion, unless influenced otherwise, travel in straight lines from source to target.

First proposed by Carey, Rignoux and Fournier in 1906 developed what might be called the first television mosaic. Their rather crude device consisted of banks of horizontal and vertical photosensitive selenium cells each of which was individually connected by means of a wire to shutters on a viewing screen. However inefficient from present day standards, simple patterns and letters were transmitted by means of this device.

The transmission and assembly of a single picture element was brought forth by Nipkow in 1884. However due to insufficient knowledge and techniques in handling small signal voltages, the scanning disc point-by-point transmission method was forced to await later and more favorable developments in the field of signal amplification.

Exceptional progress in the field of all electronic television closely followed the discoveries of the German scientist, Von Ardenne, in 1930. During these same thirties the "eyes" of American television developed, thanks to the contributions of Dr. V. K. Zworykin and Philo T. Farnsworth. Each of these progressive minds working independently brought forth his own type of camera tube, namely, the

Fig. 1. The effect of magnetic field on moving electrons. They follow a spiral path.

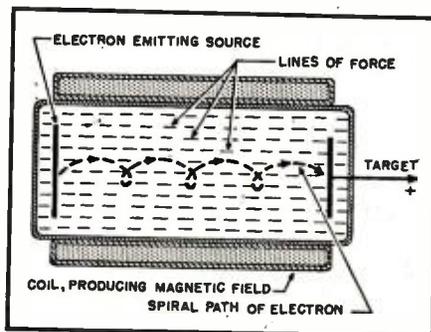

iconoscope of Dr. Zworykin and the image dissector of Farnsworth.

Many of the principles which were previously mentioned, find good application in the Farnsworth image dissector shown in Fig. 2. The tube itself consists of an evacuated glass cylinder approximately four and one-half inches in diameter, one end of which is occupied by the photosensitive cathode. A shielded target, containing a small aperture, connects directly to an electron multiplier located near the other end. A nickel coating on the tube's inner surface between the photocathode and target serves as the anode.

By means of a focusing lens an electron image is formed upon the photosensitive cathode, which, in effect, corresponds to the distribution of light and shade on the person or scene being televised. An axial magnetic field, in combination with the positive anode, forces the electron image towards the target aperture.

Transverse magnetic fields produced by coils external to the tube cause a planar deflection of the image horizontally as well as vertically. Separate low and high frequency linear saw-tooth currents make the image pass before the aperture in a series of 525 interlaced lines 30 times per second. In this way tiny areas of the image are progressively selected and passed on to the first section of the electron multiplier.

In operation, electron multipliers are, in effect, somewhat unusual in that the secondary emission characteristics of a series of increased potential anodes are used to excellent advantage. Multiplier action is based on the fact that a greater number of secondary electrons are dislodged than the incident or primary electrons engaged in the act of bombarding. Consequently this gives rise to tremendous amplification.

Multiplier gain may be calculated easily by means of the following formula:  $I = I_0 S^n$  where:

$I$  = multiplier output current


$I_0$  = photo-current passing thru image aperture

$S$  = multiplier secondary emission ratio

$n$  = number of stages

Close examination of the mosaic of a standard type of iconoscope, shown in Fig. 3, would reveal that it is composed of innumerable small silver globules distributed rather uniformly upon a thin sheet of mica. Light responsiveness is accomplished through the use of ingenious manufacturing controls which permit the addition of photo-sensitive elements. In most cases vaporization accounts for a thin film of caesium being deposited on the surface of the tiny silver globules.

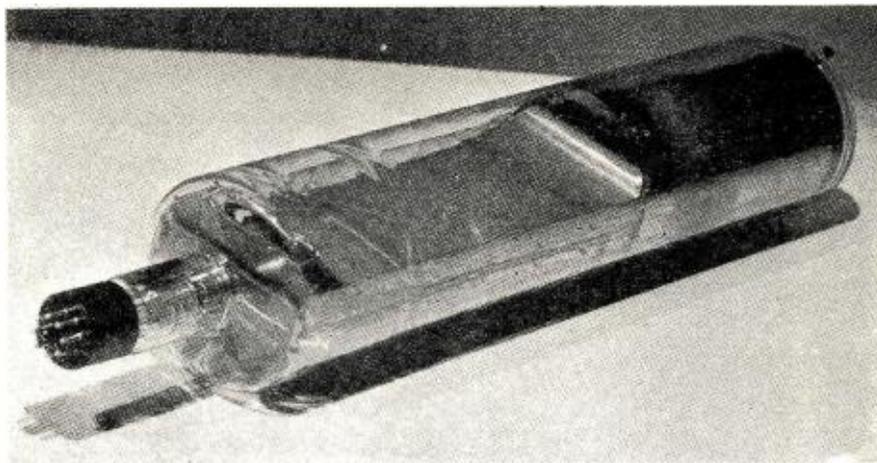Separated from each other and insulated by the mica sheet, each of these minute globules may be thought of as tiny individualized light sensitive condensers. Disproportionate charges are quickly accumulated when



The orthicon tube. Its mosaic differs from that of the iconoscope in that the back area is covered with a translucent conducting film, on which the picture is focused.

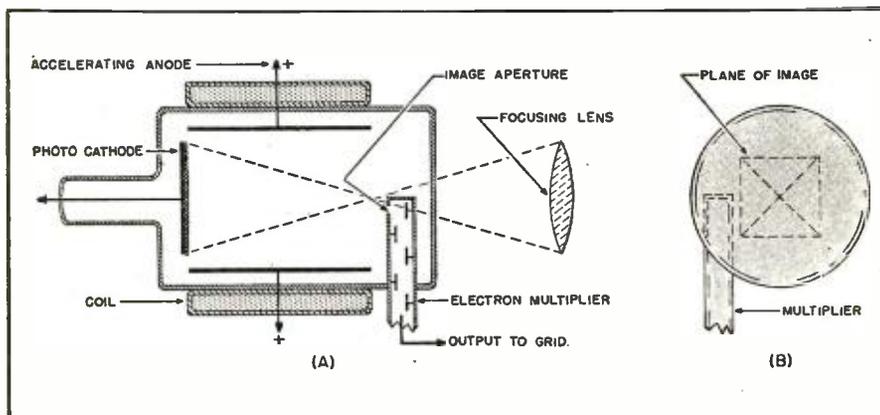


Fig. 2. Diagram illustrates the basic operation of the image dissector tube.


light from a televised object or scene is projected upon them by means of lenses. The charge may be said to increase as the illumination persists or grows in intensity.

A thin film of conducting material, which also serves as a transmission medium, covers the back of the mosaic plate described. Signal currents generated during scanning action are

passed from this point to the input of the picture amplifier.

An electron gun located in the base of the iconoscope produces what might aptly be termed "impact electrons." Concentrated into a fine needle-like beam they are then accelerated towards and against the mosaic target. In these days of jet propulsion, rockets, and supersonic speeds, one is, to

The iconoscope tube is widely used in television broadcasting work.

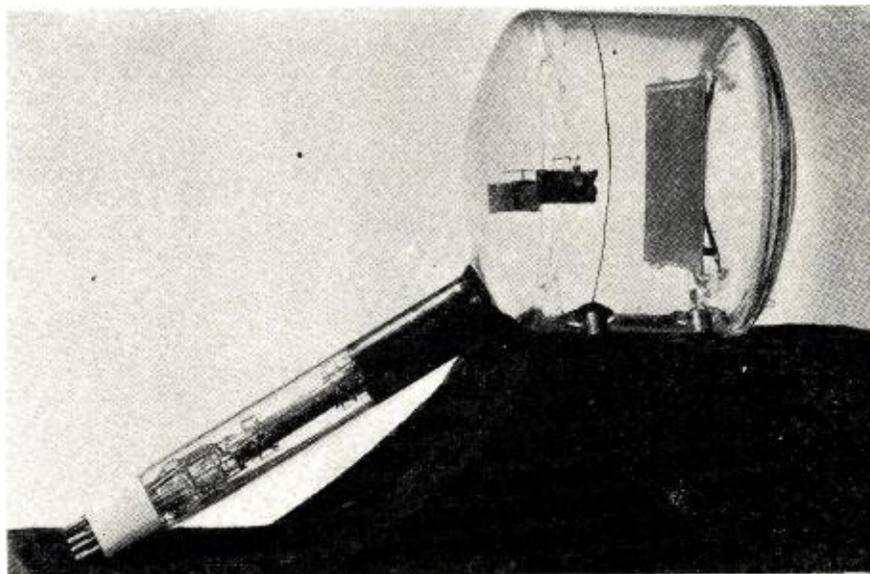

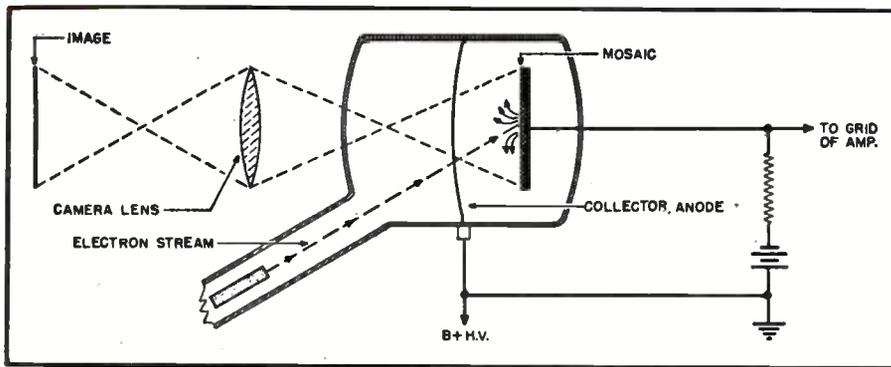


Fig. 3. Diagram illustrates the basic operation of the iconoscope tube.

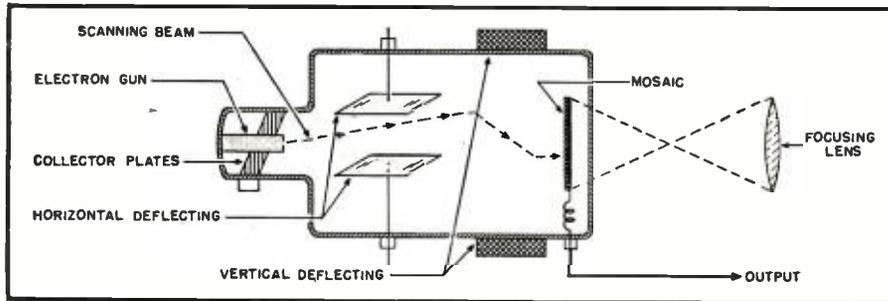


Fig. 4. Operation of orthicon tube is illustrated.

put it mildly, staggered at the velocities these infinitesimal particles attain. Assuming an accelerating voltage of, say, 10,000, these impact electrons merely lope along at  $5.86 \times 10^9$  centimeters per second.

Some form of controlling action must be devised if the mosaic is to be scanned according to standard practices. Recollecting the earlier experiments of Thompson, it becomes necessary to devise either electric or magnetic fields of force to accomplish this.

Many important considerations must be borne in mind when designing technical equipment relative to force fields. Not only does electron velocity play an important part, but, in addition, a continuous changing force potential must be maintained as the beam is swept across a mosaic line. Some means of instantaneous force reversal is also required in order to rapidly move the beam during retrace to the start of the next line. From

this explanation it is apparent that two such fields are necessary—one for influencing the scanning beam in a horizontal direction, the other in a vertical.

The solution to the problem is, however, not quite this simple as the mosaic reacts unfavorably under the influence of the scanning beam. Secondary electrons in great quantity are being emitted and they form an electron cloud which must be dissipated in one way or another.

These electrons may, in some cases, return directly to the globules from which they were ejected. However, should they venture to other parts of the mosaic, a spurious signal is generated which must be compensated for along the television camera chain.

Operating at a high positive potential, modern type iconoscopes employ what is termed a collector anode. This ring-like conductive coating which, in cooperation with the mosaic, is responsible for the icono-

scope's output, is located a short distance from the mosaic.

A goodly portion of the secondary electrons are attracted to this anode, providing a return path between the globules and the mosaic coating.

The camera tube mosaic is at this point functioning properly. Scientific analysis of mosaic action is rather complex, but reduced to fundamentals, the action is this; the electrical charge deficiency, previously predominant on each globule, has now been restored to equilibrium through the scanning beam's action. During this process the tiny condensers comprising the mosaic's surface have discharged individually, each contributing its pulse of current towards the generation of the over-all signal.

Additional development work by television engineers finally resulted in a camera tube which reduced to a negligible degree the spurious effects of secondary electron emission. Experimentation further revealed that the use of low velocity scanning electrons produced no recognizable secondary emission effects.


The beneficial signal producing effects of the secondary electrons must, however, be accounted for and, accordingly, some means must be devised to compensate for this deficiency. In the ortho-iconoscope (orthicon) a linear output is obtained by collecting the effects of low velocity scanning electrons. See Fig. 4.

Try to visualize a stream of electrons moving towards the mosaic at a fairly low rate of speed. Some of them, corresponding to the charge deficiency on the globules they contact, are naturally absorbed. Others are turned away and according to orthicon theory they return to a collector plate by paths which are more or less parallel to their original routes.


An orthicon mosaic differs somewhat from that of an iconoscope, in that its back area is covered with a translucent conducting film. The picture to be transmitted is focused upon this. As in the case of the iconoscope, photoelectrons are released to await the action of the scanning beam.

(Continued on page 186)

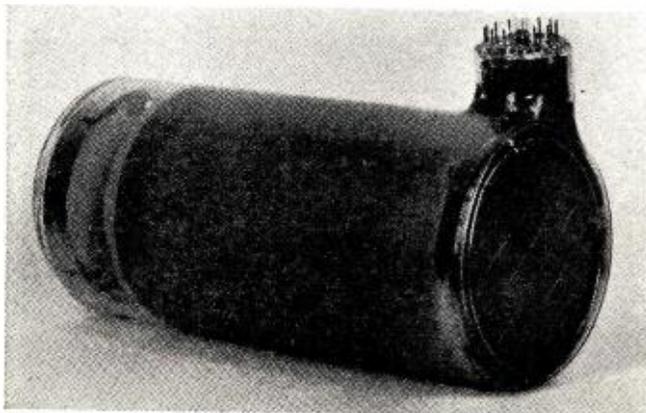Present Farnsworth image dissector television tube.



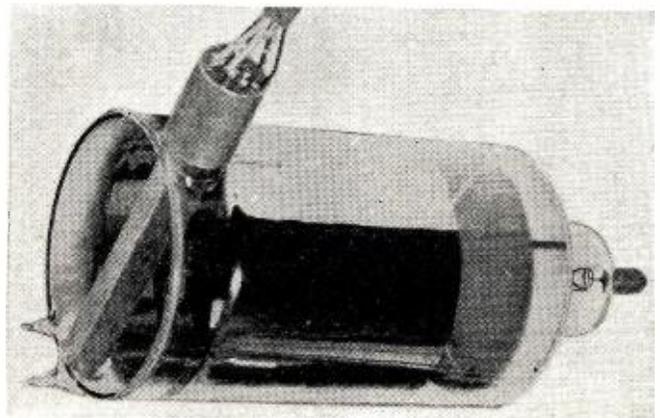Early d.c. type image dissector tube used in 1936-37.



# ALL-WAVE TELEVISION FM ANTENNA

**Single antenna that covers new FM and both TV bands. A standard 300 ohm transmission line is used.**

**W**ITH the production of television receivers hitting an all-time high, one of the most urgent requirements of the industry has become the production of suitable television antennas for all types of video installations.


One of the recently introduced antenna units consists of a relatively thin dipole which is a half-wave long at 70 mc. placed near a relatively thicker dipole which is a half-wave long at 128 mc.

The short, thick dipole is connected at its end through inductive rings to the approximate mid-points of the thin, long dipole section. These rings, besides end-feeding the short dipole, give mechanical support to the thin dipole. In the lower television band, the antenna acts as a broad-band folded dipole resonant at approximately 65 mc., with the thin member resonant at approximately this frequency and the short, heavy member end-loaded by the inductive rings at its ends.

In the higher television band, the long, thin dipole is one and one-half wavelengths in the center of the band, and the short member is ended by means of the inductive rings connecting it to the long member in such a manner that currents flow in the two dipoles approximately in-phase, thus substantially raising the radiation resistance of the antenna above a one and one-half wavelength dipole.

The most important performance characteristic of this unit is the relative impedance match between the antenna and its associated transmission line. A mismatch between the antenna and the transmission line results in a loss of signal but more important is the possible production of reflected images if the receiver match to the transmission line is imperfect.

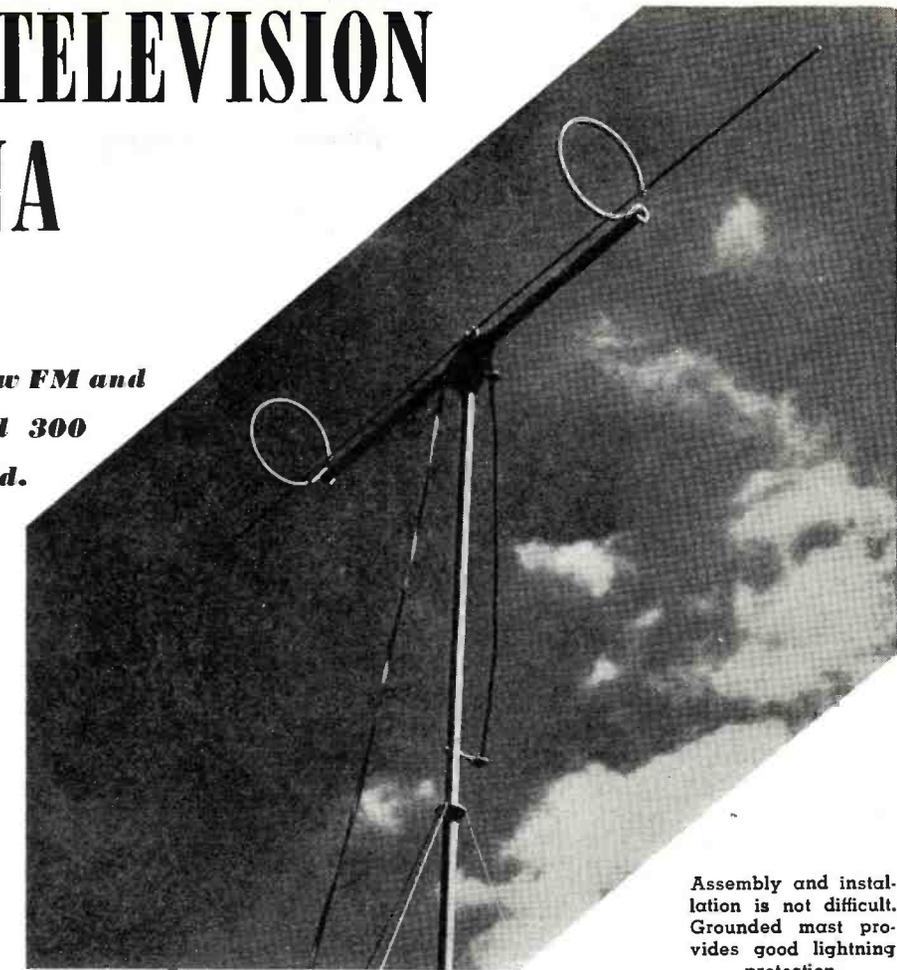A good criterion of the degree of match between the antenna and the transmission line is indicated by the




Assembly and installation is not difficult. Grounded mast provides good lightning protection.

standing wave ratio of the current or voltage along the transmission line when terminated by the antenna. This characteristic is shown in Fig. 1. It should be noted that the standing wave ratio is 4:1 or less in the low television band and under 2.8:1 in the high television band. The ideal standing wave ratio would, of course, be 1:1, but even with a ratio of 4:1, the


energy loss, or the energy reflected, is only 36% and when it is considered that the reflection at the antenna is the second reflection in the production of a second image, it may be seen that this magnitude of reflected signal is very low.

The loss in power resulting from the mismatch between the antenna  
(Continued on page 197)

Fig. 1. Performance curves of all-wave FM and television antenna.

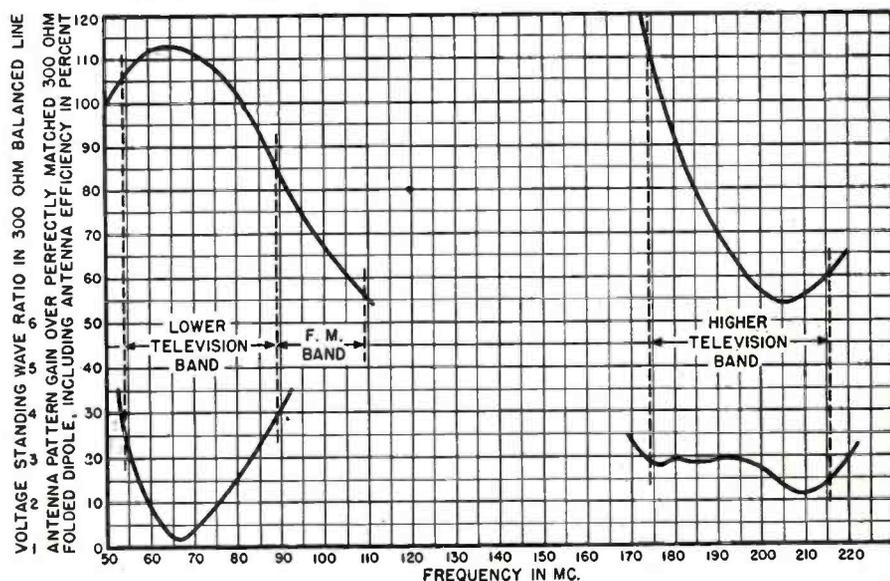

# Easy-to-Build MODULATION MONITOR

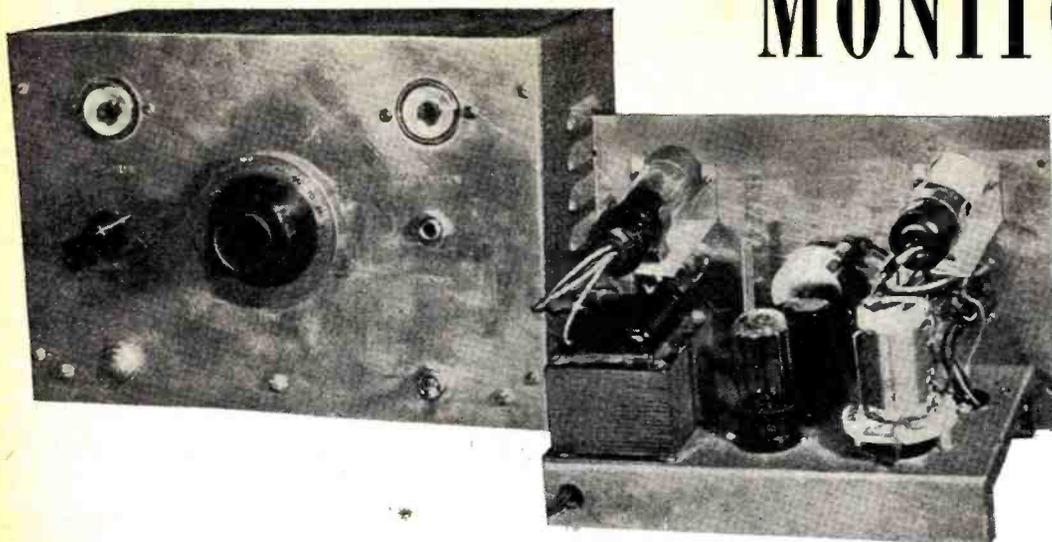

Front and rear view of the home-built modulator unit. Most of the component parts are readily available from the junkbox. The vertical shaft directly over the glass rectifier tube (rear view) is the calibration control,  $R_1$ . It is placed inside since it is adjusted during calibration only.

By C. M. DIBRELL, W5BLW

**The use of electronic tuning eyes to indicate both carrier level and 100% modulation reduces construction cost.**

**T**HE modulation meter to be described here was designed to register peaks of speech modulation by means of an eye tube. Because this type of indicator has no inertia it is superior for this type of application to the usual type of meter used for

this purpose. With a meter type modulation monitor the meter is adjusted to read 100 per-cent for a steady tone input to the transmitter modulator while it is modulating 100 per-cent. For speech modulation it is customary to keep the meter reading around 80

in order to take care of those peaks that the meter does not register.

For amateur use, where indication of 100 per-cent modulation is the main requirement, and indications of lower percentages of modulation are not very useful, an instrument using eye electron-ray tubes is a very useful piece of equipment.

One eye tube is used to indicate a reference level of r.f. signal fed into the monitor from the transmitter and the other eye tube is used to indicate when 100 per-cent modulation exists.


The circuit is simple. A pick-up coil,  $L_1$ , is mounted in inductive relation to the final amplifier tank circuit and the signal picked up is fed through twin-lead 75 ohm cable to  $L_2$  of the modulation monitor.  $C_2$ ,  $L_2$  serves to tune the input signal to resonance and feed one diode of the 6SQ7 tube. The rectified r.f. signal develops a d.c. voltage across  $R_1$ . This d.c. voltage is then fed through filter resistor  $R_2$  to the control grid of the "Carrier" eye tube.  $C_2$  is adjusted so that the eye tube just closes, thus establishing a reference level of r.f. signal input.

The audio component of the input signal is coupled through potentiometer  $R_1$  and  $C_3$  to the grid of the triode section of the 6SQ7. Output of the 6SQ7 plate circuit is coupled through monitor jack,  $J_1$ , to another diode of the 6SQ7 which serves to rectify the audio voltage. This produces a d.c. voltage which varies with modulation and is then coupled to the control grid of the "Modulation" eye tube through the delay circuit,  $R_6$ ,  $C_8$ .

After the instrument has been calibrated, operation of the unit is simple. Merely adjust bandwidth  $S_1$  to the desired band. Then adjust  $C_2$  until the "Carrier" eye just closes. Now, when speaking into the microphone, the "Modulation" eye tube will indicate

(Continued on page 188)

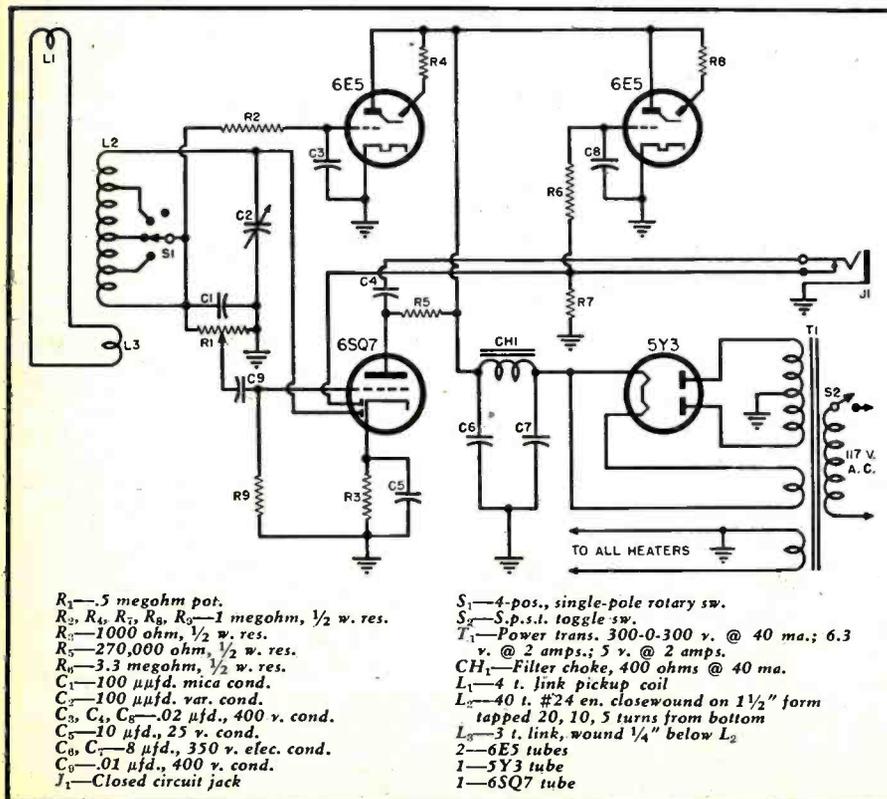Complete schematic diagram of a.c. operated modulation monitor.





Brush PL25 crystal pickup uses correctly balanced offset cartridge.

# The Recording and Reproduction of SOUND

By **OLIVER READ**  
Editor, RADIO NEWS

## *Part 8. A discussion of representative crystal cartridges and the various methods of coupling which may be used to give best reproduction.*

ONE of the greatest contributing factors to the successful reproduction of voice and music through electronic systems is the development of the modern pickup. These units are found in a variety of shapes and sizes and are usually divided into the following classifications; 1. magnetic, 2. crystal, and 3. moving coil. It should be explained, however, that there are many varieties and versions of each. From the most inexpensive type commonly employed in the average home phonograph, to the elaborate precision made instruments designed specifically for broadcast and high fidelity recording and reproduction, we find various shapes, sizes, etc., in use.


Since around 1930, the electric phonograph and radio-phonograph combinations for homes have appeared on the market in ever increasing numbers. Performance has steadily improved through the years to such a degree that reproduction of recorded sound today leaves little to be desired.

The success of these devices, as far as home recording is concerned, is due

largely to the development and improvement of pickup cartridges using crystal elements of Rochelle salts (sodium potassium tartrate). The use of this substance has resulted in improvements such as decreased needle pressure, higher output voltage, and wider frequency response.

The home recorder may employ an inexpensive preamplifier and omit complicated equalizers in conjunction with the modern crystal phono pickup and still obtain satisfactory reproduction

Fig. 1. Greatly enlarged cross-sectional view shows needle following record grooves.

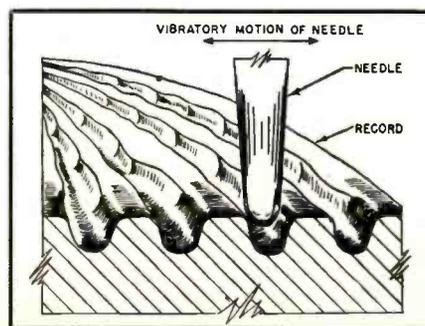

of commercial records. The voltage developed by crystal cartridges of this type is sufficient to enable them to perform satisfactorily with ordinary low gain type amplifiers. The comparatively low cost of crystal phono cartridges, together with their other advantages, has permitted radio and phonograph manufacturers to produce equipment for home use priced within the means of almost everyone.

### **The Crystal Pickup**

Back in 1880, Madame Curie, working with her husband, discovered that certain crystals would develop electrical charges on their surfaces when subjected to mechanical stresses. This phenomenon became known as the piezoelectric effect (electricity developed due to pressure or torsion). This is the principle upon which a crystal pickup cartridge functions.

The needle, following the groove of a record upon which sound has been recorded, is vibrated in proportion to the amplitude of the recorded sound. See Fig. 1. This vibration is imparted to the crystal element through a needle chuck or torque wire assembly or variations thereof. The illustration, Fig. 2, shows the construction of a low needle pressure type cartridge and a conventional removable needle type cartridge.

In both of these types a torsional crystal element (twister) is used and is so mounted that the needle vibration imparts torsional forces to the crystal element. The motion of the

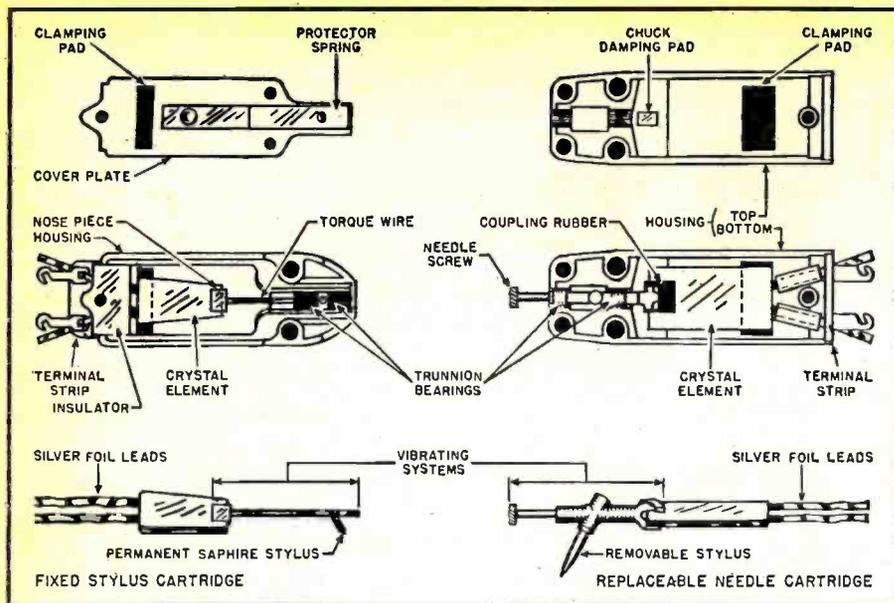


Fig. 2. Note the differences in construction between the fixed needle (left) and the replaceable needle (right) cartridge.

vibrating system is almost entirely absorbed by the twisting of the torque wire in the low pressure cartridges and the flexing of the coupling rubber in the conventional type so that the crystal, practically speaking, does not vibrate. However, the flexing of the torque wire or coupling rubber applies forces to the crystal directly proportional to the needle motion. The crystal generates voltages corresponding to these forces. Various types of rubber and other damping materials, such as Viscoloy, etc., are used for controlling output voltage, frequency response and other characteristics.

Crystal cartridges are made in a great number of styles with a wide variety of electrical characteristics in order to accommodate a multitude of various applications. The size, shape, and required needle pressure of a cartridge has a great deal to do with the styling of the pickup arm. The output voltage and frequency range of the cartridge are factors taken into consideration by equipment manufacturers when they are designing the amplifier and speaker combination with which the cartridge is to be used. Much time is spent on the circuit design of an amplifier, and a crystal

cartridge used for reproduction of records becomes one of the basic components of the amplifier input circuit. It is well-known that the various components of any circuit cannot be replaced with any but those of like characteristics without disturbing the circuit balance or changing the performance of the equipment. When it becomes necessary to replace a crystal phonograph cartridge, this should be done with an exact duplicate or substitute of the original in order to obtain optimum results.

### Requirements

The technical specifications for pickups and cartridges should be consulted prior to making selections or recommendations. Information concerning output voltage, needle pressure, and frequency range is of particular interest and value. Selection of the proper pickup and accurate installation will determine to a great extent the type of reproduction which may be obtained.

Great care should be exercised when installing a pickup arm to make sure that the motor board is perfectly level and that the pickup is mounted squarely, that is, on a direct plane with the surface of the record. Otherwise the needle will not properly track the record grooves. This would cause excessive needle and record wear. If the amplifier with which the pickup is to be used is of the high-gain, high-output type and it is necessary that the volume be kept at high level, it may be advisable to install a pickup and turntable mechanism in a compartment or cabinet separate from the speaker, in order to prevent feedback.

Certain types of turntable motors may cause a considerable amount of turntable vibration which may produce a disagreeable rumbling noise. Before installing a pickup on the motor board of a turntable using such a motor, the direction of maximum vibration should be determined. Following this, the pickup arm should then be installed so that it is parallel with the vibrating motion. Observance of this precaution will do much toward preventing this rumbling.

### Equalizers for Crystal Phonograph Pickups

It is sometimes advisable and often necessary, due to the many individual tastes involved, that an equalizer be employed in the input circuit of an amplifier in series with the phonograph pickup in order that the response of the pickup be entirely satisfactory to the listener. This is especially true of radio receivers or amplifiers which were not originally designed for phonograph operation. An understanding of the proper application of equalizers, to be covered later, is of great help to the serviceman called in for consultation and advice by the listeners whose equipment does not have enough low frequency or sufficient high frequency response to suit them.

Crystal pickup cartridges are high  
**RADIO NEWS**


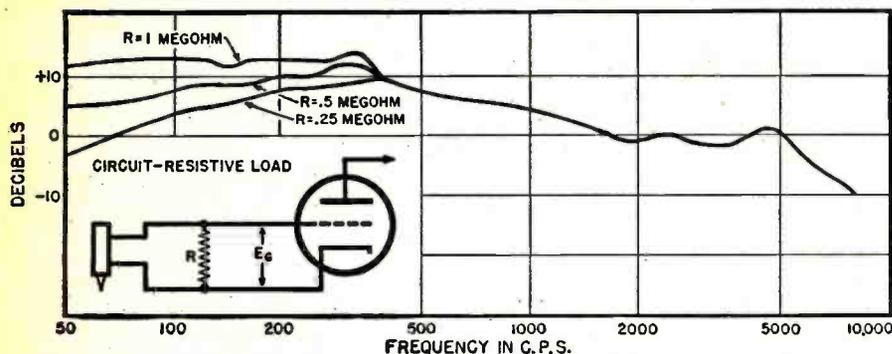


Fig. 3. Decreasing the value of R decreases bass response. A .5 megohm load is normal.

Fig. 4. Improved equalization is afforded by adding the RC circuit shown in the inset.

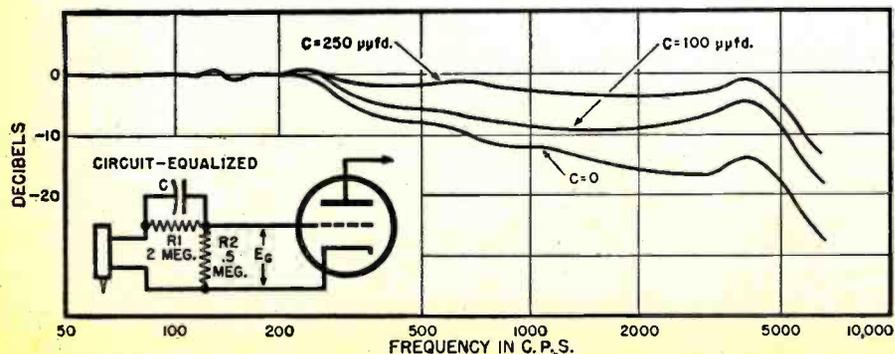

impedance devices and should, therefore, be connected across a high resistance load. The usual value employed is .5 megohm. By decreasing this value the low frequency response of the pickup cartridge may be decreased, while increasing the value will increase the low frequency response of the cartridge. See Fig. 3. However, if this value is made either too high or too low, the bass and treble balance of the cartridge may be upset. In addition, the over-all performance would be quite unsatisfactory. For best results with average crystal cartridges this value must be kept between .25 megohm and 1 megohm.

With the value of low resistance being adjusted for optimum low frequency response (optimum in this case being that which is most satisfying to the individual listener), the pickup may be further compensated by using the equalizer circuit shown in Fig. 4. The value of capacitance to be used is usually between 50  $\mu\text{fd.}$  and 500  $\mu\text{fd.}$ , depending on the amount of high frequency response desired.  $R_1$  may be between 1 megohm and 5 megohms.

When the total value of  $R_1$  and  $R_2$  is 2 megohms, maximum bass response is obtained. Any further increase in the value of  $R_1$  has no further effect on the low frequency response of most cartridges. Further increase in the value of  $R_1$  does, however, minimize the effects of increased temperatures on the low frequency response. As the temperature increases, the low frequency response of the cartridge has a tendency to decrease slightly and if a condition exists where the operating temperature varies between normal room temperature (approximately 70° F.) and 100° to 110° F., it may be advisable to employ a higher value of resistance for  $R_1$ .

It should be noted that as the value of  $R_1$  is increased, the value of capacitance should be decreased proportionately. Another important factor to remember is that when a circuit is equalized there is necessarily a reduction in output of the cartridge and, therefore, it may be that increasing the value of  $R_1$  will not allow sufficient excitation voltage to reach the input tube grid to enable the amplifier to deliver its full rated power output. If this is the case, it is best that the total values of  $R_1$  and  $R_2$  be held to 2 megohms or less. By using a slightly more elaborate circuit, such as is shown in Fig. 5, both high and low frequency response may be varied independently. One switch is used to control the low frequency response while the other switch is used to control the high frequency response.

#### Temperature and Humidity Effects

Crystal devices employing Rochelle salt crystal elements function best at temperatures between 70° and 80° F. when the relative humidity is approximately 50%. They are very much like human beings in that wherever human beings can live comfortably, the

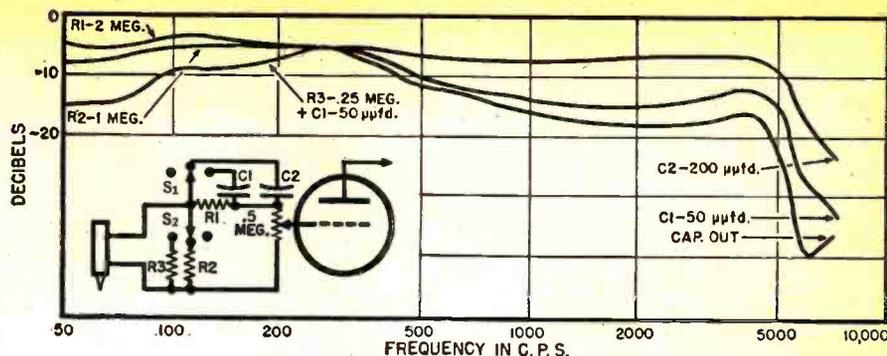


Fig. 5. High and low frequency response may be set independently with this equalizer.

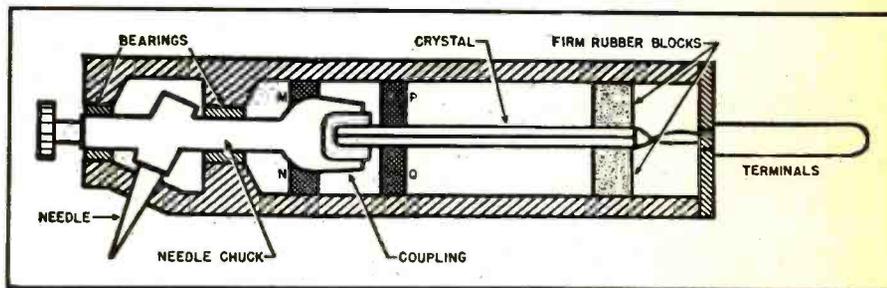


Fig. 6. Cross-section of construction details of typical cartridge employing rubber coupling between the needle and the chuck.

crystal element will function normally and have a very long life span. The piezoelectric limitations of Rochelle salt crystal pickup cartridges are between -40° F. and 120° F. If exposed to temperatures above 120° F., the crystal will lose its piezoelectric activity permanently. Adequate ventilation should be provided around the phonograph or radio cabinet in order that the temperature around the pickup be kept at the lowest possible value. Pickup cartridges and other crystal devices should not be stored near heaters or radiators nor should they be displayed in store windows or show cases where bright sunlight is apt to shine on them.

When leads are being soldered to the cartridge terminals during installation or service, the soldering iron should not be applied for a longer period of time than necessary to make a solid joint.

In extremely dry climates, crystal pickups have a tendency to become dehydrated (loss of natural moisture) when subjected to high temperatures. If the crystal becomes dehydrated, nothing can be done to restore it to normalcy. In climates where the tem-

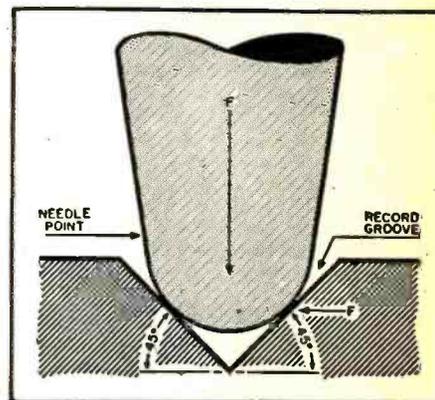



Fig. 7. Cross-sectional view of reproducing stylus in the record groove.

peratures and relative humidity are extremely high, crystal cartridges have a tendency to take on excess moisture.

#### PN Crystal Cartridges

One of the recent developments in the crystal cartridge field is known as the "PN" which differs from the Rochelle salt crystal elements  
(Continued on page 153)

Fig. 8. Motions of the needle chuck are transmitted to the crystal via lever action in this Shure-designed crystal cartridge.

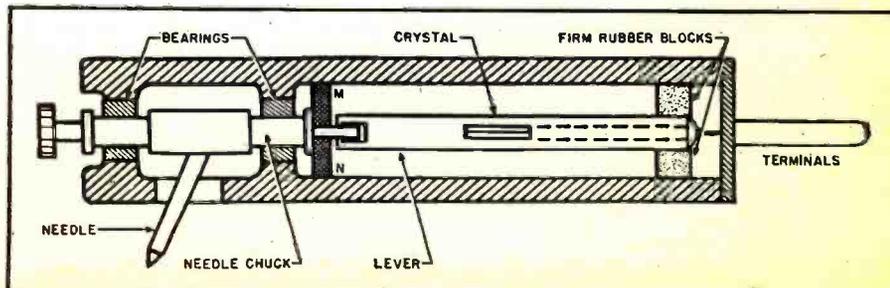

# TELEVISION

By  
W. W. WAYE



Fig. 1. The single dipole with "ribbon" lead-in and matching section is one of the simplest types of television antennas.

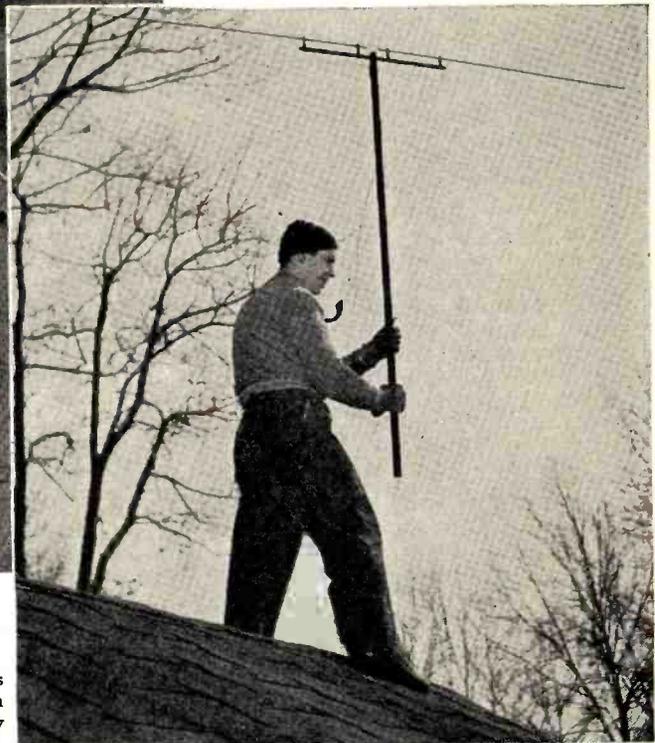


Fig. 2. Portable dipole is used to probe various roof locations for best antenna site. Lead-in connects dipole with television receiver, where relative signal strength and picture quality are observed for each of the various roof positions of dipole.

#### Lead-In—

300-ohm "twin-lead ribbon" line; similar to type K-1046, Federal Telephone and Radio Corp.

#### Matching Section—

4-foot length of 150-ohm "twin-lead ribbon" line; similar to above.

#### Stand-Off Insulators—

Polystyrene, for mounting lead-in.

#### Fibre-Head Nails—

For mounting lead-in.

#### Dipole Antenna Assembly—

Complete with metal rods of suitable length, wooden supports, and 4- or 5-foot mounting pole, with all tunable factors adjustable; similar to Shur Television Antenna, Shur-Antenna-Mount, Inc.

#### Heavy Metal Bracket—

For upright mounting of antenna pole and sufficiently versatile to permit mounting on crest of roof, sloping sides, on horizontal or vertical surfaces; similar to Adjustable Mount, Shur-Antenna-Mount, Inc.

#### Small Compass—

To locate direction of stations not visible to eye.

#### Simple Battery Telephone System—

For two-way communication between roof and receiver; any suitable, inexpensive system.

#### Tools, Soldering Iron, Nuts and Bolts.

Table 1. Necessary parts and equipment required to install television antenna.

**N**O MATTER how well designed and manufactured, a television set is inefficient or even useless unless it is properly installed. A good installation means an individual installation, designed to fit the needs and solve the problems of each particular case. This means personalized planning, constructing, siting, orienting, and tuning of the antenna system for every set installation. Adding to all this, such work in city or metropolitan areas is usually far more complex than in residential, suburban, or rural districts.

Using the simplest antenna, a single dipole, with any kind of television receiver, let's adapt the *Basic Procedure*, outlined last month, for the easiest and simplest of all installations, a remote, suburban residence.

This is a practical demonstration of an actual installation. The work illustrated is typical of the procedure for all kinds of dwellings and houses in remote, suburban districts.

The site for this installation was a two-story frame dwelling located on a rise of land near Woodcliff Lake, in northern New Jersey. There were no high buildings, metal obstructions, or mountains in the vicinity. The house was approximately 15 miles (di-

rect, or line-of-sight) from midtown New York, where the principal television stations for the area are situated.

Offering no obvious difficulties, the site was purposely chosen as being ideal for the simplest type of television installation. The site was selected by Jack McNally, New York television engineer, who also participated in the roof operations according to the *Basic Procedure of Installation*.

#### Preliminaries

After sale of a television receiver, the dealer made a good-will visit to the customer's home in northern New Jersey. His purpose—to make a preliminary survey of the place of installation, to explain some of the critical requirements of television, to determine the customer's preference of two stations for "best reception" with a single antenna, and to establish the eventual location of the receiving set.

The customer's choice for the *Primary Channel* (the station most preferred) was WABD, transmitting on Channel 5. Choice for the *Secondary Channel* was WCBS, operating on Channel 2.

The customer was advised that

**RADIO NEWS**

# INSTALLATION

## Part 2. Details covering the proper procedure to follow in installing the simplest of TV antennas.

probably *other* stations operating in the area might *also* be received on other channels, but that the receiving system was to be installed especially for reception of the *Primary* and *Secondary Channels*.

Best interior location for the television receiver was a compromise of these factors; the customer's preference for location, the viewing distance (6 feet) recommended by the set manufacturer, absence of sunlight, presence of ventilation, and a position remote from any household electrical apparatus likely to cause interference.

A quick survey, made from the ground, outside, indicated several likely sites for the antenna, somewhere along the peak or crest of the roof. The *approximate* distance of the lead-in route was then estimated—from the probable location of the antenna to the established location of the receiver.

All of this information was later turned over to the two technicians assigned to this installation. They then prepared the necessary equipment for the suburban installation. (See Table 1.)

The customer's television set had a conventional input impedance *rating* of 300 ohms. This meant that the lead-in to be connected to the receiver *also* had to be rated at 300 ohms, for best reception of the signals. Accordingly, an extra-sufficient length of 300-ohm "twin-lead ribbon" was cut for the lead-in.

The installation order called for a single dipole antenna. Since all single dipoles have an impedance rating of about 75 ohms, however, the 300-ohm lead-in could *not* be connected (later) directly to the dipole. To correct the mismatch or difference of impedances, a short piece of special wire known as a "matching section" was necessary. Consisting of a length of 150-ohm "twin-lead ribbon," the matching section was constructed and (later) connected between the dipole and the lead-in.

Length of each of the two metal rods used determines the frequency band or channel best received. A good *average* length, for reception of *all* channels, 1 to 6, is about 40 inches. However, certain channel preferences of the customer can always be favored. For this installation, each rod was cut to a length of 32 inches to favor reception of the *Primary Channel* (station WABD on Channel 5).

All equipment and tools, along with

the two technicians, were transported to the customer's dwelling.

During delivery and installation, the television set was handled with great care. After placement in its previously established location, the receiver was thoroughly checked and pronounced to be operating normally.

Outside the house, final assembly of the single dipole antenna was completed. The two metal rods were held in place by wooden insulators, allowing a 2-inch center separation between the rods. Each of the two conductors of the matching section was soldered to a terminal connector of a metal rod. The other end of the matching section was connected to the extra-sufficient length of 300-ohm "twin-lead ribbon" lead-in.

The dipole assembly, matching sec-

tion, and lead-in loop were then taken to the roof (Fig. 1). The lead-in was run loosely from the roof to the interior location of the television set, and then connected to the input terminals of the receiver. A similar, loose length of two-conductor covered wire was run between roof and receiver, and used to connect the two portable earphone-and-speaker sets of the battery operated telephone system.

### Siting the Antenna

Best site for locating the antenna was determined by a trial-and-error method, known as "probing." This is based on the principle that with a portable dipole connected to an operating receiver, the signal strength and image quality of the television picture will vary according to different roof positions of the horizontal dipole.

The method of siting the antenna is briefly this: Two technicians are required, one man on the roof with the portable antenna assembly (Fig. 2) and one man at the operating controls of the television set (Fig. 4). They maintain communication by means of the two-way portable telephone system. And, they work as a team!

The receiver is switched to the



Fig. 3. Best antenna site is the particular roof location that will provide the most favorable reception of the two desired television channels.



Fig. 4. Signal strength and picture quality are observed at TV receiver as various dipole locations are tried.

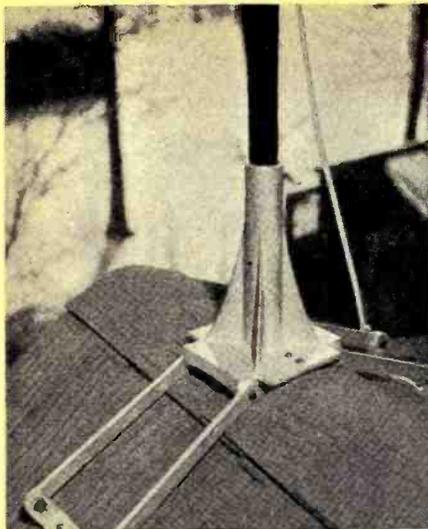


Fig. 5. Mounting bracket for dipole assembly shown attached to roof proper.



Fig. 6. Before tightening, dipole antenna is oriented for most favorable reception.

*Primary Channel* desired by the customer, and the controls are adjusted to obtain the best possible image on the screen of the set. This image may be weak or distorted, even with proper adjustment of receiver controls.

The roof technician holds the antenna assembly upright, so that the metal rods of the dipole are always in a horizontal position. Then, as the antenna is moved through various positions on the roof, the desirability of each position or site is judged *at the receiver*—in terms of signal strength and picture quality. This entire “probing” procedure is repeated for the *Secondary Channel*.

When all likely and accessible regions of the roof have been “probed,” the best locations are retested—on both of the preferred channels—until the best, single site is found for the antenna.

This is the general method of “probing.” Let’s see how it worked

in practice—for the actual installation!

The “probing” dipole was held aloft at a considerable number of potential locations on the roof, while the observer at the set reported relative signal strength and picture quality, on both *Primary* and *Secondary Channels*, for each roof location.

Because of the distance (15 miles) from the midtown district of New York to the customer’s home, television signals from both WABD and WCBS appeared to arrive from almost the same direction. Greatest signal strength and best picture quality—at any one of the roof sites—was obtained when the metal rods of the dipole faced *broadside* to the direction of the transmitters in New York. For all other bearings of the dipole, a weak signal was received on the *Primary Channel*, and no signal at all on the *Secondary Channel*.

In the vicinity of a brick chimney

protruding above the roof, the strength of all received signals was somewhat diminished, and when the portable dipole was so located that the chimney was *between* the antenna and its distant objective, the received signals vanished. It was then discovered, under a thick layer of soot, that the inside of the chimney was lined with thin copper sheet-metal, placed there years before to protect the inner brickwork.

Several roof positions just above the back door proved very unsatisfactory. Good picture reception was suddenly distorted beyond recognition, every time someone rang the doorbell!

Other causes of noise interference were centered around the kitchen of the house, where a variety of electric household appliances caused interference and distortion of the television picture.

Trouble from all of these sources of noise was eliminated by raising the dipole as high as possible and moving away from the vicinity of the electrical disturbances.

As might be expected, the only noise-free region of the roof was along its highest part, the peak, or crest. Moving along this peak, the strongest signal and best picture quality was obtained with the dipole in a position near the edge of the roof and in a direction toward midtown New York (Fig. 3). This happened to be the only part of the roof that provided a perfect, unobstructed line-of-sight path toward the two transmitters, even clearing nearby trees. This site was chosen as the best location for the antenna.

The next step was the mounting of the complete dipole assembly in an upright position by means of a heavy mounting bracket. After the metal bracket was attached to the roof, the antenna assembly was placed in position, with the long mounting pole inserted into the roof bracket. The antenna assembly was *not* fixed permanently in any position, but left free to rotate so that the dipole could next be oriented.

#### Orientation

The purpose of orienting the receiving dipole is to make certain that it is pointing *exactly* in the direction of the transmitting antenna of a desired station.

Human eyesight is far from infallible, and as the optical distance increases, many factors influence the accuracy of human vision. Directions can only be *estimated*, and then not too accurately. Thus, the only true means of orientation is to use the television receiver itself.

In this installation, the two stations preferred by the customer, WABD and WCBS, were actually located within a mile of each other in New York. But at a distance of 15 miles, signals received from either television station seemed to be coming from about the same direction.

(Continued on page 189)

Table 2. Glossary of television terms and pertinent installation data.

<p><b>“Best Reception”</b>— The installation of a single antenna to receive at least two channels preferred by customer.</p> <p><b>Channels</b>— Frequency bands used by television stations for broadcasting. Most popular channels: 1—44-50 mc.                      4—66-72 mc. 2—54-60 mc.                      5—76-82 mc. 3—60-66 mc.                      6—82-88 mc.</p> <p>Seven other channels are assigned between 172-216 megacycles. Primary Channel is the station best received after set is installed. Secondary Channel is the station received second best after set is installed.</p> <p><b>Dipole</b>— A television antenna consisting of two metal rods held in a fixed horizontal position. Has an impedance rating of about 75 ohms. Length favors one or more channels preferred by customer; rod length for each channel: 1—53.5 inches                      4—36 inches 2—44.5 inches                      5—31.5 inches 3—40 inches                        6—29.5 inches For two or more channels, take average.</p>	<p><b>Directivity</b>— The way a dipole receives; well in the two directions broadside to the metal rods, but not so well in other directions.</p> <p><b>Impedance</b>— The “ohms rating” of a dipole or lead-in. The input to each television set is also rated.</p> <p><b>Lead-In</b>— A plastic twin-conductor known as “twin-lead ribbon.” The most popular size for television is rated at 300 ohms; available also at 150 ohms, 75 ohms. Can be any length desired.</p> <p><b>Matching Section</b>— Short piece of “twin-lead ribbon” rated at 150 ohms, and connected between dipole and set lead-in. Length favors one or more channels preferred by customer: 1—48.5 inches                      4—33 inches 2—40.5 inches                      5—28.5 inches 3—36 inches                        6—26.5 inches To cover all channels use 37 inches.</p> <p><b>“Probing”</b>— The process of searching with a portable dipole, connected to set, to locate best site for antenna, based on observed picture signals.</p>
---	--

A

# Serviceman's

# TUBE TESTER

By **FRED J. LINGEL**

The Triplett Electrical Instrument Co.

**Complete construction details for a commercially built service instrument.**

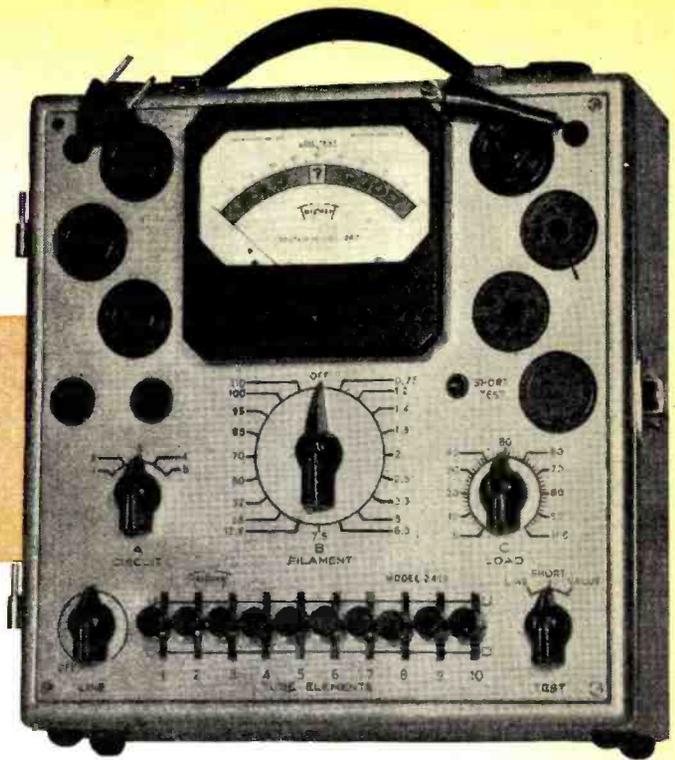


Fig. 1. Panel view of Triplett Model 2413 tube tester.

**I**N DESIGNING a serviceman's tube tester, a number of factors must be taken into consideration and the proper proportion established between these factors just as in any other design problem. In addition to the usual requirements of accuracy, compactness, and minimum cost, the serviceman's tube tester must be simple to operate and yet have maximum circuit flexibility.

Simplicity of operation is not only indicated by a minimum of control settings but a great deal depends on the number and arrangement of the controls and the straightforwardness of the circuit. For example, a tube tester with only four control settings for a tube set-up may require considerable hunting through a multiplicity of controls which are *not* moved. This takes time, and more important, increases the possibility of error. In addition, the use of "trick" switching circuits, often used to keep control settings at a minimum, makes it more difficult for the serviceman to "picture" his tester circuit. Both of these features tend to slow up the rate of making the settings. On the other hand, a tester with a few more control motions may be faster in the long run. The fewer controls and the ability to "picture" the test circuit also help reduce the chances for tube damage due to an error in the test set-up.

Fig. 1 illustrates the panel arrangement of the Triplett Model 2413 tube tester.

In order to keep the circuit straightforward, and therefore, help the serviceman to "picture" what he is doing in making a tube check set-up, this

tube tester uses a combination of lever and rotating switches with the lever switches numbered to correspond to the RMA tube pin numbers. These controls provide a maximum of flexibility and still retain clarity of circuit. This arrangement also gives maximum freedom from obsolescence due to changing tube types.

For maximum assurance against plugging tubes in the wrong socket, this tube tester provides one socket for each type of tube base. Tubes, therefore, cannot be plugged into the wrong socket simply because they will not fit! This not only is safer, but it also simplifies the set-up operation because it eliminates the reference to special sockets on the tube chart, the socket from the panel, and the operation of hunting for the special socket.

Fig. 2 shows the circuit of a Triplett Model 2413 tube tester. Most of the components may be obtained from regular radio parts suppliers. The transformer is special for this application and while generally not available on the open market, two or three separate transformers with secondary voltages as shown may be used instead. *(Editor's note: Tube tester transformers of various ratings are available from most parts dealers. Obtaining one with the exact ratings required is rather an impossibility, however as suggested by the author, two or possibly three separate transformers can be used. A transformer of this type can be home built. The article "Practical Transformer Design and Construction" published in the June, 1947 issue of RADIO NEWS will provide full details on how this can be done.)*

### All Elements Check

The circuit permits a thorough test of tube elements, shields, and taps. The check for both short-circuited and open-circuited elements is generally more complete than that obtained with a dynamic mutual conductance test alone, as commonly made in portable type tube testers. The main reason for a dynamic mutual conductance test is to check for open or misplaced elements. It does not necessarily check for continuity to the shields, such as in metal tubes. A dynamic mutual conductance test alone does not provide a means of checking element taps of the type used in some of the newer high frequency type tubes and in some of the high voltage filament types. In order to make a complete tube test, it must be possible, as in this unit, to get at each tube pin and make an open and short check.

### New Tube Types

The straightforward switching employed enables the serviceman to set up for new tubes without waiting for data from the tube tester manufacturer. This is a radically different approach to the tube testing problem not readily possible before, except in the laboratory type of tube tester. An example of such "set-up" instructions used for this tester is given below.

Use 3 or more new tubes and proceed as follows:

(a) Refer to manufacturer handbooks under the particular tube type for filament voltage and pin connections.

(b) Set "A-CIRCUIT" switch ( $S_2$ ) as follows:

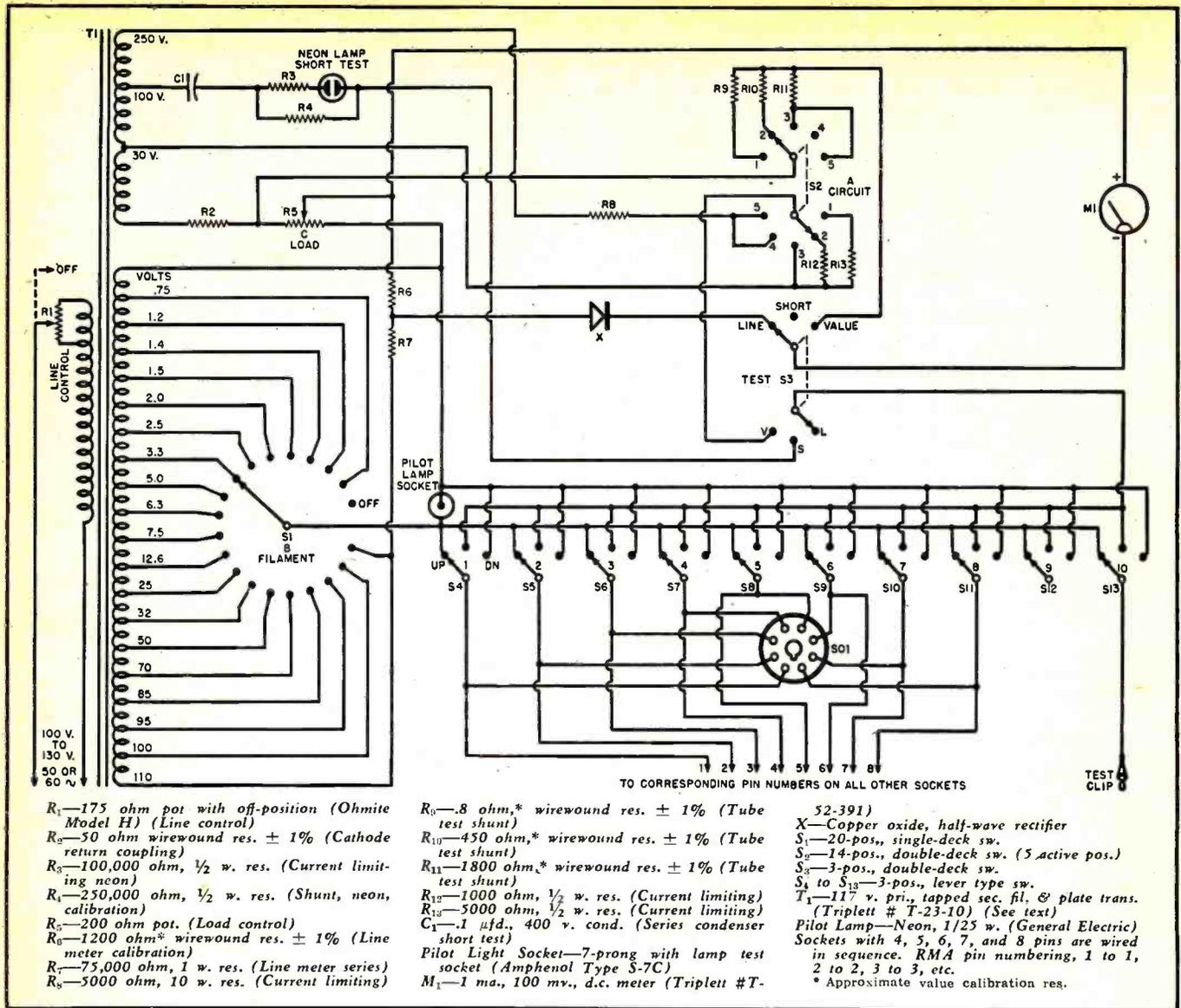


Fig. 2. Schematic diagram of tube tester. Circuit permits a thorough test of all tube elements, shields, and taps.

- "1" for diode types.
- "2" for filament types excluding diodes.
- "3" for indirectly heated (cathode) types excluding diodes.
- "4" for target or eye tubes.
- "5" for gaseous rectifiers and gaseous control tubes.

(c) Set "B-FILAMENT" switch (S<sub>1</sub>) to filament voltage.

(d) Refer to base drawing in "Manufacturer's Handbook" on tubes for the type being set up. Levers "1, 2, 3, 4, etc." (S<sub>1</sub> to S<sub>13</sub>) compare to RMA pin numbers.

(e) Set all levers in normal or center position. This is plate position and all elements in this position are tied together.

(f) Find the first filament connection pin on tube base and move corresponding lever to "UP" position. This connects one side of filament to the filament transformer.

(g) Find the second filament connection pin on tube base and move corresponding lever to "DN" position. This connects the opposite side of the filament to the filament transformer.

If filament is tapped, move corresponding filament pins to connect the two sections of filament in parallel.

(h) Find the cathode connection pin on tube base and move corresponding lever to "DN" position. This connects the cathode to one side of the filament transformer.

(i) If the tube is of the multi-section type, such as duodiodes, duotriodes, etc., find the elements not under test and move corresponding levers to "DN" position.

(j) Insert tube into proper socket.

(k) Hold "TEST" switch (S<sub>3</sub>) in "LINE" position. Turn on "LINE" control and adjust so that meter reads at "LINE TEST" mark.

(l) Hold "TEST" switch in value position. Adjust "C-LOAD" (R<sub>5</sub>) control for each tube so that the majority of the new tubes read 70 on the meter scale.

(m) List settings at end of tube chart for further reference.

Fig. 3 shows the simplified circuit of each of the several test circuits used in the tube tester. These simplified circuits are followed in most


tube test set-ups, however, in some special cases such as in sub-miniature triodes, Fig. 3A will be used even though it is primarily designed for diode checks. In general, these circuits function as follows.

In the diode check, Fig. 3A, the plate voltage at the transformer is set to 30 volts. A 5000 ohm resistor is connected between the plate transformer tap and the diode plate to limit the plate current to a safe value. Due to the low permissible diode current, it is necessary in some diode checks to add a note "Good tube reads over 20," etc. This note indicates that the maximum diode current was less than that required to deflect the instrument into the "good" section and it was, therefore, necessary to establish a lower reference point on the scale. The .8 ohm resistor in series with the negative instrument terminal is used to adjust for small variations in the potentiometer, transformer, and instrument.

The 200 ohm potentiometer provides a vernier adjustment of the instrument full-scale current. The setting of this control is determined from the


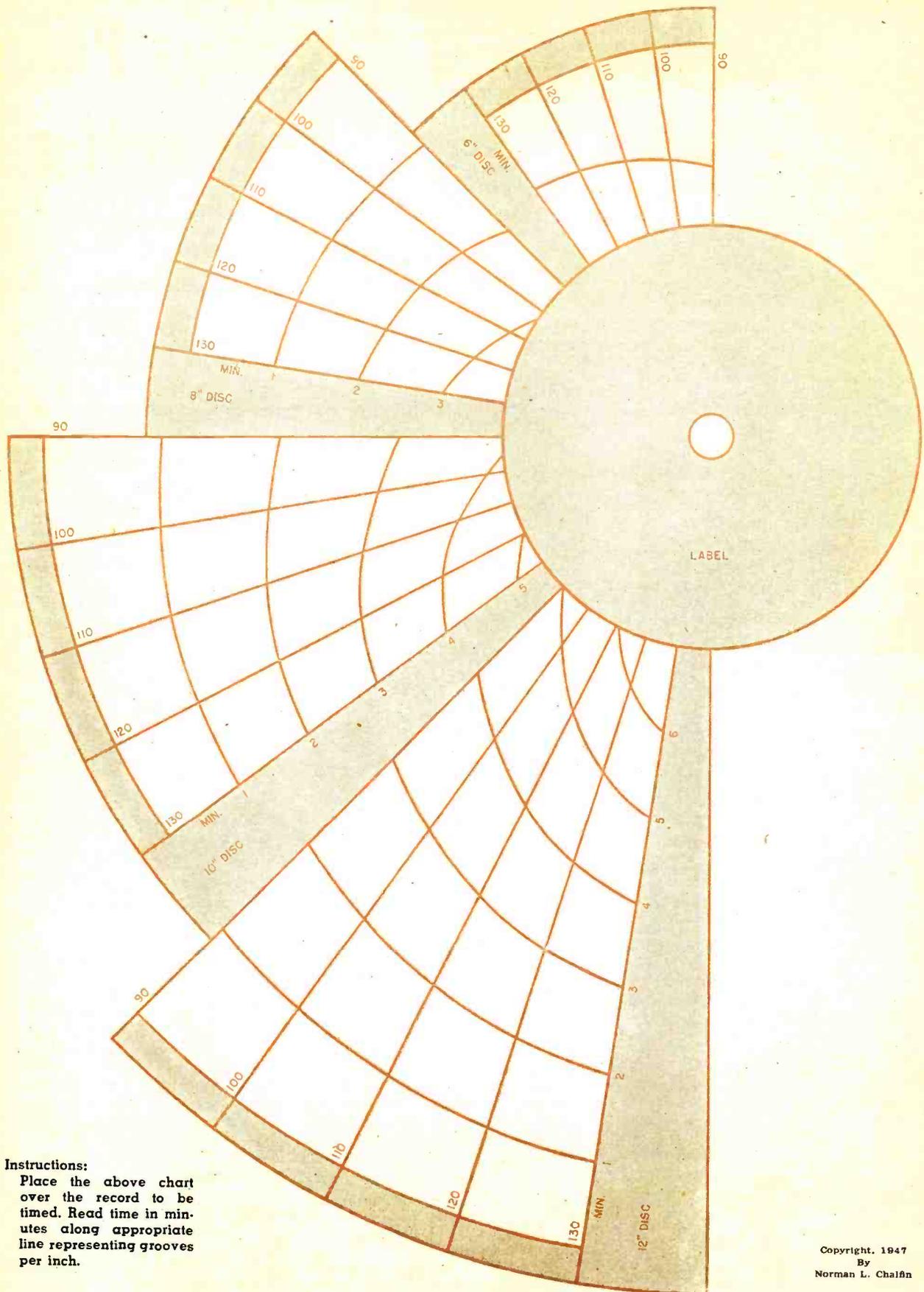
# Timing Chart For 78.26 R.P.M. Phonograph Records



**Instructions:**  
Place the above chart over the record to be timed. Read time in minutes along appropriate line representing grooves per inch.

Copyright, 1947  
By  
Norman L. Chalfin

# A 600-watt Phone Transmitter

By  
RUFUS P. TURNER, W1AY

*This low-cost transmitter, covering the 80, 40, 20, 10 and 11 meter bands, combines the advantages of good modulated carrier power (360-390 watts) and an inexpensive transformerless cathode modulator using the conventional type radio receiver tubes.*



Fig. 1. Front view of transmitter. Compare with layout sketch of Fig. 4 for identification of the various stages. Safety grille has been removed from bottom shelf to show the high-voltage power supply.

SINCE installing the transmitter described in this article, we have had the pleasant experience at W1AY of receiving from many QSO points on 75, 20 and 10 meters flattering comments on both voice quality and signal strength. The sincerity of these reports has been evidenced by requests for the circuit diagram of the modulator-final amplifier combination.

The modulation method has aroused no end of curiosity when described over the air (and the author has been compelled to mail out a number of pencil sketches), which is surprising because the system is, in reality, bewhiskered. It is a *series* cathode modulation scheme first described by Dawley a few years ago<sup>1</sup> and has been applied to this specific transmitter design. Using four parallel-connected 6L6 metal tubes as the modulator and only two 6SJ7 speech amplifier stages, the simple audio unit requires no separate plate-screen power supply, modulates 100% a final amplifier input of 660 watts, and provides a measured carrier output of 360 to 390 watts. According to the receiving operators who have heard the signal riding through typical 75-meter QRM, results belie the simple specifications.

How the modulator works in con-

junction with the final amplifier can be seen by examining the circuit schematic, Fig. 2. The four 6L6 modulator tubes are connected in parallel and their plates are connected to the filament center tap of the push-pull 810 final amplifier. The 6L6 cathodes are returned to ground through a 50-ohm resistor,  $R_{18}$ , which serves to supply fixed bias to the 6L6 tubes. As a result of this scheme, a d.c. voltage drop appears between the 6L6 plates and ground. By making the 810 plate voltage 2400, the d.c. voltage drop across the 6L6's becomes 400 volts. The center tap of the 810 grid coil  $L_{21}$  is grounded directly (that is, not returned to filament center tap), so that the final amplifier receives *fixed* grid bias voltage as a result of this cathode voltage drop, and no additional bias supply (power supply, battery, or grid resistor) is required.

The audio voltage developed by the 6L6's in the cathode circuit of the 810's is sufficient to cathode modulate the final amplifier—and no modulation transformer is required to do the job. The dynamic plate resistance of the modulator is reduced to a satisfactory value by means of degenerative feed-

<sup>1</sup>Dawley, Ray L., "Series Cathode Modulation," RADIO, December 1939


back introduced by resistor  $R_{15}$  connected between the 6L6 plates and the plate of the second 6SJ7 tube. The two 6SJ7 speech amplifier tubes also receive their plate and screen voltages from the voltage drop in the 810 cathode circuit, through the simple choke input filter ( $CH_1$ ,  $C_{30}$  and  $R_{23}$ ) which removes any ripple from the speech amplifier voltage. Thus, the final amplifier power supply furnishes operating voltage to the entire audio section as well. An effective voltage of 2000 appears between the 810 plates and filament center tap, and 400 volts across the modulator.

The speech amplifier has ample gain for the usual amateur microphones. Using an *Astatic* D104 diaphragm-type crystal microphone, we find that there is gain to spare.

The entire speech amplifier-modulator is built on a 15" x 7" x 3" chassis with ample "breathing space" both above and below the chassis. The unit is small and compact but definitely is not crowded. The separate 6.3-volt filament transformer,  $T_1$ , is mounted on the modulator chassis, although modulator filament voltage might have been obtained from a huskier exciter filament transformer. ( $T_1$ ). Fig. 3 gives a close-up view of the speech amplifier-modulator.

From Fig. 2, it will be noted that the modulator has no frills whatever. It is a straight resistance-coupled amplifier *direct coupled* to the final r.f. amplifier cathode, and is conventional in every respect except, perhaps, the use of parallel-connected output tubes. The 100-ohm resistors,  $R_{19}$ ,  $R_{21}$  and  $R_{22}$  discourage any tendency toward para-

Fig. 2. Complete schematic diagram of low-cost, 600-watt phone transmitter. See opposite page for parts list.

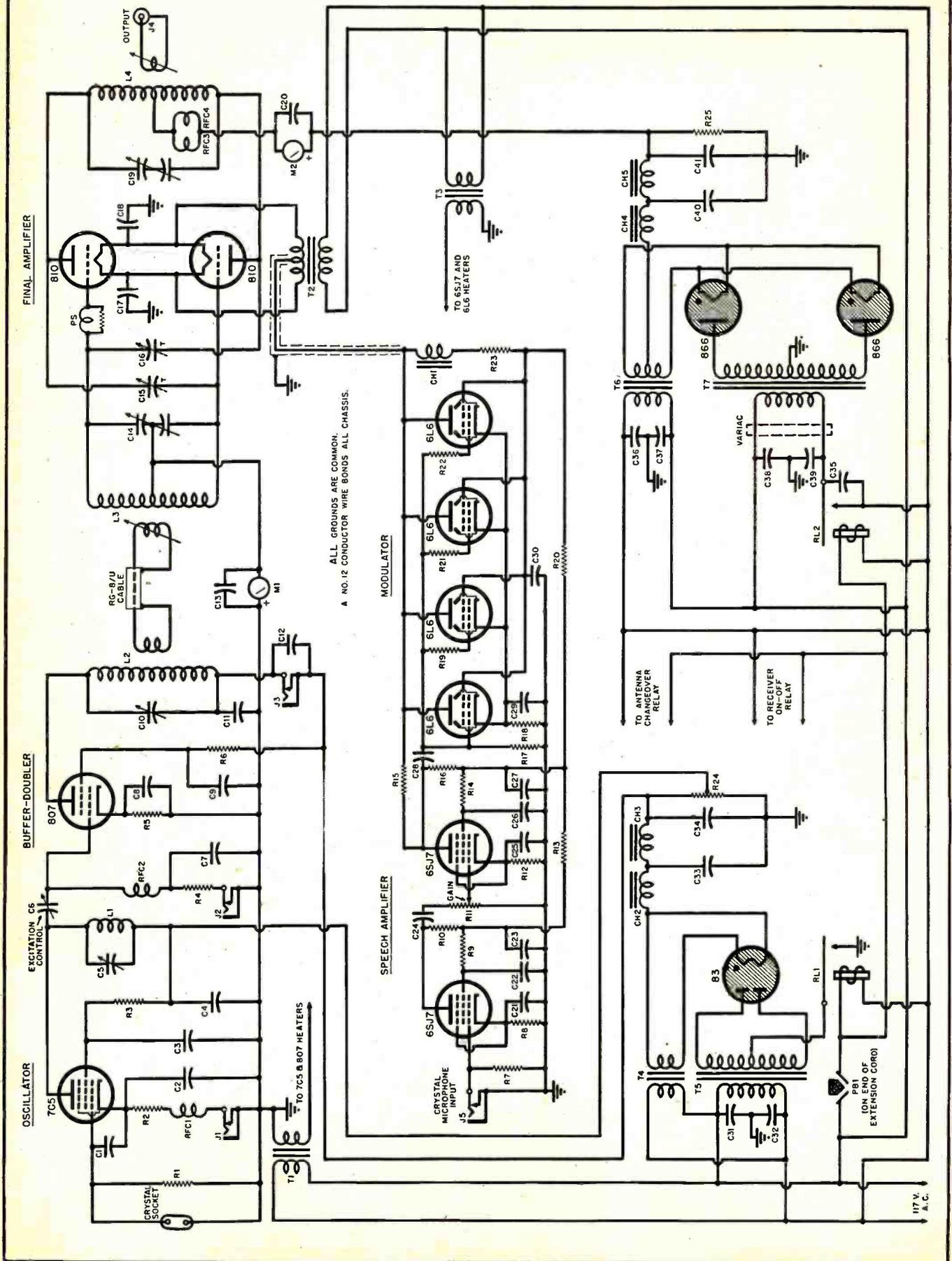

R<sub>1</sub>, R<sub>17</sub>—100,000 ohm, 1/2 w. res.  
 R<sub>2</sub>—150 ohm, 10 w. res.  
 R<sub>3</sub>, R<sub>4</sub>, R<sub>12</sub>, R<sub>20</sub>—10,000 ohm, 1 w. res.  
 R<sub>5</sub>—300 ohm, 10 w. res.  
 R<sub>6</sub>—40,000 ohm, 10 w. res.  
 R<sub>7</sub>—5 megohm, 1/2 w. res.  
 R<sub>8</sub>—2000 ohm, 1 w. res.  
 R<sub>9</sub>—2 megohm, 1 w. res.  
 R<sub>10</sub>—500,000 ohm, 1 w. res.  
 R<sub>11</sub>—500,000 ohm pot.  
 R<sub>12</sub>—500 ohm, 1 w. res.  
 R<sub>13</sub>, R<sub>18</sub>—500,000 ohm, 1/2 w. res.  
 R<sub>14</sub>—100,000 ohm, 1 w. res.  
 R<sub>15</sub>—50 ohm, 10 w. res.  
 R<sub>16</sub>, R<sub>19</sub>, R<sub>21</sub>, R<sub>22</sub>—100 ohm, 1 w. res.  
 R<sub>23</sub>—2500 ohm, 10 w. res.  
 R<sub>24</sub>—50,000 ohm, 50 w. res. (with slider)  
 R<sub>25</sub>—50,000 ohm, 200 w. res.  
 C<sub>1</sub>—40 μfd. mica cond.  
 C<sub>2</sub>—250 μfd. mica cond.  
 C<sub>3</sub>, C<sub>4</sub>—0.02 μfd. mica cond.  
 C<sub>5</sub>—50 μfd. midget var. cond.  
 C<sub>6</sub>—100 μfd. midget var. cond.  
 C<sub>7</sub>, C<sub>8</sub>, C<sub>9</sub>, C<sub>11</sub>, C<sub>13</sub>—0.05 μfd. mica cond.  
 C<sub>10</sub>—100 μfd. var. cond. (.038" spacing)  
 C<sub>12</sub>—0.05 μfd., 1000 v. mica cond.

C<sub>14</sub>—50 μfd. (per sec.) split stator cond. (.038" spacing)  
 C<sub>15</sub>, C<sub>16</sub>—2-10 μfd. neutralizing cond.  
 C<sub>17</sub>, C<sub>18</sub>—0.02 μfd., 2500 v. mica cond.  
 C<sub>19</sub>—100 μfd. (per sec.) split stator cond. (.077" spacing)  
 C<sub>20</sub>—0.05 μfd., 3000 v. mica cond.  
 C<sub>21</sub>, C<sub>25</sub>—10 μfd., 25 v. elec. cond.  
 C<sub>22</sub>, C<sub>23</sub>, C<sub>24</sub>, C<sub>26</sub>, C<sub>27</sub>, C<sub>28</sub>, C<sub>30</sub>—1 μfd., 600 v. cond.  
 C<sub>29</sub>, C<sub>37</sub>, C<sub>38</sub>—8 μfd., 450 v. elec. cond.  
 C<sub>34</sub>—0.2 μfd., 400 v. cond.  
 C<sub>35</sub>—0.5 μfd., 400 v. cond.  
 C<sub>36</sub>—50 μfd., 50 v. elec. cond.  
 C<sub>39</sub>, C<sub>40</sub>—1 μfd., 400 v. cond.  
 C<sub>33</sub>, C<sub>31</sub>—4 μfd., 1000 v. oil-filled cond.  
 C<sub>40</sub>, C<sub>41</sub>—4 μfd., 3000 v. oil-filled cond.  
 J<sub>1</sub>—Midget closed circuit jack  
 J<sub>2</sub>, J<sub>3</sub>—Midget closed circuit jack (insulated)  
 J<sub>4</sub>—Coaxial output chassis connector  
 J<sub>5</sub>—Midget closed circuit jack in shield can  
 CH<sub>1</sub>—10-12 hy., 75 ma. midget filter choke  
 CH<sub>2</sub>—5-25 hy., 225 ma. swinging choke  
 CH<sub>3</sub>—20 hy., 300 ma. smoothing choke  
 CH<sub>4</sub>—5-25 hy., 500 ma. swinging choke  
 CH<sub>5</sub>—20 hy., 500 ma. smoothing choke

RFC<sub>1</sub>, RFC<sub>2</sub>—2 1/2 mh., 125 ma. r.f. choke  
 RFC<sub>3</sub>, RFC<sub>4</sub>—1 mh., 300 ma. r.f. choke  
 M<sub>1</sub>—0-50 ma. d.c. meter  
 M<sub>2</sub>—0-500 ma. d.c. meter  
 PS—Parasitic suppressor (Ohmite P-300)  
 L<sub>1</sub>—Oscillator plate coil (See Table 1)  
 L<sub>2</sub>—807 plate coil (end link) (National AR-E)  
 L<sub>3</sub>—810 grid coil, c.t., center link (Barker & Williamson Type BCL or JVL)  
 L<sub>4</sub>—810 plate coil, c.t., center link (Barker & Williamson Type TVH)  
 PB<sub>1</sub>—S.p.s.t. push-button type sw.  
 RL<sub>1</sub>, RL<sub>2</sub>—115 v. a.c. relay, 10-20 amp. contacts  
 T<sub>1</sub>—Fil. trans. 6.3 v. @ 4 amps.  
 T<sub>2</sub>—Fil. trans. 10 v. @ 10 amps., c.t.  
 T<sub>3</sub>—Fil. trans. 6.3 v. @ 5 amps.  
 T<sub>4</sub>—Fil. trans. 5 v. @ 4 amps.  
 T<sub>5</sub>—Power trans., 475-0-475 @ 300 ma.  
 T<sub>6</sub>—Fil. trans., 2.5 v. @ 10 amps., c.t.  
 T<sub>7</sub>—Power trans., 2500-0-2500 v. @ 500 ma.  
 1—7C5 tube  
 1—807 tube  
 2—810 tubes  
 2—6S17 tubes  
 4—6L6 tubes  
 1—83 tube  
 2—866 tubes

Parts list covering all major components used in phone transmitter. Schematic diagram is shown on opposite page.

sitics in the 6L6 stage. The 6L6 tubes pass both grid and plate mils of the 810's, but they can handle this current (about 375 milliamperes) safely.

Readers desiring to apply this same scheme to modulate final amplifiers having up to 1 kilowatt input, but where a higher d.c. voltage drop than 400 volts must appear across the modulator in order to obtain sufficient audio voltage for complete cathode modulation (peak audio voltage equal approximately to 20% of the final amplifier d.c. plate voltage), will find it desirable to use two or more parallel-connected 807 tubes instead of 6L6's. Dawley has already pointed out that practice shows beam power tubes with degenerative feedback superior to triodes as series cathode modulators.

#### Exciter

The exciter section is composed of a 7C5 crystal oscillator and 807 buffer. It is advisable to operate the 807 as a straight-through amplifier in order to guarantee adequate excitation for the push-pull 810 final. However, it is permissible to double, triple, or quadruple in the oscillator plate circuit, as well as operating as a straight crystal oscillator with 10- to 80-meter crystals.

The oscillator is very active but is easy on crystals. It furnishes more than enough excitation for the 807 buffer, even when multiplying the crystal frequency. The oscillator plug-in plate coil, L<sub>1</sub>, may be wound on a 1 1/2-inch diameter form or may be purchased. The accompanying oscillator coil table (Table 1) gives numbers of turns required for the various amateur bands.

It is advisable to adjust the exciter output for not more than 5 milliamperes 807 grid current. For this purpose, an excitation control is provided—the variable coupling condenser, C<sub>4</sub>. This component allows smooth variation of the 807 grid mils over a wide range.

The 807 plate tank is link-coupled to the 810 grid tank by means of a length of Amphenol RG-8/U coaxial cable. It is recommended that either the buffer plate tank or final amplifier grid tank have a swinging link, in or-

der that the 810 excitation may be adjusted closely for proper grid mils. However, it is not necessary that both of the tanks have swinging links.

#### Exciter Power Supply

The oscillator-buffer power supply consists of transformers T<sub>1</sub> and T<sub>5</sub>, chokes CH<sub>2</sub> and CH<sub>3</sub>, filter condensers C<sub>33</sub> and C<sub>31</sub> voltage divider R<sub>23</sub>, and the type 83 tube. C<sub>31</sub> and C<sub>32</sub> are bypass condensers for the power line.

A good power supply should be employed in this position, however this unit need not be costly. Choke input is employed in the filter. The separate rectifier filament transformer permits full push-to-talk operation without the disadvantage of having the rectifier filament extinguished during standby periods.

This power supply delivers approximately 460 volts to the 807 buffer and 300 volts to the 7C5 oscillator. Series screen dropping resistors in the oscillator and buffer stages reduce these voltages to the proper screen values.

Some improvement may be expected in operation of the buffer-doubler stage by employing 600 to 700-plate volts on the 807.


#### Final Amplifier

It will be noted from Fig. 2 that the 810 final amplifier is a conventional push-pull stage neutralized in the common manner. Its only slight points of difference are the omission of a grid resistor and the returning of the filament bypass condensers, C<sub>17</sub> and C<sub>18</sub>, directly to ground, instead of to the center tap of the filament transformer, T<sub>2</sub>.

We found that the factory-made parasitic suppressor, PS, removed any tendency of the final amplifier toward self-oscillation or the generation of spurious frequencies. We found no advantage whatever, nor even a difference in operation, in either grounding the rotors of the 810 plate tank tuning condenser, C<sub>19</sub>, connecting them to "B-plus," or connecting them to ground through a bypass condenser.

(Continued on page 138)



Fig. 3. Close-up view of the speech amplifier-modulator chassis. A 6.3 volt transformer is mounted on the right of the chassis. Note shield can to left of the modulator which encloses auxiliary microphone jack mounted through side of cabinet.

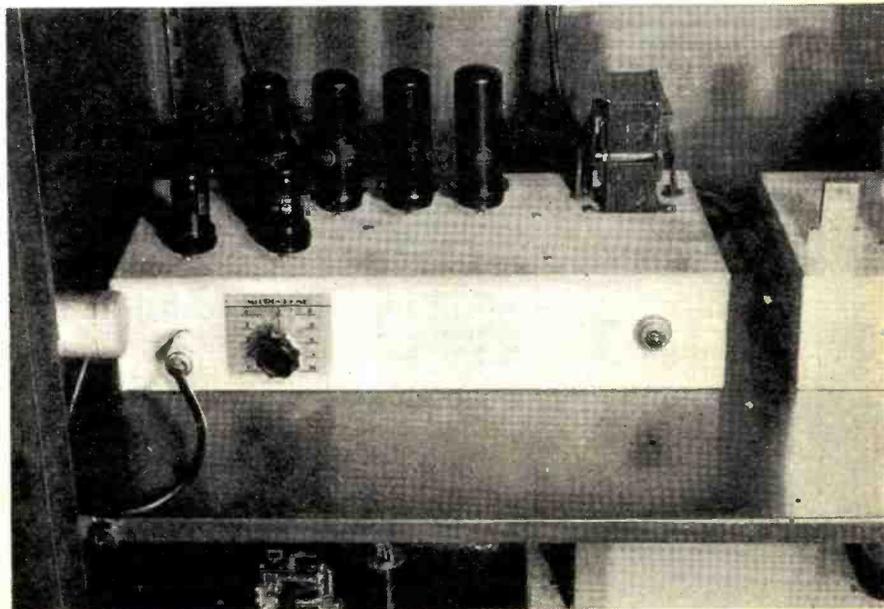

# WIRELESS PRE-AMP

By

RICHARD L. PARMENTER

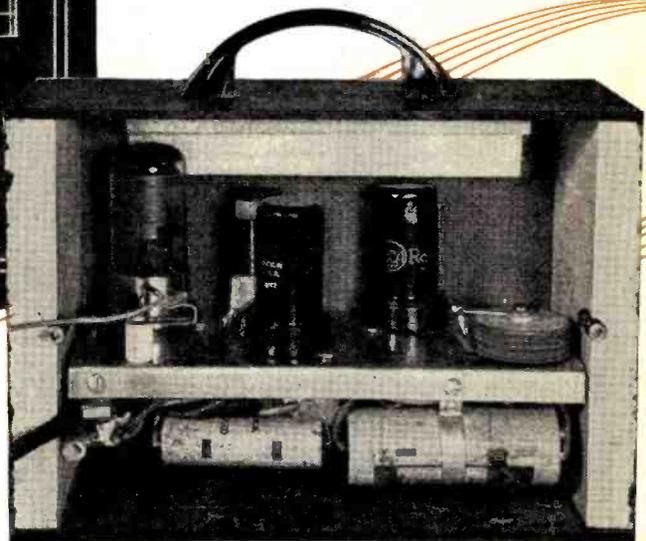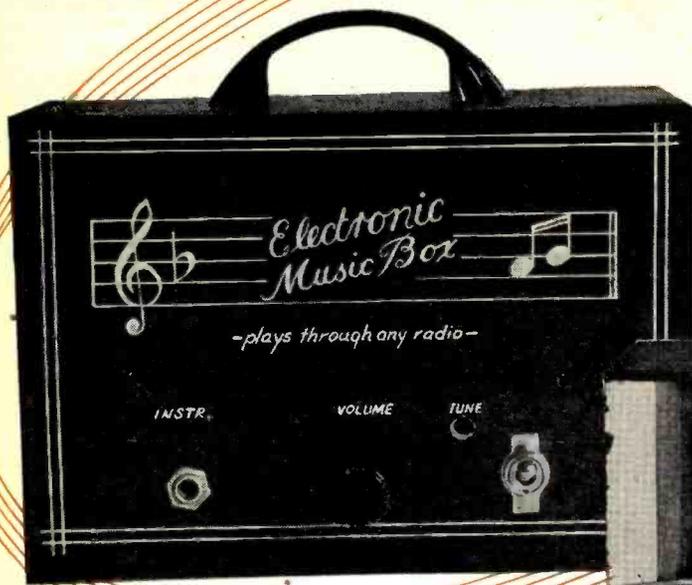

**Designed primarily as an amplifier for musical instruments, this unit is versatile in that it lends itself to various other applications. Output is picked up on any home receiver.**

Two views of the wireless pre-amp. Self-contained oscillator transmits signal to any radio.

**P**RESENTING to the musician the advantages of portability, economy, and versatility as well as having very few limitations as to location, this amplifier-oscillator should have wide appeal for those in the musical field. For the beginner and professional alike, it offers the advantages of electrical amplification for musical instruments and eliminates the need for the heavy, bulky speaker and amplifier that are usually associated with that system. It may be used in any location that has either an a.c. or d.c. power line and its fidelity is dependent almost wholly on the quality of the broadcast radio that is available. If it is desirable to play the instrument for a large gathering such as a party in a home or small hall, several radios may be placed at strategic points and by a slight extension of the antenna ample coverage can be obtained. It may also be used as a small public address system by substituting a crystal microphone for the musical instrument. This feature is often desirable for announcing or for vocalists. For the radioman and experimenter there is an opportunity to make a dollar by building these units for musically minded friends who play guitar, mandolin, violin, etc.; in fact,

almost any instrument that is suitable for electrical amplification. Since the unit is compact and uses few parts its cost is nominal and there should be a chance to make a reasonable profit. Another selling point is the fact that it can double for a phono-oscillator of the wireless type, by using the jack provided for the purpose.

## Circuit Design

Referring to the circuit diagram shown in Fig. 1 it will be noted that three tubes are used. A 6SJ7 is used as a high gain voltage amplifier, a 6J5 serves as the voltage amplifier and modulator while a 6SK7 functions as the oscillator. The 6SJ7 provides the necessary gain so that a wide variety of pickups and microphones may be used, the only requirement being that a high impedance type be selected since the input is directly into the grid of this tube. Since the unit was designed primarily for instrumental amplification, the phono-oscillator being incidental, this jack is installed on top of the chassis and is accessible by merely removing the back cover. This cover is held on by two barrel nuts which are screwed on to spade lugs, one on each side of the cabinet.

The volume control also acts as a

control for percentage of modulation and it is suggested that the builder experiment a bit with this in order to achieve the best possible quality. It would be desirable to have individual gain controls for both inputs so that mixing could be accomplished but since size was also a factor in the design of this instrument, the first stage control was sacrificed. Its use is suggested since its inclusion would be an advantage. No tone control is used since the tone can be set on the receiver being used and then left alone.

The 6SK7 tube operates as an electron-coupled oscillator and provides ample radio frequency carrier for normal uses. If the signal at the receiver being used is insufficient, a short piece of flexible wire may be attached to the antenna post of the amplifier to increase the radiation. Three to five feet should be enough for most cases. If lengths longer than this are used, precautions should be taken to see that the signal is radiating only as far as is needed for good operation. In any event the instrument should not be permitted to interfere with nearby radio receivers. The output from the 6J5 tube (audio frequency) is injected into the 6SK7 via the suppressor grid and thus modulates the electron stream flowing in that tube. The percentage of this modulation may be varied by the volume control and will be found to differ with different pickups used and/or different musical in-

struments. Over modulation should be avoided due to the inherent distortion involved.

Rather complete bypassing will be noted. This is necessary due to the high gain characteristics of the first tube. The grid leads of all three stages may have to be shielded if feedback troubles are encountered. In any event, it would be well to shield the leads of the 6SJ7 and 6J5. A decoupling network in the high voltage lead to the first tube is provided to avoid the possibility of common coupling effects. The power supply section is a conventional, half-wave affair using a selenium rectifier which saves space and contributes to the simplicity of construction. The 75 ma. size selenium rectifier was used. Care should be exercised when installing this unit to insure that the correct polarity has been observed. Connect — and + terminals as shown in the diagram.  $R_{13}$  is a current limiting resistor to hold down the initial surge of current and to prolong the life of the rectifier. The line cord resistor,  $R_{12}$ , is a standard unit of 330 ohms. For this unit a 50 watt resistor of 400 ohms could be used with the slider set at 325-330 ohms. The resistor is perhaps preferable but it should be mounted so that the heat will be dissipated properly and should not be located near the rectifier unit.

### Construction

The chassis was made of a piece of sheet metal 7" x 5½" which was bent at right angles at 2" so as to form a shelf 7" x 3½" and then a ¼" flange was bent down on the shelf. This is shown in the photo, however, these specifications need not be followed exactly as any conveniently small chassis can be used. In the rear view photo the tubes from left to right are; 6SK7, 6J5, and 6SJ7. The coil is behind the 6J5. A small standoff insulator with a *Fahnestock* clip is used for the antenna connection but an insulated binding post could be used equally well. The jack for the phono-input is mounted on top of the chassis and is behind the rectifier. It would be more convenient, of course, to have this on the front panel but the builder may use his own discretion. When mounting the parts on the chassis, plan the layout so that the adjustable padding condenser,  $C_{12}$ , is mounted on the front of the panel adjustment. This is necessary so that when using the "box" in different locations it will be possible to adjust for a clear spot on the broadcast band.

Below the chassis all wiring is done "point-to-point." Bypass condensers are mounted right at the sockets. Short leads are desirable even at the expense of appearance. Keep the filament wiring as far as possible from other wiring, especially the grid and plate leads. Run a piece of busbar the length of the chassis. Ground it at one end of the chassis and then make all ground connections to this bus. Use no external ground with the unit.

The cabinet is constructed of two

pieces of pine board 3" x 5", ¾" thick for the ends. The top and bottom are Masonite ¾" x 8½". The panel is also constructed of Masonite and this is drilled for the instrument jack, volume control, and the off-on switch. A ¼" hole through which an insulated screwdriver may be inserted to tune the padding condenser,  $C_{11}$ , is also included. Assembly is accomplished by using flat head wood screws and the whole box, except the front panel, may be painted flat black enamel. While some other finish might be preferable, flat black makes for a neat appearance and is quite durable. A dime store plastic handle is attached to the top of the box for convenience in carrying the unit.

The professional appearing front panel is achieved by using a procedure borrowed from the photo-finisher. A piece of tracing paper large enough to cover the front panel is marked for the holes to be drilled. This is then removed and the lettering and designing is done on this. Use pencil at first and then ink in the final product being sure that the solid areas in black are good and solid and that the lettering is quite heavy. Remember that what appears in black on the paper will come out white in the finished panel. Now use this drawing in place of a photographic negative and print out using Velox F3 or F4 contact paper. The exposure for most convenient handling is about 3 seconds using a 40 watt lamp about 10 inches away. Experimentation is necessary, of course.

Anyone who dabbles in photography can give you instructions and details on this or, better still, take the drawing that you have made to him and let him process it for you.


This photographic print is then mounted on the panel using some good adhesive such as *Casco* glue. Make sure that the glue contains no lumps since these would show conspicuously on the glossy panel. For greater durability this panel may be covered with a clear plastic material which may be cemented in place using clear *Duco* cement.

### Operation

After the unit has been wired and checked for correct connections the line plug may be inserted. Oscillation may be detected by running over the broadcast band on a nearby receiver. A spot should be found that will have the rushing sound of a station but there will be no modulation on it. Set the volume control on the receiver at nearly full on and the control on the "box" at about half point. Then plug a record player into the phono jack and play a familiar record to identify the carrier of the unit. If no record player is available merely touching the grid of either 6SJ7 or 6J5 will cause a motorboating sound which can help you identify the carrier. Now if the frequency is not "in the clear" adjust the padding condenser previously mentioned for a better frequency. In our location the low fre-

(Continued on page 146)

Fig. 1. Complete schematic diagram of three-tube, a.c.-d.c. operated pre-amp.

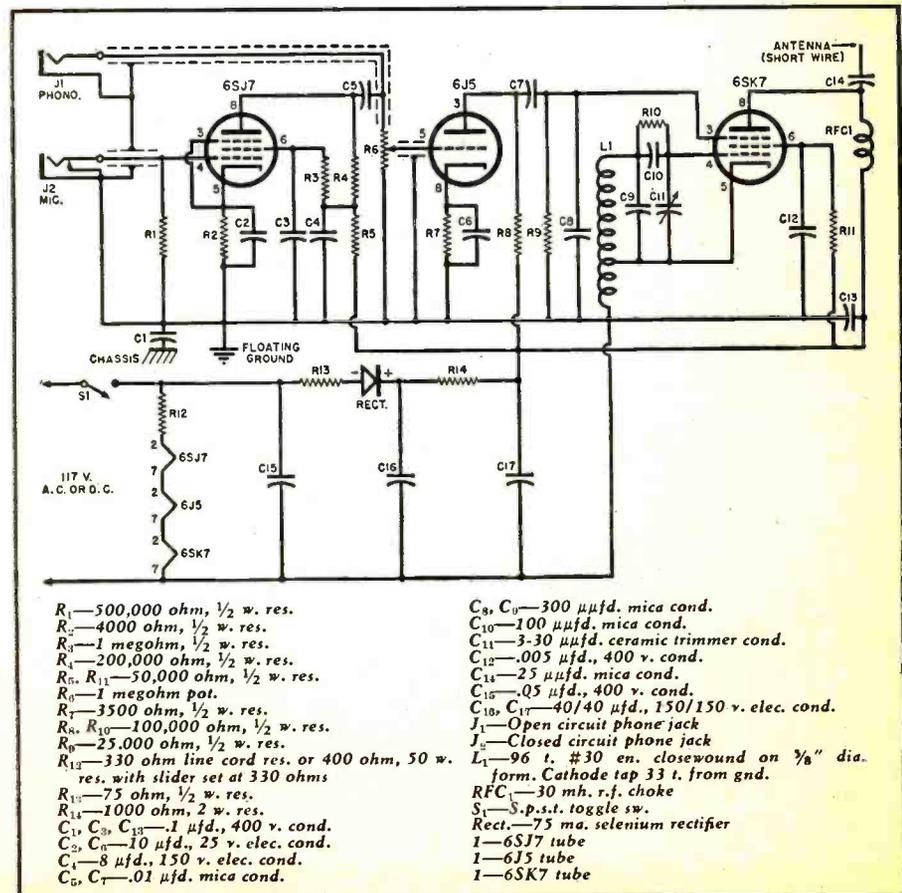

# FM RECEIVER ALIGNMENT

By  
**IRVING ABEND**

**Successful FM alignment depends on your "know-how."  
Procedure is similar to that used for AM with  
the exception of limiter and discriminator adjustments.**

**A**LIGNMENT of FM receivers can be accomplished with a minimum of equipment, consisting of a signal generator capable of generating frequencies up to 16 mc., and if r.f. alignment is required, frequencies of 42-50 mc. for the old FM band, and 88-108 mc. for the new FM band. Either a v.t.v.m. or a multimeter of at least 5000 ohms-per-volt sensitivity can be used. Some receivers may only be aligned properly by the use of a v.t.v.m. but in all cases of FM receiver alignment a v.t.v.m. is preferable.


FM alignment technique can be developed by the proper approach, and in most instances closely resembles broadcast receiver adjustment except for the discriminator and the frequencies used for the i.f. and r.f. sections.

Due to the variety of discriminator and general FM receiver designs used by manufacturers, it is always best, if possible, to review the instructions

for adjustment issued by each manufacturer before making any attempt to align an FM receiver. This procedure is advantageous and may eliminate possible troubles which may be encountered if an attempt at adjustment is made before full particulars of a set are known. The reason for this precaution is because FM receiver design is a relatively new art which has very little precedent, allowing each manufacturer to design sets to his own way of thinking, with the result that every FM set contains circuits which are the brain-children of one particular engineer. Essentially, however, the basis of circuit design is the same in every case, and the radio serviceman can recognize this if he has at least a basic understanding of FM receivers and their functions.

Referring to Fig. 1, it can be seen that an FM receiver is essentially the same as an AM broadcast set except

Fig. 1. Block diagram of a typical FM broadcast type receiver.

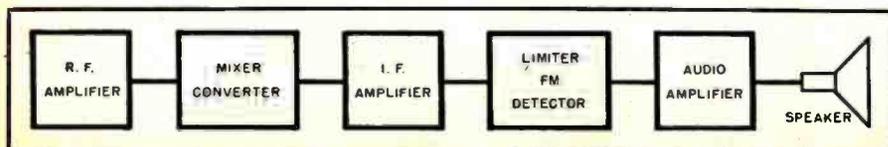

for the discriminator. It has an r.f. stage which may consist of an r.f. tube or antenna coil, a mixer or converter, an i.f. amplifier, a second detector or discriminator, and an audio amplifier.

Before an FM set is aligned, the i.f. frequency must be determined. Most prewar sets used 4.25-4.3 mc. as standard for i.f. and discriminator operating frequencies, but some receivers may use i.f.'s in the vicinity of 6.25, 8.25, 12.25, or 15 mc. The standard i.f. for the new FM band is 10.7 mc. and any sets designed for the new band will undoubtedly use this i.f. frequency. Manufacturers generally state all operating frequencies of a particular receiver in their instruction sheets, but if one is not available, the method for determining the i.f. will be explained later.

The first and most important step is the checking and adjustment of the discriminator. Extreme care should be taken in this procedure as this circuit is the heart of all FM sets. On this operation depends the proper detection, without noticeable distortion, of the FM signal. If the discriminator is not properly aligned, very noticeable audio distortion will result.

To adjust a discriminator properly, some knowledge of its operation may prove helpful, and a brief description of various circuit arrangements, all producing the same result, will be given. The most common form of FM discriminator is the Foster-Seeley circuit, which was used in most prewar FM receivers.

A conventional Foster-Seeley discriminator circuit is shown in Fig. 2A. It consists of a primary coil *A* and a center tapped secondary coil *B*. The primary is connected to the center tap of the secondary through condenser *C*, and the primary voltage appears across resistor *R*. The secondary is connected to the diode plates of *V*<sub>1</sub> and *V*<sub>2</sub>. Fig. 2B shows a simplified version of 2A. Referring to Fig. 2B, the voltage *E*<sub>p</sub> (primary voltage) is in series with each half of the secondary voltages *E*<sub>1</sub> and *E*<sub>2</sub>. *E*<sub>1</sub> is rectified by the diode tube *V*<sub>1</sub> causing a d.c. voltage drop across *R*<sub>1</sub>*C*<sub>1</sub> with polarity as shown. *E*<sub>2</sub> is rectified by diode tube *V*<sub>2</sub> causing a d.c. voltage across *R*<sub>2</sub>*C*<sub>2</sub> with polarity as shown. A signal voltage appearing across the primary and induced into the secondary will cause equal d.c. voltages to appear across *R*<sub>1</sub>*C*<sub>1</sub> and *R*<sub>2</sub>*C*<sub>2</sub> when this signal voltage is at the frequency of primary and secondary resonance. The d.c. voltages are in series and opposite in polarity with the resulting voltage appearing between point *X* (Fig. 2A) and ground equal to zero. If the signal voltage is either above or below the resonant frequency of the primary and secondary circuits, *E*<sub>p</sub> + *E*<sub>1</sub> or *E*<sub>p</sub> + *E*<sub>2</sub> will be either higher or lower in voltage depending on whether the frequency is higher or lower than resonance. Let us assume the frequency to be above and the resultant voltage *E*<sub>p</sub> + *E*<sub>1</sub> will be increased while *E*<sub>p</sub> + *E*<sub>2</sub> will decrease. A higher d.c. voltage will be

**RADIO NEWS**

developed across  $R_3C_1$  with the result that the voltage between point X and ground will be positive. If the frequency was lower than resonance a negative potential would appear between point X and ground. It can then be seen that a signal varying in frequency at an audio rate would produce a variation in voltage between point X and ground corresponding to that audio frequency. Referring to Fig. 2A,  $R_3$  and  $C_3$  comprise a de-emphasis network to attenuate the higher audio frequencies that are pre-emphasized at the FM transmitter. This network is proportioned so as to attenuate the higher audio frequencies by the same amount they are accentuated at the FM transmitter.

A variation of the circuit using a choke instead of a resistor is shown in Fig. 3A. Fig. 3B shows a circuit which eliminates  $R$  shown in Fig. 2A and uses only one bypass condenser,  $C_1$ . Fig. 3C shows a circuit with ungrounded cathode with respect to direct current.

To align the discriminator, the operating frequency must first be determined if it is not known. Connect a signal generator between point Y in Fig. 2A and ground. If two limiters are used, connect the generator to the grid of the first limiter. It is always advantageous to use a condenser of .01 to .1  $\mu$ fd., in series with the generator lead. Set the generator for maximum output, and connect the v.t.v.m. probe to point Z in Fig. 2A. If a multimeter is used, connect the multimeter as a milliammeter between  $R$  and the junction of  $R_1$  and  $R_2$ . Bypass the leads at the connections with a condenser of at least .01  $\mu$ fd. Set the multimeter to the 0-1 mil scale. (Note: a lower or higher scale may be needed depending on the signal strength and circuit components. Point Z is negative with respect to ground. The negative lead of the multimeter should be connected to the loose end of resistor  $R$ .) Vary the frequency of the signal generator between 4 and 16 mc. The frequency at which maximum deflection of the v.t.v.m. or multimeter occurs is the operating frequency.

To check the discriminator, leave the signal generator connected as before and connect the v.t.v.m. to point X, Fig. 2A, or when using a multimeter connect the negative lead to point Z, use a 50 volt or higher scale, and connect the positive lead as described below. Set the signal generator to approximately 50 kc. above the operating frequency of the discriminator. If a v.t.v.m. is used, record the voltage as to magnitude and sign. If a multimeter is used, connect the positive lead to point X and record the voltage. Now set the signal generator approximately 50 kc. below the operating frequency of the discriminator. Record the voltage on the v.t.v.m. as to magnitude and sign, or connect the positive lead of the multimeter to ground and record the


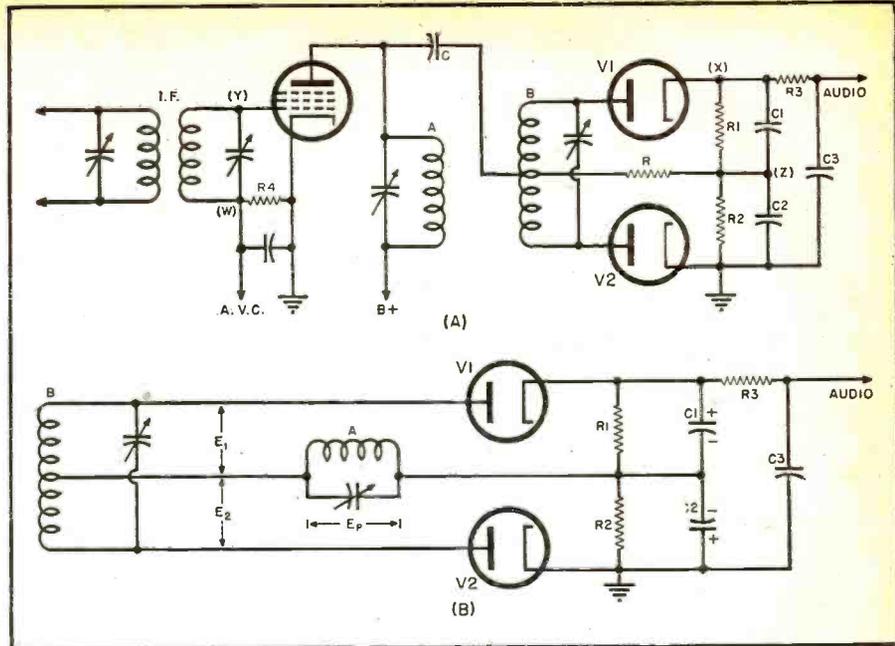


Fig. 2. (A) Schematic diagram of conventional Foster-Seeley discriminator. (B) A simplified diagram of discriminator circuit shown in Fig. 2A.

voltage. Set the generator approximately 75 kc. higher, then lower, and record the voltages as described above for the 50 kc. settings. When using

and lower frequencies should be about equal (within 10% of each other) and of the same polarity. If extremely accurate equipment is used the readings for the upper

Fig. 3. Variations of the Foster-Seeley discriminator shown in Fig. 2A. (A) Choke used in place of resistor,  $R$ . (B) Resistor,  $R$ , has been eliminated from the circuit and (C) cathode is grounded with respect to d.c.

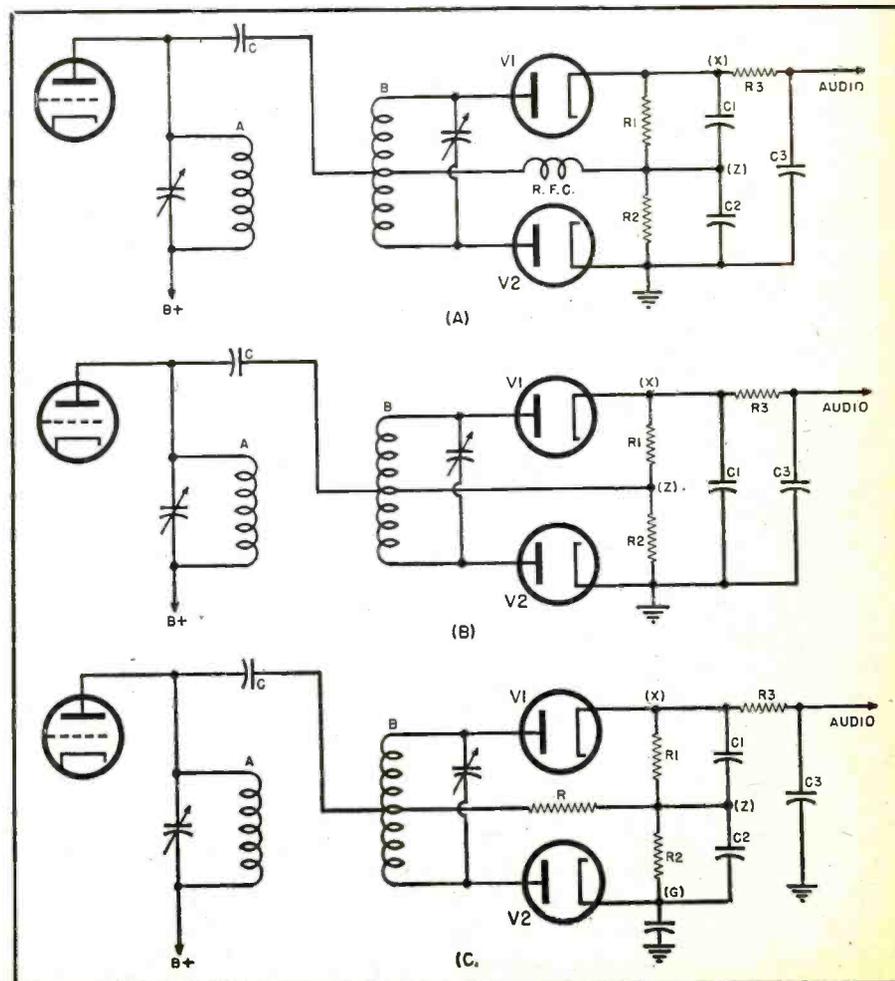



# International SHORT-WAVE



Compiled by **KENNETH R. BOORD**

**T**HIS month's ISW Department is dedicated to radio station HP5J/HP6J, "La Voz de Panama," Box 34, Panama City, Republic of Panama, and to the genial manager and director of its "Daily Newspaper of the Air," George Williams.

We are grateful to Paul Kary, Pennsylvania, and to Mr. Williams for this material.

George Williams has been in radio since 1915. In 1919, he was one of the first to talk in experiments from the British Flagship, *Queen Elizabeth*, in Scapa Flow when the U.S. fleet, led by the flagship, *New York*, was with the British fleet. After the German naval surrender, much experimenting was carried out by three officers on board the *Queen Elizabeth* and at a distance of 20 miles, speaking messages were exchanged.

As a British naval officer in World War I, George Williams was the first to pick up the German message of surrender which read: "Good morning, if you can hear, please answer." This was the first German message which led up to the surrender in 1918. It was Mr. Williams who tapped out the famous message from Admiral Beatty, Commander-in-Chief of the British fleet, to the Commander-in-Chief of the German High Fleet, which read: "The German flag will be hauled

down today, at 15:57, and not hoisted again without permission."

After this, the Germans scuttled the German fleet and salvage work was begun. Williams and others carrying out the radio experiments went aboard the German battleship, *Bayden*, after she was salvaged, to strip her of radio equipment so the British could learn about the German *telefunken* (for with this method the Germans could transmit at a given distance to avoid their signals being picked up by the enemy, and this the Allies could not do at that time, never being sure how far their signals would go!). "After acquiring this German equipment," explains Mr. Williams, "months were taken up in experimenting. Then we started on the exchange of messages by 'talking.' At that time if anyone had said that soon we would be exchanging messages so many thousands of miles as we now do, we would have called him a 'fool.'"

In 1931, Panama was not on the air. A company was formed, called "Servicio Publico de Radio S.A." Using transmitters atop La Poyera building in Panama City, and by the use of loudspeakers placed in all parts and on street corners of the city, news, music, and other entertainment was given to the public. Hundreds would gather in the evenings to listen to

these broadcasts. It was not until 1933 that Panama first went on the air—and Mr. Williams, who was then carrying his "Radio Newspaper" to the public by means of the loudspeakers, also took to the ether! Although Panama is a Spanish-speaking country, the first news broadcast in Panama was his in *English*—which was followed many months later by a Spanish newscast.

The "Voice of Panama" then took over in place of the loudspeaker system, but the company is the same, and the contract to allow the loudspeaker system to operate is still in force.

Mr. Williams explains that "La Voz de Panama" cannot be missed when you arrive in Panama City. "As soon as you leave the main railroad station, if you look right across the main street, you will see it. In fact, it is right next door to the famous nightclub known the world over as Kelly's (Mrs. Kelly is well-known in the United States for her night club entertainment in Panama). Then, if you stay at the famous International Hotel, where the Casino is situated, you will look out into the 'Voice of Panama.' Many of the guests, incidentally, have complained that the loudspeakers on the balconies of the 'Voice of Panama' building wake them up too early Sundays for 'Take It or Leave It,' which is followed by the national lottery drawings."

Not only is "Take It or Leave It" one of Mr. Williams' outstanding programs, but there is a long list of others. "World's Most Honored Music" at 1800-1830\* Sundays is a popular feature. "Green Hornet," "Lest We Forget These Great Americans," and other U.S. State Department programs; "They Lived to Tell the Tale," "America Speaks," "Story of the U.S.A.," "A Look at Australia," "A Look at South Africa," and so on are presented regularly.

There are few people in the Republic of Panama, and the Canal Zone, who do not know George Williams—for he has been on the air for 16 years in Panama "without as much as 48 hours' vacation!" He probably holds the record for "sticking to the job" as

(Continued on page 148)

Studio A of the "Voice of Panama" in Panama City showing George Williams, Director of the station's popular "Radio Newspaper," at the microphone.



\* Unless otherwise indicated, time herein is expressed in American EST; add 5 hours for GCT. "News" refers to newscasts in the English language.

# Utility Locker makes Deluxe CABINET

By  
CHARLES H. WELCH,  
W5MHK



Fig. 2. (Left) rear view of converted cabinet showing correct way of hanging doors. (Above) front panel view showing window and meter holes cut in Masonite panel.

**Your rig housing can look professional even though basic unit is a low-cost metal cabinet.**

IT IS DOUBTFUL that there is a single case on record in which a ham has viewed commercially-built broadcast equipment without wistful sighs and mutterings about wishing his rig looked as good as that. If he decided to do something about it, a quick glance at price lists on such streamlined cabinets usually was enough to pull his head down out of the clouds, but quickly. If that shoe fits you, take heart fellow, no longer need your lusty sighs rattle the pages of your log-book, for here is a cabinet which can hold up its head in any company, and you can own one like it for about thirty dollars and a very few hours' work. This is a conversion job—not a construction job, so you'll

October, 1947

need only the barest essentials in ham shack tools.

The first step, of course, is to get the cabinet which you are going to convert. The one shown in the photograph of Fig. 1 is marketed as a metal utility locker. It is first cousin to the utility cabinets usually used for kitchen storage. The utility locker differs in having greater depth and no shelves. Its dimensions are sixty-five inches high, twenty-six inches wide, and twenty inches deep. It is of all-steel construction, spot welded, and comes in several colors. It sells at furniture stores for about \$22.50. Of course, it is not necessary to obtain a cabinet identical to this one, though care should be exercised in selection,

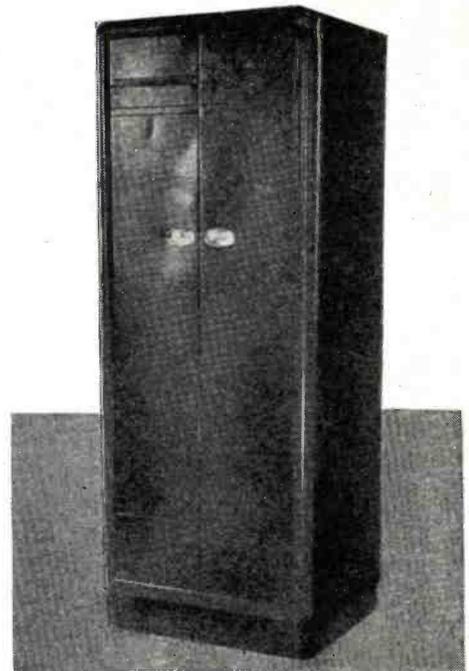


Fig. 1. Utility locker before conversion. These units are universally available.

making sure that the unit is one with rounded corners and streamlined appearance, as well as of sturdy construction.


The first step is to remove the doors, hinges and all. The hinges are spot-welded to the cabinet and should be cut free with a small cold chisel, taking care not to damage the cabinet or hinges any more than necessary. Any roughness left by the weld should be smoothed off before painting later. The door opening is then measured for the panel. The panel itself is cut out of tempered Masonite or similar material. This material has several advantages. It is inexpensive, is easily worked, and when enameled, takes a very good finish. A metal panel could, of course, be substituted if desired. The window for observation of the final amplifier tubes is of plexiglas or similar plastic. If you didn't get any of it on the surplus market, it can be obtained at your local airport in the lighter weights. The window frame is of extruded aluminum molding as sold at lumber yards for edging linoleum table-tops, etc. It comes in many shapes and sizes, so you may choose the one best suited to your panel material. The meter holes are easily cut in the panel, though it pays to use some foresight in the number and spacing, so more may be added easily later, if necessary.

An angle-iron frame should now be made. Its inside dimensions should match those of the door opening. This will be the door frame when the doors are installed in the back of the cabinet. It should be so constructed that one side of the angle-iron will bolt flat against the back, the other turning in to make the door facing. This

(Continued on page 162)

# Practical RADIO COURSE

By  
**ALFRED A. GHIRARDI**

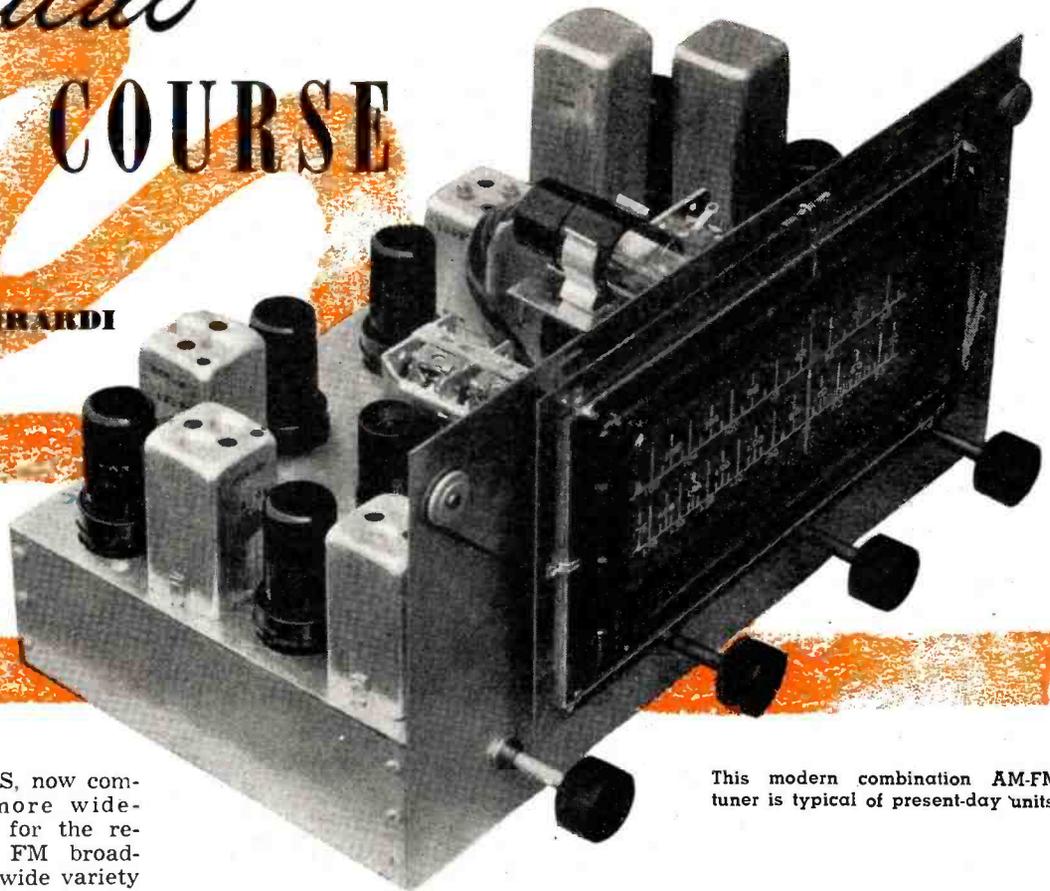

This modern combination AM-FM tuner is typical of present-day units.

**FM** RECEIVERS, now coming into more widespread use for the reception of high-fidelity FM broadcast programs and for a wide variety of FM communications services, usually employ the superheterodyne principle. Consequently, each FM receiver employs an intermediate-frequency amplifier (see Fig. 1) that contributes the major part of the r.f. gain of the receiver and provides the selectivity necessary to prevent possible interference from adjacent-channel FM transmitters.

Because FM signals have several special characteristics that differ from those of AM signals, it is necessary to design the i.f. amplifier of an FM superheterodyne receiver to have special selectivity and bandpass characteristics to meet their requirements. These requirements will be better understood if we digress from our study of intermediate-frequency amplifiers at this point in order to review briefly the fundamentals of frequency modulation and to become better acquainted with the characteristics of the FM signals commonly employed in high-fidelity FM broadcasting, and those used in FM communications work.

## Review of Amplitude Modulation

It will be recalled from the discussion presented in a previous article<sup>1</sup> of this series that when *Amplitude Modulation* (AM) is employed for modulating an r.f. carrier wave by an audio-frequency modulating voltage, the frequency of the carrier remains constant but its *amplitude* is varied in accordance with the variations in the

## Part 55. Analysis of circuits, components, and signals that make up present-day high-fidelity FM receivers.

modulating voltage. This is illustrated by the series of audio modulating voltages (drawn at the center) and the series of corresponding amplitude-modulated r.f. waves produced (each one is drawn directly above the audio modulating voltage that produced it) in Fig. 4. Observe from these illustrations that the following relations between the modulating voltage and the amplitude-modulated r.f. carrier wave hold true:

1. During modulation the *amplitude* of the transmitted modulated r.f. wave (and the radiated power) is varied, but its frequency remains unchanged. (Observe that in the amplitude-modulated waves shown at A, B, C, D, in Fig. 4, the amplitude of the r.f. wave varies but the frequency—number of cycles per second—remains unchanged.)

2. An increase in the *amplitude* of the audio modulating voltage (weak sound, to loud sound, to louder sound) causes the *amplitude* of the resulting amplitude-modulated r.f. wave to vary over a wider range. (Compare

waves A and B—also waves C and D—in Fig. 4).

3. An increase in the *frequency* of the audio modulating voltage (low frequency sound to higher-frequency sound) increases the *rate* at which the amplitude of the modulated r.f. wave is varied. (Compare waves B and C in Fig. 4).

4. The bandwidth occupied by the sideband frequency components produced depends only upon the *highest frequency* of modulation, and not upon the degree of modulation. (Study illustrations A, B, C, D; then study and compare the corresponding sideband component illustrations above them in Fig. 4).

5. Since only one pair of sidebands is produced for each modulating frequency, a bandwidth of *twice* the highest modulating frequency is sufficient for satisfactory passage of the amplitude-modulated wave under any degree of modulation. (Study illustrations A, B, C, D and the corresponding sideband frequency component illustrations in Fig. 4).

In frequency modulation (FM), the modulating is done by varying the fre-

<sup>1</sup> See Alfred A. Ghirardi, *Practical Radio Course*, Part 54, (RADIO NEWS, July 1947).

quency of the transmitted wave; its amplitude remains unchanged. Sideband frequency components are created in the frequency-modulation process, as in the amplitude-modulation process, but they can be much more numerous in FM. A summary of the more important relations that exist between the modulating voltage and the resulting frequency-modulated r.f. wave follows:

1. During modulation the *frequency* of the transmitted wave is varied but its amplitude remains unchanged. (Study frequency-modulated waves E, F, G, H in Fig. 4, and observe that the amplitude is constant in each but the frequency varies, as indicated by the occasional narrowing and widening of the r.f. alternations.) The radiated power also remains unchanged.

2. An increase in the *frequency* of the audio modulating voltage increases the *rate* at which the frequency of the transmitted wave is varied. (Study frequency-modulated waves F and G, and the audio modulating voltage wave, directly above, corresponding to each.)

3. An increase in the *amplitude* of the audio modulating voltage causes the frequency of the transmitted wave to *deviate* or be varied over a wider range. (Study frequency-modulated waves E and F, G and H, and the audio modulating wave corresponding to each.)

4. The frequency-modulated r.f. wave is the sum of a *center-frequency* component and numerous pairs of *sideband* frequency components. (The center-frequency component has the same frequency as the unmodulated carrier.) The two components comprising the *first* sideband pair have frequencies respectively higher and lower than the center-frequency component by the amount of the modulating frequency (just as in amplitude modulation). Observe this in the sideband component illustrations (directly below) corresponding to frequency-modulated waves E, F, G, H in Fig. 4. There are additional pairs of sideband components which can have appreciable amplitude and therefore be of considerable importance. For example, the *second* pair of sideband components, having frequencies that are higher and lower than that of the center frequency component by *twice* the amount of the modulating frequency, can also be important. (See frequency-modulated wave F and the illustration, directly below it, of the center-frequency component and sideband components of which it is composed.) The same is often true of the *third* pair of sideband components which are of frequency removed from the center frequency by *three* times the modulating frequency (see wave H and the illustration of its sideband components directly below it), and of higher orders of sideband component pairs whose frequencies differ from the center frequency by correspondingly greater amounts. When the modulation is slight, only the pair of sideband components nearest in fre-

October, 1947

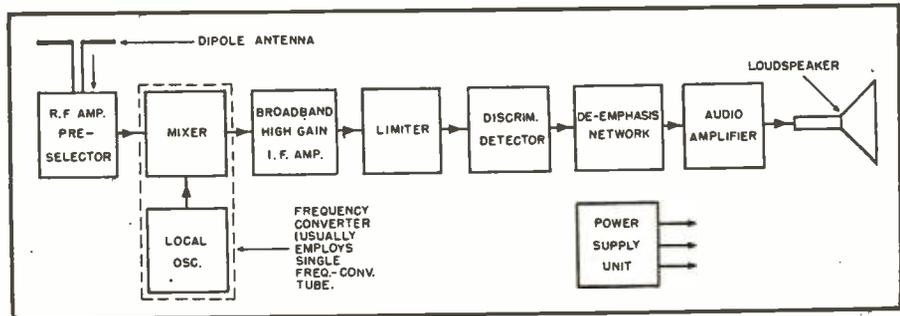


Fig. 1. Basic elements of a typical FM superheterodyne broadcast receiver.

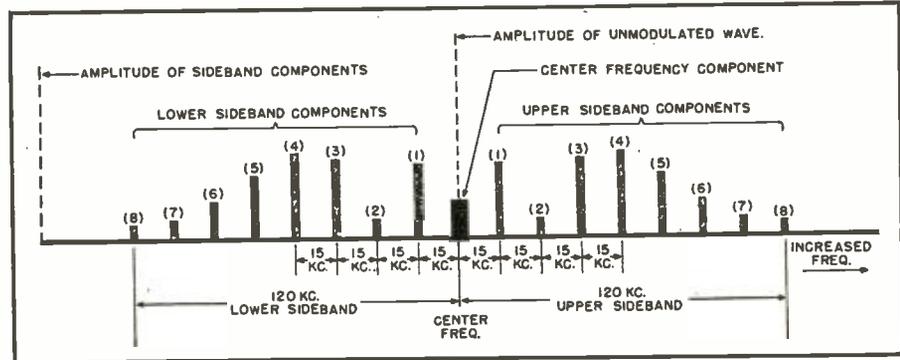



Fig. 2. Illustrating the center-frequency component and eight pairs of sideband components produced (drawn here in their relative amplitudes) when the frequency is varying over the full deviation range of  $\pm 75$  kc. (100 percent modulation) at 15 kc. per second, in FM broadcasting. The separation between each two adjacent sideband components is equal to the modulating frequency.


quency to that of the center-frequency component will have sufficient amplitude to be important. Under this condition, the bandwidth required is no greater than it would be if amplitude modulation were used instead. (Study waves A and E and observe the number and frequency spacing of the sideband frequency components produced for each.) As the extent or level of the modulation is increased (corresponding to greater *depth* of modulation in AM), more pairs of sideband components acquire appreciable amplitude and become important, so the bandwidth transmission and reception requirements become much greater than for amplitude modulation. (It will be instructive to compare both the *amplitudes* and the *frequency* separation of

the various sideband components produced by the different frequency-modulation conditions illustrated in Fig. 4, by examining and comparing, in turn, the illustrations of the sideband component composition of waves E and F, F and G, and G and H. The sideband components produced in FM may be compared directly with those produced in AM by examining, in turn, the sideband component illustrations corresponding to waves E and A, F and B, G and C, H and D (in Fig. 4).

5. The bandwidth produced in FM depends upon both the level of modulation and upon the modulating frequency. The greatest bandwidth occurs when the wave is subjected to *maximum modulation* (100%) at the *highest modulating* frequency, for then the frequency difference be-

Fig. 3. FCC standard FM broadcast signal and transmission channel specifications. The sideband frequency components set up at 100 percent modulation, when the audio modulating frequency is at the system-maximum of 15 kc., are shown at the top of their relative amplitudes.

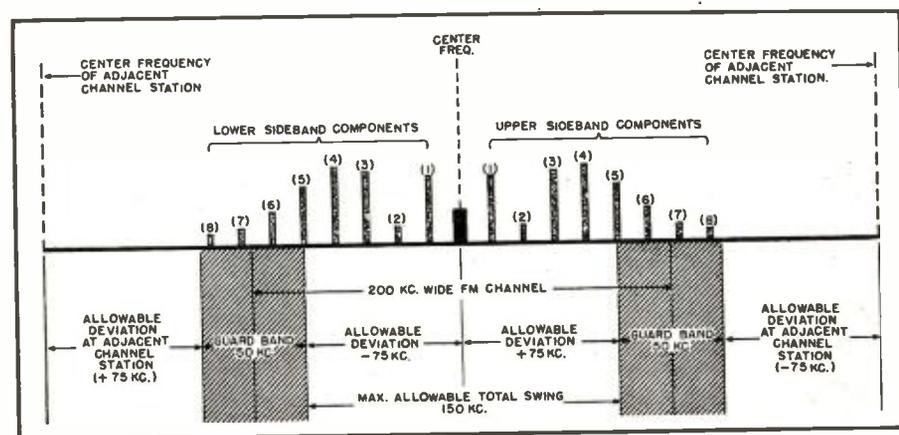

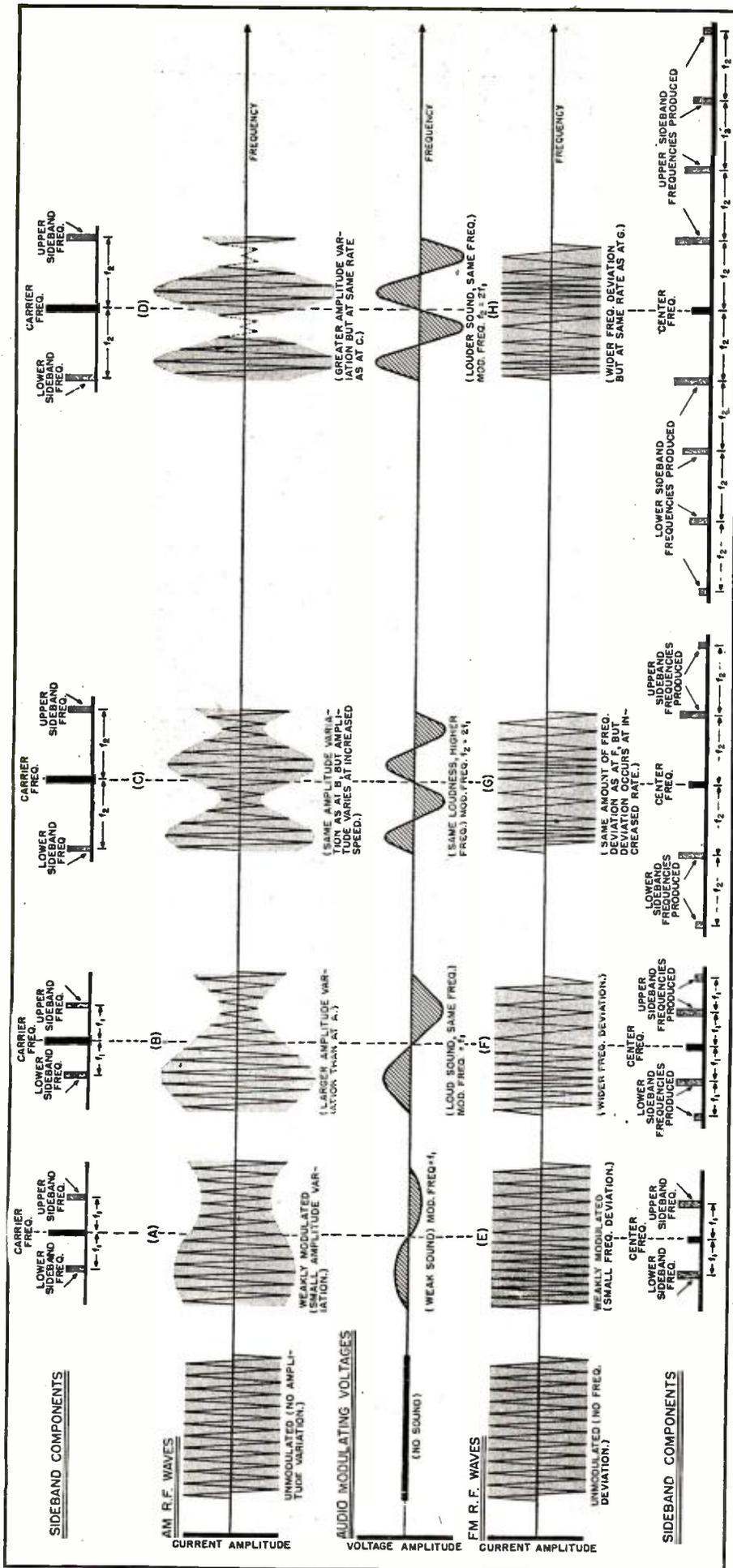

tween successive sideband components is greatest and the amplitudes of those far removed from the center-frequency are large enough to make them important (see Figs. 2 and 4). Under this condition, the bandwidth may exceed considerably the peak-to-peak frequency swing. (See strongly-modulated wave *H* and its sideband component illustration in Fig. 4.) The least bandwidth is required under a condition of slight modulation, but under any condition of modulation the total channel width is never less than the amount of twice the modulating frequency. (See weakly-modulated wave *E* and its sideband component illustration, in Fig. 4.)

It will be instructive to compare these characteristics of frequency modulation with those stated previously for amplitude modulation.

A frequency-modulated current or wave may be visualized as one of constant-amplitude, but whose frequency is caused to vary, from its "center" or "resting" value, by the audio modulating voltage. The extent to which its frequency is caused to vary from its "resting" value, from instant to instant, is governed by the amplitude of the modulating voltage at each instant. The rate at which it is caused to vary at any instant is governed by the frequency of the modulating voltage at that instant.

#### Audio Frequency Range Required for Speech

In FM communications systems, such as those employed for police radio, emergency radio, some phases of amateur radio, etc., it is usually necessary to transmit *speech* intelligence only. In such communication the highest audio modulating-frequency that must be handled for intelligible communication is of the order of only about 3000 cycles, so the sidebands required to be transmitted are comparatively narrow.

#### Audio Frequency Range Required For Hi-Fi Broadcasting


In a high-fidelity FM broadcasting system, for transmission and realistic reproduction of any sound material including a symphonic program, it is desirable that an adequate *dynamic* (volume) range and the full audio frequency range from 50 to 15,000 cycles be transmitted, received, and reproduced so that all the important overtones of musical instruments such as the violin, flute, etc., will not be lost and full realism preserved. Since frequencies higher than about 15,000 cycles are inaudible to most human ears, it has been decided that the audio cut-off in American high-fidelity FM broadcasting, should occur at about 15,000 cycles (15 kc.). This is in contrast to a cut-off value of the order of 5000 cycles which, for sev-

Fig. 4. Direct comparison of the effects produced by amplitude modulation and frequency modulation when first the amplitude, and then the frequency, of the modulating audio voltage, or sound, is increased.

# NEW!

**in 1,000 pages:**

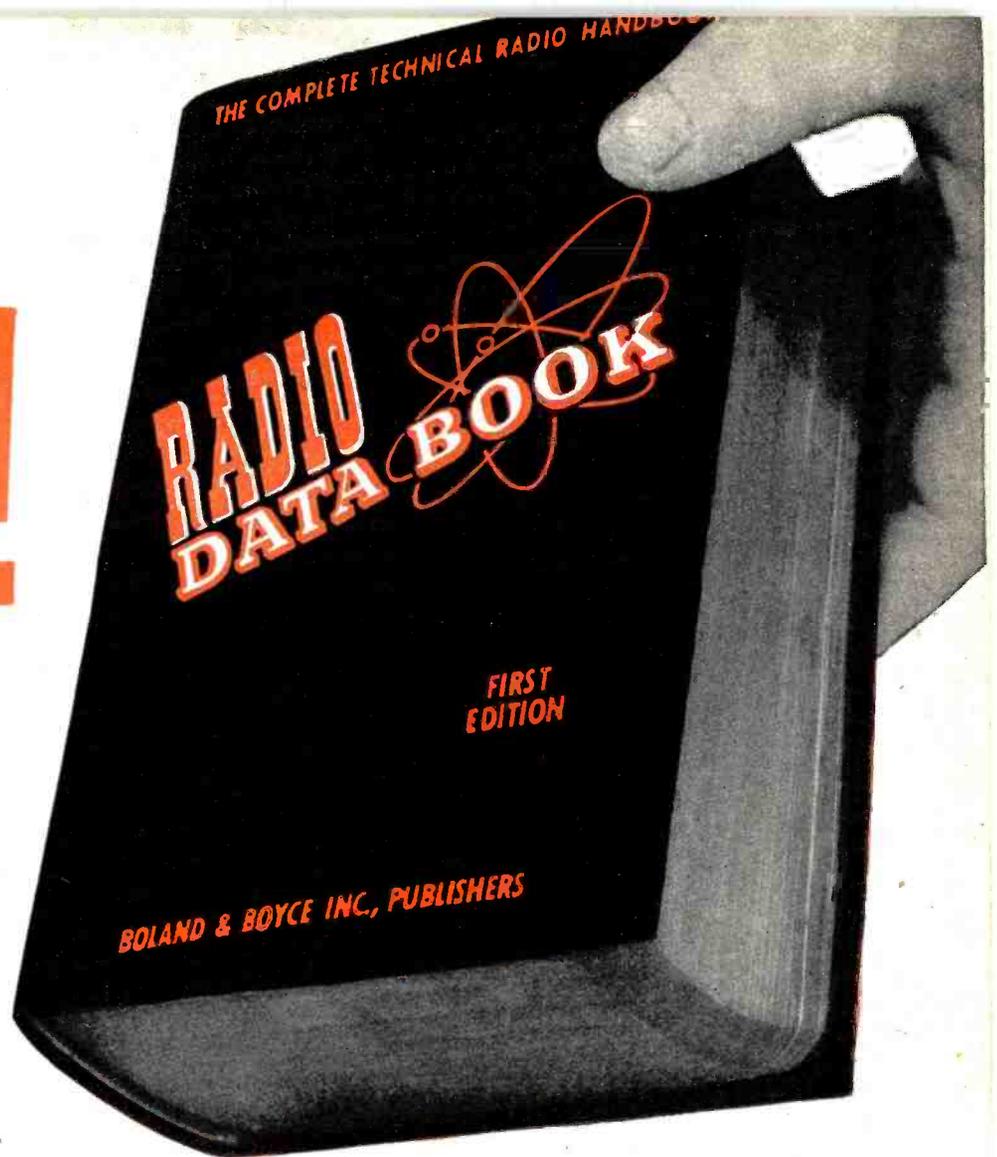**All data and basic knowledge in radio and electronics digested into 12 sections... in a complete, quick to find, easy to read, handbook form.**



Plan every operation in radio and electronics with the *Radio Data Book*. This new radio bible will be your lifelong tool... you will use it every day, on the board, at the bench, in the field! Use it for construction, troubleshooting and testing. The RADIO DATA BOOK will be your invaluable aid in design, experiment and in layout. It will help make your production better, faster and easier. In any and every operation in radio and electronics, you will use the RADIO DATA BOOK!

The RADIO DATA BOOK is a work of complete authority, prepared by engineers with many years of practical experience. They have been assisted by the Boland & Boyce staff of editors skilled in preparing electronics manuals for the U. S. Signal Corps for many years. These men have worked for several years gathering material for this book... all the knowledge of radio principles and operation... all the statistics... all the newest developments in electronics... every possible angle and detail. Eighteen months were spent digesting this material into the most concise, the clearest, and the most readable form. The result is this invaluable manual... The RADIO DATA BOOK. Whether you use this book for general reference, for scientific instruction, or for education, one thing is certain—the practical help, the daily usefulness you will derive from it will prove to be worth many, many times its astonishingly low price!

Advanced Sale... first printing, Only 10,000 available... To make sure to get your RADIO DATA BOOK, mail your order **NOW!**

**12 complete books in one only \$5.00! Less than 42c per book!**

**MAIL THIS COUPON TODAY!**

**BOLAND & BOYCE INC., PUBLISHERS**  
**460 BLOOMFIELD AVE. MONTCLAIR 3, N. J.**

Please send me a copy of

**THE RADIO DATA BOOK** Enclosed is \$5.00.

NAME .....

ADDRESS .....

CITY ..... ZONE .....

STATE .....

**BOLAND & BOYCE INC., PUBLISHERS**

**CONTENTS**

Each section is a COMPLETE coverage of its subject... 12 sections... 12 books in ONE! 1000 pages... Schematics... Accurate photographs... Specially prepared drawings... White on black charts... Diagrams... Isometric projections and exploded views.

**Section 1. THE 150 BASIC CIRCUITS IN RADIO.**

Every circuit is analysed and explained in a Johnny-on-the-spot reference for any occasion.

**Section 2. COMPLETE TEST EQUIPMENT DATA.**

Know more about the test instruments you now have... Find the new ones you want to buy... They're All in here—impartially described!

**Section 3. TESTING, MEASURING AND ALIGNMENT.**

Simplified operation of the Oscilloscope... See what's happening inside any radio circuit... Dynamic alignment—AM, FM and TELEVISION made easy with the Oscilloscope... Scientific use of the Vacuum Tube Voltmeter, Signal Generating Equipment and other basic instruments.

**Section 4. ALL ABOUT ANTENNAS.**

AM-FM-Television... design, installation, characteristics, construction and feed.

**Section 5. SOUND SYSTEMS.**

Planning, installing and servicing a PA System. A complete chapter on every component... How to select and combine components... estimating costs... even acoustic requirements!

**Section 6. ELECTRICAL AND PHYSICAL CHARACTERISTICS OF RADIO COMPONENTS.**

Know the size, the power, the shape! A quick reference on the construction and design of any circuit or equipment.

**Section 7. COMPLETE TUBE MANUAL: Receiving, transmitting and Commercial.**

A flick of the pages brings you to all the data and ratings of any tube model

**Section 8. CHARTS, GRAPHS AND CURVES.**

Quick calculation devices... Plotting curves, nomographs, rules and tables for speedy solutions to radio problems.

**Section 9. CODES, SYMBOLS AND STANDARDS.**

Handy reference to all radio symbols and abbreviations; code symbols, phrases and characters... Where you want them... When you want them!

**Section 10. 50 TESTED CIRCUITS DESIGNED FOR OPTIMUM PERFORMANCE.**

Find any circuit you want with complete parts lists and specifications... One tube receivers to complete AM, FM and Television receiver circuits... Amplifiers... Transmitters... Test Equipment and Control Circuits... All with the latest engineering refinements.

**Section 11. DICTIONARY OF RADIO AND ELECTRONIC TERMS.**

**Section 12. RADIO BOOK BIBLIOGRAPHY.**

# This Month's Specials

## GREATEST Radio Phonograph Combination VALUE of the YEAR

5 Tube AC-DC Superhet Radio, Phonograph Motor, Pick up Arm, in Attractive Table Model Cabinet.  
Extremely Fine Reception and Record Reproduction. 10" or 12" records



**\$24.95 each**  
IN LOTS OF THREE . . . \$23.95 ea.

### ★ Single Crystal Head Phones . . . Can be Used as Microphone or Head Set

**29c** EACH WITHOUT CORD

**39c** EACH WITH CORD

### ★ SERVICEMEN, BUILDERS, HAMS


Alnico 5 PM Speakers, All of Highest Quality. Fully Guaranteed, at Lowest Prices Yet.

2" PM.....\$1.19 each	5" PM 1 oz.....\$1.39 each
3" PM.....1.35 each	6" PM 1.5 oz.....1.79 each
4" PM.....1.29 each	10" PM 6.8 oz.....4.75 each
12" PM General Electric 6.8 oz.....\$6.95 each	



- ★Microphone Floor Stands—Extra Heavy Base—Adjustable, Chrome Stem . . . . . **\$4.39 ea.**
- 10 Watt AC Amplifiers—Undistorted, High Fidelity, Complete With Tubes—7N7—2—7C6 PP, 7Z4 . . . . . **\$9.95 ea.**
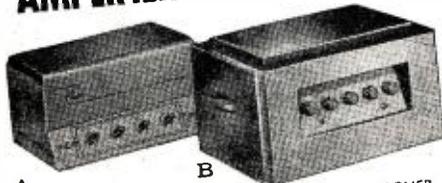
### ★ AMPLIFIER FOUNDATION CHASSIS AND COVERS



These are Attractive, Well-Constructed Chassis and Covers, used by the better Amplifier Manufacturers, at Exceptional Prices.

<b>BASE</b>	<b>COVER</b>	<b>PRICE</b>
8x12x3	A	\$1.75
9x15x3	A	2.35
11x17x3	B	2.65

### ★ SUPERIOR CONDENSERS

A new condenser line—Featuring the Five most popular Electrolytics—Designed for the user of Replacement parts—Unconditionally guaranteed. All users have been fully satisfied by these quality condensers at record saving prices.

8 MFD 450 Volt.....10 for \$2.25	20 MFD 150 Volt.....10 for \$2.25
10x10 MFD 450 Volt.....10 for 4.75	20x20 MFD 150 Volt.....10 for 3.35
50x50 MFD 150 Volt.....10 for \$4.75	

# Radio Parts Company

612 W. RANDOLPH - Dept. N - CHICAGO, ILL.

eral reasons, is the limited value employed in AM broadcasting.


### Composition of Signals in Hi-Fi FM Broadcasting

As previously explained, and illustrated in Fig. 4, for an equal maximum modulating frequency and level of modulation, the bandwidth required by FM signals is much greater than that for AM signals since a wider set of sidebands, containing sideband frequency components that are important, is produced in FM. Thus, in AM sound broadcasting since the highest modulating frequency is 5 kc., the highest-frequency sideband components that will be produced have frequencies respectively higher and lower than the carrier frequency by the amount of 5 kc. Consequently, transmission of a total bandwidth of  $2 \times 5 = 10$  kc., centered at the carrier frequency, is adequate, and AM broadcast station channels may be spaced only 10 kc. apart.

By contrast, in the case of FM signals a large number of pairs of sideband components of appreciable amplitude (and importance) may be present along with the center frequency component. Maximum bandwidth is required when the FM signal is fully modulated (100% modulation) at the highest modulating frequency, for then the frequency difference between successive sideband components is greatest and the amplitudes of those far removed from the center-frequency are large enough to make them important. (See Figs. 2 and 4.) The actual numerical value of the maximum bandwidth it is necessary to transmit depends, therefore, upon the number of important pairs of sidebands to be transmitted, as well as upon the maximum modulating frequency.

An extensive study of the sideband requirements and other factors involved in FM broadcasting has been made in order to determine how wide a frequency swing or *deviation* produced on each side of the unmodulated center frequency shall be designated as representing 100% modulation. The engineering standards of the FCC now define a frequency swing or deviation of  $\pm 75$  kc. from the center frequency (often called the *resting frequency*) as 100% modulation and, by FCC regulations, American FM broadcast transmitters are now allowed this maximum modulation swing or deviation on either side of the unmodulated center frequency. This means that when the modulating frequency is at the maximum value of 15 kc., and the modulation is 100%, the signal frequency will have deviated  $\pm 75$  kc. from its assigned center or resting frequency. This practice provides a frequency deviation ratio of 75/15, or 5 to 1, with full modulation at the highest modulating frequency.

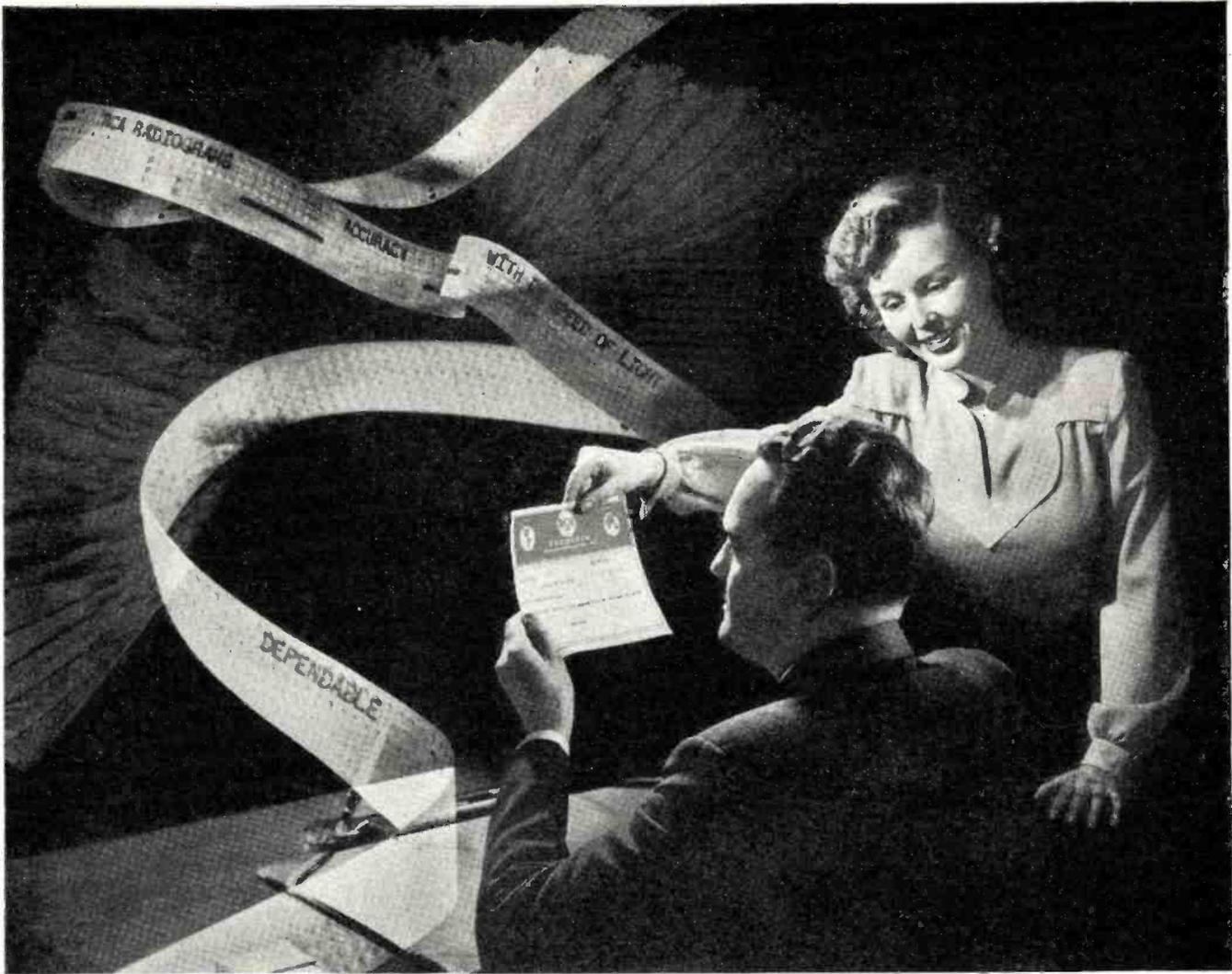It can be shown mathematically (by the use of Bessel factors) that if the frequency of the FM wave is varying over this full range of plus or minus



RCA Communications' new world-wide automatic tape relay radio system speeds Radiograms.

## ***New wings for words around the world!***

Radiograms "Via RCA" to and from overseas points now are processed by automatic machines which speed your messages through such gateway cities as New York, London, San Francisco and Manila, without delay.

This advanced technique in international radiotelegraphy is the result of wartime research and development. It gives to private messages the same speed, accuracy and dependability which were attained through its world-wide use by the U. S. Army Communications Service during the war.

"Victrola" T. M. Reg. U. S. Pat. Off.

RCA Laboratories—one of the world's foremost centers of radio and electronic research—is continually pioneering and advancing radio communications in service to the Nation and the public.

When you buy an RCA Victor radio or television receiver, Victrola radio-phonograph, or phonograph record, you are getting, thanks to RCA research and engineering, one of the finest products of its kind science has achieved.

*Radio Corporation of America, RCA Building, Radio City, New York 20. Listen to the RCA Victor Show, Sundays, 2:00 P.M., Eastern Daylight Saving Time, over the NBC Network.*



At RCA Communications, "Package-Sets" contain an automatic sending and receiving unit for a foreign gateway city. Messages, in tape form, received through these machines, are ready for quick delivery or immediate transmission to any part of the world.



**RADIO CORPORATION of AMERICA**

Another  
Radio  
Shack  
Special!

**ALUMINUM BLANK CHASSIS**

7x 9x2, Natural Finish, List	\$1.70	NET	\$1.02
7x11x2, Natural Finish, List	1.82	NET	1.09
5x 9x3, Black Wrinkle, List	1.82	NET	1.09
8x17x3, Black Wrinkle, List	3.20	NET	1.90
10x14x3, Black Wrinkle, List	3.12	NET	1.86
10x17x3, Black Wrinkle, List	3.38	NET	2.00
13x17x3, Black Wrinkle, List	5.00	NET	3.00
6x 6x6, Black Wrinkle, List	2.00	NET	1.20
6x 9x5, Black Wrinkle, List	3.00	NET	1.84



**STANDARD PICK-UP ARM**  
With Cartridge.  
EACH **\$1.50**  
Arm unpainted.



**New Standard REPLACEMENT CONTROLS**  
for Superior Performance with S.P.S.T. Switch

Cat. No.	Ohmage	Taper
501	10,000	Ant. "C" Bias
502	20,000	Ant. "C" Bias
503	50,000	Voltage Divider
504	100,000	Linear
505	1/2 meg.	Audio Taper
506	1/2 meg.	Audio Taper
507	1 meg.	Audio Taper
508	2 meg.	Audio Taper
516	1/2 meg.	Linear Taper
517	1 meg.	Linear Taper
518	2 meg.	Linear Taper

Choice **69c** Each

**AMERICAN BEAUTY SOLDERING ELEMENTS**

**\$1.85**

Takes 3/8" tip.  
100 watt.  
**COPPER TIPS, 35c ea.**



**NEW FROHM 55-65 CYCLE FREQUENCY METER**  
**\$5.95**  
Ideal for amateur use.  
List price—\$21.95

Quality at LOW PRICE!

**6 Ft. Line Cords with Plug**

EACH **15c**  
Black, Brown, White  
Per 100... \$14.00  
F.O.B. Chicago. 25% Deposit on all orders


**GUARANTEED CONDENSERS**

H.R.S. 20 MFD.	150 V.	\$0.25 each
10 For		2.00
Sprague 10 MFD.	450 V.	.35 each
10 For		3.20
Sprague 8x8 MFD.	450 V.	.45 each
10 For		4.30
Standard 8 MFD.	450 V.	.25 each
10 For		2.00

**LIMITED QUANTITY! ROTARY SWITCHES**

Single pole, 10 position Rotary Switches. Ideal for test equipment. Ceramic insulation.

**45c**

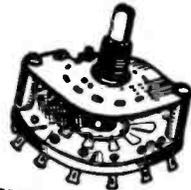

**ORDER NOW**

**Portable Record CHANGER CASE**

**\$5.95**

Black leatherette. Inside dimensions on changer base 13" x 15" with 9" depth. Will take 6" speaker.



**The Radio Shack Inc. OF CHICAGO**

630 W. RANDOLPH STREET CHICAGO 6, ILL

75 kc., at 15 kc. per second (100% modulation at the highest modulating frequency 15 kc.) a center-frequency component and eight important pairs of sideband components are present, each sideband pair having frequencies that are higher and lower than the center frequencies by  $n$  times the numerical value of the modulating frequency (where  $n$  = the pair number). The 16 individual sideband components comprising these eight pairs (labeled numerically for identification) are illustrated in Fig. 2 in their correct relative amplitudes. Observe that the amplitude of the center-frequency component is much less than that of the unmodulated wave, only 17.76 per-cent as great, in this case.


The theoretical total bandwidth required by the eighth pair of sideband components will be,  $8 \times 15 \times 2 = 240$  kc., centered at the unmodulated center frequency. Actually, it is not necessary to provide for a bandwidth as wide as this because, as can be seen from Fig. 2, the amplitude of those sideband components of frequency near the limits of this theoretical band are of comparatively small amplitude (for example, the amplitude of the eighth sideband pair is quite small, being only 1.84% of the unmodulated carrier amplitude, that of the seventh pair is 5.34%, etc.) and they appear only when the transmitter is strongly modulated at the higher audio frequencies.

**Specifications for Standard FM Broadcast Channel**

Since some relatively weak sideband components actually extend beyond 75 kc. on either side of the center frequency, to avoid the possibility of interference between powerful FM broadcast stations assigned to adjacent transmission channels, a guard band of 50 kc. is allowed between the maximum modulation swings of adjacent-channel stations. This is illustrated in Fig. 3. Since the total permissible frequency swing or deviation is  $2 \times 75 = 150$  kc., this, plus the guard band, makes a total channel width of  $150 + 50 = 200$  kc. necessary for each FM broadcast transmitter. The specifications for the standard American FM broadcast channel (FCC regulations) are illustrated in Fig. 3 for reference. The sideband frequency components that are produced at 100% modulation when the audio modulating frequency is at the system maximum of 15 kc. are shown in their relative amplitudes at the top of the illustration. Observe that those which are eliminated by the standard transmission channel specifications are the higher-frequency ones of relatively low amplitude (and importance).

By FCC regulation then, an FM broadcast channel comprises a band of frequencies 200 kc. wide (see Fig. 3). Such a channel is designated by its center frequency. In America, channels for FM broadcast stations now begin at 88.1 mc. and continue in suc-

(Continued on page 110)

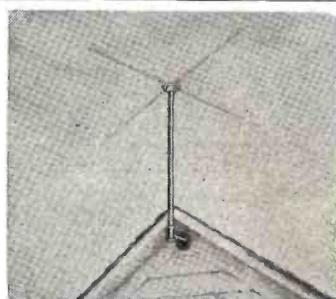

Throughout the Country the **HI-PAR non-directional FM Antenna** is replacing obsolete types.

**HI-PAR meets all present and future requirements**

If your jobber cannot supply you send us his name.

**HI-PAR PRODUCTS CO. FITCHBURG MASSACHUSETTS**


# AUDIO TRANSFORMERS for [ UNIFORM RESPONSE LOW DISTORTION

## IN 3 FREQUENCY RANGES

*Write for Catalog  
showing complete  
new stock line*
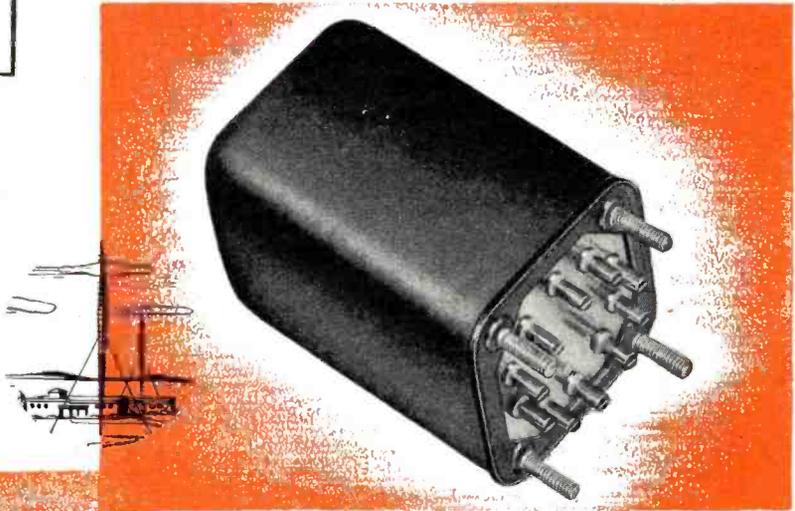
### Full Frequency Range

**30 to 15,000 Cycles**, provides uniform response over this entire band with  $\pm 1/2$  db up to 10 watts of audio power, within  $\pm 1$  db over 10 watts. Standard RMA impedances. Hum balancing coil structures and nickel alloy shielding. Included are Input, Output, Driver, and Modulation Transformers; Modulation Reactors. *Sealed in Steel* construction, stud mounting, with pin-type terminals.



### Public Address Range

**50 to 10,000 Cycles**, frequency response within  $\pm 1/2$  db up to 10 watts of power, within  $\pm 1$  db over 10 watts, throughout this range. Secondary impedances match 600 and 150-ohm lines, 16, 8 and 4-ohm reproducing systems. Listed are Driver and Output Transformers. *Sealed in Steel* construction, flange mounting, with solder lugs or wire leads.



### Communications Range

**200 to 3,500 Cycles**, affords response with variations not exceeding  $\pm 1$  db over the range of voice frequencies. For use with 600 or 150-ohm lines. Input, Output, Driver and Modulation Transformers offered. *Sealed in Steel* construction, flange mounting, with wire leads or solder lugs.



# CHICAGO TRANSFORMER

DIVISION OF ESSEX WIRE CORPORATION

3501 ADDISON STREET • CHICAGO 18, ILLINOIS

# Simplified Servicing for All AM-FM TELEVISION with **EICO** TEST EQUIPMENT

## Model 315—SIGNAL GENERATOR

Micro-cycle band spread vernier tuning. Vitally important for tuning and aligning FM and Television receivers where tuning is very sharp and critical. The extreme wide range and accuracy afforded by the micro-cycle vernier band spread dial assures accurate frequency adjustment for test or alignment of broadcast FM or Television receivers. Vernier dial divided into 100 divisions. Any frequency can be tuned and repeated within .02% accuracy. Spring loaded split gears eliminates back lash and play providing smooth, accurate tuning. Extremely accurate and stable throughout its range. Window casing encloses dial and fine pointer, protecting the pointer against being accidentally bent or jarred out of calibration.

- Range 75 KC to 150 MC.
- Complete broadcast band from 550 KC to 1700 KC is covered on one range without switching.
- Unused coils are automatically shorted out to eliminate dead spots and absorption.
- Linear dial calibration, DOES NOT CROWD UP on the high frequency end of the dial.
- Accuracy better than .5% throughout the broadcast band and 1% on the higher frequencies.
- Just as accurate at high end of dial as the low end.
- Indirect lighting of dial scale with two hooded lights.

**\$64<sup>50</sup>**

Your net



## Model 113A—MULTI-ANALYST

Permits rapid tracing or following a signal audibly through the receiver from antenna to speaker, locating the faulty section quickly. Isolates the precise cause of trouble with the VTVM section by making point to point checks giving both audible and visual indications. Perfect for checking distortion or fading. Signal may be traced through entire receiver without interfering with its normal operation.

- Wide frequency response from 30 cycles to 200 mc.
- High input impedance of 26 megohms on DC.
- All electronic AC and DC voltmeter and ohmmeter.
- DC and AC ranges 0-5, 10, 100, 500, 1000 volts.
- Ohmmeter reads from .1 ohm to 1,000 megohms in six ranges.
- Built-in speaker for monitoring either IF, RF or AF channel.
- VTVM cannot be damaged by overload.
- Will substitute for any defective stages in a radio receiver or amplifier.
- Tests—phono pick ups—microphones, etc. for distortion or voltage output.

**\$89<sup>50</sup>**

Your net

## Model 210—VACUUM TUBE VOLTMETER

A versatile test instrument for all radio and electronic service work, in manufacturing plants, laboratories, etc. Accurately measures wide ranges of resistance and voltages easily and rapidly. Visually traces signals in any receiver. Its huge 8½" meter makes readings easier and more accurate.

- No drift after short warm-up period.
- RF—AC probe permits linear readings from 50 cycles to 300 megacycles.
- DC ranges 0-5, 10, 100, 500, 1000, 5000 volts.
- AC ranges 0-5, 10, 100, 500, 1000 volts.
- Ohmmeter reads .1 ohm to 1,000 megohms, in six ranges.
- 26 megohms DC input resistance prevents loading when making voltage tests.
- Electronic on all functions.
- Meter circuit is designed to make burnout of meter impossible.
- Meter specially damped for fast accurate reading.

**\$69<sup>50</sup>**

Your net

EICO Equipment Manufactured by Electronic Instrument Co., Inc., Brooklyn, N. Y.



ORDERS FILLED SAME DAY RECEIVED—TERMS: 20% Deposit, Bal. C.O.D. or Remittance with Order

WRITE for METROPOLITAN  
TIME PAYMENT PLAN

1/3 down and up to 1 year to pay.

INQUIRE about amazingly high allowance  
for your used Test Equipment.

—WRITE FOR FREE CATALOG—

# Metropolitan ELECTRONIC & INSTRUMENT CO.

DEPT. RN-10—42 WARREN ST.  
NEW YORK 7, N. Y., U. S. A.

Cable Address: METRONICS, NEW YORK  
Phone: BARclay 7-5556


# Low Cost **TELEVISION** **IS HERE!**

*Certified*  
**TELEVISION  
RECEIVER**

**Ready for EASY  
RAPID ASSEMBLY!**

A complete television kit using a seven-inch tube which gives a 26-square-inch picture. This kit has everything, all power transformers, chokes, IF's-RF's, condensers, resistors, mounting brackets, nuts, front panel and a complete punched chassis, plus simple-to-understand schematic diagrams. This receiver is a well-engineered piece of equipment having three stages of Video IF amplification which are slug tuned for maximum gain and efficiency. Only five controls are on the front panel giving simplicity of operation. The instructions are written in an easy step-by-step system enabling accurate construction. Alignment procedure without the use of expensive test equipment is given in detail. A specially constructed glass between the scope tube and panel along with grill cloth is included. Besides all of the above, a beautifully finished front panel comes to you in choice of walnut, blonde maple or mahogany.

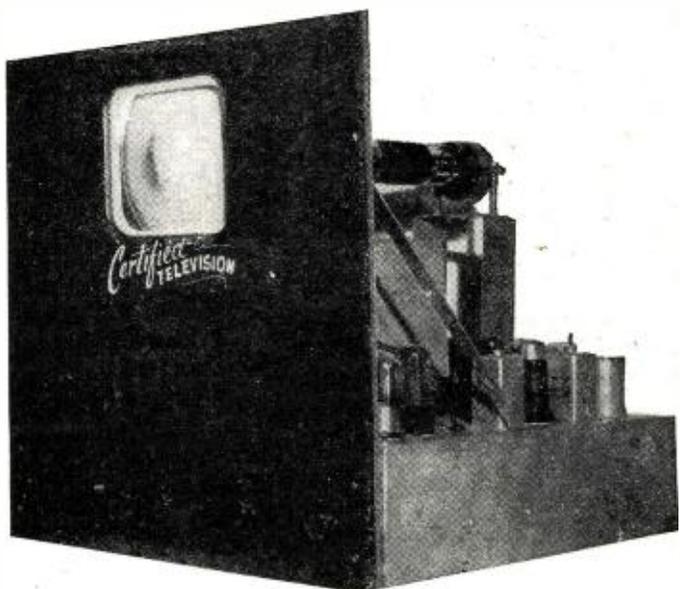... a **TERRIFIC VALUE!!** Never before have we offered so much for so little....



**THE GREATEST BUY IN TELEVISION**

**YOUR PRICE** **\$89<sup>95</sup>**  
(less tubes)  
Complete with all tubes **\$129<sup>95</sup>**

ORDERS FILLED SAME DAY RECEIVED—TERMS: 20% Deposit, Bal. C.O.D. or Remittance with Order

LARGEST STOCK OF ALL WELL-KNOWN BRANDS  
OF TEST EQUIPMENT IN THE UNITED STATES.

**WRITE FOR FREE CATALOG**

*Metropolitan* **ELECTRONIC & INSTRUMENT CO.**


DEPT. RN-10—42 WARREN ST.  
NEW YORK 7, N. Y., U. S. A.

Cable Address: METRONICS, NEW YORK  
Phone: BArcly 7-5556

**BUILDERS! EXPERIMENTERS!**


**Make ALLIED  
Your RADIO KIT  
HEADQUARTERS!**

**HI-FIDELITY  
BROADCAST  
TUNER**

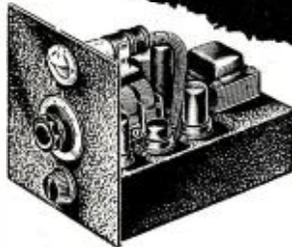

An easy-to-build high-fidelity TRF Tuner Kit. Features broad band reception for higher fidelity than obtainable in standard superhet circuits. Linear diode detection for quality demodulation; separate diode AVC for constant signal. Cathode follower output circuit. "Magic Eye" tuning. Vernier dial, 0-100, 5-1 ratio. Built-in power supply. Complete with all quality parts, including 5 tubes plus rectifier, punched chassis (10x6 1/2 x 3") and panel, matched coils and detailed 4-page instruction booklet For 110-125 volt, 60 cycles A. C. **\$2425**

**10-WATT  
HI-FI  
AMPLIFIER**

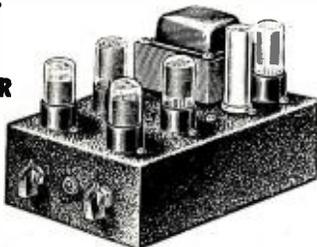

One of the finest high-fidelity audio amplifiers ever designed for home construction—a perfect companion for tuner above, or for use with crystal phone pickup. Inverse feedback for wide response  $\pm 1.5$  db from 20 to 10,000 cps. Minimum distortion. High imp. input; volume and tone controls; large output transformer matches any 6-8 ohm PM speaker. Complete with all quality parts, including 4 tubes plus rectifier, punched chassis (10x6 1/2 x 3"), and detailed 4-page instruction booklet. **\$2175**

**"BUILD-YOUR-OWN" DIAGRAMS**

- 38-034. 5 tube AC-DC Superhet
- 38-035. 2 tube "Ocean Hopper"
- 38-036. Crystal Set
- 38-037. Remote Phono-oscillator
- 38-038. 4 watt AC-DC Phono-Amp
- 38-039. 4-tube AC-DC TRF Set
- 38-040. 2-Meter Transceiver
- 38-041. TRF Broadcast Tuner
- 38-042. 10-watt HI-FI Amplifier
- 38-043. Electrical Timer
- 38-044. Radio Lab.
- 38-047. Ranger AC-DC Superhet

**5c  
EACH**

Clear, easy-to-follow instructions. Complete kits available from ALLIED.

**FREE! 164-PAGE ALLIED CATALOG!  
EVERYTHING IN RADIO  
AND ELECTRONICS AT  
LOWEST PRICES!**



**ALLIED RADIO**

ALLIED RADIO CORP.  
833 W. Jackson Blvd., Dept. 1-KP-7, Chicago 7, Ill.

- Send FREE 164-Page Catalog
- Send Kit No. 83-221
- Send Kit No. 83-222
- Send Diagrams Nos. }

Name.....  
Address.....  
City.....Zone.....State.....




**CIRCUIT PAGE**

(FOR PARTS LISTS SEE PAGE 98)


RADIO NEWS, OCTOBER, 1947

MAJESTIC MODELS 5A445, 5A445R

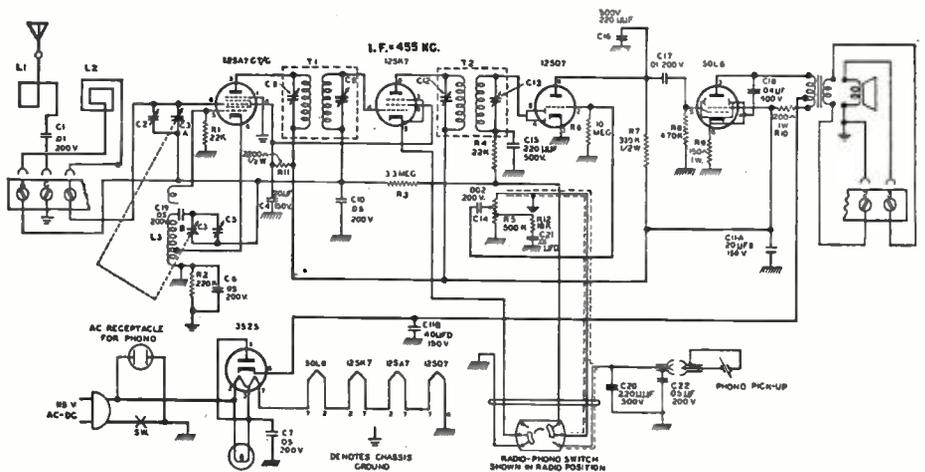


RADIO NEWS, OCTOBER, 1947

TRUETONE MODEL D2630

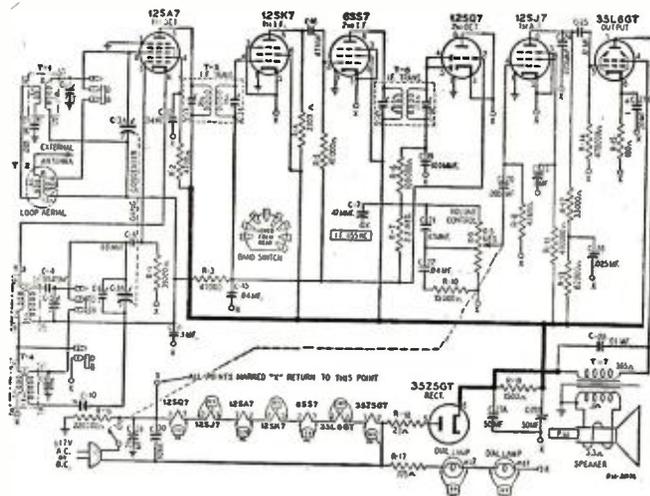

RADIO NEWS, OCTOBER, 1947


STEWART-WARNER MODELS 9002-A, B, P, R

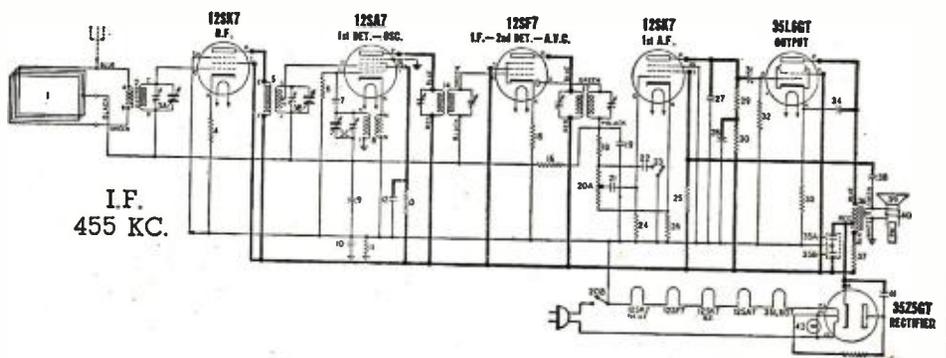

Here, and on following pages, are circuit diagrams and parts lists of many new postwar radio receivers. Radio News will bring to you other circuits as quickly as possible after we receive them from manufacturers.


RADIO NEWS, OCTOBER, 1947

GRANTLINE MODEL 510

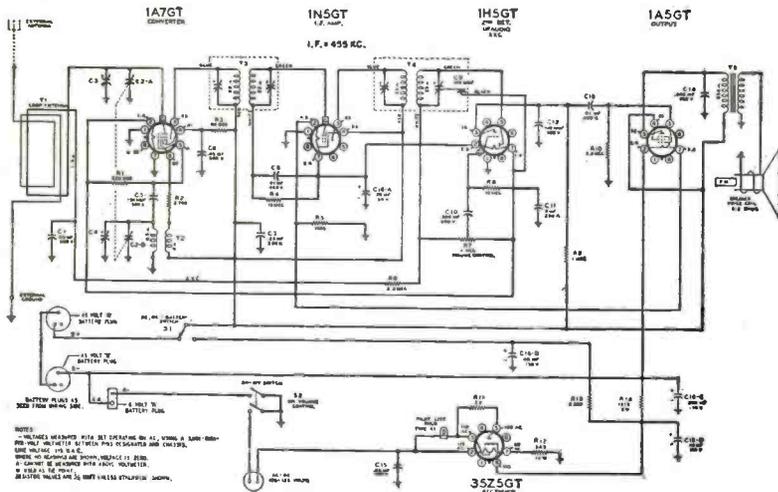


RADIO NEWS, OCTOBER, 1947

RCA MODEL 56X5

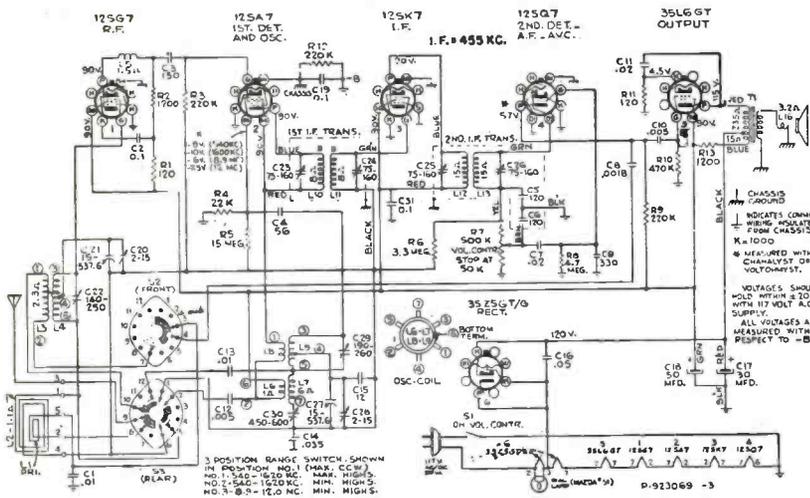


RADIO NEWS, OCTOBER, 1947

GENERAL ELECTRIC MODELS 110, 111

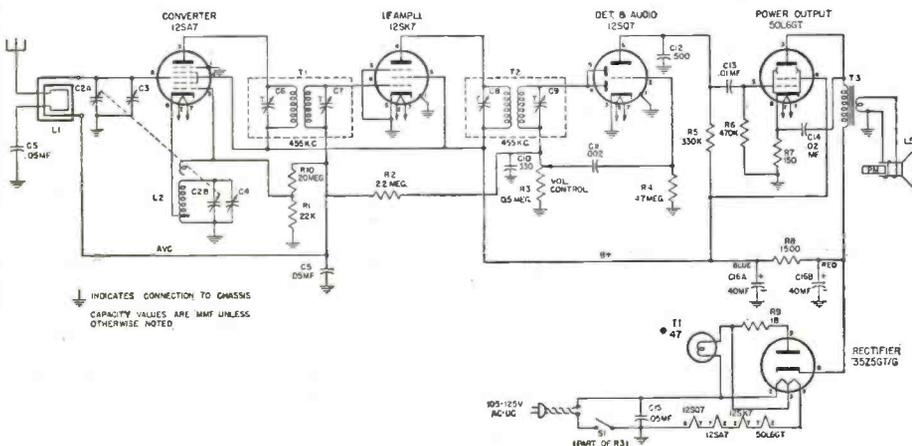
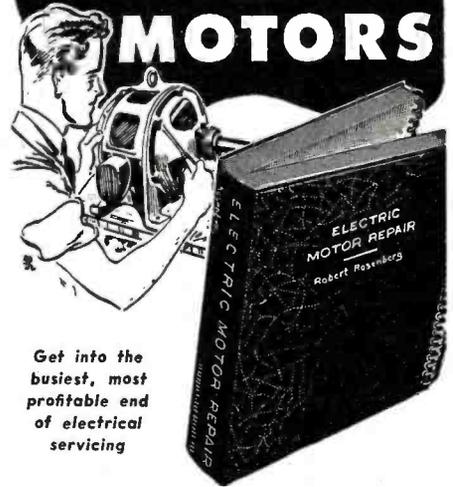
# Learn to Service and Repair all Kinds of ELECTRIC MOTORS



Get into the busiest, most profitable end of electrical servicing

## A "NATURAL" FOR ALERT RADIO MEN!

With only a little radio experience, it should be a cinch for you to qualify as a motor repair expert! **ELECTRIC MOTOR REPAIR**—the big 570-page course by the publishers of famous Ghirardi Radio-Electronic Books—can train you rapidly, at home, in spare time for only \$5 complete! It's written clearly and simply so that it can be easily understood by beginners. Every step is explained in text as well as VISUALLY by more than 900 step-by-step illustrations. It tells you exactly what to do—exactly how to do it. Best of all, it covers practically every type of motor in common use. These include both a-c and d-c motors, synchronous motors and generators AND mechanical and electrical motor control systems.

### There's Real Business Here!

The average small home has 11 motors. Big homes have many more—in phonographs, recorders, oil burners, refrigerators, fans, clocks, mixers, washers, cleaners, etc. Millions more in office and industrial equipment. Be the well-paid expert who can repair them! Now, for the first time in vocational history, you can train for this profitable work quickly at home!

### SPECIALIZE IN SOMETHING DIFFERENT

The real "cream" of the electrical service business is in motor repair. Most home appliances and industrial machines are motor driven. Good motor repair men are scarce—and are paid accordingly. It's a real opportunity—and **ELECTRIC MOTOR REPAIR** helps you cash in on every phase of it from minor repairs to complete armature rewinding.

### TRY IT FOR 5 FULL DAYS

Practice from **ELECTRIC MOTOR REPAIR** for 5 full days. Repair motors for yourself or friends. Earn while you learn! Then, if not more than satisfied this is the book for you, return it and your money will be refunded at once. You can't lose! Send coupon NOW!

## YOU CAN'T LOSE ON THIS OFFER

Dept. RN-107, Murray Hill Books, Inc., 232 Madison Ave., New York 16, N. Y.

Send me a copy of "ELECTRIC MOTOR REPAIR" for which I enclose \$5 (\$5.50 foreign); or I send C.O.D. for this amount and I will pay postman \$5 plus postal charge when he delivers it to me. If this book is not what I need, I'll return it within 5 days and you guarantee to refund my \$5.

Name .....

Address .....

City & Zone ..... State .....

# Don't Delay...ORDER TODAY!

## BC-645 TRANSMITTER-RECEIVER

BRAND NEW . . . 15 tubes interrogator-transmitter designed for airborne use, 435 to 500MC frequency range, 5 tube tuned line transmitter with 30 Watts peak-impulse power output on either two channels. With some modifications the set can be used for 2-way communication, voice or code, on the following bands: ham band: 420-450mc; fixed and mobile: 450-460mc; citizens radio band: 460-470mc; television experimental: 470-500mc; complete with all tubes, including WE Doorknob tube. Size 10½"x13¼"x4¾".

**\$14.95**

Net wt. only 25 lbs. Your cost . . . . . only  
**TWO FOR ONLY . . . . \$27.00**  
 DYNAMOTOR FOR ABOVE Model PE-101-C . . . . . \$3.95

## SPRAGUE PULSE FORMING NETWORKS

Used in small radar modulators, available in 3 sizes, 67 ohms impedance, 7.5 Kilowatt rating.

H-603, one micro second, 200 pulses per second . . . . . **\$1.95**  
 H-601, 3 micro seconds, 200 pulses per second . . . . . **\$2.95**  
 H-602, 16 micro seconds, 60 pulses per second . . . . . **\$3.95**  
**ALL THREE ABOVE FOR ONLY . . . . \$7.50**



## ANTENNA RELAY UNIT BC-442

With antenna current meter, antenna transfer relay with 3 stand-off lead-in terminals. A-1 condition. Only . . . . . **95c**

## TRANSFORMER

High voltage scope transformer, 90V 60 cps. primary; 6400 V secondary; 4 stand-off terminals . . . . . each **\$2.95**

## ANTENNA TRANSFER SWITCH SW-225

Triple-pole, double-throw, mounted on bakelite base with nine 2" porcelain stand-off mounts, BRAND NEW . . . . . **59c**

## BC 732 CONTROL BOX

With 6 position, selective switch, volume control and toggle switch. . . . . each **59c**

## COAXIAL CABLE

26 ft. of Coaxial Cable RGU8, 52 ohm. . . . . **89c**

## OUTPUT TRANSFORMERS

50L6 . . . . . 39c      6V6 . . . . . 39c

## FILTER CHOKES

### All Fully Enclosed

3:7 H. @ 145 MA. DC., 125 ohms DC. Res. **59c**

4 MTG. Studs. each . . . . . **59c**

100 mil 10H . . . . . **59c**

## I-70-D TUNING METER

Milliammeter for indicating resonance of tuned station, NEW . . . . . **49c**

## 400 CYCLE AUTOSYN MOTOR

Ideal for indicating direction of antenna systems—BRAND NEW . . . . . **95c**

## HEADPHONES

Signal Corps, 8000 ohms and 200 ohms, each . . . . . used **79c**

## RADIO PARTS

100 Resistors ¼ to 1 watt . . . . . **95c**

100 Tubular bypass condensers, assorted. 01 to .1, all 600 Volt . . . . . **\$4.69**

Electrolytic condensers 50-30, 150 Volt . . . . . ea. **29c**

½ Meg. Volume Controls 2" shaft with switch 10 for . . . . . **\$3.00**

½ Meg. Volume Controls 2" shaft without switch. 10 for . . . . . **\$1.95**

Crystal Pick-up, new light wt. . . . . ea. **\$1.79**

## BATTERY FOR "GE" PORTABLES

2-volt Willard type 27/2 the exact replacement in Pre-War Model LB 530 "GE" Portable Radios. Plastic case, size 3½"x3½"x5½" high. Shipped dry. Uses standard battery electrolyte. List value \$8.75.

BRAND NEW! Your Cost . . . . . **\$1.95**

## McELROY RADIO TELEGRAPH SIGNAL RECORDER MODEL RR2-900-42

Complete with three tubes: one—117Z6-GT; two—117P7-GT; like brand new, complete with beautiful maple finish wooden case. Each only . . . . . **\$5.95**



## NEW BC 223 AX TRANSMITTER

801 Oscillator and 801 Power Amplifiers, 2—46 modulators and 1—46 speech amplifier; 4 Xtal Frequencies and Master Oscillator on selector switch. 10 to 30 watts output. Tone voice or C.W. Mod. Ideal for 80 meter band. Black wrinkle case. Tubes included, packed in original cases, less crystals, only . . . . . **\$14.95**  
 Shipping wt. 125 lbs.

## ARC4 TRANSMITTER and RECEIVER

For operation VHF frequencies in range of 140-144 mc. Four channel crystal controlled, manufactured by Western Electric—12 or 24 V. operation. Complete with crystal and dynamotor. Used. Good condition. . . . . **\$24.95**

## WESTON MODEL 301

0-10 amps., DC. . . . . ea. **\$2.95**

## INTERPHONE AMPLIFIER

Comes in an aluminum cabinet 9¾"x4¾"x5½" DC output at 60MA, less tubes. Yours for only . . . . . **95c**

## LP-21 ADF LOOP


Low impedance loop, good for direction finder one Selsyn motor, one Selsyn transmitter, freq. range of loop 100 Kc to 1750 Kc. BRAND NEW in original cartons, each . . . . . **\$6.95**

## PE-117 UNIVERSAL POWER SUPPLY

6 or 12 volt input; output 145 volts and 90 volts; less vibrator, voltage regulator and rectifier tube; ideal mobile power supply unit; excellent condition, each . . . . . **\$4.95**

## MONTHLY SPECIAL!

### AM-61 Indicator Amplifier

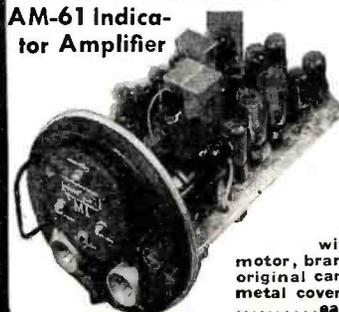

15 tubes including two VR105; 6L7GT; 6SN7GT; with blower motor, brand new in original carton, with metal cover . . . . . ea. **\$9.95**

## SELSYN INDICATORS

For use with beam rotators for indication of direction of beam. Operate from 15-24V. 60-cycle AC supply. Complete with Selsyn Transmitter and wiring instructions.



Large model, 5 inch diameter, only . . . . . **\$2.95**

Small model, 3 inch diameter, only . . . . . **\$2.45**



## TUBES

12BE6  
 6V6 6SQ7  
 6X5 12A6  
 6AG7 50B5  
 35W4 6SJ7  
 12AT6 12SL7GT  
 1S5 12J5  
 1R5 35Z5  
 50L6 6SS7  
 6AT6 12K8

**49¢**

## Transmitting MICA CONDENSERS

.0008 at 5000 VDC . . . . . 24c      .00005 at 3000 VDC. 19c  
 Assorted—100 mica condensers . . . . . **\$1.19**

## OIL-FILLED CONDENSERS

.25 MFD at 1500 VDC . . . . . 59c  
 .25 MFD at 15,000 VDC. . . . . \$6.95  
 1 MFD at 1000 VDC . . . . . 59c  
 .1 MFD at 3000 VDC . . . . . 59c  
 4 MFD at 600 VDC . . . . . 29c  
 4 MFD at 220 VAC . . . . . 29c  
 2 MFD at 600 VDC . . . . . 19c

## T-17B HAND MIKE

BRAND NEW perfect carbon hand mikes, light wt., 200 ohms, single button, press to talk switch, 5 ft. rubber cord, plug, dust cover. ONLY . . . . . **69c**

## WAVE METERS

Freq. range: 22 to 30 meg. . . . . \$24.95  
 Freq. range: 37 to 53 meg. . . . . 24.95  
 Freq. range: 155 to 230 meg. . . . . 24.95  
 AC operated, complete with carrying case and magic eye for tuning indicator, veneer tuning dial.

## CRYSTALS

10 crystals from 2 meg. to 8 meg. . . . . \$2.95

Power Converter Unit PE-104A for BC-654, each only . . . . . **\$4.95**


# ARROW SALES, INC.

59 WEST HUBBARD STREET • CHICAGO 10, ILLINOIS

Telephone: SUPERIOR 5575

# "ARROW" Will Not Be Undersold!


## BC-612

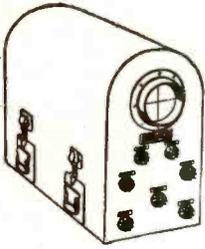

Modified BC-412, 5' Radar Oscilloscope; ideal for first class laboratory instruments; 110V 60 cycles, complete with tubes and power supply brand new in original cartons.

Each... \$49.95

## ARMY AIRCRAFT RECEIVER Model BC-946-B

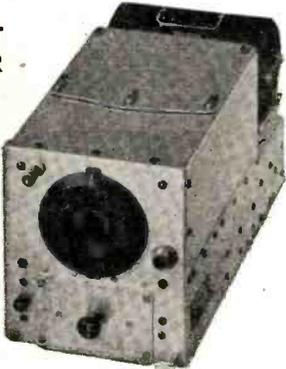

Broadcast band from 520 to 1500 kc. Tube complement: 3—12SK7, 1—12SR7, 1—12A6, 1—12K8. Designed for dynamotor operation, but is easily converted to 110 or 32 volt operation. Has two I.F. stages and three gang condenser. Comes packed in sealed carton complete with tubes and instruction manual, but less dynamotor. \$12.95

## RADIO RECEIVERS

BC-453-A; 190-550 kc, complete with tubes; BRAND NEW IN ORIGINAL CARTONS \$7.95 used... \$4.95  
 BC-454-A; 3-6 mc; complete with tubes; BRAND NEW IN ORIGINAL CARTONS \$5.95 used... 3.95  
 BC-455-A; 6-9 mc, complete with tubes; BRAND NEW IN ORIGINAL CARTONS \$5.95 used... 3.95  
 1.5 to 3 Meg... \$4.95  
 Used, in A-1 condition. Complete with 6 tubes.

## TRANSMITTERS (274N Series)

All Brand New in Original Cartons Complete with Tubes and Crystal

BC-696—3-4 Mc... \$7.95  
 BC-457—4-5.3 Mc... 5.95  
 BC-458—5-3-7 Mc... 5.95  
 BC-459—7-9.1 Mc... 5.95

## DYNAMOTOR

DM 32A. Each 95c, 3 for... \$2.00

## MODULATOR UNIT

BC-456-A... \$2.95

## REMOTE CONTROL BOX

BC-450-A... \$1.95

## ARB AIRCRAFT RADIO RECEIVER

The ARB is a six tube, four band, superheterodyne Aircraft Radio Receiver with built-in dynamotor, designed for the reception of MCW (tone or voice) or CW within the frequency range 195 Kc to 9.05 megacycles. \$16.95

## ART-13 TRANSMITTER

Used, in good condition, complete with tubes and calibrating crystal, freq. range 2,000 Kc to 18 mc; A-1, A-2, A-3 type trans. mission; power output 100 watts Each... \$67.95

## BC-929-A

Contains power supply 110 V, 400 cycles, has 7 tubes such as 3CP1, brand new, complete with tubes. Each... \$17.95 Used, ea. 14.95



## APS-15

Has 45 tubes, one 5' scope tube, one 2' scope tube, has 3 meters, 4 power supply units 110V 400 cycles, complete with tubes. Each... \$3950

## BC-348 RECEIVER

BC-348 RECEIVER. Used as is, only 40 in stock, first come—first served... ea. \$24.95

## VHF RECEIVER BC-701

Frequency range 170-180 Mc; IF 30.5 Mc; complete with 11 tubes; self-contained power supply, brand new in beautiful wooden carrying case... \$9.95

## RAX-1 3-RECEIVER COMBINATION

No. 1—4 bands, tunes from 200-1500 kc. ea. \$15.00  
 No. 2—4 bands, tunes from 1500 kc to 9 mc. ea. 15-00  
 No. 3—5 bands, tunes from 7 to 27 mc... ea. 19.95  
 Each receiver complete with tubes and 24 V Dynamotor. Used, A-1 condition. 3 Receiver combination. Complete... \$34.95

## NAVY GLIDE PATH RECEIVER

Bolt type, complete with 3 6C6 tubes and tunes from 90 to 95 Mc, operates from 12 or 24V. Brand new \$2.95

## RANGER MODEL 114-C AIRCRAFT RECEIVER

Combination Interphone, Amplifier and 6-Tube Superheterodyne Receiver designed to operate directly from a 24V aircraft battery. Tuning range 200 kc to 550 kc. complete with mounting rack, jackbox and cords. This unit is used as range receiver and interphone amplifier. Brand new... \$9.95

## GF12 and RU 17 NAVY RECEIVER and TRANSMITTER

Complete with receiving and transmitting coils, junction box, control boxes, plugs, power supply, instruction manual and spare parts which include tubes. Brand new in original carton. A real buy... \$24.95

## GO-9

Navy type low and high frequency transmitter with power supply and tubes. Operates from 200 Kc to 18,100 Kc; requires 115V, 800 cycles. Used, complete with tubes... \$39.50

## HAND-TYPE MICROPHONE RS-38

Carbon type, with PL-68 plug, brand new... \$1.95 Used... 1.00

## MICROPHONE AND RECEIVER P-60

Dynamic type, 50-ohm impedance; mike and phones interminate in 5-wire male plugs, 3-ft. cord... \$1.49

## OXYGEN MASK MICROPHONE T44C

Used with SCR-522, magnetic type complete with JK-26 and PL-179. Used, A-1 condition... 95c

Wholesalers, dealers, institutions and other quantity purchasers... Write, Wire, Phone for Quantity Prices. All Shipments F.O.B. Chicago—20% Deposit Required on all orders. Minimum order accepted \$5.00.

WRITE FOR OUR COMPLETE CATALOG

DEPT. C

## RCA AVT-112A Aircraft Transmitter

For radio-telephone communication; for 6, 12 or 24 volt source freq. range from 2,500 to 6,500 Kc. Small in size and wt. (wt. 6 lbs.). Complete with 6 tubes, oscillator circuit, power amplifier modulators, dual tuning indicator and amplifier, with instruction manual, less crystal... BRAND NEW IN ORIGINAL CARTONS—ONLY... \$12.95 each



## COMPANION (RECEIVER) FOR ABOVE RCA AVR 20. BRAND NEW \$12.95 ea. POWER SUPPLY

For the APN-4; complete with 16 tubes; 110 V 400 cycles; brand new... \$10.95 used... \$7.95

## AN18/APT-10

Pre-amplifier model K-1, designed to raise output level of magnetic type microphone, complete with 2 tubes 6SL7GT and 28D7 and hand switch, brand new in original cartons. Each \$1.95, 3 for \$5.00

## SETCHELL CARLSON RADIO RECEIVER BC-1206-C

Designed to receive A-N beam signals. 24-28 vdc 21.6 watts. Tube complement: 14H7 or 14A7, RF amplifier; 14H7 or 14J7, mixer; 14A7 or 14H7, IF amplifier; 14R7, detector and 1st audio amplifier; 28D7, output amplifier. 195 to 420 kc. 4" high x 4" wide x 6 1/2" long—wt. 3 lbs., 4 oz. Used A-1 cond... \$4.95 BRAND NEW in original carton... 6.95

## RADIO TRANSMITTER and RECEIVER APS-13

Light weight air-borne radar system, radio transmitter and receiver APS-13; tube complement: 5—6J6, 9—6AG5, 1—VR105, 2—D21; unit is brand new, complete with tubes, the tubes alone are worth more than this LOW PRICE OF \$10.95 ONLY

## GLIDE PATH RECEIVER R-89/ARN-5

Glide Path Receiver used in the Instrument Landing System covering the frequency range 332 to 335 mc; complete with the following tubes: 7—6AJ5, 1—12SR7, 2—12SN7, 1—28D7, and including three crystals 6497KC, 6522KC, 6547KC units are in A-1 condition for \$8.45 ONLY

## BC-733 D LOCALIZER RECEIVER. NOW ONLY \$8.50

## SCR-522 TRANSMITTER and RECEIVER

The standard very-high frequency airborne receiver transmitter. 100 to 156 megacycles. 4 channels selected from remote control box. Used, as is—"Complete with Tubes" \$14.95 ONLY Excellent Condition \$19.95

## BC-625

VHF transmitter, frequency range 100-156 Mc; four channels. Part of the SCR-522. Complete with tubes less crystals. Used, good condition... ea. \$9.95

## BC-624

VHF Companion receiver for above transmitter. Complete with tubes less crystals. Used, good condition. Diagram with either unit included... ea. \$8.95

## VEEDER-ROOT METER AND CASE

Counts up to 1000. Each... 95c

## WESTON OUTPUT METER No. 687

3 scales 0-50. A-1 Condition ONLY... \$6.95

**ARROW SALES, INC.**  
 59 WEST HUBBARD STREET • CHICAGO 10, ILLINOIS  
 Telephone: SUPERIOR 5575

## WAR SURPLUS


### BRAND NEW COMPONENTS FROM FORMERLY SECRET SPERRY "AUTO PILOT"

AMPLIFIER  
RACK  
WITH RELAYS  
AND METERS  
GOVERNMENT  
PAID  
\$100.00



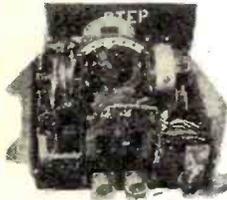**YOU PAY ONLY \$695**

Originally housed amplifiers and other instruments. Consists of magnesium cabinet that mounts 7 DPDT Allied Relays, 1 SPST Relay, a Weston O-125 AC Volt Meter, a 350 to 450-cycle Frequency Meter, a 115-volt, 400-cyc. Transformer and many other parts. This unit is of special interest to "hams!" The cabinet would be excellent for small transmitters or receivers. 12½x14x10"; 22 lbs.



VERTICAL  
**GYRO  
UNIT**  
DESIGNED  
FOR

B-29 Superfort  
ARMY PAID \$2855.00

**YOU PAY ONLY \$1495**

Less than ½¢ on the dollar!

Aluminum casing, housing one 400-cyc., 115-v., 3-ph. motor propelled Gyroscope; two 24-v. DC shunt-wound Motors; 2 Electronic Relays, Auto-Transformer; and hundreds of other parts. A masterpiece of precision. 15x14x9"; 35 lbs.

### DYNAMOTORS

9 or 18-volt in; 450-volt out. A simple change converts this unit to run on 110 volts AC. Used on ABK Receivers. Many brand new. Others never used but dismantled from ABK sets. \$3.95 for new ones; \$3.50 for dismantled. Gov't cost \$34.00 each. Made by Pioneer and Win-charger Co. 8 x 4 x 4"; 7 lbs.

You pay shipping costs.  
Send check or money order to

**SURPLEX RETAIL SALES INC.**

Dept. RN-10  
2409 S. LaSalle St.  
CHICAGO 16, ILL.

CHICAGO BUYERS, ATTENTION:  
PHONE CALUMET 9130

## What's New in Radio

### SPRAGUE "TELOHMIKE"

Designed to facilitate the checking of condensers and resistors, the new deluxe "Telohmike" Model TO-3 just introduced by *Sprague Products Company* of North Adams, Massachusetts, has several new features not found in previous models of this unit.

A "Speedy Check" feature enables



the operator to locate open, intermittent, or shorted condensers without removing them from the circuit. The "Telohmike" is a bridge-type capacitance and resistance analyzer with built-in d.c. volt-milliammeter. A direct reading calibrated dial is color coded to correspond with the selector switch. Capacity ranges are from .00001 µfd. to 2000 µfd. in four steps. Resistance ranges are from 2.5 ohms to 25 megohms in three steps. The d.c. meter range is 0-15, 150, 750 volts and 1.5, 15, and 75 ma. The insulation resistance range indicated by direct meter reading is 0-2500 megohms.

Full details will be furnished upon request to *Sprague Products Company*, North Adams, Massachusetts.

### NEW MINIATURE TUBES

*Radio Corporation of America* has recently supplemented its miniature tube line by adding three new types, the 1U5, the 6BJ6 and the 12AL5.

The 1U5 is a diode-pentode for use in portable receivers. It is similar to the 1S5 but has a different basing arrangement and utilizes an improved structure which greatly reduces any tendency toward microphonic effects.

The 6BJ6 is a remote-cutoff amplifier pentode particularly useful in mobile equipment where heater-current drain is an important consideration and in a.c.-d.c. AM and FM receivers. It features a 6.3 volt, 150 ma. heater, high transconductance, and low grid-plate capacitance.

The 12AL5 is a high-perveance twin diode like the 6AL5, but has a 12.6 volt, 150 ma. heater and is intended especially for use as a ratio detector in a.c.-d.c. FM receivers. In circuits utilizing wide-band amplifiers the low internal resistance of the 12AL5 makes it possible to obtain increased signal voltage from a low-resistance diode load.

Technical bulletins covering each of these types are available from the Tube Department, *Radio Corporation of America*, Harrison, New Jersey.

### DIAMOND NEEDLE

*Electrovox Co., Inc.* has introduced a new and popularly-priced diamond tipped phonograph needle to the trade.

Marketed under the tradename "Walco Diamond," this new unit will provide lifetime service under normal operating conditions, according to the manufacturer. The needle is composed of an aluminum alloy metal, bent and shaped to produce maximum frequency response with lowest surface noise.


Complete data on packaging, discounts, etc. will be supplied by the manufacturer, *Electrovox Co., Inc.*, 31 Fulton St., Newark 2, New Jersey, upon request.

### PORTABLE KIT

*Radio Kits Company* of New York has added a new unit to their line of ready-to-build radio kits.

The Model 210 is a portable receiver with three-way operation from a.c., d.c., or batteries. The power switch is located on the front of the set so that the type of operation may be selected without opening the case. A five-inch Alnico V permanent magnet dynamic speaker is included in the kit. The case is covered with a weather-tested aircraft material.

Details of this kit or others in the

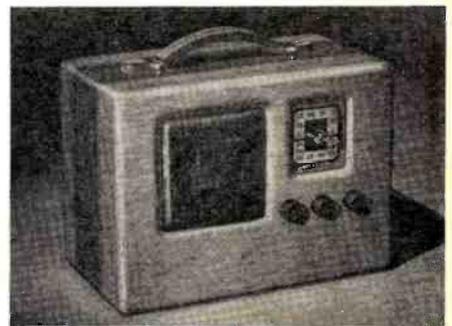

company's line will be provided upon request to *Radio Kits Company*, 120 Cedar Street, New York 6, New York.

### "FILMGRAPH" MODEL HK


Capable of recording over two million words, the new "Filmgraph" Model HK permanent recorder and instantaneous reproducer has been designed to provide automatic continuous recordings of two-way telephone conversations, hearings, conferences, interviews, reports, and dictation.

This newest unit developed by *Miles Reproducer Co., Inc.*, utilizes a single reel of 16 mm. safety film to provide 300 hours of permanent recording. 5000 feet of M2 film on which 100

**RADIO NEWS**
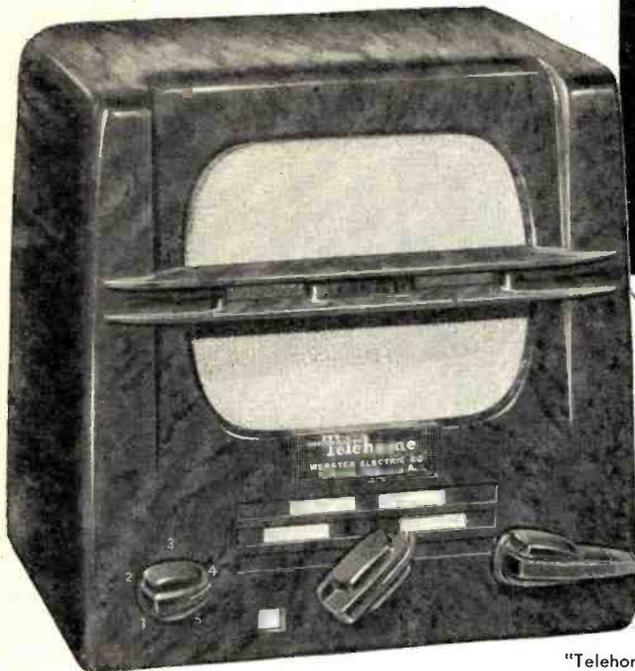
# We Tap a New Market!

... With a New Intercommunication System for the HOME



"Telehome" Master Station



BY THE MAKERS OF  
**Teletalk**

## The New Telehome Models for Living Room or Kitchen . . . Special Speaker for the Door

• Intercommunication Systems invade the home with the same high quality units that are available for commercial use.

This opens up the opportunity to sell to retail outlets and the widespread consumer market.

Designed and built specially for home use, it will be sold as a package consisting of a master unit and one speaker unit and one hundred feet of wire at a moderate price within range of everyone.

The new "Telehome" is available as a complete line, with additional speaker units available for those who want them. In addition, a special door speaker can be had separately. A Master wall-type station is provided for new home builders and is constructed as a built-in for modern kitchen cabinets or kitchen wall.

Complete promotion material is available to back up their sale with advertising in the Saturday Evening Post to tell the story to millions of consumers.

If you haven't already had the complete story, write to Webster Electric, Racine, Wisconsin for complete details.

*Licensed under U. S. Patents of Western Electric Company, Incorporated, and American Telephone and Telegraph Company.*

**WEBSTER ELECTRIC**  
RACINE WISCONSIN



Established 1909

Export Dept. 13 E. 40th Street, New York (16), N. Y. Cable Address "ARLAB" New York City

"Where Quality is a Responsibility and Fair Dealing an Obligation"

Master Station, Speaker unit and 100 feet of wire . . . complete in one package . . . \$49.50  
Extra speaker unit . . . 9.50  
Door speaker . . . 7.75  
*Prices slightly higher west of Rockies*

As  
Advertised  
in  
Saturday  
Evening  
Post

New... Instant, low-cost  
**INTERCOMMUNICATION**  
made expressly  
for home use!

By the makers of  
**Teletalk**

"Telehome" permits two-way conversation between any two or more rooms . . . or with callers at your outside doors

Saves countless time and steps . . . provides added protection and convenience

"Telehome" - the new home intercommunication system - brings you and your family within speaking distance of each other . . . if you wish, into your answer line outside door without opening it . . . gives instant and kitchen or bathroom or garage or nursery . . . By adding extra speaker units, your control master station can carry on two-way conversations with as many as three other rooms of front and rear outside doors. Think of the time and steps "Telehome" will save in your home - no more needless running up and down stairs or between distant rooms!

With all its advantages of instant, unimpeded protection, "Telehome" costs but little more than a regular telephone. It is handsome, dependable, practical and easy to install. It is a precision quality product of Webster Electric, makers of "Teletalk," the most widely used commercial intercommunication system.

Send for attractive picture booklet  
Write for the story of how "Telehome" works. A new window opens to your home. "Teletalk," "Telehome" and its many friends.

WEBSTER ELECTRIC COMPANY, Racine, Wisconsin . . . Published 1909  
Export Dept. 13 E. 40th Street, New York (16), N. Y. Cable Address "ARLAB" New York City  
"Where Quality is a Responsibility and Fair Dealing an Obligation"

**WEBSTER ELECTRIC**

Intercommunication Systems • Special Phonograph Extension • Press Time Answer and Drive Carriage for Radiogram • Fast Keys for all Distribution to Control all Services and Features for all Home Appliances • The complete line of appliances with an 800-odd items.

# ENGINEERED FOR EFFICIENT FM AND TELEVISION RECEPTION

Magic Wand Aerials for FM and television offer electrical efficiency possible only through the enthusiastic teamwork of Ward's top-drawer experimental laboratory, and production facilities.

As the world's largest producer of aerials for car and home, Ward also is pioneering in educating 33 million present, and prospective, FM and television receiver owners that a good outdoor dipole antenna is necessary if quality reception is to be enjoyed. Watch for our hard-hitting ads in the Saturday Evening Post and leading newspapers.

In addition to developing outstanding FM, television and automotive aerials, Ward also has design and production capacity available to take care of special aerial needs. Submit your aerial problems to us now for an efficient, and economical, solution.




## WARD Magic Wand FM AND TELEVISION AERIALS

THE WARD PRODUCTS CORP.  
1523 E. 45th Street, Cleveland 3, O.  
Division of The Gabriel Company  
EXPORT DEPT.: C. W. Brondes, Mgr.,  
4900 Euclid Ave., Cleveland 3, O.  
IN CANADA: Atlas Radio Corp.,  
560 King St., W., Toronto, Ont.

WORLD'S LARGEST MAKER OF AERIALS FOR CAR AND HOME

## CUT HOLES FAST IN RADIO CHASSIS

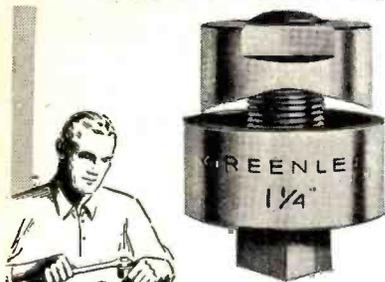

### WITH A GREENLEE RADIO CHASSIS PUNCH

• GREENLEE Punches make this tough job easy. Merely turn with an ordinary wrench . . . make accurate, clean holes in a hurry. No reaming or tedious filing. There's a GREENLEE punch for each of these sizes: 1/2"; 3/8"; 5/16"; 7/16"; 1"; 1 1/8"; 1 1/2"; 1 3/8"; 1 1/4"; 1 3/8"; 1 1/2"; 2 1/4" — for cutting holes to take sockets, plugs, etc. Also GREENLEE makes Knockout Punches and Cutters for conduit and meter holes up to 3 1/2". Write for facts. Greenlee Tool Co., 1890 Columbia Avenue, Rockford, Illinois.

TOOLS FOR CRAFTSMEN

# GREENLEE



## GOV'T SURPLUS

### TUBES

6V6—Metal.....	\$ .89
5Y3 GT.....	.45
No. 80.....	.45
.01-150V Paper.....	60 for 1.00
02—1600V Paper.....	10 for 1.00
.1—600V Paper.....	10 for 1.00
Chokes, Thordorson 12H-80 Ma DC-250 ohm.....	1.09
Resistor Kit—1/2 & 1 W assorted.....	2.00
Condenser Kit—.01—.00001—100.....	3.00
Bathtubs—3X .1, .5, 1 etc. 400V & 600V.....	10 for .89
Rect. Selenium, G.E. 28V, 300M.....	.50

### OIL-FILLED CONDENSERS

—G.E., C.D., ETC.		TRANSMITTING MICA CONDENSERS	
10 600 V	\$ .80	.002 600 V	\$ .08
8 600 V	.70	.002 2500 V	.27
8 1000 V	1.75	.003 2500 V	.33
6 2000 V	2.95	.001 2500 V	.18
4 600 V	.50	.004 2500 V	.36
4 1000 V	1.00	.00005 2500 V	.11
2 1000 V	.60	.005 600 V	.08
.05 1000 V	.15	.0005 2500 V	.15
1 2500 V	.95	.002 3000 V	.66
1 7500 V	3.25	.00005 5000 V	.95
.5 1000 V	.20	.00025 5000 V	.95
.5 2000 V	.40	.00072 5000 V	.95
1 600 V	.20	.0008 5000 V	.95
1 1000 V	.45	.0015 5000 V	.95
2 600 V	.35	KIT of 12	3.98
3 x .2 4000 V	3.95		
3 x 10 90 V AC1.40	.12	1500 V	6.95
10 x .25 600 V	.20	4000 V	2.75
75 2000 V	.55	6000 V	4.00

\$2.00 min. order F.O.B., N. Y. C. Add postage.  
50% deposit, balance C.O.D. with all orders.  
Manufacturers inquiries invited.

## TECHNICAL RADIO PARTS CO.

265 Greenwich St., Dept. C-4, N. Y. 7, N. Y.


sound tracks may be cut across the width of the film, provide 3 hours continuous recording per track. Selection of recording for playback is facilitated by "Track" and "Zone" indicators.

Complete performance details will be forwarded by Miles Reproducer Co., Inc., 812-814 Broadway, New York 3, New York.
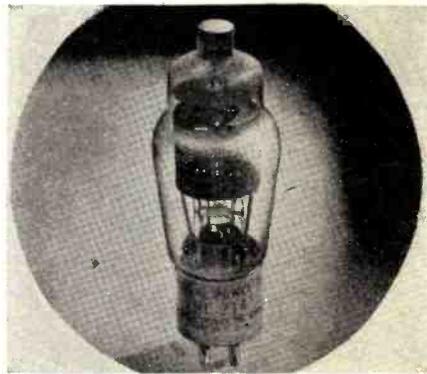
### NEW THYRATRON

A quick heating thyatron, the NL-714, has been announced by National Electronics, Inc., of Geneva, Illinois.

This industrial tube is interchangeable with the 5557/FG-17 and attains its characteristic stability by the use



of an inert gas filling in addition to the usual mercury.

A data sheet giving full details on the performance of the NL-714 is available upon request to National Electronics, Inc., Geneva, Illinois.

### TRANSFORMER IDENTIFICATION

Merit Coil & Transformer Corporation of Chicago, has announced that its line of transformers will now carry full details on the units in the form of a permanently attached strip.

This method of packaging will replace the older technique of printing name, number, and engineering application data on the box in which the unit is housed.

A strip of self-annealing material will be attached to the top of the transformer itself with full engineering application data permanently available at all times.

Details on this new line of transformers will be furnished by Merit Coil & Transformer Corporation, 4427 N. Clark St., Chicago 40, Illinois.


### COMPOSITION RESISTORS

Ohmite Manufacturing Company of Chicago has announced that its line of "Little Devil" resistors has been expanded to including 1/2 and 1 watt sizes having a tolerance of ± 5%.

Both of these units are full 1/2 and 1 watt resistors, yet the size of the 1/2 watt unit is only 3/8" long x 9/16" diameter, while the 1 watt unit is 1/2" long x 7/32" diameter. These resistors meet all test requirements for the Joint Army-Navy Specification JAN-R11 including salt water immersion cycling and humidity tests.

(Continued on page 170)

RADIO NEWS

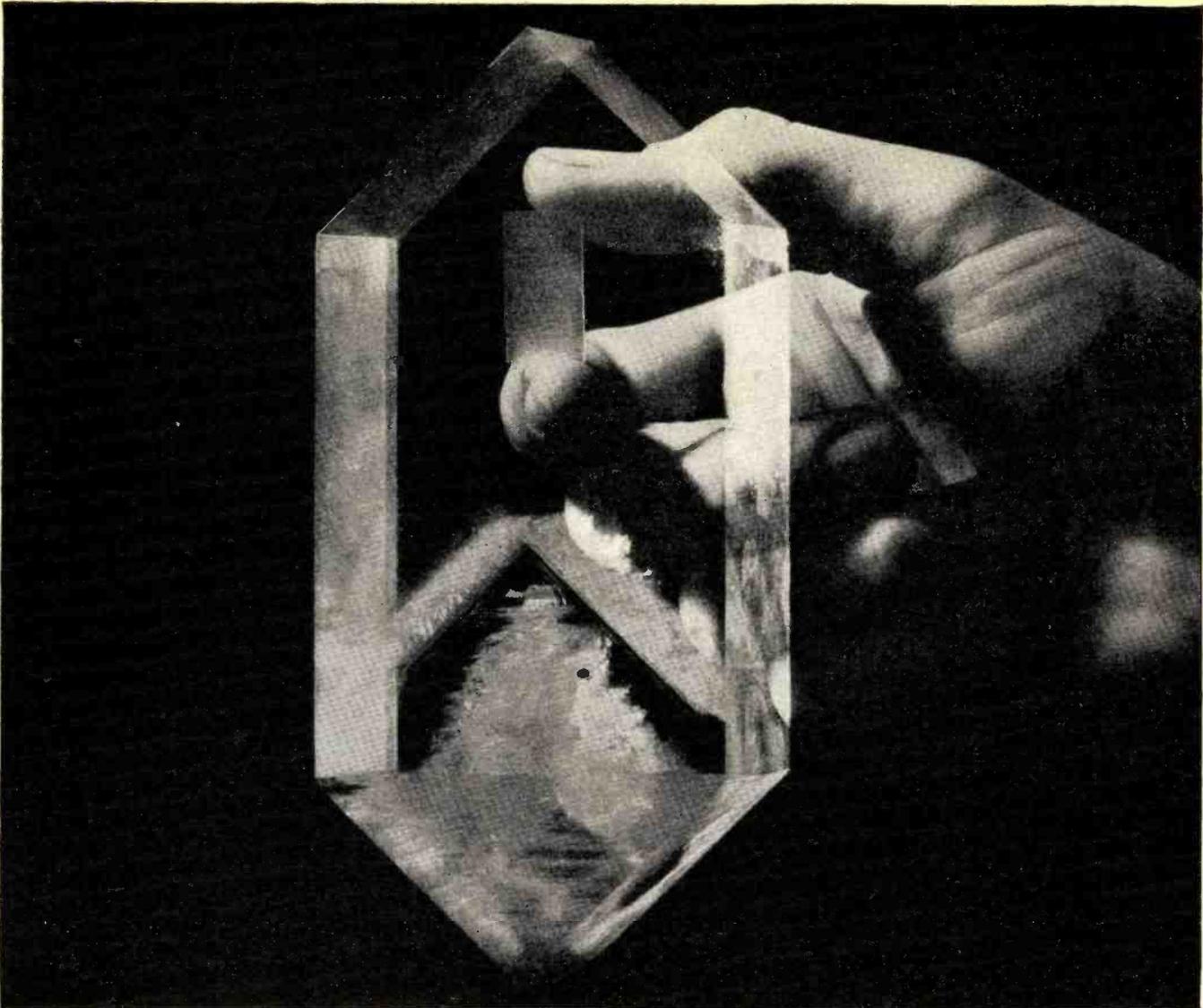

A CRYSTAL THAT GREW FROM A SEED . . . The large crystal in the foreground is an EDT (Ethylene Diamine Tartrate) crystal. It started from a seed (a piece of mother crystal) and in three months grew in a slowly cooling solution to the size shown. The small plate is cut from a large crystal, then gold-plated for electrical connection and mounted in vacuum. Cultivated EDT crystals can do the same job as quartz in separating the nearly 500 conversations carried by a coaxial circuit.

## Crystals for Conversations

AT WAR'S END, the Bell System began to build many more Long Distance coaxial circuits. Hundreds of telephone calls can be carried by each of these because of electric wave filters, which guide each conversation along its assigned frequency channel. Key to these filters was their frequency-sensitive plates of quartz.

But there was not enough suitable quartz available to build all the filters needed. Bell Telephone Laboratories scientists met the emergency with cul-

tivated crystals. Years of research enabled them to write the prescription at once—a crystal which is grown in a laboratory, and which replaces quartz in these channel filters.

Now Western Electric, manufacturing unit of the Bell System, is growing crystals by the thousands. Many more Long Distance telephone circuits, in urgent demand, can be built, because the scientists of Bell Telephone Laboratories had studied the physics and chemistry of artificial crystals.




**BELL TELEPHONE LABORATORIES**

EXPLORING AND INVENTING, DEVISING AND PERFECTING, FOR CONTINUED IMPROVEMENTS AND ECONOMIES IN TELEPHONE SERVICE  
October, 1947

# PERSONAL PORTABLE RADIO KIT ONLY \$10.95


## PERSONAL PORTABLE KIT, \$10.95

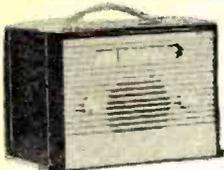

PERSONAL PORTABLE KIT MODEL K-PX. Small size leatherette covered case 8x6x7. Easy to build. Operates on self contained B and batteries. Rec. Broadcast 550 to 1600 K.C. Incorporates a standard superhet circuit with avc. Has 3 inch Alnico 5 PM speaker. Priced complete with batteries, pictorial diagram and tubes IR5, 1T4 and 354. Not AC DC, but straight battery operated. Has 2 gang cond. Everyone should have one of these personal portables. Everything furnished. Kit K-PX.....Net \$10.95

complete with batteries, pictorial diagram and tubes IR5, 1T4 and 354. Not AC DC, but straight battery operated. Has 2 gang cond. Everyone should have one of these personal portables. Everything furnished. Kit K-PX.....Net \$10.95

## 3-WAY PORTABLE KIT, \$17.95

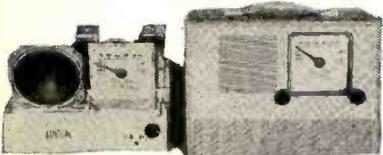

Build this powerful, 4-tube, 3-way portable kit. Operates on 110 volts AC or DC or self contained batteries. Receives broadcast 550 to 1650 K.C. Incorporates a standard superhet circuit with AVC and loop Ant. Has Alnico 5 PM Speaker, 2 gang condenser. All Parts and batteries are furnished including tubes Disc Rectifier, 1R5, 1T4, 1S5 and 354. Has attractive leatherette portable cabinet size 7x9x3. Weight 14 lbs. Kit model 3-ZA.....Net \$17.95

## RADIO-PHONO COMB. KIT, \$24.95



Build this beautiful portable combination radio phonograph. We furnish everything. Beautiful two tone portable case, latest rim drive phono motor, Astatic crystal pick-up. All parts to build high quality 5 tube AC-DC radio. Tuning broadcast 550 to 1650 K.C. has tone control, loop antenna, 6" Alnico 5 PM speaker. Tubes 12SA7, 12SK7, 12SQ7, 50L6 and 35Z5. Simple diagram furnished. Kit Model RP-12. Wt. 20 lbs. Your Cost \$24.95


## RECORD PLAYER SCOOP, \$14.95

Assemble this single record player. Only a few minutes required to mount pick up, motor and ready wired and tested amplifier. Everything furnished including tubes 12SR7, 50L6 and 35Z5. Has heavy duty Alnico V PM speaker, tone and volume controls. Has latest crystal pick up and 78 RPM phono motor. The attractive Alligator covered case is small and ruggedly constructed. (15x6 1/2 x 11). This is our leader in a portable record player. Weight 18 lbs. Kit J-20. Net.....\$14.95



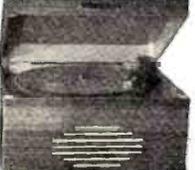
## WALNUT CABINET RECORD PLAYER \$16.95

Beautifully made, highly polished walnut cabinet with hinged lid. Plays 10" records with lid closed. Latest rim drive phono motor and high output. Astatic crystal pick-up. High power 3 tube AC-DC phono amplifier (wired and tested). Heavy duty 4" Alnico 5 PM Speaker. Single record player kit. Model WL-3. Wt. 15 lbs. Your Cost \$16.95


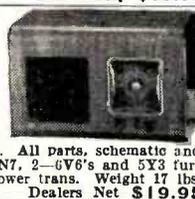
## KIT WL-3R—IN SAME CABINET AS WL-3 EXCEPT HAS 5 TUBE AC-DC RADIO AND RECORD PLAYER, \$19.95

KIT K-7A. Easily assembled into a fine working, attractive, transformer type AC broadcast receiver, 550 to 1700 K.C. Has push-pull audio, tone control and 6 1/2" Alnico 5 PM speaker. Beautifully made 14" walnut cabinet. Incorporates a standard superhet circuit, with AVC and loop antenna. All parts, schematic and tubes 6SA7, 6SK7, 6H6, 6SN7, 2-6V6's and 5Y3 furnished. Has full 90 ml. power trans. Weight 17 lbs. Dealers Net \$19.95



Deluxe AC Kit, \$14.95. Model JD5 AC. Has beautifully made 12" walnut cabinet. All parts furnished to build a powerful broadcast 5 tube AC, power transformer type, superhet. Rec. 440 to 1700 K.C. Slide rule dial, 2 gang tuning cond. Loop aerial. Heavy duty Alnico V, PM speaker. Everything furnished including photos, diagram and tubes: 6SA7, 6SD7, 6SQ7, 6K6 and rectifier. Kit JD5 AC. Net.....\$14.95

## 5-TUBE AC-DC KIT, \$9.95

Kit Model P-85. We have finally been able to achieve our goal. Here it is, a good 5-tube broadcast AC DC superhet radio receiver for less than ten dollars. The beautiful 10 inch plastic cabinet is made of the finest material. The chassis is of the standard accepted superhet design. 456 KC IFS AVC and 5 inch Alnico 5 PM speaker. Attractive venier dial. Two gang tuning condenser. Loop ant. We defy anyone to offer a better working AC DC receiver kit. Priced complete with diagram, photos and tubes 12BE6, 12BA6, 12AT6, 50B5 and 35W4. Nothing else to buy. You can't go wrong on this value. Kit Model P-85.....Net \$9.95



## NEW SUPER MIDGET KIT, \$12.95 MODEL KP-T

Build this new super Midget Broadcast Radio. Has beautifully made, highly polished walnut cabinet. Size 7 1/2 x 4 1/2 x 5 1/2. Attractive slide rule dial. Incorporates standard superhet circuit with 456 KC IFS & AVC. Has 2 gang condenser and loop ant. Every part including Alnico V, P.M. speaker and tubes. 12BE6, 12BA6, 12AT6, 50B5 & 35W4. Furnished as well as photo and easy to follow diagram. Weight 5 lbs.



## 20-WATT UTILITY AMP. KIT, \$17.95

Build this 20 watt utility 110 volt AC, 20 Watt power amplifier. Ready punched aluminum chassis, size 12 x 8 x 2 1/2 inches. Has two input circuits, one mike and one phono. Mike stage has 135 DB gain, for crystal or dynamic mike. Has bass and treble controls. Designed for use with PM speakers; has 8-16 ohm output transformer. All parts, transformers and easy-to-follow diagram furnished, including tubes: 2-6SN7, 6J5, 2-6L6GA, 5Z3. Kit Model 20-LX. Net.....\$17.95



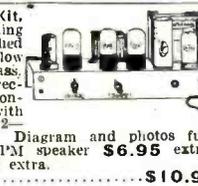
## 6-110 VOLT UTILITY AMP. KIT, \$29.95

Model 20-LX6 20 watts output. Similar in appearance to the model 20-LX except on slightly larger chassis. Has same tube line up and input circuits. Has power supply that will work on 6 Volt DC, or 110 Volts AC. Equipped with super heavy duty vibrator. Has output voltage to run a rev. AC phono motor when used as a 6 volt unit. All parts tubes and easy to follow diagram furnished. Model 20-LX6 amp. kit. Net \$29.95. Ship. weight 30 lbs. Latest 12 in. P.M. Alnico V speaker, 12 watt. Net.....\$29.95



12 WATT Amplifier Kit, \$10.95. For recording and utility use. Matched component parts assure low hum level and good bass. One control. Equipped with microphone; tone control. Priced complete with all parts and tubes: 2-6V6, 6SN7, 6SH7, 7Y4. Diagram and photos furnished. 12" Alnico V PM speaker \$6.95 extra. Crystal desk mike \$4.95 extra. Kit AC-12. Net.....\$10.95



## 9-TUBE KIT, \$24.95


AHK-11 Kit. A deluxe 9 tube, twin speaker, high fidelity receiver kit; housed in a beautiful hand rubbed walnut cabinet; of latest design with dual speaker grills in perforated gold tint plastic. Circuit employs push-pull parallel 12A6's delivering 10 watts of undistorted power to twin 6" G.E. Alnico V speakers. Other tubes: 12K8, 12SK7, 12H6, 12J5, 12SL7 and two dry disc rectifiers in voltage doubler circuit (equivalent to 11 tubes in all). Has 10" slide rule dial. Complete with instructions; ready to wire. Your Net.....\$24.95


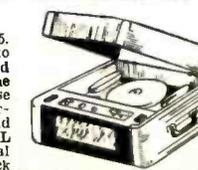
## PORTABLE RADIO RECORDER KIT


\$54.95

\$90.00 value for only \$54.95. We furnish every part to build a powerful radio and dual speed recorder. The attractive leatherette case houses the sensitive superhet broadcast radio and General Industries RPOL 35 1/2 and 78 RPM (dual speed recorder); play back mechanism. The 6 tube receiver and amplifier is all on one chassis; 12SA7, 12SQ7, 12SK7, 12SL7, mike gain; two 35L6 push-pull output; plus disc rectifier. Has plenty of gain for crystal or dynamic mike. Has 6" heavy duty PM speaker and tone control. Kit G-31, everything complete, with tubes and diagram. \$54.95. Crystal mike and desk stand \$4.95 extra. This is without a doubt one of the best values in kits we have ever offered. Wt. 40 lbs.



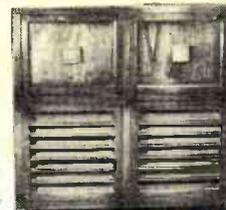
## DELUXE CONSOLE CABINET, \$39.95

- Slide Away Changer Comp.
- Record Album Compartment
- Beautiful, All Walnut Construction



This is the first time we have been able to offer a beautiful floor model console, RADIO-PHONO cabinet. Finest all walnut construction; hand rubbed finish. 34" long, 33" high, 16" deep. Holds 12" speaker, large record compartment. Slide away changer compartment will accommodate changer of the Webster 56 class and smaller. Receiver compartment is 15x14 1/2 x 7 1/2 inches. Will accommodate our Model PRK-10 kit; advertised below. Dealers, here is your chance to buy good cabinets at the right price. Convert those low-priced sets into radio-phonos combinations. Weight 50 lbs. Net. \$39.95. Price with Webster 56 changer.....\$59.90

## 8-TUBE RADIO AMP. KIT \$29.95

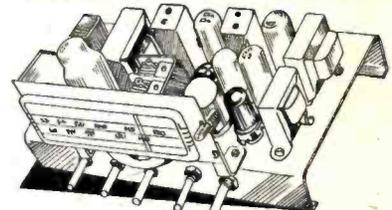

Build this High-FI Radio Amplifier

- Beautiful 8" Slide Rule Dial.
- Standard Superhet Circuit covering Broadcast 550 to 1700 K.C.
- 2-Gang Tuning Condenser.
- Offered with 12 or 15 in. PM Speakers. Push-pull 6V6 Output stage giving 15 watts of full range audio.
- Dual Tone Controls (Bass and Treble).
- Inputs for both Mike and Phono pick-up.

Here is something new in radio. A real 15 watt power amplifier with bass and treble controls. Has extra gain stage for crystal or dynamic mikes. And on the same chassis, a standard superhet radio receiver. We furnish all parts, knobs, escutcheon plate and tubes: 6SA7, 6SK7, 6SR7, 6SN7, 6SQ7, two 6V6 and 5Y3. No cabinet. Extra care in designing the power supply section assures low hum level, making this unit ideal for recording as well as P.A. use. We furnish everything as well as schematic diagram and photos of the completed chassis. Weight 35 lbs. PRK-10 Radio Amp. Kit with 12 P.M. Speaker.....Net \$29.95

PRK-10X Radio Amp. Kit with 15 in. \$30.00 value Cinnadagraph speaker.....Net \$42.95

WHY NOT ORDER A G.I. RECORDER MECHANISM AND THE CABINET, SHOWN ABOVE, WITH THIS KIT? PRICES ON G.I. UNITS ELSEWHERE IN THIS AD.

Walnut mantle table cabinet; made expressly to house the PRK-10 kit. Ready cut. Accommodates receiver chassis only, not speaker. Weight 8 lbs. Net. \$6.95

## DELUXE REC. CHASSIS, \$22.95


DeLuxe broadcast receiver chassis kit model AB-4, this kit is offered those who want a good receiver to install in their cabinet. The design is of the accepted type; standard superhet. Has power transformer, push-pull 6V6's output tubes; tone control; 2 gang condenser and 8 inch deluxe slide rule dial; similar in appearance to our PRK-10 kit; shown above; except it has no provision for mike. Offered with a 12" 15 watt Alnico 5 PM speaker. Priced complete with diagrams, photos and tubes 6SA7, 6SQ7, 6SN7, 2 6V6 and 5Y3. Wt. 22 lbs. Net \$22.95

## DALBAR AUTOMATIC PHONO RADIO SCOOP PRICE, \$39.95


Dalbar 5 tube superhet receiver 550 to 1600 K.C. (not a kit) complete chassis with tubes 12SA7, 12SK7, 12SQ7, 50L6 and 35Z5. Has heavy duty PM speaker and attractive airplane dial. We furnish everything. This Dalbar chassis, latest single post automatic record changer, and attractive ready cut walnut cabinet. You can slip the chassis into the cabinet and have a good quality radio phono comb. in only a few minutes time. Model DB-5, weight 30 lbs.
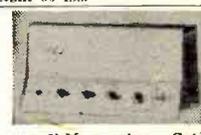
## JUKE BOX QUALITY AMPLIFIER KIT, \$29.95

This is the finest in audio amplifiers. Four 6V6 tubes in push-pull parallel and hooked up as cathode followers to drive any P.M. speaker. Gain stage for crystal or dynamic mike as well as any phono pick up. Has variable tone control and fader control. We furnish all parts, nothing else to buy. Has a streamlined spatter finished chassis with cover (ready punched). Complete with diagram, photos and tubes 6SH7, two 6SN7, four 6V6 and 5U4. Will give 18 watts of the sweetest audio you have ever heard. Wt. 25 lbs. Kit model JB-18 net \$29.95



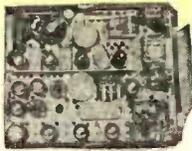**McGEE RADIO COMPANY** WRITE FOR CATALOG SEND 25% DEPOSIT—BALANCE C.O.D. 1225 McGEE ST., KANSAS CITY, MISSOURI



450 MC. TRANS.-REC.  
**\$14.95** TWO FOR **\$27.00**  
**BRAND NEW! FACTORY CARTONED**

**ARMY BC-645 I.F.F. UNIT.** Early in the war when radar picked up a plane, there was no way of knowing whether it was friendly or not. That was before BC-645 was invented. BC-645 sent out a signal that identified the plane as American. It probably saved more lives than any other piece of electronic equipment made. With some modifications the set can be used for 2-way communication, voice or code, on the following bands: ham band 420-450 mc., citizens radio 460-470 mc., fixed and mobile 450-460 mc., television experimental 470-500 mc. Equipment capable of doing the jobs of the modified set sells for hundreds and hundreds of dollars. The 15 tubes alone are worth the sale price. 4-7F7, 4-7H7, 2-7E6, 2-6E6, 2-955 and 1-WE316A. It now covers 460 to 490 mc. Each BC-645 is shipped with a Belmont factory printed conversion diagram, showing how to make AC power supply modulator and how to make Transmitter and Receiver changes. Most Hams and experimenters already have the few parts necessary. New BC-645 with tubes less power supply. Shipping weight 25 lbs. Extra WE316A Tubes \$1.29 each. 12 Volt Dynamotor ..... **\$3.95**

**BC-654 TRANSMITTER RECEIVER \$12.95**  
**GUARANTEED TO BE IN GOOD CONDITION**

7-Tube Superhet Receiver and 6-Tube Trans. with 25 Watts Power.




Order Now at this Scoop Price. Covers 3800 Kc. to 5800 Kc.

Portable voice and CW transmitter and receiver for portable, mobile, and fixed station operation. 7-tube superheterodyne receiver with 3.5 microvolt sensitivity on voice and 0.5 microvolt sensitivity on CW, and 100 milliwatts undistorted power output. 455 KC IF. Uses 3-1N5GT, 1-1A7GT, 2-3Q5GT, 1-1H5GT tubes. 6-tube transmitter, with antenna tuning network, Colpitts thermal compensated oscillator, class C final with 2-307A tubes in parallel, and crystal oscillator for checking frequency every 200 KC. 25 watts output on CW and 11.2 watts output on voice. Frequency range, transmitter and receiver, 3800 to 5800 KC. Ideal for Ham and Comes complete with cover, furnished with all tubes necessary for the operation of the trans. and rec. Less power supplies. These units are used but in good condition. Shipping weight 50 lbs. .... **\$12.95; 2 for \$25.00**  
 Send your order to our Kansas City store. This unit will be shipped from our Chicago warehouse. Immediate delivery. You can hardly tell they are used. BC-654 Less all tubes and crystal ..... **\$7.95**  
 654 VIBRATOR POWER PACK 6 OR 12 V.D.C. INPUT \$4.95 EXTRA.

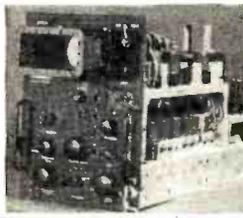
**R65 SCOPE, \$29.95**

Another receiver indicator unit; with gobs of material. Complete with 28 tubes such as: 6SA7, 6SK7, 6H6, 2X2, 5Y3, etc., plus 3BP1 scope tube. A multitude of controls, RF coils, switches, etc. All are in perfect condition; just removed from aircraft. Case size, 9x12x16". Ideal to convert to test scope and beautiful for general salvage. Weight 35 lbs. Scoop Price ..... **\$29.95**



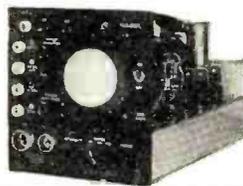**BC929 RADAR, \$14.95**

BC-929 A Radar Indicator Scoop. This unit could be rebuilt into a fine test scope. It is an ideal size. 8x9x14 priced with tubes 2-6SN7, 2-6H6, 6C5, 6X5 and 2X2. This is a red hot buy. However you will have to change the power trans. for 60 cycle use. Guaranteed to be in good condition. Scoop Price ..... **\$14.95**  
 Weight 20 lbs. Has 3 in. Cr Tube.



**NAVY SALVAGE SCOOP! \$3.95**

Navy model ZA Glide path receiver. Has 3-6C6 tubes; several controls, transformer and handy case; size 6x7x12 inches. Ideal for salvage, near new condition \$3.95. 2 for ..... **\$6.95**



**PACKARD BELL PRE-AMP., \$1.99**

Housed in a handy aluminum case 5x4x5, priced complete with tubes 6SL7, 28D7, has many usable parts. Relay and control PL68 plug and patch cord.



**SWITCH-POT. SALVAGE, 99c**

A real salvage scoop. Has 3 toggle switches, 1 band switch, 6 standard size carbon controls, knobs, etc. Scoop price .99. 3 for ..... **\$2.50**



BC-1366 Jack Box 11 bank banana plug jack and socket with 5 position single deck switch and control. 2 phone jacks. Scoop price .59 2 for **\$1.00**




**SCOOP, \$1.99**



Heavy Duty Vibrator—Made for 6-110 volt amplifiers. Freq. 60 CPS. Scoop price, \$1.99 135 ma 6-110 volt conventional power transformer, with all windings; will run phone motor. \$5.95 (Use with above vibrator.)

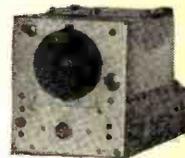**POPULAR AIRCRAFT COMMAND RECEIVERS**

These command receivers have proven to be one of the best values in war surplus. We continue to get repeat orders. Hams and experimenters buy them to convert to other frequencies and for use as they are made. Designed for 28 volts DC input and easily converted to AC DC operation, etc. For your convenience, we will include with each receiver a diagram of the Bc 454. As all of command receivers are similar, this will assist you in becoming familiar with them. Weight 8 lbs. Priced with tubes, three 12SK7, 12SR7, 12K8, 12K6.




- Brand New BC453 200 to 500 KC..... **\$6.95**
- Brand New BC454 3 to 6 MC..... **4.95**
- Near New BC454 3 to 6 MC..... **3.95**
- Brand New BC455 6 to 9 MC..... **4.95**
- Near New BC455 6 to 9 MC..... **3.95**
- Brand New BC946 550 to 1500 KC with Factory Instruction Book... **12.95**



- 28 Volt Dynamotor for 453, etc..... **\$0.95**
- Triple remote control head for SCR-274 (BC-453-B, BC-454-B, BC-455-B)..... **\$1.95**
- Flexible cable for tuning SCR-274..... **.79**
- Mounting Rack for three receivers..... **1.95**

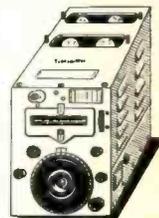**AIRCRAFT COMMAND TRANSMITTERS**


This really fits the ham's dream. Ideal for a 55 watt transmitter with 575 volts at 250 MA plate supply, or VFO to drive a high power rig. It's a companion unit to the 454-455-453 series aircraft receivers. Made by Western Electric and really rugged. The oscillator will hold the frequency, even under rough operating conditions. Has 12J5 M. O. and 2-1625 (807) in parallel as final P. A.; or buffer to feed into a high power rig. Built-in crystal dial calibration checker. Antenna loading inductance. Priced with tubes and crystal. For your convenience a diagram of the BC-457 will be sent you. All of the command transmitters are essentially the same hook-up.



- Brand New BC457 4 to 5.3 MC..... **\$7.95**
- Near New BC457 4 to 5.3 MC..... **3.95**
- Brand New BC458 5.3 to 7 MC..... **7.95**
- Near New BC458 5.3 to 7 MC..... **5.95**
- Brand New BC459 7 to 9.1 MC..... **7.95**
- Brand New BC696 3 to 4 MC..... **9.95**

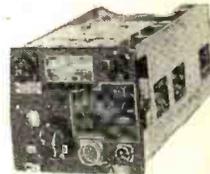**NAVY ARB RECEIVER, \$19.95**

You can convert this over, easily to a good ham receiver. It's one of the hottest values in surplus receivers. 28 volts DC input. Covers 4 bands. 195 kc to 9 mc. This is a deluxe type superhet receiver, note that the frequency coverage includes the standard broadcast band. Has 4 gang tuning condenser; can be converted to a 110 volt AC receiver. Priced complete with tubes: 12SF7, 12SA7, 3-12SF7 and 12A6. Has dial built on front of chassis. Electric driven or manual band change switch. Weight 28 lbs. Size 6x7x15 inches.



ARB Near new condition, with tubes and dynamotor..... Net **\$19.95**

**GLIDE PATH RECEIVER, \$6.95**



R-89/ARN-5 Glide Path Receiver 11 tube superhet. Formerly used for blind landing. Adaptable for many uses. Receives 326 to 335 MC. Contains six relays. 11 tubes 7-6AJ5, 12SR7, 2-12SN7, 25D7. Size 13x5x6. Weight 12 lbs. A beautiful piece of equipment. Has three crystals. Priced complete with xtals and tubes.

R-89/ARN-5 Near new condition ..... Net **\$ 6.95**

**VEEDER-ROOT METER AND CASE**



Counts number of feet of trailing wire antennae; number turns when winding on coil; applicable for many uses; beautiful bakelite case, jeweled dialite, pilot light enclosed, 3 position switch, counts up to 1000. Each ..... **95c**

**AM-26 \$1.49**

INTERPHONE SALVAGE SCOOP



AM 26 interphone amplifier. This unit is nice for parts salvage and the aluminum case is usable for receiver building etc. Size 9 1/2 x 4 1/2 x 5". Has two transformers, four tubes sockets, three filter condensers, three position panel switch, toggle switch, and many small parts. All are in perfect condition. **\$1.49; 2 for \$2.49**

**BOX SCOOP 79c**



ARMY SPARE PARTS BOX. Handy for tools or fishing tackle etc. Has water tight hinged lid. Made of 3/4" water proofed plywood. Size 3 x 11 x 5 1/2. Scoop Price ..... **79c**

**NEW KEYS 49c 10 for \$3.95**



**McGEE RADIO COMPANY**

WRITE FOR CATALOG

SEND 25% DEPOSIT—BALANCE C.O.D. 1225 McGEE ST., KANSAS CITY, MISSOURI

# RADIO SERVICEMEN! McGEE HAS THE VALUES IN RADIO TUBES AND PARTS



## HOT SPECIALS IN P.M. SPEAKERS

12" P.M. 7 oz of A.V. 18 watt only.....\$6.95  
All are guaranteed.

12" 5 oz. Alnico 5 Pm Speaker.....12 watt Net \$5.95  
8" 5 oz. Alnico 5 Pm Speaker.....10 watt Net 4.95  
8" 3.15 oz. Alnico 5 Pm Speaker.....8 watt Net 3.49  
8" 2.15 oz. Alnico 5 Pm Speaker.....6 watt Net 2.95  
6" 2.15 oz. Alnico 5 Pm Speaker.....6 watt Net 1.95  
**RED HOT SPECIAL—6" 5 oz. Alnico 3 Square Pm Speaker \$1.49; 10 for.....\$13.50**

**GENERAL ELECTRIC 5 1/2" P.M. \$1.95**  
5 1/2" G-E 1.5 oz Alnico 5 Pm Speaker with output transformer for 50L6 \$1.95 (mount for either 6 or 6 1/2" speaker.) Scoop price \$1.95; 10 for.....\$17.50

**CHOICE OF 3 1/2", 4" or 5" P.M. \$0.99**  
3 1/2", 4", or 5" Pm Speaker with 1 oz. Alnico 5 magnet. Your choice 99c each. Order all you need. May never again be sold at this price. All brand new and guaranteed perfect. Choice of 3 1/2", 4" or 5" 1 oz. Alnico 5 Pm Speaker. Scoop Price. 99c each

## DYNAMIC SPEAKERS

6 1/2" 1000 ohm Field Speaker.....\$2.49  
5" 3000 ohm Field Speaker.....1.89  
5" 1000 ohm Field Speaker.....1.89  
5" 450 ohm Field Speaker.....1.89  
4" 450 ohm Field Speaker.....1.89  
4x6" 450 ohm Field Speaker.....1.89

**SPECIALS IN TUBULAR CONDENSERS**  
Cornell-Dubilier .05 Mfd. 600 volt condenser. Scoop Price \$0.09 each. 100 for.....\$7.50

Solar Sealites .05 Mfd. 400 volt condensers or .01 400 volt \$0.07 each. 100 for.....\$5.00

**600 VOLT TUBULARS, MANUFACTURERS TYPE**

Guaranteed all good brands condensers: .001 .005 .01 .02 .05, all 600 volt. Any size \$0.08 each. 100 assorted for.....\$6.50

## POPULAR F.P. ELECTROLYTICS

in Alum. Cans. Easy Twist. Mounting all small size.

10 x 10 x 10 Mfd. 20 x 40 Mfd. 400 450 volt.....\$0.49  
30 Mfd. 450 volt.....49  
20 Mfd. 450 volt.....39  
20 Mfd. 300 volt, 10 40 x 40 Mfd. 250 450 volt.....39  
Mfd. 350 volt, 20 40 x 20 Mfd. 150 450 volt.....39  
Mfd. 25 volt.....39

## TUBULAR ELECTROLYTICS

In paper tubes with pig tail leads


Cornell-Dubilier, 8 Mfd. 450 volt \$0.39 each. 100 for.....\$32.50  
Cornell-Dubilier, 16 Mfd. 450 \$0.59 each, 10 for.....5.95  
Aerovox, 8 x 8 Mfd. 450 volt. \$0.49 each. 10 for 4.50  
Aerovox, 20 x 20 Mfd. 150 volt. \$0.39 each. 10 for 3.50  
Sprague, 50 x 30 Mfd. 150 volt. \$0.49 each. 10 for 4.25  
Solar 50 x 30 Mfd. 20 Mfd. 25 volt \$0.59 each. 10 for.....\$4.90

## RU-19 REC. \$7.95

2-Band Aircraft Receiver RU-19

Priced complete with six tubes, 3 78's and 2 77's plus twin output tube. Guaranteed to be in good condition.

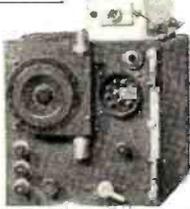RU-19 type A receives 200 to 400 KC and 4130 to 7700 KC.....\$7.95  
RU-19 type B receives 200 to 400 KC and 2500 to 4700 KC.....\$7.95



## BC-310B RECEIVER \$24.95


Bendix Radio Compass Receivers. Built-in dynamotor. 14 volts DC input. 3 gang tuning condenser. 3 bands: 150 KC through broadcast band to 1500 KC. Has 5 meter 12 tubes, (6 vol. type). A beautiful radio receiver. Easy to convert to AC operation. 30 lbs.



In good condition. Weight Net \$24.95
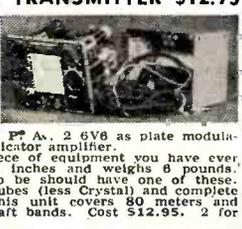
## RCA AVT-112A TRANSMITTER \$12.95

Brand new RCA aircraft transmitter Model AVT-112-A. Crystal controlled 2500 KC to 6500 KC. b Designed for 6, 12, and 24 volt DC and 950 volt DC input. 6 tubes: 6AF6 dual tuning indicator, 6V6 Pierce oscillator, 6V6 P.P. A. 2 6V6 as plate modulators, 6SL7 tuning indicator amplifier. This is the nicest piece of equipment you have ever seen. 6 x 6 x 5 1/2 inches and weighs 6 pounds. Every ham or haw to be should have one of these. All brand new with tubes (less Crystal) and complete instruction book. This unit covers 80 meters and 3105 and 6210 aircraft bands. Cost \$12.95. 2 for \$25.00.



## NEW BC-1206 \$7.95

Designed to receive A-N beam signals. 24-28 vdc. Tube complement: 14H7, 14A7, RF, 14H7, 14J7, 14A7, 14H7. IF amplifier: 14R7. detector and 1st audio: 28D7. output. 195 to 420 KC 4" high x 4" wide x 6 3/8" long. Weight 4 lbs. Net \$7.95 when purchased with AVT-112A, \$5.95.



## G.I. RECORDER MECHANISMS



Latest 1947 General Industries recording assemblies with 4 ohm magnetic cutters and crystal play back. Model R70-L-78 RPM. Net.....\$24.50  
Model R70-33 and 78 RPM. Net.....28.95  
Model R130-L-Automatic changer with cutter. 78 RPM. Net.....40.10

## MALLORY SYNC. VIBRATOR \$9.99



This is a standard type 6 volt vib. unit. Has long leads. Easily installed in the old case. A red hot item if we ever had one.

## SCOOP PRICES ON VIBRATORS

Standard 6 volt vibrators for every day replacement use—All guaranteed.

4 prong war surplus; new in bent cans.....	\$0.79
4 prong UTAH NP-42 for Philco.....	1.29
4 prong SMALL for Ford.....	1.49
4 prong OFF-Set for Delco.....	1.49
6 prong standard sync.....	1.49
6 prong reversible sync.....	1.99
7 prong reversible sync.....	1.99
5 prong OFF-Set sync.....	1.99
Sync. unit: Vibrator unit only; with cond.....	1.99
7 prong 2 volt; G. E. sync.....	1.99

## PHONO MOTOR SCOOP \$1.95

Yes that is the right price only \$1.95. Latest type rim drive 110 volt 60 cycle AC phono motor. Best type of construction. Only 2000 to sell while they last only.....\$1.95  
Latest type light weight crystal pick up arm. Has standard output crystal. Scoop price.....\$1.69

## RU-19 FOR SALVAGE \$2.95


RU-19X or ARMY equal. SALVAGE PARTS SCOOP. Has many usable parts, condensers, resistors, etc. Less tubes and plug in coils. All are in good condition. RU-19 Salvage Scoop \$2.95 ea.; two for \$5.00.

## AMERICAN XTAL CARTRIDGE \$1.49

American crystal replacement phono cartridge. Standard mounting; most one size used. Long shielded leads. Scoop price.....\$1.49
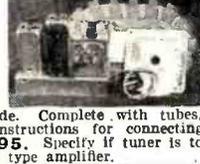
## SUPERHET BROADCAST TUNER

for connection to phono amp. or P.A. system. Compact chassis 5x3 1/2x3 inches. May be mounted inside the record player cabinet. Requires only three connections to amplifier. Uses 6SA7 or 12SA7; 6SK7 or 12SK7 and crystal diode. Complete with tubes, loop antenna, dial and instructions for connecting to any amplifier. Net \$7.95. Specify if tuner is to be used with AC or AC-DC type amplifier.



## RECORD PLAYER \$9.95

**POWERFUL SINGLE RECORD PLAYER KIT**  
Z-26. Housed in an attractive leatherette covered cabinet. Latest 78 RPM rim drive motor and light weight pick-up. Ready wired and tested 70L7 type tube amplifier. Tone and volume control. 5" PM speaker (Alnico V). This kit easily slips together. Priced complete with tubes and hook-up instructions. Kit Z-26.....Net \$9.95



## AUTO CONTROL \$3.98

Universal under-dash auto radio control; made from Crowe parts \$3.98. Choice of drive ratios 8, 10, 12, 16, or 20 to 1. To find the ratio that you need count the turns from minimum to maximum of the condenser gang and double. Specify ratio when ordering. If off-on switch is desired add \$1.00 to the price. 30" auto cables; per pair.....38c



## SCR 274 COMMAND SET \$24.95

SCR-274 Command set. Removed from planes; guaranteed to be in good condition. Here is what you get: 3 Receivers—BC-453-B (200 to 500 KC) BC-454-B (3 to 6 MC), BC-453-B (4 to 9 MC)—Triple remote tuning head, with three flexible shafts and triple shock mounting rack. Two transmitters BC-457-A (4-5.5 MC), BC-458-A (5-3.7 MC) and twin shock mounting rack. Antenna current meter, modulator and dynamotors. Each receiver has its own dynamotor. Scoop Price \$24.95, complete.

## CATHODE RAY TUBES BRAND NEW



3BP1.....Net	\$2.95
5CP1.....Net	3.95
5BP1.....Net	3.95
5FP7.....Net	3.95
7BP7.....Net	4.95
9LP7.....Net	4.95

## 75% OF ALL THE TUBES YOU USE AT 49c EACH

Guaranteed Standard Brands. Cartoned and Uncartoned

1B4	6SA7	12H6	25L6GT	78
1B5	6SC7	12J5GT	25Z6GT	80
1B6	6SD7GT	12SA7	26	1L4
1T4	6SF5	12SR7	27	50L6
3Q4	6SF7	12SH7	35L6GT	
3S4	6SG7	12SJ7	35W4	
5U4G	6SH7	12SK7	35Z3	
5Y3GT	6S7	12SL7GT	35Z4GT	
6AC7	6SK7	12SN7GT	35Z5GT	
1852	6SL7GT	12SQ7GT	39/44	
6C5	6SN7GT	12SR7	41	
6C6	6SQ7GT	14A7/7	42	
6D6	6SR7	12B7	43	
6F6GT	6V6GT	14B6	45	
6H6	6X5GT	14C7	55B5	
6J5	12AT6	14H7	56	
6K6GT	12BA6	14Q7	75	
6K7	12BE6	14R7	76	
6L7	12C8	14S7	77	

49c


7A6	7C5	7Y4	35A5	7B8
7A7	7C6	7Z4	1N5GT	
7A8	7E7	30	6A7	
7B4	7F7	32	6A8	
7B5	7H7	33	6A9	
7B6	7N7	34	1N5GT	
7B7	7Q7	35/51	1A7	

69c

1LA4	1LC5	1LE3	3Q5GT	
1LA6	1LC6	1LH4	6L6	
1LB4	1LD5	1LN5		

99c

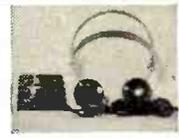Scoop Civilian type high imp. head phones (9500 ohms.) Brand new factory cartoned. Have full length regular type leads. Net \$1.29 each; 10 for.....\$10.95  
Broadcast crystal radio receiver, with crystal, \$0.99, 10 for.....\$8.90



## SELSYN INDICATORS \$2.95



Selwyn indicators. 5" diameter. Will operate on from 15 to 24 volts 60 cycle AC. Model I-82A can be used as either selwyn transmitter or selwyn receiver. Scoop Price. \$2.95. 2 for \$5.49

## BRAND NEW BC-223AX TRANSMITTER \$16.95 TWO FOR \$31.95

Brand New Factory cartoned BC 223 AX transmitter. Has 801 OSC and power amp. 2-46 modulators and 46 speech amplifier. Four special frequencies and Master oscillator. Up to 40 watts output on CW, tone or voice. Ideal for the 80 meter band. Comes with 3 coils. 2 to 3 MC. 3 to 5 MC. 3.5 to 5.25 MC. Less vital with tubes and frequency chart. Weight 120 lbs.

## NEW NAVY 6.9 MC. REC., \$7.95

Navy Aircraft Receiver R 27. 6 to 9 MC. Brand new, factory cartoned. Has black wrinkle finish. With tubes 2—12SK7, 12K8, 12SF7, 12SR7 and 12A6. This is the latest model with stabilized oscillator. Priced with tubes, 28 volt dynamotor, remote control, 6 ft. control cable. Less the power cable. Scoop Price.....\$7.95




Left to Right  
New Remote Control Head and volume control CW, MCW, MW for BC-455-B 6 to 9 MC receiver. Scoop Price. \$0.99  
BC-631-13 Jack Box, NEW. Has 10M gain control and Jones 6 screw terminal block. Salvage Price.....\$0.29  
Salvage Scoop BC-732-A Radio Control Box. Toggle switch, volume control and 6 position single pole cam-operated switch; phone jack. Scoop Price.\$0.49




**McGEE RADIO COMPANY** WRITE FOR CATALOG SEND 25% DEPOSIT—BALANCE C.O.D. 1225 McGEE ST., KANSAS CITY, MISSOURI

# FM/AM RADIO PHONO. ONLY \$95.00

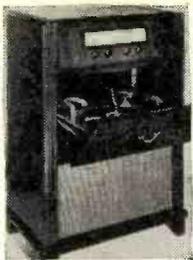

1948 Models of Meck FM/AM Radios


**JOHN MECK TRAIL-BLAZER FM/AM Radio Receiver.** Available in two styles: An attractive mantel set and a beautiful console model with automatic record changer. The 10 tube circuit meets RMA standards; covers broadcast 550 to 1750 KC and 88 to 108 MC FM. The new ratio detector eliminates the use of limiters. Base booster and tone control. Furnished with the following tubes, complete: 4-6BA6, 2-6BE6, 25L6, 25Z6, 6AT6, and 6AL5. Full 10" illuminated dial and large speaker.

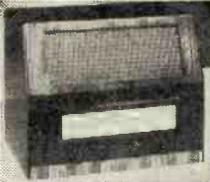

AM/FM Meck model 10A7/FA-26. Dealers net ..... \$49.90  
Lots of 3 ..... \$47.95

Console, complete with record changer, AM/FM Meck model 10A7/FA-27. Dealers net ..... \$95.00  
Lots of 3 ..... \$85.00

## MECK PEE WEE SUPER \$11.95

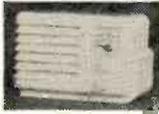

Meck, 5 tube superhet; using miniature tubes. Small plastic cabinet (7x4x5"), 2 gang condenser, loop antenna. Alnico 5 PM speaker. This is a red hot value in a small radio receiver; broadcast 550 to 1650 KC. Priced with tubes; ready to play.  
Model 800B, Black plastic cabinet ..... \$11.95  
Lots of 3 ..... \$10.95  
Model 800W, White plastic cabinet ..... \$12.95  
Lots of 3 ..... \$11.95  
Weight 5 lbs.

## MECK FM CONVERTER \$14.95

It's sensational. Makes any regular AM (ordinary radio) radio receive FM signals (88 to 108 MC). Just announced by John Meck Industries. Order your sample today. Dealers Net \$15.95. Same cabinet as Pee Wee shown above.  
Lots of three ..... \$14.95

## MECK FARM RADIO \$16.95



JOHN MECK INDUSTRIES BATTERY RADIO. Full 5 tube superhet circuit; covering broadcast band: 550 to 1650 KC. Full size Alnico 5 PM speaker and beautiful cabinet, 17x8x9". Large enough to hold 1000 hour farm battery pack. Priced complete with tubes, less battery pack: 1R5, 2-1T4, 185, and 384. Has loop antenna with provision for external antenna. Net price \$16.95. In lots of 10 ..... \$15.95  
1000 hour battery pack ..... \$4.98

## 1948 MODELS OF KARADIOS



"For Your Car" Karadio Model 80-A—The greatest radio ever offered to the street. Covers broadcast 80, 40, 20 and 10 meter bands. Here is your chance to get a communications type car radio easy to mount under dash. Has R.F. stage; separate PM speaker and beautiful cabinet, 17x8x9". Large enough to hold 1000 hour farm battery pack. Priced complete with tubes, less battery pack: 1R5, 2-1T4, 185, and 384. Has loop antenna with provision for external antenna. Net price \$16.95. In lots of 10 ..... \$15.95  
1000 hour battery pack ..... \$4.98

arate PM speaker. Designed for 6 volts D.C. input. Band 1—530 to 1700 KC; Band 2—3 to 7.3 MC; Band 3—14 to 30 MC. Net Price ..... \$79.50  
Karadio Model 80-B (airport model). Similar in appearance to model 80-A; except covers different frequency. Band 1—190 to 450 KC; Band 2—535 to 1700 KC; Band 3—2.4 to 6.8 MC. Input six volts DC. Net ..... \$62.50  
Karadio Model 1200—A fine broadcast (535 to 1700 KC) car radio. Compact size makes for easy installation (5 1/2 x 2 1/2 x 3 inches). Input six volts D.C. Has tuned R.F. stage; separate 6" PM speaker and conventional high gain superhet circuit. Similar in appearance to Model 80; shown above. Net Price ..... \$38.95

## 1948 MODEL—MIKE-BROADCASTER ONLY \$7.95

Broadcasts 800 to 1500 KC from either a phonograph pick-up or a crystal or dynamic mike. Makes any radio receiver a P.A. system, record player or recording amplifier. Gives broadcast quality. Has fader control from mike to record, simulating a regular broadcast station. This is a powerful model; using 2-35L6, 18S7, and 35Z5 tubes. Priced with tubes and connecting instructions. Works on 110 volts AC-DC. Crystal mike and desk stand \$4.95 extra. Model DE-5 truly a de-luxe mike-phonoscillator.

with tubes ready to operate, two 50B5 and 34W4. Model DE-4 Net ..... \$3.95

3-TUBE PHONO. OSC. ONLY \$3.95  
Model DE-4—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-4 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

Model DE-5—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-5 Net ..... \$3.95

# 3 HIT MODELS BY SETCHELL CARLSON




5-Tube Model 416

The 5 tube superhet model 416 is truly a post war streamlined cabinet made of plastic; covers the radio on all sides. Receives 550 to 1650 KC. Has 2 gang condenser, AVC, loop antenna and full size 12 and 50 volt tubes. Complete, ready to play. Model 416 Walnut plastic cabinet \$17.48. Lots of 3, \$16.99. Model 416 Ivory plastic cabinet \$18.19. Lots of 3, \$17.70. Weight 8 lbs.



6-Tube Model 427

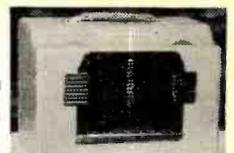The 6 tube superhet model 427 is the last word in mantel radio sets. The 3 gang condenser; fully utilizes the 6 full-size 12 and 50 volt tubes. There is no better broadcast AC-DC radio (550 to 1650 KC). Priced with tubes, ready to play. Model 427 Walnut plastic cabinet \$24.15. Lots of 3 ..... \$23.00. Ivory plastic cabinets \$25.15. Lots of 3 ..... \$24.15. Weight 9 lbs.



5-Tube Portable

Model 447 5 tube plus rectifier; portable radio is of advanced design. 5 miniature tubes and disc rectifier; 3 gang condenser, loop antenna, modern cabinet design, full 6 1/2" Alnico 5 PM speaker. This set is a distance getter. Operates on self-contained dry batteries or 110 volts AC-DC. With tubes, ready to play. Model 447, \$27.97 each. Lots of 3, \$26.60. Weight 10 lbs. 300 hour battery pack \$2.95 extra.

## MECK DISC RECORDER \$79.00



The John Meck Industries (Audar) portable disc recorder incorporates all of the latest in modern engineering. A transformer type amplifier with plenty of volume and good tone quality. Records may be cut and played back at 33 1/3 or 78 RPM. Priced complete with crystal mike and cutting and playback needles. Ready to operate; yours for only \$79.00  
Weight 35 lbs.


## MECK 3-WAY PERSONAL PORTABLE \$21.95



Model 5D-7 Broadcast superhet (550 to 1650 KC) Personal portable; only 5x6x3 inches. A big radio in a small package. Operates on 110 volt AC-DC or self-contained batteries. Has 4 miniature tubes and disc rectifier. Uses 2 45 volt 455 Eveready B battery and 3 flashlight cells. Net ..... \$21.95  
In lots of 3 ..... \$20.95  
Kit of batteries \$2.69—Extra weight 10 lbs.
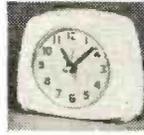
## TIME SWITCH \$4.95

Self-starting Electric Clock; with built in TIME SWITCH. Turns radio or appliance off or on at any pre-set time. Use your radio as an alarm clock.  
Scoop Price ..... \$4.95



## LAST MINUTE SPECIALS

Red hot PM speaker values. All have 20 oz. of alnico 3 magnet. Latest production. Ideal for amplifiers and radio set replacement. Fully guaranteed. Net \$5.49  
12 in. 20 oz. alnico V. 20 watts ..... Net \$5.49  
10 in. 20 oz. alnico V. 20 watts ..... Net 4.49  
8 in. 20 oz. alnico V. 15 watts ..... Net 3.98  
Thordarson power transformer scoop T 70R62 or T 44915 for 60 cycle 115 AC. 700 volts C.T. at 145 mils. 6.3 v. 4.3amps. and 3.3amps. Scoop price 3.49  
Spring wound phono motor with all hardware tunable crank etc. reg. \$8.50 value Scoop price 2.98  
Thordarson filter choke. 200 mil, 10 henry; fully shielded. Most beautifully made choke you ever saw. Weight 5 pounds. Scoop price \$1.99. 3 for R-32 Victor etc. replacement power transformer. Made by Utah. Upright mounting. Has all windings 1 1/2, 2 1/2, 5 etc. Net 4.95  
100 assorted 1/2 (3/4) watt carbon resistors; non-insulated type ..... Net 1.19  
G-E Plastic AC cord; with molded cap 6 1/2 foot 5 foot ..... 19c  
Utah VPR-1 50 mil strap mounting choke; 30 henrys. This is the standard size as used by 4, 5 and 6 tube radios. Net Price .49  
Auto aerial closets. 50.69  
4 section. Top Cowl less lead. 1.79  
3 sect. 86" side cowl. 30" lead. 2.79  
4 sect. 96" side cowl. 30" lead. 2.79  
72" ICA Uni-mount with lead. 1.79

## ARC-4 140-152 MC. \$24.95



for operation on VFH frequencies from 140 to 152 MC. Four channels crystal controlled transmitter and receiver. Designed for 12 or 24 volt DC operation. Scoop Price ..... \$24.95  
Weight 35 lbs.

## BRAND NEW RADIO COMPASS \$69.50


SCR-269-F Brand New Radio Compass; Automatic direction finder. Complete with all component parts; \$69.50. This unit was designed for Army Navy as a primary navigation compass. Constant reception is possible so that fixes can be made at any time; to establish a ship or plane's position. Plotting fixes is accomplished by selecting two or more stations and plotting these on the navigation map. The point of intersection indicates the position of the ship or plane. This equipment comes complete with 17 tubes; superhet receiver which is tunable from 200 to 1750 KC in three bands. Complete instruction manual for operation and maintenance accompanies each unit.

## MEISSNER RADIO AND DISC RECORDER \$109.50



Not much need be said about the Meissner Model radio, receiver and disc recorder. A standard transformer type broadcast (550 to 1650 KC) radio and amplifier; with tone and volume controls. Records and plays back at 33 1/3 or 78 RPM from its own radio or from crystal microphone. Priced complete with mike, ready to operate. Net Price ..... \$109.50  
Weight 45 lbs.

## 10 STATION INTERCOM \$29.95

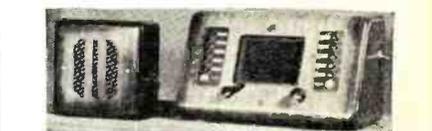

This 10 station push-button inter-com, originally cost the dealer over \$40.00. Attractive walnut finished cabinet, made by East coast manufacturer. With tubes 14F7, 50L6 and 35Z5. Master and one sub-station, net \$29.95. Extra sub \$5.95 each.


## 3-WAY REGAL SUPER-MITE \$22.95

No Taller Than a Pen  
Regal Model 747—3-way personal radio. Receives broadcasts 550 to 1650 KC. Small in size; only 4x5x8 inches. However uses full size parts with 2 gang condenser and loop. Priced complete with 4 miniature tubes and disc rectifier. Net \$22.95 each. In lots of 3 \$21.95  
Kit of batteries \$2.05 extra.

## REGAL 5-TUBE AC-DC \$14.95

A scoop value. Full-fledged; 5 tube superhet broadcast (550 to 1650 KC). Loop antenna, 5" dynamic speaker, attractive 10" plastic cabinet and slide rule dial. Order now for Christmas sales. \$15.95 each. In lots of 3 ..... \$14.95

## MAGUIRE CHANGER \$11.95

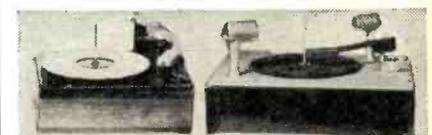

Latest Maguire 2 post record changer, plays 10 1/2" or 12 1/2" records automatically. Net ..... \$11.95  
Made to fit walnut base, \$2.49 extra.  
General Instrument single post automatic record changer plays 12 1/2" or 10 1/2" records automatically. Net ..... \$12.95  
Made to fit walnut base, \$2.49 extra.

## SCR-522 AS-IS \$12.95—Two for \$25.00

SCR-522 You are all familiar with this 100 to 156 MC Transmitter, receiver. These 522's that we have are in rough looking cases and some of the outside connectors have been damaged. However, separate the transmitter and receiver and remove the case, you will have usable merchandise. There are not many more of these units available; we have just 100 to sell.

WE HAVE A LARGE STOCK OF ALL THE RADIOS ETC. ADVERTISED ORDER FOR XMAS NOW!

**McGEE RADIO COMPANY** WRITE FOR CATALOG SEND 25% DEPOSIT—BALANCE C.O.D.  
1225 MCGEE ST., KANSAS CITY, MISSOURI

# Fall Specials

**TUBES:** Perfect condition, but not in sealed cartons. Most types in stock at up to 30% off list. Every tube guaranteed 90 days.

#20, 25, 27, 48 or 36	\$0.29
#42, 43, 75, 77, 78, 80, 89, 5Y3, 6H6 or 6K7	.39
#35, 36, 37, 39, 84, 5Y4, 6A8, 6C5, 6D6, 6H7, 6N7, 6U7, 6SA7, 6SK7, 12SA7 or 12SK7	.49
#1A7, 1H5, 1N5, 6A3, 6U5, 6X5, 7A7, 7C5, 7CA, 7Y4 or 30	.59

**TUBE CARTONS.** Plain white.

GT size (1 1/4" sq. x 3 1/4")	Per 100	1.25
Medium size (1 1/2" sq. x 4 3/4")	Per 100	1.49
Large size (2" sq. x 5")	Per 100	1.79



**PRECISION RESISTORS**  
±1%, wire-wound, Standard makes. Ohmages: 2.35, 11, 24.5, 100, 130, 405, 840, 1740, 2500, 3300, 5290, 7800, 30K, 36.5K, 50K, or 400K... .35

**SPECIAL!—GIANT "GRAB-BAG" RADIO PARTS KIT.** An outstanding buy for the Serviceman, Amateur or Experimenter. 15 FULL SIZES of resistors, condensers, wire, sockets, speaker accessories, hardware, coils, etc. **1.95**  
An amazing value at...

**RCA Victor Power Transformer** for models R-32, 45, 52 or 75. Unsolded. **\$5.95**  
**EXPERIMENTAL TUBES.** 20 asstd. receiving types for testing, research, etc. Filament tested. **1.00**  
**24 Blade Blower Fan.** 2" O.D. 1" deep. 1/4" hole. 29. With Bakelite Housing. **.98**

**ALNICO MAGNETS**

Powerful ALNICO MAGNETS of every size and shape always in stock. Write for latest fully descriptive illustrated supplement.

**MINIATURE ALNICO V MAGNETIC PHONE UNITS.** (HS-30 headset replacement.) Wide freq. response sufficient volume for use as: PM or Pillow Speaker; Dynamic or Contact Mike (using above Ouncer input); or as Hearing Aid unit. 3/8" O.D. 1/2" deep. **\$0.39**

**HANDY KITS FOR SERVICEMEN**

# 1—R.F. Antenna & Osc. coils, 10 asstd.	\$0.98
# 2—Speaker Cones; 12 asstd. 4" to 12" moulded & free-edge (magnetic incl.) Less voice coils	2.00
# 3—MOULDED BAKELITE CONDENSERS, ERS, 50 asst. .00001 to .2mfd. 200-800V. Clearly marked	2.95
# 4—TUBULAR HV-PASS CONDENSERS, 50 asstd. .001 to .2mfd. 200-800V. Standard brands	2.49
# 6—Dial Scales; 25 asstd. airplane & slide-rule (acetate & glass included)	2.98
# 7—Escutcheon Plates; 25 asstd. airplane, slide-rule & full-vision types	2.95
# 9—Wafer Sockets; 12 asstd. 4 to 7 prongs	.25
# 10—Voltage Dividers; 10 asst. multi-tapped types. High wattages included	1.98
# 14—Volume & Tone Controls; 10 asstd. wire-wound & carbon. Less switch	1.49
# 17—Dial Windows; 12 asstd. Bak & moulded acetate & convex glass	1.29
# 20—SPEAKER REPAIR KIT. A real money & time saver. Contains: 25 asstd. paper rings, 10 spiders, 25 voice coil forms, 3 yds. felt strips, 20 channels leather segments, kit of 16 shims & tube of speaker cement	2.49
# 22—RESISTOR ASSORTMENT; 20 asstd. carbon & wire-wound. 1/4 to 3 watts	.49
# 23—RADIO CEMENT & SOLVENT; 3 oz. each of all-purpose cement & thinner. With brush	.69
# 24—Shaft Extenders Reducers. Couplings; 10 asst. popular types for servicing	1.29
# 25—Spring Assortment; 45 asstd. compression & expansion for dials, push-buttons, relays	.98
# 26—SPEAKER CONE RINGS; 50 asstd. cardboard rings in popular sizes, 3 to 12"	1.49

**UTC "OUNCER" INPUT TRANSFORMERS** (7/8" x 1-3/16"). Dynamic mike or low impedance pick-up to grid. **\$0.49** ea. **12 for 5.00**

**4 TUBE SERVO AMPLIFIERS** (2-7C5, 7F7, 7Y4) 110V, 400 cycle. (See July, 47 Radio Craft for conversion to Phono & Mike Amplifier). Black crackle finish case & slide-in chassis. 8 3/4" x 4 1/2" x 3 3/4". Less tubes... **1.49**  
**R.F. PROBE** for faster servicing by impedance. Compact bakelite unit 1" x 3 3/4" with 2 test clips. Less cable... **.59**  
**RG-8/U COAX.** 52 ohm. 4 ft. lengths with two PL-250 connectors... **.39**  
**PL-250 COAX CONNECTOR.** (83-15P) Plated brass with coupling ring. Cables to 3/8" O.D... **.23**  
**PROMPT SERVICE ON ALL SPEAKER & PHONO PICK-UP REPAIRS**  
Minimum Order \$2.00—20% Deposit Required on All Orders. PLEASE ADD SUFFICIENT POSTAGE.

**LEOTONE RADIO CO.**  
MAKERS OF CONES AND FIELD COILS  
65-67 DEY STREET, NEW YORK 7, N.Y.  
WORTH 2-0284-5  
12,000 SQ. FT. OF RADIO PARTS

# Increase Your Sales With CONTESTS!

By ZENN KAUFMAN

Secure the most cooperation from your salesmen by breaking the routine with live sales contests.

**R**EACH into your wastebasket and pull out today's newspaper. You and 36 million other fairly live people bought a paper today. Why? Couldn't you live without knowing about the war in China, the budget row in Congress—or the rest of the front-page news? Sure you could. But we pay a million dollars a day for papers because we are interested in conflict—and news is a series of conflicts, crime, labor, sports, war, and politics—every headline a conflict. Harry Overstreet, a practical psychologist, says:

"Fundamental to all dramatic movement is the presence of conflict. Situations arouse us when two forces are at grips; when we are unsure of the outcome. Dullness is dull because we are not precipitated into the midst of a fight."

### People Like Conflict

People like action. Action is competition, whenever possible. Above all, people delight in conflicting action. Because we all love contests or fights, the sporting pages of newspapers are closely read. In offices, politics, or in the street, the fighting man or dog gets far more attention, proportionately, than a three-alarm fire.

George M. Cohan, while writing plays and running his own theatre, used to hold the public eye by a series of fights. Whenever he could get an interview or even in a paid announcement, Cohan devoted much space to attacking unfriendly critics with the sole purpose of inducing them to denounce him at great length. He even put out a little newspaper of his own to battle them.

### Some Novel Contests

Three beverage makers in Milwaukee together sponsored a free six-day bike race. This conflict attracted 40,000 people who were not only fed appropriate advertising plugs about the three beverages through loudspeakers, but had to buy them in quantities to quench their long-drawn out thirst. The Chevrolet Motor Company has seen its soapbox derbies grow into a world-wide conflict. With tryouts in every town, with elimination semifinals in 120 cities, the final event has assumed enough importance to rate a national radio hookup together with thousands of columns of news publicity. It all started because one Chev-

vie dealer realized that conflict—even a contest of small boys in toy automobiles—makes news.

### Use Sales Contests

Sales contests bring conflict to salesmen. Use them. No man works his hardest except (a) under fear of being fired, or (b) the white heat of competition. Since you can't continuously threaten to fire your salesmen, the only alternative (for maximum effort) is a well-planned sales contest.

The formula for successful contests is:

1. Not too long. 30 to 60 days is top.
2. An exciting theme. Try "Every Man a Millionaire." Give \$10,000 in paper money for each sale. First man to get a million gets the prize. Another good theme is "A Trip to the Savings Bank." A chart marks off into steps the route from the home office to the bank. As his sales go up, each man moves towards the bank where cash prizes are waiting.
3. Fair and simple scoring plan. Bad quota setting is responsible for more contest failures than any other single fault. Make your scoring simple.
4. Steady weekly follow-up. A scoreboard. Write letters to your men every week. Get the wives into the picture. Better to spend a little less on prizes, rather than omit proper follow-up.
5. Interesting prizes. Use (a) medals, plaques, (b) cash, (c) choice of items from a whole book of prizes, (d) trips and cruises. Keep talking about your prizes all the time. It's not what you give that counts—it's how much build-up you give it.

A contest is in itself a conflict—with a cast, plot, scenery, action, suspense—and all the elements of a real show. Harrison, a GE distributor in Newark once opened a sales contest with a visit from an orphan asylum band. When those kids got through playing at the sales meeting the average blood pressure of the salesmen was up at least 5 points. And that's what makes enthusiasm.

Prize contests bring this same element of conflict to consumer merchandising. 45 million entries are made in prize contests in an average year. Major Bowes earned \$150 a minute by pitting amateurs against each other on a national network. There's no end to the ingenuity that can be put into these contests. McCorkells, a San Pedro, California, appliance dealer, ran

# LEARN EITHER **Electricity OR Radio** IN A FEW WEEKS in the GREAT SHOPS of COYNE

**NOT "Home Study" Courses  
...All Practical Training and  
Necessary Theory Given in  
Our Famous Chicago Shops!**

Why spend years learning Electricity or Radio, when COYNE prepares you for good jobs in either field in a few short weeks? Our training not only saves time; you're ready to step into the better pay that much sooner. You make rapid progress because you work under expert instructors here in our great shops. We do not teach by mail. Select course you prefer and send coupon TODAY!

## **ELECTRICITY**



### **Including Industrial Electronics**

Big future in Power Plant Work, Motors, Armature Winding, House and Factory Wiring, Industrial Electronics, Home Appliances, Lighting, Auto Electricity, Electrical Maintenance — all covered at COYNE. Here you get "all-around" Electrical training!

### **TRAIN ON REAL EQUIPMENT**

You use, test, repair full-size apparatus — just like you'll later handle on the job. Previous experience unnecessary.



### **FREE ELECTRICAL BOOK**

Send now for big, illustrated book on COYNE Electrical Training. Many large pictures of our shops. Tells about Free Lifetime Employment Service to Coyne graduates. Other vital facts. Check coupon for "ELECTRICITY" and mail today.

## **RADIO** including **SOUND and TELEVISION**



If you prefer Radio, COYNE gives quick, practical training in Radio Construction, Testing, Repair; also Public Address, Sound Systems, FM, Television. Many branches of Radio open to you.

### **Want to be Your Own Boss?**

Hundreds of Coyne graduates have successful Radio shops of their own. We show you how to start, how to build for a lifetime future. No previous experience required to take Coyne Radio Course.



### **FREE RADIO BOOK**

Check coupon for "RADIO" to receive our big FREE book of photos and facts about Coyne Training in Radio, Sound and Television. Describes the vast new opportunities in this field, and how we make it easy to get ahead. Rush coupon NOW.



**B. W. COOKE**

## **COYNE HAS BEEN TRAINING MEN SINCE 1899**

For nearly 50 years, the great shops of COYNE have been turning out men and young men trained for better jobs in practical fields. Coyne graduates hold responsible positions in many leading electrical and radio firms.

**ADDED TRAINING in ELECTRIC REFRIGERATION included with either course**

**NON-VETERANS** who are short of cash can finance their tuition and pay it in easy monthly payments after graduation.

**VETERANS!** Coyne is authorized to accept veterans for G. I. training. Coupon brings bulletin.

**COYNE ELECTRICAL SCHOOL**  
Dept. 77-51H  
500 S. Paulina Street, Chicago 12, Ill.

## **CHECK COUPON FOR ELECTRICITY OR RADIO—MAIL NOW!**

B. W. COOKE, President,  
COYNE ELECTRICAL SCHOOL,  
500 S. Paulina St., Dept. 77-51H, Chicago 12.

Send me your **BIG FREE BOOK**—for the Course checked below, and tell me about your special plans to help me. This does not obligate me and no salesman will call.

**ELECTRICITY**       **RADIO**

NAME.....

ADDRESS.....

CITY..... STATE.....



**OLSON RADIO WAREHOUSE, INC. AKRON, OHIO**

**A Radio Man's Best Pal!**



You can read all resistor code-colors in a flash with this handy pocket guide! Revolving wheels in color show all resistance values. OLSON gives you this valuable tool (size 4 1/4" x 2 1/4") for a piffling 3c. **GET ONE NOW!**

This offer good only in U. S. A.



**and you get this big new CATALOG FREE!**  
60 rip-snortin' pages of special OLSON Bargains in Standard Radio Parts, Sound and Testing Equipment.

Clip the coupon and **MAIL TODAY**

**OLSON RADIO WAREHOUSE INC.**

73 E. MILL ST., DEPT. 97, AKRON, OHIO

I enclose 3c. Send me 1 "Resist-O-Guide" & new Free Catalog of Olson Bargains.

I am a Repair Man.  I am an Amateur or Experimenter.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

# PORTABLE SWITCHBOARDS

**BD-71:** 6 line, local battery, monocord, W/CT, repeating coils on 2 lines to permit simplexing telegraph circuit. New. **Price \$40.00 each.**

**BD-72:** 12 line, local battery, monocord, magneto type, repeating coils on 4 lines permitting simplexing for telegraph, night alarm bell, carrying strap and 4 collapsible steel legs. New. **Price \$60.00 each.**

Discounts for quantity orders

**MASPETH TELEPHONE & RADIO CORPORATION**

427 Flatbush Avenue Extension

NEvins 8-5709

Brooklyn 1, New York

a contest in which folks were asked to guess the cost of operating a refrigerator for 30 days. The *Boston Edison Company* ran an essay contest (Topic: What I Have Learned About Electric Cooking); found 18% of all entrants were in the market for a new stove. In Boise, Idaho, they ran a Cookery Quiz, asking the public to check answers to 18 questions.

Put *conflict* into your advertising. Major Bowes made \$150 a minute by presenting *conflicting* talent on the air. Dramatize the battle between appliances, the champions of health, and old-fashioned drudgery. At the New York World's Fair one of the most talked of exhibits was the one in which the power companies put on a dish-washing race between the old-fashioned gal who did it by hand and a modern miss who let Mr. Reddy Kilowatt do the job. Guess who won? Show how Kid Kilowatt puts the K.O. on lost time and particularly on hard work.

Put the element of *conflict* in your advertising—in your selling—in your windows. It's a sure-fire way to get attention. The public is always ready for a fight. If you show that your product is fighting the things that they don't like they will be quick to pick you as the winner. You'll be the odds on favorite for all bets!

(Acknowledgement is made to Harper Brothers for permission to reprint parts of "Showmanship in Business" by Goode and Kaufman.)

-30-

## FACSIMILE IN COLOR

A NEW method of facsimile reception which will be in the price range of the average pocketbook has been announced by Finch Telecommunications, Inc.

Known as "Colorfax," this new system has been designed to provide direct reception in the home, of comics in full colors as they are now printed in newspapers.

Product of joint research by W.G.H. Finch and Dr. LaVerne Philpott, this "Colorfax" machine is capable of transmitting in full color from any one point to a multiplicity of receivers, and of recording the transmission permanently on any ordinary white paper.

This new unit does not require the use of special electro-sensitive papers. Any paper, such as typewriter bond, telegraph or business machine rolls, or ordinary letterhead paper may be used. This means that the cost of servicing facsimile machines will be reduced and that home users of facsimile receivers will be able to make recordings on any type of suitable paper stock which will fit the machine.

In the first press demonstration of "Colorfax," full color pictures were transmitted and received over the system, in multicolor. In this case, four colors were used, just as in Sunday comics. Each picture was transmitted and received by line, each line carrying the full colors before tracing the next one. Additional colors, besides the basic four, were produced by surprinting just as is done in ordinary color printing from plates.

-50-

# DAVEGA COMMUNICATIONS DIVISION

## Presenting the NEW MODEL SX-43 hallicrafters

"The Radio Man's Radio"

... to give amateurs:



**MORE VALUE**  
Never before all these features at this price

**GREATER PERFORMANCE**  
AM-FM-CW . . . all essential amateur frequencies from 540 kc. to 108 Mc.

**LOWER PRICE**  
**\$169<sup>50</sup>**  
Sets available after August 1947

### MODEL SX-43

The SX-43 offers continuous coverage from 540 Kc. to 55 Mc. and has an additional band from 88 to 108 Mc. AM reception all bands. CW on four lower bands and FM on frequencies above 44 Mc.

ONLY  
**\$169<sup>50</sup>**



### ← MODEL SX-42

A truly post war radio. Greatest continuous frequency coverage of any communication receiver—from 540 Kc. to 110 Mc. in six bands. FM-AM-CW. 15 tubes.  
Speaker . . . . . 29.50

ONLY  
**\$275<sup>00</sup>**



### ← MODEL S-40A

Overall frequency range from 540 Kc. to 43 Mc. in four bands. Nine tubes, built-in dynamic speaker.

ONLY  
**\$89<sup>50</sup>**



### ← MODEL S-38

Overall frequency range from 540 Kc. to 32 Mc. in four bands. Compact and rugged. AC-DC. Built-in speaker.

ONLY  
**\$47<sup>50</sup>**

**NEW YORK**  
Downtown . . . . . 63 Cortlandt Street  
Downtown . . . . . 200 Broadway  
Hotel Commodore . . . . . 111 E. 42nd Street  
Times Square . . . . . 132 W. 42nd Street  
Madison Square Garden . . . . . 825 Eighth Ave.  
**NEW JERSEY**  
Newark . . . . . 30 Park Place  
Jersey City . . . . . 30 Journal Square  
Paterson . . . . . 185 Main Street  
**LONG ISLAND**  
Jamaica . . . . . 163-24 Jamaica Ave.  
Flushing . . . . . 39-11 Main Street  
Hempstead . . . . . 45 Main Street  
**WESTCHESTER**  
White Plains . . . . . 175 Main Street

# DAVEGA

MAIL COUPON FOR DESCRIPTIVE LITERATURE

DAVEGA COMMUNICATIONS DIVISION  
63 Cortlandt Street, New York 7, N. Y.  
Please send full information on Communications Receivers, without obligation.

NAME . . . . .  
ADDRESS . . . . .  
CITY . . . . .

RN-6

# The WORLD'S RADIO TUBES

("Radio Tube Vade Mecum")  
More than 10,000 tubes listed!  
New "1948" Seventh Edition Ready  
October or November

The Only Book of Its Kind in the  
World—and one of the world's  
largest-selling radio books.

**COMPLETE—  
In Twelve Languages!**

## CHARACTERISTIC TUBE DATA OF

- U. S.
- BRITISH
- FRENCH
- CZECH
- GERMAN
- ITALIAN
- RUSSIAN

and all other available types.

More listings than ever before.  
New, larger page size  
Better paper and appearance

Of the previous, smaller edition, ELECTRONICS said, "Here at last is the radio tube handbook radio engineers have dreamed of. . . in many carefully prepared tables and charts." "Probably the most complete and authoritative set of tube-data in existence," said RADIO CRAFT.

**RESERVE YOUR COPY NOW AT  
YOUR FAVORITE DEALER'S,** or direct by mail from us, at \$3.00 (tentative price); please add 10c to U.S.A. mail orders; foreign, 20c.

(Customers outside the Americas should send orders or inquiries on this book to P. H. Brans, Ltd., 28 Prins Leopold St., Borgerhout, Antwerp, Belgium. Price, 135 Belgian francs per copy.)

## RETAIL BOOK SERVICE

We have in stock for immediate shipment at publishers' standard prices nearly every radio book currently in print. **Same-day service** on more than 98% of all such orders. If you don't know the price of any book wanted, remit sufficient, and we'll promptly refund any overpayment. C.O.D. orders accepted in U.S.A. only. Send stamp for complete catalog.

**DEALERS:** "technical" discounts allowed on these books when purchased by the radio, book, and news trades in quantities for resale. If you don't live near or deal regularly with one of our dealers, you may order direct from us by mail.

Place your advance  
order NOW for the

# Antenna Manual

The most comprehensive antenna book yet published, with all the old tried-and-true standards, and many a new one.

Among the new, "hot" antennas described in this book are:

- \* The *BOBTAIL CURTAIN* and the *VERTICAL TRIAD*, a couple of dx-dandies for 75 and 40.
- \* The *OCTAPUSH*, a single array for 40, 20, and 10!
- \* The *X-CURTAIN*, an improved "Lazy-H."
- \* The *ELECTROTATOR*, an electrically rotated broadside curtain.

WRITTEN BY W. W. SMITH, W6BCX, Editor of the prewar "Radio" and "Radio Handbook". Many of you know him as the developer or first popularizer of the *Lazy-H* array, the *Plumber's Delight* three-element rotary, the *Bi-Square* array, the link-coupled universal antenna coupler, and various other little gems which after many years are still helping hams snag dx, save money, avoid pink tickets for harmonics, and otherwise keep them contented.

The *ANTENNA MANUAL* has the same happy combination of practical how-to-build-it data and simple underlying explanations that make the "Radio Handbook" one of the largest-selling radio texts in existence.

"Sugar-coated" radiation, propagation, antenna, and transmission line theory help you understand what's going on. Comprehensive practical data (including dimensions, of course) on all the more popular antennas—and on some brand-new ones which have never before appeared in print, but about which you are going to hear a lot on the air in the the near future.

A general antenna text, not exclusively for the ham. Antenna techniques and propagation data are given for all frequencies between 16 kc. and 1000 Mc., regardless of application.

Tentative price, \$3.00, durably clothbound. Reserve your copy now from your favorite dealer, or direct from us; please add 10c to U.S.A. mail orders; foreign, 25c.



Just Out!


**The only comprehensive book for the beginner!**

You need no other book to get your license and get on the air. Ideal for those just getting started, or getting interested, in amateur radio. Absolutely complete. How-to-build simple equipment for a complete station on all newcomer bands. Operating instructions. Simple theory. Complete section of study questions, including those needed to pass the license exams. U. S. A. Amateur radio regulations. Written by those masters of making-it-plain, the editors of the "Radio Handbook" and the prewar "Radio."

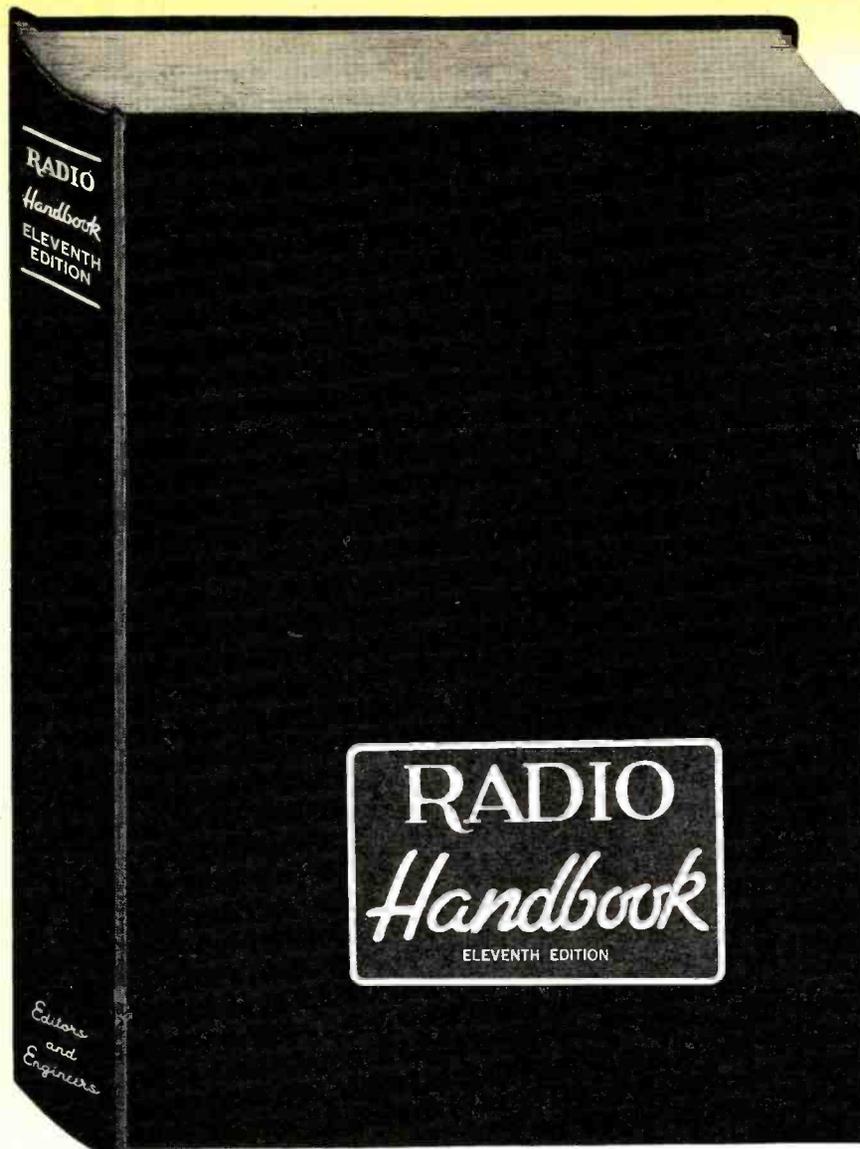**\$1.00 at your dealer, or \$1.10 postpaid from us.**

Editors and Engineers  
LIMITED

1302 KENWOOD ROAD Santa Barbara CALIFORNIA



The  
eleventh edition

# RADIO HANDBOOK

*ready in November*

•  
All New Equipment Shown

•  
Greatly Enlarged

•  
Larger-Sized, More Detailed  
Photographs

•  
Extensively Revised

•  
New, Larger Page Size  
(same size as this magazine; more  
than half again as much per page)

## *The greatest* RADIO HANDBOOK

***we've ever published.*** The greatest array of practical radio equipment ever shown between the covers of one book—all brand-new. All newly-designed, and newly-built by practical men, for practical men; all tested in our own shop in actual use.

### FEATURED IN THIS EDITION ARE:

- Dozens of transmitters for all bands, and all powers up to 1 kw.
- Six chapters on Antennas, Transmission Lines, and Propagation
- One chapter devoted entirely to rotary array construction and feed methods
- One large chapter on the conversion of widely-distributed military surplus equipment to amateur and other practical use
- New constructional data on beam-tetrode amplifiers
- One chapter on determining the operational characteristics of all types of amplifiers
- New, simple FM exciter designs
- New data on transmitter control by improved methods
- New V-F-O design
- Simplified antenna tuning device and sending-wave meter
- The most extensive tube tables of any book not devoted entirely to such data

**RESERVE YOUR COPY** at your favorite dealer's TODAY, or you may lose out on the limited-quantity first printing. Despite high costs, there's MORE PER-DOLLAR VALUE in this new, 11th edition RADIO HANDBOOK than ever before. Durably clothbound, gold-stamped, \$3.00 per copy at your dealer's in U.S.A. To mail orders, add 25c per copy in U.S.A.; foreign, 50c.


If you don't live near or deal regularly with one of our dealers, you may order direct from

*Editors and Engineers*  
LIMITED

1302 KENWOOD ROAD

*Santa Barbara* CALIFORNIA

## FOR BETTER BUYS SEE HIGHBRIDGE

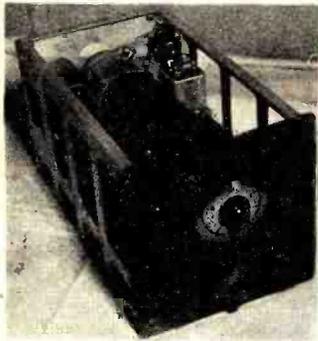


### PULSE TYPE RADIO ALTIMETER SCR 718

Invaluable as aircraft or navigation aid 110 v.—400 cy. AC. Tube complement includes 3—6A65; 1—2x2; 1—3DPJ. In perfect operating condition—schematic with each unit. Complete ..... **\$12.95**


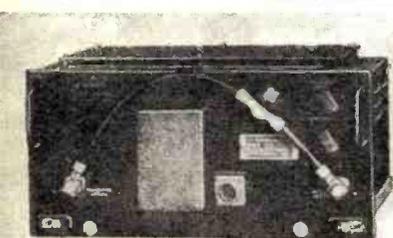
### ALTIMETER TRANSCEIVER RT-7/APN-1

Freq. 418-462 Mc: FM with 14 tubes: 3—12S17, 4—12SH7, 2—12H6, 1—VR150, 2—955, 2—9004 and 27 v. 3a dynamotor. Possible uses: aerial mapping, burglar alarms, citizens' band. In case 8 3/4"x7 1/2"x18 1/2". Wt. 25 lbs. Used ..... **\$8.95**



### RADIO TRANSMITTER AND RECEIVER APS 13

Light weight air-borne radar system, radio transmitter and receiver APS-13; tube complement 5—6J6; 9—6AG5; 1—VR105; 2—D21; unit is brand new, complete with tubes; the tubes alone are worth more than this low price of only **\$11.50**

### WESTERN ELECTRIC INPUT TRANSFORMER

Video core type; imped. ratio between windings: 1-2, 3-4, 5-6, in parallel 50-900 ohms; Freq. range 10 KC to 2 MC; made for set AN/APQ-13: Electrostatic shield between windings, oil filled; 5/4" diameter, 5" high. Wt. 5 lbs. .... **\$1.95**

### BRAND NEW 7EP4

Individually packed in original cartons. Guaranteed ..... **\$19.50**

KS-9524—Transformer Pri. 115 v-60 cycles. Sec. #1-450 v. @ 30 MA C.T. Sec. #2-6.4 v. @ 1250 MA. Rectangular metal case, stud. mtd. solder eyes—approx. size 3 1/16x2 5/16x3 3/8 with standoff 4/8. No. T2G-97 ..... **\$1.95**

All Prices F.O.B. New York City, N. Y.

## HIGHBRIDGE RADIO-TELEVISION & APPLIANCE CO.

343 CANAL NEW YORK 13, NEW YORK

# Parts Lists

(FOR CIRCUIT DIAGRAMS APPEARING ON PAGES 80 AND 81)

### STEWART-WARNER MODELS 9002-A, B, P, R

Part No.	Code and Description
502140	4—390 ohm, 1/4 w. res.
502130	6—22,000 ohm, 1/4 w. res.
502133	11—220,000 ohm, 1/4 w. res.
502291	13—4700 ohm, 1/4 w. res.
502264	15—47 ohm, 1/4 w. res.
502269	16—3.3 megohm, 1/4 w. res.
502131	18—47,000 ohm, 1/4 w. res.
502145	20A, 20B—500,000 ohm vol. control & sw.
502136	24—10 megohm, 1/4 w. res.
502135	25—2.2 megohm, 1/4 w. res.
502128	26—2200 ohm, 1/4 w. res.
502133	29, 30—220,000 ohm, 1/4 w. res.
502134	32—470,000 ohm, 1/4 w. res.
502138	33—130 ohm, 1/4 w. res.
502469	37—1500 ohm, 1 w. res.
502574	42—33 ohm, 1/2 w. res.
502123	3A, 3B, 3C—Var. gang cond.
502159	7—50 µfd. mica cond.
502155	9—1 µfd., 200 v. cond.
502158	10—2 µfd., 200 v. cond.
502262	12—25 µfd., 200 v. cond.
502160	19, 27—110 µfd. mica cond.
502453	21—002 µfd., 400 v. cond.
502470	22—0008 µfd., 400 v. cond.
502153	28—05 µfd., 200 v. cond.
502156	31—004 µfd., 400 v. cond.
502151	34—01 µfd., 400 v. cond.
500256	35A, 35B—40/20 µfd., 150/150 v. elec. cond.
502152	38—02 µfd., 400 v. cond.
502157	41—05 µfd., 400 v. cond.
502246	1—Loop ant.
502121	2—Ant. coupling coil
502146	5—R.f. coil
502198	8—Osc. coil
502102	14—First i.f. trans.
502103	17—Second i.f. trans.
502213 or 502904	36—Output trans. for R-502-208 or A-502208 speaker
500546	23—Sw. & tone control
502214 or 502903	39—Cone & voice coil for R-502208 or A-502208 speaker
R-502208	40—5" PM speaker

### GRANTLINE MODEL 510

Part No.	Code and Description
C-9B1-27	R <sub>1</sub> —220 ohm, 1/2 w. res.
C-9B1-67	R <sub>2</sub> —2700 ohm, 1/2 w. res.
C-9B1-84	R <sub>3</sub> —68,000 ohm, 1/2 w. res.
C-9B1-302	R <sub>4</sub> —15 megohm, 1/2 w. res.
C-9B1-62	R <sub>5</sub> —1000 ohm, 1/2 w. res.
C-9B1-34	R <sub>6</sub> , R <sub>10</sub> —3.3 megohm, 1/2 w. res.
101252	R <sub>7</sub> , S <sub>1</sub> —1 megohm vol. control & sw.
C-9B1-37	R <sub>8</sub> —10 megohm, 1/2 w. res.
C-9B1-31	R <sub>9</sub> —1 megohm, 1/2 w. res.
C-9B1-42	R <sub>11</sub> —22 ohm, 1/2 w. res.
130343	R <sub>12</sub> —545 ohm, 1/4 w. res.
C-9B1-66	R <sub>13</sub> —2200 ohm, 1/2 w. res.
130344	R <sub>14</sub> —1975 ohm, 6 w. res.
C-8D-10770	C <sub>1</sub> , C <sub>2</sub> —05 µfd., 200 v. cond.
B-8A-10246	C <sub>2A</sub> , C <sub>2B</sub> , C <sub>3</sub> , C <sub>4</sub> —Two-gang car. cond. including ant. & osc. trimmers. Range of freq. 14-452 µfd. (ant.) and 10-198 µfd. (osc.)
C-8F3-8	C <sub>5</sub> , C <sub>12</sub> —0001 µfd., 500 v. cond.
C-8D-10775	C <sub>6</sub> —25 µfd., 200 v. cond.
C-8D-10761	C <sub>8</sub> , C <sub>13</sub> —01 µfd., 400 v. cond.
C-8F3-8	C <sub>9</sub> —0001 µfd., 500 v. cond. (Part of 2nd. i.f.)
C-8D-10785	C <sub>10</sub> —005 µfd., 600 v. cond.
C-8D-10771	C <sub>11</sub> —1 µfd., 200 v. cond.
C-8D-10789	C <sub>14</sub> —002 µfd., 600 v. cond.
C-8D-10813	C <sub>15</sub> —05 µfd., 400 v. cond.
119-123	C <sub>16A</sub> , C <sub>16B</sub> , C <sub>16C</sub> , C <sub>16D</sub> —40/20/40 µfd., 50/150/10/150 v. elec. cond.
B-13E-10250	T <sub>1</sub> —Loop ant. assembly
A-13E-10239	T <sub>2</sub> —Osc. coil
108201	T <sub>3</sub> —Input i.f. trans.
108200	T <sub>4</sub> —Output i.f. trans.
105127	T <sub>5</sub> —Output trans.
125153	S <sub>1</sub> —Line-battery sw.

### GENERAL ELECTRIC MODELS 110, 111

Part No.	Code and Description
URD-081	R <sub>1</sub> —22,000 ohm, 1/2 w. res.
URD-129	R <sub>2</sub> —2.2 megohm, 1/2 w. res.
RRC-037	R <sub>3</sub> , S <sub>1</sub> —5 megohm vol. control & sw.
URD-137	R <sub>4</sub> —4.7 megohm, 1/2 w. res.
URD-109	R <sub>5</sub> —330,000 ohm, 1/2 w. res.
URD-029	R <sub>6</sub> —150 ohm, 1/2 w. res.

URF-053  
URE-007  
URD-153  
UCC-019

RCT-017  
UCC-028

UCU-1040  
UCU-2045  
UCC-025  
UCC-026  
RCE-040

RAB-043

RLC-031  
RTL-035  
RTL-036  
RTO-023

### Part No.

Code and Description	
30189	R <sub>1</sub> , R <sub>11</sub> —120 ohm, 1/4 w. res.
30731	R <sub>2</sub> —1200 ohm, 1/4 w. res.
14583	R <sub>3</sub> , R <sub>9</sub> , R <sub>12</sub> —220,000 ohm, 1/4 w. res.
30492	R <sub>4</sub> —22,000 ohm, 1/4 w. res.
38785	R <sub>5</sub> —15 megohm, 1/4 w. res.
12928	R <sub>6</sub> —3.3 megohm, 1/4 w. res.
36242	R <sub>7</sub> , S <sub>1</sub> —Vol. control & power sw.
30931	R <sub>8</sub> —4.7 megohm, 1/4 w. res.
30648	R <sub>10</sub> —470,000 ohm, 1/4 w. res.
6134	R <sub>13</sub> —1200 ohm, 1 w. res.
70652	C <sub>1</sub> , C <sub>13</sub> —01 µfd. cond.
70617	C <sub>2</sub> , C <sub>19</sub> , C <sub>21</sub> —1 µfd. cond.
39632	C <sub>3</sub> —150 µfd. mica cond.
39622	C <sub>4</sub> —56 µfd. mica cond.
70412	C <sub>5</sub> , C <sub>8</sub> , C <sub>20</sub> , C <sub>22</sub> , L <sub>12</sub> , L <sub>13</sub> —Second i.f. trans.
70711	C <sub>7</sub> , C <sub>11</sub> —02 µfd. cond.
70712	C <sub>9</sub> —0018 µfd. cond.
39640	C <sub>10</sub> —330 µfd. mica cond.
70627	C <sub>10</sub> , C <sub>19</sub> —005 µfd. cond.
70635	C <sub>14</sub> —035 µfd. cond.
39606	C <sub>15</sub> —12 µfd. mica cond.
70615	C <sub>16</sub> —05 µfd. cond.
39152	C <sub>17</sub> , C <sub>18</sub> —30/50 µfd., 150/150 v. elec. cond.
39838	C <sub>20</sub> , C <sub>21</sub> , C <sub>22</sub> —Var. tuning cond.
70416	C <sub>23</sub> , L <sub>3</sub> , L <sub>4</sub> —Antenna coil
70411	C <sub>23</sub> , C <sub>24</sub> , L <sub>10</sub> , L <sub>11</sub> —First i.f. trans.
39839	C <sub>25</sub> , C <sub>30</sub> —190-260 µfd./450-600 µfd. adj. mica cond.
39841	L <sub>1</sub> , L <sub>2</sub> —Antenna loop
70418	L <sub>5</sub> —Peaking coil
39892	L <sub>6</sub> , L <sub>7</sub> , L <sub>8</sub> , L <sub>9</sub> —Osc. coil.
36800	T <sub>1</sub> —Output trans.
39837	S <sub>2</sub> , S <sub>3</sub> —Range sw.

### MAJESTIC MODELS 5A445, 5A445R

Part No.	Code and Description
9-184	R <sub>1</sub> , R <sub>4</sub> —22,000 ohm, 1/4 w. res.
9-182	R <sub>2</sub> —220,000 ohm, 1/4 w. res.
9-206	R <sub>3</sub> —3.3 megohm, 1/4 w. res.
13-28	R <sub>5</sub> —5 megohm vol. control & sw.
9-160	R <sub>6</sub> —10 megohm, 1/4 w. res.
9-89	R <sub>7</sub> —330,000 ohm, 1/2 w. res.
9-207	R <sub>8</sub> —470,000 ohm, 1/2 w. res.
9-251	R <sub>9</sub> —150 ohm, 1 w. res.
9-216	R <sub>10</sub> —1200 ohm, 1 w. res.
02-100	R <sub>11</sub> —2200 ohm, 1/2 w. res.
9-269	R <sub>12</sub> —18,000 ohm, 1/4 w. res.
5-57	C <sub>1</sub> , C <sub>17</sub> , C <sub>21</sub> —01 µfd., 200 v. cond.
7-24	C <sub>2</sub> , C <sub>3</sub> —Ganged tuning cond.
19-32	C <sub>4</sub> —20 µfd., 150 v. elec. cond.
5-40	C <sub>5</sub> , C <sub>7</sub> , C <sub>10</sub> , C <sub>19</sub> , C <sub>22</sub> —05 µfd., 200 v. cond.
19-24	C <sub>8</sub> , C <sub>9</sub> , C <sub>12</sub> , C <sub>18</sub> —Trimmer cond. (Part of gang)
5-52	C <sub>11</sub> —20/40 µfd., 150 v. elec. cond.
6-151	C <sub>14</sub> —002 µfd., 200 v. cond.
5-58	C <sub>15</sub> , C <sub>16</sub> , C <sub>20</sub> —220 µfd., 500 v. cond.
3-116	C <sub>18</sub> —04 µfd., 400 v. cond.
3-117	T <sub>1</sub> —First i.f. trans.
	T <sub>2</sub> —Second i.f. trans.

### TRUETONE MODEL D2630

Part No.	Code and Description
B84393	R <sub>1</sub> —39,000 ohm, 1/2 w. res.
B84472	R <sub>2</sub> —4700 ohm, 1/2 w. res.
B84473	R <sub>3</sub> , R <sub>5</sub> —47,000 ohm, 1/2 w. res.
B84332	R <sub>4</sub> —3300 ohm, 1/2 w. res.
B85104	R <sub>6</sub> —100,000 ohm, 1/2 w. res.
B85225	R <sub>7</sub> —2.2 megohm, 1/2 w. res.
B85475	R <sub>8</sub> —4.7 megohm, 1/2 w. res.
36X309	R <sub>9</sub> —5 megohm vol. control & sw.
B84153	R <sub>10</sub> —15,000 ohm, 1/2 w. res.
B85474	R <sub>11</sub> , R <sub>14</sub> —470,000 ohm, 1/2 w. res.
B84333	R <sub>12</sub> —33,000 ohm, 1/2 w. res.
B84823	R <sub>13</sub> —82,000 ohm, 1/2 w. res.

# 15-100 MC



**A Significant Advance in VHF Design**

**with BLILEY BH6 CRYSTAL UNITS**


Crystal performance in the range 15-100 mc is an accomplished fact with the new BH6 unit. New processing techniques produce paper thin quartz plates operating on third, fifth, and seventh overtones. Stability, precision, and reliability have all been proven in this outstanding design—another triumph of Bliley engineering and craftsmanship.

Crystal holders look pretty much alike externally but the internal assembly is the vital spot. In the BH6 unit a pair of ceramic rings rigidly clamp the delicate quartz crystal in position. The crystal, lapped as thin as .004", is processed to micro-tolerances and

silver plated to insure long term precision. Every step is carefully controlled and inspected before the complete assembly is hermetically sealed in its metal case.

The finished BH6 crystal unit is not a prima donna—it will meet the most rigid service requirements in your VHF equipment. Design engineers are invited to write for recommendations covering oscillator circuits best suited for optimum performance; stating qualifications such as drive requirements to the following stage, frequency tolerance, and temperature range over which tolerance must be maintained.

**Bliley**  
CRYSTALS

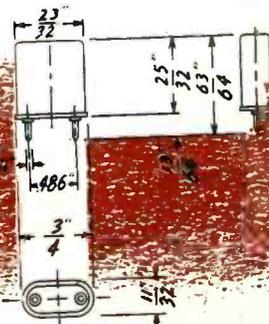

BLILEY ELECTRIC COMPANY • UNION STATION BUILDING, ERIE, PENNSYLVANIA  
October, 1947

# Leo's 275 watt XMTR Kit


Get on the air with Leo's 275 Watt sensation of the year available on Easy Pay plan. And remember, Leo offers you more for your transmitter or receiver—in many cases it will be enough for the down payment. Complete with all parts, tubes, meters, cabinets, one-set of coils.

**KIT FORM WIRED \$376.45**  
**\$351.45 AS LOW AS \$70**  
 down


Write for prices of individual sections.




A

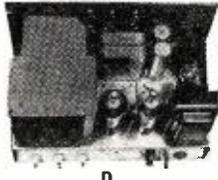

B

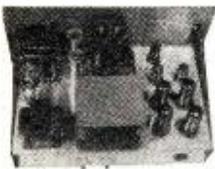

C

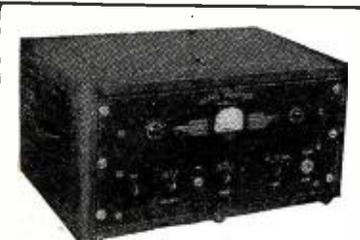

**W.R.L. Globe Trotter XMTR Kits**  
 Amateurs the nation over are praising the performance of this high quality low cost rig. It's a 40 watt input kit including all parts, chassis, panel and streamlined cabinet. Write for export prices.  
 Cat. No. 70-300 Less tubes... **\$69.95**  
 Cat. No. 70-312 Same as above  
 wired..... **\$79.50**  
 1 set coils, meters, tubes, extra... **17.15**

FOR ANYTHING IN RADIO—  
 YOU'LL GET THE BEST DEAL  
 FROM LEO, WOGFO



Immediate Delivery



## Compare These Features With Any Kit

A versatile, advanced design transmitter kit that will give you efficient performance on 8, 10, 20, 40, and 80 meter bands on phone & C.W. Available in complete kit form or in individual sections. There's nothing like it on the market for quality, features, and price.

**A—RF Exciter Section**—Here is one of the most efficient exciter driver units available. Capable of 40 watts input on all bands including 8 meters. 8 meter output from 2E26 tube obtained by using crystal frequencies from 8335 to 9000 KC. 40 meter crystals do a F.B. job for the 10 and 20 meter bands. 7C5 regenerative type crystal oscillator, with provisions for ECO, driving the new 2E26, giving high efficiency on all bands. Voltage regulation is provided for oscillator tubes and screen of 2E26 offering high stability to both stages. Tube line-up: 7C5 oscillator; 2E26 buffer relay rack panel when used with Final RF section. Chassis size 7"x12"x3". Uses 8 3/4"x19" relay rack panel when used with Exciter Section. Weight 10 lbs.

**B—Final RF Section**—Another brand new feature never before used in transmitters is a front panel Coupl-Trol that controls the amount of coupling of the antenna to the final amplifier. The latest in easy to drive triodes, the V70D's are used in the final amplifier. Designed for the shortest RF leads and used to eliminate the presence of parasites and self-oscillation. Tube line-up: two V70D's. Chassis size: 10"x12"x3". Utilizes 8 3/4"x19" relay rack panel when used with exciter section. Weight 16 lbs.

**C—Speech Amplifier and Modulator Section**—The latest in circuit design and the use of zero bias on the four 6L6's gives more power than ever before with very low static plate current. The use of resistance coupling up to 8P8 driver gives excellent reproduction of audio frequencies, and incorporation of a high quality audio transformer from the 6P8 to the 6L6's gives more efficiency and better matching between stages. Power consumption is cut down and heat dissipation is held to a minimum by this improved circuit design. Plate voltages are relay controlled for ease of operation. This new speech amplifier and modulator is capable of modulating inputs from 300 to 350 watts. Tube line-up: 6SJ7; 6C5; 6P8; four 6L6's and 83 rectifiers. Load: 450 volts at 250 amps. Chassis size: 12"x17"x3". Utilizes 8 3/4"x19" relay rack panel. Net weight 48 1/2 lbs.

**D—Dual Power Supply Section**—Tube line-up: 5Z3; two 866A's. Load: 800 volts at 200 amps, and 1150 volts at 300 amps. Chassis size: 12"x17"x3". Utilizes 8 3/4"x19" relay rack panel. Net weight 38 lbs.

Part No.  
 B84181  
 B83224  
 B84270

43X214  
 C83152  
 B66102  
 17A152

14A148  
 46X289  
 17A174

47X463  
 47X466  
 17A234

B66104  
 B66403

47X446  
 47X476  
 B66502

47X467  
 B66103

B64253  
 45X342

D66204  
 D66104  
 9A1443

9A1818 or 9A1792  
 9A1444

9A1442

9A1793  
 9A1894  
 51X118

Code and Description  
 R<sub>15</sub>—180 ohm, 1/2 w. res.  
 R<sub>10</sub>—220,000 ohm, 1/2 w. res.  
 R<sub>17</sub>—775 ohm, 28 w. wire-wound res.  
 R<sub>18</sub>—27 ohm, 1/2 w. res.  
 R<sub>19</sub>—1500 ohm, 1 w. res.  
 C<sub>1</sub>—0.01 μfd., 200 v. cond.  
 C<sub>2</sub>, C<sub>3</sub>—2-25 μfd. ant. & osc. trimmer  
 C<sub>3A</sub>, C<sub>3B</sub>—Gang cond.  
 C<sub>4</sub>—0.0475 μfd., 180 v. cond.  
 C<sub>5</sub>—2-25 μfd. osc. trimmer  
 C<sub>6</sub>—Part of C<sub>3</sub>  
 C<sub>7</sub>—47 μfd. mica cond.  
 C<sub>8</sub>—68 μfd. mica cond.  
 C<sub>10</sub>—250-525 μfd., 600 kc. padder  
 C<sub>11</sub>, C<sub>12</sub>—1 μfd., 200 v. cond.  
 C<sub>13</sub>, C<sub>14</sub>, C<sub>15</sub>—0.4 μfd., 200 v. cond.  
 C<sub>16</sub>, C<sub>17</sub>—Part of T<sub>5</sub>  
 C<sub>18</sub>, C<sub>19</sub>—47 μfd. mica cond.  
 C<sub>17</sub>, C<sub>18</sub>—Part of T<sub>8</sub>  
 C<sub>19</sub>—100 μfd. mica cond.  
 C<sub>20</sub>—0.05 μfd., 200 v. cond.  
 C<sub>21</sub>—470 μfd. mica cond.  
 C<sub>23</sub>, C<sub>25</sub>—0.1 μfd., 200 v. cond.  
 C<sub>20</sub>—0.25 μfd., 200 v. cond.  
 C<sub>21A</sub>, C<sub>21B</sub>, C<sub>21C</sub>—50/50/20 μfd., 150/150/25 v. elec. cond.  
 C<sub>20</sub>—2 μfd., 400 v. cond.  
 C<sub>20</sub>—1 μfd., 400 v. cond.  
 T<sub>1</sub>—"D" range ant. coil assembly  
 T<sub>2</sub>—"B" band loop ant.  
 T<sub>3</sub>—"D" range osc. coil assembly  
 T<sub>4</sub>—"B" band osc. coil assembly  
 T<sub>5</sub>—First i.f. trans.  
 T<sub>6</sub>—Second i.f. trans.  
 T<sub>7</sub>—Output trans.

—30—

## LONG DROP

WORD has recently been received by the engineers of General Electric Company's Tube Division that an electronic tube that fell 10,000 feet from a Flying Fortress survived to power a radio transmitter.

The electronic tube's descent, following an attack by the Luftwaffe on a formation of Flying Fortresses in 1943, was described in a letter received by the company from A. A. Bliek, Enschede, Netherlands who reported that the tube is still functioning.

During the battle several airplanes exploded and shortly thereafter a package fell to the earth. Upon examination, it was discovered that the package contained a GL-211, a standard transmitting tube, and that no damage had been done to the filament or other elements. The tube is now in operation in V.E.R.O.N.'s (a Netherlands radio amateur group) transmitter.

According to the company engineers, the fall is remarkable in view of the fact that the filament of the tube is made of thoriated-tungsten, an extremely brittle substance, and its envelope is glass.

—30—

**FREE**

World Radio Laboratories  
 Department R-10  
 Council Bluffs, Iowa

Send latest Free Flyer  
 Send more data on 275 Watt XMTR  
 Send data on the Globe Trotter XMTR  
 Send data on your Good Surplus

Send more data on.....

Name.....  
 Address.....  
 City.....  
 Zone..... State.....

Call letters.....

**LEARN TELEVISION ELECTRONICS RADIO**

Modern Completely Equipped Laboratories

DAY AND EVENING CLASSES  
 G.I. Approved—Veterans Receive Subsistence

ENROLL NOW!  
**ELECTRONICS INSTITUTE, INC.**  
 21 Henry, Detroit 1, Mich.

Now! **VIBRATORS \$1.00**

GUARANTEED FACTORY REBUILD


SEND OLD VIBRATORS. ANY MAKE OR KIND OF VIBRATOR REBUILD LIKE NEW. NON-SYNCHRONOUS—REBUILD FOR \$1.00. SYNCHRONOUS TYPE—REBUILD FOR \$1.50.


48 HOUR SERVICE  
 RUSH OLD VIBRATORS TO  
**BEST VIBRATOR CO.**

COD ORDERS ACCEPTED BOX 5802—CLEVELAND 1, OHIO

**LCETI**

"SEE PAGE 10"

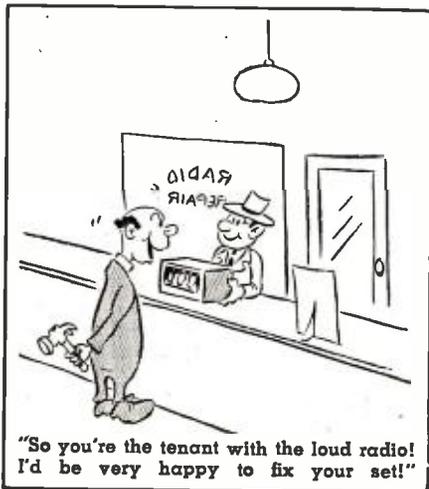

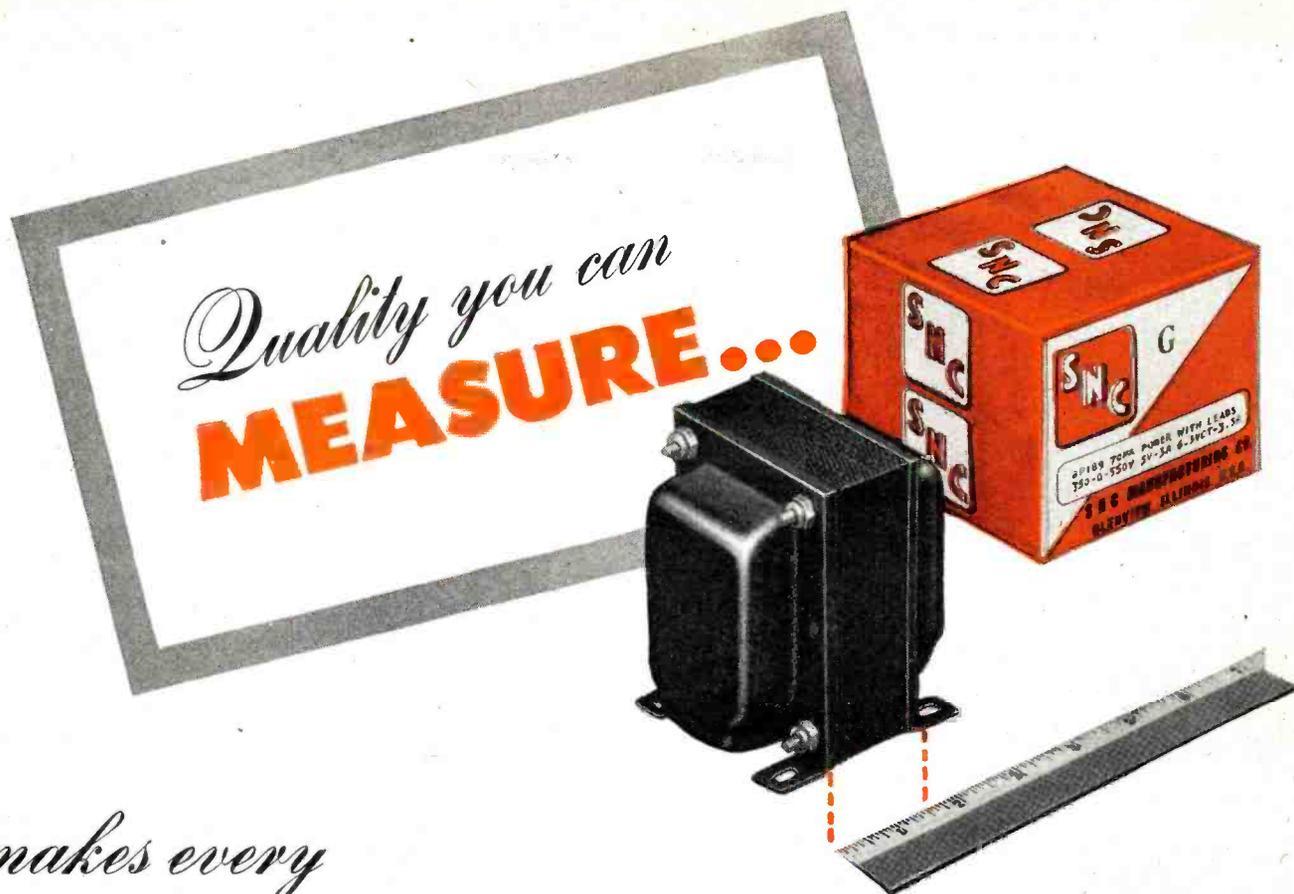

*makes every*  
**SNC TRANSFORMER** *give outstanding performance*



Join the increasingly large number of manufacturers, retailers, hams and other component part buyers who rely on SNC for quality, trouble-free equipment. Write for catalog today.


Place a rule against the stack of an SNC No. 8P189 transformer and the *extra* width clearly indicates the added quality built into every item in the complete SNC line.

Skillful engineering, latest production techniques and highest quality materials . . . backed by careful workmanship, exacting step-by-step inspection and rigorous final testing . . . are just a few of the reasons why SNC transformers keep rejects at a minimum and give outstanding performance.

**Remember! SNC gives MORE applications with  
 SMALLER inventories for GREATER profits!**

**SNC MANUFACTURING CO., INC.**  
*Quality Transformers*  
 WEST LAKE AVE. NEAR LEHIGH • GLENVIEW, ILLINOIS
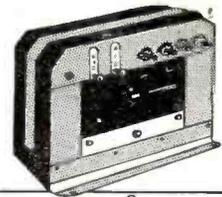
# HERSHEL offers extra discount in celebration



**Brand New Automatic Direction Finder RADIO COMPASS**  
 SCR-269 F  
 COMPLETE WITH COMPONENT PARTS  
**\$75.00** NO. OT-100

The radio compass SCR-269-F was designed to be the primary radio navigation compass for the United States Army and Navy Air Forces. Constant reception is possible day or night so that fixes can always be made to establish the plane's or ship's location.

Plotting fixes is accomplished by selecting two or more stations and plotting these on the navigation map. The point of intersection of these lines indicates the location of the craft.

This equipment comes complete with 17 tubes superheterodyne receiver which is tunable from 200-1750 KC in three bands. A complete instruction book for operation and maintenance accompanies this equipment.

**NEW BC-223 AX TRANSMITTER**  
**\$14.95** NO. OT-109

Complete with tubes and tuning unit covering 80 meter Ham band, including frequencies charts, less Xtals.

**BK22K Relay**  
**\$2.95** NO. OT-110

Used in conjunction with SCR269F, changeover contains 29V, step relay, 5 deck, 6 position switch. 12V D.P.S.T.

**IKW MODULATION TRANSFORMER**  
**\$14.95** NO. OT-111

RCA Mod. Trans. conservatively rated at 550 Watt audio to modulate that new KW rig. Audio Watts—550 Sec. 1—430 Mils Sec. 2—80 Mils Turns Ratio—Pri. Sec. 7:1:1 Pri. Sec. 12 Top—25:1 Impedance Ratio—Pri. 1:1:1 Sec. Pri. Sec. 7:2:5:1 Pri. Sec. 2 Top—25:1. DC Resistance—Pri. 125 ohms Sec. 1, 112 ohms Sec. 2, 99 ohms. Transformer insulation tested. Pri. 6000 V<sub>a</sub> Sec. 1-11-000V<sub>a</sub> Sec. 2-2000V<sub>a</sub>. In the rest of the coils and core. Primary center-tapped for Class "B" modulators. Secondary #2 will carry 80 Mill to modulate screens of beam power or screen grid tubes. Primary will match any Class "AB" tubes up to 10,000 ohms plate to plate, such as 810's, 751's, 805's, 2B 150's, 202's, HFS12's, 813's, 828's, 805's, 2032's. Size 9 1/2" wide, 7 1/2" deep, 7 1/2" high. Heavy channel iron mounting bracket. Weight approx. 40 lbs.

**EXTRA SPECIAL! R.L.T. Tube Tester**  
**\$39.95** NO. OT-108


Tests all tubes up to 117 V  
 Tests shorts and leakages  
 Tests individual sections  
 Works on 90-125 V 60 cycle AC  
 Comes in portable cabinet complete with all operating instructions.

**BUY FROM HERSHEL & SAVE!**

**CORONA BALLS**  
 Grid and plate connections for VT 127-230 TH etc. Round Ball type heat dissipating silver plated.  
**10¢** 100 Doz.

**VARIABLE CONDENSER**  
 6 Gang silver plated, Sec. 1: 350 M.M.F.D., Sec. 2: 3, 4, 5, 60 M.M.F.D., Sec. 6: 80 M.M.F.D. NO. OT-101  
**89¢**

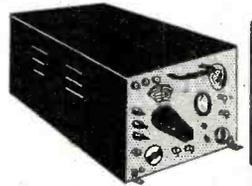**SQUIRREL CAGE BLOWER**  
 2" outlet, 110AC, 60cy Silent Ball Bearing Motor, with mounting bracket NO. OT-164  
**\$7.95**



**ARR7 Air Borne VERSION OF HALLCRAFTERS SX28A**  
**129.00** NO. OT-112

With 3 RF stages (one re-radiation suppressor), 12 tubes. Motor and manual tuning. X-meter, F-selectivity control, crystal filter, AVC, phasing control, AM, etc. Also furnishes video output for scope, and panoramic output for scanning. Complete with tubes and Xtl, but without power supply. Power requirements: 270v, at 135 ma. New, in sealed case.



**IF TRANSFORMER**  
 mounted in aluminum shield can, 1500 KC, with air trimmer, impedance coupled type. NO. OT-115  
**95¢**



**FILAMENT TRANSFORMERS**  
 110-V, 60 cy. Pri. sec.—5V—\$1.49 NO. OT-163  
 3A. Shelled Case.  
 110-V, 60 cy. Sec.: 2.5V at 5.25 amps. Shelled Case... \$2.45 NO. OT-162  
 110-V, 60 cy. Sec.: 1, 5V at 10 amps.; Sec.: 2, 5V at 10 amps.; Connected in series will give 10V at 10 amps. Shelled Case... \$3.95 NO. OT-166

**SECONDARY FREQUENCY STANDARD**  
**\$29.50** NO. OT-107


Complete with spare tubes 1000 KC to 45,000 KC. 1000—100—10K KC  
 Check points. 100 to 250 V., 25-60 cycles.

**FREQUENCY METER BC-439**  
**\$24.50** NO. OT-113

Xtal controlled check points. Frequency range 100 MC—120 MC, including 5 tubes and Xtals. Operates from 110 V, 60 Cy supply. Ideal precision instrument for high frequency measurement. Used, in good condition.

**BN IFF TRANSMITTER & RECEIVER**  
**\$9.95** NO. OT-102

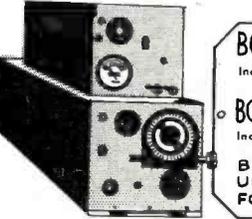Widely used on 144MC and now also successfully used as a television receiver, this being made possible by the wide band 30 MC I.F. channel and video amplifier: being sold at this exceptionally low price for the encouragement of television. Original diagram furnished. Less tubes and power transformer, wt. 100 lbs.



**BC-AR230 Transmitter**  
 Including 4 tubes and RF Amps. meter.  
**BC-AL229 Receiver**  
 Including 6 tubes. Used in aircraft.  
**BOTH UNITS FOR ONLY \$9.95** NO. OT-105



**BC-654-A PORTABLE RECEIVER-TRANSMITTER**  
**\$12.50** NO. OT-114

The frequency range of both transmitter and receiver is continuous from 3700 to 5800 Kilocycles; all stages gang tuned by anti-back lash worm gear drive mechanisms. The BC-654-A is 18" wide, 14" high, and 9 1/2" deep. Weight 4 1/2 pounds. Power required for Receiver—1.5, 4.5, and 90 volts D.C. Power required for Transmitter—1 1/2, 6, 51, 84 volts D.C. and 500 volts D.C. at 160 Ma. Operates from Dynastator PE-103-A. Complete with carrying case.

**CERAMIC INSULATORS**  
**\$1.00** NO. OT-103  
 HIGH VOLTAGE FEED THRU

**Scope Transformer**  
**\$3.95** NO. OT-104  
 110V Pri: 60 cy, Sec: 4000 ✓ at 10MA. Size 6 x 4 x 3 1/2


**Shalcross AKRA-OHM WIRE WOUND**  
 ±1%  
**1 MEG 89¢** NO. OT-165

**SOCKETS FOR ACORN TUBES..** NO. OT-117... \$ .19  
**POWDERED IRON 3/8 SLUG...** NO. OT-118... .10  
**JACKS-PL55, PL68...** NO. OT-119... .15  
**ASST. MICA CONDENSER. per 100...** NO. OT-120... 1.95  
**3 LBS. ASST. HARDWARE...** NO. OT-121... 1.00  
**PIN STRAIGHTENER for min. tubes...** NO. OT-122... .49  
**VARIAC 1AMP.** NO. OT-123... 3.95  
**EAR PHONES, 2000 OHMS, used...** NO. OT-124... .95  
**JOHNSON SOCKETS #210-25W...** NO. OT-125... .39  
**5V FILAMENT TRANS. 60AMP...** NO. OT-126... 5.95  
**SCR 625 MINE DETECTOR...** NO. OT-127... 49.50

**HERSHEL RADIO CO.**  
 5249 GRAND RIVER AVE. DETROIT 8, MICH.  
 All Orders F.O.B. Detroit—Minimum order \$2.00—Mich. Customers add 3% tax.
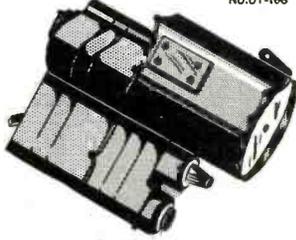
# of 35 Years in RADIO ELECTRONIC FIELD!

MICA CAPACITATOR **49¢**  
 .002MFD, 3000 VDC  
 NO. OT-166




**SNIPERSCOPE  
 INFRA-RED DETECTOR**  
**\$100.00**  
 NO. OT-133

This sensational sniperscope that was so widely used in World War II, to combat the enemy in night warfare, is now, for the first time, being released. This unit comes complete and ready to operate from 110V, A.C. or D.C. source—this being made possible by the use of the following tubes: 1G54—117N7—1P25 image tube. Rubberized carrying case included.



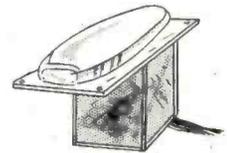**COPPERWELD  
 #18 WIRE**  
 3000 FEET **\$2.95**  
 NO. OT-155




**HIGH SPEED PHOTO  
 FLASH TUBE**  
**\$8.95**  
 NO. OT-156

12,000,000 lumens light output. Stops all action. Ignition coil included on back of bulb. 10,000 flashes. Diagrams furnished.

**PYRANOL  
 CAPACITATOR**  
**\$2.95**  
 NO. OT-132  
 General Elect. 1 MFD,  
 5,000 VDC, 4" x 4 1/2" x  
 3 3/4".



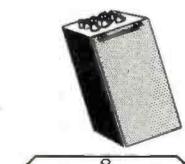
**POWER  
 TRANSFORMER**  
**\$1.95**  
 NO. OT-134



**POWER  
 TRANSFORMER**  
**\$1.95**  
 NO. OT-144



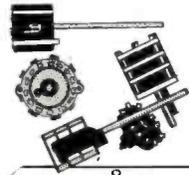**POWER  
 TRANSFORMER**  
**\$1.95**  
 NO. OT-145



**ROTARY TAP  
 SWITCHES**  
 KIT OF  
 6 SWITCHES **\$1.85**  
 NO. OT-154

**BUTTERFLY  
 CONDENSERS**  
 Oscillator assembly 76 to 300  
 MC with screw tube socket  
 mounted on condenser. **1.95**  
 Type B—frequency range  
 300 to 1000 megacycles. **95¢**  
 BC4 antenna condenser.  
 105-330 MC. **1.95**  
 Oscillator 105-330 MC. **1.95**

**LIP MIKE**  
 WITH  
 HEAD BAND  
 AND  
 CORD **95¢**  
 NO. OT-131

**1 POUND  
 SOLDER**  
 60/40  
 ROSIN  
 CORE **50¢**  
 NO. OT-135

**COMPLETE HALLICRAFTER  
 KNOB SET** **95¢**  
 FOR SX28 NO. OT-143

**RESONANCE  
 INDICATOR**  
 with neon  
 bulb and  
 alligator  
 clip. **19¢**  
 NO. OT-146

**POWER  
 TRANS.**  
 110V, 60 Cy. Pri. Sec. 255V  
 ea. side of center at 80 Ma, 5  
 5V at 4 Amps, 6.3V at 3.8  
 Amps. Hermetically sealed  
 case. **1.29**  
 NO. OT-153

**30 MC IF  
 TRANSFORMER**  
**29¢**  
 NO. OT-157  
 SLUGGED TUNE

**250 MFD  
 AT 10V.**  
 ROUND CAN  
 7/8 x 2" **14¢**  
 NO. OT-130

**MATCHING  
 TRANSFORMER**  
**69¢**  
 NO. OT-136  
 500 Ohms to grid, hermetically sealed.

**THORARSON  
 CHOKE**  
**\$1.85**  
 NO. OT-152  
 at 200MA. Shell cased.

**OVERLOAD  
 RELAYS**  
**\$1.95**  
 NO. OT-161  
 Potter and Brumfield, Relay  
 #1, 5,000 Ohms, Coil Current  
 10 MA., Relay #2,  
 110V, 60 Cy, AC coil  
 S.P.D.T.

**GENERAL ELECTRIC  
 METER**  
**\$3.95**  
 NO. OT-158  
 type D041, 0-1  
 MA, meter scale  
 graduation 0-5  
 D.C. Kilo V and  
 0-10 MA D.C.

**SHORTING  
 TYPE**  
 INTERLOCKING  
 MALE AND  
 FEMALE **12¢**  
 NO. OT-139

**DISCHARGE  
 RESISTOR**  
**95¢**  
 NO. OT-138  
 General elect. type  
 type 31, 120 V, A.C. or  
 D.C.

**ELECTROLYTIC  
 Condenser**  
**95¢**  
 NO. OT-137  
 8.8 MFD., 450  
 W.V.D.C. inverted  
 type screw metal  
 round aluminum  
 can.

**IRC TYPE HE**  
**49¢**  
 NO. OT-147  
 100W, bleeder consisting of  
 5 sections 750 Ohms, 23  
 Ohms, 23 Ohms, 7,500  
 Ohms, 3,000 Ohms. Total  
 11,296 Ohms.

**TOGGLE  
 SWITCH**  
**39¢**  
 NO. OT-151  
 D.P.D.T. 30 Amps, in  
 black bakelite case.

**T17 CARBON  
 MICROPHONE**  
**89¢**  
 NO. OT-160  
 LIKE NEW

**VARIABLE  
 RESISTOR**  
**49¢**  
 NO. OT-142  
 100  
 WT

**TUBES**  
 813 .595 872A 1.95  
 VR150 .69 9004 .65  
 955 .65 9006 .89  
 9002 .89 50B5 .89  
 6J6 .93 829 2.95  
 RK60 .95 VT127A 2.95  
 9001 .89 35W4 .69  
 6J4 1.50 3AP1 2.95  
 5FP7 2.95 3BP1 2.95  
 78P7 3.95 6J5 .49  
 91P7 4.95 5BP1 3.95  
 6N7 .89 6H6 .59  
 114 — 3Q4—6SN7 .59  
 354—5W4  
 65A7—5U4 **59¢** ea.  
 12M6—1G5 **65¢** c  
 6SH7

**PAPER  
 COND.**  
**9¢**  
 NO. OT-138  
 .05-.05-.05, 300  
 VDC, in round  
 can. Approx. 1"  
 x 1"

**Transformer**  
**95¢**  
 NO. OT-148  
 Audio sec. transformer with output  
 and feedback winding.

**5 GANG VARIABLE  
 CONDENSER**  
**\$1.95**  
 NO. OT-149  
 5 Gang, approx. .50  
 M.M.F.D. per section  
 with individual  
 air-tuned padders  
 18 to 1 vernier  
 drive.

**CHASSIS**  
**\$1.95**  
 NO. OT-150  
 containing: 110 AC relay,  
 3 miniature sockets with  
 tube shields, 5 condensers  
 and 6 res. 3" x 5" x 1".

**COLLINS FILTER  
 CHOKE**  
**1.69**  
 NO. OT-159  
 8 HT, 150 MA, D.C.  
 res 100 Ohms, Tot  
 V 2500.

**VOLTAGE  
 REGULATOR**  
**95¢**  
 NO. OT-141  
 Carbon pile, magnetic  
 type, coil current, 103  
 Ma. Load Max 5 Amps at  
 125V.

**ELECTROLYTIC  
 Condenser**  
**39¢**  
 NO. OT-140  
 30MFD, 100 W.V.D.C.,  
 round aluminum can,  
 plug-in type. Fits any  
 oval socket.

**6MH-300MA**  
**19¢**  
 NO. OT-139  
 Pie wound on ceramic  
 form.

**THORARSON  
 CHOKE**  
**\$1.85**  
 NO. OT-152  
 at 200MA. Shell cased.

**OVERLOAD  
 RELAYS**  
**\$1.95**  
 NO. OT-161  
 Potter and Brumfield, Relay  
 #1, 5,000 Ohms, Coil Current  
 10 MA., Relay #2,  
 110V, 60 Cy, AC coil  
 S.P.D.T.

**GENERAL ELECTRIC  
 METER**  
**\$3.95**  
 NO. OT-158  
 type D041, 0-1  
 MA, meter scale  
 graduation 0-5  
 D.C. Kilo V and  
 0-10 MA D.C.

**TUBES**  
 813 .595 872A 1.95  
 VR150 .69 9004 .65  
 955 .65 9006 .89  
 9002 .89 50B5 .89  
 6J6 .93 829 2.95  
 RK60 .95 VT127A 2.95  
 9001 .89 35W4 .69  
 6J4 1.50 3AP1 2.95  
 5FP7 2.95 3BP1 2.95  
 78P7 3.95 6J5 .49  
 91P7 4.95 5BP1 3.95  
 6N7 .89 6H6 .59  
 114 — 3Q4—6SN7 .59  
 354—5W4  
 65A7—5U4 **59¢** ea.  
 12M6—1G5 **65¢** c  
 6SH7

**PAPER  
 COND.**  
**9¢**  
 NO. OT-138  
 .05-.05-.05, 300  
 VDC, in round  
 can. Approx. 1"  
 x 1"

**Transformer**  
**95¢**  
 NO. OT-148  
 Audio sec. transformer with output  
 and feedback winding.

**5 GANG VARIABLE  
 CONDENSER**  
**\$1.95**  
 NO. OT-149  
 5 Gang, approx. .50  
 M.M.F.D. per section  
 with individual  
 air-tuned padders  
 18 to 1 vernier  
 drive.

**CHASSIS**  
**\$1.95**  
 NO. OT-150  
 containing: 110 AC relay,  
 3 miniature sockets with  
 tube shields, 5 condensers  
 and 6 res. 3" x 5" x 1".

**COLLINS FILTER  
 CHOKE**  
**1.69**  
 NO. OT-159  
 8 HT, 150 MA, D.C.  
 res 100 Ohms, Tot  
 V 2500.

**HERSHEL RADIO Co.**  
 5249 GRAND RIVER AVE. DETROIT 8, MICH.  
 All Orders F.O.B. Detroit—Minimum order \$2.00—Mich. Customers add 3% tax.

**HERSHEL RADIO Co.** 3249 Grand River Avenue  
 DETROIT 8, MICHIGAN

"Please send me your latest free bulletin on hundreds of  
 electronic bargains."

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

*Whatever You Need  
You'll Find it at Resco!*

**CONDENSER SPECIALS**



First quality, guaranteed electrolytic condensers. Place your order immediately—quantities limited. Compare these rock-bottom prices. Buy 10 of a type or an assortment of 10 and save still more.

10 mfd	25 V	.29	10 for 2.60
20 mfd	150 V	.35	10 for 3.15
40 mfd	150 V	.39	10 for 3.50
8 mfd	450 V	.35	10 for 3.15
16 mfd	450 V	.54	10 for 4.90
20x20	150 V	.52	10 for 4.70
50x30	150 V	.65	10 for 5.85

**VOLUME CONTROLS**



Another RESCO super special from our Bargain Basement. First quality, guaranteed volume controls. Complete with hardware. Get 10 of a type or an assortment of 10 & save still more.

Tapped with switch.	55c	10 for 5.50
No tap with switch	55c	10 for 5.00
Tapped no switch	50c	10 for 4.50

Available at these low prices in 1/2 meg, 1 meg, 1 meg, and 2 meg values. Just specify your assortment.

**ANTENEX INDOOR AERIAL**  
No outdoor aerial needed. Perfect reception. **Only 60c**

**PM Speaker Specials**

Size	Alnico 5 Magnet	Wt. (oz.)	Price
3"	1	1	1.40
4"	1	1	1.45
5"	1	1	1.49
6"	1	1	1.79

**Broadcast Band Loop**

Has primary winding for outdoor antenna and instructions for adjusting inductance of secondary for matching to tuning condenser and oscillator coil. 50c

**Miracle Adhesive**

Sticks fast wet or dry, hot or cold. Use it on almost anything, including metal, glass, plastics, tile, plaster, mirrors, etc.

Ctn. of 24 tubes 3.60 **15c TUBE**

**Special! 2-Gang Superhet TUNING CONDENSER**

Oscillator section 220 MMFD. RF section 420 MMFD. Trimmer condensers 3 to 30 MMFD attached to both sections. Screw adjustment for centering rotor. 1 3/4" x 1 3/4" x 2 1/4". Shaft 1/2" long, 1/4" OD. Front or bottom holes for mounting—79c. 10 for 7.00

Write for Big, Value-Packed Bulletin. Include Postage with Cash Orders.

**Radio Electric SERVICE CO. OF PENNA., INC.**

7TH AND ARCH STREETS, PHILA. 6, PENNA.  
Branches: 5133 Market St. and 3145 N. Broad St. in Phila.  
Also in Wilmington, Del., Easton, Pa., Allentown, Pa., Camden, N. J.

# Successful Retail Operation Features Personalized Service

"PEOPLE are music-hungry. I believe the retailing of radios, phonograph combinations, records, and appliances will be a bigger business than we ever thought possible."

The speaker is Helen Gunnis, owner of one of Milwaukee's most successful music specialty shops. The influence of twenty-five years in the radio and appliance field is evident in the casual, intimate atmosphere of her shop at 765 North Broadway.

Pale green walls, deeper green record cases and counters, six soundproof blonde wood record booths, with built-in red leather seats, and informally placed chairs and tables make up the furnishings of the first floor. On the mezzanine, there are four soundproof display parlors, for the sale of radios and radio-phonograph combinations. Fluorescent lighting is used throughout.

Special merchandising campaigns and a new window display every week stimulate interest with both the old and new customers.

"We try to keep the atmosphere informal at all times. Our customers are never urged to make a purchase. And a clerk never approaches a buyer until he indicates that he would like some help. People are free to come and go, and to examine any of the instruments or record albums we have on display.

"I think it is well for every music dealer to specialize in some phase of the radio accessory field, as well as merely selling the instruments. For example, our shop is known as the best source of classical record albums in Milwaukee. Thus our customers depend upon us not only when they buy their instruments, but afterward, when they want new records."

Three salespeople, besides Miss Gunnis, and her sister and business manager, Miss Estelle Gunnis, make up the sales staff of the shop. All have some musical education and a thorough

working knowledge of radios and phonographs. "We believe you cannot sell people music, unless you know music."

The first dealer in the country to use the "self-service" system in selling phonograph records, Miss Gunnis still believes that method is the most successful. "We let the buyer browse, make his selections and try them at his leisure. Of course, here we do not have the one great problem that department stores or very large shops have. Our records are never stolen. The personal contact we have with our customers eliminates this possibility."


Among the services that the shop offers its customers is that of making up libraries of records. "Trying to give them well-balanced selections of the better music is not a simple job. It involves much paper work before I can even decide what to choose. Take this job I just completed recently. A man from upstate sent me a letter saying that he wished to increase his music library by buying \$300 worth of classical albums. He enclosed a list of those he already had, and wanted me to select the rest. That meant making out a large chart so that he got a proportioned, well-balanced selection of the best in the classical field available today. I enjoy this sort of work however, and find that it always brings other customers in for advice, not only in selecting their library albums, but often in buying their instruments as well."

Gunnis Music Shop advertisements appear in the local daily newspapers and other periodicals. However, the greater part of the shop's advertising appears in concert and theatrical programs. "After all, we try to serve a certain group in the buying public, and it is only logical to advertise where they will read. We find our program insertions are always quite successful. But then, that is only advertising. It is being able to serve our customers satisfactorily that is our main concern." —30—

A restful, unhurried atmosphere makes this record store a pleasant place to shop.



this is the house . . . . .

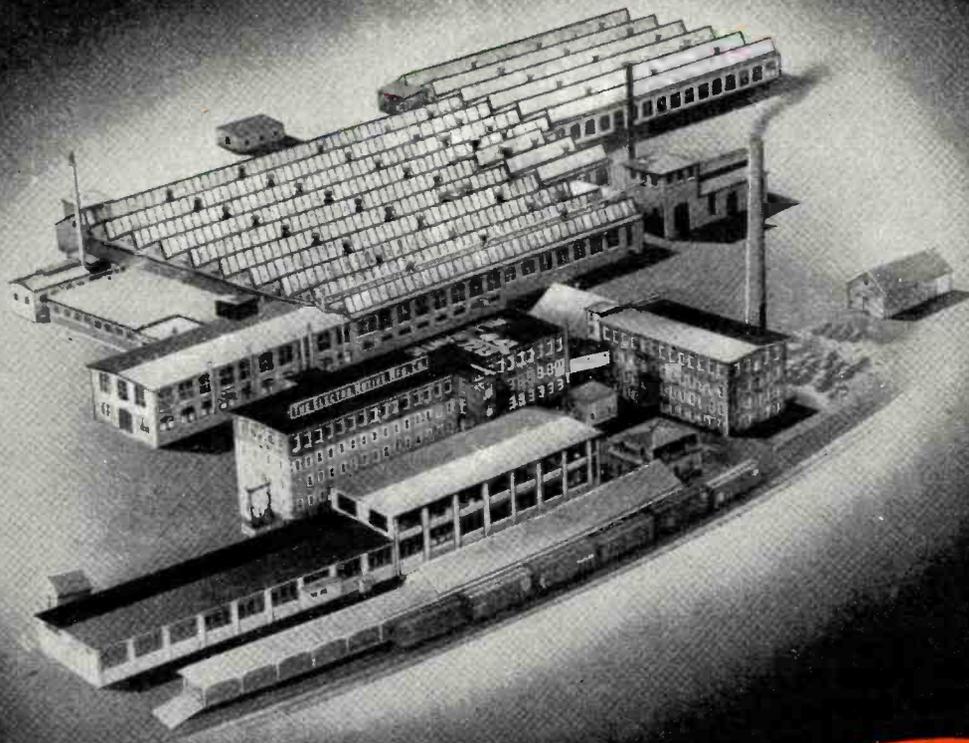

. . . that El-Menco built!

Size is not necessarily a sign of greatness. But when size is the result of consistently steady growth, based on an ever-widening demand for a product, then it is truly indicative of outstanding quality.

Year after year, in more and more instances, El-Menco Capacitors become first choice with manufacturers who are proud of their products.

Send for samples and complete specifications.

Foreign Radio and Electronic Manufacturers communicate direct with our Export Department at Willimantic, Conn., for information.

**THE ELECTRO MOTIVE MFG. CO., Inc., Willimantic, Conn.**



Write on firm letterhead for samples and catalog.




**MOLDED MICA**

# El-Menco CAPACITORS

**MICA TRIMMER**

October, 1947

105

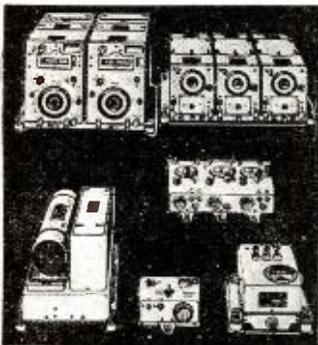


**SCR-274N COMMAND SET**

The greatest radio equipment value in history.

A mountain of valuable equipment that includes 3 receivers covering 190 to 550 KC; 3 to 6 MC; and 6 to 9.1 MC. These receivers use plug-in coils, and consequently can be changed to any frequencies desired without conversion. Also included are two Tuning Control Boxes; 1 Antenna Coupling Box; four 28 V. Dynamotors (easily converted to 110 V. operation); two 40-Watt Transmitters including crystals, Preamplifier and Modulator. 29 tubes supplied in all. Only a limited quantity available, so get your order in fast. Removed from unused aircraft and in guaranteed electrical condition. A super value at \$29.95, including crank type tuning knobs for receivers.

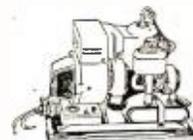**PE-109 32-VOLT DIRECT CURRENT POWER PLANT**

This power plant consists of a gasoline engine that is direct coupled to a 2000 watt 32 volt DC generator. This unit is ideal for use in locations that are not serviced by commercial power or to run many of the surplus items that require 28-32 V. D.C. for operation. The price of this power plant is only \$100. We can also supply a converter that will supply 110v AC from the above unit or from any 28-32v DC source for \$29.95.



**LORAN INDICATOR OSCILLOSCOPE**, complete with 26 tubes and a 5" cathode ray tube, government instruction manual included—\$39.95.

**5" SO RADAR PPI OSCILLOSCOPE**, complete with 9 tubes. This unit contains magnetic deflection yokes and a Selsyn motor—\$39.95. **SO RADAR ECHO BOXES, THE PERFECT CALIBRATED CAVITY WAVEMETER—\$10.00.**

**Range Unit RT-1579** consists of a three stage high gain, high fidelity amplifier and a Helmholtz coil for manually introducing phase shift from 0° to 360°. The amplifier is cascade 6SJ7s driving a 6F6 in the output, also on the same chassis is the 110v 60 cycle power supply. The Helmholtz coil is rotated by a vernier drive mechanism which has a dial that contains 4000 ¼ inch divisions. Your cost—\$14.95.


**RAYTHEON VOLTAGE REGULATOR**, will maintain a constant 115 V AC at the load even though the input voltage varies from 95 to 130 volts. The regulation is ½ of 1% with a 75 watt load. Shipping weight 20 pounds. Your cost \$8.95.



**SCR-610 TRANSMITTER-RECEIVER** ready to operate on 10 meter phone by connecting it to 6, 12 or 24 VDC—\$49.95.

**Relay Box BC-616** contains 3 high speed DPDT DC relays, that may be used as keying relays, resistors and a 150 MFD condenser. The aluminum box, with cover, measures 5½x6½x2 inches. While this terrific bargain lasts—\$1.95.

**BC 221 FREQUENCY METERS** with calibrating Crystal and calibration charts. A precision frequency standard that is useful for innumerable applications for laboratory technician service man, amateur, and experimenter, at the give-away price of only \$39.95.

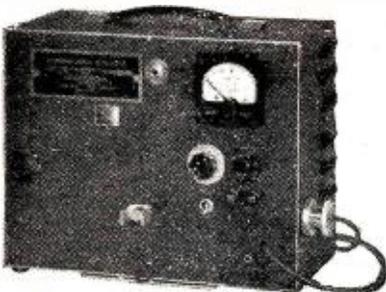

Model 78-B Standard Signal Generator. Two Frequency Bands between 15 and 250 megacycles.

**AT LAST YOU CAN AFFORD A LABORATORY STANDARD SIGNAL GENERATOR**

The famous Measurements Corp. Model 78B, 5 Tube Laboratory Standard Signal Generator (currently selling new, FOB Boonton, N. J., for \$310.00 net), is available in perfect condition for 25 to 60 cycle, 115 V AC operation. Until now this is the sort of top-flight lab equipment that discriminating buyers have only vainly hoped would be released at a bargain price. Worth every cent the manufacturer asks, but available FOB Buffalo while our limited supply lasts for only \$79.95.

"REMEMBER THAT A STANDARD IS ONLY AS RELIABLE AS ITS MAKER."

**INTRODUCTORY OFFERING OF OUR OWN BRAND CAR RADIO ANTENNAS**

All of our car radio antennas are made of triple plated Admiralty Brass Tubing, complete with low loss shielded antenna leads and have high quality fittings.

**SIDE COWL—BR-1**, 3 sections extend to 66". Your price—single units—\$1.50; in lots of 12—\$1.35 ea.

**SKYSCRAPER—BR-2** has 4 heavy duty sections that extend to 98". Your price—single units—\$2.45; in lots of 12—\$2.25 ea.

**TILT ANGLE—BR-3**, may be adjusted to all body contours. 3 sections extend to 66". Single unit price—\$1.50; 12 lot price—\$1.25 ea.

**VERSATILE—BR-4**, single hole fender or top cowl mounting may be adjusted to conform with all body contours. 4 sections extend to 56". Single unit price—\$2.90; 12 lot price—\$2.75 ea.

**THE MONARCH—BR-5**, single hole top cowl mounting. 3 sections extend to 56". Single unit price—\$1.90; 12 lot price—\$1.75 ea.

**HENDIX SCR 522—Very High Frequency Voice Transmitter-Receiver—100 to 156 MC.** This job was good enough for the Joint Command to make it standard equipment in everything that flew, even though each set cost the Gov't. \$2500.00. Crystal Controlled and Amplitude Modulated—HIGH TRANSMITTER OUTPUT and 3 Microvolt Receiver Sensitivity gave good communication up to 180 miles at high altitude. Receiver has ten tubes and transmitter has seven tubes, including two 832's. Furnished complete with 17 tubes, remote control unit, 4 crystals, 24 volt dynamotor and the special, wide band VHF antenna that was designed for this set. These sets have been removed from unused aircraft and are guaranteed to be in perfect condition. We include free parts and diagrams for the conversion to continuously variable frequency coverage in the receiver. The cost of this unit is only \$37.95. Brand new 12 volt dynamotor for SCR 522—\$12.00. Used SCR 522, less dynamotor, remote control unit and antenna—as-is—\$19.95.

Minimum order \$3.00 . . . All prices subject to change . . . 25% deposit with C.O.D. orders



BR1 BR2 ER3 BR4 BR5

**BUFFALO RADIO SUPPLY, 219-221 Genesee St., Dept. 10N, BUFFALO 3, N. Y.**  
CABLE ADDRESS BUFRAD

**SERVICEMEN**

Check This Column for Lowest Prices on Quality Parts

**TUBES:** all types in stock. 60% off on all tubes if ordered in lots of 10 or more.

**POWER TRANSFORMERS**—Half-shell type, 110V 60 cy. Centertapped HV winding. Specify either 2.5 or 6.3 filament when ordering.

For 4-5 tube sets—650V, 40MA, 5V & 2.5 or 6.3V.....\$1.49  
 For 5-6 tube sets—650V, 45MA, 5V & 2.5 or 6.3V..... 1.75  
 For 6-7 tube sets—675V, 50MA, 5V & 2.5 or 6.3V..... 1.90  
 For 7-8 tube sets—700V, 70MA, 5V & 6.3 or two 2.5..... 2.35  
 For 8-9 tube sets—700V-90MA; 5V-3A; 2.5V-3.5A; 2.5-10.5A..... 2.85  
 For 9-11 tube sets—700V, 100MA, 5V & 6.3 or 6.3V-4A..... 2.85  
 For 9-15 tube sets: 600V, 150MA; 5V & 6.3V..... 2.95

**TRANSFORMERS**—All types in stock. **AUTO-TRANSFORMERS:** Steps up 110v to 220v, or steps down 220v to 110v—\$1.95. **FIL. TRANS.:** 6.3v, 8 Amps.—\$1.98; 5v, 10 Amps.—\$1.98; Universal Output Trans. 8 Watt—89c; 18 Watt—\$1.29; 30 Watt—\$1.69. **AUDIO TRANSFORMERS:** S. Plate to S. Grid 3:1—79c; S. Plate to P.P. Grids—79c; Heavy Duty Class AB or B, P.P. inputs—\$1.49; Midget Output for AC-DC sets—69c; **MIKE TRANSFORMER** for T-17 Shure microphone, similar to UTC pincer type—\$2.00. Stator 22 or 25 ohm to line grid—\$1.95.

**CONDENSERS—PAPER TUBULAR** 600 WV.—001; .002; .005—8c; .01; .05—9c; .1—10c; .25—23c; .5—36c; **ELECTROLYTICS:** 8mfd 200v—20c; 10mfd 35v—20c; 30mfd 150v—23c; 20/20mfd 150—35c; 30/20 150v—46c; 50mfd 150v—43c; 8mfd 475v—34c; 16mfd 350v—55c; **OIL CONDENSERS:** 4mfd 600v—49c; **BATH TUB TYPE CONDENSERS:** 3X, 1mfd—20c. **RESISTORS:** All types in stock at the lowest prices: Resistor Kits—100 2 watt resistors—\$1.95.

**FILTER CHOKES:** 200, 300, 400, 500 ohm light duty—59c; 200 or 300 ohm heavy duty—99c; 250 ma 35 ohm, made for U.S. Navy, fully shielded—\$1.95; 75 ohm 125 ma—25c or \$4.25; "Melssner type" tapped filter chokes—25c; 8 amp. iron core A filter—79c; Choke-condenser combination, ideal to replace any size speaker field when installing PM speakers—79c.

**110 V. CIRCUIT BREAKERS** of Magnetic type: Following Current Ratings in Stock: 1.25, 3, 4, 8 Amps. Please Specify. \$1.95 each.

Seven Assorted I.F. Transformers—\$1.98; Five Ass'd. Oscillator Coils—69c.

**SPEAKERS—PM dynamic type—4"**—\$1.55; 5"—\$1.55; 6"—\$1.95; 8"—\$3.95; 10"—\$5.95; 12"—\$7.50.

**HEADPHONES**—Highest quality Signal Corps headsets with 12" cord and plug \$1.25. 5' rubber covered patchcords with phone plug & socket—45c.

**SELENIUM RECTIFIERS**—Dry disc type 1½" by 1" 1.2 Amp. maximum, suitable for converting DC relays to AC, for supplying filament source in portable radios, converting DC meters to AC applications, and also may be used in low current chargers—90c.

**METER RECTIFIERS**—Full wave, may be used for replacement, or in construction of all types of test equipment—\$1.25 Half Wave—90c.

**LINE FILTERS**—each unit contains two 2 mfd. oil filled condensers and a 15 amp. iron core choke. This filter has innumerable uses such as oil burner line filter, etc. A ten dollar value for 96c.

**WILLARD** rechargeable 2v storage batteries for portable radios or any other purpose—\$2.95.

**PUBLIC ADDRESS AMPLIFIERS**—25 watts peak output. This unit has separate input circuits for microphone and phono. The gain of the microphone circuit is 122 db. The phono circuit has a gain of 82 db. The frequency response is flat from 50 to 12000 cycles. A \$65 value for only \$32. Miniature pliers set contains one of each of the following: Needle nose, flat nose, patrol nose, standard nose. All contained in a leatherette case. Your cost—\$1.98.

**FLUORESCENT LIGHT BALLASTS**—Single 30 or 40 watt—\$1.68; Dual 40 watt—\$3.50.

**ATR battery eliminator.** Handy for servicing car radios or any other purpose requiring 6 or 12v at 14 amps. Net price—\$36.00.

**SOCKET WRENCH SET** consisting of 5 sockets ranging in size from 5/16 to 3/4 and 3 handles—79c.

**AUTOMATIC WIRE STRIPPERS** will strip up to 1000 wires per hour, a handy tool for any service job—\$3.52.

Six Foot Asbestos Insulated Flat Iron Cords, one end has a male plug, the other end has a standard flat iron socket. Your price—70c each or 10 for \$5.

**FREE THIS MONTH ONLY.**  
 A HIGH GRADE CRYSTAL PICK-UP WITH THE PURCHASE OF EACH PHONO MOTOR AT \$4.95.

**MICROPHONES**—All nationally known brands. Bullet crystal \$5.45; Bullet Dynamic—\$7.45; Mike Jr.—60c; Handy Mike—90c; Label Mike—93c; SHURE T-17 MIKES, with a u.s. to talk switch—99c.

**20 ASST'D COIL FORMS**, including 11 ceramic, 3 polystyrene, and 6 fiber. All useful sizes—50c.

**VARIABLE CONDENSERS:** 350 MMFD, 5 gang—\$1.95; 4 gang—\$1.49; 3 gang—83c; 2 gang—79c; 7.5 to 20 MMFD, 1750v spacing, extra long shaft Hammarlund—69c; miniature variable—25 MMFD—39c; 50 MMFD—49c; 75 MMFD—59c; 100 MMFD—69c; 140 MMFD—79c.

**TRANSFORMING RF CHOKES:** 1 PIE, 350 Ma.—25c or 3 for \$1.00.

**INTERRUPTION FREQUENCY COILS** for super-regenerative receivers or the tremendously popular FM adapters for stand. and broadcast sets. Iron core with a resonant frequency of 50 KC—39c; Air Core, 100 KC—29c.

**30 MC IF TRANSFORMERS** double slug tuned—25c.

**VIDEO AMPLIFIER PLATE COILS**—Slug Tuned—25c.

**REMOTE CONTROL UNIT:** Aluminum case 4x3x2" containing 2 potentiometers, triple pole switch, 4 knobs, gear mechanism, counter and phone jacks—59c.

**MODULATION TRANSFORMERS:** 30 watt, open type—\$1.95; 40 watt, cast aluminum case—\$2.95; Class "B" input transformers, cast aluminum case—\$1.95; Transceiver audio transformers—65c; Transceiver modulation transformers—65c.


**GENERAL ELECTRIC RT-1248 15-TUBE TRANSMITTER-RECEIVER**

**TERRIFIC POWER**—(20 watts) on any two instantly selected, easily pre-adjusted frequencies from 435 to 500 Mc. Transmitter uses 5 tubes including a Western Electric 316 A as final. Receiver uses 10 tubes including 955's, as first detector and oscillator, and 3 7H7's as IP's, with 4 slug-tuned 40 Mc. IF transformers, plus a 7H7, 7E6's and 7F7's. In addition unit contains 8 relays designed to operate any sort of external equipment when actuated by a received signal from a similar set elsewhere. Originally designed for 12 volt operation, power supply is not included, as it is a cinch for any amateur to connect this unit for 110V AC, using any supply capable of 400V DC at 135 MA. The ideal unit for use in mobile or stationary service in the Citizen's Radio Telephone Band where no license is necessary. Instructions and diagrams supplied for running the RT-1248 transmitter on either code or voice, in AM or FM transmission or reception, for use as a mobile public address system, as an 80 to 110 Mc. FM broadcast receiver, as a Facsimile transmitter or receiver, as an amateur television transmitter or receiver, for remote control relay hook-ups, for Geiger-Mueller counter applications. It sells for only \$29.95 or two for \$53.90. If desired for marine or mobile use, the dynamotor which will work on either 12 or 24V DC and supply all power for the set, is only \$15.00 additional.

RT1463 7 tube amplifiers containing 3-7F7, 1-7Y4, 3-7N7, 4 potentiometers, numerous resistors, filter and bypass condensers, filter chokes, power and audio transformers, and six sensitive plate circuit relays. A military development that provided amazing stepless control proportional to correction required, for alevous, rudder and elevator. In the original application. A control amplifier of the ordinary type would deflect the rudder by some arbitrary amount when the ship was blown off the course to port or starboard. The result would either be that the correction was insufficient and the plane continued off course, or the correction would be too great, starting a series of tackings that would greatly increase fuel consumption and elapsed time in reaching the objective. This phenomenal unit, with its 3 amplifiers and six 5000 ohm relays in bridge circuits, will accurately control any 3 operations, related or unrelated, in minutely adjustable uniquely quantitative variations in either forward or reverse directions. 9"x7"x8" black crackle aluminum case. Brand new in original carton \$12.95, or used \$9.95.

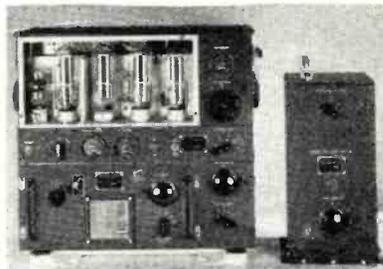**BRAND NEW BC 348 COMMUNICATIONS RECEIVER**

Featuring coverage from 200 to 500 Kc. and 1500 to 18000 Kc. on a direct reading dial with the finest vaneur drive to be found on any radio at any price—high sensitivity with a high degree of stability—crystal filter—BFO with pitch control—standard 6 volt tubes. Contains a plate supply dynamotor in a compartment within the black crackle finished cabinet, the removal of the dynamotor leaves plenty of room for the installation of a 110V, 25 or 60 cycle power supply. These receivers, which make any civilian communications receiver priced under \$200.00 look cheap and shabby by comparison, are only \$69.95 brand new. Power supply kit for conversion to 110V 25 or 60 cycles is only \$8.50 additional.



**GENERAL ELECTRIC 150-WATT TRANSMITTER**  
 Cost the Government \$1800.00  
 Cost to you \$44.50!!!

This is the famous transmitter used in U. S. Army bombers and ground stations, during the war. Its design and construction have been proved in service, under all kinds of conditions, all over the world. The entire frequency range is covered by means of plug-in tuning units which are included. Each tuning unit has its own oscillator and power amplifier coils and condensers, and antenna tuning circuits—all designed to operate at top efficiency within its

particular frequency range. Transmitter and accessories are finished in black crackle, and the milliammeter, voltmeter, and RF ammeter are mounted on the front panel. Here are the specifications: **FREQUENCY RANGE:** 200 to 500 KC and 1500 to 12,500 KC. (Will operate on 10 and 20 meter band with slight modification.) **OSCILLATOR:** Self-excited, thermo compensated, and hand calibrated. **POWER AMPLIFIER:** Neutralized class "C" stage, using 211 tube, and equipped with antenna coupling circuit which matches practically any length antenna. **MODULATOR:** Class "B"—uses two 211 tubes. **POWER SUPPLY:** Supplied complete with dynamotor which furnishes 1000V at 350 MA. Complete instructions are furnished to operate set from 110V AC. **SIZE:** 21½ x 23 x 9¼ inches. Total shipping weight 200 lbs., complete with all tubes, dynamotor power supply, five tuning units, antenna tuning unit and the essential plugs. These units have been removed from unused aircraft and are guaranteed to be in perfect condition.

**BC-947A ONE KILOWATT HIGH FREQUENCY TRANSMITTER**

This relay-controlled transmitter includes a 115V, 60 cycle power supply, protected by 3 magnetic circuit breakers, that alone is worth more than the price we are asking for the whole rig, even on today's surplus market. On the front panel are six 3½" GE or Weston meters, including 250 MA, 50 MA, 1000 MA, 150V AC, and 1500V DC at 1000 ohms per volt for screens and plate. The rack-type 21"x15"x36" unit contains six amplifier and rectifier tubes aggregating over \$60.00 at WAA current wholesale prices. Western Electric's price to the government was \$1500.00. Shipping weight 500 lbs. Your cost, as is, only \$69.95.

**ARMY BC 312 COMMUNICATIONS RECEIVER**

This receiver covers the frequency range of 1.5 MC to 18 MC in six direct reading bands. The dial, that is driven with split gears to prevent backlash, has 4500 logging divisions per band with approximately 600 divisions on the 20 and 40 meter ham bands and 1000 divisions on 80 meters. Two stages of RF before the converter in this set give it a very high signal to noise ratio and maximum sensitivity. Outstanding features of this receiver are: BFO with pitch control, send-receiver relay, jacks on the front panel for headphones and speaker output and mike and key input, all tubes are standard 6 volt types. This receiver was designed to withstand rough usage in the field and for operation from vehicles while in motion, so it is ruggedly constructed and contains a dynamotor power supply.—Your cost \$49.95. Conversion kit to 110 VAC is available for \$6.50.

**BC-654 TRANSMITTER-RECEIVER**—This medium power transmitter and the very sensitive receiver is a natural for 80 meter operation (phone or cw). These units are brand new and come complete with 17 tubes, key, microphone and 200 KC calibrating crystal—\$39.95.

Minimum order \$3.00—All prices subject to change.—25% deposit with C.O.D. order.

**UNIVERSAL  
LEADS AGAIN**

**TELEVISION  
KITS  
IN STOCK!**

EASY TO ASSEMBLE AND WIRE...  
THOROUGH STEP BY STEP INSTRUCTIONS COVERING ASSEMBLY, ALIGNMENT AND OPERATION ARE PACKED WITH EACH KIT.

**7" TELEVISION KIT** (less tubes) **\$77.50**  
TUBE KIT FOR ABOVE \$42.77

**FEATURES**

- Uses simplest, most advanced television receiving circuits.
- Pretuned I.F. coils. (Only slight adjustment needed for best picture detail).
- All holes in steel chassis are drilled.
- Sound reception is high fidelity F.M.
- Performance guaranteed.
- 17-tube television receiver.



CABINET FOR EITHER KIT.....\$29.50  
WALNUT FRONT PANEL, ONLY.....\$10.00  
Cabinets, Panels and Kits 5% Higher  
West of Rockies

**10" TELEVISION KIT** (less tubes) **\$124.50**  
TUBE KIT FOR ABOVE \$72.34

**FEATURES**

- First to use the new TTI interlock circuit for horizontal and vertical sync control—holds the picture stationary even at low signal strength and in noisy locations.
- Electro Magnetic scanning and focusing.
- Pretuned I.F. coils. (Only slight adjustment needed for best picture detail).
- 10,000 volt Electronic power supply for 10" tube.
- Two separate low voltage power supplies used to prevent interaction between circuits.
- Sound reception is high fidelity F.M.
- Performance guaranteed.
- 19-tube Television receiver.

SEND YOUR ORDER TODAY!

**UNIVERSAL  
RADIO SUPPLY CO.**  
1404 - 06 VENICE BOULEVARD  
LOS ANGELES 6, CALIF.

# LOW RANGE OHMMETER

By  
**S. C. GAINES**

*This accurate service tool provides  
1 and 10 ohm midscale readings.*

HERE is an instrument which is very useful to the serviceman and experimenter, i.e., an ohmmeter with a backup scale and two low ranges (0-50-500) and having 1 ohm and 10 ohms at midscale.

A voltage regulator tube is used to stabilize the power supply so that full scale adjustment can be maintained. The high voltage is used to give the unit extreme accuracy as far as the power supply is concerned. The maximum errors the power supply introduces are .35 of 1% on the 500 ohm range and .035 of 1% on the 50 ohm range. These figures are in contrast to errors of 8% and .8% which would have occurred if a 4.5 volt battery had been used.

The meter used in this unit was an old iron cased 2" d.c. ammeter with the shunt removed. The fundamental range of the movement was 15 ma. A resistance scale was obtained from a 3" meter and was then photographed and enlarged to match the meter used.

In the construction of this unit  $R_1$  and  $R_2$  should be about 5000 ohms at the beginning and then their resistance may be reduced as needed. In building this ohmmeter make sure that the power supply leads are connected directly to the binding posts  $H$  and  $C$ ; that resistor  $R_1$  is connected between posts  $H$  and  $L$  and that the meter leads, between posts  $L$  and  $C$ , are heavy and as short as conveniently possible.

Two precision resistors are needed for calibrating this instrument. These resistors should be equal to the value at midscale (or some point near midscale) of each range. A 1 ohm and a 10 ohm resistor were used to calibrate the original model. The resistance measured at  $L$  and  $C$ , with the power supply disconnected, must be equal to the value at midscale on the low range. The resistance measured at  $H$  and  $C$  must be equal to the value at midscale on the highest range.

When the construction of the unit has progressed sufficiently to get a full-scale reading on the meter,  $R_2$  and  $R_3$  can be calibrated. At this point in the construction  $R_1$  can be of any low value. To calibrate the low range,  $R_2$ ,  $R_3$  and




Front panel view of ohmmeter. An inexpensive 15 ma. d.c. meter is used.

$R_1$  must be adjusted so that the meter pointer indicates full-scale when no calibrating resistor is connected to  $L$  and  $C$ , and so the pointer indicates 1 ohm when the 1 ohm calibrating resistor is directly connected to  $L$  and  $C$ . During this procedure the value of  $R_1$  may need to be lowered to keep the VR105 operating. Never adjust  $R_1$  low enough to let the VR105 dissipate more than 30 ma. When the calibration of  $R_2$  and  $R_3$  has been completed,  $R_1$  should be adjusted so that the VR105 dissipates 20 ma. when the line voltage is 115 to 117, and the meter indicates full scale.

To complete the calibration  $R_1$  must be adjusted so that the meter pointer indicates 10 ohms on the highest range when the 10 ohm calibrating resistor is directly connected to  $H$  and  $C$ . Adjust  $R_3$  to get a full scale reading. Long test leads should not be used when measuring low resistance.

-50-

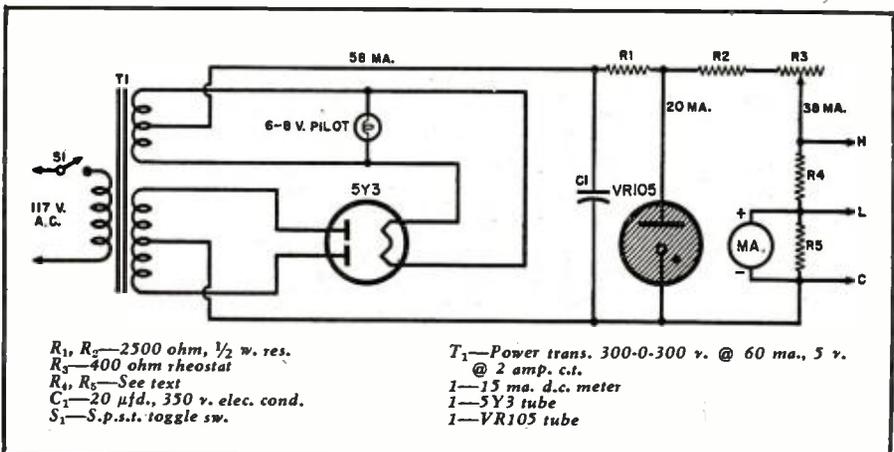Schematic diagram and complete parts list for low range ohmmeter.



**Now**

YOU CAN HAVE IMPROVED No-DRIFT FM  
in the Sensational New 1948

# MIDWEST RADIOS

**NEW SERIES  
16\*  
SUPER DELUXE  
AM-FM  
CHASSIS**

Here is the finest radio Midwest has ever produced in its 28 years of manufacturing—a world-ranging, 5-band radio with improved Midwest No-Drift FM . . . plus Standard Broadcast and 3 short wave bands, Television Audio Switch-over, and Color-Ray Tone Selection. The Series 16\* Super De Luxe Chassis is a powerful, magnificently-toned radio that challenges comparison for performance, sensitivity, selectivity, and advanced engineering features. Supplied with satin stripe copper finish panel—ready to mount in your present cabinet. Send today for the FREE 1948 Midwest Radio Catalog. Buy your radio direct from the manufacturer on Easy Terms and 30 Days Trial and SAVE!




**14 1/2" PANASONIC SPEAKER**

**5 WAVE BANDS**

\*SERIES 16 CHASSIS USES ALL THESE LATEST-TYPE TUBES

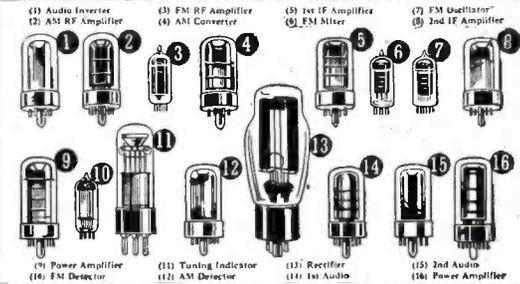**30 DAYS TRIAL**      **LOW FACTORY-TO-YOU PRICES**      **EASY TERMS**

A COMPLETE LINE OF FINE RADIOS AND RADIO-PHONOGRAPHS . . . Available in Separate Chassis Like the Powerful Series 16\* AM-FM Model above, or in beautiful Radio-Phonograph Consoles like this:



Scores of NEW features such as the Exclusive MIDWEST TRI-MAGNADYNE COIL SYSTEM and COLOR-RAY TONE SELECTION



## SYMPHONY GRAND AM-FM RADIO-PHONOGRAPH CONSOLE with NEW Intermix AUTOMATIC RECORD CHANGER

Our Finest! A superbly beautiful musical instrument . . . a masterpiece of furniture design and radio engineering that offers the sensational Midwest NO-DRIFT FM, Automatic Intermix Record-Changer, Exclusive Color-Ray Tone Selection, World-ranging 5-Band Reception, Television Audio Switch-Over, and many more new and exclusive features.

**Rush for Free Catalog!**

FILL IN COUPON AND MAIL TODAY OR JUST SEND YOUR NAME AND ADDRESS ON 1c POSTCARD.


MIDWEST RADIO CORP.  
Dept. 47-K, 909 Broadway  
Cincinnati 2, Ohio  
Gentlemen: Please send me your new FREE catalog and details of your liberal 30 Days Trial.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**MIDWEST RADIO CORP.**  
Dept. 37-K • 909 BROADWAY • CINCINNATI 2, OHIO

# THE MASTERS CHOICE!
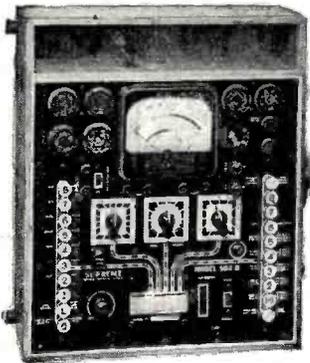
## SUPREME MODEL 504B TUBE AND SET TESTER



Any craftsman distinguishes himself by the appearance of his tools and equipment. For 19 years SUPREME equipment has identified thousands of successful radio service engineers. SUPREME equipped repair shops distinguish themselves for their professional appearance, dependability, and profitable operation.

One among the complete group of SUPREME radio testers is the Model 504B Tube and Set Tester.

- **METER**— large 4-inch square-face meter, 500 microamperes.
- **SPEED**— push-button operated.
- **FLEXIBLE**— simple, yet Universal Floating Filaments feature insures against obsolescence.
- **SIMPLICITY**— roll chart carries full data for tube setting. No roaming test leads when using multi-meter—only push a button.

**SPECIFICATIONS**  
 DC VOLTS — 1000 Ohms per volt: 0.5-25-100-250-500-1000-2500.  
 AC VOLTS — 0.5-10-50-250-1000.  
 OUTPUT VOLTS. 0.5-10-50-250-1000.  
 OHMMETER. 0-200-2000-20,000 Ohms  
 0-2-20 Megohms

**Condenser Check:**  
 Electrolytics checked on English reading Scale at rated voltages of 25-50-100-200-250-300-450 volts.

**Battery Test:**  
 Check dry portable "A" and "B" batteries under load.

# SUPREME

SUPREME INSTRUMENTS CORP.  
 GREENWOOD, MISS.  
 U. S. A.



"SUPREME BY COMPARISON"

See the complete SUPREME line.  
 Write for new SUPREME catalogue  
 No. 447.

## Practical Radio Course

(Continued from page 76)

cessive steps of 200 kc. to and including 107.9 mc. The FM broadcast band extends, therefore, roughly from 88 to 108 mc. In order to further reduce the possibility of adjacent-channel interference between their signals, it has been the policy of the FCC to assign FM broadcast stations that serve the same service area to transmission channels whose center frequencies are spaced 400 kc. apart.

### Elements of Superheterodyne FM Receiver

A block diagram of a conventional FM receiver, illustrating the essential units employed, and their sequence in the signal circuit, is shown in Fig. 1. It will be instructive to briefly review the function of each.

The received FM radio-frequency signal voltage from the dipole receiving antenna is usually applied to a tuned r.f. amplifier stage designed with a passband approximately  $75 \times 2 = 150$  kc. wide, and employing an r.f. pentode tube for good gain. This tuned r.f. amplifier supplies an overall r.f. gain of the order of about 20 to 50 and thus improves the signal-to-noise ratio. It serves also to reject signals of image frequency,<sup>2</sup> and strong signals at the intermediate frequency, which might otherwise reach the i.f. amplifier and cause serious interference in the output.

In accordance with superheterodyne principles, the amplified FM signal voltage from the r.f. amplifier, and the constant-amplitude r.f. voltage generated in the local oscillator section of the frequency converter, are applied to separate control grids of the frequency converter tube. (A frequency converter comprising a separate mixer and oscillator are shown in Fig. 1.) Frequency conversion takes place, and the component of plate current at the "difference" frequency is fed to a broad-band, high gain intermediate frequency amplifier. As in AM receivers, this i.f. amplifier must contribute the major part of the r.f. gain and provide the selectivity necessary to prevent possible interference from signals of adjacent-channel FM transmitters. Two stages of high gain amplification employing r.f. pentode tubes are usually necessary in the i.f. amplifier of FM receivers, since the gain per stage that can be realized in practice is rather low because of the necessity of using a rather high intermediate frequency (10.7 mc.) in the amplifier.

Since most types of FM detector (demodulator) circuits are responsive to amplitude as well as frequency variations (modulations) that are present in the detector input voltage

<sup>2</sup> The image frequency is that frequency which differs from the desired signal frequency by twice the intermediate frequency, and which lies on the same side of the desired signal frequency as does the oscillator frequency. See Alfred A. Ghirardi, *Practical Radio Course, Part 54*, (RADIO NEWS, July 1947).



Net \$135<sup>00</sup> Inc. Tax

"THERE'S NO PLACE LIKE HOME"

AND NEVER A TONE SO TRUE, AS IN THIS

### ELECTRAPHONE AMPLIFIER!

MODEL A-101 AMPLIFIER FOR HOME USE  
 This ELECTRAPHONE AMPLIFIER has been especially designed for the reproduction of classical music in the homes of discriminating music lovers.

IT'S TONE HAS BEEN THRILLING HOLLYWOOD! Copper tube encased grid leads, linear standard transformers and the finest of tone control circuits provide life-like character to its reproduction of your favorite artists.

Write to-day for our catalog of exclusive speakers, wide band tuners and special turntables and pickups.—All for home use.

**ELECTROPHONE CO.**

8689 MELROSE AVENUE  
 HOLLYWOOD 46, CAL.

## SENSATIONAL SELLER!



### LAKE DELUXE CHANGER

Revolutionizes the Industry!  
 A Sensational Seller!

#### 11 Outstanding Features:

- Positive Intermix
- Service Adjustments Eliminated
- Minimizes Record Wear
- Single Knob Control
- Plays ALL Records
- Pick-up may be grasped at any time and changer will not be thrown out of adjustment
- Resonance-free ball bearing tone arm
- Easily operated—any child can do it
- Completely Jam-proof
- Records Gently Lowered on Sound —not dropped
- Automatic Snut-off on last record

Dimensions: 13 1/8" W x 12 1/4" D x 7 3/8" H.  
 No. 116A.....YOUR NET \$28.73

**SERVICEMEN—RETAILERS**  
 Write for our new, illustrated 16-page catalog NR-116. It's free. Get on our mailing list!  
 Write for our Special Catalog on Microphones, Amplifiers and Sound Equipment!

## Lake Radio Sales Co.

615 W. Randolph Street  
 DEPT. A

Chicago 6, Ill.

RADIO NEWS

during reception of FM signals, a device called a *limiter* must precede such detectors.<sup>3</sup> It is called a limiter because its function is to reduce or limit all (undesired) amplitude modulation that may be present in the frequency-modulated signal. Such amplitude modulation, if not removed, would cause interference in the output of the receiver. Amplitude modulations can get into the signal input to the receiver as a result of such things as interference from nearby electrical ignition systems of motor vehicles, atmospherics, electrical interference from household electrical appliances, fading, noise bursts, reflection of the transmitted signal from moving objects, etc. It is apparent that proper design and effective functioning of the limiter tube is very important, for such amplitude modulations must be removed. With an effective limiter located immediately ahead of the detector, and with sufficient r.f. amplification in the receiver to raise the signal up to that necessary to obtain limiting action, amplitude variations due to noise and interference will be removed, for the limiter is designed to pass *frequency* variation but prevent a "saturated" condition to voltage *amplitude* variations. This ability to remove objectionable noise impulses from the received signal without affecting the "quality" of the reproduction is one of the important advantages of the FM broadcasting system over the AM system. In some FM broadcast receivers two

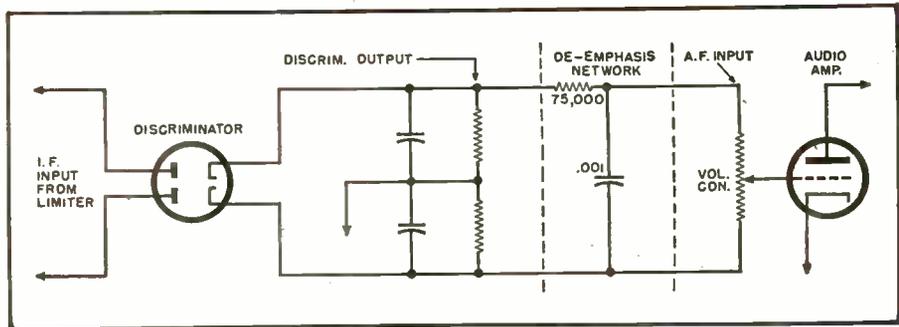


Fig. 5. Typical 75 microsecond de-emphasis network and its position in the frequency modulation broadcast receiver.

limiter tubes are used in cascade to insure most effective quieting.

The output of the limiter is the FM signal, still at intermediate frequency and substantially free of disturbing impulses. It is now necessary to derive the audio-frequency components from the frequency-modulated wave. This is *demodulation*. Demodulation is performed by an FM detector tube in which *frequency* deviations or changes in the FM signal ap-

plied to the input of the device result in direct current *amplitude* changes at the output which are directly proportional to the r.f. modulation at the source.

The type of FM detector used usually employs two diodes arranged to deliver an output voltage whose polarity depends upon whether the applied instantaneous signal frequency is *higher* or *lower* than the mean frequency of the input tuned circuits, and whose amplitude depends on the extent by which the applied frequency differs from the mean frequency. Therefore, since such detectors are able to discriminate between frequencies above and below the mean frequency of the coupled tuned circuits, they are called *discriminators* and are most often referred to by this name.

<sup>3</sup> The ratio detector is an exception. When one is used, the limiter is unnecessary.  
<sup>4</sup> In FM broadcast service it is desirable in the interest of noise reduction at the higher audio frequencies to employ (in the transmitter) a.f. pre-emphasis networks that make the frequency deviation (modulation) relatively greater at the high audio frequencies (that is, when the modulation frequency increases). Pre-emphasis is usually expressed as the time constant in microseconds of an R-C circuit giving the desired frequency characteristics. In America the FCC has now standardized the use of 75 microseconds pre-emphasis in the signals from American FM broadcasting stations.

Since a standardized pre-emphasis<sup>4</sup>

# Fahnestock Clips


## RADIO'S GREATEST CONVENIENCE
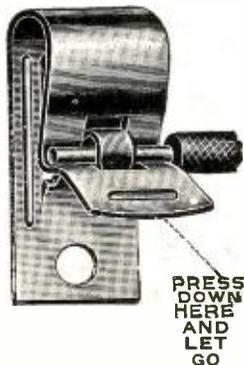
### FAHNESTOCK SPRING BINDING POST GRIPS THE WIRE BY THE ACTION OF A SPRING



No tools required to make the connection. Grips the wire with just the right pressure for good electrical contact. Simply press down, insert the wire and let go. Does not injure wire, hence connection can be made or opened as often as desired. Available in large variety of types and sizes to fit any radio purpose and any requirement as to position, space or method of attachment. You will find them in the better sets.

Positive contact; cannot jar loose. Brass or bronze—nonrusting.



### FAHNESTOCK ELECTRIC COMPANY, Inc.

46-44 ELEVENTH STREET  
LONG ISLAND CITY 1, N. Y.

Dept. 12

Please send us at once, Descriptive Literature, Prices and Delivery Schedule on

### FAHNESTOCK CLIPS

For .....

Name .....

Address .....

City..... State.....

# GIANT

War Surplus  
Radio Scoop!



**12<sup>95</sup>**

### VIBRATOR UNIT PE-125 BX

A versatile unit adaptable to many amateur purposes. Uses 2 RK-80 tubes. INPUT: 24 VOLTS DC at 7.2 AMPS.; continuous duty. OUTPUT: 475 VOLTS DC at 200 MA. Complete with tubes.  
Shipping Weight approx. 78 lbs.....\$12.95

**WAVE GUIDES**  
5 foot lengths.....per foot \$ .95

**CORD**  
78" lengths; two conductor; color coded .....12 for \$1.15  
Terminal lugs on each end.

**VIBRATOR FREQUENCY GENERATOR**  
60 cycle output with 12 VOLTS DC input ..... 3 for \$1.00

**DYNAMOTOR - DM - 21 - CX**  
Complete with all necessary output filtering condensers.  
INPUT: 28 VOLTS DC at 1.6 AMPS.  
OUTPUT: 235 VOLTS DC at 90 MA.  
INPUT: 14 VOLTS DC at 3.3 AMPS.  
OUTPUT: 235 VOLTS DC at .090 AMPS.  
Shipping Weight 7 lbs.....\$2.59

**RECEIVING DYNAMOTOR**  
INPUT: 12 VOLTS DC at 8 AMPS. or 24 VOLTS DC at 4 AMPS.  
OUTPUT: 12 VOLTS DC at 3 MA. or 275 VOLTS DC at 110 MA.  
Continuous Duty.  
Shipping Weight 8 lbs.....\$4.95

**TRANSMITTING DYNAMOTOR**  
INPUT: 12 VOLTS DC at 4 AMPS. or 24 VOLTS DC at 2 AMPS.  
OUTPUT: 500 VOLTS DC at 50 MA.  
Duty Int. RPM 3800  
Shipping Weight 8 lbs.....\$4.95

### MONEY BACK GUARANTEE

IF MERCHANDISE NOT AS SPECIFIED  
\$1.00 minimum order, f.o.b. Chicago, 25% deposit.  
10% discount on orders over \$50.00

**UNITED SURPLUS MATERIALS**  
3313-19 W. Ogden Ave. Chicago

of 75 microseconds is purposely employed in FM broadcast transmitters to increase the amplitude of the high-frequency components of the audio-modulation, FM broadcast receivers must incorporate corresponding *de-emphasis* to compensate for this and bring the amplitude of the high-frequency components of the detected (demodulated) signal down to the same proportion with respect to the lower-frequency components that exist in the original audio modulating voltage—if an over-all linear audio characteristic for the entire system is to be attained. This function is usually performed by a 75 microsecond *de-emphasis* attenuating network connected in the discriminator output. This network usually consists simply of a 75,000 ohm resistor in series with the discriminator output circuit and a .001  $\mu$ fd. condenser shunting this output, as shown in Fig. 5. Other combinations of *R* and *C* that will provide the same 75 microsecond *de-emphasis* can be used of course.

In other FM services, where a different value of pre-emphasis may be applied at the transmitter a *de-emphasis* network having different values of *R* and *C* than those specified above will be necessary in the receiver in order to exactly compensate for the pre-emphasis applied at the transmitter.

The demodulated, *de-emphasized* audio signals are fed to a high-fidelity audio amplifier and then to a high-fidelity acoustic system. It is important that *both* of these have adequate wide-range characteristics and introduce negligible distortion, for the capabilities of a well-designed FM receiver are limited only by those of the audio amplifier and acoustic system associated with it.

This completes the FM broadcast receiver system!

It is evident that the functional elements of the FM superhet broadcast receiver differ from those in AM superhet broadcast receivers only in the limiter, discriminator, and *de-emphasis* network. However, it must be remembered that in the FM broadcast receiver the r.f. circuits operate at frequencies in the 88-108 megacycle spectrum and their selectivity characteristics must be such as to enable them to pass a band approximately 150 kc. wide; the i.f. circuits operate at much higher frequencies than do those in AM broadcast receivers (as we shall presently see) and also are required to pass a frequency band approximately 150 kc. wide; the audio-frequency circuits and acoustic system must respond satisfactorily over a wide audio frequency range from 50 to 15,000 cycles-per-second.

Now that we know *what* performance characteristics are required in the i.f. amplifier, we are ready to study various phases of its design in greater detail.

(To be continued)

## "America's Best Buy"

### TUBULAR ELECTROLYTICS

Fresh Stock. Fully Guaranteed

	Each	10	100
20 mfd..... 150V	\$0.21	\$1.79	\$16.95
20-20 mfd..... 150V	.29	2.49	22.98
8 mfd..... 450V	.19	1.85	17.98

### BY-PASS CONDENSERS


	\$0.06	\$0.55	\$ 4.60
.01..... 600V	.06	.55	4.75
.02..... 600V	.06	.55	4.95
.05..... 600V	.07	.65	5.49
.1..... 600V	.11	.98	8.95
.005..... 1700V	.14	1.25	9.95
.01..... 1700V	.15	1.30	10.20
.02..... 1700V	.16	1.40	10.95

### RESISTOR ASSORTMENT

100 assorted  $\frac{1}{4}$ - $\frac{1}{2}$  watt carbon resistors.  
All RMA color coded. Special \$1.29.

### CRYSTALS 74c each

Your frequency plus or minus 10 KC

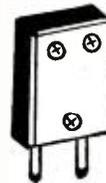

80 Meter, 3500-4000KC  
40 Meter, 7000-7300KC  
for multiplying into  
20 Meter, 7300-7425KC  
10 Meter, 7300-7425KC  
6 Meter, 6250-6750KC  
2½ Meter, 8000-8222KC

Postage extra. 20% deposit on COD.  
Write for latest bargain list featuring

"America's Best Buys."

POTTER RADIO CO.

1314 McGee St., Kansas City 6, Mo.



THIS IS THE  
BUSINESS

YOU DREAM ABOUT

QUICK, STEADY PROFITS

# CORADIO

The Coin Operated Radio

Every day more and more men and women are going into the fabulous coin operated radio business. It's new, fast-growing depression proof. Coin operated radios are placed in hotels, tourist courts, clubs, hospitals, etc. on a commission basis... plays 1 or 2 hours for 25c and produces immediate profits. You continue to draw your profits every single month for years to come.

The best and most popular coin operated radio is the CORADIO.

ACT NOW

Here is a golden opportunity to start your own business, full or part time. Be your own boss at your own hours.

Send for Free Illustrated Catalogue and Complete Information

WRITE TODAY—Dept. R.N.

# CORADIO

COIN OPERATED RADIO  
108 W. 31st ST. N. Y. 1, N. Y. WISCONSIN 7-5902

RADIO NEWS

## FM Receiver Alignment

(Continued from page 67)

ings should be equal, but with average equipment, percentage of error is greater. Care should be taken that the generator settings above and below the operating frequency are the same with regards to frequency separation from the center or operating frequency, to give more accurate results. If voltage readings, as described, are not within 10% of each other the discriminator will need adjustment.

Connect generator and v.t.v.m. or multimeter as described when testing to determine the operating frequency. Set the generator to the known operating frequency, and adjust the primary trimmer or primary adjustment for maximum meter deflection. Connect the v.t.v.m. to point X (Fig. 2A) or multimeter negative lead to point Z and use a 50 volt or higher scale. Adjust secondary trimmer, or secondary adjustment until the v.t.v.m. reads zero. (Note: When tuning the secondary the meter will swing first from one polarity maximum, and then the other, crossing through zero. The correct setting is between these two maxima, which is zero). When using the multimeter, the positive lead must be connected first at point X (Fig. 2A) and then to ground. The secondary is adjusted until the meter readings at these two points are equal. In some cases of very bad misalignment this procedure may have to be repeated with the primary adjustment, if adjustment is found to be wrong when checked as described above in checking discriminator alignment. The circuits shown in Fig. 3A, 3B, and 3C may be aligned in the same way as described above with the following exceptions. In Fig. 3B one end of a resistor of between 1 and 2 megohms should be soldered at point Z and the v.t.v.m. should be connected between ground and the free end of the resistor for primary adjustment. Secondary adjustment may be made as described, between point X and ground. A multimeter is not recommended for use in aligning the circuit of Fig. 3B. In Fig. 3C point G is used instead of ground for all purposes of alignment.

Fig. 4 shows one circuit of the new ratio detector. This is essentially the same as the previous FM detectors shown except for a few minor circuit changes. A and B are primary and center tapped secondary. T is a tertiary winding wound over A, taking the place of the primary with regards to connections to the center tap of the secondary. T takes the place of the primary A in developing the voltage  $E_p$  shown in Fig. 2B. The diodes  $V_1$  and  $V_2$  with condenser C, are connected in such a way as to eliminate amplitude modulation effects. Alignment is the same as previously described, point Z and ground are used for primary adjust-

**AUTOMATICALLY PLAYS TWELVE 10" OR TEN 12" RECORDS**



GI-RC130  
Combination Record-  
Changer Recorder

**CUTS RECORDS UP TO 10"**

**ONE SIMPLE LEVER ADJUSTMENT**

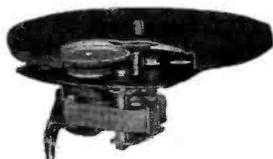
## Smooth Power COMBINATION RECORD-CHANGER • RECORDER



GI-RM4 Rim Drive, Heavy-Duty  
Electric Recording Motor



GI-R90 Dual-Speed, Home  
Recording and Phonograph  
Assembly



LX Rim Drive, Constant-Speed  
Electric Phonograph Motor

Your customers will like the simplicity and fine performance of this unique combination *Smooth Power* unit.

They'll enjoy the ease of operation with one simple lever for quick changing from one size record to another, to remove records or to set for manual operation and recording. They'll appreciate the smoothness and quietness of the record-changer. They'll admire the brown iridescent finish and streamline plastic trim on self-indicating "Reproducer" and "Recorder" arms.

And, of course, they'll value the quiet, vibration-free operation of the *Smooth Power* Motor.

Send for details. Ask us for complete information on this popularity-building combination that can add new sales appeal to your products . . . and on the complete line of *Smooth Power* Phonomotors and Recorders.



THE GENERAL  
INDUSTRIES CO.

DEPT. MR

ELYRIA, OHIO

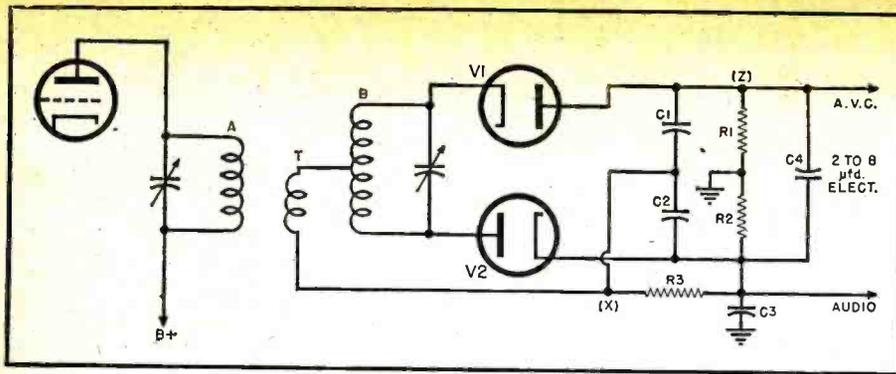


Fig. 4. Diagram of the relatively new ratio detector circuit.

ment, and point X and ground is used for secondary alignment.  $C_3$  is the de-emphasis condenser and  $C_1-C_2$  are r.f. bypass condensers. Audio output is taken from point X. A multimeter may be connected to point Z and X when aligning the detector and will act the same way as the v.t.v.m. at point Z and the secondary is adjusted for zero scale readings for multimeter or v.t.v.m. A 5000 ohm-per-volt meter and 50 volt scale must be used. This type of detector eliminates the use of limiting tubes before the discriminator.

The i.f. alignment can be accomplished equally well with a v.t.v.m. or multimeter. Read the manufacturer's instructions if available, and note whether the i.f. transformers should be aligned stage-by-stage or over-all.

If instructions are not available, over-all alignment may be used without serious trouble.

Connect one end of a 1 or 2 megohm resistor to point W in Fig. 2A, and attach the v.t.v.m. probe to the free end. If a multimeter is used, remove the grounded end of  $R_4$  from ground and connect the negative lead to the free end of  $R_4$  and the positive lead to ground. Use the 0-1 milliamper scale at first, switching to a higher or lower scale if necessary. An alternative method is to connect the v.t.v.m. or meter to point Z (Fig. 2A) as in discriminator primary adjustment and align the i.f.'s for maximum scale deflection. If stage-by-stage alignment is indicated, connect the signal generator successively between grid and ground of each i.f. stage starting with the last

and ending with the mixer or converter signal grid, adjusting each i.f. transformer primary and secondary for maximum meter deflection. If over-all alignment is followed, connect the signal generator to the mixer or converter grid and adjust the i.f. transformers starting with the last one. When using a v.t.v.m. keep the signal generator output adjusted so the v.t.v.m. reading is approximately 5 to 10 volts when making all i.f. adjustments. If a multimeter is used the output current should be kept between 50 and 100 microamperes. Any i.f. coils associated with limiter stages are aligned in the same manner as the regular i.f.'s.

Some i.f. transformers are triple-tuned (three adjustments) and it is best they be left undisturbed unless a wobulator and oscilloscope is available for visual alignment, by someone experienced in that procedure.

An r.f. alignment is generally not necessary unless the r.f. circuits have been disturbed or it is known that they are not set correctly. If they need adjustment, connect the v.t.v.m. or meter as described under i.f. alignment. Connect the signal generator to the mixer or converter signal grid. Set the tuning mechanism to the high end of the band. Set the signal generator at the dial reading of the receiver. (Note: The upper frequency of the old FM band is 50 mc. and of the new band is 108 mc. These are the usual frequencies of adjustment at the

# Why WE ARE ENTHUSED ABOUT OIL FILLED CONDENSERS!

### PUSH BUTTON TUNER



A ten push button assembly, operating a 4 gang silver plated variable condenser. Each shielded section has silver plated APC type ceramic air trimmers. Drum dial manual tuning. An outstanding surplus value at lowest prices ever offered. **\$250**

### OIL FILLED BATHTUB CONDENSERS

200 Volt in .5, 1., dual .5, MFD	20 FOR \$1
400 Volt in .1, dual .1, triple .1, .2, .25, .5, 1., MFD	15 FOR \$1
600 Volt .1, dual .1, triple .1, dual .2, .2, .25, dual .25, .5, 1., MFD	10 FOR \$1

### FLEXIBLE COAXIAL CABLE



RG-8/U is the ideal cable for feeding receiving and transmitting antennae for all frequencies up to 250 mc. and can be used up to 3,000 mc and down to dc. Priced at less than WAA wholesale. This is the last big lot — order while available.

**Only 4¢ PER FT.**

### METERS

Weston, 2½ 0-60 amps D.C., incl. shunt	\$2.95
Westinghouse, 2½ 0-240 amps DC, incl. shunt	2.95
G. E. 3½ 50-0-50 amps DC	2.95
Triplet Model 321 0-300 MA.	3.45
Weston output meter 2" in wood case, used	1.00
Ammeter 0-6 amps 2" flg. mtg.	1.00
Simpson 2½ 0-3V DC	1.95
Weston Model 507 2½ 0-1 amps RF	2.45
Meter Kit containing one R.F. Ammeter, one D.C. Voltmeter and one D.C. Milliammeter. Removed from aircraft radios.	4.95

Send for Meter List

### MICA TRANS. CONDENSERS

CAP	W.V.D.C.	PRICE
.002	6000	\$3.49
.0002	5000	1.49
.0001 ± 2%	3000 A.C.	.75
.002	2500	.69
.005	1200	.39
.02	1200	.59
.01	1200	.39

Send for list on high voltage micas

CAP	WVDC	PRICE	CAP	WVDC	PRICE
5	400	.39	2	1000	.69
5-5	400	.79	4	1000	.90
4	500	.49	8	1000	1.00
5	600	.59	8-8	1000	1.95
8	600	1.00	.25	1500	.49
2.5-2.5-5	600	1.50	1.5	1500	.79
5-5-5	600	1.95	4	2000	1.50
8-8-8	600	3.95	8	2000	1.95
5-5	600	1.00	2	2500	1.95
.1	1000	.29	.1	3000	1.20
.25	1000	.39	.25	3000	1.30
1	1000	.49	.05	7500	2.50

## The HEATH COMPANY

BENTON HARBOR, MICHIGAN


# The BEST in SURPLUS

## BC 457A TRANSMITTERS

Brand new transmitters covering 4-5.3 MC. Contains M.O. 1625, two 1625's as P. A., these make excellent VFO from conversion in May 1946 CQ. Complete in original cartons with tubes.....



**\$4.95**

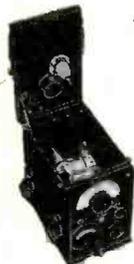

## BC 222 WALKIE TALKIE

Supplied new with antenna. The latest type covering 28-52 MC, includes crystal calibrator, range 15 miles. Only 130 available at this low price..

**\$19.50**

## BC 455B RECEIVER

Six-Tube Western Electric superheterodyne, 3 gang condenser, R. F. stage, two I. F. stages, tunes 6-9.1 MC. Offered brand new in original carton for the price others ask for used war-weary sets, with six new tubes. 3-12SK7, 1-12SR7, 1-12A6, 1-12K8. Our price.....



Dynamotor for BC455B.....

**\$1.95**



## TUBES

3B7/1291 V.H.F. Twin Tr. \$1.50  
3D6/1299 V.H.F. Tetrode. 1.50  
814 Transmitting Beam Power. 3.95  
6AC7, 6AG7..... .89

Send for Tube List

New Bulk Packed  
GSN7 6H6 6J5  
GSJ7 6J6 1G6GT  
GSL7 6AQ6 1LH4  
GSA7 6AK6 12C8  
6A6 3A4 1619  
6Y6 955

**49¢**

## BC-605 INTERPHONE AMPLIFIER

The famous tank interphone, thousands bought for intercommunicating systems, call systems, etc. Uses two 1619 tubes (2.5V fil. 6L6's) used, in excellent condition, lowest price ever offered, with tubes.....


**\$2.95**



## BC 223 TRANSMITTER

One of the most desirable military transmitters, 4 crystal-controlled frequencies and master oscillator. Meters for Osc., Ant., and total current. Uses 46 speech amplifier, 2-46 modulators, 801 each as oscillator and power amplifier. Practically no conversion necessary, plug in crystal, mike and connect power supply and it's ready to operate. Brand new, with tubes and tuning units to cover 2000 KC. to 5250 KC.

**\$14.95**

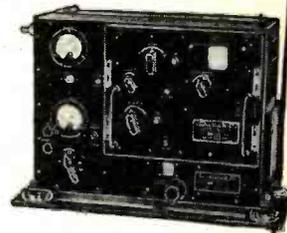

## POTENTIOMETERS

Mallory 600 ohm 4 watt W.W. 1" Shaft  
Mallory 1000 ohm 4 watt W.W. 1/2" Shaft  
Mallory 5000 ohm 4 watt W.W. 3/4" Shaft  
W.E. 10,000 ohm 4 watt W.W. 3" Shaft  
C.T.S. 10,000 ohm Carbon 3/8" Shaft  
Mallory 20,000 ohm 4 watt W.W. 1" Shaft  
Mallory 25,000 ohm 4 watt 3/4" Shaft  
Clarostat 40,000 ohm 3 watt W.W. 1/2" Shaft  
Centralab 100,000 ohm carbon 2" Shaft

**29¢**

EACH

Any 12 above, 12 for \$2.50

## KITS

Kit of ten ceramic variable air trimmers, 12 M. M. F. to 50 M. M. F. \$1.95  
Kit of assorted mica and silver mica condensers, all marked. 25 for \$1.00  
Kit of assorted ceramic condensers. 20 for \$1.00  
Kit of Potentiometers long shafts, 600 ohms to 200M ohms. 10 for \$1.95  
Kit of tube sockets, miniature, loctal, octal. 20 for \$1.00  
Kit of power rheostats, 25 and 50 watt. 6 for \$2.95  
Kit of 4 Dynamotors, easily converted to motors for fans, movie projectors, toy sets, etc. 4 for \$4.95  
Experimenter's Kit, a paradise of condensers, coils, transformers, resistors, etc., all useful parts. 5 full pounds for \$1.00  
Resistor Kit 1/2 -1-2 Watt, all excellent sizes, color coded. 100 for \$1.95  
Kit of Microswitches. 3 for \$1.00  
Kit of amphenol connectors, excellent for converting military sets. 10 for \$1.00  
Kit of bypass condensers, .01 to 25 MFD, 200 to 600 volts, all marked. 15 for \$1.00  
Kit of toggle switches, SPDT, SPST, DPST, etc. 6 for \$1.00  
Kit of vitreous resistors, 5 and 10 Watt. 15 for \$1.00  
Kit of Selenium Rectifiers. 4 for \$1.00  
Kit of transmitter crystals, assorted between 2000 and 6000 KC in holders. 4 for \$1.00  
Kit of R.F. Chokes, excellent assortment. 10 for \$1.00  
Kit of power, microphone and headphone cords, rubber covered, with plugs. 10 for \$2.95  
Kit of screw driver type Potentiometers. 10 for \$1.00  
Kit of Metal Tubular Bypass Condensers. 20 for \$1.00  
Kit of Bathtub Bypass Condensers .1 M.F.D. to 1 M.F.D. 20 for \$1.00  
Kit of Relays, excellent assortment. 5 for \$2.50  
Kit of Rotary Switches, Mallory, Centralab, etc. 5 for \$1.00

## Specials

455 KC slug tuned I.F.'s square can. 39¢, 3 for \$1.00  
4-gang 147 MMF silver plated variable condensers, long shaft, a buy at. \$1.00  
Ceramic variable condensers, 50 MMF. Screw driver adj. Special 5 for \$1.00  
Choke, 20 henry 50 MA, cased. \$1.00  
Choke, 10 henry, 200 MA, cased. \$1.50  
HS30 miniature type headphones, similar to hearing aids with band and cord. \$1.00  
12 MFD 150V Mallory electrolytics, extra special. 6 for \$1.00  
.01-600V paper tubular condensers. 20 for \$1.00  
.05-600V paper tubular condensers. 15 for \$1.00  
Interphone control box, BC606, contains potentiometer, pilot lite, switch, etc. 2 for \$1.00  
Tuning Unit, BC-746 contains receiver ant. coil, tuning condenser, and crystal, transmitter crystal, slug tuned tank coil sockets, etc. Ideal foundation for Walkie-Talkie or small amateur rig. \$1.00  
Dynamotors, Western Electric, 12V input, 220V at 80 MA output in original carton. \$1.95  
Dynamotors, Western Electric, 24V input, 220V at 80 MA output in original carton. \$1.50  
Dynamotors, BD-77, 12V input, 1000V at 350 MA output. \$7.95  
Circuit Breakers, G. E., 50 Amp. 220V 2 pole in original carton. \$2.95  
Lip Microphones in original sealed cartons. \$1.00  
Mine Detectors SCR 625 in excellent used condition. \$19.50  
BC 729C Antenna Tuning units from BC 610. Matches 500 watt transmitter to antenna made by Hallicrafters. Has 0-15 RF Ammeter. Brand new. \$14.95  
BC 306A Antenna Tuning Units. Mfg. by General Electric. Matches 150 watt transmitter to antenna. Brand new. \$3.95  
35' Mast Antenna, Steel, Sectional, with Guys, Base, 50' Coax Lead In, canvas case. \$29.50  
U.H.F. Loctal Sockets, Mica filled cinch. 10 for \$1.00  
Thermocouple for R. F. Ammeters. New. 3 for \$1.00  
Technical Manual on BC312 and BC34 Receivers, instructions and circuit diagrams, etc. .50  
Technical Manual on BC375 and BC191 Transmitters. .50  
Extension phone cords with plugs, 6 ft. .25  
Extension microphone cords with switch and plugs, 7 ft. .25  
4.3 MC. IF Transformers, double slug tuned. 25¢, 5 for \$1.00  
Power Transformer cased 120V 60 cy. pri. Sec. 400V 30 MA, 6.3V at 2.35A, 6.3V at 1.1A, 6.3V at .6 A. Extra Special. .89  
Power Transformer RCA cased pri 100V 60 cy. Sec. 640V CT at 105 MA, 5V at 3 A, 2.5V at 5 A, 6.3V at .4 A or 12V at .1 A A real buy. .98  
Power Transformer, 110V 60 cy. pri. from Hammerlund Super-Pro, cased, supplies 465V at 160 MA, 300V bias at 11 MA, 6.3V at 7.5A, 5V at 3A, and 5V at 2A. Ideal for PA systems and quality amplifiers. \$4.95  
Power Transformer, 110V 60 cy. pri. General Trans. Corp., cased, 500V at 25 MA, 6.3 V at 3.25 A, 5V at 2 A. \$1.49

WE WILL SHIP C. O. D. . . .  
NO ORDER UNDER \$2.00

**FREE**

Free AT 30 throat microphone with each order over \$10.00




The HEATH COMPANY

BENTON HARBOR, MICHIGAN

# READ FOR PROFIT!

Just Out!

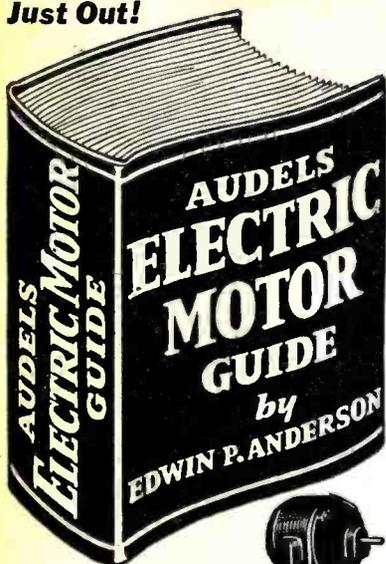

## 1000 PAGES OF PRACTICAL MOTOR INFORMATION

AUDELS ELECTRIC MOTOR GUIDE covering the construction, hook-ups, control, maintenance and trouble shooting of all types of motors including armature winding. Explains entire subject in every detail. 31 Chapters, 617 Illustrations & Diagrams. A Handy Guide, Fully Indexed for Electricians and all Electrical Workers.

**\$4 COMPLETE • PAY ONLY \$1 A MONTH**  
Step up your own skill with the facts and figures of your trade. Audels Mechanics Guides contain Practical Inside Trade Information in a handy form. Fully Illustrated and Easy to Understand. Highly Endorsed. Check the book you want for 7 days Free Examination. Send No Money. Nothing to pay postman.

### CUT HERE MAIL ORDER

AUDEL, Publishers, 49 W. 23 St., NEW YORK 10, N. Y.

Please send me postpaid for FREE EXAMINATION books marked (x) below. If I decide to keep them I agree to mail \$1 in 7 days on each book ordered and further mail \$1 monthly on each book until I have paid price. Otherwise, I will return them.

- ELECTRIC MOTOR GUIDE, 1000 Pages . . . \$4.
- ELECTRICIANS EXAMINATIONS, 250 Pages . . . 1.
- WIRING DIAGRAMS, 210 Pages . . . 1.
- ELECTRICAL DICTIONARY, 9000 Terms . . . 2.
- ELECTRICAL POWER CALCULATIONS, 425 Pgs. . . 2.
- ELECTRONIC DEVICES, 216 Pages . . . 2.
- RADIOMANS GUIDE, 914 Pages . . . 4.
- HANDY BOOK OF ELECTRICITY, 1340 Pages . . . 4.
- ELECTRIC LIBRARY, 12 vol., 7000 Pgs., \$1.50 vol. . . 1.
- OIL BURNER GUIDE, 384 Pages . . . 1.
- REFRIGERATION & Air Conditioning, 1280 Pgs. . . 4.
- POWER PLANT ENGINEERS GUIDE, 1500 Pages . . . 4.
- PUMPS, Hydraulics & Air Compressors, 1658 Pgs. . . 4.
- AUTOMOBILE GUIDE, 1540-Pages . . . 4.
- DIESEL ENGINE MANUAL, 400 Pages . . . 2.
- WELDERS GUIDE, 400 Pages . . . 2.
- BLUE PRINT READING, 416 Pages . . . 1.
- SHEET METAL WORKERS Handy Book, 388 Pgs. . . 4.
- SHEET METAL PATTERN LAYOUTS, 1100 Pgs. . . 1.
- AIRCRAFT WORKER, 240 Pages . . . 1.
- MATHEMATICS & CALCULATIONS, 700 Pgs. . . 2.
- MACHINISTS Handy Book, 1600 Pages . . . 4.
- MECHANICAL Dictionary, 968 Pages . . . 4.
- MARINE ENGINEERS Handy Book, 1280 Pages . . . 4.
- MECHANICAL DRAWING GUIDE, 160 Pages . . . 1.
- MECHANICAL DRAWING & DESIGN, 480 Pgs. . . 2.
- MILLWRIGHTS & Mechanics Guide, 1200 Pgs. . . 4.
- CARPENTERS & Builders Guides (4 vols.) . . . 6.
- PLUMBERS & Steamfitters Guides (4 vols.) . . . 6.
- MASONS & Builders Guides (4 vols.) . . . 6.
- MASTER PAINTER & DECORATOR, 320 Pgs. . . 2.
- GARDENERS & GROWERS GUIDES (4 vols.) . . . 6.
- ENGINEERS and Mechanics Guides . . . 12.
- Nos. 1, 2, 3, 4, 5, 6, 7 and 8 complete . . . 12.
- Answers on Practical ENGINEERING . . . 1.
- ENGINEERS & FIREMANS EXAMINATIONS . . . 1.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
Occupation \_\_\_\_\_  
Employed by \_\_\_\_\_ RN

upper end of the bands). Wobble the receiver tuning control and note whether the maximum meter deflection occurs at the correct setting. If it does not, adjust the oscillator trimmer with the generator and receiver dials at the same setting with regard to frequency, until maximum meter deflection occurs. Now check the low end of the band (42 or 88 mc.); the receiver dial should read the same as the generator. If this is not true the oscillator inductance is not correct or the dial pointer on the receiver may be off scale. Check the dial pointer travel to ascertain its correct operation, adjust it if necessary, and realign as before.

If the oscillator is incorrect it may be adjusted if very badly off, but it is generally advisable to leave this part of the receiver alone. Connect the signal generator to the antenna and adjust the r.f. and antenna trimmers at the high end of the band with the receiver and signal generator at the same setting for maximum meter deflection. It may be necessary in most cases to rock the receiver tuning control for maximum meter deflection when adjusting the r.f. trimmer.

If inadequate or inaccurate equipment is used for the above adjustments very serious misalignment causing reduced sensitivity and possible audio distortion may result. If test equipment is doubtful and a receiver seems to be properly adjusted it is best to leave well enough alone and avoid possible trouble. FM is not akin to AM where inaccurate adjustment is concerned, and this is especially true of the FM detector.

-30-

## V.H.F. FORUM

A NOVEL "over the air" discussion was instituted recently by members of the Midwest V.H.F. Club of Chicago. A bi-weekly program of technical discussions has been planned.

The central station used for control is W9ENP/W9DXX, located on the 36th floor of the Skyline Athletic Club. The antenna proper is located on the 46th floor, and the station is consistently heard within a radius of 100 miles from Chicago.

The round table each meeting consists of a narrator, two experts on the subject to be discussed, and two typical hams to ask questions. Subjects dealing solely with v.h.f. are discussed. The first program dealt with a discussion of antennas for v.h.f. work, and the guest expert was Jack Brown of the Andrew Co. Listeners are invited to suggest topics for future discussion.

The proceedings of the original meeting were retransmitted by at least five stations in the Chicago area and reports of reception have been received from five surrounding states. It is planned to eventually extend the coverage to the entire Midwest by means of relay stations.

Evidence of the interest in this program was the complete silence of the 144 mc. band during the hour-long transmission, with the exception of the participating stations.

-30-

## Amsco PRESENTS . . .

- MICRO AMMETER—  
Beede 0-200 D.C. . . . \$3.29
- MILLIAMPER METER—  
Beede 0-1000 D.C. . . . \$3.19
- METER RECTIFIERS  
Full Wave . . . . . \$0.95  
Half Wave . . . . . .65
- Dynamotor (Slightly Used)**  
Input 24 V D.C. 12 Amp. 300 V D.C.  
.26 Amp. Output 150 V D.C. .01 Amp.  
14.5 V D.C. 5 Amp. With Voltage  
Regulator and Filter System . . . \$4.95  
Klystron Osc. Tube 2K25/723AB operates on 3 cm. . . . . 5.75
- PHOTO-CELL AMPLIFIER 110V. 60  
Cy. panel type has 0-50 Micro Ammeter on front panel with tube 6V6, 6J7, 45, 80, VR105 . . . . . 12.95
- BUTTERFLY TUNERS—80 to 300 Mc.,  
300 to 1000 Mc. New in Cartons. . . . . 1.95
- PARABOLIC REFLECTORS—15" spun  
alum. Alzak fin. for 1200 Mc. up.  
Pr. . . . . 3.95
- PHASE SHIFT CONDENSERS—2 sections,  
split stator 4-15 mmfd. silver  
plated . . . . . .69

**SERVICE KIT**  
Kit includes assortment of:  
100 Resistors, 1/2 and 1-watt. . . . .  
50 Condensers, paper, mica, electrolytic & can. . . . .  
10 Switches, Toggle, Gang & Rotary. . . . .  
100 ft. Spaghettil, various sizes. . . . .  
12 Knobs, round and bar. . . . .  
2 lbs. Hookup wire. . . . .  
20 Fuses. . . . .  
6 Volume Controls. . . . .  
10 Tube Sockets. . . . .  
1 lb. Hardware (screws, nuts, lugs, etc.). . . . .

10 Wire Wound Resistors, 10 & 25 watt. . . . .  
25 Connectors, Plugs, Ties. . . . .  
10 Jacks (Phone) & Tip. . . . .  
12 Padlock Condensers. . . . .  
12 Terminal Boards. . . . .  
25 Ceramic Insulators. . . . .  
2 Panel Lights (1 neon). . . . .  
1 Screw Driver. . . . .  
1 Tube Puller. . . . .  
2 Allen Wrenches. . . . .  
2 Panel Fuse Holders. . . . .  
4 Binding Post Strips, and many other valuable items.

Your Cost \$9.95 Complete

FREE—“Experimenter’s Kit” “1 Pr. Headphones” or “Lip Mike” with first 500 orders.

New 1947 Circular Available Write Today  
**AMERICAN SALES CO.**  
1811 W. 47th St. Chicago 9, Ill.

## BEST BUYS IN Television—Surplus—F.M.

Signal Generator—made by Western Electric, B.C. 423 modified for F.M. and Television tuning, 54 to 106 Mc. Pulse modulated, 110 V. 60 cycle operation. With calibration chart and full instructions. The use of harmonics will naturally extend this frequency range. Other frequencies of equal ratio available from 10 to 250 Mc. Write for frequencies desired. Only . . . . . \$19.75

4500 W. Transformer (air core) for high voltage R.F. type power supply. Ideal for television, etc. . . . . \$5.75  
10000 V. and 30000 V. transformer similar to the above . . . . . \$6.75  
Circuit diagram for power supply with each coil. Write for details about our high voltage R.F. type power supply kits.

Dynamotor—the famous PE 103 A, 500 V.D.C. at 160 Ma. (cont. rating) output. The input may be either 6 V. or 12 V. Complete with all circuit breaker, filters and 10 ft. cables, brand new. . . . . \$8.50  
Dynamotor—output is 110 Ma. at 275 V. plus 500 V. at 30 Ma. with 12 V. input. May also be operated with 6 V input and 110 Ma. at 115 V. plus 50 Ma. at 210 V. output. Complete with filters, brand new . . . . . \$5.75  
Handset—TS-13, French phone type. Has 200 ohm carbon mike and high impedance 2000 ohm phone. With push to talk switch. Complete with 6' cord and 2 plugs, brand new. . . . . \$3.75

Aluminum case— for scopes, television, mobile rigs, power supplies, etc. With punched front panels and chassis. Size 12 x 14 x 2 1/2 inches. New Duco finish . . . . . \$4.95  
Shock-mount assembly— heavy duty type for above case . . . . . \$9.95  
14 prong socket assembly for cathode ray tube with mechanism for forward and angular adjustment of tube . . . . . \$1.50  
Variable ceramic condenser— dual 7-45 MMFD., 500 V. D.C.W. Use them as trimmers or padders.

Will cover a wide range when used in series or parallel (3.5 MMFD. . . . . 90 MMFD. Max.) Silvered plates, negative Temp. Coeff. Ideal for television, F.M. etc. 8 for . . . . . \$1.50  
Shock-mounts—aircraft type 12 x 10—5.50; 9 x 10—3 for . . . . . \$1.50  
Knobs—1 1/2" Dia. round black knobs with white engraved arrow. For use with 1/4" shaft. 75 for . . . . . \$4.00  
Rubber inserts—used on hearing-aid type phones. May be used for gromets, insulators, rubber feet, etc. 300 for . . . . . \$1.00

COMBINATION OFFER—Aluminum case heavy duty shock-mount and 14 prong socket assembly. All for . . . . . \$9.50

Please Add Sufficient Postage.  
25% with C.O.D. orders. FOB Hempstead.


**ALGERADIO**  
385 Jackson Street Hempstead, N. Y.

# Just Out!

THE GREAT NEW COMPLETE

# CONCORD

# Radio Catalog

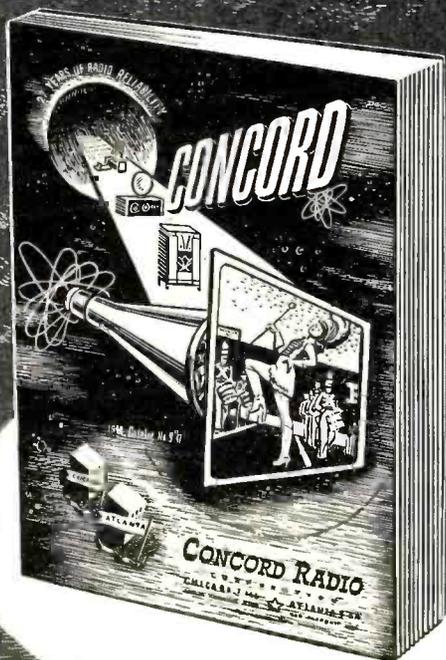

**RADIO PARTS  
RADIO SETS  
AMPLIFIERS  
TESTERS  
ELECTRONIC  
EQUIPMENT  
HAM GEAR**

**160  
VALUE-PACKED  
PAGES**

## MAIL COUPON BELOW FOR FREE COPY

It's ready now—the new Concord Radio Catalog offering the greatest, latest and most complete presentation of radio, electronic and television equipment and supplies in radio history! Just off the press, this new Concord catalog is packed from cover to cover with thousands of items to fill every radio and electronic need—Radio Parts, Radio Sets, Amplifiers, Sound Systems, Test Equipment for every purpose, Record Players, Record Changers, Television Equipment, Ham Gear, Kits, Receivers, Transmitters—

160 pages of everything and anything in Radio and Electronics. Complete showing of Amplifiers and Sound Equipment—including famous Concord Multi-Amp Add-A-Unit Amplifiers. Special bargain section offers hundreds of money-saving values in top quality, standard-make parts—including scores of new items from nationally-famous makers. Immediate shipment from stocks in two huge Concord warehouses centrally located in CHICAGO and ATLANTA. Mail the coupon now for your FREE copy.

**WANTED—TRADE-INS ON COMMUNICATIONS EQUIPMENT**—Depend on Concord for highest trade-in values on communications receivers. Write, phone or call to tell us what you have—or send it in for free appraisal.  
**TIME-PAYMENT PLAN**—Buy your Radio and Electronic Equipment from Concord on EASY PAYMENTS—Communications Receivers, Transmitters, Radios, Radio-Phonos, Sound Equipment, Test Equipment. Write us your needs.

# CONCORD

**RADIO CORPORATION**  
LAFAYETTE RADIO CORPORATION  
**CHICAGO 7, ILL.**      **ATLANTA 3, GA.**  
901 W. Jackson Blvd.      265 Peachtree St.

Concord Radio Corporation, Dept. E-107  
901 W. Jackson Blvd., Chicago 7, Ill.

Yes, rush FREE COPY of the comprehensive new Concord Radio Catalog.

Name.....

Address.....

City..... State.....

**"away ahead"**  
 "...in a comparison check, the BUD VFO-21 is away ahead in stability..."  
 WRITES

**Edward Zimmerman W4FNQ**

He says: "The performance of the VFO-21 is very satisfactory in every respect. In a comparison check with the Bud and one selling for a little more than twice as much money, the Bud is away ahead in stability. In using the VFO-21 "as is," into a medlocre antenna system on 40 meters, I have been able to work consistently into Cuba, the Bahamas and around the state, the tone reports being almost invariably TXN. Its use in conjunction with my final amplifier, (push-pull) 807's at 150 watts input) is entirely satisfactory, the output being enough to overdrive the 807's." It is unsolicited letters like this from our satisfied customers that convince us that the BUD VFO-21 is an instrument that belongs in your shack.

**THE BUD VFO-21**

Your Cost \$52.50



1. Compact and entirely self-contained.
2. Stability comparable to crystal.
3. Plug-in coils for highest efficiency.
4. A dual purpose unit having V-F-O operation, with provision for switching to crystal operation.

SEE IT AT YOUR LOCAL DISTRIBUTORS

**BUD CAN SUPPLY ALL YOUR NEEDS**

... with the latest types of equipment including: condensers—chokes—coils—insulators—plugs—jacks—switches—dials—test leads—jewel lights and a complete line of ultra-modern cabinets and chassis.



**BUD RADIO, INC.**

CLEVELAND 3, OHIO

**R**ADIO station WWV, of the National Bureau of Standards, is broadcasting six important technical services to the nation and five to the world, 24 hours a day.

Standard radio frequencies, time announcements, standard time intervals, the standard musical pitch of 440 cycles per second, and standard audio frequencies are transmitted continuously to the corners of the earth. As an additional service, ionospheric and radio propagation disturbance notices are broadcast twice each hour, stating whether or not radio disturbances are expected.

Eight transmitters are used on frequencies of 2.5, 5, 10, 15, 20, 25, 30 and 35 megacycles. All of the frequencies are broadcast continuously except 2.5 megacycles which is broadcast only at night. Because of the range of frequencies provided, reliable reception is, in general, possible throughout the United States and North Atlantic Ocean area at all times.

The basic component of all the services, with the exception of the radio propagation disturbance warnings, is a quartz crystal-unit with a series-resonance frequency of approximately 100,000 cycles per second. Using electron tube circuits, the crystal oscillates continuously and the resulting frequency is multiplied and divided to give the appropriate frequencies for the five services. Three separate crystal-units and associated apparatus are maintained at the station. As the entire service depends upon the maintenance of constant frequency, the crystal-units are sealed in painstakingly insulated boxes and kept in a vault approximately 25 feet below the surface of the earth, under conditions of constant temperature and humidity.

The national standard of frequency, of which the National Bureau of Standards is the custodian, is fundamental to much of the work in radio, electronics, acoustics, and other fields where measurements require accurate frequencies. Any desired frequency, including those throughout the microwave region, may be precisely measured, by reference to the standards broadcast by the station, with the aid of one or more auxiliary oscillators, harmonic generators, and radio receivers. The accuracy of each of the transmitted radio and audio frequencies is better than one part in 50 million.

Eastern Standard Time is announced in International Morse Code every five minutes, using the zero to twenty-four system with 0000 at midnight. The exact moment to which the time refers is the moment of interruption of the audio frequencies of 440 and 4000 cycles per second.

The standard time intervals, transmitted on each of the carrier frequencies, utilize a special pulse of .005 second duration broadcast every second. Heard as a faint "tick" in the background of the broadcast, the .005 second pulses working each second provide an indispensable standard time interval for purposes of physical measurements, for quick and accurate calibration of timing devices, and for the adjustment of very low frequency oscillators. Intervals of one second, as broadcast, are accurate to one millionth of a second. One, four, and five minute intervals, accurate to one part in 50 million, are marked by the beginning and ending of the pe-

riods when the audio frequencies are off, and are synchronized with the series of seconds pulses. The 59th in each series of 60 second pulses is omitted to designate the end of each minute.

The standard musical pitch of 440 cycles per second, A above middle C, is broadcast for four minutes and interrupted for one. This sequence is continuous on each of the radio carrier frequencies. The service is used by musicians and those concerned with the manufacture or maintenance of musical instruments. Since 1925 that frequency has been the standard musical pitch in the United States' music industry.

A warning of radio propagation disturbance is broadcast in code on each of the standard radio carrier frequencies at twenty and fifty minutes past the hour. If radio propagation disturbance over the North Atlantic is expected or is in progress, a "warning," or series of six "W's" in telegraphic code, follows the time announcement; if no disturbance is in progress or expected, a "no warning," or series of eight "N's," follows the time announcement.

A warning means that ionospheric and radio propagation disturbances are anticipated within 12 hours or are in progress, with their most severe effect on radio transmission paths crossing the North Atlantic. These are the paths which lie in or near the northern auroral zone (the region of maximum occurrence of aurora) which is the seat of most ionospheric disturbance.

A radio propagation disturbance is characterized by low received intensities, accompanied by flutter or rapid fading and often a complete fadeout on the frequencies normally used at a given time of day. By shifting to lower-than-normal frequencies for the time of day during which a storm is predicted, it may be possible to get signals through, although with lower-than-normal intensity. Due to the increased auroral-zone absorption during the disturbance, usable transmission may be impossible on any high frequency. Moreover, direction-finding equipment is likely to be unreliable during such a period.

Users of the technical broadcast services select the frequency which reaches them best, either by empirical observation, or by making use of the available techniques for prediction of best frequencies.

Although a great number of variables affect radio wave propagation and the distance range, the National Bureau of Standards has developed techniques for the prediction of best frequencies over any specific path during any future month. By means of such techniques and the prediction service of the National Bureau of Standards, it is possible for a user to prepare for his locality a graph, or table, showing the best frequency for any period of the day in any month, three months in advance. Basic radio propagation predictions and instructions for using them are prepared by the staff of the Bureau's Central Radio Propagation Laboratory under the title "Basic Radio Propagation Predictions Three Months in Advance," and are available from the Superintendent of Documents, U. S. Government Printing Office, at the rate of 15 cents per copy or \$1.50 for a year's subscription.

**BIAS TRANSFORMER**

120-0-120 v. at 50 ma.  
4 1/4"x3 1/2"x3 1/2". Wgt. 3 lbs. **98¢**



**JOHNSON No. 234 SOCKET**

For 705A, 715A, 715B, WE5D21, Raytheon  
RK72, RKR72. **98¢**

**SELENIUM RECTIFIERS**  
Full Wave Bridge Type

INPUT		OUTPUT	
up to 18v A.C.	up to 12v D.C.	1 Amp.	\$1.95
up to 18v A.C.	up to 12v D.C.	5 Amp.	4.45
up to 18v A.C.	up to 12v D.C.	10 Amp.	7.45
up to 18v A.C.	up to 12v D.C.	15 Amp.	9.95
up to 18v A.C.	up to 12v D.C.	30 Amp.	14.95
up to 36v A.C.	up to 28v D.C.	1 Amp.	3.45
up to 36v A.C.	up to 28v D.C.	5 Amp.	7.45
up to 36v A.C.	up to 28v D.C.	10 Amp.	12.45
up to 36v A.C.	up to 28v D.C.	15 Amp.	18.95
up to 115v A.C.	up to 100v D.C.	25 Amp.	2.95
up to 115v A.C.	up to 100v D.C.	6 Amp.	6.95
up to 115v A.C.	up to 100v D.C.	5 Amp.	19.95

**HALF WAVE TYPE**

up to 196v A.C.	up to 158v D.C.	.075 Amp.	\$2.95
up to 396v A.C.	up to 330v D.C.	.075 Amp.	3.95
up to 396v A.C.	up to 330v D.C.	.110 Amp.	4.95

**OIL CONDENSERS:**  
G.E., AEROVOX, CD., ETC.

All Ratings, D.C.

1mfd. 600v.	\$.35	2mfd. 2000v.	\$1.75
2mfd. 600v.	.35	3mfd. 2000v.	2.75
4mfd. 600v.	.60	4mfd. 2000v.	3.75
8mfd. 600v.	1.10	15mfd. 2000v.	4.95
10mfd. 600v.	1.15	1mfd. 2500v.	1.25
1mfd. 1000v.	.70	5mfd. 2500v.	1.45
2mfd. 1000v.	.95	5mfd. 3000v.	1.75
4mfd. 1000v.	1.95	.05mfd. 3000v.	1.95
8mfd. 1000v.	2.10	1mfd. 3000v.	2.25
10mfd. 1000v.	2.25	25mfd. 3000v.	2.65
15mfd. 1000v.	2.95	5mfd. 3000v.	2.85
20mfd. 1000v.	2.95	1mfd. 3000v.	3.50
24mfd. 1500v.	6.95	12mfd. 3000v.	6.95
25mfd. 2000v.	1.05	2mfd. 4000v.	5.95
5mfd. 2000v.	1.15	1mfd. 5000v.	4.95
1mfd. 2000v.	.95	1mfd. 7000v.	2.95

**SPECIAL! 2 mfd. 3000v. .... \$4.45**

**HIGH CAPACITY CONDENSERS**  
All Ratings, D.C.

4000 mfd.—18WVDC	\$1.95
4000 mfd.—30WVDC	2.95
1000 mfd.—15WVDC	.99
2000 mfd.—50WVDC	1.95

**ART/13 MODULATION KIT**

Consists of driver, speech amplifier, sidetone amplifier assembly and modulation transformer. With complete diagram for the famous ART/13 transmitter. **\$8.95**  
SUPER BUY at

**GIBSON GIRL TRANSMITTER**  
(SCR-578B)

Emergency life transmitter. 100% complete; includes balloon, hydrogen generator, kite, signal lamp, antenna and instruction manual. Self-powered merely by turning crank. Automatically transmits S.O.S. on 500 cycles. **FULLY GUARANTEED \$29.95**

**PORTABLE F M TRANSMITTER**  
(SONOBUOY)

Operates on standard 67 1/2v Minimax and 1 1/2v Flashlight cells. Frequency 72 mc (easily doubled to 144 mc). Complete with 5 tubes and diagram. (Less batteries.) **EXCEPTIONAL BUY at \$12.95**

**DYNAMOTORS**

Ideal for Mobile  
Input: 6 or 12 volts.  
Output: 500 VDC at 160 ma.  
Voltage Regulated and Filtered.  
PE-103 (slightly used) **\$5.95**

Input: 24-28 volts. Output: 150 VDC at 260 ma. 150 VDC at 10 ma. 14.5 VDC at 5 amp.  
Voltage Regulated and Filtered  
DA-3a (slightly used) **\$4.95**

**PERMALLOY SHIELDS**  
for  
**CATHODE RAY TUBES**

3" Shield **\$1.49**  
6" Shield **1.98**

**TUBES (Brand New)**

Army-Navy Inspected

1B24	\$13.95	311	\$ 5.95
2AP1	2.25	371B	5.95
2C40	2.79	450TH	44.50
2D21	1.49	703A	1.50
2V3G	1.25	705A	4.95
2X2	.84	715B	4.95
3AP1	3.00	721A	4.95
3BP1	2.95	726/AC	7.50
3E29	2.95	801	1.75
5BP1	3.95	202	1.75
5BP4	4.95	803	8.95
5CP1	3.95	804	9.95
5JP1	19.95	805	3.75
5LP1	19.95	806	14.95
5R4GY	.98	807	.95
5Y3	.59	808	2.95
6AB7	.99	809	1.50
6AC7	.99	810	4.95
6AG5	.99	811	1.95
6AG7	.99	812	3.95
6AJ5	1.89	812H	6.95
6AK5	.90	813	5.95
6AL5	.99	814	4.45
6AR6	1.29	815	3.95
6B4G	1.29	826	2.25
6C4	.69	829-A-B	3.80
6C5	.49	832	2.25
6F6	.89	833A	49.50
6F6G	.59	834	2.95
6I4	1.50	835	2.95
6J5	.59	836	1.75
6J6	.89	837	2.50
6L6	1.25	838	3.75
6L7	.98	841	1.20
6N7	1.39	861	89.95
6SH7	.59	866	.99
6SL7	.89	872A	2.50
6SN7	.89	884	1.10
6SR7	.89	885	1.10
7A4	.95	902	2.25
7F7	1.25	913	3.00
7L7	1.59	954	.75
9JP1	14.95	955	.75
10Y	1.50	956	.75
12X3	1.50	957	.75
15E	1.50	958	.75
HK24	1.75	959	.75
28D7	.75	1005	1.98
30	.75	1616	2.95
35T/TG	3.50	1619	.75
VR90	.75	1624	.90
VR105	.75	1625	.75
VR150	.75	1626	.75
100TH	7.95	8001	8.95
100TS	3.00	8003	9.95
211	1.25	8005	4.95
75T	2.95	8011	3.75
250TH	14.95	8016	1.65
257B	14.95	8025A	3.95
304TH	9.95		

**SCR-522 100-156 MC.**  
**RECEIVER AND TRANSMITTER**

Licensed for Railway and Taxicab Use

The ideal all-purpose transmitter-receiver for work in the 100-156 mc. spectrum. Four channel push-button operation, crystal-controlled, AM, phone, mobile or fixed station service. Ideal for amateur, aircraft, marine, railroad, taxicabs, police and experimental. Amplitude modulated—High transmitter output. Receiver has 10 tubes and transmitter has 7 tubes including two 832's. 60 cycle operation. Complete conversion instructions and schematic furnished with each unit. Tube complement 2-832; 3-12A6; 1-6G6; 2-6557; 1-12J5GT; 1-12C8; 1-9002; 3-9003; 1-12AH7 GT and 3-12SG7. Complete with tubes. **\$14.95**

**BC-348 RECEIVER**

Built for continuous duty, this band switching, six band receiver with a freq. range of 200 to 500 kc. and complete 1500 kc. to 18,000 kc. Has automatic noise compensator—constant sensitivity on all bands—output at 300 or 4000 ohms—xtal filter AVC-MVC-BFO; Smooth vernier tuning; 90 turns of tuning for each band. Complete with built-in dynamotor for 28v DC. 8 tubes. Conversion instructions and schematics. Wonderful **\$49.50**  
Conversion kit for 110v-60 cyc. operation, complete \$7.50

**TRANSFORMERS—115 V 60 CYC.**  
**HI-VOLTAGE INSULATION**

1600v at 4ma; 700v at 150ma; 6.3v at 8A.	\$8.50
3710v at 4ma; 2x2.5v at 3A	9.95
2500v at 10ma	6.50
2150v at 15ma	6.50
1750v at 4ma; 6.3v at 3A	7.95
1540v at 4ma; 340-0-340 at 240ma	7.50
550-0-550v at 150ma; 5v at 3A; 2x6.3 at 3 amp	7.95
500-0-500v at 100ma; 5v ct at 3A	4.95
442-0-442v at 1000ma	9.95
425-0-425v at 150ma; 6.3v at 7.5A; 6.3v at 3A; 5v at 3A	5.95
400-0-400v at 200ma; 5v at 3A	4.95
350-0-350v at 150ma; 6.3v at 6A; 5v at 3A; 78v at 1A	4.95
350-0-350v at 35ma-XLNT for VOLT-DBLR	1.49
300-0-300v at 65ma; 2X 5v at 2A; 6.3v at 2 1/2A; 6.3v at 1A	3.49
325-0-325v at 120ma; 10v at 5A; 6.3v at 7A	3.49
350-0-350v at 85ma; 2X 5v at 2A; 6.3v at 6A; 6.3v at 3.75A	7.50
250-0-250v at 100ma; 2X 6.3 at 4A; 6.3v at 5A; 6.3v at 1A	4.95
2.5v at 2A; 5v at 3A	2.95
2.5v at 10A	3.25
5v at 115A	9.95
5v at 190A	17.50
6.3v at 6.6A	3.25
6.3v at 3.1A	1.95
6.3v at 21.5A; 6.3v at 2A; 2.5v at 2A	6.95

**FILTER CHOKES**

**HI-VOLTAGE INSULATION**

4 Hy at 250ma	\$1.98	12 Hy at 300ma	\$3.95
10 Hy at 250ma	2.49	15 Hy at 100ma	2.95
10 Hy at 400ma	4.95	15 Hy at 125ma	3.25
12 Hy at 100ma	2.95	30 Hy at 70ma	1.95
4 Hy at 600ma	5.95	1 Hy at 5 Amps	6.95
10 Hy at 200ma	1.98	15 Hy at 75ma	1.49
200 Hy at 12ma	1.39	10/20 Hy at 85ma	1.95

**BLOWER**

Hi-air blast, designed for transmitting tube service. Motor operates on 100-125v 60 cycle at 7000 RPM. Noise free with self contained chokes and filters. Enclosed in satin finish, aluminum cabinet. Measures 4" high x 2 3/4 x 3 1/4". Many uses. **Super buy at \$5.95**

**ATTENTION!**

**INDUSTRIALS—LABS—SCHOOLS—AMATEURS**

Let us quote on components and equipment that you require. We have too many items to be listed on this page. Place your name on our mailing list now for new catalog.

**RADIO HAM SHACK Inc.**  
63 DEY STREET • NEW YORK 7, N. Y.

# THEY SAID 'IT CAN'T BE DONE' !!! MONEY BACK GUARANTEE\*

For the  
**FIRST TIME**

The pure, perfect F M Tuner gives you the kind of reception you hoped for.

- No drifting
- No fading
- Hair fine selectivity
- Band coverage 87.75 to 108.75 Mc.
- The Safety Requirements of This set have been TESTED
- The MODEL is listed with the UNDERWRITER'S LABORATORIES


### WARNING!

There can be no compromise on quality of parts for F M Tuners or Receivers. F M Tuner is built up to the highest known standards.

- 3 gang copper condensers
- 13 tube performance
- Heavy duty transformer
- Own power supply
- Handsome walnut wood cabinet
- Tuned R.F. stage for increased sensitivity
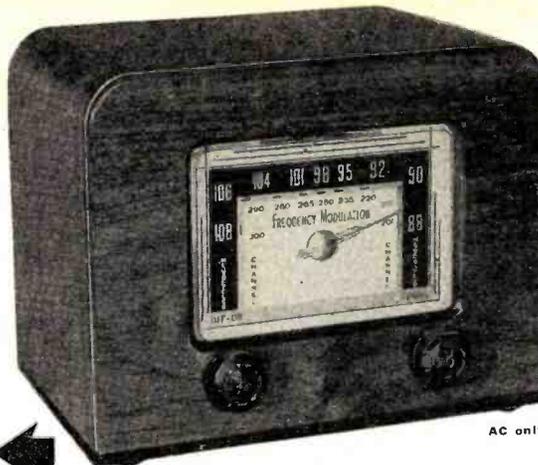
### ONLY THE F M TUNER Can Make These Claims

With these unsurpassed specifications this unit can not be duplicated for \$100.00.



AC only

**\$29<sup>95</sup>**

**A Complete Unit Includes**  
Gorgeous HAND RUBBED WALNUT CABINET  
Built-in FM Antenna  
AT NO EXTRA CHARGE


The F M Tuner modernizes your present radio. It brings all obsolete AM-FM sets up to date. You will certainly want this sensational tuner to allow you to enjoy the finest FM reception from your own radio—or phonograph. It is the new wonder worker that adds glorious frequency Modulation to any regular AM set. Precision velvet tuning. Available for immediate Delivery—Straight to Your Door.

\* If we fail to send you what we specify in our ad

All prices F.O.B., N.Y.C.; 20% Deposit, Bal. C.O.D.

**MANUEL KLEIN** 74 CORTLANDT ST.  
NEW YORK 7, N. Y.

## FS-135-C FREQUENCY STANDARD

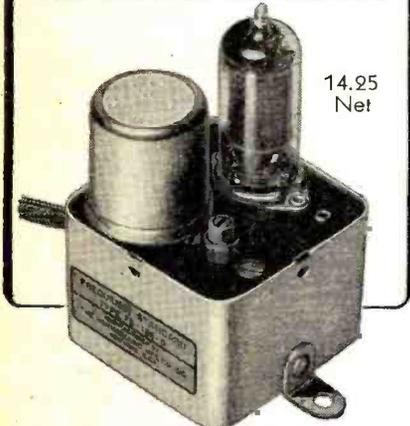

14.95  
Net

**Keeps you  
"ON THE BEAM"**

No more "hoping" you're in the band. Mount the FS-135-C Frequency Standard in your receiver, zero beat it with WWV and you'll have a frequency meter that is really accurate.


# HAMMARLUND

THE HAMMARLUND MFG. CO., INC., 460 W. 34<sup>TH</sup> ST., NEW YORK 1, N. Y.  
MANUFACTURERS OF PRECISION COMMUNICATIONS EQUIPMENT

120

## Quickest Delivery On The New TRANSVISION

**12  
INCH  
KIT**

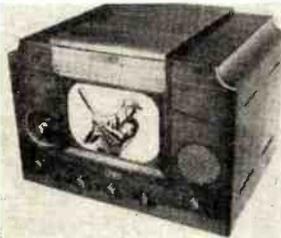

The Television Kit that is as modern as today's newspaper! Includes all latest circuit refinements . . . Big 12 Inch Picture Tube, Magnetic Type . . . Sub-assembly Units factory wired and pre-tuned to assure satisfactory operation. Price for Standard Model includes Antenna, everything needed . . . (less cabinet) **\$289**

### DELUXE MODEL

Same as Standard Model above, but with a superb built-in FM receiver covering the entire FM and Television Bands. Cut-off switch eliminates unused tubes when operated only as FM receiver. **\$359**

Write for Dealer Prices

### COMPONENT PARTS

We offer the broadest selection in the South of Television component parts for those who desire to assemble their own TV receiver. Write for FREE Manufacturers folders on TRANSVISION Kits and parts, Telectron Basic Parts, etc.

**W H O L E S A L E  
RADIO PARTS CO., Inc.**  
311 W. Baltimore St.  
**BALTIMORE 1, MD.**

## Within the Industry

(Continued from page 30)

Siegel, Ohmite Manufacturing Company.

Chairman S. P. Taylor, distributor sales manager of *Western Electric Company*, named five section chairmen for the Transmitter Division: Aviation Section, H. M. Hucke, *RCA Victor Division of Radio Corporation of America*; Broadcast Transmitter Section, C. W. Miller, *Industrial Electronic Division, Westinghouse Electric Corp.*; General Communications Section, Natale Gada, *General Electric Company*; Marine Section, C. E. Maass, *Western Electric Company*; and Transmitter Tube Section, A. Frankel, *Lamp Division, Westinghouse Electric Corp.*

\* \* \*

**WILLIAM M. MAGUIRE** has been transferred from the Salem, Massachusetts plant of *Sylvania Electric Products Inc.*, to the Distributor Sales Department of the Radio Tube Division of the company.



In his new post Mr. Maguire will serve as a products

specialty salesman in cooperation with *Sylvania* sales division managers and distributors in the eastern half of the United States.

Mr. Maguire joined *Sylvania* in 1930. During the war he was active in proximity fuze tube production and also served as a member of the electronic test equipment standardizing committee.

\* \* \*

**MARK SIMPSON MANUFACTURING CO., INC.**, manufacturers of a line of packaged sound equipment and accessories, have appointed the *W. H. Connors Company* of Denver, Colorado, as their factory representative for the states of Colorado, New Mexico, Utah, Wyoming, and parts of Idaho and Montana.

W. H. (Bill) Connors, founder and owner of the firm, is assisted by his son Carl in the business.

\* \* \*

**STEPHEN J. DEITZ** has been named head of Sales Engineering for the *Industrial Control Division of The Langevin Manufacturing Corporation*, manufacturers of broadcast audio facilities and custom-built sound installations.



Mr. Deitz was formerly connected

with *Ripley Company* where he was responsible for the design and engineering of industrial electronic controls manufactured by that organization.

The company also announced the appointment of Ralph J. Hugh as sales

**RADIO NEWS**

**MONEY BACK GUARANTEE** We believe units offered for sale by mail order should be sold only on a "Money-Back-If-Not-Satisfied" basis. We carefully check the design calibration and value of all items advertised by us and unhesitatingly offer all merchandise subject to a return for credit or refund. You, the customer, are the sole judge as to value of the item or items you have purchased.

## The New KT-30 CHANNEL ANALYZER

*The Ultimate in Signal Tracing Includes . . .*

**METER**—For direct reading of signal intensity

**SPEAKER**—For listening to the signal

**PHONE**—For checking distortion and listening to the signal in low-gain channels

Comparative signal intensities indicated directly on the meter as Probe follows the signal. A special 4 1/2" P.M. speaker with oversize Alnico V magnet is used for quality checks. Many previously designed Signal Tracers were unable to measure and check low signal intensities. This disadvantage has now been overcome for the Model KT-30 incorporates a special circuit which permits the meter to be put across the output of the Signal Tracer. To accomplish this it is necessary only to flip a front panel switch. This results in additional gain and sensitivity permitting measurement of low signal intensities. An ear-phone provided with the unit permits listening to the signal in low-gain channels. Incidentally, insertion of the phone automatically cuts out the speaker.

**\$29<sup>95</sup>**  
NET

Complete with detector probe, test leads, self-contained batteries and earphone. Heavy-gauge crystalline cabinet.



## The New Model 650-A A.C. Operated SIGNAL GENERATOR



- Operates on 110-120 Volts 50 to 60 Cycles A.C.


- R.F. Frequencies from 100 Kc. to 35 Mc. on Fundamentals in 5 bands by front panel switch manipulation. One additional band provides Harmonics from 30 to 105 Mc.
- Audio Modulating Frequency—400 Cycles Pure Sine Wave. Distortion less than 2%.
- Attenuation: Features a newly designed 3-step ladder type of attenuator (T pad). The first step provides lowest output and can be multiplied by 10 and by 100 by turning the multiplier switch.

- Hartley Excited Oscillator Electron coupled to a Buffer Amplifier. Frequency stability is assured by modulating the amplifier stage.

Complete with coaxial cable, test leads and instructions. Heavy gauge grey crystalline cabinet with beautiful two-tone etched front panel. Size 9 1/2" x 10" x 6".

**\$39<sup>95</sup>**  
NET

## The New Model CA-11 SIGNAL TRACER

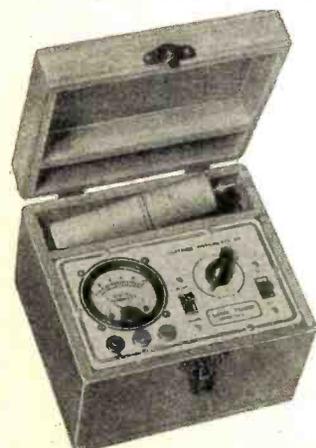

**SIMPLE TO OPERATE . . . BECAUSE SIGNAL INTENSITY READINGS ARE INDICATED DIRECTLY ON THE METER!**

- ★ SIMPLE TO OPERATE — only 1 connecting cable—NO TUNING CONTROLS.
- ★ HIGHLY SENSITIVE — uses an improved Vacuum Tube Voltmeter circuit.
- ★ Tube and resistor-capacity network are built into the Detector Probe
- ★ COMPLETELY PORTABLE — weighs 5 lbs. and measures 5" x 6" x 7".
- ★ Comparative Signal Intensity readings are indicated

directly on the meter as the Detector Probe is moved to follow the Signal from Antenna to Speaker.

- ★ Provision is made for insertion of phones.

THE MODEL CA-11 COMES HOUSED IN A BEAUTIFUL HAND-RUBBED WOODEN CABINET. COMPLETE WITH PROBE, TEST LEADS AND INSTRUCTIONS.

**\$18<sup>75</sup>**  
NET

## The New Model 670 SUPER METER

A Combination  
**VOLT-OHM-MILLIAMMETER plus CAPACITY REACTANCE, INDUCTANCE and DECIBEL MEASUREMENTS**

D.C. VOLTS: 0 to 7.5/15/75/150/750/1500/7500. A.C. VOLTS: 0 to 15/30/150/300/1500/3000 Volts. OUTPUT VOLTS: 0 to 15/30/150/300/1500/3000. D.C. CURRENT: 0 to 1.5/15/150 Ma.; 0 to 1.5 Amps. RESISTANCE: 0 to 500/100,000 ohms, 0 to 10 Megohms. CAPACITY: .001 to .2 Mfd., .1 to 4 Mfd. (Quality test for electrolytics). REACTANCE: 700 to 27,000 Ohms; 13,000 Ohms to 3 Megohms.

INDUCTANCE: 1.75 to 70 Henries; 35 to 8,000 Henries.  
DECIBELS: -10 to +18, +10 to +38, +30 to +58.

THE MODEL 670 COMES HOUSED IN A RUGGED, CRACKLE-FINISHED STEEL CABINET COMPLETE WITH TEST LEADS AND OPERATING INSTRUCTIONS. SIZE 5 1/2" x 7 1/2" x 3".

**\$28<sup>40</sup>**  
NET



## The New Model 450 TUBE TESTER

Speedy operation—assured by the newly designed rotary selector switch which replaces the usual snap, toggle, or lever action switches.

### SPECIFICATIONS

- Tests all tubes up to 117 volts.
- Tests shorts and leakages up to 3 Megohms in all tubes.
- Tests both plates in rectifiers.
- New type line voltage adjuster.
- Tests individual sections such as diodes, triodes, pentodes, etc., in multi-purpose tubes
- Noise Test detects microphonic tubes or noise due to faulty elements and loose internal connections.
- Uses a 4 1/2" square rugged meter.
- Works on 90 to 125 volts 60 cycles A.C.

EXTRA SERVICE—May be used as an extremely sensitive condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

**\$39<sup>50</sup>**  
NET



**GENERAL ELECTRONIC DISTRIBUTING CO.** Dept. RN-10, 98 Park Place  
NEW YORK 7, N. Y.

# LOWEST

**EVER and ALWAYS**  
at **STANDARD** of HEMPSTEAD

**7 TRANSFORMERS for RECEIVING, HAM and TELEVISION SETS**  
We defy all competition!

1. Trans., Filament Mfg. Raytheon, Pri. 120 V. 60 cy. Sec. 7.5 V. at 2.5 amps. Sec. 10.0 V. at 6.5 amps. Sec. 10.0 V. at 13.0 amps. All sec. are C.T. and brought out to ceramic ins. on top. .... ea. **\$2.50**
2. Mfg. Raytheon, Pri. 115 V. 60 Cy., Sec. 6.3 V. C.T. at 0.6 amp. Herm. sealed, glass lead thru ins. Round can, dia. 2" x 2 1/2" H. Turret lug term. .... ea. **\$.95**
3. #U-8380 Power Trans. cased, 4x3 1/2 x 5 1/2" H. Ceramic ins. term. Pri. 115 V. at 60 cy. Sec. 580 V. C.T. at .055 amp. Sec. 6.3 V. at 2.0 amp. Sec. 5.0 V. at 3 amp. Conservatively rated. Good for 70 mils. .... ea. **\$1.75**
4. Trans. Scope & Tel. #CYS-301229 Mfg. Sola. Sh. H.V. Trans., Round Can 3" dia. x 4" H. Herm. sealed and all term. glass bead ins. Pri. 110, 115, 120V. 60 cy. Sec. 1515 V., .015 amp. Tap. at 415 V. .... ea. **\$1.95**
5. #CYS-302153 mfg. Sola same as above but smaller size. Pri. 110, 115, 120V. 60 Cy. Sec. 735 V. at .010 amp. Sec. 2.5 V. at 3.0 amp. .... **\$1.75**
6. #C-12A-1160 Sh. Rect. case, 3x3 1/2 x 6" H. ceramic ins. Pri. 117.5 V. at 60 cy. Sec. 1400.0 V. at 0.010 amp C.T. Sec. 5.0 V. at 3.0 amp. Sec. 6.3 V. at 1.2 amp. .... ea. **\$1.95**
7. #777-1 Upright enclosed with leads. 2 27-32x3 1/2 x 3 1/2" H. Pri. 115 V. 60 Cy. Sec. 2500 V. at 2 ma. Sec. 6.3 V. at 6amp. Sec. 2.5 V. at 1.75 amp. .... ea. **\$4.95**

## TELEVISION

Space does not permit to describe our NEW STOCKS of Television Kits, Parts and Tubes. Check literature desired. A post-card will suffice.

- Television Kits
- Television Parts
- Television Tubes
- Television R.F. Supply
- R C A Television Components

20% deposit, balance C.O.D. Please include sufficient payment for transportation. Overpayment will be refunded

**Standard Parts Corp.**

235 Main Street, Dept. RN, Hempstead, N. Y.  
122

director of the *Industrial Control Division*. Mr. Hugh was formerly sales manager of the *Ripley Company*.

**TRADIO, INC.**, manufacturers of coin-operated radios, have announced the completion of a new plant in Asbury Park, New Jersey. Covering 20,000 square feet in area, the factory has a capacity of 15,000 sets per month.

The building houses the company's administrative offices as well as a new experimental laboratory. A cafeteria for employees has been set up adjacent to the factory.

**M. B. LESKIN** has been appointed head of jobber sales and advertising at *Permoflux Corporation*.

This new appointment is in line with the company's recently announced intention to enter the jobber field after years of engineering and manufacturing experience in the supplying of speakers for radio set producers.


### TELEX "MONOSET" CONTEST

**THERE** is still time for amateurs with a flair for writing to enter the Telex contest which is offering \$175.00 in cash and 25 Telex Monosets as prizes.


The contest consists of writing a 50-word statement on the subject "Why the Telex Monoset is better than old-style earphones." The first prize is \$100.00 cash and a Monoset; second prize is \$50.00 cash and a Monoset; the third prize winner will receive a Monoset and \$25.00 in cash, while the next 22 runners-up will receive Monosets.

Complete contest rules and official entry blanks are available at local jobbers. Entries must be postmarked by midnight October 15, 1947.

A new projection television receiver, said to embody the world's largest screen, was recently demonstrated to the press by the Telicon Corporation of New York City. Designed primarily for public meeting halls, taverns and other public places, this unit which provides three square feet of screen, can be viewed by several hundred people at a distance of approximately 100 feet under ordinary room lighting conditions. Set is operated by push-button tuning system.

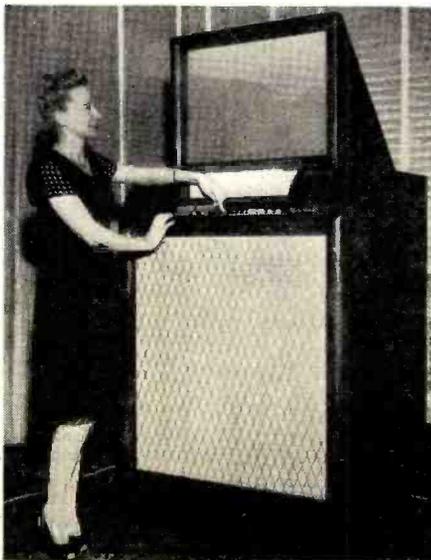

## NEW F. M. TUNER!

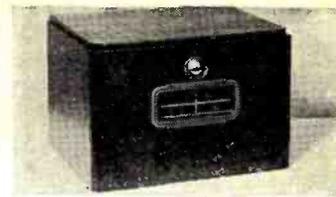

Here is what you have been waiting for to attach to your present amplifier or radio to give you staticless, quiet radio reception characterized by the Frequency Modulation method of transmission.

The new 11 tube **COLLINS FM** tuner is supplied as a chassis unit, with rack panel or in attractively styled cabinets (illustrated) presented in a variety of leatherette finishes. Its utility is therefore three-fold in being readily adaptable to any existing set-up: console mounting, recording studios and broadcast stations or in the living room of your home, blended perfectly with the surroundings.

Not a competitive tuner but the best.

See your local jobber and if he cannot supply you write us direct.

**COLLINS AUDIO PRODUCTS CO., INC.**

126 PARK ST. WESTFIELD, N. J.

### FALL CLEARANCE SPECIAL STANDARD BRAND RADIO TUBES ALL TYPES — 50% OFF LIST

Five Tube Superhet Kit. Attractive bakelite cabinet (9x6x5) & complete parts for 5 tube superhet, using 50L6, 35Z5, 12SA7, 12SQ7 and 12SK7. (Less tubes) **\$10.45**

G.E. Solenoid operated contactor #C12820—controls 6 circuits—operates on 115V. 60CY., 4 1/2 x 9 3/4, 15 amps contacts double break each circuit. G.E. Catalog price \$25.00. Your price ..... **\$4.95**

Three Tube Phono Amplifier, with tone and volume control. Price less tubes... **\$2.95**

5" PM Speakers \$1.25; 50L6 output 55c; 100 1/2 watt carbons. PER HUNDRED... **1.90**

U.T.C. "S-6" Input Xtnr-line or mike to grid; Dealer's price \$3.10. Your cost... **1.25**

Weston #476—3 1/2" Bakelite: .0-8V AC ..... **\$3.95**  
Weston #506—2 1/2" metal case, scale mkd .0-3V, movement 0-5 ma. . . **2.95**  
Weston #507—2 1/2" metal case scale mkd .0-10, movement 0-2 ma. .... **1.95**  
GE 0-15V DC, 2 1/2" bakelite case. . . **2.95**  
GE 0-15V AC 800 cycles bakelite case, 2 1/2" ..... **2.50**

Advance Relay 115V 60cyc. DPDT. 10 amp contacts ..... **\$1.95**

Leach 6V DC 3 pole norm. open. #1024... **1.25**

GE 110V DC, S.P.D.T., 10,000 ohms resist., operates on 8 mills. .... **.75**

Allied 24V DC, D.P.D.T., 10 amp contacts ..... **.40**; 3 for **1.00**

Westinghouse Filter chokes—4 hy @ 90 mills, 300 ohms res. hermetically sealed 2" can ..... **.69**; 5 for **3.00**

3" Vibrating Bell, 115V, 60 Cyc. Rugged Construction .SPECIAL **\$1.25**


5 pole, on & off rotary switch with knob; 10 amps. @ 120V Mfg. Arrow H&H ..... **.59**; 10 for **5.00**

25% deposit with order; balance COD; save COD charges, send full amount. Schools—Labs—Industrials—Send us your requirements. Get on our mailing list.

**RADIO DEVELOPMENT & SALES CO.**  
382 State Street Brooklyn 2, N. Y.

**RADIO NEWS**
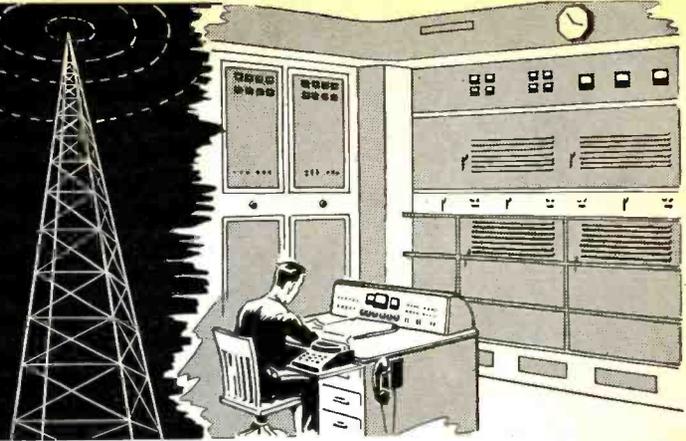
# You can be a BROADCAST TECHNICIAN or ENGINEER...



## ADD TECHNICAL TRAINING TO YOUR PRACTICAL EXPERIENCE

USE CIRE TRAINING AND COACHING SERVICE—AND GET YOUR "TICKET" IN A FEW SHORT WEEKS!

Employment opportunities are plentiful. Now is the time to get in on the ground floor. Permanent employment—steady, good pay. Advancement to those who are qualified. These are only a few of the attractive features of this interesting, pleasant employment!

Get your license without delay. Let Cleveland Institute prepare you to pass the FCC license examinations, and to hold the jobs which a license entitles you to, with CIRE streamlined, post-war methods of coaching and training.

## Your FCC Ticket Is Recognized in All Radio Fields as Proof of Your Technical Ability

More than ever before an FCC Commercial Operator License is a sure passport to many of the better paying jobs in this New World of Electronics.

Employers frequently give preference to the license holder, even though a license is not required for the job. Hold an FCC "ticket" and the job is yours!

### Hundreds of Satisfied, Successful Students

"I have taken the first class phone license examination and received my first class ticket last Saturday, May 31. In closing I must say yours is an excellent radio course, and I really appreciate your help and the fine service you have rendered me."

Student #2876N12

"I passed the FCC examination in radiotelephone 2nd class, at Detroit on June 3rd, and I want to thank you for your ready assistance as my instructor on Section I of Nilson's Master Course."

Student #2799N12

"I have had my 1st class radiotelephone license since March of this year, and plan to continue with your course since I find it a great help in studying transmitters."

Student #2779N12

"After sending in Lesson E-9 I took the commercial operator's license examination for 2nd class radiotelephone, and passed O.K. I received the license last week."

Student #2772N1

**FREE BOOKLET**—Tells you the Government requirements for all classes of FCC commercial licenses. (Does not cover Amateur License examinations.) Use coupon below for Booklet B.

## OTHER

Cleveland Institute Home Study Courses Offer Complete Technical Radio Training from Low-Level to College-Level, for the Radioman with Practical Experience!

### COURSE A—Master Course in Radio Communication

A complete course covering the technical fundamentals of radio-electronics, for the radioman who wants a general review. Includes preparation for Broadcast station employment.

### COURSE B—Advanced Course in Radio Communication Engineering

A genuine college-level radio engineering course, completely mathematical in treatment. For the advanced radioman with considerable practical experience and training.

### COURSE C—Specialized Television Engineering

An advanced college-level course for the radioman who has had formal training equivalent to A and B.

These three courses in radio-electronics offer a complete, thorough technical training for the radioman who wants to cover the field. Available separately or combined.

**FREE CATALOG**—Describes all Cleveland Institute home study courses—tells of CIRE unique, post-war methods of training. Use coupon below for Catalog A.

How To Pass  
FCC  
LICENSE  
EXAMINATIONS

CLEVELAND INSTITUTE  
of  
RADIO ELECTRONICS  
Terminal Tower - Cleveland, Ohio

Don't Delay—  
Write Today!

Approved for  
Training  
Under "G-I  
Bill of Rights"

## HOW TO PASS Commercial Radio Operators' FCC LICENSE EXAMINATIONS...

CLEVELAND INSTITUTE OF RADIO ELECTRONICS  
Contractors to the Canadian Broadcasting Corporation

RN-10 TERMINAL TOWER

CLEVELAND 13, OHIO

Cleveland Institute of Radio Electronics  
RN-10 Terminal Tower, Cleveland 13, Ohio

Gentlemen:  Please send me your Booklet B, "HOW TO PASS THE FCC COMMERCIAL LICENSE EXAMINATIONS," and information about your home study course for preparation for FCC License Examinations. (Does not cover Amateur License Examinations.)

Please send me your Catalog A, describing all of your home study radio-electronics courses.

I desire training in course  A  B  C.

Veterans check for enrollment information under G-I Bill. NO OBLIGATION—NO SALESMEN.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

ZONE \_\_\_\_\_

STATE \_\_\_\_\_

### CONSTANT VOLTAGE STABILIZER

G.E. Cat. #69 G 30152, Input 103 to 127 volts vs. to 63 c.p.s. Output taps 110, 115, 120 and 125 volts. Volt. Reg.  $\pm 1\%$  at norm. freq., 850 V.A., 7.7 Amps at 93 F.F. Dimensions 30" x 15" x 10". Net wt. 280 lbs. @ \$59.50

**TACHOMETER GENERATOR** G.E. Type CM-5 Model 2CMS5EA @ \$59.50

**A.C. GEN. VOLTAGE REGULATOR**, made for 7.5 KVA, 120 V., 60 cycle Gen., Field current 0.2 Amps.. Max. regulated field resistance 750 ohms. With external variable 150 ohm resistor for predetermined voltage settings. Ward Leonard type 5680 @ \$4.95 each. Ten for \$39.50

**FILAMENT TRANSFORMER**, G.E., 110 volt, 60 cycle input, 2.5 volt 40 Amp. Output, 100 KVA 3KV, Insulation @ \$2.75 each. Ten for \$17.50

**STEP DOWN TRANSFORMER**, Jefferson Electric, 115 volt 60 cycle primary 20 volt, 10 Amp. secondary, mounted in watertight box @ \$3.95 each, Ten for \$39.00

**VARIABLE RHEOSTAT**, Ward Leonard 8" Class, 20 ohms 4.05 Amps. Complete with all hardware @ \$3.50 each. Ten for \$29.50

**INSULATION TESTER** 0-20 and 0-200 Megohms. Full scale, 0.5 and 0.5 Megohm, center scale. The original unit, The Weston Model 796 Insulation Tester, operated at 500 volt test potential supplied by eight 67 1/2 volt batteries. This has been modified by us to utilize two 1 1/2 volt, standard #6 dry cells and a vibrator for the 500 volt test potential, thereby eliminating the high replacement cost of batteries. Enclosed in a hardwood carrying case 8 3/4" x 9 1/4" x 8 1/4". The Weston Model 801, 4 1/2" Rectangular 0-50 microampere meter assures extreme accuracy on all ranges. Surplus-New—Guaranteed @ \$39.50 each.

**PORTABLE CURRENT TRANSFORMER** Weston Model 461, type 4. This unit can be used with any precision 5 Ampere A.C. Meter to extend the ranges of the meter to 50, 100, 200, 500 or 1000 Amperes A.C. Accuracy within 1/4 of 1%; Normal Secondary Capacity—15 VA; Binding Posts for 50 Ampere tap; Inserted—100, 200, 500, 1000 and 1000 Amperes; Insulated for use up to 2500 volts. List Price \$98.00; only \$35.00 each.

### METERS

Simpson, 25, Signal Strength ("S") Meter, 3 1/2" rd fl bake case. Use this on the plate circuit of your receiver to show the relative strength of incoming signals. Sc calibrated in dB, 100 dB above 1 microvolt. 5 MA zero right mvt with translucent sc. for internal sc illumination from rear of meter. Comp with socket, lamp and leads. For further details refer to pages 164-165 & Fig. 730 B of Radio Amateur's Handbook @ \$4.50

Weston, 30, Type 21 Standard Decibel Meter, 5 1/2" rd fl bake case, minus 10 to plus 6, 6 M.W., 600 ohms; General purpose type, 0.5-0.7 Second to final reading, 45-60% overdrive, 5000 ohms internal resistance at ODB. Ideal for home recorders. \$8.50

Voltage Polarity Phase Rotation Tester, Triplett 337 AVP, Checks 115, 220 and 440 line voltage; locates open circuits, blown fuses, damaged wiring, etc.; Indicates whether A.C. or D.C. and polarity of D.C.; Checks phase rotation to determine direction of rotation of motors, operation of controls, etc. Consists of a 3" square meter and 3 small polarized vane movement in small handy sized case. Complete with 36" leads with test clips. \$10.00

Time Totalizer Indicates up to 9,999.9 hours for 50 or 60 cycles operation on 105 to 130 volts. Black scale, 3" rd fl bakelite case, clamp mounted. Made by Industrial Timer Corp. \$4.00

Weston 667, Output Meter, 3 full scale ranges 0-2, 0-10, 0-50 Volts, Audio Frequency, complete with 3" lead with pin plugs and plug (PL 55). \$7.50

Weston 507, 750 MA, sc cal 0-10 Antennae Current Indicator comp with test clips, 2 1/2" rd fl bake case, black scale. \$2.95

Weston 507, 3 A, black scale, 2 1/2" rd fl bake case. \$3.50

W.H., NT-35, 3 A, 3 1/2" rd fl bake case. \$5.50

Weston 301, 500 V, D.C., 1000 ohms per volt, rd fl bake case. \$9.00

Weston 301, 3 1/2" 4 K.V., with external precision resistor. \$8.50

G.E., DO-41, 2.5 KV, black sc, with 1000 ohms per volt, external wire wound resistors. \$6.95

W.H., NX-35, 1.5 KV with 1000 ohms per volt, ext prec wire wound resistor & mtg clips. 3 1/2" rd fl bake case. \$7.25

W.H., NX-35, 20 KV with ext prec wire wound 1000 ohms per volt resistor and mtg clips. \$21.00

Simpson 25, 1 MA, 3 1/2" rd fl bake case. \$4.50

Simpson 25, 15 MA, 3 1/2" rd fl bake case. \$4.50

Simpson 25, 200 MA, 3 1/2" rd fl bake case. \$4.50

G.E., DO-41, 200 microampere mvt., knife edge pointer, sc mtd "Set Carrier" supp with paper V.O.M.A. sc, 3 1/2" rd fl bake case. \$4.95

Triplett, 100 ua mvt, rd fl bake case, made for 666-SC Analyzer; sc cal in Volts, MA & Ohms, 3 1/2" 50 fl bake case. \$6.95

Weston 476, 30V, 3 1/2" rd fl bake case. \$4.95

W.H., NA-35, 15 V, (100 MA) 3 1/2" rd fl bake case. \$3.95

W.H., NA-35, 150 V (10 MA) 3 1/2" rd fl bake case. \$5.50

Weston 476, 4 A, A.C. 3 1/2" rd fl bake case. \$4.95

### SPECIAL COMBINATION OFFER

A set of 8 useful meters which can be used to build the following:

Radio Circuit Analyzer Repair Shop Test Panel  
Electro Plating Panel Lighting Plant Panel

**SPECIAL OFFER \$925**  
ALL 8 METERS

A.C.-D.C. VOLTMETER Sterling 2" dia. ring mtd. stamped metal case polarized vane type. 250 Volts 5% Accuracy.

A.C.-D.C. AMMETER Sterling 2" Sq. stamped metal case, polarized vane type. 15 Amperes, 5% Accuracy.

D.C. MILLIAMMETER G.E. DW-41, 2 1/2" rd fl bake case, 1 MA mvt. Complete with paper Volt-Ohm-Milliammeter scale, 2% Accuracy.

D.C. AMMETER W.H. F1 (NX-35) 2 1/2" rd fl bake case. Black scale, 150 Amp. with ext. shunt, 2% Accuracy.

D.C. VOLTMETER G.E. DW-51, 2 1/2" rd fl bake case, black scale, 15 Volt, 2% Accuracy.

AUTOMOTIVE AMMETER U. S. Gauge Co. 2" dia. clamp mtd. polarized vane type. 30-0-30 Amp. charge & discharge, 5% Accuracy.

R.F. AMMETER G.E. DW-44, 2 1/2" rd fl bake case; Black scale, 6 Amperes Radio Frequency. 2% Accuracy.

A.C. VOLTMETER G.E. AW-41, 2 1/2" rd fl bake case, black scale, 15 Volts, 800 cycle. Accuracy within 2% on 800 cycle and 7% on 60 cycle.

All Prices Net, F.O.B., N. Y.—include sufficient postage, excess will be refunded. C.O.D.'s not sent unless accompanied by 25% Deposit.

All items are Surplus-New-Guaranteed. Orders accepted from rated concerns, public institutions, etc., on open account.

The above is only a partial listing of the many items we have in stock. Send for free circular. MANUFACTURERS, EXPORTERS, DEALERS.—we invite your inquiries.

### MARITIME SWITCHBOARD

336 Canal Street New York 13, N. Y.  
Worth 4-8217

### Mobile FM Rig

(Continued from page 45)

fundamental range of 9053 kc. to 9900 kc. is required in the oscillator.

The controls as seen in the front view, Fig. 1 are, lower left, oscillator tuning condenser  $C_{10}$ ; lower center, tripler plate tuning condenser  $C_{16}$ ; lower right, meter jack. The connections for the antenna and receiver are located on either side of the six prong male Jones plug used for the power terminals. The final tank condenser control ( $C_{21}$ ) may be seen near the right hand side.

Because of their small size, regular male single contact microphone connectors were used for the antenna and receiver connections. To provide as much ventilation as possible, a series of 1/4 inch holes was drilled in the bottom of the cabinet and along the upper sides. The cabinet is mounted

to a wooden base by means of four one-pound shock mounts. As the total weight of the unit is only three and one-half pounds, this method of mounting provides adequate cushioning against mechanical shock.

Only five of the six terminals on the power plug are necessary for this application so two of the terminals were tied together and used for the high voltage terminal. By removing the link between these two terminals, a modulation transformer may be connected, and the rig plate-modulated by any modulator capable of 15 watts of audio.

The phase splitting network across the oscillator coil, consisting of  $C_3$  and  $R_3$ , uses values that are quite different from those usually used in transmitters of this type. The particular values used were derived by calculation according to the figures given in "Frequency Modulation" by Hund. With the values given, the reactance of condenser  $C_3$  is approximately 2000

### IDENTIFYING CATHODE-RAY TUBES

THE rapidly expanding field of uses for CR tubes and the development of phosphors with characteristics adaptable to special applications has made it increasingly difficult to determine a tube's exact characteristics at a glance. There is, however, a standard system for designating such tubes, administered by the Data Bureau of the Radio Manufacturers Association, and used by most manufacturers with one or two exceptions.

The section governing the nomenclature of these tubes is quoted for your information and future reference:

"RMA Standard M8-402: It shall be standard to use the following system of type designation for television picture tubes:

"The designation shall consist of three groups of symbols. The first symbol will be a number to correspond to the nominal maximum bulb diameter in inches. A tube having a maximum diameter within plus or minus one-half of an integer shall be assigned that integer. A tube falling exactly on a one-half inch dimension shall be assigned the next larger integer. The second symbol shall be a letter or a double letter to distinguish between tubes having the same nominal maximum bulb size. The third symbol shall consist of the letter P and a number to designate screen characteristic."

The screen characteristic is defined by two properties, color and persistence, and is coded by further RMA standards under the designations P1, P2, etc. As an example, consider a 5LPI. From the designation it may be determined that the tube is a 5" unit of the "L" series and has a green medium persistence screen such as used in oscilloscope or radar work.

Table 1 gives a breakdown of screen characteristics for the various screen number designations. Approximate definitions of the terms used for qualitative description of persistence are given in Table 2.

Long:	Visible for more than 1 second.
Medium:	Luminescence is below 10 per-cent of initial brightness within 30 milliseconds or less.
Short:	Luminescence is below 10 per-cent of initial brightness within 3 milliseconds or less.
Very Short:	Luminescence is below 10 per-cent of initial brightness within 30 microseconds or less.


Table 2

Table 1

Phosphor	Color	Persistence	Principal Application
P1	Green	Medium	Oscilloscope & Radar
P2	Blue-Green	Long	Oscilloscope
P3	Yellow	Medium	Oscilloscope
P4	White	Medium	Television
P5	Blue	Very Short	Oscilloscope (high-speed photography)
P6	White	Short	Color Television
P7	Blue	Long	Oscilloscope & Radar
P10	Purple	Very Long	Oscilloscope & Radar
P11	Blue	Short	Oscilloscope (Photography)
P14	Blue	Long	Radar

Courtesy of General Electric Company
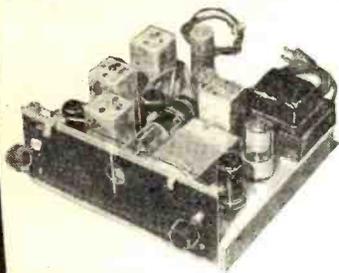
# ROCK BOTTOM PRICES! ON ALL TOP QUALITY ITEMS




## F. M. TUNERS (88-108 MC.)

Armstrong circuit. 8 tubes: 1 rf. mixer osc. 2 I.F.'s, 1 limiter, 1 disc. rectifier, tuning eye (not furnished), 3 gang tuning condenser, built in 110V A.C., 300 V power supply, 300 ohm dipole input. Each unit checked and guaranteed. Completely wired, ready to plug in. Supply limited.

**\$24.95**  
With 7 Tubes

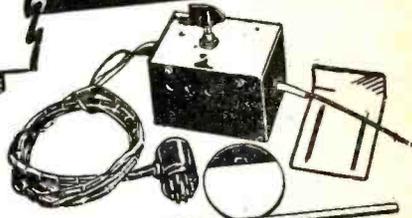
*Special Purchases!!*  
**LIMITED SUPPLY ONLY**  
**ALL ITEMS SUBJECT**  
**TO PRIOR SALE**  
*Order Now!*



## F. M. CONVERTER

From old 42-50 Mc. band to new 108-88 Mc. F.M. band. Bring your old F.M. set up to date with this easy to install converter. Formerly \$15.00. They won't last forever!

**Our Price \$5.00 Complete**

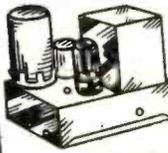

## 12V Vibrator Pack

Output 270 V.D.C. @ 65 Ma. Ideal for aircraft or boats.

**\$7.50**

## 12V Vibrator

4 Prong.  
**75¢ Each**  
**10 for \$5.00**



## CRYSTAL PHONES

200-600 ohms. Unusually sensitive. Less rubber pads. Used. Guaranteed perfect working order.

**50¢ Each**  
**10 for \$4.00**



## SOLDERING IRON \$1.50 Each

100 Watt 110V AC



# TUBES!

YOUR CHOICE **50¢**

OZ4	6J5	12C8
1G5	6K7	12SA7
1A7	6J7	12SF7
1R6	6B8	12SG7
155	6SA7	12SH7
1T4	6S7	12SK7
2C26	6SJ7	12SN7
1LC6	6SN7	12SQ7
354	6SK7	31
5R4	6SQ7	35L6
5U4	6V6	35W4
VR150	6X5	35Z4
5Y3	6Y6	50B5
5Z3	7F7	50L6
6AB7	7N7	VR105
6AC7	12A6	954
6AG5	12AT6	955
6AG7	12AH7	956
6C4	12BA6	9004
6F6	12BE6	9006
6H6		2051


6SL7	\$0.75	3B24	\$3.00
100TH	5.00	5CP1 with socket	3.96
250TH	5.00	715B	3.00
6B4	.75	724B	1.00
1LH4	1.00	1N5	.75
2C40	2.50		

Special bonus: Deduct 10% for orders of \$20 or over.  
All popular brands, some in original cartons, money back guarantee.

## XTAL DIODES

1N22 1N27 50¢ Each  
1N23 1N29

## THIS MONTH'S FEATURE KITS!

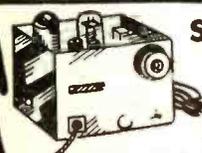

## Short Wave Experimental Receiver Kit

2-30 MC. 2 dual triodes. 6SL7 and 12SN7, provide 4 tube sock. Kit comes complete, except speaker

**4.00 Per Kit**

## BROADCAST BAND TRF



**\$6.95**  
Less cabinet. Includes speaker, tubes, wound oscillator coil, etc., etc.

Most amazing 2 tube circuit on the market, provides 4 tube operation. Has nearly as much sock as ordinary 6 tube superhet. Ideal for the beginner, student or hobbyist. Can be built in several hours.

## WALKIE TALKIE



**\$10.00**  
**2 for \$18.50**

Freq. ranges: 10, 5, 2 1/2 meters. 2 tubes gives 4 tube operation. Operates off 90V battery. Operating range up to 20 mi. Includes speaker, tubes, etc.

## 25 POUNDS OF RADIO PARTS

We are swamped with tremendous quantities of parts that cannot be placed in our regular stock. Worth many times selling price. We must sell at the ridiculously low price of

**25 lbs. for \$3.00**

25% Deposit on All C.O.D. Orders. All Items F. O. B. Chicago, Ill.

# GUARANTEED NEW AND PERFECT METER BARGAINS

YOUR CHOICE **\$3.00**

- Sangamo 0-50 DC MA, both sides center, 3" round.
- Triplet 0-15 RF Amps, 3" round.
- McClintock 0-15 DC MA; 0-150 MA; 0-300 MA; 3" square face.
- Weston 0-200 MA, 3" round.
- Aero Frequency Meter 330-420 cycles per sec.; 125V; 3" round.
- McClintock 0-5 MA, 3" round.

Westinghouse A.C. Industrial Meters  
KA-25 Type, 6" Square Face, Brand New! Original Cartons

YOUR CHOICE **\$15.00**

- 0-200 Amps
- 0-250 Amps
- 0-300 Amps
- 0-150 Kilowatt
- 0-600 Volt with Shunt

# IRVING JOSEPH

220 S. Halsted St., Chicago 6, Ill.

*Built so You  
Can Read it!*

**MULTIPLEX**  
VOLT - OHM - MILLIAMMETER



This is your instrument for all day, every day use. The Multiplex Model 458 is a rugged, accurate, portable, bench-type V.O.M. built to high industrial standards by one of America's pioneer makers of test equipment.

**Multiplex Features:**

Big 5½" d'Arsonval movement meter. 1000 ohms per volt. Multipliers accurate within 1%. Rotary range selector. Copper oxide rectifier for A.C. range accuracy. Priced remarkably low for **\$26<sup>00</sup>**—NET an instrument of this quality—only.

See Your Jobber or Write for Bulletin 458

**CHICAGO INDUSTRIAL INSTRUMENT CO.**  
536 West Elm Street - Chicago 10, Illinois

**All Popular Ranges:**

- Volts D. C. . . . . 0-5/10/50/100/500/2000
- Volts A. C. . . . . 0-12.5/25/125/250/1250
- Milliamperes D. C. . . . . 0-1/10/100
- Milliamperes A. C. . . . . 0-2.5/25/250
- Ohms Full Scale 1000/200,000/2,000,000
- Ohms Center Scale . . . . . 50/2250/22,500
- Output . . . . . -5 to +55 Decibels

ohms or one fifth the value of  $R_p$ . As reactance tubes are very sensitive to voltage changes, the plate voltage for the 9001 is obtained from the voltage regulator. Stabilization of the voltage in this manner prevents any undesired frequency shift caused by varying plate voltage.

When first tried, the frequency drift due to warm up was quite serious. However, with the values of condensers shown in the oscillator circuit, this drift has been reduced to where the starting frequency and final frequency difference is only 900 cycles after 15 minutes' operation. This value is better than most crystal oscillators. In other mechanical layouts it would

**NEW NBFM AUTHORIZATION**

A NEW order recently promulgated by the Federal Communications Commission specifies the frequencies and types of emission available for the operation of amateur radio stations. The order includes the authorization for use of the band 5650-5925 mc. which the Commission recently allocated to replace the amateur band 5650-5850 mc. The allocation of the wider band contained a qualification to the effect that amateur operations between 5775 and 5925 mc. are subject to such interference as may result from the operation of industrial, scientific, and medical devices assigned to the frequency 5850 mc.

The order also authorizes the use of narrow band frequency modulation for radiotelephony in the bands 3850-3900 kc. and 14,200-14,250 kc., by Class A amateur radio operators at stations licensed to the holders of Class A amateur radio operator licenses. In addition, the holder of any class of amateur radio operator license is authorized to use narrow band FM radiotelephony at any licensed amateur radio station on frequencies from 28.5 to 29.0 mc. and from 51 to 52.5 mc.

This authorization is on an experimental basis until further order of the Commission, but in no event to continue beyond August 1, 1948. The Commission stresses the fact that this authorization is on a temporary experimental basis, subject to cancellation at any time, if after a reasonable trial period, experience shows that NBFM is not desirable in portions of the amateur phone bands also occupied by AM amateur signals.

probably be necessary to use different values of compensation.

The microphone used is a surplus T-17 type. As there was much more audio available than necessary, this was reduced somewhat by the inclusion of a 200 ohm resistor in the microphone lead. This also improves the audio quality as the microphone voltage is reduced to a low value.

When construction has been completed, the shorting link across the power plug should be opened and the 2E30 tripler removed from its socket. The deviation control  $R_2$  should be set at minimum.

An accurately calibrated receiver or frequency meter, capable of tuning the range of 9000 kc. to 10,000 kc.,

**RADIO NEWS**

*Every Radio Serviceman Needs This*

**FREE**

68 PAGES

**AC-DC BALLAST TUBE MANUAL**

To get YOUR FREE COPY of this indispensable manual (value \$1.50) merely mail in to JFD Factory 12 flaps from JFD Radio Dial Belt envelopes; include 10¢ in postage to cover mailing cost. (Buy your JFD Dial Belts and Belt Kits from your nearest parts jobber.)

JFD's new 68-page Ballast Manual is a treasury of information for Radio Servicemen and Dealers — Lists more than 3000 radio ballasts — ACDC Ballasts for Fluorescent lights and electrical appliances — 220 volt to 110 volt Stepdown Ballasts.

Send 12 Envelope Flaps to:  
**J.F.D. MANUFACTURING CO. INC.**  
4109-4123 FT HAMILTON PKWAY. BKLYN 19, N. Y.

**R. C.'S BARGAIN SPECIALS FOR OCTOBER**

Wire player kit No. 200 consists of 1 Alliance motor & turntable, Crystal pickup, control ws., AC cord and 3" open type base—the kit . . . . . \$7.95

Webster 56 changer, a 3" leatherette covered base given free with each changer. . . . . \$26.66

Wet electrolytics, 18 mfd.-300 V., each. . . . . 19

6" PM speakers special, each. . . . . \$1.49

In lots of ten, each. . . . . \$1.35

A complete portable sound system, consists of 25 watt amp., leatherette covered dual case. 2-12" PM speakers, 2-25' speaker cords and plugs and CX Turner desk mike with cord and stand . . . . . \$64.50

A small portable sound system consists of 15 watt amp., leatherette covered case with back, 1-12" PM speaker and 25' cord with plug and crystal desk mike with cord and stand. Complete . . . . . \$41.65

1 lb. bundles 36" length hook up wire. . . . . 59

500M ohm volume controls ws. ½" or 1" shaft —your choice, each. . . . . 39

500M ohm controls ws. and 2" shaft, each . . . . . 49

CRYSTALS: 80 meter 3500-4000, 40 meter 7000-7425KC, 10-20 meter 7300-7425KC. All crystals mounted in FT243 holders, ea. . . . . 74

Crystal finishing kit. . . . . 79

8" pressed fibre car radio speaker, baffle grey, wrinkle finish, each. . . . . 98

16 x 8 mfd. 450 V. upright lug mounting, each . . . . . 79

Dual 20 mfd. 150 V. tubular 4 leads out, each . . . . . 32

96" side cowl car ant., 34" leadin, ea. . . . . \$1.79

All items subject to prior sales. 20% deposit with order.

Write Dept. RN18 for latest circular

**R. C. RADIO PARTS & DISTRIBUTING CO.**  
731 Central Ave. Kansas City 6, Kansas

# SPRAGUE TRADING POST

## SWAP—BUY OR SELL

**FOR SALE**—10" meter receiver, 1851-HY615-6F8; with coils, tubes, less power supply \$14; 5 band coil switch turret assembly, 75 watts, \$4; T-200, good condition \$5; high voltage replacements for \$72 rectifiers, exact substitute, will deliver 8000v d-c, \$2.50 ea., \$4.50 pair. Bill Benner WoPJo, 145 S. Maple, Webster Groves 19, Mo.

**FOR TRADE**—30 watt, 80 meter, fone, c-w transmitter complete with tubes, coils, power supply and mike. Want TR4 with tubes and power supply or similar 2 meter transceiver. James Rector, W6ZRB, 3555 W. 109th St., Inglewood, Calif.

**FOR SALE**—Melssner communications 14" receiver, 5 band 38 to 555 meters with 12" dynamic speaker in excellent condition, everything included, \$125. Donald E. Schultz, Edcouch, Texas.

**SELL OR TRADE**—BC-312 receiver, revamped, write for details. Want IJ1289 or what have you? Meyer Birnbaum, 70 Tolson Ave., Winnipeg, Manitoba, Canada.

**SELL OR TRADE**—Recorder, Presto K, \$280 or swap for HalliCrafter transmitter HT9 or Collins 32-RA for 10 meter operation or a comparable phone-CW transmitter. W6PFK, Eichenberg, 2271 Hayes St., San Francisco, Calif.

**FOR SALE**—Complete 200 watt transmitter with 813 final, mod. 811's in rack cabinet; Sky Champ receiver and spare parts of all kinds including CR tubes, transmitting tubes, etc. Jim King, WJZM, Clarksville, Tenn.

**FOR SALE**—Millen R-9'r, complete with GAK5, \$20. Want Stancor P-6170 or equivalent. George M. Boyd, W9S1T, 2457 Armitage Ave., Chicago 47, Ill.

**FOR SALE**—Latest HalliCrafter S-39 Ranger portable 9 tube battery or ac-dc operated communications receiver. Aligned and complete with batteries and instruction manual; used less than 100 hours, \$100. W. H. Horton, W4FHB, Box 666, Stanford University, Calif.

**FOR SALE**—HalliCrafter 15 tube receiver, SX-28; 550 kc—42 mc, including matching HalliCrafter-Jensen bass reflex cabinet with 12" speaker. Excellent condition, \$200. Otto Pollei, Jr., 2122 Edgeland Ave., Louisville, Ky.

**FOR SALE**—HalliCrafter S-36, practically new \$300; also partly assembled Meissner traffic master \$75. Lon G. Rankin, 738 Patterson Ave., San Antonio, Texas.

**SELL OR TRADE**—BC957A radar receiver-indicator including 31 tubes, 5HP4 and WE708B, UHF grounded grid amplifier; 13 tube receiver with 7 IF's; sweep generator and amplifier; video amplifier; 115v-60r. H.V. supply, etc.; sold by W.E. for \$2500. Want communication receiver or 5" oscilloscope. W. G. James, 93 Georgia Ave., Oak Ridge, Tenn.

**FOR SALE**—Signal Corps bug, J-36 used little \$4. Omar Evans, Hazelton, W. Va.

**FOR SALE**—New Dumont 5" oscilloscope, Philco audio signal generator, small amplifier, 35 watt phone-cw transmitter. Wayne Storch W9FOC, Beecher, Ill.

**WILL TRADE**—100 watt, 7 tube transmitter, 4 bands M.O.P.A. 3—807's. Want good communications receiver, good tube tester or what have you? Gordon Simkin, 5-65 Farago Ave., El Monte, Calif.

## FREE! This Giant Sprague TEL-U-HOW WALL CHART

— from your Sprague Distributor

Ask your nearest Sprague jobber for your copy of the SPRAGUE TEL-U-HOW WALL CHART. Just the thing for hanging on the wall of your shop. Its professional appearance impresses customers. The material it contains will help you do jobs easier, better, faster.

Beautifully lithographed in colors, size 22" x 28", the chart includes handy service application data; diagrams and descriptions of common circuit troubles involving capacitors; general replacement data on electrolytics; formulas; transformer, resistor and capacitor color codes; schematic; and similar invaluable service information. Everything is arranged for quick, easy reference. Popular Sprague Capacitors and Koolohm Resistors are illustrated. Don't miss it!



**FOR SALE**—DeLuxe Midwest radio, 16 tubes A-1 condition, chassis, all tubes and speaker. Needs re-alignment on high frequency bands. \$35—Frank Bou, W3ESX, 3131 N. Percy St., Philadelphia 33, Pa.

**FOR SALE**—HalliCrafter model SX11 receiver complete with matched 12" speaker. Recently installed new bypasses, filter condensers, and aligned set, covers .55 to 37.5 mc. \$40. W. M. Skinner, W8ROV, 6208 Neff Road, Detroit 24, Mich.

**WILL TRADE**—TR-4 on 2 meters with tubes less supply. Want communications receiver in good condition or what have you? Wm. A. Yeager, W9OAE, Wisconsin Rapids, Wis.

**WANTED**—HalliCrafter S-38 receiver also battery portable. Charles Holstein, 246 E. 148th St., Bronx, N. Y.

**FOR SALE**—3 tube communications receiver, 9 wave bands designed by M. Silver; 12" Jensen speaker in bass reflex cabinet \$75. J. G. Deutsch, 4715 Sprlan Ave., Pittsburgh 7, Pa.

**FOR SALE**—BC-645, new partially converted for ham operation, 12v dynamotor for BC-645A, RG8U cable or will trade for BC-654 in good condition. J. H. Gagnon, Shirley Mills, Me.

**FOR SALE**—National FR7, 11 tube communications receiver with speaker and power supply \$35. Also Zenith 6 tube superhet radio either portable or 110 volts, new batteries, good selectivity \$50. Phillip Mills, Box 241, Oswego, Kans.

**SELL OR TRADE**—National ham hand-spread NC81X receiver, Xtal filter; Foth-Derby camera f2.5, 1/500 second; U.S. M.S. radio correspondence course, all assignments completed and corrected. Want oscilloscope, high-fidelity loudspeaker. Arthur Freund, Whittier St., Hartsdale, N. Y.

**FOR SALE**—HRO5TA1, 7 months old, complete with speaker and power supply and 4 sets of B.S. coils. Like new, \$200. C. H. Einsberger, W2VSKY, Romulus, N. Y.

**SELL OR TRADE**—Western Electric 242-A tubes and 205-D tubes. All inquiries answered. A. L. Oliveira, W1PWL, 94 Potomosa St., New Bedford, Mass.

**FOR SALE**—Ham equipment, transformers, chokes, coils, condensers, sockets, etc.; both new and used. Must break up station. James P. Melvren, W9SSS, Box 211, Tinley Park, Ill.

**FOR SALE**—National NC100-XA receiver with speaker. Perfect condition \$170. B. B. Barker, 7W 4th St., Sterling, Ill.

**SELL OR TRADE**—Have complete 8 mm photographic apparatus including fan cooled projector, camera, screen, tripod, color and BW films and splicing unit to trade for good short wave receiver with at least three bands. Cash or trade. E. Machovec, 710 N. Glover St., Baltimore 5, Md.

**FOR SALE**—Radio and electronic magazines from 1937 to 1944. Send for list; also Schwinn racer bicycle \$45. Don G. Harmer, W3MO, 3542 S. St., N.W., Washington 7, D. C.

**FOR SALE**—Combination radio (2 short wave bands) recorder, record changer and player, with 300 popular records and full supply of recording blanks and needles. \$325. Roxy Recording Studio, Brentford, S. Dak.

**WANTED**—100 watt transmitter capable of 10 meter phone. Cash or will trade German Mauser 32 automatic and Reflecta full view range finder; F4.5 lens camera. Charles F. Schmidt, 505 Bayard Park Drive, Evansville 13, Ind.

**FOR SALE**—Two transceivers, batteries, phones and mikes, antennas, tubes and parts for changing from 6 to 2 meters included. Perfect condition. Each unit \$24 or \$40 for two. Bob Crum, 1419 Schilling Ave., Chicago Heights, Ill.

**FOR SALE**—HalliCrafter S-40 almost new; complete with home-made S-meter, uncalibrated but accurate. \$85. Marion Calvert, 1310 S. 9th St., Lawrenceville, Ill.

**WILL TRADE**—Components for 3 stage TRF, 6E5, 6J7, 76's, 2A3's, 12" Jensen, matching transformer, FP38 and phono motor. Want homebuilt midget oscilloscope and multimeter or \$55. P. Morgan, 190 Wentworth South, Hamilton, Ont., Canada.

**WANTED**—HalliCrafter SX28A, not over \$100; also preselector to cover 10-18-20-25 and 31 meter bands. Write full details, Jose Vezquez, 2640 S. 9th St., Philadelphia, Pa.

**FOR SALE**—TBY-8 portable transmitter-receiver, 28-30 megacycles; phones, mike, antenna, carrying case \$40; also single tube amplifier \$10. Edward Matthews, Jr., 171-35 Courtney Ave., Flushing, N. Y.

**FOR SALE**—100 watt input phone transmitter, 6V9 osc. 6V6 doub. B29 final. 6SE5, 6SF7, 6N7, 815 class B modulator. Two power supplies, 868 Jr. & 83 rectifier tubes, 500 volts, 300 mills & 450 volt, 250 mills. Complete with Turner xtal mike, 40 meter xtal and B & W coils for 10 meter band, \$100. Frank L. Rigg, 5328 East Drive, Rockford, Ill.

**WANTED**—Stancor 10-P transmitter. Also SW-3 coils and coil rack. Arthur C. Wells, Sr., 1205 South L St., Arkansas City, Kans.

**FOR SALE**—300 tubes, all types, 25 assorted speakers, 15 Philco aerial kits; 2 portable phono with 3 tube amplification; phono pickups; power transformers; 6 volts filaments, Eastman 16mm projector, etc. Sell part or all. Write for list of items and prices. William Gorges, Atlantic Radio Service, Atlantic, N. Carolina.

**WANTED**—TU-17A tuning units for BC-223A and dynamotor power supply. Keenewaw Radio Shop, Calumet, Mich.

**FOR SALE**—Phone CW crystal rig, 40 watts, tubes 7C5, 6S37, 6J5, 3-6L6, 20, 40, 80 and 10 meter band. Complete with coils, tubes and power supply. \$50. Frank Bou, c/o Bot. Dept. & of P., 38th & Woodland Ave., Philadelphia, Pa.

**SELL OR TRADE**—Johnson 10 meter KW coil, 80 meter CL adjustable KW coil & base; B & W JTEL 75 watt turret assembly 2A band hopper coils and VLS 80, 500v coil & base. Want various hnd coils such as ML5-80 & base, OLS-80, OEL-10, etc. Verne L. Whynot, Box 512, Bridgewater, N.S., Canada.

**FOR SALE**—Two BC-1335 transceivers, F-M 27.9 to 30 Mc, FB for 11 or 10 meter mobile operation. Self contained 6 volt power supply, \$20 ea. crystal controlled. Gus Slack, 2328 44th St., Des Moines 10, Iowa.

## YOUR OWN AD RUN FREE

The Sprague Trading Post is a free advertising service for the benefit of our radio friends. Providing only that it fits in with the spirit of this service we'll gladly run your own ad in the first available issue of one of the six radio magazines in which this feature appears. Write CAREFULLY or print. Hold it to 40 words or less. Confine it to radio subjects. Make sure your meaning is clear. No commercial advertising or the offering of merchandise to the highest bidder is acceptable. Sprague, of course, assumes no responsibility in connection with merchandise bought or sold through these columns or for the resulting transactions.

Dept. RN-107 SPRAGUE PRODUCTS COMPANY

North Adams, Mass.

(Jobbing distributing organization for products of the Sprague Electric Co.)

ASK FOR SPRAGUE CAPACITORS and \*KOOLOHM RESISTORS by name!

\*Trademark Reg. U.S. Pat. Off.

**RADIOMEN!  
ELECTRICIANS!**

240 Page BOOK on "HOW TO  
START A SHOP  
OF YOUR OWN"  
**FREE**

Here's an unusual "get acquainted" offer! This new 1947 book, "Starting & Operating a Profitable Electrical or Radio Business" is yours, absolutely FREE! It tells how to start and run a paying service shop right, on small capital, full or part time. Packed with practical information to help you get ahead in a shop of your own or working for some one else.

10 to 1 Satisfaction  
GUARANTEE

"I personally guarantee that at the end of 1 year from date of receipt, my "Applied Practical Radio" set will have earned for you at least 10 times its cost, or you may return it and I'll return every cent you paid."




B. W. Cooke, Pres.

**HOW TO GET YOUR FREE BOOK**  
You get this book Free just for looking over—without cost or obligation—the sensational new 3-volume Coyne set "APPLIED PRACTICAL RADIO". It's just off the press. Here's everything you want to know about radio, from basic principles to up-to-the-minute Television and FM! PA, short-wave, aviation-auto radio, multi-bands, tele-transmission, etc., all clearly explained. Shows how to construct, install, service all types of apparatus. Step-by-step photos break equipment down before your eyes! Newest testing methods. Hundreds of subjects, almost 1000 pages, 600 illustrations, diagrams. Written for home training and field reference—so complete, so up-to-date and practical that every man interested in radio should see it.

**SEND NO MONEY!** You can see how much this Set can mean to your future, without cost or obligation. I'll send "APPLIED PRACTICAL RADIO" postpaid, for you to look over for 7 days FREE—and with it, the "Business Starting" book as an outright Gift! This book is yours to keep free whether or not you decide to keep the 3-volume set!

**Coupon is Not an Order**  
Just a Request to See the Set Free

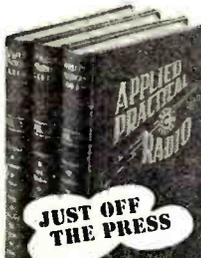You are not buying the 3-volume set when you send this coupon. You are merely asking to see the books free for 7 days. This coupon becomes an order only if you decide to keep the set after 7 days Free Examination. Free Book Offer is limited—so mail coupon today.



JUST OFF THE PRESS

**FREE BOOK COUPON**

B. W. Cooke, Pres., COYNE ELECTRICAL SCHOOL, Dept. 77-T3, 500 S. Paulina Street, Chicago 12, Ill. Send me the NEW 3-Volume Coyne Set "APPLIED PRACTICAL RADIO". Also send me the book, "Starting & Operating a Profitable Radio or Electrical Business", which I am to keep FREE whether or not I keep the 3-book Set. I'll either return the 3-book Set in 7 days and owe nothing, or pay \$3 within 7 days and \$3 a month until \$10.75 is paid—or I'll send the cash price of \$9.75. You also include FREE one full year of Consultation Service.

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_

TOWN \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

Check here if you want to pay postman cash price of \$9.75 (you save \$1.00) on delivery. Same Money-Back Guarantee after 7 days' trial.

should be used to set the oscillator frequency. The oscillator tuning condenser  $C_{10}$  should be set at minimum capacity during this operation and the bandset condenser  $C_9$  rotated slowly until the oscillator frequency is approximately 9900 kc. In the unit described this occurred with the bandset condenser at approximately half scale.

When the high frequency end has been set the tuning condenser should be turned to minimum and the frequency again checked. The frequency should now be approximately 9050 kc. Insufficient range is an indication of too little inductance in the oscillator coil. Forcing the turns of this coil closer together or adding a turn or two will increase the inductance.

In the event the frequency range is too great, a turn or two should be removed from the coil, or the turns spread slightly. When the proper range has been attained, the coil should be coated with a good coil dope to prevent further changes.

The 2E30 tripler may now be placed in its socket, the shorting link reconnected, and the tuning condenser  $C_{16}$  tuned for resonance. A neon bulb touched to the stator plates of the condenser will indicate maximum output. At this point, the use of an absorption type wavemeter is desirable to prevent tuning to the wrong harmonic. With the values given, resonance will occur at about mid-scale.

A 0-10 ma. meter should now be inserted in series with the grid leak of the final,  $R_{10}$ . It is essential that the r.f. choke be used in series with the grid leak if sufficient excitation is to be obtained. No choke is needed on the tripler due to the high value of grid leak used.

Retuning the tripler should give a grid current of 6 to 10 ma. as indicated on the meter. When plate voltage is applied to the final this will drop to approximately 5 ma.

A load may now be connected to the final, consisting of a 25 watt lamp coupled to the final tank by a one or two turn link. Removing the dummy phone plug will apply voltage to the final. A 0-200 ma. meter should be plugged in the meter jack  $J_1$ . The final should be quickly tuned to resonance as determined by the brightness of the bulb, and minimum plate current.


Power requirements are 6 volts at 2.15 amps. and 350 volts at 150 ma. A 350 volt dynamotor was used in this installation, although one of the surplus PE-103 units could be used. If the PE-103 unit is used, it will be necessary to make  $R_{11}$  a 3000 ohm, 20 watt unit to reduce the voltage on the oscillator and tripler to the proper value.  $R_{12}$ , the screen resistor in the final stage, should also be changed to a 10,000 ohm value.

The link will vary depending on the type of antenna feed used. With a quarter-wave antenna mounted on the car bumper, and fed with 52 ohm co-ax, a one turn link gave a loading of 90 ma. If a 500 volt plate supply is



**HOBCO  
HAS IT!**

**BRENTWOOD 14-WATT  
AMPLIFIER**

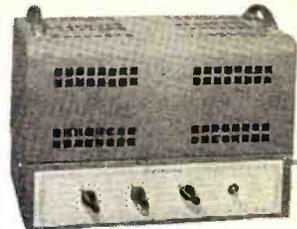

Your cost,

**\$26<sup>95</sup>**

Complete with tubes and cover

Designed and built by one of the world's largest manufacturers of amplification equipment, this amplifier is outstanding for its rich, natural tonal qualities. It features two separate high impedance inputs for phono and microphone, separate gain controls for mixing and fading, tone control, push pull beam power output. Output impedances 2, 4, 8, 16, and 500 ohms. Operates on 110-120 volts AC 50-60 cycles.

Write for our Radio Parts  
Bulletins — issued monthly.

Henry O. Berman company, inc.

10 & 12 E. LOMBARD STREET  
BALTIMORE 2 • MD.

ELECTRONIC EQUIPMENT AND REPLACEMENT PARTS

**JUST OUT! Gov't Surplus**

**NEW Solid Brass Portable**

**RADIO ANTENNAS**

**3 SIZES, 12 Ft., 9 Ft. and 7 Ft.**

12 Ft. \$15 Val. \$4.95—9 Ft. \$10 Val. \$2.95

7 Ft. with Mounting Bracket \$8 Val. \$1.99

Sent Postpaid Upon Receipt of Price  
or Mailed C.O.D. Plus Postage

**FOR HOMES  
BOATS or AUTOS**

Same as used on Army tanks. These telescopic, rustproof antennas have tremendous pickup, eliminate dangerous wiring. Solid Brass throughout, practically insuring

**NOISE FREE RECEPTION**

Exceptionally Rugged Sections  
Compress from 1 ft. to 1 ft. 4 in.  
Handy for Camping Trips, also Useful for Transmitting, FM and Television sets.

**EASY TO INSTALL ANYWHERE**  
Each antenna comes with clamps, nut, lug, and wire. 7 ft. model with bumper mount.

**QUANTITY LIMITED**


**MAIL ORDER TODAY**

Send check or money order today for \$4.95, \$2.95 or \$1.99. Your antenna will be sent postpaid or mailed C.O.D. plus postage.  
Money back in 10 days if not satisfied.

**RADIO HOSPITAL**  
1113 Lexington Ave., Dept. R7  
New York 21, N. Y.

# Here it is

## BC-728-A FOUNDATION KIT

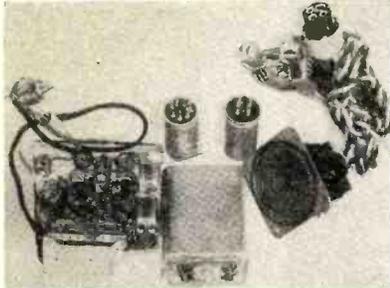

Nowhere except at Niagara will you find such a bargain offered. At very low war surplus prices the value of the individual pieces total to more than \$25.00—yet Niagara gives you more than \$25.00 worth of equipment for less than \$10.00. The kit consists of the following pieces as pictured above:

- 1—spare receiver as illustrated value \$ 1.79
- 1—4" P.M. speaker with output transformer value 15.00
- 1—4 prong Vibrator value 1.79
- 1—7 prong 2 V. Vibrator value 2.20
- 1—2 V. Storage Battery value 3.49
- 1—Cord with plug value 1.25
- Complete total value.....\$26.71

All of the above complete with schematic diagram with broadcast conversion data at the Giant Bargain Price of....\$9.95  
Complete Set of 6 Tubes, list value \$13.20—  
Our Special Price.....\$5.95

# \$9.95

### DO YOU OWN AN SCR-522?

We have a complete power supply, including a separate voltage regulated bias supply, chassis and schematic—all in kit form. This kit will supply all voltage necessary for normal operation of the set. All parts guaranteed. Complete at the amazingly low price of.....\$14.95

### BC-348 Owners

**CONVERTER FOR BROADCAST BAND**  
Convert that BC-348 without any alteration in your circuit. Our special converter takes power from receiver. Just tune your set to 450 kc. and forget it. All tuning is done on a converter panel covering 550 to 1600 kc.—double conversion means High Sensitivity. Excellent Fidelity, and Higher Selectivity—complete basic kit with schematic and full instructions—less chassis dial and tuning knobs. Terrific Buy at.....\$6.50

**POWER SUPPLY KIT for AC Conversion**  
Complete—Contains all necessary components for 110 v. 60 cy. conversion of BC-348. A Hot Special. No rewiring of the set is necessary.....\$7.50

### CRAMER TIMER



Type #7766346P2 adjustable from 1-30 sec. S.P.D.T. with starting relay for remote control motor and contacts separate.....\$9.95  
Type #7766346P4 adjustable from 4-120 sec. S.P.D.T. normally closed motor and contacts separate.....\$6.95

### TRANSFORMER SCOOP PLATE

- G.E.—Pri. 110 or 220 v.—Sec. 1160-0-1160 v. @ .5 A.....\$17.95
- G.E.—Pri. 110 or 220 v.—Sec. 612-612 v. @ .213 A. or 593-0-593 v. @ .204 A.....9.95
- I.T.C.—Pri. 115-125 v.—Sec. 435-0-435 v. @ 250 Ma.—Hermetically sealed.....4.95

### FILAMENT

- Thermador #CS 8709—Pri. 200/220/240 v., 50 cy.—Sec. #1 6.3 v.—411 A., Sec. #2 6.3 v.—0.9 A., Sec. #3 5 v. CT—2 A., J.A.N.—115 v. 60 cy.—Sec. #1 2.5 v., 10 v., Sec. #2 2.5 v.—10 A., 15000 v. inverse peak.....4.95

### Combination Offer

Both Items

# \$225



### HS-16 HEADSET


- 8000 ohms Hi-impedance
- Noise proof
- Most sensitive phone built
- May be used as a sound powered intercom.

Light, durable, efficient. Molded neoprene earcups shaped to completely envelop entire ear. Adjustable steel headband extends or retracts. Especially suited to hams, commercial operators, aircraft pilots, recording engineers and many others. Can be used with simple Xtal to make complete radio receiver. Special.....\$1.89

Original Cost \$25.00  
6 foot extension cord.....\$0.49
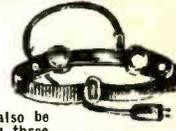
### CARBON THROAT MICROPHONE

This microphone will work into any 200 ohm impedance input circuit. Has adjustable strap to fit any neck. In operation this microphone is strapped around the throat thereby facilitating full freedom of both hands and head movement. Ideal for ultra high frequency mobile work for hams. Can also be used as a hi-grade Carbon Mike by simply drilling three holes in case. Sensitivity of this mike equal to mikes costing \$10 and \$15. Supplied with strap, 10' cord and plug. Your cost.....\$4.9c



# 49c

### PERMALLOY SHIELDS for CATHODE RAY TUBES

3" Shield.....\$1.49

Mallory Vibrapack 12 v. Input, 150 v. @ 85 mils output—Extra Special at.....\$3.75

75,000 ohm bleeder, 200 watts Ohmite—Special.....\$1.65

50,000 ohm bleeder, 100 watts, I.R.C.....89c

### PIONEER GENEMOTOR HIGH POWER ON WHEELS

Delivers output 500 V. @ 160 mils, input 6 or 12 V.—completely filtered—has relays and magnetic circuit breakers in specially constructed casing. The job that will deliver the watts to that mobile rig. Slightly used, test condition. Specially priced.....\$5.95

### SCR-522 100-156 MC.

#### RECEIVER AND TRANSMITTER

Licensed for Railway and Taxicab Use  
The ideal all-purpose transmitter-receiver for work in the 100-156 mc. spectrum. Four channel push-button operation, crystal-controlled. AM, phone, mobile or fixed station service. Ideal for amateur, aircraft, marine, railroad, taxicabs, police and experimental. Amplitude modulated—High transmitter output. Receiver has 10 tubes and transmitter has 7 tubes including two 832's. Easily converted to full 110 volt 60 cycle operation. Complete conversion instructions and schematic furnished with each unit.  
Tube complement 2—832; 3—12A6; 1—6G6; 2—6557; 1—12J5GT; 1—12C8; 1—9002; 3—9003; 1—12AH7GT and 3—12SG7.  
Complete with tubes.....\$14.95  
Complete with dynamotor & pushbutton control box.....\$39.50

### NEW, STANDARD BRAND TUBES

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
1A3	.98c	12SN7GT	.79c	808	2.95
1A7GT	1.10	12S07GT	.99c	809	1.50
1H4G	.98c	12K8	.99c	811	1.95
1R4	1.10	1486	.99c	812	3.25
1T4	1.10	28D7	.75c	812H	6.90
1H5	.99c	30	.78c	813	8.95
1N5GT	1.10	34	.98c	814	4.49
1N218	.35c	35Z3	.99c	815	2.25
1LNS	.92	35L6	.99c	821	1.75
1R5	1.10	35W4	.89c	828	.95
1S5	1.10	37	.69c	830B	5.25
3Q4	1.10	38	.69c	832A	2.25
3Q5GT	1.10	39/44	.59c	837	2.50
3S4	1.10	41	.69c	838	3.75
6AB7/1853	.99c	42	.64c	840	3.00
6AG5	.99c	45	.65c	5514	3.95
6AG7	.99c	47	.90c	7193	.49c
6AL5	.99c	50B5	.59c	8055	1.25
6AL6	.99c	50B6	.99c	8011	4.95
6AL5	.99c	70L7	1.49c	8012	4.95
6AT5	.99c	71A	.69c	8016	1.49
6BA7	1.29	75	.69c	8024	1.25
6BB6	.89c	713A	1.49c	2D21	.75c
6BB8	.99c	717A	1.25	2K2	1.95
6C4	.64c	954	.75c	3B24	1.95
6C5	.51c	955	.75c	4C/35	7.95
6C21	12.95	956	.75c	5R5Y	1.15
6D6	.75c	957	.75c	5T4	.98c
6F5	.51c	958A	.75c	5U4	.98c
6F6	.80c	9001	1.15	5Y4G	.59c
6F7	1.25	9002	.98c	5Z3	.89c
6F8	1.10	9003	.98c	5Z4	.98c
6G6	1.10	9004	.98c	6X5	.89c
6H6	.59c	9005	.98c	25Z6	.99c
6H6GT	.89c	9006	.69c	35Y4	.99c
6J4	1.50	10Y	1.50	35Z5	.99c
6J5	.59c	15E	1.50	80	.75c
6J6	.89c	HF100	6.95	82	.98c
6J7	.80c	HY79	.83c	84	.94c
6K6	.69c	HY75	1.25	83V	.98c
6K7	.75c	HY619	1.25	217C	7.50
6L6	1.25	T20	1.25	250R	1.95
6L8	1.25	T24D	2.95	836	1.15
6L6G	1.20	V70D	6.90	866A	.75c
6L7	.98c	100T8	3.00	872A	2.25
6N7	1.25	2C26A	.75c	884	.75c
6R7	.98c	2C34	1.15	901	.50c
6SA7	.90c	2C40	2.60	2051	.90c
6SC7	.85c	2C44	1.75	2051	.90c
6SF5	.79c	2E25	3.95	8020	5.95
6SG7	.89c	2E30	2.25	8K72	1.25
6SH7	.65c	2J32	20.00	8K60	3.50
6SJ7GT	.69c	2J33	20.00	VR78	.75c
6SK7	.75c	211	1.25	VR90	.75c
6SL7	.89c	2J56	20.00	VR105	.75c
6SN7GT	.69c	3C24	1.35	VR150	.75c
6SQ7	.89c	3E29	2.95	2225	1.95
6SR7	.89c	75T	2.95	874	1.95
6SS7	.75c	304TH	9.85	1613	.95c
6S7	.89c	104L	4.95	1616	2.95
6Q5G	.98c	307A	6.25	1619	.95c
6Q5	.98c	446A	2.60	1624	.98c
6V6GT	.89c	6C4	6.40	1625	.98c
6Y6G	.89c	703A	7.50	1626	2.25
7A7	.75c	705A	4.95	3AP1	3.45
7C4	1.50	715B	4.95	3BP1	2.95
7F7	1.25	723A/B	9.95	58P4	3.95
7L7GT	1.39	800	2.25	58P4	5.45
12A76	1.30	801A	1.25	5CP1	3.95
12SA7GT	.99c	802	1.49	5PP7	7.95
12SG7	.89c	803	8.95	933	3.00
12SH7	.89c	805	3.75	7DP4	14.95
12S17	.79c	807	.95c	7EP4	18.95
12SK7	.89c				

NO MAIL ORDER FOR LESS THAN \$5.00

# NIAGARA RADIO SUPPLY CORP.

160 Greenwich St. New York City 6, N. Y.

Write for latest Bulletin 10RN  
All prices F.O.B. New York City.

# "TELEVISION SPECIALISTS"

Announcing—

## NEW TELEVISION SWEEP GENERATOR

**THE NEW TELE-SWEEP**—Available now at all leading radio distributors. The Vision **TELE-SWEEP**, an inexpensive sweep signal generator designed specifically for alignment of television receivers, broad band amplifiers, etc. A must for radio servicemen, schools, and experimenters. The low cost of this unit brings it within the reach of everyone. Write for circular giving complete details.

**PRICED AT ONLY.....\$68.50**

## DESIGN DATA & PARTS

• **NEW TELEVISION COIL KIT 510**—Build a 10" or 15" television receiver. • Complete kit of permeability tuned video IF, RF, and Sound Coils for high quality television receiver designs. Contains all necessary coils for 3 stage 4mc. wide video, 2 stages sound, discriminator, peaking, oscillator, and IF. Complete instructions included. Priced at Only.....**\$9.95**  
**TELEVISION COIL KIT 500A**—Including 10 matched coils for low cost 7" television receiver design described in booklet. Only.....**\$4.95**

### "Design and Construction of a Modern 5 or 7" Television Receiver" New 2nd Edition

More Pages, Greater Detail, Drawings, Photographs, Designed for Good Performance, Simplicity, Economy. For Experimenters, Servicemen... any technicians that prefer to build their own.

### "Design and Construction of a Visual Alignment Sweep Signal Generator"

Build a Television Sweep Generator, inexpensive, simple, yet professional in performance. A "must" for servicemen... for alignment of Television Receivers.

Included with each booklet is an 11 x 17" working diagram.

### We Carry a Complete Line of Television Parts for the Experimenter!

R.F. & I.F. Coils C.R. Tubes  
 H.V. & L.V. Transformers Punched Chassis  
 Complete line of Resistors, Condensers, Special CR Tube Sockets, etc.  
 Magnetic Deflection Components.

SEND FOR OUR LATEST PARTS LIST



P. O. Box No. 52, Kew Gardens 15, N. Y.

Enclosed is \$..... (check or money order).  
 Quantity

- ..... Television Receiver Bklet.....\$1.75 ea.
- ..... Sweep Signal Generator Bklet...\$1.75 ea.
- ..... Television Receiver Coil Kit 500A \$4.95 ea.
- ..... Permeability Tuned Coil Kit 510. \$9.95 ea.
- ..... Send circular on the Tele-Sweep.

Name .....

Address .....

City..... Zone.....

State .....

Order direct or through your local distributor!

130

used, the maximum final current should be held to 75 ma.

In operation it is possible to vary the output frequency by over 100 kc. with no noticeable decrease in output without retuning the transmitter. With an input to the final of 32 watts, the measured output was 22.5 watts.

When tuning of the r.f. section has been completed, the microphone should be connected, and the deviation control slowly advanced as the microphone is spoken into. A receiver should be used to monitor the transmission as this is done. The deviation should be kept as low as possible, consistent with satisfactory reception. In the rig described, using the T-17 microphone, the deviation control is normally set at slightly less than 3/4 full on.

A receiver, especially designed for use with the transmitter, and of approximately the same size, is currently being designed. This receiver will afford either narrow-band FM or AM reception.

-30-


## DAD TAKES OVER

**THE** Federal Communications Commission has granted the plea of Ernest Melvey, 6416 Francis Avenue, Seattle, Washington for permission to change his amateur station call letters from W7HVS to W7HUX.

In order to do this, the Commission waived Section 12.81 of its rules which requires that amateur calls be assigned systematically to prevent partiality. The extenuating circumstances which caused the Commission to make this exception was Mr. Melvey's desire to use the call letters of an amateur station which had been operated by his late son, Robert, who died in action aboard the cruiser "Nashville" when that ship was hit by a Japanese suicide plane during the war.

The Commission was impressed by the father's wish to perpetuate his son's call letters on the air "in remembrance of the good times" the two had together. In granting this particular request, however, the Commission indicated that it did not mean that it was relaxing its long adhered to policy against transfer of amateur call letters or requests for particular amateur calls.

-30-

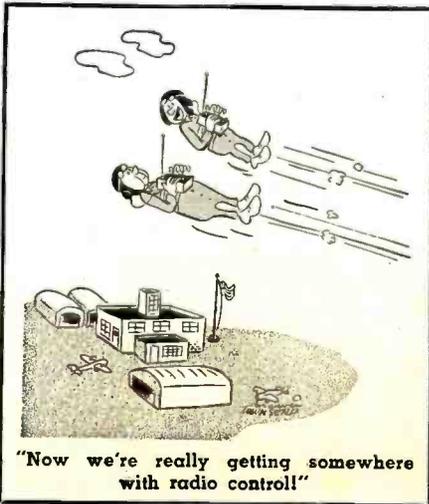

# WAR SURPLUS!

All merchandise is the product of nationally known manufacturers under government contract—no "off" brands. This merchandise is all **BRAND NEW, UNUSED!**

- Oscilloscope, BC-1268, 5" C-R tube, contains 24 octal tubes.....\$27.50
- Instructions for converting BC-1268 to a laboratory type oscilloscope, excellent for television work, includes schematics, lay-outs, etc. .... 1.50
- Remote Control Panel, RM-25A. A large unit containing lever switches, multi-contact push switches, relays, condensers, chokes, transformers, signal lamps, etc., all mounted on a 8 1/2 x 19 rack panel..... 12.50
- Microphone, T-24, carbon, hand type, American Microphone Co., for mobile rigs, etc. .... 1.95
- Antenna, MS-56, 3/4" dia. x 37 1/2" long copper plated steel tubing with mounting bushing. Suitable for dipoles, verticals, whips, beam elements, etc. Easily cut to length..... 19c
- Pilot Lamp, 1" jewel, enclosed type, for S-6, 115 v. bulb, Dialco #9387 (Specify color) 43c
- Pilot Lamp, jeweled enclosed type, for bay-net base bulb, any color jewel (Specify color) ..... 19c
- 0.5 mfd. 200 vdc paper condenser, Micamold. In lots of 50, each..... 5c
- 4 mfd. 500 vdc, paper condenser, excellent for replacing electrolytic filters, will give superior service ..... 59c
- In lots of 50, each..... 49c
- 8 mfd. 450 vdc electrolytic, popular inverted can, pal-nut mtg., Cornell-Dubilier KR-508 32c
- 16 mfd. 150 vdc, electrolytic, aluminum cased tubular, Cornell-Dubilier BR-1615 ..... 26c
- 10-10-10 mfd. 4 sect. electrolytic, all 400 vdc, Mallory FP can type..... 79c
- Speakers, large stock at low prices. Write for details.
- Tubes, large stock Receiving, Xmitting, C-R, etc.

We have thousands of choice items in our warehouses too numerous to mention. Let us know your requirements. Drop us a card to receive our regular bulletins and flyers.

## Price RADIO Laboratories

2816 Hemlock Ave., Baltimore 14, Md.

F.O.B. our warehouse. Minimum order \$2.00. We also ship C.O.D., 10% with order.



### Model 730

Range: AC-DC 1v to 3000v (7 bands.)  
 Zero center scale for F.M. alignment.  
 Ohm Scale: 10 Ohms to 10 Megohms.  
 Frequency Range: Audio to 110 MC.  
 Input: 100 Megohms AC or DC.  
 Tubes: 6X4, OA2, 6AQ5, 2-12AU7, 2-A4522.

High gain Signal Tracer with enclosed speaker. No amplifications needed in receiver—no hum.  
 8" illuminated dial.

**\$89.95**  
 Net



Write for catalog sheet  
 Dept. 10A

## Coastwise Electronics Co., Inc.

130 North Beaudry Ave., Los Angeles 12, Calif.  
 New York Office & Warehouse  
 258 Broadway, New York 7, N. Y.

**RADIO NEWS**

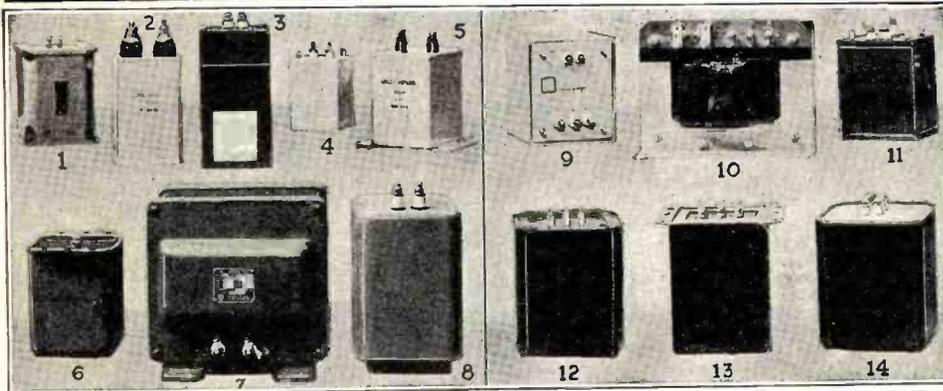
# Every day is bargain day at WALTER ASHE



Here's your opportunity to obtain the rig of your dreams at a really important saving! Select your new Receiver or Transmitter from this list. Tell us what you have to trade. We'll respond with an extra-liberal offer on your used equipment. Act now! Get your trade-in deal working today!



As headquarters for extra Special Deals on used Test Equipment you'll always find us equipped to furnish what you want at a price you want to pay. And if you're interested in trading new for old, our complete stocks and bigger-than-ever trade-in allowances on your used equipment are sure to be handy. Write for details or use the



## Look at These Bargains in Surplus CHOKES, TRANSFORMERS and CONDENSERS

- (1) FILTER CHOKE. 12HY @ 200 MA, 200 ohms DC Res. Steel Case. **\$3.50**
- (2) TRANSMITTING FILTER CONDENSER. 2 Mfd. 5000 VDC, Dykanol, regular net price \$29.63. Our low bargain price. **\$7.51**
- (3) DUAL CHOKE. 12 HY @ 200 MA per section. 150 Ohms DC res. Steel case with stand-off insulators. No. 2785. **\$4.95**
- (4) FILTER CHOKE. 4 1/2 Hy. 150 MA. 70 ohms Res. DC. Hermetically sealed in case. Stand-off insulators. No. 5209. **\$1.29**
- (5) TRANSMITTING FILTER CONDENSER. 2 Mfd. 4000 VDC. oil filled. Regular net price \$25.44. Our give away bargain price. **\$4.50**
- (6) FILTER CHOKE. 4 Hy. 300 MA. 40 ohms DC resistance. Hermetically sealed in case, screw terminals. No. 6317. **\$4.95**
- (7) HIGH VOLTAGE FILTER CHOKE. 6 Hy. at 1.2 Amps. 27 ohms. DC resistance. 12500 volt breakdown insulation. Shielded case and standoffs. No. 6813. A super buy at. **\$17.95**
- (8) FILTER CHOKE. 8 Hy. at 500 MA. 55 Ohms DC res. Very high quality. Hermetically sealed. No. 8056. Net **\$11.85**
- (9) PLATE TRANSFORMER. 2500 VCT. 150 MA. Pri. 115 VAC. 60 CY. Steel case with stand off insulators. No. 161919. **\$9.95**
- (10) RCA 1 KW MODULATION TRANSFORMER. Primary will match class "B" tubes up to 10000 ohms plate to plate. Secondary No. 1. 450 MA for beam tube plate. Secondary No. 2. 80 MA for screen grid. **\$14.95**
- (11) SCOPE / TELEVISION TRANSFORMER. 2100 volts at 10 MA. Pri 115 VAC. 60 Cy. Steel case with stand off insulator. No. ST. 1. **\$4.25**
- (12) PLATE TRANSFORMER. 2010 VCT 200 MA Pri. 105-125 VAC 60 Cy. Steel case. screw terminals. No. 8275. **\$9.95**
- (13) PLATE TRANSFORMER. 1400/1200 VCT at 200 MA. Pri. 115 VAC 60 Cy. Steel Case. screw terminals. No. 4891-N. **\$7.45**
- (14) PLATE TRANSFORMER. 1400/1200 VCT at 260 MA. Pri. 115 VAC 60 Cy. Hermetically shielded steel case, screw terminals. No. 8931. **\$7.95**

- SELSYN MOTORS**  
115 VAC 60 Cy. Navy Surplus Heavy Brass Case. Large, continuous duty type. No. 806—per pair. **\$12.50**
- THORDARSON 10 WATT TUNER-PHONO AMPLIFIER**  
T-31K11 Tuner-Phono Amp. Kit, complete with tubes. **\$44.10**  
T-31W11—Same as above but wired and tested. **\$64.68**
- G. E. RELUCTANCE PICKUP** **\$4.67**  
**PRE-AMP for above** **\$5.82**
- WEBSTER CHICAGO MODEL 80 WIRE RECORDER** **\$149.50**  
**WEBSTER CHICAGO MODEL 79 WIRE RECORDER. CHASSIS only** **\$52.92**  
**RCA WIRE RECORDER** **\$139.50**

### Sensational New Hi Power Foto Flash Kit

Unit can be fired every 3 seconds if necessary. Complete kit, including AM-GLOW tube, carrying case, etc., with simple assembly and operating instructions. **\$77.50**  
Write for detailed description and price list

## YOUR FAVORITE BRANDS OF TEST EQUIPMENT

- |                      |                      |               |
|----------------------|----------------------|---------------|
| Hickok               | Industrial Equipment | Reiner        |
| Jackson              | Cornell Dubilier     | R.C.A.        |
| Precision            | Coastwise Electronic | Billiey       |
| Simpson              | Superior             | Manlan        |
| McMurdo Silver       | Waterman             | Monitor Piezo |
| Radio City Products  | Du Mont              | Weston        |
| Robson-Burgess       | Feller               | Sprague       |
| Chicago Industrial   | Messner              | Supreme       |
| Special Products Co. | Triplatt             |               |

RECEIVERS IN STOCK	
Hallcrafters S-38	\$ 47.50
Hallcrafters S-40A	89.50
Hallcrafters SX-42 (less speaker)	275.00
Hallcrafters SX-43 (less speaker)	169.50
Hammarlund HQ-129X (with speaker)	189.15
Hammarlund HQ-129X (with speaker and pwr supply)	398.25
National NC-240DT (less speaker)	225.00
National NC-173 (less speaker)	179.50
National NC-46 (less speaker)	97.50
Piepsner KP-81 (complete)	367.65
RME-45 (with speaker)	198.70
RME-84	98.00
RME VIF-152A	86.60
RME DB-22	60.00
Collins 75A-1	375.00
TRANSMITTERS	
Hallcrafters HT-9 (less coils)	\$350.00
Supreme AF-100 (complete)	150.00
Neck T60-1 (one set coils)	69.50
Hallcrafters HT-17	120.00
Hammarlund Four-20	110.00
Hallcrafters HT-18	120.00
Nielsner Signal Shifter	72.45
Sonar MB-611	87.45
Sonar VFX-680	

All Prices F.O.B. St. Louis, Mo.

### COMING!

A new, bigger, better Walter Ashe Catalog. Ask to have your name placed on our mailing list.

### MAIL THIS COUPON TODAY

Walter Ashe Radio Co.  
1125 Pine St., St. Louis 1, Mo. **RN-10**  
Please send money-saving details of your Liberal Trade-In Offer on  
 Receivers  Transmitters  Test Equipment

I would like to trade \_\_\_\_\_ for \_\_\_\_\_  
(describe equipment)

\_\_\_\_\_  
(make, model)  
 Please give me information concerning your extra-special deals on top condition, slightly used Test Equipment.  
 Am interested in the following equipment \_\_\_\_\_  
 Put me down for "priority delivery" of the big new Walter Ashe Catalog, when issued.


Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

W6JWD W6ULH W6WTM W9NRF W6IYD W6PGI W6QDF

**Walter Ashe RADIO CO.**  
1125 PINE ST. • ST. LOUIS, MO.

**BEST SURPLUS . . .  
BEST CONDITION —  
BEST APPEARANCE —**

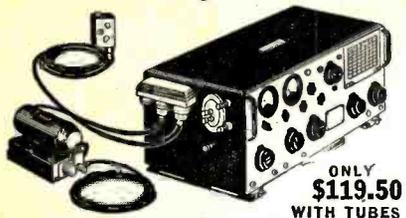You Can NOT Buy Better Surplus For Less Money Because The Electrical, Mechanical and Physical Condition Determines The Price. For 100% Top Quality Our Prices Are LOWEST ! ! !



**Collins Art-13 Transmitter**


• Look just like new. Perfect Operating Condition. We have the finest lot of these sets ever sold as surplus. Range 2000-18,000Kc. in 10 channels, voice and CW or MCW. 100 Watts Output on Fone. This famous Auto-Tune Xmtr is sold complete with Tubes, Dynamotor, Control Box and Cable Connectors. **OUR PRICE . . . . . \$119.50 WITH TUBES**

YOU GET LESS IF YOU PAY LESS!!!

**BC-221 FREQUENCY METER**

• The most-wanted surplus item. Guaranteed accuracy 0.01%. Complete with tubes, crystal and Calibration Chart. Uses batteries. Power pack or vibrapack. Just like new — beautiful condition, hand-picked by us for discriminating buyers. . . . . \$39.95 Net

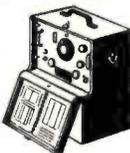**WE BOUGHT THE FINEST—AT A HIGHER PRICE—FOR YOUR PROTECTION!**



**BIG BARGAIN !!  
6L6 AMPLIFIER**

• Not war surplus, but a manufacturer's over-stock. Sold for less than the net cost of parts. Complete, ready to operate, in gray crackled cabinet. Made for 24-hour continuous service. Big, husky power supply. All new parts throughout, new RCA tubes. Relay and counter (counts up to 10,000 record playings). Input for magnetic or crystal pickup, or 600-ohm phone line for wired music systems. Separate tone, treble and bass controls. A SUPER BUY!! Only \$49.50 net. (List \$147.50.)




**ONLY A FEW LEFT  
BC-645 . . . . . \$16.85**

This 15-tube set will operate on frequencies for Citizens' Radio, Amateur, etc. Tubes alone worth \$28.00 net. Too well known to require description. Be safe. Order yours TODAY!! Our Price . . . . . ONLY \$16.85 Two for Only . . . . . \$30.90

**12/24V. DYNAMOTOR, P.E. SUPPLIES AL POWER FOR BC-645. 400V. 135MA. DC. ALSO 9V. 1.2a. AC. ONLY \$9.95 NET**

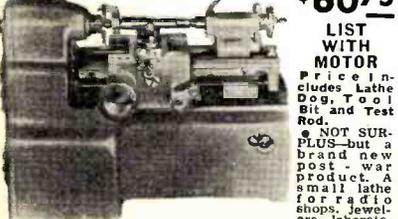**SMALL PRECISION LATHE 110-V. A.C. \$6075**



**LIST WITH MOTOR**  
Price includes Lathe Dog, Tool Bit and Test Rod

• NOT SURPLUS—but a brand new post war product. A small lathe for radio shops, jewelers, laboratories, dentists, etc. Automatic Feed. Work capacity 3" between centers. Swing over bed 2". Constructed of steel and cast iron. Accurately machined and finished. Fan-Cooled. Motor mounted inside the base. Complete with 1 1/2" face plate, 2 lathes centers, tool post and rocker. 4-jaw chuck available at \$11.00 additional. Drill chuck \$5.50 additional. Orders filled in rotation. Delivers now.

**QUANTITY DISCOUNTS TO DEALERS**

Send 20% Deposit. Balance C.O.D.  
4-HOUR MAIL-ORDER SERVICE

**OFFENBACH & REIMUS CO.**  
372 Ellis St., San Francisco 2, Calif.  
TELEPHONE: ORdway 3-8551

**Serviceman's Tube Tester**

(Continued from page 59)

instrument full scale current to permit an accurate setting of the 200 ohm potentiometer "C" load control.

In the heater cathode type triode and pentode check, Fig. 3C, the plate voltage at the transformer remains at 30 volts and is connected directly to the tube under test. The 1800 ohm resistor in series with the negative instrument terminal still further increases the instrument full scale current to permit proper instrument indication.


In the eye tube and gaseous rectifier check, Fig. 3D, sufficient voltage is applied to the plate to insure proper ionization of the gas. The 5000 ohm resistor in series with the 250 volt plate tap protects the tube against excessive current flow yet it is low enough to insure full plate loading on gaseous rectifiers. The 1800 ohm resistor in series with one of the instrument terminals increases the current required for full scale deflection of the test instrument.

An eye tube is checked by visual inspection of the tube itself. 250 volts are applied to the eye control electrode plate for the eye-closed check and 0 volts for the eye-open check (250 volts are applied to the target in both tests).

The short-test circuit, Fig. 3E, consists of 100 volts a.c. applied to all elements through suitable limiting resistors, 100,000 and 250,000 ohms. The .1 μfd. blocking condenser in series with the 100 volt transformer tap prevents the neon lamp from glowing due to electron flow in the tube under test. By following the short-test procedure given in the instructions, a short check is made between each element of the tube including the shield. This test will generally indicate "shorts" of 500,000 ohms and less.

A continuity test of each element to its base pin and of all internal taps may be made as shown in the operating instructions. Moving an element connection will result in a change in instrument indication as the element connection is broken by the lever switch. Satisfactory internal pin connections, such as taps and jumpers, are

Fig. 3. Simplified circuit diagram of each of the several test circuits incorporated in tube tester: (A) for diode type tubes, switch S<sub>2</sub> in position 1; (B) for filament type triode and pentode tubes, switch S<sub>2</sub> in position 2; (C) for indirectly heated cathode type triode and pentode tubes, switch S<sub>2</sub> in position 3; (D) for target and eye tubes, switch S<sub>2</sub> in position 4 and for gaseous rectifiers and gaseous control tubes, switch S<sub>2</sub> in position 5; (E) short check, switch S<sub>2</sub> in "Short Check" position. Switch positions refer to the schematic diagram, Fig. 2.

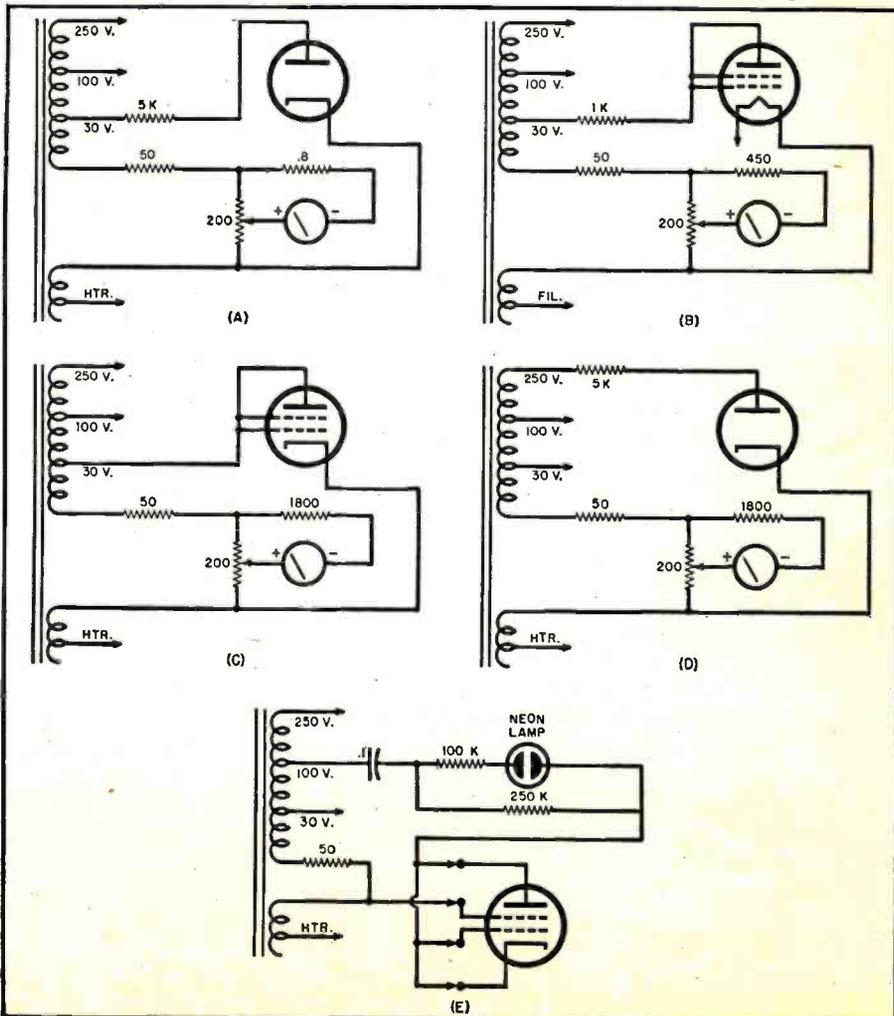

# TRANSVISION KITS

## BUILD YOUR OWN TELEVISION and FM SETS

Acclaimed TOPS IN TELEVISION VALUE! Engineered for easy, rapid assembly. Completely equipped. Nothing else to buy.

**12" TELEVISION KITS—STANDARD and DELUXE MODELS—**Picture size 1½ times larger than with 10" tube. . . . A big 75 square inch picture!

Sharp, steady picture achieved with advanced Transvision television circuit . . . Picture has remarkable brightness even in lighted room (no darkening of room is required).

• **NO TECHNICAL KNOWLEDGE REQUIRED FOR ASSEMBLY.** Complete, easy-to-follow instruction sheets provide all the knowledge needed for assembling this high quality television receiver.

• **SAVES YOU HUNDREDS OF DOLLARS—**By assembling your own receiver with the Transvision Television Kit you save several hundred dollars on the cost of a high quality set.

• **IDEAL for HOME and COMMERCIAL installations.**

**12" TRANSVISION TELEVISION KIT . . . Standard Model . . . FEATURES:** 12" picture tube . . . Picture size 1½ times larger than with 10" tube . . . RF Unit designed for 13 channels; factory wired and pre-tuned for 7 channels (no areas have been assigned more than 7 channels; however if desired, up to 6 more channels may be added at very nominal cost) . . . 4 mc bandwidth for full picture definition . . . High fidelity F.M. sound reproduction . . . picture size 75 square inches . . . 9000 volts second anode potential for brightness and contrast . . . maximum picture sensitivity better than 50 microvolts . . . 22 tubes and 12" picture tube, antenna, lead-in wire, etc. Cabinet extra, if desired. . . . **LIST \$289.00**

**12" TRANSVISION TELEVISION KIT . . . DeLuxe Model with Superb Built-in F.M. RADIO.** Same characteristics as the Standard Model, plus the following **ADDITIONAL FEATURES:**—50-216 mc continuous tuning . . . Covers the entire F.M. band and all 13 television channels . . . Cut-off switch eliminates unused tubes when set is used only as F.M. receiver. . . . **LIST \$359.50**

**7" TRANSVISION TELEVISION KIT . . . Standard Model . . . Lowest Priced . . . Biggest Value in the Field. FEATURES:** 18 tubes including 7" picture tube . . . Newly designed sweep and synchronizing circuit . . . 3000 volt second anode voltage . . . 3.5 megacycle bandwidth in picture circuit . . . High signal sensitivity—100 microvolts for picture circuit . . . RF unit factory wired and pre-tuned for local stations . . . Complete with front panel. . . . **LIST \$169.00**

**ALL TRANSVISION KITS ARE COMPLETE—**Nothing more to buy! All Transvision Television Kits are COMPLETE with all tubes, including picture tube, wired and pre-tuned RF units and IF's, high gain folded di-pole antenna with 60 ft. lead-in cable, wire and solder.

**TRANSVISION TELEVISION CABINETS . . . Beautiful, sturdily built cabinets with handsome rubbed wood finish. Fully drilled. . . . LIST \$44.95**

**12" Table Model Cabinet. . . . LIST \$74.50**

**12" Console Cabinet with compartment for record changer. . . . LIST \$32.50**

**7" Table Model Cabinet. . . . LIST \$32.50**

**Transvision F.M.-1 . . . 8-tube F.M. High Fidelity Radio RECEIVER KIT . . . COMPLETE—** Nothing else to buy. When wired this is a high quality F.M. Radio which retail for 2 to 3 times the cost. Complete instructions for easy, rapid assembly. Makes an F.M. Receiver of the highest quality and fidelity. Easily assembled, this F.M. Receiver covers the entire F.M. band from 87.5 to 108.5 megacycles. **NO PERCEPTIBLE FREQUENCY DRIFT** from a cold start. Complete with wired Transvision FMF-2 tuner front end and Transvision F.M. 107R IF amplifier, and 10" 1-M speaker and a matched set of 3 tubes: (3-6AK5, 1-6C4, 1-6V6, 1-5V3, 1-6AL5, 1-6SN7) . . . All component parts are of the highest quality. Assembly is simple to from our easy to follow instructions. For operation on 110 volts, 50-60 cycles AC. **Model FM-1 . . . LIST \$64.95**

Beautiful furniture-finish cabinet available at additional cost. Also, **BASIC ESSENTIAL PARTS** of the Transvision 8-tube F.M. Radio Receiver available separately.

**Transvision FMF-2 2-tube F.M. TUNER Front End . . .** A high fidelity 2-tube Tuner Front End, completely wired, can be used with a wide band 2 or 3 stage IF amplifier (10.7 mc such as the Transvision F.M. 107 or 107R) to form a complete F.M. tuner. **FEATURES:** Tuning range 87.5 to 108.5 megacycle . . . Input matches 300 ohm line **NO PERCEPTIBLE FREQUENCY DRIFT** from a cold start . . . Intermediate frequency to be used is 10.7 megacycles . . . Voltage requirements—6.3 volts at .45 amps, 100 volts at 10 milliamps . . . Positive mechanical drive—no backlash . . . Tube complement—6AK5 mixer, 6C4 local oscillator (tubes not supplied with tuner) . . . Chassis size 4½"x4½" (mounting hole dimensions 3¼" x 3¼") . . . When used with our FM107 I.F. Amplifier a 15 microvolt signal will give to within 5 DB of absolute alignment. . . . **LIST (less tubes) \$21.65**

**Model FMF-2 . . . F.M. 3-tube IF AMPLIFIER KIT . . .** Characteristics same as the above, with the following differences: 3 tubes—6J6 RF Amplifier, 6AK5 Mixer, 6C4 Local Oscillator—Added RF stage; RF stage gain is 8 minimum Image ratio is 500-1 minimum . . . Chassis size is 7¼"x4½" (mounting hole dimension 3¼"x3¼") . . . Voltage requirements, 6.3 volts at 1.05 amps, 150 volts at 30 mills. **NO PERCEPTIBLE FREQUENCY DRIFT** from a cold start. **Model FMF-3 . . . LIST (less tubes) \$30.75**

**Transvision F.M. 107 (10.7 mc) . . . F.M. 6-tube IF AMPLIFIER KIT . . .** A six tube high gain, broad band, intermediate frequency amplifier designed for use with either the Transvision FMF-3 or FMF-2 Tuner Front Ends. Also useful in other applications where an amplifier of this type is required. For optimum performance three 6AG5's used in the intermediate amplifier, two 9001's are used as limiters and a 6AL5 as a demodulator. IF frequency is 10.7mc. Bandwidth is 150KC. Chassis size is 13" x 2½" wide. Mounting hole dimension 12" x 2¼". . . . **LIST (less tubes) \$41.20**

**Transvision F.M. 107R (10.7 mc) . . . F.M. 3-tube IF AMPLIFIER KIT . . .** A three tube broad band intermediate frequency amplifier for use with either the Transvision FMF-2 or FMF-3 Tuner Front Ends. Comprised of a ratio detector and 2 stages of I.F. Bandwidth 150 KC. A 6AL5 Dual diode tube used as a ratio detector also provides AVC voltage for a tuning indicator. Unusually high gain is obtained by the use of 2 6AK5's and in the two I.F. stages. Chassis size 2¼" x 8". Mounting hole dimension 2¼" x 7¼". **Model F.M. 107R . . . LIST (less tubes) \$21.65**

**Transvision Television FOLDED DI-POLE ANTENNA . . .** Especially designed for broader antenna tuning and matched impedance to the 300 ohm transmission line. Range, 44-88 mc . . . Complete with 60 ft. of 3000 ohm lead-in wire . . . Mast and wall stand-off insulators . . . Metal mast with universal base mount . . . Aluminum Di-pole elements . . . **LIST \$12.00**

**Transvision Television ANTENNA REFLECTOR KIT . . .** Converts Folded Di-pole model Antenna to Folded Di-pole with Reflector model. Provides maximum directional gain of the desired signal and eliminates undesirable and interfering reflections. . . . **LIST \$6.45**

**Transvision Television PICTURE BLOW-UP LENS . . .** Brilliantly enlarges any 7" and 10" television picture to equivalent picture of 12" television set at substantial savings. This plastic lens gives 75 square inch picture in place of original 25 or 52 square inch pictures of any 7" and 10" television sets . . . Provides high fidelity enlarged optical image . . . ½ weight of glass lens of similar magnification power . . . **OPTICALLY GROUND AND POLISHED TO HIGH ACCURACY (Not a molded product) . . . LIST \$39.95**


**50% greater light transmission than equivalent glass lens. . . . LIST \$3.25**

**Transvision FEATHERWEIGHT SOLDERING IRON . . .** Fingertip control. High working output. Low current drain. A revolutionary 3 ounce featherweight soldering iron that delivers the working output of a big 200 watt iron with only a fraction of the current drain. NOTE THESE NEW, REMARKABLE FEATURES: Weighs only 3 ounces (without the cord) . . . Delivers working output of 200 watt iron at fraction of current normally consumed by heavier irons . . . Heats up in 20 seconds . . . Fingertip control . . . Cool grip . . . Retains heat (with switch off) up to one minute . . . Featherweight permits long periods of soldering without fatigue . . . Economical—intermittent control feature prevents tip corrosion and necessity of frequent cleaning . . . Long, thin tip permits soldering in tight corners . . . Tips are interchangeable to suit work at hand . . . For operation on 110V AC, 60 cycles. Complete with 6 volt transformer . . . **LIST \$13.95**

**Lectrovision 7EP4 7" Picture Tube . . .** Gives brilliant, sharp contrast. . . . **LIST \$23.00**




12" KIT (Table Model)

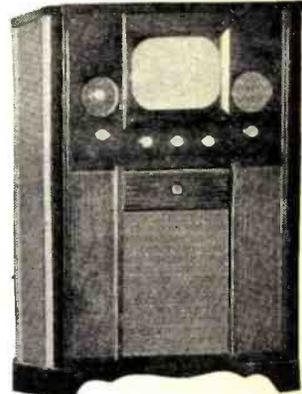


12" KIT (Console Model)



7" KIT (Table Model)

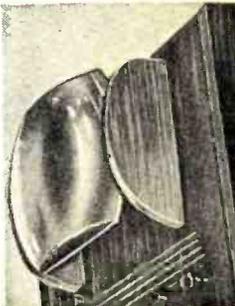


BLOW UP LENS

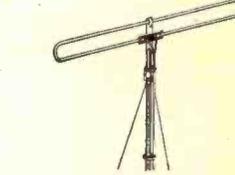


Folded Dipole Antenna



Reflector Kit

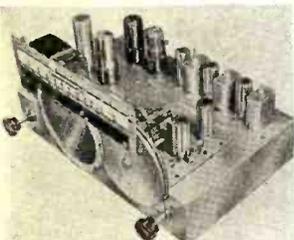


FMF-1 FM Radio Receiver

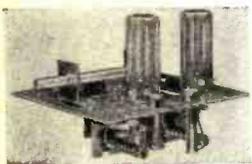

FMF-2 FM Tuner Front End



FMF-3 FM Tuner Front End

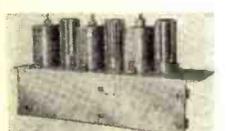

FM107 FM IF Amplifier Kit



FM-107R FM IF Amplifier Kit



Featherweight SOLDERING IRON

All prices listed above are 5% additional west of the Mississippi. All prices are fair traded. See your local distributor, or for further information write to:  
**TRANSVISION INC., Dept. R. N. 385 North Ave., New Rochelle, N. Y.**  
 October, 1947 133

# Here's News!

## ABOUT OUR AM-FM TUNER

It's the finest quality that money can buy. Latest design features are all included—uses all miniature tubes. Ideal for use in a custom radio installation or may be installed in any cabinet.



### 8 TUBE MODEL TU 6 AM-FM TUNER

#### Controls:

- Off-On — Phono — Television
- Band Switch (AM-FM)
- Tuning Control

### SPECIAL FEATURES

1. Automatic Frequency Control — First time used on any tuner. Makes this tuner free from the usual drift. Eliminates the need of a tuning indicator. On FM this tuner tunes like a standard broadcast receiver. Only one response point.
2. Large slide rule type dial, calibrated in Megacycles on FM and in Kilocycles on AM. Edgelighted for maximum beauty and brilliance.
3. Tuned RF stage for FM
4. RF Amplifier for AM.
5. 5 Gang Tuning Condenser.
6. Frequency Range:
  - FM — 88 — 108 MC
  - AM — 550 — 1600 KC
7. Polished chrome chassis for the ultimate in long-lasting beauty.
8. Top Quality Performance. Extreme sensitivity and selectivity. Highest quality reception of any AM-FM tuner.
9. 105-125 Volt AC operation.
10. Built-in loop antenna on AM. Built-in dipole antenna for FM reception.
11. Separate IF transformers for both AM and FM to insure maximum performance.
12. Band switch is ultra new "Flat" type permitting extremely short leads for best performance.
13. Phonograph input provided on tuner chassis for playing records. Phonograph switch included.
14. Television tuner input also provided on this model with switch.

The 2 above features provide great versatility in application for this tuner. The TU 6 tuner represents the absolute ultimate in AM-FM tuner design. All of the very latest, most modern features are included.

**THIS TUNER MAY BE USED WITH OUR AK 20—HIGH FIDELITY AMPLIFIER**

USE THE COUPON BELOW for free information on one or both of these products.

The RADIO CRAFTSMEN, Inc.  
Makers of craftsmen built Products  
1341 SOUTH MICHIGAN AVENUE  
CHICAGO 5, ILLINOIS  
Cable address: "Radcraft"

THE RADIO CRAFTSMEN, INC.  
1341 South Michigan Avenue  
Dept. N, Chicago 5, Ill.  
Gentlemen: I am interested in:

Send complete information without obligation.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

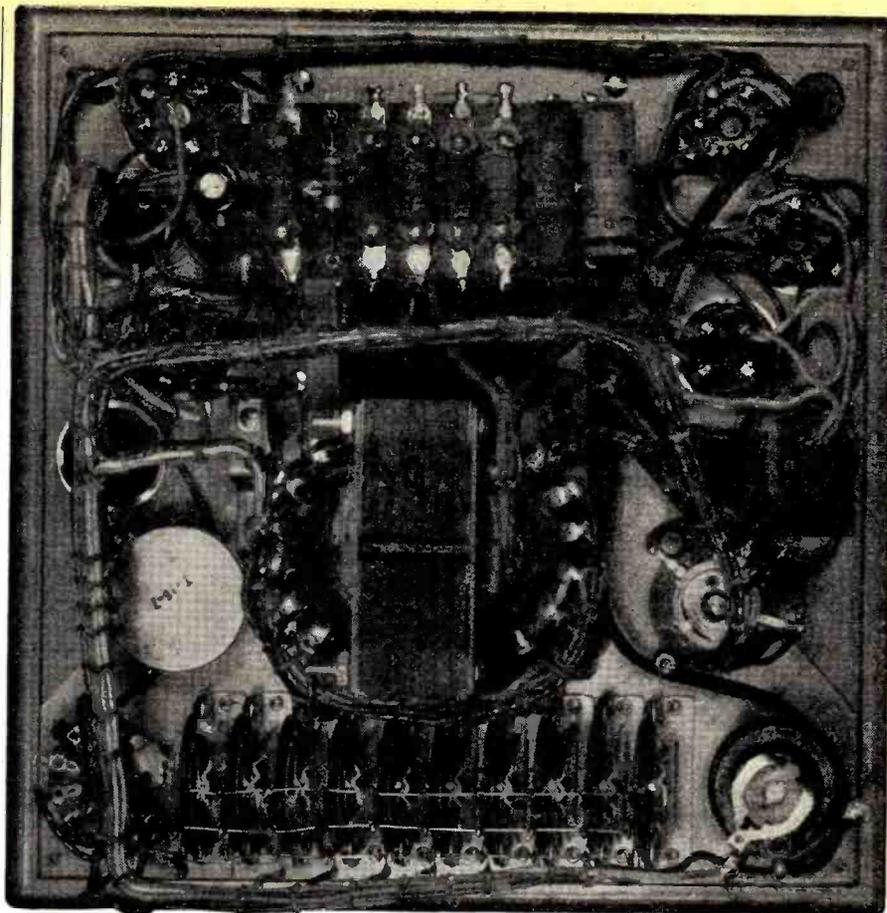


Fig. 4. Internal wiring and placement of component parts of the tube tester.


indicated by a glow of the "short-test" lamp with the test knob in "SHORT" position.

Changes in line voltage and variations due to different filament currents are compensated for by adjustment of the line control knob (R.). This changes the transformer primary volt-

age and the correct voltage is indicated by a rectifier type voltmeter connected across the transformer 100 volt secondary winding. The "GOOD-BAD" indicating instrument is converted to a simple rectifier type voltmeter by turning the "test" switch to "LINE" position.

—30—

Two great titans of the transportation world were linked recently when passengers aboard the General Motors' "Train of Tomorrow" talked to persons aboard the H.M.S. Queen Elizabeth in Mid-Atlantic. The 152-162 mc. band was used for the transmission. A Motorola transmitter-receiver was installed in the train and used for talk-out only. An a.c. operated receiver was used to pick up the talk-back from the ship. An aerial pickup of the transmission was made and then carried over leased wires to WGN where it was carried over Mutual landlines to New York, then via ship-to-shore radio to the ship. Inset shows the ground plane antenna with quarter-wave whip used on train.

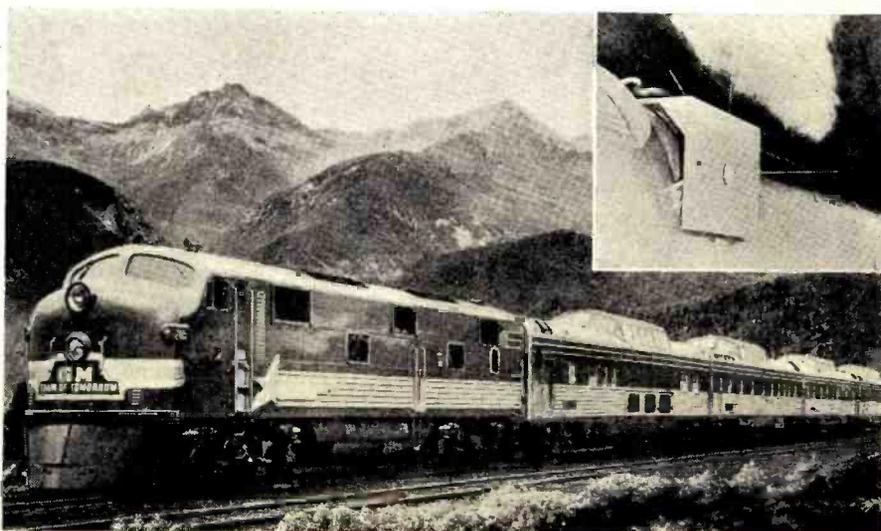

IT'S

**Wells**


FOR

**COAXIAL CABLE  
and CONNECTORS**



We have many types of coaxial cable in stock available for immediate delivery. It is all of the highest quality, government inspected material and is attractively priced. Popular RG8U 52 ohm cable only \$2.95 per hundred feet.

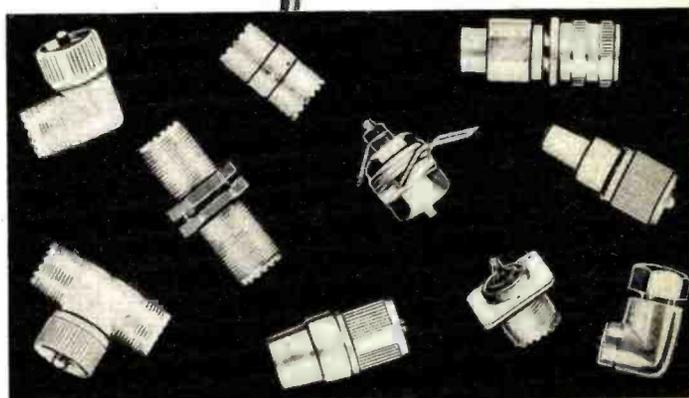All standard and British type connectors are carried in stocks adequate for the largest users. Most single contact connectors priced at only 40c each. Most twin contact connectors are 45c each. Send us your requirements or write for coaxial cable and connector listing 100A.



Our inventory of radio-electronic components is one of the world's largest. Write for special listings on relays, wire wound resistors, volume controls, wafer switches, micro-switches, transmitting tubes, mica and silver mica condensers, transmitting tubes, tube sockets, terminal strips, transmitting capacitors, oil filled paper condensers, wire, and Amateur Catalog H200B.

**WELLS  
SALES, INC.**

All Wells Material Available Through  
Your Jobber at Advertised Prices

320 N. LA SALLE ST., DEPT. R-10, CHICAGO 10, ILL.

-In New Jersey...  
...it's **VARIETY**-

Sensationally New

# TRANSVISION

## 12" TELEVISION KIT

**STANDARD MODEL**—Picture size 75 square inches. 22 tubes and 12 inch picture tube. High fidelity FM sound reproduction. Advanced television circuit provides exceptionally clear pictures.

### DELUXE MODEL

—with Super B Built-in FM Radio.

12" Standard Television Kit.....\$289.50\*

12" DeLuxe Television—FM Radio Kit. 359.50\*

7" Television Kit.....159.50\*

(\*Complete with tubes, less cabinet)

Dealers Prices on Request.

Cabinet for 12" Television Receiver... 44.95



### NEW! PREMIER Model 570 MICROMASTER Band Spread Dial SIGNAL GENERATOR

For testing and aligning BROADCAST, SHORT-WAVE, FM and TELEVISION RECEIVERS. Exclusive Band Spread Dial geared to the tuning condenser and main dial, giving a total scale length of approximately 60 inches. Three-color dial directly calibrated in Kilocycles and Megacycles. Range: 75 KC—50MC. Size: 12 1/2" x 12" x 5 1/4"

COMPLETE WITH TUBES AND CO-AXIAL CABLE. \$54.75 NET



### 6" PM SPEAKERS 5 for \$7.49

1/2 meg. VOL. CONTROL with SWITCH (Clarostat) 3/4" length shaft. 10 for \$4.59

1/2 meg. VOL. CONTROL without SWITCH (Clarostat) 1 1/2" length shaft. 10 for \$2.49

HOWARD SAMS Photo Fact Folders ea. \$1.50  
HOWARD SAMS Photo Fact Folders Vol. I and II.....ea. 18.39

### Bargain! Guaranteed!

100 Assorted Bypass Condensers 600V Value \$11.00. SPECIAL \$6.95

### SUPERIOR Model 670 Super-Meter

A Combination Volt - Ohm Milliammeter plus Capacity Reactance Inductance and Decibel Measurements.

Complete with test leads and instructions. \$28.40



Full line of Weston-R.C.P.-Supreme-Superior-E.M.C.-Test Equipment

Write Dept. RN-10. 20% Deposit with order required. Please add sufficient postage. Excess will be refunded.

**Variety ELECTRIC CO., Inc.**  
601 Broad St., Newark 2, N. J.

# Technical BOOKS

**"HIGHWAYS IN THE SKY—THE STORY OF THE AACCS"** by Louis Shores. Published by *Barnes & Noble*, New York. 252 pages. Price \$3.00.

Major Louis Shores, historian for the AACCS, has written a thrilling and thoroughly readable report on the often unappreciated work of the Army Airways Communications System. Although the general public rarely heard of the work of these men, many aviators, following the skypaths laid out by these radiomen, owe their lives to the fact that this ingenious and hard-working part of the Army had blazed unmistakable trails across the uncharted wilderness of the sky.

Although the wartime usage of the AACCS system is a thing of the past, the stations and routes set up by this group can now provide new highways for the ever-growing, world-wide commercial aviation network.

Beset by difficulties and tragic shortages of materials, the work of the AACCS and this book stand as a tribute to American radiomen. The teamwork displayed by this widely scattered branch of the service is worthy of the best radio tradition.

We would like to recommend this book enthusiastically to our readers because it is moving tribute to that unsung profession which can be depended upon in a crisis to make good bricks without straw—or rather workable equipment from materials at hand. All royalties on this book have been assigned to the AAF Aid Society so in purchasing this book you are not only letting yourself in for a lot of good reading but helping out a very worthy cause.

**"AIRCRAFT ELECTRICITY FOR THE MECHANIC,"** by Charles Edward Chapel. Published by *Coward-McCann, Inc.*, New York. 461 pages. Price \$5.00.

There are few texts on the market today that are devoted exclusively to a single phase of the electrical field as applied to a specific industry. Sensing the need for a practical, "how-to-do-it" book on the subject of aircraft electricity, the author has prepared a thoroughly workable text which may be used either as a home study volume or in formal classroom work.

Since the problems encountered in the servicing of aircraft differ greatly from those to be found in other electrical fields, the book deals directly with electrical circuits as they are found in modern aircraft. After a brief but necessary discussion of the fundamentals of electricity, the author swings into the aircraft field with a discussion of the aircraft storage battery, generators, generator control systems, motors, ignition systems, aircraft electric instruments, engine starting systems, lighting, landing gear circuits, remote control battery sys-

tem, electric propeller control systems, wire identification systems, etc.

Diagrams have been used extensively to illustrate the material under discussion. In addition, a series of review questions accompany each chapter in order that the student may check his grasp of the subject and so prepare for licensing examinations.

Three especially valuable chapters deal with aircraft electrical inspections, outlining the procedures and requirements; how to get a job; and a listing of the tools which the aircraft maintenance electrician will need in his trade.

**"SLIDE RULE SHORT CUTS"** by W. P. Miller, San Diego, California. 15 pages. Price \$1.50.

The second edition of this slide rule handbook has been especially designed to assist radio and electronic engineers, and technicians with a practical guide to slide rule techniques.

Particular attention has been paid to the location of the decimal point in calculations by slide rule. In addition, short cut methods for calculating voltage, current, resistance, wattage, inductance, capacity, frequency, reactance, resonant frequency, joint resistance and joint capacity, power factor and reactive factor, series impedance and power factor, parallel impedance and power factor, high-Q impedance, and converting decibel values are given.


This booklet should be particularly useful for the technician who must devote many hours to the solving of electrical and radio formulas.

**"FAR EAST TRADE DIRECTORY"** Published by *Trade Guide and Directory, Far East, Inc.*, New York. Price \$7.50.

This is the first postwar trade directory of the Far Eastern countries, including the Indian Empire.

Designed to meet the need for an accurate and up-to-date list of Far Eastern exporters, importers, manufacturers, distributors, manufacturers' agents, and other firms, all of which are classified according to the service they render, this new directory is particularly valuable for the American business firm working in the export field.

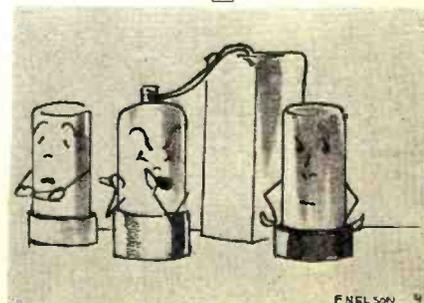Each listing has been checked and rechecked during the past 14 months to insure accuracy and reliability of the information contained in the book.



"I wouldn't be caught dead on the same chassis with her!"

# COMMUNICATIONS

## HIGHEST VALUES—LOWEST PRICES!



### TUNING UNITS

Tuning Units for TCE & GP7 in following freq:  
 A—350-800 Kc, B—800-1500 Kc, C—1500-3000 Kc, E—4525-6500 Kc, F—6200-9050 Kc.  
 Contains all coils, etc. Complete set of 5. **\$11.00**  
 Units C or F, Each. **2.75**  
 Units A, B, E, Each. **2.00**  
**From BC191 and BC375** contains coils, chokes, dials, condensers. Range 400 Kc to 12.5 Mc. State your approx. freq. **\$2.75**

### MICROWAVE PLUMBING

#### 1.25 CENTIMETER

Wave Guide Section 1' cover to cover. **\$2.00**  
 T section choke to cover. **4.50**  
 Mitred Elbow cover to cover. **3.00**  
 Mitred Elbow and "S" sections choke to cover. **3.50**  
 Flexible Section 1' long choke to choke. **3.00**  
 Tunable Cavity with Coax input and output. **6.00**

#### 3 CENTIMETER

T Sections. **\$5.50**  
 Wave Guide Sections 2.5' long silver plated with choke flange. **5.75**  
 Wave Guide 90 deg. bend E plane 18" long. **4.00**  
 Wave Guide 90 deg. bend E plane with 20DB directional coupler. **4.75**  
 Wave Guide 18" long "S" curve. **2.00**  
 Feedback Dipole Antenna, choke input, (used with parabola). **4.50**  
 Rotary joint wave guide in/out choke to choke joint. **6.00**  
 Rotary Coupler choke input: round guide output. **5.25**  
 S curve Wave Guide 8' long cover to choke. **5.95**  
 Wave Guide 2.5' long, silver plate, 180 deg. bend choke to cover. **10.00**  
 Duplexer section using 1B24. **10.00**  
 Wave Guide with slotted section and rotary joint. **4.00**  
 Wave Guide 5' length per foot. **1.50**  
 Pick-up loop with adjustable tuning section, used in duplexer. **1.50**

#### 10 CENTIMETER

Sand Load (Dummy Antenna) wave guide section with cooling fins app. 23" high. **\$28.00**  
 Wave Guide to coax with flange, gold plated app. 10" high. **17.50**  
 Rigid Coax Directional Coupler CU-90/UP 20 DB drop, has short right angle, about 8". **5.50**  
 10 CM Dipole Ant. with Bar Reflector 3" high S.P.—coax conn. **2.75**  
 Standing Wave Detector rigid coax 58 ohms Coax Rotary Joint with mounting plate. **8.00**  
 Antenna in lucite ball for use with parabolic. **5.00**  
 Flexible Coaxial Connector, rigid coax to rigid coax 7/8" diam. **2.50**

#### SPECIAL

**Maguire Wavemeter**—No. 1539TFX, 3cm vernier dial and resonant cavity. **\$20.00**

#### THERMISTORS

D167332 bead. **\$0.95**  
 D170396 bead. **.95**  
 D168391 button. **.95**  
 D167613 button. **.95**

Decade Resistance Box. Two circuit 0-1250 ohms in 250 ohm steps 3"x4"x6". **\$1.00**

#### MAST BASES

With rubber shaft. **\$1.00**  
 Spring type. **1.50**  
 Rocker arm type. **2.00**


**RADIOSONDE TRANSMITTER** with 3A5 tube made to hang on parachute. **\$2.75**  
 4 1/4"x2"x2"

Leach DPDT Ceramic ant changeover relay—160 ohm coil. Plate current of 140 ma will close. Use in B—lead. Each. **\$1.25**


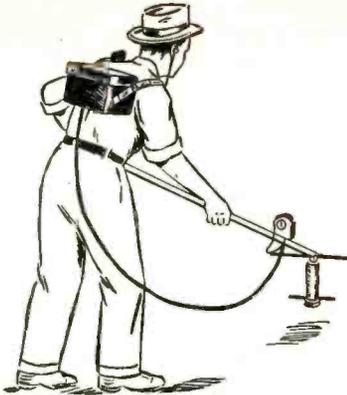
#### CROSSPOINTER INDICATOR


Two 200ua movements in one case. **\$1.89**



**MINE DETECTOR AN/PRS 1**—Will indicate buried metallic and non-metallic objects. Includes Detector unit amplifier in case, all tubes, cables, etc. New complete unit. **\$10.00**
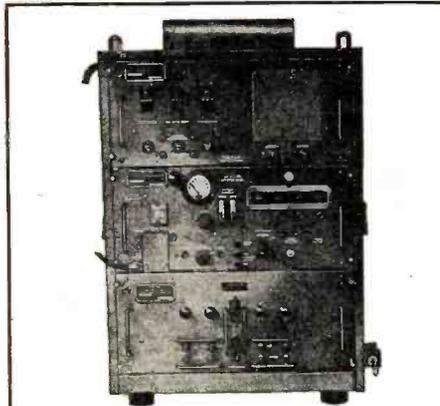
### MICROWAVE TUBES

3J31 (1cm) **\$17.50**  
 Magnet for 3J31. **8.00**  
 2J26 (10 cm) **25.00**  
 2J32 (10 cm) **25.00**  
 Magnet for 2J32. **10.00**  
 2J38 (10 cm with Magnet) **37.50**  
 WE700A (L band) **45.00**  
 WE720BY (S band 1000 KW) **25.00**  
 2K25-723AB Klystron. **7.75**  
 QK 59, QK 60, QK 61, QK 62 Tunable packaged Magnetrons (10cm) **45.00**



**RC 145**—154-186mc. 1 kw pulse output 117 VAC. Power supply and Indicator with Selsyn for beam control. Plenty of room for exciter stages. Includes blower and rack—29 1/4"x29 1/2"x20 1/2". **\$200.00**  
**RC 148**, consists only of transmitter and power supply. Both units with tubes. Used. **\$47.50**


### RELAYS

**MINIATURES**  
 SPDT 24 VDC. **\$0.40**  
 SPST 28 VDC. **.40**  
 DPDT 28 VDC. **.40**  
 SPST 100 V Overload 380/1800 cy. **.40**  
**TELEPHONE TYPE**  
 SPDT with cover. **\$1.05**  
 DPST. **1.05**  
**MISCELLANEOUS TYPES**  
 SPDT 5 VDC in can 5 pr base. **\$0.85**  
 DPDT 6 VAC Struthers Dunn. **1.45**  
 DPST 6 VAC Struthers Dunn. **1.35**  
 2 sect DPDT 6VAC Wheelock type **1.10**  
 SPDT 115 AC Leach. **\$1.00**  
 SPDT 115 AC WE Wheelock type. **1.26**  
 SPDT 115 AC Kurman latch. **2.49**  
 SPDT 115 AC GE with SPDT thermal delay section. **1.95**  
 DPST 24 DC Allied. **.75**  
 DPDT Leach ANT with SPST rec sect 24DC & 12 DC. **1.25**  
 4PDT 24VDC GM. **.85**  
 Solenoid Contactor 24 VDC Leach. **1.05**  
 Thermal Delay 45-60 sec Edison 1503 w 4pr base. **2.95**  
 6 VDC Relay panel with 3DPST & 2SPST on 10"x7" panel. **2.75**

ALL MERCHANDISE GUARANTEED. Mail orders promptly filled. All prices F. O. B. New York City. Send Money Order or Check. Shipping charges only sent C.O.D.
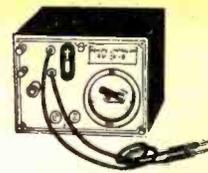
# COMMUNICATIONS EQUIPMENT CO.

131-N Liberty St., WH 4-7658, New York City 7, N.Y.



### Remote Control Unit RM-29.

Ideal for telephone Intercommunication over distances up to several miles. Includes ringer. Two units complete with handsets for 2-way communication. **\$14.00**  
 RM-29, each. **5.50**  
 Handsets, each. **2.00**

### TRANSFORMERS

Power Pair—Use 2 for FW 1900V CT at 330ma pri 117V 60 cycle—3 Taps. Ea. Transf is cased. 950V no CT. Per Pair. **\$10.00**

#### All Primaries 117V 60cy Secondaries:

No. 5084—1000V CT @ 250ma, 6.3V @ 1.5A. **\$6.95**  
 No. 5114—1500V CT @ 200ma and 5V @ 3A. **6.95**  
 No. 5190—6180V @ 200ma. **14.75**  
 No. 5057—6.3CT 1A, 5V CT 3A, 5V CT 3A. **2.75**  
 No. 5104—6.3V @ 1A, 6.3V @ 1A, 6.3V @ 1A. **2.45**  
 No. 5126—5V CT 3A, 5V CT 3A, 5V CT 6A. **3.25**

### CHOKES

Amertran—RMS test 15KV, 1 Hy, .8 amp DC, DC resistance 7.5 ohms. **\$8.95**  
 8.5 Hy. 125ma, 1780V Test. **1.45**  
 Dual: 7Hy. 75ma. 11 Hy. 60ma, 1780V test. **1.95**  
 6 Hy. 150ma. **2.00**

(Conservative Ratings)

### OIL CONDENSERS

**— SPRAGUE, AEROVOX, C D**  
 15 mf 220 AC 600 DC. **\$1.75**  
 5-5 mf 400DC. **1.05**  
 1-1 7000DC GE. **2.00**  
 Lots of 50. **1.50**  
 10 mf 600DC. **.85**  
 1 mf 1000DC. **.75**  
 2 mf 1000DC. **.89**  
 4 mf 1000DC. **1.00**  
 2 mf 660AC. **.85**  
 1 mf 3000DC. **4.95**  
 1 mf 7500DC. **12.50**  
 .25 mf 20000DC. **17.50**  
 2 mf 1000DC Sprague. **.50**  
 1MF 400V. **.30**  
 1MF 600V. **.35**  
 2 mf 600DC CD. **.40**  
 200mf 250DC. **2.00**  
 4000 mf 30DC CD. **2.50**

### MICAS

.002 mf 15000V Sangamo. **\$20.00**  
 .002 mf 6000V. **8.50**  
 .005 mf 15,000V. **22.00**  
 .006 mf 10,000V. **17.50**

**MFRS**—Send your requirements for Bath-tubs, Micacs, Resistors, Hardware, Connectors

### BC 191 & 375 Transmitters

Used condition. Supplied with one tuning unit of freq. closest to your request. The best buy in surplus... **\$9.95**

**B29 Computer Amplifier.** Contains 8 relays, 8 6SN7 tubes, 5 neons, 1 6x5. Completely wired with all components. New. **Only \$9.95**

**Headgear Dynamic Mike and Headset Combination, sound powered. No battery required. Mike and ear-phones. Complete. \$2.75**  
 New, U.S. Air Corps insert type HS 30, comfortable, lightweight, efficient 500 ohms. **\$0.85**  
 Output trans to match 500 to 8000 ohms. **\$0.35**




# CONVERT YOUR DRY BATTERY RADIO INTO MOST EFFICIENT AC RECEIVER!

GET THE FACTS AND SAVE WITH

**Electro**  
ELECTRICAL AND RADIO EQUIPMENT

## BATTERY ELIMINATORS

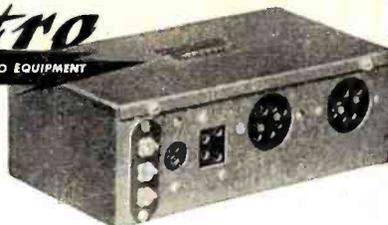

Requires less space than your batteries. Low cost operation. Hum free. Sturdy, trouble-free. Insures superb dependable reception



Ideal for Camps, Summer Cottages, Autos, Boats, Farms, etc. For stationary or portable radios.

### MODEL "Q"

Operates any 1.4 volt, 4, 5 or 6-tube radio from 6-volt storage, or dry battery or Wincharger.

### MODEL "R"

Operates 2-volt, 4, 5, 6 or 7-tube radio from 6-volt storage, or dry battery, or Wincharger. (0.5 amp. filament max.)

### MODEL "P"

Operates any 1.4 volt, 4, 5 or 6-tube radio from 110-volt 60 cy. source. Cuts down current, saves batteries for portable use.

### MODEL "E"

Operates any 2-volt, 4, 5, 6 or 7-tube radio from 110-volt 60 cy. source. (0.5 amp. filament max.)

Send for descriptive folder and name of distributor nearest you.

## ELECTRO PRODUCTS LABORATORIES

549 W. RANDOLPH STREET, CHICAGO 6, ILLINOIS

WE SHIP ANYWHERE IN THE WORLD

*Internationally Famous*

**FLANAGAN RADIO CORP.**

RADIO TUBES UP TO 80% OFF STANDARD LIST PRICES



**FREE CATALOG**

Send for free catalog and prices of hard-to-get Radios, Radio Tubes, Radio Parts, Pickups, Motors, Condensers, Tube Checkers, Volt and Ohm Meters, Signal Generators, Signal Tracers, etc.

**FLANAGAN RADIO CORP.**

America's Largest Stock of Radio Tubes

MAIL ORDER DIVISION  
5251 MARKET ST.  
PHILA. 39, PA.

It's

**Legri S**

Inquire Today!

for

**RESISTORS**

HALF - ONE - TWO WATT

Immediate Delivery!

FROM STOCK

- INSULATED
- ANY TOLERANCE
- (Resistors calibrated within 1 and 2%)
- ANY QUANTITY
- ANY MAKE
- ALL SELECTED

AND SORTED

WE SHIP THE SAME DAY YOUR ORDER IS RECEIVED

**LEGRI S COMPANY, INC.**

Electronic Parts and Components  
846-850 AMSTERDAM AVENUE  
NEW YORK 25, N. Y.

AC 2-0018

## 600-watt Transmitter

(Continued from page 63)

It will be observed that the spacing of  $C_{10}$  is uncommonly low for a phone transmitter. This advantage is afforded, of course, by cathode modulation. The plate spacing is no greater than that ordinarily required for c.w. and the cost of the condenser is appreciably lower than that of the widely-spaced component usually employed at 2000 volts modulated.

Cathode modulation is likewise more lenient as regards excitation. The 807 furnishes sufficient grid drive for cathode modulated 810's. Type 8005 tubes probably would be still easier to drive.

The final amplifier output is link coupled through the coaxial fitting,  $J_1$ . This makes it possible to run a length of neat-appearing coaxial cable, such as *Amphenol* RG-8/U between the transmitter and a remote antenna coupler.

### High-Voltage Power Supply

The main power supply must be capable of delivering 2400 volts of well-filtered d.c. to the transmitter. This voltage divides between the 810's and the 6L6's, with 2000 volts effective between the 810 plates and filament center tap and 400 volts across the modulator unit. The writer employed a variac in the primary circuit of the high-voltage transformer,  $T_1$ , as shown in Fig. 2. This was because the d.c. voltage delivered was nearer 2600 than 2400 and needed to be reduced. However, if the d.c. output voltage is near the 2400-volt mark in a reader's transmitter, the variac will not be a *must*, although an added refinement.

### Metering

A plug-in d.c. milliammeter is used in the various circuits of the exciter. Plugged into jack  $J_1$ , this meter reads oscillator cathode current. At jack  $J_2$ , 807 grid current is indicated; and at jack  $J_3$ , 807 plate current is read. The meter should have two ranges, 0-10 and 0-100 ma. Oscillator cathode current (under full buffer load) will be approximately 65 milliamperes. 807 grid current will vary from nearly zero to nearly 20 ma., depending upon the setting of  $C_6$ , but should be adjusted to 5 milliamperes maximum. 807 plate current must not exceed 100 milliamperes.

For personal safety and the prevention of short circuits, the 807 plate jack,  $J_3$ , must be insulated from the chassis and should be recessed sufficiently to prevent contact with the fingers when the meter plug is inserted. The 807 grid jack,  $J_2$ , must be connected "backwards" (that is, the jack frame must not be grounded, as is the case with  $J_1$ , but must be connected to the lower end of resistor  $R_1$ . If this is not done, the meter connections will have to be reversed when reading 807 grid current.

Grid and plate milliammeters are

**RADIO NEWS**

# Start your own RADIO SERVICE SHOP

Choose one of these  
3 GREAT NEW DEALS

\$99<sup>50</sup>

\$179<sup>50</sup>

\$350<sup>00</sup>

Includes TEST EQUIPMENT, TUBES, PARTS, TOOLS

3 complete going-in-business packages. (If necessary they can be changed to suit your needs.)

There never was a better opportunity than now to start a profitable business of your own. No fuss, no worry. Here's everything you need. Details upon request. Write, wire or phone!

## Featherweight Miniature TEST INSTRUMENTS

Compact — Accurate — Priced Right!

- Jeweled Meter • Range Selector Switch
- All multipliers bridge tested for 1% accuracy
- Zero adjustment—built in batteries
- Molded bakelite case only 3-15/16" x 2-7/8" x 2"

### MODEL 451A AC-DC Volt—Ohm— Milliammeter



A dependable instrument of wide utility—sensitivity 1000 ohms per volt. Ranges: Volts AC, DC, and Output Ranges, 0-10/50/100/500/1000; Ohms full scale, 500,000; Ohms center scale, 7200.

NET complete with batteries

14<sup>90</sup>

### MODEL 312 Volt—Ohm— Milliammeter



An economy pocket meter featuring a 2" moving vane meter. Reads: AC-DC volts, 0-25/50/125/250; Mills AC-DC, 0-50; Ohms, 100,000; mfd., .05-15. Jacks provide range selection.

NET Complete with cord and plug. . . . . 6<sup>75</sup>

### TRIPLETT FAMOUS "LITTLE TRIPLETT'S"

The Little Testers with the big 3" Meters Bakelite cases 3 1/4" x 5 3/4" x 2 1/4" Range selection switch—long, easy to read scales. We made a good buy—here they are at rock-bottom prices—The greatest buy ever offered in precision testing equipment.

### MULTI-RANGE MILLIAMMETERS

Two types—for A.C. or D.C. measurements

MODEL 671—for A.C. current. Seven switch selected ranges of 0-5, 10, 25, 100, 250, 500, and 1000 milliamperes.

MODEL 675—for D.C. current. Eight switch selected ranges of 0-1, 5, 10, 25, 100, 250, 500, and 1000 milliamperes.

Here are two meters you can't afford to pass up—just the thing for radio servicing, transmitter trouble-shooting, general lab and experimental work.

A One-Time only Special buy at

7<sup>95</sup>

### Model 606B-VOLTAGE TESTER



Checks voltage and polarity. Range: 0-440 AC-DC volts—definite indications for 115, 220, and 440 volt lines. Separate polarized vane for AC or DC indication. Built in test leads. Excellent for checking wiring, fuses, general factory installation and maintenance. Every plant—every electrician needs several at this low price. Regular net 16.67 Special at . . . . . 8<sup>95</sup>

### PHONO PICKUP CRYSTALS

Standard types—Set Manufacturers close-out—all Guaranteed



Webster F2—Replaces L26-L40-L70 etc.—pin type terminals—1 oz. pressure—1 volt output—5000 cycle cutoff. List price \$5.00—you pay us. . . . . 14<sup>9</sup>



SHURE P93—W57A—pin type terminals—1/2 oz. pressure—1.6 volt output—6000 cycle cutoff. List price \$4.45—our Special. . . . . 1<sup>98</sup>



Astatic L-70—new post war design—solder terminals—1 1/4 oz. pressure—1 volt output—4000 cycle cutoff. List price \$5.55—we quote you 1<sup>98</sup>

### MIDGET I. F. TRANSFORMERS



400-500 Kc range—1 1/4" square x 2 1/2" high—ceramic based mica trimmers—high gain iron cores—pep up old receivers—ideal for new construction. List price \$2.10—up to 88% discount—stock up now for future use.

Each 2<sup>9c</sup> Dozen 3<sup>39</sup> Hundred 2<sup>500</sup>



### MULTI-USE WIRE

Stranded No. 22 tinned wire—glass "ROCKBESTOS" 1000 volt insulation—fireproof aircraft wire—a wartime development—at this low price you can use the best—

100 feet . . . . . 45<sup>c</sup> 1000 feet . . . . . 3<sup>89</sup>

### TRIPLETT VOLTMETERS



Panel meters by Triplett! Top quality instruments—new—boxed—five popular types—priced right—your chance to get those meters you've always wanted—

- MODEL 332—0-150 A.C. volts—3" round flush mounting black brass case.
- MODEL 231—0-150 A.C. volts—2" round flush mounting bakelite case.
- MODEL 237—0-150 A.C. volts—2" square flush mounting bakelite case.
- MODEL 221—0-30 D.C. volts 2" round flush mounting bakelite case.
- MODEL 324—0-400 D.C. volts—3" round projection mounting—bakelite case.

Supply limited—order now—list models you desire.

2<sup>95</sup>  
EACH

### GENERATOR CONDENSERS



PHILCO part No. 61-0177—5 mfd.—3/4" x 1 1/4"—4" lead-slotted mounting strap for easy installation—Standard Merchandise—not war surplus—Present list price \$1.00. Our special—over 85% off . . . . . 14<sup>c</sup>

### OUTPUT TRANSFORMERS

Clean stocks — long leads — mounting feet — made to fit where you need them.

For 6F6-6K6—to 4 ohm voice coil—size 2" x 1 3/8" x 1 3/8". 50L6-35L6-25L6 to 4 ohm voice coil 1 3/4" x 1 3/4" x 1 3/4". Specify quantity of each type you need at . . . . . 49<sup>c</sup>



49<sup>c</sup>

### RESISTANCE LINE CORDS



Standard 3 terminal 135 ohm AC-DC cords—sturdy construction—flexible—5 1/2' long—complete with plug—for sets having approximately 69-75.2 volts drop in the filaments—Regular list price 1.17—

Only 33<sup>c</sup>

### Pep-Up PHILCO CHANGERS

At last! All the parts you need to restore brilliant tone and volume to "sick" changers! You'll need all three items—sell your customer a 100% reconditioning job—

- Selenium cell only, no holder . . . . . \$1.80
- Sapphire needle only, no mirror . . . . . \$1.20
- Special original equipment lamp . . . . . 27<sup>c</sup>
- RECONDITIONING KIT—all three above items—postpaid—special at . . . . . 3<sup>21</sup>

### CATHODE CONDENSERS



10 Mfd. at 25 working volts—1 1/4" x 1 3/4" tubular type—aluminum cans—overall cardboard sleeve—tinned leads—quality construction by a national manufacturer—backed by the famous R. S. & E. guarantee—list price 75c. Priced to make you money at 12c each lots of 10 for . . . . . 1<sup>08</sup> 100 for . . . . . 9<sup>00</sup>

Order from the Ad  
Write - Wire - Phone

Include full remittance with orders of \$3.00 or less. Include 25% deposit with all C.O.D. orders of \$3.00 or more. All shipments sent express collect if postage is not included. Prices subject to change without notice.

SEND FOR FREE CATALOG

# RADIO SUPPLY & ENGINEERING CO., Inc.


129 SELDEN AVE.

DETROIT 1, MICH.

**FREE! SEND FOR IT**

**ALLIED'S 164-Page RADIO CATALOG**

Save on Everything in Radio!

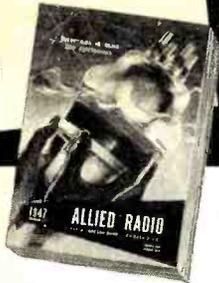

Here is everything in radio—in one **BIG**, easy-to-use book—at prices that save you money! New radios, phonos, complete PA equipment, test instruments, Ham equipment, thousands of parts, tubes, tools, books, diagrams, kits—everything for the experimenter, builder, serviceman, amateur. Send today for this **COMPLETE** Buying Guide. Get everything you need—save at **ALLIED**, Radio's expert, dependable supply source.

**RADIO BUILDERS!**



**Low-Cost 5 Tube Kit**  
Complete with Cabinet, Loop Antenna & Tubes  
The first ultra-modern 5 Tube AC-DC Superhet kit at so low a price!

Here's what you get—full broadcast coverage (550-1600 Kc); built-in loop antenna; latest 5" PM dynamic speaker; handsome walnut plastic cabinet. Easy to build; no special tools required. Sockets are riveted in place; just assemble, wire and slip into cabinet. Outstanding power and tone quality. Highest grade components. Complete with all parts, tubes and full instructions. Nothing like it at the price!  
Shipping weight, 10 lbs.  
No. 83-275. Complete. **ONLY \$14.95**



More than 10,000 items—Complete lines of all leading makes. Largest stocks of hard-to-get parts. Lowest money-saving prices. Get everything you need in Radio from **ALLIED!**



**Public Address**—entirely new line—new styling, new design features. Packaged Ready-to-Use Sound Systems; everything in amplifiers, speakers, mikes, intercom and recording.



**Amateur Gear**—immediate delivery on latest communications receivers. Time payment plan; trade-ins accepted. Headquarters for all ham and experimenters' needs.



**Handy Radio Books**  
Radio Formulas and Data Dictionary of Radio Terms  
Radio Circuit Handbook  
Radio Builder's Handbook  
Simplified Radio Servicing  
Radio Data Handbook  
ALL SIX BOOKS No. 37-799 . . . \$1.00  
Parallel Resistance and Series Capacitance Calculator. No. 37-960 . . . 25c  
R-F Resonance and Coil Winding Calculator. No. 37-965 . . . 25c

**ALLIED RADIO**

ALLIED RADIO CORP.  
833 W. Jackson Blvd., Dept 1-K-7, Chicago 7, Ill.

- Send FREE 164-Page Catalog
- Send Kit No. 83-275
- Send 6 Books No. 37-799
- Send Calculator No.

Name .....  
Address .....  
City ..... Zone ..... State .....

permanently installed in the final amplifier. The ranges of these two meters have been selected to place normal operating currents in the upper quarter of each scale.

**Push-to-Talk Circuit**

For rapid changeover from transmitting to receiving, a simple push-to-talk system has been included in the transmitter. By means of separate 115-volt relays, exciter plate and screen voltages and final amplifier plate voltage are applied when the push-button is depressed. At the same time, a similar relay switches the antenna from receiving to transmitting, and another interrupts the receiver plate-screen power supply. When the push-button is released, the antenna is switched over to the receiver, the receiver power supply is placed in operation, and d.c. voltages are removed from exciter and final amplifier stages of the transmitter.

Since the modulator and speech amplifier receive their d.c. operating voltages from the final amplifier, the relay controlling the high-voltage power supply switches the audio stages on and off as well.

The 115-volt coils of the several relays are connected in parallel and the line voltage is fed to them through the push-to-talk push-button.

**Keying**

For c.w. operation, oscillator keying may be accomplished by plugging the key leads into jack J<sub>1</sub>. The 6L6 modulator tubes must be left running in order to provide final amplifier grid bias. For final keying, a 4000-ohm, 20-watt grid resistor must be connected temporarily between the center tap of the 810 grid coil, L<sub>3</sub>, and meter M<sub>1</sub>. This resistor must be removed before the transmitter subsequently is used on phone. When keying with the modulator tubes running, care should be taken to remove the microphone and/or reduce the setting of the gain control to zero.

It appears that *electronic keying* of the final amplifier might easily be accomplished by means of a keyed d.c. voltage applied to the control grids of the 6L6 modulator tubes, that is, across resistor R<sub>1</sub>. The speech amplifier gain control, of course, would have to be turned to its "OFF" position and the microphone removed. The voltage applied to the grids would have to be

Table 1. Complete winding specifications for oscillator plate coil. L<sub>1</sub>.

BAND (METERS)	SPECIFICATIONS
80	37 t., #20 en. wire. Close-wound
40	21 t., #20 en. wire. Spaced by diameter of wire.
20	9 t., #20 en. wire. Spaced to winding length of 1½ inches.
10.11	3 t., #20 en. wire. Spaced to winding length of ¾ inch.

All coils wound on 1½" diameter forms

**DEPENDABLE  
D. C. Power Supplies**

Whatever your need may be, we have as a standard model or can custom build to your order a dependable source of low voltage direct current. Whether you need a power source for laboratory use, production testing, industrial application, or for powering equipment designed originally for battery use, we can help you.

If your requirements are not filled by the models listed, a letter to our engineering department, giving voltage, current requirements and intended application, will be promptly answered.

Models listed below all plug into standard 115 volt-60 cycle A.C. lines; are housed in attractive metal cabinets, finished in wrinkle enamel; and are equipped with fuse, on-off switch, protective circuit breaker, and pilot light.

**MODEL V-12-30** delivers 12 amperes of filtered direct current within the range of 2-28 volts. Voltage continuously variable by means of control knob. This unit is complete with voltmeter and ammeter. Fine for aircraft radio servicing, production testing, etc. . . . . **Net \$84.50**

**MODEL I-12-12** delivers 12 volts at 12 Amperes filtered D.C. Ideal for operation of your 12 volt surplus equipment requiring 12 Amperes or less. . . . . **Net \$32.50**

**MODEL I-24-10** delivers 24 v. at 10 Amp. filtered D. C. For 24-28 volt equipment requiring up to ten amperes. . . . . **Net \$45.75**

**MODEL I-24-24** delivers 24-28 v. at 24 Amp. Filtered D.C. Unit is suitable for powering ART-13 or BC-375E transmitters and dynamotors in I.C.A.S. operation. . . . . **Net \$87.50**

**MODEL I-24-2** delivers 24 v. at 2½ Amp. of filtered D.C. operating relays, and other low current applications. . . . . **NET \$16.65**

Terms: Check or M.O. with order or 20% with order, balance C.O.D. — F.O.B. Brooklyn, N. Y.

**ELECTRONIC CONTROLS COMPANY**

3124 Avenue I NAvarre 8-5278  
BROOKLYN 10, N. Y.



**TRIG TOWER**  
makes all the difference

**Trig Tower is Rugged**  
Supports top load of 9000 pounds in 90 mile wind. Precision-built of aluminum alloy; triangular, tapered design. Ladder, integral with Tower.

**Trig Tower is Economical**  
Light weight cuts cost of shipping, assembly, footing, erection. Three practical heights: 30 ft., 20 ft., 10 ft., at low net prices.

**Trig Tower is Easy-To-Set-Up**  
Delivered knocked-down with complete instructions, drawings, marked parts. One man can assemble with wrenches alone; two men "walk" Tower into position.  
**TRIG: trim, trusty, sound, firm. . . Webster**

Dept. R

See your local dealer today or write  
**ROSTAN CORPORATION**  
202 East 44th Street, New York 17, N. Y.

**RADIO NEWS**

**SEE  
YOUR  
DISTRIBUTOR**

*Save with Surplus*  
**electronic  
equipment**

**Authorized WAA Electronics Distributors**

**EASTERN**

- |  |   |
|--|---|
| Automatic Radio Mfg. Co., Inc.<br>122 Brookline Ave.<br>Boston, Mass.    | Johanns & Keegan Co., Inc.<br>62 Pearl St.<br>New York, N. Y.         |
| Carr Industries, Inc.<br>1269 Atlantic Ave.<br>Brooklyn, New York, N. Y. | Newark Electric Co., Inc.<br>242 West 55th St.<br>New York, N. Y.     |
| Tobe Deutschmann Corp.<br>863 Washington Street<br>Canton, Mass.         | Radio Parts Distributing Co.<br>128 West Olney Road<br>Norfolk, Va.   |
| Electronic Corp. of America<br>353 West 48th Street<br>New York, N. Y.   | Smith-Meeker Engineering Co.<br>125 Barclay Street<br>New York, N. Y. |
| Emerson Radio &<br>Phonograph Corp.<br>76 Ninth Ave.<br>New York, N. Y.  | Standard Arcturus Corp.<br>99 Sussex Ave.<br>Newark, New Jersey       |
| General Electric Co.<br>Bldg. 267; 1 River Road<br>Schenectady, N. Y.    | Sylvania Electric Products, Inc.<br>Emporium, Pa.                     |
| General Electronics, Inc.<br>1819 Broadway<br>New York, N. Y.            | Technical Apparatus Co.<br>165 Washington St.<br>Boston, Mass.        |
| Hammarlund Mfg. Co., Inc.<br>460 West 34th Street<br>New York, N. Y.     | Tung-Sol Lamp Works, Inc.<br>95 Eighth Ave.<br>Newark, New Jersey     |
| Hytron Radio & Electronics Corp.<br>76 LaFayette St.<br>Salem, Mass.     | W. & H. Aviation Corp.<br>Municipal Airport<br>Rochester, New York    |

**MIDWESTERN**

- |  |  |
|--|--|
| American Condenser Co.<br>4410 N. Ravenswood Ave.<br>Chicago, Ill. | Electro-Voice, Inc.<br>Carroll & Cecil Streets<br>Buchanan, Michigan |
| Belmont Radio Corp.<br>3633 S. Racine Ave.<br>Chicago, Ill.        | Essex Wire Corp.<br>1601 Wall Street<br>Fort Wayne, Indiana          |
| E. F. Johnson Co.<br>206 Second Ave., S. W.<br>Waseca, Minnesota   |  |

**SOUTHERN**

- |  |   |
|--|---|
| Navigation Instrument Co., Inc.<br>P. O. Box 7001, Heights Station<br>Houston, Texas | Southern Electronic Co.<br>512 St. Charles Street<br>New Orleans, La. |
|--|---|

**PACIFIC**

- |  |   |
|--|---|
| Cale Instrument Co.<br>1320 S. Grand Avenue<br>Los Angeles, Calif. | Hoffman Radia Corp.<br>3761 S. Hill Street<br>Los Angeles, Calif. |
|--|---|


**JOBBERS  
WHOLESALERS  
MANUFACTURERS**

You'll save—save—save when you purchase surplus electronic equipment from these Approved Distributors. They are offering electronic tubes, devices and equipment which were declared surplus by the Armed Forces. Fill your needs—now—while inventories still permit large purchases and wide selection.

Purchasing of this equipment has been simplified to a high degree. These WAA Approved Distributors were selected on a basis of their ability to serve you intelligently and efficiently. Write, phone or visit your nearest Approved Distributor for information concerning inventories, prices and delivery arrangements. You'll find you can "Save with Surplus".



Offices located at: Atlanta • Birmingham • Boston • Charlotte  
Chicago • Cincinnati • Cleveland • Denver • Detroit • Grand Prairie,  
Tex. • Helena • Houston • Jacksonville • Kansas City, Mo. • Little Rock, Ark.  
Los Angeles • Louisville • Minneapolis • Nashville • New Orleans • New York  
Omaha • Philadelphia • Portland, Ore. • Richmond • St. Louis • Salt Lake City  
San Antonio • San Francisco • Seattle • Spokane • Tulsa 1322

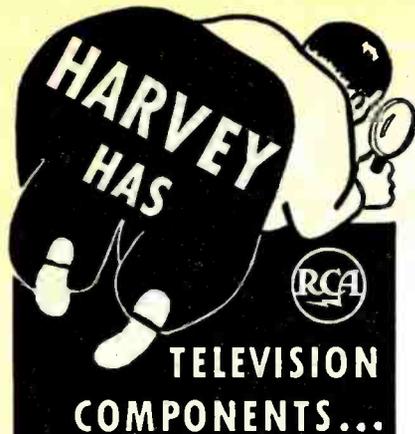

## HARVEY HAS TELEVISION COMPONENTS...

for engineers, experimenters, servicemen and set builders. These genuine RCA components plus everything else you need.

201R1, Width Control .....	.78
201R2, Projection size control.....	1.32
201R3, Horizontal linearity control .....	.84
204X1, I.F. and Video control kit	19.80
204L1, Filament choke.....	.18
208T8, Horizontal synch-discriminator .....	2.85
201D1, Deflection yoke, direct view.....	6.25
201D2, Deflection yoke, projection .....	8.94
201X1, Yoke mounting hood.....	1.62
202D1, Focus coil.....	5.46
203D1, Ion trap magnet .....	3.90
204T1, Horiz. output transformer	13.80
204T3, Horiz. output transformer	8.73
211T1, Horiz. output transformer	10.11
211T2, Horiz. output transformer	13.65
204T2, Vertical output trans. ....	5.40
208T1, Horiz. bl-osc. transformer	3.60
208T2, Vertical bl-osc. trans.....	3.42
208T3, Horiz. bl-osc. trans.....	2.73
RCA 13-channel RF assembly (complete front end for tele receiver)	58.65

### TELEVISION TUBES

RCA 5BP4.....	27.50
RCA 7DP4.....	27.00
Phillips 7EP4.....	23.25
RCA 7GP4.....	24.25
RCA 5TP4.....	67.50
RCA 9AP4.....	62.50
RCA 10BP4.....	49.50
RCA 12AP4.....	75.00
DuMont 15AP4.....	129.50
DuMont 20AP4.....	270.00

Note: All prices are Net, F.O.B. N.Y.C. and are subject to change without notice.

Telephone: **3** Longacre 3-1800

**HARVEY**  
RADIO COMPANY INC.

103 West 43rd St., New York 18, N. Y.

negative and high enough in value to reduce the final amplifier plate current to zero. The circuit would be arranged so that depressing the key would remove this cut-off voltage from the grids. One way of accomplishing this would be to connect a keying relay in the circuit in such a way that its normally-closed upper contacts would be in series with the negative voltage and the 6L6 grids. The contacts then will be opened and the cut-off bias removed when the key is depressed and the relay coil energized.

### Antenna Coupling

A coaxial cable, attached to  $J_1$ , may be employed to link-couple the transmitter to a conventional antenna coupler which then may be placed at the point where the antenna feeders enter the shack.

If a doublet antenna is used for transmitting, the far end of the coaxial line may be connected directly to the center of the antenna, no antenna coupler being required.

The variable link on the 810 plate tank coil,  $L_4$ , permits convenient and smooth variation of final amplifier loading.

### Construction Hints

The various circuits of the transmitter are, in general, so conventional that all of the rules of good design and layout applied to other transmitters pertain equally well here.

In the exciter section, care must be taken to isolate the input and output circuits of the 807 stage. With this in mind,  $C_5$  and  $L_1$  must be enclosed in a heavy-gauge shield box or else mounted below chassis.  $C_{10}$  and  $L_2$  must be kept above chassis. An external shield can must enclose the 807 tube and extend as high as to the bottom of the plate electrode. If there is any tendency toward parasitics in the 807 stage, 50-ohm, 1-watt carbon resistors must be connected in the 807 grid and screen leads.

There should be ample room on the final amplifier chassis for free circulation of air. However, over-long leads must be avoided. This applies especially to leads run between tuning condensers and coils. All external connections must be made to reliable terminal strips mounted on the backs of chassis.

Metal 6L6 tubes must be used in the speech-amplifier-modulator. Results are not nearly so satisfactory when 6L6G's are employed. Leads in this stage must be kept as short as practicable. The microphone jack,  $J_5$ , and the first grid resistor,  $R_1$ , should be enclosed in a small metal can to minimize hum and r.f. pickup. For the same reason (hum), filament transformer  $T_1$  and filter choke  $CH_1$  must be mounted on the end of the chassis farthest away from the 6SJ7 tubes. It is a good idea to mount the filament transformer on top of the chassis and the choke underneath. The lead connecting the 6L6 plates to the 810 filament center tap must be shielded with

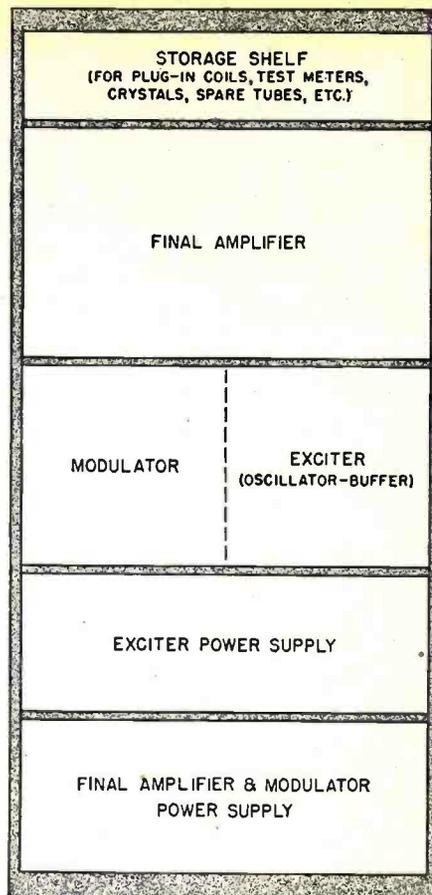


Fig. 4. Transmitter arrangement. Compare with Fig. 1. Cabinet measures 71 inches high, 37 inches wide and 20 inches deep.

metal braid and this shield must be connected to the modulator chassis on one end and to the final amplifier chassis on the other end.

The separate chassis must be bonded together electrically with a heavy conductor wire (at least No. 12) which, in turn, must be connected to the best available ground in the shack, for example to the cold water pipe. This is an important matter which must not be overlooked by the operator. Personal safety and stable operation are enhanced by this ground connection.

### Assembly

Most amateurs undoubtedly will favor rack and panel construction, which is entirely permissible. Our personal preference is the plain chassis type of construction, since this allows us to place each component in its best electrical position with no concern as to the final appearance of controls on a front panel.

The accompanying photographs show how our transmitter is arranged. The separate chassis have been mounted on the adjustable-height shelves of a regulation steel utility cabinet. This cabinet, which is 71" high, 37" wide, and 20" deep, was obtained at an office-supply house and is usually known as an "office storage cabinet." The four lower shelves hold the transmitter chassis, while the top one is used to store extra plug-in coils, crystals, spare tubes, meters, and other trans-

# All Brand New RADIO TUBES!

Save up to 80%

### ALL STANDARD BRANDS

Type	Price
*02A	\$1.10
1A5GT	.75
1A7GT	.90
1B5/25S	.90
1C5GT	.90
1G4GT	.90
1H4G	.90
1H5GT	.75
1L4	1.10
1L4A	1.60
1L4A	1.60
1L4B	1.60
1L4C	1.60
1L4D	1.60
1L4E	1.60
1L4F	1.60
1L4G	1.60
1L4H	1.60
1L4I	1.60
1L4J	1.60
1L4K	1.60
1L4L	1.60
1L4M	1.60
1L4N	1.60
1L4O	1.60
1L4P	1.60
1L4Q	1.60
1L4R	1.60
1L4S	1.60
1L4T	1.60
1L4U	1.60
1L4V	1.60
1L4W	1.60
1L4X	1.60
1L4Y	1.60
1L4Z	1.60
1L5	1.10
1S4	1.10
1S5	1.10
1T4	1.10
1T5GT	1.10
1U4	1.10
1V	.62
2A3	1.32
2A6	1.10
30A	1.10
30SGT	1.10
3S4	1.10
3V4	1.10
*5T4	1.32
SUN	.67
5V4G	1.10
5W4GT	.62
5X4G	.75
5Y3GT	.47
5Y4G	.52
5Z3	.75
*5Z4	.90
6A6	1.10
6A7	.67
*6A8	.90
*6A87/1853	1.32
6AC5GT	.90
*6AC7/1852	1.32
6AD7G	1.10
6AF6G	1.10
6AG5	1.60
*6AG7	1.60
6AK5	.90
6AL5	.90
6A05	.90
6A07GT	1.10
6AT6	.75
6B4G	1.32
6B7	.90
*6B8	1.32
6B8A	.90
6BE6	.90
6C4	.75
*6C5	.75
6C6	.67
6C8G	1.10
6D6	.67
6DBG	1.10
6E5	.75
*6F6	.75
6F8G	.90
6G6G	.90
*6H6	.75

\* METAL TYPES

### ALL IN CARTONS

Type	Price
6J5GT	\$.62
6L6	1.32
*6J7	.90
6K5GT	.95
6K6GT	.67
*6K7	.75
6K8GT	.90
6L5G	.75
6L6G	1.32
*6L7	1.10
6N7GT	1.10
6P5GT	.90
*6Q7	.90
6R7	1.10
6SA7GT	.75
*6S87Y	1.32
*6SC7	.90
6SD7GT	1.32
6SF5GT	.90
*6SF7	.90
*6S7	.90
6SH7GT	.90
6SJ7GT	.75
6SK7GT	.75
6SL7GT	1.10
6SN7GT	.90
6SO7GT	.75
*6SR7	.75
*6SS7	.67
*6ST7	1.10
6U5/6G5	.90
6U7G	.67
*6V6	1.32
6V6GT	.75
6X5GT	.67
6Y6G	1.19
7A4	.90
7A5	.90
7A6	.90
7A7	.90
7A8	.90
7B5	.90
7B6	.90
7B7	.90
7B8	.90
7C5	.90
7C6	.90
7C7	.90
7C8	.90
7E5	.90
7E6	.90
7E7	1.10
7E7	1.10
7F7	1.10
7F8	1.32
7G7/1232	1.32
7H7	1.32
7J7	1.32
7K7	1.32
7L7	1.32
7M7	1.32
7Q7	.90
7V7	1.60
7Y4	.90
*12A6	1.32
12A8GT	.67
12AT6	.75
12BA6	.90
12BE6	.90
*12C8	1.32
*12H6	.75
12J5GT	.67
12J7GT	.75

\* METAL TYPES.

### ALL IN CARTONS

Type	Price
12K7GT	\$.67
*12K8	1.10
12Q7GT	.62
12SA7GT	.90
*12SC7	.90
12SF5GT	.75
*12SF7	.90
*12SH7	.90
*12SH7	.90
12SJ7GT	.75
12SK7GT	.75
12SL7GT	1.10
12SN7GT	.90
12SO7GT	.75
*12SR7	.75
12Z3	.57
14A7/12B7	1.32
14H7	1.32
14Q7	1.10
14R7	1.10
14T7	.67
25L6GT	.75
25Z5	.67
25Z6GT	.67
26	.52
27	.47
30	.90
32L7GT	1.60
35/51	.67
35A5	.90
35L6GT	.67
35W4	.57
35Y4	1.10
35Z3	.90
35Z4GT	.55
35Z5GT	.57
36	.67
37	.57
38	.75
39/44	.67
41	.57
42	.57
43	.90
45	.55
45Z3	.75
45Z5GT	.75
46	1.10
47	.75
50B5	.90
50L6GT	.75
50Y6GT	.75
53	1.10
55	.75
56	.55
57	.62
70L7GT	1.95
71A	.62
75	.57
76	.62
77	.62
78	.62
78	.62
80	.47
81	1.32
82	.90
83	.90
84/624	.75
85	.62
89	.27
117L7/M7GT	1.95
117N7GT	1.60
117P7GT	1.60
117Z6GT	1.10

\* METAL TYPES.

# Hot Radio Values AT SUN RADIO

## 100 WATT BENDIX TRANSMITTER TA12



CHECK THESE VALUES: Three 807 Tubes, four 12SK7, one 2 inch 5 amp. RF meter, four Separate Master oscillators. (These can be easily changed to cover 20-40-80 meters and by using crystal for the 10-meter band you will have a complete coverage transmitter.)


Four separate output tanks. One 4 position selector channel switch having seven sections which changes the ECO, IPA and output tanks simultaneously. All the controls are mounted on the front panel. The housing is cast aluminum; shields and case are sheet aluminum. Dimensions 11x12x15 inches, weight 35 1/4 lbs. Complete, simple instructions for conversion furnished. Complete with tubes..... **\$49.95**



## SUPERHETERODYNE RECEIVER

This crystal fixed frequency receiver comes with full conversion instruction for variable tuning of all ham bands and broadcast. A highly selective superheterodyne receiver, 110 V.A.C. power supply built in. Uses the following tubes: 6K7—RF Amplifier; 6K8—Mixer and Oscillator; 6K7—I.F. Amplifier; 6F7—Detector and A.V.C.; 6C8—Output and Noise Suppressor; 80—Rectifier. Dimensions—3 1/2x19x11 1/2 inches. Comes complete, brand new, with one set of coils and two sets of **\$16.95** tubes. Extra set of coils..... **\$1.95**

## HAM and POLICE SUPERHET TUNER

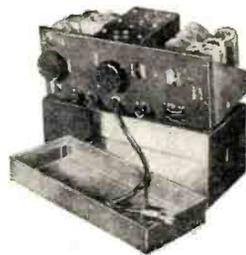

Brand New. Complete with 7V7 (1 Stage T.R.F.), 7Q7 (1st IF & Osc.), 7V7 (2nd IF), 7F7 (Audio) and 7V7 (BFO). Frequency 2.4 to 16.3 mc. Filament voltage required 6.3 AC or DC—2.1 amp. Plate voltage required 135V DC—30MA. Only 4 1/2x 9 1/2x3 3/4", and weighs only 6 1/2 lbs. Ideal for Ham and Police..... **\$14.95**

## G. I. PORTABLE WINDUP PHONOGRAPH



A high quality, sturdily built, full toned windup phono originally built for armed forces as morale phono. Special triple spring motor plays 3 records on 1 winding. Speed adjustable from 33-78 revs. Brand new, packed with 100 multiple **\$19.95** play needles....

## MICROPHONE

**\$1.79**

Brand new single button carbon hand mike by "Shure" with push to talk switch.



## D.C. MILLIAMMETER

Brand new General Electric 2" round panel meters 0-300.



**\$2.97**



## AUTOMATIC Record Player

Including Webster No. 50 changer, three tube amplifier, 5" Alnico V Speaker in a deluxe leatherette case. List..... **\$57.50**  
YOUR COST..... **\$31.95**



## VM RECORD CHANGER

Brand New. Mixes 10 and 12" records.... **\$16.95**  
Wood Base for above **\$3.49**




## V.H.F. TRANSMITTER

Here is one of the greatest offerings in war surplus! Hundreds sold at \$20 and now closed out at an amazingly low price. Brand new. Battery operated (6 1/2 v B and 1 1/2 v A.) Frequency 80 to 105 mc. Complete with 2—1G4 tubes and full instruction manual. Ready to go on the air. **\$6.95**  
Less batteries.....

All Items F.O.B., Washington, D. C. All orders \$30.00 or less cash with order. Above \$30.00, 25 per cent with order, balance C.O.D. Foreign orders cash with all orders, plus exchange rate.
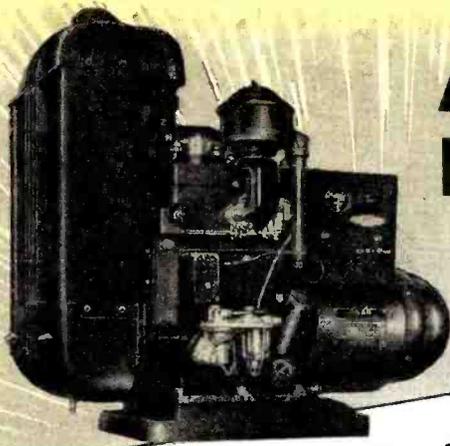
# SUN RADIO

OF WASHINGTON, D. C.  
938 F STREET, N. W. WASH. 4, D. C.



# A.C. OR D.C. POWER

PORTABLE,  
STANDBY OR  
STATIONARY

You can simplify any power-for-electronics problem with an ONAN Electric Plant. A wide range of models and sizes makes it easy to choose the right plant for the particular application.

Lightweight one or two-cylinder air-cooled models for easy portability—A.C.—350 to 5,000 watts, D.C.—600 to 5,000 watts. Onan two, four and six-cylinder water-cooled models are built for continuous heavy-duty operation, stationary or mobile. A.C.—3,000 to 35,000 watts, D.C.—3,500 to 10,000 watts.


ONAN Electric Plants: A.C.—350 to 35,000 watts in standard voltages and frequencies. D.C.—600 to 10,000 watts, 115 and 230 volts. Battery chargers—500 to 6,000 watts, 6 to 115 volts.

**D. W. ONAN & SONS INC.**  
4788 Royalston Ave. Minneapolis 5, Minn.

For—  
Radio Station Standby  
Geophysical Survey  
Railroad Radio  
"Spot" Recording  
Mobile Radio Units  
Municipal Signal Standby  
Amateur Radio  
Write for Folder



## ONAN ELECTRIC PLANTS

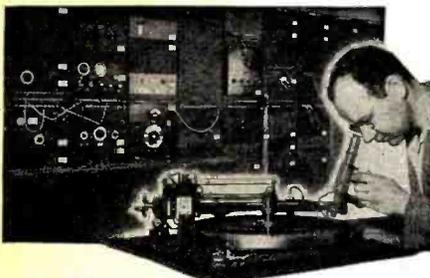

### School of SOUND RECORDING and TRANSMISSION ENGINEERING

Learn sound recording and transmission engineering techniques of the professionals, as used in Motion Picture, Broadcast, F-M, Television, and Commercial Recording Studios.

A nine months practical engineering course, devoted exclusively to the technique of sound recording and transmission measurements. Well equipped studios, professional recorders and circuit laboratory containing latest model test equipment installed for student training. A portion of our laboratory is pictured above.

● New classes admitted the first School day of Jan., Apr., July, Oct.  
*H.W. Tremaine*  
Director  
Affiliated with the Don Martin School of Radio Arts  
Approved for Veterans



Write for literature • Sound Department  
*Don Martin* SCHOOL of RADIO ARTS  
1655 Cherokee • Hollywood 28, California

IT'S HERE!

## TRANSVISION 12" TELEVISION KIT



This 12" television kit is tops in television. Set, less cabinet . . . .

**\$289<sup>00</sup>**

For this low cost you get a kit complete with 22 tubes, 12" picture tube, specially designed dipole antenna with 60 ft. of lead-in wire. Nothing more to buy. Easy-to-follow instructions come with each set. No tools or skills necessary.

De luxe with continuous tuning including FM Broadcasting reception. **\$359<sup>00</sup>**

Table model cabinet in walnut finish for 12" model . . . . **\$449<sup>5</sup>**

Console model in walnut finish for 12" model . . . . **\$745<sup>0</sup>**

Same kit with approximately 50% larger picture. Uses 15" C.R. tube, additional **\$75<sup>00</sup>**

25% with order, balance C.O.D.

**TELETRONICS SERVICE AND SUPPLY CORP.**  
264 WEST 40TH STREET NEW YORK 18, N. Y.  
Phone PENnsylvania 6-8730

mitter accessories. A protective grille made of metal lath normally covers the front of the lowest section, which houses the high-voltage power supply, but was removed temporarily for the photograph, Fig. 1.

The units on the various shelves are identified in Fig. 4.

The microphone is plugged into the left-hand side of the cabinet at the level of the third shelf which holds the modulator. An auxiliary microphone jack has been inserted through this cabinet wall and is protected electrically by a small microphone shield can, seen in Fig. 3. This jack is connected by a short length of shielded cable to a shielded plug which is shown plugged into the microphone jack on the modulator chassis in Fig. 3.

### Adjustment and Operation

When the 810 final amplifier is operating properly, its grid current will be approximately 33 milliamperes; its plate current approximately 330 milliamperes. After carefully neutralizing the final amplifier and testing for and correcting any parasitics in this stage, the transmitter may be adjusted in the following manner:

1. Be sure that the 6L6 tubes have finished heating up before ever applying plate voltage to the 810 stage!

2. Tune exciter throughout.

3. Connect dummy antenna to transmitter output jack and tighten output coupling by swinging link at least three-quarters in on amplifier tank coil  $L_1$ .

4. Apply excitation to final amplifier and tune 810 grid tank to resonance. Reduce speech amplifier gain control to zero.

5. Apply 810 plate voltage and tune 810 plate tank to resonance. If 810 plate current is higher than 330 ma., and grid current is higher than 35 ma., reduce excitation and retune  $C_1$  until plate current is normal. But if 810 plate current exceeds 330 ma. and grid current is 33 ma. or lower, reduce 810 plate current by decreasing antenna coupling (swinging link out of  $L_1$ ). If, on the other hand, 810 plate current is lower than 330 ma., increase antenna loading, excitation, or both, until proper grid and plate currents both are obtained.

6. Advance speech amplifier gain control to about half-scale and whistle into microphone. The modulation should cause some movement, usually downward, of 810 grid milliammeter, but only slight movement of plate milliammeter.

7. At this point, an oscilloscope and, if available, some form of carrier shift indicator should be employed to examine the modulation pattern and percentage. The signal should be listened to with a diode or crystal monitor. If good linearity and resultant good speech quality are not obtained, further adjustments should be made to excitation, antenna loading, and audio level until pleasing results are secured. After several tune-up sessions, the operator will become thor-

# "TAB"

That's A Buy

NEW GUARANTEED


ELECTRONIC PARTS



**VACUUM CONDENSERS**  
 GE 50MMF/7500V ..... \$ 3.95  
 GE 100MMF/7500V ..... 4.95  
 JEN 50MMF/20000V ..... 6.95

**GTD OIL CONDENSERS**  
 10MFD/600VWDC ..... \$ 1.25  
 20MFD/600VWDC ..... 2.50  
 2MFD/330VAC/1000VWDC ..... 1.00  
 13MFD/330VAC/1000VWDC ..... 3.00  
 2MFD/3000VWDC ..... 2.00  
 3MFD/2000VWDC ..... 3.00  
 8MFD/660VAC/2000VWDC ..... 3.00  
 2MFD/3000VWDC ..... 4.00  
 4MFD/3000VWDC ..... 5.00  
 2MFD/5000VWDC ..... 10.00  
 4MFD/5000VWDC ..... 20.00  
 1MFD/1000VWDC ..... 20.00  
 2MFD/12500VWDC ..... 25.00  
 1MFD/25000VWDC ..... 75.00  
 0.5MFD/15000VWDC TLA. 2 for 1.00  
 1MFD/500VWDC/10 for \$1; 0.1/2000V. 2 for 1.00  
 0.1mfd/3000VWDC/\$1.25; 0.3/7500V ..... 1.98  
 .0016/15000VWDC \$4.95; .6MFD/400VWDC ..... 3.00  
 STROBO FLASHES 4 VOLT GE Panel .05MFD/300V/50 for \$1; 2x.05/300V/30 for \$1; 32 MFD/660VAC/2000VWDC ..... 8.95  
 3X.05mfd/300V/20 for \$1; 1.22mfd/600V/2 for MICA CONDENSERS RATED WVDC 25MIMFD/10000V wkg NEW ..... 3 for 4.00  
 .00015mfd/5000V/\$3.49; .0003mfd/10000V ..... 1.95  
 .01mfd/600V/7 for \$1; .01mfd/1200V/3 for ..... 1.00  
 .03mfd/600V/3 for \$1; .03mfd/1200V/2 for ..... 1.50  
 0.5mfd/500V mica \$3.95; 0.015mfd/2500V ..... .95  
 TUBES 808, 446/2C40 ..... TWO for 5.99  
 954/50c—Five for \$2; 3BP1 & socket ..... 2.90  
 955, 56, 57, 58A, 59 & socket ..... Each .80  
 6AK5/90c; Five for \$4.25; 6AC7/1852 ..... Each .80  
 WRITE FOR TUBE LIST "TABOGRAM"

Dynamotor inpt28V/1amp, outpt250V/60ma, cont duty, wgt 2 lbs; operates on 12V fields in parallel, also 110VDCmotor (ARC5) ..... \$ 1.85  
 Dynamotor DM-4, inpt120V24V, outpt225V/110ma & 440V/200ma, cont duty Rugged dsqn Gov't Cost \$79. Special ..... 6.75  
 Dynamotor DA3A, inpt28VDC, outpt300VDC/260ma, 150V/10ma; 14.5V/5amp cont duty, for Radio set SCRS32, Special ..... 3.85  
 Dynamotor PE-91A, BENDIX MG-1A, DC inpt 24-28V, outpt300V/260ma, 150V/10ma, 14.5V/5A, inpt outpt filters, Voltage regulator & Starting relays cased. Special ..... 9.95

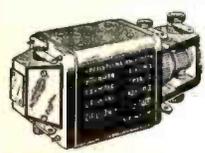


**DYNAMOTOR NEW**  
 HIEFF P MAGNET  
 ALNICO I2/24V inpt TAB  
 TESTED GTD 6V inpt/3Amp, output 240V/100ma or 125ma int duty Rated 500V/50ma at 123.49  
 Dynamotor 12 or 24V inpt, 275V/110V ma & 12V/3A ..... \$1.95

**INPT FILTERS** ..... .49

Generator 430VDC/180ma, cont duty ..... \$ 8.95  
 Oscilloscope 3" Tube & pwr-supply kit ..... 16.95  
 TR Vibrapack & Batteries new ..... 9.95  
 TBV's used fair condition ..... 2.95  
 I-222 Crystal calibrat Sig Generator, 115V/60cy Freq Mtr, Monitor 6to1.5643to7 times, useable on harmonics to 230MC's, precision unit, rugged dsqn complete ..... 39.95  
 Navy RBC Receiver & 4 to 27mc's 16 tubes best HAM rcvr all features used L.N. .... 75.00  
 CWRCRVR New Complete & data ..... 14.50  
 CW & F3 Coils 5-1-10 to 6.95  
 Power Supply RA4 110-240V/60cy Input for BC191, Hi current & volts ..... 49.95  
 IT&T Sel Rect 6B8AV1, FW83V/2.4Amp ..... 6.95

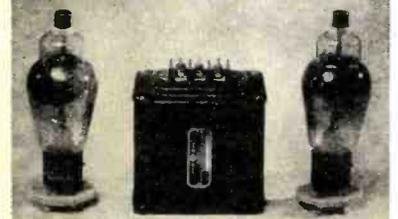**866A'S COMBINATION TRANSFORMER & SOCKETS**



CONSISTS OF TWO JAN NEW 866A TUBES, TRANSFORMER GARDNER ELCC CASED 2.5V 10 AMP, 115V/60cyinpt, H.V. instd 9000V wkg similar to illustrated units. Tested 16000 VAC Test; Same mtg as KENYON T389—SOCKETS CERAMIC JOHNSON 224. **"TAB" SPECIAL** ..... \$5.95  
 TRANSFORMER ONLY for Two 866A's ..... \$ 3.95  
 872A'S COMB. TRANSFORMER, sockets ..... 12.00  
 872A TRANSFORMER 115 60cy ..... 6.95

W.E. Telephone jacks Type 223 four for ..... \$ 1.00  
 RM-13G Remote Control Telephone Amplifier ..... 14.95  
 RM-53 Telephone remote control ..... 2.95  
 BC605D Interphone Amplifier ..... 7.95

FOR S.C. TECH MANUAL write to TAB MICROSWITCHES 2 for 39c ..... TEN for \$1.49  
 MICROSWITCH lead SPDT 15A/125V ..... TWO for 1.08  
 MICROSWITCH Plunger safety SW. TWO for 1.00  
 EDISON TIME delay Relay 115V/100 amp ea. 1.49

TRANSF cased pri 50-800cv/80-115V sec 1000VCT & 300V/110ma; 6.3V/5V/3A. 3X 6.3V/165A, 6.3V/125A & 2H cased chokes 10Hy/100ma & 2 oil condns 3mrd/330VAC/1000 WV & R60/1641 tube ..... \$ 9.95  
 Transf. 9800V/15ma, Pri 115V/60 & 400 cy 9.95  
 Transf. 15000V/35ma, Pri 115V/60cy ..... 15.95  
 Transf. 2500V/15ma, Pri 115V/60cy csd ..... 5.00  
 Transf. plate to line 98c; Line to V.C. .... .98  
 Transf. multi-tap line to line ±1DB csd ..... 1.95

WE Dynamic microphone & 20 ft. cord ..... \$7.95  
 Switch AH&H 60amp/6000V; 250amp/125V(\$28) 1.00  
 Switch door interlock GET460330-64 (\$2.50) ..... .69  
 METAL BOX NAVY 5 1/2" H10L9 3/4" hasp & hdles 1.45  
 AUDIO BAND pass filter 60, 90 & 150 cycles totally encased shld each \$1.95 ..... THREE for 4.50  
 Tuning slugs with screw asstd ..... 50 for 1.00

STORAGE Battery 2 volt \$1.98. TWO for \$ 2.98  
 IF STRIP 30mc's/8-BAK5 & 1-6AL5 ..... 9.49  
 HANDIE TALKIE BC611 Chassis, coils ..... 7.95  
 Revr BC455A & tubes ARC5 4V.50, Dyn. .... 6.39  
 GAS GENERATOR SET output 275VDC/400 Watts & 115VAC/1400 Watts ..... 100.00  
 BC1073 51G wavemtr ..... 24.95  
 SCRS22 RCVR & XMITTER 100-158mc's 18.00  
 Navy sound powered telephones, used ..... 9.95

CRYSTAL DIODE TEST SET 268U, NEW ..... \$16.95  
 METER Rectifier Dual bridge BRADLEY ..... .98  
 CRYSTAL DIODE IN21 @ 45c ..... THREE FOR 1.00  
 CRYSTAL DIODE LN26 @ \$1 ..... TWO for 1.50  
 CRYSTAL DIODE IN34 @ \$1.39 ..... TWO for 2.40

WRITE FOR THE MONTHLY "TABOGRAM" FOR TS&M S.C. TECH-MANUALS C "TAB"

SUPREME 540MULTIMTR 5000ohmsperv/24range Volts AC&DC to 1500; ohms 2 meg, DR/50, used, LN GTD ..... \$15.95  
 Test mtr like WESTON 697VOM reads 0-7.5/15/150/750VAC&DC/1000ohms perV, 7.5&75mohms/1000ohms. New in Oak case with test leads ..... 18.95  
 Leather case Velvet lined for 697VOM ..... 2.95  
 SUPREME227 like WESTON 227, 150V scale, 3-30/300 600VDC, ohms1000/10000/100m/1meg LN ..... 13.95  
 Tester reads 15-150/300VAC&DC ohms 5000/5meg; 0-60/120/300/600ma DC LN ..... 10.95

TELEPHONE inverter converter ringing machine KS-5492-0111 inpt 43-47VDC output 75 90V/20cy; new WESTON 227, 150V scale, 3-30/300 600VDC, ohms1000/10000/100m/1meg LN ..... 13.95  
 SCRS22 RCVR & XMITTER 100-158mc's 18.00  
 TELERING BD-90 TELCOR model H inpt 110V/60cy, outpt 90V/120cy ..... 9.95  
 WRITE TAB TELEPHONE PARTS & EQUIPMENT

VOLTAGE REGULATOR RAYTHEON complete inpt aditaps 95-130V/60cy; outpt 115V/55amp case 1/2 of 1% regulation \$10.95  
 HV Duty Voltage Regulator Relay, 2-30/30 400VDC, ohms1000/10000/100m/1meg LN ..... 13.95  
 Output 220V/500watts, 1/2 of 1% regulation, Rugged dsqn Totalized wgt 70 lbs new ..... 39.95  
 TRANSF 155 or 230V/50-60cy/1400watts 19.95  
 Antenna SCM50/18.5ft & ins base & grd ..... 4.95  
 Transf 110c&220 to 220-440V/190watts ..... 4.50  
 Transf. Modulation PP parallel 6L6's or 807's to RF 807's/200ohm load-cased ..... 2.95

SONAR QBF exchoring equipment ..... \$1000.00  
 SC-1 RADAR GE NEW IN TEN CASES ..... 2000.00

Autosyn synchro differentials 115V/60cy ..... \$ 6.95  
 Autosyn Type 5/50V, 115V/60cy ..... 2 for 8.95  
 Autosyn AV16.5/24-28V/60c/4cy PR ..... 3.95  
 AUTOSYNS XXI REPEATER 115V/60cy, pair ..... 8.95  
 SYN REPEATER TYPEIII/115V/60cy, pair ..... 18.00

GR. VARIAC 200B/Variable 0-135V60c/1A.59.95  
 Transf 115V/60c pri; 1200VCT/300ma ..... 5.98  
 Transf. 115V/60c pri; 700VCT/120ma/6.3V/2.4A, 5V2/2Amp, \$2.69 ..... 2 for 5.00  
 TR 115V/60c pri; 500VCT/60ma, 6.3V/4A TR 11 ..... 1.49  
 TR 115V/60c pri; 350VCT/150ma/8.3V/5A/5V/2A CASED UTC ..... 7.50  
 TR 115V/60c pri; 1100VCT/212ma csd ..... 6.50  
 TR 115V/60c pri; 640VCT/154W/250ma csd ..... 4.95  
 BLOWER 100CFM & Trans. 115V/60cy's ..... 5.95  
 BLOWER 125CFM/115V/60c enclosed ..... 8.95

Choke 20Hy/100ma/98c; 50Hy/150ma csd ..... \$1.49  
 Choke swinging 7.5/20Hy/150ma csd ..... 2.95  
 Choke GE 12Hy/300ma cased HVins ..... 2.95  
 Choke 15Hy/400ma/or20Hy/300ma/15KV ..... 7.95  
 Choke 12Hy/300ma/85ohms csd HVins ..... 9.95  
 Choke 3Hy 40ms/3 for \$4; 0.5Hy/100ma/4 for 3Hy/400ma/15ohms \$2.75; 8Hy/200ma/2 for 2.89

Transf. Thordarson 115V/50-60cy; 1100 VCT/150ma, 6.3V/3A, 3V/3A HVinstid.S 3.95  
 Extension cord HVduty 16ft & M&F plug, 1.00  
 Antenna bowl ht 24" D & rd. 115V/60cy ..... 9.98  
 Variable Condns 18-157mmf/3000V ..... .98  
 Antenna SCM50/18ft & ins base & grd ..... 3.95  
 Antenna SCM50/18.5ft & ins base & grd ..... 4.95  
 Antenna sections SCM50/391/4" ..... 12 for 1.00  
 Antenna parabolic, Drive & selsyns MTR. .... 16.95

\$2 Min. order FOB N.Y.C. Add Postage all orders and 25% deposit. Worth 2-7230. Send for catalog 99. Specialists in International Export, College & Industrial trade. Money-back "TAB" Guarantee.

**PRECISION RESISTORS**  
 IRC, SHALLCROSS  
 MEPCO, INST. RES. CO.,  
 OHMITE, WE, for METERS  
 BRIDGES, AMPLIFIERS



ACCURACIES \*1/2%, \*\*5%, 10% (REST 1%)

1	2	3	4	5
20	25	30	75	80
100	101	150	300	260
400	500	1250	1500	2000
2142*	4000	4300	4800	5000
1950*	8000	9710	10000	12000
15000*	17000	20000*	30000*	50000
80000	84000	90000	147000	166750

Above sizes asstd. .... TEN for \$2.50  
 2000\* 50000 ..... 100000\* ..... 150000  
 150000 186750 201000 229000 250000

Above sizes asstd ..... 39c ea ..... TEN for \$3.00  
 330000 402000 500000 800000 950000

Above sizes asstd ..... 60c @ ..... TEN for \$5.00  
 ONE Megohm WW 1% accy ..... THREE for \$2.00  
 2meg, 4.5meg, 5meg, 10meg ..... SIX for \$3.00  
 Sprague Megomax 100r12megohm/10KV ..... \$1.49  
 WESTON 1/2of1% precision 2.5meg resistor ..... 4.95  
 IRC Navy precision 1meg 1/2 of 1% MF ..... 1.69  
 IRC Navy precision 2meg 1/2 of 1% ..... 4.95  
 WSTGHSE "DB" MTR332 SQklesd10plusDB 4.95  
 WSTGHSE one Mamtr 31/2" SQklesd ..... 4.50  
 McClintock 3 1/2" BC 0-1ma mtr ..... 3.95  
 De Jur 2 1/2" B/C 0-1ma mtr std scale ..... 2.95  
 GE RF mtr 2 1/2" B/C either 1 or 5 amp ..... 3.95  
 WESTON 476AC 15 voltmtr 3 1/2" SQklesd ..... 4.95  
 WESTON 506 mtr-10plus6DB2 1/2" B/C ..... 4.50  
 GE DW54 mtr-10 plus 6DB 2 1/2" B/C Case ..... 3.95  
 GE Galvo 3 1/2" B/Csd 2.5&2.5ma 0 center ..... 3.95  
 GE DW41mtr2000V/1000ohmsV&resists ..... 5.95

GE AO22 mtr 50VAC & LAB STD 3 1/2" B/C ..... \$3.00  
 GE AO22 mtr 0-150VAC 3 1/2" B/C ..... 4.95  
 Meter 0-150VAC, two inch case ..... 3.50  
 Voltmeter 0-200VDC/1000ohmsperv3 1/2" csd ..... 4.25  
 WESTON 0-250ma, 2 1/2" B/Csd ..... 3.25  
 WSTGHSE AN 0-100&100-0-100micromtr ..... 3.95  
 WSTGHSE less0adjo-100-100-100micromtr ..... 1.95  
 GE inst Voltage Control relay PJV/115V/60cy self reset, Calib 70/35/110/160V ..... 5.95  
 GE thermostat adj 250V/25amp; 70to170°F ..... 3.95  
 CH luminous tip switch SPDT ..... 4 for 1.00

**Autosyns**  
 NEW Type 5  
 115V/60cy  
 Bendix  
 Hobart, etc.  
 per pair \$18



KIT RESISTORS BT 1/2" & 1W50to2megs. 100 for \$2.50  
 KIT CONTROLS 50-2megs potsABJ ..... 10 for 2.50  
 KIT SILVER & MICA CNDNSRS ..... 50 for 2.00  
 KIT LUGS RADIO TYPE ASSTD ..... 100 for 1.00  
 KIT FUSES ASSTD LITTLE FUSE ..... 300 for 1.95  
 KIT GROMMETS RADIO TYPE, etc. .... 100 for 1.00  
 KIT SOCKETS OCTAL/OCTAL, etc. .... 50 for 2.95  
 KEY CLICK FILTER RFC, RES&CDRSRS ..... 2.95  
 CINCH miniature dual xtal sockets ..... 8 for 1.00  
 CRYSTAL socket 242 holder 3pins ..... 3 for 1.00  
 Socket for axial holders 1/2 & 4" sp ..... 2 for .25

**COLLINS**  
 ART/13  
 SPEECH  
 AMPLIFIER  
 COMPLETE  
 INPT



DYNAMIC OR CARBON MICROPHONE OR LINE INPT: Output PP class "B" GRID'S Noise Level down-55DB. INCLUDES INPT TRANSF, 1st audio to PPGrids MODULATOR TUBES, 6V6 sidetone AdJ Audio osc AMP & Hdphone monitoring jack. WT 5LBS. DIM 7-3/4" 3 1/2" W"H, minus tubes & power supply. **"TAB" SPECIAL** ..... \$4.95  
 WITH TWO 6V6 & 6SJ7 ..... 7.49

WE 125 to 250 Watt multi-cellular, nine Driver trumpet complete, NEW ..... \$125.00  
 REFLEX REENTRANT TRUMPET projector 35 to 55 watts with W.E. head complete ..... 29.95  
 W.E. Driver PMheads 25to55 watt waterproof conservative rating \$12.95 ..... TWO for \$21.95  
 W.E. Diaphragm ES671349-3 for PM heads ..... 3.95  
 Speakers PM 4" Alnico 5/\$1.30; 5" size ..... 1.45  
 Universal tube & Voice Coil transformer ..... .98

"TAB" • Dept. 10RN, Six Church Street, New York 6, N.Y., U.S.A. • "TAB" THAT'S A BUY • CORNER CHURCH & LIBERTY STS., ROOM 200 • THAT'S A BUY

*Kiver has  
done it again!*

## "F-M SIMPLIFIED"

by Milton S. Kiver

Registered Professional Engineer

An Amazingly Simple Approach  
that Lifts Frequency Modulation  
Radio out of the Fog!

With the same clarity of explanation and interest-provoking style that won high places for his other works—"U.H.F. Simplified" and "Television Simplified"—Mr. Kiver takes F-M apart, puts it back together again, and makes it work in *your mind*. He throws light in the dark corners of doubt concerning principle, apparatus and characteristics. You get complete procedures for aligning receivers—full accounts of tuners—and all the other information needed for installation, operation and servicing. You'll welcome the wealth of vital information—the absence of mathematical detail.

### HUNDREDS OF ILLUSTRATIONS

Simplified Diagrams,  
Charts and Tables of Data!

Graphic examples of every step and phase that lead to complete mastery of this increasingly important subject are included. Nothing is omitted that would help the reader apply his knowledge in practical work without further study.

Readers treasure this book, because it is quick to grasp—easy to understand and remember. There are no loose ends that leave you dangling—it is wrapped up in one 352-page package—concise, compact, complete, and crystal clear!

No Radio Library is Up-To-Date  
Without

## "F-M SIMPLIFIED"

For Free Examination of this Great  
New Book Mail the Coupon Below

---MAIL THIS COUPON---

D. VAN NOSTRAND COMPANY, Inc.  
250 Fourth Avenue, N. Y. 3, N. Y.

Please send me a copy of "F-M SIMPLIFIED." After 10 days I will either return the book or send you \$6.00 plus few cents postage. (If you send \$6.00 with this coupon, we will pay the postage, same return privilege guaranteed.)

NAME.....

ADDRESS.....

CITY.....ZONE.....STATE.....

RN—OCT. 1947

oughly familiar with the proper settings of the various controls for highest output, good quality, and high modulation percentage.

8. After all adjustments are made, remove dummy antenna and substitute regular transmitting antenna. Adjust antenna coupler, if any, for maximum loading consistent with good quality and high modulation percentage. If no antenna coupler is employed, adjust final amplifier loading by variation of the output link coupling.

—30—

### Wireless Pre-Amp

(Continued from page 65)

quency end of the broadcast band is more "open" than the high so this end was used. With the values given a tuning range from approximately 580 kc. to 730 kc. is provided. If it is desirable to have this range nearer the high frequency end of the band use a smaller size mica condenser for  $C_6$ , e.g., 100  $\mu\text{fd}$ .

### TELEVISION'S NEW EYE

**T**ELEVISION has brought forth many developments in a multitude of fields until, today, pictures receivable in the home are rapidly increasing in clarity and quality.

One of the latest additions to the industry's growth was demonstrated for the first time over the air July 21, and met with immediate enthusiastic reception. This optical development, known as the Zoomar Lens, is designed to augment any existing camera facilities without severe mechanical or electrical adaptation problems. Invented by the physicist, Dr. Frank G. Back, already well-known from his work on the stomach camera and optical equipment for wartime projectiles, its primary purpose was for 16 mm. camera work. Later adapted for 35 mm. and television, it consists of a single unit, automatic focusing lens system which will cover the entire field previously scanned by a tri-turret assembly of 4-inch to 13½-inch lenses.

Installation of the unit on existing facilities accomplishes many purposes, a particularly important factor being the release of equipment previously tied up in multi-camera coverages of studio and remote presentations. It is designed in two models, one for outdoor or indoor sports events and the other for indoor stage type studio programming.

In its initial demonstration over the air on WCBS-TV, the double header ball game between the Brooklyn Dodgers and the Cincinnati Reds was given

a coverage and a continuity never before screened for TV fans. The most dynamic illustration is in the case of a long fly ball to deep field. Initial focus is made on the pitcher-batter combination for the windup and the toss. When the ball is hit, the scanned width is enlarged as the ball soars toward the outfield, and is in sight on the screen at all times. As it nears the fielder about to make the catch, the field of vision is narrowed down and moved in on this player so at the time of the catch the fielder appears as large on the screen as did the batter at the time of the hit. It gives the viewer the impression of riding a camera boom to far outfield to closer observe the action taking place.

A study of the above description is self introductory to studio uses. For a small stage production, such as a play, the camera unit may be set up 25 or 30 feet from the action on a fixed mount and the entire proceedings scanned from this point. Full stage scenes, shifting to sectional action and close ups of individual actors, can be accomplished with smooth precision and on only one camera unit. Automatic elimination of moving dollies, heavy cabling, and hoarsely whispered instructions readily produces a large and much desired drop in stage noises. A new technique in following the action is easily developed, and the over-all gain in quiet operation and fluid continuity of view will pay off in large dividends.

—30—

New Zoomar lens attached to an NBC television camera. These new single-unit, automatic focusing systems replace multi-camera systems usually required for complete coverage.



# SAVE TIME!

# SAVE MONEY!

## Free!


A book full of schematic diagrams and conversion information on war surplus equipment such as BC-375-E, SCR-274-N, SCR-522, BC-221, APN-4, APN-1 and many others.

R & M Engineering Department has worked out the latest and many new ways to eliminate the worry and headaches of converting surplus equipment. This book contains wiring diagrams of each equipment and conversion information on how to adapt with wiring changes. One of these books free with each equipment you purchase. We have selected the most desirable and choice radio gear and present them to you with a **SATISFACTION GUARANTEE!** You save money when you deal with us.



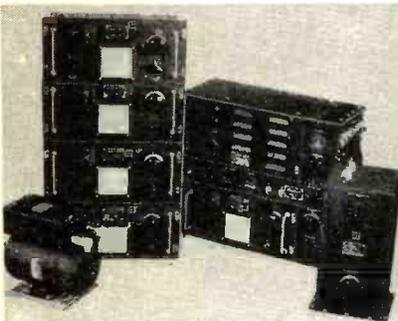**SCR-274-N COMMAND SET COMPANION OR STANDBY**

Here are a couple of things you can do with equipment included in the SCR-274-N Command Set. The transmitter VFO driver stage gives you the BC-375-E higher RF output—as high as 150 watts. Make swell standby receivers with the BC-348 on round table "rag chews." Includes all this equipment: 3 Receivers—190-550 kc, 3-6 and 6-9.1 mc; two transmitters, 4-5.3 mc, 5.3-7 mc; four dynamotors—28 volts DC input; 1 modulator with carbon mike input; two tuning control boxes; one antenna coupling box with r-f ammeter; antenna relay and 5000 volt 50 mmfd. WE vacuum condenser (antenna relay can be used with most rigs); and a complete set of tubes for each unit—29 POPULAR TUBES in all. Mechanical cables with tuning receivers supplied for \$1.00 extra. Complete diagrams and instructions on other conversions and uses furnished with set. only **\$19.50**



**ARMY AIR FORCE BC-375-E TRANSMITTER**

It's been written about and talked about—just the thing for beginner or old-timer. Has five tubes, 5 tuning units. Transmitter designed to operate from 200 kc to 12 mc (less BC band). Equipped with antenna tuning unit—BC-306-A—variometer and tap switch. Dynamotor (PE-73-C) complete with relay, fuses and filter. Diagram and instructions for its use supplied with each set. Weight approximately 275 lbs. only **\$29.50**

### →SPECIAL COMBINATION← THIS MONTH ONLY

One SCR-274-N Command Set and One BC-375 Transmitter as shown in the illustrations above

**BOTH FOR ONLY \$39.50**

## Famous "PUTT-PUTT"

(HRU-28) DC POWER SUPPLY  
24-28 VOLT at 70 AMPS—2000 WATTS

This unit is just fine for your Field Day, to operate your BC 375, ART/13 Collins trans., BC 348 Rec., and all your gear.


This gasoline engine generator power supply is a one-cylinder, two-cycle gasoline engine, approximately 4 horsepower. Automatic starting when 24-volt battery is attached. Voltage regulator adjustment can adjust from 12 volts to 35 volts, DC. Ideal power supply to operate all war surplus radio equipment (24 volt DC). These units are slightly used but in excellent condition and guaranteed operative. Each power supply is given an operating test before being shipped. They are substantially crated for domestic shipment. Complete as shown; ready to operate.

only **\$69<sup>50</sup>**

- AMATEUR RADIO STATIONS
- BOATS, LIGHT SYSTEMS
- FARM LIGHTING (AUXILIARY)
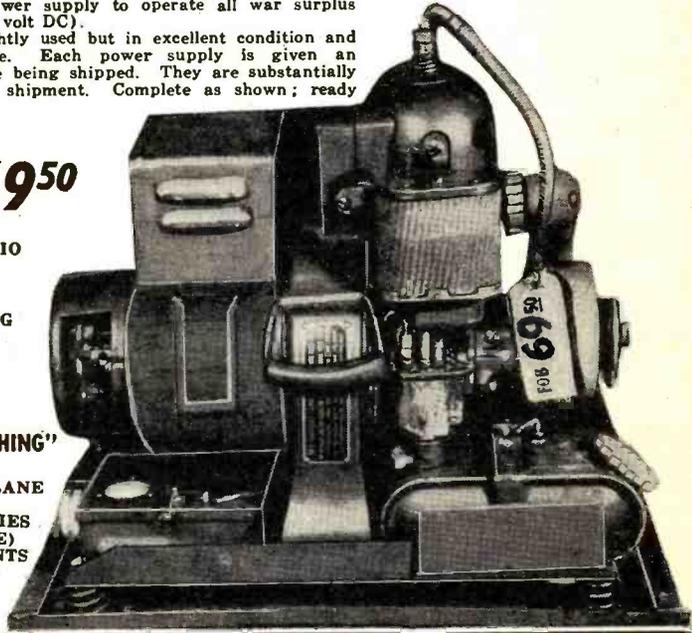
### "OPERATES EVERYTHING"

- STARTING AIRPLANE ENGINES
- CHARGES BATTERIES (FAST CHARGE)
- FARM IMPLEMENTS
- POWER MOWERS
- WELDERS




The HRU-28 gasoline engine generator is the same as the commercial designation C-10.

Over-all dimensions:  
Height 21½ inches.  
Width 17½ inches.  
Length 24¾ inches.  
Weight 115 pounds.
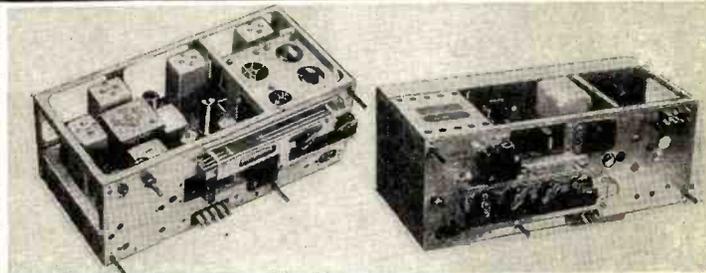
### MOUNTS

Shock mounts and rack mounts of all types available for BC-348, SCR-274-N, BC-375 and SCR-522. Available at a very low cost. Write for listing of mounts today!



**BC-624 VHF RECEIVER**  
2 METER

10 tubes, 4 crystal channels, tunes from 100 to 156 mc. Excellent receiver for the VHF experimenter. Does a fine job on 144 mc. Makes basic unit for conversion of FM or television. only **\$8.00**

**2 or 6 METER RADIO TRANSMITTER**  
BC-625-A

The famous SCR-522 transmitter only, covers from 100-156 mc., crystal control, four crystal channels, seven tubes, two of which are 832's. 8 watts power output, 100% modulation, built-in modulator. Steady, reliable, beautifully made of finest components. Can be made to furnish 50 mc and 144 mc. Can be used as drive for any frequency above. only **\$12.50**

## IMMEDIATE DELIVERY!

### SPECIAL ON ANTENNAS

A 40-foot, heavy duty, light tubular steel, five section, telescopic antenna mast. Collar of each section has 3 guy wire points and uses cotter pins or bolts to secure sections. An ideal mast for mounting UHF directional arrays, television mast or all purpose antenna.

**\$19.50 each: two for \$35.00**

October, 1947


We save you time and money by shipping direct to you from our nearest warehouse . . . located in the East, Mid-West and West Coast.

SAVE C.O.D. CHARGES BY REMITTING IN FULL DIRECT . . . TO R & M RADIO CO. . . . OR SEND 25% DEPOSIT ON ALL ORDERS

# R & M RADIO COMPANY

1426 N. QUINCY STREET • ARLINGTON, VIRGINIA

# FOR HIGH FIDELITY AT LOW COST! -the UNIVERSITY TWEETER

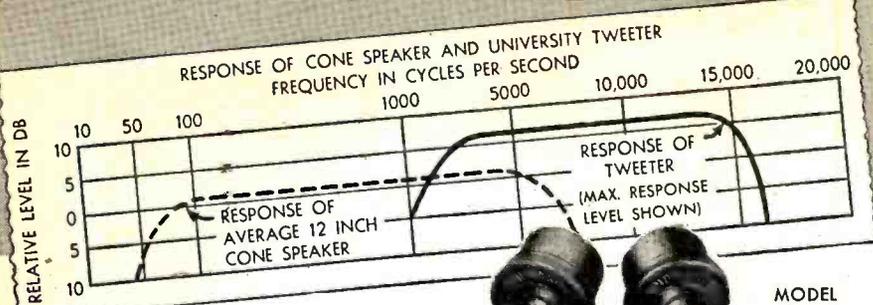

MODEL 4402

**MODEL 4404—**  
Dual Tweeter in Walnut Cabinet with High Pass Filter and Volume Control.  
List Price \$60.00

**MODEL 4402—**  
Dual Tweeter only.  
List Price \$40.00

**MODEL 4405—**  
High Pass Filter and Volume Control  
List Price \$10.00

The reproduction of music and voice with breath-taking realism, is now possible with the new UNIVERSITY Dual Tweeter. Used in conjunction with any standard 12" cone speaker in FM and AM radio equipment and wide range phonograph amplifiers, it adds the brilliant "highs" so frequently carried through all stages of amplification, only to be lost in the bottleneck of a single unit reproducer. Frequency response is 2,000 to 15,000 cycles. The die-cast dual horn design permits 100° horizontal distribution and 50° vertical distribution. A high pass filter with auxiliary high frequency volume control, permits easy connection by merely attaching two wires to the existing speaker. Mounting space only 2 3/4" high x 9 1/4" wide. Power handling capacity 16 watts, impedance 16 ohms. For complete information write today to UNIVERSITY LOUDSPEAKERS, INC., 80 South Kensico Avenue, White Plains, New York.

## University Loudspeakers



### Ne-O-Lite Tester Wire Stripper Dial Belt Kit Alignment Kit

#### G-C SERVICEMEN'S DIAL BELT KITS

Fine woven replacements for all sets. Easy to install. Supplied in kits of various quantities with steel box.

No. G-25—Kit of 25 belts.  
List \$6.70

#### G-C WIRE STRIPPER

Strips insulation from 750 to 1000 wires per hour, sizes No. 8 to No. 30. Ideal for radio men, mechanics, etc.

No. 733—12 to 20 wire.  
List \$6.00

Other types available.

#### G-C No. 5024 PROFESSIONAL ALIGNMENT KIT

Complete kit in leatherette case; contains 30 different tools, services any set. Handy to carry in roll type case. List \$19.95

#### G-C NE-O-LITE TESTER

Handy, inexpensive Ne-O-Lite Tester that every serviceman, experimenter, etc., should have. Can be used on 60 V.A.C. to 500 V.A.C. or D.C.

No. 5100—Single tester on card.  
Only 50c each

No. 5100-D—Display of 20 testers.  
List \$10.00

SOLD BY ALL JOBBERS  
Write for our complete catalog!  
RADIO DIVISION DEPT. H

**GENERAL CEMENT Mfg. Co., Rockford, Ill., U.S.A.**  
Manufacturers of over 3,000 products  
Sales offices in principal cities

### YOU CAN'T MISS!



with these  
*Federated*  
Values



#### 10 MFD—1000 DC. W.V. Oil-Filled Condenser

In rectangular can. Porcelain insulators, mounting flanges. Made by well-known manufacturer. UNUSUAL VALUE;

Your Cost, Each..... \$1.29

10 Mfd 1500 Volt similar to above, Each..... \$2.49

#### REPLACEMENT CRYSTAL CARTRIDGE

Webster model E-9. Will replace Astatic type L-40. L-26. L-70 cartridges. Very special value! Each \$1.39

#### CRYSTAL MIKE SPECIAL!

Here's a HOT value for YOU! High quality crystal mike, for ham work, home recordings, public address, etc. Can be used either as hand mike or desk mike. Hand mike slips out of base with one twist. Handsome brown lacquer finish. Equipped with 7-ft. R.C. cable.

All Yours for only..... \$3.95

#### ACORN TUBES

Types 954, 955 TEN for \$2.90  
Lo-Loss Sockets for Acorn Tubes. Ten for \$2.90  
Mail Orders: 25% Deposit, Balance C.O.D.  
Minimum Order \$5.00.

**Federated Purchaser**  
INCORPORATED  
distributors of RADIO-ELECTRONIC  
and SOUND EQUIPMENT  
8080 PARK PLACE, N. Y. 7  
Phone: WH 4-2080

There are numerous types of electronic musical instrument pickups on the market, some of them using the magnetic principle and others the vibration type. Needless to say, price and the musician's preference will be the determining factors in any choice made regarding these units. In any radio catalog or music store types such as the *Turner, Brush, Amperite, Lectrolab* and others may be found. Any of these are suitable if they are the high impedance type. Similarly, any electric guitar may be plugged in to the instrument jack and any phono player may be used in its respective jack.

For the experimenter and radio builder this should prove to be a worthwhile project especially if one has musically minded friends who have or are interested in the electronic type of instrument. Compared with the cost of amplifiers ordinarily used for this type of reproduction, the cost of this unit is very nominal and it offers advantages to the professional or semi-professional musician as a supplement to his regular amplifier or for emergency use.

-50-

### International Short-Wave

(Continued from page 68)

well as for the length of time he has aired his voice—dating back to 1919—well, that's something of a world's record, it seems to us.

Before the Japanese attack on Pearl Harbor, George Williams knew of the grave situation existing and on October 1, 1941, placed his radio facilities at the disposal of U.S. authorities in the Canal Zone. He was one of the first to start a radio program for the promotion of the War Bond Drive. On September 9, 1942, Arnold Bruckner, chairman, War Savings Bond Committee, Balboa Heights, Canal Zone, wrote him: "At the conclusion of the series of War Bonds programs which have been broadcast weekly since April 26, 1942, over the station, 'The Voice of Democracy,' I want to again thank you for your generous cooperation in making the broadcasting facilities available for this purpose. The ever-mounting sales of War Savings Bonds and Stamps in the Canal Zone are evidence of the fact that these broadcasts have materially aided in stimulating interest in the program, and I earnestly hope that you will be able to make these facilities available to us again in the event the programs are resumed, or for any special program that might be arranged."

Mr. Williams is an ardent supporter of democracy and the United States' "Good Neighbor" policy. He has often been heard to say: "Good will can do more to bind the Americas together—and thus keep war from our shores—than the doubling of the United States Navy, the building up of the Army, and even the two large oceans which divide us from the Old World and its continuous wars."

His campaign on behalf of democracy has not ended in Panama. He has written articles for every democratic paper that would print them in all parts of the Americas. As early as December, 1940, over a year before Pearl Harbor, he wrote in "Central America Express" of Costa Rica: "Are we callous to the sufferings of the world? Are we immune to the fate of democracy everywhere? Do we think that because, in the past, we have escaped, we shall forever be safe? To maintain peace we must expel war from the world—and to do this, we must help in stopping those that believe as their slogan 'Rule or Ruin' and those who use brute force as their weapon."


The magazine, "Export Trade & Shipper," January 20, 1941, reported that "George Williams with his famous 'Radio Newspaper' in Panama, has been doing an excellent job with his broadcasts on behalf of the U.S.A. and good will between the Americas, that his name and program were mentioned on the floor of Congress the other day by the Hon. John M. Coffee, Congressman, and an expert on Latin American affairs." Congressman Coffee wrote Mr. Williams, "Words fail me in attempting adequately to express on behalf of all liberty-loving American citizens the gratitude we feel because of the good will you have created for us."

During the war, radio entertainment for the Armed Forces from HP5J/HP6J did not stop with remote control broadcasts, although these programs took Mr. Williams as far away from the studio as Rio Hato. Special line service was installed by the Army Signal Corps and extended as far as the Limits, then into the Panama Electric Light Company circuit direct to the studios. From the studios, Mr. Williams conducted such programs of the Office of War Information as "You Can't Do Business With Hitler" and "This Is Our Enemy," and the "Victory Spots." Troops in the area tagged Mr. Williams as the "Silver Dollar Bondman" as they looked forward to his program conducted from various USO clubs and Army posts, giving away silver dollars and Savings Bonds to witty servicemen. But this all came to an end with the inauguration of the Armed Forces Radio Network and the banning of commercial broadcasting, which was perhaps a woeful loss of silver dollars for the boys in the Services! Mr. Williams continued, however, to broadcast for the spiritual welfare of the troops with his program, "The Ave Maria Hour," and a rebroadcast of religious services under the direction of Joseph R. Koch, department chaplain, Quarry Heights, Canal Zone.

Mr. Williams describes his "Daily Newspaper of the Air" as designed "to give a news-hungry public what they want, when they want it—short, informative, pertinent facts about current events." He admits that he often scoops leading U.S. commenta-

October, 1947

## SHURE Proudly Presents

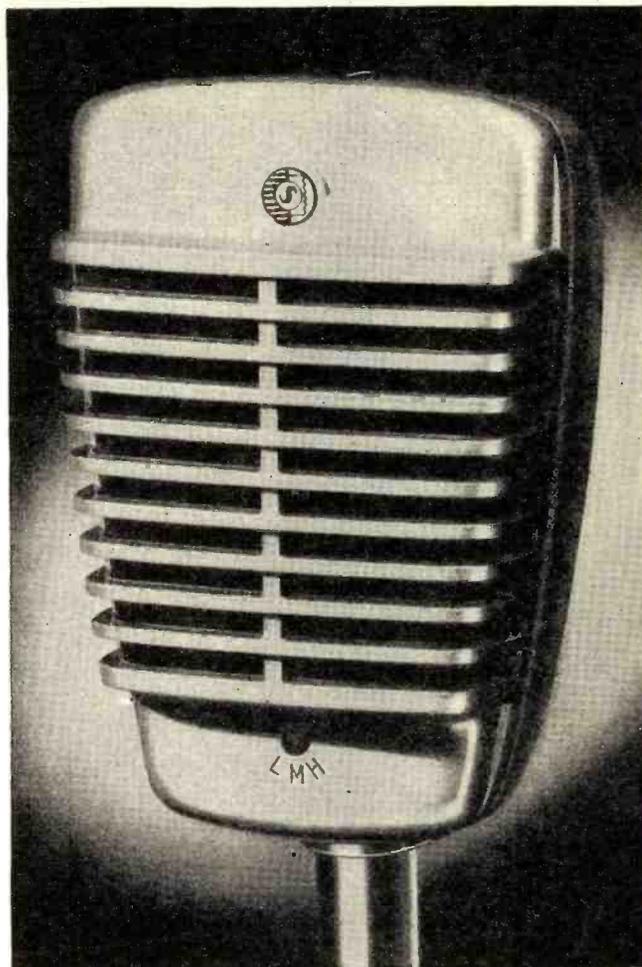

### SONODYNE

#### A MULTI-IMPEDANCE DYNAMIC MICROPHONE

Here is *the* microphone in its class—a high output dynamic that was designed to out-sell . . . out-perform . . . out-smart even higher-priced microphones. The Model 51 Sonodyne features a multi-impedance switch for low, medium, or high impedance—plus a high output of 52 db below 1 volt per dyne per sq. cm. It has a wide-range frequency response (up to 9000 c. p. s.) and semi-directional pickup.

SONODYNE—Model 51—List Price \$31.00—Code: RUSON

*Shure Patents Pending*

**SHURE BROTHERS, Inc.**

Microphones and Acoustic Devices

225 West Huron Street Chicago 10, Illinois

Cable Address: SHUREMICRO



# THOR ELECTRONICS BEST BUYS!

ORDER NOW! IMMEDIATE DELIVERY ON ALL ITEMS

## BROADCAST BAND CONVERTER

100 KC to 1550 KC. For owners of Army-Navy surplus receivers. Adapter supplied uses a 6SA7 tube mixer-oscillator. Beats BC signal against 3 Megs. Tune in on short wave. Tested with BC-312, 342 NC100-ASD, BC-348 and others. In ordering state model. New low price **\$12.95**



## 10 METER CONVERTER

27 to 30 Megacycles

Designed for Army surplus receivers such as the BC342, BC348, BC312, etc. Uses a single 6SA7 fixed oscillator at 16 Megs. Adjust plate output and grid input signal for maximum. Calibrate and tune the entire band on your receiver. The power for the converter comes from the receiver. Our special adapter secures the power from the receiver by a plug-in arrangement. When this is not possible instructions will indicate the correct tapping point. In ordering be sure to mention the model receiver. This is an assembled parts kit. Complete instructions and plans. **\$ 1.00**

Kit of parts and plans for complete operation **12.00**

Complete unit wired and tested **18.00**



## U. S. SIGNAL CORPS 2-WAY TALKING SYSTEM

A Western Electric Product

Use them for inter-office communication, house to garage, mother's room to baby's crib, on the farm, and many other places. Sensitive enough to pick up sounds 100 to 200 feet away from speaker-microphone. Has push-to-talk switch. Tube line up: 5Y3, 6SJ7, and 6K6. The small unit is a speaker-receiver and can be placed up to a mile from the master. Use as many

as 10 in parallel. Comes ready to operate. Just plug it into 110 v. AC line and connect two wires to speaker. Complete with master and one speaker-receiver and 100' wire **\$39.00**

Extra Speaker-Receiver. \$4.95



## HOT SPECIALS

- Kit of 50-1 and 2 Watt resistors, sizes 25, 150, 1000, 3000, etc. **\$1.00**
- 800 Ohm 15ma choke 40 henrys. **24c**
- RA-20 Power Supply—for Signal Corps Receiver BC-342. Replace battery pack on BC-312 to convert to 110v. AC operation. **\$15.95**
- 5 lbs. Radio Parts Junk, new. **\$1.00**
- 12 Volt Relay, 90 Ohm Coil. **39c**
- Fuse Holder, front panel mount. **19c**
- Gn 45 Generator less handles. 400 and 10 Volts output. **\$3.95**
- Dynamotor, 28 Volts to 250 Volts at 90 mls. **\$1.95**
- Aviator's Throat Mike, new. **79c**
- Transformer to match throat mike to grid of any amplifier. Use above combination as a home broadcast unit. **\$1.25**
- 20.7 Megacycle double iron core tuned 1F Transformers. Four to a complete set. Use them for FM or Video. Can easily be trimmed down to 10 Mega. with a single ceramic condenser. Set of four matched coils. **\$3.98**
- HS 30 Headset, new. **\$1.69**
- HS 30 Headband, new. **19c**
- Kit of 10 1R Coils. **\$1.00**
- BC-312, 342 1F. Crystal Transformer, resonant at 470 KC. Replace that 1F. with this unit and separate those crowded ham-bands. **\$7.95**
- Pwr.-Trans. 350-0-350, 60 Mills, 6.3v @ 3a 5v @ 2a **\$2.15**
- 1619 Tube. Characteristics same as 6L6 only with a 2½ Volt filament. Use as a replacement for a 47 or a 2A5 **49c**
- 4" PM Speaker, new. **\$1.49**

ALL MERCHANDISE GUARANTEED AS REPRESENTED  
Cash—Check—or Money Order  
Write Dept. N-0

# THOR ELECTRONICS

5051 N. Clark St., Chicago 40, Ill.

tors. He numbers among his friends many of the leading commentators, including Lowell Thomas, who autographed a photo for George with this quip: "May you live forever!"

(Incidentally, we understand that Mr. Williams uses four radio receivers—two are *Halicrafters*—tuned to c.w. whence he gets much of the news he broadcasts on his "newspaper.")

HP5J operates in the 31-meter band on 9.605, and HP6J operates on 1360 kcs. (220 meters) in the broadcast band. Daily schedule of programs directed by Mr. Williams is 1230-1300 and 1800-1830, except that on Saturday the last transmission runs 1800-1900, the final half-hour being the religious program, "Haven of Rest." The "Daily Newspaper of the Air" is broadcast at 1230 and 1800. Various programs of HP5J/HP6J are sponsored by firms in Panama, in the United States, and in Canada. Daily schedule of the station is 0700-2235.

## Other Panama Stations


Other Republic of Panama stations are listed as HP5A, 11.695, Panama City, "Cadena Panama de Radiodifusion," 500 watts, 0700-2300; HP5G, 11.780, Panama City, "Radio Panamericana," 800 watts, 0630-2230; HOB, 6.175, Panama City, "Radio Panamericana," 0630-2230; HOLA, 9.505, Colon, "Radio Atlantico," 0800-1300, 1600-2200; HP5K, 6.005, Colon, "La Voz de la Victor," 800 watts, 0730-2300 (uses some *English*); HP5H, 6.122, Panama City, "La Voz del Pueblo," 500 watts, 0700-0000; HOXA, 15.100, Panama City, "Radio Centro Americana," 7.5 kw., now temporarily off the air; and HP5B, 6.030, Panama City, "Radio Miramar," 800 watts, current schedule not known but is probably 1800-2300.

## Facts About Panama

In 1513 Vasco Nuñez de Balboa forced his way through the jungles to discover the Pacific Ocean, and in 1538 Spain's Emperor Charles V. established the Real Audiencia de Panama with jurisdiction over Nicaragua to the north and all the Spanish Provinces to the south as far as the Strait of Magellan (including the Provinces of Cartagena, Peru, Chile and what is now the Argentine). Panama became independent from Spain by a movement of its own, November 28, 1821, and subsequently joined the Great Colombian Confederation formed by Venezuela, Colombia, and Ecuador. It broke away from Colombia on several occasions but never fully succeeded in separating until November 3, 1903, when it finally seceded and became an independent Republic. It was recognized as such by the United States on November 13th of that year.

Panama occupies the entire isthmus of that name, connecting North and South America, lying between the Caribbean Sea on the north and the Pacific Ocean on the south. Panama is one of the six Central American or Middle American countries.

# SURPLUS SPECIALS

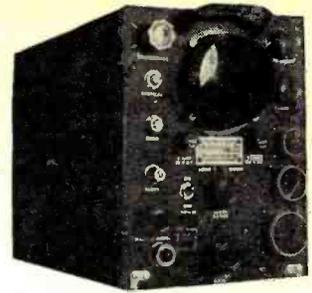

- Cathode Ray Scope, 3" radar indicator ID-93/APG-13A, 115 volts 400 cps, 10 tubes plus 3" cathode ray tube. Power supply and sweep circuit need modification to make fine scope. New, made by G.E. **\$25.00**
- RCA Cathode Ray Scope, 5" screen, model 160 B, regularly priced at \$185.00, our price for the new instrument **\$135.00**
- RCA Voltohmyst model 165, electronic voltometer, 0-1000 volts AC & DC in 6 ranges, 0-1000 megohms in 6 ranges, new **50.00**
- RCA Beat Frequency Audio Oscillator, model 154, 30-1500 cps, attenuator. Very useful for P-A work, new **60.00**
- Bendix Radio Compass Receiver, Freq. Range 150 to 1500 KC, 12 tubes, 12 volt dc operation, new **50.00**
- Clough Brengle AC Capacity, Resistance and Turns Ratio Bridge, model 230, new **55.00**
- General Radio Precision Wavemeter, type 724-A, 16 KC to 50 megacycles, 0.25% accuracy, V.T.V.M. resonance indicator, complete with accessories and carrying case, new **200.00**
- BC 947A Radar Transmitter with 10 cm magnetron, less power supply **40.00**
- Wide range signal generator, Triplet model 1632, continuous frequency coverage from 100 Kc to 120 megacycles in 10 bands, metered output, direct reading frequency dial, in good working order **65.00**

## ELECTRO IMPULSE LABS.

P. O. Box 250 Red Bank, New Jersey

# 75,000 Sold!

## REFERENCE DATA for RADIO ENGINEERS

### Now Ready—New Printing of enlarged 2nd edition

Contains a wealth of important new data needed by every electronics engineer and student. Enlarged from 200 to 336 pages, with over 400 charts and diagrams. Compiled jointly by specialists of Federal Telecommunication and International Telephone and Telegraph Corporations. New edition hailed by educators and communications experts. "Indispensable," says DR. LEE DE FOREST.

"A Must" ALLEN B. DUMONT, PRES.  
Allen B. Dumont Laboratories, Inc.

"Certain to meet with universal acclaim"—BRIG. GEN. F. L. ANKENBRANDT, U. S. Army. "REFERENCE DATA" makes quickly available the answers to problems that normally arise in practical radio work. The large volume of last-word ready reference data is one reason for rapid sale of 75,000 copies.

The new 2nd Edition, in durable green fabrikoid binding, is ready in a new printing. Price \$2.00. Many purchasers take advantage of low quantity price for 12 or more to a single address (\$1.60 each).

Federal Telephone and Radio Corp.  
67 Broad St., New York 4

ORDER NOW!

USE COUPON

Federal Telephone and Radio Corporation  
Pub. Dept. A18, 67 Broad St.,  
New York 4, N. Y.

I enclose .....dollars,  
for which send me .....copies  
at \$2.00 per copy. (\$1.60 for 12 or more to one  
address.)



NAME.....

ADDRESS.....

CITY.....ZONE.....STATE.....
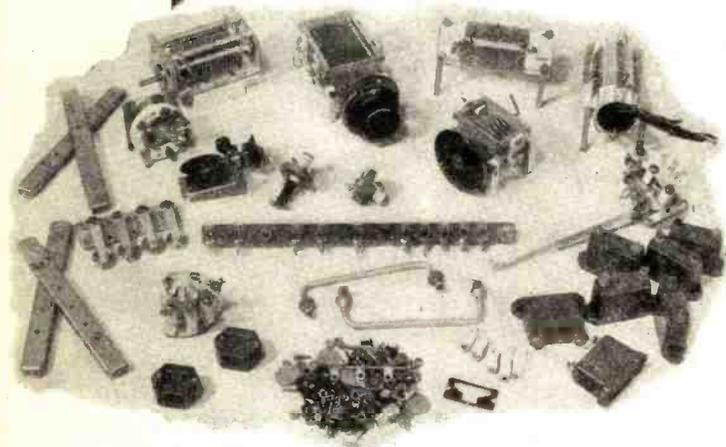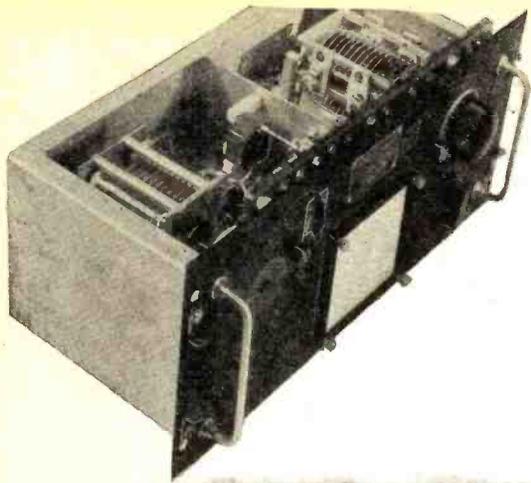
# Words Fail Us!

We Wells people have never liked sensational advertising but when we find a piece of equipment like this G. E. Tuning Unit offered for a tiny fraction of its real value, it's hard to be modest about it. Naturally, these units tune to frequencies outside of the ham bands. But we have yet to see a real Radio Amateur who can't cut a few coil turns to build a useful piece of equipment.



## Brand New G. E. Tuning Units \$2<sup>50</sup> each

Easily Converted to:

**MASTER OSCILLATOR TUNER  
C. W. TRANSMITTER  
RESONANT LINE TUNER**

### PARTS ALONE WORTH 20 TIMES OUR PRICE

Practically every part in the unit fits right into Amateur requirements. So we suggest that you order extras to be dismantled for spare parts.

### Look At These Parts — All For \$2<sup>50</sup>

- 1—Aluminum Panel 16<sup>3</sup>/<sub>4</sub>" x 7<sup>3</sup>/<sub>4</sub>"
- 1—Micrometer Drive unit for 1/4" shaft
- 1—GE Planetary Drive unit for 1/4" shaft
- 1—150 MMFD Trans. Plate Tuning Cond. 31 plate, ceramic insulated
- 1—125 MMFD Trans. Plate Tuning Cond. 25 plate, ceramic insulated
- 1—35 MMFD Transmitting Plate Tuning Cond. 7 Plate
- 1—Single pole 6 Pos. Heavy duty Ceramic band switch with knob
- 2—2 Pole Double Throw Heavy duty Ceramic band switch with knob
- 3—100 MMFD Transmitting mica cond. 3000 WVDC
- 1—60 MMFD Transmitting mica cond. 2000 WVDC
- 3—90 MMFD Transmitting mica cond. 3000 WVDC

- 2—40 MMFD Transmitting mica cond. 2500 WVDC
- 2—Ceramic coil forms 5" long, 2" dia. wound with No. 14 wire
- 1—Micalox strip 12" x 3/4" x 1/4" with Banana Plug jacks
- 1—Gang of 4 transmitting neutralizer condensers
- 2—Aluminum handles 5" long, 1 1/4" dia.
- 2—Ceramic flexible shaft couplings
- 15—Ceramic standoff insulators. Tapped ends
- 8—Aluminum standoffs tapped ends
- Brackets, screws, lugs, misc. wire and ventilated case, lock washers, etc.
- 1—5 millihenry 300 MA choke RF
- 1—6 millihenry 300 MA choke RF
- 1—15000 ohm 5 watt resistor

#### Two Models Available:

TU 5B 1.5 to 3 Mc — \$2.50 each

TU 10B 10 to 12.5 Mc — \$2.50 each

Black crackle dustproof cabinet for above — 50c each

These tuning units may be ordered directly from us or through your local Jobber.


We Think We Have Enough for Everybody

# WELLS

**SALES, INC.**
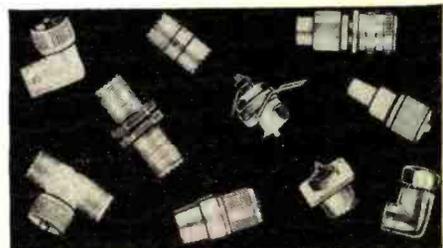
#### CO-AX CONNECTORS

We carry large stocks of all "83" series connectors in stock. Write for listing 100A or order from your Jobber.



Write for Amateur Radio Catalog H200-A

320 N. LA SALLE ST., DEPT. R-10, CHICAGO 10, ILL.



**BC-348**

**COMMUNICATION RECEIVER**

Excellent selectivity, sensitivity and stability makes this the most outstanding of any receiver yet available from government surplus. This Receiver will give outstanding performance wherever used. Built to withstand vibration and features gear driven 100-1 ratio vernier tuning control. Six bands—500 Kc. and 1.5-18 Mc. Two stages RF, 3 stages IF, BFO, crystal filter, manual or AVC. Complete with tubes and 24 V. DC dynamotor. Easily converted to 110V AC operation. These Receivers are used, but can hardly be told from new. Guaranteed operation. Supply limited.

Price .....\$48.75

**AIRCRAFT TRANSMITTER  
T19-A.R.C. 5**

Ideal to make over for master oscillator. Priced complete with tubes. Has built-in crystal for dial calibration. Used but in good condition. 3-4 MC or 4-5.3 MC. FREE Mounting Rack with order of two or more.



Price \$4.95

**NEW WILLARD RECHARGEABLE  
STORAGE BATTERY**



New 6 Volt battery in spill-proof clear plastic case, housed in metal case for easy mounting. Applicable for a wide range of uses where battery power is needed. Shipped dry. Uses standard battery electrolyte available everywhere.

Special Price while they last .....\$4.35  
two for ..... 8.25  
Without metal case each ..... 3.85  
two for ..... 7.50


**AIRCRAFT RECEIVER R-23 ARC-5**

This Receiver is very selective and sensitive. Has RF stage and BFO. Offered complete with tubes 12K5, 3-12SK7, 12SR7 and 12A6, also dynamotor which snaps on Receiver Chassis. Used but good condition 19-55 MC Receiver as above Each. . . . \$4.95



FREE Mounting Rack with order of 3 or more.

**INTERPHONE AMPLIFIER RL-9**

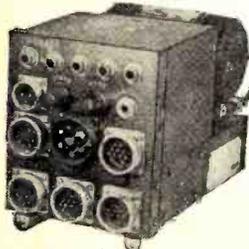

Convert to High fidelity phone Amp. or speech Amp. Complete with tubes and dynamotor, for 24 V. DC operation. Used but in good condition.

Special Price  
Each \$3.95

TERMS: CASH WITH ORDER

**AMERICAN SURPLUS  
PRODUCTS CO.**

537 N. CAPITOL AVE.  
INDIANAPOLIS, IND.

By a treaty of November 18, 1903, ratified February 23, 1904, and with a supplemental (Taft) agreement in the same year, the United States acquired the right to construct the Panama Canal across the isthmus, a strip (the Canal Zone) extending for five miles on each side of the Canal, the terminal cities of Cristobal, adjacent to Colon, and Balboa, adjacent to Panama City, and islands for defensive purposes in the bay, in perpetuity and exclusive control for police, judicial, sanitary, and other purposes. The United States also has complete jurisdiction over sanitary and quarantine matters in the two cities of Colon and Panama and owns and operates the Panama Railroad, 47 miles long, connecting these cities. In return, the United States paid Panama \$10,000,000 outright, and \$250,000 gold a year rental, beginning after the lapse of nine years.

A new treaty with the United States, replacing the Taft agreement (abrogated June 1, 1924) and modifying the treaty of 1904, was signed in Washington, March 2, 1936, by which the United States renounced its guarantee of Panamanian independence specified in the treaty of 1903, also the right to intervene to maintain order in the cities of Panama and Colon. The annual rental charge of \$250,000 in gold was changed (retroactive to February 26, 1934, in consequence of the dollar devaluation) to 430,000 balboas, the currency of Panama (equivalent in value to the U.S. dollar). The treaty further provided that no new private business be established in the Canal Zone, and only Government employees be allowed to reside there.

Of the total area of Panama, five-eighths is unoccupied and only a small portion of the remainder is properly cultivated. Immigration is restricted. The forest resources are great. Stock raising is carried on extensively. Chief exports are bananas, cacao, and coconuts. Area is 33,667 square miles and the 1941 estimated population, 635,836. Panama City is the capital.

The Roman Catholic religion prevails but other faiths have representation. Education is compulsory for all children between the ages of 7 and 15. There are 588 primary schools, 7 secondary schools, a college for the higher instruction of boys, a secondary school for girls, a professional school for girls, and crafts and trades schools for boys. The National University is in Panama City. Spanish is the official language and its use is compulsory.

In taking our leave of HP5J/HP6J in Panama City, we suggest you tune in George Williams' "Daily Newspaper of the Air" at 1230 and/or 1800 on 9.605 to hear his familiar voice "broadcasting the news of the day from the Crossroads of the World!"

**Fernando Po Data**

More information concerning the projected super-powered Spanish station now under construction comes this month from Lee Johnson, Maine,

who has translated this clipping from a Madrid newspaper.

"Work began early this year on the island of Fernando Po, south of Nigeria, on the west coast of Africa, for a radio station to be known as 'Radio Atlantic.' This station is to be operated by the Sociedad de Radio-difusion Intercontinental, a Spanish organization.

"It is expected that the station will be completed in about 17 months. The transmitter site occupies about 60 acres and is located at Mosula, about 40 miles west of the capital city of Santa Isabel.

"The direction of the antenna system will be Madrid but—augmented by beam antennas—the programs will be directed also in four directions—Europe, Africa, United States, and South America.

"Transmissions will utilize mainly Spanish, English, German, Portuguese, Italian, and French.

"Radio Atlantic will have 200 kw. power in the antenna and will operate in the 13- and 17-meter bands. Thus, it will be the most powerful commercial station in the entire world. There are two other stations of the same power in California, but they were constructed for military service in 1946. These California stations radiate programs and propaganda destined exclusively for Japan, Korea, and Manchuria and are heard there with such great strength that it seems the stations are in those countries.

"The Voice of Spain will be heard in all parts of the world. This will be, in the first place, a demonstration of our progress technically, and of our high ambitions, and, in the second place, no less important, Spain will be able to speak in a strong voice to people in every spot in the world, directly and definitely, without necessity of obscure intermediates."

(Fernando Po is an island—771 square miles—in the Bay of Biafra, and in the past was known as an exile for political offenders.)

\* \* \*

**Lamphouse Annual**

The 1947 Lamphouse Annual, published in New Zealand, is now available. It contains complete U.S., Australian, and Asiatic broadcast logs, s.w. log, and New Zealand "ham" addresses; log covers 30 pages. Can be had for five 5-cent stamps or 5 IRC's, from Arthur T. Cushen, 212 Earn Street, Invercargill, New Zealand.

\* \* \*

**Club Notes**

Germany—Berlin now has a radio club—Deutscher Amateur Radio Club—Berlin (DARC), address is Berlin-Rudow, Fuchsienweg 51; its publication will be "QTC." The German s.w. club was established in June at a meeting of German amateurs in Stuttgart. All previously-formed clubs were merged into DARC, with divisions in the American Zone, the British Zone, and in Berlin proper. Address of the German QSL Section is now DARC, QSL Section, Christoph Str. 27, Stuttgart. This information

**RADIO NEWS**

comes from Horst Miers, (7) Berlin No. 18, Barnimstr. 8, Germany, who adds: "I presume that following the war many German special (*wehrmacht*) tubes have come to America and other countries. I can give extensive information about all German special tubes to amateurs who are interested."

**Verifications**

Correct address for reports to Radio Nacional de Espana is Director of Programs and Broadcasts, Aveneda del Generalisimo, 40, Madrid, Spain (Espana). This station verified in both Spanish and *English*; latter card-verified said: "Radio Nacional de Espana verifies your perfect report of reception dated 30-4-47 and sends you its kind greetings;" signed by E. Thomaas de Carranza. (Casey)

ZPA-5, 11,948, Encarnacion, Paraguay, sent nice card in red, white, and blue, with large overprint of call letters ZP-5 and ZPA-5; printed frequency on card is 11,950. PCV, Kootwijk, Netherlands, 18,070, verified on prepared form from General Direction of Postal and Telecommunication (Continued on page 158)

**Sound Recording**

(Continued from page 53)

usually employed in the manufacture of phono pickups. The "PN" (primary ammonium phosphate) will temporarily stand temperatures as high as 212° F. with no permanent damage. They will withstand operating temperatures of 140° to 160° F. for a considerable time without suffering any permanent damage. Compared with the Rochelle salt crystal elements a "PN" element with the same dimensions and in the same assembly will produce a slightly higher open circuit output voltage. (Open circuit

**TELEVISION COVERAGE**

A RECENT FCC report has disclosed that the number of applicants for commercial television transmitting licenses has dropped from a high of 140 in October, 1945 to 75 as of June 5th this year.

The FCC has granted a total of 65 commercial television construction permits in 37 cities in 24 states. Of this number 11 stations are already on the air and 54 are required to be on the air within the next 12 to 18 months. In addition, there are ten more applications pending before the Commission—for a total of 75 commercial stations. The metropolitan population of the 37 cities to be served is around 44,000,000 with an additional 11,000,000 suburban residents within range of the stations.

The 11 stations now on the air are serving eight cities with a population of 27,000,000 persons, i.e., Albany-Schenectady, Philadelphia, Washington, St. Louis, Detroit, Chicago, and Los Angeles.

There are approximately 54,000 television receivers in the United States at the present time.

**FREE! NEW**

*Lafayette*

**FALL FLYER**


*packed with spectacular bargains in Radio, PA and Ham Equipment*

See the latest, greatest bargains the market offers today. Write for Lafayette's FREE Flyer C-40. It's packed to the hilt with slashing, smashing super values that have been typical of Lafayette for years. New, top quality items; speedy delivery. Send for Flyer C-40 now and save.

*typical Lafayette super values*

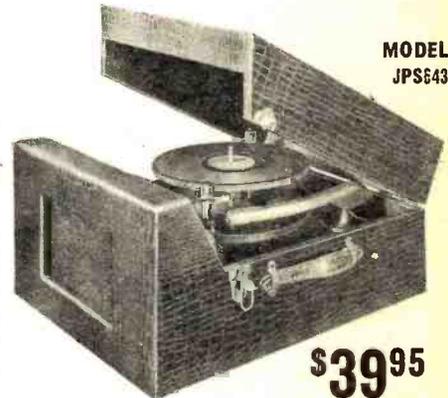**PORTABLE RECORD CHANGER-AMPLIFIER**

Sturdy construction; gentle action. Latest model record changer plays a stack of 10" or 12" records. Automatic or manual operation. Built-in amplifier uses tubes: 35Z3, 50L6, 14H7. Tone and volume controls. Alnico 5 PM speaker. Smart, 2-tone leatherette case with flexible handle and chromium fittings. 16"x19½"x9". Shpg. wt.: 23 lbs.



MODEL JPS643

**\$39.95**

**PORTABLE RECORD PLAYER** . . . . . Model JPS642

Super buy in a compact, lightweight single record player. Plays 10" or 12" records. The 5-inch speaker produces clear, undistorted tones; has built-in amplifier. Featherweight, tangent-pickup holds any needle. Rugged 5-ply wood case with handsome leatherette cover. 110 V. 60 cycle AC. 16½"x13"x7¼". Shpg. wt.: 15 lbs. **\$17.95**



MODEL 79

**\$52.92**

back and erases), an oscillator coil, a 15-minute spool of recording wire and an instruction sheet with suggested circuit diagram. The unit takes any standard Armour type recording spool; can make recordings up to full hour. 10½"x8¾"x5½" (3½" below main plate; 2" above). Net wt.: 10 lbs.

**WEBSTER-CHICAGO WIRE RECORDER FOUNDATION UNIT**

Make your own professional wire recorder at a phenomenal saving with this now famous Webster foundation unit. This is the same model used in the Webster Portable Wire Recorder. Has complete wire transporting mechanism, a triple-purpose recording head (records, plays

*Lafayette Radio*  
RADIO WIRE TELEVISION, INC.

100 SIXTH AVE. . . . . N. Y. 13  
542 FORDHAM RD. . . . . BRONX 58, N. Y.  
110 FEDERAL ST. . . . . BOSTON 10  
24 CENTRAL AVE. . . . . NEWARK 2, N. J.

FILL IN COUPON AND MAIL NOW

LAFAYETTE RADIO  
DEPT. RJ-7  
100 Sixth Ave.  
New York 13, N. Y.

Send Model No. . . . . at once. Enclosed  Money Order  
 Check  
 Rush Flyer C-40

Name . . . . .  
Address . . . . .  
City . . . . . Zone . . . . . State . . . . .


# SPECIAL SURPLUS SALE



**(A)** PE-73 Dynamotor ..... **4.95**  
 PE-103 Dynamotor New lot, only ..... **7.45**  
 Brand new, in original Signal Corps packing; delivers 160 mls at 500 volts; operates from 6 to 12 volts d-c; complete shock-mounted assembly includes breakers, switches, relays, filters, and cables.



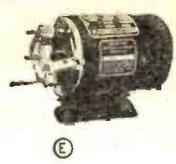**(C) RECEIVERS (274N Series)**  
 B.C. 454A. 3-6MC ..... **\$3.95**  
 B.C. 455A. 6-9.1MC ..... **3.95**  
 B.C. 453A. 190-550KC ..... **4.95**



**(A) ANTENNA TUNER**  
 A. BC. 306-A National "Velvet Vernier" dial with 100-0 scale. 5 position heavy duty high voltage—3 section RF switch. Two high voltage standoff insulators with spring type binding posts. Low frequency varlocoupler. Overall dimensions approx. 18½" high, 8" wide, 8" deep ..... **\$1.66**



**(B) ANTENNA RELAY UNIT**  
 B. 0-10 Meter Weston Thermo-couple unit with 50 MMF, 5000 V Vacuum cond. (Illustrated as B-A). Complete ..... **\$2.45**



ball bearing brand new. Ideal for power tools, fans and 100 other uses. In lots of 10. ..... **\$4.69**  
**F.** Band Pass Filter, 1000 cycle, close tolerance. .... **1.98**  
 Dual Choke—12 HY-200 MA 550HM D.C. resistance. Steel case with stand-off insulators. New. .... **2.95**

**TRANSMITTERS**  
 B.C. 456A. 3-4MC (VFO) ..... **\$4.95**  
 B.C. 457A. 4-5.3MC ..... **3.95**  
 B.C. 458A. 5-3.7MC ..... **3.95**  
 B.C. 459. 7-9.1MC (VFO) ..... **7.95**

**EXCELLENT CONDITION**  
**MODULATOR UNIT**  
 B.C. 456A. ..... **\$ 3.95**  
 S.C.R. 522 VHF XMTR-RCVR NEW. **29.75**  
 B.C. 348 RECEIVERS Xint Cond. ... **29.95**  
 B.C. 348 RECEIVERS New ..... **44.95**  
 D. Antenna Mounts, Mobile. .... **.99**  
 E. Electric Motor—110V, 60 cycle heavy duty const. Fractional H.P.

Also thousands of additional special items such as condensers, tubes, capacitors, transformers, insulators, radar equipment. Inquiries solicited. Get your name on our mailing list. Terms: 25% with order. Balance C.O.D.

**ESEGE SALES, Ltd.**  
 1306 Bond Street  
 LOS ANGELES, CALIF.

## NOW—IMMEDIATE DELIVERY TRANSVISION New—Sensational 12 Inch Television Kit

Picture large enough for 60 or more people.



**\$289**

**PRICE (Complete, less cabinet)**  
 Deposit of \$25 required. Will ship COD for the balance. Includes FM sound, 23 tubes including 12 inch picture tube, folded dipole antennae and 60 ft. lead-in wire. Nothing else to buy. All complex units pre-assembled at the factory and fully guaranteed for 90 days. Complete step-by-step wiring instructions, including pictures and wiring diagrams. Absolutely no instruments or technical knowledge required. All you need are pliers, screwdriver and soldering iron. Beautiful Walnut Table Model Cabinet. **\$44.95**  
 Beautiful Console Cabinet, with provisions for Record Changer and 12-inch Speaker ..... **74.50**  
 Plastic Lens for enlarging 7-inch or 10-inch pictures to 12-inch. .... **49.50**  
 Adaptor for above lens. .... **3.25**

Write for Special Dealers' Discount

**NATIONAL RADIO DISTRIBUTORS**  
 899a Southern Blvd., N. Y. 59, N. Y.



**Ever Sit On A Gold Mine?**

YOU can build a business of your own NOW — either part or full time — with TRADIO, the radio functionally designed for coin-operation in hotels, motels, stopovers, hospitals, etc. Big earnings . . . Steady income . . . and no clock to punch unless you want to.

### ★ ONLY SMALL INVESTMENT NEEDED

Tradio has pioneered in this new and fast growing industry. Get in on the ground floor and assure yourself of financial independence for life.

### ★ TRADIO IS TRIED, TESTED and PROVEN

Thousands of others all over the country have learned that "Tradio Pays While It Plays." Send for complete information today.



Write To Dept. P-10

**TRADIO, Inc.** ASBURY PARK  
 NEW JERSEY

means no load resistance, cable capacitance, or other impedances connected to the element.)

The capacitance of a typical Rochelle salt crystal cartridge element is approximately 1500  $\mu\text{fd.}$ , while that of a "PN" element having the same dimensions is about  $\frac{1}{10}$ th this value. Because of this comparatively low capacitance, a "PN" type cartridge cannot be used to replace a Rochelle salt type crystal cartridge directly for two reasons: 1. The additional capacitance of the cable or wire connected to the cartridge causes considerable loss of output. 2. The lower capacitance of a "PN" element requires that the load resistance used in pickup applications be approximately ten times the value used with a corresponding Rochelle salt unit if it is desired to obtain the same frequency response. This means values of from 5 to 50 megohms. When these high values of resistance are used at the input of a high gain amplifier, difficulties with insulation and noise pickup are much more severe than with the conventional low values. Certain manufacturers have employed "PN" crystal cartridges with equipment especially designed for their use.<sup>1</sup>

We mentioned previously that there were many varieties and versions of the crystal type pickup. In any pickup the torsional motion of the needle is transmitted to the crystal through a needle chuck. The needle is quite brittle and torsionally stiff. Therefore, if the needle were connected directly to the crystal, the pickup would present a high needle point impedance to the record. This would result in poor tracking and high record wear. For proper performance, the torsional stiffness of the crystal must be decreased by a ratio of roughly 25:1. Previously this has been done by interposing an elastic rubber block between the needle chuck and the crystal. The pickup cartridge, shown in cross section, Fig. 6, typifies this construction. The crystal is held at its lead end by means of two firm rubber blocks. At the front end the crystal is coupled to the needle chuck by means of a soft rubber coupling. Torsional motions of the needle compress the rubber coupling. The pressure thus developed acts upon the crystal and produces an output voltage proportional to the pressure.

The record groove is capable of transmitting only a limited torque to the needle chuck. This can be seen by examination of Figs. 1 and 7. This shows the groove and the needle point in cross section. The walls of the groove are inclined at approximately 45°. Therefore, the side force upon the needle point cannot exceed the vertical pickup force, otherwise the needle rides "uphill," resulting in distortion and record wear. Torque is force times distance. The maximum theoretical torque,  $T_m$ , which can be applied by the record to the needle

<sup>1</sup> Poff, J. K.: "The Crystal Phonograph Reproducer—Its Application and Care." Service Engineer, The Astatic Corporation, Conneaut, Ohio.

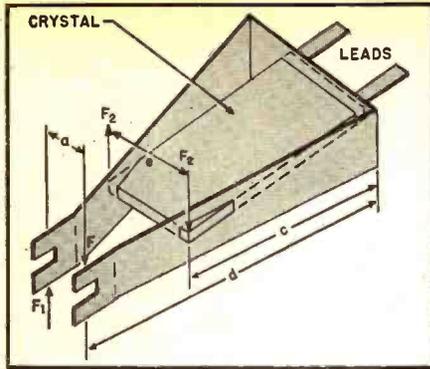


Fig. 9. An isometric drawing of the lever system design.

chuck of a pickup is given by the following formula:

$$T_m = Fh \text{ dynes-cm.} \dots \dots \dots (1)$$

Where:  $F$  is the vertical pickup force in dynes;  $h$  is the vertical distance from needle to needle chuck axis in cm.

The maximum torque is, therefore, limited by the needle force and by the length of the needle which, because of practical considerations, cannot exceed  $\frac{1}{2}$  to  $\frac{3}{4}$  of an inch. The actual torque is considerably less than the value indicated by (1). Because of unevenness of records, turntables, and the inertia effects of the tone arm, a part of the torque actually generated is lost in the needle chuck areas. In a conventional pickup, what remains of the original torque is transmitted into the rubber coupling in the crystal. The potential energy due to this torque is divided between the crystal and the rubber coupling in proportion to their respective compliances.

Inasmuch as the coupling compliance is related to the crystal compliance by a ratio of 25:1, it is seen that 25/26ths of the energy received from the record is spent in compressing the rubber coupling and is wasted. The remaining 1/26th is actually applied to the crystal. If means are employed for more efficient transmission of energy into the crystal, the output voltage may be increased theoretically by the square root of the energy ratio or approximately 5 to 1. This indicates the desirability of eliminating the elastic rubber coupling. But if the elastic coupling is eliminated, the impedance presented by the crystal to the needle is too great for proper tracking. To remedy this it is necessary to resort to an impedance matching device. Transformers for electrical matching are well-known to radio engineers. However, in mechanics, the lever plays the counterpart of an electrical transformer.

In the new pickup described here and developed by *Shure Brothers*, a torsional lever system was developed to lower the needle point impedance and to efficiently transmit the needle chuck torque into the crystal.

#### Lever Type Pickup

The new pickup developed by *Shure* is illustrated in cross section in Fig. 8. Fig. 9 shows an isometric drawing of

# Whether RADIO AMPLIFIER or QUANTOMETER



PHOTO COURTESY RADIO STATION WOR & WESTERN ELECTRIC

Cannon Electric Type DPB Connector using gold-plated contacts in Studio Control Booth Console, Type 120 Amplifier in the low level side. Plug-in connector greatly increases ease of servicing and maintenance.

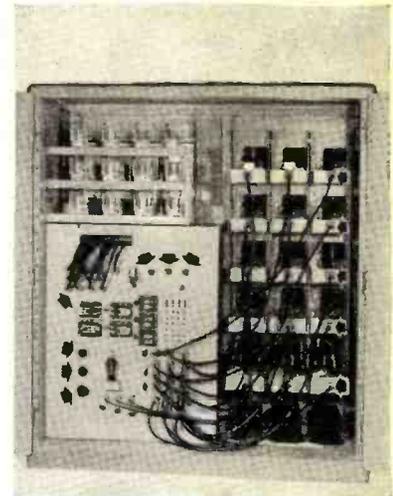


PHOTO COURTESY APPLIED RESEARCH LAB., GLENDALE, CALIF.

Arrows point to Cannon Electric Type "K" fittings connecting a maze of circuits on the Quantometer, a direct-reading spectrometer which determines chemical analysis of metals in 45 seconds. Rear view shown.

## Plug-in with CANNON PLUGS



K-21 Plug



RK-24C Plug

**TYPE "K"**—made in 3 general shell types with nearly 190 insert arrangements available for a wide variety of wire sizes, including coaxials.



**TYPE DPB**—rack type pin and socket assemblies (both for fixed mounting) carry standard, coaxial and twinax contacts. Six basic layouts available in DPB, many more in the larger DPD shell size.



**NEW EDITION C-46-A CATALOG**—For a complete survey of the majority of Cannon Electric products, send for this C-46-A Catalog, containing prices on many items. Also included are the names and addresses of our distributors. Write Department J-228.



## CANNON ELECTRIC DEVELOPMENT COMPANY

3209 Humboldt Street, Los Angeles 31, California

Canada & British Empire — Cannon Electric Co., Ltd., Toronto, Ontario • World Export Agents (excepting British Empire) Frazar & Hansen, 301 Clay St., San Francisco 11, Calif.

# RADIO-ELECTRONIC SCOOPS from MID-AMERICA

**Order by Mail While  
Limited Quantities Last!**

Listed here are a few of the hundreds and hundreds of radio and electronic bargains Mid-America has to offer right now! Order direct from this ad for quick delivery, and ask for Mid-America's great, new catalog that lists many other big buys just like these!

## 274N-TYPE TRANSMITTERS

Complete with Crystals and All 4 Tubes  
Transmitters in this series have a 1625 temperature-compensated oscillator circuit, two 1625's in parallel as RF power amplifiers, and a 1629 resonance indicator for the crystal calibration circuit. These units were designed for voice, MCW and CW transmission. 4.0-5.3 MC. Used but in good condition.  
4500 KC crystal. MA-2120.....\$3.95 ea.  
2.0-3.0 MC. Brand new units. 2500 KC crystal. MA-2121.....4.95 ea.  
3.0-4.0 MC. Used but in good condition.  
3500 KC crystal. MA-2122.....3.95 ea.

## SPECIAL! Antenna Assembly AN-104-B

Used with SCR-522, 274-N, and ARC-5. Approximately 1/2 wave on 100-150 MC. Coaxial connector in base. Use anywhere; has silver weather-proof finish. Two of these make an excellent dipole for FM or television; large cross-sectional spacing permits broader than usual band tuning. **79c**  
MA-2153.....Ea.

**GREAT PARTS VALUE!** Brand new APA-1 radar indicating equipment. Amplifier contains 11 tubes: 2x2/879, 6H6, 6G6G, 6X5GT, 7-6SN7GT. Chassis loaded with resistors, condensers, etc., contained in handsome metal cabinet. Control unit in separate cabinet has switches, potentiometers, connectors, etc. Scope indicator with 3BP1 CRT tube enclosed in metal shield; has rubber-tipped visor and 6 feet of 11-conductor shielded cable. All new, with tubes and operating handbook. MA-2123 **\$19.95**

**SPARE PARTS CHEST**—53 popular tubes, hundreds of resistors and condensers, transformers and chokes, wired amplifier with 115 V, 60 Cy power supply, plugs, switches, connectors, cables, hardware, sockets, etc. Hardwood cabinet 30 1/2 x 30 1/2 x 32 1/2 with storage compartments and 5 20" drawers makes **\$49.50** excellent workbase. MA-2096.....

**MARKER BEACON RECEIVER BC-1023-A**—with tubes (6SQ7, 6U6GT, 6SC7, 12SH7). 12-14 **\$4.45**  
VDC input. MA-2107.....Ea.  
**SCR-518 ABSOLUTE ALTIMETER**—Complete equipment with tubes, power supply, scope indicator, etc. MA-2106.....Ea. **\$49.50**

## TUBULAR ELECTROLYTIC CONDENSERS

	mfd	VVDC	Ea.
MA-829	50/30	150	79c
MA-831	8	450	29c
MA-832	16	450	45c
MA-833	8/8	450	45c
MA-835	30	25	29c
MA-836	40	150	49c
MA-838	150	25	39c
MA-115	100	15	19c

## PLATE-MOUNTING METAL-CASED FP CONDENSERS

	mfd	VVDC	Ea.
MA-826	8	250	49c
MA-442	16	500	89c
MA-806	25	25	29c
MA-837	40/40/30	150	98c
MA-443	125	300	98c

**ORDER NOW!** Send 25% deposit with orders. Order by stock number. We ship fastest possible way C.O.D. for balance and shipping charges. Send orders to Mid-America's store address. Address orders to Desk E-107.

## FREE CATALOG

Rush your name and address for Mid-America's great new catalog that lists thousands of items at prices that defy competition. Get your name on our mailing list for monthly bulletins that keep you up-to-date on the latest bargains in top-quality radio parts, and electronic equipment. Address requests to Desk E-107.

## MID-AMERICA CO. Inc.

STORE 2412 S. MICHIGAN AVE. CHICAGO 16, ILL.  
WAREHOUSE 2307 S. ARCHER AVE. CHICAGO 16, ILL.

the lever system. The lever consists of a single strip of thin aluminum perforated to receive the crystal and bent in a trapezoidal shape. The rear portion of the lever and crystal assembly is held in the cartridge case between two firm rubber blocks. The ends of the lever engage the needle chuck through two composition pads which serve to provide longitudinal shock isolation between the chuck and the lever but have negligible transverse compliance. For all intents and purposes, the motions of the needle chuck are faithfully followed by the ends of the lever. This particular type of lever pickup has an important structural advantage over most conventional pickups because it does not depend upon soft rubber couplings, or other materials which deteriorate with age, for generation of voltage.

The structure of the lever pickup is dynamically simple. Since the lever is rigidly coupled to the needle chuck,

the system has only one degree of freedom and can be damped therefore, with a single set of damping pads, *M* and *N* in Fig. 8. In contrast to this, the conventional pickup (Fig. 6) has two degrees of freedom; the needle chuck and the crystal which are loosely coupled by the rubber coupling member. Two separate sets of damping pads *MN* and *PQ* are therefore required. The selection and control of two sets of damping pads has made it difficult to control such pickups in production. In the design of the lever type pickup, care is taken to hold the lateral mass referred to the needle point to a very low value. The needle chuck is made of a very light alloy. When used with an aluminum shank needle, it presents to the record a mass of less than 50 milligrams. Tests on frequency records with needle forces of one ounce indicate good tracking at all frequencies.

(To be continued)

## GERMAN HOME RADIO RECEIVER

BY KARL GREIF

**A** NEW radio receiver of German manufacture which is being marketed under the tradename "Saba" has several new features which are of interest to the radio industry.

The receiver features an enormous slide-rule dial, with the names of cities located in such a manner that when the pointer is in a certain marked rectangle on the dial, that city is "in tune". This feature is in addition to the regular calibration in kilocycles and meters.

Tuning is accomplished with a very heavy fly-wheel, high ratio cable, and pulley system. The tuning knob is at the right end, as well as the band switching control. Possible selections

included "Phono," "150-400 kc.," "500-1500 kc.," "30-92 meters" and "13.5-36 meters." At the left of the front panel is located the "on-off" and volume control—pulling out on this knob turns the set on with any 50-60 cycle voltage from 110 to 220 volts, in steps. The other knob on the front, at the right, is for tone control. Dual range is provided by pulling out on this knob.

The circuit is very selective and extremely sensitive. Forty-two clear stations have been logged without advancing the volume above local station level. Background noise is at an absolute minimum. The set uses a separate i.f. resonant circuit for each band. -30-

Product of a German company, this "Saba" home receiver could be classed as "above average" in the European market. The usual type of receiver manufactured on the Continent is of the two- or three-tube regenerative variety.




RADIO NEWS

# UNBELIEVABLE VALUE!!

a Multi-Range VOLT-OHM MILLIAMMETER **AND** ALL-WAVE SIGNAL GENERATOR



**BOTH FOR ONLY \$34.85**

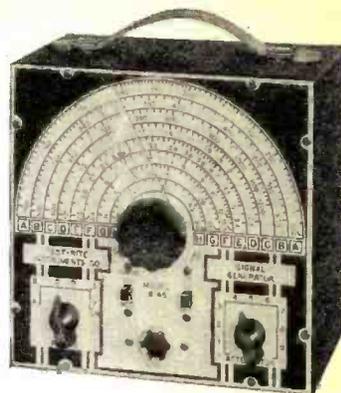

Don't pass up this amazing introductory offer! Rush your order now for this sensationally low-priced combination. Skeptical? . . . of course . . . but rush your order anyhow we guarantee to refund your money in full if the units do not meet with your complete approval after a 10 day FREE trial.

### Specifications of Model M-50


- Accurate Pocket size V.O.M. using full size D'Arsonval meter
- 4 A.C. VOLTAGE RANGES: 0-15/75/300/1500 volts.
- 4 D.C. VOLTAGE RANGES: 0-15/75/300/1500 volts.
- 2 D.C. CURRENT RANGES: 0-15/150 MA.
- 2 RESISTANCE RANGES: 0-10,000 ohms; 0-1 Megohm.
- Attractive modern black and white panel.
- Beautiful hand-rubbed oak case. Complete with test leads and all operating instructions

### Specifications of Model B-45

Generates RF frequencies from 150 Kc. to 50 Mc. Modulation is accomplished by grid-blocking action—equally effective for alignment of amplitude and frequency modulation as well as for television receivers. Self-contained batteries. All calibrations etched on front panel for DIRECT READING. Beautiful processed dualtone front panel in heavy gauge crystalline steel cabinet. Complete with test leads and batteries.

20% deposit required on all C.O.D. orders.

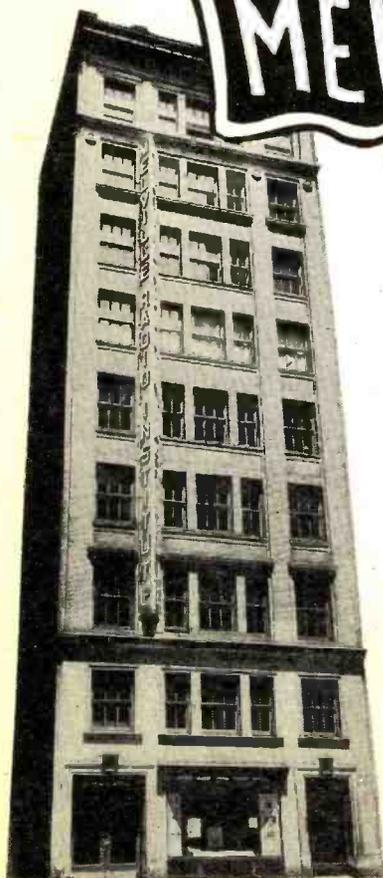MOSS ELECTRONIC DISTRIBUTING CO. 68 WESTCHESTER SQUARE  
Dept. RN-10, NEW YORK 61, N. Y.



## RADIO INSTITUTE

Outstanding PRE-WAR Technical Training Center for

# TELEVISION & RADIO

Under the personal direction of Frank Melville, former Airlines, Merchant Marine, and Broadcast technician, you may soon qualify as:

- RADIO TECHNICIAN
- AIRLINES RADIO OFFICER
- PT. TO PT. TELEGRAPHER
- RADIO AMATEUR
- MERCHANT-MARINE RADIO OFFICER
- TELEVISION TECHNICIAN
- HOME RECEIVER REPAIRMAN
- VISUAL TELEGRAPH OPR. (SLIP TAPE)

MELVILLE RADIO INSTITUTE believes vocational training means vocational training. Thus we, like many radio schools, teach ample theory. But, unlike most schools, two-thirds of our technical students' time is spent in laboratories and shops, where, with superior equipment, they learn by doing — not memorizing.

FREE employment service is available to all MELVILLE graduates.

Visit the 10-story MELVILLE Building today as our guest and observe the school in operation.

Day and evening classes approved for veterans. Licensed by the State of New York.

### MELVILLE RADIO INSTITUTE

Melville Building  
15 West 46th St., N. Y. 19 • BRyant 9-5080

### MAIL THIS COUPON NOW!

MELVILLE RADIO INSTITUTE R.N.  
Melville Building  
15 West 46th St., New York 19, N. Y.

Gentlemen: Send me Free information about your school.

Name.....

Address.....

For Faster Soldering

**5-SECOND HEATING**

Ready to solder in 5 seconds.

**LESS TIP RETINNING**


Heats only when needed.

**FAST COOLING**

Ideal for service calls.

# WELLER

## SOLDERING GUN

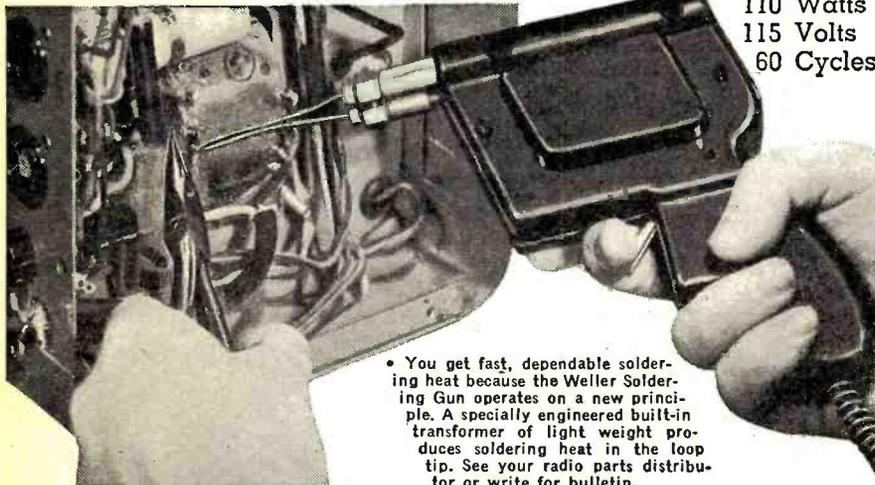

110 Watts  
115 Volts  
60 Cycles

• You get fast, dependable soldering heat because the Weller Soldering Gun operates on a new principle. A specially engineered built-in transformer of light weight produces soldering heat in the loop tip. See your radio parts distributor or write for bulletin.

**WELLER MFG. CO. 810 Packer St., Easton, Pa.**

In Canada: Atlas Radio Corp., Ltd., 560 King St., N. W., Toronto, Ont.  
Export Dept.: 25 Warren St., New York 7, N. Y.

## GREENWICH SALES SURPLUS BARGAINS

T-12 TRANSFORMERS 115v-60 cycle, primary; Sec. #1—6.3v @ 2 amp; Sec. #2—2.5v @ 6 amp. Hi-volt insulation, grey case, porcelain terminals; new ..... **\$2.50**

T-14 Primary 105/110/115/120v—60 cycle Amertran; Sec. 2.5v @ 10 amp; 2.5 KV insulation; new ..... **\$1.95**

L-8 DUAL CHOKE SPECIAL 6.5 Henry-40 mils; 200 ohm resistance each section; new ..... **\$1.00**

S-52 UTC BIAS TRANSFORMER—will deliver from 75-400v DC @ 200 mils; within 6% of desired value. Brand new ..... **\$5.95**

TA-12 BENDIX AIRCRAFT TRANSMITTER—1 channel MOPA—807 buffer; pr. of 807 output; good condition, with tubes and conversion; excellent value at ..... **\$35.00**

PHILLIPS HEAD TYPE SCREWDRIV. ER-6" Blade; new; 3 for ..... **\$1.00**

### 50c TUBE SPECIALS

GUARANTEED: 6V6GT—6J7G—6H6—6K6G—1L4—1629.

### 65c TUBE SPECIALS

6SJ7—6SK7—E1148—6C4—955—956—5U46—6K7.

### 75c TUBE SPECIALS


9006—5R4GY—VR75—VR150—1A7—1H5—1N5—6SQ7—6F8G—6K8.

SPECIAL 307A (RK75) Two for \$3.00.

25% deposit required on all C.O.D. orders. Prompt delivery assured. Write Dept. RNS. Include postage with order

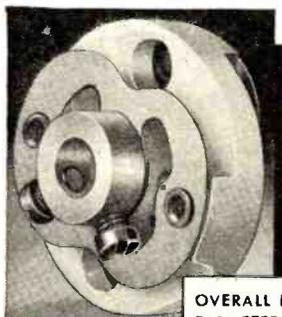**GREENWICH SALES CO.**

59 Cortland St. Whitehall 3-3052  
NEW YORK CITY 7, N. Y.



OVERALL DEPTH  $1\frac{3}{16}$  INCH  
DIAMETER  $1\frac{1}{4}$  INCH  
HUBS DRILLED FOR  $\frac{1}{4}$  INCH  
SHAFTS

## FC-46-S INSULATED FLEXIBLE COUPLING

The FC-46-S is a sturdy flexible coupling which will provide a linkage between angularly misaligned shafts without causing backlash or play.

The forces developed in the coupling are uniform as the shaft is rotated, which gives you that SMOOTH feeling as you turn the shaft.

WRITE FOR FOLDER

# HAMMARLUND

THE HAMMARLUND MFG. CO., INC., 460 W. 34TH ST., NEW YORK 1, N. Y.  
MANUFACTURERS OF PRECISION COMMUNICATIONS EQUIPMENT

## International Short-Wave

(Continued from page 153)

Services, 12 Kortenaerkade, The Hague; stated, "PCV is one of the Netherlands PTT commercial transmitters, also used for the radio-telephone traffic from Amsterdam to Paramaribo (Surinam)." The Direction Generale des Telegraphes de Suede verified reception of a Swedish fone station as "one of the Swedish transmitting stations, SAT3-10, situated at Horby in the very south of Sweden, and used since March 1947; SAT-4 (the one reported) has a frequency of 13.862.5." A verie-letter was received from PJD, 11.900, St. Maarten Island, N.W.I.; station is located at Phillipsburg and is crystal-controlled; signed by Acting Chief of Radio Station PJD, C. Peterson; duration 32 days. Omdurman Broadcasting Station, % Public Relations Office, P.O. Box 282, Khartoum, Anglo-Egyptian Sudan, operating on 13.320 and 9.650 with 250 w., verifies within 6 weeks by mimeographed sheet. THA, L'Ingeneur Techniques de la Radiodiffusion, 10, Rue Hoche, Algiers, Algeria, operating on 11.835 with 12 kw., QSL'd by English letter, also sending schedules; duration 3 months. COCX, 9.273, 1 kw., % Estacion de Onda Larga CMX, Mil Diez, Reina 314 (Altos), Habana, Cuba, sent letter-erie in Spanish in 6 weeks for report sent in Spanish. (Kary)

### This Month's Schedules

(Note: By now some stations will have returned to Standard Time from Summer Time—making certain schedules herein one hour earlier than listed.—K.R.B.)

Alaska—WXEG, 12.255, Adak, is still often heard calling Seattle around 0105. (Nankervis)

Algiers—THA, 11.838, has been heard in West Virginia around 1945 to 2030 sign-off—with Arabic chant, singing, and news (French); used "La Marseillaise" at sign-off. (McLaughlin)

Andorra—Radio Andorra, about 5.990, still has English session, mostly music, at 1600-1630 daily. (Peddle) Still asks for report and says will play request numbers. (Miers)

Angola—CR6RA, 9.470, Luanda, is heard in Sweden from around 1415 to approximately 1600; sign-off varies slightly. Suffers QRM from TAP, 9.465, Ankara, until 1530. (Skogsberg) Is heard in Newfoundland. (Peddle) Good level in Australia, closes with Portuguese National Anthem. (Gillett)

In verifying for Paul Kary, Pennsylvania, in record time of 32 days, CR6RL gave this data: CR6RA, 11.035, 400 watts, Collins transmitter; CR6RC, 11.730, 150 watts, Phillips transmitter; CR6RL, 16.172, 9.500, 7.299, 1 kw., Standard transmitter; and CR6RN, 9.742, 1 kw., RCA transmitter. No schedules were sent. Report was forwarded registered airmail and verification came same way.

CR6RB, 7.175, "Radio Clube de Louanda," is heard in South Africa from 1300 to sign-off at 1430; fair signal. (Laubscher) Call clashes with that of Benguela, 9.165, so Luanda's 7.175 outlet may be "CR6RD."

Argentina—LRS-2, 11.970, Buenos Aires, heard from 2030 with excellent signal; announces "LR-4 en Buenos Aires y LRS, LRS-1, LRS-2 ondas cortas, Emisoras Radio Splendid." LRS on 9.316 has fair signal with some CWQRM, at same time, and LRS-1 on 5.986 is seldom audible. (Kary) LRS-2 is heard in New Zealand daily to 2300 sign-off, fine level. (Cushen)

Australia—Melbourne's VLR2, 6.150, is being heard in South Africa from 1500 sign-on; has news at 1545 and runs to around 1715. (Laubscher)

VLB, 9.54, has replaced VLC8, 7.280, in the daily beam to Britain, 1245-1415; VLA8, 11.76, still parallels. (Pearce)

The evening transmission to Eastern North America, 1900-2015, on VLA7, 17.800, is inaudible to only fair; VLC9, 17.840, used in parallel to South America, is usually obliterated by Moscow. News at 1930.

Frequencies of 17.840 and 15.200 are reported in dual to South America daily, opening at 1615.

Australia—Sendergruppe Rot-Weiss-Rot, 9.575, has been heard in Britain at 0000 giving calls of Sender-Salzburg, Sender-Linz, and Sender-Wien; has news in German and program details; often carries orchestral concerts from Vienna around 0115. (Pearce)

Belgian Congo—A station identifying as "Ici Radio Congolia, Leopoldville," at 1300 sign-on is heard on 9.21 daily, in South Africa; program is in an African language with African-type music; signs off at 1330, also with French announcement, followed by Belgian National Anthem; signals poor with severe CWQRM. (Laubscher) May be OQ2RC.


Leopoldville uses 9.745 and 17.770 in parallel in the daily (*English*) period, 1530-1645; news at beginning and headlines just before closedown; the 16-m. outlet has the better signal here in the East.

At times it appears that Leopoldville's 16-m. outlet is on 17.746 (measured) rather than listed and announced 17.770 (Arthur)

Belgium—ORF, 18.467, Ruiselede, heard calling WOF-2, New York, at 1500; modulation only about 80 percent; goes to scrambled telephony after making contact; slight CWQRM from PJY on 18.464. (Kary)

Ceylon—SEAC's 15.120 has much improved signal here in the East now, mornings, and on Sundays in the 1130-1330 beam to Britain; announces 17.770 in parallel for this Sunday period and use of 9.520, 6.075, and 3.395 to India and East Asia. The 17.770 frequency is heard here in parallel at 0730 when news is given; two wavelengths in the 19-m. band are used at that time—15.120 and 15.230, the latter is heard with very weak level and bad QRM. Roger Legge, New York, informs me that the 15.230 channel is

## BA Bargain Scoops!

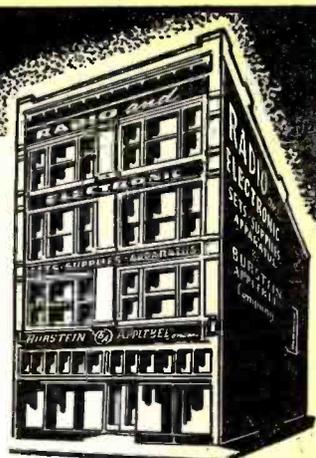

### 52 OHM COAX CABLE

**BRAND NEW 60 Foot COILS COMPLETE WITH CONNECTORS..... \$1.25**

It's genuine Amphenol RG-5/U—use it in place of RG-8/U. Has smaller diameter (.332), less capacity between center conductor and shield, less weight, easier to handle than RG-8/U. Rated at 1100 watts at 30 Mc. Supplied complete with standard Amphenol 83-1SP-(PL 259) connectors attached at each end.

No. 4A496—60 ft. coil with connectors..... **\$1.25**  
Any number coils connect together with 83-1J connectors (below)

### Extra Connectors

For use with above

Choice Each..... **35c**

83-1SP 83-1R 83-1AP 83-1J

### 10 Hy. - 200 Ma. Thordarson Filter Choke

200 ohm D.C. resistance, 2000 V. RMS. Size 3 3/8" sq. x 4 5/8" high. Wt. 5 1/2 lbs. Has 12" leads at side.

No. 13A266 Special Each..... **\$1.88**

### 80, 75 and 40 Meter CRYSTALS, 10 for \$3.95

In FT 243 holders, cut from highest quality quartz, accurately ground and acid etched. Frequency marked on each within 2 KC. Sorry we must sell them in assts. our pick of frequencies—but you can't go wrong! There are plenty of choice frequencies for 80, 75 and 40 meters or for doubling to 20 and 10 meters in each asst. Every one guaranteed to be an active oscillator.

Stock No. 21T3991 **\$3.95**  
Asst. of 10 only

### OIL FILLED CONDENSERS

10 mfd. 1000 volts CD Dykanal TJU List \$12.00  
No. 17A268 Spec. Ea..... **\$1.95**

8 mfd. 1000 volts Sprague List \$10.80  
No. 18A367 Spec. Ea..... **\$1.45**

5 mfd. 600 volts Sprague List \$7.00  
No. 18A366 Special Each..... **65c**

### JOHNSON VARIABLE

Dual section, 200 mfd. per section, 2000 V. breakdown. Spacing .045". Type 200FD20. List \$10.  
No. 18A510 Special Ea..... **\$2.95**

Johnson variable, dual section, 304 mfd per section. Spacing .045". Type 300ED20. List \$9.95.  
Stk. No. 18A509, Special Each **\$3.45**

Our terms: Cash with order or COD with 20% deposit please. Add Postage

### HANDSET TS13

Combines a 200 ohm carbon mike and 2500 ohm ear phone with butterfly switch for "listen" and "talk". Has 6 ft. flexible rubber cord with 1 each PL55 and PL68 plugs attached. Attractive bakelite case, light weight.

Ideal for interphone outfits for home or industry, mobile and many other applications. Made to rigid Signal Corps spec.

A Truly Outstanding Surplus Bargain. Every One BRAND NEW.

No. 17A407, Special Each..... **\$3.95**

### \$250 Value For 99c

**CURVED NEEDLE NOSE**

6" Crescent Tool Co. Drop forged "Crestoloy" steel, cadmium plated. Very handy for close quarters. At this price, every tool kit and bench should have one.

No. 16A376.

### Compact Rechargeable STORAGE BATTERY

Willard 2 Volt in Spill-Proof Clear Plastic case. Only 2 3/8" square and 6" high—(about the size of the ordinary #6 dry cell) make it applicable for a wide range of uses where battery power is needed. Rated at 24 AH. Gangs nicely for other voltages in multiples of 2 volts.

Shipped dry. Uses standard battery electrolyte available everywhere. Every One Brand New. While They Last, **\$1.95**

No. 5A133. Special Each

### The "Tops" in Headphones

At a Fraction of Original Cost

8000-ohm impedance, highly sensitive. Best quality Alnico magnets in molded black bakelite cases, concealed terminals. Headband fully adjustable, leather covered spring steel. 12" cord with PL54 plug attached at side out of way. Jack and rubber cord supplied to extend length to 5 1/2 ft.

Extremely lightweight, only 9 oz., with removable rubber ear cushions of comfortable design. Made to Air and Signal Corps specs. Brand New—a 13.50 Value. **\$2.49**

Stk. No. 17A37, Special Per Pair

## BURSTEIN-APPLEBEE Company

1012-14 MCGEE STREET, KANSAS CITY 6, MISSOURI

Did You Get It? The New B-A Catalog No. 471

# SAVE on WIRE

**SV Cord—18-2 Service Cord**  
Ideal for vacuum cleaners, washers, etc. **\$5.33**  
Per 250 ft . . . . .

Aerial Kits, 50 ft. wire, lead-in and insulators. . . Complete **\$ .41**

POSJ—18-2 Zip Cord, per 250 ft. . . . . **3.50**

## SPEAKERS

12" P.M. Speakers—  
Alnico . . . . . **\$5.49**  
4" P.M. Speakers—  
Alnico . . . . . **1.89**  
Hi-Par Non-Directional FM Antennas (Uses 300 Ohm Line) . . . . . **\$8.97**



### A Real Buy!

Deluxe 25-Watt Amplifier in Portable Case with two 12" Speakers. A few left at **\$59.50**

**FREE** a high-powered magnifying glass with every order amounting to \$5.00 or more.

### BC-654-A Portable Voice and Code Radio RECEIVER-TRANSMITTER

Use it for **PARTS TUBES TRANSMITTER RECEIVER** While they last **\$14.95** as is less dynamotors  
One-third deposit with order, balance C.O.D., F.O.B. shipping point.

JT-30 Astatic Mikes . . . . .	\$10.17
Hi-Imp. Dynamic Mikes . . . . .	9.75
Bogen 2-Way Intercoms	
Sub—with Switch . . . . .	24.60
Sub—less Switch . . . . .	23.10
Bogen Hi-Fidelity Amplifiers—	
PV-10, Net . . . . .	45.60
Model P Battery Eliminators . . . . .	8.82

**"It's D & H for Dependable Parts Service"**

# D & H

RADIO PARTS DIVISION

DISTRIBUTING CO., Inc.  
311 S. Cameron St., Harrisburg, Pa.  
31 East Lee St., Baltimore 2, Md.

used principally for the Indian transmissions although it does carry a few English sessions.

**Chile**—CE-1227, 12.270, is heard evenings; announces "Radio Ejercito en Punta Arenas, Republica de Chile;" has news in Spanish at 1943-1950. (Kary)

**China**—XMAG, 4.275, Nanking, 1 kw., heard with news from AFRS in Los Angeles at 0800; signs off at 1000; QRA is XMAG, S.S.O., Army Advisory Group, A.P.O. No. 909, % PM., San Francisco, California. (Cushen)

In verifying its 9.730 channel for Kary, Pennsylvania, XGOA, Nanking, stated that the 11.835 transmitter uses a center-fed, half-wave, delta-matched antenna running east-west, and that the antenna for 9.730 runs parallel.

Actual frequency of XGOY's 31-m. outlet is 9.663, scheduled during summer at 0535-0735. (Dilg) The 19-m. outlet announced as 15.170 appears to be actually 15.165. (Baxter, Dilg)

In an airmail letter dated July 4, Fung Chien, director of Chinese International Broadcasting Station, XGOY, Chungking, notified Kary, Pennsylvania, that "XMPA is the Chinese Armed Forces Radio Station, 720 and 12,200 kcs., broadcasting every day at 0700-0800, 1200-1400, and 1800-2300 hours Nanking time (1700-1800, 2200-0000, and 0400-0900 EST). Its address is No. 10, Snake Mountain, Hanchungmen, Nanking, China."

Director Fung Chien sent along these current schedules:

XGOA—Nanking, 15.35 and 9.73—1900-2200, news at 2010 and 2130, and talks (English) at 1910, 2040 (news commentary), 2100; on 15.35 at 0300-0900, news at 0420, 0500 (commentary), 0800, and talks (in English) at 0310, 0740; listed in parallel at 0700-0730 are 9.730 and 11.835, and the same frequencies are listed to parallel at 0815-0900 sign-off. (Possibly by now the 11.835 channel will have replaced 15.35 in the 0300-0900 transmission.)

XGOY—Chungking, 11.913, to Australia, New Zealand and East Asia, 0355-0530, no English except that on Saturdays carries "Back to the Bible" at 0500-0530, and on Sundays has "The Baltimore Gospel Hour" at 0430-0530; 9.658 and 7.153, to East Asia and South Seas, 0535-0735, news at 0600 and repeat at 0630 (except Sunday when carries Peking Opera), and has "Sermons in Song" on Wednesdays at 0635; 15.17 and 7.153, to North America and Europe, 0745-1000, news at 0800 (re-layed from XGOA, Nanking), and 0900 (but on Sunday has Foreign Ministry news in code at 0900-0935); 15.17 and 7.153, to Europe, China and South Seas, 1000-1050, news at 1000, closing with National Anthem.

Location of the station heard on 11.685 at 0800 with AFRS news is yet unknown. Call sounds like "XGAF." (Dilg) Sanderson, Australia, lists call as XGAS and as heard at 0730 with news in Chinese and music.

**Colombia**—HJDE, 6.145, Medellin, "La Voz de Antioquia," has a nice signal at 2300; signs off around 2310. (Norris)

LEARN NOW!

## ELECTRONICS

- RADIO
- F.M. and TELEVISION
- PUBLIC ADDRESS SYSTEMS
- SHORT WAVE COMMUNICATIONS

Men! Women! Find successful careers in this fascinating field! Ample equipment for all to use in practical classes. *You start practice when you enroll!*

**Approved for Veterans**  
**HOLLYWOOD SOUND INSTITUTE**  
1040 N. Kenmore Ave., Dept. A  
LOS ANGELES, CALIF.

ALL NEW AND GUARANTEED

### ● RECEIVERS

BC348 brand new, including RA20 AC power supply . . . Both Units **\$65.00**  
BC324 (12 volt BC348) used, in good condition with RA20 power supply . . . . . **\$45.00**

### ● TRANSMITTING TUBES

35T . . . . . **\$1.85** 250TH . . . . . **\$8.75**

### ● FILTER KITS

11Hy @ .600 amp herm sealed choke and 2 condensers 2mfd @ 5000 volts. Only **\$15.95**  
11Hy @ .600 amp herm sealed choke and 1-8mfd @ 2500 VDC condenser. Only **\$12.25**  
8Hy @ .250 amp herm sealed choke and 2 condensers 8mfd @ 10000 VDC. Only **\$5.95**

TERMS: 30% with order. Balance C.O.D. All shipments F.O.B. Chicago.

RUSH ORDERS TO

**SCHUH'S RADIO PARTS**  
1251 Loyola Avenue • Chicago 26, Ill.

### BEAM ROTATORS

Plenty husky for any beam a ham can dream up! Navy SO-1 radar type. Beautifully built mechanically and electrically. Instantaneously reversing. No overswing. Brand new complete with 110 cycle 60 cycle power supply. Write for details. **\$89.00**

### 1 K.W. MOTOR GENERATORS

Ideal for D.C. power district use, marine radio, or radar, etc. 115 volts D.C. input at 14 amps. 120 volts A.C. output at 10.4 amps. 60 cycles single phase. 1000 watts continuous duty. 3600 rpm. Centrifugal starter. Fully covered splashproof. Built to Navy specifications by the Allis Chalmers Co. Brand new . . . . . **\$87.50**  
Identical machine—230 volts D.C. input . . . . . **\$125.00**

All prices f.o.b. Tuckahoe, N. Y.  
**ELECTRONICRAFT, Inc.**  
5 Waverly Place • Tuckahoe, N. Y.  
Tel. Tuckahoe 3-0044

*Cyrenaica*—Vague reports have been received that *Radio Cyrenaica*, in North Africa, is being heard around 1530 on a frequency of 15.320. (Harrison)

*Dominican Republic*—HI1R, 6.430, "La Voz de Fundacion," signs off at 2005 with Dominican National Anthem; listed location is San Cristobal, but announces Ciudad Trujillo. After HI1R leaves the air, TGWB, Guatemala City, "La Voz de Guatemala," can be heard; this is apparently a new frequency for the Guatemala outlet; is no longer on 6.534. (Kary)

*Dutch Borneo*—Pontianak, 6.65, is heard in Australia at 0600 with musical program. (Sanderson) Schedule is only 45 minutes. (Dilg)

*Ecuador*—HC5HC, 4.960, Riobamba, has fair signals from 2115 until after 0000; announces "Estaciones Ondas del Chimborazo en Riobamba"; suffers bad aircraft QRM. (Kary) Is low-powered.

*Ethiopia*—Radio Addis Ababa, ETA, listed at 15.074 but actually lower, around 15.057, is still heard irregularly; reported by Dilg on West Coast around 0900; is heard here in East as early as 1300 to around 1458 sign-off. Appears to be on daily, including Sunday. At times has severe interference from WNC, Hialeah, Florida, used to contact South American points. ETA uses both Amharic and English for announcements, and plays many old records, mostly of American origin. Is heard in Britain as early as 1220 with dance recordings (Pearce). Heard there by Brownless as early as 1205, so transmission probably begins at 1200.

Frequency varies a great deal, has been logged in New York as low as 15.055. (Legge)


The 9.620 outlet of Radio Addis Ababa is heard in Australia at good strength prior to sign-off at 1100. (Gillett)

(Continued on page 179)
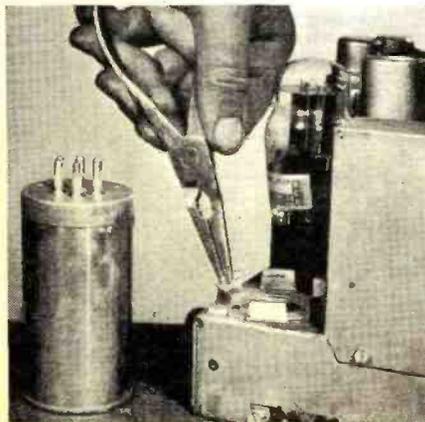
### KEEP VIBRATOR SPRING TIGHT

**T**O keep noise at a minimum and the vibrator prongs in perfect contact it is essential that the spring holding clamps have good tension against the vibrator case.

These clamps may be adjusted with pliers as shown. . . . . H. L.



October, 1947

## REPAIR RADIOS THIS FAST, EASY WAY!

Complete, easy instructions for diagnosing and repairing common troubles in practically every home and car radio in use today



### NOT A STUDY BOOK!

You don't have to be an expert! You don't have to have a lot of costly test equipment in order to repair most radios—NOT when you have A. A. Ghirardi's famous RADIO TROUBLESHOOTER'S HANDBOOK at your finger tips. Bothered with "fading" on a certain model? "Noises" on another? "Poor volume?" A "dead" set or whatnot? Just look up the receiver's make and model in the 404-page Case History Section of the HANDBOOK. Nine times out of ten, it will tell you EXACTLY what the trouble is—and EXACTLY how to fix it. No lost time! No needless tedious testing! The HANDBOOK tells you—automatically!

Over 300 additional big manual-size pages contain other invaluable radio service data—Color Codes, Tube Data, Tube and Part Substitutions, I-F alignment and Transformer information and literally dozens of charts, graphs, diagrams, data and helpful hints that will help you repair any radio ever made EASIER, BETTER and TWICE AS FAST! Weighs over 4 lbs. Only \$5—and you actually don't risk a cent. 5-DAY MONEY-BACK GUARANTEE.

PAYS FOR ITSELF Pronto!

RADIO TROUBLESHOOTER'S HANDBOOK will pay for itself in time saved the first time you use it! "Thanks to the HANDBOOK, I repaired my radio an hour after it had been returned as 'unrepairable' by a local radio shop," writes J. L. Fizzell of Kansas City. "The Case Histories take you right to the trouble and save hours of testing," says Julius Siske, Jr., of Maryland.



## Prepare for a Real Future in PROFESSIONAL RADIO-ELECTRONIC REPAIR WORK

LEARN AT HOME . . . without an Instructor

### GET WHERE THE BIG MONEY IS!

Ghirardi's MODERN RADIO SERVICING is the only single, inexpensive book giving a complete course in electronic servicing by scientific professional methods. Contains over 706 clear illustrations. Quick to read—easy to understand.

Who will service the millions of new radios and complicated television, F-M and facsimile equipment to be sold within the next few years? Who will install and service the countless electronic devices now going into industry? Never before has there been such a demand for professionally-trained technicians who know their stuff—and this means training of exactly the type that A. A. Ghirardi gives you in his big 1300-page, profusely illustrated MODERN RADIO SERVICING. It is the ideal book for home study! Explains all types of service test instruments—how to use each one; how to make preliminary trouble checks; how to analyze circuits scientifically; how to troubleshoot; how to repair or replace parts or make substitutions; how to install equipment—and literally hundreds of additional subjects including How to Start and Operate a Successful Service Business of Your Own. Sold on 5-DAY MONEY BACK GUARANTEE. You can't lose. Send coupon today!

### MAIL ORDER . . . Rush Coupon Now!

Murray Hill Books, Inc., Dept. RN-106  
232 Madison Ave., New York 16, N. Y.

Enclosed find \$ . . . . . for books checked; or  
 Send C.O.D. (no foreign C.O.D.'s) for this amount plus postage. It is understood I may return the books for refund within 5 days if not satisfied.

RADIO TROUBLESHOOTER'S HANDBOOK \$5 (\$5.50 foreign)       MODERN RADIO SERVICING \$5 (\$5.50 foreign)

MONEY-SAVING COMBINATION OFFER: Both big books, over 2040 pages of the finest service data—only \$9.50 for the two (\$10.50 foreign).

Name . . . . .

Address . . . . .

City & Dist. . . . . State . . . . .

### GET BOTH BOOKS AT A BARGAIN

#### SPECIAL OFFER!

Let Ghirardi's RADIO TROUBLESHOOTER'S HANDBOOK save you time and money on common radio service jobs—let MODERN RADIO SERVICING train you for complete professional, electronic service training!—Get BOTH BIG BOOKS at the special price of only \$9.50 for the two. Use coupon today. Check "MONEY-SAVING COMBINATION OFFER."

## 5-DAY MONEY-BACK GUARANTEE

**NOW YOU TOO CAN BUILD  
15 RADIOS**

COMPLETE  
KIT  
\$14.75



**ABSOLUTELY NO KNOWLEDGE  
OF RADIO NECESSARY**

**You Need No Additional Parts**

The PROGRESSIVE RADIO KIT is THE ONLY COMPLETE KIT. Contains Everything You Need: Instruction Book, Metal Chassis, Tubes, Condensers, Resistors and All Radio Parts.

The 36-Page Book written by Expert Radio Instructors teaches you to build radios in a professional manner. You will learn to wire and solder like an expert. You start with a 1-tube receiver. Before you are done with this kit, you will have built 11 Receivers, 1 Public Address System and 3 Transmitters.

**SPECIAL FREE OFFER!**

Electrical and Radio Tester with each PROGRESSIVE RADIO KIT

PLUS membership in Progressive Radio Club. Entitles you to free expert advice and consultation service with licensed radio technicians. Complete Kit shipped C.O.D. plus postage, or send check or money order for \$14.75 and we will pay postage. Or write for further information.


**PROGRESSIVE ELECTRONICS CO., Dept. RN-2**  
22 Havemeyer St., Brooklyn 11, N. Y.

- Check or money order enclosed. Postage Prepaid.
- C.O.D. I will pay postage.  Please send me further information.

NAME .....

ADDRESS .....

CITY.....ZONE.....STATE.....

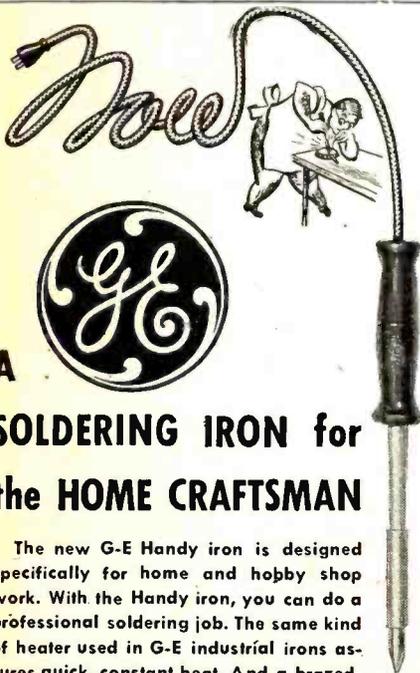


**A  
SOLDERING IRON for  
the HOME CRAFTSMAN**

The new G-E Handy iron is designed specifically for home and hobby shop work. With the Handy iron, you can do a professional soldering job. The same kind of heater used in G-E industrial irons assures quick, constant heat. And a brazed-on tip flows the heat to your work faster. Built for a wide variety of home soldering jobs, the Handy iron is a tool you'll use often. Only \$3.95. Ask to see it at your dealer's. Or write to Dept. F667-3K, Apparatus Dept., General Electric Company, Schenectady 5, N. Y.

FREE: A "how to solder" manual with every iron 667-3K

**GENERAL ELECTRIC**

**Presenting  
DONGENE  
LABORATORIES**

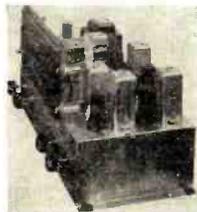

**New  
FM-AM TUNER**

1. TUBES: 13, including tuning indicator.
2. FM SECTION: Temperature compensated ceramic capacitors used throughout, thereby minimizing frequency drift.
3. IF TRANSFORMERS: FM-IF coils are wound on ceramic coil forms. Iron core type used on AM and FM.
4. FIDELITY: Broad band AM-IF amplifier.
5. POWER SUPPLY: Self contained, for operation on 117 volt, 50-60 cycle power line.
6. DIAL: Large 3 color, edge lighted, slide rule dial.

See it at your dealer, or write us for name of nearest one.  
Its the best buy at any price.

**DONGENE LABS. Inc.**  
95 VANDAM ST.

New York 13, N.Y. Tel. WAlker 5-4662

**Deluxe Cabinet**  
(Continued from page 69)

can be seen in the rear-view photograph, Fig. 2 (left). This frame should be of rather light angle-iron, and may be either welded or bolted. Incidentally, the smaller sizes of angle-iron are sometimes difficult to find, and a good source of one-inch size is old iron beds. They use several feet of it on either end for stiffening.

Mark off the opening you are going to cut in the back. It should be marked to the *inside* dimensions of the frame. After the opening is cut, a few minutes spent with a hammer will roll the edge inside so that the frame will fit. This is an added stiffening measure although it is not absolutely necessary. Drill a one-quarter inch hole at each corner of the marked-off opening, and start down the scribed lines with a cold chisel. This is easier than you may think, and is a matter of only five minutes or so with a small, sharp chisel. When the opening is cut, roll the edge and slip the frame in place. Drill through frame and cabinet back, and bolt with a dozen bolts.

With the frame bolted in place, you are now ready to hang the doors. This is done by simply drilling and bolting the same hinges which were removed from the front. Angle-iron door stops should be installed. The doors originally fastened with spring catches. These may still be used. Since the doors are made so that one must be opened before the other, a single interlock switch is sufficient. The one used in the illustrated cabinet is a s.p.d.t. plunger-type *Micro-Switch* (war surplus). It is hooked up to turn on a green pilot light as it opens the high voltage circuits.

The chassis mount or shelf is simply a frame made up of angle-iron, and bolted through the sides of the cabinet. This method has been found satisfactory, though there are many other ways to do it. With this type of mounting, all connections to each chassis are made through a multi-contact *Cannon* plug or a terminal strip. It is then possible to remove the knobs on the front of the panel and slip the chassis out the back as is done with home radio receivers. It is inadvisable to try to hang a chassis from the Masonite panel if it is carrying transformers or other heavy components.

Painting the cabinet is a simple but important part of the procedure. Many combinations of colors and shades are possible. *Raytheon* broadcast equipment, for instance, is done in two-tone brown; *General Electric* in blue. Both are exceptionally good looking units, and there are many other combinations which would look as well. The cabinet shown in the photographs is two-tone gray. The contrast is accented by a one-eighth inch stripe of Chinese vermilion at the edge of the dark gray on the sides. Any good fin-

ish will do. The cabinet illustrated was enameled. The finish is of a nationally known brand, and brushed on carefully. Spraying would, of course, be better and in that case the use of automobile finishes is to be recommended. Masking tape was used in applying the stripes and darker color. If you are not already familiar with masking tape, your paint dealer can supply it and explain its use.

It has been the intention in this article to deal in generalities, so that the idea could be suited to your cabinet and requirements. There are many variations possible. For instance, the front opening could be beefed up so that standard rack-mounting panels would fit. Another variation is to leave the doors on the front and mount a sub-panel behind them so that the transmitter could be closed up when not in use. A console containing speech amplifier, cathode-ray modulation monitor, and remote controls for the transmitter could be built to set on the operating table. The utility cabinet mentioned earlier could be used for lower power rigs, if allowance is made for its shallower depth. No provision has been made for ventilation, as it should be tailored to the particular layout you use.

There you have it, a cabinet capable of housing a half-kilowatt without crowding, and also capable of holding its head up alongside the best of broadcast equipment as far as looks is concerned—and all for about thirty dollars.

### TUBE SYMBOLS


AN INTERIM report, based on a total of 4211 replies out of 25,000 ballots in the Howard W. Sams & Co., Inc. balloting, shows that 35.4% of radio service engineers prefer "Method 3" (see figure below) for designating tube symbols on service schematics.

Runner-up, with a total of 24.1%, is "Method 7" which is more or less in standard use in the radio tube manuals.

The method which is being selected by the greatest number of service engineers provides base pin connections numbered in conformance with RMA basing standards. Sequence of the pins is arranged for clarity of circuit presentation and not in the same order as the tube socket. The various tube elements are shown in the drawing.

The results of this survey, which was conducted at the request of the RMA Service Committee, will be turned over to the committee for presentation to members of Radio Manufacturers Association.

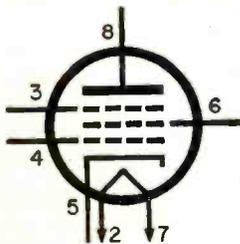Editor's Note: Readers will undoubtedly recognize "Method 3" as one that has, for some time, been used by RADIO NEWS. In conformance with the suggestions made in this survey, we plan to add the pin numbers to the tube symbols appearing in the schematic diagrams of construction type articles.



## GREAT BUYS FOR HAMS, EXPERIMENTERS!




**BC-645 XMTR-RECVR**  
15 TUBES 435 to 500 Mc.  
Only a few left! Tubes alone worth twice the price! Operates on Citizen and Ham frequencies. ALL BRAND NEW, complete with tubes each... **\$14.95**  
TWO FOR ONLY **\$27.00**

PE-101C DYNAMOTOR for above... **\$3.95**
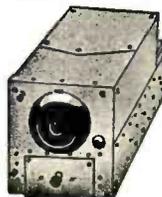
### ARMY AIRCRAFT RECEIVER— BC-946-B

Covers 520 Kc to 1500 Kc Broadcast Band. Tubes: 3—12SK7, 1—12SR7, 1—12A6, 1—12K8. Designed for dynamotor operation; can be easily converted to 110 volt or 32 volt use. Two IF Stages. Three-gang tuning cond. BRAND NEW, in sealed carton, with tubes and instruction manual, less dynamotor... **\$12.95**  
Dynamotor DM-32A... **\$1.95**



### RADIO RECEIVERS—

#### All Brand New in Original Cartons

BC-453-A 190 to 550 Kc complete with tubes... **\$7.95**  
BC-454-A 3 to 6 Mc complete with tubes... **5.95**  
BC-455-A 6 to 9 Mc complete with tubes... **5.95**

BC-458 TRANSMITTER 5.3 to 7 Mc. BRAND NEW... **\$5.95**

#### NEW BC-223-AX TRANSMITTER

Ideal for 80-meter band! 801 osc., 801 P.A., 2—46 modulators, 1—46 speech amp., 4 xtal freq and master osc., on selector switch. 10 to 30 watt output, tone, voice or C.W. Black wrinkle case, complete with freq chart and tubes in original cases, less xtals. BRAND NEW, sensationally low price, shpg. wt. 125 lbs... **\$14.95**

#### AN/PRS-1 MINE DETECTOR SET

Used for detecting metallic and non-metallic equipment buried in ground, complete with instruction manual, BRAND NEW in tool chest type carrying case... **\$14.95**



### SETCHEL-CARLSON BEACON RADIO RECEIVER BC-1206-C

Receives A-N beam signals, operates on 24-28 V. DC. Tubes: 3—14H7, 14R7, 28D7. Tunes 195 to 420 Kc. Size 4"x4"x6 1/2" wide. 4 lbs. Slightly used, A-1 condition. Each... **\$4.95**  
Same as above, BRAND NEW, in original carton... **\$7.95**

Astatic R-3 Crystal Handmike, with 6-ft. R.C. mike cable... **\$4.50**  
ASTATIC crystal pickups, with L-26 crystal cartridge... **\$1.79**

#### DC METER SPECIAL!

BEEDE METER, new, black bakelite case, 3" round 0-1000 DC Ma. Special... **\$1.95**

#### WILLARD 6-VOLT STORAGE BATTERY 20 amp. hrs.

3-cell battery, transparent plastic case, very specially priced... **\$4.50**

#### WILLARD 2-VOLT BATTERY 2-amp. hrs. similar to above, but single cell.

... **\$2.75**

#### ONE-QUART BOTTLE BATTERY ELECTROLYTE

Made by Willard, for above storage batteries. 1 quart sufficient for two 2-volt cells. Hermetically sealed. SPECIAL. per qt. bottle **95¢**

7-PRONG 2-VOLT RADIO VIBRATOR for Portable and Farm Sets Replacement for GE LB 530... **\$1.65**

Please Include 25% Deposit with Order—Balance C.O.D. Minimum Order \$3.00

**G&G GENUINE MAJESTIC RADIO PARTS SERVICE**  
53 VESEY STREET • NEW YORK 7, N.Y.

Phone: WOrth 2-1739-1898-9191

### SCR-522 VHF XMTR-RCVR

100 to 156 Mc.

10-tube xtal controlled superhet rcvr, extremely sensitive; 7-tube xmtr, temperature stabilized. Delivers 15 Watts. Used on AAF and RAF planes—now yours at tiny fraction of original cost! Easily converted to 110 volt 60 cy. operation. Complete with 17 tubes, A-1 condition only... **\$14.25**  
Dynamotor power supply for SCR-22 above, BRAND NEW... **\$3.95**



### HEADPHONES— All Brand New!

Individually packed, complete with phone plug. HS-33 600 ohms, in lots of 3... **\$1.85 each**  
HS-23 2000 ohms, in lots of 3... **1.65 each**  
HS-30 headphones, with earplugs, LOTS OF 12... **44¢ each**

### HANDSET

Cradle-type handset with butterfly switch, unbreakable black plastic, 4-ft. 3 wire cable, BRAND NEW, individually packed... **\$2.75 each**  
Same as above but slightly used, each **\$1.65**



### HANDMIKE T-17

Shure model T-17 mike, 200-ohm carbon single button, with press-to-talk switch, 5-ft. rubber cord and plug. BRAND NEW, individually packed, in lots of 3, each... **88¢**

### LIP MICROPHONE MODEL T-45

Small single button carbon mike, worn on upper lip. Complete with face straps, ALL BRAND NEW, in lots of 3, each... **45¢**



### PE-104-A VIBRATOR POWER SUPPLY

Works on 6 volt or 12 volt battery. Supplies 84 volts and 51 volts DC, also 1.4 volts "C" bias. Size 7"x4"x3 3/4". Can be used to operate many types of receivers now on market. ALL BRAND NEW, very low price... **\$4.95**




140 MMFD MIDGET TUNING CONDENSER  
Special for Hams! Long shaft. Lots of 3, each... **44¢**

250 MMFD TRANSMITTING CONDENSER  
Very Special Ham Value! 31 plates, Airgap .109" overall length 4 1/4", ceramic insulation, normal list price \$11.85. YOURS FOR ONLY... **99¢ each**
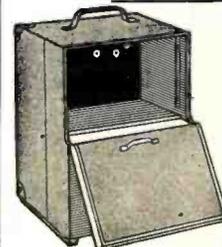
### WESTINGHOUSE "RECTOX" DRY DISC RECTIFIERS All Brand New!

6 Amps DC at 25 volts... each **\$2.95**  
8 Amps DC at 25 volts... each **3.95**




### METER CABINET for BC-221 Series Frequency Meters

Here's a terrific buy! BRAND NEW case. Has three compartments including pocket for charts, and schematic of BC-221 freq meter. Massively constructed. Overall size 14 1/2" high, 10 1/2" wide, 10" deep. Value \$20.00!

WHILE THEY LAST, only... **\$2.95**
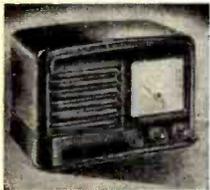
# 4 TREMENDOUS VALUES PROFESSIONALLY DESIGNED RADIO KITS

Kit Model FM-7, a splendid, low-priced, self-contained table model Frequency Modulated Radio Receiver Kit



Complete with tubes, speaker and beautiful Bakelite cabinet. The FM-7 has a frequency response of 86-110 MC, can also be used as a TUNER with a high quality amplifier. A

phonjack is provided in the rear of the chassis with double pole, double throw switch control for feeding signal to either the radio speaker or to the phonjack. An additional jack for connecting extra loud speaker is included. The R.F. section of kit is pre-tuned at factory. This kit uses 2 I.F. stages, 1 limiter stage and 1 discriminator. Miniature tubes used throughout. Price of Model FM-7 complete as described .....\$29.95



Kit Model R-3, a 3-tube receiver of the regenerative type

This receiver is the 110 volt type and operates at a frequency of 550 Kc. to 1500 Kc. by means of


a plug-in coil. The power supply is self-contained in the receiver thus eliminating the need for a separate power pack. Price of Model R-3, less tubes.....\$6.00



Kit Model S-5 uses the universally accepted super-heterodyne circuit

Containing the following tubes: 12SA7, 12SK7, 12SQ7, 50L6, 35Z5 and tunes from 550 Kc. to 1600 Kc.

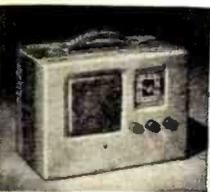Price of Model S-5, less tubes.....\$10.95



Kit Model 210, a Three Way Portable Receiver

Operating on either AC or DC or self-contained batteries power switch conveniently located on front of set so that "battery" or "A.C.-DC" may be selected without opening case. Five-inch Alnico 5 permanent magnet dynamic speaker, and case covered with weather tested aircraft material.

Price of Model 210, complete with tubes.....\$18.95

All kits accompanied by a detailed, illustrated instruction sheet. Many other kit models available, write for catalog K.

**RADIO KITS COMPANY**  
120 Cedar St. New York 6, N. Y.

# Manufacturers' Literature

Readers are asked to write directly to the manufacturer for the literature. By mentioning RADIO NEWS, the issue and page, and enclosing the proper amount, when indicated, delay will be prevented.

## FREE PHOTOFAC T AIDS

Howard W. Sams & Co., Inc. have prepared three new service information folders which are available without charge to all radio servicemen.

The first of the folders is a complete cumulative index to more than 1000 postwar radio receivers, combinations, record changers, recorders, and sound amplifiers. The second folder is designed for "Photofact" subscribers and describes five simple ways to file the folders. The third folder is a specimen "Photofact" folder covering a popular radio-phonograph combination.

All three of these servicing aids are available without charge to radio servicemen and may be obtained from local parts jobbers or by writing direct to Howard W. Sams & Co., Inc., Indianapolis 6, Indiana.

## CONDENSER CATALOGUE

The new Pyramid Electric Company catalogue, J-4, is now available for distribution to those requesting a copy.

The new catalogue lists a wide variety of d.c. dry electrolytic condensers in cardboard or metal containers. Capacities of the units range from 5  $\mu$ fd. to 2000  $\mu$ fd. at voltages of from 6 to 600 working volts.

A special section of the catalogue is devoted to the company's new "Twist-Mount" line of condensers and includes capacity, working voltage, can sizes, physical dimensions, and prices for the entire line.

Copies of catalogue J-4 may be secured from Pyramid Electric Company, 155 Oxford, Paterson, New Jersey.

## SELENIUM RECTIFIERS

Selenium Corporation of America has recently issued a series of data sheets covering characteristics, applications, and design factors of the company's line of selenium rectifiers.

Included in the listing are instrument rectifiers, selenium barrier-layer cells for replacement in photoelectric radio-phonograph sets, and power rectifiers. Complete data on all of these types is given in such a form as to make the bulletin of value to design engineers.

Copies of these data sheets may be secured by writing Selenium Corporation of America, 2160 E. Imperial Highway, El Segundo, California.

## SPEAKER DATA

Complete data on 52 types of PM speakers, 54 types of electromagnetic speakers, and 20 types of transformers are included in the new 4-page

bulletin just issued by Permoflux Corporation.

The data supplied includes characteristic specifications for all types, sizes, flux density, voice coil diameters and impedance, watts, dimensions and recommended transformer sizes. In addition, transformer specifications include primary and secondary impedance, primary d.c., and ma., watts, and application data.

The bulletin is available free of charge from Permoflux distributors or from Permoflux Corporation, 4900 West Grand Avenue, Chicago 39, Illinois, or 236 South Verdugo Road, Glendale 5, California.

## FM TRANSMITTERS

The Broadcast Equipment Section of Radio Corporation of America is now offering an 8-page booklet covering their 250 watt, 1 kw., and 3 kw. FM transmitters to FM station owners and prospective owners.

All of the transmitters featured in this booklet are in stock and ready for immediate shipment. This line includes the BTF-250A, the BTF-1C and the BF-3B. Details about the RCA lightweight "Pylon" antenna are also given.

Copies of this booklet may be obtained from the Broadcast Equipment Section, Engineering Products Department, Radio Corporation of America, Camden, New Jersey.

## RESONANT RELAYS

The newly published catalogue sheet No. 116A contains complete information on the new Stevens-Arnold resonant relays.

Designed for remote control applications, the new resonant relays have been extended in range downward to 20 c.p.s. The line includes a 60 c.p.s. unit as a standard model. This particular 60-cycle relay is useful because of the general availability of that frequency.

A copy of catalogue sheet No. 116A will be forwarded to those writing Stevens-Arnold Inc., 22 Elkins Street, South Boston 27, Massachusetts.

## HAM BOOKLET

A new technical reference folder, designed especially for the nearly 100,000 radio hams in this country and containing a roundup of tube information, some of it never before published, has just been issued by the RCA Tube Department.

Titled "Headliners For Hams," the new folder is a combination technical bulletin, price list, catalogue, and sales brochure. It contains design information and covers a selected group of

TRIPLE BONUS...TRIPLE BONUS

the GREATEST--

yes, the GREATEST--  
TEST EQUIPMENT story ever told

1000 pieces of LATEST MODEL, Standard Brand Test Equipment to be sold this month. TUBE CHECKERS, SIGNAL GENERATORS, OSCILLOSCOPES, VTVM's, MULTITESTERS, etc.

LABORATORIES, SCHOOLS, RADIO DEALERS, SERVICE MEN, HAMS, EXPERIMENTERS, STUDENTS:

Get a TRIPLE BONUS on EACH piece of equipment valued at \$40.00 or more. Just fill out the coupon below. Act now!

*Buy for cash, on time-payment plan, or Radiomart lay-away plan*

# Radiomart

INC.

Dept. RNA  
149 Riverdale Ave.  
Yonkers, New York

I am interested in learning more about the greatest test equipment story ever told. Please send details of your great triple-bonus plan. I am particularly interested in buying the following equipment:

Name .....


Address .....

- |                                       |                                       |
|---------------------------------------|---------------------------------------|
| <input type="checkbox"/> Laboratory   | <input type="checkbox"/> Service Man  |
| <input type="checkbox"/> School       | <input type="checkbox"/> Ham          |
| <input type="checkbox"/> Radio Dealer | <input type="checkbox"/> Experimenter |

October, 1947


## Tops for FM

STANDARD BROADCAST  
AND SHORT WAVE

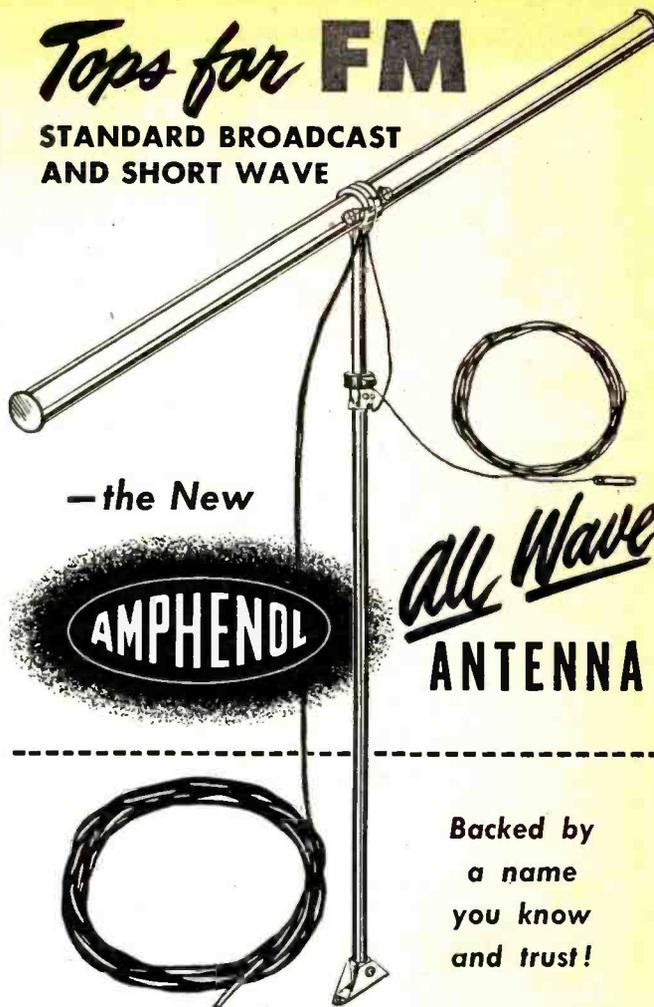

*Backed by  
a name  
you know  
and trust!*

- In actual tests, over the 500 kc-108 mc frequency range, the new Amphenol All-Wave Antenna out-gains the best double doublet. It assures interference-free reception, even in areas of low signal strength.
- The All-Wave Antenna combines a horizontally polarized FM dipole with a 65-foot copper wire antenna for standard broadcast and short wave. A special wave filter channels energy to receiver input. A leadin of 52 ohm coaxial transmission line reduces interference to the minimum.
- The All-Wave Antenna is individually packaged for unit sale with installation instructions, all hardware (except guy wires), and a guy wire clamp.

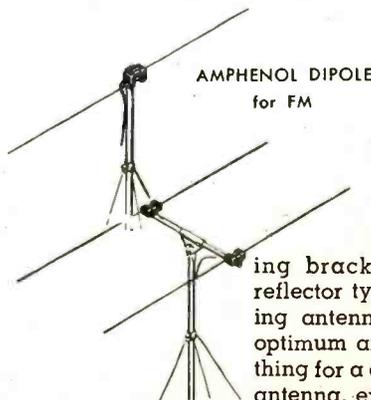

- Amphenol dipoles, and reflector arrays, build up ample gain for finest reception of FM. Efficient, even in areas of low signal strength, they virtually eliminate multipath reception. Mounting bracket and masthead (of reflector types) swivel, thus allowing antenna plane to be tilted to optimum angle. Kit contains everything for a complete 88-106 mc band antenna, except guy wires.

Amphenol Dipole Antennas are available now thru your jobber, or get prices and technical data by writing direct.

**AMERICAN PHENOLIC CORPORATION**

1830 SOUTH 54TH AVENUE • CHICAGO 50, ILLINOIS

COAXIAL CABLES AND CONNECTORS • INDUSTRIAL CONNECTORS, FITTINGS AND CONDUIT • ANTENNAS • RADIO COMPONENTS • PLASTICS FOR ELECTRONICS

**YOU  
CAN'T MATCH  
THESE SENSATIONAL  
VALUES!**



**THE "MIKE" BUY OF  
THE YEAR!**

Astatic crystal microphone complete with stand and 7 feet of crystal microphone cable. May be used either as a hand- or desk-type unit. . . . . **\$3.95**

**EIMAC 304TH X'MITTING TUBES**

Brand new! These \$50 tubes at an amazingly low price. Filament 25 amps at 5 volts—12.5 amps at 12.5 volts—3000 plate volts—300 watt plate diss.—while they last. . . . . **\$6.95** only.

**PHONO MOTOR AND CRYSTAL  
PICK-UP**

Build your own record player! "ALLIANCE" motor with 9" flocked turntable PLUS astatic crystal pick-up. BOTH for only. . . . . **\$4.95**



**TUBULAR ELECTROLYTIC  
CONDENSERS**

All "name brands"! Fresh Stock!  
25 mfd.—25 volt—15c  
40-40 mfd.—150 volt—45c  
50-30 mfd.—150 volt—45c  
Mfd. by "C.D.," "SOLAR," "SPRAGUE,"  
30, 20-20 mfd.—150-25 volt—45c  
10 mfd.—450 volt—29c each  
FP can-type condenser—40, 20-100 mfd.—150-12 volts—59c each

**TUBES—TUBES—TUBES!**

All brand new! "Standard brands"—"R.C.A.," "SYLVANIA," "HYTRON," etc.  
6L6GA—\$1.10 each 6SG7—\$.59 each  
6V6GT—\$.69 each 35L6GT—\$.59 each  
117Z6GT—\$.89 each  
Kit of 5 AC-DC Miniature Tubes—A MUST at all times; an extraordinary value NOW!  
Kit includes one each of 12BA6—12BE6—12AT6—35W4—50B5. Complete kit for ONLY \$2.75

**AUTO VIBRATORS**

4 prongs—non-synchronous—manufactured by one of America's largest vibrator suppliers. Perfect for practically all "MOTOROLA" and "PHILCO" auto radios. . . . . each **\$1.19**

**BARGAINS IN P.M.  
SPEAKERS**

5" P.M. with "ALNICO V" Magnet. . . . . each \$1.39  
12" P.M. with "ALNICO V" Magnet. . . . . each \$5.95  
Will handle 8-10 watts.



**C. R. L. 1/2 MEG. VOLUME CONTROL**  
With long shaft and on-off switch. . . . . each **\$4.45**

All merchandise listed is **BRAND NEW** and **FULLY GUARANTEED**

Write for quantity prices. New bargain flyer due soon. Send us your name and address and we will send you a copy as soon as it's off the press.

**AUDIVIEW RADIO PARTS CO.**

325 CANAL STREET  
NEW YORK 13, NEW YORK

RCA's most popular amateur tubes. Information in the colorful three-page folder includes new ratings on the 807, 808, 810, 813, and 829-B; new operating conditions for frequency doublers; and new data on modulators.

The folder is available without charge from RCA tube distributors or from the Commercial Engineering Section, Tube Department, Radio Corporation of America, Harrison, New Jersey.

**NEUTRALIZING CONDENSERS**

A four-page folder describing the new NZ-10 Neutralizing Condenser has been released by The Hammarlund Manufacturing Company Inc. and is now available for distribution.

The new NZ-10 unit replaces the company's N-10 condenser which is no longer being manufactured. Application data, construction details, and features of the NZ-10 are included in the folder.

Copies of the booklet are available to manufacturers, experimenters, and amateurs who make their request to The Hammarlund Manufacturing Company Inc., 460 West 34th Street, New York 1, New York.

**IMPEDANCE VECTORGRAPH**

A leaflet, "Sound Advances," which describes a newly developed Impedance Vectorgraph is now available from Sound Apparatus Company of New York.

The laboratory instrument described in this four-page leaflet is designed for measuring the input impedance of loudspeakers, microphones, headphones, pickups, recording heads, transmission lines, filters, transformers, etc.

A functional diagram and complete specifications on the Impedance Vectorgraph are included in the bulletin which may be obtained from Sound Apparatus Company, 233 Broadway, New York 7, New York.

**POWER SUPPLY BULLETIN**

Carter Motor Company of Chicago, manufacturers of rotary electric power supplies for radio communications equipment, have just released their latest sales bulletin, No. 447-J.

This bulletin illustrates many models, including the company's Super Dynamo, the Super Converter, the Multi-Output Dynamo, the Carter Genemotor, and the Magmotor.

In addition, the bulletin includes graphic presentation of voltage input and output, and outstanding features of each of the previously mentioned products.

Copies of Bulletin No. 447-J may be secured by writing Carter Motor Company, 2664 N. Maplewood Avenue, Chicago, Illinois.

**RESISTANCE STANDARDS**

Rubicon Company of Philadelphia has recently published a new 12-page illustrated bulletin which is now available for distribution.

Bulletin No. 100 describes in detail the company's complete line of re-

**NOW AVAILABLE!  
Full Range Reproduction**



A revolutionary development in amplifiers cleverly designed to defy obsolescence and amazing in its performance. New circuits, new materials and new processes are actually combined in this one amplifier to produce the most satisfying musical amplifier the world has ever known. If you are one of those discriminating persons for whom anything less than the best is a disappointment, you are one for whom the ACA-100DC was designed. Send for technical literature.

**AMPLIFIER CORP. of AMERICA**

398-2 Broadway  
New York 13, N. Y.

**A CAREER WITH  
A FUTURE!  
TELEVISION**

Shop Work • Shop Techniques • Theory  
**FULLY EQUIPPED LABORATORIES**

- RADIO SERVICE & REPAIR
- F. M. & TELEVISION
- TRANSMITTER COURSES  
Preparing for F.C.C. LICENSES
- RADIO TECHNOLOGY  
A Junior College Level Course preparing for positions in Radio-Electronic Engineering Field.

Morning • Afternoon • Evening Classes  
**MODERATE RATES • INSTALLMENTS**

**Available Under G. I. Bill**  
Come In and See Our Students at Work

**DELEHANTY SCHOOL OF**  
**RADIO • ELECTRONICS • TELEVISION**  
105 East 13 St., N. Y. 3, N. Y. • Dept. S.  
LICENSED BY STATE OF NEW YORK

**STONE • COLOR  
PERFORMANCE  
St. Louis  
RUGGED MIKE**



New! ST. LOUIS is ready with a really rugged dynamic microphone that will last a lifetime, for all component parts are replaceable. Range: 40-9000 cycles, ± 4 db. Variable impedance output adjustable by switch to low, 200, 500 or high impedance. 15 ft. double conductor shielded cable. Alnico V magnet. Use in or out doors in all weather, rain, snow, coastal regions, tropics, salty atmosphere, rough and extreme conditions. May be dropped successively without failure. Immediate delivery in grey, maroon, green, blue, chrome. Ask your dealer or write today for full details.

Licensed under U. S. Pats. American Tel. & Tel. Co. and Western Elect. Co., Inc.

**St. Louis Microphone Company**  
2726-28 Brentwood Blvd. St. Louis 17, Mo., U. S. A.

sistance standards and resistance bridges. Operation, application, construction, and other pertinent data is furnished on Wheatstone, Kelvin, Mueller and Limit bridges which are available in a variety of models for laboratory, plant, and field use.

Standard resistors of the Bureau of Standards and Reichsanstalt types, standard shunts, and a wide range of decade resistance boxes are also described. Individual decade resistors suitable for use as components in equipment are also listed.

Copies of Bulletin 100 will be sent upon request to *Rubicon Company*, 3666 Ridge Avenue, Philadelphia 32, Pa.

-30-

### Spot Radio News

(Continued from page 18)

until final tariffs are filed." When that will be is anybody's guess.

**PROGRAMMING IN TELEVISION** continues to be highly experimental and often unsatisfactory—but our bet is that the boys will keep pitching around until they hit on some very successful material. Latest try was the first art telecast of Washington's world-famous National Gallery, late this summer. In black and white, television broadcast some of the Gallery's masterpieces with such clarity that still pictures were successfully taken and reproduced in newspapers the following day. Dramatization of the story behind one of the pictures was featured in the telecast, but some difficulty was experienced because three separate rooms had to be used. Critical comment: "As an experiment, the National Gallery's venture was fascinating, but the results did not prove that the medium was up to it," in the words of Jane Watson Crane, Washington art critic.

**ANOTHER PERMANENT ITEM** on the radio news roster, from the looks of things, will be what the National Association of Broadcasters and the Radio Manufacturers Association chose to call "freedom of communication" and the FCC terms "public service responsibility of broadcasters." Carrying the torch for the RMA-NAB groups is Judge Justin Miller, NAB president, whose stand on FCC's criticism of what goes on the air has been that any Federal interference would infringe on freedom of speech. Backing him up this summer were leading representatives of all U. S. media, meeting at NAB headquarters in Washington. Accepting invitations were such notables as the president of the newspaper publishers association, the publisher of *Collier's*, and representatives of books, movies, and radio. Supplementing the opposition to FCC was an affirmative attack by the RMA advertising committee, which recommended sponsoring another radio listener contest during National Radio Week, Oct. 26-Nov. 1. RMA

October, 1947

Here...  
At Last!  
AND WORTH  
WAITING  
FOR...

THE

New

# REKOKUT

MODEL T-12 12-INCH Dual-Speed  
TRANSCRIPTION TURNTABLE

Promised Since V-J Day



Professional Studio  
Performance at  
Home

Look AT THESE Features:



**TURNTABLE** . . . Lathe turned and balanced. Made of laboratory tested Aluminum Alloy casting.

**TURNTABLE SHAFT** . . . Ground to a micro finish and lapped into the bearing for a precise fit.

**CHASSIS** . . . Flush mount . . . Aluminum, ribbed L beam type rectangular dimensions easily fitted into a cut out motor panel.

**IDLERS** . . . Made of special Neoprene formula which gives maximum traction.

**MOTOR** . . . Constant speed fitted with REK-O-KUT exclusively designed motor pulley.

**MAINTENANCE** . . . Minimum attention due to self oiling features.

Sold by leading Radio Parts distributors  
and Graybar Electric Co.

PRICE \$79<sup>50</sup>  
NET


## REK-O-KUT COMPANY

146 Grand Street  
New York, N. Y.

Export Division  
MORHAN EXPORTING CORP.  
458 Broadway, New York, N. Y.

167

More  
MONEY  
in your  
POCKET

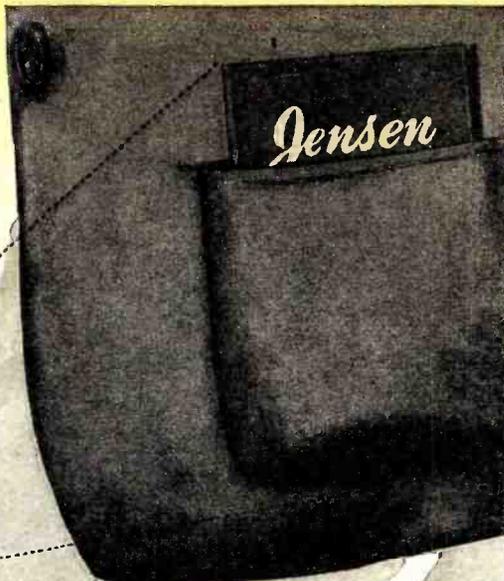

when you carry the handy Jensen Saleskit.

Radio Servicemen who take the Jensen Phonograph Needle Saleskit on service calls say they would not be without it. This handy kit, shown above, helps demonstrate fine needles, sells on sight, adds \$\$\$s to your income.

Contains 3 Jensen Concert Needles retailing at \$1 each, and 3 Jensen Genuine Sapphire Needles

at \$2.50 each. Needles are beautifully packaged. Adds profit to every call. What's more, Jensen phonograph needles augment your work, assure full, clear tone of the instruments you repair, make all records sound better.

Generous discounts to servicemen boost your income. WRITE TODAY for complete details.

JENSEN INDUSTRIES, Inc., 331 SOUTH WOOD ST. • CHICAGO 12, ILL.

## B19 TRANSMITTING and RECEIVING SET

Complete with spare parts..... **\$46.50**  
Less 12 volt Power Supply..... **39.95**  
A.C. Conversion Diagram..... **.50**



### A. C. METER

(Illustrated to left.)

125 volt scale luminous dial in metal case. Size: 9"x2 3/4"x3". Also two momentary switches, one SPST switch, and 100 OHM rheostat. **\$2.00**

### 0-500 MICROAMMETER

0-15 and 0-600 D.C. volt scale, luminous dial, with multipliers **\$2.50**

Resistor Asst.—100 assorted 1/4, 1/2, 1 and 2 watt, carbon and wire wound. **\$1.75**

### PAPER TUBULAR CAPACITORS:

.1 and .025 mfd. 500 volt..... 12 for **\$1.00**  
.1 mfd. 1000 volt..... 6 for **1.00**  
.1 mfd. 1500 volt..... 5 for **1.00**  
Electrolytic—2 mfd. 400 volt..... 5 for **1.00**  
Electrolytic—12 mfd. 50 volt..... 5 for **1.00**  
Electrolytic—32 mfd. 450 volt (large size)..... 5 for **1.00**

### VIBRATOR

6 volt, 4 prong—Popular replacement for more than 300 sets of different types. Size: 1 1/2"x2 1/2" **\$1.10** each; 5 for **\$5.00**.

WE CAN FURNISH ANY ITEM FOR B19 SETS

25% Deposit required on C.O.D. orders.  
Shipped F.O.B. Lima, Ohio.

**FAIR RADIO SALES**  
223 S. MAIN ST. • LIMA, OHIO

## 2-WEEK DELIVERY!! ON TRANSVISION'S NEW 12" TUBE TELEVISION KIT

... THANKS TO BEACON TELEVISION'S FORESIGHT IN PLACING A LARGE ORDER FOR THIS "MIRACLE" KIT SEVERAL MONTHS AGO.

At only **\$289<sup>50</sup>**

You Get Larger Image Than In Sets Selling at \$500

Here is a television receiver with a 7 1/2"x10" screen—easy to assemble in about 20 working hours. Designed and constructed by Transvision engineers with the same technical skill which goes into their 7" kit.

- Just tally some of these features:
1. 12" magnetic type picture tube.
  2. Receives all television channels on the air with provision for factory to add new channels as they open at NO EXTRA COST!
  3. 4 mc band width for full picture definition.
  4. 9,000 volts second anode potential for brightness and contrast.
  5. Ratio detector for sound gives highest quality FM reproduction.
  6. 22 tubes and picture tube.
  7. Complete with antenna, tubes, pre-assembled and tuned R.F. Unit. . . . even solder!
- Kit comes with simple step-by-step assembly instructions. Factory guarantees clear, sharp reproduction comparable to sets selling at twice the price.

Here's a value you can't beat! Order now and be one of the first to have one of these beautiful, new Transvision sets. A \$25 deposit will assure you early delivery. Beautifully turned walnut cabinet available at \$44.95. 7" tube Transvision kit equipped with new FM sound available at \$169.50.

SEND FOR FURTHER DETAILS

**Beacon Television, Inc.**

Distributors for Transvision Television Products  
Department B

143 East 49th Street, New York 17, N. Y.

**DEALERS:** We invite your inquiry regarding an attractive money-making deal we are prepared to make with live-wire radio men!

will cooperate with the NAB Association of Women Broadcasters which conducted the contest last year. . . . Meantime, the industry's opposition to FCC "censorship" is concentrating on an attack on FCC's "Blue Book" criticizing some of the Commission's attitudes toward broadcasting generally and commercials in particular.

**SUMMING UP** for the industry, Judge Miller says: "Within the proper scope of its authority, the Commission is performing a tremendous task well, working with me and with the broadcasters, generally, on a very friendly and cooperative basis." But he adds: "While it is entirely proper and desirable for informed critics to analyze and challenge practices and performances of radio broadcasting, it is an entirely different proposition for a government agency which is engaged in 'regulation of interstate commerce' to be stirring up such criticism. It is as if the Postmaster General, in administering the law concerning the use of second-class mail privilege, by magazines and newspapers, should issue a 'report' condemning the contents of such publications and urging critics to attack them. If additional regulation is necessary," he said, "it should come from the industry itself and from the listening audience, in the manner similar to the practice followed in the press, the motion picture industry, and in the professions." Adding that the large majority of Americans like present-day broadcasting as it is conducted in this country, he stated that "Americans do not want government-operated broadcasting or governmentally controlled broadcasting."

**ON THE PRODUCTION FRONT,** business continues to be good. Latest tabulations show that a total of 8,610,644 radio and television receivers were produced by RMA members during the first half of the year. More television receivers were produced in June alone than in the entire year 1946, and the half-year output of FM-AM receivers was up two-and-a-half times that of the previous year. June's record output of 11,484 television receivers brought the semi-annual total to 46,389 as contrasted with only 6476 all during '46. . . . A total of 445,563 FM-AM receivers were produced by RMA member-companies during the first six months of 1947 as compared with only 181,485 in '46. June's output was off to 76,624 as compared with 84,507 in May. This was a seasonal decline that had been anticipated. . . . FM-AM's are on the upgrade in another respect—the percentage of these receivers to the total set production rose from 1.4 to more than 5 during the first half of the year. Consoles were far in the lead in the FM-AM field, but table models are now showing gains. A total of 361,689 radio-phonograph combinations, 15,615 straight consoles, and 68,259 table models were produced during the six month period. . . . Auto radio produc-

tion during the same period also exceeded the 1946 total. In the first six months of this year, 1,208,159 were built; 1946 total—1,153,458.

**IN CASE YOU** didn't hear about it, radio played a leading role in all of the summer record flights, and was a special feature in the light plane field. Tiny, powerful radio units were used in the Piper Supercruisers round-the-world Evans-Truman jaunt. An unusual aspect of the equipment was provision for v.h.f. transmission. A Bendix v.h.f. transmitter was installed, making possible not only line-of-sight, static-free two-way transmission but also use of ground controlled approach radar equipment here and abroad. Lightness was another feature. The pilots specified a maximum of forty pounds. Bendix filled all requirements—radio communication and navigation equipment, a range and broadcast receiver with crystal-controlled spot tuners for reception of 6440 kilocycles and 2870 kilocycles, direction-finding facilities, medium frequency transmitter and the v.h.f. and kept the total weight at 26.87 pounds. The outfit enabled each flier to do a rounded job of radio navigation. They could transmit over long distances by using the 6440 kilocycle channel, using either voice or telegraph. On the receiving end were Army, Navy and CAA stations abroad. By using spot-tuners on the PAR-70 receiver, they got the benefit of two extra frequency channels—2870 kilocycles and 6440 kilocycles. In addition to the tunable frequencies normally used on this type of small receiver, this unit also covers the 200-400 kc. and the 550-1500 kc. bands. This latter channel is used by broadcast stations. By using a rotatable loop antenna, the two bands were employed as a radio compass for direction finding. The 2870 and 6440 kilocycle frequencies provided by the spot tuners were also used to pick up control towers and enroute stations and were available for GCA. The 200-400 kilocycle tunable frequency range permitted flying the airways radio ranges in continental United States.

-30-



October, 1947

# GOVERNMENT SURPLUS

We have on hand a large selection of Radio and Electronic Equipment purchased from the United States Government, and solicit your inquiry on practically any equipment or component parts used by the Army or Navy. Listed below are only a few of the many items we now have in stock. Send for flyers on items not listed.

Scope, 5", 110 V, 60 cycle input. Control unit BC-1266, 15 Tubes including 5CP1. Has all power supplies built in except for 300 Volt amp. B. voltage agc. .... \$40.00  
Indicator I-221A. Uses Selsyn with indicating rose, 100TH power tube, assorted breakers, high voltage condensers, etc. Good for antenna and transmitter control and remote modulator basic kit, 110 V, 60 cyc. .... \$27.50



## SAVE EIGHT DOLLARS!

Purchase both of these packed in original shipping case and crate. Shipping wt. 400 lbs. .... \$59.50




SCR-274-N Receiving and Transmitting Set. As illustrated, set consists of one each of the following: 4-5.3mc

BC-457A and 5.3-7mc BC-458A transmitters; 3-6mc BC-454A; 190-550kc BC-453A; 6-9.1mc BC-455A Receivers. Also BC-456A Modulator Unit. Includes all of the tubes required, as well as four dynamotors, control box and Antenna Tuning Unit with 0-10 Amp. RF Meter and vacuum condenser. Everything necessary for an Operating Installation .... \$39.95

SCR-625 Mine Detector. Useful for locating metals buried in the ground. Uses 1000 cycle balanced search coil. Sensitive. Will detect slightest unbalance. Plumbers, prospectors, miners, all need this very useful easy to use metal locator. Complete with carrying case .... \$49.95  
Replacement search coil for above 4.95



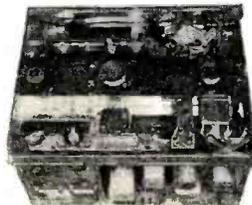Handset TS13. 200 ohm carbon mike and 2500 ohm ear phone with butterfly switch. Has 6 ft. rubber cord with 1 each PL55 and PL68 plugs attached. Bakelite case, light weight. .... \$3.95



SCR-522 Receiver Transmitter. Get this swell VHF Transceiver. One of the finest and most economical 2-Meter rigs you can buy today. Now available for

a small fraction of the original cost. Covers 100-156 MC. Ideal for aircraft communication, airport control and taxi-cab radio. Furnished with 17 tubes. Price .... \$19.95

BC-348 Receiver. 6 Band, 8-Tube, Superhet. Covers 200 kc to 18.0 mc (excluding BC). Complete with tubes and 24 V dynamotor. .... \$49.95

Plate Transformer. 2880 VCT at 1.362 KVA. Variable tap primary 105/115/125 volt input. Cast iron end bells. Flash over arrester. Bendix A 27050. .... \$22.95  
Filter choke 8 H @ 700 MA insulated for 4 kv DC, Western Electric, enclosed .... \$11.59  
300 ohm Twin-lead transmission line—ft. .... \$0.03  
Jeweled lamp assembly. 1" panel mount. Drake type 75. .... \$0.29  
Message Holder. Excellent for station logs, regular letter size 8 1/2 x 11" with extra clip for holding spare sheets, also protective cover. Reg. Signal Corps type .... \$0.95  
Spark Plug Suppressors—6 for .... \$0.35  
Box of 50 .... \$2.25  
Electrolytics, 10x10x10 @ 400 V Mallory F-P can. .... \$0.89  
Neon Bulbs, GE 1/4 W 115 V Bayonet or Candelabra base—box of 10 .... \$1.20  
SHURE featherweight, Crystal Pick-ups. New .... \$2.95  
RG8/U Coax. 52 ohm. 50' and over—per foot .... \$0.07  
Empire cloth. .015" thick. Westinghouse Tuffnell. sq. yd. .... \$0.65  
Resistors. 1/2 Watt. Kit of 100. Assorted .... \$2.49  
Relay, 24 Volt, 60 Cycle Coil. Contact 15 Amp. DPST. Normally open. Ward Leonard .... \$1.95  
Relay, 2.5 V or 5 V Coil. 60 Cycle. Contacts 150 Watts SPST. Guardian Elec. .... \$1.25  
Whip Antenna. 3 removable sections to make 9 ft. Whip w/insulated Mast Base Type MP-22-A. Constructed to swivel when hit by obstruction. Excellent for Mobile Antenna .... \$5.50  
Linesman's pole climbers with straps and pads .... \$4.50  
Safety belt with strap. State belt size wanted .... \$5.75  
Terminal strips. Molded bakelite 16 screw terminals. 8 circuits. 5 1/4" long x 2" wide. Barriers between terminals. Mfg. GE—10 for .... \$1.20  
Micropress sleeves. 19-20 and 22 wire. Box of 250 .... \$0.49  
Telephone Switch board lamps 32 and 40 V. T2 style. Box of 100 .... \$2.95  
HS-30 Headset Ear Inserts. Box of 20 .... \$0.39  
10 Amp. Cartridge Fuse 250 V 10 for \$0.39  
45 V BA-26 Heavy Duty "B" Batteries 8x4 1/2 x 7 1/2". Date of Mfg. May 1945. Carton of 4. .... \$1.98  
Lots of 100. .... \$0.25  
6 V Lantern Battery. 2 1/2 x 2 1/2 x 3 1/2". Date of Mfg. June 1945. .... \$2.75

Be prepared for Electrical Fires — Get our 1 qt. Carbon Tet. Fire Extinguisher, complete with bracket. Stempel. Wgt. 8 lbs. New. .... \$9.89


## PHOTOGRAPHIC PRINT PAPER

4x5 single wt. glossy white, Cykon. Contrast 0, 1, 3—1 gross. .... \$0.79  
8x10 single wt. glossy white, Cykon. Contrast 2—1 gross. .... 1.89  
Prices on Print Paper only are postage prepaid. Paper outdated but good. Satisfaction guaranteed or money refunded.

Prices F.O.B. Baltimore. Minimum Order \$2.00. 10% Deposit on C.O.D. orders.


**The Abell Distributing Company**  
5 E. Biddle St. Baltimore 2, Md.

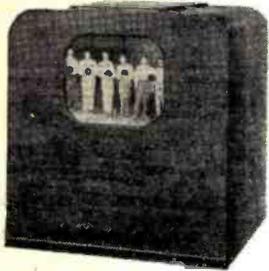10 inch  
**TELEVISION**  
now **124.50**  
LESS  
TUBES



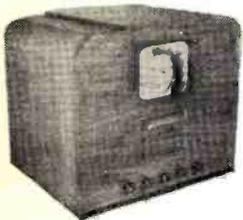**TEN INCH TELEKIT \$124.50**

Easy-to-build Telekit is a big ten-inch television kit comparable to television sets costing THREE TIMES ITS PRICE when assembled. Complete, easy-to-follow instruction books show every step of the way with photographs, diagrams and detailed instructions. Thousands of students in leading schools complete during training. **GUARANTEED** first quality parts and **GUARANTEED** to work. Telekit Ten, \$124.50, less tubes. Cabinet, \$29.50. Complete tube kit, including RCA 10BP4 (ten-inch picture tube), \$64.50.



**SEVEN INCH TELEKIT \$77.50**

Telekit Seven is an easy-to-assemble television receiver kit that is **GUARANTEED** to receive sound and video of superior quality. Complete instruction books with pictures, diagrams and other illustrations show every step of the way. Pre-tuned I.F. coils and simple circuit make the Telekit Seven easy-to-assemble by anyone. Telekit Seven \$77.50, less tubes. Cabinet \$24.50. Tube kit complete with RCA 7GP4 (seven inch picture tube) \$42.50.

Authorized Telekit Service Stations in every television city to help you. Telekit is easy-to-assemble by anyone. Ask to see Telekit at your jobber or write to us for **FREE BOOKLET** and information.

**TELEKIT**

**ELECTRO-TECHNICAL INDUSTRIES**  
121 NORTH BROAD STREET PHILADELPHIA 7, PA.

**What's New in Radio**

(Continued from page 86)


These resistors are completely sealed and insulated by molded plastic. Leads are soft copper wire, hardened immediately adjacent to the resistor body, strongly anchored, and hot solder coated. Each unit is individually marked with resistance value and wattage in addition to the color code.

*Ohmite Manufacturing Company*, 4980 West Flournoy Street, Chicago 44, Illinois, will forward bulletin on these resistors and advise where they may be purchased if you will drop them a line asking for the "Little Devil Bulletin."

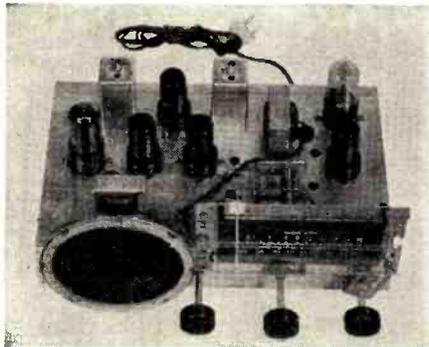**B.C. AND S.W. KIT**

The *Radio Craftsmen* of Chicago are announcing a new radio receiver kit, the Model RK6S, which covers the standard broadcast band from 550 to 1600 kc. and short-wave bands lying between 5.5 and 18 mc.

This receiver operates on either a.c. or d.c., 105-125 volts. The set



uses six standard tubes which are furnished with the kit. The kit has been engineered to produce good results whether the unit is assembled by a novice or an experienced radio-man.

A complete 20-page instruction booklet accompanies the kit. Nine photograms showing various assembly steps are used to illustrate the text material. Assembly details are given in easy-to-follow numbered steps and a large-sized blueprint of the circuit is also included in the instruction manual.

The *Radio Craftsmen*, 1341 South Michigan Avenue, Chicago 5, Illinois, will supply additional information on the Model RK6S to those requesting it.


**V.H.F. CRYSTAL**

*Bliley Electric Company* of Erie, Pennsylvania, has just announced a new v.h.f. crystal designed for the 15-megacycle range.

This new unit, the Type BH6, employs a paper-thin quartz plate operating on third, fifth, and seventh overtones. The crystal, lapped as thin as .004", is processed to micro-tolerances and silver plated to insure long term precision. A pair of ceramic rings clamp the delicate plate rigidly in position. Recommendations covering oscillator

**TRANSMITTER KIT**

**\$12.95**

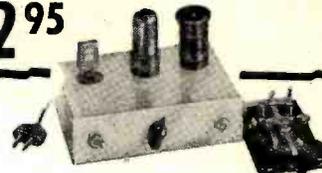

APPROX. 10 WATTS INPUT

**COMPLETE** with built in power supply for 115V AC and DC


Key (as Illustrated) with Plug ..... \$1.25 additional  
Extra coil ..... .75  
Crystal mounted, within 10 KC of freq. .... 1.50 additional

Parts all mounted on metal chassis. Just a few wires to connect. Ready to operate in fifteen minutes. Plug in coil provided for either 80 or 40 meter band. State choice. This transmitter capable of covering distances of 500 miles or more. We will assemble and test this kit for \$2.00 additional.

Terms: 20% deposit, balance C.O.D.

**TEK-KIT LABS**

P. O. BOX 6,  
Kew Gardens 15, N. Y.

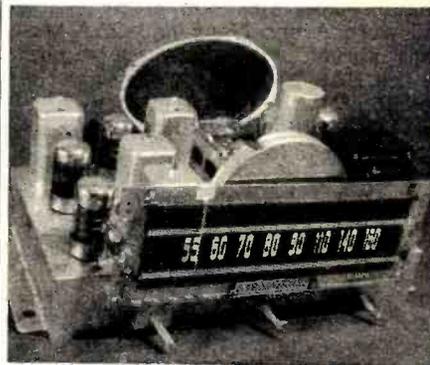

**HERE AT LAST**

A SUPERBLY DESIGNED A.C. SUPERHETERODYNE, engineered to meet the exacting requirements of the radio man who knows quality.

Adjustable iron core R.F. and Ant. coils provide for perfect tracking which accounts for the very high sensitivity and excellent selectivity obtained.

Latest type Loctal tubes used include 7A7 R.F. Amp.; 7Q7 Converter; 7A7 I.F.; 7B6 2nd Det, AVC & 1st AF; 7B5 output and 5A2A Rectifier.

Beautiful 8 3/4" edge lighted Slide Rule type dial assembly. Escutcheon plate included.

All parts guaranteed to be free of defects. Complete kit includes full set of tubes, 8" PM speaker, all transformers, coils, resistors, condensers, wire, etc. Also complete assembly instructions and diagrams.

Kit as described, wired and tested . . . \$35.90  
Radio completely wired and tested . . . \$4.50

Quantity prices supplied on request. 20% deposit with order. Balance C.O.D.

**ROY A. BREADY & CO.**

108 So. Delacey St. Pasadena 2, Calif.

**RADIO MEN**

Write for Giant  
**BARGAIN CATALOG**  
**BUYERS SYNDICATE**

786 Carew St., Springfield 4, Mass.

**ELECTRICAL TRAINING**

Intensive 32 weeks' residence course in fundamentals of industrial electrical engineering, including radio, electronics. Prepares for technician, engineering aides. Approved for veteran training. 54th year. Catalog.

**BLISS** **ELECTRICAL SCHOOL**  
7898 Takoma Ave.  
Washington 12, D. C.




**RADIO NEWS**

circuits best suited for optimum performance will be made by the manufacturer on request. Address inquiries on this new unit to *Bliley Electric Company, Erie, Pa.*

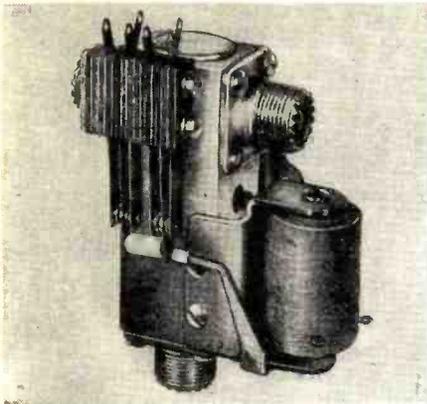**NEW RELAY**

*Advance Electric & Relay Co.*, of Los Angeles, California, is currently manufacturing a new relay designed for s.p.d.t. switching of 50 ohm coaxial lines.



Known as the *Advance Series 7200 a.c.* or *8200 d.c.*, this relay features an inspection port at the top of the unit for easy access to the internal  $\frac{1}{4}$ " silver contacts and  $\frac{3}{16}$ " silver contacts for simultaneous control of indicator lights and other associated circuits.

*Advance Electric & Relay Co.*, 1260 West 2nd Street, Los Angeles, California, will supply full details on request.

**TEST RECORD**

Of special interest to servicemen engaged in the adjustment and testing of record changers and coin operated phonographs is the new test record just announced by *Walter L. Schott Co.* of Beverly Hills, California.

The new *Walsco* standard test record embodies a patented principle which permits accurate adjustment to the proper set-down and tripping position of the pickup through the use of a series of three consecutive tones.

**Fixing Radios the Old Hard Way?**



**Throw Away Your Old Instruments**  
**Remarkable New STETHOSCOPE Method**  
**Guaranteed to Lick Toughest Jobs**

Why let old-fashioned methods and equipment hamper your servicing ability? Thousands of radio men—many with little experience—are already fixing radios this remarkable "automatic" way. It's as simple as A.B.C., because *Stethoscope Servicing* is the newest, most basic method yet devised to simplify all repairs. Right at this very moment, you probably have on your bench one of those familiar "stumpers" for repair. But now you can fix these "headaches" in a jiffy—the *Stethoscope* way. **STETHOSCOPE SERVICING** is guaranteed to speed up and improve your servicing ability, or your money will be refunded. You owe it to yourself to find out how you, too, can begin cashing in. Don't delay! Get the **FREE** bulletin; just send coupon on penny post card today!

**Amazing — Sensational — New Pocket STETHOSCOPE**

Think of it—a complete A.C. operated *Stethoscope* so compact it fits into the palm of your hand or can be tucked away in your pocket. It's the only pocket-sized instrument of its kind made today. Years ahead in design, the new TS-5 gives you advanced features. Only 2 3/8" x 4 1/2" x 8 3/4"; weighs only 4 lbs. Has line isolating transformer. 4 ultra-modern tubes in new circuit. Converts your present volt-ohmmeter into R.F.—V.T.V.M. and output meter. Full 3" PM speaker. Thermal-rate-of-flow ventilation permits compact size. Send coupon today. Learn how you can obtain this remarkable instrument for only... **\$28.95**

**OTHER MODELS AVAILABLE**  
*Stethoscopes* are available also in standard-sized battery-operated and A.C. models, priced from \$9.85 to \$34.95. Just send coupon on penny postcard for large illustrated bulletin.

Sold by leading Radio Distributors. A few choice territories still open.

BULLETIN  
**FREE**



**FEILER ENGINEERING CO.**  
 422 So. Dearborn St.  
 Chicago 5, ILL., Dept. 1H7

Rush free bulletin on *Stethoscope Servicing*.

Name .....

Address .....

City ..... State .....

**U. S. GOVERNMENT SURPLUS  
 RADIO BARGAINS**

MODEL AN-PRS-I  
**NEW  
 MINE  
 DETECTORS**

EACH  
**\$9<sup>95</sup>**



**3-TUBE AMPLIFIER**

Using 2—1N5 and 1—1G6.  
 Complete with tubes.... **\$2<sup>95</sup>**

**BEACON  
 RECEIVERS**

BC-1206-C

NEW ..... **\$4<sup>95</sup>**

USED ..... **\$2<sup>95</sup>**

GOOD CONDITION

12 OR 24 VOLT **49c**  
**Dynamotors** EACH

**VITAMIN "Q"  
 CAPACITATOR**

Special Impregnated  
 Highly Efficient

2X2 MFD 600 V.D.C.  
 EACH ..... **79c**

**B.D. 77 DYNAMOTORS**

12 V. input; 1000 V. output, 6 V. input, 450 V. output, 350 MA. **\$4<sup>95</sup>**  
 EACH

**INVERTERS**

27 V. input, 115 V. 400 cycle output at approximately 1500 watts. **\$7<sup>95</sup>**  
 NEW, EACH .....

**HIGH VOLTAGE  
 TRANSFORMERS**

90 V. Primary, 6400 V. Secondary, 100 Mills. **\$1<sup>95</sup>**  
 NEW, EACH .....

**EAR PHONES** **50c**  
 USED—IN GOOD CONDITION SET

**12 MFD, 150 V. SMALL  
 SOLAR or MALLORY**

DOZEN ..... **\$1<sup>50</sup>**


**Co-Ax Connectors**

M359—Right Angle. Package of 10 ..... **79c**

**GRAB  
 BOX**

Approximately 10 lbs. of miscellaneous radio parts. All usable—All new.

BOX EACH ..... **\$1<sup>00</sup>**

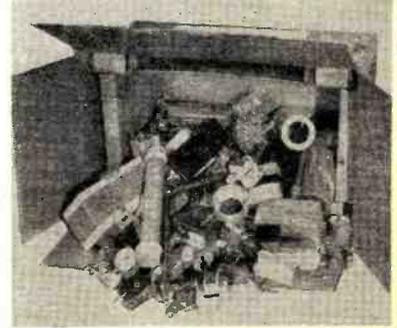

All Orders F.O.B. DETROIT, Shipped RAILWAY EXPRESS

No order under \$5.00—Please send check or money order. Orders shipped C.O.D. subject to 25% advance deposit.

**RADIO CENTER**

2530 E. DAVISON AVE. DETROIT 12, MICH.

Buy Our Coil Kit and  
**BUILD YOUR OWN  
HIGH QUALITY 7 IN.  
TELEVISION SET**

for approx-  
imately **\$125<sup>00</sup>**


**THE HOME CONSTRUCTOR**

who wishes to build a television set able to receive 6 channels with FM sound, now has an unparalleled opportunity to use the best the market affords, at this **LOW TOTAL COST**, which **INCLUDES** purchase price of our

**Complete  
TELEVISION  
COIL KIT**

plus detailed Construction Manual for 20 tube, 7-inch Picture Tube Television Set, for

Only **\$23<sup>50</sup>**

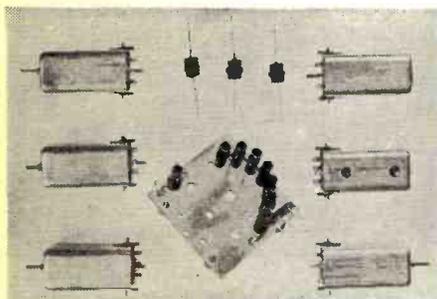

**LOOK AT THESE FEATURES!**

- Video IF Bandwidth of 4.25 MC that can operate ANY size picture tube with maximum resolution.
- Five stages Video IF, permeability tuned with sound and adjacent channel rejection traps, in shielded cans.
- 6 Channel RF Tuner, permeability tuned, mounted on switch assembly plate.
- FM Sound Discriminator for TRUE FM.
- Can provide Video Operation for 10, 12, 15 or 20-inch picture tube upon further construction.
- Video Peaking Chokes to maintain bandwidth.
- Detailed Construction Manual & Parts List with every kit.
- Continued Service Bulletins.



**SATISFIED CUSTOMERS WRITE**

"Excellent bandwidth with good trap rejection" . . .  
"Thoroughly pleased and satisfied with your coil kit."  
"This manual most complete description of television receiver I have ever seen."

**ORDER DIRECT OR THRU LOCAL DEALER  
TERMS**

Shipped Parcel Post prepaid on receipt of check or money order. Or P.P. Collect on receipt of 25% deposit with order, balance COD.

Manual Only, \$1.00 plus 15c postage. Television parts, Deflection Components, CR Tubes in stock. Send for free listing to Dept. J.

**RAY-LECTRON CO.**  
706 Tenth Avenue  
BELMAR, N. J.

The lead-in grooves are modulated from the outer edge of the record in a series of three consecutive tones. In testing the record changer, proper adjustment is attained when only two tones are heard.

Suitable for thousands of tests, the record is made of high quality material, scientifically designed, and provision made for flatness, concentricity, thickness, and accelerated pitch grooves.

Additional information will be supplied by *Walter L. Schott Co.*, 9306 Santa Monica Boulevard, Beverly Hills, California.

**TELEVISION KIT**

The *Telekit Sales Division of Electro-technical Industries* has just introduced a new seven inch television kit which contains all necessary component parts except tubes.

Pretested instruction books accompany each unit and explain every step of the assembly process. Photographs, diagrams, and full details put the assembly of this receiver within the range of any mechanically minded person.

The company is also marketing a ten inch kit which provides electro-magnetic scanning and focusing.

Full details, including prices, on these kits will be supplied by *Electro-technical Industries*, 121 N. Broad Street, Philadelphia, Pennsylvania.

**CRYSTAL CONVERTER**

Receivers designed to operate in the old FM band can now be converted to provide operation in the 88-108 mc. band through utilization of a new crystal converter which is being marketed by *Crystal Devices Co.*

Using germanium crystal diode units, this converter requires no power connections from the set. The antenna is connected to the unit and the output is wired to the antenna terminals of the receiver. Two screwdriver adjustments are used to set the semi-fixed tuning.

The converter is shipped, pretuned to the center of the new band, with complete instructions on installation and operation. Details may be secured by writing *Crystal Devices Co.*, P.O. Box 380, G.P.O., New York 1, New York.

**PICTURE TUBE MASK**

*Telectro Components* of Belleville, New Jersey, is offering manufacturers of television sets and equipment a new combination picture tube mask and protective plate made of optical plastic.

This new unit masks the image with an opaque white finish. Shaded corners are eliminated, allowing full view of the entire picture tube surface at the proper aspect ratio. The protective plate follows the contour of the picture tube surface. The complete unit allows the picture tube to be installed forward in the cabinet permitting a wider viewing angle and

**MORE FOR YOUR MONEY**

**PHONO AMPLIFIER**

3 Tube A.C.-D.C.

Volume and Tone controls; approx. 2.5 Watts output; uses 12SK7, 50L6, 35Z5



Kit Form	\$2.35
Completely wired and tested	2.85
Kit of 3 Tubes for above 12SK7, 50L6, 35Z5	1.95
5" ALNICO P.M. SPEAKER	1.45
50L6 OUTPUT TRANSFORMER	.55
SHURE GLIDER CRYSTAL PICKUP	1.95
ASTATIC L-70 CRYSTAL PICKUP	1.95
ALLIANCE PHONO MOTOR	3.25
RECORD PLAYER—ATTACH TO ANY RADIO, ALLIANCE PHONO MOTOR, ASTATIC CRYSTAL PICKUP, WALNUT FINISH CABINET	8.95
PORTABLE RECORD PLAYER KIT—3 TUBE PHONO AMPLIFIER, ALLIANCE PHONO MOTOR, ASTATIC CRYSTAL PICKUP, 5" ALNICO P.M. SPEAKER, SIMULATED LEATHER CARRYING CASE	17.95
ASSEMBLED AND TESTED	21.50
RECORD PLAYER KIT—Same as above but with WALNUT FINISH CABINET	15.50
ASSEMBLED AND TESTED	17.75
MAGUIRE AUTOMATIC RECORD CHANGER	13.95
V.M. AUTOMATIC MIXER-CHANGER	17.95

All Prices F.O.B. Our Warehouse N. Y.  
25% Deposit Balance C.O.D.

**RAYTONE ELECTRONIC COMPANY**

25A Frankfort St. New York 7, N. Y.

**RISCO HAS IT**

All Changers Brand New

**V. M. MIXER CHANGER**



PLAYS 10" and 12" Records at the same time.

SEEBURG. \$19.50  
DETROLA. 13.75  
OAK 2 POST 17.00  
G.I. 14.50  
MAGUIRE. 10.95  
AUTOMATIC STOP WALNUT BASE \$4

**\$15.50**

SINGLE POST V.M. MIXER, MODEL L-400, \$20.00  
Also Easily Attached to Any Radio or CAN BE USED WITH AMPLIFIER BELOW

**PHONO AMPLIFIER**



3 TUBE AC-DC

Wired Vol. & Tone Control

**\$2.95**

Uses 12SK7, 50L6, 35Z5 Complete with 3 tubes and 5-inch speaker. Wired and tested \$7.50

DIAGRAMS for any radio sent prepaid 50c ea. to cover cost of printing & mailing.  
25% on C.O.D. orders. Free Catalog. Orders Filled as Received. BE. 3-8554  
Free Catalog Just Out. We Specialize in Mail Orders.

**RISCO ELECTRONICS  
WHOLESALE DISTRIBUTORS**

22 Warren St., New York 7, N. Y.

**LEARN RADIO!**

IN ONLY 10 MONTHS  
**PREPARE FOR A GOOD JOB!**  
COMMERCIAL OPERATOR (CODE)  
BROADCAST ENGINEER  
RADIO SERVICEMAN

Television Servicing—15 Months

(Approved for Veterans)  
SEND FOR FREE LITERATURE  
**BALTIMORE TECHNICAL INSTITUTE**  
1425 EUTAW PLACE, BALT. 17, MD.

**ROTA-BASE**

NEW HANDY LAB. DIAL actually gives a "prong" picture of radio tube connections. Simply turn the dial to the tube number desired on the ROTA-BASE and complete correct connections are instantly indicated on the "prong" diagram. No more valuable time lost thumbing pages or on lengthy readings. Filament, grid, plate, cathode, etc., etc. MORE THAN 300 tube types are given. PRICE NOW ONLY \$1.00 postpaid or sent C.O.D. plus postage. Order NOW, money refunded if you are not delightfully pleased.

**REED MFG. CO.** 124 W. 4th St. Los Angeles 13, Calif.

a simplification of the design and construction of cabinets.

Prices will be quoted by the manufacturer on request. Address inquiries to *Telectro Components*, 141 Belleville Avenue, Belleville 9, New Jersey.

**TV RECEIVER PARTS**

*Vision Research Laboratories* has announced a complete line of television receiver parts and accessories.

Of particular interest to the receiver designer is the No. 510 permeability tuned television coil kit. This coil kit contains a total of thirteen components including video i.f., sound i.f. peaking coils and traps. These coils have been designed for use in high definition television receivers where bandwidths of approximately 4 mc. are required. The kit also includes a discriminator transformer. The coils are available either in complete kit form or as separate items.

Additional details on these or other television components may be secured by writing *Vision Research Laboratories*, P.O. Box 52, Kew Gardens, New York.

**DALMOTRON INTERCOM**

*Dalmo Victor Company* of San Carlos, California, is currently marketing a low-cost intercommunication unit which has been designed specifically for the small office, store, plant, or shop.

This new *Dalmotron* Model 101 incorporates a patented circuit which requires the use of only half an amplifier. The calling unit utilizes the



amplifier of each of the other units as well as its own—a feature which contributes to the compactness of the intercom.

Each *Dalmotron* is a master station which can either transmit or receive. Designed for maximum simultaneous usage, a six unit system can handle two separate two-way conversations while the rest of the system remains open for paging.

*Dalmo Victor Company*, San Carlos, California, will supply literature and additional details on the Model 101 and other units in their line, upon request.

**FM CONSTRUCTION KIT**

*Radio Kits, Inc.*, has started marketing a new FM radio receiver kit, the Model FM-7.

This table model receiver kit, which


**it's NEWARK for BETTER SERVICE - BIGGER VALUES!**



*You can use this!*  
**BEACON RECEIVER**  
BC-1206-B

Truly sensational buy for Hams, Experimenters! 5-Tube Set, tunes 195 to 420 Kc. (A-N beam signals). Operates on 28V DC; easily changed to 110V. 4"x4"x6 1/2" long. Wt. 3/4 lbs. Complete with tubes, slightly used, A-1 condition, and it's all yours for only **\$3.95**

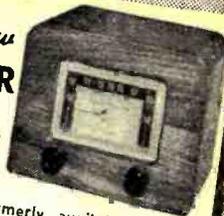*Amazing New*  
**PILOTUNER**  
adds F-M to ANY Receiver!



Simple to connect, it brings you all the benefits of FM reception formerly available only in expensive models . . . now at an astonishingly low price that everybody can afford! Features: 5 tubes plus selenium antenna; 3-gang cond.; Built-in FM Antenna; self-contained AC power supply; handsome walnut wood cabinet. YOU can own it, for only **\$29.95**

**MILLEN "R9er"**

Bring those 6 and 10 meter signals out of the noise with this new Antenna Matching Preamplifier. At least 30 db. gain in both bands! Uses 6AK5 tube. Complete with coil unit for 10-11 meters, less tube. **\$24.75**  
6 or 20 meter coils, each **\$3.15**  
6AK5 Tube **90c**  
MILLEN #90800 50-Watt Transmitter-Exciter **\$42.50**



*Only A Few Left!*

**SCR-522 TRANSCEIVER**



One of our most sensational values! These wonderful surplus 2-meter rigs for practically a song! Receiver and transmitter less power supply and control box. Some have crystals, some may be missing. But the basic unit is there — ready to operate. Can be converted to 110V AC. Schematic included. Shpg. wt. 75 lbs. Limited quantity at this amazing price. **\$14.95**  
The whole works, as is, for only . . .

Available F.O.B. New York only

**HANDSET TS-13**

We've SMASHED the price on this fine handset! 200 ohm carbon mike, 2500 ohm earphone, butterfly switch, PL68, PL55 plugs, 6 ft. rubber cord. BRAND NEW, and it's yours for **\$2.39**



**THORDARSON 'SCOPE TRANSFORMER**

Gen'l purp. Pri: 110V 60cy. Sec. 750VCT @ 160Ma, 1450V @ 2Ma, 6.3V @ 1 amp. SMASHING LOW PRICE!  
No. S-542 **\$3.49**

**THORD. ALL-PURP. FILAMENT TRANS.**

Pri: 105 to 250V 60 cy. Sec: 6 1/2V @ 20 amps, 6.3V @ 3 amps, 5V @ 3 amps. NOW YOURS FOR ONLY **\$3.49**  
No. S541



**Look at this TERRIFIC BUY!**

**MARK II**  
40 & 80 Meter Complete XMTR-RCVR



You've got to SEE it to BELIEVE it! Complete mobile rig, suitable for truck, boat, auto. Dynamotor power supply included, works on 12 or 24 volt battery. Easy to rewire set for 110V 60 cycle AC. Schematic included. And it's all yours, Transmitter, Receiver, Dynamotor Power Supply, complete with tubes, less ext'l accessories, shpg. wt. 130lbs. **\$29.50**


**YOUR COPY of our GIANT BARGAIN BULLETIN #4-N** is ready now . . . **SEND FOR IT TODAY!**

Complete Line of **RCA TELEVISION** components in stock. All makes of **Television Kits, ELECTROTECH, TRANSVISION, etc.**

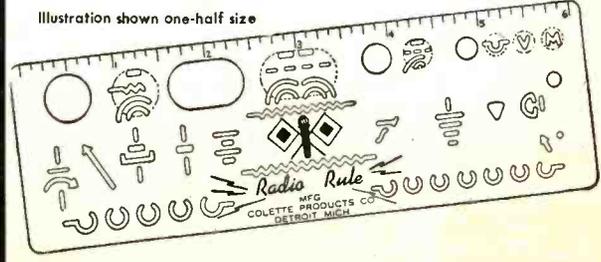**BUY OVER \$75 WORTH OF EQUIPMENT Take ONE YEAR to PAY 20% Down—Pay Monthly**

**NEW YORK** Offices & Warehouse 242 W. 55th St., N.Y. 19  
**NEWARK** **ELECTRIC COMPANY, INC.**  
**CHICAGO** 323 W. Madison St. Chicago 6, Ill.  
New York City Stores: 115-17 W. 45th St. & 212 Fulton St.

**The New Improved RADIO RULE**  
FOR ALL RADIO STUDENTS, ENGINEERS, DRAFTSMEN, TECHNICIANS and HAMS



This sensational new Radio Rule was developed by a Radio Engineer for quicker, more accurate and uniform circuit diagram drawing. It is ideally suited for school and university work as well as for the experienced technician.

Made from clear, laminated plastic . . . pocket size. Money back guarantee.

**\$2.00 each**  
See your LOCAL DEALER or send Money Order to

**COLETTE PRODUCTS COMPANY 8653 GRAND RIVER DETROIT 4, MICHIGAN**

# CLOSE OUT! MANUFACTURER Clearance! OVERSTOCKED 1000 12 IN. SPEAKERS



We can't use the manufacturer's name but these are the best quality that can be made.

Custom quality — every one thoroughly tested perfect. Satisfaction guaranteed or your money refunded.

## THIS IS NOT SURPLUS STOCK!

Every speaker brand new. Completely dustproof. Widely used for QUALITY TONE installations in the public address and radio field. 6.80 oz. ALNICO V Permanent Magnet. Voice coil impedance 6-8 ohms. Easily handles 14 to 18 watts of power.

Shipping weight 6 lbs.....

# \$5.95

Order 1 - A Dozen - A Gross or All. We'll Fill Orders as Received as Long as the 1000 Last. (which won't be long!)

## WARD RADIO CO.


One North LaSalle Street  
CHICAGO 2, ILLINOIS

### Get a new UNGAR ELECTRIC SOLDERING IRON FREE

... and assemble your own

### MAGI-KLIPS

RADIO & ELECTRONIC EXPERIMENTER'S KIT

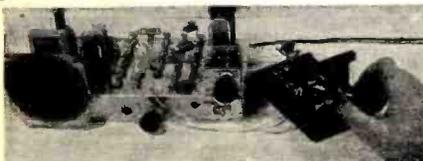

This is the same MAGI-KLIPS Kit—complete with all parts—that we sell ready assembled for \$29.75.

In knocked-down form with full instructions for assembly, it is now available at the new low price **\$19.75**... complete with an Ungar Electric Soldering Iron—the ideal iron for wiring your unassembled MAGI-KLIPS Kit.

Remember, you build 18 different experiments with your MAGI-KLIPS Kit. You actually teach yourself radio and electronics and have a lot of fun at the same time.

RADIO RECEIVER, HOME BROADCASTER, PHOTOELECTRIC RELAY, CODE PRACTICE OSCILLATOR, SIGNAL TRACER, REMOTE CONTROL RELAY, Phonograph Transmitter, Intercommunication Amplifier, Code Transmitter, Radio Frequency Oscillator, Telephone Line Amplifier, Electronic Switch, Phonograph Amplifier, Temperature Control Relay, Contact Detector, Electronic Metronome, Interval Timer (one-shot), Interval Timer (repeating).

Send for your copy of FREE booklet, "Electronics Made Easy."

### DEER & TAYLOR COMPANY

Dept. N 1340 Milvia St. Berkeley 9, Calif.

## RADIO TUBES

For immediate shipment

R.M.A. Guaranteed

Below Distributor Costs

Individually Sealed Cartons

Type	Price
6K6GT	.40
6K5GT	.46
6V6GT	.46
6SA7GT	.46
6SJ7GT	.46
6SK7GT	.46
6SQ7GT	.46
6X5GT	.40
12SA7GT	.58
12SQ7GT	.46
12SK7GT	.46
12SJ7GT	.46
35L6GT	.40
35Z5GT	.32
50L6GT	.46

MANY OTHER TYPES AVAILABLE

RATED ACCOUNTS—2% 10 DAYS

ALL OTHERS 2% C.O.D.


10% DISCOUNT ON LOTS OF 50 OR MORE

### RAVAC ELECTRONICS CORP.

432—4th Avenue  
New York 16, N.Y.

sells in the low-priced field, is completely self-contained or can be used as a tuner in connection with a high quality amplifier. The FM-7 covers the full range from 86 to 110 mc. A phono jack is provided in the rear of the chassis. This jack is connected with a d.p.d.t. switch which feeds the signal either to the speaker in the radio or to the phono jack. The kit is also provided with an extra jack for connecting an additional loudspeaker, if desired.

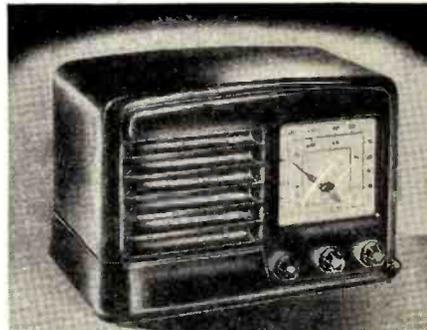The kit comes complete with tubes, speaker, and cabinet. The r.f. section is pretuned at the factory. The kit uses two i.f. stages, one limiter



and one discriminator. Miniature tubes are used throughout.


Additional information will be supplied on request to Radio Kits, Inc., 120 Cedar Street, New York, New York.

### BENCH GRINDER

Speedway Manufacturing Company has announced a new popularly priced bench grinder for service shops.

The Model 117 operates on 110-120 volts, a.c., and features a speed of 3400 r.p.m. The unit is rated at 1/15 h.p. intermittent duty. It is equipped with self-aligning bronze bearings.

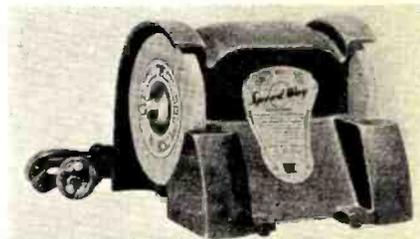The unit is 8" x 6" and weighs 7½ pounds. The grinder is finished in



blue crackle and comes complete with two grinding wheels, one coarse and the other fine, a built-in thumb switch, and a 6 foot rubber covered cord with unbreakable plug.

Speedway Manufacturing Company, Cicero, Illinois, will furnish prices and additional details on the Model 117 upon request.

### NEW MODEL B MOTOR

Alliance Manufacturing Company of Alliance, Ohio, has announced the production of a new Model B small motor.


This newest addition to the company's line of "Powr-Pakt" motors may be used as a power source for driving fan blades, magnetic tape, disc,

RADIO NEWS

and wire recorders, and similar devices.

The motor is rated a 1/70th horsepower at 1600 r.p.m. when operated on 115 volts, 60-cycles. Within its recommended usages, the motor is good for continuous duty operation without additional external cooling.

The Model B is a semi-enclosed four-

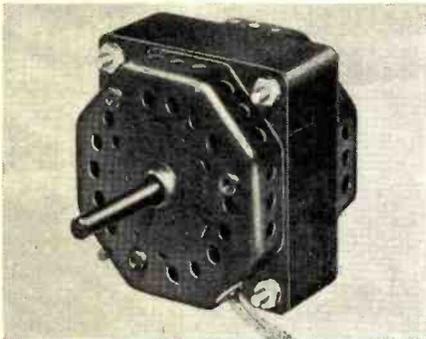

pole, shaded pole induction motor. It measures 3 3/8" square and has a length of 2 7/8" over the main portion of the end bracket and approximately 3 1/4" over the bearing housing.

Engineering specifications and performance details on the Model B motor will be supplied by *Alliance Manufacturing Company*, Alliance, Ohio, on request.

### LICENSE REVISIONS

**T**HE Federal Communications Commission has announced the first step in its plan to place the commercial radio operator examinations and licenses in step with the advancements which have been made in the industry.

The plan provides, in part, for three classes of broadcast operator licenses authorizing operation of standard, international, FM, facsimile, television, developmental, and auxiliary broadcast stations. At the present time only the first class radiotelephone operator's license authorizes operation of these stations.

Under the new plan the three new classes of broadcast operator's licenses would be valid for operator duties as follows: "Broadcast Engineer-Operator"—Chief Engineer or Staff Operator of any standard, international, FM, facsimile, television, developmental, and auxiliary stations; "Broadcast Technician-Operator"—Chief Engineer of a standard broadcast station of not more than 1 kw. power employing a non-directional antenna system, or an FM broadcast station, or the Staff Operator of any standard, international, FM, facsimile, television, developmental, and auxiliary station; "Broadcast Radio-Operator"—Staff Operator of a standard broadcast station not exceeding 1 kw. power employing a non-directional antenna system, or the Staff Operator of an FM broadcast station of not more than 1 kw. effective radiated power.

All broadcast stations would be required to employ at least one Engineer-Operator with the exception of FM broadcast stations, standard broadcast stations of 1 kw. or less with non-directional antenna. The excepted stations could employ at least one Technician-Operator in lieu of the Engineer-Operator.

-30-

October, 1947

**your  
basic  
3R's  
for correct  
current control**

Ward Leonard  
**RELAYS**

Ward Leonard  
**RESISTORS**

Ward Leonard  
**RHEOSTATS**



SEND FOR  
FREE CATALOGS

Write for Amateur Relay Catalog No. D-111, and for Resistor-Rheostat Catalog No. D-2.

**RELAYS**—provide convenient circuit control, protection, and greater operating efficiency . . . help reduce length of connecting leads. Amateur Relays available from stock: Antenna Change-Over, Antenna Grounding, Keying, Band Switching, RF Break-In, Safety, Overload, Underload, Latch-In, Remote Control, Sensitive, Time Delay. Also Industrial and General-Purpose Relays.

**RESISTORS**—exclusive features of VITROHM wire-wound resistors insure that extra performance needed in critical circuits. Fixed type in 8 stock sizes from 5 to 200 watts. Adjustable type in 7 stock sizes from 10 to 200 watts. Wide range of resistance values. Stripohm, Discohm, and Plaque types also available.

**RHEOSTATS**—for fixed or variable close control. Protected by tough, acid resistant, crazeless vitreous enamel. Sizes: 25, 50, 100, and 150 watts, in wide range of resistances.

Authorized Distributors Everywhere

**WARD LEONARD ELECTRIC COMPANY**


Radio and Electronic Distributor Division

53-N West Jackson Blvd., Chicago 4, U. S. A.

**WARD LEONARD**  
**RELAYS • RESISTORS • RHEOSTATS**

Electric control devices since 1892

**Permoflux SPEAKERS**

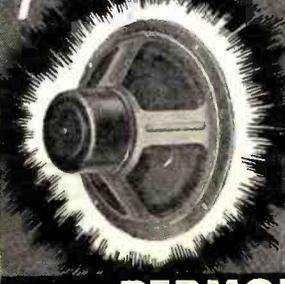

*An OLD name in Speakers  
a NEW high in Performance\**

**ANNOUNCES . . .** a COMPLETE JOBBER LINE of standard replacement and hi-fidelity de luxe loud speakers with both permanent and electro-magnet fields. These quality speakers embody the same skillfully engineered features used in the units that PERMOFLUX now supplies to major set manufacturers.

\* Sound room laboratory tests prove greater uniformity in frequency response, than other comparable makes.

TWO COMPLETE  
FACTORIES TO SERVE YOU

**PERMOFLUX**

WRITE FOR  
FREE BULLETIN

PIONEER MANUFACTURERS OF PERMANENT MAGNET DYNAMIC TRANSDUCERS

**PERMOFLUX CORPORATION**

4900 WEST GRAND AVE., CHICAGO 39, ILLINOIS  
236 SOUTH VERDUGO ROAD, GLENDALE 5, CALIFORNIA

175

# SPECIALS NOW AVAILABLE!

IT4 TUBES POPULAR MAKE, BULK  
PACKED..... .50 ea.  
10 for \$4.50  
JAN INSPECTED, INDIVIDUALLY PACKED.

## RECEIVING TUBES

5U4G..... ea. \$0.60 6H6..... ea. \$0.55  
6J5..... ea. .54 6SN7GT..... ea. .66  
6V6GT..... ea. .69 6E5..... ea. .65  
6X5GT..... ea. .55 6AG5..... ea. .98

## Transmitting & Special Purpose Tubes

2x2/879..... \$1.90 ea. 3E29..... \$2.75 ea.  
6AK5..... .89 ea. 2C26..... .50 ea.  
9006..... .65 ea.

## KIT

Kit consisting of 300—1/2W, 125—1W and 10—5W. Resistors. Fully Insulated RMA coated. Ranging from 68 OHMS to 1 MEG OHM. 70 MICA and molded paper condensers, also Misc. Hardware and Terminal Strips. Each type and item individually packaged.

\$60.00 VALUE SPECIALLY PRICED \$16.95

## CAPACITORS

Sprague 4MFDX600V Rectangular Can..... ea. \$0.79  
Incco .2MFDX5000V Rectangular Can..... ea. 4.45  
Sprague 1MFDX3600V Rectangular Can..... ea. 3.45  
Incco 7MFDX800V Rectangular Can..... ea. 1.69  
Micamold 7MFDX600V Rectangular Can..... ea. 1.39  
Incco 2MFDX1000V Rectangular Can..... ea. 1.39  
Micamold Triple Section Capacitor 2.5x2.5x5.0 MFDX  
600V Rectangular Can..... \$1.49 ea.

## FILAMENT TRANSFORMERS

(5000 Volt Insulation)

115V 60 cycle PRI. \$1.6.3V @ 5 amp. \$2.2.5V @ 9 amp.  
\$3.2.5V @ 4 amp..... \$2.95  
115V 60 cycle PRI. \$1.6.4V @ 12 amp. \$2.6.4V @ 10.6  
amp. \$3.5.0V @ 3 amp. \$4.5.0V @ 3 amp. \$5.5.0V @ 3  
amp. \$6.2.5V @ 1.75 amp..... \$4.95

## PLATE TRANSFORMERS

(5000 Volt Insulation)

115V 60 cycle PRI. 2100 V @ 100 MA Secondary.. \$8.45  
115V 60 cycle PRI. 860 VCT @ 300 MA Secondary.. 4.95

## CHOKES

Choke, 59 Henrys—100MA/850 Ohms..... \$2.95  
Dual Choke, 12 Henrys—100 MA/150 Ohms..... 2.45  
DRAKE JUMBO JEWELS, AMBER AND RED ea. 0.49  
Circuit Breakers, 117V 10 Amp..... 1.75  
Circuit Breakers, Time Delay Magnetic..... 1.75

## AMPHENOL RG CABLE CONNECTORS

2-piece straight with Molded Low-Loss Mica Filled Insert  
Connector..... \$0.39  
Angle Plug Adapter Polystyrene Insert Pin and  
Socket..... \$0.59  
Receptacle Chassis or Box-type Low-Loss Mica Filled  
Insert..... \$0.39  
Hood for R. G. Cables, 80, 100, 110, 220, 630, 650. .15  
MCCLINTOCK 0-1 MA METER—3 1/2"..... ea. \$3.75

## GLASS FUSES

1AMP 3AG..... 10 for \$.20  
3AMP 3AG..... 10 for .20  
5AMP 3AG..... 10 for .20

## LITTLEFUSE EXTRACTOR

Fuse Post for 3AG Fuse..... \$1.13 ea.  
10 for \$1.20

Minimum order \$2.00. 25% deposit  
on all orders—balance C.O.D.

ALL MERCHANDISE NEW AND  
GUARANTEED

**W & H SALES CO.**  
1815 SOUTH KEDZIE AVENUE  
CHICAGO 23, ILLINOIS

## Signal Generator

(Continued from page 43)

checked by connecting a pair of headphones to the audio output jack. When  $S_2$  is in the modulation "ON" position, a steady audio note should be heard. With the a.f. transformer specified, a note of about 400 cycles is obtained. If it is desired to change the frequency of the a.f. oscillator, this may be accomplished by changing the values of  $C_1$  or  $R_2$ . Increasing the value of either of these components will produce a lower frequency note, while reducing the value will produce a higher pitched note. Another method of reducing the frequency of oscillation is to connect a small mica condenser across the grid coil; the larger the capacity, the lower the resulting frequency. At any rate, the note finally chosen should be one which is pleasing to the ear of the individual, as he will doubtless listen to it over extended periods of time.

## Calibration

Several methods of calibration are possible, the most practical being a direct comparison between the output signals of the generator and a known standard. The known frequency standard may be a heterodyne frequency meter, if available. Otherwise, the generator may be calibrated by using a receiver and a crystal calibrator, or another signal generator for a standard. If the receiver calibration is sufficiently accurate, it may be used alone. Irrespective of the standard used, the final calibration accuracy can be no better than that of the standard, and a certain amount of care should be exercised to preserve as much of this available accuracy as possible.

Before beginning the actual calibration, the band limits should be set. With the signal generator connected to a receiver, turn to Band A, and set the tuning condenser at maximum capacity. Now adjust the slug in coil  $L_1$  until the output is on 170 kc. As the average "All-Band" receiver does not tune below 500 kc., it will be necessary to listen to a harmonic of the signal generator. With the generator set at 170 kc., the 4th harmonic should be heard at 680 kc., the 5th harmonic at 850 kc., and so on at 170 kc. intervals. Check at least two adjacent harmonics to be sure that they are 170 kc. apart. If not, the separation between two adjacent harmonics will be equal to the generator frequency and indicate what adjustment is necessary to move the generator to the desired frequency. Moving the iron slug into the coil reduces frequency, while withdrawing the slug increases frequency.

After the low frequency end of Band A is set, turn the tuning condenser to the minimum capacity and adjust trimmer condenser  $C_1$  for an output frequency of 500 kc. Successively repeat these two adjust-


ments of upper and lower limits until both are as desired. This is necessary because one adjustment will affect the other, and both must be adjusted correctly to give the desired tuning range.

The other band limits may now be adjusted by the same general method except it will be simpler tuning to the fundamental frequency of the generator, instead of harmonics. The band limits of the instrument illustrated were set as follows: Band A—170 kc. to 500 kc.; Band B—500 kc. to 1500 kc.; Band C—1.5 mc. to 5 mc.; and Band D—5 mc. to 15 mc. These values are given mainly as an illustration, and need not be followed exactly, as the adjustments allow for considerable change to suit personal preferences.

After the limits have been set, they should not be altered. The actual calibration may now be undertaken. Assuming that another signal generator is to be used as a standard, the procedure is as follows.

Connect the output of the standard and the output of the signal generator to the antenna terminals of a receiver. Set the standard to 170 kc. and tune the receiver to a harmonic of the standard, with the beat frequency oscillator of the receiver turned on. Once the standard signal has been tuned in, the beat oscillator is turned off and the signal generator to be calibrated is tuned to the low end of Band A. A beat will be heard as the generator crosses 170 kc. Carefully tune the generator to zero beat and then scribe a mark on the dial which will be labeled 170 kc.

Fig. 5. Details of coil construction.

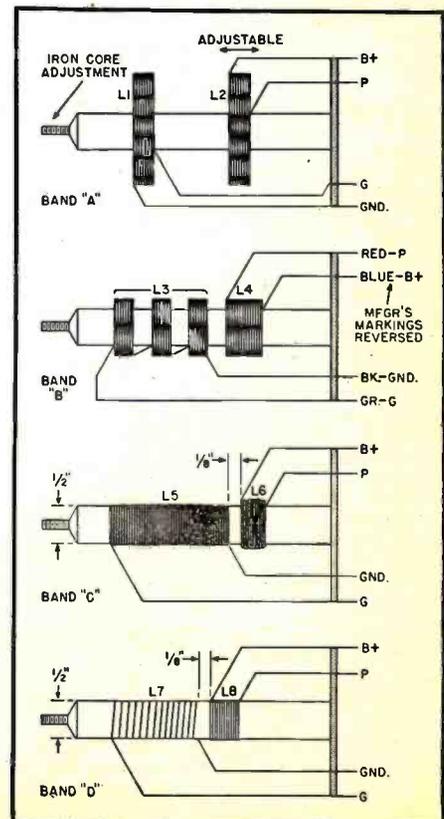

# TELEVISION

- ★ 4.5 Band Width
- ★ 10,000 Volts 2nd Anode Potial
- ★ 5 stages picture IF
- ★ 2 stages Aligned and Pretuned IF coils
- ★ 29 Tubes plus 10" or 12" CR Tube
- ★ Chassis 17" x 19" x 3" IF Strip



## IN SIMPLE ASSEMBLY FORM

No Eye Strain

BRIGHT

STEADY

CLEAR

The first Flat Surface Screen Picture available with 10" (51 sq. in. picture). Also 12" (75 sq. in. picture) in assembly form. This is not a kit but a complete assembly.

Superior performance is obtained with a new \*IF video and sound strip, and front end feature, engineered, aligned and tested, all wired and pretuned ready to use when delivered.

Ratio detector provides High Fidelity for Sound, FM Reproduction.


Easier to operate than your home radio.

### FRONT END

Will handle 13 television channels. It is so flexible that any number of channels from 1 to 13 can be used. This allows a start with the channels now in use 2-4-5-7-9-11-13 and then install the others at a slight additional cost.

Also included 29 RCA tubes plus 10" or 12" Flat Surface CR Tube—Heavy duty RCA 6.8 oz. slug 12" PM speaker—Specially designed dipole antenna with 60 ft. lead-in—Complete pictorial and schematic diagrams.

\* Pat. Pending.

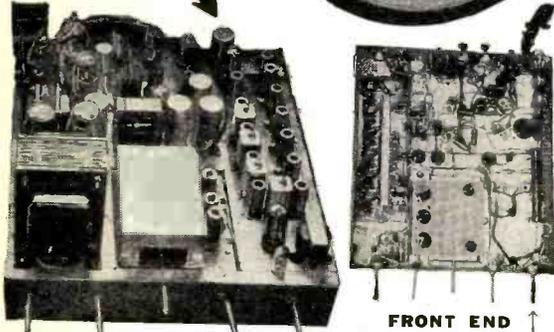

FRONT END

### GUARANTEED

To operate to your satisfaction when simple directions are followed.

**10" PICTURE TUBE \$229<sup>50</sup>** ALSO AVAILABLE **12" PICTURE TUBE \$259<sup>50</sup>**  
 51 Sq. In. Picture 75 Sq. In. Picture

10% DEPOSIT WITH ORDER—BALANCE EXPRESS COLLECT—ALL PRICES F.O.B. BROOKLYN, N. Y.

## TELEVISION ASSEMBLY CO. 387 BRUNSWICK AVE. BROOKLYN 6, N. Y.

NEVER BEFORE AT THESE LOW PRICES

RADIO PARTS BARGAINS

LIMITED QUANTITIES HUGE SAVINGS

DEALERS—SERVICE MEN

### RADIO TUBES

Standard Brands in Individual Cartons

BRAND NEW Below Regular Distributors Prices

OZ4	\$.89	6H6GT	\$.58
1A7GT	.69	6J5GT	.45
1H5GT	.59	6K6GT	.51
1LA4	1.10	6K7GT	.51
1LA6	1.10	6L6G	.99
1LB4	1.10	6Q7GT	.47
1LC6	1.10	6SA7GT	.55
1N5	.69	6SJ7GT	.55
1R5	.89	6SK7GT	.55
1S5	.89	6SQ7GT	.55
1T5GT	.89	6V6GT	.55
2A5	.69	12A7GT	.55
2A7	.89	12BA6	.69
3Q5GT	.89	12BE6	.69
6U4	.51	12SA7GT	.69
6V4	.89	12SJ7GT	.55
6W4GT	.45	12SK7GT	.55
6Y3GT	.35	12SQ7GT	.55
6Y4	.39	25L6GT	.55
5Z3	.55	25Z5	.49
6A7	.51	25Z6GT	.55
6A8GT	.51	35L6	.55
6AC5GT	.69	35W4	.43
6AR5	.55	35Z5	.43
6AT6	.55	41	.43
6AU6	.69	42	.43
6C5GT	.51	43	.55
6C8	.55	47	.55
6D8	.55	50B5	.68
6F6	.45	50L6GT	.55

MINIMUM ORDER 25 TUBES

• Please Include 20% deposit with orders; balance C.O.D. Orders under \$10.00—remit in full.

• All Parts, Kits, Chassis are sold with our money-back policy, thus guaranteeing your complete satisfaction.

• No C.O.D. on Canadian and foreign shipments.



Don't Pass These Up— All for Immediate Shipment

AC—Alliance Phono Motors with Turntable	\$2.65; case of 10, \$24.50
AC—Ballantine Phono Motors with Turntable	3.25; case of 10, 29.95
Astatic Curved Arm Crystal Pickup	1.50; case of 10, 14.00
Shure Glider Crystal Pickup	1.50; case of 10, 14.00
GE 12" Alnico 5 6.8 oz. Magnet PM Speaker	6.75; case of 6, 36.00
ROLA 10" Alnico 5 PM Speaker Heavy Slug	5.75; case of 6, 30.00
GI 8" Alnico 5 PM Speaker	3.25; case of 6, 18.00
6" PM Speaker: Special Alnico Heavy Slug	1.65; case of 10, 14.00
5" PM Speaker: Alnico Heavy Slug	1.20; case of 10, 11.00
8" PM FAMOUS BRAND Alnico with 50L6 output trans.	1.59; case of 10, 13.95
Cornell Dubilier 50x30 Aluminum Can Self Support Leads	\$0.39; 10 for 3.45
Universal Output Heavy Duty 18 Watt Single PP 4000 ohms to 14,000 CT.	1.30; 10 for 11.00
Universal Output Heavy Duty 18 Watt Single PP 4000 ohm to 14,000 CT.	1.55; 10 for 12.75
Single 50L6 output transformer 3.5 ohm Impedances.	.39; 10 for 3.50
1/2 Meg Volume Control IRC with Switches	.49; 10 for 3.95
1/2 Meg Volume Control Less Switch	.29; 10 for 2.45
Punched Chassis Slide Rule 4"x 10"x2"	.29; 10 for 2.50
Punched Chassis Side Dial 4"x10"x 2"	.29; 10 for 2.50
Superhet Variable Cond 420-165 MMF 2 gang.	1.10; 10 for 9.50
TRF VARIABLE Cond 420-420 MMF 2 Gang.	1.25; 10 for 11.00
IF Coils Matched Set 456 KC Litz Wound Double Tuned.	1.00; 10 for 9.00
High Gain Loop Antenna	.79; 10 for 3.00
90 MA Power Transformer 700V CT 6.3V 2 Amp.	3.25; 10 for 27.00
70 MA Power Transformer 700V CT 6.3V 2 Amp.	2.95; 10 for 23.00

### AMERICA'S FINEST RADIO KIT VALUE

5 Tube AC-DC Superhet with Tone Control. Complete with Plastic Cabinet (Dim. 12 3/4" x 8 3/4" x 7 1/2"). Your choice of Colors: Brown, White, Blue, Rose, Green, Red. 5 Inch Alnico 5 PM Speaker. Matched High Gain IP's. 8 Pages of Pictorial Instructions, as used by many schools and Veteran Organizations. Anyone can complete. Chassis Assembled. Special, \$14.95, Less Wire and Solder.

Matched Kit of RCA, Sylvania or N-U Tubes Included. Your Money Back If Not 100% Satisfied.

CABINET CHASSIS AND DIAL ONLY \$2.95. Your Choice of Colors, same as above.



### KIT SPECIALS

5 TUBE AC-DC Superhet. All Components Including Instructions—Less Tubes, Wire, Solder, 5" Alnico 5 PM Speaker, Litz IP's Loop Antenna. Fine Value, \$6.95; 10 for \$65.00.



### RECORD CHANGER SPECIALS

VM Single Post 10" and 12" records	\$14.95
In lots of ten	13.50
Newest model K two post Seeborg	19.95
In lots of ten	18.50
Webster model 56	21.50
In lots of ten	19.50

All Brand New in Individual Cartons and Guaranteed

## AMERICAN RADIO SUPPLY CO.

120 CEDAR STREET :: NEW YORK 6, N. Y.

# LECTROHM RESISTORS

Completely Satisfy—  
**ALWAYS**

because—

- (1) Resistance wire is silver soldered to solder lugs in all Lectrohm Resistors, by special process, assuring perfect electrical bond under all conditions.
- (2) Lectrohm Resistors are designed and made by specially resistor engineers—99% of Lectrohm's production is resistors.



Ask for the new Lectrohm Catalog and data book containing pertinent information on these Resistors and much valuable reference information.



8131 West 25th Street, Cicero 50, Illinois

Division of

National Lock Washer Co., Newark, N. J.



- (3) Every Lectrohm Resistor is an integral unit with all parts completely embedded in vitreous enamel.
- (4) You will find all types and ratings in the Lectrohm Line, also power line and R. F. Plate Chokes and accessories.
- (5) Delivery is prompt.

Then proceed to the next point to be calibrated, say 175 kc. and repeat the same procedure, namely: 1. Set the standard generator to the desired frequency; 2. Tune the receiver to this signal; 3. Tune the generator under calibration to zero beat with the standard. The output level of both generators should be kept low, to give a sharp and well defined zero beat.

The number of points to be calibrated is a matter of wide speculation. Theoretically, the more points calibrated, the more accurately the generator may be adjusted to a given frequency. Practically speaking, a fewer number of calibration points, clearly and accurately located, prove to be more useful than a dial which is cluttered up and hard to read.

## Operation

Once calibrated, the operation is straightforward and conventional. A shielded lead is desirable for the output lead, and may be fitted with test clips for convenience. When plugged into the "R.F. Output" jack, signals will be available for checking receiver circuits from 170 kc. to 15 mc. Higher frequencies may be obtained by using harmonics of the generator. The r.f. output is of sufficient amplitude to work directly into the diode second detector of a conventional receiver, which is a desirable feature for locating receiver troubles.

With the same output lead connected to the "A.F. Output" jack, a variable level audio signal is available for rapid checking of the operation of audio amplifier stages.

In general, the instrument provides all that is required from a simple signal generator at a minimum expense and using only parts that are readily available.

-30-

## BARGAIN SPECIALS

	Your Cost
LEE RADIO, A.C.-D.C. 4-Tube Compact Model, HOT retailer at \$12.95.....	\$ 9.75
ELECTRIC PORTABLE PHONOGRAPH, Original list \$29.95.....	14.90
SUPERIOR SIGNAL TRACER #CA-12, latest model, all purpose.....	34.85
RADIO MECHANICS REPAIR STAND, holds chassis while repairing.....	8.95
BROOKS INVERTER, 50 Watts, 110 V.....	8.95
35Z5, 50L6, 12SA7, 12SK7, 12SQ7, Complete Tube Kit.....	2.31
35W4, 50B5, 12BA6, 12BE6, 12AT6, Complete Tube Kit.....	2.31
RADIO CHASSIS KIT, build your own 5-tube Radio, less wire and cabinet.....	10.95
PHONOGRAPH MOTOR, standard brand with 9" Turntable.....	2.95
PICK-UP ARM, crystal type, complete with hardware.....	1.75
TELEVISION ANTENNA, list \$14.50.....	7.25
100 FEET 300 ohm lead-in wire.....	2.25
100 FEET COAXIAL CABLE RG59U, 72 ohms.....	6.90
ELECTRIC HEATER, Floor Model, U.L. Approved, sells for \$24.40.....	8.95
ELECTRIC BROILER, original price \$19.17.....	8.45
ELECTRIC IRON, automatic, lists \$9.95.....	5.25

Note—All items are TOP QUALITY, sold with a money back guarantee. We invite sample orders. Don't delay as some items are subject to prior sale.


WIRE—WRITE—PHONE

**BROOKS RADIO DISTRIBUTING CORP.**

80 Vesey Street (Dept. B) New York 7, N. Y. CO 7-2312
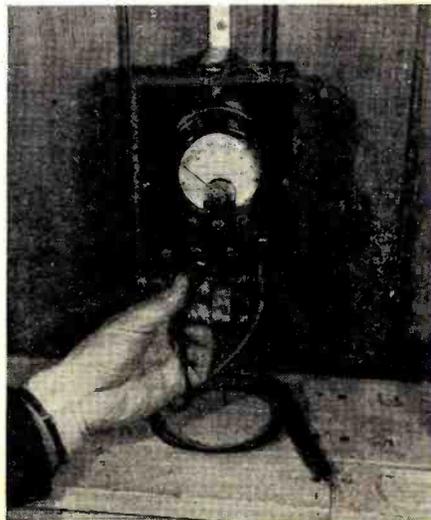
## METER MOUNT

**D**ID you ever pull an expensive meter right off the table or workbench when you jerked the test leads a bit too strongly? I did once, so now I have the meter fastened securely to the wall by means of two L-shaped brackets. Short screws passing into the case of the meter at the top and the bottom permit the instrument to be turned in the most convenient direction. . . . D. J. B.



## ELECTRONIC VOLT-OHM-METER

\$11.95

110 VOLTS AC 20 RANGES  
0.5/10/50/100/500/1000/5000 volts  
DC and AC. 0-1,000,000,000 ohms  
in six overlapping ranges. Sensitivity:  
over MILLION OHMS per VOLT on 5  
volt range.

POSTPAID

Complete kit includes all component parts, tubes, punched and drilled chassis and beautifully enameled panel. Easily assembled and wired.

Special slideback circuit developed during war by scientist at the California Institute of Technology gives amazing sensitivity and flexibility while completely eliminating necessity of batteries and expensive meter. Each instrument is individually calibrated. Dial scale over nine inches long!

In addition to performing the usual volt-ohm functions, this instrument easily measures these voltages: SUPERHER OSCILLATOR, AVC, AFC, TRUO GRID BIAS AT THE GRID, BIAS CELLS without affecting the circuit. Measures the exact leakage resistance of INSULATION, TUBES, CONDENSERS. It can be used with a signal generator for SIGNAL TRACING.

**STERLING ELECTRONIC COMPANY**

Dept. 3  
BOWLING GREEN, KENTUCKY

## SCHEMATICS

8" x 11" photostats for: BC348Q, N & J; BC348H, K, L & R; BC224, F & K; BC191; BC375E; SCR522; AN/ART13; AN/APN1; BC474A; SCR269G; BC624C; R47/ARN5; R89/ARN5; BC1033A; BC461; RC103A; GF-11/RU-16; Mark II; SCR288; AN/ARN7; BC453A; BC454A; BC455A (includes FT220 & BC450A); BC457A (includes BC696A, BC456A, BC458A, BC459A, FT266A, BC451A, and BC442A). 63c each postpaid, check or m.o. Please do not write for diagrams not listed here.

BC375 tuning units, used, clean, each, postpaid \$ 2.95  
BC348 receivers, converted to AC, guaranteed, FOB Flushing, N. Y. 65.00  
50 watt 3000 ohm and 7500 ohm, vitreous enamel resistor, ea. .20  
7 watt wire wound 126 ohm, ea. .10  
25 watt 4000 ohm wire wound resistor, ea. .15  
50 watt 3600 ohm wire wound vitreous resistor, ea. .17  
1/2 watt, 39000 ohm, fixed carbon, 10 for .30  
50 watt, 20 ohm, fixed vitreous resistor, ea. .14  
M-299 Microphone Adapter (for SCR522), new, ea. 1.35  
MC211A Right Angle Drive for SCR274N, ea. .75

**LONG ISLAND RADIO COMPANY**  
164-21 Northern Bl., Flushing, N. Y., Flushing 9-3918

## International Short-Wave

(Continued from page 161)

**France**—North American Service of the French Broadcasting System, Paris, is scheduled at 1700-1715 on 15.24, 15.35, 17.85, and at 1915-2015 on 9.55, 11.845, 15.35.

**Freetown**—Sierra Leone, 8.125, is heard irregularly on Sundays only from 1530; tests are prior to opening up of radio-telephony service to Bathurst, Accra, and Lagos; asks for reports. (Pearce) Call has been reported as SHV-3, and as ZHV-5. May also use 15.840 on occasion. Transmitter is said to be a *Marconi* SWB-8E, running 1 kw.

**French Indo-China**—Saigon's 49-m. outlet has been moved down to 6.165 from 6.193. (Dilg) The 11.780 channel parallels and has good signal mornings in the East; news at 0500 and 0900.

"The Voice of Vietnam," 9.470, has *English* at 0705-0715. (Dilg) News in French at 0545; location Hanoi. (Sander-son)

**Germany**—AFN, 6.080, Munich, has news and weather forecast at 1400. (Pearce) Now signs off around 1700 after short newscast. (Harrison) AFN on 7.470 is heard Saturdays and irregularly other days with relays of special events; usually has baseball game to about 0930. (Harrison)

Berlin, 6.710, has been heard in Britain at 1530 with Forces' request records; bad CWQRM; often takes dance music from British Forces' Network, Hamburg, at 1630; signs off at 1700 with "God Save The King." (Peace) Is in British Sector.

U. S. stations at Munich operate 1200-1700 on 7.290, 11.870, 9.540.

Leipzig now opens at 9.730 at 2200; Hamburg, 6.115, opens at 2300. (Beck) Measured Frequency of Leipzig is 9.728. (Arthur, Norris)

**Gold Coast**—From Head Office, Broadcasting Department, P.O. Box 250, Accra, Gold Coast Colony, the superintendent of broadcasting informs Kary, Pennsylvania, that while we are pleased to hear that our 19-m. transmissions (15.430) have been reaching you well in the past, it is not proposed at present to use that channel on regular schedules as our programs are normally directed within the Colony, thus requiring lower frequencies.

The 4.910 outlet is heard in New Zealand to 1300 when signs off with "God Save the King." (Cushen)

**Greece**—SVR, 13.670, Athens, has been heard around 1820 instead of SVS for relaying network reporters; after the broadcast, has been heard announcing as going over



October, 1947

## CURRENT CONVERSION

WITH **ATR** QUALITY PRODUCTS



## ATR "A" BATTERY ELIMINATORS

For DEMONSTRATING  
and TESTING AUTO RADIOS

New Models . . . Designed for Testing D.C. Electrical Apparatus on Regular A.C. lines. Equipped with Full-Wave Dry Disc Type Rectifier, Assuring Noiseless, Interference-Free Operation and Extreme Long Life and Reliability.

- Eliminates Storage Batteries and Battery Chargers.
- Operates the Equipment at Maximum Efficiency.
- Fully Automatic and Fool-Proof.
- Type 60-ELIA . . . Rated Output 6.3 Volts at 6.5 Amperes.

Dealer Net Price \$22.80

- Type 120C-ELIO . . . Rated Output 6.3 Volts at 14 Amperes.


Dealer Net Price \$37.20



## ATR AUTO RADIO VIBRATORS

Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction for Longer Lasting Life. Price are approximately 15% lower.

## ATR STANDARD AND HEAVY DUTY INVERTERS

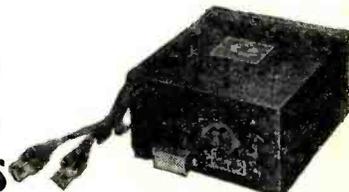


For Inverting D.C. to A.C. Specially Designed for Operating A.C. Radios, Television Sets, Amplifiers, Address Systems, and Radio Test Equipment from D.C. Voltages in Vehicles, Ships, Trains, Planes and in D.C. Districts.

Write for New ATR Catalog—Today!

AMERICAN TELEVISION AND RADIO CO.

Quality Products Since 1931

SAINT PAUL 1, MINNESOTA — U. S. A.

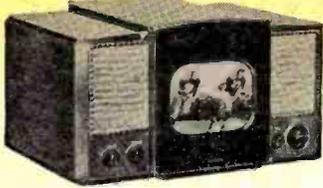

**RCA VICTOR  
EYE WITNESS TELEVISION RECEIVERS**

Flato Face Pictures, 13 Channels.  
Model 621TS—7" Set. . . . . \$296.80  
Model 630TS—10" Set. . . . . 432.60  
Model 641TV—10" Console, including Television,  
Automatic Gramophone, F.M. and A.M. radio. . . . . 888.00  
Prices above include original RCA factory installation in  
their service areas as well as guarantee for 12 months on  
the set and kinescopes. City sales tax where applicable  
added.

**LATEST TELEVISION COMPONENTS**

Part No.	Price
47204X	RCA FRONT END consisting of a complete television 13 channel tuning assembly including tubes, coils, switch, input converter, IF transformer, and fine tuning capacitors, ready to attach to a suitable IF input. . . . . \$97.50

**TELEVISION I-F AND VIDEO COIL KIT**

47204X1	RCA IF and Video coil kit contains all the necessary IF and video coils for a complete 4 megacycles wide band-pass as well as the sound IF and discriminator transformers for a complete television set . . . . . \$33.00
	I.F. Video frequency—25.75 MC
	I.F. Sound frequency—21.25 MC
47201D1	Deflection YOKE for use with 7DP4, 10DP4, 15DP4 magnetically deflected tubes . . . . . 13.75
47201D2	Deflection YOKE for use with 5TP4 projection kinescope . . . . . 14.90
47201X1	Yoke mounting hood for above yokes. . . . . 2.75
47202D1	Magnetic focusing coil for 5TP4, 10BP4, 15DP4 for use in series with divider. . . . . 9.10
48202D1X	Magnetic focusing coil for same as above but 10,000 ohm D.C. resistance. . . . . 9.90
47203D1	Ion trap magnet for tubes 7DP4 and 10BP4 . . . . . 6.50
47211T1	Horizontal output transformer with 9000 volt kick-back output for 2nd anode. . . . . 16.85
47208T8	Horizontal blocking sync. discriminator transformer as used in RCA AFC circ. . . . . 4.75
47208TX	Horizontal blocking oscillator transformer UTC high perm. iron. SPECIAL. . . . . 2.75
47201R1	Horizontal width control for use with 7DP4, and 10BP4 or 15DP4. . . . . 1.30
47201B1	Spherical mirror for use with 5TP4 in projection systems . . . . . 150.00
47201P2	Aspherical correcting lens to use with above mirror . . . . . 50.00
47204T2	Vertical output transformer. . . . . 9.00
47208T2	Vertical blocking oscillator transformer RCA . . . . . 5.70
475218	FRAME with shatterproof glass and rubber mask for use with 12AP4 tube. . . . . 8.00
475300	H.V. capacitor, .03 mfd 7500 volt working, grounded negative GE Pyranol. . . . . 3.75
475301	H.V. capacitor, .1 mfd 7500 volt working, grounded negative GE Pyranol. . . . . 7.50
475302	H.V. capacitor, 2x.1 mfd 7000 volt working, grounded negative GE Pyranol. . . . . 9.00
475303	H.V. capacitor, .05 mfd 18000 volt working, grounded negative Sprague. . . . . 9.90
475305	TRANSVISION 7 inch Television Kit, all parts and tubes included. . . . . 159.50
475306	Transvision 12" Television Kit. . . . . 289.50
473007	Thordarson Transformer, 15000 Volt AC and filament winding as required. . . . . 27.00

**RCA HIGH FREQUENCY SWITCH  
AND COIL ASSEMBLY**

RF unit, used in TRK12 RCA television receivers consisting of 5 band range switch with shield plate and mounting studs, including 5 polyester antenna coils, permeability tuned, each consisting of primary ring, secondary coil and primary mica capacitors. The assembly can be used in TELEVISION, F.M. and other HIGH FREQUENCY APPLICATIONS.  
CATALOG No. 5210—Special price. . . . . \$5.60

**RCA VARIABLE TUNING CERAMIC CAPACITOR**  
To be used in conjunction with the above switch assembly 2-4.5 MMFD.  
CATALOG No. 5211—Price. . . . . \$2.10

**CATHODE RAY TUBES**

Type	Make	List Price	Your Price
5BP1	DUMONT	\$24.75	\$ 7.95
5BP4	RCA	27.50	7.95
5CP1	PHILLIPS	24.50	7.95
5JP4	DUMONT	90.00	7.95
5TP4	Projection RCA	.....	67.50
7DP4	RCA	.....	14.95
7EP4	DUMONT	.....	23.25
7GP4	RCA	.....	24.25
9AP4	RCA	.....	62.50
10BP4	RCA	.....	49.50
12AP4	RCA	.....	75.00
15AP4	DUMONT	.....	129.50
20BP4	DUMONT	.....	270.00

All tubes are brand new, perfect, in factory sealed cartons, late production.  
Send 50 cents for complete catalog including diagrams for RCA, G.E., Dumont, Andrea and Viewtone Television Receivers.

World's First Specialized House in Television.

**TELETRONICS SERVICE AND SUPPLY CORP.**  
264 WEST 40TH STREET NEW YORK 18, N. Y.  
Phone PEnnsylvania 6-8730

to telegraphy. (Kary) Normally, SVS, 13.725, works WQV, 14.800, New York, evenings. (Arthur)

**Guatemala**—TGWA is back on normal schedule of 0730-1500 on 15.17; 1700-0015 on 9.76. TGOA, 6.102, signs off at 0000 except Saturdays when runs to 0100 (Sunday). (Beck)

**Haiti**—The new Haitian station, HHCN, 5.660, Port-au-Prince, is being heard fair early evenings to 2032 sign-off; has had aircraft QRM. (Kary)

**Hawaii**—KRHO, Honolulu, is scheduled 2030-0200 and 0230-0345 on 17.800; 0400-1000 on 15.250.

**Holland**—Lately, the "Happy Station Programs" from PCJ, Hilversum, have been shortened to 75 minutes, and usually have been preceded by a 15-minute newscast; it is expected that the full 90-minute session will be resumed shortly, according to Eddie Startz, who produces and presents the "Happy Station" periods.

"News on the Netherlands" is now presented daily (including Sunday) at 2130 and 2300 on 9.590, 11.730, and 6.020, beamed to North America; is also heard on these frequencies at 1730 to South America; at 1300 to Europe and South Africa; and is beamed on 17.77, 15.22, and 6.020 at 0430 to the Pacific Area.

**India**—Mysore's VU7MC, about 6.085, has been heard in California with a weak signal around 0630-0700. (Nankervis)

English periods listed by AIR include 2130, 15.190, 11.830, 11.760, 9.670, 7.290; 2230, 21.510, 17.830, 15.290, 15.160, 11.870, 0030, 21.510, 17.830, 15.190, 15.160, 11.870; 0130, 21.510, 17.830, 15.290, 15.190, 15.160, 11.870; 0300, 17.760, 15.290, 15.190, 11.830, 9.670; 0500, 21.510, 15.290, 15.160, 11.870; 0630, 21.510, 17.830, 15.190, 11.870; 0730, 17.760, 15.130, 11.830, 9.670; 0930, 21.510, 15.160, 11.870, 9.590; 1030, 21.510, 17.760, 15.160, 11.870, 11.830, 9.670, 9.590, 7.290; 1100 (BBC relay), 21.510, 11.870, 9.670.

I have had good reception recently of news from AIR at 0730 on the 15.130 channel; others listed for that time are weak here in the East.

**Iran**—EPB, 15.100, Teheran, has been heard here in West Virginia with erratic signals lately; some days is almost local in character, on others is wholly inaudible. A man reads the news at 0715 and sign-off is 0730.

**Java**—Radio Batavia appears to use approximate frequencies of 9.545, 10.365, 9.685, and 15.145 at 0530 when has news. At 0930-1000 use is made of 15.145 and 11.440, beamed in English to the United States. Frequencies of 19.350 and 18.600 are used usually around 1100-1200, last fifteen minutes being English to Europe.

Cushen, New Zealand, says Radio Batavia uses additional frequencies of 6.180, 10.060, and 4.960 in the 0530 newscast period, and also announces a frequency "in the 41-meter band" as parallel. Gillett, Australia, lists latest frequency of Radio Batavia as 6.175.

Ricardo, Holland, informs me that

**Etude's October Special  
BC-348  
RECEIVER**

Converted to 117 Volt 60 Cyc.  
A.C. Ready to Plug In and Use

- Heaters are completely rewired to 6.3 volt winding on power transformer
- Separate Power Switch
- AVC, STANDBY, MVC (Combined manual control operates RF & Audio Gain)
- Crystal Filter
- Beat Freq. Osc.
- Dual Phone Jack output 4000 ohms, with 300 ohm tap available internally
- High Ratio Vernier drive with Precision stability, no Backlash
- Six Bands cover ranges from 200 to 500 Kc. and 1.5 to 18 Mc.

We have a limited quantity of these excellent receivers at this special price. Send 20% deposit on all C.O.D. orders.

**\$5850**  
COMPLETE With 9 Tubes

Write for Bulletin describing other Etude specials and bargains

**ETUDE ELECTRONIC LABORATORIES**  
1133 Findlay Ave., New York 56, N. Y.

**"SOMETHING OLD,  
SOMETHING NEW"**

The "something old" is your amplifying system, the "something new" is

**"EXTENDED RANGE EXPANSION" and  
"ELECTRONIC ACOUSTIC  
EQUALIZATION"**

The combining result will be

**"PRESENCE OF SOUND."**

A listening ecstasy that no other amplifier can attain. Invert your frequency response curve in logarithmic relationship creating an augmented illusion of "DEPTH" in sound. Control your ACOUSTICS electronically. Submit a wiring diagram of your equipment and we will engineer these features to meet with individual characteristics and requirements of your circuits.

We will return your diagram and a complete set of blueprints and specifications including construction data from which you can build this adaptor that will combine all the above features within your instrument. Send Money Order or Check for \$15.00 to

**NATIONAL ENGINEERING SERVICE**  
POST OFFICE BOX 1449  
LONG BEACH 1, CALIFORNIA

**MEN ARE NEEDED FOR  
RADIO ENGINEERING  
TELEVISION  
ELECTRONICS**

Thorough training in radio, including fundamentals, math, repair, sales, broadcasting, communications, with modern laboratory facilities and experienced faculty.

**APPROVED FOR VETERANS TRAINING**  
Moderate tuition and living costs  
New Classes Start Each Month  
Dept. 1 Albuquerque, New Mexico

**EGGERT RADIO INSTITUTE**

**12 lbs. SURPLUS  
RADIO PARTS \$2.00**

A gold mine of parts for repairmen, amateurs, and experimenters. sockets, condensers, resistors, transformers, coils, hardware, wire, etc., etc. An outstanding bargain in usable parts! Send \$2.00 cash, check or M.O. today! (Pay small express charges on receipt.)

**ELECTRONIC DISTRIBUTORS, Inc.** Dept. A4  
622 W. Randolph St. Chicago 6, Ill.

**A. C. 110-VOLT MOTORS**

Selsyn Syncro Differential—New in Original Package.

A Bargain at **\$1.75** While They Last.

**LYELL HARDWARE**  
P. O. Box 5 Rochester 11, New York

the Bandoeng-Batavia stations (PMA, 19.345, PLA, 18.600, YDC, 15.145) are 3 kw. each and employ beam antennas N.W.-S.E., so as to be directed towards Malacca, Holland, Great Britain, Australia, and New Zealand; and that the 11.44 transmitter uses a rhombic antenna, directed towards San Francisco; PMA and PLA also use rhombic antennas, while YDC has a horizontal antenna system. He lists *English* transmissions on 15.145 and 11.440 at 0930-1000 daily, and on 19.345 and 18.600 at 1145-1200 daily; the 15.145 and 11.44 stations have Indonesian programs at 1730-2030, 2230-0130, and 0630-0925; Dutch at 0430-0630 and 1000-1100; these programs are relayed by "regional" stations on 28.9 m., 31.4 m., 3 kw., and on "local" stations on 61.7 m. and 115.3 m., 300 watts. Mr. Ricardo explains that call in *English* is, "This is Radio Batavia, Java;" for Dutch transmissions, "Hier is Radio Batavia;" and for Indonesian transmissions, "... disinih-la Poesat Radio Rismi Indonesia."

*Kenya*—Nairobi's VQ7LO appears to have settled down on 4.865; is seldom heard now on 4.885. (Pearce)

*Malaya*—Singapore's 15.300 and 15.275 channels of the British Far-Eastern Broadcasting Service are heard in Britain at 1145 with news. (Brownless) The 15.275 transmitter is best here in the East, mornings, but usually is only fair level.


The British Far-Eastern Broadcasting Service in Singapore has informed *Radio Australia* that they recently started using a 10-kw. short-wave transmitter; they plan to add at least two more to their service, for relay purposes, and to provide a service in the Malayan Union not covered by medium-wave programs, the letter stated. A South Australian listener recently reported test transmissions from Singapore in the 49- and 60-meter bands, which may be the new Malayan transmitters in operation.

*Mexico*—XDY, 9.925, heard on West Coast in Spanish at 2005-2035 and at other times. (Nankervis)

*Mozambique*—Lourenco Marques is fair level in Australia around 1600 on 3.490 while the 4.925 outlet, in relay, is a very fine signal. (Gillett)

Beira, in verifying for Gerald Nankervis, California, sent a nice card of red and green parallel stripes down through, on white background. Listed power as 300 watts, calls and frequencies as CR7IB, 7.255 (this one was heard by Nankervis), and CR7IC, 3.498; gave schedule of 0145-0545 and 1300-1500 daily; Sundays at 0400-0700 and 1300-1500. Verification was sent airmail but took 48 days to reach California.

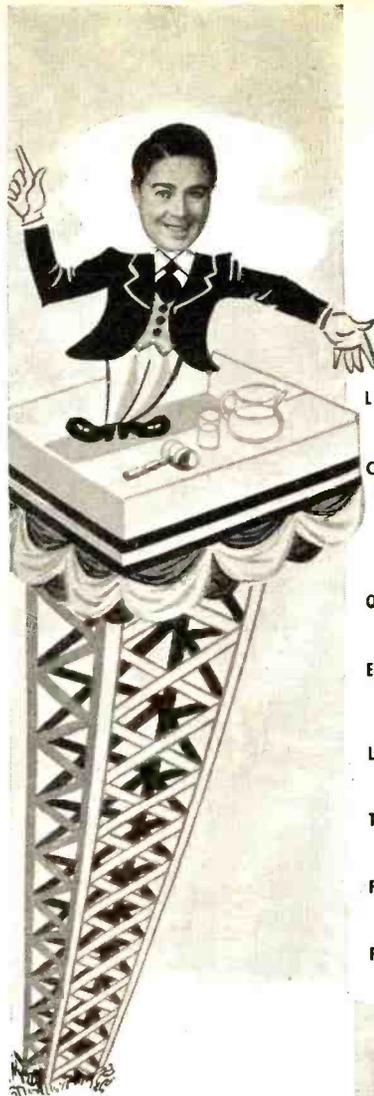The special program on July 13 from Beira lasted an hour; was directed to the United States and consisted of popular Portuguese music with requests for reports and calls to G. Nankervis in between discs. (Laubscher) The broadcast was inaudible in the United States, according to several monitors both East and West whom I asked to check it.



# BOB HENRY'S PLATFORM

## LOW PRICES

I guarantee to sell to you as cheap as you can buy anywhere.

## COMPLETE STOCKS

Hallcrafters, National, Hammarlund, Collins, Millen, RME, Pierson, Temco, Meissner, Supreme Transmitters, Meck, Gordon, Amphenol-Mims, RCA, Vibroplex, Sonar, all other amateur receivers, transmitters, beams, parts, etc. If it is amateur or communications equipment—I can supply it.

## QUICK DELIVERY

Mail, phone, or wire your order. *Shipment within four hours.*

## EASY TERMS

I have the world's best time sale plan because I finance the terms myself. I save you time and money. I cooperate with you. Write for details.

## LIBERAL TRADE-IN ALLOWANCE

Other jobbers say I allow too much. Tell me what you have to trade and what you want.

## TEN DAY FREE TRIAL

Try any receiver ten days, return it for full refund if not satisfied.

## FREE NINETY DAY SERVICE

I service everything I sell free for 90 days. At a reasonable price after 90 days.

## FREE TECHNICAL ADVICE

and personal attention and help on your inquiries and problems.



*Orders from outside continental U. S. A. also welcomed.*

*Write, wire  
or phone today*

Butler, Missouri **HENRY RADIO STORES** Los Angeles 25, Calif.

"WORLD'S LARGEST DISTRIBUTORS OF SHORT WAVE RECEIVERS"

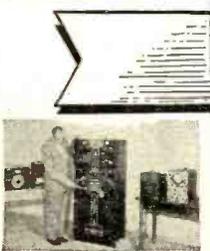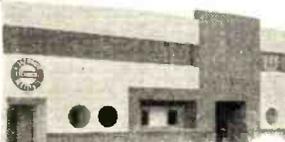**A Profession, Good money, and Independence. Train NOW for success tomorrow. Investigate Our Courses Today. Visit our classrooms.**



ALL CLASS ROOMS HAVE NEW and LATEST TEST AND LABORATORY EQUIPMENT AVAILABLE FOR STUDENTS' USE

**Learn RADIO-ELECTRONICS**  
APPROVED FOR TRAINING UNDER GI BILL

BIG OPPORTUNITIES now available for well trained men. Learn the magic of Television, Frequency Modulation, Transmitter and Receiver Theory. Instruction with Sound Motion Pictures. Start a spare time business while learning.

WITHOUT OBLIGATION SEND ME YOUR  
FREE 1947-1948 YEAR BOOK

Name..... Address.....  
City..... State.....

**ELECTRONIC TECHNICAL INSTITUTE**  
771 Venice Blvd., RM-9 Los Angeles 15, Calif., RICHMOND 9573

I am Interested in:  
 AMATEUR RADIO  
 COMMUNICATIONS  
 Television  
 Radio Servicing & General Electronics  
 Home Training  
 Amateur Radio  
 Correspondence Course

# Munger ELECTRO-BEAM Rotator

Illustrated Bulletin  
on Request




PRICED  
AT ONLY  
**\$69.50**

COMPLETE  
**ORDER ONE  
NOW!**

- Price Includes Reversible Electro-Beam Rotator and Accurate Direction Indicator.
- Foolproof Potentiometer and Meter Circuit. Calibrations in Both Degrees and Directions.

A SENSATIONAL VALUE!

Inquire About Our  
Time Payment Plan

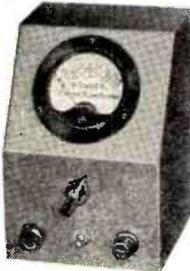

## Don't Lose those Good QSO'S While Turning Your Beam by Hand

There's no longer any need to run down stairs, out in the back yard to turn your beam. The Munger Electro-Beam Rotator's positive-action drive saves you those trips in any weather, any time of the day or night. A reversing switch mounted on the calibrated direction indicator permits you to peak up your own and received signals in a few seconds. Enjoy the thrill of holding those rare DX contacts right through heavy QRM! Ruggedly built for all-weather, year 'round operation without attention. Swings any 10 meter beam or a light 20 meter array at 1 R.P.M. Rotator weighs only 10 1/2 lbs. 115 V., 60 cycle operation.

### FREE Inspection Offer — No Risk

Send your check for \$69.50 for one Electro-Beam Rotator complete with Direction Indicator and instruction sheet. Pay small shipping charge upon arrival. If you are not completely satisfied, return the units in ten days and your money will be instantly refunded in full. You can't go wrong! Order your Munger Electro-Beam Rotator today! (Control-power cable supplied at 10c per foot in 50' or 100' lengths.)

MANUFACTURED AND SOLD  
EXCLUSIVELY BY

**Rex L. Munger Company**  
4707 Sheridan Road Chicago 40, Illinois



W9LIP

## TRANSCEIVER RT/7APN1 \$7.50

### ALTIMETER TRANSCEIVER RT/7APN1:

CONTAINS: 14 tubes: 3—12SJ7, 4—12SH7, 2—12H6, 1—VR150, 2—955 2—9004, Dynamotor, resistors AND GOBS of other valuable items.

A STEAL AT.....\$7.50

### FLEXIBLE TUNING SHAFTS:.....ONLY 15c per Ft.

Lengths 3 ft. to 30 ft. standard spline fittings—ideal for Rotary Beams! NEW!—SPECIFY LENGTH.

### WHIP ANTENNA: 24 ft. long.....Complete \$5.00

Comes complete in 8 sections that screw tightly together—made for SCR 284. Many Uses—You name it!

### THROAT MIKES:—Complete with chest switch..... 1.00

Includes—T46 chest switch, adapter and 9 ft. Jack. Get them now while they last!! —New!

### KEYS: BRAND NEW—J 38.....3 for 1.00

ALL MERCHANDISE CARRIES MONEY BACK GUARANTEE  
LIMITED STOCK! WRITE NOW

## ASSOCIATED SURPLUS CO:

10838 Ventura Blvd.

North Hollywood, California

### Mr. Radio Service Dealer

"Speed is our Motto"

One day service on all orders. None too small. Only Nationally Advertised Merchandise (No Surplus Handled). TUBES—Any quantity 50% off list.

Mail us your orders.  
Illustrated list on request.

**Bill Sutton's**

Wholesale  
Electronics

Fifth at Commerce

Fort Worth, Texas

## EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.

ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.



## INSTRUCTOGRAPH COMPANY

4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS

CR7IB has not been heard in Britain since April. (Pearce)

**New Zealand**—Latest information from Cushen, New Zealand, about the long-promised s.w. stations in Wellington is that the two 10-kw. transmitters with frequencies in the 19-, 25-, and 31-meter bands are expected to begin operations towards the end of the year. Mr. Cushen also reports ZLO, Waiouru Military Camp, North Island, is using call of *Radio Waiouru* in broadcasts daily on 6.800 from as early as 0145 to after 0430; no set schedule; gives sports results and plays modern recordings for troops in Japan; studios are at the camp, but it is likely that the transmitter is the old ZLT7 of the Post and Telegraphs Dept. in Wellington. (ZLT7 formerly operated on 6.715 around 0430 daily.)

**Northern Rhodesia**—ZQP is now scheduled on announced "31-, 41-, and 76.6 meters" at 1000-1200, daily except Saturday, to Africans only; no English; Saturdays, to Africans and Europeans, 1000-1200, with musical program (dance, cowboy, African, and request music), using English and African announcements; Sundays, 0400-0530 to Europeans in English only, and at 1030-1130 in English and African, including church service for Africans, hymns, and other sacred music. Woman announces both daily and Sunday. In daily beam, sign-on is with beating of tom-toms, on Sundays has march introduction. Usually has local news following sign-on. The 41-m. frequency appears around 7.285 and not 7.220 as listed by the station. (Laubscher) The 31-m. outlet (9.710) is heard irregularly in California, usually around 1000. (Dilg)

**Norway**—LCR is the call of the Oslo fone station on 19.930. Has been heard very weak at 0713 calling New York. (Kary)

**Palestine**—The Forces' Broadcasting Unit, Jerusalem, tested during July on 7.250, but on August 1 resumed regular schedule on JCKW, 7.220, at 1200-1600, except Sunday and Wednesday when carries a late night transmission at 1605-1800. Sometimes acknowledges reports over the air. (Laubscher) Tests heard in Britain. (Pearce) Were good level in Sweden, but at times suffered QRM from Rome on the same frequency; it was announced that after August 3, schedule on 7.250 would be 1600-1800 on Sundays and Wednesdays; said reception reports would be welcomed by No. 1, The Forces Broadcasting Unit, Jerusalem, British Forces in Palestine. (Zachrisson)

In verifying the 6.170 frequency for Flitcraft, Indiana, officials of the Jaffa station stated they had a "new" station on 11.720 and wished reports on that frequency. Roger Legge, New York, has heard this station (actually on 11.725) signing on at 2250.

**Panama**—HOLA, 9.505, Colon, is scheduled weekdays to 1700 when signs off with the Panama National Anthem; has English at 1600-1700; on

Sundays, signs off at 1600, on which day the *English* period runs 1530-1600. (Company)

**Philippines**—Cushen, New Zealand, has been advised by KZPI, Manila, that its sister-station, KZOK, is to be used *only* for Spanish-Tagalog transmissions, leaving KZPI for *English* broadcasts throughout. Cushen has heard KZOK on a medium-wave frequency of 1000 kcs.

KZPI has moved to about 9.500; the sister-station, KZOK, is using 9.695 (listed 9.692); these are *not* in dual. (Dilg) KZOK is believed to operate 1630-1100 daily, that being its schedule in the medium-wave band (1000 kcs.) (Radio Australia)

According to the Philippines Radio Training Magazine, the Government of the Philippines may acquire the surplus 50-kw. short-wave transmitter at Malolos from the U.S. State Department. It is proposed to utilize this transmitter to publicize and acquaint peoples of other nations with the development of the Philippines. (Radio Australia)

KZRH, 9.640, Manila, is heard weakly in South Africa from around 1000 to 1100 sign-off. (Laubscher)

**Portuguese China**—Radio Clube de Macau, in verifying by card and airmail letter, reported use of 200 watts to a pair of Osran MT9F tubes, antenna center-fed Hertz with tuned feeders; gave schedule as in Chinese, 0330-0600, and a Portuguese-*English* service at 0600-0830, with news (*English*) at 0650. (Cushen) Frequency is about 9.354.

**Portuguese Guinea**—Bissau, 16.350, has been logged after 0700; the 7.100 outlet has been heard at 1700-1745. (ISWC)

**Rumania**—Transmission from Bucharest on 9.25 begins at 1330 in Rumanian; German, 1345; French, 1400; *English*, 1415; begins and ends *English* period with announcement, "This is the Rumanian short-wave station, Radio Dacia Romana on 25- and 32.4 meters." Seems to be off Sundays. Signals weak in South Africa on 9.25, and the 25-m. outlet has not yet been logged. (Laubscher) Only the 9.25 outlet is heard in Britain. (Pearce)

**South Africa**—Capetown's 5.885 is still good throughout the 2345-0130 transmission, while Johannesburg's 6.007 is sometimes heard signing on in dual; latter is much the weaker; re-lays BBC news at 0100. (Beck)

Johannesburg's 3.450 outlet is fair strength in Australia to sign-off at 1605; also operates on 9.875 and is heard with BBC news at 1100. On Saturdays, Capetown's 5.885 appears to run to 1700. (Gillett)

**Spain**—Kenneth Dobeson, representative in Britain for Radio Nacional de Espana, lists Madrid, 9.368.4, 40 kw., French at 1330; German, 1400; Italian, 1410; Portuguese, 1420; Russian, 1435; *English*, 1500; Arabic, 1530; Spanish, 1545 to 1600 closedown; on Sundays schedule is slightly modified, with news (*English*) at 1545. Is also used daily to Latin America, 1830-2202. Alicante, 7.914.7, 1.2 kw., 0700-



## TELEX MONOSET— WHEREVER, WHENEVER HEADSETS ARE REQUIRED

MODERN • LIGHTWEIGHT • COMFORTABLE

Cleverly designed in tough durable Tenite, the TELEX Monoset is quickly replacing old-style, cumbersome headsets because it is made to wear under the chin instead of over the head. Precision-built magnetic receiver assures excellent fidelity.

The NEW Monosets incorporate a volume control feature that permits the wearer to control volume of sound at the point of reception. Write Department AU for information.

### Specifications

#### IMPEDANCE

2000 ohms—Part No. 2568  
500 ohms—Part No. 2569  
128 ohms—Part No. 2570

#### SENSITIVITY

88 d.b. above 000204 dynes per square centimeter for 10 microwatt input.

HEARING AT ITS BEST



**TELEX Inc.**

ELECTRO-ACOUSTIC DIVISION

TELEX PARK  
Minneapolis, Minn.

Canadian Distributors:

Addison Industries, Ltd., Toronto

**RCA Institutes, Inc.**  
Offer thorough training courses in all technical phases of Radio and Television

WEEKLY RATES      DAYS—EVENINGS  
**VETERANS:** RCA Institutes is approved under G. I. Bill of Rights  
For Free Catalog write Dept. RN-47  
**RCA INSTITUTES, Inc.**  
A Service of Radio Corporation of America  
75 Varick St., New York 13, N. Y.

**HARD-TO-GET WAR SURPLUS**

BC-221-AK FREQUENCY METERS. (With Modulation.) Like New	574.50
BC-454 RECEIVERS (3-6 MC.) Includes Tubes, Tuning Knob, Speaker Transformer. New	5.95
RA-20 POWER SUPPLIES 110 VAC. For the BC-312 and BC-342 Receivers	6.00
PE-103-A DYNAMOTORS 6-12 VDC. Input. 500 VDC. @ 160 MA. Output. New	7.50
OIL FILLED CONDENSERS. 3 MFD. 4000 VDCW. Sprague. New	4.95
813 TUBES. New. Filament Guaranteed	6.50

**NILES RADIO SUPPLY, Niles, Michigan**

**RECORD PLAYER**

**AT ONLY \$985 COMPLETE**



A complete kit at a new low price. Powerful rim drive motor. High output low pressure crystal pickup. Five inch Alnico 5 speaker. Dual tube amplifier. All wood cabinet. Durable leatherette covering. Including all necessary hardware, wire and solder. Model RP410 complete with all instructions, nothing else to buy. Ship. wt. 7 lbs. Cash with order or C.O.D. with 20% deposit. Send for our new free bargain list.

**HALLMARK ELECTRONIC CORPORATION**  
592 Communipaw Ave. Jersey City 4, N. J.

# GREATEST ACHIEVEMENT

in Recording History



**NO WIRE! NO TAPE!  
NOT A CYLINDER!  
INSTANTANEOUS RECORDING!**

The hit of the I. R. E. Show  
at Grand Central Palace!  
The sensation of the R.M.A.  
Chicago parts show!

10" wide, 13" long, 8" high \$79.50 F. O. B.  
Approx. 15 lbs. packaged \*N.Y.

Records a full 30 minutes on a 4 1/4" plastic disc! Costs less than 1/2c per minute! Full range high-fidelity music and voice recording!  
**YOU DON'T HAVE TO WAIT—Experimenters!**

Technicians! Hams!

It will be many months before the complete Wagner-Nichols unit—with speaker and amplifier—will be available to the general public.

However, there are a limited number of "knock-down" units immediately available for recording experts. Attachment to your own equipment is a matter of only a few minutes!

Read: TELE-TECH, June, 1947, pgs. 55-56—AUDIO ENGINEERING, May, 1947, p. 24, ff.—SCIENCE DIGEST, August, 1947, back inside cover—SCIENCE ILLUSTRATED, October, 1947.

Expert's Unit Includes:

Dual-function crystal recording and play-back recorder head (frequency response 50-5000 cycles flat within +2 D. B. signal to surface noise ratio, 35 D.B.) SPECIAL Sapphire Embossing stylus (.0005 radius) for both recording and reproducing—foolproof precision tracking mechanism embosses 416 lines per inch!—3 3/4" G.I. gear reduced motor set in shock-proof mounting for minimum vibration. D. B. meter mounted and wired directly on panel. Completely wired switches and special attachments, circuit diagrams and descriptive booklet—PLUS 1 doz. 4 1/4" vinylite recording discs. Additional discs supplied at \$2.00 per doz.  
\* 20% deposit required on C. O. D. orders. We pay shipping charges if payment accompanies order.

DISTRIBUTED BY  
**SOUND EMBOSERS, Inc.**  
P.O. Box 503, Times Square Station,  
NEW YORK 18, N. Y.

## CORRESPONDENCE COURSES IN RADIO and ELECTRICAL ENGINEERING

**ELECTRICAL ENGINEERING** Get good grasp of wide electrical field. Prepare yourself at Low Cost, for secure future. Modern course. So simplified anyone can understand quickly.  
**RADIO ENGINEERING** Extra fine course in radio, work. Trains you to be super-service man, real vacuum-tube technician. Servicemen needed badly. Diploma on completion. Many graduates earning big pay.  
Write Send postcard for Free Copies of \$25 Either school catalog. Full details, all Course about deferred payment plan, experimental kit, etc. Lincoln Engineering School, Box 931-R109, Lincoln 2, Neb.

Serving Radio & Appliances  
**SERVICE DEALERS**  
With FROM COAST TO COAST  
**4 JOB CARDS**  
ASK FOR SAMPLES  
**RADIO PRESS** MORGANTOWN WEST VIRGINIA

1000, 1400-1800. Tenerife, Canary Islands, EAJ43, 7.558, 0730-0900, 1230-1700. Radio Seu, Madrid, 7.141, EDV10, 10 kw., 1100 or 1200 to 1700. Oviedo, FET22, 7.130, 25 kw., 0730-0900, 1345-1830. Cuenca, EAJ7, 7.100, 2 kw., 0800-1000, 1400-0700. Cordoba, FET15, 7.042, 2 kw., 1400-1600. Valencia, 7.035, 1 kw., 0700-1000, 1400-1800. Malaga, EAJ9, 7.025, 2 kw., 0830-1000, 1500-0700. Valladolid, FET1, 7.006, 0730-0900, 1500-1800. Tetuan, Spanish Morocco, 7.067, 0230-0300, 0830-1000, 1330-1800, with French at 1445, Arabic at 1500-1600. Mr. Dobeson reports that four 100-kw. short-wave transmitters are being built in Spain by *Marconi Espanola*, type TBS802, as used by the BBC for its Overseas Services, and that the contract is worth 270,000 English pounds. He says that Radio International, Tangiers requests reports on its 6.200 outlet, power 1 kw., scheduled 0800-1100, 1400-0700; QRA is Herbert R. Southworth, Director General, Radio International, 34, Calle Goya, Tangier, Morocco.

*Sweden*—The Swedish Solar Eclipse Expedition in Brazil, SH2-D, was heard in Sweden. Listeners can QSL via S.S.A., Stockholm 8, Sweden (Sverige).

*Switzerland*—Roger Legge, New York, furnishes us with this current list of Swiss stations (those marked with an asterisk are now in use): HED5, 9.545; HED6, 9.655; HED7, 15.120; HED8, 17.770; HED9, 26.020; HEI2, 6.345; HEI3, 7.210; HEI4, 9.539; HEI5, 11.715; HEI6, 11.775; HEI7, 15.320; HEI8, 17.795; HEI9, 21.605; HER2, 6.055; \*HER3, 6.165; \*HER4, 9.535; \*HER5, 11.865; \*HER6, 15.305; \*HER7, 17.784; HER8, 21.520; HER9, 25.640; HEU2, 9.520; HEU3, 9.665; HEU4, 11.718; \*HEU5, 11.815; \*HEU6, 15.315; HEU8, 17.775; HEU9, 21.705.

*Trinidad*—By this time it is likely that VP4RD, Port-of-Spain, will be on the air with regular transmissions. Watch for this one around 0600 on 9.625; other frequencies that may be used are 6.085 and 12.950.

*U.S.S.R.*—Moscow's 11.630 outlet is heard signing off with "The Internationale" at 1900. (Kary)

North American morning beam is announced for 0745-0815 on 11.75, 15.11, 15.17, 15.23, 17.83, 21.53; the evening period runs 1820-1950 on 11.89, 15.17, 17.83, with 15.23 in use 1820-1930. (Beck) A frequency of about 17.839 is heard with loud signals in the 1820-1950 beam, and sometimes 17.860 is used also.

Miers, Berlin, lists *English* broadcasts from Moscow, presumably beamed to Britain, at 11.30, 15.36, 11.63, 9.61 (one-half hour, news, Soviet papers review, music and on Thur., Fri., Mon., Tue. has "Russian By Radio at 1145); 1330, 15.36, 11.63, 9.61, 6.02 (news, commentary); 1500, 15.36, 11.63, 9.61, 6.02 (news, commentary and on Thur., Fri., Mon., Tues. has "Russian By Radio"); 0730, 15.36, 11.63 (one-half hour, news); on Saturdays at 1500 and Sundays at 1145 presents "Letter-

## ORDER NOW

SCR 522 (with tubes, good condition control box, and plugs) . . . . . \$28.50  
BC 348 Army Receivers (Good Condition). \$39.50  
300 Ohm Amphenol Twin Lead, per 100 ft. . . . . \$ 2.90  
75 Ohm Amphenol Twin Lead, per 100 ft. . . . . \$ 2.00  
Kilowatt 75 Ohm Amphenol Twin Lead, per 100 ft. . . . . \$ 7.20  
Complete stock of 80 and 40 meter MONITOR Crystals in holders, any frequency within 1 KC . . . . . each \$ 2.80  
3 Gang 410 Mmfd. Per Sect. Cond. . . . . \$ 2.95  
Excellent quality . . . . . \$ 3.00  
National ACN Dials . . . . . \$ 3.00  
24G Transmitting Tube . . . . . \$ 1.00  
2C40 Lighthouse Tube . . . . . \$ 3.95  
2" PM Speaker (Bakelite Cased) . . . . . \$ 1.95  
Used in Walkie Talkie . . . . . \$ 1.25  
LM 13 Portable frequency meter boxes in canvas case (New) . . . . . \$ 1.25  
SIREN, Commercial type hand operated, very loud noise, gov't cost \$21.00. Spec. \$ 4.95


Send for Our Special Bulletin of Government Surplus Items

## DOW RADIO

1759 E. COLORADO ST. PASADENA 4, CALIF.  
Pasadena Phone—SYcamore 3-1196  
Los Angeles Phone—RYan 16683

Building A TELEVISION Set? Use A KILOVOLTER

HIGH VOLTAGE POWER SUPPLY

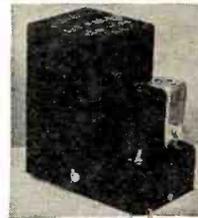

4000-6000 VOLTS D.C. \$17.95

- It's Safe
  - Saves Trouble
  - Small 4x6x6: 2 Pounds
- SEND CHECK, M.O. OR SEE DEALER  
Write for Folder

Model 6  
**C-B MFG. CO.**  
412 W. 37 ST. N. Y. 18, N. Y.

## COMPARE THESE VALUES!

Your Choice **50c** Each

DRY ELECTROLYTICS 150 WVDC

SOLAR . . . . . 40x20x20 MFD 100%  
SOLAR . . . . . 20x20x20 MFD  
SPRAGUE . . . . . 50x30 MFD  
SPRAGUE . . . . . 40x20 MFD

Buy as many as you need. No order too small or too large. Subject to prior sale.

Write today for parts bulletin.

**INTERSTATE RADIO & PARTS CO.**  
6357 So. Ashland Ave. Chicago 36, Ill.  
Phone GROvehill 7588

## RADIO

Technician and Radio Service Courses  
**FM and TELEVISION**

American Radio Institute  
101 West 63rd St., New York 23, N. Y.  
Approved Under GI Bill of Rights  
Licensed by New York State

## SENSATIONAL VALUE

5000 OHM PER VOLT MULTIMETERS  
0/8/150/300/1500 . . . . . D.C. VOLTS  
0/0.5/8/30/150 . . . . . D.C. MILLIAMPERES  
0/5000/10,000/500,000/5 MEG. . . . . OHMS  
0/8/30/150/600 . . . . . OUTPUT & A.C. VOLTS  
-8 TO +50 . . . . . (4 Ranges) . . . . . DECIBELS  
REGULAR PRICE—\$25.00 OUR PRICE—\$15.00  
Test Prods—59 cents

**REMER RADIO**  
5904 S. Princeton Chicago 21, Illinois

box Program," asking for reports to Radio Moscow, Overseas Service, English Programs, Moscow, Soviet Union. This schedule also given by Harrison, England.

Vatican—HVJ, 9.660 and 15.095, heard with news at 0900. (Harrison) During the winter this period will be at 1000 instead of 0900.

\* \* \*

### Last Minute Tips

Mervyn Laubscher, South Africa, reports that CR6AA, Angola, "is definitely on the air again; heard to sign-off at 1430 on about 7.17-7.18; difficult to determine sign-on due to terrific amateur QRM, but is heard just after 1300, so presume signs on at that hour; this is *not* a 'Radio Clube' station; only gives call as far as I can make out. Slightly below CR6AA is another strong signal from 'Radio Clube de Louanda;' call sounds like CR6RB, although this closes with Benguela; schedule is 1330-1430 daily. A 'new' Portuguese-speaking station is heard on about 9.29 with very weak signals, signing off at 1400, sometimes as early as 1330."

Pearce, England, says the Arabic transmission on about 6.782, reported by some as from Baghdad, Iraq, is heard to 1600 sign-off, after time-pips; he believes this is Jaffa's 6.790 outlet, and *not* Baghdad.

Freemantle Overseas Radio, Ltd., 18, Park Street, London, W.I., and New York, no longer represent *Radio*

*Andorra* and cannot provide information or verifications. (ISWC)

*Radio Makassar*, 9.365, now signs off as "the capital of East Indonesia of the Indonesian Archipelago." (Dilg) Should be running now to 0930, with news (*English*) at 0800 on Mon., Wed., and Fri.

Recently when signing off in *English* at 1528 on the 6.030 frequency, *Radio Moscow* announced would be pleased to receive letters from listeners, addressed to Listeners Section, Radio Moscow, U.S.S.R. (Pearce)

The *S.S. America*, heard on July 22 when 1000 miles from New York, verified on prepared form sent the station, and enclosed colorful postcard view of the ship; transmitter used is *RCA* 8009-A, 600 watts output, with four 813's in the final amplifier stage. (Kary) Call appears to be WEDI.

Peddle, Newfoundland, sends these schedules of VONH, 5.970, St. Johns: 0830-1230 and 1630-2200; news 1200, 0530, 0615, 2100 (BBC), and 2130. Mr. Peddle says that VONH has been heard in England, Gibraltar, North Africa, Barbados, eastern U.S., Canada, and Greenland, although power is listed as only 300 watts. Studios are in the Newfoundland Hotel in St. John's; programs are fed by underground cables to the transmitter at Mount Pearl, a park about 6 miles away. A dipole antenna is employed.

A new Dutch station in Java has been heard on 11.030 with bad CWQRM; identification was frequent-

ly given but not understandable; program consisted chiefly of music with lots of Forces' request records and messages from Holland; gave schedule as 1830-2030, 1030-0130, and 0430-1130. (Laubscher)

A station using a Scandinavian language is heard on 6.120 until closing at 1600; believed to be OIX-1, Finland. (Gillett)

*Radio Noumea*, 6.16, New Caledonia, is scheduled 1800-1900 and 0330-0500. (Gillett)

British radio publications list Azerbaijan, Iran, at 1200-1300 on 12.180. (Harrison) This may be a harmonic of *Radio Tabriz*, listed 6.087. A station heard in Australia at 0815 on 11.965 is believed to be *Radio Tabriz*; had native-type music to 0830, then 5 clock chimes were sounded; left air abruptly at 0920. (Gillett)

Moscow's Latin American beam is on 17.83, 15.36, 15.17, 11.63 (Lenin-grad), 2000-2230. CBLX, 15.09, Montreal, now often runs as late as 2200. (Beck)


XGOA, 15.35, Nanking, has news at 0400; 9.73 outlet carries a separate program at that time. (Balbi)

Due to space limitation, the s.w. list recently compiled by Arne Skoog, Swedish DX-er, for "Roster i Radio," Box 16174, Stockholm 16, Sweden (Sverige) had to be run in three issues of that publication; anyone desiring this list can obtain the three issues by sending two IRC's to the address just given. . . . . K. R. B.

# Red Hot

## BROADCAST RECEIVER

BC-946-B

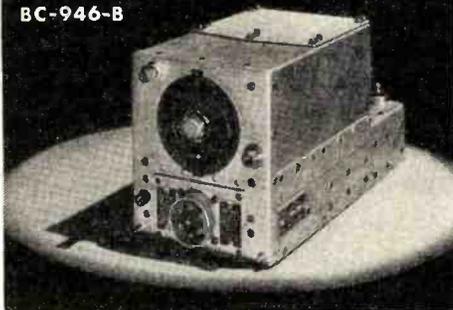

### At low cost

An extremely sensitive 6 tube receiver for the broadcast band with calibrated dial. Has one RF and two IF stages all with iron core coils and air trimmers. Compactly built. Makes an exceptionally "hot" car radio, portable, P.A. tuner, or home radio. Brand new, complete with tubes and modification data, less power supply. Stock No. B-422. Shipping wt. 9 lb.


We have sold hundreds of these receivers at \$14.95. **\$12.95**  
Now a new shipment at a new lower price of only --

### SPARE PARTS KIT

- 3 - BK-35 SPDT Relays Stock No. B-712
  - 6 - AF Chokes 23 hy, 3 ma.
  - 6 - RF Chokes 15.8 microhenry Shipping
  - 2 - 17 mmfd Var. Condensers weight 5 lb.
  - 2 - Bakelite Octal Sockets
  - 2 - Ceramic Octal Sockets
  - 30 - Mica Capacitors (4 values)
  - 10 - .01 mfd 400V Molded Paper Capacitors
  - 5 - .5 mfd 400V metal cased paper capacitors
  - 10 - 50 mmfd ceramic capacitors
  - 30 - 1/2 watt carbon resistors (5 values)
  - 6 - small ceramic feed-thru insulators
- And other miscellaneous parts.

The relays alone are worth more than the cost of the kit. Originally used in Marker Beacon Receivers, they have SPDT contacts and are very sensitive. Closing current .5 ma, opening when current drops to .2 ma, 10800 ohms DC resistance. Ideal for keying monitors and all types of plate current control circuits.

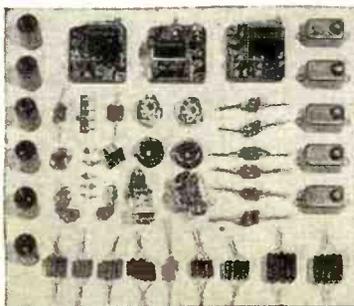Over \$40.00 worth of brand new useable radio parts - all for only **\$5.95** PER KIT



Special 5BP4/1802-P4 Cathode Ray Tube - 5 inch medium persistence, white fluorescence screen. Used in BC-412 and BC-612 Radar **\$3.95** ea. Scopes. Excellent for television receivers and oscilloscopes. For only -

### RCA AVT - 112 A AIRCRAFT TRANSMITTER

- Operates on 6 to 12 volts, easily converted to 24 volt operation.
- Frequency coverage 2500 to 6500 kc.
- 6V6 Xtal Osc., 6V6 Pwr. Amp., 2-6V6 modulators.
- Electron-eye Tuning Indicator.
- Intercom Circuit Incorporated.
- Compactly built (5-3/8"x6-1/4"x4-7/8") for aircraft use. Makes an ideal portable xmttr for hams and other services.
- Complete with 6 tubes and instruction book, less power supply and xtals.


Stock No. B-652 **\$12.95**  
Shipping weight 8 lb.


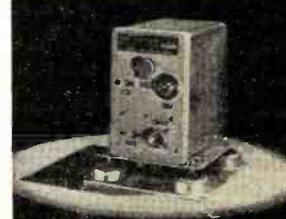
### BC - 1023-A MARKER BEACON RECEIVER

- Designed for reception of modulated Marker Beacon signals on the 75 mc. band.
- Variable tuning permits 62 to 80 mc coverage.
- Sensitive relay circuit can be used to control indicator lamp, or external circuits for opening doors, etc.
- Plates and filaments operate directly from any 12 to 14 volt DC supply.
- Brand new complete with tubes, shock mount and instruction book. Dimensions 3 1/2" x 5-3/8" x 5-3/8".

Stock No. B-567 **\$4.95**  
Shipping weight 4 lb.



### 75 to 150 mc. HETERODYNE FREQUENCY MONITOR

- For checking frequency of transmitters and receivers in the range of 75 to 150 mc. Battery operated - accurately calibrated. Calibration charts and diagram furnished. Complete with 3 tubes, less batteries.

Stock No. B-697 **\$14.95**  
Shipping weight 7 lb.

One set of batteries \$2.59



TERMS: Orders under \$3.00, cash with order; orders over \$3.00 require 20% deposit, balance C.O.D.

**SREPCO**  
STANDARD RADIO & ELECTRONIC PRODUCTS CO.  
135 E. SECOND ST. DAYTON 2, OHIO.

All prices are net, f.o.b. Dayton, O.

# SENCO DECLARES A BUYER'S DIVIDEND

## 100,000 RADIO TUBES

Every tube guaranteed. Every tube in carton.

Type	Lots of 10		Type	Lots of 10	
	Each	Each		Each	Each
1H5GT	59c	45c	7X7	44	35
1U5	36	30	7AF7	44	35
1N5GT	59	45	14X7	44	35
1V	45	39	12A8GT	54	45
1L4	55	49	12C8	80	70
2A5	65	55	12J5GT	49	39
3Q5	79	70	12J7GT	45	39
5U4G	55	40	12K7GT	45	39
5W4GT	40	36	12K8	65	59
5Y3GT	40	37	12Q7GT	45	39
5Y4G	40	37	12SA7GT	40	32
5Z3	40	37	12SQ7GT	40	32
6A7	55	45	12SK7G7	45	35
6A8GT	59	44	12SJ7GT	55	50
6AC7	65	60		39	30
6BA6	50	45	41	45	40
6B7	55	49	42	47	42
6C6	45	37	45	49	39
6C8G	45	37	47	49	41
6D6	45	37	56	49	39
6F6GT	45	40	57	45	39
6H6GT	45	40	58	45	39
6J5GT	55	50	71A	39	29
6J7GT	42	38	75	50	40
6K7GT	49	40	76	45	39
6N7	95	83	77	40	32
6Q7GT	47	42	80	40	38
6U7G	40	35	84/6Z4	45	36
6V6GT	59	49	25L6GT	60	50
6X5GT	49	40	25Z5	59	47
6SA7GT	44	37	25Z6GT	55	43
6SJ7GT	44	37	35L6GT	60	50
6SK7GT	44	37	35W4	45	40
6SL7GT	55	47	35Z3	44	35
6SN7GT	55	47	35Z5GT	49	39
6SQ7GT	47	42	50L6GT	55	45
6SG7	44	39	11Z23	55	45
6ZY5G	45	40	11Z26GT	99	89
7B6	44	35	12A7E	55	45
7B7	44	35	12BA6	55	45
7C6	44	35	12BE6	55	45
7C7	44	35	50B5	42	32
7Y4	44	35	32L7GT	60	50

### VM MIXER CHANGER

Model 200B, 2 Post.

Sensational! Plays 10" and 12" records intermixed with no adjustment. Light, crystal pickup. One control knob for on, off, manual, automatic, press to reject. 110 Volt, 60 cycle, noiseless motor. 15 x 14 x 7 7/8" H. Wgt. 16 lbs. Only \$15.95

### SPEAKER SALE Limited Quantity

4" P.M. Speaker	\$1.19
5" P.M. Speaker	1.15
6" P.M. Speaker	1.55
8" P.M. Speaker	2.75
Lot of 12	30.00
12" P.M. Speaker	5.95
Alnico 5 magnet	ea. 5.95
Lots of 12	66.00

General Instrument De-Luxe Record Changer With Automatic Stop  
Plays ten 12-inch or twelve 10-inch records at one loading, and stops automatically after last record is played... \$18.95

### OAK RECORD CHANGER-AC

110 Volts 60 cycle 2 Post—plays 10—12" or 12—10" records. Lightweight Crystal Pick, up. Noiseless Motor. \$17.45

\$29 Push Pull twin-unit. Beam power amplifier tube... \$1.49 ea.

40 x 40 Electrolytic Cond. 150 V. \$ .49  
50 x 30 Electrolytic Cond. 150 V. \$ .49  
30 x 20 at 150 V. and 20 mid. at 25 Volts. \$ .45

120 Mil Power Transformer  
Primary 110 V. Secondary 6.3 Rectifier 5 V. H.V. 600 V. C.T. \$3.25

225 Mil Power Transformer  
Primary 110 V. Secondary 6.3 Rectifier 5 V. H.V. 600 V. C.T. \$4.25

Mallory 6 V-4 Prong Auto Vibrator \$1.19

### LEADING BRAND AC PHONO MOTOR

60 cycles, 115 volts with Turntable with Standard Make Crystal Pickup. Complete \$4.35



25% deposit on all orders, balance C.O.D., F.O.B. N.Y.

**SENCO RADIO, Inc.**  
96 WARREN ST., N. Y. 7, N. Y.  
TEL. CORTLANDT 7-6065

### Television Tubes

(Continued from page 48)

If serious aberration of the televised scene is to be avoided, it is of major importance in low velocity scanning that the electrons strike along axial lines perpendicular to the mosaic. The rather unique effects of combined electric and magnetic fields act to produce this. Horizontal deflection is caused by means of an axial magnetic field acting in conjunction with a transverse electrostatic field. Electrons in motion through this combination are forced to move sidewise, that is, at right angles to their original paths.

A transverse magnetic field generated by the vertical deflecting coils accounts for the downward and retrace vertical motions of the scanning beam. Force fields in operation are indeed a thought provoking subject. Their efficient application in the orthicon attests to their remarkable versatility in later developments.

Highly advantageous results can oftentimes be achieved through a combination of similar and yet diverse electronic techniques. The image iconoscope is an excellent illustration. Its sensitivity range is notably increased through the actions of both image dissector and basic iconoscope principles.

Up to this point consideration has been given to camera tubes containing but a single mosaic. In the image iconoscope good use is made of the photoemissive properties of an additional mosaic called the photocathode.

Optical to electrical conversion is accomplished by focusing the televised image upon the back area of the photocathode. The front area is covered with the light sensitive globules. Light energy, proportional to the scenes' characteristics, passes through this plate thereby releasing electrons from its front surface.

An opposite mosaic, chiefly responsible for the camera tube's output, is located at the other end of the glass enclosed envelope. Electrons emitted by the photocathode are drawn to this. Increased numbers of corresponding secondary electrons are re-

leased when photocathode electrons strike this surface.

Scanning action is accomplished at this point by means of an electron gun located in the side of the tube. Additional electrons released by the scanning beam are picked up by the collector anode. From here on the operation and signal conversion is appreciably the same as in the conventional iconoscope.

A rather interesting feature of the image iconoscope is the scanned mosaic. This usually consists of a china-coated, flat metal or mica plate having high secondary emissive characteristics.

With the introduction of the image orthicon, Fig. 5, leading broadcasters have agreed that the art of television has at last grown to its full maturity. Its unique adaptability to both indoor and outdoor televising is amazing. Football, baseball, and tennis games, in fact, all outdoor activities can now be televised easily without too much worry about overcast or cloudiness. Its sensitivity is so great that this tube is said to be capable of televising a person by the light of a single candle placed some five or six feet away.


By means of lens action, a photosensitive surface inside the face of the glass envelope absorbs light from the televised object or scene. Photoelectrons emitted from this source, which incidentally has a greater sensitivity than either the orthicon or iconoscope mosaic, are then attracted towards a fine sieve-like grid.

With the exception of this grid which is kept at positive potential with respect to the photocathode, photoelectric action up to this point is quite similar to that of the orthicon.

Most electrons upon reaching the grid are accelerated through it to strike upon a thin sheet of specially prepared glass placed directly behind. Secondary electrons in greater proportion than primary or incident electrons are thereupon released. The glass target consequently develops a positive charge which appears on its opposite surface.

Glass was always thought to have good insulating properties. In the image orthicon, however, the glass is only about .0001 of an inch in thick-

Fig. 5. Simplified functional diagram of the image orthicon tube.

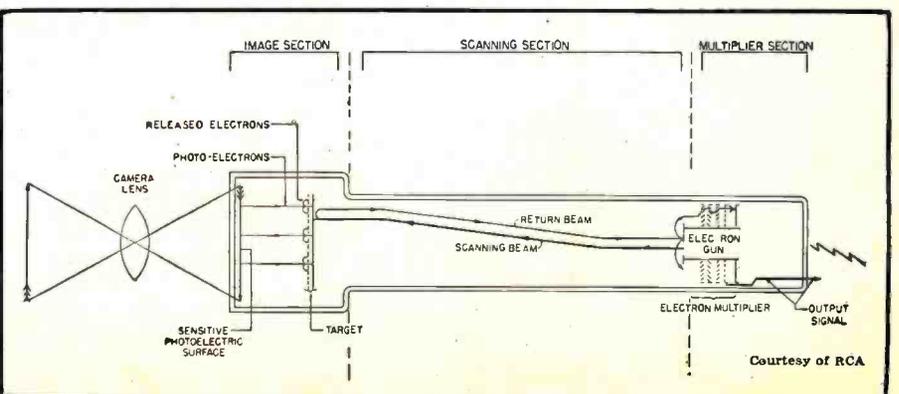

ness and through the magic of electron physics what happens to one side of it also happens to the other.

Scanning is accomplished by influencing the action of an electron stream, the velocity of which is accurately controlled. This enables the electrons to hit the target area, rebound and return to a collector by appreciably the same path. Modulation of the return trace is responsible for a signal appearing at the input of the electron multiplier located in the base of the tube.

Electron beam modulation occurs in accordance with the charge distribution over the scanned area. Predominantly positive areas absorb a greater number of electrons from the scanning beam, therefore fewer return and multiplier action corresponds to low signal levels.

Darker portions of the scanned area, being less positive, attract fewer of the electrons. The greater number of electrons present at the multiplier's input is therefore comparable to increased signal output.

Television, up to the present, has been fraught with grief, but a glimpse into the future seems to justify the hours of experimentation as coast-to-coast television, inter-continent programming and transoceanic television move a step closer to reality.

The author wishes to express his appreciation to Mr. E. L. Bragdon, Department of Information, Radio Corporation of America, and Mr. E. E. Ferrey, Assistant Director of Public Relations, Farnsworth Television and Radio Corporation for their efforts in securing data pertinent to the preparation of this article.

**BIBLIOGRAPHY**

Dunning, J. R. and Paxton, H. C.: "Matter, Energy and Radiation," McGraw-Hill Book Company, Inc., New York.  
 Fink, Donald G.: "Principles of Television Engineering," McGraw-Hill Book Company, Inc., New York.  
 Larson, C. C. and Gardner, B. C.: "The Image Dissector," Electronics, October, 1939.  
 Maloff, I. G. and Epstein, D. W.: "Electron Optics in Television," McGraw-Hill Book Company, Inc., New York.  
 Rose, A., and Iams, H.: "The Orthicon, a Television Pick-up Tube," RCA Review, October, 1939. "The Orthicon," Electronics, July, 1939.  
 Zworykin, V. K., Morton G., Flory, L.: "Theory and Performance of Iconoscope," Proceedings of the IRE, August, 1937.  
 Zworykin, V. K.: "Iconoscopes and Kinescopes in Television," RCA Review, July, 1936.

-30-

"We now leave the air due to a bad coil in your radio. Call Waymouth 4216 for a Repairman!"

# Masco News

## NEW BIG VALUE INTERCOM. MODEL JMR MASTER AND REMOTE U. L. APPROVED!

**Opens Up New Markets**

OFFICES

HOMES

DOCTORS

Stores, dentists, lawyers, merchants, farms all potential sales.

**Complete, Ready-to-Use**

Model JMR consists of a packaged Master and Remote, including tubes and 50 feet of cable. Latest design! Top quality! Low priced! Simple to install. Easy to operate.

List Price..... **\$39.95**  
 Add 5% West of Rockies  
 Contact your local Masco dealer for immediate delivery.

**Features of Model JMR**

- 117 Volt AC or DC operation.
- 2.5 watts of power.
- 4 in. PM Alnico V Speaker.
- Volume control with on-off switch.
- Separate press-to-talk switch.
- Remote station has press-to-talk switch.
- Attractive cast aluminum housing, Hammertone finish.

**ALSO AVAILABLE...** A complete line of U.L. Approved Intercommunication Equipment.  
 For descriptive literature or other information write directly to factory. Dept. N.

**MARK SIMPSON MANUFACTURING CO., Inc.**  
 32-28 49th Street, Long Island City 3, N.Y.

**SOUND SYSTEMS and Accessories**

Ravenswood 8-5810-1-2-3-4

## U.S.R.S. MONTHLY SPECIAL

Stock No.	No. Tubes	Net Price	Plate V.	Ma.	1st V.	Fil. A.	2nd V.	Fil. A.	Mtg. Centers	Wt. Lb.
15-000	4	<b>\$1.67</b>	650	40	5.0	2	6.3	2	2 x2½	2
15-001	6	<b>1.98</b>	675	50	5.0	2	6.3	2	2 x2½	4
15-003	8-11	<b>3.24</b>	700	100	5.0	3	6.3	4	2½x3½	6
15-011	6	<b>1.98</b>	675	50	5.0	2	2.5	7.5	2 x2½	3

## POWER TRANSFORMERS

Made of selected materials. Conservatively rated. Conforms to RMA standards. Primaries 115 Volt, 50-60 cycle AC.

## U.S.R.S.

**U. S. RADIO SUPPLY**  
 5116 HARPER AVENUE  
 CHICAGO 15, ILLINOIS  
 DEPT. NE 9


## UNIVERSAL OUTPUT TRANSFORMERS

To match impedance of single or push-pull tubes. Secondary 1.25 to 4.95 ohms. Housed in horizontal channel Mounting centers 2¼". Shpg. wt. 1 lb. 15-055 Transformer—net 79c.

Write for Free Illustrated Buying Guide
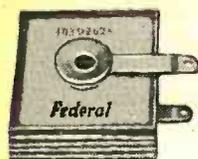
# PEERLESS PACKS Value PUNCH

The more you buy, the more you save  
Peerless Scoops the Market



100 MA  
**FEDERAL  
SELENIUM  
RECTIFIERS**

**64c**

in lots of 12 or more

List price . . . \$1.60

6 to 11 . . . 69c

1 to 5 . . . 75c

The Famous Federal Selenium Rectifiers at a fantastically low price. They're 100 mill rectifiers and suitable for any number of purposes in rectifier circuits. Replaces 29 different types of rectifier tubes, including 11726, 11723, and 3523. Size: 1 1/4" x 1 1/4" x 1 1/8". Fits almost anywhere, has an extraordinarily long life and runs continuously cool. Gives instantaneous starting. A real money-saver!

Sensational value! Famous brand!

**6-tube, AC-DC Superhet**

**RECEIVER \$1395  
CHASSIS**

with tubes  
completely wired  
and tested.

Worth \$34.95

We can't tell you the name, but you'll recognize this famous brand instantly! They're being sold everywhere at full list. Only PEERLESS can bring you this fabulous value.

Imagine getting all this for only \$13.95: 6-tube AC-DC Superhet radio receiver. Receives standard broadcast band. Licensed under Hertz patents. Has a full-vision, illuminated slide-rule dial and scale. Powerful, full-range, 5" Alnico V PM speaker. Has exceptionally high sensitivity with high signal-to-noise ratio and high power output with low distortion. RF stage precedes converter tube. Beam power output. Tube complement: 2-12SK7; 1-12SA7; 1-12SQ7; 1-35Z5; 1-35L6. For 105-125V, 50-60 cycle AC operation. Mounted on laminated base, ready for installation. Dimensions: 3 3/4" x 10" x 7 1/4". Shpg. wt. 10 lbs.

**HAMS**

PEERLESS PROVES  
IT WITH PRICES

Hallicrafters S38 . . . comp. . . . \$47.50

Hallicrafters S40A . . . comp. . . . 89.50

National NC-46 . . . comp. . . . 107.40

All prices F.O.B. Jamaica, New York.  
Include postage. Write Dept. RN4.

**Peerless**

**RADIO DISTRIBUTORS, INC.**

92-32 Merrick Rd., Jamaica 3, New York

Branch: 71 Murray St., New York 7, N. Y.

# TELEVISION

**... KIT!**


Only **\$165**

You Can Build Your Own

No knowledge of television, radio or the ability to read circuit diagrams is required. If you can use simple tools and possess an average mechanical aptitude, you can easily assemble this expertly engineered television receiver into a device that will net long hours of unending pleasure.

It's Easier to Build the Best!

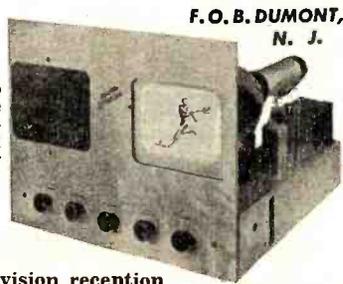- FM sound—high fidelity for clearest tone
- 20 tubes—pre-tested to assure perfect television reception
- 5 channel pre-wired RF Unit—3 channels tuned to your locality
- 7" brand name picture tube—pre-tested for accuracy
- Complete antenna—60' lead-in
- Hardwood veneer front panel
- 3.5 megacycle band width



F. O. B. DUMONT,  
N. J.

TRADE INQUIRIES  
INVITED

See your Dealer or write . . .

**REPUBLIC TELEVISION, INC.** DEPT. RN-10  
DUMONT, NEW JERSEY

## AUTOMATIC IRON TESTER

Pilot light flashes on  
and off with thermostat

Invaluable for checking temperatures, accurately resetting thermostats. Registers in fabric graduations—Rayon, Silk, Wool, Cotton, Linen. Also in degrees, 200° to 700° F. Has a specially designed precision thermometer, unsurpassed in quality, accuracy and performance. ONLY \$18.50 postpaid. MONEY BACK GUARANTEE. Write for circular.



(Pat. appl. for)

**HANLAN CO.** 1419-C, West Jefferson  
Los Angeles 7, Calif.

## RADIO SERVICEMEN

Increase your profits Now. Make yourself the OUTSTANDING Radio-Technician in your community by using the new original sales helps story form advertising. Easy to read—Catches the eye—Leaves a smile on the reader's face. Sure-fire Results. It is now being used in Hollywood with great success by a choice few. GET Yours Now. All for only \$1.00.

**WHAT YOU GET FOR \$1.00**

- 2 Advertising Story Forms
- 1 Hot tip (Money Maker)
- 1 Page of News Briefs Covering television in Hollywood

**SHAIN'S RADIO SALES HELPS**  
1203 N. WESTERN AVE.  
HOLLYWOOD 27, CALIF.

## Modulation Monitor

(Continued from page 50)

the peaks of modulation clearly.  $R_s$ ,  $C_s$  causes the eye to remain closed long enough to indicate all peaks clearly. The capacity of  $C_s$  can be adjusted, if desired, to provide either slow or fast action of the "Modulation" eye closure during modulation. The larger the value of  $C_s$ , the slower will be the re-opening of the eye tube.

Calibration of the monitor may be accomplished with the aid of an oscilloscope by feeding the transmitter into a dummy antenna and then either whistling a sustaining note or feeding a tone into the transmitter speech input system. Next adjust the speech gain for 100 per-cent modulation as indicated on the oscilloscope.  $R_1$  in the modulation monitor should not be adjusted until the "Modulation" eye is closed. At the same time  $C_2$  should be adjusted for full closure of the "Carrier" eye. The monitor is now calibrated.

Audible monitoring is possible by plugging headphones into jack,  $J_1$ . This disconnects the "Modulation" eye tube grid, since both visual and audible monitoring is not possible at the same time with this instrument. Audible monitoring provides for a "quality" check of the transmitter.

Most hams can construct this instrument from available parts. The one built by the author and shown in the photographs, was constructed in a metal box measuring 10 x 7 x 6 inches. The left eye tube is for "Carrier" while the right eye is for "Modulation" use. The bandswitch is mounted under the left eye tube, while the phone jack is installed under the right eye tube. The center dial is for tuning. Arrangement of parts is not critical but all of the audio wiring should be shielded to prevent r.f. from getting into the audio circuits.

This monitor is a pleasure to use. It is possible to turn up the speech gain and speak into the microphone in a natural, relaxed voice from a distance of a foot. The operator can operate in this manner without fear of overmodulating since he can watch the indicator and speak loudly enough to hit 100 per-cent on peaks.

Using the monitor also reduces the possibility of BCL interference, a point not to be overlooked. It is known that a carrier modulated in excess of 100 per-cent acquires sharp cut-off periods which cause high damping to create a broad signal and can generate spurious frequencies at odd places on the dial. This can bring about shock excitation in nearby receiving antennas and powerlines.

There is no reason why this circuit could not be built right into the transmitter, obtaining its power from the transmitter or speech amplifier filament and plate supplies. The instrument constructed by the author was used for checking police radio stations

**RADIO NEWS**

and thus had to be self-contained.

If the monitor is constructed as part of the transmitter an additional switch could be placed in the control grid circuit of either eye tube and the circuit arranged so as to place the grid of the eye across a resistor in the grid return circuit of each stage in the transmitter. The grid current flowing through the resistor would indicate excitation to that particular stage. Since the eye tube is connected by the switch across the resistor, it could also be used as an indication of the excitation. Thus, the eye could be used to tune up each stage of the transmitter and then switched over to function as a modulation indicator.

This modulation monitor was compared directly with a broadcast station modulation monitor and the indication on this instrument coincided with that of the broadcast monitor.

-30-

### Television Installation

(Continued from page 56)

This condition considerably simplified the procedure of orientation.


Since the sky was overcast during the installation, the technician on the roof first "got his bearings" by use of a small hand compass. From his knowledge of the geographical location of the two transmitting antennas, he was able to estimate the direction or bearing of both distant stations.

Selecting the *Primary Channel*, WABD, for orienting first, the dipole was turned broadside to the estimated direction of the WABD transmitting antenna and the television receiver was switched to the *Primary Channel*.

The technician on the roof next slowly rotated the entire dipole assembly in the mounting bracket (Fig. 6) while the man at the set observed strength and quality of pictures received at various bearings of the antenna.

Best antenna position for receiving

Fig. 7. The dipole is tuned by adjusting space separation between two metal rods, results being observed at TV receiver.

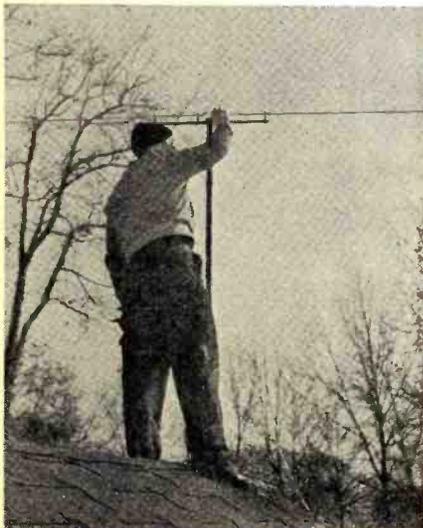

## It's RADIONIC . . . for RELIABILITY Look TWICE at these VALUES

You won't believe 'em the first time

### ALL BRAND NEW

MICA CONDENSERS—500 volt wkg. .00001, .000025, .00005, .0001, .00025, .0005, .001, .002, .005. Any assortment . . . **20 \$** for

CERAMICON CONDENSERS—.000003, .000005, .00001, .000025, .00005, .0001. Any assortment . . . **15 \$** for

CERAMICON TRIMMERS—Variable. 1.5 to 7, 3 to 13, 5 to 20, 4 to 30, 7 to 45 mmf. Any assortment . . . **7 \$** for

POWER RESISTORS—4000 ohm, 12 watt; 300 ohm, 10 watt; 2000 ohm, 20 watt. Any assortment . . . **10 \$** for

SOCKETS—Low loss phenolic octal with retainer ring . . . **15 \$** for

COIL FORMS—Ceramic, grooved 6/8 in. long, 2 in. dia. . . **12 \$** for

CARBON RESISTORS—Available in 1/2 watt and 1 watt except as indicated in footnote below.

6.8\*, 7\*, 8\*, 15\*, 38\*, 100\*, 150\*, 200, 300, 400#, 500, 600#, 700#, 800, 1000#, 1250, 1500#, 2K, 2.5K#, 3K, 3.5K, 4K#, 5K#, 6K, 7K, 7.5K, 8K, 9K, 10K#, 12K, 15K#, 17K, 20K#, 25K#, 30K, 40K, 50K#, 60K, 70K, 75, 100K#, 125K, 150K, 200K, 250K, 300K, 400K, 500K, 750K, 1M, 2M, 3M, 4M, 5M, 6M, 7M, 8M, 9M, 10M.

1/2 watt, any assortment (100 for \$1.75) . . . **50 \$** for

1 watt, any assortment (100 for \$2.25) . . . **40 \$** for

2 watt, any assortment (100 for \$3.75) . . . **25 \$** for

\*1/2 watt only; #also 2 watt; K=1000; M=1 meg.

### ALL GUARANTEED

OSCILLATOR COIL—Meissner, unshielded for 6SA7, 12SA7, etc. 456 kc. . . . . **10 \$** for

R. F. CHOKE—2 millihenry, universal wound . . . . . **12 \$** for

I. F. TRANSFORMERS Input, Output, 456 kc. iron core, litz wound, shielded . . . **2 \$** for

VOLUME CONTROLS 1 meg. 1/2 in. shaft **10 \$** for 1 meg. 1 in. shaft **7 \$** for 1/2 meg. auto type **12 \$** for

RUBBER POWER PLUGS—Heavy duty standard prong . . . **12 \$** for

TUBES IU5, 3 for \$1—12SQ7-GT & 12SA7GT . . . . **2 \$** for

**NATIONAL**  
HRO-7 (complete) . . . \$311.36  
NC-173 (with speaker) . . 189.50  
NC-240-D (with speaker) 241.44  
NC-46 (with speaker) . . 107.40  
110-A (complete) . . . . 67.50

**HALLICRAFTER**  
S-38 (complete) . . . . \$ 47.50  
S-40A (complete) . . . . 89.50  
SX-42 (less speaker) . . . 275.00  
S-47 (less speaker) . . . . 200.00  
SP-99 (panadaptor) . . . . 99.50

HT-9 (100 watt transmitter) . . . . . 350.00  
R-42 (speaker for SX-42 & S-47) . . . . . 29.50  
**HAMMARLUND**  
HQ129X (with speaker) . \$173.25  
SPC-400-X (complete) . . 398.25

**Chancellor TELEVISION SETS • KITS AND COMPONENTS • PARTS • RADIOS • TEST INSTRUMENTS • INTER-COMMUNICATORS • DISC AND WIRE RECORDERS • PUBLIC ADDRESS • TUBES • AMATEUR EQUIPMENT • HARDWARE • RECORD CHANGERS • TECHNICAL BOOKS • ACCESSORIES**

TERMS: Remittance with order plus postage or 25% deposit, balance C.O.D.

**RADIONIC EQUIPMENT COMPANY**  
DEPT. 510 TRIBUNE THEATRE ENTRANCE 170 NASSAU ST., N. Y. 7, N. Y. WOrsh 2-0421  
CABLE "CHANSLOR"

**Have you got our FREE CATALOG?**

**MAIL TODAY**

RADIONIC Equipment Co., Dept. 510  
170 Nassau St., New York 7, N. Y.

Gentlemen:  
Please send your free catalog #47, listing products of leading manufacturers of radio electronic parts and equipment, especially designed for Service Dealers, Amateurs, Industrials, Institutions, Government Agencies; also, all literature as published.

Name .....  
P.O. Box or Street .....  
Town .....  
Zone ..... State .....

### RADIO ENGINEERING!

DEGREE IN 27 MONTHS

COMPLETE Radio Engineering Course. Bachelor of Science Degree. Courses also in Civil, Electrical, Mechanical, Chemical, Aeronautical Engineering, Business Administration, Accounting, Secretarial, Science. Graduates successful. 64th year. Enter Sept., Jan., March, June. Write for catalog.

TRI-STATE COLLEGE 18107 College Ave. ANGOLA, INDIANA

### PEN-OSCIL-LITE

Extremely convenient test oscillator for all radio servicing; alignment • Small as a Pen • Self powered • Range from 700 cycles audio to over 600 megacycles u.h.f. • Output from zero to 125 v. • Low in cost • Used by Signal Corp. • Write for information.

**GENERAL TEST EQUIPMENT**  
38 Argyle Buffalo 9, N. Y.

## VERIFIED SPEAKERS

"They speak for themselves"

**WRIGHT inc.**  
2232 University Avenue St. Paul 4, Minnesota

## WESTERN BUYERS — EASTERN BUYERS

A Large Stock of Scarce Items  
All Items New (N) Unless Indicated (U)  
All Used Items Clean and Tested

SCR284A 3800-5800KC complete set.....	\$ 59.50
BC654A Tran. Rec. tubes, xtal.....	19.95
PE104A 6 volt vibrapak.....	5.95
PE103A 6 or 12 volt dynamotor.....	8.95
CD501A Cable for PE103A.....	1.95
LS-7 Speaker.....	4.50
LS-3 Speaker (U).....	5.95
GN45A Hand Crank Generator, stand.....	4.95
<b>SCR288 Field Set 2300-6500KC</b>	
BC474 with tubes, manual.....	37.50
BC474 with tubes, (U) tested.....	27.50
GN44A hand crank generator, stand.....	4.95
<b>SCR522 for 2 meters, tubes, xtal dynamtr, rem. cont'l plugs (U).....</b>	<b>34.50</b>
<b>SCR522 Rec. Tran. Tubes (U).....</b>	<b>24.50</b>
<b>SCR522 rec'r converted to center panel tuning, band sprd. in CS48 case.....</b>	<b>35.00</b>
<b>W6VSF522 conversion kit, instruct.....</b>	<b>7.00</b>
<b>SCR522 trans. tubes, case (U).....</b>	<b>15.00</b>
<b>BC375E trans. tubes, dynamotor, compl. with 6 tuning units (U).....</b>	<b>22.50</b>
Transmitter with tubes (U).....	11.00
TU tuning units with case.....	3.50
TU tuning units without case.....	2.50
<b>SCR274N Command Sets, (U), clean.....</b>	<b>29.95</b>
BC696A 3-4 MC Trans, tubes (U).....	5.95
BC459A 7-9 MC Trans, tubes.....	6.95
BC457A 4-5 MC Trans, tubes (U).....	4.95
BC458A 5-7 MC Trans, tubes (U).....	4.95
BC453B 190-550 KC Rec. Tubes (U).....	3.95
BC454B 3-6 MC Rec, tubes, (U).....	5.95
BC455B 6-9 MC Rec., tubes, (U).....	5.95
<b>BC312 Rec., 1500-18, 000KC (U) clean.....</b>	<b>44.95</b>
<b>BC344 Rec., 150-1500KC, 115VAC (U).....</b>	<b>44.95</b>
<b>BC348 Rec., 200-500, 1500-18, 000KC (U).....</b>	<b>39.95</b>
<b>BC348 Rec., 200-500, 1500-18, 000KC.....</b>	<b>49.95</b>
(Add \$20.00 to BC348 for 115VAC)	
<b>RBL3 Rec., 15-600KC, 115VAC, tubes.....</b>	<b>44.00</b>
<b>RAK7 Rec., 15-600KC, 115VAC, tubes.....</b>	<b>27.50</b>
<b>BC357J Beacon Rec., 75MC, tubes.....</b>	<b>3.45</b>
<b>R8-ARN8 Beacon Rec., 7 tubes.....</b>	<b>5.95</b>
<b>BC654A Trans. Rec., 470MC, tubes.....</b>	<b>16.45</b>
<b>BC221 Freq. Meters, tubes, xtal.....</b>	<b>57.50</b>
<b>BC221 Freq. Meters, tubes, xtal (U).....</b>	<b>39.00</b>
<b>I222A Sig. Gen., tubes, 8-15, 150-230MC.....</b>	<b>49.00</b>
<b>BC1267A Trans. Rec., 150-230MC, tubes.....</b>	<b>49.00</b>
<b>TCS9 1500-12,000KC trans. rec, tubes, 115VAC power supply, ant. (U).....</b>	<b>109.00</b>
<b>RG8U Coax cable 50 Ft. Min. (52-ohm)/ft.....</b>	<b>.06</b>
<b>RG8U Coax cable 51 Ft. with conn.....</b>	<b>2.95</b>
<b>RG8U Coax cable 26 Ft. with conn.....</b>	<b>1.65</b>
Low loss chassis conn.....	.50
<b>HS-33 8000 ohm headset.....</b>	<b>1.29</b>
<b>HS-23 600 ohm headset.....</b>	<b>1.29</b>
Extension cords, PL55 plug.....	.40
<b>HS-30 Ear plug headset.....</b>	<b>.95</b>
<b>HS-30 Ear plug Headset (U).....</b>	<b>.50</b>
Matching transformer, H830.....	.50
<b>H23U Handaets.....</b>	<b>3.45</b>
<b>TS13 Handaets.....</b>	<b>3.45</b>
Trim Commercial 17000 ohm headset.....	4.25
Sound Powered chest set \$3.95 each.....	pr. 7.50
Sound Powered headset \$16.00 each.....	pr. 30.00
<b>115 VAC 1/4 hp. motor with 250V 600 MA amp-dyne generator.....</b>	<b>18.75</b>
<b>200FD20 Johnson var. dual cond.....</b>	<b>1.19</b>
<b>MC1855 Bud 100MMD midget var.....</b>	<b>.69</b>
<b>Power transformer: 2500-0-2500 300 ma or 2000-0-2000 500 ma, 115VAC, oil cooled, filled, from BC-610.....</b>	<b>32.95</b>

### Oil Filters

3 mf. 4000V.....	6.75	1 mf. 7000 V.....	3.95
8 mf. 2000V.....	5.25	8 mf. 1500 V.....	4.50
6 mf. 1500 V.....	2.95	12 mf. 2500V.....	9.75
4 mf. 600V.....	.95	10 mf. 1000V.....	2.50
23 mf. 2000V photoflash capacitor.....			10.00
1 amp. Varise (U) (Clean).....			7.95
80 V. A. Sola constant volt xtmr., 115VAC 60 cycle (U).....			13.50

Mark II, Trans., Rec., with all spares..... 39.00  
A large stock of tubes, wire, cables, meters, blank chassis and other surplus gear at prices in line with tested quality. Write us your needs. Minimum orders \$2.00. Prices FOB Pasadena. 25% deposit on all orders.

## PHOTOCON SALES

1060 N. Allen Pasadena 7, Calif.

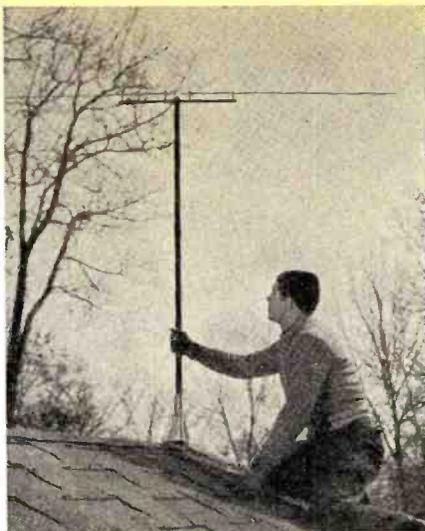


Fig. 8. Dipole assembly mounted permanently and roof installation completed. Fastening lead-in in place is next step.

the *Primary Channel* was found easily, and indicated by a pronounced, brilliant glow of intensity when the dipole was turned broadside to the transmitting station on the *Primary Channel*. This position checked closely with the *estimated* position and direction. The receiver was then switched to the *Secondary Channel*, the dipole was aimed in the *estimated* direction, and the entire orienting procedure was repeated (Fig. 6).

Only a very slight movement of the dipole was necessary, however, to determine the best antenna position for reception of the *Secondary Channel*. Even though the signals *seemed* to be coming from the same direction, there was a difference in bearings for the two television stations. There was also a difference in signal strength, by comparison of the reception of the *Primary* and *Secondary Channels*. Station WABD was considerably stronger than the *Secondary Channel*.

For this reason, the dipole was permanently oriented in the direction of the weaker station on the *Secondary Channel*. Some slight loss could be tolerated in reception of the (stronger) *Primary Channel* in an effort to obtain a better signal from the station on the *Secondary Channel*. This position, for receiving *both* stations, was double-checked several times, by switching back and forth between the two stations while observing and comparing the intensity and quality of the two received signals.

No unusual picture effects or distortion were observed during orientation of the single dipole.

### Tuning the Antenna

After orientation, the dipole was tuned by adjusting the amount of space separation between the two metal rods of the dipole assembly.

When the antenna was first assembled, this distance was not particularly critical. A distance of about 2 inches was adequate, but for precise tuning of the dipole for the individual

## BONAFIDE VALUES



**SHURE  
T1TB  
Push Button  
Carbon Mike**

**\$198**

With Cord  
and Plug  
Value \$12.00

**SHURE  
CRYSTAL  
MIKE**

**\$695**

With Stand,  
Base, and  
7 Ft.  
Cable  
Value  
\$18.50



Detroita Record Changer.....	\$14.69
Webster 56 Automatic Stop.....	25.95
Seeburg 2 Post Changer.....	21.97
McGuire 2 Pos. Changer, Automatic Stop.....	11.95
G1 or Alliance AC Motor.....	2.95
Astatic L-70 Crystal Pickup.....	1.95
5" PM Speaker (Alnico).....	1.39
#3 Heavy Slug Speaker—Nylon Cone.....	1.98
#2 Heavy Slug Speaker or Mike Comb.....	1.39
1/2 Meg. Vol. Cont. & Sw.—Lots of 6.....	.49
Federal Selenium Rect.—100 Mill—Lots of 6.....	.69
100 IRC Resistors Assorted Sizes & Watts.....	1.79

25% DEPOSIT, BAL. C.O.D. PLUS CHARGES  
WRITE FOR LATEST CATALOG

## BONAFIDE RADIO CO.

89 1/2 Cortlandt St., Dept. A, N. Y. 7, N. Y.

# S.S.S.

"Servicing by Signal Substitution"

Learn about this modern dynamic approach to radio servicing with ONLY BASIC TEST EQUIPMENT.

... Fully described in a 120 page book available from your Precision Distributor or factory at 35¢.

... Schools are invited to inquire regarding quantity orders from our Educational Division.

## PRECISION

APPARATUS COMPANY INC.  
ELMHURST 9, N. Y.

Manufacturers of Fine Test Equipment  
RADIO • TELEVISION • ELECTRICAL • LABORATORY

## FMT ★ FM Tuner Permeability Type

A complete fully assembled, tested oscillator-mixer that tunes in the 88 to 108 MC FM broadcasts. Enjoy noise free high fidelity radio reception. FMT output feeds into usual FM I.F. amplifier which you can easily build, or into the older FM-45 receivers (I.F.) to change them to the new FM band. All parts, including tube, are combined into a single compact unit measuring only 2 3/4" x 1 1/2" on chassis, to which you connect aerial wire and three voltage wires. It works right every time. It is very sensitive to weak signals, and under favorable weather conditions has tuned in low power FM stations clearly 200 miles away. The FMT is calibrated to feed into 10.7 MC and other I.F. Introductory Price \$6.50 (less tube) postpaid. State I.F. used. Complete directions and drawing with each unit.

Est. 1922 J-M-P Mfg. Co. STATION "K"  
Order Today MILWAUKEE, WIS.

## Radio Technician and Announcers

A practical 15-month course in First Class Radiotelephone Operation and Announcing is offered by Don Martin School of Radio Arts. Most stations these days require combination men. We specialize in this type of training and maintain a placement bureau for our graduates. Serving the industry for 10 years, the School of Radio Arts can train you. Write for our catalogue outlining the courses offered. Classes can be arranged so you can do part time work on the side.

APPROVED FOR VETERANS

DON MARTIN SCHOOL OF RADIO ARTS  
1655 North Cherokee St. Hollywood 28, Calif.



**NOW Sound**  
FOR YOUR SILENT PROJECTOR  
Economically

**\$5995**

Convert your 16mm silent projector to sound (regardless of make) with Apex sound head & radiofilm adapter. Guaranteed excellent performance. Write today for free information.

APEX VIDEO • 12209 J Branford St. • Roscoe, Calif.

RADIO NEWS

installation, this distance between the two metal rods required more critical adjustment.

With the receiver switched to the *Primary Channel*, the space separating the two metal rods was adjusted so that the strongest picture signal was received. The receiver was then switched to the *Secondary Channel*, and readjustment of the spacing was attempted (Fig. 7) in an effort to obtain a brighter picture on the *Secondary Channel*. Readjustment was small, but it resulted in an improved signal.

An *average* value of space separation for good reception of *both* channels was then estimated by the roof technician, and the spacing readjusted accordingly. Using this amount of separation, the receiver was switched back and forth between the *Primary* and *Secondary Channels* to make certain both signals were of about the same intensity and good quality.

#### Final Work

With all antenna adjustments completed, the position of the complete antenna assembly was permanently secured in the metal mounting bracket (Fig. 8). One bolt, through the bracket and mounting pole, held the dipole antenna assembly in a fixed position. Being sufficiently rigid, no guy wires or other antenna supports were considered necessary.

Next, the lead-in "ribbon" was permanently installed. Using poly-



Fig. 9. Typical test pattern as received on primary channel of this installation.

styrene stand-off insulators, when available, the "twin-lead ribbon" lead-in was installed by the roof technician, following a downward route, and avoiding pipes and large metal objects wherever possible.

During installation of the lead-in, the man at the receiver observed picture images on the *Secondary Channel*—the weakest station, in terms of signal strength—to detect any aberrations or distortion effects which might have been introduced by an unsatisfactory lead-in route. Since no distortion, reflection, or other interference was encountered, the entire lead-in was secured in place. Considerable slack in the lead-in was removed at the receiver, and the "twin-lead ribbon" was then recon-

needed to the 300-ohm input terminals of the receiver.

After attachment of necessary lightning arrestors and completion of minor construction work, the operation of the television set was given a final test for "best reception." The observed reception of a test pattern on the *Primary Channel*—WABD—was bright, clear, and distinct. (Fig. 9.)

The owner was furnished with operating instructions, and one of the technicians aided him in the actual operation of the receiver. Then—and *only* then—was the installation pronounced complete!

The procedure used is basic, and important! It is the exact procedure used for all suburban dwellings, houses, and similar locations. In addition, it forms the first part of much more highly complicated installations, which are *not* simple and certainly *not* trouble-free.

Received pictures are not always ideal (Fig. 9) using a single dipole antenna. All too often the pictures are badly distorted by noise interference and by reflected signals of the originally transmitted signals. These produce multiple images, or "ghosts," of the same station, at the same time, on the screen of the television set. However, these typical "troubles" are minimized or entirely eliminated by using a *directional antenna*.

(To be continued)

#### MODEL 205



Engineered by specialists in the development of broadcast receivers, built in our own modern laboratory. Four times the power of pre-war radio sets. Handsomer in appearance and more efficient in operation. Visual slide rule tuning dial with built-in Regalooop, and super Alnico No. 5 permanent magnetic speaker, with automatic volume control.

#### FEATURES

- Five Tubes—including Rectifier
- Single Band Super-Heterodyne
- Broadcast Band 540 to 1650 K.C.
- Automatic Volume Control
- Super Sensitive Iron Core Transformers
- 5" Alnico Wonder Speaker
- Illuminated Slide Rule Dial
- Built in Regalooop

**\$19.95** LIST PRICE

● ALSO AVAILABLE IN IVORY



Size:  
4" wide  
5" high  
8" long

#### MODEL 747

The REGAL Super-Mite! AC, DC or BATTERY. Small enough to be packed in a suitcase, yet uses standard full size components! Parts interchangeable anywhere! The only set of its size with 5 "A" batteries and 1 "B" battery. Average life—100 hours!

#### FEATURES

- 4 1/2" Alnico No. 5 speaker with a heavy duty slug weighing 1.47 oz.
- Selenium rectifier (no rectifier tube necessary)
- Super-Heterodyne
- Available in six different colors
- Full size 2-gang variable condenser

**\$29.50** LESS BATTERIES

#### CLOSEOUT SPECIAL

WARREN 5 TUBE AC-DC SUPERHETS  
COMPLETE WITH TUBES

**\$12.95**

BRAND NEW

#### CLOSEOUT SPECIAL

FAMOUS MAKE PORTABLE PHONES  
3 TUBE AMPLIFIER  
MODEL MPA3

**\$15.95**

BRAND NEW

#### CLOSEOUT SPECIAL

WARREN 7 TUBE AC-DC PORTABLES WITH SHORT WAVE BAND LIST, \$69.50

**\$28.95**

NET, LESS BATTERIES

#### CLOSEOUT SPECIAL

WARREN AC-DC 6 TUBE RADIOS WALNUT CABINET BROADCAST—S.W. BANDS—MINIATURE TUBES

**\$20.95**

## WARREN DISTRIBUTORS

3145 Washington St., Jamaica Plain 30, Mass.

WRITE FOR DEALER DISCOUNT SCHEDULE

# "TIK" for KITS

**Servicemen Amateurs Jobbers**  
**Look at these values**

Mica Condensers Assorted. 100 for .....	\$3.49
Allen Bradley, etc., Volume Controls. 50 ohm to 1 meg 12 for .....	\$2.59
Carbon Resistors, Color Coded, ½, 1 & 2 watt. 100 for .....	\$2.50
Wire Wound Resistors, Ward Leonard, etc. 5 to 75 Watt. 20 for .....	\$2.98
Fuses, Buss & Littlefuse. 100 for .....	\$1.89
Assorted oil filled condensers, tubular and bathtub type, 400 V, 600 V, 1000 Volts. 12 for .....	\$2.49
Octal and 4 prong Ceramic Sockets (without rings). 100 for .....	\$3.98
Condensers, .05 mfd, 2000 volt to .25 mfd 3,000 WVDC. 6 for .....	\$3.59
Precision Wire Wound Resistors, Shallcross, Mepco, etc., ¼, ½ and 1 Watt, 15 for .....	\$2.98

**SPECIAL COMBO KIT**  
**OUR INTRODUCTORY OFFER**

Excellent Assortment—Big Value—  
Tremendous Savings

This kit includes a quantity of items  
listed in the above kits, PLUS many  
others. It's our New Customer Special. **\$10.98**

Minimum Order \$2.00  
25% deposit required on all C.O.D. orders  
Add postage Write Dept. RNO

**"TIK"** 55 WALKER ST.,  
NEW YORK 13, N. Y.  
phone CAnal 6-7485

## SPECIALS for OCTOBER

### AERIAL WIRE

100 ft. coil, 7/23, tinned aerial wire 69c each  
50 ft. coil (same as above)..... 36c each

### PUSH-BACK WIRE

Solid or stranded, tinned copper conductors  
with cotton serve and waxed cotton outer braid  
for easy push-back; available in all standard  
colors.

Per 100 ft. coil—	22 Ga. Solid .....	61c
	22 Ga. Stranded .....	68c
	20 Ga. Solid .....	71c
	20 Ga. Stranded .....	82c
Per 1000 ft. spool—	22 Ga. Solid .....	\$5.72
	22 Ga. Stranded .....	6.45
	20 Ga. Solid .....	6.51
	20 Ga. Stranded .....	7.38

### 18 GAUGE SOLID FIXTURE WIRE

Solid, tinned copper conductor with weather-  
proof compound under lacquered braid; Type  
R.F. Underwriters Approved; a real buy at  
this low price:

**\$6.50 per 1000 ft.**

We carry in stock for immediate delivery many  
types of wire and cable in gauges of from 23  
to 2, in addition to various types of multi  
conductor cable for many uses. We also man-  
ufacture cord sets and cables to specifications.  
Send us your inquiries for prompt attention.


**OUR NEW CATALOG IS NOW**  
**AVAILABLE FOR DISTRIBUTION**  
Write for your copy today.

**COLUMBIA WIRE & SUPPLY CO.**  
5740 NO. ELSTON AVE.  
CHICAGO 30, ILLINOIS

# NEW RECEIVERS for Fall Market
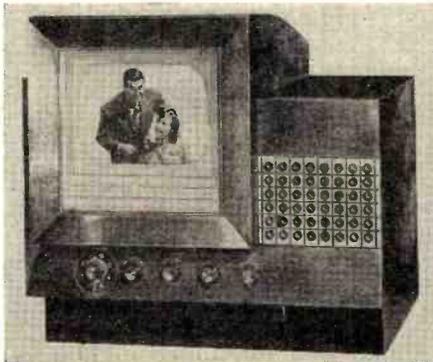
## PHILCO TV RECEIVER

Philco Corporation is now present-  
ing several new television receivers to  
the trade, one of which, the Model  
1000, features a 10 inch picture tube  
of sufficient brilliance to permit pro-



grams to be viewed in normal light  
without darkening the room.

Another feature of this direct-view  
table model receiver is the Philco  
Electronic Control, a new develop-  
ment that automatically brings in sta-  
tions perfectly tuned, sharply focused,  
and firmly synchronized without need  
of adjustments by the viewer. The  
company's new Automatic Level Con-  
trol which is also incorporated in this  
receiver compensates for signal varia-  
tions and avoids fading and fluctua-  
tions in sound and picture.

The Model 1000 is in the moderate  
price class and further details on this  
receiver and other units in the com-  
pany's line will be supplied upon re-  
quest to Philco Corporation, Philadel-  
phia, Pa.

## FM TUNER

Pilot Radio Corporation has re-  
cently introduced their new Pilo-



tuner," Model T-601 for tuning the 88-  
108 mc. FM band.

The unit includes an r.f. stage, a  
mixer, an i.f. stage, a driver and a  
ratio detector. Power is supplied by

a selenium rectifier and the set is de-  
signed to operate on a.c. only. The  
set has a built-in antenna with ex-  
ternal connection for a dipole unit.  
Temperature compensated ceramic  
tuning assemblies with copper con-  
denser plates and machine stamped  
r.f. coils provide good stability.


The "Pilotuner" may be connected  
directly to any audio amplifier, record  
player, or into the phono input of an  
AM receiver. It is housed in a wooden  
cabinet 8¼" x 6¼" x 5½".

Further information on the Model  
T-601 will be supplied by Pilot Radio  
Corporation, 37-06 36th Street, Long  
Island City 1, New York.
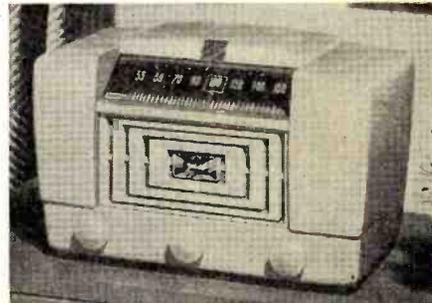
## LOW PRICED TABLE RADIOS

Two new table model radios which  
feature advanced styling at low prices  
have been announced by Radio Corpo-  
ration of America.

Known as the Models 66X11 and  
66X12, these units feature easy-to-read  
straight line tuning dials with a



pointer that frames the calibration  
numbers. In addition, these receivers  
have two-point tone control, extra  
large built-in magic loop antenna,  
built-in ground, a.v.c., a.c.-d.c. opera-  
tion, selective superheterodyne circuit,  
and the RCA "Golden Throat" tone  
system. The receivers have five tubes  
plus a rectifier.

The Model 66X11 is furnished in  
walnut finished plastic while the  
Model 66X12 comes in an antique ivory  
finish.

Details on either, or both, of these  
receivers will be furnished by the RCA  
Victor Home Instrument Department,  
Radio Corporation of America, Cam-  
den, New Jersey.

## CHAIRSIDE RECORDER

Audar Inc. is currently offering a  
combination disc recorder with built-  
in radio and automatic record changer  
for use in the home.

Designated the Model RER-9, this  
new unit features one 4-position switch  
for radio, recording radio, record play-  
ing, and microphone recording. The

switch automatically switches all tone compensation circuits to provide maximum bass and treble adjustment for each operating condition. The speaker baffle design provides for cone back pressure relief through the front grille for high fidelity bass reproduction.

The recorder-changer mechanism will record up to 10 inch discs and



will play ten 12" records or twelve 10" records. A magic eye tube is used as a tuning indicator for the radio position and as a volume level indicator in the radio and microphone recording positions.


This model is housed in a modernistic cabinet finished in fine-grained plastic coated fabric with hand rubbed mahogany panels and trim. The unit measures 31" x 20" x 17".

Additional information on the Model RER-9 will be supplied upon request to *Audar, Inc.*, Argos, Indiana.
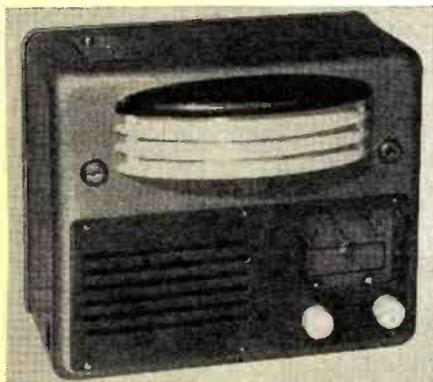
#### COIN RADIO

Designed primarily for restaurants, cafes, snack-bars, and drug stores, *Music Menu Inc.* of Los Angeles has recently introduced a new coin operated radio receiver which provides several new features.

The die-formed aluminum cabinet, trimmed with chrome steel and red



plastic, has a smoked pearl Hammer-tone baked enamel finish which houses a six tube *RCA* licensed chassis, 12½" x 10½" x 6".

The radio is equipped with two cylinder type locks and a *National* slug rejector. An electric credit unit makes it possible to accept up to 24 coins at one time and an electric coin counter maintains an actual coin record. A *Haydon* synchronous timing motor controls the playing time from one

# THE MEISSNER RADIO - PHONO - RECORDER

*A Four-Way Performer*



- A VERSATILE RECORDER
- A HIGH-FIDELITY RECORD PLAYER
- A SENSITIVE, SELECTIVE RADIO RECEIVER
- AN AUXILIARY P.A. AMPLIFIER

Here is the combination you have been waiting for and the outstanding entertainment value of the year. A four-way performer, the new Meissner Radio-Recorder combines the functions of a versatile home recorder; a high quality, high fidelity record player; a sensitive superheterodyne radio receiver and a low power public address system . . . all in one compact unit that easily surpasses anything now being offered. Compact in design, precision-built and easy to operate, this unit is at your jobber's now. See it today or write for full information to the address below:

*Meissner*

**ELECTRONIC DISTRIBUTOR AND  
INDUSTRIAL SALES DEPARTMENT**

**MAGUIRE INDUSTRIES, INCORPORATED,  
936 N. MICHIGAN AVENUE, CHICAGO 11, ILL.**

EXPORT SCHEEL INTERNATIONAL,  
4237 N. LINCOLN AVENUE, CHICAGO  
CABLE HARSHEEL

## HERE IS A TREAT FOR EVERY APPLIANCE REPAIRMAN AND MANUFACTURER



**DHD**  
AUTOMATIC IRON TESTER

An AUTOMATIC IRON TESTER with proper temperature settings, calibrated from 0° to 800° F. The meter reads directly for silk, rayon, cotton, wool, or linen,—there is nothing confusing about this tester, it does the work for you. It's not new, for thousands of service shops and manufacturers have taken the guess work out of appliances with our iron tester. We guarantee satisfaction on all our products, or your money is refunded.

Complete, ready to use..... **\$2750**

**DHD ELECTRONICS AND APPLIANCE CO.**

3150 Menlo Dr., Glendale 8, Calif.

Distributor inquiries invited

# SELENIUM RECTIFIERS

## FOR ALL APPLICATIONS

### HALF WAVE TYPES

Input	Output	Current	Price
From 0-18 V.A.C.	From 0-14 V.D.C.	3 AMP.	\$2.25
0-18 V.A.C.	0-14 V.D.C.	5 AMP.	2.95
0-18 V.A.C.	0-14 V.D.C.	10 AMP.	4.95
0-18 V.A.C.	0-14 V.D.C.	15 AMP.	6.95
0-18 V.A.C.	0-14 V.D.C.	20 AMP.	8.95
0-18 V.A.C.	0-14 V.D.C.	25 AMP.	10.95

Input	Output	Current	Price
From 0-36 V.A.C.	From 0-28 V.D.C.	3 AMP.	\$2.95
0-36 V.A.C.	0-28 V.D.C.	5 AMP.	4.95
0-36 V.A.C.	0-28 V.D.C.	10 AMP.	7.95
0-36 V.A.C.	0-28 V.D.C.	15 AMP.	10.95
0-36 V.A.C.	0-28 V.D.C.	20 AMP.	13.95
0-36 V.A.C.	0-28 V.D.C.	25 AMP.	16.95

### FULL WAVE BRIDGE TYPES

Input	Output	Current	Price
From 0-18 V.A.C.	From 0-14 V.D.C.	5 AMP.	\$4.95
0-18 V.A.C.	0-14 V.D.C.	10 AMP.	7.95
0-18 V.A.C.	0-14 V.D.C.	15 AMP.	10.95
0-18 V.A.C.	0-14 V.D.C.	20 AMP.	13.95
0-18 V.A.C.	0-14 V.D.C.	25 AMP.	16.95
0-18 V.A.C.	0-14 V.D.C.	30 AMP.	19.95


Input	Output	Current	Price
From 0-36 V.A.C.	From 0-28 V.D.C.	5 AMP.	\$7.95
0-36 V.A.C.	0-28 V.D.C.	10 AMP.	13.95
0-36 V.A.C.	0-28 V.D.C.	15 AMP.	19.95
0-36 V.A.C.	0-28 V.D.C.	20 AMP.	25.95

It would be impossible to give a complete listing of all our rectifier types. Our engineering staff is at your service to help you work out the application of selenium rectifiers to your specific problems. Write us for quotations or further information.

Send check or money order  
25% Deposit required on all C.O.D.s.

**OPAD GREEN COMPANY**  
191 GREENWICH STREET  
NEW YORK 7, N.Y.

## New G.E. "CIRCLINE" Fluorescent

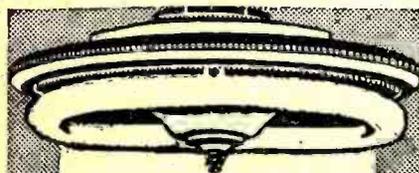

### OVERHEAD FIXTURE

ALL WHITE BAKED ENAMEL

The newest, fastest selling Overhead Fixture in America today.

The new G.E. 32 watt "CIRCLINE" lamp gives the SAME AMOUNT of light as the ordinary 100-watt incandescent bulb.

For Kitchens, Basements, Halls, Workshops, etc. Comes with 4" cup or for Flush Mounting.

With Bulb List \$18

**\$10 YOUR COST**

Remit in Full and we pay postage. West of Mississippi 50c extra for postage.

**RISCO ELECTRONICS**

22 Warren Street BE 3-8554 New York 7, N. Y.

"Look for our other advertisement"

minute to two hours depending on whether the unit is set to receive 1, 5, 10 or 25 cent pieces.

Standard radio tubes, Hi-Q coils, built-in master volume control, and standard external volume control are added features of the unit. Operation is on 110 volt, 60-cycle a.c., with units for 50-cycle operation also available.

Music Menu Inc., 207 West Pico Blvd., Los Angeles 15, California, is the manufacturer and will supply added details on request.

### HOME TV RECEIVER

Remington Radio Corporation is now in production on a new television receiver designed for the home, the "Rembrandt" Model No. 80.

The unit houses a 12" cathode-ray




tube which provides an image size of approximately 8" x 10". The DuMont Inputuner incorporated in this receiver provides continuous tuning from 44 to 216 mc. and FM coverage. All thirteen television channels may be received on this set without adjustments being made.

The cabinet is 39" x 24" x 18" and is made of 3/4" mahogany veneer.

Remington Radio Corporation, 80 Main Street, White Plains, New York, will supply prices and shipping dates on this unit upon request.
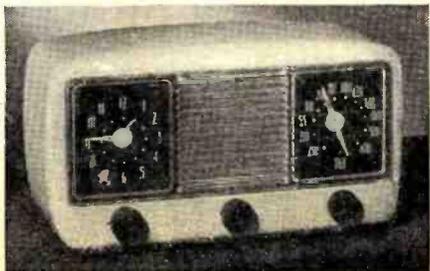
### THE "RADALARM"

A new table model receiver which combines a plastic-housed radio with an electric alarm clock has been in-



troduced by Garod Radio Corporation as one unit in the new fall line.

The "Radalarm" is housed in a plastic case with a contrasting clear plastic clock and dial face. The specially designed electric clock which incorporates the Telechron movement is smooth and quiet in operation.

## RADIO AND ELECTRONIC BARGAINS

250 ass'd coded RESISTORS; 1/2, 1, 2 W; pop sizes #Mx11.....\$4.95  
50 ass'd MICAS pop sizes mxd or coded #Mx12..... 1.95  
21 TRANSMITTING MICAS .00003 to .02, 600 and 1200 WVDC, Solar XCB and Ilicamold (3 ea. size) #Mx13..... 2.25  
MILLIAMMETER, Weston 2 1/2", 0-100 ma #M11..... 3.15  
TRANSFORMER, Hi voltage, 1200v 12 ma, 110v 50-60 c in #T31..... 2.25  
CHOKE, Plate; 600 hy, 6000 ohms, 1 to 3 ma Raytheon, #T32..... .57  
30 hy CHOKE; Amertran Linear std. 110 ma, 600 ohms, hvy shld #T33... 2.25  
CHOKE, ftr; 15 hy 500 ohms, 10 ma, UTC 73073 shld #T34..... .39  
CHOKE, ftr; 4 hy 300 ohms 90 ma, Westinghouse shld #T35..... .39

Hundreds of other Bargains. Also Test Equipment Kits Designed and Developed by ROBERT G. HERZOG—Write for free data, circuits and lists.

UNIVERSAL GENERAL CORP.  
365 Canal St., New York 13 Walker 5-9642

## HERE IT IS!

### 45 Proven Circuits

For the Technician, Serviceman and Experimenter

Home Recorders, Phono, Oscillators, Intercom. Systems, Amplifiers, etc.

Price \$2.00

Check or P. O. Order

At Your Dealer or Mail to

OS-TRONIC PUBLICATIONS

196 W. 37th Place  
LOS ANGELES 7, CALIF.

## PRACTICAL TECHNICAL TRAINING FOR YOU

Specialize in Electronics, Radio, Electricity, Refrigeration, Heating and Air Conditioning, or Welding. Prepare in one year for position as Technician, or in two additional years secure your E.S. Degree in Electrical Engineering with major in Machinery or Electronics.

Write for booklet "Career Building"

**MILWAUKEE SCHOOL OF ENGINEERING**  
"A Technical Institute"

RN-1047, N. Broadway and E. State, Milwaukee, Wis.

Transvision—Television Kits, Complete..... \$159.50  
Telekits, 7" Less tubes..... 77.50  
Superior Volt-Ohmmeter, Model 570..... 28.40  
X-tal Pick-up Arm with Astatic L72 crystal..... 1.59  
Headphones with Rubber Cushions & Leather Headbands HS23-5000 ohms..... .98  
Radio City Products Signal Generator, Mod. 710..... 17.95  
Hand Mike, T-17 B (used)..... .79  
Willard 2-volt Storage Battery, exact replacement..... 2.49

RADIO PARTS SALES CO.  
5220-5222 South Vermont Avenue  
Los Angeles 37, Calif. TW. 9178

### RADIO SERVICE MEN!

• RCA RADIOTRON • SYLVANIA  
• TUNGSO • TUBES, PARTS AND EQUIPMENT  
Serving Eastern New York State  
Distributors of RADIO EQUIPMENT

**CHIEF ELECTRONICS**

104 MAIN STREET, POUGHKEEPSIE, N. Y.  
The Square Deal Supply House

### MILES "TELEMIKE"

A midget unit (1 1/4"x1 1/4"x1 1/4") requiring no physical contact to telephone. PICKS UP BOTH SIDES OF TELEPHONE CONVERSATIONS for group loud speaker listening or for recording when used with standard amplifier or recorder. PRICE \$25.00 postpaid. Write for details on our complete line of FILMGRAPH TELEPHONE—CONFERENCE—DICTATION—"TALKIE" RECORDERS & REPRODUCERS.

**MILES REPRODUCER CO., Inc.**  
Dept. RN-10, 812 Broadway, New York 3, New York.

A built-in loop antenna in the radio unit provides pickup over the entire broadcast band. The controls include volume and station selector knobs as well as a radio-alarm switch and time-setting knob. This radio is in the moderately-priced field.

Garod Radio Corporation, 70 Washington Street, Brooklyn 1, New York, will supply additional details on this new line.

#### TV CONSOLE

The Model T-502 television receiver, which was especially designed to meet the requirements of the home owner,



has been announced by *United States Television Mfg. Corp.* of New York.


One-third more compact than earlier television consoles, this new receiver features automatic frequency control as well as automatic picture lock-in. Besides providing a 54 square inch television picture, this receiver also incorporates FM, AM, and short-wave reception and a choice of *Seeburg*, *Webster*, or *Garrard* phonograph units which will handle ten 12" records or twelve 10" records.

The cabinet can be supplied in either Georgian design in dark mahogany with matched crocheted veneers, or in modern bleached mahogany. The unit measures 36" x 40" x 22".

*United States Television Mfg. Corp.*, 3 West 61 Street, New York 23, New York will supply full details on request.
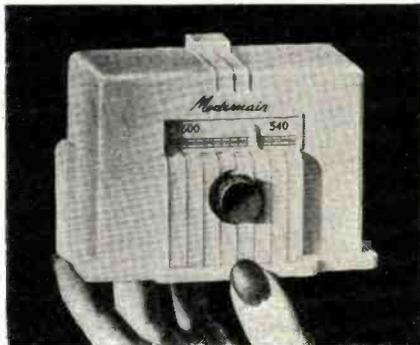
#### MIDGET BATTERY RADIO

The new *Modernair* 500 radio which measures only 4 3/8" x 3" x 3" and op-



erates from standard midget type batteries has been announced by *Modernair Corporation* of Los Angeles.

This plastic miniature unit uses a specially designed condenser to give full broadcast reception despite its

October, 1947

**BUILD BIGGER PROFITS**

with  
**ESPEY**  
CUSTOM BUILT CHASSIS

YES! These ESPEY custom-built radio receiver chassis are really designed to make bigger profits for YOU—the Serviceman and Serviceman-Dealer! They are ruggedly constructed of only the finest materials, and are electronically designed to give your customers maximum reception-pleasure over the years ahead, thereby assuring your reputation as "knowing your stuff!"


Engineered to meet all requirements for an excellent receiver chassis to be installed in your customer's cabinets, these ESPEY models are priced far within the competitive range. With three models to select from, your replacement worries are over. May we suggest that you contact your regular jobber, and examine these sets at your leisure? We feel certain that you will be just as enthusiastic about them as we are!

In the event that your jobber does not have these chassis as yet, write us for full details!


"Radios for Everyone . . . Everywhere"

**ESPEY MFG. CO., INC.**


528 EAST 72ND ST., N.Y. 21, N.Y.

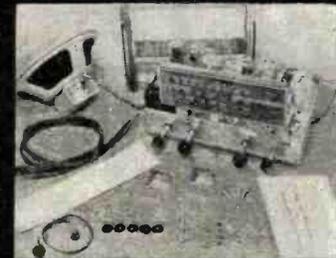

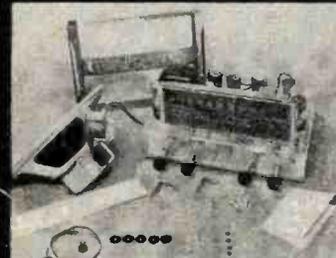**MODEL 7-B:** 11 tube Superhet AM-FM. For 105/125V AC. Automatic and full range volume controls. 10" Alnico V speaker, wired for phono, AM-FM antennas supplied. RMA listed. Supplied complete, ready to install and operate.



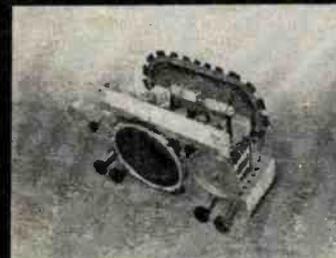**MODEL RR-14:** 8 tube Superhet. For 105/125V AC. Automatic and full range volume controls. 10" speaker. Covers Broadcast and 2 short wave bands. Wired for phono. Built-in loop. All climates.




**MODEL 97A:** 6 tube Superhet. 105/125V AC/DC. 6" speaker. Automatic and full range volume controls. Broadcast and shortwave. Wired for phono. Built-in loop. Tone control. RMA listed. Complete and ready to install.

**RADIO OPPORTUNITIES**  
WRCI Specialized Training prepares you for a successful technical career in Commercial Radio Operating (FCC exams.) and in Radio-Television Servicing. WRCI graduates earning above average salaries. Investigate these opportunities. Morning or afternoon classes. Register now. Approved for veterans.  
**WESTERN RADIO COMMUNICATIONS INSTITUTE**  
631 W. 9th St., Los Angeles 15, Calif.

**LCETI**  
"SEE PAGE 10"

**NOW IN STOCK!**  
**The Famous NEW SIMPSON model 260 VOLT-OHM-MILLIAMMETER . . . for Radio and Television Servicing**  
(20,000 ohms per volt D.C.)  
AC-DC Volts: 0-5000  
DC Milliamperes: 10, 100, 500  
DC Microamperes: 100  
Decibels: -10 to +52 db.  
Ohms: 0-20 megohms  
Complete with test leads.  
NET PRICE—\$38.95  
Model 260 RT—Same, but with Roll Top Case . . . \$43.75  
SEND FOR FREE CATALOG!  
Please Send 25% Deposit with C.O.D. Mail Orders.  
**SCENIC RADIO** 53 Park Pl. Dept. O, New York 7, N.Y.
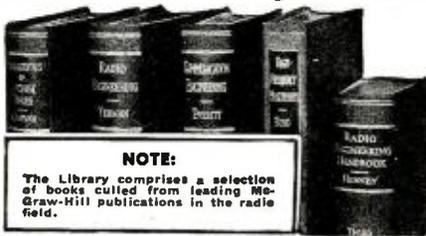
# NOW—A REALLY HIGH-POWERED— Radio Engineering Library



**NOTE:**

The library comprises a selection of books culled from leading McGraw-Hill publications in the radio field.

- especially selected by radio specialists of McGraw-Hill publications.
- to give most complete, dependable coverage of facts needed by all whose fields are grounded on radio fundamentals.
- available at a special price and on easy terms.

THESE books cover circuit phenomena, tube theory, networks, measurements, and other subjects—give specialized treatments of all fields of practical design and application. They are books of recognized position in the literature—books you will refer to and be referred to often. If you are a practical designer, researcher or engineer in any field based on radio, you want these books for the help they give on hundreds of problems throughout the whole field of radio engineering.

**5 VOLUMES, 3559 PAGES, 2558 ILLUSTRATIONS**

1. Eastman's FUNDAMENTALS OF VACUUM TUBES
2. Terman's RADIO ENGINEERING
3. Everitt's COMMUNICATION ENGINEERING
4. Hund's HIGH FREQUENCY MEASUREMENTS
5. Henney's RADIO ENGINEERING HANDBOOK

10 days' examination. Easy terms. Special price under this offer less than books bought separately. Add these standard works to your library now; pay small monthly installments, while you use the books.

**10 DAYS' FREE EXAMINATION—SEND COUPON**

**McGraw-Hill Book Co.**  
330 W. 42nd Street, New York 18, N. Y.

Send me Radio Engineering Library, 5 vols., for 10 days' examination on approval. In 10 days I will send \$2.50 plus few cents postage, and \$4.00 monthly till \$26.50 is paid or return books postpaid. (We pay postage on orders accompanied by remittance of first installment.)

Name .....

Address .....

City and State .....

Company .....

Position .....

small size. Battery cost is said to average less than one cent an hour. The new Hi-Mu 1L4 pentode which is used in this set provides low current drain with resultant long battery life.

This Model 500, which comes in red, white, or blue Tenite plastic, is equipped with an antenna connection wire and a small spring clip. A ground connection on the back panel of the unit is provided for use with an outside antenna.

Modernair Corporation, 925 S. Grand Avenue, Los Angeles 15, California, will furnish additional details on this unit to those making their request direct to the company.

**NEW RECEIVER LINE**

Sparks-Withington Company of Jackson, Michigan, have introduced their new fall line of Sparton Challenger radio receivers to the public.




The line includes both console and table model receivers and covers a wide range of prices and styling. One table model receiver in the line, the Utility Model No. 100, is a 5 tube, a.c.-d.c. unit which uses a 5" speaker and a built-in loop antenna. This set provides full broadcast band coverage. The cabinet is of polished ivory plastic.

Details of this receiver and others in the Sparton line will be supplied on request by Sparks-Withington Company, Jackson, Michigan.

**TABLE MODEL FM RECEIVER**

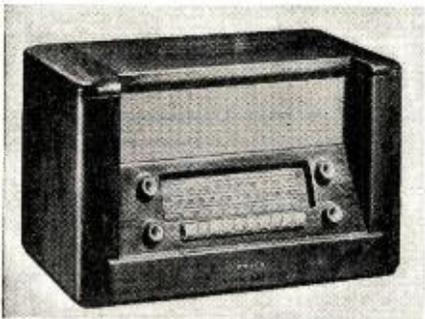One of the outstanding units in the new Philco line is the company's Model 482 table radio which incorpo-



rates FM, standard broadcast, and short-wave reception.

This new receiver provides separate tone controls for treble and bass, ten push-buttons, and a beam power pentode audio system which furnishes three watts of undistorted volume.

The unit uses eight tubes plus a

## HAMS! RADIOMEN!

Compare our prices on choice Government Surplus items listed below:

5" SCOPE BC-1268, 25 tubes including 5CP1. Schematic parts list, HV condensers, pots, dial drive, rotation counter, etc.	\$24.95
Precision resistors, 5000 ohms 1%	.10
4 mfd. 500w paper, metal case, lugs	.69
REMOTE CONTROL UNIT RM-25, controls Xmtrs, Rcvrs, 4 station interphone, rack mount operates on 48 V DC	14.95
1 mfd 200v, molded paper, solar MPV	.05
MICROPHONE AMPLIFIER BC-737, 6x6x2, Aluminum case, less 2-6CS's	3.75
BX-13 Battery Boxes for SCR-195	.30
TRUMPET, 12 watt, University 1B8, NEW	13.95
Coax Plug, 72 ohms, WE #337A	.69
Coax Jack, 72 ohms, WE #464A	.89
0-1 MA DC Weston 301, 3 1/2"	4.95
50 Assorted Condensers, Mica, Paper, etc.	2.29
Kit of 100 1/2 watt popular resistors	1.89
ROTARY BEAM BRAKE, heavy duty	1.49
2 mfd 250v, Metal case, W.E.	.19
RELAY, 12 V DC coil, 50 Amp. conts.	.79

**Clothing Specials—Flyers Available**

Navy Blue Chambray Shirts, NEW	\$1.49
Navy Heavy Denim Dungarees, NEW	1.98
Army Blankets, 100% Wool	4.89
White Overalls, NEW	1.98

F.O.B. Baltimore. Minimum order \$2.00  
Request Flyers W3MQF Ham Dept.

**EASTERN ELECTRONICS SALES**  
31-B Cedar Drive Baltimore 20, Maryland

## GREY LOCK RADIO TUBES

All GT, Glass, and Miniature Types

List Price each, up to \$1.00	
Your Cost, each	29c
List Price each, up to \$2.00	
Your Cost, each	39c
List Price each, over \$2.00	
Your Cost, each	49c

All Tubes carry RMA 90-Day Guarantee.  
**PM SPEAKERS**

4" Alnico No. 5	each \$1.19
5" Alnico No. 5	each 1.29

TERMS: Net C.O.D. No order accepted for less than \$5.00.  
Write for Bargain Catalog  
GREYLOCK ELECTRONIC SUPPLY CO.  
30 Church Street New York 7, N. Y.

## AMPLIFIER

For Call System or  
Phono. Amplifier



25%  
Deposit  
Required

**\$1.95**  
COMPACT-WIRED  
READY TO OPERATE  
USES 35Z5-50L6

**SINGER RADIO & TELEVISION**  
553 Market St. Dept. A Newark 5, N. J.

## COMMERCIAL RADIO INSTITUTE

A RADIO TRAINING CENTER FOR 27 YEARS  
Resident Courses Only • Broadcast, Service, Aeronautical, Television, U.H.F., Preparatory Course. Frequency Modulation, Radar and Marine telegraphy classes forming for Fall Term Oct. 1. Entrance examination Sept. 15.

Literature upon request. Veteran training  
Dept. A, 38 West Biddle St., Baltimore 1, Maryland

## New Vinylite Frequency Record

33 1/3 & 78 RPM; 50 to 10,000 CPS; voice announcements; unmodulated grooves for checking rumble content. Available your local jobber or

**UNIVERSAL RECORDING CORP.**  
20 North Wacker Drive  
Chicago, Illinois

## FREE CATALOG

BIG G. & E. CATALOG OF RADIO, REFRIGERATION AND ELECTRICAL PARTS. at today's lowest prices. Hundreds of newest items in stock, immediate shipment. Send for your copy today.

**G. & E. EQUIPMENT SUPPLY CO.**  
400 N. Sangamon Street  
CHICAGO 22, ILLINOIS



## TRAIN FOR RADIO IN MIAMI

Prepare for a radio career in one of America's most beautiful cities—busy, romantic Miami—at the crossroads of two continents.

Embry-Riddle's internationally known Government-approved School of Aviation offers a full year Radio Course, designed to qualify you for important jobs in the Radio Industry. Approved training under G.I. Bill. Immediate enrollment.

FOR FREE INFORMATION  
MAIL THIS COUPON—TODAY!

Dean of Enrollments—Dept. 55  
EMBRY-RIDDLE SCHOOL OF AVIATION  
Miami 30, Florida

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Check One:  Veteran  Non-Veteran

rectifier and is housed in a duotone cabinet of solid walnut and birdseye maple-grained hardwood with a gold and tan open-weave grille. The cabinet is 12" x 20" x 12 $\frac{1}{2}$ ". The unit comes complete with a built-in triple aerial system.

Philco Corporation, Philadelphia 34, Pennsylvania will supply prices and additional details upon request.

-30-

### All-Wave Antenna

(Continued from page 49)

and the transmission line is negligible.


The second most important characteristic of this new "All-Wave Antenna" is the direction from which maximum reception is obtained. This is important since in the majority of receiving set installations all signals in the television and FM bands will be received from approximately the same directions, as it is the present practice to install television and FM transmitting antennas on the tallest buildings within any city. It is desirable, therefore, that the maximum reception from the antenna be from the same direction no matter what the frequency. The curves of Fig. 2 show field patterns for the Model 300 antenna at representative frequencies in the frequency range under consideration.

The field patterns shown are all with respect to 100 per-cent response in the maximum direction, hence the relative antenna gain cannot be determined from these figures. The curve of Fig. 1 illustrates the antenna pattern gain with respect to a perfectly matched 300-ohm folded dipole.


A transmission line impedance of 300 ohms was chosen since it represents the tentative standard of the RMA and because of its economy and extremely low attenuation. Noise

(Continued on page 199)

Fig. 2. Curves show horizontal field pattern of the antenna at 55, 88, and 195 mc.

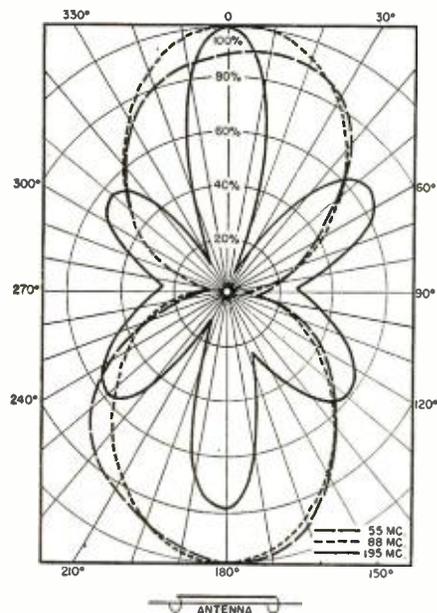
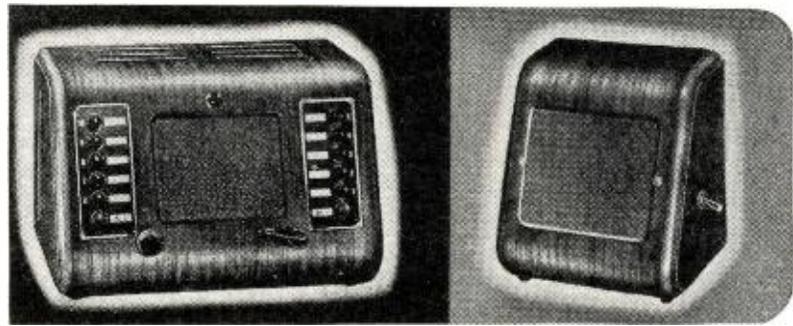
## Tok Fone De Luxe 10 STATION INTERCOMMUNICATION SYSTEM



The TOKFONE DeLuxe represents the culmination of many years experience in the manufacture and sale of Intercommunication Systems. It is by far the most efficient, most economical and the fastest means of carrying on direct, two-way, amplified intercommunication between two or more persons, offices or departments.

The basic system comprises one DeLuxe Master Unit (left) and one DeLuxe Remote Station (right), although Additional Remotes may be added (to the total of 10) to meet the specific requirements of any business.

The DeLuxe System utilizes PUSH BUTTON CONTROL. By simply pressing one button on either side you automatically connect the circuit between the Master and any one Remote. Two-way conversation is made possible by means of the talk-listen key.

The flexibility of this unit may be judged by the fact that when set up for its maximum communication possibilities, 10 Remote stations may be connected to the Master. These are arranged in two groups of 5 each. The Master may call one single station in either group or one station in each group at the same time or may call and converse with all 5 Remotes in either group or all 10 Remotes in both groups at one time. If desired, any Remote can call the Master at any time.

One of the exclusive features of the TOKFONE DeLuxe System is that it is designed so that it may be used with either a two-wire or three-wire cable.

Licensed by Electrical Research Products, Inc., under U. S. Patents of American Telephone and Telegraph Company and Western Electric Company, Inc.

#### SPECIFICATIONS

Cabinet: Hand Rubbed, sloping front walnut finish, wood cabinets.  
 Size: Master 6 $\frac{1}{2}$ " x 7 $\frac{1}{2}$ " x 11 $\frac{1}{2}$ "  
 Remote 4 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ "  
 Circuit: Latest type, push button control. Master utilizes a powerful 4 tube circuit.  
 Power Supply: Operates on 110-120 volts A.C. or D.C. Comes complete with switch on remote station.  
 Power Consumption: 30 watts.

#### FLEXIBILITY

When used as a 3-wire system a switch at the side of the cabinet enables a Remote station to carry on a running conversation with the Master, once the circuit is completed. It also permits the Remote to remain silent when the circuit is not in use and prevents the Master from listening to trivial or non-pertinent conversations at the Remote.  
 When a two-wire cable is used, both the Master and Remote stations always remain open so that a running conversation is possible at all times when the "all" button is depressed or in a closed position.

#### LIST PRICE

Basic System comprising one Master DeLuxe unit (743S) and one remote DeLuxe unit (743SV) \$75.00  
 Additional Remote DeLuxe units (743SV) each... 15.00  
 SPECIAL Master and one Sub-station..... Net \$27.50  
 Each additional Sub-station..... Each 4.45  
 TERMS:—25% deposit with order, balance C.O.D.

WRITE FOR OUR LATEST CUT-PRICE PARTS BARGAIN BULLETIN

CALIFORNIA RADIO & ELECTRONIC CO.

711 N. VERMONT, LOS ANGELES 27, CALIF.

### RADIO ENGINEERING TELEVISION ELECTRONICS

Courses in every phase of radio and electronics open to high school graduates. Thorough training, modern courses. Enrollments limited. Approved Veteran Training.


VALPARAISO TECHNICAL INSTITUTE  
 Dept. RS Valparaiso, Indiana

**10-15 BLUEPRINTER** PRINT COPIES OF SKETCHES, SCHEDULES, ALL DIAGRAMS, AND ENGINEERING DATA. GET EXACT CORRECT COMPLETE DATA AS ORIGINAL. EASY TO MAKE PRINTS COPIES DIRECT FROM WRITTEN, PLOTTED, OR TRACED ON NEGATIVES. IDEAL FOR SHOP ORDERS, RECEIPT LETTERHEADS, STATEMENTS, ETC. BLUE LINE FEATURE INCLUDED. COPIES COST 2¢ PER COPY. RUSH ORDER NOW! 25¢ PER COPY. PAY FOR 15¢ PER COPY.  
**BEST VIBRATOR CO.**  
 BOX 5802, CLEVELAND, I. OHIO

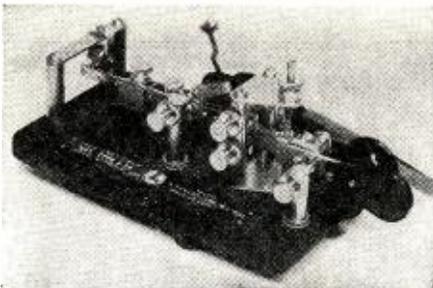**UTICA TOOLS**

ALL TYPES FOR MORE TOOL MILEAGE  
 Ask Your Dealer

**UTICA DROP FORGE AND TOOL CORPORATION**  
 UTICA 4, NEW YORK



### HIGH QUALITY SPEED KEY . . . \$6.95

DON'T MISS THIS BARGAIN! Made by Lionel on pattern made famous by another mfr. of speed keys. W/plug & shorting switch. NEW, ORIGINAL BOXES—\$6.95. Four for \$27. Money back if not pleased.

**ALTIMETER TRANSCEIVER RT-7/APN-1.** FM 418-462 Mc, w/14 tubes, dynmr. and diag. New or like new. See our ad Aug. "RN." Still a few left at this low price. . . . \$9.88

**TUBES: WE WILL NOT BE UNDERSOLD** on indiv. cartoned, guaranteed tubes. See our ad Sept. "RN."

**HALLICRAFTER SX-28** and matching speaker. Look like new, guaranteed. . . . \$150

### PORTABLE FIELD TELEPHONE EE-8



Local and common battery w/handset, generator, ringer, ind. coils, etc., in leather or heavy web case (please do not specify). Fine for intercom, farm phones, garage extension. NEW— \$15.95, two for \$31

**GOOD USED—** \$11.95, two for 23

**USED, FAIR—** \$7.95, two for 15

### ODDS 'N' ENDS

**WIRE:** #18 stranded hook-up, plastic insul. 10 colors: red, blue, green, purple, black, white, brown, yellow, orange, grey. 100 ft. any color—\$1. 1000 ft. any one color. . . . \$6.88

**WHIP ANTENNA:** Light-wt. snap-to type. 10 1/2 ft. extended, 17" collapsed. Unused, shop-worn, \$1.29. Two for . . . . 2.35

**TEST LEADS:** Insulated tips & prods, pair \$3c. 2 pr. for . . . . 1.00

**CONDENSER:** Mica, 500 mmf 8000V, 3a @ 300kc, stand. brand. 115VAC makes each of 3 contacts 80 times per minute. See our ad Aug. "RN." . . . . 4.88

**TRANSFORMERS:** 250VDC 150ma, 5v 3a, 6.3v 3a shielded Jern. #1138. . . . 3.78

312VDC 85ma, 5v 3a, 6.3v 2a, shield, #1159 2.65

**CHOKES:** 12 by 200ma 105 ohm Thord. T15C45 equiv. . . . . 1.88

Postage extra. Minimum order \$2.00. FREE LIST. TERMS: Net cash, 25% deposit on C.O.D.'s.

### ELECTRONIC SUPPLIES

317 East 2nd St. Tulsa 3, Okla.

## THE SIMPLEST FM CONVERTER



Don't throw away your 40-50 mc. FM tuner! Convert to 88-108 mc. operation with our Model 1002A FM converter. Connects in series with the antenna lead-in at the receiver. No power required. Works with all superheterodyne FM tuners or receivers. List price \$10.00.

Write for information or See Your Local Parts Jobber

Watch for announcement of our new model 1003A UHF probe for service alignment with any oscillograph and model 1004A narrow band FM converter for amateur communications receivers.

### Crystal Devices Co.

P.O. Box 380 G.P.O. New York 1, N. Y.

# Classified

Rate 20c per word, Minimum 10 words.

## RADIO ENGINEERING

RADIO Engineering Broadcasting, Aviation and Police Radio, Servicing, Marine Operating and Electronics taught thoroughly. Expenses low. Write for catalog. Valparaiso Technical Institute, Dept. N, Valparaiso, Ind.

### FOR SALE

NEW and used Hallicrafters, National, Hammarlund, Collins, RME, Pierson, Millen, Temco, Supreme, other receivers, transmitters, parts, etc. Lowest prices. World's best terms financed by me. Reconditioned S41 \$19.00, S38 \$35.00, S20R \$49.00, S40 \$59.00, SX28 \$139.00, SX42 \$199.00, HQ120X \$99.00, S39, SX16, SX17, SX24, SX25, SX32, S36A, HRO, NC240D, NC173, HQ129X, SPC400X, SPC400SX, etc. Shipped on trial. Send \$5.00. Pay rest COD. Write. Henry Radio, Butler, Mo.

**SOUND Recorder** (less amplifier). Records and plays back on film mechanically, no processing. Complete with cutter, crystal pickup, 2000 foot reel of film and all accessories and instructions. Will swap for 16 inch disc recording turntable, or sell. Paul Schultz, 525 Wilson, Manchester, New Hampshire.

**RADIO Tubes—Dealers, order your needs—be surprised at prices.** Address Radio Tubes, Box 108, Elizabeth City, N. C.

**FREE wholesale bulletin.** Tubes, parts. Bargain prices. Henshaw Radio Supply, 3313 Delavan, Kansas City, Kansas.

**WRITE Dept. RN18** for our free wholesale list of radio parts & accessories. R. C. Radio Parts & Distributing Co., 731 Central Ave., Kansas City 6, Kansas.

**F. M. WALKIE Talkie (B.C.1000A)** with 18 tubes, 2 antennas, hand set and ear phones. 42 to 48 Mc. Easily converted to 6 meters. Shipping wt. 62 lbs. Price, \$29.50. S.C.R. 610 (B.C. 659J) Portable F.M. Transmitter and Receiver, 14 tubes, antenna, built in loud speaker, 120 Crystals, etc. With vibrator and battery supply for 6, 12, 24 volt D.C. Frequency range 27 to 39 Mc. Shipping wt. 127 lbs. Price \$59.50. Used, sold as are, F.O.B. A&N Supply Company, Richmond, Va.

**WIRE recorder magazine.** Limited quantity, made for Army, and Air Corps. New, includes 10,000 feet stainless steel wire, spools, level-wind, brake control, automatic switches, elapsed time indicator, etc. in a fully assembled, dust-proof unit. Price \$45.00. McCoy Sales Co., P.O. Box 335, Berea, Ohio.

**LOWEST Prices.** Radio Tubes, parts. Bargain lists 3c. Potter, 1314 McGee, Kansas City 6, Mo.

**SELENIUM Rectifiers,** full wave, 1/2 ampere, \$1.85; 1 ampere, \$2.50. Half wave 5 amperes, \$4.50; 2.2 amperes, \$2.25; 1.5 ampere, \$1.85. Bulletin. Bursma Radio, Route 5, Grand Rapids, Mich.

**PANORAMIC Adapter and Cro, AN/APA-10,** 60 cy. conversion. Complete \$95.00. 29 W. 18, Hutchinson, Kansas.

**CAMERA Suppliers to the Radio Profession.** Special prices on Argus, Revere, Keystone, Briskin cameras, etc. We buy and trade. Just write: Charles Wolfe, 167 Canal Street, N. Y. 13, N. Y.

**SCHEMATIC Diagrams, BC-348, SCR-522, SCR-274-N transmitter and receiver.** \$1.00 each. Neal Brown, Ingleside, Texas.

**SCHEMATIC for ten tube hi-fi phono amplifier,** \$1.00. Bob L. S.—WØBPR, 2213 Fremont S., Minneapolis 5, Minn.

**QUALITY radio parts at quantity prices.** See our ad this issue. Write for special parts bulletin. Interstate Radio & Parts Co., 6357 S. Ashland Avenue, Chicago 36, Illinois.

**AVAILABLE** now a new FM kit, 7 tubes with frequency response of 86-110 MC, completely self contained receiver. The RF section is pretuned at the factory. 2 I.F. stages, 1 limiter stage and 1 discriminator. Miniature tubes used throughout. Price \$29.95. Special for the month, 10 inch television kit, Price \$124.50 less tubes. 7 inch television kit \$77.50 less tubes. Details forwarded on request. Radio Wholesalers Supply Co., 120 Liberty St., New York, N. Y.

### WANTED

**WANT to buy cheap,** 4 used American-Beauty soldering irons. State price. A. Morgan, 410 McCready Ave., Louisville, Ky.

**SCR-5 36's.** State condition, price, quantity. Fliderblum, 49 Cliff Ave., Yonkers, N. Y.

**TELETYPEWRITERS** used or new, parts, accessories. Box 447, % Radio News, 185 N. Wabash Ave., Chicago 1, Ill.

**TRC7 RADIO Equipments, RT-53 Receiver-Transmitters, AS-12 Antennas.** Box 448, % Radio News, 185 N. Wabash Ave., Chicago 1, Ill.

**WESTERN Electric Carrier Telephone or Telegraph Filters, equalizers, repeating coils, etc.** Also CF1 and CF2 carrier equipment and parts. Box 450, % Radio News, 185 N. Wabash Ave., Chicago 1, Illinois.

**W E or Kuthe Type 394A Grid Controlled Rectifiers.** Box 451, % Radio News, 185 N. Wabash Ave., Chicago 1, Illinois.

## CORRESPONDENCE COURSES

USED correspondence courses and educational books bought, sold, rented. Catalog free. Educational Exchange, Henagar, Ala.

**CORRESPONDENCE Courses and self-instruction books,** slightly used. Sold. Rented. Exchanged. All subjects. Satisfaction guaranteed. Cash paid for used courses. Complete information and 100-page illustrated bargain catalog FREE! Write Nelson Company, Dept. 59, Chicago 5, Ill.

USED Correspondence Courses and Educational Books sold or rented. Inexpensive. Money-back guarantee. Write for Free Catalog listing 4000 bargains. — (Courses Bought.) — Lee Mountain, Pisgah, Ala.

**AMATEUR radio licenses.** Complete code and theory preparation for passing amateur radio examinations. Home study courses. American Radio Institute, 101 West 63rd Street, New York City 23.

## SITUATIONS WANTED

**FIRST class Commercial Radiotelephone license.** Maintenance experience. Position desired. J. Martin, Box 66, Citronelle, Ala.

## HELP WANTED

**WANTED Servicemen also Service Organizations** for television sets in all television cities from New York to Los Angeles. Experienced. Apply in writing describing experience in full. United States Television Mfg. Corp., 3 West 61st Street, New York 23, N. Y.

**SALESMEN and Sideline Salesmen** wanted by manufacturers and originators of record and album hassocks. Also a complete line of record carrying cases, storage albums and accessories. Our line includes many hot items for the Phonograph and Radio trade; also Department and Furniture stores. Inquire: P. O. Box 406, Mt. Vernon, N. Y.

**INSTRUCTORS in Radio-Electronics and Television.** Prefer former Navy Radio Technician Instructors with Teacher Training. Must be willing to locate in Detroit, Mich. Write to Box 452, % Radio News, 185 N. Wabash Ave., Chicago 1, Ill.

## PATENT ATTORNEYS

**PATENTS—U.S. and Foreign Patents Secured.** Trade-marks and Copyrights registered. Searches made to determine Patentability and Validity. Patent, Trade-mark and Unfair Competition Causes. Lancaster, Allwine & Rommel, Registered Patent Attorneys, Suite 414, 815 15th St., N.W., Washington 5, D. C.

## MISCELLANEOUS

**ELECTRIC meter laboratory.** Electrical instruments, tube checkers, and analyzers repaired, checked and calibrated. Prompt and reliable service guaranteed. Hazleton Instrument Co., 140 Liberty St., New York 6, N. Y. Tel. Barclay 7-4239.

**ELECTRICAL Instruments.** All makes and models repaired. Correspondence invited. Haledon Elect. Instrument Co., 319 Belmont Ave. (Haledon), Paterson 2, N. J.

**WHOLESALE Radio Service** at reasonable rates, quick service, no job too big. Write for full information. Elkins Radio, Elkins, W. Va.

**RADIOMEN, servicemen, beginners.** Make more money, easily. \$250 weekly possible. We show you. Information free. Merit, 216-32R 132nd Ave., Springfield Gardens 13, New York, N. Y.


**DELUXE "Silver on Black"** specially gummed labels. Write for free folder J-10. Professional Press, 801 Wisconsin Ave., Oak Park, Ill.

**FCC License.** How to prepare for theory examination in four weeks. Method of study, \$1.00. Box 41, Steubenville, Ohio.

**SPECIAL Attention:** Radio and Appliance men. Get immediately your copy of this copyrighted manual released for the first time to the radio and appliance industry. It fully covers all angles of post-war servicing, merchandising, and customer-getting psychological techniques. Increase your business efficiency and raise your income by knowing how to handle your customer and sell your services. Researched and written by professional service and broadcast engineers who have been through the mill. This manual now available to all interested parties at \$2.00, postpaid or C. O. D. Satisfaction guaranteed. Address: Sparks and Kahanek, Service and Broadcast Engineers, 206 West California St., Midland, Texas.

**TESTING Equipment.** All types and models. Expertly repaired and calibrated. Free estimates. Metropolitan Electronics, 42 Warren St., N. Y. 7, N. Y.

# TELEVISION CONVERSION

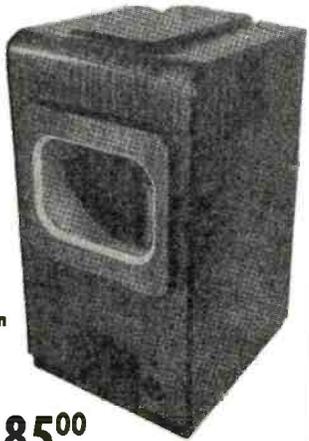

15" Television Set


**\$485<sup>00</sup>**

Build yourself in two hours your own 15" or 20" Television Set from a new RCA latest Model 7" Television Receiver.

We supply you with Cabinet, new RCA 13 Channel Television set complete with tubes, 15" or 20" Picture tube, Focusing Coil, Focus Control and diagram of changes.

Same, but with 20" Tube and Larger Cabinet..... **\$67500**

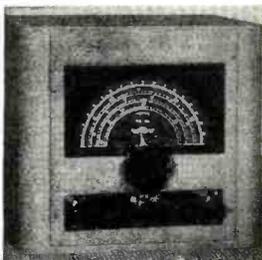World's First Specialized House in Television  
**TELETRONICS SERVICE AND SUPPLY CORP.**  
264 West 40th Street New York 18. N. Y.  
Phone PEnnsylvania 6-8730



## AMATEUR GEAR

Checked before Delivery

Here it is!  
RME  
VHF-152A

**2-6-10-11 METERS.** Superior in all ways—calibrated band spread—band switching—separate antenna connections for each band—voltage regulation—transformer type AC power supply. Enjoy these interesting bands—image free.  
Price **\$86.60** (\$16.60 with order, balance COD)

James Knights Stabilized Crystals—any amateur frequency, with holder, only **\$2.80.**

A Good Buy! ARC 5 Receiver. 3 to 5.1 mc. Good condition. With tubes. **\$3.95.**

**ART A. JOHNSON SALES (W9HGQ)**  
1117 CHARLES ST. ROCKFORD, ILL.

**Amazing! POCKET OR PURSE SIZE**  
**NEW RADIO**

**WORLD'S SMALLEST RADIO KNOWN!**  
Wt. only 1/4 lb. Beautiful Silver Black plastic case. Has Inductive Slide Tuner—W4 Crystal Diode—NO TUBES, BATTERIES OR ELECTRIC "PLUG IN" NEEDED! Should last for years!

**GUARANTEED TO PLAY** **NEW 1948 MODEL**  
on local stations if complete instructions sent are followed. Use it at home, in bed, in many offices, hotels, cabins—most anywhere! **HUNDREDS OF SATISFIED CUSTOMERS ALL OVER THE WORLD!**

**SEND ONLY \$1.00** (Cash, M.O. Check) and pay postman \$2.99 plus delivery fees on arrival or send \$3.99 for Post Paid delivery. Complete as shown—ready to play with self-contained personal phone. **WONDERFUL GIFTS FOR CHILDREN!** Order now at this low bargain price—Prompt shipment on orders sent now—today! Be the first to get YOUR Pocket Radio! (All foreign orders \$5.00 U. S. cash with order.)

**Pu-Kette Radio Co., Inc. Dept. RN-10 Kearney, Neb.**

pickup on the transmission line is admittedly poorer with a balanced unshielded transmission line than with a fully shielded coaxial or fully shielded "Twinax" cable. However, if the 300 ohm line is transposed by twisting (one twist per foot of length), the noise pickup is only 1.5 times as bad

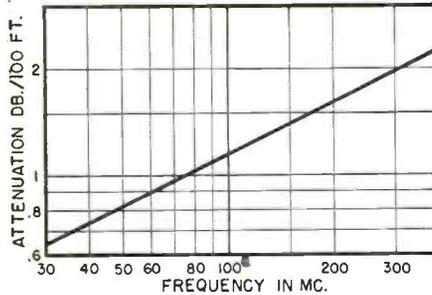


Fig. 3. Antenna line attenuation.

as that obtained with standard RG/59U coaxial cable. This comparison was made with both cables matched at both ends. As mentioned before, this cable has extremely low attenuation, lower, in fact, than similar type cables having lower impedances. The actual line attenuation over the frequency range of interest is shown in Fig. 3.

As may be seen from the photograph, all elements of the antenna are securely grounded to the support member. This permits grounding of the support member to insure protection from lightning. This precaution should be taken in any installation where the antenna is as high, or higher, than surrounding objects such as trees, buildings, etc.

This new Model 300 All-Wave television and FM antenna was produced through the combined efforts of *Tri-craft Products Company* and *Belmont Radio Corporation*, both of Chicago.

-50-


## ADD A NAIL FILE TO YOUR SERVICE KIT

**A FINGER nail file of the type shown will find many uses in the service kit.**

The handle should be taped to avoid shocks and a notch filed near the pointed end will increase the usefulness of the tool.

Wires may be pulled on to check connections—using the notched end of the file—contacts in switches may be cleaned and like tasks performed.

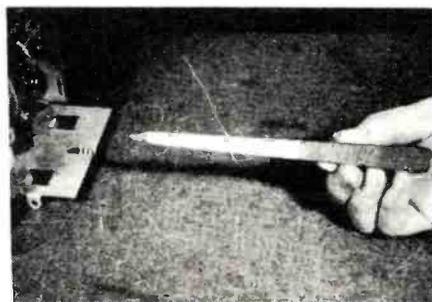Some may prefer to grind the small end of the file flat to use as a screw-driver . . . . . H. L.



# WAR SURPLUS SALES

RADIO - ELECTRICAL - ELECTRONIC EQUIPMENT - PARTS - SUPPLIES

## ARMY AIR FORCE TRANSMITTER RECEIVER

SCR-522

It's the best all round 100-156 Mc job. Crystal controlled, extremely sensitive, superheterodyne; easily worked by anyone. 4 crystal controlled channels, push-pull operation. Receiver has 10 tubes—transmitter 7 tubes with 15 watt output. Can be easily converted to 110 volt, 60 cycle AC operation.

This wonderful buy comes complete with all tubes. Like new. All for only **\$14<sup>50</sup>**


## RECTIFIER & BATTERY CHARGER COMBINATION

No. RA-91A—Selenium plate, full wave 115 or 230v AC; 50-60 cycle, single phase input; output is 6 to 48v DC at 2 to 15 amp; manually controlled complete with overload input and output switches. 0-15 amp DC meter. Excellent for laboratories, servicemen, service-stations. Shipping weight 150 lbs. Price **\$39<sup>50</sup>**
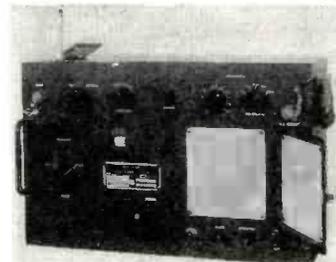
## Crystal Calibrated Signal Generator 1-222-A **\$54<sup>50</sup>**

Operation from 110-117 volt, 60 cycle source, power consumed 40 watts. Self-contained power supply.

**COMPLETE WITH TUBES**  
Within the ranges of the FM and television IF freq and the Police, Taxi, Aircraft, RR, etc. VHF. Instruments are individually hand calibrated and use an accurate vernier-scale planetary dial.




A combination signal generator and heterodyne wavemeter. It consists of a 5 megacycle crystal-controlled oscillator used as frequency standard calibrator, a variable two-range oscillator, an untuned detector with two stages of audio amplification, a sliding-rod stub antenna, a rough pi-type RF attenuator, a frequency calibration chart and a power supply. Coverage of the test oscillator on the low range setting is from 8 to 15 megacycles; the high frequency range coil covers from 45 to 76 megacycles and since the third harmonic is utilized, this gives a coverage of from 135 to 230 megacycles.

The signal generator cabinet measures 19 1/2" wide, 12" high, 7 1/2" deep; weight 50 lbs. Tubes in BC-1298 Power Supply — 16 — 6SN7GT; 1 — 5Y3GT/G; 2—6H6; 1—6SA7; 2—6V6GT; 1—6SJ7. Tubes in 1—222-A: 1—6J5; 2—9006; 2—6SJ7; 1—5Y3GT/G. An additional extra power supply and tubes, with many other small items including cables packed in wooden chest is included in this price. Gross wt. of entire equipment 490 lbs.

Prompt Delivery—Write Dept. RNO  
25% deposit required on C.O.D. order  
Shipped F.O.B. New York Min. Order \$2.00
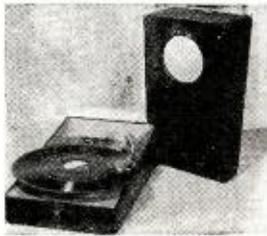
## MICHAEL STAHL, INC.

39 VESEY ST.  
Tel. Cortland 7-5980 New York 7, N. Y.



## DUAL-SPEED 16" TRANSCRIPTION PLAYER

- ★ 3-POUND RIGID PLASTIC TABLE
- ★ POSITIVE RIM DRIVE
- ★ 78-33 1/2 R.P.M. "WOWLESS" MOTOR
- ★ INSTANT SPEED CHANGE
- ★ CENTER BALL BEARING THRUST MOUNT
- ★ HIGH QUALITY PLAYBACK AMPLIFIER
- ★ COMPACT SIZE: 10" W. x 14" D. x 23" L.
- ★ HEAVY DUTY PM SPEAKER
- ★ ATTRACTIVE, DURABLE, LUGGAGE TYPE CASE
- ★ PLAYS ALL RECORDS INCLUDING 16"
- ★ MINIMIZED TANGENTIAL TRACKING
- ★ 20 GRAMS NEEDLE PRESSURE
- ★ PERMANENT SAPPHIRE GUARDED NEEDLE

Here at last is a 16" transcription player that answers all of the exacting requirements of broadcast station, advertising agency, or school use. This professional portable instrument embodies in a readily portable compact case, high quality reproduction, plenty of power, and dependable operation.

Your Net Cost **\$86<sup>00</sup>**  
Complete

Ready to Operate

For 110 V.A.C. 60 Cycle  
AC-DC Universal \$106.00

**ELECTRAPHONE CO.**  
8689 Melrose Avenue  
WEST HOLLYWOOD 46, CALIF.

# FREE

Up-to-the-Minute  
Buying  
Information



- Radio Repair Parts
- Sound Systems ● Tools
- Kits ● Phono Equipment
- Tubes ● Test Instruments
- Experimenters' Supplies

**REGULAR SUPPLEMENTS  
KEEP YOU POSTED**

Catalog sent immediately upon request. Price and Data Supplements, issued regularly, assure you of up-to-the-minute information—give exact and current data you need for profitable buying. Send the coupon today for this helpful buying service.

**BIG VALUES, LARGE STOCKS,  
FAST, DEPENDABLE SERVICE.**

## FREE...SEND TODAY

RADOLEK CO., Dept. B131  
601 W. Randolph St., Chicago 6, Ill.  
Please send your Free Profit Guide Catalog and regular Supplements.

Name .....

Address .....

City ..... Zone ..... State .....

## SAVE AT RADOLEK

200

## INDEX OF ADVERTISERS October, 1947

Advertiser	Page	Advertiser	Page
Abell Distributing Company, The	169	Fahnestock Electric Company, Inc.	111
Air King Products Corp.	31	Fair Radio Sales	168
Algeradio	116	Federal Telephone & Radio Corp.	6, 150
Allied Radio Corp.	9, 80, 140	Federated Purchaser, Inc.	148
American Phenolic Corp.	165	Feiler Engineering Co.	171
American Radio Institute	184	Flanagan Radio Corporation	138
American Radio Supply Co.	177	G & E Equipment Supply Co.	196
American Sales Company	116	G & G Genuine Majestic Radio Parts Service	163
American Surplus Products Co.	152	General Cement Manufacturing Co.	148
American Television, Inc.	24	General Electric	179
American Television & Radio Co.	179	General Electric Company	32
Amplifier Corp. of America	166	General Electronics Distributing Co.	121
Apex Video	190	General Industries, The	113
Arrow Sales, Inc.	82, 83	General Test Equipment	139
Ashe Radio Co., Walter	131	Greenwich Sales Co.	158
Associated Surplus Co.	182	Greenlee Tool Co.	86
Audel, Publisher	116	Greylock Electronic Supply Co.	196
Audiview Radio Parts Co.	166	Hallcrafters Company	5
Baltimore Technical Institute	172	Hallmark Electronics Corp.	183
Beacon Television, Inc.	168	Hammarlund Mfg. Co., Inc.	38, 120, 158
Bell Telephone Laboratories	87	Hanlan Company	188
Berman Company, Inc., Henry O.	128	Harvey Radio Company, Inc.	142
Best Vibrator Company	100, 197	Heath Company	114, 115
Bliley Electric Co.	99	Henry Radio Stores	181
Bliss Electrical School	170	Hershel Radio Company	102, 103
Boland & Boyce, Inc., Publisher	73	Highbridge Radio-Television & Appliance Co.	98
Bonafide Radio Co.	190	Hi-Par Products Co.	76
Bready & Company, Roy A.	170	Hollywood Sound Institute	160
Brooks Radio Distributing Corp.	178	Instructograph Company	182
Bud Radio, Inc.	118	Interstate Radio & Parts Co.	184
Buffalo Radio Supply	106, 107	J. F. D. Manufacturing Co., Inc.	126
Burstein-Applebee Co.	159	J-M-P Manufacturing Co.	190
Buyers Syndicate	170	Jensen Industries	168
C-B Mfg. Co.	184	Jensen Manufacturing Co.	202
California Radio & Electronics	197	Johnson Sales, A.	199
Cannon Electric Development Co.	155	Joseph, Irving	125
Capitol Radio Engineering Institute	34	Klein, Manuel	120
Centralab, Division of Globe-Union, Inc.	22	Lake Radio Sales Co.	110
Chicago Industrial Instrument Company	126	Lectrohm, Inc.	178
Chicago Transformer, Division of Essex Wire	77	Leeds Radio	201
Chief Electronics	194	Legri S Company, Inc.	138
Cleveland Institute of Radio Electronics	123	Leotone Radio Co.	92
Coastwise Electronics Co., Inc.	130	Lincoln Engineering School	184
Colette Products Co.	173	Long Island Radio Company	178
Collins Audio Products Co.	122	Lyell Hardware	180
Columbia Wire & Supply Co.	192	Maguire, Industries, Inc.	193
Commercial Radio Institute	196	Mallory & Co., Inc., P. R.	27, 3rd Cover
Communications Equipment Co.	137	Maritime Switchboard	124
Concord Radio Corporation	117	Martin School of Radio Arts, Don.	144, 190
Coradio	112	Maspeth Telephone & Radio Corp.	94
Cornell Dubilier Electric Corp.	2nd Cover	Melville Radio Institute	157
Coyne Electrical School	93, 128	Merit Coil & Transformer Corp.	18
Crescent Industries, Inc.	30	Metropolitan Electronic & Instrument Co.	78, 79
Crystal Devices Co.	198	Mid-America Co., Inc.	156
D & H Distributing Co.	160	Mid West Radio Corp.	109
DHD Electronics & Appliance Co.	193	Miles Reproducer Co.	194
Davega Stores	95	Milwaukee School of Engineering	194
Deer & Taylor Company	174	Minnesota Mining & Manufacturing Co.	33
DeForest's Training, Inc.	17	Moss Electronic Distributing Co.	157
Delco Radio	15	Munger Co., Rex L.	182
Delehanty School of Television	166	Murray Hill Books, Inc.	16, 81, 161
Dongene Laboratories, Inc.	162	McGee Radio Company	88, 89, 90, 91
Dow Radio	184	McGraw-Hill Book Company	196
Eastern Electronics Sales	196	McMurdo Silver Company, Inc.	10
Editors & Engineers	96, 97	National Company, Inc.	35
Eggert Radio Institute	180	National Engineering Service	180
Electraphone Company	110, 200	National Radio Distributors	154
Electro-Impulse Labs.	150	National Radio Institute	3
Electro Motive Mfg. Co., Inc.	105	National Schools	29
Electro Products Laboratory	138	Newark Electric Co.	173
Electro-Technical Industries	170	Niagara Radio Supply Corp.	129
Electronic Controls Co.	140	Niles Radio Supply	183
Electronic Distributors, Inc.	180	Offenbach & Reimus Co.	132
Electronic Supplies	198	Ohmite Manufacturing Company	36
Electronic Technical Institute	181	Olson Radio Warehouse	94
Electroncraft, Inc.	160	Onan & Sons, D. W.	144
Electronics Institute, Inc.	100	Opad & Green	194
Embry Riddle School of Aviation	196	Os-Tronic Publications	194
Esege Sales Co.	154		
Espey Mfg. Co., Inc.	195		
Etude Electronic Lab.	180		

RADIO NEWS

Advertiser	Page
Pa-Kette Radio	199
Peerless Radio Distributors, Inc.	188
Permoilux Corporation	175
Philco Radio	19
Photococon Sales	190
Potter Radio Company	112
Precision Apparatus Company, Inc.	190
Presto Recording Corp.	11
Price Radio Laboratories	130
Progressive Electronics Co.	162

R & M Radio Company	147
RCA Institutes, Inc.	183
R. C. Radio Parts & Distributing Co.	126
Radio Center	171
Radio Corporation of America	23, 75
Radio Craftsman, Inc., The	134
Radio Developments & Sales Co.	122
Radio Electric Service Co.	104
Radio Ham Shack, Inc.	119
Radio Hospital	128
Radio Kits Company	164
Radio Maintenance Magazine	20, 21
Radio Parts Company	74
Radio Parts Sales Company	194
Radio Press	184
Radio Shack, Inc. of Chicago, The	76
Radio Supply & Engineering Co.	139
Radio Wire Television, Inc.	153
Radiomart, Inc.	165
Radionic Equipment Co.	189
Radolek Company	200
Ravac Electronics Corp.	174
Ray-lectron Company	172
Raytone Electronic Company	172
Reed Mfg. Co.	172
Rek-O-Kut Company	167
Remer Radio	184
Republic Television Corp.	188
Rider Publisher, Inc., John F.	12
Risco Electronic Wholesale Distributors	172, 194
Rostan Corp.	140

SNC Manufacturing Co., Inc.	101
Sams & Co. Inc., Howard W.	26
Scenic Radio	195
Schuh's Radio Parts	160
Senco Radio, Inc.	186
Shain's Radio Service	188
Shure Bros., Inc.	149
Simpson Mfg. Co., Inc., Mark	187
Singer Radio & Television Corp.	196
Snap-On-Tools Corp.	25
Sound Embossers, Inc.	184
Sprague Products Company	127
Sprayberry Academy of Radio	7
St. Louis Microphone Co.	166
Stahl, Inc., Michael	199
Standard Parts Corp.	122
Standard Radio & Electronic Products	185
Standard Transformer Corp.	13
Sterling Electronic Company	178
Stevens Walden, Inc.	28
Sun Radio of Washington D. C.	143
Supreme Instruments Corp.	110
Supreme Publications	37
Surplex Retail Sales Inc.	84
Sutton's Wholesale Electronics, Bill	182

TAB	145
Technical Radio Parts Co.	86
Tek-Kit	170
Telectronics Service & Supply Corp.	144, 180, 199
Television Assembly Co.	177
Telex, Inc.	183
Thor Electronics	150
TIK	192
Tradio, Inc.	154
Transvision, Inc.	8, 133
Triplett Electrical Instrument	14
Tri-State College	189

U.S. Radio Supply	187
United Surplus Materials	112
Universal General Co.	194
Universal Radio Supply Company	108
Universal Recording Corp.	196
University Loudspeakers, Inc.	148
Utica Drop Forge & Tool Co.	197

Valparaiso Technical Institute	197
Van Nostrand Company, Inc., D.	146
Variety Electric Company	136
Vision Research Laboratories	130

W & H Sales Co.	176
War Assets Administration	141
Ward Leonard	175
Ward Products Corp.	86
Ward Radio Co.	174
Warren Distributors	191
Webster Electric	85
Weller Manufacturing Co.	158
Wells Sales, Inc.	135, 151
Western Radio Communications Institute	195
Wholesale Radio Parts Co., Inc.	120
World Radio Laboratories, Inc.	100
Wright, Inc.	189

## Adapting the TBY-7

(Continued from page 41)

more than justified its original cost and the small amount of work involved in adapting it for amateur

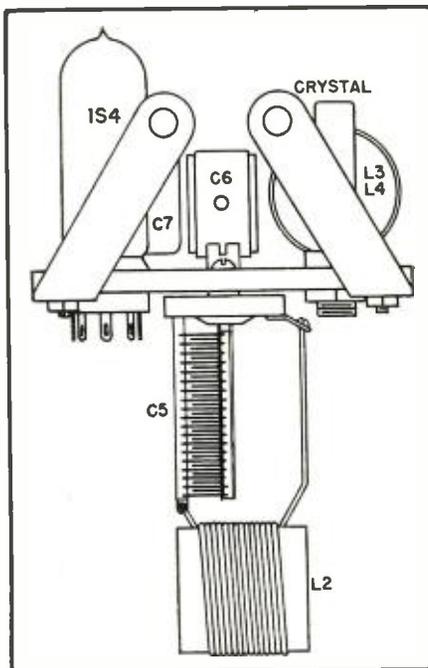


Fig. 3. Rear view of crystal oscillator stage shows placement of component parts.

use. It is an ideal set for cross-town contacts, either as a mobile or stationary installation.

### ERRATA

In the article "A Local Contact Rig" appearing in the July, 1947 issue of RADIO NEWS, the parts list on page 53 omits a value for C7. This should be a .01  $\mu$ f., 600 v. cond.


Two items in the August, 1947 issue are incorrect as printed. In the article, "The Recording and Reproduction of Sound," the formula appearing in the center column of page 58 should be  $H = \frac{B}{\mu}$  instead of  $H = \frac{\mu}{B}$ . The accompanying text is correct.

In the second article, "A 3-Element Rotary Beam," the formula appearing in the first column on page 111 should be  $.66\lambda/4 = 165/f$  or  $57\frac{1}{4}$ .

### Photo Credits

Page	Credit
44, 45	Arthur Haug, Staff Photographer
46, 47	RCA
48	Farnsworth Television & Radio Corp.
49	Tricraft Products Company
51	Brush Development Company
54, 55, 56, 189, 190	Walter Steinhard, Staff Photographer
57	The Triplett Electrical Instrument Co.
68	La Voz de Panama
70	Browning Laboratories, Inc.
105	Gunnis Music Shop
122	Telecon Corporation
134 (bottom)	General Motors
134 (inset)	Motorola, Inc.
146	National Broadcasting Company
191	Allen B. DuMont Laboratories, Inc.

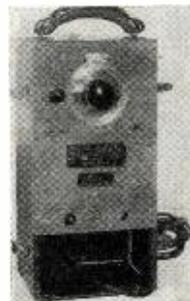LEEDS • The house you have known for 25 years



### BC 438 FREQUENCY METER

110 V. AC operated. Range 195 to 215 megacycles; complete with tubes, crystal, calibration curves and schematic; only... **\$9.95**

### LABORATORY POTENTIOMETER

Wire wound, 100,000 ohm; made to G.R. Co. specifications; 25 watt, 6" diameter. Brand New **\$1.95**



RELAYS—G.E. high current, 24v coil; contacts 200 amps... **39c**  
Sigma sensitive plug-in type; 5 prong, 2000 ohm; coil set at 4 Ma DC; hermetically sealed... **95c**

### METERS

0-1 Ma. G.E.—3" bakelite... **\$3.50**  
0-1 amp RF G.E.—2" bakelite... **\$2.45**  
50 millivolts basic movement, 3" bakelite, will give any range required by use of shunts or resistors... **\$1.95**

### HEINEMANN CIRCUIT BREAKERS

Magnetic type, in 5-20-35-65 amp sizes... **95c**  
Telegraph key J-37;  $\frac{1}{2}$ " silver contacts... **49c**  
DICTAGRAPH carbon hand MIKE, chrome plated; with push to talk switch; while they last... **\$1.45**

### Radio Transmitter & Receiver APS 13

410-420 mc. light weight; fully enclosed; 30 mc. I.F. Complete with 17 tubes, including 5-6J6; 9/6A65; 2/2D21; 1/VRI05. SCHEMATIC supplied with each unit. Only... **\$11.95**



### OIL FILLED CONDENSERS

1 Mfd 5600 V DC. \$2.95	7 Mfd 330 V AC. \$1.25
4 Mfd 500 V DC. .35	0.02 Mfd 8000 V DC. .98
10 Mfd 600 V DC. .98	2 Mfd 2000 V DC. 1.75
16 Mfd 400 V DC. .98	

IN21B Crystal DIODES 3 for \$1. Telescoping antenna 30"..... **25c**  
Ouncer Mike to grid 25:1, low to high impedance 35C; 10 for..... **\$2.95**

PILOT LIGHT Assembly WITH DIMMER, bayonet base type; Ired or White..... **19c**

G.E. 0.1 Mfd 7500 V DC oil condenser..... **\$1.75**  
TOBE 3x 0.2 Mfd; 4000 V DC..... **98c**

## SUPREME—Model 537 \$9.95 VOLT-OHMMETER

BRAND NEW—EXPORT PACKED 3" Full Vision type Scale, with basic 100 Microampere D'Arsonval type movement.

A completely self contained pocket type multimeter, with functions for the measurement of DC voltage from 0.1 to 600 volts in 4 ranges. Measurement of resistances from 1 ohm to 1,000,000 ohms (1 megohm) can be made in 4 ranges. Height 5 3/4", width 3 3/4", depth 2 3/4". Shipping weight 3 lbs. Complete with operating instructions and circuit diagram.

### BEST BUY OF THE MONTH

24 conductor rubber covered cable, 25 ft. lengths; with H. B. Jones connector on each end..... **75c**

If not rated 25% with order, balance C.O.D. All prices F.O.B. our warehouse New York. No order under \$2.00. We ship to any part of the globe.

## LEEDS RADIO CO.

75 Vesey St., Dept. RNO  
Cortland 7-2612 New York City 7

# Listen

it's a

# Jensen

## SPEAKER

# 3 New

## CONCERT\* SERIES PM SPEAKERS

with Alnico 5 "R" Motors

The new JENSEN Concert Series speakers illustrated are now available at price levels only slightly higher than the well-known Standard Series models P12-S, P10-S and P8-S. These new "R" speakers offer unequalled values in power handling capacity, in efficiency, and in response-frequency. Overall performance is just a notch below that of the famous JENSEN PM12-H (now P12-Q), PM10-H (now P10-Q) and PAH-8 (now P8-Q), at substantial price savings.

Model P12-R, ST-103 - 12 watts . . . . \$19.50  
 Model P10-R, ST-121 - 10 watts . . . . 18.50  
 Model P8-R, ST-169 - 9 watts . . . . 15.25

For complete information on *all* models in the Concert series, as well as on other JENSEN equipment, send today for JENSEN Catalog No. 1010. Use the handy coupon below.

JENSEN MANUFACTURING CO.  
 6617 South Laramie, Chicago 38, Illinois  
 Please send me a copy of the 1947 Jensen catalog.

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_


\*Trade Mark Registered

JENSEN  
 MANUFACTURING  
 COMPANY


In Canada: Copper Wire Products, Ltd.  
 11 King St. W., Toronto 1



MODEL P8-R

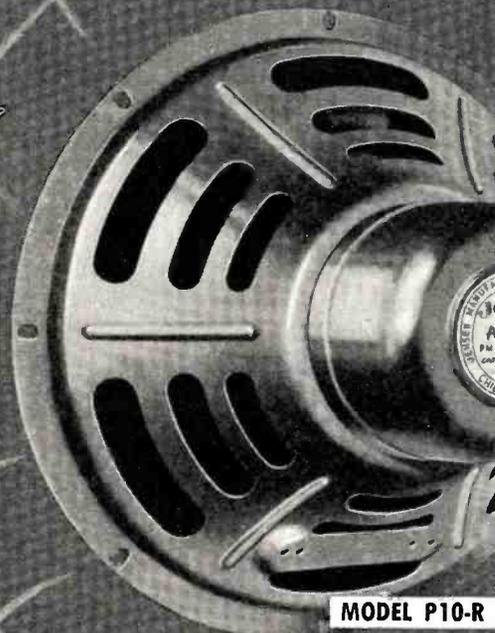

MODEL P10-R

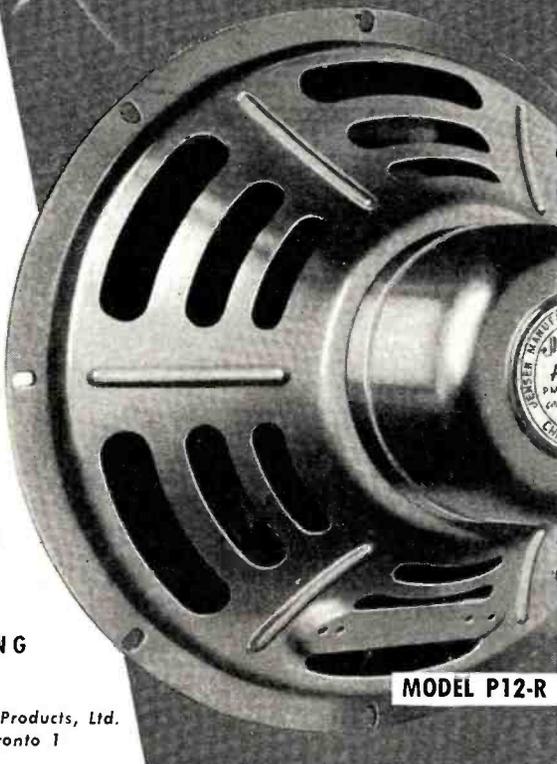

MODEL P12-R





**T**HE Vitreous Enamel Resistors emerging from these huge Mallory baking ovens are famous everywhere for fine performance. Wound with an accuracy of  $\pm 5\%$  they are coated with a high grade enamel, evenly applied, which gives them maximum protection from moisture and corrosion—assures uniform heat distribution too.

You can depend on these resistors to dissipate heat rapidly, to withstand tough atmospheric conditions, to remain free from failures, to stay accurate — to be everything implied in an Approved Precision Product. You pay no more for this premium quality.

Available in fixed and adjustable types, Mallory Vitreous Enamel Resistors run from 10 watts to 200 watts and have a wider range of convenient stock resistance values. You'll find them at your Mallory distributor—a distributor ready to give you detailed information about prices and catalog numbers, and willing to serve you in any other way.

**YOU EXPECT MORE AND GET MORE FROM MALLORY**

**P. R. MALLORY & CO. Inc.**  
**MALLORY**

VIBRATORS . . . VIBRAPACKS\* . . . CAPACITORS . . . VOLUME  
 CONTROLS . . . SWITCHES . . . RESISTORS . . . FILTERS  
 . . . RECTIFIERS . . . POWER SUPPLIES.

\*Reg. U. S. Pat. Off.

**APPROVED PRECISION PRODUCTS**

*National Radio Week*  
 Oct. 26—Nov. 1

**P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA**

# Why the *Lock-In* tube is at home **ON THE SEA!**

**ULTRA-HIGH FREQUENCIES . . . HANDLED WITH EASE**  
Lock-In is *the* tube specifically engineered to more than satisfy the requirements of marine radio equipment—handles ultra-high frequencies with ease! Electrical features include: short, direct connections . . . fewer welded joints—less loss; getter located on top . . . shorts eliminated by separation of getter material from leads.

**COMPACT . . . MADE TO FIT SMALL SPACES**  
This famous Sylvania product is ideal for use in seaborne radio equipment—it's so compact . . . has reduced overall height and weight. Has no top cap connection . . . overhead wires are eliminated! Rugged . . . *no* soldered joints—elements can't warp or weave.

**STAYS PUT IN SOCKEY...THROUGH LOCK-IN FEATURE**  
No matter how rough the sea, the tubes in a ship's radio will stay in their sockets—if those tubes are *Lock-Ins*. Specially designed "lock-in" locating lug on each tube keeps it in place—assuring firm socket contact. See Sylvania Distributors or write Radio Tube Division, Emporium, Pa.

# SYLVANIA ELECTRIC



**SYLVANIA'S LOCK-IN TUBE . . .**  
. . . the radio tube whose electrical and mechanical superiority makes it the ideal choice for marine radar, equipment in the air, on the road, FM and television.