

JANUARY

1952

35¢

In Canada, 40¢

# RADIO & TELEVISION NEWS



## HIGH-SPEED TANDEM WINDING MACHINES

One of the many new machines that makes possible mass-production of uniform condensers (SEE PAGE 45).

THE QUALITY OF RCA TUBES IS UNQUESTIONED



# Extra Performance

as a matter of course...with RCA tubes


The RCA-developed "A" frame construction—used in 6 of the metal-type r-f amplifiers—is one of the many improvements that contribute to the extra performance of RCA tubes.

The "A" frame—shown in red—consists of a top member, two vertical members, and a bottom cross member. The ribbed uprights are welded to the cross member . . . the feet of the uprights are welded to the grounded metal header. In effect a truss, this rigid "A" frame acts as the supporting member for the tube elements. Its increased resistance to vibration reduces the possibility of electrode displacement due to wear on the holes in the mica spacers . . . and thereby

plays an important role in reducing microphonics and maintaining uniform tube characteristics.

In addition to imparting rigidity to the tube elements, the top and bottom members of the "A" frame serve as shields. The two ears on the top member add to its effectiveness in reducing grid-to-plate capacitance . . . the tab on the lower member—which extends down to the stem—provides additional shielding between grid and plate leads.

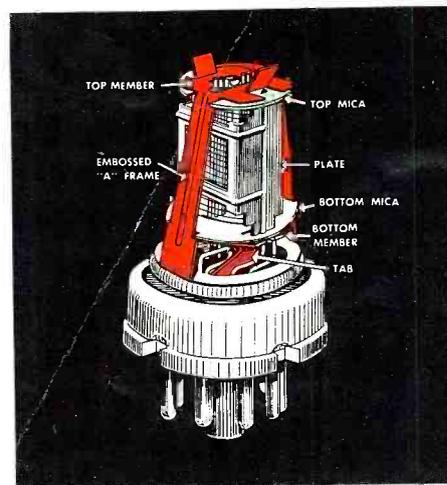The extra performance built into RCA tubes accounts for their high quality, long life, and dependability. They cost no more. Why not use them for your daily tube requirements?




Keep informed—keep in touch with your RCA Tube Distributor



**RADIO CORPORATION of AMERICA**  
ELECTRON TUBES  
HARRISON, N. J.


# There's No Comparison!

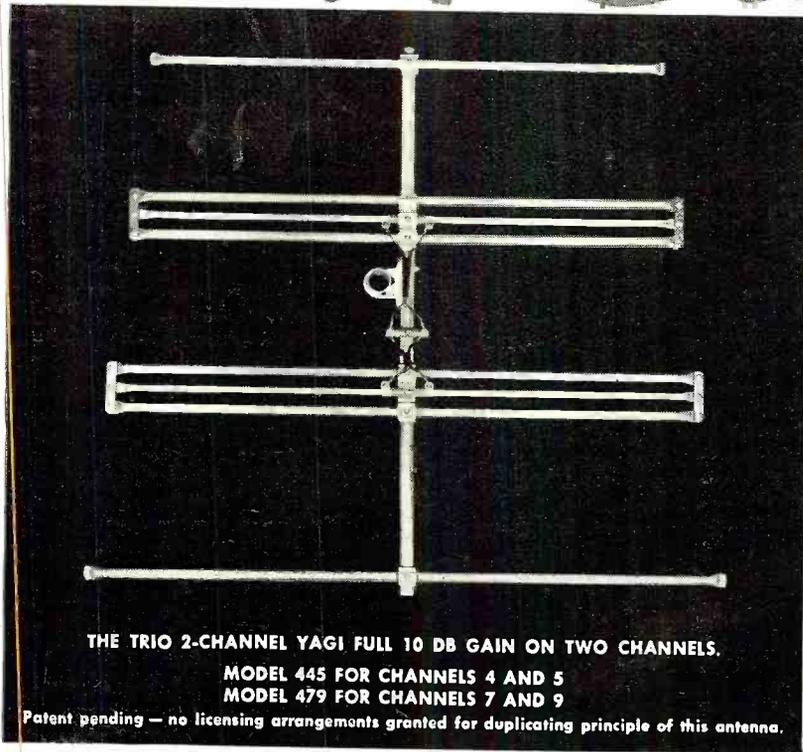


THE TRIO 2-CHANNEL YAGI FULL 10 DB GAIN ON TWO CHANNELS.

MODEL 445 FOR CHANNELS 4 AND 5  
MODEL 479 FOR CHANNELS 7 AND 9

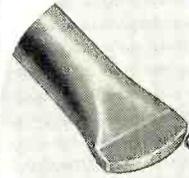
Patent pending — no licensing arrangements granted for duplicating principle of this antenna.



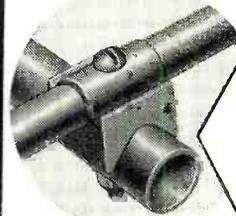Yagi elements of .035" thick seamless aluminum, are full 5/8" in diameter. Ends are crimped for greater strength and to cut down vibration. Prevents entrance of dirt and moisture.



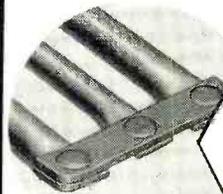An extra clamping member permits taking up bolts tight without putting undue strain on element. Cast aluminum V block assures perfect right angle alignment. No detail of design or construction has been overlooked to make the TRIO 2-Channel Yagi the finest fringe area TV antenna available anywhere — at any price!



Double-folded dipole sections have heavy gauge aluminum brace bars securely riveted to element ends thus providing positive electrical connection and extreme rigidity. Workmanship throughout is of the highest order.

## TRIO-TOPS ALL IN DESIGN, CONSTRUCTION, PERFORMANCE

*The Original*

2-CHANNEL YAGI

One of the most widely imitated antennas on the market today, the TRIO 2-Channel Yagi still stands alone in efficiency and strength.

TV buyers — and sellers — are discovering that "look alike" is not enough — that imitations are never as good as the original.

There is no secret to TRIO's marked superiority. The simple truth is that TRIO slights no construction detail, overlooks no design feature. This means unparalleled

efficiency — rugged dependability for both installer and TV set owner.

Installers! Avoid profit eating call-backs caused by poorly made imitations! Set owners! Enjoy years of dependable, efficient TV reception! Compare the TRIO 2-Channel Yagi with any other TV antenna at any price. Yes, compare — then you, too, will insist on an original TRIO — the 2-Channel Yagi that set the standards.

## TRIO the "Trouble-proof" TV Rotator



For years of dependable, unfailing service — in good weather and bad — you can't beat the new TRIO TV Rotator and Direction Indicator.

Sturdy and completely weatherproof, the TRIO Rotator will support the heaviest TV arrays — even in 80 MPH winds! Its sound design and construction has been proven by 3 years of extensive field testing under every extreme of weather. The TRIO Rotator will not freeze up!

### 2 HEAVY DUTY MOTORS

Two separate 24 volt motors are used — one for each direction of rotation. Thus, each motor operates just 50% of the time — cannot burn out. Positive acting electrical stops at both ends of 360° turn eliminates lead damage.

Housing is die-cast aluminum for greater strength, lighter weight and perfect alignment of parts. The TRIO Rotator is precision built throughout.



SMARTLY STYLED  
DIRECTION  
INDICATOR

The TRIO Direction Indicator is housed in a sturdy plastic cabinet of graceful lines. It is a beautiful instrument that will blend harmoniously with any furniture style.

Utmost ease in selecting the desired antenna direction is provided by a new "finger-tip" control that operates at a light touch and the easy-to-read dial face that clearly and instantly indicates the exact antenna position.



*Trio*

MANUFACTURING COMPANY  
GRIGGSVILLE, ILLINOIS

**Editor**  
**OLIVER READ, D.Sc., D.Litt.**

**Managing Editor**  
**WM. A. STOCKLIN, B.S.**

**Technical Editor**  
**H. S. RENNE, M.S.**

**Assistant Editor**  
**HAROLD BECKER**

**Midwest Editor**  
**RAY FRANK, W9JU**

**Assistant Editor**  
**P. B. HOEFER**

**Television Consultant**  
**MILTON S. KIVER**

**Short-Wave Editor**  
**KENNETH R. BOORD**

**Staff Artist**  
**R. S. KUPJACK**

**Chief Draftsman**  
**B. L. NEWMAN, W9ROB**

**Advertising Manager**  
**L. L. OSTEN**

**Midwest Adv. Manager**  
**JOHN A. RONAN, JR.**

**Western Adv. Manager**  
**JOHN E. PAYNE**

**Art Director**  
**HERMAN R. BOLLIN**

# RADIO & TELEVISION NEWS

Reg. U.S. Pat. Off.

Radio News Trademark Reg. U. S. Pat. Office • Television News Trademark Reg. U.S. Pat. Office.

First in  
 radio-television-electronics

Average Paid Circulation over 200,000

## CONTENTS

## JANUARY, 1952

Radio on the Main Line.....	Leo G. Sands	31
Successful Servicing of Automobile Receivers.....	I. J. Saltzman	34
A Phased TV Beam Antenna.....	T. A. Prewitt	36
Low-Pass Phonograph Filter Design.....	Robert A. Sinker	38
A Vacuum Tube Keyed Transmitter.....	Jack D. Gallagher, W5HZB	39
A Shirt Pocket Radio.....	George L. Johnson, Jr., W9LQX	42
High-Speed Tandem Winding Machines.....	Sylvan A. Wolin	45
A V.T.V.M. Adapter.....	Ivan L. Joy, W0KKR	46
A Beat-Frequency V.F.O.....	H. W. Kline, W2DKE	48
Simple Service Aids.....	Walter H. Buchsbaum	50
Slide Tuning the 75-Meter Loading Coil.....	Jack Najork, W2HNN	52
Audio Simplified (Part 5).....	David Fidelman	54
A Compact High-Gain Amplifier.....	Lloyd B. Hust	58
Artificial Hangover in Audio Circuits.....	Glen Southworth	60
Mac's Radio Service Shop.....	John T. Frye	62
Crystal Diodes in Modern Electronics (Part 4).....	David T. Armstrong	63
Practical Sound Engineering (Conclusion).....	H. M. Tremaine	66
Built-in Home TV Systems.....	Ira Kamen	78
Radio-TV Service Industry News.....		142



COVER PHOTO: A high-speed tandem paper condenser winding machine in use at the Pyramid Electric Co. factory. Such units insure uniformity and help to cut production costs. (Ektachrome by Jay Seymour)

**Chairman of the Board and Publisher**  
**WILLIAM B. ZIFF**

**President**  
**E. G. DAVIS**

**Secretary-Treasurer**  
**G. E. CARNEY**

**Vice-Presidents**  
**H. J. MORGANROTH**  
**Productions Director**  
**LYNN PHILLIPS, Jr.**  
**Advertising Director**  
**H. G. STRONG**  
**Circulation Director**

### BRANCH OFFICES

**CHICAGO 111**  
 185 N. Webster, AN 3 5293

**LOS ANGELES 1141**  
 815 S. Hill St., TU 6 9213

### DEPARTMENTS

For the Record.....	The Editor	8	Short-Wave.....	K. R. Boord	57
Spot Radio News.....		16	What's New in Radio.....		90
Within the Industry.....		26	Manufacturers' Literature.....		97
Technical Books.....		153			



COPYRIGHT 1951  
 ZIFF-DAVIS PUBLISHING COMPANY  
 366 Madison Ave., New York 17, N. Y.  
 VOLUME 47 • NUMBER 1



Member  
 Audit Bureau of  
 Circulations

**RADIO & TELEVISION NEWS** is published monthly by the Ziff-Davis Publishing Company at 366 Madison Ave., New York 17, N. Y. Copyright under International copyright convention. All rights reserved. Entered as second-class matter July 21, 1948, at the Post Office, Chicago, Ill., under the act of March 3, 1879. Entered as second-class matter at the Post Office Department, Ottawa, Canada. "Postmaster—Please return undeliverable copies under Form 3589 to 64 East Lake St., Chicago 1, Ill." **SUBSCRIPTION RATES:** in U. S., Canada, Mexico, South and Central America and U. S. Possessions, \$4.00 for twelve issues; in British Empire, \$5.00; all other foreign countries, \$5.00 for twelve issues. **RADIO & TELEVISION NEWS** is published monthly by the Ziff-Davis Publishing Company at 366 Madison Ave., New York 17, N. Y. Copyright under International copyright convention. All rights reserved. Entered as second-class matter July 21, 1948, at the Post Office, Chicago, Ill., under the act of March 3, 1879. Entered as second-class matter at the Post Office Department, Ottawa, Canada. "Postmaster—Please return undeliverable copies under Form 3589 to 64 East Lake St., Chicago 1, Ill." **SUBSCRIPTION RATES:** in U. S., Canada, Mexico, South and Central America and U. S. Possessions, \$6.00 for twelve issues; in British Empire, \$7.00; all other foreign countries, \$7.00 for twelve issues. Subscribers should allow at least two weeks for change of address. All communications about subscriptions should be addressed to the Director of Circulation, 185 N. Wabash Ave., Chicago 1, Ill. **CONTRIBUTIONS:** Contributors are advised to retain a copy of their manuscripts and illustrations. Contributions must be accompanied by return postage and they will be handled with reasonable care, but this magazine assumes no responsibility for their safety. Any copy accepted is subject to whatever adaptations and revisions are necessary to meet the requirements of this publication. Payment covers all author's, contributor's and contestant's rights, title, and interest in and to the material accepted and will be made at our current rates upon acceptance. All photos and drawings will be considered as part of the material purchased.

**RADIO & TELEVISION NEWS**

**NOW... GET EVERYTHING YOU  
NEED TO LEARN AND MASTER**

# TELEVISION

**RADIO-ELECTRONICS  
AT HOME!**

Use REAL commercial-type equipment to get practical experience

Your future deserves and needs every advantage you can give it! That's why you owe it to yourself to find out about one of the most COMPLETE, practical and effective ways now available to prepare AT HOME for America's billion dollar opportunity field of TELEVISION-RADIO-ELECTRONICS. See how you may get and keep the same type of basic training equipment used in one of the nation's finest training laboratories... how you may get real STARTING HELP toward a good job or your own business in Television-Radio-Electronics. Mail the coupon today for complete facts — including 89 ways to earn money in this thrilling, newer field.

**D.T.I., ALONE, INCLUDES BOTH MOVIES and HOME LABORATORY** In addition to easy-to-read lessons, you get the use of HOME MOVIES — an outstanding training advantage — plus 16 big shipments of Electronic parts. Perform over 300 fascinating experiments for practical experience. Build and keep real commercial-type test equipment shown at right

Get BOTH of these information packed publications FREE!

**89 WAYS TO EARN MONEY IN TELEVISION RADIO-ELECTRONICS**

**YOU GET ALL 6**

**MODERN LABORATORIES**

If you prefer, get all your preparation in our new Chicago Training Laboratories—one of the finest of its kind. Ample instructors, modern equipment. Write for details!

**MILITARY SERVICE!**

If you're subject to military service, the information we have for you should prove very helpful. Mail coupon today.

**ACT NOW! MAIL COUPON TODAY!**

DE FOREST'S TRAINING, INC. Dept. RN-1-1  
2533 N. Ashland Ave., Chicago 14, Ill.


Without obligation, I would like your Opportunity News Bulletin showing "89 Ways to Earn Money in Television-Radio-Electronics"; also, the folder showing how I may prepare to get started in this thrilling field.

Name.....Age.....  
Address.....Apt.....  
City.....Zone.....State.....



ABOVE: Build and keep a real 17 INCH commercial TV receiver. Optional after completing regular training at moderate added cost.

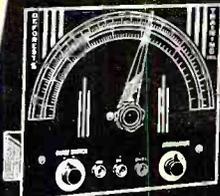
**Here's the REAL THING!  
SET UP YOUR OWN HOME LABORATORY**




**R-F Signal Generator**



**Oscilloscope**

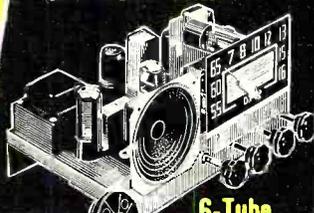

**6-Tube Radio Home Movies**

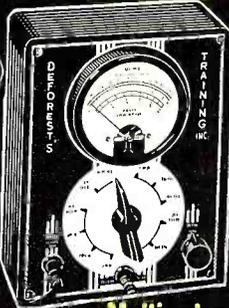

**Multimeter**

**"ONE OF AMERICA'S FOREMOST TELEVISION TRAINING CENTERS"**

**De FOREST'S TRAINING, INC.**

**CHICAGO 14, ILLINOIS  
A De VRY INSTITUTION**



# Service Clinic!

Engineering information to help you better service Raytheon

## THE RATIO DETECTOR


The ratio detector is used to detect frequency modulation and reject amplitude modulation. The improved A.M. rejection of this type of detector requires less stages of limiting in the sound I.F. amplifier.

The circuit of the ratio detector illustrated uses a 6AL5 (or 6T8 etc.) duo-diode, that has balanced capacitance and permeance, and is tuned to the TV intercarrier frequency of 4.5 megacycles.

The 4.5 M.C. sound I.F. provides the input to the resonant

primary of T2 (Ep of Fig. 1) which will induce a voltage across the tertiary winding (Et of Fig. 2) that will for vector study be referred to as zero degrees.

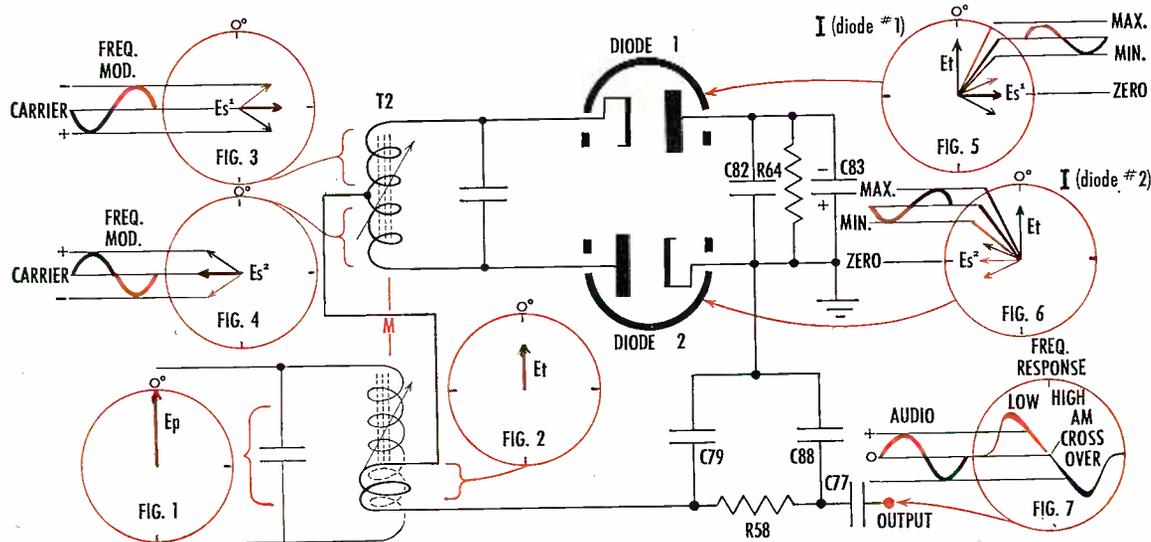The primary will also induce a voltage into the resonant secondary through the loose coupling mutual of M so as to provide approx. 90° phase shift. The secondary will furnish two voltages of opposite (180°) polarity with respect to the center tap. These voltages (Fig. 3 and Fig. 4) will shift in phase angle with frequency modulation of the carrier due to off resonance leading or lagging reactance.



The center tapped secondary is connected to the diodes in a manner such as to place the tertiary in series with each half of the secondary. This will vectorially add the voltages  $E_s$  and  $E_t$  to change the diode current balance as shown in Fig. 5 and Fig. 6 when frequency modulation exists.

However, amplitude modulation does not disturb the balance and will be load limited by the shorting action of the diodes per the time-constant of R64, C82, and C83 lytic.


Only the unbalanced FM currents will appear across C79 (R.F. bypass) and into the R58—C88 de-emphasis filter to produce the audio output resulting from the response curve as shown in Fig. 7. The tuning of the T2 secondary and the value of C79, effect the AM rejection cross-over point illust. in Fig. 7.

Improved circuitry such as this is one of many reasons why you can feel free to recommend Raytheon TV to a friend or customer.

Raytheon TV Presents JOHN CAMERON SWAYZE Sundays on NBC. See local paper for time and station.



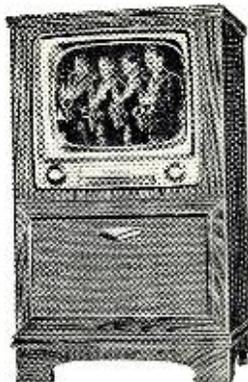Belmont Radio Corp., 5291 W. Dickens Ave., Chicago 39, Ill.  
Subsidiary of Raytheon Manufacturing Co.



Dependably Built for Dependable Performance




THE STARLIGHT—Model RC-1720

RADIO & TELEVISION NEWS



Aluminum Voice Coil  
**SPEAKERS**

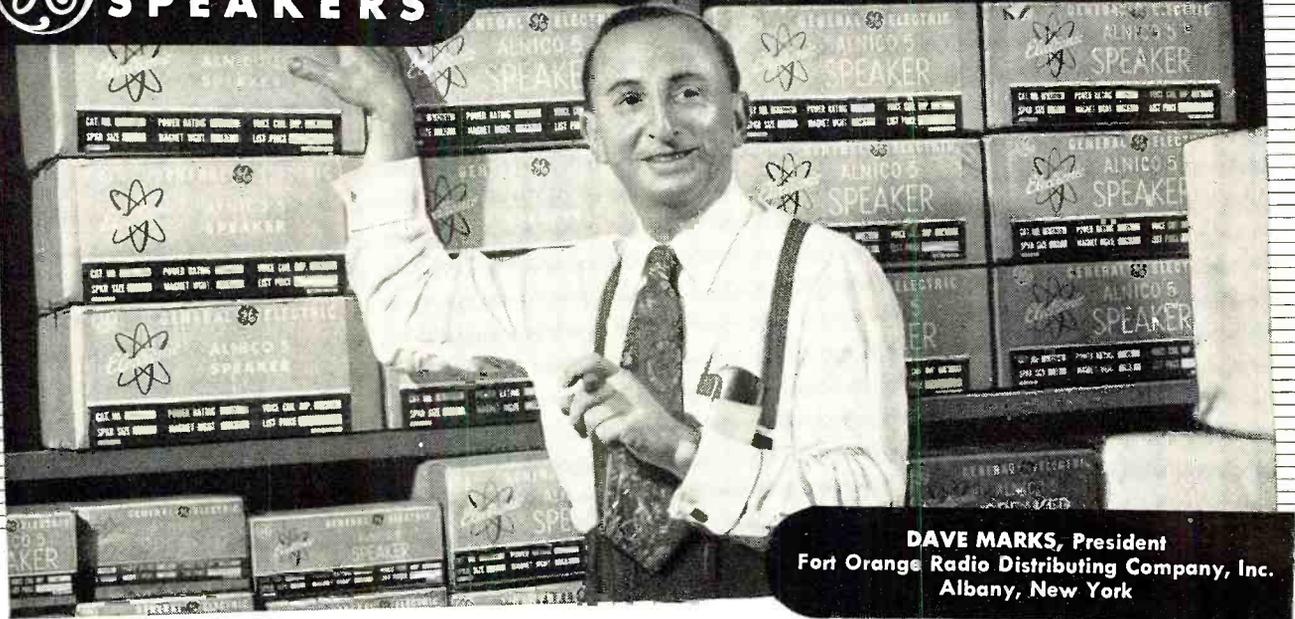

**DAVE MARKS, President**  
Fort Orange Radio Distributing Company, Inc.  
Albany, New York

# "OUR FASTEST SELLING SPEAKER LINE FOR THE PAST 7 YEARS!"

## Quality Product Plus Smart Promotion Spell Success for Aggressive Parts Jobber

**M**y dealer customers don't bother to open the cartons — as they do with other brands — before buying G-E speakers. They know that General Electric factory-packed Alnico units come to them in perfect shape, ready for use. Customer confidence pays off. Because I stock all 27 G-E models, my dealers know I can fill any speaker need."

What Dave Marks does not mention is that his merchandising skill has made him one of the top parts distributors in the East. He makes frequent and profitable use of all G-E sales tools: catalogs, booklets, envelope stuffers, display pieces of all kinds. They're available to you, too, through your General Electric distributor or representative. Call him today for your share of these sales helps.



**Drive-In Theatre Speaker Sales Hot!** With G.E.'s special weather-tested outdoor speaker, Dave Marks, shown here with general manager Ted Sharaf, has increased his drive-in business four times over in two years!

### DEALERS AND SERVICEMEN

Here's a complete new service manual on all General Electric television receivers — 102 models manufactured since 1945! You get 80 pages packed with circuit diagrams, symbols and numbers, tube locations, top and bottom chassis views. Plus photographs and lists of service aids. Mail coupon for it today. Only \$1.00.



General Electric Company, Section 912  
Electronics Park, Syracuse, New York

Send me.....copies of the new 80-page service manual on General Electric TV receivers at \$1.00 each. I enclose \$.....

Check  Money Order

NAME.....

ADDRESS.....

CITY..... STATE.....

**GENERAL ELECTRIC**

# Specially Designed



For ticklish TV soldering, there's no tool like the new 135-watt Weller Gun. Dual spotlights eliminate shadows. Precision balance assures accurate soldering. Long length reaches deep into chassis. 5-second heating saves time and current. Your Weller Gun pays for itself in a few months.



### Check This Exclusive Combination of Features

- **5-SECOND HEATING**—No waiting. Saves power.
- **OVER/UNDER DESIGN**—Tube construction gives bracing action to tip, and improves visibility.
- **DUAL SOLDERLITE**—Prefocused spotlights completely eliminate shadows—let you see clearly.
- **LONGER REACH**—Slides easily into the most complicated set-up. Reaches tight corners.
- **COMPACT DESIGN**—Streamlined and precision balanced for delicate "pin-point" soldering.
- **TRIGGER-SWITCH CONTROL**—Adjusts heat to the job. No need to unplug gun between jobs.
- **DUAL HEAT**—Single heat 100 watts; dual heat 100/135 watts; 120 volts, 60 cycles. Handles all light-duty soldering.

See new Model WD-135 at your distributor, or write for bulletin direct.

- **SOLDERING GUIDE.** Get your new copy of "Soldering Tips"—revised, up-to-date and fully illustrated 20-page booklet of practical soldering suggestions. Price 10c at your distributor, or order direct.



# WELLER

ELECTRIC CORP.

810 Packer Street, Easton, Pa.

## For the RECORD.

BY THE EDITOR

### TELEVISION SERVICE MATURES

ONE year ago in this column we predicted, "The year, 1951, finds the entire television industry facing severe curtailments in production as the result of our defense program and the scarcity of cobalt, aluminum and other materials and components. This curtailment of production is another real reason for sitting tight until Industry can come up with a compatible television system. As a matter of fact, this period of shortages might actually force the FCC and the Industry to shelve immediate plans for color television." Now, because of Charles Wilson's action to put the brake on commercial color television, we can, at least for the present time, direct our attention to other and equally serious television problems.

The beginning of the year 1952 finds the television industry beset with "inventory difficulties" at a time when material shortages are supposedly restricting new set production. Why then, should there be a fearful inventory condition at both manufacturing and dealer levels when we've been told, sets will soon be in short supply?

The answer undoubtedly lies in the need of both the producer and the seller for immediate capital if they are to look forward to a profitable future. The situation is a dangerous one in that a great deal of capital is tied up in warehouse stock by both the dealer and the manufacturer. The future can hold a frightful condition in which the manufacturer unloads large inventories to well-financed dealers and thus undersells the whole market, thereby placing the average dealer in an untenable position.

Considering the problem as it exists, there is certainly a need for a greater selling of television as a medium since approximately only 40% of the television market is sold. Radical corrective measures are necessary in the TV industry, from the telecaster to the dealer.

The one basic factor in this whole TV picture that has not been too "polluted" by outrageous underselling has been Service. To read the set manufacturer's advertising on both the local and the national basis, we can only come to the conclusion that the biggest difference between a good set and a bad set is the service involved. More and more manufacturers are becoming inclined to place the sale of the service contract as an adjunct to the sale of the set. Thus the service dealer finds himself in an enviable position for he, in most cases, is becoming the medium for the sale.

There is a pitfall that lies ahead, of which the serviceman should be cognizant. The pitfall is "priced-service." It is generally recognized today that one of the greatest deterrents to successful selling has been the sale of television receivers below cost. The situation has become so bad that the only profit margin available to the dealer in the sale of a set is the sale of a service contract. Let the serviceman not find himself in the same disreputable position. Since the consumer values service so highly, service should not be sold except as a fair price. To commit yourself to the sale of "priced-service" now would be suicidal to yourself and to the industry in the future.

In the past few months, many manufacturers have announced price reductions in all or part of their line. In some cases these price reductions have been offset by excessive charges for the parts warranty. The cost of a parts warranty should not exceed that of the expected expense in supplying new parts to replace those which may prove defective.

At least one manufacturer has recognized this problem and has included the cost of the warranty in the price of the receiver, avoiding any possibility of misrepresentation.

The increased importance of service has been recognized by the set manufacturers in the appointment of a "service coordinator" by the RTMA. There were undoubtedly many reasons for this appointment; outstanding of which was the acknowledgment that the consumer was being swayed by the importance of reliable service in the purchase of a television receiver. In some respects the coordinating job revolved about the development of a sound public relations program to make the consumer aware of the television service available. The more quickly the industry can resolve the issues with service, the more quickly a coordinated sales and service program can be established.

During the past year great strides have been made by local service organizations to not only place their establishments on a firmer footing but also to make the consumer aware of the importance of good television service. The forward progress of local associations is advancing the day when the service industry will be represented by one spokesman. When the national association comes into being, service will then be able to promote its program more thoroughly and place itself on an equal footing with sales . . . . . O.R.

RADIO & TELEVISION NEWS

**IN STOCK AT  
ALLIED**

**EICO**

**Test Instrument Kits**  
Lab Precision Quality at Lowest Cost

Quick and Easy to Assemble



**221-K Vacuum Tube Voltmeter.** 15 ranges; 26 meg DC input res. Zero center  $4\frac{1}{2}$ " meter; ranges: AC-DC volts, 0-5-10-100-500-1000; res., 0-1000 ohms and 0-1-10-100-1000 meg; db, -20 to +16. With all tubes and parts ready to wire.  $6\frac{1}{2} \times 9 \times 5$ ". Shpg. wt., 10 lbs. **83-152. Only..... \$25.95**



**526-K Standard Multimeter.** 1000 ohms-per-volt; 31 ranges;  $3\frac{1}{2}$ " meter. Ranges: AC-DC volts, 0-1-5-10-50-100-500-5000 at 1000 ohms/volt; res., 0-700, 0-100,000 ohms, 0-1 meg; AC and DC current, 0-1-10 ma, 0-0.1-1 amps; 6 db ranges, -20 to +69. Accuracy: AC  $\pm 5\%$ , DC  $\pm 3\%$ . Ready to wire.  $6\frac{1}{4} \times 3\frac{3}{4} \times 2$ ". Shpg. wt., 3 lbs. **83-166. Only..... \$13.90**



**555-K 20,000 Ohms-Per-Volt Multimeter.**  $4\frac{1}{2}$ " meter, 50 micro-amp D'Arsonval movement. 31 ranges: DC, AC and output volts, 0-2.5-10-50-250-1000-5000 (DC at 20,000 ohms/volt, AC at 1000 ohms/volt); 5 db ranges: -12 to +55; res., 0-2000-200,000 ohms, 0-20 meg; DC current, 0-100 micro-amps, 0-10-100-500 ma, 0-10 amps. Ready to wire.  $6\frac{3}{4} \times 5\frac{1}{4} \times 3$ ". Shpg. wt., 4 lbs. **83-167. Only..... \$29.95**




**511-K Volt-Ohm-Milliammeter.** 3" meter; germanium crystal for AC. Ranges: DC volts, 0-5-50-250-500-2500; AC, output volts, 0-10-100-500-1000; DC current, 0-1-10-100 ma, 0-10-100-500-100,000 ohms, 0-1 meg; db, -8 to +55. Complete, ready to wire.  $8 \times 4\frac{1}{2} \times 3$ ". Shpg. wt.,  $3\frac{1}{2}$  lbs. **83-153. Only..... \$14.95**




**145-K Multi-Signal Tracer.** Traces audibly all IF, RF, video and audio circuits in AM, FM and TV sets. Built-in 4" PM speaker; panel jacks for use of VTVM; germanium crystal diode probe. Response to over 200 mc. Complete, ready to wire.  $10 \times 8 \times 4\frac{3}{4}$ ". Shpg. wt., 9 lbs. **83-158. Only..... \$19.95**

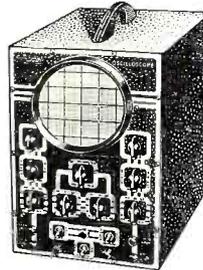**425-K 5" Oscilloscope.** For AM, FM, TV alignment; push-pull deflection. Sensitivity .05 to .1 rms volt/inch. Range, 5 cps to 500 kc. Wide-range multi-vibrator sweep circuit 15-75,000 cps. Provision for ext. sync. Z-mod. and direct input to CR tube plates. With all tubes and parts, ready to wire.  $8\frac{1}{2} \times 17 \times 13$ ". Shpg. wt., 30 lbs. **83-155. Only..... \$44.95**



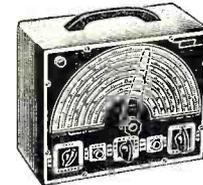**320-K RF Signal Generator.** Uses Hartley oscillator. Covers 150 kc to 34 mc on fund., to 102 mc on harmonics. Unmodulated or 400 cycle AM modulated output. Dial calibrated in 7 bands. Quickly aligns AM, FM sets; aligns RF with any standard AM set. Ready to wire.  $10 \times 8 \times 4\frac{3}{4}$ ". Shpg. wt., 10 lbs. **83-154. Only..... \$19.95**




**322-K RF-AF Signal Generator.** Improved 150 kc to 34 mc instrument, with individual calibration for each of 5 bands. Selects pure RF, mod. RF, or pure AF. Colpitts audio osc. generates 400 cy. pure sine wave voltage. Ready to wire. **83-168. Only..... \$23.95**

**315-K DeLuxe RF Signal Generator.** For AM, FM, TV work. 1% accuracy. Freq. range, 75 kc to 150 mc in 7 calibrated bands; vernier micro-cycle band; volt. reg. power supply. 400 cycle sine wave modulation, less than 5% distortion. Complete, ready to wire.  $12 \times 13 \times 7$ ". Shpg. wt., 20 lbs. **83-162. Only..... \$39.95**



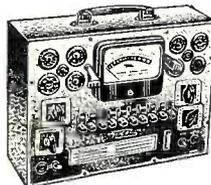**625-K Tube Tester.** Tests all standard AM, FM and TV tubes, including 9-pin miniatures.  $4\frac{1}{2}$ " meter; illuminated chart shows test settings. Tests for shorts and open elements; spare socket for new tubes; built-in power supply. Ready to wire.  $12\frac{1}{2} \times 9\frac{1}{2} \times 4\frac{1}{4}$ ". Shpg. wt., 13 lbs. **83-161. Only..... \$34.95**



**360-K Sweep Generator.** Use with any standard scope for visual TV-FM alignment. Covers 500 kc-228 mc. Variable sweep, 0-30 mc. Crystal marker osc. with variable amp.; external marker can be injected; phasing control; each TV channel center marked on front panel. Ready to wire.  $10 \times 8 \times 6\frac{3}{4}$ ". Shpg. wt., 12 lbs. **83-159. Only..... \$34.95**



**950-K Resistance-Capacitance Bridge.** Measures, tests all resistors, 0.5 ohms to 500 meg., and all condensers, 10 mmfd. to 5000 mfd. Also gives instant R-C-L comparison with any ext. component as standard. 0-500 DC v. source. Tests for leakage, polarization, power factor. Magic eye indicator. Ready to wire.  $10 \times 8 \times 4\frac{3}{4}$ ". Shpg. wt., 10 lbs. **83-164. Only..... \$19.95**



**1171-K Resistance Decade Box.** Supplies resistance values from 0 to 99,999 ohms with  $\frac{1}{2}\%$  precision. Has 5 separate 10-position switches. Includes comparator position and binding posts for instant substitution of actual equivalent component. Complete with all parts, ready for wiring.  $3\frac{1}{2} \times 12 \times 3$ ". Shpg. wt., 3 lbs. **83-165. Only..... \$19.95**



**1040-K Battery Eliminator and Charger.** For charging and all auto radio testing. Gives 0-13 v. output. Has 4-stack rectifiers in full-wave bridge, 10,000 mfd condenser for well-filtered output. Delivers 10 amps DC at 5-8 volts continuously, 20 amps intermittently. Meter measures current and voltage output. Ready to wire.  $10\frac{1}{2} \times 7\frac{3}{4} \times 8\frac{3}{4}$ ". Shpg. wt., 15 lbs. **83-163. Only..... \$25.95**



**EICO PROBE KITS**

With Germanium crystal; for signal tracing and measurement up to 200 mc;  $6\frac{1}{2} \times 1\frac{1}{2}$ ". **83-156. P75-K RF Probe for 221-K VTVM. \$3.75**  
**83-157. P76-K RF Probe for 425-K Scope. \$3.75**  
**83-160. High-voltage probe HVP-1. Adapts Eico 221-K VTVM, Eico 555-K or any other VTVM or 20,000/ohm/V VOM to read up to 30,000 v.  $10 \times 2$ ". \$6.95**

ALL OF THE ABOVE UNITS ARE ALSO AVAILABLE FACTORY-WIRED AND TESTED—SEE YOUR ALLIED CATALOG OR WRITE FOR PRICES

**FREE 212-PAGE 1952 CATALOG**

Send today for ALLIED's authoritative, complete buying guide to all electronic supplies. ALLIED offers the world's largest stocks of tubes, parts, test instruments, audio equipment, industrial components—complete quality lines at lowest prices. Get every buying advantage—speedy delivery, expert personal help, complete satisfaction on every order. Send for your FREE ALLIED Catalog today.

**ALLIED RADIO**

ALLIED RADIO CORP., Dept. 1-A-2  
833 W. Jackson Blvd., Chicago 7, Ill.


Please ship the following Eico Kits.....


\$..... enclosed.  Full Pay.  Part Pay (Bal. C.O.D.)  
 Send FREE 1952 212-Page Catalog.

Name.....

Address.....

City..... Zone..... State.....

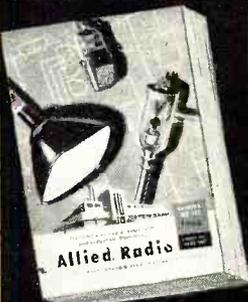

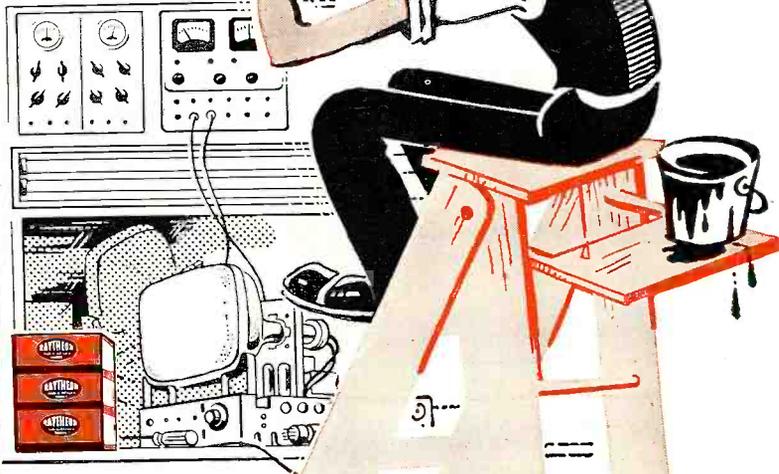


**T**oday's wary customers are more interested in the *business ethics* of a Television and Radio Service Dealer than they are in his *technical ability*.

They look for a Service Dealer who will treat them fairly, a Service Dealer whose guarantee is sound, and then take it for granted that the results will be satisfactory.

The RAYTHEON *Bonded* Electronic Technician Pro-

gram gives customers just what they are looking for. If you can qualify as a Raytheon *Bonded* Electronic Technician your 90-day guarantee on service and parts is cash-protected by a *bond* issued by the American Mutual Liability Insurance Company. You are presented with a Registered Bond Certificate, Creed Displays and Identification Cards all featuring an 8-point Code of Ethics that will convince the most skeptical customers of your integrity and ability.

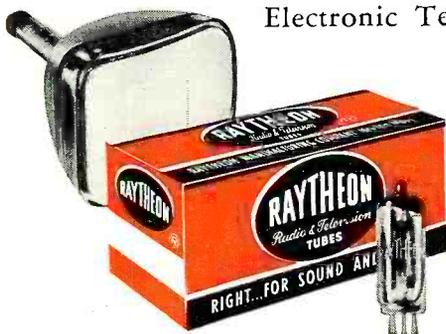Back up your business with the Raytheon *Bond*. Ask your Raytheon Tube Distributor if you qualify for this exclusive business asset. It's yours *at no cost*, if you can.



RIGHT... FOR SOUND AND SIGHT®



**RAYTHEON MANUFACTURING COMPANY**

Receiving Tube Division

Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

*Excellence in Electronics*

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • GERMANIUM DIODES AND TRANSISTORS • RADIAC TUBES • MICROWAVE TUBES

**RADIO & TELEVISION NEWS**

# TRAIN

# for Security! Good-Paying Jobs!

## MAKE THE MONEY YOU'VE ALWAYS DREAMED OF!



# LEARN RADIO -TELEVISION AND ELECTRONICS BY EASY SHOP METHOD TRAINING AT HOME!

You get  
all the parts—even tubes!—  
for this modern Superheterodyne Receiver.  
You learn to build it step by step. And you  
keep it! Get all the facts. Mail coupon now.

Let **NATIONAL SCHOOLS**—a resident-training school for nearly 50 years—train you at home for today's unlimited opportunities in Radio-Television-Electronics. National Schools is one of the largest schools of its kind. It is located in Los Angeles—the center of Radio and TV world! It has four large buildings of modern shops and labs. Its faculty is considered tops in the business.



You learn from lessons prepared by experienced instructors and engineers. Men who are successful Radio and Television technicians. Men who have trained 1000's of men like YOU!



## FREE BOOK TELLS YOU HOW!

Page after page—in color—tells you everything you want to know. Mail the coupon. Get this valuable book today. And if you hurry—YOU GET A FREE SAMPLE LESSON, TOO! Shows how easy National Schools Home Training is. Mail the coupon today.

### You Train At Home—In Your Spare Time

National Schools Shop Method Home Training gives you basic and advanced instruction in all phases of Radio-TV-Electronics. And remember—your training is based on resident school training principles. You learn fast from hundreds of diagrams and pictures. All instructions are written by experienced technicians who work in Radio and TV every day. All instructions have been developed and tested in National Schools' own labs and studios, which are equipped with the latest RCA equipment. No wonder this National Schools course is so up-to-date, practical, interesting. And so easy to learn! And no wonder it is held in such high regard by leaders of American industry! Approved for eligible Veterans.

### We Teach You How To Make Welcome Extra Money—While You Learn!

Many National Schools students—men like you—make plenty of extra dollars each week in spare time! Fixing neighbors' radios, appliances—and other ways we teach you. You start learning and earning from the day you enroll. From the very first lesson!

### WE SEND YOU LOTS OF PARTS LIKE THIS!



With National Schools Shop Method Home Training, you get basic principles and plenty of practical training. You learn by doing. No wonder you learn so fast! We send you many parts—all of professional, modern quality. You do lots of practical experiments. You advance day by day, step by step. Until you can even build the modern Superheterodyne Receiver you see above—plus other important testing units. The free book tells you all about it. The free sample lesson shows how easy the training is. Use the coupon. Send today — without fail!



### Only National Schools Gives You This Professional Multi-Tester!

You get this amazing, new testing instrument—factory-made and tested—complete—ready to use! Simple to operate. Accurate and dependable. An instrument every Radio-TV man needs. Light enough to carry around—so you can use it at home or on service calls. You'll be proud to own this valuable equipment.

### Here are only a few of the Good-Paying Jobs You Can Choose

Radio Station Engineer, District Service Manager, Aircraft Radio Inspector, Own Your Own Repair Shop, Inspector Technician, Service Specialist, Special Government Jobs, Complete TV Service, Sound Truck Operator. Many more! National Schools graduates have secure, good-paying jobs like these! So don't wait—mail the coupon today. Now—while you're thinking about it!

### Attention! Men Going into Service Soon!

National Schools' course quickly prepares you for many important jobs in the Armed Services. With National Schools Training you have an opportunity to get into special service classifications—with higher pay and grade—immediately!

### FREE SERVICE FOR GRADUATES

National Schools uses its great influence and prestige to help you find your place in the field of your choice. Don't put it off! Start yourself toward a skilled trade! Get the big pay you've always wanted!

## NATIONAL SCHOOLS

LOS ANGELES 37, CALIFORNIA • ESTABLISHED 1905

### Today's Shortage of Trained Technicians Creates Chance of a Lifetime For You!

Think of it! With guided missiles, radar, and other electronic devices so important to national defense! With big, new developments in TV. With over 90,000,000 home and auto radios, over 12,000,000 TV sets. With more than 3100 radio stations...over 100 TV stations—and more building every day...yes, imagine the great opportunity you have today! YOU are wanted in Radio-Television-Electronics! America's fastest-growing field. High-pay jobs—the kind you've always wanted—are waiting for YOU!

### Job Security! Big Money! For YOU! in Today's Expanding Industries!

Trained Radio and Television technicians really make important money these days. Thousands of National Schools graduates—men just like you—are earning good money all over the country. Why not you? And—National Schools graduates get the personal satisfaction of being highly-skilled technicians. Men people respect. Men who enjoy their work—rather than having to drag along in just any old job.

### National Schools Has Trained 1000's of Successful Men! Why Not YOU?

In almost every state—and many foreign countries—National Schools graduates are filling big jobs with famous companies. Or running their own successful businesses. What are YOU waiting for? National Schools training is complete training. So when you graduate you can take advantage of today's big opportunities in Radio-Television-Electronics—fast.

**DON'T PUT  
IT OFF!  
GET THE  
BIG SALARY  
YOU HAVE  
ALWAYS  
WANTED!**

### MAIL THIS COUPON TODAY—WITHOUT FAIL!

NATIONAL SCHOOLS, Dept. HR-12  
4000 South Figueroa Street  
Los Angeles 37, California

Mail in envelope  
or paste on  
penny post card.

Mail me FREE the book mentioned in this ad. Also a free sample lesson. I understand no salesman will call on me.

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

Check here if you were released from the Service less than 4 years ago.


Eliminates mismatch! Outperforms standard Yagis!

# Z-MATCH YAGI\*

600 Series

- Perfect match to 300 ohm line, single or stacked.
- Wider spaced elements for higher gain.
- 100% gain in stacking!
- Completely preassembled.

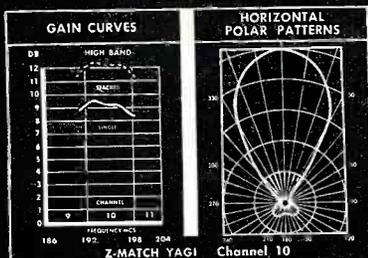Reaches farther for single-channel reception.



\*Patent Applied For

### How The Z-Match Yagi Works

When antennas are stacked, the center feed bars of the folded dipoles are removed, automatically creating a perfect 300 ohm match for the entire stacked Yagi array. These same center bars are then used as half-wave connecting rods. This means

**YOU DON'T PAY FOR STACKING BARS!**

developed by

## CHANNEL



## MASTER

For **"Far Reaching" Results**

There's only ONE

# SUPER FAN


313 Series

The most widely used antenna in the nation.


The highest gain broad-band antenna ever developed.

New reinforced fibreglas inserts in all elements and reflectors.

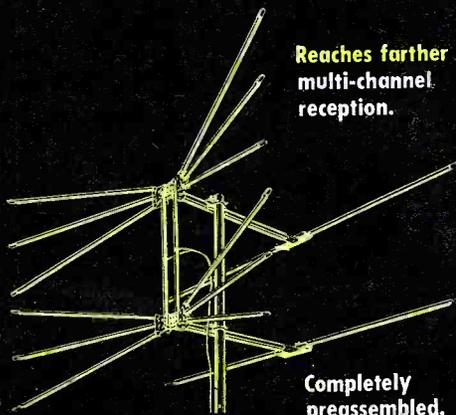Reaches farther for multi-channel reception.




Completely preassembled.

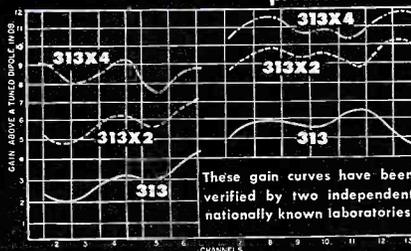

Write for technical literature on these 3 outstanding products.

**CHANNEL MASTER CORP.** ELLENVILLE, N. Y.

RADIO & TELEVISION NEWS

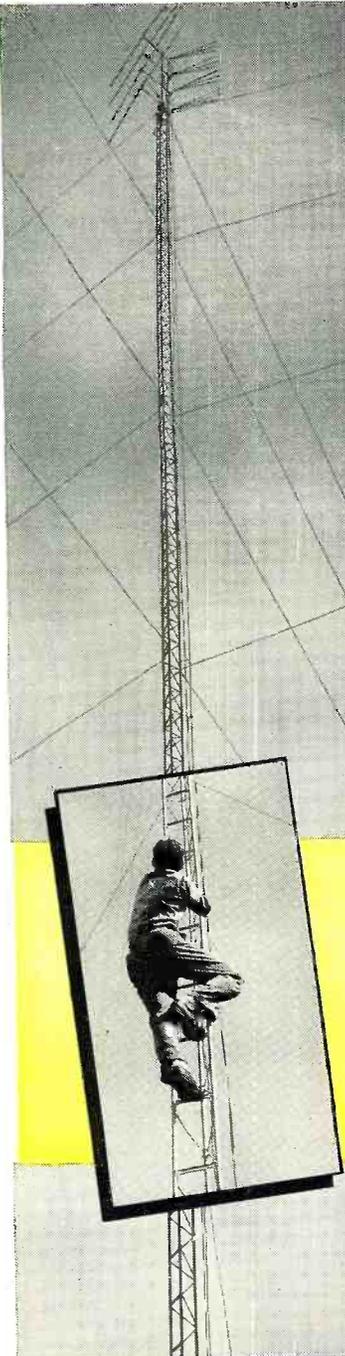


## new! TOWERS


by Channel Master

- Steel tubular uprights.
- Built-in ladder with no obstructions.
- One standard interchangeable section which can be used as a top, middle or bottom section.
- Universal base mount.
- Dual purpose mast or rotator mounting brackets.


For accurate  
flexible and  
quick tube  
testing at  
low cost...  
model 3413-A

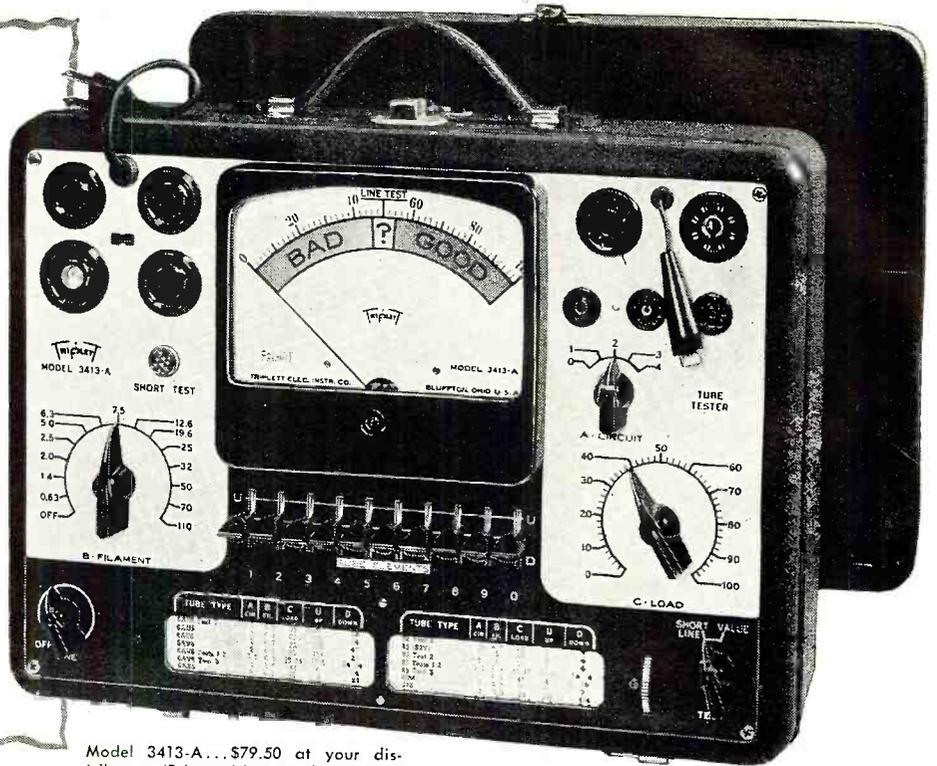

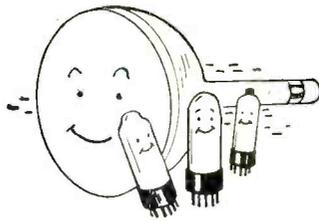
Model 3413-A...\$79.50 at your distributor. (Price subject to change.) BV Adapter, \$7.90 Add'l.



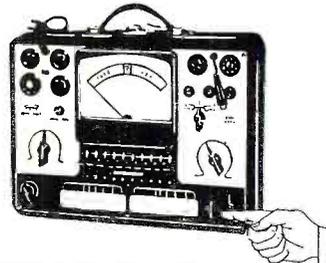
1. YOU CAN TEST MORE TYPES of tubes, also appliances for shorts and open circuits.



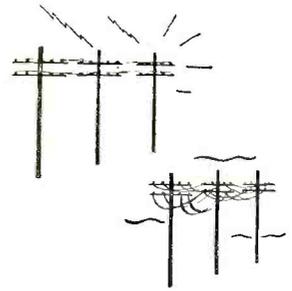2. JUST SPIN THE KNOB—for correct, last-minute data, on the speed roll chart. Lists 700 tubes.



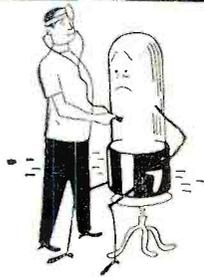3. YOU CAN COMPENSATE for line voltage—just throw snap-action switch.



4. YOU CAN TEST EACH ELEMENT in each tube—by a simple flip of the switch.




5. YOU CAN TEST THE NEW TUBES—including those with low cathode current.



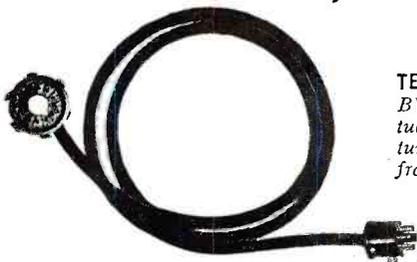6. YOU GET NEW TUBE DATA—immediately, while it is still news. No waiting.

*Nearly Half a Century of Service to the Service Man*




TESTS PICTURE TUBES, TOO! With this BV Adapter, Model 3413-A tests every tube in a TV receiver, including the Picture Tube—without even removing tube from receiver or carton! Saves time!

FOR THE MAN WHO TAKES PRIDE IN HIS WORK

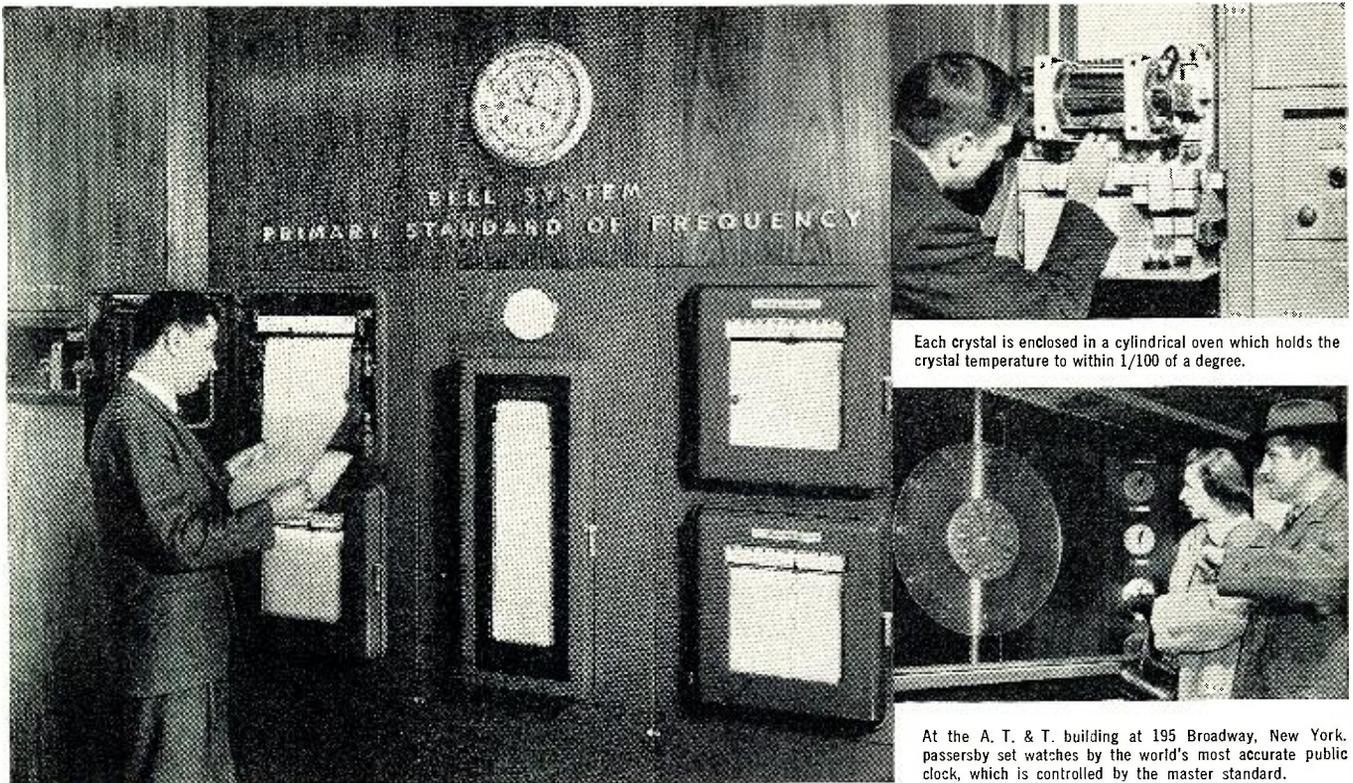**Triplet**


TRIPLETT ELECTRICAL INSTRUMENT CO., BLUFFTON, OHIO, U.S.A.



Each crystal is enclosed in a cylindrical oven which holds the crystal temperature to within 1/100 of a degree.

At the A. T. & T. building at 195 Broadway, New York, passersby set watches by the world's most accurate public clock, which is controlled by the master standard.

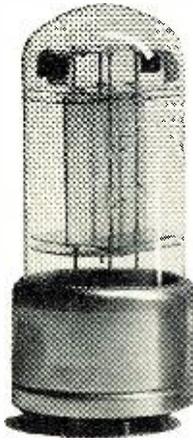↑ Front of the new frequency-time standard at Bell Telephone Laboratories. In the rear there are 600 electron tubes and 25,000 soldered connections. Room temperature is maintained within two degrees.



The controlling quartz crystal vibrates in vacuum at 100,000 cycles per second. The standard is powered by storage batteries, with steam turbo-generator standing by, just in case of emergency.

## A vibrating crystal keeps master time

Ever since Galileo watched a lamp swinging in the Cathedral of Pisa three centuries ago, steady vibration has provided the practical measure of time. In the 1920s Bell Laboratories physicists proved that the quartz crystal oscillators they had developed to control electrical vibration frequency in your telephone system could pace out time more accurately than ever before.

The Laboratories' latest master standard keeps an electric current vibrating at a frequency that varies only one part in a billion, keeping time to one ten-thousandth second a day.

Through secondary standards, a master oscillator governs the carrier


frequencies of the Bell System's ship-to-shore, overseas and mobile radio-telephone services, the coaxial and *Radio-Relay* systems which transmit hundreds of simultaneous conversations, or television. In the northeastern states, it keeps electric clocks on time through check signals supplied to electric light and power companies.

The new standard also provides an independent reference for time measurements made by the U. S. Naval Observatory and the National Bureau of Standards. Thus, world science benefits from a Laboratories development originally aimed at producing more and better telephone service.

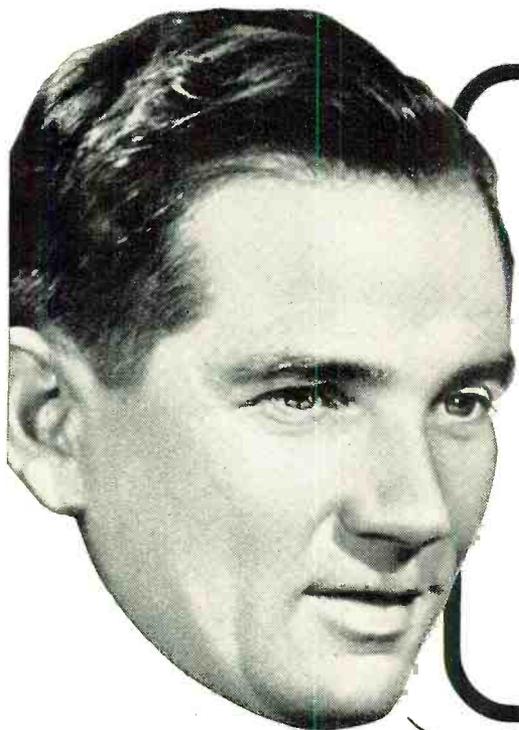
## BELL TELEPHONE LABORATORIES



Improving telephone service for America provides careers for creative men in scientific and technical fields.



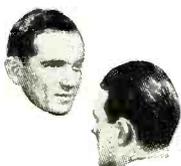*How come you  
sell so many  
picture  
tubes,  
Sam?*



"I'm using the CBS-Hytron Easy Budget Plan, Joe. My CBS-Hytron distributor gave it to me."




"Tell me more."

"Well, CBS-Hytron's Plan helps me sell TV picture tubes and service to many a customer who just doesn't have \$50 cash. My customer now pays for the job painlessly a few dollars a month. Yet I get my cash right away."



"Fine! How does it work, Sam?"

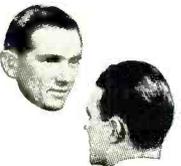"Simple. I introduce my customer to the finance company authorized by CBS-Hytron. The finance company does the rest . . . acts as my credit department . . . arranges all details. My customer gets his tube and I get my cash — at once."



"That's swell, Sam! I've sure been losing sales I shouldn't. I need that CBS-Hytron Easy Budget Plan. CBS-Hytron tubes are tops, too. Thanks for the tip. I'll see my CBS-Hytron distributor today."



**SAVE THE SALE** No need for *you* to miss a single profitable picture-tube sale . . . just because your customer does not have the cash. Get the details on this original CBS-Hytron service for you. See *your* CBS-Hytron jobber . . . or mail this coupon . . . today!



MAIN OFFICE: SALEM, MASSACHUSETTS

HYTRON RADIO & ELECTRONICS CO.  
SALEM, MASSACHUSETTS

Please rush me details on the CBS-Hytron Easy Budget Plan.

NAME.....  
(Please print)

STREET.....

CITY.....STATE.....

# ATR

**AUTO RADIO VIBRATORS**  
*have Ceramic Stack Spacers*



**A COMPLETE LINE OF VIBRATORS . . .**

Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction, featuring Ceramic Stack Spacers for Longer Lasting Life. Backed by more than 20 years of experience in Vibrator Design, Development, and Manufacturing.



"A" Battery Eliminators, DC-AC Inverters  
 Auto Radio Vibrators

*See your jobber or write factory*

**AMERICAN TELEVISION & RADIO CO.**  
*Quality Products Since 1931*  
 SAINT PAUL 1, MINNESOTA-U. S. A.

## Spot Radio News

★ Presenting latest information on the Radio Industry.

By RADIO & TELEVISION NEWS'  
 WASHINGTON EDITOR

**NATIONAL DEFENSE AND ELECTRONICS**, which once again are closely allied in a global program of strategy, production and operation, have begun to dominate all spheres of activity in Washington with the same impact of the '40 to '45 era. The so-called temporary buildings, erected for interim tennacy during the war days, are once more bulging with the staffs of countless defense agencies. Every official building and numerous private and business quarters leased for government business have become the roaring headquarters of hundreds of departments established for the defense effort. Once more, meetings and conferences are highlighted by talks of members of officialdom, with the military playing their usual key role and revealing sharply our present problems and possible solutions.

During one such report covering the state of the Armed-Forces' requirements, Rear Admiral John R. Redman, who was recently named Director of Communications and Electronics on the Joint Chiefs of Staff, told members of the RTMA Transmitter Division that more than ever before industry and the military are partners in an enterprise to provide operational aids that will insure superiority over any potential enemy, on the land, on the sea or in the air. "Some of the military (supply) problems have their roots in the different organizational structure of the three military departments," he added, "as well as the different areas of responsibility of organizational divisions, common civilian-military functions, relationship with our allies in the North Atlantic Treaty Organization, relationship with other friendly nations, impact of the present Korean action and last but not least, the constantly changing world situation."

Noting that one of the major advantages we enjoy today over any potential enemy is our productive capacity, the naval specialist pointed out that this feature can be traced clearly to the standardization gains that have been made in all fields of endeavor.

Describing for the first time just how equipment for the military is transferred from an idea to the battlefields, the Admiral said that the gear usually grows from a statement of a requirement by an operational component of the military. Classified as a statement

of military characteristics, it is passed on to the research and development activities of the military, with action on the requirement monitored by the research and development board. This Group is charged with coordination of all of the *Department of Defense* research and development activities. When the equipment has been developed and must be evaluated, operational personnel of the military appear on the scene again. The evaluation procedure was described as quite different from that practiced in the civilian world where the decision usually centers on one factor, profit or loss. In the military consideration, it was said, the freezing of the development must be evaluated in a less tangible economic fashion. In this instance, the factors to be considered are the number of battles that can be won and the bloodshed that could possibly be avoided.

The industry committee was told, after the equipment is evaluated and found satisfactory by operational personnel of the Armed Forces, procurement actions by the various departments are initiated so that industry can produce. At this point the Munitions Board enters the picture, since it is responsible for the allocation of industrial potential and materials to satisfy production requirements. It was pointed out that the board also serves as the focal point in equipment standardization problems.

Reviewing the personnel serving on the joint communications-electronics committee of the Joint Chiefs of Staff, who correlate the requirements of the Armed Forces, the naval chief said that all the branches of the services are represented: Major General G. I. Back, Chief Signal Officer of the Army; Major General R. C. Maud, Director of Communications of the Air Force, and Captain W. B. Goulett, Director of Naval Communications. Six assistants from the Army, Air Force and Navy complete the staff.

In a summarization of the job to be done, Admiral Redman declared that the military is doing its best to supply clear requirements so that industry can satisfy the wants of the military and take pride in a job well done. He pointed out that industry is developing the state of the art at a rapid pace, developing manufacturing techniques which produce reliable

**RADIO & TELEVISION NEWS**



Let Us Put This Magnificent New 1952

# MIDWEST TELEVISION

CONSOLE With Its MAMMOTH

# 20-Inch

PICTURE TUBE  
IN YOUR HOME ON  
30 DAYS TRIAL




## FACTORY-TO-YOU

You be the judge! See and hear Mammoth-Picture Midwest Television right in your own home for 30 days. If you are not 100% satisfied, any money you have paid will be promptly refunded. Send today for the new 1952 catalog of the finest Midwest line in 32 years.

We Pay Transportation Charges

LOW FACTORY PRICES

### Special Bonus

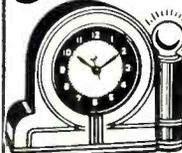


## GIFT!

Illuminated  
TELEVISION CLOCK

Given With Every  
Purchase of a MIDWEST  
RADIO or TELEVISION  
LIMITED TIME ONLY!

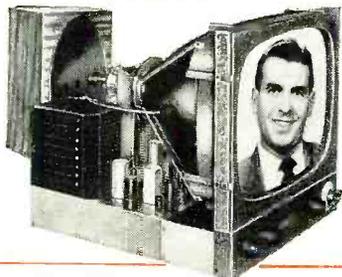MIDWEST 20-Inch  
TELEVISION CHASSIS  
Ready for easy installation in  
your own cabinet.



## EASY TERMS

WRITE or PHONE  
For This NEW 1952

### FREE MIDWEST RADIO CATALOG

If You Live In One of These Cities  
Phone and Ask for Your Catalog

NEW YORK MURRAY Hill 2-6810  
CHICAGO STATE 2-5600  
PITTSBURGH GRANT 1-0609  
CLEVELAND PROSPECT 1-7450  
DETROIT WOODWARD 3-1233  
ST. LOUIS GRAND 1161  
PHILADELPHIA LOCUST 4-1035




or Send Coupon Below

WRITE IN NAME AND ADDRESS (PLEASE  
PRINT) ON COUPON OR 1c POSTCARD

MIDWEST RADIO & TELEVISION CORP.  
Dept. 376, 909 BROADWAY • CINCINNATI 2, OHIO  
Please send me your new FREE 1952 Catalog.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

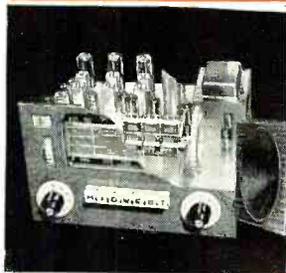Also—Powerful New 1952 World-Ranging  
**MIDWEST Series of RADIOS**  
For Beautiful Consoles and Complete Chassis




An entirely new line of  
radios featuring the  
powerful Series 16 five  
wave band AM-FM  
Radio Chassis and the  
magnificent Symphony  
Grand Radio-Phonograph  
with 3-Speed Automatic  
Intermix Record Player.

*Easy Terms*



**MIDWEST RADIO & TELEVISION CORP.**  
DEPT. 376, 909 BROADWAY, CINCINNATI 2, OHIO

# HERE'S THE "SECRET!"

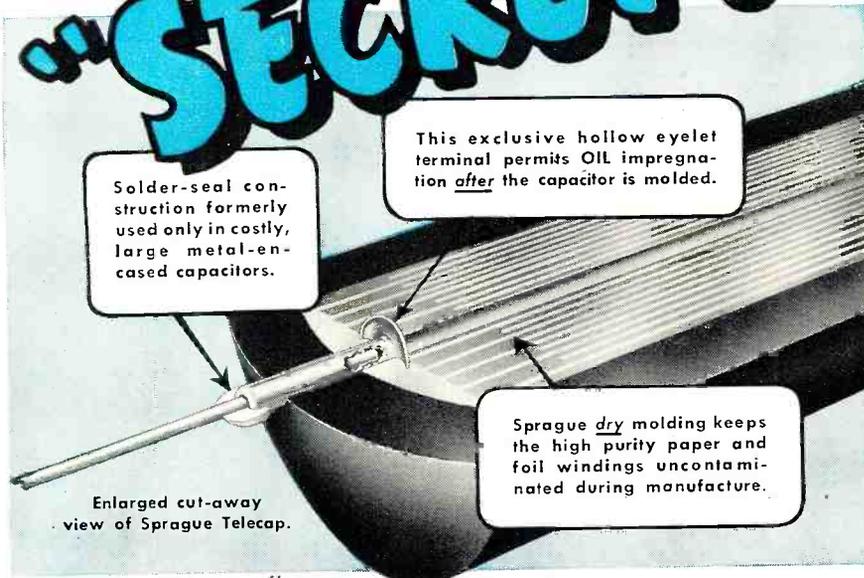

Solder-seal construction formerly used only in costly, large metal-encased capacitors.

This exclusive hollow eyelet terminal permits OIL impregnation after the capacitor is molded.

Sprague dry molding keeps the high purity paper and foil windings uncontaminated during manufacture.

Enlarged cut-away view of Sprague Telecap.

## ..... that makes **SPRAGUE TELECAPS®** outperform and outlast other molded tubulars

Actual, on-the-job performance *proves* the superiority of Sprague "Black Beauties" beyond question. To find the secret that explains just why they're so much better, however, you've got to see inside of a Telecap itself.

The big feature is that every Sprague Telecap is molded into its sturdy Bakelite phenolic shell while its windings are still *dry*. Any chance of contamination by moisture or dust during manufacture is avoided. After molding, the capacitor is vacuum-impregnated with mineral oil through a tiny eyelet. The lead is then inserted, the terminal is solder-sealed—and you have a capacitor that has maximum resistance to heat and moisture... extra high insulation resistance and superior capacitance stability. *In short, a capacitor that brings you premium quality at no extra cost!*

... And that's the secret behind the fact that Sprague Telecaps are more widely used by leading television set makers... and why they're first choice of service technicians who value their reputations for good work!

*Write for "Telecap" Bulletin. It's free!*



**SPRAGUE PRODUCTS CO.**

51 Marshall Street  
NORTH ADAMS MASSACHUSETTS

**BLACK BEAUTY  
TELECAPS®**

TELEVISION'S MOST WIDELY USED  
MOLDED TUBULARS

equipment expeditiously and in quantity... a performance proudly hailed by everyone.

**IN ANOTHER DEFENSE INDUSTRY** meeting, described as one of the most significant of the year, which had been called to review the edict to stop color-set production, the halls of Washington overflowed with the members of the manufacturing, alphabet agency and Armed-Forces world. Among those who appeared were Brig. General David Sarnoff and Frank M. Folsom, board chairman and prexy of *RCA*, respectively; *CBS* President Frank Stanton; Dr. Allen B. DuMont of *DuMont Labs*; Barney Balaban, *Paramount Pictures*; William Balderston, *Philco*; Benjamin Abrams, *Emerson Radio*; Paul V. Galvin, *Motrola*; Dr. W. R. G. Baker and Herbert M. Estes, *G.E.*; Richard A. Graver, *Admiral*; Richard Hodgson, *Chromatic Television Labs*, the *Paramount Picture* unit which announced recently that it would produce a tricolor tube; Arthur Matthews and C. J. Burnside, *Color Television, Inc.*; Lewis Clement, *Crosley*; Fred Gluck, *Fada*; W. A. McDonald, *Hazeltine*; John A. Rankin, *Magnavox*; W. L. Viergever, *John Meck Industries*; Joe Friedman, *Trav-Ler*; H. A. Gumz, *Webster-Chicago* (which had announced that it would produce converters and adapters for Columbia color); Robert S. Alexander, *Wells-Gardner*; F. M. Sloan, *Westinghouse*; R. J. Sherwood and Ernest Kohler, *Hallicrafters*; Louis A. Movins, *Paramount Film Distributing Corp.*; and attorneys Paul Porter (*Paramount*) and William A. Roberts (*DuMont*).

There were varied opinions on the propriety of the defense chieftain's order, but all said that they certainly would comply with the request to halt color chassis making as long as research could continue. Some legislators at the meetings appeared to be quite miffed at the ruling, declaring that the effort to avoid a growing black and white set market, the continuing "incompatible - compatible" argument placed before the FCC, was completely negated and any chance of popular acceptance of the disc system at a remote date was now an impossibility. Particularly caustic in his criticism of the *ODM* ruling was Senator Edwin Johnson, who had pressed for a color decision. He felt that the edict could have been withheld since the material required was trivial. Others believed that Wilson was entirely proper in his request, particularly in view of the need for nearly a quarter of a million fractional horsepower motors, which are not around in any substantial quantities now and which may become scarce as the copper situation becomes more and more critical.

As the color-set lines shut down, the labs continued their round-the-clock studies to evolve an electronic compatible system which might be mar-

*(Continued on page 114)*

**RADIO & TELEVISION NEWS**

**TV TROUBLE SHOOTER**  
Must have production line experience on tuners; good pay.  
Flonbin Wireless Corporation  
63 St John St, Terc Ist St a Ort

**TV SERVICE MAN**—For bench work and outside calls; experienced preferred; paid vacation and company benefits.  
McIntosh-Wood, 11261 21st St  
Hollywood, Calif. 91604

**TELEVISION serviceman**—With car. Must be experienced. Apply before 12.  
3020 W. Irving St

**TELEVISION SERVICE MAN**  
Some experience. Call DAY 1-4100

**TV BENCH MEN**  
needed only, good opportunity for men, small growing concern, salary insurance ability. 1-10 0300.

**TELEVISION & RADIO MAN**  
Expt. AA-1 Radio & Appliance Repair.  
10th MacArthur Driv. N.Y. 10016

**TV JUNIOR ENGINEER**  
Experienced on front end I. F. design. Handy with tools and model making. College or radio institute graduate.  
11110, E1 1100

**RADIO OR TV BENCHMEN**  
PERMANENT! GOOD CONDITIONS  
apply if you have less than three years experience on radio or TV repairs.  
11110, 1110 Broadway at 87 St

**TV-RADIO SERVICEMAN**  
have car, able to make estimates in home. Top man wanted. See TV.  
11110, 1110 Broadway at 87 St

**TV SERVICEMAN**  
Wanted for man with good background.  
Call Ma Roberts BV 8-4177.

**TV-RADIO MECHANIC**  
Wanted. High salary.  
3 Westchester Ave, Yonkers  
N.Y. 10516

**TELEVISION SERVICE, CAR, HIGH**  
Wanted. High salary.  
11110, 1110 Broadway at 87 St


**GRAD, \$1 14 1/2 HR**  
Wanted. High salary.  
11110, 1110 Broadway at 87 St

**TELEVISION SERVICEMAN**  
Wanted. High salary.  
11110, 1110 Broadway at 87 St

**TV SERVICEMAN, experienced.** I radio knowledge preferred. Must be in appearance, willing to co-operate assume responsibility. Good salary. St employment for right person. Local suburban town, 45 minutes from address replies to 3310 times.

**TELEVISION SERVICEMAN**  
Car. Top salary, car allowance; only men with 2 or more yrs exp apply. Also Television Benchman, top pay for expd man. Advancement.  
11110, 1110 Broadway at 87 St

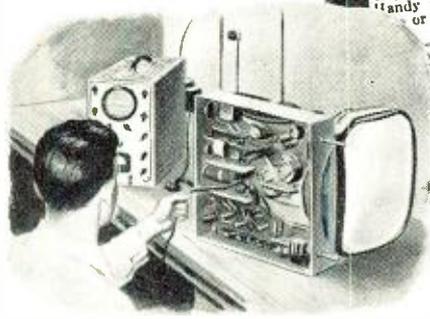**WANTED**  
**2 EXPERIENCED TV INSTALLATION MEN**  
**1 EXPERIENCED OUTSIDE SERVICE MAN**  
APPLY AT



# GOOD JOBS waiting for trained TV servicemen

LOOK AT THE ACTUAL "HELP WANTED" advertisements above. They are typical of the opportunities now open to TV servicemen offering financial security and permanent employment.

**PLENTY OF OPPORTUNITIES—NOW**

As a trained and experienced TV serviceman, you may choose from several good-pay jobs with excellent futures.

Immediate and future employment opportunities cover a wide range. Installation or trouble-shooting of TV receivers in homes . . . bench technician in radio-TV service shops . . . inspector, tester and repairman with manufacturers of TV receivers . . . testing, analyzing and repairing with electronic instrument manufacturers . . . trouble-shooting and repairing with companies with military contracts for electronic equipment. If you prefer, you can be your own boss by

operating a TV service shop of your own. Even in the Armed Forces your qualification as a TV serviceman will open the door for you to win rapid promotion and better pay.

**RCA INSTITUTES HOME STUDY COURSE TRAINS YOU TO QUALIFY**

Men now in the radio-electronics industry as well as radio servicemen, with no experience in TV servicing, here is your golden opportunity to convert your skill to the important money-making field of TV servicing. Don't pass up this chance of a bright and profitable career in TV.

The RCA Institutes Home Study Course gives you a sound knowledge of television fundamentals . . . intensive practical instruction in the proper maintenance and servicing of complex TV receiver circuits . . . teaches you the "short cuts" on TV installation and trouble-shooting, saving you many hours of

on-the-job labor. Learn TV servicing from RCA engineers and experienced instructors—pioneers and leaders in radio, television and electronic developments.

**RCA INSTITUTES HOME STUDY COURSE PLANNED TO YOUR NEEDS**

You keep your present job in radio—television—electronics. In your spare time, you study at home. You learn "How-to-do-it" techniques with "How-it-works" information in easy-to-study lessons prepared in ten units. Cost of RCA Home Study Course in Television Servicing has been cut to a minimum—as a service to the industry. You pay for the course on a "pay-as-you-learn" unit lesson basis. You receive an RCA Institutes certificate upon completion of the course. The RCA Institutes Home Study Course in Television Servicing is approved by leading servicemen's associations.

RCA Institutes conducts a resident school in New York City offering day and evening courses in Radio and TV Servicing, Radio Code and Radio Operating, Radio Broadcasting, Advanced Technology. Write for free catalog on resident courses.

**Send for FREE BOOKLET**

Mail the coupon—today. Get complete information on the RCA INSTITUTES Home Study Course in Television Servicing. Booklet gives you a general outline of the course by units. See how this practical home study course trains you quickly, easily. Mail coupon in envelope or paste on postal card.



**MAIL COUPON NOW!**

RCA INSTITUTES, INC.  
Home Study Department RN-152  
350 West Fourth Street, New York 14, N. Y.

Without obligation on my part, please send me copy of booklet "RCA INSTITUTES Home Study Course in TELEVISION SERVICING." (No salesman will call.)

Name \_\_\_\_\_ (Please Print)  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**RCA INSTITUTES, INC.**  
A SERVICE OF RADIO CORPORATION OF AMERICA  
350 WEST FOURTH STREET, NEW YORK 14, N. Y.

# SYLVANIA NATIONAL ADVERTISING

**5 Stars Endorse  
Your Business in these  
Smashing Magazine  
ads**

**Jane Russell says:**

For the finest radio and television service, I advise my friends to depend on the man who displays the Sylvania sign. Believe me, he's a past master at keeping sets in splendid shape.



It's right, Jane! The man behind this Sylvania sign is a radio and television expert. He can banish radio squeaks, television streaks and make your set like new. Of course, he uses Sylvania Radio and Television Tubes—best made anywhere.

**RADIO TELEVISION SERVICE**  
SYLVANIA RADIO TUBES

**SYLVANIA TUBES**  
RADIO AND TELEVISION PICTURE

Sylvania Electric Products Inc., 1720 Broadway, New York 19, N. Y.

**June Haver says:**

"I've made a wonderful discovery. When I have trouble with my radios or TV set, I simply call the man who displays the Sylvania service sign. He gives me prompt, courteous and competent repair service. Try him and see if you don't agree."



It's right, June! The man behind this Sylvania sign is a radio and television expert. He can banish radio squeaks, television streaks and make your set like new. Of course, he uses Sylvania Radio and Television Tubes—best made anywhere.

**RADIO TELEVISION SERVICE**  
SYLVANIA RADIO TUBES

**SYLVANIA TUBES**  
RADIO AND TELEVISION PICTURE

Sylvania Electric Products Inc., 1720 Broadway, New York 19, N. Y.

**Says Leo Durocher:**

"Lorraine and I don't fool around with just any radio and TV service. We like an expert who knows how to call things right. That's why we call the man who shows the Sylvania sign."



You, too, will appreciate the prompt, dependable service offered by the man who displays this Sylvania sign. He's a trained technician who will spot trouble instantly with Sylvania's precision test equipment and install long-lasting Sylvania Tubes.

**RADIO TELEVISION SERVICE**  
SYLVANIA RADIO TUBES

**SYLVANIA TUBES**  
RADIO AND TELEVISION PICTURE

Sylvania Electric Products Inc., 1720 Broadway, New York 19, N. Y.

**says Ann Blyth**

"I've found a man who knows all the answers—at least to radio and TV troubles. It's the man who displays the Sylvania radio and television service sign. So whether I'm in Hollywood or in New York, I look for this sign for dependable service."



You, too, can enjoy true-to-life radio performance, and keep television reception clear as a polished mirror by calling the expert who displays this Sylvania sign. He uses those extra fine Sylvania Radio and Television Tubes.

**RADIO TELEVISION SERVICE**  
SYLVANIA RADIO TUBES

**SYLVANIA TUBES**  
RADIO AND TELEVISION PICTURE

Sylvania Electric Products Inc., 1720 Broadway, New York 19, N. Y.

**Every one of your prospects** will see and read these appealing ads in famous national magazines. These ads recommend *your* service . . . when you display the Sylvania Service Emblem, shown above. So, make sure these emblems are on your doors, your windows, and trucks. They're FREE from your Sylvania Tube Distributor NOW!

**These ads will appear in the 4 famous magazines your prospects read most**



# Will Sell Your RADIO-TV SERVICE in '52

Nation-wide weekly TV Show "BEAT THE CLOCK" will sell your service to every TV set owner



You're an "expert, reliable service-man who does a tough job well," Bill Shipley, crack CBS-TV announcer, tells your prospects. And, he adds: "Always look for that Sylvania Service Emblem." That's how the hard-hitting, full-minute commercials on Sylvania's CBS-TV show, "Beat the Clock," put Bill Shipley, Roxanne, and Bud Collyer on your sales staff.



Roxanne and Bud Collyer are seen weekly over CBS-TV in 35 cities... selling your service... when you display the Sylvania Service Emblem.



**Make this great national ad campaign pay off in your store**

Mail the coupon below for FREE, full-color folder giving complete details about Sylvania's compelling Spring Service Dealer Advertising Program. It contains everything to identify you unmistakably as the dealer advertised in Sylvania's magazine and TV advertising. If you want more business, you can't afford to miss it. But, time's awastin'... get that coupon in the mail NOW!



# SYLVANIA

RADIO TUBES; TELEVISION PICTURE TUBES; ELECTRONIC PRODUCTS; ELECTRONIC TEST EQUIPMENT; FLUORESCENT TUBES, FIXTURES, SIGN TUBING, WIRING DEVICES; LIGHT BULBS; PHOTOLAMPS; TELEVISION SETS

Sylvania Electric Products Inc.  
Dept. R-2301, Emporium, Pa.


Please send me full details about Sylvania's powerful business-building campaign for Service Dealers.

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**TELEPHONE TYPE RELAYS**

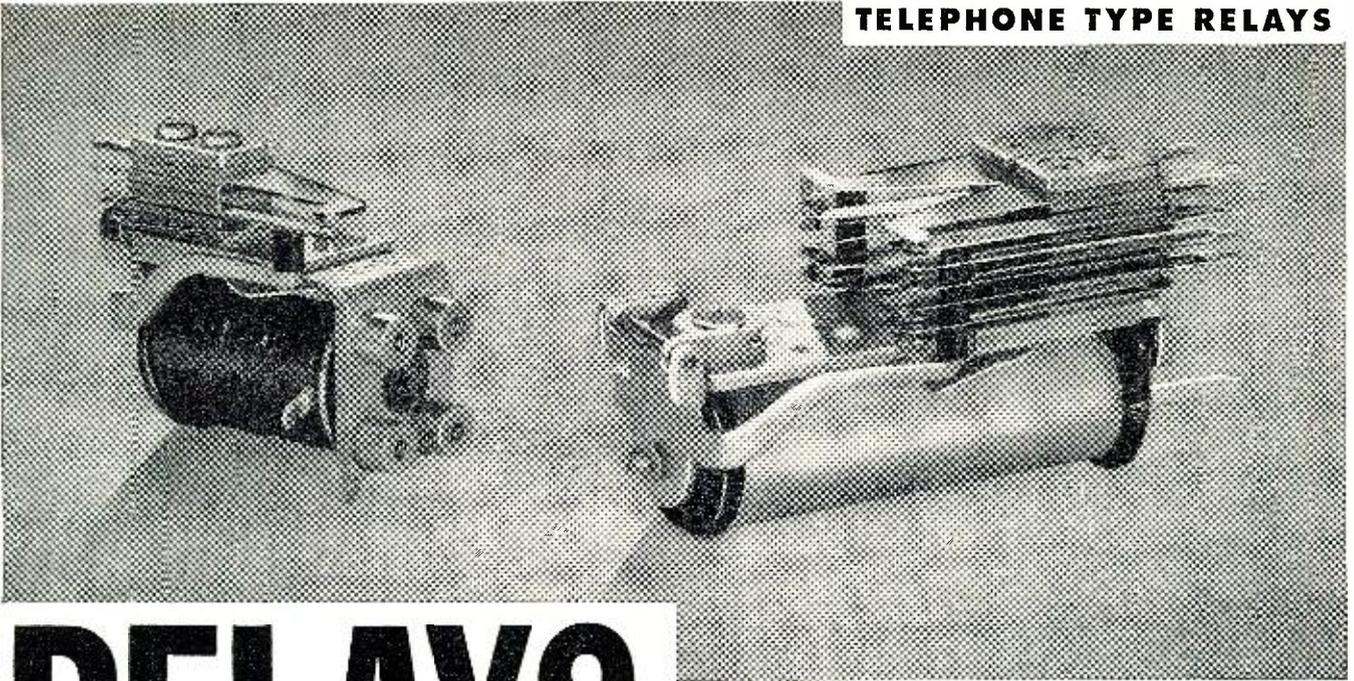

# RELAYS

This list represents only a small part of more than a million relays in our stock—one of the world's largest. All relays are standard, brand new in original packing, and fully guaranteed by Relay Sales. Send us your relay requirements. If the items are in stock we can make immediate delivery at substantial savings in cost to you.

**STANDARD TELEPHONE RELAYS**

STK. NO.	VOLTAGE	OHMAGE	CONTACTS	UNIT PRICE
R-806	115 VAC	900	1A	\$2.05
R-161	6 VDC	10	2B&1A	1.10
R-873	6 VDC	12	3C-3A MICALEX	3.00
R-305	12 VDC	50	2A Split Cerm.	1.35
R-360	24 VDC	200	1C	1.50
R-484	24 VDC	200	2A, 1C	1.35
R-337	24/48 VDC	1200	1A, 2B Split	2.65
R-101	24 VDC	1300	2A	2.50
R-868	30/162 VDC	3300	1C	1.90
R-365	52/162 VDC	3300	4C	3.95
R-518	85/125 VDC	6500	1C	3.60
R-918	52/228 VDC	6500	1C	3.60
R-852	52/228 VDC	6500	1C, 1A	3.00
R-341	75/228 VDC	6500	4C @ 4 Amps	3.65
R-633	180/350 VDC	10,000	1C @ 5 Amps	2.90
R-344	72/300 VDC	11,300	3A, 1B	2.45
R-332	100/350 VDC	40,000	2A	3.50
R-664	110 VAC	...	2B&1A/OCT.SOCKET	2.45
R-667	6 VDC	75	1B/10AMP. 1A/3AMP.	1.45
R-632	6 VDC	12	5A&1C	3.25
R-154	6/12 VDC	200	1A	1.50
R-517	12 VDC	250	2A	1.50
R-116	85 VDC	3000	1B	3.05
R-631	100/125 VDC	3300	2A	1.90
R-545	110/250 VDC	7000	1C	2.40
R-124	300 VDC	12,000	1A	1.55
R-511	24 VDC	200	W/MICRO N.O	3.05
R-160	6 VDC	12	3C&3A	3.00
R-851	52/228 VDC	6500	1C, 1A	3.00
R-691	6 VDC	40	1B&1C	1.35
R-155	12 VDC	100	4A&4B	1.45
R-520	200/300 VDC	14,000	2C	3.45
R-159	6 VDC	50	2A	1.35
R-158	6 VDC	50	4A Cerm.	1.85
R-381	6/8 VDC	100	1A Split	2.50
R-382	6/12 VDC	200	1B Split	2.50
R-153	12 VDC	200	1C&1A	1.55
R-304	12 VDC	200	4A Split Cerm.	2.50
R-383	6/12 VDC	500	1A Split	2.50
R-385	6/12 VDC	500	1B Split	2.50
R-384	6/12 VDC	500	3A Split	3.00
R-576	12 VDC	200	2A	2.50
R-316	24 VDC	200	1C	1.50

**SHORT TELEPHONE RELAYS**

STK. NO.	VOLTAGE	OHMAGE	CONTACTS	UNIT PRICE
R-635	12 VDC	100	1C&1B	\$1.35
R-308	12 VDC	100	2C @ 4 Amps	1.85
R-343	12 VDC	100	1C	2.00
R-826	12 VDC	150	2C, 1B	1.55
R-770	24 VDC	150	1A/10 Amps	1.45
R-368	8/12 VDC	200	1B	1.40
R-771	24 VDC	200	1A/10 Amps	1.45
R-603	18/24 VDC	400	2A	1.55
R-575	24 VDC	500	2C	2.40
R-764	48 VDC	1000	1C&2A	2.00
R-417	5.5 ma	5800	2C	2.50
R-563	60/120 VDC	7500	1A	2/3.10
R-213	5/8 VAC 60 Cy.	...	2A	2.50
R-801	115 VAC	...	NONE	1.45
R-589	12 VDC	125	2A	1.30
R-113	12 VDC	150	4A	1.55
R-689	12/24 VDC	255	1C	1.55
R-799	24 VDC	500	NONE	1.00
R-115	24 VDC	500	1C	1.70
R-110	24/32 VDC	3500	1C	2/3.45
R-121	150 VDC	5000	2A&1C	2.05
R-122	150 VDC	5000	2C/Octal Base	2.50
R-634	150/250 VDC	6000	1A&1B	2.45
R-369	8/12 VDC	150	2A, 2B	1.60
R-908	6 VDC	15	4A @ 4 Amps	1.50
R-800	12 VDC	150	2C&1A	1.55
R-537	12/24 VDC	150	2C&1B	2.00
R-750	24 VDC	400	1A	1.60
R-367	10/16 VDC	195	2C	2.50
R-335	20/30 VDC	700	2A, 1C	2.00
R-366	30/120 VDC	4850	1C	2.50

**OTHER RELAY TYPES IN STOCK**

- Keying Relays
- Rotary Relays
- Contactors
- Midget Relays
- Voltage Regulators
- Differential Relays
- Sealed Relays
- Special Relays


Telephone

**Seeley 8-4146**

**Manufacturers and Distributors:**  
Write for the new Relay Sales Catalog.

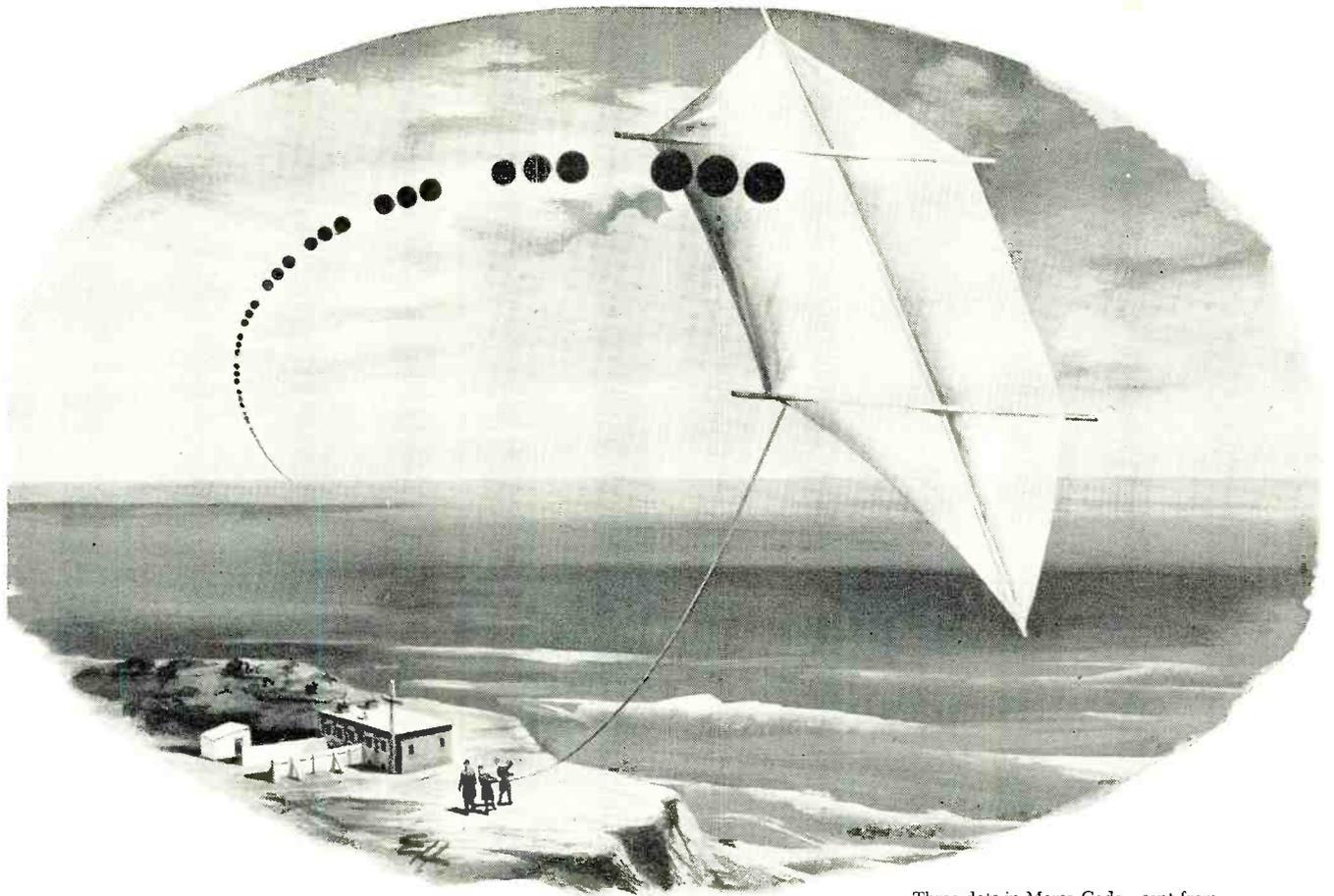**833 W. CHICAGO AVE., DEPT. R-5, CHICAGO 22, ILL.**





Three dots in Morse Code—sent from England and received by Marconi in Newfoundland—proved that wireless signals could span the Atlantic.

# Three dots that opened a new era!

When Marconi, on December 12, 1901, heard a “3-dot” radio signal—the letter “S” in Morse Code—across 1,800 miles of sea, it was an experimental triumph that opened a new era in communications.

Before this historic event, wireless telegraphy had been limited primarily to communications between the shore and ships at sea. Marconi’s success, however, was the forerunner of many other developments which led eventually to RCA world-wide radiotelegraph service that now operates more than 80 direct circuits to 66 countries.


As radio progressed, its usefulness was ex-

panded by invention and development of the electron tube, the harnessing of short waves which made world-wide transmission a reality, and the automatic transmission and reception of messages at high speed.

Radio, with its magic of spoken words and music broadcast over the world . . . television, the miracle of pictures in motion transmitted through the air . . . these mediums of modern communication have added notable links in the chain of electronic advances first forged in 1901 from the mere sound of three dots.

\* \* \*

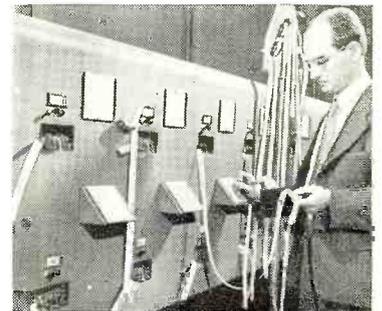See the latest wonders in radio, television, and electronics at RCA Exhibition Hall, 36 West 49th St., N. Y. Admission is free. Radio Corporation of America, RCA Building, Radio City, N. Y. 20, N. Y.



Today RCA Communications sends and receives about 81 million words each year across the Atlantic; the messages are automatically recorded on tape, for error-free transmission.



**RADIO CORPORATION of AMERICA**

*World Leader in Radio — First in Television*

# PRICES Slashed

**OUR \$50,000 STOCK OF RECONDITIONED, "GOOD-AS-NEW" EQUIPMENT MUST GO AT A RECORD-BREAKING SACRIFICE TO MAKE ROOM FOR NEW MERCHANDISE!**

**SAVE UP TO 50% during GIGANTIC CLEARANCE SALE of USED TEST and COMMUNICATION EQUIPMENT**

Only the popularity of our "Surprise" Trade-In Allowance policy enables us to offer these wanted, late-model units at unheard-of low prices.

All equipment thoroughly checked and guaranteed to be in normal operating condition when shipped. While the following is only a partial list of our huge inventory (available at the time this publication goes to press) bargains like these simply can't last! So act now and avoid disappointment. Wire, write, phone or use the handy coupon today! When ordering, indicate first, second and third choice. All merchandise subject to prior sale.



COLLINS 75A-1



NATIONAL HRO-50



HICKOK 505 Test Instrument

**USED COMMUNICATION EQUIPMENT**

COLLINS 75A1 RECEIVER AND SPEAKER .....	\$275.00
HALLICRAFTERS HT18 VFO.....	89.50
HALLICRAFTERS S38B RECEIVER	42.50
HALLICRAFTERS SX42 RECEIVER LESS SPEAKER.....	225.00
HALLICRAFTERS SX43 RECEIVER LESS SPEAKER.....	134.50
HALLICRAFTERS SX71 RECEIVER LESS SPEAKER.....	159.50
NATIONAL HRO5TA1 with Power Supply, less Speaker and 4 Coils	175.00
NATIONAL HRO-50 RECEIVER WITH SPEAKER AND 4 COILS.....	289.50
NATIONAL NC183 RECEIVER AND SPEAKER .....	209.50
RME HF10-20 CONVERTER.....	59.00
SONAR XE10 FM EXCITER.....	14.95

## FREE!

Complete list of used test and communication equipment bargains. Thoroughly checked and tested. Many of them are late

model units. All are offered at sacrifice prices. Send for your free list today.

All Prices

F. O. B. St. Louis

Phone CHestnut 1125

### USED TEST EQUIPMENT

PRECISION EV10 VTVM.....	\$ 49.50
RCA RIDER CHANALYST.....	89.50
HICKOK 305 3" OSCILLOSCOPE..	89.50
HICKOK 505 5" OSCILLOSCOPE..	139.50
RCA 155 3" OSCILLOSCOPE.....	47.50

Walter Ashe Radio Co. R-52-1  
1125 Pine St., St. Louis 1, Missouri

Rush my order for Used Equipment as follows:  
(1st choice) .....  
(2nd choice) .....  
(3rd choice) .....


Remittance for \$..... is enclosed.  
 Send FREE List of Additional Used Equipment Bargains.

Name .....

Address .....


City..... Zone..... State.....



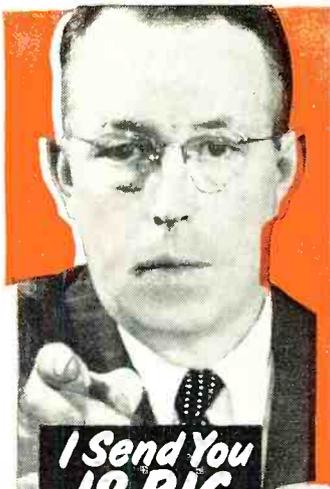
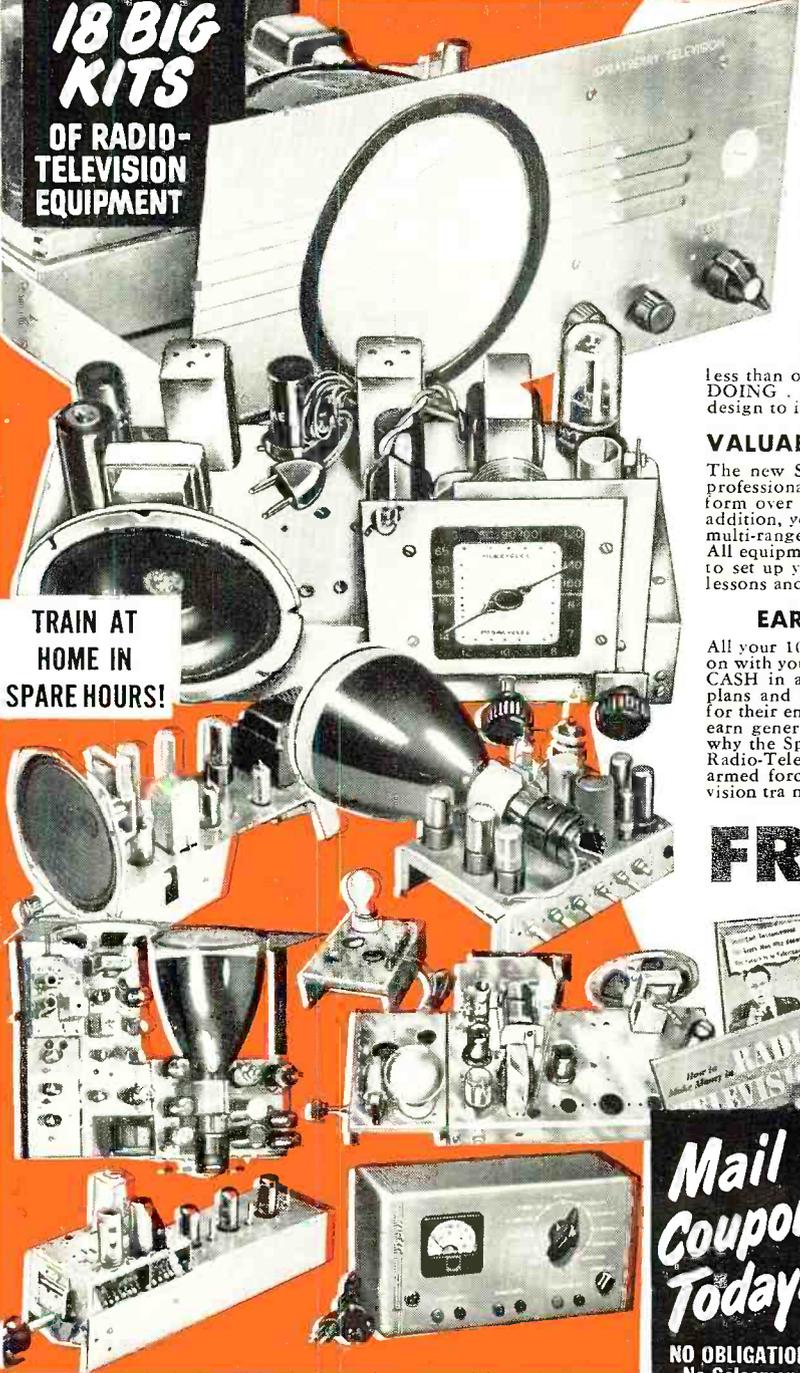
# NOW—Be a Fully Trained, Qualified RADIO TELEVISION TECHNICIAN IN JUST 10 MONTHS OR LESS

**I Send You  
18 BIG  
KITS  
OF RADIO-  
TELEVISION  
EQUIPMENT**



**TRAIN AT  
HOME IN  
SPARE HOURS!**

**New "Package" Unit Training Plan  
PAY AS YOU LEARN—YOU SET THE PACE!**

**No Monthly Payment Contract to Sign!**

Now . . . be ready for Radio-Television's big pay opportunities in a few short MONTHS! Frank L. Sprayberry's completely new "Package" training unit plan prepares you in just 10 MONTHS . . . or even less! Equally important, there is NO MONTHLY payment contract to sign . . . thus NO RISK to you! This is America's finest, most complete, practical training—gets you ready to handle any practical job in the booming Radio-Television industry. In just 10 months you may start your own profitable Radio-Television shop . . . or accept a good paying job in this fascinating expanding field at work you've always wanted to do. Mr. Sprayberry has trained hundreds of successful Radio-Television technicians—and stands ready to train you in less than one year, even if you have no previous experience. You learn by DOING—actually working with your hands with equipment of special design to illustrate basic theory instead of relying on books alone.

**VALUABLE EQUIPMENT INCLUDED WITH TRAINING**

The new Sprayberry "package" plan includes many big kits of genuine, professional Radio-Television equipment. While training you actually perform over 300 demonstrations, experiments and construction projects. In addition, you build a powerful 6-tube standard and short wave radio set, a multi-range test meter, a signal generator, signal tracer, many other projects. All equipment is yours to keep . . . you have practically everything you need to set up your own service shop. The interesting Sprayberry book-bound lessons and other training materials . . . all are yours to keep.

**EARN EXTRA MONEY WHILE YOU LEARN!**

All your 10 months of training is AT YOUR HOME in spare hours. Keep on with your present job and income while learning . . . and earn EXTRA CASH in addition. With each training "package" unit, you receive extra plans and ideas for spare time Radio-Television jobs. Many students pay for their entire training this way. You get priceless practical experience and earn generous service fees from grateful customers. Just one more reason why the Sprayberry new 10 MONTH-OR-LESS training plan is the best Radio-Television training in America today. If you expect to be in the armed forces later, there is no better preparation than good Radio-Television training.

**FREE 3 BIG RADIO TELEVISION BOOKS**

I want you to have ALL the facts about my new 10-MONTH Radio-Television Training—without cost! Act now! Rush the coupon for my three big Radio-Television books: "How to Make Money in Radio-Television," PLUS my new illustrated Television Bulletin PLUS an actual sample Sprayberry Lesson—all FREE with my compliments. No obligation and no salesman will call on you. Send the coupon in an envelope or paste on back of post card. I will rush all three books at once!

**SPRAYBERRY ACADEMY OF RADIO**  
Dept. 25-E, 111 North Canal St., Chicago 6, Ill.

**Mail  
Coupon  
Today!**  
NO OBLIGATION  
No Salesman  
Will Call

**SPRAYBERRY ACADEMY OF RADIO, Dept. 25-E  
111 North Canal St., Chicago 6, Ill.**

Please rush to me all information on your 10-MONTH Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me.

Name..... Age.....

Address.....

City..... Zone..... State.....

Please check Below About Your Experience

Are You Experienced?  No Experience

**IF YOU ARE EXPERIENCED IN RADIO** Men already in Radio who seek a short intensive 100% TELEVISION Training with FULL EQUIPMENT INCLUDED are invited to check and mail the coupon at the right.

# new!



ACTUAL SIZE

## PYRAMID

TINY TYPE 85LPT

### TUBULAR PAPER CAPACITORS

Fit anywhere!

Suitable for  
85°C. operation!

CAPACITANCE RANGE:  
.0001 TO .5 MFD.

VOLTAGE RANGE:  
200 TO 600 V., INCLUSIVE

Sturdily built in phenolic-impregnated tubes. Ends are plastic-sealed.

WRITE FOR COMPLETE LITERATURE  
Representatives and Distributors  
Throughout the U.S.A. and Canada



## PYRAMID

### PYRAMID ELECTRIC COMPANY

1445 Hudson Boulevard

North Bergen, N. J., U. S. A.

TELEGRAMS: WUX North Bergen, N. J.  
CABLE ADDRESS: Pyramidusa

# Within the INDUSTRY

**ROBERT T. PENNOYER**, manager of the *General Electric Company's* Buffalo Tube Works, has been appointed manager of the newly-established tube department advanced manufacturing section in Schenectady.



He will be succeeded at Buffalo by Harry R. Hemmings of Syracuse who has been purchasing supervisor for cathode-ray tubes at the *G-E* Electronics Park plant.

The new advanced manufacturing section will be devoted to the improvement and development of tube manufacturing processes.

Mr. Pennoyer, who holds a B.S. in electrical engineering and a master's degree, joined *G-E* in 1933.

\* \* \*

**W. F. E. LONG** of Washington, D. C., has been named director of statistics for the Radio-Television Manufacturers Association.

Mr. Long who took office in November of last year is in complete charge of all of the Association's statistical activities, most of which have been handled previously by *Haskins & Sells* of Philadelphia.

He resigned as director of the statistical division of the National Paint, Varnish and Lacquer Association to take this new post.

\* \* \*

**DR. LAN JEN CHU**, internationally-known physicist, has been named director of research for *The Gabriel Company* of Cleveland. Two divisions of the parent firm are active in the radio and television field, *The Ward Products Division* and *The Workshop Associates Division*.



Dr. Chu is a graduate of Chiao Tung University in Shanghai where he received his B.S. degree in Electrical Power in 1934, and his M.S. degree in 1935. In 1938 he received his doctorate in electrical engineering at M.I.T. Before joining the staff of the Radiation Laboratory of M.I.T. in 1942, Dr. Chu was consultant on electromagnetic problems to the Radiation Laboratory and Radio Research Laboratory.

\* \* \*

**GENERAL ELECTRIC COMPANY'S** Electronics Division has announced plans to use two buildings and part of a third at Bridgeport, Conn. for the design and manufacture of military

electronics equipment. Approximately 150,000 square feet of floor area will be turned over to the new operation . . .

**PAUL ROSENBERG ASSOCIATES**, consulting physicist firm, has moved to new and larger quarters at 100 Stevens Avenue in Mount Vernon, New York . . . **ELECTRONIC ENGINEERING COMPANY OF CALIFORNIA** is now occupying its new two-story building at 176 S. Alvarado Street, Los Angeles. The new quarters provide enlarged engineering offices and laboratory facilities . . . **ASTRON CORPORATION**, manufacturers of condensers and r.f. interference filters, has acquired additional space at 255 Grant Avenue in East Newark, N. J. to handle the increased demand for its products.

\* \* \*

**GEORGE W. HENYAN**, manager of *General Electric Company's* industrial and



transmitting tube operations for the past three years, has accepted a temporary appointment as chief of the components branch of the National Production Authority's electronics division.

A veteran of 33 years with *G-E*, he will make his headquarters in Washington, D. C. He joined the company in 1916 after receiving his degree in electrical engineering from the University of Texas and has been with the company continuously except from 1917 to 1919 when he served with the armed forces.

\* \* \*

**WESTINGHOUSE AIR BRAKE COMPANY** has acquired all of the capital stock of **MELPAR, INC.** of Alexandria, Va. and Cambridge, Mass. The new subsidiary will continue in the field of research and development on radio and electronic equipment. . . Alfred W. Russell has announced the formation of **RUSSELL REINFORCED PLASTICS CORPORATION** to manufacture low pressure laminates and flat board stock of Fiberglas-polyester construction. The company's main office is at Hicksville, N. Y. . . **MAGNO RECORDING STUDIOS** is the corporate name of a new firm established to provide facilities for personal transcriptions and commercial recordings on tape and discs. Studios have been set up at 37 W. 57th Street in New York City. A. J. Dash heads the new organization . . . The formation of **AUDICRAFT INC.** has been announced by Alan Abrahams, president. The Brooklyn firm, located at 77 South 5th Street, is manufacturing horn loudspeakers

**RADIO & TELEVISION NEWS**

# PRESENTING **COLLINS** AM-FM "PRE-FAB" TUNERS

**NOW** you can  
build a Collins  
AM-FM tuner from  
the Pre-Fab units  
shown below!

**COMPLETE VERSATILITY** is the byword in this new tuner design. Through the addition of the AM circuit, the Collins tuner will meet all requirements for home music systems and installations where a fine tuner is required.


**ECONOMY:** The very finest in tuner design is offered you at exceptionally low prices. Collins quality is your assurance of a fine product that will work to your complete satisfaction. You cannot duplicate this tuner in its completed form at *twice the price!*

**3 Ways to purchase  
COLLINS Tuner . . .**


1. As an AM tuner kit
2. As an FM tuner kit
3. As an AM-FM tuner kit




FM Tuning Unit **\$15.25**

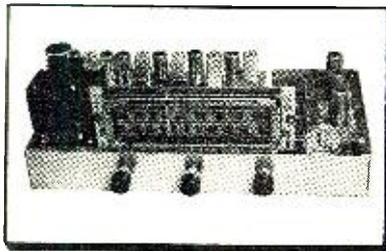

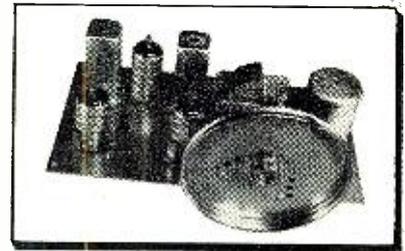
The Collins FM-AM Pre-Fab Tuner Assembled  
(Total Kit Cost **\$69.00**)



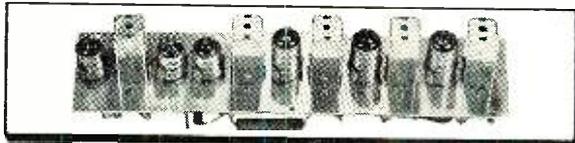AM Tuning Unit  
(Includes IF and Audio Amplifier) **\$19.25**



FM IF Amplifier **\$19.75**

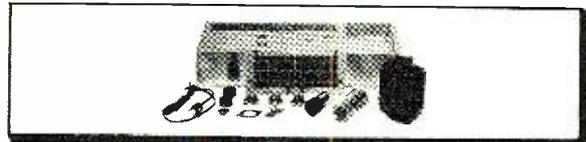

UC-2 Universal Chassis Kit **\$14.75**

Tuning Eye Kit Available At **\$2.85**

The FM tuning unit employs 6J6 RF amp., 6AG5 converter, and 6C4 oscillator. Permeability tuned, stable, and drift-free. The IF amplifier for FM uses 6BA6, (4) 6AU6, and 6AL5 discriminator high gain, wide band for high fidelity reception. Distortion less than 1/2%. Frequency response 20 to 20,000 cycles at detector output.

The AM tuning unit employs three tubes, one of which performs the function of both detector and first audio amplifier stage. AM IF amplifier also is included in the tuning unit. Tubes used: 6BE6, 6BA6, and 6AT6.

Tuner kit is supplied with AM/FM selector switch, volume control and AC switch, and tuning knob. Complete instruction manual with schematics and pictures included.

**MAIL ORDER COUPON  
TODAY!**

TO: COLLINS AUDIO PRODUCTS CO. INC.  
P.O. Box 368, Westfield, N.J.

Enclosed Find  Check  Money Order For

AM Tuning Unit

FM Tuning Unit

FM IF Amplifier

UC-2 Chassis Kit


M-1 Tuning Eye Kit

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

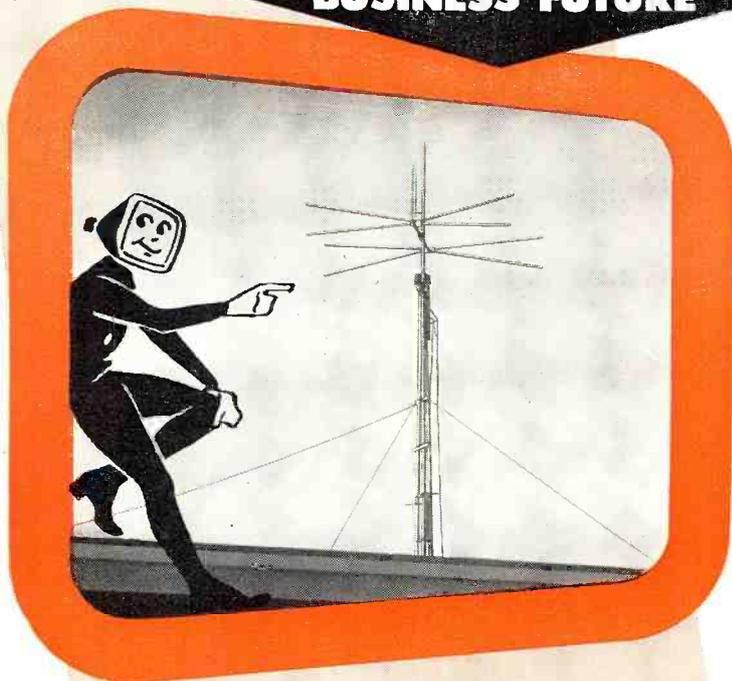Gives a  
**CLEARER PICTURE**  
 of Your  
**BUSINESS FUTURE**



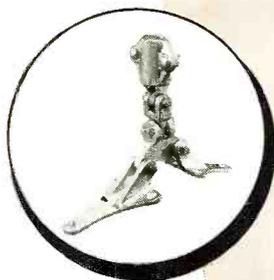**PRODUCT DEVELOPMENT ENGINEERING**  
 by **PENN Teletower**



**POLE BASE MOUNT-PBM5.** Construction permits mounting on peak of ridge so erection can be made from either ridge or side.

To know what tomorrow's developments in tower engineering and merchandising may be . . . keep posted on what's happening today at Teletower! Almost since T-V came out of the laboratories and into the living rooms, Teletower has been first with the important product developments. The Teletower itself . . . the improved T-X section . . . the adjustable roof mount . . . the built in base . . . these were simply forecasts of even bigger "firsts" to come.

Stay tuned in with Teletower! Watch this publication for our advertising . . . the advertising of the tower that tops all others in sales.

CANADIAN REPRESENTATIVE: Atlas Radio Corp., Ltd., 560 King Street, W. Toronto, Canada.

**PENN** Teletowers  
 Triftowers  
 Penna-Mast  
 Hardware

**PENN BOILER & BURNER MFG. CORP., LANCASTER, PA.**

. . . The **CROSLY DIVISION** has purchased the physical assets of **BRAND AND MILLEN, LIMITED**, a radio and television manufacturing firm of Long Branch, Ontario. The Canadian firm will be operated as a wholly-owned subsidiary.

\* \* \*

**H. LAWRENCE KUNZ** has been named general manager of the Capacitor Division of *Sangamo Electric Company*.



He has been with the company 25 years, having joined the organization after receiving his degree in electrical engineering from the University of Illinois.


He has served as sales manager of the division he now heads for the past six years and prior to that was assistant general sales manager.

Mr. Kunz will make his headquarters at the division plant in Marion, Illinois.

\* \* \*

**FREDERIC J. ROBINSON** has been named director of the international sales division of *Sylvania Electric Products Inc.* He has been the company's sales manager for Latin America since 1943 . . . **KEETON ARNETT** has joined the *Allen B. Du Mont Laboratories, Inc.* as general assistant to the president . . . The new sales manager for *Transmitter Equipment Manufacturing Company, Inc.* is **WALTER B. BROWN**, a former colonel in the Signal Corps . . . *Triad Transformer Manufacturing Co.* of Los Angeles has named **ERNEST CLOVER** to the post of director of jobber sales . . . **W. D. RENNER** is the new manager of sales engineering for *Howard W. Sams & Co.* He has been with the firm since its inception . . . *Pickering & Company* of Oceanside, Long Island has announced the appointment of **GEORGE P. PETETIN, JR.** to the post of assistant sales manager . . . **JOHN B. PATTERSON** is the new national advertising manager for *Federated Purchaser, Inc.* of New York. He was formerly with *Telrex, Inc.* . . . **FRANK B. ROGERS, JR.** has joined *Reeves Soundcraft Corp.* as vice-president in charge of sales . . . *Westinghouse Electric Corporation* has named **JAMES L. BROWN** sales manager for receiving tubes and cathode-ray tubes. He has been with the company for 14 years . . . **CHARLES ROBERTS** is the newly appointed advertising and sales promotion manager of *Fada Radio & Electric Co., Inc.* . . . The newly-created post of manager of the radio sales section for the *Crosley Division* is being filled by **HERBERT F. KOETHER** . . . **WILLIAM CARLIN** is the new manufacturing manager of the Cathode-Ray Tube Division of *Allen B. Du Mont Laboratories, Inc.* . . . **PAUL ECKSTEIN**, sales manager of *Hallcrafters*, has resigned to establish his own electronic manufacturers' sales representative. (Continued on page 109)

**RADIO & TELEVISION NEWS**

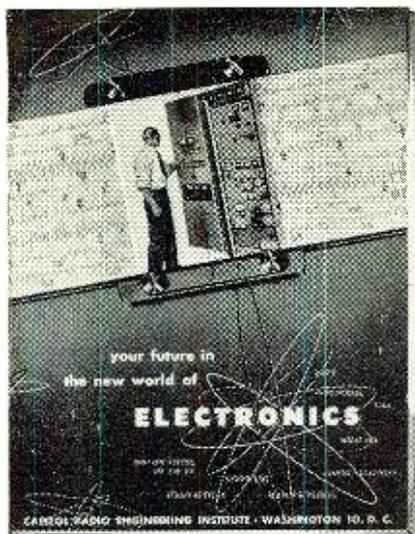

*How far ahead can you be  
next year . . .*

## IN TV AND ELECTRONICS?

◀ **Send for this free CREI booklet today...  
and find out!**

▶ **THIS BOOKLET** can mean the difference between small, w-i-d-e-l-y s-p-a-c-e-d salary increases—and rapid advancement. Between routine work—and challenging opportunity. Between constantly defending your job against better-trained men—and dynamic confidence. Between short-circuited hopes—and high-powered ambition.

An exciting new world has opened up with such super-speed that even the most optimistic electronic experts fall short in their predictions of expansion.

Think of the 1,500 TV stations within the next 5 years and the 2,500 stations within 10 years, as predicted by the Chairman of the FCC. Think of the 13,000,000 TV sets now in use. *Remember that we weren't supposed to reach that figure until 1954.* Think of the 100,000,000 radios in current operation. (95% of the nation's homes have one or more sets.) Think of the tremendous defense orders now being placed for electronic equipment and installations.

Think of the thousands of radio-equipped fire and police departments throughout the U.S. Of the many radio-equipped railroads, of the hundreds of cities with 2-way radio service for cars and cabs. Think of the wide-ranging field of aviation communications—radio-controlled aircraft, navigation-and-traffic control, airport stations.

Think of the maritime world with its navigational aids, fathometers, ship-to-shore and ship-to-ship communications and radar. Think of electronic heating, fax and ultra-fax, of electronic medicine, and all the other applications of electronic know-how.

Countless positions must be filled—in development, research, design, production, testing and inspection, manufacture, broadcasting, telecasting and servicing. Who will get those positions? You—if you prepare today—if you are alert and have the ambition to advance your knowledge. You—if you take 2 minutes to send for a free copy of "Your Future in the New World of Electronics."

This helpful book shows you how CREI Home Study leads the way to greater earnings through the inviting opportunities described above.

However, being an accredited technical school, CREI does not promise you a "bed-of-roses." You have to translate your willingness to learn into saleable technical

knowledge—via *study*. Since its founding in 1927, CREI has provided thousands of professional radiomen with technical educations. During World War II, CREI trained thousands for the Armed Services. Leading firms choose CREI courses for group training in electronics at company expense, among them United Air Lines, Canadian Broadcasting Corporation, Trans Canada Airlines, Sears Roebuck & Co., Bendix Products Division, All-American Cables and Radio, Inc., and RCA-Victor Division.

CREI courses are prepared by recognized experts, in a practical, easily-understood manner. You get the benefit of time-tested materials, under the personal supervision of a CREI Staff Instructor. This complete training is the reason why CREI graduates find their diplomas keys-to-success in Radio, TV and Electronics. CREI alumni hold top positions in America's leading firms.

At your service is the CREI Placement Bureau, which finds positions for students and graduates. Although CREI does not guarantee jobs, requests for personnel currently exceed supply by far.

Talk to men in the field and check up on CREI's high standing in electronics instruction. Determine for yourself right now that your earnings are going to rise with your knowledge—and that you get your rightful place in the Age of Electronics. All this CREI can promise you, provided you sincerely want to learn. Fill out the coupon and mail it today. We'll promptly send you your free copy of "Your Future in the New World of Electronics." The rest—the future—is up to you.

### MAIL COUPON FOR FREE BOOKLET

#### CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 111D, 16th & Park Rd., N.W., Washington 10, D. C.

Send booklet "Your Future in the New World of Electronics" and course outline.

CHECK  TV, FM & Advanced AM Servicing  Aeronautical Radio  
FIELD OF  Practical Television Engineering  Engineering  
GREATEST  Broadcast Radio Engineering (AM, FM, TV)  
INTEREST  Practical Radio Engineering

Name .....

Street .....


City ..... Zone ..... State .....

If residence school in Wash., D. C., preferred, check here

**EICO**  
TEST INSTRUMENTS

*Guard*

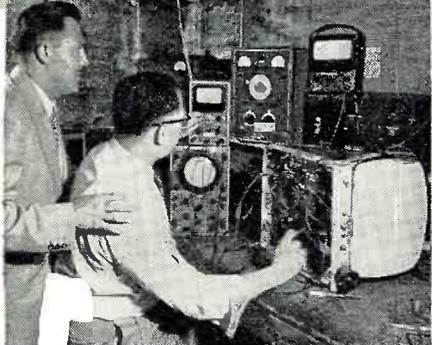*CBS-Columbia Inc.*  
HIGH STANDARDS OF  
TELEVISION PRODUCTION QUALITY



In the CBS-Columbia design laboratories, Al Goldberg takes some important readings with the EICO Model 221 Vacuum Tube Voltmeter and Model 555 Multimeter, as Harry R. Ashley looks on.



Mr. Al Goldberg, Assistant Chief Engineer of CBS-Columbia, and Harry R. Ashley, President of EICO, inspecting the use of the EICO Model 221 Vacuum Tube Voltmeter and Model HVP-1 High Voltage Probe at the Sweep Frequency Troubleshooting Position on the CBS-Columbia Television production lines.

**KITS**  
WIRED INSTRUMENTS



**NEW** 555K MULTIMETER  
KIT \$29.95 WIRED \$34.95  
20,000 ohms/volt



320K SIG. GEN. KIT \$19.95. WIRED \$29.95

**NEW** 322K SIG. GEN. KIT \$23.95. WIRED \$34.95



**NEW** 950K R-C BRIDGE & R-C COMP. KIT \$19.95  
WIRED \$29.95



**NEW** 1040K BATTERY ELIM. KIT \$25.95. WIRED \$34.95



511K VOM KIT \$14.95  
WIRED \$17.95



**NEW** 526K MULTI-METER KIT \$13.90  
WIRED \$16.90  
1000 ohms/volt



**NEW** 1171K RES. DECADE BOX KIT \$19.95  
WIRED \$24.95




**NEW** 315K DELUXE SIG. GEN. KIT \$39.95  
WIRED \$59.95



145K SIG. TRACER KIT \$19.95  
WIRED \$28.95



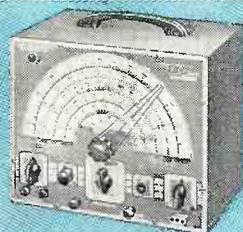**NEW** 625K TUBE TESTER KIT \$34.95  
WIRED \$49.95



360K SWEEP GEN. KIT \$34.95  
WIRED \$49.95

*For Laboratory Precision at Lowest Cost—  
the Leaders Look to EICO!*

**WHY**

does CBS-Columbia, Inc., another one of America's leading TV manufacturers, use EICO Test Instruments on both its production lines and in its design laboratories?

**BECAUSE**

— like Emerson, Tele-King, Tele-Tone, Majestic, and many another famous TV manufacturer coast to coast, CBS-Columbia knows that . . .

*Only EICO Test Equipment  
delivers All 10 EICO nomical Features!*

1. Laboratory Precision
2. Lowest Cost
3. Lifetime Dependability
4. Speedy Operation
5. Rugged Construction
6. Quality Components
7. Latest Engineering
8. Super-Simplified Assembly and Use Instructions
9. Laboratory-Styled Appearance
10. Exclusive EICO Make-Good Guarantee

Before You buy any higher-priced equipment, be sure You look at the EICO line—in Wired as well as Kit form! Each EICO product is jam-packed with unbelievable value. YOU be the judge—compare, see EICO instruments today—in stock at your local jobber—and SAVE! Write NOW for FREE newest Catalog 1-R.


**FOLLOW THE LEADERS . . . INSIST ON EICO!**



**NEW** 221K VTVM KIT \$25.95  
WIRED \$49.95



HIGH VOLTAGE PROBE \$6.95

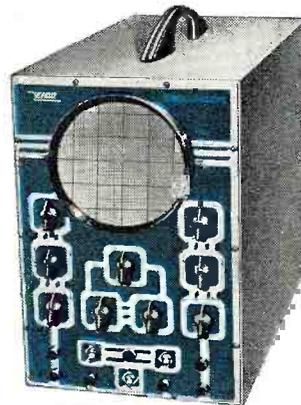

**NEW** 425K 5" PUSH-PULL SCOPE KIT \$44.95. WIRED \$79.95

**EICO**

ELECTRONIC INSTRUMENT CO., Inc.  
276 NEWPORT STREET, BROOKLYN 12, NEW YORK

©1951, Electronic Instrument Co., Inc.  
Prices 5% higher on West Coast. Due to unstable conditions, prices and specifications are subject to change without notice.


# Radio On The MAIN LINE

By  
**LEO G. SANDS**

General Sales Manager  
Boque Electric Mfg. Co.



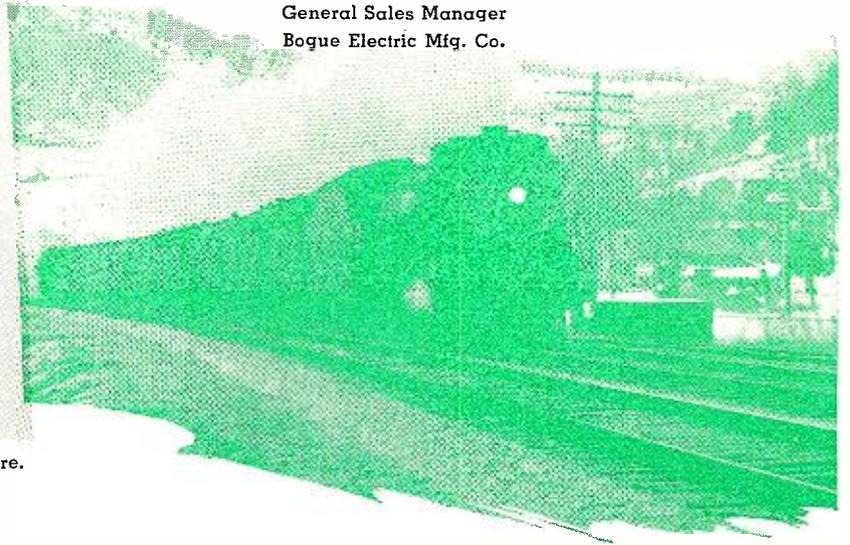Control base station at B & O Ore Dock, Baltimore.



**Licenses to operate two-way radio systems have been issued to 96 railroads in the U.S. Approximately 8½ million dollars have been invested in such equipment.**

LICENSES have been issued covering the use of radio communications equipment on 5253 railroad locomotives, cabooses, and other rolling stock, at 365 yard or terminal base stations and wayside stations as of July 5, 1951 according to the Federal Communications Commission. This represents an investment of approximately \$8,500,000 in equipment and appurtenances.

Of the nation's 131 class 1 roads, 52 are using two-way radio. The other 44 railroads using radio are terminal companies or short lines not listed in the category of class 1 railroads. The total number of railroad companies of all classifications in the United States is 1070. There are 476 line haul operating railroad companies and 213 operating switching and terminal railroad companies in the United States exclusive of the 131 class 1 roads.

The first permanent authorization to be granted to a railroad on a regular basis in the railroad radio service was to the *Denver & Rio Grande Western* on February 27, 1946. The *Baltimore & Ohio* received authority on August 15, 1946 to operate on a regular basis its radio communications system which


had been authorized on an experimental basis on August 20, 1945 for operation at its yards near New Castle, Pennsylvania. Several other grants on a regular basis were issued soon after, some covering installations already in service on an experimental basis. The *Rock Island Line* was the first railroad to receive an experimental authorization to test two-way radio in rail operations on the 152 to 162 mcgacycle band. This permit was applied for on April 20, 1944 and was granted on February 26, 1945. At this stage of the railroad art, it had not yet been settled in the minds of all concerned that the 152 to 162 mcgacycle band was the most desirable part of the radio spectrum for railroad radio. The *Rock Island Line* conducted tests on frequencies as high as 2600 megacycles. Many tests using the 152-162 mcgacycle band were made by several railroads in conjunction with equipment manufacturers who were interested in getting into this new field.

The engineers of the *Bendix Radio Division of Bendix Aviation Corporation* with an extensive background of wartime v.h.f. experience were among the advocates of the 152-162 mcgacycle

band. Using the famous SCR-522 which *Bendix* engineers designed for American military production, tests were conducted on several railroads in all parts of the country and under a multitude of conditions to prove that v.h.f. radio was a practical means of providing communications with moving trains and switch engines.

The SCR-522, an amplitude modulated airborne radio transmitter and receiver unit, was designed to operate on frequencies between 100 and 156 megacycles. It was possible to coax it to operate on 156.525 megacycles without modification. This frequency was made available by the FCC for railroad radio tests. Although designed to withstand the vibration and shock encountered in fighter planes, the SCR-522 would not stand up under the very different kind of shock and vibration to which it was subjected in railroad service.

The SCR-522, however, should be given credit for speeding the advent of the widespread use of radio by the railroads because it provided an immediate source of equipment operable at the desired frequencies. Based on the original SCR-522 design, present day railroad radio equipment has come through several stages. The equipment of today is less expensive and more compact than the early railroad radio equipment of 1945 and 1946. This early equipment is by no means obsolete today. Almost every piece of railroad

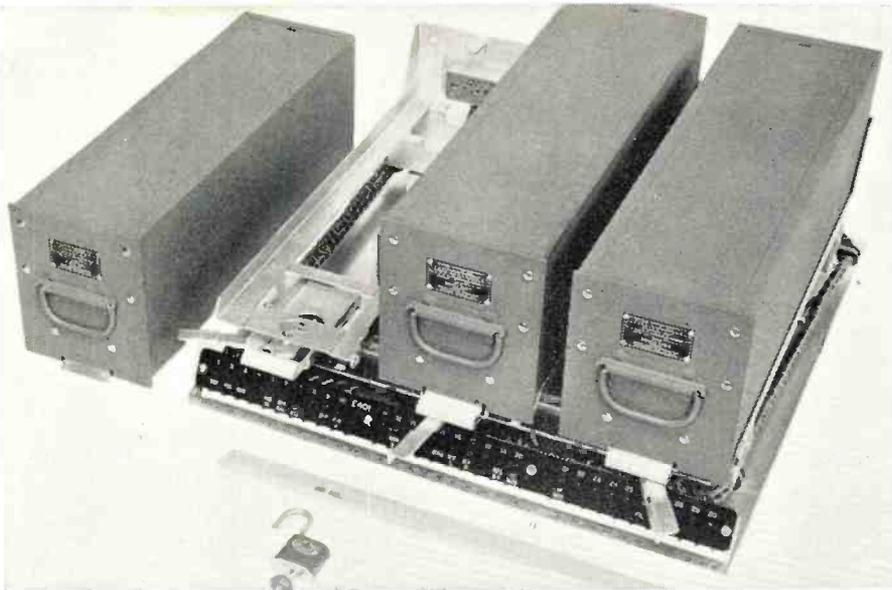

Bendix Type MRT-8 railroad radio unit. Transmitter, receiver, and power supply are shock mounted and may be locked in place to prevent unauthorized operation.

Up-to-date list of American railroads that are authorized to use two-way radio.

Alabama Great Southern	Delaware, Lackawanna & Western	New York, Chicago & St. Louis
Alton & Southern	Denver & Rio Grande Western	New York, New Haven & Hartford
Apache	Des Moines & Central Iowa	Niagara Junction
Atchison, Topeka & Santa Fe	Detroit, Toledo & Ironton	North Louisiana & Gulf
Atlantic Coast Line	Duluth, Mesabi & Iron Range	Northern Pacific
Baltimore & Ohio	Elgin, Joliet & Eastern	Pacific Electric
Baltimore & Ohio, Chicago Terminal	Erie	Pennsylvania
Bangor & Aroostock	Fort Worth & Denver City	Pittsburgh & Ohio Valley
Barre & Chelsea	Florida East Coast	Richmond, Fredericksburg & Potomac
Bessemer & Lake Erie	Georgia Northern	River Terminal
Birmingham Southern	Grand Trunk Western	St. Louis-San Francisco
Boston & Maine	Great Northern	St. Louis-San Francisco & Texas
Brooklyn Eastern Dist. Terminal	Green Bay & Western	Seaboard Air Line
Carbon County	Gulf, Mobile & Ohio	South Buffalo
Central of Georgia	Illinois Central	Southern Pacific
Central Railroad of New Jersey	Jacksonville Terminal Co.	Southern
Central Railroad of Pennsylvania	Kansas-Oklahoma & Gulf Lake Terminal	Stellton & Highspire
Chattahoochee Valley	Lehigh Valley	Texas & Pacific
Chesapeake & Ohio	Los Angeles Junction	Texas & New Orleans
Chesapeake-Western	Louisville & Nashville	Texas & Northern
Chicago & Eastern Illinois	Louisiana & North West	Texas City Terminal
Chicago & North Western	Maryland & Pennsylvania	Toledo Terminal
Chicago, Burlington & Quincy	McKeesport Connecting	Union Pacific
Chicago Great Western	Minnesota, Dakota & Western	Union (Pittsburgh)
Chicago, Milwaukee, St. Paul & Pacific	Missouri - Kansas - Texas of Texas	Walla Walla Valley
Chicago, Rock Island & Pacific	Missouri Pacific	Washington & Old Dominion
Chicago, South Shore & South Bend	Modesto & Empire Traction	Western Maryland
Columbus & Greenville	Monessen Southwestern	Western Pacific
Colorado & Southern	Monongahela Connecting	West Virginia Northern
	New Orleans Terminal Co.	Point Comfort & Northern Railway
	New York Central	

radio equipment that has been sold is in regular use today.

Going back to the very beginning, radio was used to communicate with moving trains in 1914 by the *Delaware, Lackawanna & Western Railroad*. Many tests on frequencies high and low had been conducted through the years, but it was not until 1945 that radio was given serious consideration by the railroads. Before 1945, the lack of suitable equipment and the state of the art prevented concrete action.

Now that radio communication has proved itself to be a valuable working tool, the rate at which railroads are installing radio is at an all-time high. The mere fact that equipment and frequencies were available was not enough to create immediate wide scale adoption of radio by the railroads. Many problems had to be overcome which involved operating rules and procedures, cooperation by labor, maintenance, primary electrical power, conversion from steam to diesel motive power, availability of versatile skilled maintainers, and the skepticism of a great number of men who had done the same thing the same way for the last fifty years.

The men who maintain railroad radio equipment fall into many categories depending on the size and vitality of the railroad. On some roads, the radio technician must be an expert on telephone carrier equipment, teleprinters, and other communication devices associated with wire lines. On the *Santa Fe*, radio is handled by a highly skilled group specializing in electronics.

Maintaining radio equipment on a major railroad is not as easy as taking care of equipment for a police department or taxicab operator where all mobile units return to a base every day. On a railroad 2000 miles long, a locomotive with a radio unit requiring attention can be 2000 miles from the maintenance shop. This problem is being met by storing serviceable radio units at major points along the way so they may be interchanged enroute. Some roads maintain one service center, others several, shipping defective

A main line fireman talks to crew in caboose a mile behind.



Engineer on a diesel switch engine keeps in touch by radio.



units to service centers for repair. A planned preventive maintenance program helps reduce the number of equipment failures and cuts down the need for field service calls.

No accurate figures were found available on the number of persons engaged in maintaining railroad radio. It is hard to estimate the number because so few handle radio maintenance exclusively.

The Communications Section of the Association of American Railroads plays a major role in coordinating the assignment of frequencies and in the preparation of equipment performance standards. Representatives of the railroads who make up committee #4 of the A. A. R. Communications Section, prepare specifications to be used by manufacturers as a guide in designing equipment for railroad service and by the railroads to assist them in planning their radio facilities.

At first, the railroads installed radio at yard offices and on switching locomotives to expedite the movement of freight through yards and terminals. The savings effected by the use of radio could be more readily measured in this type of operation.

On the main line, the advantages of radio communication from engine to caboose seemed obvious, because the

conductor and engineer, who are often separated by a train a mile long, normally cannot communicate with each other. With radio, the conductor can advise the engineer when to "high ball" after clearing a section of slow track and he can order the engineer to apply the brakes from the front end when necessary. Before radio, the brakes were often applied from the rear end when an emergency arose with the result that the train was often torn in two.

The economic advantages of radio for end-to-end communication have been measured and are attractive. However, the electric power source on the caboose was a source of major expense, much more than the cost of the radio equipment.

The normal approach would be the installation of a standard 32-volt train battery and an axle driven generator. Some railroads have installed butane or diesel engine driven generators to provide power. However, more machinery meant additional maintenance cost.


A more practical and less expensive solution was the installation of a 12-volt truck battery on the caboose which is kept charged by an axle or wheel driven generator or alternator-rectifier. This particular method has been

adopted by many of the railroads with considerable success.


Heretofore, moving trains were out of touch with the outside world except for the limited one-way transmission of intelligence through the signal system. At certain points, written messages could be exchanged by train crews and wayside operators.

Several railroads are equipping waystations and trains with radio which will permit instantaneous contact with train crews. The *Chicago, South Shore & South Bend Railroad* was one of the first to equip its entire line with point-to-train radio communications facilities. The *Erie* has installed radio from Chicago to Jersey City, the *Baltimore & Ohio* from Fairmont, West Virginia to Connellsville, Pennsylvania and the short line *Washington & Old Dominion* along its entire, right-of-way. The *Northern Pacific* is installing a main line train radio system extending across North Dakota to Montana which will permit waystation operators as well as the dispatcher, when necessary, to talk directly with train crews. The *Milwaukee Road* is installing point-to-train radio in South Dakota. News like this is getting common in the railroad trade journals. Radio has found its place on the main line.

-30-

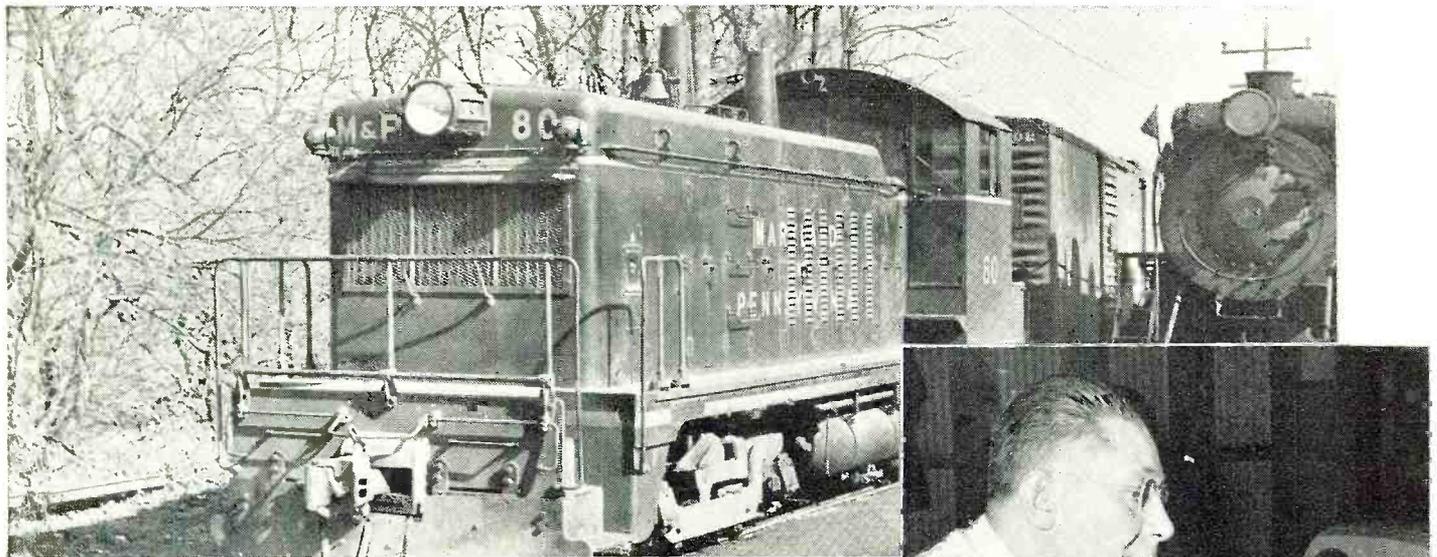

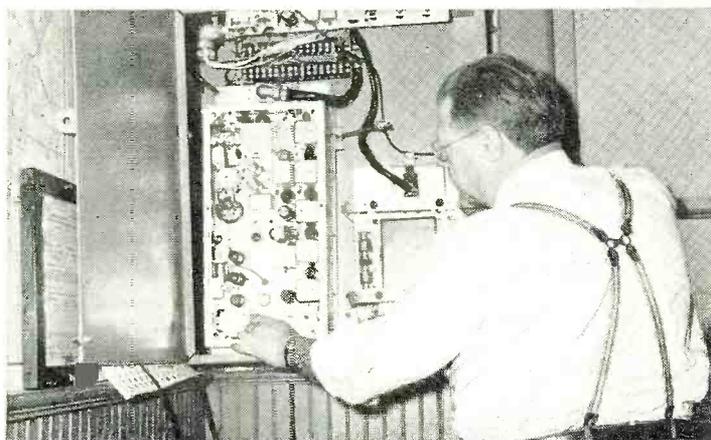A radio-equipped locomotive operated by the Maryland & Pennsylvania R. R.



A yardmaster directs train crews by means of radio, thus keeping trains and freight moving without delays.


Lee Kemberlin checks the base station equipment at the Toledo Terminal Railroad office. Similar installations throughout the country help speed important freight shipments.

# SUCCESSFUL SERVICING OF AUTOMOBILE RECEIVERS

By  
**I. J. SALTZMAN**  
Globe Radio & Sound Service

**N**OST radio technicians shy away from auto radio service because of their reluctance to get their hands dirty. Auto radio servicing is not white collar work but it is profitable. It has many advantages over television servicing and/or home radio servicing. Briefly, the greatest advantage to the auto radio technician is that the customer must drive his car to the radio shop, so the radio technician can use his time for radio servicing and not spend half of it traveling around from one service call to another. The technician can spend almost all of his time at his shop, do more repairs at lower rates, and end up making more money. Even when a job doesn't turn out 100%, the technician is protected to a great extent. True, the job must be done over again on a no-charge basis, but at least he does not have to travel out to the customer's house. Also, the customer is less apt to complain about imaginary troubles for he must use some of his free time to bring his car to the shop. As a result, you can safely say most auto radio complaints are true complaints, unlike television servicing where the customer only has to lift his telephone to call the TV technician to spend an hour of his time for some pseudo-reason. Unlike service shops handling home radio work, a successful auto radio shop must maintain a large parts inventory, a comprehensive accessory inventory, and must give faster service.

Many of the service troubles found in auto radios, such as the replacement of tubes or a vibrator, are quick repair jobs. Where this can be accomplished in the car, without removing the radio, a flat charge of two dollars plus parts is made. However, where the radio must be removed from the car and taken into the shop for repairs, an additional charge is made to cover the cost of removing the radio from the car, checking the radio on the bench, and re-installing it in the car. The charge will depend on how difficult a radio it is to remove and re-install. After the radio is checked on the serv-

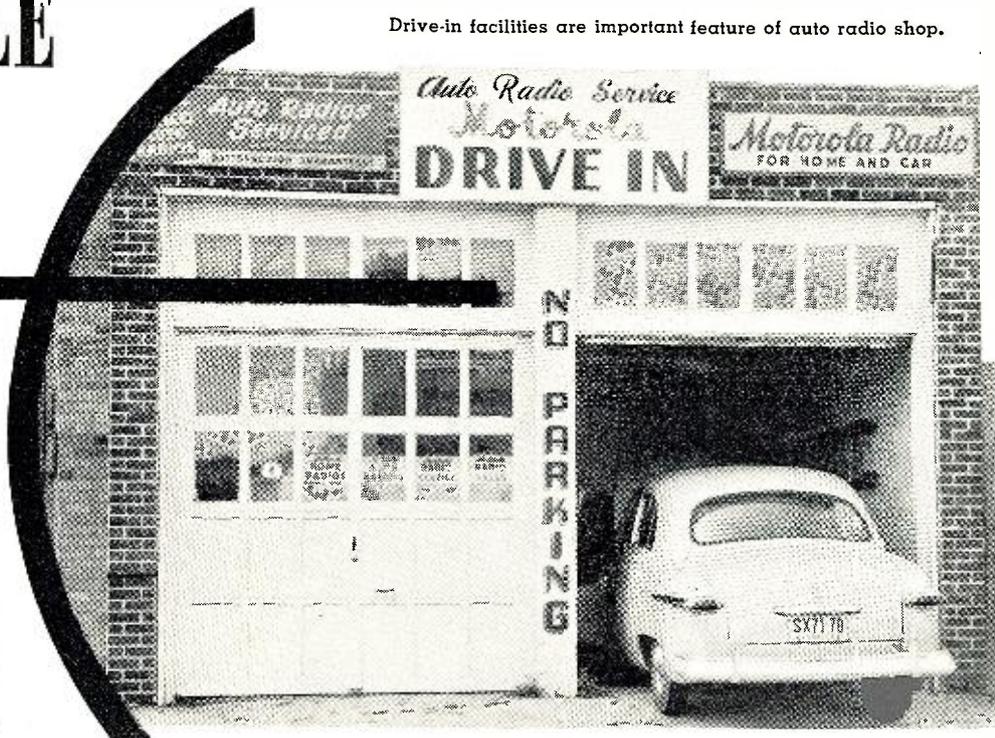

***There is money to be made in car radio work—all it takes is the know-how and a few special tools.***

ice bench, the customer is informed as to the nature of the repairs that have to be made, and the total cost of the job. If he agrees, all is well and good. If he decides not to have the job done, the radio is re-installed in the car and he pays only the price agreed upon to cover the cost of removing, testing, and re-installing his radio. It is only on rare occasions that he does not have the repairs done.

### **Quick Service Expected**

To be a successful auto radio technician, you must very frequently complete the job while the customer waits around. (While the customer is waiting around, somebody in our organization takes this opportunity to show him what we have for sale besides our services.) It is important to have a technician available when a customer calls at the shop. "The man is out to lunch" or "The man is out on a job and will be right back" does not satisfy the customer.

There are many customers who come around during their lunch hours or while driving past the shop and do not have much time to spend. This does not present any problem. To satisfy these customers, it is only necessary to remove the cover from the radio and replace a tube or vibrator or remove the radio from the car and take it into the shop for repair. The customer can usually drive away in less than fifteen minutes and call the shop later in the

day for an estimate of the necessary repairs to his radio if it was necessary to remove it from the car. In a similar manner, he need spend only a short time at the shop while his radio is being re-installed.

We never charge for replacing a burned out fuse, for you know full well that there must have been a good reason for the fuse burning out and it is apt to happen again until the source of the overload is found and corrected. We explain this to the customer and inform him that if the fuse blows again, it will be necessary to check the radio. Once we replace the fuse at no charge, the next job on the radio is ours, and we can then trace down the overload at the customer's expense.

For auto radio work, you must have the correct physical size of parts as well as the correct electrical specs. Physical size is very important since auto radios are built quite compactly. Probably one of the greatest headaches is volume controls, which vary in size and shape with almost every car radio. Stocking the exact replacement parts is an expensive item. While having the exact parts on hand makes it possible to do a better job in less time, it must also be remembered that such parts, because of their very nature, cannot be used in but one or two models and so create quite an inventory problem. It becomes necessary to stock one or two pieces each of a great number of special parts. Parts for each manu-

**RADIO & TELEVISION NEWS**

facturer's radios must be ordered from another distributor as no one distributor can represent all the different automobile and radio manufacturers. Many of these parts will lay in the parts bins and never be used, but this is one of the hidden expenditures in auto radio servicing. However, it is because of this stock of special parts that people come to the shop to have their auto radios repaired.

Years ago, different manufacturers used different vibrators. Today, one or two types of vibrators will satisfy 90% of your needs. Volume controls and speakers are another matter. Each manufacturer has a different size bushing or shaft and most of them are dual controls. There is only one solution—stock the original part, bought directly from the manufacturer—universal controls are only a slight help.

We must stock antennas of various shapes and sizes to fit every car on the road. We do not stock cheap antennas for once one is installed on the customer's car, it is always before his eyes and as soon as it shows signs of rust or poor service, he automatically thinks of us. We do not try to compete with some of the chain auto accessory stores on cheap auto antennas. We sell something they can't sell—good service and better parts.

Regard the customer's car as you would his living room. Don't sit in his car with a screwdriver in your hip pocket for it is very likely to puncture the upholstery on the seat. Cover the seat with a seat cover or blanket. When working on the motor side of the firewall, cover the fender with a blanket. A perfect radio repair job cannot assure your customer satisfaction if you scratch his fender or in some other way do some slight damage to his car. Carbon tetrachloride is a most valuable chemical around any service shop, but it is even more valuable for removing spots from the customer's upholstery which somehow or other just were not there before the technician repaired the radio. We have a cardinal rule that the service technician must not smoke in the customer's car. Upholstery and slip covers burn easily.

### Promoting Auto Service

Sources of business are varied. The car manufacturers will enter into agreements with service stations to repair, during the warranty period, auto radios sold through car dealers. They have a flat rate—\$2.00 for minor repairs and \$3.50 for major repairs. It is only necessary to write the manufacturer and list your qualifications and, after an inspection, you can be listed as an authorized service station. Used car dealers have to recondition and repair radios in cars before they sell the cars. New car dealers repair "out of warranty" radios for their customers as an accommodation. Some manufacturers expect the car dealer to maintain his own radios. Used car dealers are expected to deliver a car with a working radio. After the cus-

tomers has taken delivery, the car dealer sends the customer with a purchase order to our store—we repair the radio and bill the dealer.

The average family car is your biggest source of business—but special sources, such as police cars, ambulances, trucks, and reporters' cars will be tapped too by a wide-awake organization.

It is advisable to have drive-in facilities for the installation and repair of radios. There is a great deal of business done during rainy and inclement weather when men who are unable to work at their ordinary trades—such as those in building trades, out-of-door workers, concessionaires, etc.—find this time ideal to have their auto radios repaired.

### Proper Tools

The days of removing and installing an auto radio with a pair of pliers are over. In order to do speedy and efficient work, it is necessary to have the proper tools. A trip through an auto parts store will show you the various wrenches with ratchets and deep sockets, and with these it is possible to get into the most inaccessible places with ease. We use a special  $\frac{1}{4}$ " ratchet wrench to remove P.K. screws and in that way are able to replace tubes and vibrators in auto radios without removing the set from the car.

Our work bench has one 6 volt battery outlet. We also have built-in PM speakers and special lugs and fittings to adapt our speakers to the various plug and jack arrangements the different manufacturers use. We do not use a stock battery eliminator because we find that this device picks up r.f. signals from the a.c. line and the set will operate better on the bench than in the car. We use regular auto antennas mounted on the work bench. You must be sure, however, to adjust the antenna trimmer after the set is installed in the car. We also use pilot lights, in series with speakers, to prevent voice coil burnout when the speaker is incorrectly plugged into the radio field coil outlet.

The extraordinary "signal-seeking" push-button sets that came out this



An extensive inventory of repair parts is a "must" for the auto radio service shop.


year are very tricky, but reading the manufacturer's service manual will help in locating and repairing the trouble. They are different and unusual, but not impossible.

We have been in this business for over twenty years. We started when it was necessary to remove the roof upholstery and use screen wire as an aerial under the roof fabric of the car. Then we graduated to aerials under running boards, which is also a thing of the past. All cars now use cowl aerials or antennas through the roof. We have a set of *Greenlee* punches of various diameters and we cut a hole to mount the aerial without drilling and reaming and filing—another example of the importance of the correct tools in auto radio service. Some car manufacturers and auto aerial manufacturers supply templates to show just what spot to install the aerial so that it will clear everything underneath and stand up straight. We file these away and use them when the occasion demands, although with the new swivel top and "eight-ball" aerials they can be adjusted to almost any contour of automobile.

Auto radios require more frequent service than home radios. The reason for this is that the tubes and com-



*(Continued on page 85)*

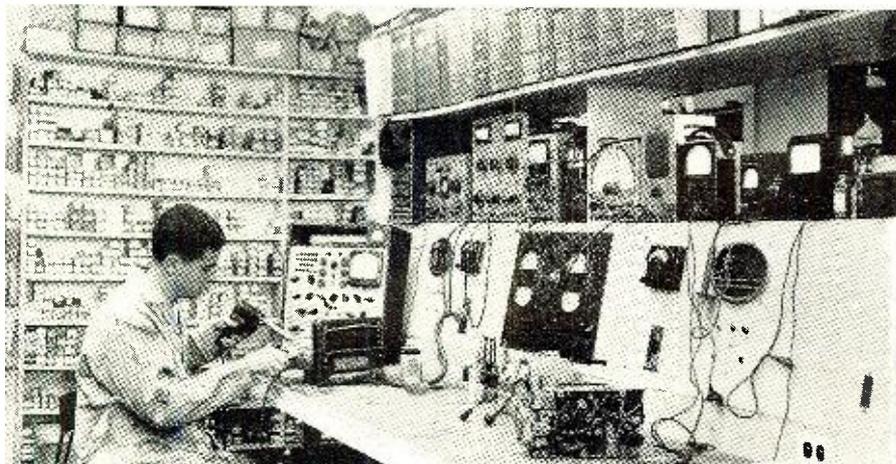Complete and accessible test equipment is important in speeding up auto radio work.



# A PHASED TV BEAM ANTENNA

By  
**T. A. PREWITT**

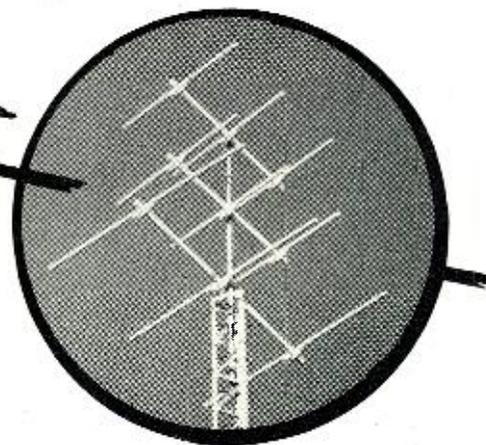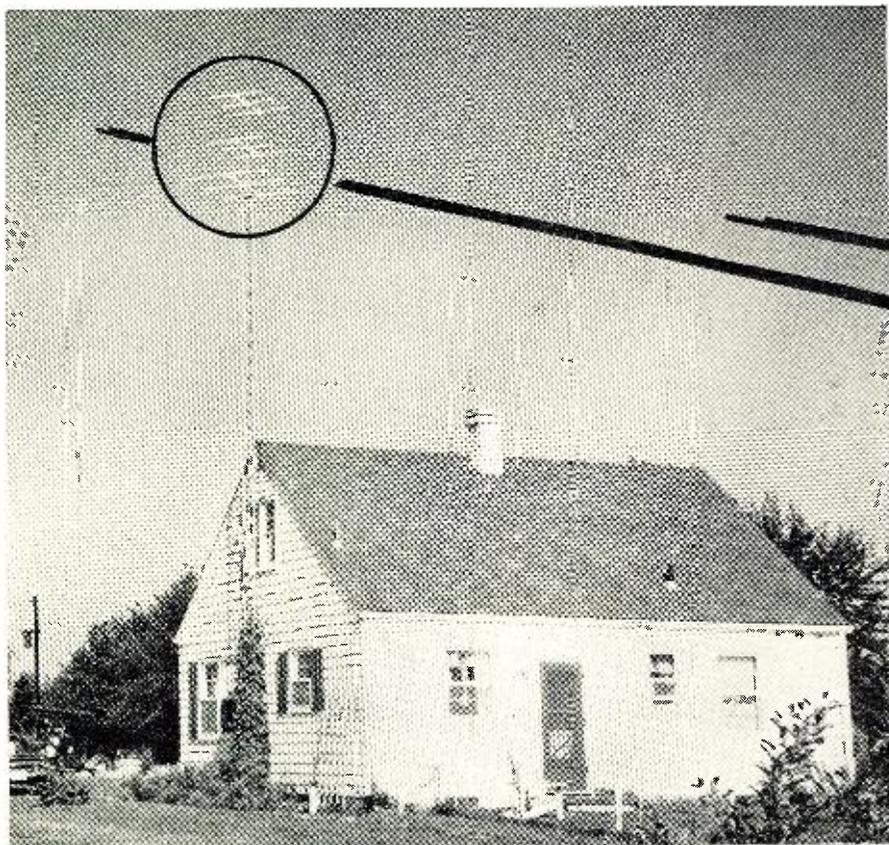

Close-up view of the phased TV beam built and installed by the author.

The two-bay 144 megacycle antenna as installed atop the single-bay FM antenna in use at the author's house.

**Can be built to include all TV channels, the entire FM band, and the 2 meter amateur band. Provides good TV reception within radius of 40 miles from station.**

THE antenna shown in the accompanying photographs owes its existence to the present-day shortage of aluminum tubing. Although made from inexpensive, non-critical materials, it has a moderate forward gain of 4 db, a good front-to-back ratio (31 db on any one selected channel), and enough bandwidth to cover three adjacent low band TV channels, the entire FM band, or most of the high TV band with negligible loss of gain. It is light in weight, neat appearing, easily built, and surprisingly sturdy. An early model, which has been in use nearly one year, has withstood three windstorms and a small tornado without damage.

Electrically, the antenna consists of three folded-dipole elements, made of wire strung on wooden element supports. Quarter-wave lines used for phasing and impedance transformation are so adjusted that signals picked up by each of the three elements from a station in front of the antenna will add in phase, but from a station in back the signals received by the front and back elements cancel the signal received by the center element. In theory, complete cancellation of the signal

from the back side is possible; practical antennas show measured front-to-back ratios of more than 30 db. At the third harmonic of the design frequency, each element is three half-waves long and the phasing lines are three quarter-waves long. These conditions approximately satisfy the requirements for proper phasing, and it will be found that an antenna cut for Channel 3, 4, or 5 will also perform quite well in the high TV band.

Best front-to-back ratio is obtained when the impedance of each of the outer elements appears to the trans-

Correct element lengths and spacings for all TV channels, FM, and the 2 meter band.

BAND OR CHANNEL	ELEMENT LENGTH	ELEMENT SPACING
2	98	52
3	88	47
4	81	43
5	70	37
6	65	35
7	31	16½
8	30	16
9	29	15½
10	28	15
11	27	14½
12	26	14
13	25	13½
FM	54	30
2 METERS	38	20

mission line as being twice the impedance of the center element. For mechanical simplicity, all elements are made alike, and the necessary impedance step up is obtained in the quarter-wave phasing lines. Due to coupling between elements, the impedance of the three folded dipoles is something other than their free space value of 288 ohms, and is difficult to calculate. For this reason the phasing line impedance giving best front-to-back ratio was determined experimentally. No. 18 wire spaced 3½ inches, No. 20 spaced 2¾ inches, or any other size between No. 16 and No. 24 spaced 85 times its own diameter may be used for phasing lines. Fig. 2 shows a typical field strength pattern, in this case that of an antenna cut for the FM band. Many of the measurements made during the development of the antenna were made using steady signals received from an FM station twenty miles distant. Some work was done with scale models at a frequency of 420 mc., and a laboratory generator and field strength meter were used to make still other checks on Channel 5. Similar gains and patterns were observed in all instances.

Construction of the antenna is extremely simple, and only common woodworking tools are required. Clear white pine is recommended for the boom and element supports because it withstands weather without warping or splitting. Element supports are made by ripping 1 x 2 inch stock into two 1 x 1 inch pieces. The boom used on FM, 2 meter amateur, and high TV

band antennas may be a 1 x 2, while that used for larger antennas should be made of heavier stock, such as 2 x 2 (or two 1 x 2's nailed together). Three braces made from one-inch stock strengthen the joints between the element supports and the boom. Assembly is started by cutting three one-half inch deep notches in the boom, spacing them as shown in Fig. 1. The width of the notches should be carefully measured to insure a snug fit when the elements are later assembled. Next, the three braces are notched to a depth such that when held in place under the boom, the top of the brace is flush with the bottom of the notch in the boom. Again, the notches should be measured for a snug fit. Holes are now drilled and countersunk in each of the three braces, which are then fastened to the boom with one flathead wood screw in each brace. The ends of the element supports are drilled to receive the antenna conductor wires, and two holes are drilled in each element support for the screws which hold it to the brace. After the element supports have been assembled to the boom, the entire framework should be given two coats of weather-resistant paint before the wires which form the elements are added. Observe carefully the element layout shown in Fig. 3, which permits three elements and two transmission lines with only three lengths of wire. Be sure to transpose the phasing line between the center and rear elements a half-turn, keeping the spacing between conductors constant. Joints should be soldered securely. Suitable insulators may be used to stand the elements and phasing wires off from the framework, although no serious loss of performance will result if they are omitted. This is true because the ends of the element supports are at the same r.f. potential as the ends of the elements, and the only effect is a small change in impedance. The midpoint of the center element may be grounded to the mast for static protection, since this point is at r.f. ground potential. If this is done, no lightning arrester will be needed if the mast is well grounded. Since all elements are driven, the frequency response is much wider than that of a parasitic or yagi beam, and no tuning or adjusting is needed after completion if the antenna is constructed as shown.

Performance of the antenna has been quite gratifying. FM stations in Chicago, 130 miles distant, are received with satisfactory quality most of the time, while stations in Wisconsin, Michigan, Ohio, and other locations up to 250 miles distant are often heard. Either WFMT, Chicago, or WCNB-FM, Connersville, Indiana, both on 100.3 mc. may be received without interference from the other by rotating the antenna. Although they do not have the extreme gain necessary for consistent operation in fringe areas, TV antennas of this type perform well in such locations on nights when signals are strong and co-channel interference is severe. In average locations at dis-

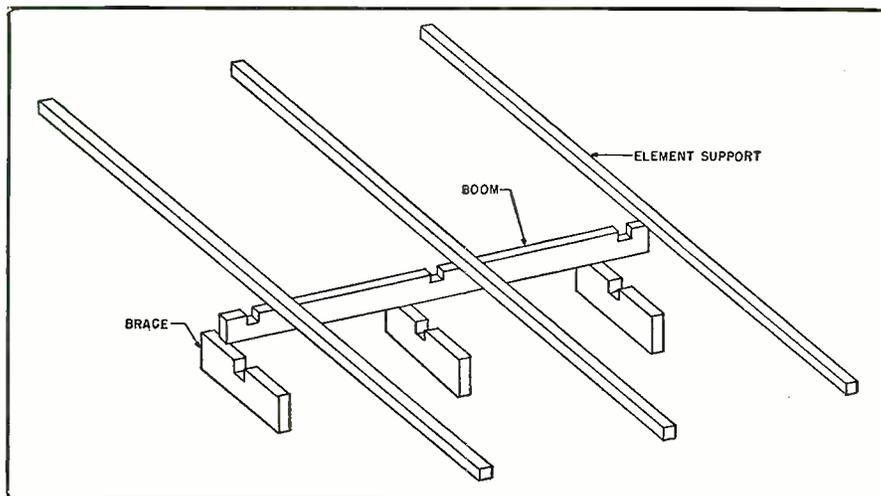


Fig. 1. "Exploded" view of the antenna frame showing how parts are assembled.

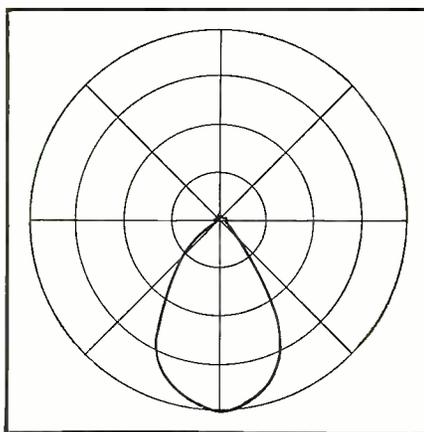


Fig. 2. Typical field strength pattern for phased TV beam antenna. Frequency is 100 mc. The generator was a Boonton 202B unit.

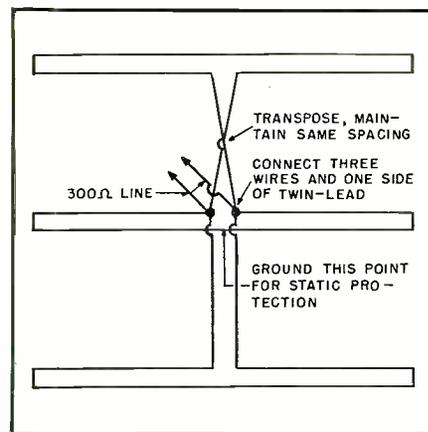



Fig. 3. Layout of the elements comprising TV beam. The phasing line between the center and rear elements must be transposed.

tances of forty miles from a low-band TV transmitter, the antenna will deliver an adequate signal if installed at a height of thirty feet above ground.

Multiple stacking, of course, may be used to give added forward gain without loss of front-to-back ratio.

-30-

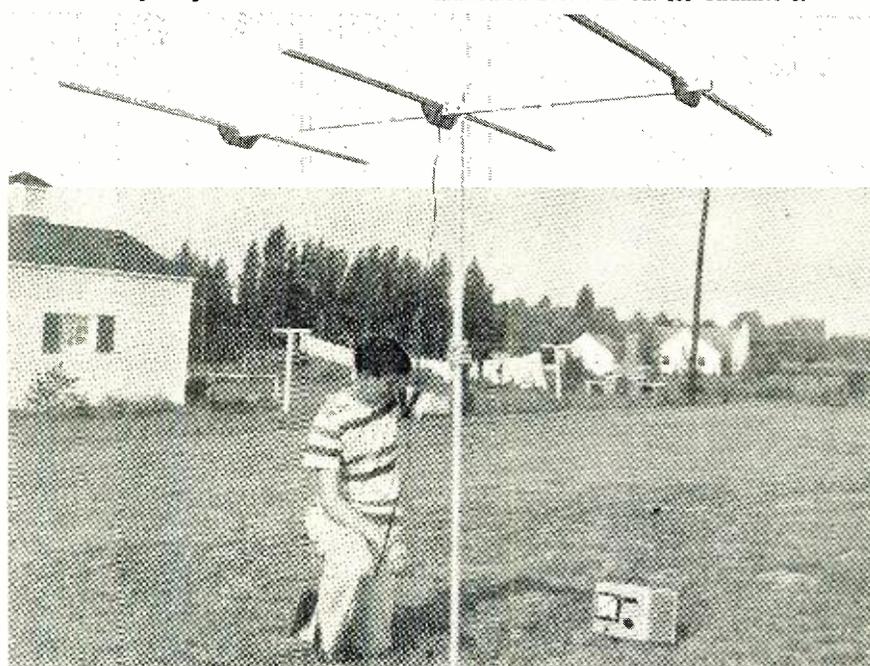Pattern checks on this antenna are made using a field strength meter and a test signal generator. The antenna illustrated below is cut for Channel 5.



# Low-Pass PHONOGRAPH FILTER DESIGN

By

**ROBERT A. SINKER**

Research Analyst  
Northrop Aircraft Company

**Details on an L-C-R filter designed to attenuate record surface noise. It can be used with various cartridges, including variable reluctance pickups.**

THE propriety of using filters or tone controls in conjunction with a wide range high fidelity amplifier is a subject which finds considerable difference of opinion among audio enthusiasts.

One school of thought contends that the object of an ideal audio system is to create, at the ear of the listener, an exact reproduction of sounds he would hear were he listening to the original program material. This group argues that the only control which should be made available to the listener is one over power output. (The controversy of volume control vs. loudness control is purposely being side-stepped as not being pertinent to this article.) The reproduction system, according to this philosophy, should be of flat bandpass over the entire audio frequency spectrum. A high fidelity tuner and the best quality recordings are to be used to provide the signal source for this audio system in order to justify the exact reproduction.

An opposing group argues for a greater degree of listener control over the sound reproduction. They present the incontestable thesis that the ultimate object of the sound system is the entertainment of the listener. They maintain, therefore, that the listener should be able to "season" the music to his personal taste. Inasmuch as the concert goer may sit in that section of the hall which provides the most pleasant tonal balance to his ear, so the listener should be provided with tone controls to create the most pleasing balance to his ear, according to this philosophy.

The low-pass filter for phonograph systems, which is the subject of this article, does not violate the principles of either school of thought. This control provides the listener with a means of reducing the high frequency range of a phonograph system in order to attenuate the record surface noise, or "scratch." The "hands off" school of thought would have a difficult time trying to convince this writer that music

full of "scratch" represents a more faithful reproduction of the original orchestra than music which has been attenuated in the high frequencies with the resultant decrease in noise level.

In the final analysis the listener chooses a sound system which provides the most listening enjoyment to him personally. This writer has a large collection of classical records which have been acquired over a period of many years. This library represents a considerable investment and many of the selections are irreplaceable. Most of the records, including all of those which cannot be replaced, are shellac base discs. The noise characteristics of these records are well known. A


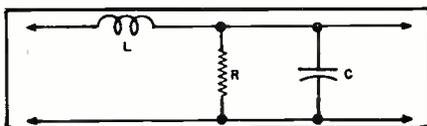


Fig. 1. A single-section low-pass filter using inductance, capacity, and resistance. A filter of this type has a sharper cut-off than the straight RC type circuit.

Fig. 2. Cut-off characteristic of low-pass filter (Fig. 1) for several values of Q.

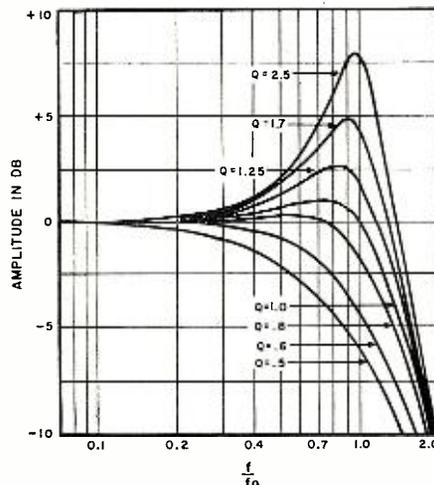

low-pass filter with an adjustable cut-off frequency enables a control over the frequency spectrum of the sound which provides a considerable increase in the pleasure I derive from listening to these records.

A filter using inductance, capacity, and resistance is preferable in this application. Such a filter provides a sharper cut-off than it is possible to obtain by using only capacity and resistance elements. Fig. 1 shows the configuration of a single-section, low-pass filter using all three elements. The resonant frequency and Q of this circuit may be computed from the following well-known formulas:

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$Q = \frac{R}{2\pi f_0 L} = 2\pi f_0 C R$$

Fig. 2 is a graph showing the characteristics of this low-pass filter circuit in the vicinity of the resonant frequency, for several values of Q. The frequency has been plotted as the ratio of the applied frequency to the resonant frequency in order to make the presentation independent of the resonant frequency of a particular filter. It can be seen that a Q of 2.5 results in an undesirable peak in the response at the resonant frequency, while a Q of 0.5 results in too gradual an attenuation curve. The response of the filter with a Q of 1 provides a sharp cut-off while limiting the resonant rise to a negligible one decibel. Specifying a value of one for Q allows a simplification of the second equation to:

$$R = 2\pi f_0 L$$

High quality audio inductors are considerably more expensive than resistors and condensers. They also have an annoying tendency to increase the hum level by coupling to stray magnetic fields from heater and "B" supply circuits. However, those record players which use variable reluctance pickups already contain an inductance suitable for use in the low-pass filter of Fig. 1. A variable reluctance pickup is equivalent to a voltage generator in series with the self inductance of the pickup. By shunting a resistor and condenser across the input to the pre-amplifier, the inductance of the vari-

(Continued on page 107)

Front view of the vacuum tube keyed transmitter from oscillator end. Regulator tubes are behind osc. coil. Keyer is right of tubes.

# A Vacuum Tube KEYED TRANSMITTER

By  
**JACK D. GALLAGHER,**  
W5HZB

**A compact transmitter for c.w. hams. It includes a break-in system and can be adapted for phone.**

A LARGE majority of the transmitters which have been described in various radio magazines provide a real stimulus for prospective builders. There are band-switching transmitters, single-control transmitters, two control transmitters, and just plain "rigs." Either c.w. or phone, or both is used in all of them. If c.w. is used, the method of keying varies from cathode keying, screen keying, primary keying, grid-block keying to vacuum tube keying. If phone is used, the methods of modulation vary from frequency modulation, plate modulation, screen modulation, grid modulation, to clamp-tube modulation.

If the reader is a c.w. ham only, he will scan the various c.w.-phone transmitters and see how he can vary them for strictly c.w. operation. If he likes both, he will dislike something about the c.w. keying arrangement provided, or he will want to modify the modulator to suit his needs. If he is a phone man, he will disregard the method of keying entirely and concentrate on the modulation method used and change it or leave it alone.

It is not the purpose of this article to present a complete all-band phone-c.w. transmitter for the beginner or the "old timer." It is hoped, however, that the transmitter to be described will provide a compact rig with clickless, chirpless keying for the c.w. ham; can be adapted for any type of modulation; and will provide a keyer for break-in operation for c.w., or will eliminate the standby switch for either phone or c.w. Such a transmitter, if properly designed, can incorporate clickless, chirpless keying and all of

the other features just mentioned without causing undue hardship for the potential builder.

A Clapp oscillator was chosen for its stability and one-half of a 12AU7 was wired as such. To isolate the oscillator from the following stages, the second section of the 12AU7 was used as a cathode follower. To boost the output, a 6AC7 was employed as an amplifier-doubler. The remainder of the transmitter is straightforward. A 6V6 can be substituted for the 6AQ5 with very few circuit modifications. Either one or two 807's can be used depending on the desired output.



A 5" x 5" area on the 12" x 17" x 3" chassis was allotted to the v.f.o. All other components both above and below the chassis were kept clear of this area until it was found that shielding the oscillator was not necessary.

After the transmitter was complete-

ly wired and ready for testing, various keying methods were tried. The first type was cathode keying of the 6AC7 amplifier stage. This method was ruled out immediately upon hearing the oscillator running when the key was not closed and noticing a perceptible click in keying characteristics.

The second method of keying tried was keying the cathode follower stage alone. Again, poor results were ob-

Fig. 1. (A) Basic vacuum-tube keying circuit. (B) Vacuum tube keyer and break-in relay tube keyer. With the key open, R<sub>1</sub> should be adjusted so that no current flows through the relay. The sensitive relay can be obtained from a surplus BC-1023-A beacon receiver or may be found as a separate item at some of the larger radio supply houses. Any fast operating relay which works on current of from 1 to 3 ma. can be used. All leads to relay contacts should be as short as possible in order to prevent pickup.

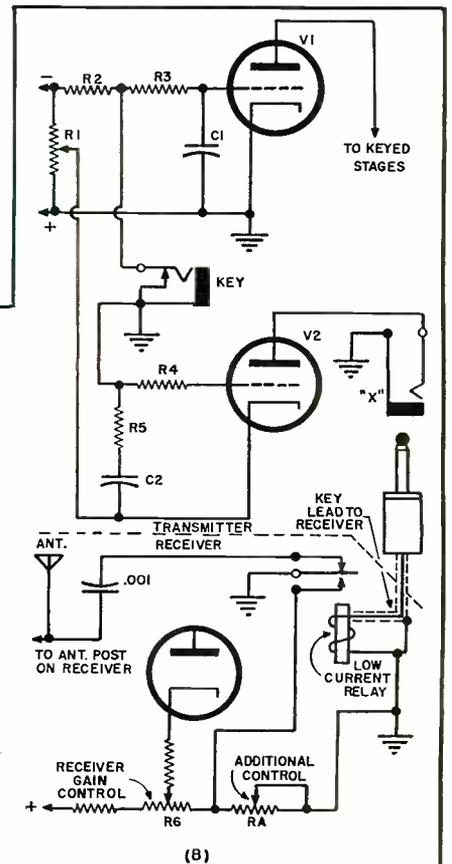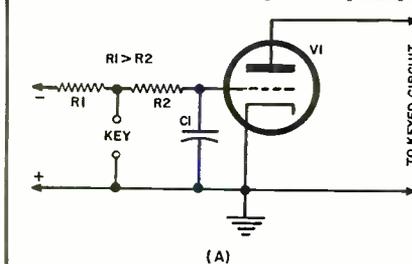


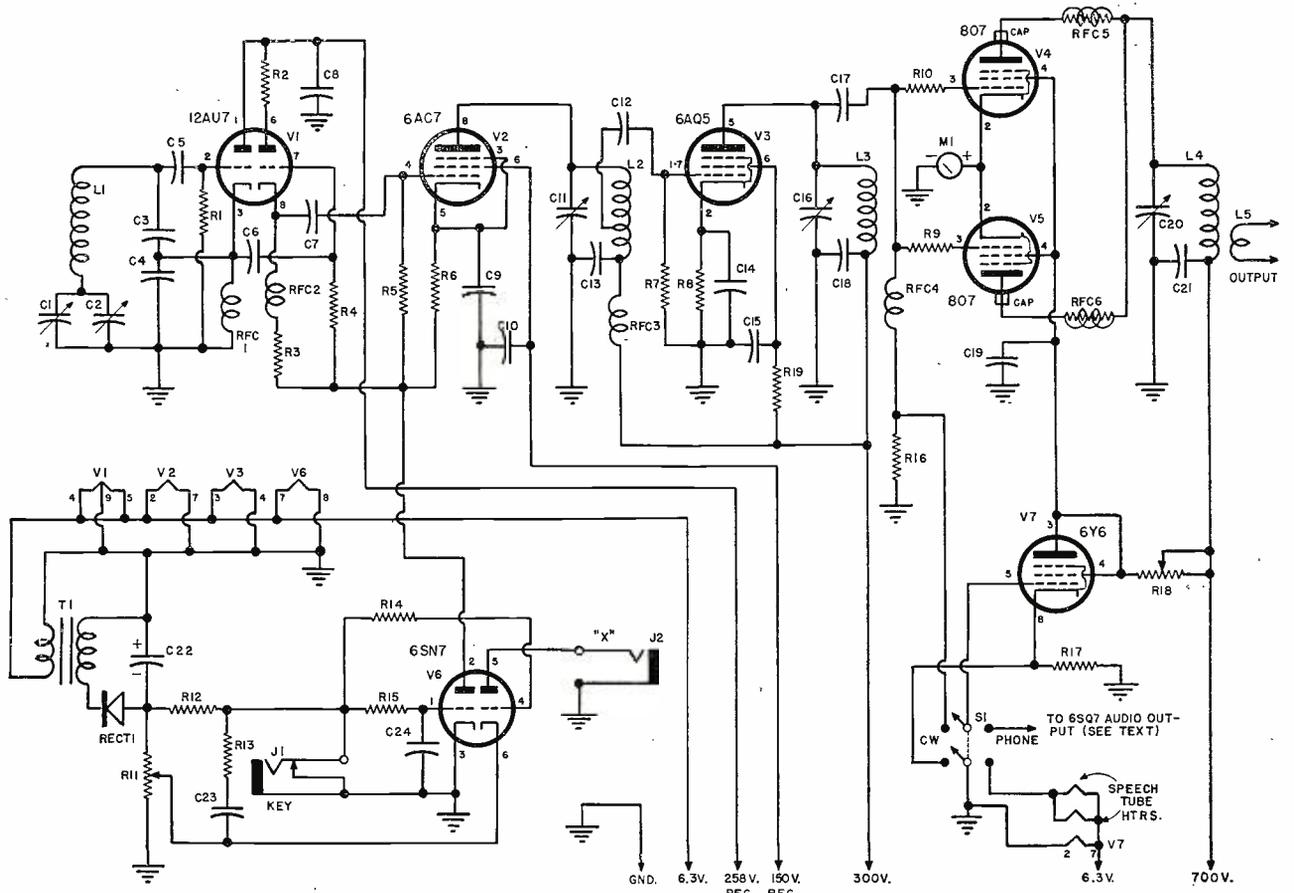


Fig. 2. Complete schematic diagram of the vacuum-tube keyed transmitter including operating frequency chart.

Fig. 3. Schematic of the power supply unit to be used with v.t. keyed transmitter.

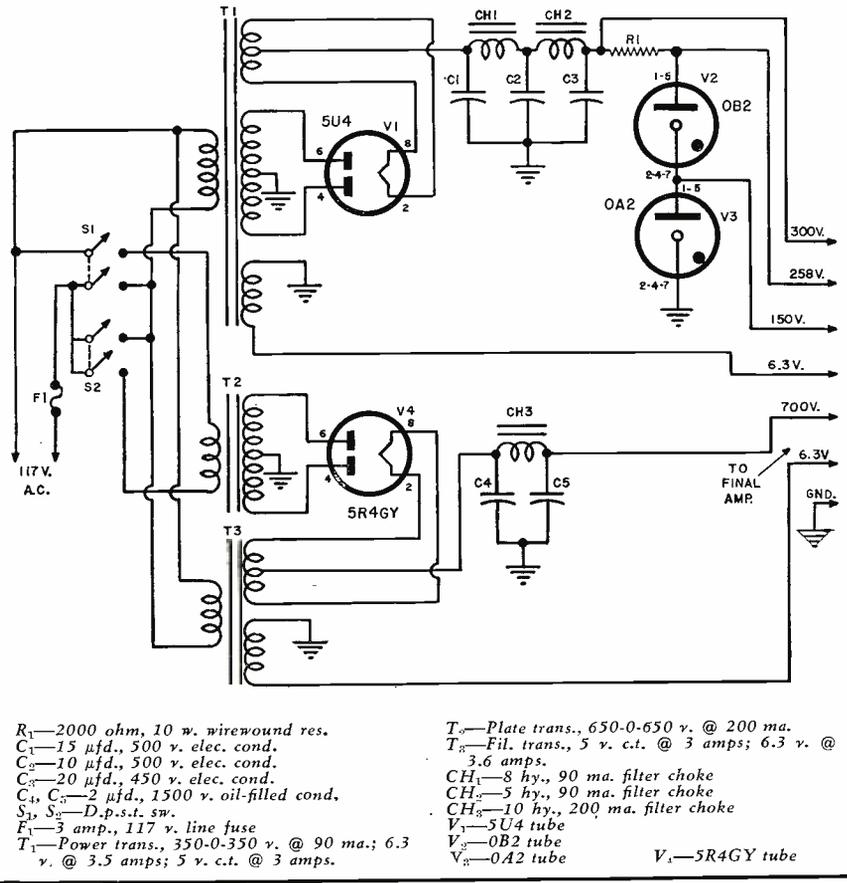

Freq. Output	L <sub>1</sub>	L <sub>2</sub>	L <sub>3</sub>	L <sub>4</sub>
80	160	80	80	80
40	160	80	80	40
20	160	80	40	20
10	80	40	20	10

This chart shows the different coil combinations which work successfully with transmitter. For optimum results, L<sub>1</sub> should be an airwound coil.

- R<sub>1</sub>, R<sub>2</sub>—100,000 ohm, 1 w. res.
- R<sub>3</sub>—12,000 ohm, 1 w. res.
- R<sub>4</sub>, R<sub>13</sub>—500,000 ohm, 1/2 w. res.
- R<sub>5</sub>—330 ohm, 1/2 w. res.
- R<sub>6</sub>—50,000 ohm, 1 w. res.
- R<sub>7</sub>—400 ohm, 1 w. res.
- R<sub>8</sub>, R<sub>10</sub>—47 ohm, 1 w. res.
- R<sub>9</sub>—100,000 ohm pot
- R<sub>11</sub>—1.2 megohm, 1/2 w. res.
- R<sub>12</sub>—150,000 ohm, 1/2 w. res.
- R<sub>14</sub>—6.8 megohm, 1/2 w. res.
- R<sub>15</sub>—20,000 ohm, 10 w. wirewound res.
- R<sub>16</sub>—1250 ohm, 10 w. wirewound res.
- R<sub>17</sub>—25,000 ohm, 25 w. wirewound var. res.
- (See text)
- R<sub>18</sub>—25,000 ohm, 10 w. wirewound res.
- C<sub>1</sub>, C<sub>11</sub>, C<sub>16</sub>—100 μfd. var. cond. (APC type)
- C<sub>2</sub>—50 μfd. var. cond. (APC type)
- C<sub>3</sub>, C<sub>4</sub>—0.01 μfd., 500 v. silver mica cond.
- C<sub>5</sub>, C<sub>6</sub>, C<sub>7</sub>, C<sub>12</sub>, C<sub>17</sub>—100 μfd. mica cond.
- C<sub>8</sub>, C<sub>9</sub>, C<sub>10</sub>, C<sub>13</sub>, C<sub>14</sub>, C<sub>15</sub>—0.1 μfd., 400 v. cond.
- C<sub>18</sub>—0.01 μfd., 1000 v. mica cond.
- C<sub>19</sub>—100 μfd. var. cond., .070" spacing
- C<sub>20</sub>—0.1 μfd., 2000 v. mica cond.
- C<sub>21</sub>—40 μfd., 150 v. elec. cond.
- C<sub>22</sub>—0.5 μfd., 200 v. cond.
- C<sub>23</sub>—0.04 μfd., 400 v. cond.
- RFC<sub>1</sub>, RFC<sub>2</sub>, RFC<sub>3</sub>, RFC<sub>4</sub>—2.5 mhy. r.f. choke
- RFC<sub>5</sub>, RFC<sub>6</sub>—See text
- M<sub>1</sub>—0.200 ma. d.c. meter
- T<sub>1</sub>—Fil. trans., 6.3 v. @ 1 amp.
- Rect<sub>1</sub>—75 ma. selenium rectifier
- J<sub>1</sub>—Key jack
- J<sub>2</sub>—Jack (See Fig. 1B)
- S<sub>1</sub>—D.p.s.t. sw.
- V<sub>1</sub>—12AU7 tube
- V<sub>2</sub>—6AC7 tube
- V<sub>3</sub>—6AQ5 tube
- V<sub>4</sub>, V<sub>5</sub>—807 tube
- V<sub>6</sub>—6SN7 tube
- V<sub>7</sub>—6Y6 tube


tained because the 6AC7 amplifier stage picked up enough of the oscillator to cause it to be heard when the key was open. Keying characteristics were superior to those found when using cathode keying in the 6AC7 amplifier stage. In both of these cases, the oscillator was running continuously on 160 meters with the final on 40.

At this point, it was decided that a suitable means of keying should be incorporated in the transmitter. Experiments proved that both the cathode follower stage and the 6AC7 amplifier stage should be keyed to prevent amplification of the oscillator during key-up conditions. Keying the cathodes of both of these sections would be unsatisfactory because of clicks resulting from comparatively large keying currents. After trying innumerable keying filters and other methods of keying as well, a vacuum-tube keyer seemed to be the logical answer to the problem. Excessive keying currents could be eliminated quite easily by this method; however, the known types of vacuum tube keyers required a power supply and two or three tubes. Further investigation revealed that a small triode could be used to accomplish cathode keying if changes were made in the original circuit.

To eliminate a cumbersome power supply on an already "full" chassis, a 6.3 volt, 1 ampere filament transformer was selected to furnish the necessary voltage for the keyer tube. A small selenium rectifier supplied the necessary d.c.

The basic circuit of a vacuum tube keyer is shown in Fig. 1A. The negative voltage keeps the keyer tube beyond cut-off with the key up. When the key is closed, the grid voltage becomes zero by discharging  $C_1$  through  $R_2$ . When the key is opened,  $C_1$  charges through  $R_1$  and  $R_2$ . Thus a desirable keying characteristic is achieved in that the "make" time is shorter than the "break" time.

In order to provide break-in operation, some means of shutting off the receiver before the transmitter is keyed and turning it on after the transmitter has been keyed, must be made. The schematic shown in Fig. 1B will serve the purpose quite well. Its explanation is as follows: With the key open,  $V_1$  does not conduct because of the high bias on its grid.  $V_2$  does not conduct because its grid is more negative than its cathode. When the key is closed,  $V_2$  conducts first because its grid is made positive with respect to its cathode. The cathode side of  $C_2$  is negative with respect to the grid of  $V_2$ .  $V_1$  conducts next because  $C_1$  is discharged through  $R_2$ . When the key is again opened,  $V_1$  stops conducting because of the high bias immediately placed upon its grid.  $V_2$  will stop conducting after the cathode side of  $C_2$  has become positive with respect to  $V_2$ 's grid. The amount of delay between the time the key is opened and  $V_2$  stops conducting can be easily increased by increasing the values of  $C_2$  or  $R_2$ , or both.

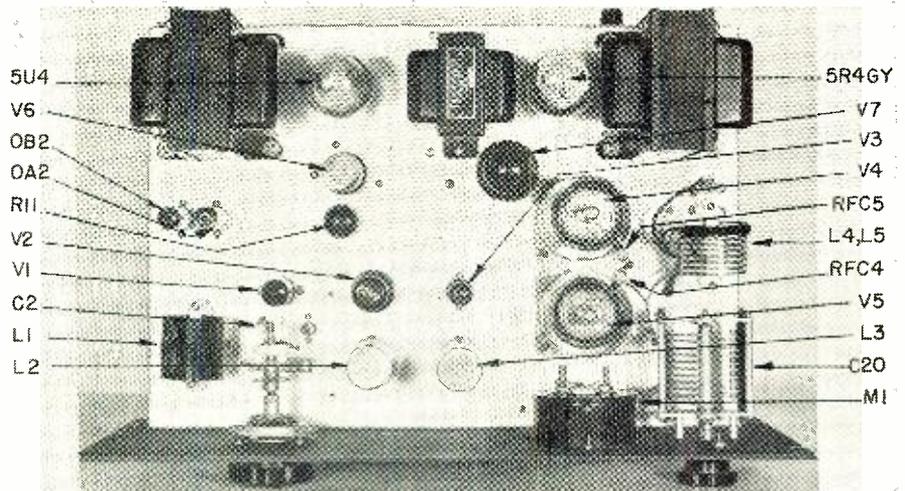

Top chassis view of transmitter showing layout. T<sub>1</sub> (Fig. 3) is at upper left. R<sub>1</sub>, shown in the diagram of Fig. 1B, is below keyer tube. The final power supply occupies upper right hand third of chassis. See Fig. 2 for identification of parts.

A sensitive relay is placed in the plate circuit of  $V_2$  to shut the receiver off by the Rice method as shown in Fig. 1B. This method was developed by Henry E. Rice, Jr., W1PMT, and has been the simplest, fastest break-in system found by the author. In Mr. Rice's original circuit, the transmitter was keyed by the relay which required a battery. Another key lead was also needed from the relay to the transmitter. Here, the entire vacuum-tube keyer and relay keyer tube is incorporated in one tube in the transmitter. Only one pair of wires to the receiver is needed to control the relay, while the keying lead to the cathode follower and 6AC7 stage is kept as short as possible inside the transmitter.

If, by chance, some other means of break-in operation has already been incorporated in the receiver, it is a simple matter to eliminate  $V_2$  and all associated connections including the potentiometer. This will not affect the operation of  $V_1$ .

**Osc. Coil**  
 $L_1$ —160 m.—Bud, OCL, or OEL 160 or equiv.  
 80 m.—Bud, OCL, or OEL 80 or equiv.

**6AC7 Plate Coil**  
 $L_2$ —80 m.—92 t. #30 en. wound on Millen 74001 shielded form, 1/2" dia., 1" long. Slug removed. Tap 60 t. from plate end  
 40 m.—47 t. #30 en. wound on Millen 74001 shielded form, 1/2" dia., 1" long. Slug removed. Tap 32 t. from plate end


**6AQ5 Plate Coil**  
 $L_3$ —80 m. & 40 m.—Identical to  $L_2$  except coil not tapped.  
 20 m.—22 t. #30 en. wound on Millen 74001 shielded form, 1/2" dia., 1" long. Slug removed

**Final Plate Coils**  
 $L_4$ —80 m., 40 m. & 10 m.—Bud, OEL 75 v. coils or equiv.

Coil data. See Fig. 2 for identification.

The adjustment of the transmitter is not complicated and no trouble should be encountered in tuning. With either one of the line switches controlling the power transformers turned "On," all filaments will be on and plate voltage will be applied to all stages except the final. With the oscillator (Continued on page 110)

Bottom view showing oscillator section at lower right. All of the a.c. power wiring is held close to chassis at extreme left. The oscillator, amplifier-doubler, and buffer-doubler, power supply components are at upper right portion of chassis. Filament transformer, T<sub>2</sub> of Fig. 3, is at top center and keyer tube power supply below and to the right. For identification of parts see the diagram of Fig. 2.

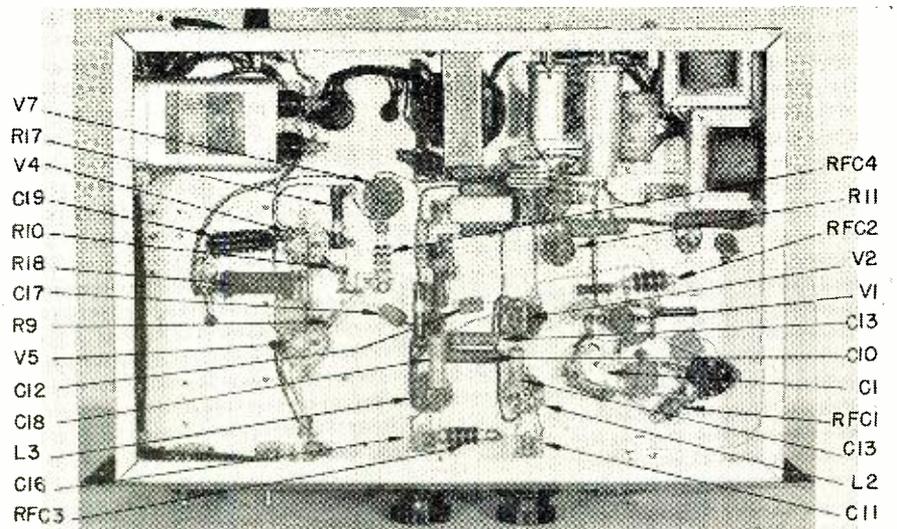


# A SHIRT POCKET RADIO

*Built of standard parts, this receiver features a loop antenna and low drain.*

By

**GEORGE L. JOHNSON, JR.**  
W9LQX

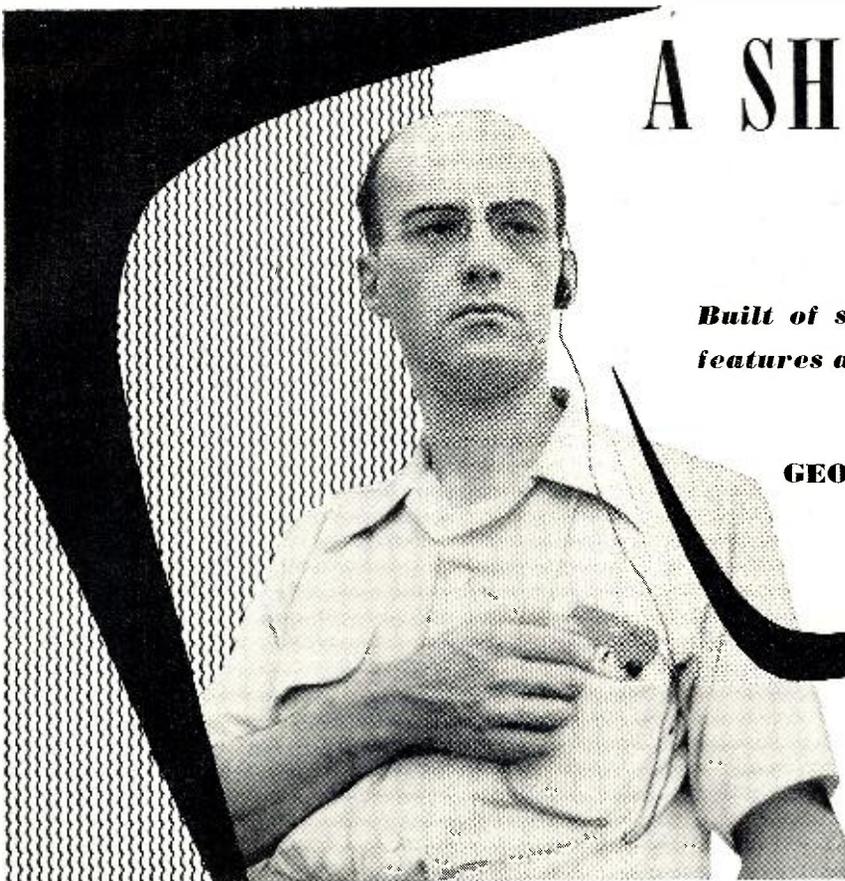

Separate controls for tuning and regeneration allow signals to be peaked for best reception.

POCKET radios are not new, yet the design of a truly pocket-sized set which combines real performance with simplicity of construction and extreme battery economy is new and this author believes that he has achieved such a design in the little radio described in this article.

The current drain of the set is only 140  $\mu$ a. on the "B" battery and 20 ma. on the "A" battery. Under these conditions the "B" battery gives practically shelf life (about 1000 hours or one year of normal use) while the "A" battery, a ten cent penlite cell, will give about 100 hours' service. This should set an all-time low for cost-per-hour of listening as the "B" battery practically never wears out and the "A" cell, which will run the set two hours a day for a month, costs a dime.

The output voltage is ample for comfortable earphone volume on the average local (25 miles distant or less) station. For all its economy of plate current, this little radio is capable of delivering a "rattling the cans" signal on nearby stations. The over-all dimensions of the set are: 6 inches long, 3 inches wide, and  $\frac{3}{4}$  inch thick—a size that will fit easily into the average shirt pocket.

The antenna is a self-contained loop wound on the outside of the case to provide approximately 18 square inches of loop pickup area. This is equal to the size of the loops found in most commercially-built "personal" portables.

Thus, we have a personal radio which may be worn, not carried. If

the pocket is large enough for concealment and a hearing aid type earphone is used, the wearer may listen to the radio in a public place and no one will be the wiser! Other places for use of this set are; sports events, beaches, picnics, or one may do as the author did—catch a morning newscast while riding to work on a streetcar!

Enough of this idle chit-chat. Just what is this little marvel, you say, and how do I go about building it? Which brings us to a discussion of the circuit. To be brief, it is a pentode regenerative detector feeding a one-stage pentode audio amplifier. The main loop winding is in the grid circuit of the detector, and conventional plate feedback is applied through a small "tickler" winding, wound on top of the loop over a layer of Scotch masking tape. Both the detector and amplifier tubes are Raytheon type CK512AX flat hearing aid type voltage amplifier pentodes. They are designed for a maximum plate voltage of 22½, and each tube's nominal filament rating is .625 volt at 20 milliamps. Thus the tubes' filaments are connected in series across a single 1.5 volt dry cell for "A" supply. The "B" supply is a Burgess type U15E 22½ volt battery. Tuning of the set over a range of 540-1300 kc. is done with a standard 9-180  $\mu$ fd. compression mica trimmer. This is easily modified from screwdriver to knob tuning as will be described later. Control over the regeneration is accomplished by varying the amount of r.f. bypass in the plate circuit of the detector, and another 9-180  $\mu$ fd. con-

denser is used here. The control is very smooth and gradual to the point of maximum feedback, and the detector finally breaks into oscillation but with no "plop" or instability. As with all regenerative sets, maximum sensitivity is secured with the maximum amount of feedback obtainable without oscillation. Selectivity of the set is good, as 15 local stations in the Chicago area were easily tuned in and separated. This includes one fifty kilowatt only ten miles away.

## Earphones

The earphone of the original set is a prewar vintage Brush single unit crystal headset. The efficiency of this type of phone is quite good, and what is more important, the high impedance of a crystal phone matches the output load impedance of the tiny CK512 tube. With such a small power output stage, it is absolutely necessary not to lose any useful audio power through poor impedance matching. Any crystal type phone, single or double unit, may be used in the set with no circuit changes. A good quality magnetic phone may also be employed with good results if the phone has high impedance. One word of caution on this. There are certain types of cheap headsets on the market now which have very low efficiency. They may require as much as three or four volts of signal across their terminals in order to deliver a good, usable signal to the ear, whereas with the crystal type one volt is plenty. Beware of the "98 cent special" phones when buying for this set. They are OK for bigger radios, but not this one. When using a magnetic type phone, the 180,000 ohm resistor in the audio plate circuit may be omitted.

Should a hearing aid "ear plug" type phone be used? Admittedly, for a pocket radio, the appeal of this type is high. It is of course the lightest in weight of all phones. The air seal from the diaphragm of the phone to

the ear drum is perfect, and so the maximum transfer of sound energy into the ear is possible. This means an apparent increase in loudness when compared to an earphone that does not plug into the ear. All this is well and good, however, hearing aid phones have certain disadvantages which it is well to consider before deciding on this type. First of all, there is the price, which may easily run double the cost of even a first class single unit crystal phone. Second, is the problem of fitting the phone to the ear of the individual concerned. In fitting a person with a hearing aid, a mold is made of the individual's ear. From this a custom fit plug is made, and of course, it fits well and is comfortable to the one person for whom it is designed. However, this is very expensive and hardly practical for pocket radio use. The average builder who tries to use a hearing aid earpiece will have to get along with a so-called "universal ear mold." These are just about as "universal" as a "universal" hat or "universal" pair of shoes would be. The phone is likely to be too loose or too tight or be uncomfortable. It may fall out at just the wrong time. It is certain to become messy due to the natural secretions of the ear, and cannot be readily passed around to friends, as one would like to do with a novel radio such as this. For these reasons, this author says of hearing aid phones—"Not recommended for the average builder." Should you decide to use one anyway, a crystal type is preferable, and if a magnetic type is used, a matching transformer to match the phone to the CK512 plate must be used. Most magnetic hearing aid plugs have about 125 ohms impedance. The CK512 operates best with 100,000 to 200,000 ohms in the plate circuit, hence the need for a matching transformer. Such a transformer is small, and may be easily incorporated into the set as there is extra space.

### The Receiver Chassis

The major component parts of the receiver are mounted on a 3"x6"x3/32" bakelite board which also serves as the front panel of the cabinet. Two such boards are required, for the front and back, and together they form all the cabinet that is necessary as the sides are formed by the loop antenna and its protective cover. The corners of the plates are rounded off just a bit, to permit easy insertion into a pocket.

### The Loop Antenna

One of the major problems in pocket radio design is getting the signal into the set. Conventional wire antennas are practically useless for a radio which must be carried on the person. Attempts to use the earphone cord as the antenna have been made, but the amount of signal such an antenna can deliver across the primary of an antenna coil is very small for two reasons. The most obvious is that the cord is very short. The second reason, and just as important, is that there is no

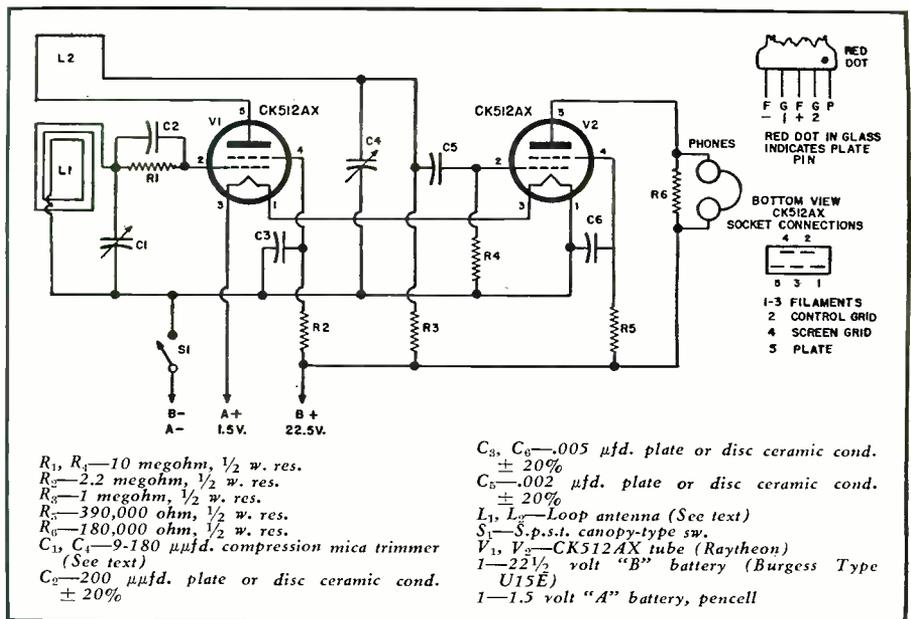


Fig. 1. Complete schematic diagram and parts list for the "Shirt Pocket" radio.


ground return for a tiny chassis carried on the person. There is certainly no direct ground, and very little capacitive ground as the capacity of the person to the set and that of the person's body to the ground are effectively in series, and so the resulting capacity path is high impedance. Also, wire antennas are even less desirable for regenerative receivers, as the moving antenna causes detuning and general instability. For these reasons, the loop type of antenna, which requires no ground, is used in the majority of portable receivers.

The loop antenna  $L_1$  is wound on a form consisting of four pieces of  $\frac{5}{8}$ " dia. dowel rod  $\frac{3}{8}$ " long which are nailed into place on the four corners of the main chassis with  $\frac{1}{2}$ " carpet tacks. The main winding, which consists of 50 turns of #30 double cotton covered wire, is wound directly on the four dowels. There is not sufficient room to wind 50 turns in a single layer on the  $\frac{3}{8}$ " long dowel, so the author resorted to a form of "bank

winding." First, three turns are wound on the form. Then the next two turns are wound in the two grooves directly on top of the first three turns. Then the next three turns are wound on the form; the next two on top of them, and so on. Thus, the winding is composed of ten little groups or "banks" of five turns each. But only a linear winding space for thirty turns is required. This method of winding gives as low a distributed capacity as a single layer winding, yet permits almost twice as many turns to be wound in a given space. Too much distributed capacity in the loop would decrease the tuning range. Should your local stations fall in the 1300-1650 kc. range, wind the loop with eight turns less. This will make the tuning range approximately 600-1650 kc.

After the loop is wound, a coat of quick drying cement is applied to give the required rigidity. Model cement may be used for this purpose. After this cement has dried, wrap a layer

Fig. 2. Correct placement of the components is illustrated in rear view of set.

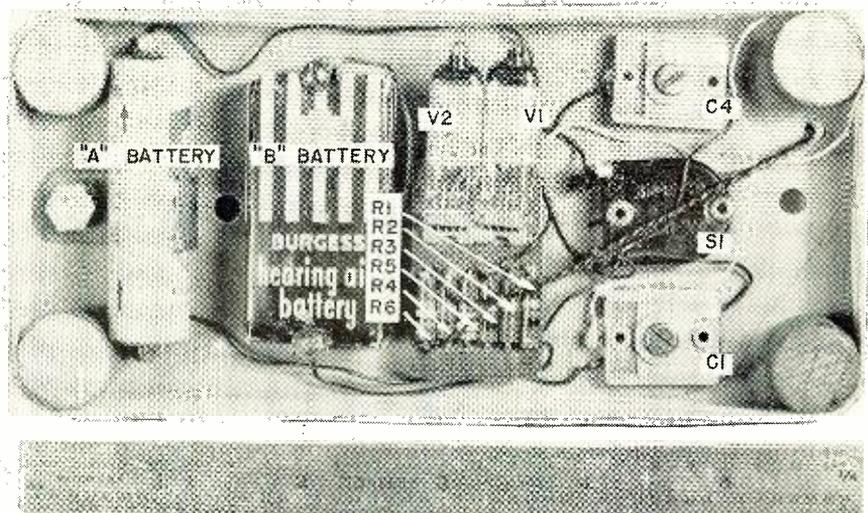

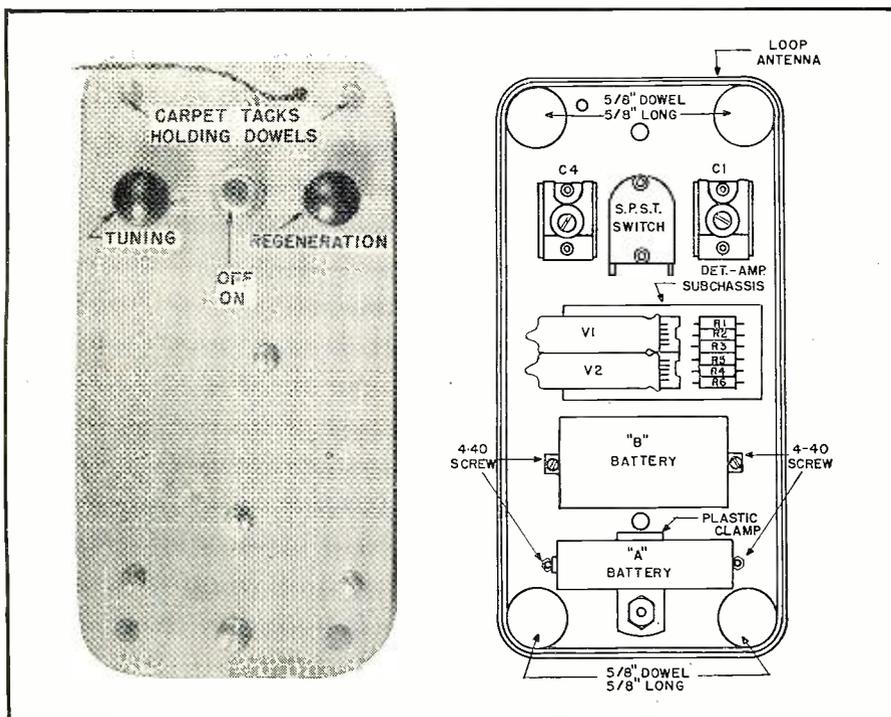


Fig. 3. Front view of the receiver (left) showing location of the various controls. Mechanical drawing indicates how the various component parts should be placed.


of Scotch masking tape around the loop to serve as additional protection, and as a base for the tickler winding  $L_2$ . This may now be wound at the filament end of the loop using 20 turns of #36 plain enameled wire, close spaced. The loop should be connected so that the end nearest the body (when the set is worn) connects to  $C_1$ . This minimizes detuning effects from the set swinging back and forth away from the body. After the tickler winding is wound, coat it with a layer of cement, and then a strip of leatherette may be wrapped around the finished loop both for protection and to give a decorative touch to the cabinet.

#### Modifying the Condensers

The next step in the construction of the set is to change over the screw-driver adjustment compression mica trimmers to knob tuning. First, pre-

pare the shafts. Take a 6-32 bolt, and cut two  $\frac{3}{8}$ " long pieces from it. File the ends flat and remove the burrs. Next make a center punch mark in one end of each piece, being as careful as possible to get it in the center. If a lathe is available to do this, so much the better, but a fair job of centering can be done by hand. Now drill a  $\frac{1}{8}$ " deep hole with a #44 drill on the center punch marks. This hole just fits the small unthreaded end of the #3 screw in the trimmer. Place a small dab of soldering paste in the hole and a small chunk of solder (about  $\frac{1}{16}$ " square) on top of the paste. Using a small hammer, gently drive the little shafts on to the ends of the trimmer screws. Place a tiny drop of oil (light machine oil) on the threads of the trimmer. This guards against any solder running down into them. Holding the trimmer in a vise,

Fig. 4. A detailed under chassis view showing the detector-amplifier subchassis.

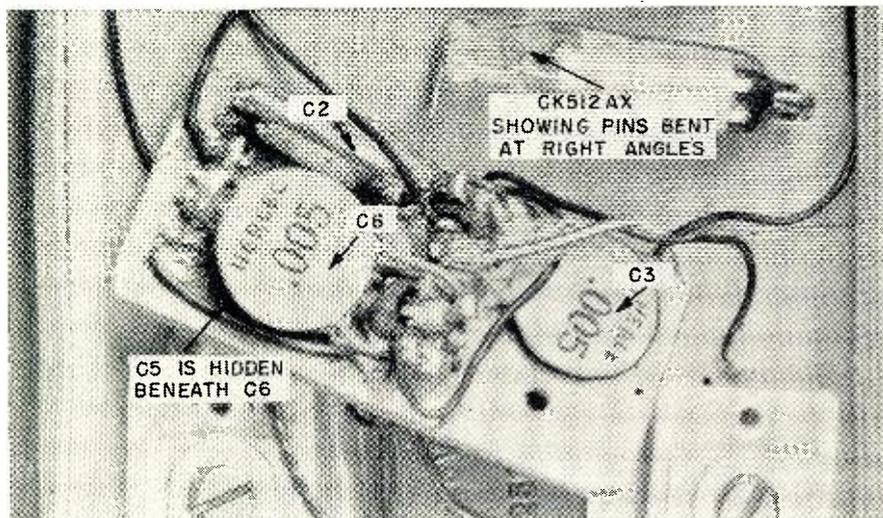

carefully align the shaft. Then apply a hot soldering iron to the free end of the shaft. If all the previous steps have been followed, the flux and solder will melt and just "sweat" the shaft into place.

For knobs, a pair of common bakelite "B" battery terminal nuts serve very well. All that is necessary is to drill and tap them for a 4-40 setscrew and screw them into place on the modified shafts.

#### Detector-Amplifier Subchassis

The two tubes and their associated small resistors and condensers are mounted on a 1" x 2" piece of  $\frac{1}{16}$ " bakelite. The holes for the tube sockets are first drilled, then filed to size, and the sockets are cemented in place with model cement. The resistors are mounted by bending their leads at right angles, poking them through small holes in the bakelite board, and then crimping and clipping them off on the opposite side. They make a fine little terminal board for this size chassis. The ceramic condensers are mounted by their wire leads, and lie flat next to the board. Wiring may be done with an ordinary 100 watt iron, but it is best to provide a small tip for the iron to facilitate a neat job. For hookup wire, the #30 d.c.c. used in the antenna serves well and is fairly easy to handle, as the bare copper wire tins easily. The wiring layout is not critical. No particular precautions must be taken as to lead length or dressing, and this makes the electrical end of building this set quite easy. Concentrate on doing a sound mechanical job and the rest will take care of itself.

#### Final Assembly

After the subchassis is finished, it is laid in place and the leads from the batteries, loop, switch, and tuning condensers are wired in. Then it is fastened to the main chassis board with a single 4-40 screw and  $\frac{1}{4}$ " spacer. The 4-40 screw fits into a tapped hole in the subchassis board (see photo). The trimmer condensers are mounted to the main chassis by their own crimp lug mountings. The "B" battery is bolted into place with two 4-40 bolts and then the leads are soldered to it. A plastic cable clamp is used as the holder for the "A" cell, which makes its contacts to a pair of 4-40 screws fastened to the main chassis. The earphone lead feeds in through a small hole in the front of the case. Connect it up, bolt on the "back" of the case, and the set is complete.

#### Tuning the Receiver

The sensitivity of the set is such that, if it has been properly built, nearby stations should be heard at once. Some degree of volume will be obtained even if the regeneration control is not set for maximum sensitivity. In fact, on the original set, station WCFL (seven miles from the author's home) is so loud that no regeneration (Continued on page 94)

# HIGH-SPEED TANDEM WINDING MACHINES


By  
**SYLVAN A. WOLIN**  
Vice Pres., Pyramid Electric Co.

***Tandem paper-condenser winding machine makes possible the mass production of uniform condensers.***

**N**EW refinements in condenser production equipment have played a great part in increasing plant output. The tandem paper condenser winding machine in daily use at *Pyramid Electric* is one of the best examples of mass-production processes now in use. Its rate of output is four times greater than that of previous machines, with no sacrifice in the accuracy or quality of the finished product.

In production, a very close tolerance is maintained during long runs of condensers ranging from .001 to 1.0 microfarad. From the standpoint of the eventual users of such units—manufacturers, service technicians, experimenters, and amateurs—these advantages spell economy and reliability. Conventional paper condensers are rolled-up “sandwiches” of two layers of metal foil separated and covered by several layers of high-quality dielectric paper. In the non-inductive type, the layers of foil are offset alternately on the paper. When the “sandwich” is rolled completely, foil sticks out from both ends of the tight little roll, and pigtail wires are soldered to them. In the inductive type, the layers of foil are centered on the paper, and special pigtails or tabs are inserted between the foil and paper during the winding operation. In both cases, the relative position of foil and paper must be maintained precisely or the capacitance would then be something other than the desired value. Also, if during the winding operation either foil or paper were to become wrinkled, this would result in loss of life characteristics, “shorts” in pro-

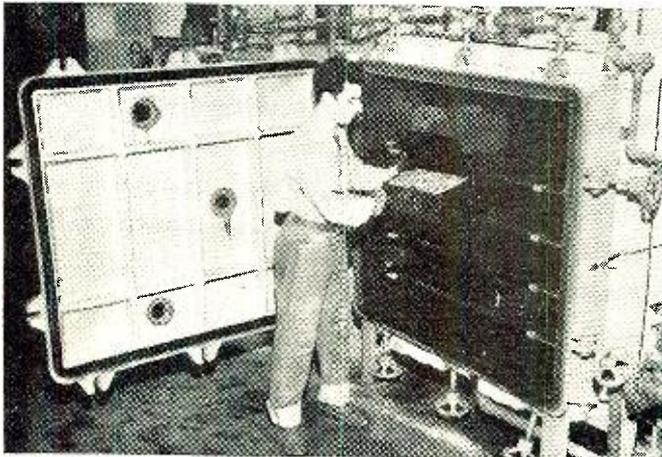Large vacuum oven in which capacitors are dried and then impregnated. Capacity of this oven is several thousand units.



Machine seals metal-glass ends of capacitors to tubular metal cases. Open U-shaped loop, in which ends of cases are placed individually, is fed by 3 kw. of r.f. energy at 3 mc.


duction, and other evils. In the new winding machines, the long, curved channels guide both foil and paper accurately to the winding head so that the sections wind freely and properly thus guaranteeing units free from wrinkling and its resultant problems.

Starting the production procedure, the operator adjusts levers which begin the winding operation. Then an automatic mechanism stops the winding head when the prescribed number of turns for a particular capacitance have been wound. Actually, since each machine has been designed for dual winding, each operator produces two condenser sections during each single winding operation.


Many of the condenser sections coming off the new machines are being put into tubular metal containers with special metal-glass ends. These hermetically-sealed units, because of their extremely small size and weight and their excellent electrical characteristics over a wide range of temperatures, are in great demand for ultra-compact military equipment.

The glass discs through which the terminal wires pass are fitted with outer rings of (Continued on page 111)

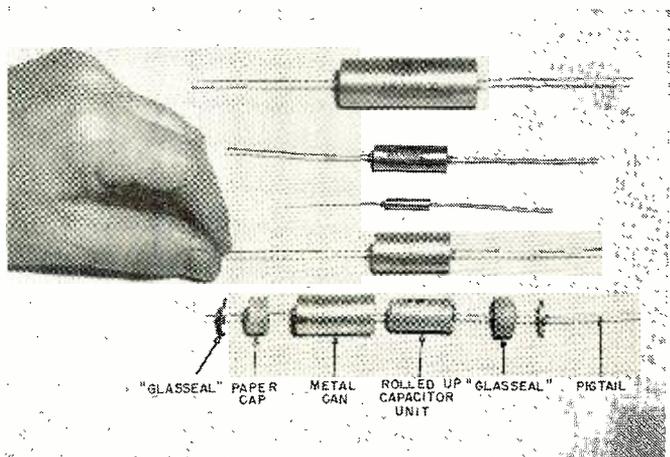Typical (Pyramid) “Glasseal” capacitors. At the bottom is an unassembled unit; immediately above it is an assembled one.



# A V.T.V.M. ADAPTER

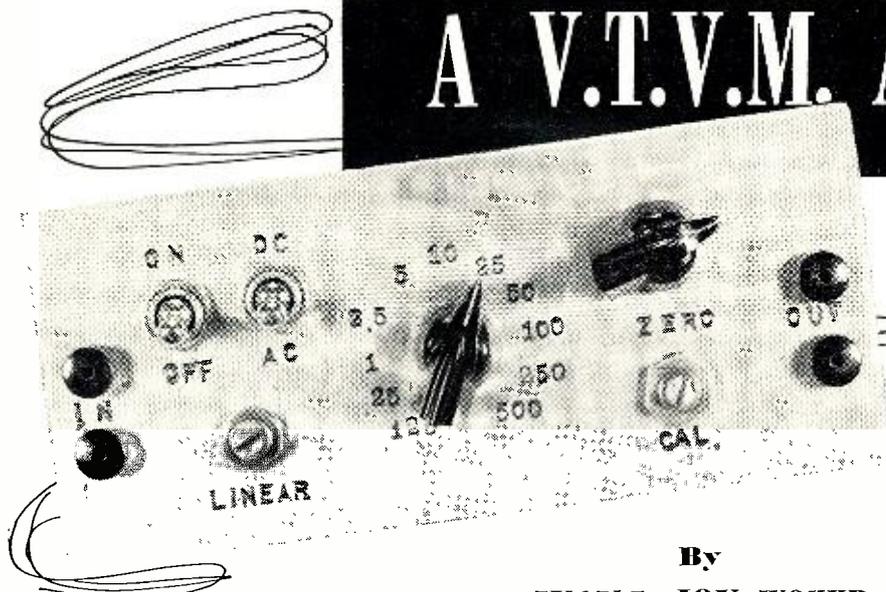

Front panel view of v.t.v.m. adapter. All controls are mounted to front flange of a metal box measuring 7 x 6 x 3 inches.

By  
**IVAN L. JOY, W0KRR**

**A completely battery-operated test unit that connects directly into your present multimeter. The adapter has 44 megohms input impedance and voltages as low as .125 volt can be measured.**

THE need for an electronic voltmeter, combined with the necessity for economy, resulted in the development of this simple circuit which may be used with the type of meters most technicians have on hand.

A vacuum tube voltmeter which had a sufficiently low range cost more than the author was willing to spend so he decided to build an "adapter" for his present multimeter.

After the decision was made, experimentation was begun using various direct current amplifier circuits. It was necessary to keep the amplifier compact and simple yet maintain its linear amplification so that the existing meter scale could be used without alteration. The circuit described herein seems to meet the requirements.

The vacuum tube voltmeter adapter gives a conventional multimeter an input impedance of 44 megohms. The simplicity of the circuit permits the use of the scales already incorporated in the meter by adjusting the linearity control and then setting the calibration control.

Batteries are used to provide complete isolation for the adapter. The filaments are lighted with a small lantern battery and the plate current is supplied by two small 45 volt batteries in parallel. If the builder experiences any difficulty in securing sufficient amplification after the circuit has been made linear, it may be necessary to connect the batteries in series. Battery drain is only 7.5 mils.

The multiplier for the adapter should be chosen for the meter with which it is to be used. The *Triplet* 625-NA, with which this adapter was employed, has a 50  $\mu$ a. movement and with the

meter set in the 50  $\mu$ a. position, it takes .125 volt to the input of the adapter to give full-scale deflection of the meter. It is better to select a voltage for the multiplier that is higher than that required since any over-deflection can be adjusted by means of  $R_{14}$ . The formula for determining the various resistors is:

$$\frac{R}{E_1/E_0} = R_m$$

where:

$R$  is the input resistance chosen or the total resistance of all the multiplier resistors,

$E_1$  is the voltage input to be measured,

$E_0$  is the grid voltage necessary to give full-scale deflection of the multimeter chosen, and

$R_m$  is the resistance from the  $E_1$  point on  $S_1$  to ground.

For example, to select the 500-volt-to-ground resistor for a 50  $\mu$ a. meter, the values substituted in the formula would be:

$$\frac{44 \text{ megohms}}{500/.125} = 11,000 \text{ ohms}$$

The resistor between the 50 volt point and ground is 110,000 ohms. Since there are 55,000 ohms in the circuit from the 100 volt point to ground, 55,000 ohms should be inserted between the 50 volt point and the 100 volt point. With 60  $\mu$ a. meters the value for  $E_0$  in the formula should be .2 and for 100  $\mu$ a., meters .3 should be used. The overall input resistance can be chosen to fit the type of resistors you plan to use. The total input resistance could very well be 40 megohms if desired.

The batteries, tubes, and multiplier

resistors are mounted in a metal box measuring 7" x 6" x 3" as this will provide sufficient room for the various components required. The unit can, however, be built in any convenient sized box which will hold the batteries the builder has on hand. On the low scales there will be some pickup from the leads in the presence of a.c., therefore, it is best to have the unit shielded in a box which is grounded to the circuit being tested.

Care should be taken so that the leads do not touch the metal box when the multimeter is connected to the adapter. If one of the leads should touch the metal while the second lead is plugged in and the meter is on the 50  $\mu$ a. position, the meter is liable to be damaged.

## Adjusting the Unit

From several flashlight cells select two units whose voltages are the same, as measured without the adapter connected. Next connect the adapter to the multimeter with the multimeter range switch turned to 10 v. This will protect the meter in case  $R_{13}$  should be badly out of adjustment.

Set  $R_{13}$  so that the meter reads zero, then change the multiplier switch to the 50  $\mu$ a. position. Should the meter be the type that reads 100  $\mu$ a. on the lowest range, use this position with the multiplier designed for use with this particular meter.

Turn the adapter multiplier switch to the 5 volt position and measure the voltage of one cell, using the adapter, and then the voltage of the two cells in series. If the reading of the two cells is less than twice the voltage of a single cell,  $R_{17}$  should be decreased, giving less bias. Should the reading be more than twice the value of a single cell,  $R_{17}$  should be increased, thus increasing the bias. After  $R_{17}$  is carefully adjusted, three cells and three linear points can be used.

After  $R_{17}$  is all set, the next adjustment is  $R_{14}$ . Connect a known source, such as 3 volts, with  $S_1$  set on 5 volts. Adjust  $R_{14}$  so that the meter reads 3 volts on the 5 volt scale. This adjustment takes care of calibration for all d.c. ranges and the adapter is ready for use on d.c. voltages.

It may be well to have more than two 3Q4's on hand when setting up this circuit as they are not too well matched as a rule. Ordinary carbon resistors were used in the construction of the adapter but it would be possible to use precision units if the builder wants the added accuracy possible with such components.


To measure a.c. volts, turn the multimeter to 2.5 volts a.c. and throw switch  $S_3$  so that it opens and puts  $R_{15}$  in the calibration circuit. Resistor  $R_{15}$  is the calibration resistance and can be chosen by measuring a known a.c. voltage, such as filament voltage. Set the adapter multiplier switch to the 1 volt position, which represents 10 volts a.c. A multimeter with a 10,000 ohms-per-volt input requires a 33,000 ohm resistor in order to provide the proper reading. Perhaps the easiest way to establish the value of  $R_{15}$  is to connect a 50,000 ohm potentiometer across  $S_3$  in place of the fixed resistor and adjust the pot so that the meter reads 6.3 volts on the 10 volt scale of the multimeter with the adapter set at the 1 volt position. Next measure the potentiometer and replace it with a resistor of the correct value. If desired, the potentiometer for this adjustment could be mounted and left in the circuit. This adjustment calibrates all a.c. ranges and the adapter is ready for use on a.c. voltage.

#### Using the Adapter

In actual use the operation of the meter is straightforward. For example, to measure a.v.c. voltage, set the multimeter on 50  $\mu$ a., turn the adapter multiplier to 10 volts, close  $S_3$ , connect the negative lead from the adapter to the ground of the receiver, then connect the positive lead of the adapter input to the a.v.c. voltage and read d.c. volts on the d.c. 0-10 volt scale. Change the leads on the multimeter for deflection to the right rather than using the positive adapter input lead to the ground connection of the work as stray pickup will be apt to affect the readings.

To use the adapter for a.c. volts, change the multimeter switch to the 2.5 volt a.c. position, open  $S_3$ , and set the adapter multiplier switch to 10 volts for 100 volts, 50 for 500, etc. Be sure to take the a.c. reading on the a.c. scale of the multimeter. The a.c. volts can be read from the grids or plates of an audio amplifier without disturbing the circuit with any appreciable load. When this can be done, voltage gain on any stage can be easily determined.

One observation made was to get .4 full-scale deflection from a high impedance dynamic microphone by using the adapter with  $S_3$  in the d.c. position and the multimeter in the 2.5 volt a.c. position. This gives more gain but gives erroneous readings on the multimeter. Nevertheless it is possible to go through an audio circuit, starting at the microphone or phonograph pickup, checking the voltage gain of everything. With the adapter set on the

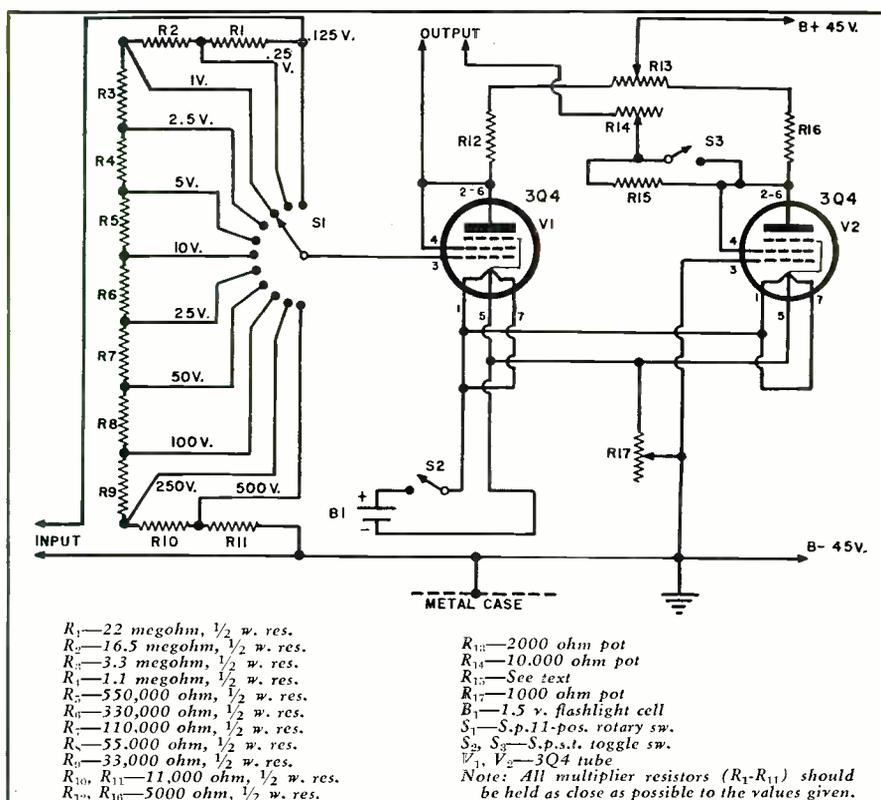


Circuit diagram of the vacuum tube voltmeter adapter. It is versatile to the extent that it can also be used as a preamplifier for an oscilloscope or audio amplifier.

.125 d.c. position, voltage as low as .0025 volt represents one division of the 50  $\mu$ a. scale. With the adapter set on .125,  $S_3$  closed, and the multimeter set on 2.5 volts a.c., the lowest voltage reading will be about .005 volts.

This adapter can be used as a pre-

amplifier for an oscilloscope or an audio amplifier as it is very linear. Should it be necessary to measure smaller voltages, two such amplifiers can be used in series and linearity maintained as long as the amplifiers are not overloaded.

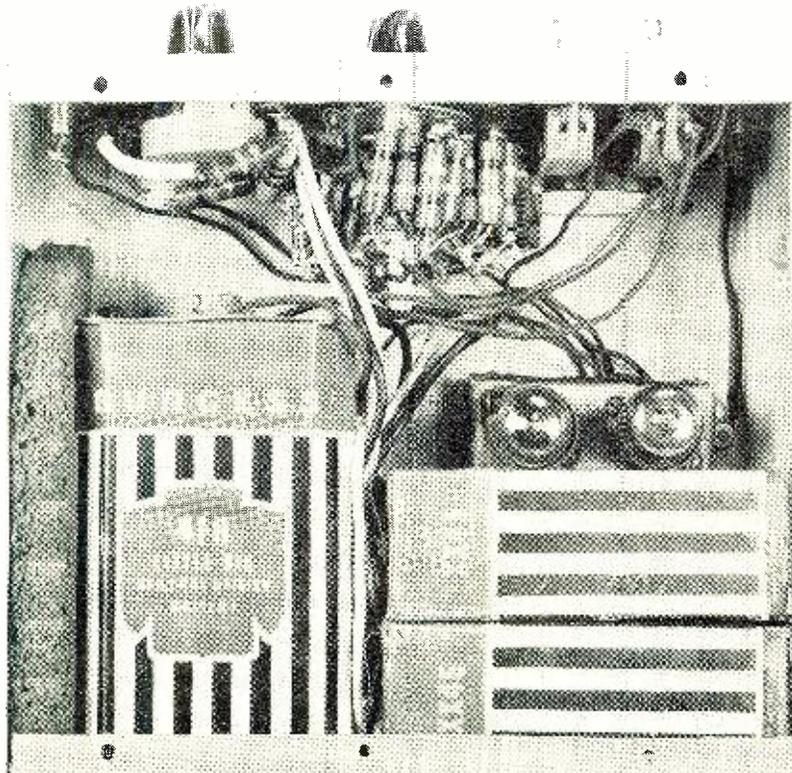
View of completed v.t.v.m. adapter. All components are mounted under the chassis.



# A Beat-Frequency V.F.O.

By  
**H. W. KLINE**  
**W2DKE**

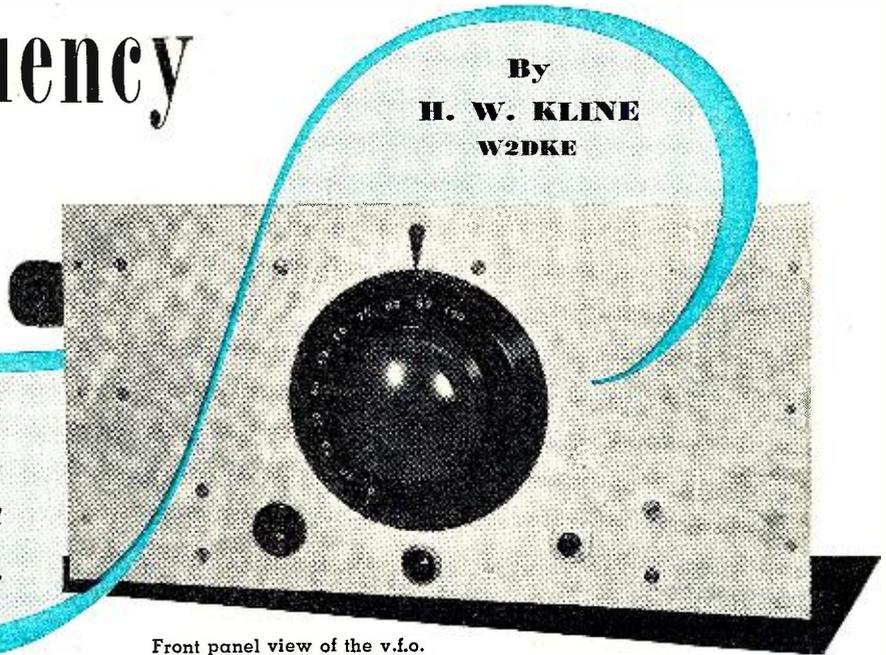**For the ham—complete details on a reliable unit. This v.f.o. has the stability of a crystal controlled oscillator circuit.**



Front panel view of the v.f.o.

A BEAT-FREQUENCY oscillator for transmitting on any frequency within the harmonically related amateur bands and with stability equal to that of crystal control has been in use at W2DKE, Schenectady, N. Y., for over a year. Its reliability and performance have been found to be entirely satisfactory.

Modern requirements for communication demand that the frequency regulating section of the transmitter have certain fundamental operating characteristics not needed in the past. Such features are particularly important where the transmitter is used for telegraphic transmissions. For amateur transmissions the important features are as follows:

1. The transmitter must be instantly operative for high speed, break-in transmissions during the process of receiving.
2. The keying time constant of the keyed portion of the transmitter should be such that five letter code groups up to 60 or 70 groups per minute may be switched.
3. The oscillator, used for maintaining the desired carrier frequency, should be easily tunable and run continuously; should not be keyed; and, should in no way be reacted upon by the keying process.
4. The carrier frequency should change no recognizable audio-frequency amount to the human ear when heterodyned by either a local, low sensitivity monitor or by a distant, high sensitivity receiver.
5. There should be no recognizable

clicks or thumps either leading or lagging an "on" increment of carrier.

6. No fundamental or harmonic signals should be present from a v.f.o. that might be picked up within the desired communication bands on a sensitive communications receiver.

In the past it was found that a transmitter oscillator could not be left "on" continuously while receiving on the same frequency. A continuous signal was obtained from the oscillator which could not be satisfactorily reduced except through the expedient of total shielding of the oscillator. It was found that total shielding of the oscillator was next to impossible or at least a satisfactory approach was expensive.

When keying an oscillator employing a self biasing circuit certain disadvantages are inherent. The starting of an oscillator requires an excessive slug of plate current because at the instant of starting, the oscillator tube has no initial bias and it draws a surge of saturation plate current. Attempts to limit this surge of current result in other complications which either alter or add something to the desired response. For this reason it is desirable to design a v.f.o. so that it may be run continuously while keying is accomplished at other points in an exciter.

The beat-frequency v.f.o. employs two oscillators. The oscillators can run continuously without any interference to reception. The unit can be keyed for the fastest break-in operation. Frequency drift has been found to be negligible and the over-all operation is

thoroughly reliable. It provides output at 1 watt level, 300 ohms impedance over a frequency band of 3.5 to 4.0 megacycles.


Cathode follower output at 300 ohms impedance was decided upon so that lines to amplifiers or multipliers could be made from cheap TV receiver transmission line. The unit can be coupled to many existing transmitters simply by removing the crystal and oscillator tube and connecting a small coil across the end of the 300 ohm line (which may be of any length) and placing this coil in the former crystal oscillator tank coil.

One of the oscillators employed operates at a constant frequency of 1 megacycle while the other is tunable over a band of 2.5 to 3.0 megacycles. A novel feature, which greatly increases the stability of the unit, is that of using a twin triode for both oscillators. This feature plus those of regulated plate voltage, oscillator coils of approximately equal physical dimensions, and selected oscillator circuits, were responsible for the high degree of stability obtained.

An investigation of self-oscillators over a period of time showed that two oscillators tended to drift in such manner that the sum frequency remained substantially constant. Long period drifting was due to changes in ambient conditions while short period drifting was due to changes in the tubes. It was found that when the tube elements were contained within a common envelope, short period drifting became negligible while room or ambient temperatures caused little change. A block diagram, Fig. 1, shows a general arrangement of the v.f.o.

The frequencies selected were those believed to give the least harmonic response in any of the amateur bands thus allowing the oscillators to be run continuously. Tests with a sensitive communications receiver actually showed no interference on any har-

Fig. 1. Block diagram showing the general arrangement of the beat-frequency v.f.o.

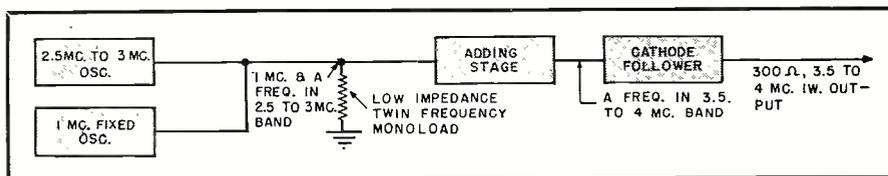

monic multiples that might occur within the amateur bands.

Fig. 2 shows the wiring of the v.f.o. less a conventional power supply. Either oscillator circuit is similar to the well-known *Lampkin* circuit which differs from the *Clapp* circuit in that the grid and cathode are tapped to low reactance points in the inductance branch of the tank circuit rather than to low reactance points in the capacitive branch of the tank circuit. Degen-erative resistors are inserted in series with the cathodes to improve wave-forms and substantially reduce harmonic outputs.

The "monoload" is a single resistor common to both oscillators or both frequencies. Its chief purpose is to allow the outputs of the oscillators to be combined and extracted simultaneously, without any reaction between the oscillators. Usually, the plate of an oscillator tube would be bypassed to the chassis with a condenser of negligible reactance, however, in this case a very low impedance, common to both plates, is inserted between the plates and chassis. This impedance can consist of a non-reactive resistor having a value of from 300 to 500 ohms. A wirewound resistor should not be used.

The two frequencies across the "monoload" resistor, of substantially equal amplitudes, are applied to the grid of a plate-type rectifier consisting of a type 6AC7 tube operating with cathode bias to near cut-off. This tube operates as an adder, the plate tank being tuned to cover the frequency range of 3.5 to 4.0 megacycles. The tuning condenser is ganged with the tuning condenser of the 2.5 to 3.0 megacycle oscillator thus allowing single frequency control of the unit.

The output of the adder is applied through an anti-hash resistor of 1000 ohms to the grid of a cathode follower. A cathode follower will tend to develop hash when operating in cascade with a high gain rectifier due to a multivibrator action unless such oscillations are prevented. A 1000 ohm resistor, connected in series with the cathode follower grid, was found to prevent this effect. Without it the hash was present.

All components were of usual com-

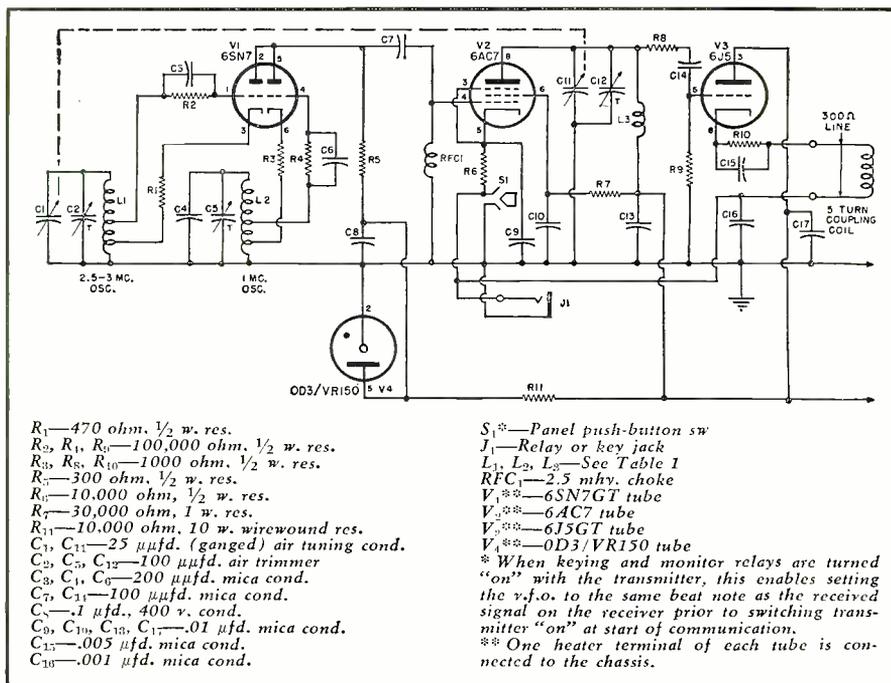


Fig. 2. Circuit diagram of the v.f.o. An external power supply is required.

COIL FREQUENCY	EN. WIRE	CATHODE TAP	GRID TAP	TOTAL TURNS
L <sub>1</sub> 2.5-3 mc.	No. 26 B & S	10 t.	20 t.	48
L <sub>2</sub> 1 mc.	No. 26 B & S	12 t.	24 t.	64
L <sub>3</sub> 3.5-4 mc.	No. 26 B & S			24

Table 1. Data for winding coils L<sub>1</sub>, L<sub>2</sub>, and L<sub>3</sub>. See text for additional details.

mercial grade except the coils which were wound according to data given in Table 1.



All coils were wound with no spacing on compound tubing of good quality having an outside diameter of 1 1/4 inches. The "Q's" averaged about 130. The coils were fixed with Amphe-nol No. 912 Coil Dope. The values of "Q" are not restrictive. Coils having higher "Q" values may be used if desired. In the model the oscillator coils were mounted at right angles to each other in the same shielding compartment. The steatite socket for the 6SN7GT oscillator tube was offset on studs mounted on the side of the compartment shield so that the tube was outside the compartment and heat from it could not be transferred to the compartment. The tube was in a

horizontal position for better heat radiation. No shield was used over the tube and the design was such as to allow no restriction of air circulation around the tube. The idea in back of this was to subject both coils to ambient temperature only with no added effects due to tube heat. Since this was done initially, the degree to which it assisted in maintaining constant frequency was not determined. It was considered to be advisable, however.

The individual oscillators can be aligned approximately by listening to them on a communications receiver. Adjusting a trimmer on either oscillator after this will permit setting the operating dial as desired. For the values given, the 3.5 to 4.0 megacycle band will be covered with a 180 degree  
(Continued on page 126)

Top chassis view showing the special shielding compartments.

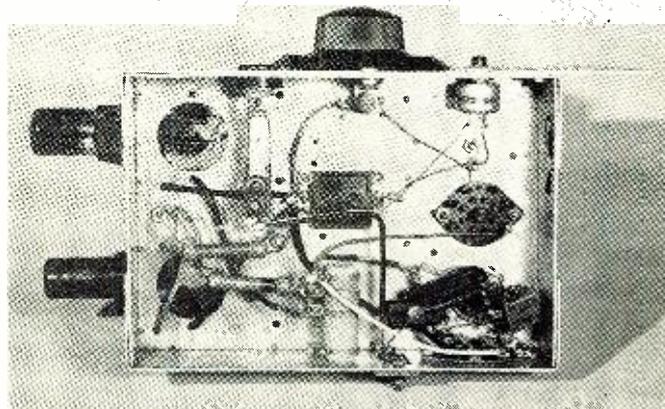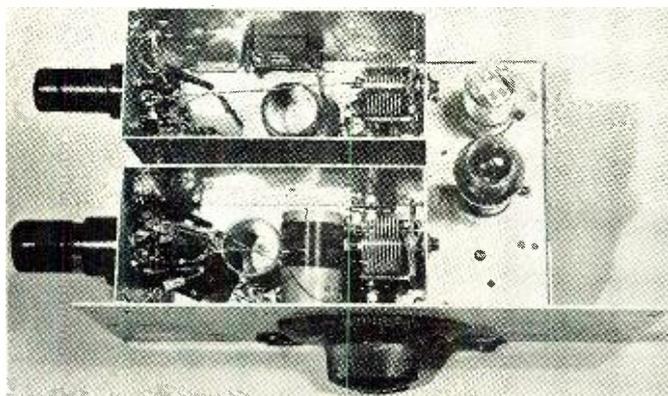Under chassis view. Tubes are operated in horizontal position.



# Simple SERVICE AIDS

**Time savers • Reduce your  
TV service time • Use these  
simple tools to cut cost.**

Fig. 1. A variable condenser box.

**By WALTER H. BUCHSBAUM**

Author, "Television Servicing"

AS TECHNICIANS become more proficient in their work, the tendency is to find shortcuts and time savers to increase the number of sets that can be repaired in a given length of time. The greatest time saver, of course, is a thorough understanding of TV circuitry and some simple logic. But there are many other tricks to speed up servicing. Probably the simplest is the use of clip leads. A rubber-covered black or red test lead with a covered alligator clip at each end can be a genuine time saver. By means of clip leads, suspected parts can be shorted out temporarily; other components can be connected into the circuit and switched around to different points while the set is in operation. A good example is the case of excessive 120 cycle hum in a TV set. To locate the defective filter condenser, connect the can of a good replacement condenser to the "B minus" bus in the receiver and the center terminal to the center of the suspected filter condenser in the set. If this is done with wire and soldering iron, the set must be turned off each time, but if insulated clip leads are used you can observe the results right on the screen. It is a simple matter to shift the "hot" clip lead to other "B plus" points in the set until the defective filter section is located. Shunting good resistors across suspected ones, grounding a.g.c. or bias voltages, or checking for open coils can all be done while the set is in operation by means of a simple set of clip leads.

Most technicians already use clip leads extensively and it is the purpose of this article to illustrate several other items designed to speed up and simplify TV servicing. Fig. 5 shows two potentiometers which can be used to good advantage in TV troubleshooting. For ease of connection, insulated

clip leads are brought out from one end and from the center terminal of the control. The entire control is taped up and its maximum resistance value marked on the bottom for easy reference. The taped body prevents shorts and shocks when the control is connected in the chassis. A busy technician will find it worthwhile to have a set of such controls around, ranging from 2 megohms to a 5000 ohm potentiometer. In the lower ranges the potentiometer should be of the 2 or 5 watt type to permit its use on circuits carrying larger currents. The applications of these controls are too numerous to list here, but some of the most frequent uses deserve mention. Whenever a resistor is burned and its value is not known, clip a taped control in its place. If the resistor is larger than 1 watt try the lower ohm range control first. Set the control for maximum resistance, turn the set on, and wait for results. Adjust the control for best operation of the particular circuit, turn the set off, and read the correct resistance value of the control with an ohmmeter. Then solder a resistor coming closest to the ideal value into the circuit. Another use for these handy controls is to locate defects due to resistors being off-value or to verify the need for values other than those originally used. A typical case is in vertical sweep circuits where the series resistors in the hold and height control may be satisfactory for one particular tube, but do not quite meet specifications when a different tube is used. In many big picture tube conversions such problems come up and the controls shown in Fig. 5 are real time savers there. Just clip them into the circuit, turn the set on, and set the hold and height controls to a center position. Then adjust the clip-controls for proper height and hold. Measuring the resistance with an ohmmeter tells you at once what permanent resistors to use. Once a set of these clip-controls

is made up you will find so many uses for them that you wonder how you ever managed without them.

An item similar in its use to the clip-controls, is shown in the photograph of Fig. 1. This is a very inexpensive, home-built condenser box. Far from being an exact laboratory instrument, this little box covers the most frequently used condenser values from 110  $\mu\text{fd.}$  to .1  $\mu\text{fd.}$  in ten steps. It is possible to make up a much more elaborate condenser box and cover a greater number of values, but for everyday service work we have found the type shown in Figs. 1 and 2 to be adequate. The principal use for this condenser box is probably in custom installations, big picture tube conversions, and similar work where you cannot be sure which condenser value will do the best job. In many cases where inadequate width and high voltage are observed, the coupling condenser to the grid of the horizontal output amplifier may have insufficient capacity. Connecting the condenser box into the circuit will quickly show the value needed for best results. In video peaking networks, tone control circuits, or de-emphasis filters the use of the condenser box permits quick selection of proper values under operating conditions.

Fig. 2 shows the circuit of this condenser box. A ten-position, double-deck, rotary switch was used here and the seven condensers are arranged in such a manner that they combine in series and parallel connections to give the values shown in Fig. 1. If you want to make a more elaborate device out of this condenser box, add more positions on the switch, another deck, or else a separate range switch to get the intermediate values missing in our present simple design. The author found the condenser box shown here adequate to give an indication in all cases where doubt existed as to what value condenser should be used in a particular circuit.

It should be understood that this condenser box is not usable at i.f. or r.f. frequencies, nor will it show exact values in resonant circuits such as are used in horizontal oscillator circuits. The distributed capacity and the relatively long leads make it unsuitable for anything above about 10 mc. It can be used to check the operation of bypass and decoupling condensers in AM and FM sets, r.f. high voltage power supplies, video and sound amplifiers, etc. It is especially useful in conjunction with the clip controls described previously when working out RC time constants for discharge networks, multi-vibrators, feedback circuits, and similar applications where the value of the condenser and resistor are dependent on each other and only one set of values gives optimum performance.

The condenser box is not suitable for r.f. and i.f. circuits above 10 mc., but the unit shown at the right in Fig. 4 is used for just such work. We took a 3/8-inch polystyrene rod and cut a slot into one end into which was inserted a .005  $\mu$ fd. ceramic disc type condenser. This simple gadget permits us to put this condenser into the circuit as a shunt for any r.f. or i.f. bypass condenser which might be open. It is not possible to hold this little condenser with the fingers since the hand capacity will detune the resonant circuits in the i.f. or r.f. section and thus give a false indication of the trouble. A good example of the application of this condenser holder is the case of an oscillating video i.f. section. Whenever the hand is brought near, the oscillation stops, but since the hand cannot be installed with the set, the defective part must be located. After checking the alignment with a bias battery to cut out the oscillation, the conclusion is that a defective bypass or decoupling condenser is causing the oscillation.

Touching the .005  $\mu$ fd. bypass condenser across each of the bypass condensers in the i.f. section will eventually locate the defective one by stopping

the oscillation. Ordinarily you might have unsoldered several bypass condensers, checked them or replaced them before locating the defective one. By using the condenser holder the defect is located in just a few minutes.

In order to increase the efficiency of this little gadget we turned the other end down to about 1/4-inch diameter and cut another slot there. This can either be used to hold another, smaller value condenser or else to twist and poke wires and connections in the search for intermittent or cold solder joints.

The Z-shaped item on the left of Fig. 4 is also used mainly in the r.f. and i.f. stages. The handle and main piece is a 1/4-inch polystyrene rod, having a tuning slug on each end. One of the slugs is a powdered iron core from a discarded i.f. coil, the other is a copper slug salvaged from an old TV booster. The brass studs of each tuning slug were heated with a soldering iron and then forced into a smaller diameter hole in the polystyrene. Polystyrene softens under the heat, but regains its firmness as soon as it cools off. To permit easier insertion of the tuning slugs into the coil forms, round off the edges with sandpaper. Instead of the copper tuning slug a 1/4-inch round solid copper or brass rod can be used.

The tuning stick described can be used to great advantage in checking the alignment of r.f. or i.f. sections. Set an AM signal generator to the correct i.f. frequency of a particular coil and connect a v.t.v.m. across the second detector load resistor. Now insert the powdered iron core into the coil. If the meter reading decreases, the coil does not need additional inductance. Next insert the copper core. If the meter dips again the coil is tuned to the correct frequency. If the reading on the v.t.v.m. increases when the copper core is inserted, the inductance should be reduced. If the meter reading increases as the powdered iron slug is inserted, more inductance is required.

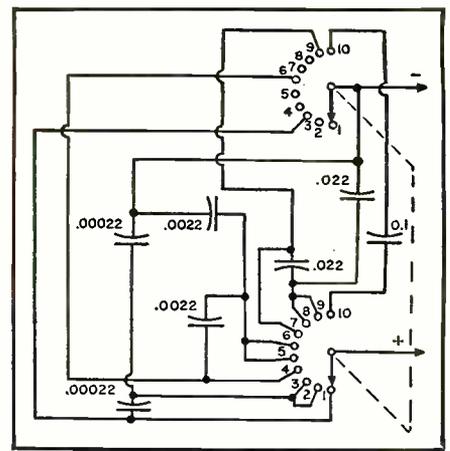


Fig. 2. A simple variable condenser box.

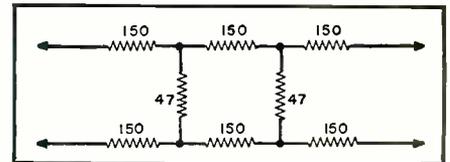


Fig. 3. Circuit of a 35 db attenuator.

In checking the performance of boosters and r.f. tuners this is particularly handy. There the adjustment can be done with a picture on the screen and the coils can be tuned for best picture and sound. Many r.f. tuners and boosters use fixed coils made of heavy copper wire. To increase or decrease the inductance squeeze or spread the turns as the tuning stick may indicate. When in doubt as to the operation of any coil, insert both slugs of the tuning stick and check for a reaction. If no change is observed, the circuit may be inoperative.

A type of construction which may be used for the tuning wand is a piece of large diameter spaghetti tubing with the slugs inserted in the ends.

The last item on our list of simple service aids is the attenuator pad (Continued on page 94)

Fig. 4. Tuning stick and condenser holder.


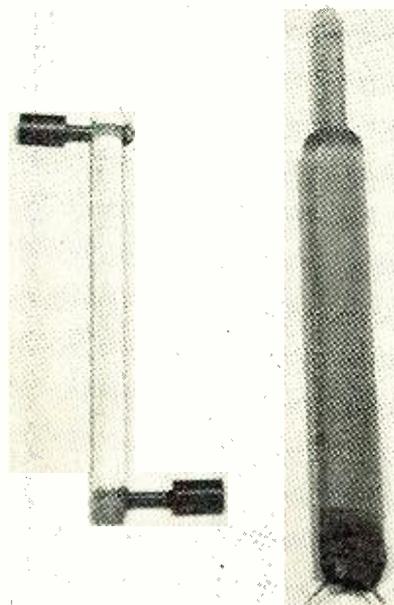


Fig. 5. Clip leads for parts substitution.

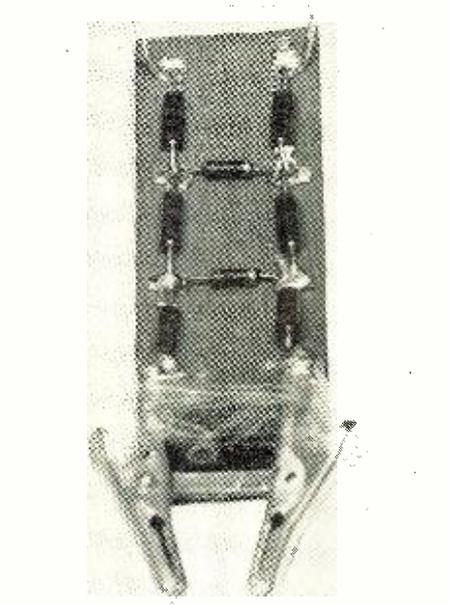

Fig. 6. Simple r.f. attenuator for TV work.



# SLIDE TUNING THE 75-METER LOADING COIL



The number of turns in the coil may be readily adjusted by means of the sliding clip to permit antenna to be tuned to exact resonance.

***Methods of adjusting the electrical length of a whip antenna to provide greater field strength.***

By

**JACK NAJORK, W2HNH**

**N**EARLY everyone who has tried mobile operation on 75 meters becomes a fanatic on the subject of antennas. Being no exception, the author digested most of the current literature on the topic and then started on a series of coil winding and whip hacking experiments that, to date, have ended up with the version to be described. Hams being what they are, it is doubtful that the "ideal" goal will ever be reached—however, the present design comes close to meeting all the major requirements and has proven itself in over five thousand miles of driving.

Initial tests showed that a quarter-wave, center-loaded whip was capable of excellent performance—provided it was correctly tuned and loaded. The final search thus narrowed down to a reliable and foolproof system of tuning this type of antenna. This is not nearly as simple as it sounds when one considers the requirements or, more specifically, our requirements. Electrically, the system should have high efficiency; be continuously tunable across the entire band; and finally, it should be capable of quick and accurate reset. In short, we wanted an antenna that we could hop out and retune during a traffic light change.

Mechanically, the antenna should be rugged enough to slap tree branches and underpasses at 50 mph without disintegrating; it should have low wind resistance, and it shouldn't make the XLY too unhappy from an aesthetic viewpoint.

Because of the very high "Q" of a short, electrically-loaded whip, the antenna must be critically tuned to the operating frequency if it is to take power and do a good job of radiating. Tuning is accomplished in this design by a loading coil whose inductance can be varied in one turn steps by means of a sliding clip arrangement.

Anyone who has probed an energized, center-loaded whip with a neon bulb soon learns that the loading coil is really "loaded" with r.f. Although there are "pros" and "cons" as to whether the coil does most of the radiating, we decided to get it up in the air high enough to clear the top of our *Studebaker* and thus give that r.f. a chance to go places if it had a mind to. However, a coil that high in the air stops a lot of breeze at high speeds and after picking up the remains of an earlier model, we learned that the wind resistance has to be low and the coil weight has to be small. So it appears a compromise is in order. You can either use a large, very high "Q" coil near the base of the antenna, or you can sacrifice some "Q" with a smaller coil and stick it up high.

As shown in the photograph, our version has the coil positioned about four feet above the base of the antenna. The coil is topped with a seven foot whip section for an over-all antenna height of slightly more than eleven feet. Many hams, seeing this antenna for the first time, look up and gasp at the height. However, our antenna is still in one piece after five thousand miles of highway and city driving so we consider this height entirely practical. Of course if you do most of your driving on streets lined with low tree branches you may want to reduce the height

somewhat. This will lower the radiation efficiency of the system somewhat but we're not at all sure that the station at the other end will notice the difference on his "S" meter.

The loading coil is wound on a piece of polystyrene rod one and five eighths inches in diameter and four inches long. Although it is not essential that poly be used, its heat-softening characteristics make it ideal in this application, as will be seen later. The coil is constructed in two sections. The top half, which is contacted by the sliding clip, is spacewound with 33 turns of #22 tinned, bare wire, while the bottom half is wound with 33 turns of #24 plastic insulated wire. The smaller wire size is used on the lower half in order to obtain the necessary inductance on the comparatively small coil form used.

A very neat job of space winding can be done by securing the wire and a length of twine to a support and then rolling the coil form in the hands so that the twine falls between wire turns. When this section of the coil has been wound, anchor the last turn to the form by pressing it with a hot, clean soldering iron. Do not remove the twine—yet! Next, take the soldering iron and anchor the wire to the coil form on either side of a vertical channel about half an inch wide. This is the portion of the top winding that is contacted by the sliding clip so be sure that each turn is individually pressed into the coil form with the soldering iron. These turns must be secure on both sides of the channel, otherwise the pressure of the clip will spread the wire and contact will become intermittent. Follow the same procedure on at least two other sections of the

winding on the upper length of the coil so that all the bare turns are permanently locked in place. Now remove the twine and wipe the coil lightly with a rag moistened with carbon tet. This method of securing the wire to the coil form is superior to cementing and is just about a necessity in this design unless a grooved coil form is used.

The coil is completed by splicing on and winding the insulated wire on the bottom half of the form.

Our coil had a measured inductance of 92 microhenrys and a "Q" of 240. It resonates with the eleven foot antenna at 3800 kc. with four turns shorted out. However, don't make the mistake of pruning your system to these exact specifications in the hopes of duplicating these conditions because the body contours of your car and the location of the antenna will affect the resonant frequency considerably. The most practical procedure is to wind the bottom of the coil full of wire and then peel off turns one at a time until the system resonates at the low end of the band with one or two turns shorted out by the clip. We allowed some spare inductance so that the antenna could be tuned down into the c.w. portion of the band but this is a personal choice that does not have to be duplicated.

The ends of the coil windings are brought to suitable fittings at the top and bottom of the coil, and these can be anything you can dig out of the junk box. We used a microphone connector collar bolted to the lower end with a 1/4"-20 bolt so that the coil and upper whip section can be demounted without the use of tools. A 1/4" brass rod was heat-fitted into the upper end of the coil body. The appropriate mating fittings are press-fitted into the whip sections and then soldered. The whip itself is a surplus 12' section of the type that screws together.


A piece of #14 phosphor bronze wire is used for the vertical clip guide bar. It is secured to the top of the form by a small, self-tapping screw, and a soldered connection is made from this point to the whip fitting. The clip is made from a small piece of phosphor bronze spring, bent and drilled as shown in the photographs. With the clip on the guide, the bottom end of the guide is secured to the bottom side of the coil form by pressing it directly into the body with a hot soldering iron. Don't use a self-tapping screw at this spot! We did, on the first model, and discovered that the several thousand volt potential between this point and the bottom turns of the coil resulted in an arc right through one eighth inch of the coil body. Because of this potential, the vertical clip guide bar should be spaced at least a quarter of an inch away from the bottom turns of the coil, otherwise you'll have some unexpected fireworks! Adjust the tension on the sliding clip by bending the upper part of the guide bar so that the clip fits snugly in place between adjacent turns.

The antenna is mounted on the car with a ball-joint fitting but a base

spring is not used. Unless you can find an unusually stiff spring, it is best to use none at all because whipping of the antenna, (or more specifically, back-swaying at high speeds) changes the capacity between the antenna and the car body enough to almost completely detune the system. Without the spring, the top of the antenna sways slightly but there is no detuning.

Low impedance coaxial cable is used to feed the antenna at its base. In our case, a twelve-foot section is run to the dash where the transmitter is located. The outer braid is grounded to the car body at both ends. A two-turn link, wound over the cold end of the final amplifier tank circuit, is used to couple the transmitter to the coax.

Tuning should be done in a location at least ten feet from trees, buildings, etc. Dip the final amplifier tank circuit to resonance with the coax disconnected at the transmitter end. Then connect the coax to the transmitter and adjust the clip on the loading coil until the final amplifier plate current rises. The effects of your body will completely detune the system, so you have to make an adjustment and then step back four or five feet and observe the effect on the plate current meter. It should be possible to pass through a plate current peak by sliding the clip one turn at a time (with power off the transmitter during the sliding) and the correct setting is the one that produces maximum plate current. When this setting has been reached, redip the final to tune out the reactance of the feed cable. If the coil tap is correct, only a very slight readjustment should be necessary. A large readjustment indicates that the position of the clip is incorrect, and in this case, loosen the coupling to the final amplifier tank and repeat the procedure. In most cases it will be found that the amount of

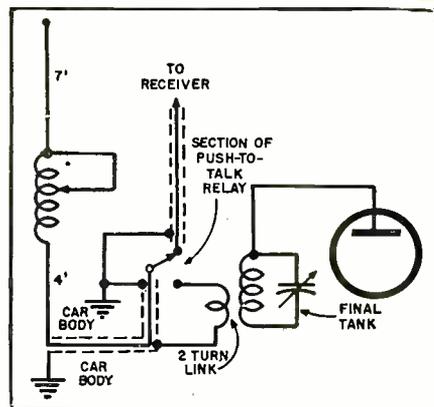

Coupling and antenna switching connections.

coupling used with the transmitter on the conventional half-wave home antenna will be much too great when the center-loaded whip is used because of the much higher "Q" of the latter system. If insufficient loading is encountered it can be corrected by increasing the link turns or by increasing the "C" and reducing the "L" of the final amplifier tank circuit.

If several crystals are available in widely separated sections of the band, the clip settings for each frequency can be marked on the coil with a dot of colored nail polish (i.e., "flamingo red" for 3817 and "purple passion" for 3910). With an eleven foot antenna, it is possible to QSY about fifteen kilocycles off the center frequency to which the system is originally tuned without causing the loading to drop off more than twenty per-cent.


The coil is waterproofed by cementing on a double layer of polyethylene "skin." This material is widely used in grocery stores to package apples, potatoes, etc., and is also marketed in five and dime stores for use as refrigerator storage bags. The vertical channel contacted by the sliding clip is, of course, left uncovered, but the remainder of the coil is entirely sealed. It is not necessary or desirable to apply cement to the entire coil for this operation. Cut the covering to size and then cement it only at the top, bottom, and cut-out portions of the coil. After this has dried, go over the joints at the top, bottom and cut-out sections of the coil with more cement to make sure that everything is sealed up tightly.

Results? 120 mobile QSO's to date, practically all non-scheduled, with W1, 2, 3, 4, 8, VE2 and VE3 during daytime driving in central New York State. Many of these stations were 100 to 300 miles away and the majority of them were raised by calling CQ. The transmitter runs 25 to 30 watts input to a 6L6, modulated by another 6L6.

Although the coil described was designed for 75 meters, there appears to be no reason why this type of construction cannot be used for a coil which can be resonated to the higher frequency bands as well. Right now, we're sold on 75, and we're trying to dope out a way to slide that clip without leaving the driver's seat. Any ideas?

-30-

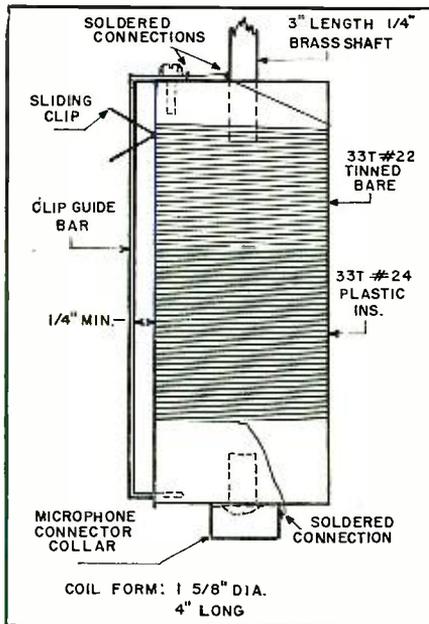**Mechanical details of the coil construction.**  
It is important that the construction be as rigid as possible for mechanical strength.




# AUDIO

# Simplified

By

DAVID FIDELMAN

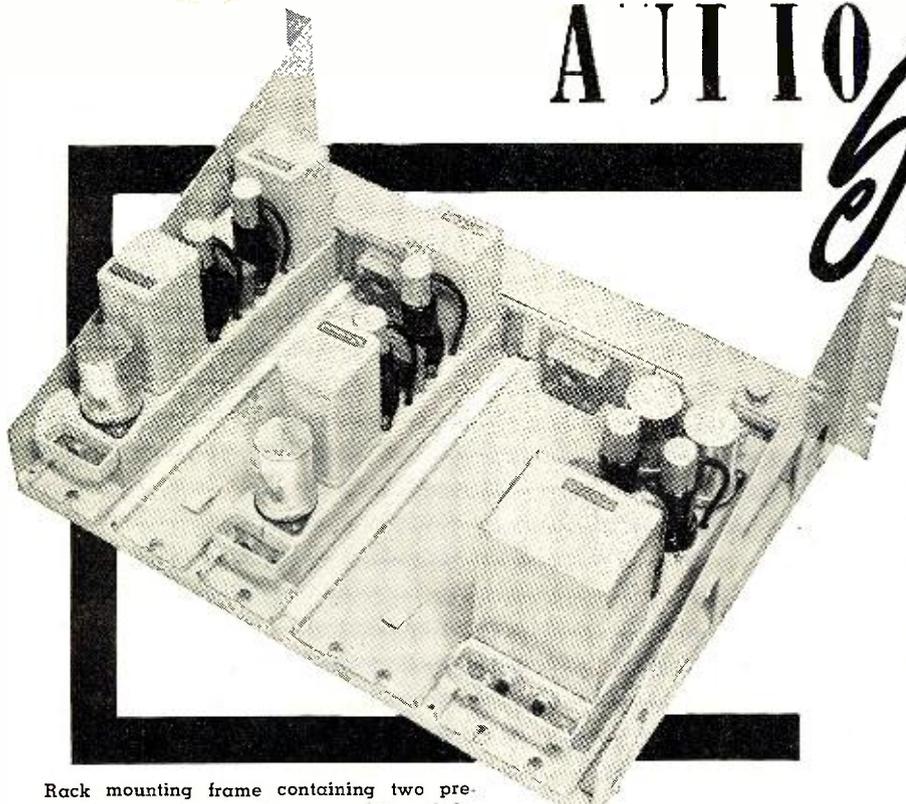

Rack mounting frame containing two preamplifiers and one voltage amplifier of the type described in the schematic of Fig. 8.

## Part 5. How plate characteristics and load lines are used in designing audio amplifier circuits.

IN ANY audio reproducing system, after the electrical signal from the microphone or pickup has been raised in level by use of a low-noise preamplifier, it must then be further amplified by a fairly high-gain voltage amplifier. This additional amplification serves two functions: (a) it increases the signal to the voltage necessary to obtain full power output from the power amplifier through the driver amplifier, or for further mixing, equalization, transmission over telephone lines, etc.; and (b) it makes up for any insertion loss introduced by the use of any mixing, equalization, or transmission units in the sound reproducing system.

The reproducing system may be set

up in a number of different ways, according to the specific requirements of the individual application. Mixing or equalization may take place ahead of the voltage amplifier directly after the preamplifier (or even in the preamplifier unit), or after one section of the voltage amplifier. In either case, the input signal to the voltage amplifier is at a higher level than the input signal to the preamplifier, therefore the introduction of noise in the voltage amplifier is not the major factor that it is in the preamplifier. In the voltage amplifier, the major requirement is high gain without distortion or instability.

The voltage amplifier consists essentially of a number of amplifier stages


whose total gain and output voltage meet the system requirements. The individual amplifier stages may be either triodes or pentodes—the choice depending upon both the requirements of the circuit and the individual preference of the designer (since there is still considerable discussion concerning the relative merits of triodes and pentodes). The procedure followed in the design of the amplifier is to start from the knowledge of the input and output voltages, the required input impedance, and the impedance of the load which the output of the amplifier sees. Then the various amplifier stages and impedance-matching circuits are designed for the required voltage gain and impedance.

### Voltage Amplifier Stage

The most important single component of any complete amplifier is the single vacuum-tube amplifier stage (since the amplifier is essentially a combination of single stages), and the correct design and operation of each stage is necessary for proper operation of the system. For any experimenting in sound and audio reproduction, it is essential for the experimenter to understand the basic operation and the fundamental principles of design of amplifiers, so that he can better understand the circuits with which he is working. He can then design more intelligently in construction of equipment, and will find it much easier to troubleshoot more intelligently and quickly in case of circuit failure. The design of the amplifier is done graphically by use of the curves of tube operation published by the tube manufacturer, and does not require the use of complicated mathematical formulas or extensive calculation.

The use of these curves in the design makes it possible to predict in advance what the performance will be, without the necessity of first building the circuit in order to find out whether it meets the requirements. The most important curves of vacuum tube operation are called the *plate characteristics*, which consist of a number of curves in which the plate current is plotted against the plate voltage, each curve being for a different constant grid-cathode voltage. These are the tube characteristic curves which are most

Fig. 1. Use of plate current characteristics and load line to design amplifier stage. (A) Plate current characteristics of a typical triode tube, showing curves of plate current against plate voltage for different constant grid voltages. Also incorporated on the graph is a load line representing voltage at plate of any tube connected to 300 volt "B" supply through a 100,000 ohm resistor. (B) An amplifier stage designed from the curves of (A).

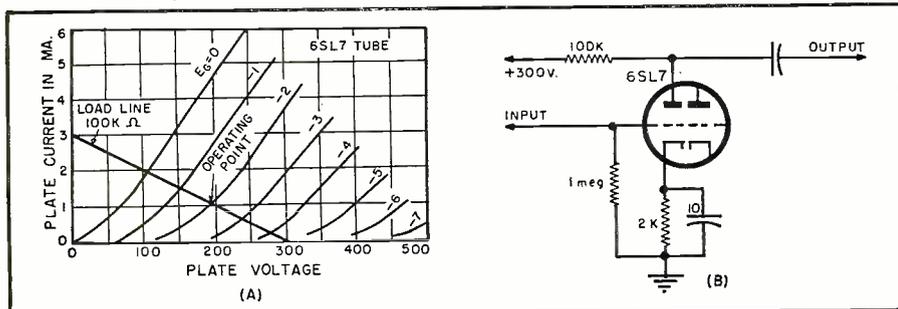

generally given by the manufacturers in the tube manuals, and are most often used in the amplifier design procedure. The plate characteristics of a typical widely used triode (one section of the type 6SL7 dual triode taken from the RCA tube manual) are shown in the diagram of Fig. 1A. These curves show the variation of plate current with plate voltage, for different constant values of grid voltage from 0 to -7 volts. The various tube factors (plate resistance, amplification factor, etc.) are determined from these curves.

In a graph of current plotted against voltage, consider the straight line which is drawn as shown in Fig. 1A. This line represents a resistance in series with the plate of the tube, and the line will be the same regardless of what tube characteristics are drawn on the same graph. Any point on this line shows the voltage from plate-to-ground for the particular current which is indicated. For example, when the tube draws no current the full supply voltage is on the plate since no voltage is developed across the resistor, and when the entire voltage is developed across the resistor then the voltage from plate-to-ground is zero. This line is known as the *load line*, since it represents the plate voltage of the tube for this specific value of load resistance.

If a load line is drawn over a set of plate characteristics of a specific tube, the resulting curves will give the operating characteristics of the tube for the particular power supply voltage and plate resistance which have been selected. Consider, for example, the set of plate characteristics and the load line which are drawn together in the graph of Fig. 1A. These particular curves represent a typical triode amplifier stage and practical circuit values which are widely used in audio amplifier design. The tube characteristics are those of Fig. 1A, and the load line represents a 100,000 ohm plate resistance for a "B+" voltage of 300 volts d.c. The load line is drawn by knowing the two facts that (a) when there is no current the voltage from plate-to-ground is 300 volts, (b) when the voltage from plate-to-ground is zero the voltage across the resistor is 300 volts, resulting in a current of 3 ma. through the resistor, and by connecting these two points with a straight line. All the points along this line then show the operation of the tube under these conditions. For example, if the grid voltage of the tube is selected as -2 volts, then the current through the tube is given by the intersection of the load line with the -2 volt plate current line, showing that the current is approximately 1 ma. and the voltage from plate-to-ground is approximately 200 volts.

This information can be used to design the amplifier stage shown in Fig. 1B. The grid-cathode bias voltage is obtained by means of a bypassed 2000 ohm resistor between cathode and ground. The effect upon the plate cir-

cuit of a signal voltage applied to the grid can be seen by taking the different points along the load line and observing the plate voltages and currents. Thus, a peak grid swing of +1 volt to -1 volt will cause the grid-cathode voltage to swing between -1 and -3 volts, and the voltage at the plate will swing from 155 to 245 volts—which is 45 times the grid signal voltage.

### Equivalent Plate Circuit

The circuit of Fig. 1B can also be redrawn in another way which makes it possible to predict the frequency response and output impedance of the amplifier stage without the necessity of building the circuit in order to measure it. This method of redrawing the tube circuit is shown in Fig. 4A, drawn to also include the grid input circuit of the following tube. The amplifier circuit has the same characteristics for the a.c. signal as if the voltage  $-\mu e_g$  were applied in series through a resistor equal to the plate resistance of the tube to the load circuit, which consists of the plate load resistor to ground and through the coupling condenser to the grid and grid resistor of the next stage. Also in the circuit are the plate-cathode capacity and the plate circuit wiring capacity to ground. The circuit of Fig. 4A is called the *equivalent plate circuit* of the amplifier.

The manner in which the equivalent plate circuit can be used to predict the amplifier performance can be seen from the three circuits shown in Fig. 4B, which are derived from the circuit of Fig. 4A. These circuits show the components which are important at

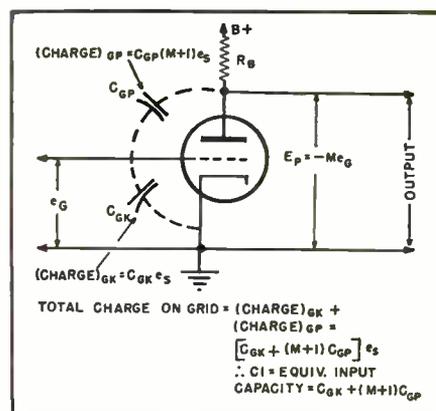


Fig. 2. Miller effect increase in input capacity due to amplification of the tube with the resistive plate load.


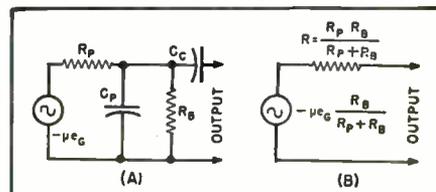


Fig. 3. Method of determining the output impedance of an amplifier. (A) Equivalent plate output circuit of the amplifier shown in Fig. 2. (B) The effective output circuit at the middle frequencies.

the low, the middle, and the high frequencies. At middle frequencies the series coupling condenser can be replaced by a short circuit and the shunt condensers by open circuits, leaving only the resistances in the circuit. The gain is then determined by the voltage divider composed of the  $R_B$  and  $R_p$  parallel combination in series with  $R_p$ . If the resistance of  $R_B$  is parallel with

Fig. 4. (A) Equivalent plate circuit of the amplifier stage shown in Fig. 1B, including the grid input circuit of the following tube. (B) Simplified forms of circuit of (A) which are accurate at low, middle, and high frequencies. (C) Frequency response at low and high frequencies due to shunt and coupling capacities.

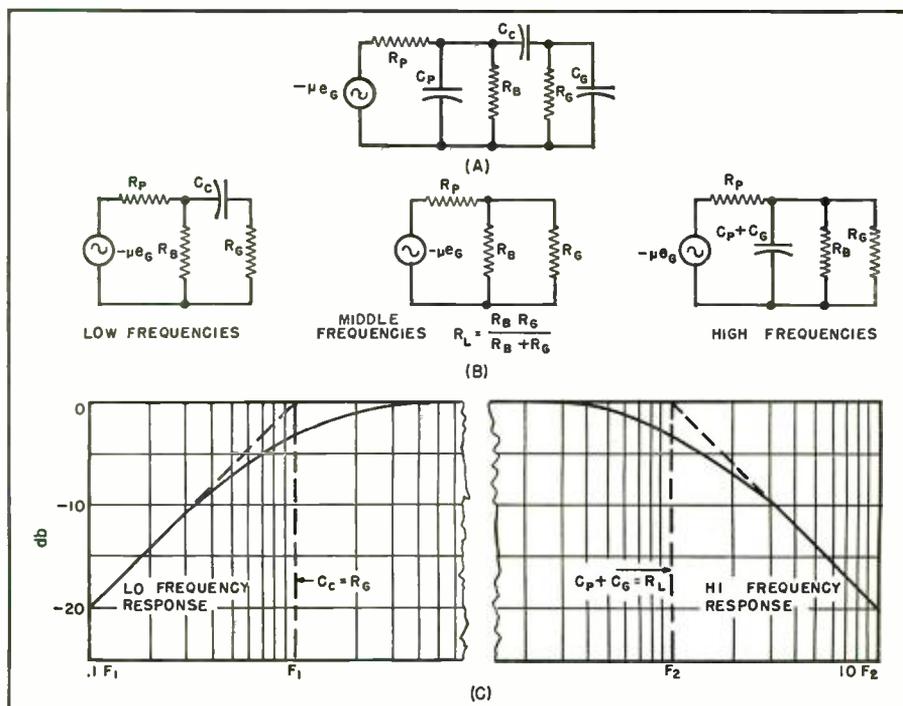

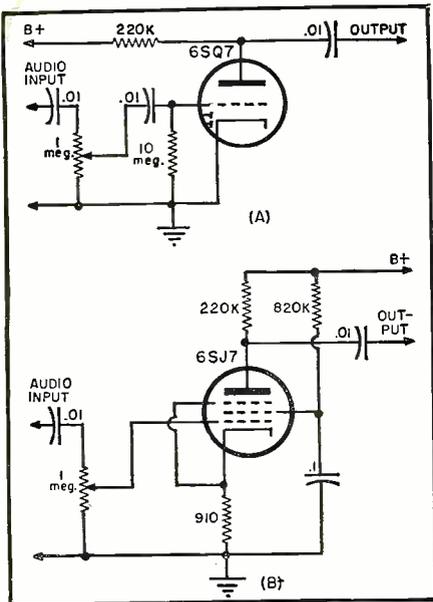


Fig. 5. (A) Typical high gain triode amplifier. (B) Pentode amplifier which can be used in place of the triode in (A) to provide an improved frequency response.

$R_o$  is calculated and called  $R_L$ , then the gain of the stage from grid input signal to signal applied to the next grid is equal to  $-\mu_e R_L / (R_p + R_L)$ . This value is negative, because the signal in the plate circuit of a vacuum tube is opposite in phase to the grid input signal.

At low frequencies, the impedance of the coupling condenser must be considered in series with the following

grid resistor. This impedance determines the low-frequency response of the amplifier circuit, since it forms one arm of a voltage divider whose output decreases as the condenser impedance increases from lower frequencies. The response is 3 db down at the frequency where the impedance of the coupling condenser is equal to the grid resistor, and approaches a falling off of 6 db for every octave below this frequency.

At high frequencies the shunt capacities must be considered. The shunting capacity is the total capacity to ground on both the plate and grid sides of the coupling condenser. This capacity determines the high-frequency response of the amplifier stage since it is in parallel with the shunt arm of the plate resistance/load resistance voltage divider and causes the output voltage to decrease as the capacitive impedance decreases for higher frequencies. The response is 3 db down at the frequency where the impedance of the total shunt capacity is equal to the combined resistance  $R_L$ , and approaches a falling off of 6 db for every octave above this frequency.

The effects of these capacities account for the frequency range limitations of resistance-coupled voltage amplifiers. The resulting frequency response due to these effects is of the type shown in Fig. 4C.

#### Miller Effect

An extremely important factor which imposes certain limitations on the practical design and choice of tubes in

audio amplifiers is the *Miller effect*. In the equivalent circuit of the amplifier, shown in Fig. 4B, it can be seen how the capacity in the grid circuit of the following stage affects the response at high frequencies. Thus, if the input capacity of the following stage is high, the effect on the high-frequency response may be considerable. This input capacity is not a constant of the tube and is different when there is a load in the plate circuit than when there is no load. This effect is known as the *Miller effect*. When there is a resistive load in the plate circuit of a tube, as shown in Fig. 2, the voltage on the plate is  $-M$  times the voltage on the grid ( $M$  being the amplification of the stage). The total charge on the grid due to the grid-plate capacitance and the potential difference due to the gain of the tube acts as if the capacity were  $(M + 1)C_{gp}$ . Therefore the tube has an input capacity of:

$$C_i = C_{gk} + (M + 1)C_{gp}$$

In high gain triodes this effect is quite large, whereas the Miller effect is negligible for pentodes because they have such a low grid-plate capacity.

As an example of the importance of the Miller effect, consider one section of a 6SL7 as a voltage amplifier.

$$C_{gk} = 3.4 \mu\text{fd}; C_{gp} = 3.2 \mu\text{fd}.$$

$$M = 41$$

$C_i = 3.4 + (41 + 1)3.2 = 137.8 \mu\text{fd}$ , which is 21 times the input capacity of  $6.6 \mu\text{fd}$ , with no load in the plate circuit. This is quite a high capacity, and if this input capacity is located in a high-impedance circuit (such as the plate circuit of a pentode amplifier stage, or a 1 megohm volume control), it will cause a serious loss of high frequencies. In the worst cases, this high frequency loss cannot even be compensated by equalization. For example, in a 1 megohm volume control the attenuation at 10,000 cps may vary between 0 and 10 db, depending upon the volume control setting, and no one equalization curve will effectively compensate for all volume control settings. The only practical method of eliminating the problems of the Miller effect is to avoid the use of high gain triode stages in high impedance circuits whenever good high frequency response is desired, and to design the circuit and choose tube types with this limitation in mind.

#### Design Procedures

From the information contained in the plate characteristic curves and the equivalent circuit of the amplifier stage, its performance can be quite accurately predicted. The actual details and arithmetic of these procedures, that is, the basic practical steps in selecting the circuit values for an amplifier design, together with a brief summary of the most essential points which have been described in the previous sections of this article, are presented in the following few paragraphs:

- (a) Gain of the stage is determined
- (Continued on page 136)

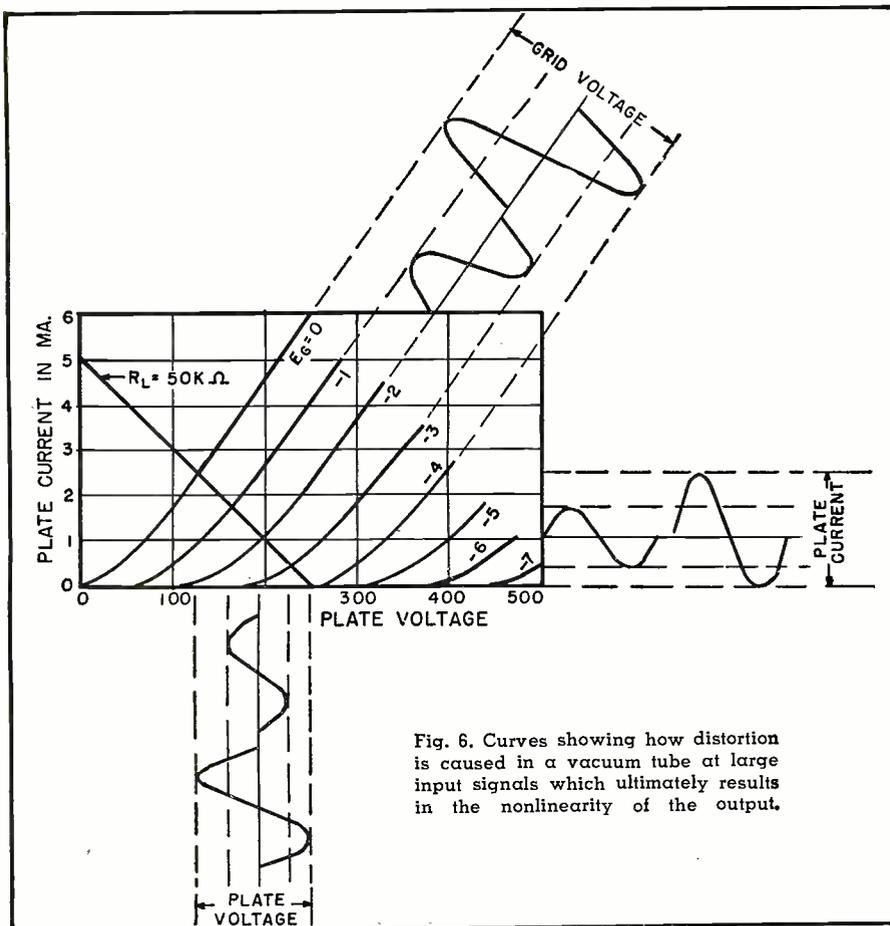



Fig. 6. Curves showing how distortion is caused in a vacuum tube at large input signals which ultimately results in the nonlinearity of the output.



# International

# SHORT-WAVE

Compiled by **KENNETH R. BOORD**

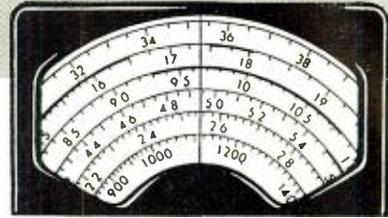

IT IS a pleasure this month to dedicate the *ISW DEPARTMENT* to radio in Japan. Our thanks go to Hal Stein, San Francisco, and to Isamu Yamazaki, chief of the International Broadcasting Section, Nippon Hoso Kyokai (Broadcasting Corporation of Japan), Tokyo, for this interesting data.

Mr. Yamazaki airmails that "our short-wave transmissions are made at present for two purposes—one is for the benefit of Japanese nationals in the Far East awaiting their repatriation to Japan (Far Eastern Service) and the other is for transmission to various key stations in Japan of the same programs sent on the air by NHK in Tokyo. All short-wave transmissions are radiated from the stations at Nazaki, Yamata, and Kawachi which belong to the Telecommunications Ministry.

A recent Associated Press dispatch from Tokyo announced that the Japanese Government will shortly resume overseas broadcasts of news, commentary, and music, beamed to North America, China, the Philippines, Indonesia and India. The transmissions are to be five hours a day in English and Japanese.

Current schedules sent by Mr. Yamazaki are—First transmission relay and communication for Domestic Service, JKH, 7.2575, Yamata, 5 kw., 1530-0900; JKI, 4.910, Nazaki, 5 kw., 1530-1715 and 0255-0900; JKI-2, Nazaki, 9.655, 5 kw., 1725-0245.

Second transmission relay for Domestic Service, JKJ, 7.285, Nazaki, 5 kw., 1530-0900; JKM, 4.940, Kawachi, 5 kw., 1530-1715 and 0310-0900; JKM-2, 9.695, Kawachi, 5 kw., 1725-0300.

Far Eastern Service, JBD, 9.505, Kawachi, 7.5 kw., 1530-0505 and 0255-1000; JBD-2, 9.560, Kawachi, 5 kw., 0255-1000; JBD-3, 15.225, Kawachi, 7.5 kw., 1915-0245; JBD-4, 15.235, Kawachi, 5 kw., 2200-0245, and JKI-4, 11.800, Kawachi, 5 kw., 1530-2145.

All communications should be addressed to International Broadcasting Section, Nippon Hoso Kyokai, Radio Tokyo Building, Tokyo, Japan.

NHK has 8 regional stations, 38 local stations, and 31 rebroadcast stations, covering 9,250,194 registered listening households as of June 1, 1951. Since an average of 4.5 listeners utilize radio in one household—according to a survey—approximately 55.8 per-cent of the Japanese nation has been served

by NHK. Except for rebroadcast stations and a few local stations, each station transmits two different network programs; the major part is provided by Tokyo, interrupted by local and regional broadcasts.

In March 1951, NHK observed its 26th birthday. Tetsuro Furukaki, president of NHK, says: "Since the termination of war, the Japanese radio has worked itself more and more into the life pattern of the people, and today it has become, for good or for evil, an indispensable part of our national life. . . . Our motto in the NHK is 'Radio Links Us With the World.' This is the sentiment that symbolizes what we do, for we feel that radio can be a powerful influence in establishing world peace and international brotherhood."

NHK officials point out that with the termination of the war, Japan made a new start on the road towards the establishment of a democratic nation. And that since governmental control on radio was lifted, NHK drew up new Articles of Corporation and began to put forth efforts towards improving and expanding its facilities with the idea of establishing a free and independent radio enterprise and of becoming truly a people's radio. In view of the importance of the radio in the construction of a democratic and peaceful nation, the Broadcast Law, designed to bring the radio in line with the welfare of the public, was passed in 1950 and enforced. The present NHK, based on this Law, succeeded to all the facilities and staff of the former Broadcasting Corporation of Japan. "It is now prerequisite for NHK to consider itself operated by the concerted will of the general public and to conduct broadcasts that are acceptable to the people."

A Japanese radio official summarizes like this:

"NHK's broadcasts can be heard all over Japan—in the hills, in the fields, in the cities and towns, and in the remote villages. The radio brings people together to enjoy collective listening.

(Note: Unless otherwise indicated, all time is expressed in American EST; add 5 hours for GCT. "News" refers to newscasts in the English language. In order to avoid confusion, the 24 hour clock has been used in designating the times of broadcasts. The hours from midnight until noon are shown as 0000 to 1200 while from 1 p.m. to midnight are shown as 1300 to 2400.) The symbol "V" following a listed frequency indicates "varying." The station may operate either above or below the frequency given. "A" means frequency is approximate.

The radio brings peace among the people. And the world culture is being diffused among the Japanese people through the radio. For the people, the day starts out with the radio and ends with the radio. The radio brings happiness and joy to the people. And that is connected with the path towards the construction of a peaceful Japan and, in a larger sense, towards the establishment of world peace."

Our best wishes go to the Broadcasting Corporation of Japan and all its personnel in their efforts to expand and strengthen the services of NHK!

\* \* \*

### New WRH Available

North American SWL's will be interested to learn that the new (1951-52) edition of *World Radio Handbook*, compiled by O. Lund-Johansen, Copenhagen, Denmark, is now available for \$1.50 postpaid from Ben E. Wilbur at his new QRA—1000 Connecticut Avenue, N. W., Washington 6, D. C. *WRH* is in *English*.


\* \* \*
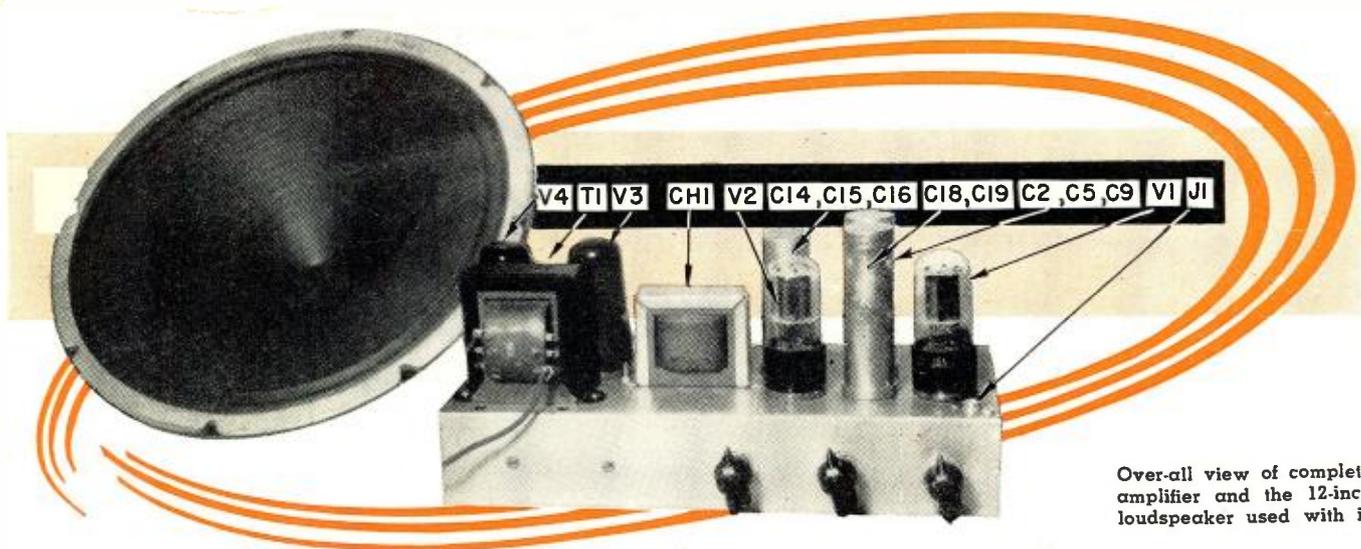
### This Month's Schedules

*Afghanistan—Radio Kabul*, 9.975, noted weekdays to 1150; Sundays to (Continued on page 118)

The Radio Tokyo (NHK) building in Tokyo. It is a six-story building with studios, control rooms, office rooms, etc. Programs presented in the studios are carried by land lines to the transmitting station. Plans are underway for construction of another building at the rear of this one to provide enlarged broadcasting facilities.





Over-all view of complete amplifier and the 12-inch loudspeaker used with it.

# A Compact High-Gain AMPLIFIER

By  
**LLOYD B. HUST**

*A low-cost and compact unit which has provision for both phono and microphone-tape head inputs.*

THE design possibilities of audio equipment are practically limitless with the wide variety of tubes and other components which the builder has at his disposal at the present time. Good audio equipment may range all the way from the small ultra-compact amplifiers used in modern hearing aids to the multi-watt jobs used for public address work for large outdoor gatherings. In fact, this might be termed the age of specialization as far as audio equipment is concerned. No longer is it necessary to rely upon one all-purpose amplifier for one's needs. The up-to-date sound shop will have several types of amplifiers available for many different types of service. One type will be suitable for large outdoor coverage, another will be suited for auditorium service where pickup from several microphones may be necessary, while still another type may be required for the recording studio. The serious experimenter may wish to specialize, to some extent, adapting his audio equipment to his specific need. If one takes into consideration his requirements for a particular type of amplifier, its design and construction need be neither difficult nor expensive.

The amplifier to be described here is a good example. The author needed a small, inexpensive, high-gain amplifier for microphone reproduction, the playing of phonograph records, and the playing of tape recordings. Because

compactness was necessary and because the design of the associated playback equipment made it necessary for the amplifier to be mounted very near to the phono pickups and tape playback head, it was decided that the conventional power transformer be eliminated from the amplifier. The mounting arrangements were such that if a power transformer were used, hum pickup would be intolerable.

The elimination of the power transformer introduced two other problems, however. One was the lower power output that could be expected if the output tubes were operated at line voltage. The other was the problem introduced by the difficulty of filtering the half-wave output of a rectified line voltage with its associated 60 cycle ripple, as compared with the ease of filtering the 120 cycle ripple from the output of a full-wave rectifier such as would be used with a power transformer.

The problem of lower power output was solved quite satisfactorily by using a voltage doubler circuit in which two 150 milliamperes selenium rectifiers were used. The fact that filter condensers of relatively high capacitance were used also helped to solve the second problem. Theoretically, the use of a voltage doubler circuit will provide direct current at a voltage nearly double that of the line. However, load conditions modify, to some extent, this

voltage rating. Measurement with a vacuum tube voltmeter showed the voltage at the input to the filter to be 210 volts. At the plates of the output tubes, 190 volts was measured. The line voltage at time of measurement was approximately 120 volts. These were full-load measurements.

In connection with the power supply it should be noted that resistors  $R_{22}$  and  $R_{23}$  are used to prevent damage to the rectifiers and associated equipment due to line surges with the resultant high peak voltages encountered. The use of these resistors does not materially decrease the usable voltage obtainable from the voltage doubler circuit. Also, it should be kept in mind that condenser  $C_{13}$  is not essentially a filter condenser. Its size does not materially affect the ripple content of the plate supply (filtering is taken care of by  $C_{18}$  and  $C_{19}$ ); its function is to discharge in series with the line voltage and hence bring about voltage doubling action. For that reason an increase in the capacitance of  $C_{13}$  may result in improved regulation and slightly higher voltage, but it will not aid much in the reduction of hum.  $C_{18}$  and  $C_{19}$  are rated at 30  $\mu$ fd., 300 volts, but if improved filtering is desired, 40 or even 50  $\mu$ fd. of capacitance can be used.  $CH_1$  is rated at 8 henries at 100 milliamperes, but it was found that the use of a 250 ohm, 10 watt wirewound resistor in place of  $CH_1$ , caused very little increase in the ripple content of the output.


It was obvious that the use of a conventional a.c.-heated series filament string would introduce hum problems, especially as relatively high gain was desired from the amplifier. It was found that the heaters of the tubes could be supplied with pure d.c. very easily and at low cost by using a third 150 milliamperes selenium rectifier with a filter condenser across each tube filament to ground. Four such condensers

were used:  $C_{14}$ ,  $C_{15}$ ,  $C_{16}$ , and  $C_{17}$ .  $C_{14}$ ,  $C_{15}$ , and  $C_{16}$  are parts of a three-section 150 volt electrolytic condenser with 20  $\mu$ fd. to the section.  $C_{17}$  is a low voltage unit—50  $\mu$ fd. at 25 volts—and it is used from the filament of the first 12SL7 ( $V_1$ ) to ground. This arrangement gives the greatest amount of filtering at the place where hum pickup would be most likely. It will be noted that each of the tubes draws 150 milliamperes of heater current and that the voltage rating of each tube is such that the total voltage drop across the string is approximately that of the line voltage. This set of conditions eliminates any necessity for dropping or shunt resistors. Since the filter condensers are of the "FP" multiple unit type and since the selenium rectifiers are compact and can be easily mounted, the entire power supply, both plate and heater, takes up very little space.

The amplifier as illustrated was built on a chassis measuring 3½" x 11" x 2". This size was desired because of the limited mounting space available for the amplifier in conjunction with the equipment with which it was to be used. If this extreme compactness is not desired, an extra inch in the width of the chassis will allow for somewhat greater ease of construction. However, this size chassis will accommodate all components very nicely if the parts layout, as shown in the photographs, is followed. Since the selenium rectifiers will run quite warm under full load, no ends were used in the chassis, and it was mounted in such a way that adequate ventilation eliminated any possibility of overheating.

At first, miniature tubes were considered for use with this unit, but it was found that the space saved by the size of the tubes was negligible since most of the bulk of the amplifier was due to other components. The first two stages are taken care of with a single 12SL7 which was chosen for its high gain characteristics. Since any high gain amplifier introduces the problem of "motorboating," care was taken to decouple each plate of this tube through a suitable resistor-condenser combination. It was desired to mix the signals from a microphone and phonograph using separate controls. However, it was not desirable to add a separate tube for this purpose, so this mixing was accomplished by using isolating resistors  $R_8$  and  $R_{10}$  in their respective control circuits. This method gives very satisfactory results and very little interaction between controls is noticeable.

Although all ground leads are brought to the chassis—a practice not always followed in high-gain amplifiers—little hum appears to be picked up in this way. This is probably due to the absence of a.c. gradients in the chassis due to the d.c. filament supply. However, to guard against ground loops, etc., all grounds for each tube were made at one common point, that is, all grounds for  $V_1$  were made at one point on the chassis, all grounds for  $V_2$  at another point, etc. Since the amplifier

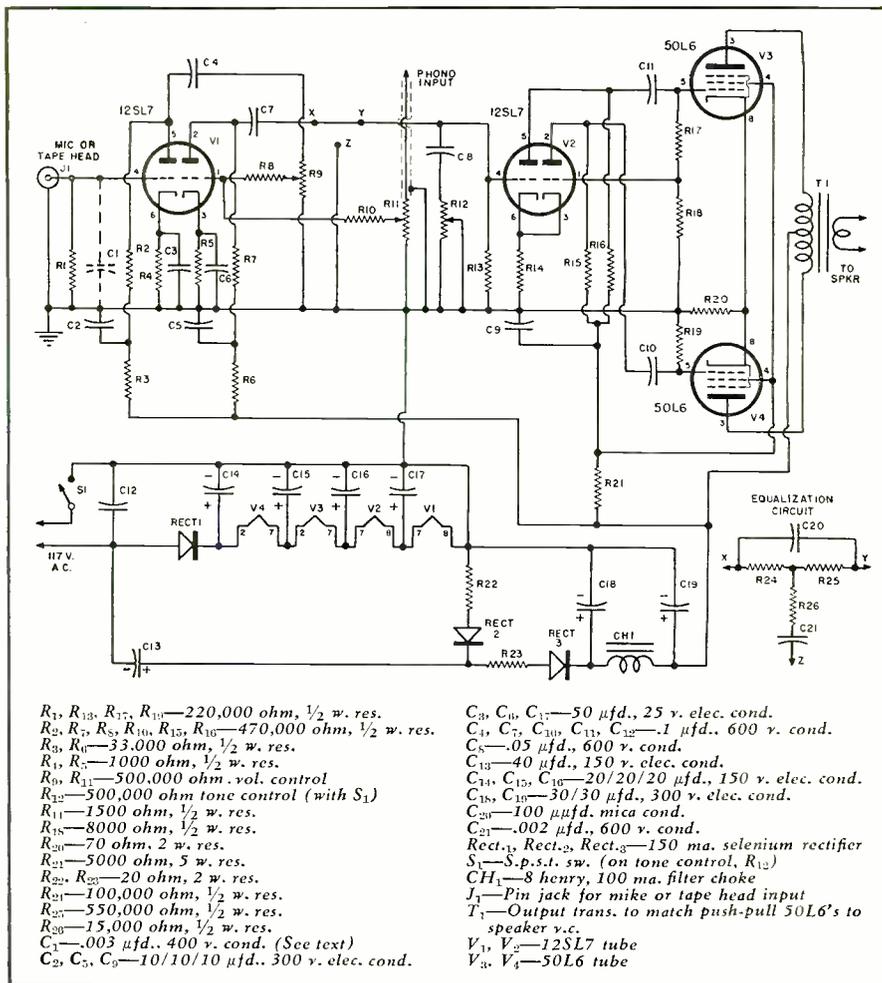


Complete circuit diagram and parts list covering the high-gain amplifier unit.

was to be mounted in a wooden case and the mike and phono plugs mounted on the panel of the case, a pin plug was used in the chassis to take the mike lead from the jack on the case, and a shielded wire was run from the chassis to the phono jack on the case. The builder can follow this procedure or he can mount jacks on the chassis, depending upon the application of the amplifier.

It was assumed in writing this article that most of the readers who might be interested in the construction of the amplifier would need such an amplifier

for mike and phono work only. For that reason, the schematic is shown without equalizing circuits, as those needed will vary with the various equipment used. However, plenty of gain is available to take care of any loss introduced by an equalizing circuit should the builder desire to use one. The insert accompanying the schematic diagram of the amplifier shows one type of equalizer which can be included if desired. Since this amplifier is used to play back tape recordings, the equalizer was inserted in the author's  
(Continued on page 140)

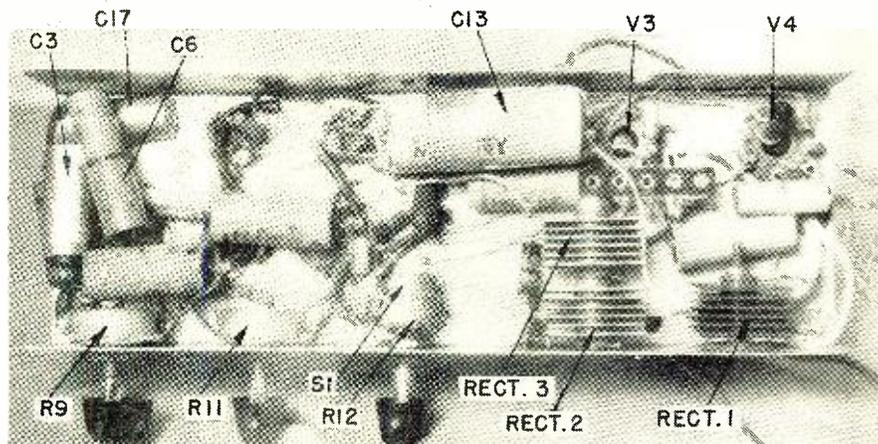
Under chassis view of amplifier with the principal components identified.



# ARTIFICIAL HANGOVER

## In Audio Circuits

By  
**GLEN SOUTHWORTH**

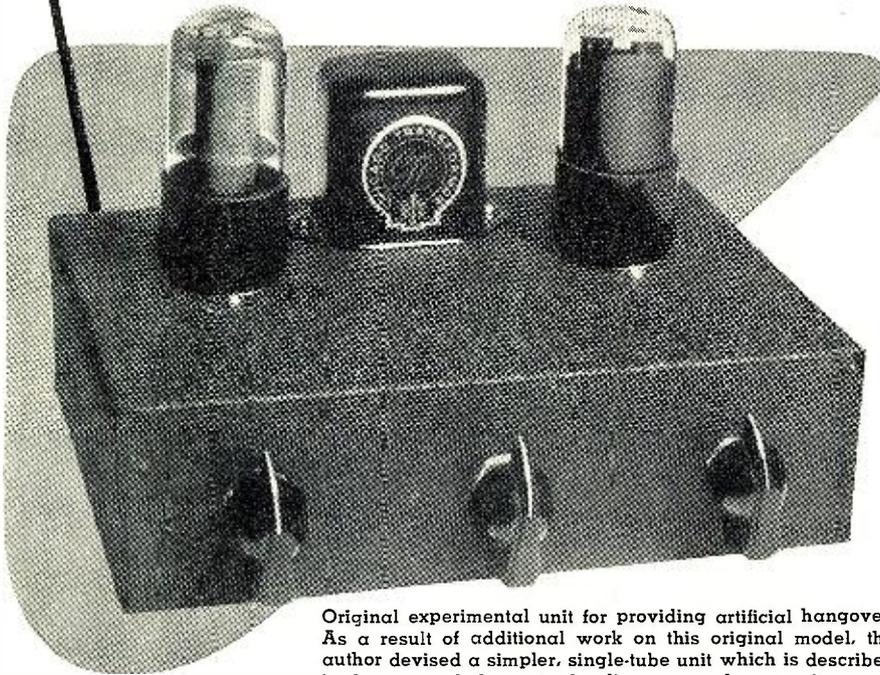

Original experimental unit for providing artificial hangover. As a result of additional work on this original model, the author devised a simpler, single-tube unit which is described in the text and shown in the diagram on the opposite page.

**Design data on a novel experimental unit. Controlled hangover adds depth to tonal quality of your system.**

**S**INCE the earliest days of formal music reproduction one of the most serious problems facing both the musician and listener has been that of proper acoustics. The concert hall must be considered as more than a device to keep out the weather inasmuch as it can strongly affect both the audibility and the tonal character of the instruments playing therein. In the home reproduction of music this factor is a serious though often little recognized problem.

In considering speech or music in terms of the relative audibility of various frequency ranges, attention must be paid to the fact that the ear judges the apparent strength of sounds on the basis of the average power contained in the tonal envelope rather than the peak power produced. As a result, a sound of very high intensity but short duration may produce no greater audible effect than a tone of relatively low peak intensity produced for an appreciable interval of time. This is a very important fac-

tor in musical reproduction or the enjoyment of live music, inasmuch as the ratio of peak-to-average power of virtually all orchestral instruments is relatively great. The result of this factor is that the audibility of an orchestra and the apparent balance between various instruments is very strongly influenced by the additional average power content given to tran-

### ADVANTAGES OF ARTIFICIAL, CONTROLLABLE HANGOVER

CORRECTION FOR ROOM ACOUSTICS  
CORRECTION FOR NOISE LEVELS, NONLINEARITY, VOLUME LEVELS  
CAN IMPROVE CHARACTER OR QUALITY OF INSTRUMENTS  
CAN GIVE CORRECTION FOR LACK OF TRANSIENT RESPONSE IN LOUDSPEAKERS  
GIVES GREATER SPEAKER AND AMPLIFIER EFFICIENCY  
REDUCES EFFECTS OF MODULATION DISTORTIONS  
CAN IMPROVE APPARENT SIGNAL-TO-NOISE RATIO  
CAN PRODUCE INCREASED APPARENT DYNAMIC RANGE  
SMOOTHS OUT AUDIBILITY VARIATIONS CAUSED BY RESONANCES  
ACTS AS A TONE CONTROL AFFECTING ONLY TRANSIENT WAVEFORMS

sients by the acoustic "hangover" or echo produced by the acoustic environment. An example of this is shown in the accompanying diagram in which it will be noted that a linearly damped wave train of ten cycles will contain five times the average energy as a pulse of a single cycle, even though the peak power handled is no greater.

Aside from the additional emphasis

of certain transients another beneficial result may be obtained from good acoustics. When listening to live music under conditions in which no hangover is present, such as an outdoor concert, a pronounced difference in the character of various instruments can be noted. In the case of instruments producing relatively strong modulations, such as the percussion, tubas, etc., the nonlinear characteristics of the listener's ear may cause him to hear "sidebands" or undesirable frequencies considerably removed from the fundamental tone of the instrument. Virtually all of the instruments which produce acoustic output in the lower octaves will generate modulated wave trains and due to the greater sensitivity of the ear to high frequencies the upper sidebands may produce the greatest audible effect, with the result that the listener may perceive negligible low register output in the music. A good concert hall will tend to reduce the audible effects of steeply modulated wave trains, due to the relatively long decay period of the room which tends to demodulate the wave train, and thus makes possible a more accurate perception of the fundamental tone generated by the instrument.

In considering home reproduction of music a rather complex problem is presented in that for optimum reproduction the original sound should be matched in character to the acoustics of the room in which it is to be reproduced. Much of present day program material would be thoroughly acceptable if played over high quality equipment in a large hall, but is greatly out of place if played over the same equipment in a small living room. One tentative solution to the problem of the small listening environment, currently offered by some American and European recording companies, is to make the original pickup with a microphone placed near the rear of the concert


hall. In this way the low frequency decay characteristics of the original hall are included in the recording and tend to compensate for the lack of low frequency reinforcement in a small living room. Although representing a distinct improvement there are several possible drawbacks including interference between the two sets of acoustics and the need for good linearity in the reproducing chain.

hall. In this way the low frequency decay characteristics of the original hall are included in the recording and tend to compensate for the lack of low frequency reinforcement in a small living room. Although representing a distinct improvement there are several possible drawbacks including interference between the two sets of acoustics and the need for good linearity in the reproducing chain.

Once it is realized that both musical character and the apparent balance between various frequency ranges depends to a very large degree upon the relative duration of transient sounds, then it becomes obvious that an extremely useful technique in correcting for acoustic deficiencies may be obtained by introducing artificial, controllable decay characteristics in the reproducing system. Such a system may be easily devised using an electrical delay network and feedback system closely analogous in operation to the effects produced by conventional acoustic environments. A system of this nature provides a new and useful type of "tone" control, which has only incidental relationship to the conventional variable equalizer, and which appears to more closely produce the effects desired by the listener's ear.


Up to the present time "hangover" in an audio system has been judged undesirable due to the fact that it may take several objectionable forms. One of the primary examples of this is in the case of a sharply tuned circuit, either electrical or mechanical, which tends to produce hangover emphasizing only a single frequency. This produces an unwanted effect and is additionally aggravated by the fact that such circuit elements often can be shock-excited into ringing by an unrelated tone. Similarly, such circuit elements often require appreciable time to build up to maximum amplitude, with the result that the initial portions of a transient wave train may be highly distorted.

When circuits are designed specifically for the purpose of producing hangover, the previously mentioned characteristics may be eliminated. Smooth decay characteristics may be obtained over an appreciable number of frequencies, there are no ringing resonances to be shock excited, and very little distortion of the initial cycles of the transient is produced. A very simple circuit for producing controlled hangover over a limited frequency range is shown in the accompanying diagram. The circuit shown is a variation of the little known phase delay oscillator. The principle of operation is that the output signal is delayed at least one-half cycle and then fed back to the input. The effect produced is quite different from conventional positive or negative feedback, wherein only the polarity of the signal which is fed back is altered. In the phase delay system a signal will continue to recirculate through the amplifier for a period of time after the original excitation has ceased. The length of time that the signal will continue is dependent upon the gain of the feedback loop, which of course can be made greater than unity at a given frequency, and in which case sustained oscillations will take place. In the circuit shown, a simple three element RC delay network is used to obtain artificial delay characteristics over a limited frequency range. Networks handling a wider range of frequencies

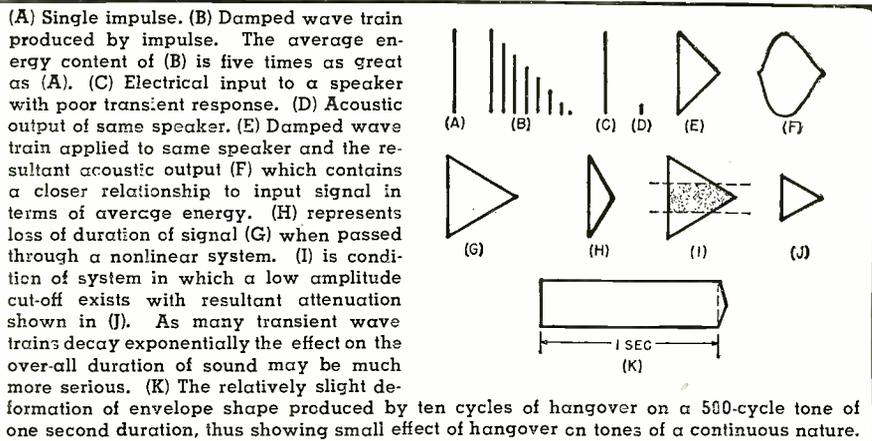

may be devised but require additional gain and circuit complexity. Ideally, a circuit should be available to produce 180 degrees or more constant phase shift over the entire audio range without any attenuation, as this would allow hangover to be applied to all frequencies simultaneously. In practice, however, it will more usually be desired to emphasize certain frequency ranges to fill in "gaps" in the hangover pattern of the acoustics. In the case of small rooms, one of these gaps will be in the region below about two or three hundred cycles where the dimensions of the room are insufficient to offer any sort of reinforcement. Regarded from this standpoint, a rationalization appears to exist for the popularity of some commercial radios in which strong cabinet and loud-speaker hangover produces the semblance of some low frequency response in small rooms. The results produced by the electronic hangover method are much superior and make it possible to get good, clean, audible bass reproduction in small areas without resorting to extremely high volume levels, conventional bass boost circuits, or other methods.

In designing a delay network for an artificial hangover system, a phase shift of 45 degrees per section will occur when the reactance of the condenser leg is equal to that of the resistive leg and increases with an increase in condenser reactance although the output voltage available from the network will decrease. In the one tube circuit shown, the circuit elements are proportioned so that hangover takes place below 200 cycles. If it were desired to introduce hangover in the high frequencies, for example around 2800 cps in order to emphasize the "brass" instruments, then the circuit elements of the delay network should be altered until the reactance of the capacitive elements is about equal to that of the resistors at that frequency. With the circuit shown, it appears to be desirable to use dissimilar elements in the three legs of the delay network, both to get operation over a wider frequency range and to reduce the loading effect of one section on the others. Similarly, with the circuit shown, it should be noted that

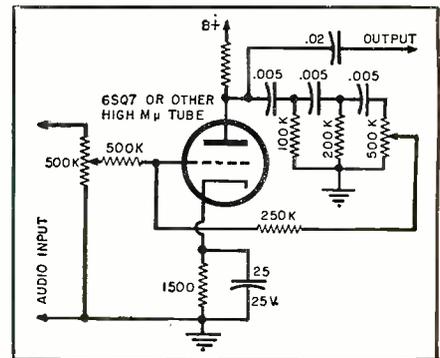


Schematic of simple one-tube circuit for obtaining controllable hangover over a limited frequency range. Circuit constants shown are for the range below 200 cycles.

the frequencies above the point of operation of the phase shift network are fed back essentially 180 degrees from the input, with the result that they suffer attenuation.

Circuits with phase delay effects sometimes exist in conventional amplifier systems and may give the effect of superior bass reproduction due to the hangover produced. One example of this is the case of an amplifier using inverse feedback over several stages having small coupling condensers. Another example is the multi-stage amplifier in which a relatively small capacity is used in the plate filter circuit and insufficient decoupling is present. In order to prevent this effect, if it is considered undesirable


(Continued on page 103)

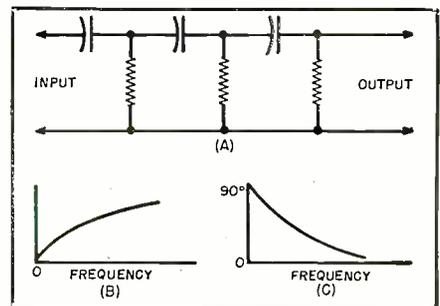(A) Simple form of delay network. Phase shift per section equals 45 degrees when reactance of condenser and resistor is equal. (B) Gain characteristics of the phase shift network (1 leg). (C) Phase characteristics of one leg of delay net.



# Mac's RADIO SERVICE SHOP

By JOHN T. FRYE

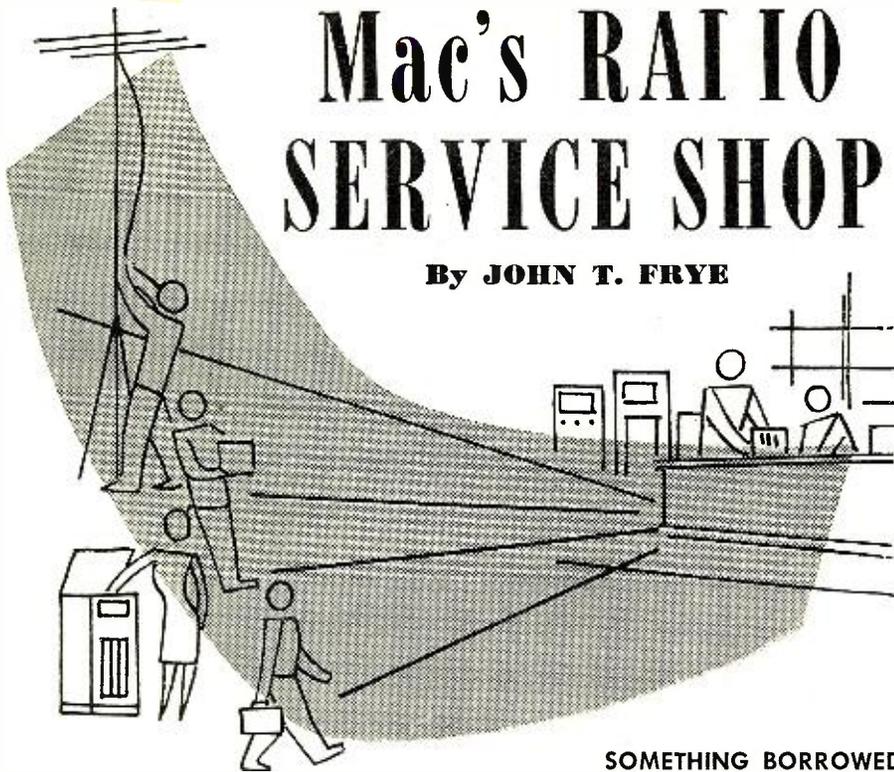

## SOMETHING BORROWED

**“W**HEW! What a day!” Barney exclaimed as he stamped into the service shop brushing the snowflakes from his wool jacket. “If it keeps on snowing like this all day, a man is going to have to have a dog-team to get home tonight —s-a-a-y,” he broke off as he stepped into the service department, “what have you been up to over the weekend? I can’t tell if I’m in a radio store or a barber shop! Where did you get all that mirror behind the bench?”

“Like it?” Mac, Barney’s employer, asked with a self-satisfied grin. “A little barber shop over on Seventeenth Street just closed up, and I bought the big mirror very cheap because of a couple of small flaws in it. After I had these cut out, I still had left two mirrors six feet long and two-and-a-half feet wide. That is just right to give us a continuous mirror behind the whole length of the service bench.”

“I’ll say I like it,” Barney exclaimed as he leaned forward for a closer admiring inspection of his reflection. “It will be a real pleasure to do servicing with a handsome devil like that working opposite me all day long.”

“All right, Narcissus; but that was not quite the idea,” Mac drawled. “I simply grew tired of squinting into a small mirror and trying to get a good view of a TV screen while I was making adjustments on the set. No matter how hard I tried, I never seemed to be able to tilt the mirror so that I could see the exact corner of the tube I wanted to see. Now we’ve really got that whipped.”

“Yeah, and that mirror will be the old mustard for working on record-changers,” Barney pointed out. “When the changer is sitting on a stand on the bench, a guy will be able to see what is

going on on both sides of the mechanism at the same time; and believe me with a lot of changers these days, you almost have to be able to do just that.”

“There’s still another good feature I’ve found out,” Mac added. “You know how tools and screws and parts dearly love to hide by snuggling up against the far side of a chassis on which you are working, don’t you? Well, they won’t be able to do that on this bench. With that mirror to let you see the surface of the bench from dozens of angles, not even a knob set-screw can hide. It is almost as good as having an extra eye on the end of a stick that you can poke around behind the chassis.”

“That’s a gruesome way of putting it,” Barney commented.

“That’s not the only haul I made at the defunct barber shop,” Mac said over his shoulder as he disappeared into the storeroom. “Take a look at this,” he said as he reappeared pushing what looked like the granddaddy of all flower stands. “The guy had a dilapidated old barber chair that he said I could have if I wanted it; so I brought it along, discarded the chair part of it, mounted this thirty-inch-square platform solidly on the old chair-supporting bracket, and then put those four heavy-duty casters underneath the base.”

“Fine, but what’s it for?”

“For holding a TV chassis while you’re working on it,” Max explained. “That weighted base makes it almost impossible to push over; the platform can be pumped up or let down through a range of several inches so that it will be just the right height for comfortable working; and the set can be easily twirled around to any position. Instead of having to drag a heavy chassis all

over the work-bench, we simply roll this dolly up to whatever instrument we want to use. When we need to make adjustments both above and below the chassis in rapid sequence, the set is placed on its side on the platform and then any part of it is easily and comfortably accessible simply by turning the platform.”

“Let me try it,” Barney begged as he sat down on the platform and whirled himself around. “I always did want to do this with a barber chair but never got the chance. Wh-e-e-e! This is fun! Did you steal any other ideas from the barber shop?”

“No, but I’ve been snooping around some other ‘service’ concerns in search of tools or ideas that I could borrow for doing radio and TV service, and I’ve come up with several that are well worth adopting. Take this jeweler’s loupe, for example,” Mac said as he screwed the black magnifying eyepiece into his eye-socket and peered owlishly through it at his assistant. “It really is the thing for finding a broken coil end, for discovering a tiny chipped place on a jeweled pickup needle, or for examining a TV tuner mechanism for dirt and corrosion. This one focuses at a distance of about five inches from the eye, which my jeweler told me would be the best for all around work; but they come in various powers. I think that we shall need an eye-aid of this sort more and more in the future. The Signal Corps admits that much of its present effort is directed toward miniaturization of equipment. Judging from the few samples of this effort we have seen in magazines, the eye is going to need all the help it can get to see trouble in the midget components and printed circuits that will go into civilian sets in the not-too-distant future.

“And here is another little sight-aid I picked up from the doctors and dentists,” he went on as he self-consciously slipped on a head-reflector and carefully adjusted the mirror so that it shined directly into Barney’s blinking eyes. “One thing a technician never has enough of is hands, and when all ten of your fingers are busy in a dark corner of the chassis this handy little gadget will light up that corner just as well as you could do with a third hand holding a flashlight.”

“Yes, Doctor,” Barney mockingly agreed.


Mac slipped off the reflector and picked up three shiny little steel rods. “You probably have seen something like these before,” he said to Barney. “They are the instruments the dentist uses to break loose the calcium deposits from teeth, and they are surprisingly strong.”

“I’ll say they are,” Barney agreed with feeling. “I’ve had a dentist lift me right out of the chair with one of those nasty little cusses.”

“Their toughness and small size makes them ideal for working over loose tube socket contacts, bending switch contacts back in place, and per-

*(Continued on page 134)*

# CRYSTAL DIODES In Modern Electronics

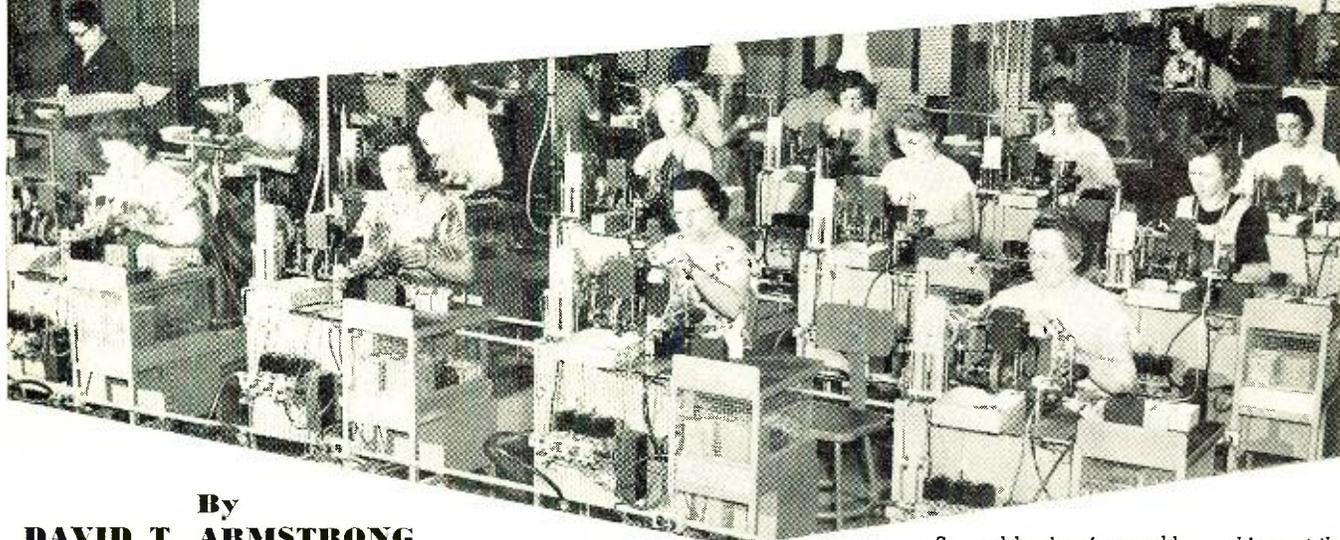

By  
**DAVID T. ARMSTRONG**

## *Part 4. Various applications of germanium crystal diodes as employed in present-day FM circuitry.*

Several banks of assembly machines at the Clyde, New York plant of General Electric Company. This factory is devoted exclusively to the manufacture of germanium assemblies and other similar products.

IT IS assumed here that the reader has a basic understanding of FM and that he is familiar with the function of limiters, frequency discriminators, and ratio detectors. These are the important parts of an FM circuit in which crystals are beginning to play a significant role. Only those aspects of circuit considerations will be treated here which deal specifically with the application of germanium diodes to functions heretofore performed entirely by diode tubes of the 6H6 and 6AL5 types.

Crystals function exceptionally well in any type of FM circuit, on i.f.'s ranging from the 4.5 mc. of the intercarrier sound system, through 10.7 and 25.75 mc., to the new 44 mc. frequency now coming into use in modern television receivers. The FM section may be a distinct entity of an FM receiver, or it may be the FM sound system in a modern television circuit. The material presented here applies equally well to any type of modern FM circuitry.

### **Limiter Circuits**

One of the basic requirements of an FM system is a limiting device to eliminate amplitude variations before they reach the detector. The function of the limiter is to remove amplitude modulation and to pass on to the detector a frequency modulated signal of constant amplitude. To operate

successfully, the limiter must be supplied with a sufficiently large signal voltage so that the amplitude of its output will not change with rather wide variations in signal amplitude. Noise, which causes little frequency modulation but much amplitude modulation of the received signal, is virtually wiped out in a limiter stage. Automatic volume control may be used with an FM receiver, but when a limiter is operating properly, a.v.c. is neither necessary nor desirable.

The limiter is part of the final i.f. amplifier stage; its main function is to remove amplitude variations which might reach the detector and appear as distortion in the audio output. The limiter, then, is a gate which removes amplitude variations from a signal above a predetermined level and passes on a signal that is constant in amplitude.

The positive and negative peaks of the FM signal will be truncated and flattened. See Fig. 1. This does not introduce distortion into the FM signal as it might in an AM signal because the modulation component or intelligence is contained in the frequency deviations of the signal and not in the amplitude variations of the signal. Frequency deviations due to modulation are not affected by limiter action.

The actual FM response curve is neither ideal nor flat topped. Hence the

various frequencies making up the total frequency deviation will not have the same relative amplitude at the input to the limiter. The center frequency and the frequencies close to it will have greater amplitude than those considerably removed from the center frequency due to the action of the i.f. tuned circuits. This is demonstrated in Fig. 2. The unequal amplitude of the various frequencies appearing at the input to the limiter would cause severe distortion if something were not done in the receiver to compensate for it.

A limiter is sometimes regarded as a device for removing all noise. This is not so. A limiter will function efficiently (but not perfectly) when the voltage level (amplitude) at the input to the limiter of the greatest frequency deviation component (this is the frequency  $\pm 75$  kc. from the mean frequency) is greater than the limiting level. Limiter output will be constant when a total band of 150 kc. is passed at a constant level, for then all the frequencies making up the total deviation will be reproduced in their proper relation, and without distortion due to AM or random noise.

The limiter characteristic represented by the graph at A in Fig. 2 will permit AM distortion because the i.f. signal is below the limiter level. Note that the limiter level is gauged by the characteristic curve of the voltage-fre-

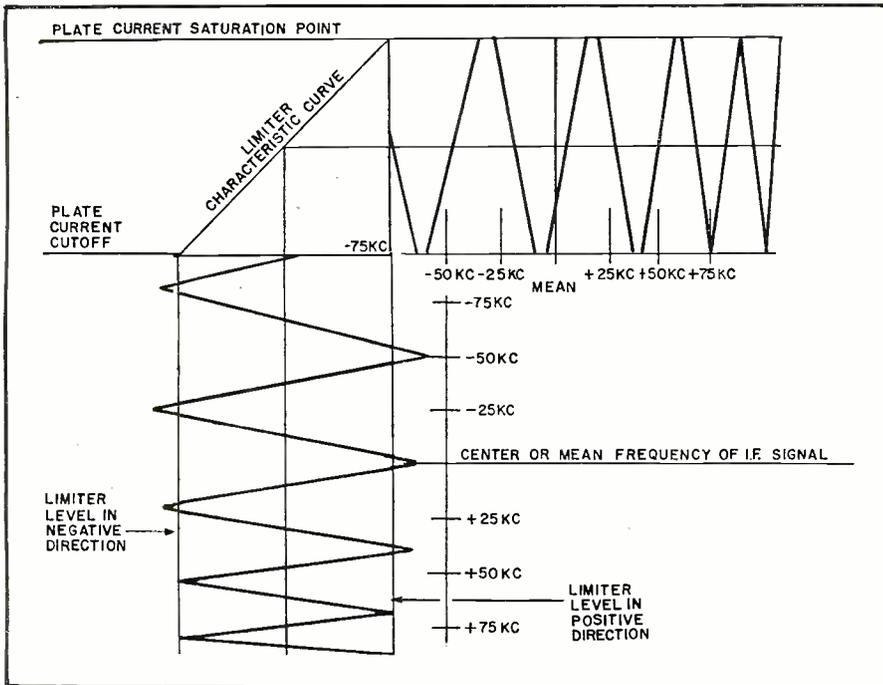


Fig. 1. Limiter action for a strong i.f. signal. Note that the amplitude of the input wave at the highest frequency deviation components of the FM wave is above the limiter level, and that the input level of the i.f. signal over the entire range of the frequency deviations is above the limiter level. Also note that positive and negative peaks of the output FM wave are truncated. The output of the limiter is constant over the entire range of the frequency deviation.


quency graph. The signal at B will permit no distortion because the lowest signal input level is above the limiter level. Hence all AM components and/or random noise are "hedge

clipped" by the action of the limiter.

#### Diode Dynamic Limiter

Any residual amplitude modulation and noise riding the FM wave should

Fig. 2. Effect of limiter action on varying limiter input signals. (A) Noise voltage reproduced in the output of limiter. (B) Noise is removed by limiter action. Note that when the input level of the i.f. signal over the entire range of frequency deviation is above the limiter threshold, as in (B), no noise voltage is reproduced in the output of the limiter but when the input level of the i.f. signal is below the threshold of limiter action, the limiter cannot function and the noise will be reproduced as shown in (A).

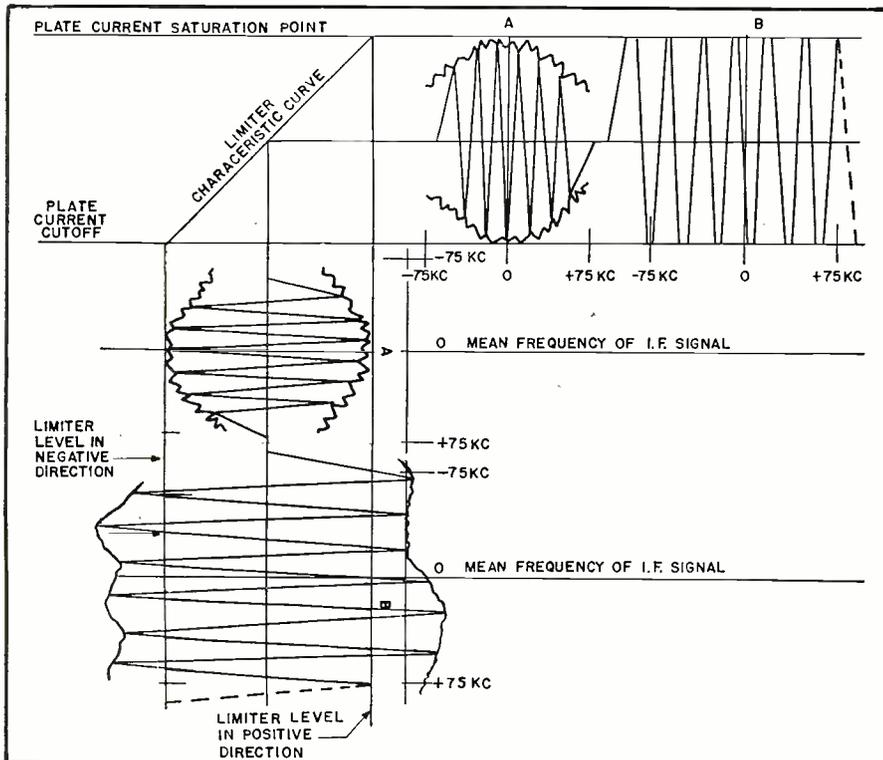

be suppressed. The limiter component desired must be an effective supplement to the action of the FM detector to reduce random noise and AM interference. This is necessary because a balanced discriminator completely suppresses AM at but one frequency, and a ratio detector is critical to align and balance. Maximum AM rejection may not occur at that alignment adjustment which provides the most desirable linearity.

It is of course recognized that a cascade type grid bias limiter is capable of nearly complete AM suppression; but two additional tubes are necessary and this type of circuit is relatively expensive. A comparative set of curves for one diode, two diodes, and a cascade limiter is shown in Fig. 3. The single and double diode curves are variable threshold devices that show AM reduction factors ranging from 6 to 10 db better than the cascade limiter for signal levels below the threshold of the cascade type limiter.

Fig. 4 shows a dynamic limiter circuit employing a type 1N48 or 1N56 as the germanium crystal diode. This is a simple and highly effective type of amplitude modulation limiter for both an FM receiver and a TV sound channel. This limiter provides a variable threshold action that extends to small signal levels and effects a significant degree of quieting on weak signals as well as for interchannel background noise.

Any signal of such peak amplitude as to be above the threshold level will have its residual amplitude variations suppressed by this limiter. The ideal limit of suppression may be more nearly approached by a germanium crystal than by a vacuum tube, because the crystal exhibits so much greater conductance than a tube. In addition to high conductance, the crystal diode exhibits extremely low capacitance.

This variable threshold limiter device uses a resistance-capacitance network with a time constant long compared to the lowest expected amplitude modulation frequency, and the limiter adjusts itself automatically to the varying average signal amplitude. A time constant of 0.1 second is sufficient to insure rejection of AM components down to 10 cycles.

For a given frequency there is a loss caused by the insertion of a diode in a transmission system. It is the ratio, expressed in decibels, of the power delivered before the insertion to the power delivered after the insertion; this is commonly referred to as "insertion loss." Since for any given signal level the insertion loss of the limiter becomes greater as the resistance is reduced, the resistance value is governed by the allowable limiter insertion loss and the desired degree of small signal AM rejection. 10,000 ohms is a reasonable compromise among all the factors which obtain.

To achieve a time constant of 0.1 second the value of the electrolytic type condenser then becomes 10  $\mu$ fd.; for a 20,000 ohm resistor it would be

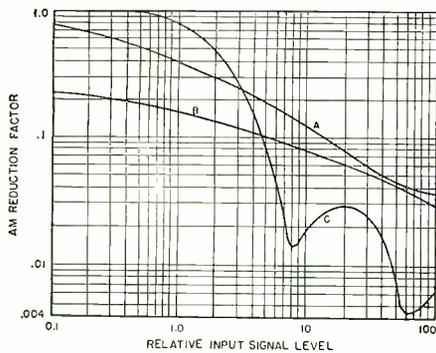


Fig. 3. Comparison of single and double diode dynamic limiters with cascade type grid bias limiter. (A) Single diode dynamic limiter (1N56), (B) Double diode dynamic limiter (2-1N56's) and (C) Cascade limiter using 2-6SJ7 tubes.

5  $\mu$ fd. The small 500  $\mu$ fd. mica condenser bypasses the high frequency i.f. components.

With this type variable threshold limiter AM reduction varies smoothly with signal level, AM noise decreasing as the signal level increases, and approaching zero as the signal voltage is increased by virtue of improvement in crystal efficiency at high signal voltages.

The biased high conductance diode 1N48 or 1N56 is shunted across the tuned circuit which is the primary of the detector input transformer, either limiter-discriminator or ratio detector type. Whenever the "Q" of the tuned circuit exceeds 25, the damping provided by the diode is effectively integrated over the i.f. cycle. Voltage regulation is predominantly in the tuned circuit, and the diode helps maintain essentially constant voltage across the circuit.

This type dynamic limiter is not critical with respect to characteristics of the particular crystal employed; virtually any germanium diode will perform well in this circuit. This is a worthwhile consideration in connection with replacement of one unit by another. Further, the back resistance of the crystal also serves to augment the action of the limiter. Finally, a receiver using a dynamic limiter would require only  $\frac{1}{2}$  to  $\frac{1}{3}$  the input signal voltage at the antenna to produce a given amount of quieting.

Of course this limiter is not capable of as great AM suppression as the cascade grid bias type limiter. However, the variable threshold action tends to extend the range of operation to low signal levels. Thus the use of such a dynamic limiter in simplified FM receivers is attractive because of the significant quieting on weak signals, even with but slight over-all gain. In the absence of a signal some squelch action occurs as a result of partial limiting on receiver background noise.

In a TV receiver with intercarrier sound this type dynamic limiter helps to reduce the audio buzz which sometimes accompanies excessive modulation depth of the picture carrier.

The double diode dynamic limiter circuit shown in Fig. 5, used in con-

junction with an FM detector, helps suppress residual AM in frequency modulation type receivers or sound circuits of TV receivers. A high conductance diode like the 1N56 provides exceptionally effective limiter action, particularly at signal levels as low as 5 volts or less. The low dynamic impedance and the low diode capacitance produce a minimum of reactive loading across the source and minimize any loss traceable to limiter insertion at low signal levels.

The two biased diodes are so polarized that they conduct in opposite directions. The net improvement in AM reduction factor (ratio of the percentage modulation of output signal to input signal) is so exceptional that it is shown graphically in Fig. 6.

Many television receivers use a limiter stage ahead of the discriminator, even when a ratio detector is used as the detector. The function of the limiter is to clip off any amplitude variations of the sound i.f. signal that may be caused by noise or non-uniform i.f. amplification over the frequency band. Wherever the normal amplification of the grid biased limiter is not necessary, a biased diode may be used more economically.

The basic limiter circuit in Fig. 4 illustrates this effectively. The diode with a bias voltage equal to the normal signal level is placed across a tuned circuit. The diode will conduct only on peaks that exceed the normal signal level; hence noise peaks will be automatically shorted out. Harmonic distortion as a result of such clipping action may be minimized by using two diodes to clip both the positive and negative peaks, as in Fig. 5. This is, in effect, a full-wave limiter.

The bias is usually obtained from an RC circuit so designed and with such a time constant configuration that it automatically adjusts itself to the signal level. This use of crystal diodes is one of the most inexpensive means of securing desirable limiter action. These germanium diodes are quite likely to be used widely in discriminator circuits. They may be wired directly to the transformer and mounted in the shielded can to facilitate elimination of contact potential feedback and filament hum problems.

#### Discriminator Circuits

One of the basic requirements of an FM system is that the detector be a device for converting frequency changes into amplitude variations which may then be amplified as audio signals. In the widely used Foster-Seeley discriminator the signal frequency varies back and forth across the resonant frequency of the discriminator and an a.c. voltage of the same frequency as the original modulation is developed and passed on to the audio amplifier.

The discriminator in an FM circuit corresponds to the detector in an AM circuit in that both demodulate the intelligence from the carrier wave. The process is different, but the net

(Continued on page 127)

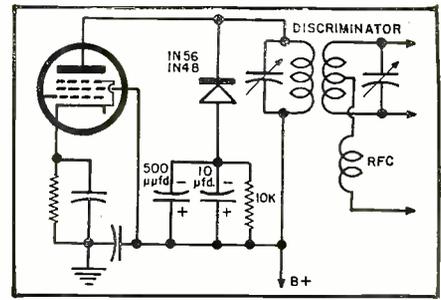


Fig. 4. Single diode dynamic limiter. The values of the 10,000 ohm resistor and the 10  $\mu$ fd. condenser may be chosen to suit the signal frequency and degree of clipping desired. Values of the resistor may range from 5000 to 50,000 ohms. Condenser values will depend on the time constant desired. The time constant of this circuit is approximately 0.1 second. Where high impedances are desirable G-E types 1N52 or 1N63 or Sylvania type 1N54 may be employed.

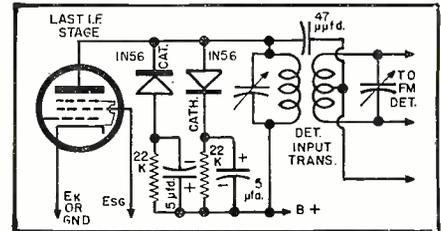


Fig. 5. Double diode dynamic limiter circuit.


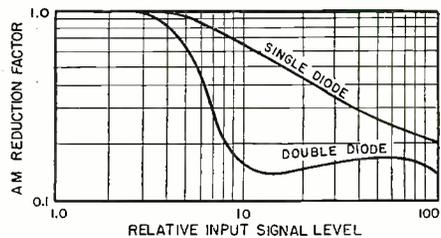


Fig. 6. Comparison of AM reduction factor for single and double diode dynamic limiter.

★ ★

Fig. 7. Characteristic curve for a discriminator. Note that output voltage of unit is greater for a high input voltage level as shown in curve B as compared with lower input level for curve A. Also the quality of response depends on linearity of curve from -75 kc. to +75 kc. deviation from center frequency of i.f. response. This graph demonstrates that output of the discriminator may vary with changes in signal level (which is AM variation since curves for B and A show characteristics for different signal levels).

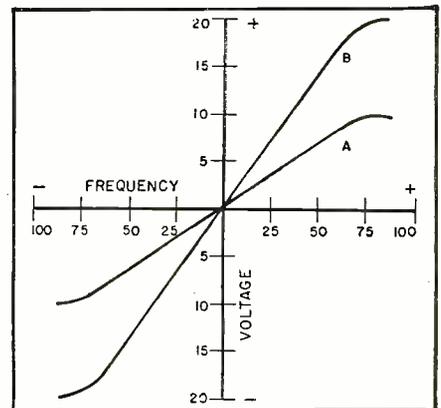

# Practical

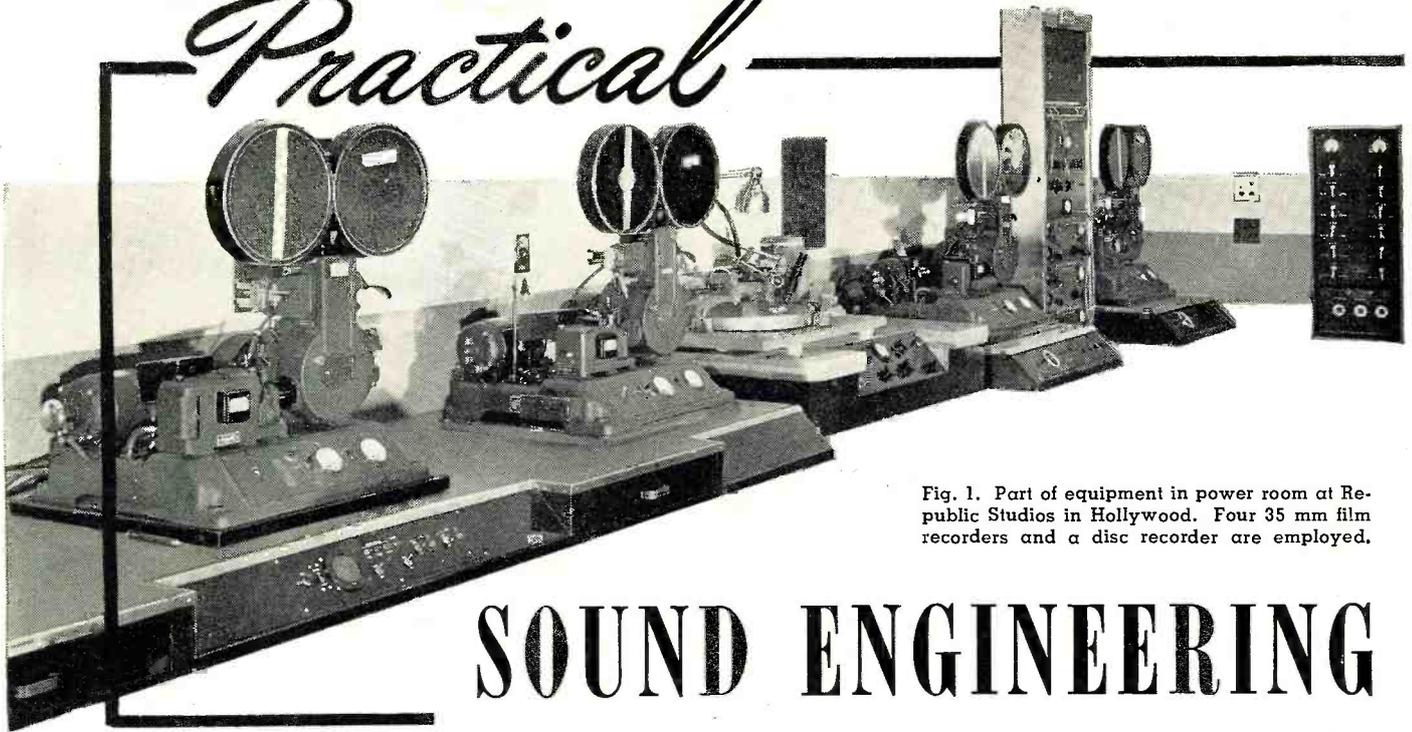


Fig. 1. Part of equipment in power room at Republic Studios in Hollywood. Four 35 mm film recorders and a disc recorder are employed.

## SOUND ENGINEERING

By

**H. M. TREMAINE, D.Sc.**

Audio Consultant

**Part 11. The concluding article of this series detailing how a complete distribution system achieves flexibility by means of patch bays.**

CONVENIENCE of operation and flexibility are the main factors which have resulted in the development of the patch cord, jack strip, and patch bay. The term "bay" originated in the telephone industry, and is used to designate a group of racks. Thus, a patch bay or amplifier bay may be one or several racks containing similar type equipment.

Fig. 3 is a typical motion picture sound recording installation at the Republic Studios in Hollywood, California. The equipment pictured is used

for the recording of music, re-recording, and "dubbing," and represents four complete recording channels. The first two racks at the left contain microphone preamplifiers and phototube preamplifiers used with the film reproducers shown in Fig. 5. The next two racks contain the recording and compressor-limiter amplifiers for channels 1 and 2. Racks 5 and 6 house the "transmission" measuring equipment consisting of a gain set (transmission set), distortion factor meter, filters, repeat coils, audio oscillator, and two

special low-noise amplifiers for film measurements. Racks 7 and 8 contain channels 3 and 4, which are similar to the other two channels. The next four racks hold four 60-watt monitoring amplifiers and associated equipment. Two racks which are not shown contain signal and talk-back equipment.

For flexibility all equipment is interconnected by a system of "normal jacks." Except for the monitor amplifiers, all equipment is operated from high and low voltage d.c. power supplies situated in a power room in another part of the building. This type operation and design prevents the picking up of stray magnetic fields. Each group of power supplies is fed from a constant source of a.c. voltage through voltage regulators. On the right-hand side of the room are four 35 mm film recorders and a disc recorder, shown in Fig. 1. The rack at the right end holds the noise reduction amplifiers for the film recorders and a "cross-modulation" oscillator for film processing tests. The recorder motors are driven from master distributor systems, controlled from the panel at the extreme right.

The greater percentage of circuit jacks found in sound installations and audio frequency laboratories are of the "normal" type. These jacks are designed to permanently connect various pieces of equipment which are used in conjunction with each other for the making of measurements or other purposes. The equipment so "normalled" may be used as a complete unit without the necessity of connecting them by means of patch cords. When desired, however, any one of the units connected to the jacks may be used individually. Figs. 4A and 4B show the physical construction and circuit connections of two jacks, a "normal" and an "open circuit" type.

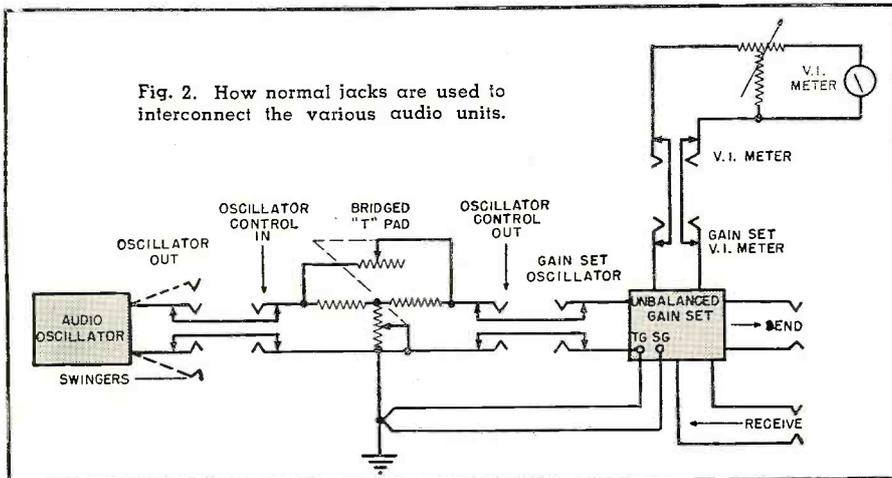


Fig. 2. How normal jacks are used to interconnect the various audio units.

It will be noted that the normal jack differs from the open circuit jack in that it has a small inner leaf spring called the "normal spring" and is normally in contact with the upper spring, known as the "swinger." This inner or normal spring is not used in the open circuit type jack.

When it is desired to continuously operate a number of circuits or pieces of equipment together, normal jacks are employed. The normal springs (inner) are connected so as to form a continuous circuit from one pair of jacks to another. For example: an oscillator, oscillator output control, gain set, and a v.i. meter are generally used together in the making of gain frequency measurements.

Fig. 2 illustrates the manner in which normal jacks are used to connect these pieces of equipment together into a continuous circuit, so that all units are permanently interconnected, yet may be operated independently of each other, if desired. The use of normal jacks also provides a means of substituting equipment in case of failure of any one unit normally used. The normal springs of the jacks at the output of the oscillator are connected to the normal springs of the oscillator control input jacks. The output of the control is then normally to the gain set oscillator jacks.

When it is desired to pick up only the oscillator, a patch cord is inserted in the oscillator output jacks. When the tip of the patch cord plug enters the jack, it moves the "swingers" outward, breaking the circuit between it and the normal spring, as shown by the dotted lines in Fig. 2. This action disconnects the oscillator output from the oscillator control, and allows the oscillator to be picked up independently of the control. The same action will take place if a patch cord is inserted in any other portion of the circuit.

When it is desired to connect several circuits or pieces of equipment in multiple (parallel) by means of patch cords, a "strap jack" is employed. Strap jacks consist of several open circuit jacks connected in parallel, as shown in Fig. 8B. Frequently, several such strap jacks are included in an installation to facilitate the interconnection of equipment. Generally, a group of five constitute a strap; at least one strap jack is included in each group of high or low level jacks.

Jacks may also be referred to as "multiples." This type connection differs from the strap jack in that it is connected permanently in parallel with a particular circuit or piece of equipment to provide additional connections. A multiple connection is shown in Fig. 8A.

Patch cords employed in the transmission laboratory, as well as in other parts of the plant, may be single (tip and sleeve) or double circuit type, as shown in Figs. 6 and 7. A single circuit plug consists of a brass "sleeve" and "tip." A small rod connects to the tip, and runs back through the brass

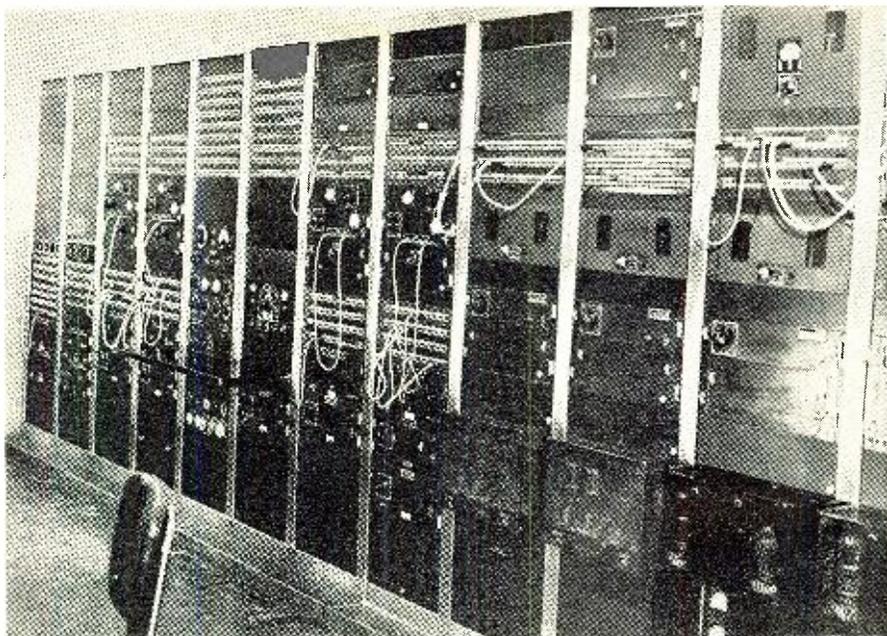


Fig. 3. Typical motion picture sound recording installation at Republic Studios.

sleeve through an insulated bushing to the "body," where a terminal screw is provided for connection to the cord. The sleeve is always connected to the ground, or "low potential" side of the circuit, while the tip is connected to the high potential or "hot side" of the circuit. A bakelite sleeve fits over the rear end to protect the connections inside the body and also to provide a grip for the plug.

The double circuit plug is practically standard throughout the recording and broadcast industries. The plug consists of two single circuit plugs in a dual mounting and is similar in all respects to the single circuit plug except that the plug floats in the body and thus allows for variations in jack strip mountings. The bakelite body of this plug has a group of notches on one


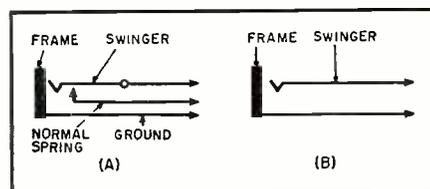


Fig. 4. The physical construction and circuit connections of (A) a normal jack and (B) an open circuit type recording jack.

side to indicate the polarity of the plug. Corresponding jacks are spaced to prevent improper insertion of the plugs.

When patch cords are assembled they are polarized by connecting the corresponding tips and sleeves of each end together through the cord. Single plug type patch cords can only be inserted into a jack one way. However,

Fig. 5. The film reproducers used in connection with the equipment shown in Fig. 3.

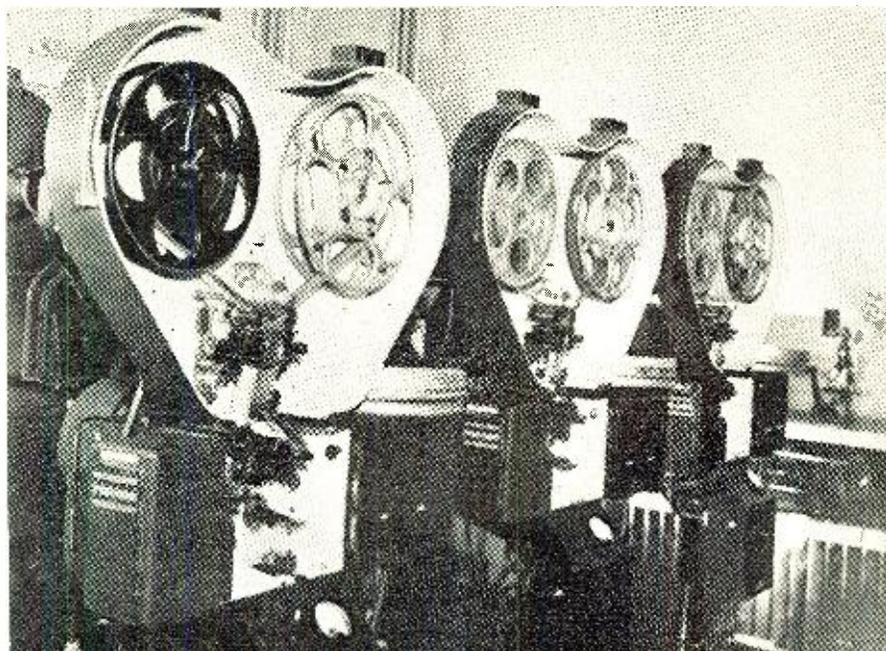

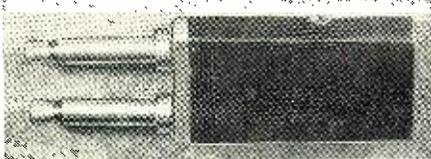


Fig. 6. Double circuit type patch cord.



Fig. 7. A single circuit type patch cord.

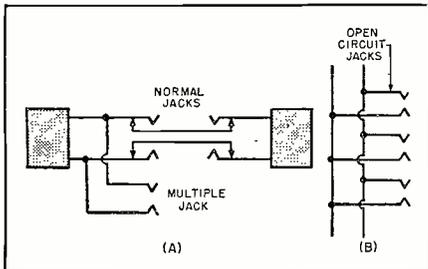


Fig. 8. (A) Method of connecting strap jacks and (B) multiple jack connection.

DEVICE	OUTPUT LEVEL
Mikes	-65 to -50 dbm
Preamps	-20 to -6 dbm
Mixers	-50 to -20 dbm
Booster Amp.	-30 to -10 dbm
Line Amp.	0 to +4 dbm
Bridging Amp.	+10 to +30 dbm
Recording Power Amp.	+4 to +45 dbm
Monitor Power Amp.	+20 to +46 dbm

Table 1. Approximate circuit levels that may be expected in an average installation.

the double plug can be turned over 180 degrees and thus reverse the circuit. This might upset the circuit balance or short out the signal completely. To prevent this, the circuits to the jacks throughout the installation are polarized by connecting the left hand (facing the rack) jack of a pair to the low potential or grounded side of the circuit. The patch cord plug is always inserted with the notched side to the operator's left as he faces the rack.

Single circuit plugs are generally used for signal lights and "order wire" circuits; however, if a large number of circuits are to be placed in a small area, the single jack may be used.

Some of the radio networks have adopted a jack and plug known as a "tip-ring-sleeve" type, which is a three-circuit device. This plug is similar in appearance to the single type, except that between the tip and sleeve is a ring contact insulated from the tip and sleeve. The tip carries the hot side of the circuit, the ring the low potential side, and the sleeve the ground, which is connected to a flexible metal shield covering the cord. A similar type plug is also used for telephone circuits in switchboards. The jack for this type plug has two swingers, one for the tip and one for the ring. The frame is grounded.

Separate ground wires are run to each group of jack frames, and then to the main ground at the bottom of the rack. The low-level ground wires

are carried on the left, and the high-level wires on the right.

When signals of extremely low level are carried over patch cords, it is the practice to use a shielded type, thus preventing pickup from circuits of higher level and surrounding equipment. In large installations, all jack frames are grounded and supply a ground for shielded patch cords. However, if the shield of the patch cord is grounded at both ends, it will result in a ground loop between two jack strips; therefore, it is grounded at one end only.

Shielded pairs comprising the cable forms terminate at terminal blocks located at the bottom of the rack. Lines from external equipment and other parts of the installation come to these blocks first, then tie to the proper circuits in the cable forms. Such practices allow equipment to be terminated differently as changes are required in the installation. Circuits carrying d.c. from power supplies and ground wires, are carried in the low level section of the gutter.

Impedance matching of equipment is of extreme importance in audio installations. If the terminal impedances match the "surge" or "characteristic" impedance of the line, reflections along the line which create a loss of power will be at a minimum, and a maximum transmission of power will result. However, audio engineers deal with relatively low frequencies, 30 to 20,000 cycles, therefore the surge impedance is small and may be disregarded. The line impedance is generally considered to be that of the impedance terminating the line, or very close to it.

If the audio power is one watt (plus 30 dbm) or less, the shielded transmission line shown in Fig. 9 may be used. Circuits carrying higher powers should be of wire that has a very low d.c. resistance per foot, because at high powers this resistance may reduce the energy at the far end of the line by several decibels. For large speaker systems where 50 to 100 watts of power must be transmitted, the lines are generally run in metal conduit using #10 to #14 common rubber-covered wire.

The loss of power due to line resistance may be determined by referring to a wire table, finding the "resistance-per-foot" for a given size, and then calculating the power loss. It must be remembered that the line is a pair and the footage is the length for both wires.

It is not good practice to run lines of low impedance (15 ohms or lower) over great distances, as the effective

d.c. resistance of the line may become of such value that the impedance of the circuit is upset, in addition to creating a loss of power.

A better method is to transmit the signal over a 500- or 600-ohm line, and then reduce the impedance at the far end by the use of an impedance-matching transformer. This permits a high voltage-low current transmission of the signal which reduces line losses. In the case of the low-impedance line, power losses are greater because the voltage is low and the current is high, and the d.c. resistance of the line becomes important. Transformers used for impedance matching must have a low insertion loss, to prevent a loss of power.

The percentage of impedance mismatch between different units of an installation may vary up to 10 to 15 per-cent without seriously affecting its operation. Of course, the greater the mismatch, the greater the transmission loss in power. In some instances the frequency response of the device may be affected if the mismatch is too great. If the mismatch is held to within 10 per-cent, it is considered to be satisfactory.

The running of high- and low-level lines in the same cable form should be avoided. High- and low-level lines should not be adjacent to each other unless they are separated by a space of several inches. It must be understood that the shielding on the cable pair provides a fixed amount of "crosstalk" reduction and its effectiveness depends on the level of the signal in the circuit.

As a rule, most low-level circuits may be cabled in the same form when the signal difference is not more than 40 db. If circuits with levels between minus 20 and zero dbm are present in the same area, they must be cabled into separate forms and separated by a distance of one inch or greater.

Sometimes it is necessary to run unshielded a.c. power cable forms inside the frame of a rack. To secure greater separation and to obtain a certain amount of magnetic shielding, the lines are laid in the "channel-iron" sides of the rack. However, it is the best practice to run all a.c. lines either in steel tube or flex at the rear of the racks. The flex is carried from the power source directly to the equipment.


High-level pairs running to loud-speaker systems should be carried as directly as possible to the speakers and run inside the rack frame to prevent coupling to the lower-level pairs.

Circuits carrying high voltage d.c. for plate supply are treated as a low-level line, and run on the low-level side of the rack as are d.c. heater voltages.

The values given in Table 1 are not intended to represent any particular installation, but to show the range of levels that may be encountered.

The material contained in this article was supplied by and through the courtesy of Hollywood Technical Institute, 3359 Cahuenga Blvd., Hollywood, California.

Fig. 9. Construction of a shielded pair.

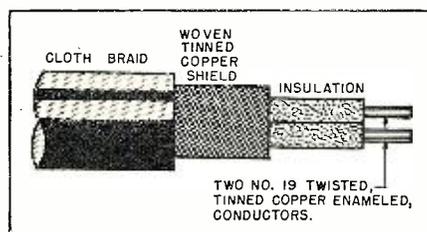



# TUBES

FROM **Niagara Radio Supply**

AT **50%** TO **90%** OFF


RECEIVING		6R7GT \$ .84		12AX7 \$1.20		30X \$ .78		2J54B \$37.50		274B \$1.95		927 \$1.25	
00A	\$1.60	5W1GT	\$.80	12AY7	3.00	36	.78	2J55	87.50	276A	9.95	931A	4.75
0A2	1.54	5X4G	.88	12B7	1.10	38	.59	2K23	45.00	282A/B	8.25	954	3.35
0A3 VR75	1.25	5Y3GT	.62	12BA7	1.19	39/44	.25	2K25	39.50	283A	9.25	955	.40
0A4G	1.19	5Y1GT	.72	12BD6	1.00	41	.74	2K28	35.00	284D	7.50	956	.40
0B2	1.64	5Z3	.88	12BE6	.86	42	.71	2K29	22.50	286A	9.95	957	.40
0B3 VR90	1.25	5Z4	.88	12B6	.83	43	.74	2K33	3.75	287A	2.75	958A	.40
0Y4	2.40	6A3	1.24	6SD7GT	.97	45	.88	3AP1	12.50	290A	4.95	967	4.95
0Z4G	.72	6A4 LA	1.34	6SF5GT	1.00	45Z3	.88	3B22	2.75	291A	4.95	975A	12.95
01A	.72	6A5G	1.95	6SF7	.97	45Z3GT	.79	3B24	5.75	293A	2.75	991	3.35
IA3	.72	6A6	.91	6SG7	.97	46	.81	3B26	3.75	301A	4.95	1603	5.00
IA1P	1.29	6A7	.98	6SH7GT	.72	47	.88	3B27	3.75	304TH	60.50	1613	.99
IA5GT	.77	6A8GT	1.04	6SJ7GT	.88	48	.75	3B28	8.50	304TH	19.50	1616	1.50
IA6	.84	6AB4	1.00	6SK7GT	.88	48	.75	3B28	8.50	304TL	60.50	1619	.35
IA7GT	.94	6AB5/6N5	1.33	6SL7GT	.97	49	.84	3B29	8.50	307A	19.50	1620	4.75
IA89	.79	6AB7/1853	.404	6SN7GT	.97	50	2.48	3C21/24G	8.50	307A	19.50	1621	1.20
IA95	1.10	6AC5GT	1.19	6SQ7GT	.74	50A5	.94	3C27B	3.25	310A	7.50	1623	2.00
IA95	1.10	6AC7/1852	1.14	6SR7GT	.84	50B5	.94	3C31	17.50	311A	6.75	1624	1.50
IB3GT	1.21	6AD7G	1.34	6SS7GT	.99	50C5	.94	3C345	1.75	327A	.75	1625	.39
IB4P	1.14	6AE6G	.88	6ST7	1.04	50C6G	1.45	3D21A	4.75	327A	.75	1625	.39
IB5 25S	.94	6AF6G	.94	6SV7	1.24	50L6GT	.84	3DP1	4.75	328A	13.75	1626	.45
IB7GT	1.21	6AG5	.88	6SZ7	1.20	50X6	1.10	3E29	14.50	331A	12.50	1629	.99
IC5GT	.81	6AG7	1.54	6T7G	1.19	50Y6GT	.84	3EP1	3.50	334TL	8.50	1630	9.00
IC6	.72	6AH6	1.39	6T8	1.17	50Z8GT	1.00	3FP7	3.75	350B	3.75	1631	.99
IC7G	.72	6AJ5	1.14	6U4	1.20	50Z7G	.90	3GP1	4.50	354C/D	19.95	1632	.75
IC8	.75	6AK5	1.49	6U5	.94	52	1.95	3HP7	3.75	357A	39.50	1634	.70
ID3GP	.72	6AK6	1.11	6U6GT	.97	53	.97	4AP10	4.75	367A	3.25	1636	3.00
ID7G	.72	6AL5	.81	6V6GT	.97	55	1.10	4B22	9.75	371A	1.25	1638	.50
ID8GT	.72	6AL7G	1.33	6V5GT	1.95	56	.75	4C27	28.00	374A	3.75	1642	.65
IE5GT	.72	6AQ5	.91	6V6GT	1.95	57	.75	4J26	99.50	374A	2.75	1644	.90
IE7GT	1.18	6AQ6	.86	6V6GT	.88	58	.84	4-65A	20.00	393A	5.95	1645	1.98
IF4	.72	6AQ7GT	1.20	6V7G	.90	59	.94	4-65A	14.21	398A	6.95	1649	1.25
IF5G	.72	6AR5	.78	6W4GT	.84	60	.88	4-250A	41.25	399A	2.50	1654	2.00
IF6	.75	6AS5	.99	6W5G	1.33	71A	.58	4-250A	29.50	400A	3.25	1655	1.25
IF7G	.72	6AT6	.72	6W6GT	1.00	72	.75	5AP1	3.50	401A	1.95	1651	1.75
IG4GT	.72	6AU5GT	1.24	6W7G	1.04	76	.45	5BP1	4.95	417A	8.95	1660	.70
IG5G	.75	6AU6	.92	6X4	.72	77	.59	5BP4	3.50	464A	12.95	2050	1.25
IG6GT	.72	6AV5GT	1.33	6X5	1.33	78	.78	5BP4	4.95	527	12.50	2051	1.35
IH4G	.88	6AV6	.72	6X5GT	.74	79	.79	5CP1	4.95	531	4.95	5610	1.00
IH5GT	.74	6AW6	1.33	6Y6GT	1.95	80	.88	5CP1A	9.95	532A	4.95	5654	4.50
IH6GT	1.04	6AX5GT	.83	6Y6GT	1.95	81	2.34	5FP7	6.95	575A	13.50	5670	5.50
IJ5	.95	6B4C	1.60	6Y7G	1.24	82	.88	5FP14	70.00	701D	17.95	703	4.45
IJ6GT	.97	6B5	1.60	6Z4	.90	83	.83	5GP1	4.95	703A	6.95	8005	5.95
IL4	.72	6B6G	.98	6Z5G	1.95	83V	1.14	5HP1	4.95	704A	.99	8011	1.75
IL6	1.33	6B7	.97	6Z5Y5G	.88	84	.84	5HP4	4.95	705A	2.50	8013A	2.75
ILA4	.88	6B8G	.84	7A4	.78	85	.88	5J23	12.50	706BY	37.50	8020	1.20
ILB4	1.05	6B9G	.84	7A5	.88	86	.88	5J29	12.50	706C	37.50	8020	1.20
ILC5	.88	6BA7	1.14	7A6	.88	87	.88	5J31	12.50	707B	14.95	9001	1.25
ILD6	.97	6BC5	.97	7A7	.84	88	.88	5J32	12.50	708A	4.95	9002	1.25
ILD5	.97	6BC7	1.33	7A8	.88	89	.88	5J32	12.50	709A	29.50	9003	1.75
ILE3	.84	6BD5	1.60	7AD7	1.60	90	.94	5J35	14.95	710A	1.70	9004	.59
ILG5	.84	6BD6	.99	7AF7	1.00	91	.94	5L1P	19.50	710A	1.70	9005	1.95
ILH4	.88	6BE6	.94	7AG7	1.04	92	.94	5L1P5	9.95	713A	1.40	9006	.39
ILN5	.94	6BF6	.78	7AH7	1.10	93	.94	5L1P5	9.95	715B	6.75	9006	.39
IN5GT	.88	6BG6G	1.18	7AJ7	.90	94	.94	5N1P	5.50	715B	6.75	9006	.39
IP5GT	.78	6BH6	.96	7AU7	1.10	95	.94	5N1P	5.50	715B	6.75	9006	.39
IQ5GT	.72	6BJ6	.96	7B4	.84	96	.94	5N1P	5.50	715B	6.75	9006	.39
IQ6	1.10	6BK6	.75	7B5	.84	97	.94	5N1P	5.50	715B	6.75	9006	.39
IR4	.72	6BL7	1.45	7B6	.84	98	.94	5N1P	5.50	715B	6.75	9006	.39
IR5	.72	6BM6	1.32	7B7	.84	99	.94	5N1P	5.50	715B	6.75	9006	.39
IS4	.72	6BQ6GT	1.34	7B8	.90	99V	1.60	5P1P	24.50	707B	14.95	9001	1.25
IS5	.84	6BT6	.75	7C4	.78	99X	1.60	5P1P5	24.50	708A	4.95	9002	1.25
IS6	1.10	6BU6	.83	7C5	.84	99X	1.60	5L1P	19.50	710A	1.70	9004	.59
IT4	.84	6BY5	1.33	7C6	.84	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
IT5GT	.72	6C4	.78	7C7	.84	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
IT6	1.20	6C5GT	.78	7C8	.84	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
IU4	.88	6C6	.78	7E5	.74	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
IU5	.88	6C8G	.97	7E6	.78	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
IV	.71	6CB6	.97	7E7	.88	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
IV2	.75	6CD6	2.94	7F7	.88	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
IV5	1.10	6D6	.84	7F8	1.33	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
IW4	1.33	6D8	.88	7G3	1.33	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
IW5	1.10	6E5	1.10	7H7	.84	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
IX2	1.17	6E6	1.33	7J7	1.33	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
IX2A	1.33	6E7	1.95	7K7	1.19	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
2A3	.75	6F5GT	.78	7L7	.97	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
2A4G	.85	6F6	.94	7N7	.97	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
2A5	.45	6FG6T	.83	7P7	.82	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
2A6	.45	6F7	.88	7R7	.82	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
2A7	.45	6F8	.94	7S7	.97	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
2B7	.40	6G6	1.14	7V7	.94	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
2E5	.45	6H4GT	1.33	7W7	1.04	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
2X2	.64	6H6GT	.78	7X6	1.10	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
2X2A	1.59	6J5GT	.68	7X7	1.09	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
2Z2	1.95	6J6	1.19	7Y4	.74	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
3A5	.89	6J7GT	.81	7Z4	.84	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
3A8GT	2.10	6J8	1.60	10	1.05	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
3B7	.45	6K5GT	.88	10Y	.88	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
3C6/XB	1.60	6K6GT	.78	12A5	.64	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
3D6	.45	6K7GT	.72	12A6	1.60	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
3E	1.33	6K8GT	.72	12A6	1.60	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
3FL4	.94	6L5	.86	12A6GT	1.45	99X	1.60	5L1P5	9.95	713A	1.40	9005	1.95
3O4	.84	6L6G	1.74	12A7									

# Features OF THE NEW 1952



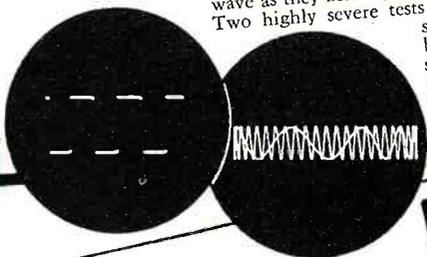
## PROOF OF THE NEW O-7 OSCILLOSCOPE'S OUTSTANDING PERFORMANCE

Below are actual, unretouched photographs showing the outstanding frequency response characteristics of the NEW 1952 HEATHKIT OSCILLOSCOPE, MODEL O-7. To the left is a 10 KC sine wave — to the right a 4 MC sine square wave — as they actually appear on the screen. Two highly severe tests to make on any scope (only the best of scopes will show traces like these) — and the O-7 really comes through.



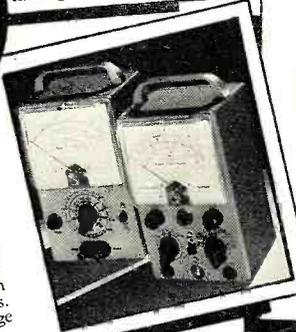
## COMPANION VACUUM TUBE VOLTMETERS

Here are the two NEW 1952 VACUUM TUBE VOLTMETER COMPANION PIECES. Matched instruments of new design to open up the whole field of DC, AC, and resistance measurements for you. The new greatly reduced size combines style, beauty, and compactness — The V-5 and AV-1 have the new panel and cabinet construction as shown on the right. A tremendous pair of voltmeters. Small in size but virtual giants in the range of measurements they make.


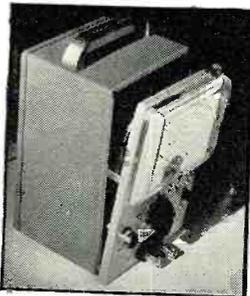
## NEW STYLE AND BEAUTY


Style that's modern, yet functional — that's the trend of today — and Heathkits are right up to the minute. Note the cut showing the new V-5 and AV-1 cabinet and panel construction. The front panel and rear cover slide right over the recessed flange of the case thereby eliminating sharp edges and pointed corners. The voltmeter kits aren't "shelf" or "mounted" instruments — they're moved about on the bench a lot and thus the new compact size and specially designed cabinets — Another 1952 Heathkit feature.



## A STATEMENT FROM SIMPSON ELECTRIC CO.

In choosing Simpson Meters for their Heathkit VTVM, the Heath Co. has set a new high standard of kit meter quality. The same high quality of material, workmanship and design that has given Simpson the reputation for building "Instruments That Stay Accurate" is found in the Heathkit Meter Movement.

SIGNED  
SIMPSON ELECTRIC CO.

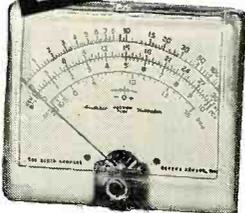

## A STATEMENT FROM CHICAGO TRANSFORMER

It is indeed gratifying to note the outstanding sales records you are building with our Heathkits.

This sales success is readily understandable, since we are cognizant of the high quality standards you have established for your component suppliers.


We at Chicago Transformer are proud that our product has contributed to the recognized quality and increasing popularity of Heathkits.

CHICAGO TRANSFORMER DIVISION  
Essex Wire Corporation

L. S. RACINE  
Vice-President and Sales Manager

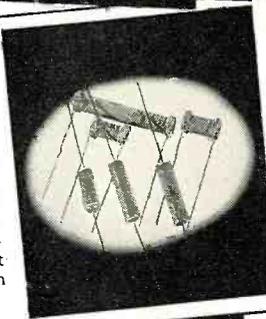
## HEATHKIT PRECISION RESISTORS

Where exact resistance values are required for instrument accuracy, the Heath Co. has spared no effort in supplying the finest resistors available. Precision resistors as manufactured by Continental Carbon Inc., and Wilcor Corp., meet the rigorous JAN (Joint Army-Navy) specifications and are small in size, extremely non-inductive, highly stable, have a low temperature coefficient, and can be held to great accuracy. You'll find quality components in Heathkits.


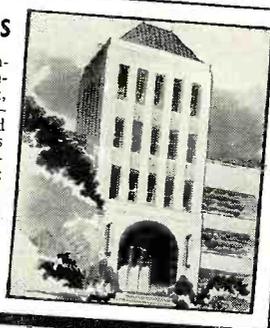
## COLLEGES USE HEATHKITS

Colleges and Universities throughout the country are using Heathkits in their electrical engineering, radio, and physics laboratories — Heathkits are the answer to good test equipment at low cost, plus being rugged, dependable, and accurate. Trade schools are having their students build Heathkits to obtain a first hand working knowledge of test equipment and to get the practical experience gained by construction. Heathkits fill school needs.



YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT  
ROCKE INTERNATIONAL CORP.  
13 E. 40th ST.  
NEW YORK CITY (16)  
CABLE: ARLEA-N. Y.

# The HEATH COMPANY

... BENTON HARBOR 15, MICHIGAN

# New LABORATORY LINE HEATHKITS



MODEL AV-1  
Shipping weight 5 lbs.

## NEW *Heathkit* A.C. VACUUM TUBE VOLTMETER KIT

Now — as a Heathkit — at a price anyone can afford, an AC VTVM. A new kit to make possible those sensitive AC measurements required by audio enthusiasts, laboratories, and experimentors. Here is the kit that the audio men have been looking for. Its tremendous range of coverage makes possible measurements of audio amplifier frequency response — gain or loss of audio stages — characteristics of audio filters and attenuators — hum investigation — and literally a multitude of others. Ten ranges consisting of full scale .01, .03, .1, .3, 1, 3, 10, 30, 100, 300 volts RMS assure easy and more accurate readings. Ten ranges on DB provide for measurements from -52 to +52 DB. Frequency response within 1 DB from 20 cycles to 50 KC.

The ingenious circuitry incorporates precision multiplier resistors for accuracy, two amplifier stages using miniature tubes, a unique bridge rectifier meter circuit, quality Simpson meter with 200 microampere movement, and a clean layout of parts for easy wiring. A high degree of inverse feedback provides for stability and linearity.

**\$29.50**

Simple operation is accomplished by the use of only one control, a range switch which changes the voltage ranges in multiples of 1 and 3, and DB ranges in steps of 10.

The instrument is extremely compact, cabinet size — 4 1/8" deep x 4-11/16" wide x 7 3/8" high, and the newly designed cabinet makes this the companion piece to the VTVM. For audio work, this kit is a natural.

## NEW *Heathkit* AUDIO FREQUENCY METER KIT

MODEL AF-1  
Shipping weight 12 lbs.



**\$34.50**

A NEW Heathkit Audio Frequency Meter — the ideal instrument for determining frequencies from 20 cycles to 100 KC. Set the selector switch to the proper range — feed the signal into the input terminals — and read the frequency from the meter — completely simple to operate, and yet dependable results.

Quality Simpson 200 microampere meter has two plainly marked scales (0-100 0-300). These scales, read in conjunction with the seven position selector switch, give full scale readings of 100, 300, 1000, 3000, 10,000, 30,000, and 100,000 cycles. Convenient ranges for fast and easy readings.

For greatest accuracy, the 1-3-10 ratio of ranges is maintained and each range has individual calibrating control.

Input impedance is high (1 megohm) for negligible circuit loading. A signal and a change in signal voltage between these limits will not affect the meter frequency of either sine wave or square wave input.

The tube complement consists of a 6SJ7 amplifier and clipper, 6V6 amplifier and clipper, 6H6 meter pulse rectifier, 6X5 power supply rectifier, and OD3/VK150 voltage regulator.

Construction is simple, and quality components are used throughout.

## NEW *Heathkit* INTERMODULATION ANALYZER KIT

Intermodulation testing of audio equipment is rapidly being accepted by more and more engineers and audio experts as the best way to determine the characteristics of audio amplifiers, recording systems, networks, etc. — shows up those undesirable characteristics which contribute to listening fatigue when all other methods fail.

The Heathkit Intermodulation Analyzer supplies a choice of two high frequencies (3000 cycles and a higher frequency) and one low frequency (60 cycles). Both 1:1 or 4:1 ratios of low to high frequencies can be set up for IM testing, and the ratios are easily set by means of a panel control and the instrument's own VTVM. An output level control supplies the mixed signal at the desired level with an output impedance of two thousand ohms. The Analyzer section has input level control and proper filter circuits feeding the instrument's VTVM to read intermodulation directly on full scale ranges of 30%, 10% and 3%. Built-in power supply furnishes all necessary voltages for operating the instrument.

You won't want to be without this new and efficient means of testing



MODEL IM-1  
Shipping wt. 18 lbs.

**\$39.50**


## NEW *Heathkit* SQUARE WAVE GENERATOR KIT

The new Heathkit Square Wave Generator Kit with its 100 KC square wave opens an entirely new field of audio testing. Square wave testing over this wide range will quickly show high and low frequency response characteristics of circuits — permit easy adjustment of high frequency compensating networks used in video amplifiers — identify ringing in circuits — demonstrate transformer characteristics, etc.

The circuitry consists of a multivibrator stage, a clipping and squaring stage, and a cathode follower output stage. The power supply is transformer operated and utilizes a full wave rectifier tube with 2 sections of LC filtering.

As a multivibrator cannot be accurately calibrated, a provision is provided to allow the instrument to be accurately synchronized with an accurate external source when extreme accuracy is required.

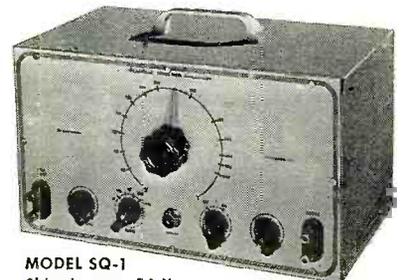The low impedance output is continuously variable between 0 and 25 volts and operation is simple. You'll really appreciate the wide range of this instrument, 10 cycles to 100 kilocycles — continuously variable. Kit is complete with all parts and instruction manual, and is easy to build.



MODEL SQ-1  
Shipping wt. 14 lbs.

**\$29.50**

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT  
ROCKE INTERNATIONAL CORP.  
13 E. 40th ST.  
NEW YORK CITY 16  
CABLE: ARLAB-N.Y.

The **HEATH COMPANY**

... BENTON HARBOR 15, MICHIGAN


THE *New* 1952  
*Heathkit*  
**OSCILLOSCOPE  
 KIT**

MODEL O-7  
 SHIPPING WEIGHT 24 LBS.

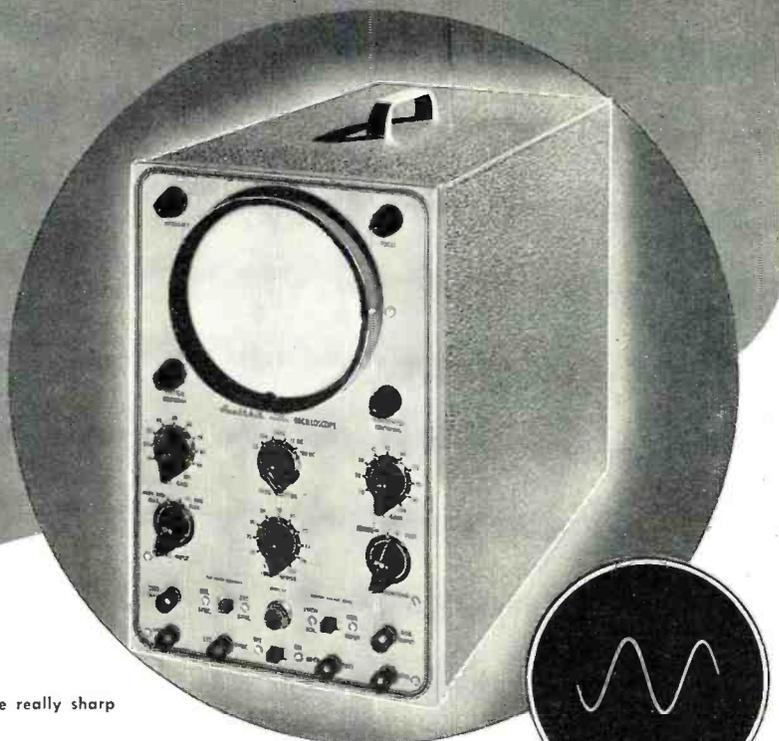**\$43.50**

*Features*

- New "spot shape" control for spot adjustment — to give really sharp focusing.
- A total of ten tubes including CR tube and five miniatures.
- Cascaded vertical amplifiers followed by phase splitter and balanced push-pull deflection amplifiers.
- Greatly reduced retrace time.
- Step attenuated — frequency compensated — cathode follower vertical input.
- Low impedance vertical gain control for minimum distortion.
- New mounting of phase splitter and deflection amplifier tubes near CR tube base.
- Greatly simplified wiring layout.
- Increased frequency response — useful to 5 Mc.
- Tremendous sensitivity .03V RMS per inch Vertical — .6V RMS per inch Horizontal.
- Dual control in vernier sweep frequency circuit — smoother acting.
- Positive or negative peak internal synchronization.



The performance of the NEW, IMPROVED, HEATHKIT 5" OSCILLOSCOPE KIT is truly amazing. The O-7 not only compares favorably with equipment costing 4 and 5 times as much, but in many cases literally surpasses the really expensive equipment. The new, and carefully engineered circuit incorporates the best in electronic design — and a multitude of excellent features all contribute to the outstanding performance of the new scope.

The VERTICAL CHANNEL has a step attenuated, frequency compensated vertical input which feeds a cathode follower stage — this accomplishes improved frequency response, presents a high impedance input, and places the vertical gain control in a low impedance circuit for minimum distortion. Following the cathode follower stage is a twin triode — cascaded amplifiers to contribute to the scope's extremely high sensitivity. Next comes a phase splitter stage which properly drives the push-pull, hi-gain, deflection amplifiers (whose plates are directly coupled to the vertical deflection plates). This fine tube lineup and circuitry give a sensitivity of .03V per inch RMS vertical and useful frequency response to 5 Mc.

The HORIZONTAL CHANNEL consists of a triode phase splitter with a dual potentiometer (horizontal gain control) in its plate and cathode circuits for smooth, proper driving of the push-pull horizontal deflection amplifiers. As in the vertical channel, horizontal deflection amplifier plates are direct coupled to the CR tube horizontal deflection plates (for improved frequency response).

The WIDE-RANGE SWEEP GENERATOR circuit incorporates a twin triode multivibrator stage for producing a good saw-tooth sweep frequency (with faster retrace time). Has both coarse and vernier sweep frequency controls.

And the scope has internal synchronization which operates on either positive or negative peaks of the input signal — both high and low voltage rectifiers — Z axis modulation (intensity modulation) — new spot shape (astigmatism) control for spot adjustment — provisions for external synchronization — vertical centering and horizontal centering controls, wide range focus control — and an intensity control for giving plenty of trace brilliance.

The Model O-7 EVEN HAS GREAT NEW MECHANICAL FEATURES — A special extra-wide CR tube mounting bracket is provided so that the vertical cascade amplifier, vertical phase splitter, vertical deflection amplifier, and horizontal deflection amplifier can mount near the base of the CR tube. This permits close connection between the above stages and to the deflection plates; distributed wiring capacity is greatly reduced, thereby affording increased high frequency response.


The power transformer is specially designed so as to keep its electrostatic and electromagnetic fields to a minimum — also has an internal shield with external ground lead. You'll like the complete instructions showing all details for easily building the kit — includes pictorials, step-by-step construction procedure, numerous sketches, schematic, circuit description. All necessary components included — transformer, cabinet, all tubes (including CR tube), completely punched and formed chassis — nothing else to buy.

NEW INEXPENSIVE *Heathkit*  
**ELECTRONIC SWITCH KIT**

The companion piece to a scope — Feed two different signals into the switch, connect its output to a scope, and you can observe both signals — each as an individual trace. Gain of each input is easily set (gain A and gain B controls), the switching frequency is simple to adjust (coarse and fine frequency controls) and the traces can be superimposed for comparison or separated for individual study (position control).

Use the switch to see distortion, phase shift, clipping due to improper bias, both the input and output traces of an amplifier — as a square wave generator over limited range.

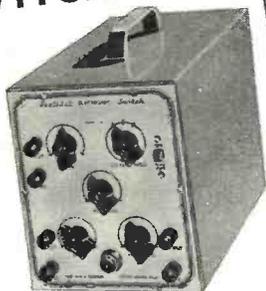The kit is complete; all tubes, switches, cabinet, power transformer and all other parts, plus a clear detailed construction manual.



Model S-2  
 Shipping Wt. 11 lbs.

*Only*  
**\$19.50**

**YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE**

EXPORT AGENT  
**ROCKE INTERNATIONAL CORP.**  
 13 E. 40th ST.  
 NEW YORK CITY (16)  
 CABLE: ARZAB-N.Y.

*The* **HEATH COMPANY**

**... BENTON HARBOR 15, MICHIGAN**

THE *New* 1952

# Heathkit VTVM KIT

MODEL V-5  
SHIPPING WT. 5 LBS.

## \$24.50

### Features

- New styling, — formed case for beauty.
- New truly compact size. Cabinet 4 1/8" deep by 4-11/16" wide by 7 3/8" high.
- Quality 200 microamp meter.
- New ohms battery holding clamp and spring clip — assurance of good electrical contact.
- Highest quality precision resistors in multiplier circuit.
- Calibrates on both AC and DC for maximum accuracy.
- Terrific coverage — reads from 1/2V to 1000V AC, 1/2V to 1000V DC, and .1 to over 1 billion ohms resistance.
- Large, clearly marked meter scales indicate ohms, AC Volts, DC Volts, and DB — has zero set mark for FM alignment.
- New styling presents attractive and professional appearance.

A real beauty — you'll have only highest praise for this NEW MODEL VACUUM TUBE VOLTMETER. Truly a beautiful little instrument — and it's more compact than any of our previous models. Note the new rounded edges on the front panel and rear cover. The size is greatly reduced to occupy a minimum of space on your workbench — yet the meter remains the same large size with plainly marked scales.

A set of specially designed control mounting brackets permit calibration to be performed with greatest ease — also makes for ease in wiring. New battery mounting clamp holds ohms battery tightly into place, and base spring clip insures a good connection to the ohms string of resistors.

The circuitry employs two vacuum tubes — A duo diode operating when AC voltage measurements are taken, and a twin triode in the circuit at all times. The cathode balancing circuit of the twin triode assures sensitive measurements, and yet offers complete protection to the meter movement. Makes the meter burn-out proof in a properly constructed instrument.

Quality components are used throughout — 1% precision resistors in the multiplier circuit — conservatively rated power transformer — Simpson meter movement — excellent positive detent, smooth acting switches — sturdy cabinet, etc.


And you can make a tremendous range of measurements — 1/2V to 1000V AC, 1/2V to 1000V DC, .1 to over 1 billion ohms, and DB. Has mid-scale zero level marking for quick FM alignment. DB scale in red for easy identification — all other scales a sharp, crisp black for for easy reading.

A four position selector switch allows operator to rapidly set the instrument for type of reading desired — positions include ACV, DC+V, DC-V, and Ohms. DC- position allows negative voltage to be rapidly taken. Zero adjust and ohms adjust controls are conveniently located on front panel.

Enjoy the numerous advantages of using a VTVM. Its high input impedance doesn't "load" circuits under test — therefore, assures more accurate and dependable readings in high impedance circuits such as resistance coupled amplifiers, AVC circuits, etc. Note the 30,000 VDC probe kit and the RF probe kit — available at low extra cost and specially designed for use with this instrument. With these two probes, you can make DC voltage measurements up to 30,000V, or make RF measurements — added usefulness to an already highly useful instrument.


The instructor manual is absolutely complete — contains a host of figures, pictorials, schematic, detailed step-by-step instructions, and circuit description. These clear, detailed instructions make assembly a cinch.

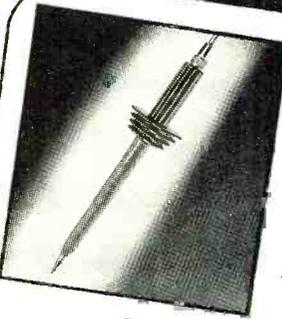And every part is included — meter, all controls, pilot light, switches, test leads, cabinet, instruction manual, etc.



**Heathkit 30,000V DC PROBE KIT**  
A new 30,000 V DC. Probe Kit to handle high voltages with safety. For TV service work and all other high voltage applications. Sleek looking — Two color molded plastic — Red body and guard — jet black handle — Red body with connector, cable, and PL55 type plug. Plugs into Heathkit VTVM so that 300V scale is conveniently multiplied by 100. Can be used with any standard 11 megohm VTVM. **\$550**

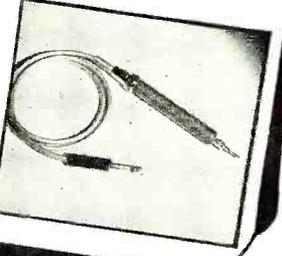No. 336 High Voltage Probe Kit  
Shipping Wt. 2 lbs.



**Heathkit RF PROBE KIT**  
This RF Probe Kit comes complete with probe housing, crystal diode detector, connector, lead and plug and all other parts plus clear assembly instructions. Extends range of Heathkit VTVM to 250 Mc. ± 10%. Works on any 11 megohm input VTVM. Specify No. 309 RF Probe Kit. **\$550**

Ship. Wt. 1 lb.

**YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE**

ROBEK INTERNATIONAL CORP.  
13 S. 48th ST.  
NEW YORK 17, N.Y.  
CABLE ADDRESS: ROKO

**The HEATH COMPANY**

**... BENTON HARBOR 15, MICHIGAN**

# Heathkit SIGNAL GENERATOR KIT

Model SG-6  
Shipping Wt. 7 lbs.

The new Heathkit Signal Generator Kit has dozens of improvements. Covers the extended range of 160 Kc to 50 megacycles on fundamentals and up to 150 megacycles on useful calibrated harmonics; makes this Heathkit ideal as a marker oscillator for TV. Output level can be conveniently set by means of both step attenuator and continuously variable output controls. Instrument has new miniature HF tubes to easily handle the high frequencies covered.

Uses 6C4 master oscillator and 6C4 sine wave audio oscillator. The kit is transformer operated and a husky selenium rectifier is used in the power supply. All coils are precision wound and checked for calibration making only one adjustment necessary for all bands.

New sine wave audio oscillator provides internal modulation and is also available for external audio testing. Switch provided allows the oscillator to be modulated by an external audio oscillator for fidelity testing of receivers. Comes complete, all tubes, cabinet, test leads, every part. The instruction manual has step-by-step instructions and pictorials. It's easy and fun to build a Heathkit Model SG-6 Signal Generator.




## Heathkit CONDENSER CHECKER KIT

Only  
**\$19.50**

Model C-2  
Shipping Wt. 6 lbs.

Checks all types of condensers — paper — mica — ceramic — electrolytic. All condenser scales are direct reading and require no charts or multipliers. Covers range of .00001 MFD to 1000 MFD. A Condenser Checker that anyone can read. A leakage test and polarizing voltage for 20 to 500 V provided. Measures power factor of electrolytics between 0% and 50% and reads resistance from 100 ohms to 5 megohms. The magic eye indicator makes testing easy.

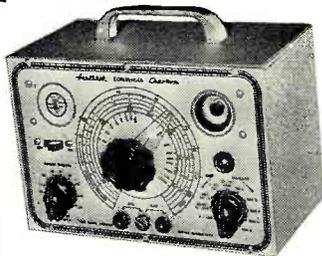The kit is 110V 60 cycle transformer operated and comes complete with rectifier tube, magic eye tube, cabinet, calibrated panel and all other parts. Has clear detailed instructions for assembly and use.




## NEW Heathkit SIGNAL AND UNIVERSAL TEST SPEAKER KIT

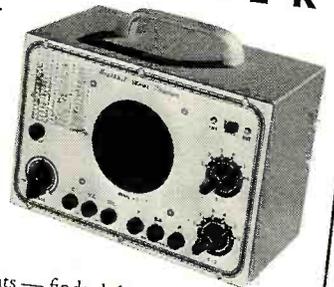**\$19.50**

Model T-2  
Shipping Wt. 7 lbs.

The popular Heathkit Signal Tracer has now been combined with a universal test speaker at no increase in price. The same high quality tracer follows signal from antenna to speaker — locates intermittents — finds defective parts quicker — saves valuable service time — gives greater income per service hour. Works equally well on broadcast, FM, or TV receivers. The test speaker has an assortment of switching ranges to match either push-pull or single output impedances. Also tests microphones, pickups and PA systems. Comes complete: cabinet, 110V 60 cycle power transformer, tubes, test probe, all necessary parts, and detailed instructions for assembly and use.



Model TC-1  
Shipping Wt. 12 lbs.

**\$29.50**

## Heathkit TUBE CHECKER KIT

The Tube Checker is a MUST for radio repair men. Often customers want to SEE tubes checked, and a checker like this builds customer confidence. In your repairing, you will have a multitude of tubes to check — quickly. The Heathkit tube checker will serve all these functions — it's good looking (with a polished birch cabinet and an attractive two color panel) — checks 4, 5, 6, 7 prong Octals, Loctals, 7 prong miniatures, 9 prong miniatures, pilot lights, and the Hytron 5 prong types. AND IT'S FAST TO OPERATE — the gear driven, free-running roll chart lists hundreds of tubes, and the smooth acting, simplified switching arrangement gives really rapid set-ups.

The testing arrangement is designed so that you will be able to test new tubes of the future — without even waiting for factory data — protection against obsolescence.

You can give tubes a thorough testing — checks for opens, shorts, each element individually, emission, and for filament continuity. A large BAD-?-GOOD meter scale is in three colors for easy reading and also has a "line-set" mark.

You'll find this tube checker kit a good investment — and it's only \$29.50.

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT  
ROCKE INTERNATIONAL CORP.  
13 E. 40th ST.  
NEW YORK CITY (16)  
CABLE: AREAB-N.Y.

The **HEATH COMPANY**

... BENTON HARBOR 15, MICHIGAN

RADIO & TELEVISION NEWS

NEW 1952 *Heathkit*  
**BATTERY ELIMINATOR  
 KIT**



- Can be used as battery charger.
- Continuously variable output 0 - 8 Volts — not switch type.
- Heavy duty Mallory 17 disk type magnesium copper sulfide rectifier.
- Automatic overload relay for maximum protection. Self-resetting type.
- Ideal for battery, aircraft and marine radios.
- Dual Volt and Ammeters read both voltage and amperage continually — no switching.

The new Heathkit Model BE-2 incorporates the best. Continuously variable output control is of the variable transformer type with smooth wiper type contacts.

There are no switches or steps and voltage between 0 and 8 Volts is available at 10 Amperes continuous and 15 Amperes intermittent. Maximum safety from overloads and shorts provided by automatic overload relay which resets itself when overload is removed.

The new rectifier is a 17 plate Mallory magnesium copper sulfide type. This is the most rugged type available for long trouble-free use.

Output is continuously metered by both a 0 - 10 Volt Voltmeter and a 0 - 15 Amp Ammeter. Shorted vibrators indicated instantly by ammeter.

Equip now for all types of service — aircraft — marine — auto and battery radios — this inexpensive instrument vastly increases service possibilities — better be ready when the customer walks in.

Model BE-3  
 Shipping Wt. 17 lbs.

NEW *Heathkit*  
**SINE AND SQUARE WAVE  
 AUDIO GENERATOR KIT**


Designed with versatility, usefulness, and dependability in mind, the AG-7 gives you the two most needed wave shapes right at your fingertips — the sine wave and the square wave.

The range switch and plainly calibrated frequency scale give rapid and easy frequency selection, and the output control permits setting the output to any desired level.

A high-low impedance switch sets the instrument for either high or low impedance output — on high to connect a high impedance load, and on low to work into a low impedance transformer with negligible DC resistance.

Coverage is from 20 to 20,000 cycles, and distortion is at a minimum — you can really trust the output wave shape.

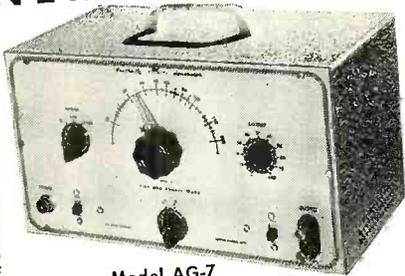Six tubes, quality 4 gang tuning condenser, power transformer, metal cased filter condenser, 1% precision resistors in the frequency determining circuit, and all other parts come with the kit — plus, a complete construction manual — A tremendous kit, and the price is truly low.



Model AG-7  
 Shipping Wt. 15 lbs.

**\$34.50**

THE NEW *Heathkit*  
**HANDITESTER KIT**

A precision portable volt-ohm milliammeter. Uses only high quality parts — All precision 1% resistors, three deck switch for trouble-free mounting of parts, specially designed battery mounting bracket, smooth acting ohm adjust control, beautiful molded bakelite case, 400 micro-amp meter movement, etc.

DC and AC voltage ranges 10 - 30 - 300 - 1000 - 5000V. Ohms range 0 - 3000 and 0 - 300,000. Range Milliamperes 0 - 10 Ma, 0 - 100 Ma. Easily assembled from complete instructions and pictorial diagrams.



**\$13.50**

Model M-1  
 Shipping Wt. 3 lbs.

NEW *Heathkit*

**T.V. ALIGNMENT GENERATOR KIT**

Here is an excellent TV Alignment Generator designed to do TV service work quickly, easily, and properly. The Model TS-2 when used in conjunction with an oscilloscope provides a means of correctly aligning television receivers.

The instrument provides a frequency modulated signal covering, in two bands, the range of 10 to 90 Mc. and 150 to 230 Mc. — ALL ALLOCATED TV CHANNELS AS WELL AS IF FREQUENCIES ARE COVERED.

An absorption type frequency marker covers from 20 to 75 Mc. in two ranges — therefore, you have a simple, convenient means of frequency checking of IF's, independent of oscillator calibration.

Sweep width is controlled from the front panel and covers a sweep deviation of 0-12 Mc. — all the sweep you could possibly need or want.

And still other excellent features are: Horizontal sweep voltage available at the front panel (and controlled with a phasing control — both step and continuously variable attenuation for setting the out put signal to the desired level — a convenient instrument stand-by position — vernier drive of both oscillator and marker tuning condensers — and blanking for establishing a single trace with base reference level. Make your work easier, save time, and repair with confidence — order your Heathkit TV Alignment Generator now!

Model TS-2  
 Shipping Wt. 20 lbs.

**\$39.50**



**YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE**

EXPORT AGENT  
**ROCKE INTERNATIONAL**  
 12 E. 40th ST.  
 NEW YORK CITY  
 CABE, ARLAB-N.Y.

*The* **HEATH COMPANY**

**... BENTON HARBOR 15, MICHIGAN**

# Heathkit IMPEDANCE BRIDGE KIT



Model 1B-1B  
Shipping Wt. 15 lbs.

**\$69.50**

This Impedance Bridge Kit is really a favorite with schools, industrial laboratories, and serious experimenters. An invaluable instrument for those doing electrical measurements work. Reads resistance from .01 Ohms to 10 meg., capacitance from .00001 to 100 MFD, inductance from 10 microhenries to 100 henries, dissipation factor from .002 to 1, and storage factor from 1 to 1000. And you don't have to worry about selecting the proper bridge circuit for the various measurements — the instrument automatically makes the correct circuit when you set up for taking the measurement you want. Bridge utilizes Wheatstone, Hay, Maxwell, and capacitance comparison circuits for the wide range and types of measurements possible. And it's self powered — has internal battery and 1000 cycle hummer. No external generator required — has provisions for external generator if measurements at other than 1000 cycles are desired. Kit utilizes only highest quality parts, General Radio main calibrated control.

Mallory ceramic switches, excellent 200 microamp zero center galvanometer, laboratory type binding posts with standard 3/4 inch centers, 1% precision ceramic-body type multiplier resistors, beautiful birch cabinet and ready calibrated panel. (Headphones not included.)

Take the guesswork out of electrical measurements — order your Heathkit Impedance Bridge kit today — you'll like it.

## Heathkit LABORATORY RESISTANCE DECADE KIT



**\$19.50**

Shipping Wt. 4 lbs.

An indispensable piece of laboratory equipment — the Heathkit Resistance Decade Kit gives you resistance settings from 1 to 99,999 ohms IN ONE OHM STEPS. For greatest accuracy, 1% precision ceramic-body type resistors and highest quality ceramic wafer switches are used.

Designed to match the Impedance Bridge above, the Resistance Decade Kit has a beautiful birch cabinet and attractive panel. It's easy to build, and comes complete with all parts and construction manual.

## Heathkit LABORATORY POWER SUPPLY KITS

*Limits:*

No load.....	Variable	150-400V DC
25 MA.....	Variable	30-310V DC
50 MA.....	Variable	25-250V DC

Higher loads: Voltage drops off proportionally




**\$29.50**

Model PS-1.....Ship. Wt. 20 lbs.

Every experimenter needs a good power supply for electronic setups of all kinds. This HV supply and a 6.3 V filament voltage source. Voltage control allows selection of HV output desired (continuously variable within limits outlined), and a Volts-Ma switch provides choice of output metering. A large plainly marked and direct reading meter scale indicates either DC voltage output in Volts or DC current output in Ma. (Range of meter 0-500V D.C., 0-200 Ma. D.C.). Instrument has convenient stand-by position and pilot light.

Comes with power transformer, filament transformer, meter, 5Y3 rectifier, two 1619 control tubes, completely punched and formed chassis, panel, cabinet, detailed construction manual, and all other parts to make the kit complete.
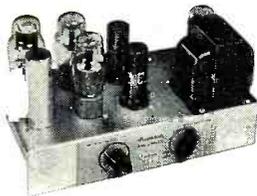
## Heathkit ECONOMY . . . 6 WATT AMPLIFIER KIT



Model A-4  
Ship. Wt. 8 lbs.

**\$12.50**

No. 304 12 inch speaker . . . **\$6.95**

This fine Heathkit Amplifier was designed to give quality reproduction and yet remain low in price. Has two preamp stages, phase inverter stage, and push-pull beam power output. Comes complete with six tubes, quality output transformer (to 3-4 ohm voice coil), husky cased power transformer and all other parts. Has tone and volume controls. Instruction manual has pictorial for easy assembly. Six watts output with response flat  $\pm 1\frac{1}{2}$  db from 50 to 15,000 cycles. A quality amplifier kit at a low price. Better build one.

## Heathkit HIGH FIDELITY . . . 20 WATT AMPLIFIER KIT



**\$33.50**

Shipping Wt. 18 lbs.

Our latest and finest amplifier — the model A-6 (or A-6A) is capable of a full 20 Watts of high fidelity output — good faithful reproduction made possible through careful circuit design and the use of only highest quality components. Frequency response within  $\pm 1$  db from 20-20,000 cycles. Distortion at 3 db below maximum power output (at 1000 cycles) is only .8%. The power transformer is rugged and conservatively rated and will deliver full plate and filament supply with ease. The output transformer was selected because of its exceptionally good frequency response and wide range of output impedances (4-8-16-150-600 ohms). Both are Chicago Transformers in drawn steel case for shielding and maximum protection to windings. The unit has dual tone controls to set the output for the tonal quality desired — treble control attenuates up to 15 db at 10,000 cycles — bass control gives bass boost up to 10 db at 50 cycles.

Tube complement consists of 5U4G rectifier, 6SJ7 voltage amplifier, 6SN7 amplifier and phase splitter, and two 6L6's in push-pull output. Comes complete with all parts and detailed construction manual. (Speaker not included.)

**MODEL A-6:** For tuner and crystal phono inputs. Has two position selector switch for convenient switching to type of input desired.

**MODEL A-6A:** Features an added 6SJ7 stage (preamplifier) for operating from variable reluctance cartridge phono pickup, mike input, and either tuner or standard crystal phono pickup. A three position selector switch provides flexible switching. **\$35.50**

Shipping Wt. 18 lbs.


YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER — USE ORDER BLANK ON LAST PAGE

EXPORT AGENT  
ROCKE INTERNATIONAL CORP.  
13 E. 40th ST.  
NEW YORK CITY (16)  
CABLE: ARLAB-N.Y.

The **HEATH COMPANY**

. . . BENTON HARBOR 15, MICHIGAN
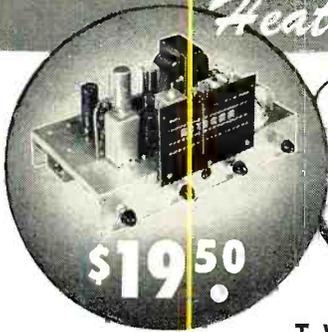
# Heathkit RECEIVER & TUNER KITS for AM and FM



Model BR-1 Broadcast Model Kit covers 550 to 1600 Kc. Shipping Wt. 10 lbs.

**\$19<sup>50</sup>**



Model AR-1 3 Band Receiver Kit covers 550 Kc. to over 20 Mc. continuous. Extremely high sensitivity. Shipping Wt. 10 lbs.

**\$23<sup>50</sup>**

## TWO HIGH QUALITY *Heathkit* SUPERHETERODYNE RECEIVER KITS

Two excellent Heathkits. Ideal for schools, replacement of worn out receivers, amateur and custom installations.

Both are transformer operated quality units. The best of materials used throughout—six inch calibrated slide rule dial—quality power output transformers—dual iron core shielded. I.F. coils—metal cased filter condenser. The chassis has phono input jacks, 110 Volt output for phono motor and there is a phono-radio switch on panel. A large metal panel simplifying installation in used console cabinets is included. Comes complete with tubes and instruction manual incorporating pictorials and step-by-step instructions (less speaker and cabinet). The three band model has simple coil turret which is assembled separately for ease of construction.



Model FM-2  
Ship. Wt. 9 lbs.

**\$22<sup>50</sup>**

## TRUE FM FROM *Heathkit* FM TUNER KIT

The Heathkit FM Tuner Model FM-2 was designed for best tonal reproduction. The circuit incorporates the most desirable FM features—true FM.

Utilizes 8 tubes: 7E5 Oscillator, 6SH7 mixer, two 6SH7 IF amplifiers, 6SH7 limiter, two 7C4 diodes as discriminator, and 6X5 rectifier.

The instrument is transformer operated making it safe for connection to any type receiver or amplifier. Has ready wound and adjusted RF coils, and 2 stages of 10.7 Mc IF (including limiter). A calibrated six inch slide rule dial has vernier drive for easy tuning. All parts and complete construction manual furnished.



MAIL TO THE  
**HEATH COMPANY**  
BENTON HARBOR 15,  
MICHIGAN

## ORDER BLANK

From \_\_\_\_\_  
\_\_\_\_\_

SHIP VIA

- Parcel Post
- Express
- Freight
- Best Way

Quantity	Item	Price	Quantity	Item	Price
	Heathkit Oscilloscope Kit — Model O-7			Heathkit H.V. Probe Kit — No. 336	
	Heathkit VTVM Kit — Model V-5			Heathkit R.F. Signal Gen. Kit — Model SG-6	
	Heathkit FM Tuner Kit — FM-2			Heathkit Condenser Checker Kit — Model C-2	
	Heathkit Broadcast Receiver Kit — Model BR-1			Heathkit Handitester Kit — Model M-1	
	Heathkit Three Band Receiver Kit—Model AR-1			Heathkit Power Supply Kit — Model PS-1	
	Heathkit Amplifier Kit — Model A-4			Heathkit Resistance Decade Kit — Model RD-1	
	Heathkit Amplifier Kit — Model A-6 (or A-6A)			Heathkit Impedance Bridge Kit — Model IB-1B	
	Heathkit Tube Checker Kit — Model TC-1			Heathkit A.C. VTVM-KIT — Model AV-1	
	Heathkit Audio Generator Kit — Model AG-7			Heathkit Intermodul. Analyzer Kit—Model IM-1	
	Heathkit Battery Eliminator Kit — Model BE-2			Heathkit Audio Freq. Meter Kit — Model AF-1	
	Heathkit Electronic Switch Kit — Model S-2			Heathkit Square Wave Gen. Kit — Model SQ-1	
	Heathkit T.V. Alignment Gen. Kit — TS-2				
	Heathkit Signal Tracer Kit — Model T-2				
	Heathkit R.F. Probe Kit — No. 309				

On Parcel Post Orders, include postage for weight shown and insurance. (We insure all shipments.)

On Express Orders, do not include transportation charges—they will be collected by the Express Agency at time of delivery.

Enclosed find  Check  Money Order for \_\_\_\_\_

Please ship C.O.D.  Postage enclosed for \_\_\_\_\_ lbs.

ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE

EXPORT AGENT  
**ROCKE INTERNATIONAL CORP.**  
15 E. 40th ST.  
NEW YORK CITY 16  
CALL: ARL-8-N.Y.

# The HEATH COMPANY

... BENTON HARBOR 15, MICHIGAN


# BUILT-IN HOME TV SYSTEMS

By  
**IRA KAMEN**  
Director of Sales  
Brach Manufacturing Corp.

**The steady increase in multi-set homes provides a new market for TV technicians.**

*Complete*  
**TUBE TESTER**  
and  
**SET ANALYZER**

**HICKOK**

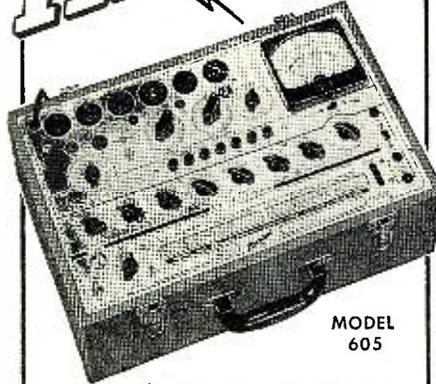

MODEL  
605

Lower cost . . . Handier size  
Ideal for house calls

**INCLUDES: HIGH SENSITIVITY  
MULTIMETER**

**YOU NEED THIS**—at a price of only \$12.60 more than the standard HICKOK Tube Tester you get a built-in multimeter that uses a vacuum tube for its rectifying element to provide a better multimeter than any other you can buy. Measures volts, resistance, current and also capacitance—a very important servicing measurement.

All this is included in addition to the HICKOK Dynamic Mutual Conductance Tube Tester circuits. The 605 is complete. Entirely built to the high HICKOK standards.

## DESIGN FEATURES

- Scale readings in micromhos for most accurate tube evaluation Ranges: 0-3,000, 6,000, 15,000 micromhos.
- HICKOK tube gas test.
- Tests tubes under simulated operating conditions.
- Contains all the latest tube sockets and complete built-in reference chart.
- Test leads included.
- Write for detailed information or see your HICKOK jobber today.

**THE HICKOK ELECTRICAL INSTRUMENT CO.**  
10524 Dupont Avenue • Cleveland 8, Ohio

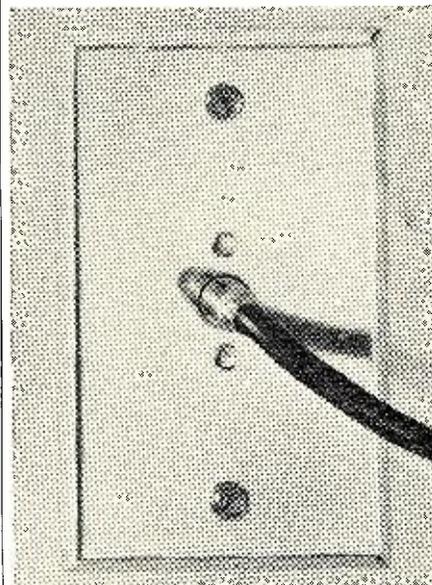


Fig. 1. Over-all view of the "Mul-Tel" unit which is designed to provide multiple outlets for single family dwellings. The box is placed out of sight near the antenna.

**N**OW that more and more families are keeping their small-screen television receivers as a second set, a new and profitable market has opened up for the technician.

The development of a small, home-sized master television and FM antenna system is expected to further stimulate consumer interest in retaining or purchasing a second receiver. Designed to be installed during the construction of a new dwelling or added to older structures, this unit provides four antenna outlets in the house, their locations being a matter of choice at the time of installation. Since the system also carries FM signals one of the outlets can be used in the room in which an FM receiver is to be connected. All

Fig. 2. Close-up of the receptacle which is the only part of system visible in room.



wiring is within the walls, the only visible evidence being the receptacle plate which appears on the wall at each of the four outlets. One such unit is shown in Fig. 2.

The key to this new system is the four-set coupler developed and produced by Brach Manufacturing Corporation. This simple device, shown in Fig. 1, is connected to any good antenna with a 300 ohm, ribbon-type transmission line. Four receptacles are provided at the bottom of the box's panel to accommodate four coaxial connectors, from which four coaxial lines run to the outlet locations.

The four outlets provide signals which are only 6 db lower than the signal from the antenna itself as the four-set coupler divides the antenna signal into four equal parts. None of the signal is dissipated in a dummy load, as is the case in resistor systems,


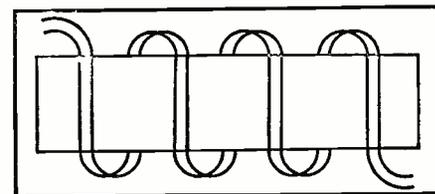


Fig. 3. How transmission lines are set up as bifilar windings around a coil form.

Fig. 4. Schematic of the four-set coupler.

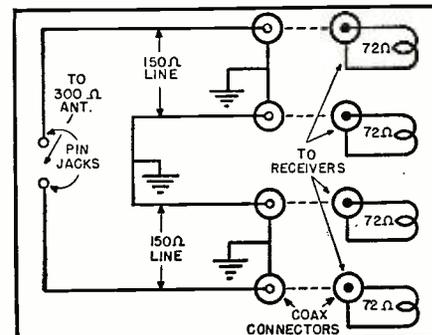

## DYNAMOTORS

Type	Input Volts Amps.	Output Volts Amps.	Radio Set
PE86	28 1.25	250 .060	RC 36
DM416	14 6.2	330 .170	RU 19
DM33A	28 7	540 .250	BC 456
PE101C	13/26 12.6	400 .135	SCR 515
		800 .020	
BD AR 93	28 3.25	375 .150	
23356	27 1.75	285 .075	APN-1
35CO458	28 1.2	250 .060	
ZA-085	12/24 4/2	500 .050	
ZA-056	12/24 8/4	12/275 3/110	Mark II
B-19 pack	12 9.4	275 .050	
D-104	12	225 .100	
		440 .200	
DA-3A	28 10	300 .060	SCR 522
		150 .010	
		14.5 .5	
5053	28 1.4	250 .060	APN-1
PE73CM	28 19	1000 .350	BC 375
CW21AAX	13 12.6	400 .135	
	26 6.3	800 .020	
		112 .110	
PE94	28 10	300 .200	SCR
		150 .010	522
		14.5 .5	

## SPECIAL CONVERTER

IN: 115VDC, OUT: 12/26VDC, 500V  
BRAND NEW..... \$99.50

## INVERTERS

PE 218-E: Input: 25 28 vdc. 92 amp. Output: 115 v, 350-500 cy. 1500 volt-amperes. Dim: 17"x6 1/2"x10". New (as shown)..... \$49.50

PE 218-H: Same as above except size: 16 1/2" x 6" x 10". New..... \$49.50

PE 206: Input: 28 vdc. 38 amps. Output: 80 v, 800 cy. 500 volt-amps. Dim: 13" x 5 1/2" x 10 1/2". New..... \$22.50

## SAVE THAT FINAL!!!

Variable overload protection with this new device. Continuously variable from 30 MA thru 250 MA, with dial marked at following points:  
30-35-40-45-50-60-75-100-150-200 MA  
Other intermediate points may easily be marked on polished dial. Husky Relay has DPST contacts that will handle 10 amps. May be used for grid-drive protection as well as in H-minus lead of HV supply, only 20V drop, completely enclosed in metal case, designed for front panel mounting. Size 5 1/2" H x 3 1/4" W x 2 3/4" D. Manufactured by Westinghouse and G. E. Thyrite protection. Brand new in original cartons. White Tray Last!..... \$3.95

**MOBILE CIRCUIT PROTECTOR**  
Klixon Type PM—opens at 35A. Thermal overload—won't pop off when starting. Miniature—easy Mtg..... \$0.59

## LINE FILTERS

LINE FILTER, GE 100 Amp Filter w/2x5Mfd 50V oil cond. Operates on 110VAC DC..... \$1.39

1KW LINE FILTER, clean up BC1 & TV1. Easy to Mount..... \$3.95

Noise Filter, Jx51E, 10 Amp..... \$1.29

Noise Filtr. Jx55D, 4 Amp..... 35c

## 932 PHOTO TUBE



Gas Phototube having S1 response, particularly sensitive to Red and Near Infrared Radiation. Can be used with incandescent light source. Send for Data..... 75c

## OIL CONDENSERS

Mfd.	Volts	Price
5	50	50.45
650	80	1.95
15	220AC	2.20
0.5	1000	.69
2x0.5	1000	.75
1	1000	.85
2	1000	.90
3x.01	1200	1.35
1	1500	1.30
1.5	1500	1.40
2	1500	1.45
2x0.1	2000	1.10
2x0.1	4800	1.20
0.1	6000	2.39
2x0.1	7000	3.75
0.1	7500	1.25
2x0.15	8000	4.75
.015	16000	8.95
.0016	15000	5.95
.25	20000	
1	25000	
.5	25000	
1	7500	

## SILVER MICA BUTTONS

MMF.	MMF.	MMF.
40	175	500
50	180	
100	185	

\$7.50 PER 100

## TEST SETS

TS 56A/AP	
TS 102/AP	
TS 62/AP	
TS 35/AP	
TS 12 UNIT 2	
TS 69/AP	
TS 33/AP	
CW60-ABM	
LU-1	
LU-3	
TS 159	
TS 226	
TS 89	
I-203-A	
TS 11/AP	
BC 438	
CS60-ABW	
I-158	
I-222	
I-185	
TS 268/U	

Send for Further Info. and Price

## MANY OTHERS


B-19 MK11 TRANS-RECEIVER  
Less Power Pack \$32.50  
B-19 Power Pack \$8.95

ID-24 ARN-9  
Dual 0-200 Microamp. Movement in 3" Case. ILS Equipment \$9.95



ARC5 MODULATOR  
MD7/ARC5 Plate Modulator w/dynamotor complete w/Tubes I-12J5, 2-1625, 1-VR50. Good cond. Price..... \$7.95

# "Communications"

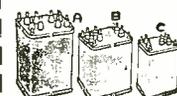

TRANSFORMERS  
ALL PRIMARIES  
115V, 60 CYCLE

## COMBINATION TRANSFORMERS

Stock No.	Rating	Price
CT-77B 5500V	.002 2.5V/2A, 12KV TEST, 6.3VCT/6A, 4600V TEST	\$12.95
CT-75B 1200VCT	600MA 2X5VCT/6.2A, 6.3VCT/3A, 6.3V/3A	14.95
CT-75-2 600VCT	200MA 5V/6A	4.95
CT-825 360VCT	.340 6.3VCT/3.6, 6.3VCT/3A	3.95
CT-626 1500V	.160 2.5/12, 30/100	9.95
CT-15A 350VCT	.070 6.3/6.6, 6.3/1.8, 3lbs.	2.95
CT-071 110V	.200 33/200, 5V/10, 2.5/10	4.95
CT-378 2300V	.4MA 2.5/10	6.95
CT-367 580VCT	.050 5VCT/3A	2.25
CT-721 550VCT	.100 6.3/1, 2.5VCT/2	2.95
CT-99A 2x110VCT	.010 6.3/1A, 2.5VCT/7A	3.25
CT-403 350VCT	.026MA 5V/3A	2.75
CT-610 1250V	.002MA 2.5V/2.1A, 2.5V/1.5A	4.95
CT-137 350VCT	.026MA 5V/3A	2.75
CT-456 390VCT	.30MA 6.3V/1.3A, 5V/3A	3.45
CT-160 800VCT	100MA 6.3V/1.2A, 5V/3A	4.95
CT-319 660VCT	.085A 5V/2A, 6.3/7.5A, 6.3/3A	3.25
CT-931 585VCT	.86MA 5V/3A, 6.3V/6A	4.95
CT-441 50-40V	200MA 110VCT/2A	2.75
CT-442 525VCT	.75MA 5V/2A, 10VCT/2A, 50V/200MA	3.85

**KLYSTRON TRANSFORMER**  
PRI: 115V, 60 CY.  
SEC: 1050V, 10MA, MINUS 625V/5MA, 26.3V/4.5MA, 2x2.5V/3A, 6.3V, 3A.  
Stock No. CT-341. Only a few left at..... \$22.45

## FILAMENT TRANSFORMERS

Stock	Rating	Price
FT-104	6V/5A	\$ 4.78
FT-924	3.25V/21A, 2x7.75V/6.5A, 2x26V/2.5A	17.95
FT-824	16V/1A, 7.2V/7A, 6.4V/10A, 6.4V/2A, 2x26V/2.5A	12.95
FT-357	9VCT/45A	14.75
FT-781	866 Trans. 2x2.5/5A	2.25
FT-674	8.1V/1.5A	1.10
FT-157	4V/16A, 2.5V/1.75A	2.95
FT-101	6V/25A	.79
FT-55-2	7.2V/21.5A, 6.5V/6.85A, 5V/6A, 5V/3A	8.95
FT-986	16V @ 4.5A or 12V @ 4.5A	3.75
FT-38A	6.3/2.5A, 2x2.5V/7A	4.19
FT-A27	2.5V/2.5A, 7V/7A, TAP 2.5V/2.5A, 16KV TEST	18.95
FT-340	2x2.5V/3A, 7V/7A—23KV TEST	24.95
FT-038	6.3V/500A, WELD	29.45
FT-364	6.3V/2A, 6.3V/4.5A	2.29

## PLATE TRANSFORMERS

Item	Rating	Each
PT-614	4730VCT/500MA, 12KV INS.	\$29.95
PT-976	Auto: 120VCT/10MA	.69
PT-31A	2 x 300V/5 MA	.79
PT-033	4150V/400 MA 1 1/2" x 9 1/4" W x 9" D 70 lbs.	49.95
PT-403	Auto: 70V/1A	2.29
PT-160	115VCT/770 MA, 590VCT/82 MA, 50 lbs.	24.95
PT-170	Auto: 156/146/137/125—71A	3.29
PT-31A	2 x 300V/5 MA	.79
PT-976	120VCT/10MA	.79
PT-12A	280VCT/1.2A	2.95
PT-919	1200-0-1200 200 MA	8.95

## SPECIAL FIL. TRANSFORMERS

Item	Pri.	Output	Price
STF-946	210/220/230	2.5V/4A, 3 1/2" H x 2 1/4" x 2 1/4" D.	\$ 1.29
STF-638	230	5V/9A, 5 1/2" H x 4 1/2" x 3 3/4"	1.25
STF-682	220	30-25-20V/1 MA	.69
STF-968	230	2.5V/6.5A	1.10
STF-405	230/115	5V/12/9A	2.95
STF-370	22/440	3 x 2.5V/57, 2.5V/15A 5 1/2" x 5 x 4 1/2"	5.25
STF-619	11/220	2.5V/500A, 7 x 5 1/4" x 5	19.95
STF-11A	220	2 x 40V/05/2 x 5V/6A, 12.6/1A	2.95
STF-631	230	2 x 5V/27A 2 x 5V/9A, 103/4H x 5 x 7 30 lbs.	24.95
STF-370	220/440V	3 x 2.5V/5A, 2.5V/15A	9.95
STF-085	220/440V	2.5V/60 ACT	15.95
STF-083	220/440V	5VCT/30A, 3000VTEST	17.50

## VARISTORS

D-167176	\$0.95
D-172155	2.25
D-172307	1.75
D-167208E	1.85
D-168687	.95
D-171812	.95
D-171528	.95
D-162356 (308A)	1.50

## THERMISTORS

D-166288	\$1.50
D-167332 (tube)	1.50
D-170396 (head)	1.50
D-167613 (button)	1.50
D-164699 for MTG	
"X" band Guide	2.50

## BC605 INTERPHONE AMPLIFIER

Easily converted to an ideal inter-communications set for office—home—or factory. Complete w/conversion diagram for 110V operation.  
Brand New..... \$4.75



## UNIVERSAL POWER TRANSFORMER

Pri: Vibrator Input @ 6/12/24/110VDC  
AC Input: 110/220V, @ 60 CY.  
Sec: 230-0-230V — 40MA, 6.3V I.S.A. Ea..... \$1.49

## "BEAM-BOOM"

A NATURAL FOR THAT NEW 2-OR-3 ELEMENT PLUMBERS DELIGHT 5 FT. LONG OF TUBULAR STEEL CONSTRUCTION. END BRACKETS FOR MOUNTING ELEMENTS. MAST MFG. CUP 3" DIAMETER. ONLY 20 LBS., NET WT. TAKE 'EM AWAY FOR ONLY..... \$4.95

## RADAR

APS-2	APN-4	QBF
APS-4	SCR-518	QBG
APS-10	SCR-545	QCJ
APS-15	FDMK-4	QCL
MA-SC-SN	AK-10	QCO

## RADIO

APN-4	QBF
SCR-518	QBG
SCR-545	QCJ
FDMK-4	QCL
AK-10	QCO

## SELENIUM RECTIFIERS

UP TO 18 VAC IN—	UP TO 14 VDC OUT
2A.....	5 2.50
4A.....	4 4.00
6A.....	6 6.00
10A.....	7 7.50
12A.....	8 9.00
24A.....	18 18.00
UP TO 36 VAC IN—	UP TO 28 VDC OUT
1A.....	5 3.00
2A.....	4 4.00
4A.....	8 8.00
10A.....	14 14.50
12A.....	18 18.00
24A.....	36 36.00
UP TO 54 VAC IN—	UP TO 42 VDC OUT
2A.....	56 56.50
4A.....	80 80.50
UP TO 120 VAC IN—	UP TO 100 VDC OUT
2A.....	111.00
10A.....	48.00
12A.....	60.00

## PRECISION RESISTORS

OHMS	OHMS	OHMS
5	150	7,000
5.05	250	10,500
10	430	12,000
18	468	17,000
82	800	20,000
120	920	30,000
125	1100	35,000
128	4300	84,000
30c EACH.....	10 FOR \$2.50	
100K 120K 150K 220K		
40c EACH.....	10 FOR \$3.50	
1 MEGOHM.....	EACH 75c	

## HI-FI UNIVERSAL OUTPUT TRANSFORMER

Amertran Silecor. PRI: 20,000/16,000/5000/4000 ohms. Sec: 500/15/7.5/5/3.75/1.25 ohms. 30 db. contin. Flat to 20,000 CY. w/Dialog..... \$4.75



## AUDIO TRANSFORMERS

AT501 HI-FI Special: PRI: 3000 ohms P-P/Sec: 4/16/12/50/200 ohms 60-10000 CY.—1 db 50W as shown.	\$3.49
AT152 HI-FI Driver PRI: 10,000 ohms Sec: 40,000 ohms PP Grids 50-15 KC/1 db.	\$1.49
AT063 Output to H.S. or line PRI: 14,200 ohms SEC: 8000/600 ohms	\$1.19
AT449 HI-FI Driver (5000 ohms) to P.P output grids (4,000 ohms) 100-10,000 CY 10 W. 6V6 to PP 805's	\$2.39
AT666 Intercom Input: Spkr (4-8 ohms) to grid (	



for flawless reproduction  
**NO OTHER CARTRIDGE CAN  
 PERFORM LIKE A PICKERING**

**patented design**  
 provides **DYNAMIC COUPLING\***  
 throughout the entire audible range

**\* DYNAMIC COUPLING ASSURES**

- constant stylus contact with the record grooves over the entire audio spectrum (20-20,000 cps)
- full frequency response
- full transient response

**NO RESONANCES  
 NO MISTRACKING  
 NO GRINDING OF GROOVE WALLS**

Pickering Cartridges transmit all of the sounds in the musical spectrum, without loss of definition, just as a fine optical lens passes all of the colors in the rainbow.

For literature address Dept. C

Well-informed engineers and technicians, schooled in the science of electro-mechanics, know that only wide-range frequency response provides full transient response; the electronic phenomena which enables the reproduction of orchestral music with all the subtle sounds that give each musical instrument its individual character.

Pickering engineers and designers have but one objective . . . to produce products that will please the music lovers' insatiable appetite for the flawless recreation of recorded music . . . for the utmost in quality insist upon Pickering Audio Components.



**FOR BETTER TOWERS  
 AT LOWER COST!  
 Ask about AERO**

- COST LESS**  
 Because AERO TOWERS are aircraft-designed, lower manufacturing costs and lower weight are passed on as savings to you.
- LAST LONGER**  
 Quality galvanized steel DIP-COATED inside and out with aluminum enamel keeps AERO TOWERS bright and new. Rust resistant—will not brown.
- STRONGER**  
 AERO TOWERS are ALL-TUBULAR in construction—the proven aircraft design for years of service.
- EASY TO CLIMB AND SERVICE**  
 Strong electric aircraft welds at EACH joint (not just one or two) prevent wavy. Tubular construction provides sturdy, safe, comfortable, ladder-like cross members.
- QUICKER TO INSTALL**  
 Aircraft precision tolerances assure accurate fit of components. Light and easy to erect. Strong durability and attractiveness assure customer satisfaction.

Ask about the "JIFFY"—a new, inexpensive tower for 20, 30 and 40 foot installations. Write for your nearest jobber.

**AERO TOWER DIVISION**  
 Knepper Aircraft Service  
 1016 Linden Street  
 Allentown, Pa.

LEOTONE • LEOTONE • LEOTONE • LEOTONE

**Leotone** Crystal Diodes!!  
 1N23, \$1.29; 10/10.00  
 Sq. Ceramic Insul., 1 x 1 x 1, 40 lbs.

8/32 thrd. 12c each . . . . . 10/.98  
 Radio Builders' Library for Beginner & Advanced Hams . . . 15 Sets of S.W. Receiver & Transmitter Construction Data for only . . . . . .98  
 AN-74A Blade Antennas (SCR-522), new . . . . . .69  
 1/20 H.P. GE Moto. . . . . 17.25  
 RPM, dble. 3/8" shaft. 110-110B VDC/7A O.D. 3/4"x5 1/2" . . . . . 2.95  
 W-110B Field Wire . . . . . 1/2c ft.  
 100-400 ft. only . . . . . 17.50  
 W-110B on original Steel Reels 1/2 Mile Reel (Wt. 80 lbs.) . . . . . 8.95  
 1 Mile Reel (Wt. 164 lbs.) . . . . . 17.50  
 Shpd. F.O.B. N.Y.C. cheapest way.  
 Rosette Screws . . . 12/19c; 100/1.25  
 6/32" . . . 12/19c; 100/1.25  
 Crystal Hand Mike . . . High Fidelity, hi-imped. Moulded black bakelite case. . . . . 3.95  
 Mike Chassis Connector (PCIM) sigle. cont. . . . . .15  
 Acoustic Celotex Cabinet Lining, 14x14 1/2" . . . . . .49

**TUBES!! TUBES!! TUBES!!**  
 90-Day Guarantee—Plain white cartons.  
 # 24, 27, 39, 41, 42, 55 or 89 . . . . . .39  
 23Y2, 6C5, 6F5, 6E5, 6J7, 6K7, 6SA7, 6SD7, 6SF5, 6SK7, 7, 7B or 85 . . . . . .49  
 1A7, 6A3, 6A8, 6F6, 6U7, 7A7, 7A4, 7A8, 7B6, 7B8, 7C5, 7Q7 or 3520 . . . . . .69  
 4-Screw Tight Strips . . . 3/\$1.00, 3-sect. 10/1.00  
 50L6 Outputs . . . strap mtg. . . . . .39c; 6/1.98  
 Ornamental Metal Grille . . . Gold finish diamond (2"x12"—98c; 16"x16"—\$1.59; 13"x18"—\$1.39; 18"x18"—\$1.98; 18"x24"—\$2.69; 24"x24"—\$3.75  
 3CP1 C-R Tube . . . calib. face. BRAND NEW . . . . . 2.95

Bargain Kits! . . . Speaker Cones . . . 4" to 12" incl. free-edge. Less Voice Coils. 12/\$1.98  
 Speaker Repair Kit . . . Liberal assortment of V.C. for use with Chamois Leather, Rings, Spiders, Cement, Shim Kit & Instructions. 2.49  
 Special—Both Cone & Repair Kits . . . only 3.95  
 Jumbo Radio Parts Kit . . . 17 Full Lbs. Coils, Sockets, Wire, Resistors, Condensers, Switch, Jacks, Chassis, etc., etc. . . Shpg. wt. 21 lbs. . . . . 3.95

Phono Turntable Flats . . brown. 10"/29c; 12"/50.39  
 Tube Cartons plain white. Prices per 100:  
 Min (1" sq. x 2 3/4")—\$1.20; CT (1 1/4" sq. x 3 1/4") 1.45  
 Med (1 1/2" sq. x 4 1/4")—\$1.65; Large (2" sq. x 5") 1.98  
 Experimental Tubes for Testing, Research, Schools. Fil. tested. 40 ass'd. revr. types. . . 1.98  
 "Ainico Magnet Special" . . . "U" type, polished. 3/4"x5/4"x3/8". . . . . 6/2.49  
 Ainico Magnet Kit . . . powerful Bar. Block. "U". Rod, etc. Kit of 10 ass'd. . . . . 1.98  
 Radio Hardware Treasure . . . Full lb. can of Nuts, Screws, Washers, Lugs, etc. . . . . 69c; 3/1.98

(WRITE FOR "AINICO MAGNET" SUPPLEMENT)  
 "FACTORY SPEAKER REPAIRS SINCE 1927"  
 Min. Order \$3.00 20% deposit on all C.O.D.'s  
 Please add sufficient postage—excess refunded  
 Full remittance with foreign orders

**LEOTONE RADIO CORP.**  
 67 Day Street  
 New York 7, N.Y.

LEOTONE • LEOTONE • LEOTONE • LEOTONE

since the coupler employs transmission-line techniques.

The four-set coupler contains two transmission lines, each of 150 ohms characteristic impedance. The circuit of this unit is shown schematically in Fig. 4. At the input end, the lines are in series with the center of the system, grounded for balance. The two 150 ohm lines, with input ends in series, constitute a 300 ohm impedance to match the 300 ohm antenna transmission line to which the input is connected.

The output end of each line has, of course, an impedance of 150 ohms. Across this impedance two 75 ohm (nominally 72 ohm) receiver inputs are connected in series, thus terminating each line in its characteristic impedance to prevent reflections. It is not necessary to have the receiver inputs facing an impedance of the "correct" value, since this does not cause reflections and the only result of the method used is to divide the energy appearing at the output end of each line in two, accounting for the 6 db signal loss in the forward direction between antenna and any receiver. If fewer than four receivers are used, the unused outlets should be terminated with a dummy load resistor. These are supplied with each coupler in the form of three dummy coaxial plugs with built-in resistors.

There were two major problems involved in the design of this unit, i.e., compressing the two transmission lines into a very small box, and introducing a large amount of high-pass filter action to prevent interference in the i.f. bands from passing through the system. Both problems have been solved at one stroke. The transmission lines are manufactured as bifilar windings around a coil form in the manner shown in Fig. 3. The spacing of the two wires determines the characteristic impedance of the line which is not altered by the fact that the winding appears to be a coil.

The fact remains, however, that it is a coil and as such it has a certain inductance and a certain distributed capacitance. These elements have been calculated so that they form a high-pass filter with a cut-off in the 50 mc. region. The filter action effectively prevents the passage of interfering signals below 50 mc.

The coupler as a whole might be considered as a transformer with a single 300 ohm primary and four 72 secondaries, preceded by an *m*-derived high-pass filter. It is not actually a transformer, however, and it has at least one very important advantage because of its unique method of impedance changing. The antenna looks into an impedance equal to its own (300 ohms) and the output end of each transmission line looks into an impedance equal to its own (150 ohms—two receivers in series). Thus there is a maximum transfer of energy from input to output of the system.

Energy radiated from the oscillator of any receiver and appearing at the antenna terminals does not feed back


# hallicrafters

**new communications "TOOL" for industry!**

the

*littlefone*<sup>®</sup>

**2-WAY FM RADIO-TELEPHONE**

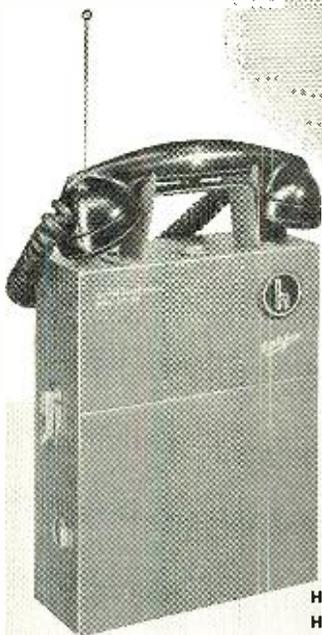

10 lb. lower powered models also available

**HAND CARRY**

HT-21 (25-50 Mc.)  
HT-22 (150-174 Mc.)

A new Hallicrafters product—the "littlefone"—is now ready for thousands of important uses in hundreds of industries.

This light, rugged, dependable radio-phone will be offered through Hallicrafters distribution organization—by the men who know communications best.

**USES OF "LITTLEFONE" CHALLENGE YOUR IMAGINATION!**

There are literally thousands of industrial uses for the "littlefone" radio—anywhere where powerful, dependable, "on the move" contact is required.

- FULL TWO-WATT ANTENNA OUTPUT\*
- Weighs only 14 pounds!
- Complete, self-contained 2-way radio-telephone station!
- Powered by Dry, or Wet Rechargeable Batteries (can be recharged from car battery or 117 Volts AC)
- Rugged, weatherproof
- 22 sub-miniature tubes!

\*On 25-50 Mc. • One-Watt output on 150-174 Mc.

**CENTRAL STATION**

HT-23 (25-50 Mc.) HT-24 (150-174 Mc.)

Same performance and specifications as the "Littlefone" Hand Carry.

- AC-operated Central Station
- Audio-amplifier, providing one watt of audio for loudspeaker
- Power consumption is 35 watts
- Plugs in any AC outlet (117 Volts)

Where one or more extra stationary receiving stations are desired, Hallicrafters economical S-81 receivers may be added.

**AMONG THE MORE IMPORTANT PRESENT USES ARE:**



- RAILROADING
- FREIGHT HANDLING
- WAREHOUSE OPERATIONS
- RANCHING & LARGE FARMS
- MINING (Above & Below Ground)
- PIPE LINE INSPECTION
- ROAD BUILDING
- SHIPPING (Dock Operations)
- CONSTRUCTION
- LUMBERING

**hallicrafters**  
*"The Radio Man's Radio"*

World's Leading Manufacturer of Precision Radio and Television — Chicago 24

**Snyder**  
PHILADELPHIA

**YEARS AHEAD**

**Directronic**  
MOTORLESS  
**TV AERIAL SYSTEMS**

**360° ELECTRONICALLY SWITCHED BEAM**

GIVES SAME CLEAR PIX AS MOTOR  
DRIVEN AERIALS AT  $\frac{1}{3}$  THE COST

SIMPLE FLICK OF SWITCH  
CLEARS PICTURE **INSTANTLY**  
**NO WAITING**





**OPENS BIGGEST  
REPLACEMENT MARKET  
IN TV HISTORY**

MAIL THIS COUPON TO-DAY!

**SNYDER MFG. CO.**  
22nd & Ontario Sts., Phila. 40, Pa.

Please send me free copy of authoritative  
booklet **TENNA TIPS** on Directronic and  
all other types of aerials, plus catalogs.

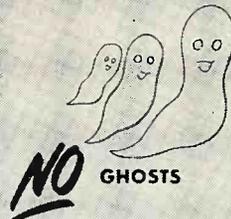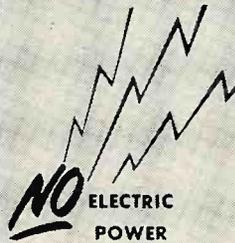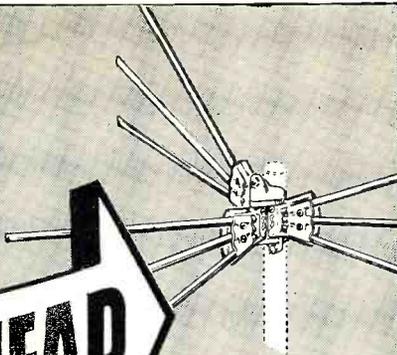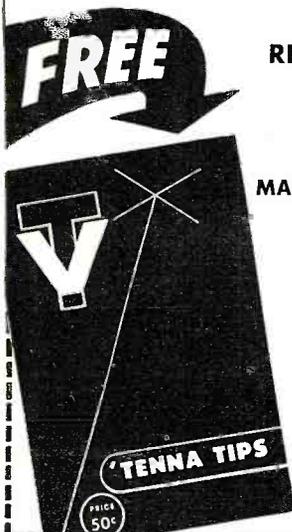NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_



through the system with anything like the same efficiency. The 75 ohm output of any receiver sees, not its own impedance of 75 ohms, but a high impedance composed of all the other impedances of the system in series, i.e., three 75 ohm receivers and a 300 ohm antenna for a total of 525 ohms, taking its own internal impedance into account, 600 ohms. The gross mismatch makes for very poor efficiency. As a result, oscillator re-radiation interference between one set and any of the others is greatly attenuated. While it is true that not all the re-radiation goes from the oscillator to the antenna of a receiver through the same path as the input signals and is not subject to quite the same impedance considerations, additional attenuation beyond that directly calculable takes place because the re-radiated oscillator signals do not find impedance matches anywhere and most of the energy is lost through reflection.

Even though most receivers are designed for 300 ohm inputs, the use of 75 ohm cable does not result in an appreciable loss of signal strength, especially if a good antenna has been installed on the roof. One to four receivers can be operated simultaneously, no matter to which channels they are tuned. This is so because, although there is only a 6 db loss of signal in the forward direction, there is a 16 db loss in the reverse direction, which is the isolation between receivers as far as oscillator radiation is concerned. In addition, the four-set coupler acts as a high pass filter to eliminate any interfering signals the antenna may pick up in the i.f. bands.

Working in cooperation with electrical contractors on original installations or independently in existing homes, the TV technician can add to his income by installing such multiple set systems. -50-

**TV IN ARGENTINA**

**ARGENTINA'S** first television station, which officially went on the air in Buenos Aires on October 17 of last year, is one of the largest and most modern in the world.

Operating on Channel 7, the new station features a 5 kw. transmitter and a unique 8-bay triangular loop antenna which gives the station an effective radiated power of 45 kw.

The transmitter equipment for this installation was furnished by Federal Telecommunication Laboratories, Inc., of Nutley, N. J. -50-

**NEW BRAZILIAN STATIONS**

**ORDERS** for three complete television stations and a microwave link have been placed with General Electric Company by the Brazilian radio chain, Emissoras Unidas.

Two of the television stations will be installed at Sao Paulo and one at Rio de Janeiro. This will make a total of three stations at Sao Paulo and two at Rio.

The microwave link will provide communication between Rio and Sao Paulo, a distance of over 200 miles. -50-

**RADIO & TELEVISION NEWS**

free

send for it

212-PAGE

# ALLIED Catalog



**the only complete up-to-date catalog for Everything in Radio, Television & Industrial Electronics**

Send for the Buying Guide that's used daily by thousands of service technicians, engineers, Amateurs, sound men, builders and experimenters. Make your selections from the world's largest stocks of quality equipment—at lowest money-saving prices. Get every buying advantage at ALLIED—speedy delivery, expert personal help, and complete satisfaction on every order. Make ALLIED your single, dependable source for electronic supplies.

SEND FOR FREE CATALOG

## ALLIED RADIO

ALLIED RADIO CORP., Dept. 1-AA-2  
833 W. Jackson Blvd., Chicago 7, Ill.

Send FREE 212-Page ALLIED Catalog

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

Zone \_\_\_\_\_ State \_\_\_\_\_

Information on conventional circuits, selenium cell ratings, typical selenium rectifier stacks, and data on stack connections is also included.

Engineers desiring copies of this catalogue should make their requests direct to the company.

### SIGNALING DEVICES

*Lee Electric Co.*, 132 Beckwith Avenue, Paterson, New Jersey, has recently released a new 8-page catalogue covering its line of signaling devices.

Included in the booklet is information on bells and buzzers, transformers, lamp ballasts, push-buttons and accessories, and other electrical specialties. The company will supply a copy of this catalogue to anyone making a request direct to the firm.

### SOUND SYSTEMS

*Bell Sound Systems, Inc.*, Columbus 7, Ohio, is currently offering copies of its new catalogue No. 5152.

This 20-page booklet carries data on the company's line of amplifiers, recorders, record players, portable p.a. systems, industrial equipment, intercommunication systems, accessories, speakers, and line matching transformers.

### B-A CATALOGUE

A new catalogue for dealers, technicians, hams, engineers, and experimenters has just been released by *Burstein-Applebee Co.*, 1012-14 McGee Street, Kansas City, Mo.

This 1952 catalogue contains 136 pages and lists thousands of items used in the radio and electronic fields. The listing includes amateur equipment, amplifiers, antennas and accessories, auto receivers, speaker baffles, batteries and plugs, cabinets of all

types, TV boosters, chassis, audio components, communications receivers, radio parts, servicing tools, tubes, hardware, kits, TV accessories, recorders, etc.

Copies of this handy catalogue are available from the company on request. Please ask for Catalogue No. 521.

### PARTS CATALOGUE

*Radiolab*, 1608-14 Grand, Kansas City 8, Missouri has just issued a comprehensive new catalogue for dealers, technicians, and manufacturers covering radio, television, and electronic parts.

Known as Catalogue 86, the new publication is a veritable handbook of components and equipment. The index is a particularly complete one and in addition to listing equipment by type, products are listed by manufacturers' names.

A copy of this 1952 catalogue will be forwarded upon written request to the company.

### INDUCTION HEATING BOOKLET

Westinghouse Electric Corporation has announced a new 12 page booklet on the subject of induction heating.

The booklet presents case histories of how induction heating has increased production from 50 to 2000 percent, reduced space requirements up to 90 percent, and cut production costs. It also tells how batch handling can be changed to in-line production methods and how in one case an induction heating machine handles 432 different parts.

A copy of this booklet, B-4782, may be had by addressing a request to *Westinghouse Electric Corporation*, Box 2099, Pittsburgh 30, Pa. -30-

The official opening of the 3d Armored Cavalry Regiment's MARS station recently gave Fort Meade its second MARS station. Dedicated by Col. James O. Curtiss, Jr., commanding officer of the 3d Cavalry Regiment, who sent a message to a detached element of his unit, the new station has been assigned MARS call letters AA3WAX and a regular ham call of K3WAX. Sgt. Stuart Robinson, regimental signal supply sergeant, is in charge of the new station and is seen at Col. Curtiss' left.





# PLATT WISHES YOU ALL A HAPPY NEW YEAR


**20 POUNDS OF ASSORTED RADIO PARTS**  
ONLY \$279



Once again Platt can offer this terrific bargain. The last time it was advertised, everything was sold out—but fast! So order today to be sure you get your supply.
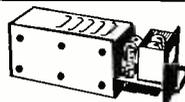
### TURBO AMPLIFIER

4 tube Amplifier used by U. S. Air Force. 115 V, input at 400 cycles. Without tubes—**BRAND NEW . . . . . SPECIAL \$1.49**



### TRANSMITTER-RECEIVER

Navy Model ABA-1 (CG-43AAG)  
Army Model SCR-515A, known as the BC-645  
450 MC  
15 Tubes



#### BRAND NEW—ORIGINAL CARTON

Can be easily converted for phone or CW 2-way communication. Covering for the following bands: 420-450 MC ham band, 450-460 MC for fixed or mobile, 460-470 MC for citizens, 470-500 MC television experimental. Size 10 1/2 x 13 1/2 x 4 3/4. Contains 15 tubes: 4—7F7, 4—7H7, 2—7E6, 2—6F6, 2—955, 1—WB-316A door knob. Complete as shown above.

ONLY \$24.95

### SHIP-TO-SHORE BC-223 TRANSMITTER



A 30 watt Transmitter, ideal for ship-to-shore or Ham Rig. Crystal or MO control on four preselected channels. 2000 to 5250 KC. Use of 3 plug-in coils, five tubes: 2—801 and 3—46, and TU 17-18-25 tuning units. TRANSMITTER . . . \$39.95  
TUBES . . . . . 5.95

TUNING UNITS . . . . . Each 4.25  
PE-125 VIBRATOR POWER SUPPLY FOR BC-223 . . . . . 18.95



**Field Telephones**  
Army surplus, completely reconditioned and electrically tested, using 2 flashlight cells and a pair of interconnecting wires. GUARANTEED like new.

\$20.95



**FL-8 RADIO FILTER**

Can easily be converted for use with many types of transmitters and receivers.

ONLY \$1.29



**AIRBORNE EQUIPMENT**  
Designed for Aircraft  
T-85/APT-5 UHF Transmitter Radar Set AN/APT-5 operates on 80 or 115 volts A.C. at 400 to 2600 cycles requiring 640 volts amperes at 0.90 power factor. Complete with all tubes. Brand new in original packing. **\$129.50**

### Radio Compass R5/ARN-1

Primarily used for aircraft navigation. Frequency range: 100 KC to 1750 KC in 4 bands. Operates on 115 volts, 400 cycles A.C. Complete installation consists of the following: Radio Compass Receiver R-5/ARN-7, Radio Control Box C4/ARN-7, Loop LP-21, Loop Dehydrator, Indicator I-81-A and I-82-A, Relay BK-22, Coupling MC-203, Cord CD-365, Plugs PL-112, 118, 122. Thoroughly tested and reconditioned by experienced personnel presently engaged in manufacturing for defense.



ONLY \$149.50

**... AND TO MAKE IT HAPPIER, HE CONTINUES HIS SENSATIONAL ANNIVERSARY BARGAIN SALE!**  
**5% OFF ANY PRICE IN THIS ADVERTISEMENT FOR EVERYONE!**



### OHMITE TAP SWITCHES

5, 6, 7, 8, 9, 10, 11 POSITION.  
All Porcelain—Vitreous Enamelled. 50 and 100 wattages.  
5, 6, 7, 8 POSITION . . . . . \$1.29  
9, 10, 11 POSITION . . . . . 1.69

### HEADSET H-16/U

8,000 ohms with adjustable head band and ear cups. Includes 2 Receiving Units.

ONLY \$395



### HEADSET ADAPTER MC-385

Used with headsets HS-33 or HS-38—raising the impedance from low to high. Comes complete with PL 55 Plug. . . . . ONLY 49c

### HEADSETS

HS-33 low impedance with cord and plug, used, fine condition. \$1.89  
HS-23 high impedance. BRAND NEW with ear pads. . . . . 4.25  
HS-33 low impedance. BRAND NEW with ear pads, cord and PL54 plug. 4.95  
HS-30 with ear plugs, low impedance, used, good condition. . . . . 1.69  
CD-307A Cords, 6 ft. NEW. . . . . .89



### TIME CLOCKS

12 and 24 hour cycle timing. Unlimited uses. Needs minor repairs. AN EXCELLENT BUY—HOW CAN YOU GO WRONG!

ONLY \$9.95



### BC-348 RECONDITIONED GUARANTEED LIKE NEW


All letters. Frequency Range 200 to 500 KC. 1 1/2 to 18 meg. OLD RELIABLE OF WORLD WAR II. SPECIAL: \$179.50



### ARMY TEST UNIT 1-236


Meter is contained in a metal box 5 1/2" long x 3 3/4" wide x 3 1/4" deep. Comes complete with test leads and instruction book. Can be used for testing between AC and DC measuring resistances of circuits, checking fuses and testing capacitors.

ONLY \$5.95

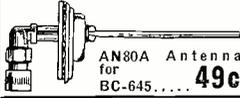

### AN80A Antenna BC-645 . . . . . 49c
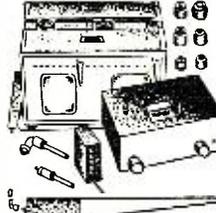
### VHF Excellently Reconditioned Guaranteed



### SCR-522 AIRBORNE COMMAND EQUIPMENT

Frequency Range 100 to 156 mcs. in 4 channels receiver and transmitter. Crystal controlled. Complete equipment. Consists of trans/rec. dynamotor PE-94. AN104 antenna, plugs, etc. Power input with PE-94 is 28 v.

Electrically Tested—Complete as Shown. Only \$99.50

### NOW! Fill Your Battery Only Twice a Year



with Automatic Battery Filler  
Made by leading Detroit Auto Mfr. Doubles battery life over ordinary care, prevents battery breakdowns, fits all cars, instantly installed.  
ONLY \$1.95 COMPLETE

### DUAL PURPOSE EMERGENCY UNIT




Made by leading Detroit Auto Mfr. Especially recommended for oil, gas and electrical fires. Guaranteed by mfr. against defects. Order two—one for your home; one for your car in case of flats or fires.  
ONLY \$2.29 each



### SCR-27N

### COMMAND and ARC-5 Equipment

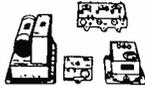

### RECEIVERS

	USED	NEW
BC-453-190 to 550 KC. . . . .	\$17.95	\$37.50
BC-454-3 to 4 MC. . . . .	11.95	18.95
BC-455-6 to 9 MC. . . . .	8.95	11.95

### TRANSMITTERS

BC-457-4 to 5.3 MC. . . . .	7.95	12.95
BC-458-5.3 to 7 MC. . . . .	8.95	13.95
BC-696-3 to 4 MC. . . . .	16.95	29.95
BC-459-7 to 9.1 MC. . . . .	16.95	27.50


### ADDITIONAL EQUIPMENT

BC-456 Modulator . . . . .	3.95	6.95
BC-450 Control Box (3 Receiver) . . . . .	1.49	2.95
BC-451 Control Box (Transmitter) . . . . .	1.29	2.45
BC-442 Relay Unit (ANT) . . . . .	2.95	3.95
Plugs: PL-147, 148, 151, 152, 153, 154, 155—EACH. . . . .	1.25	
Flexible Shafting with gear to fit Receivers . . . . .		1.69
3 Receiver Rack . . . . .	2.25	
2 Transmitter Rack . . . . .	1.69	
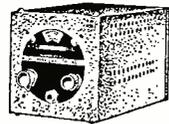
### BEACON RECEIVER BC-1206-C

Manufactured by Satchell-Carlson

Frequency Range—195 KC to 420 KC, IF Frequency—135 KC, Receiver Sensitivity—3 Microvolts for 10 Milliwatts output. Output Impedance—300 Ohms and 4000 Ohms to be selected internally. Power Output—230 Milliwatts, Volume Control—RF Gain Control, Power Supply—24-28 Volts Aeroplane Battery, Current—.75 Amperes.



BRAND NEW—ONLY \$10.95



### PRE-AMPLIFIER MODEL K-1

The K-1 is used to amplify output level for microphones and headphones. Operates on 24-28 VDC. Can be converted to 110 AC. Comes complete with PL 55 plug and 2 foot 119-B cord, 2 terminal blocks and instruction book.

BRAND NEW \$4.95



### SENSATIONAL SAVING! DYNAMOTOR

For DY-12 Power Supply for ART-13.

NOW ONLY \$19.95 complete

### Multimeter Foundation BIAS METER I-97A

Contains a zero center 3 1/2" round Marion voltmeter calibrated 0-100 volts each side. Movement is one mill each side of center. The unit is mounted in a steel box 7" x 5" x 4 1/2" and contains 8 contact push button, line cord dual 100 MFD at 200 V DC condenser, a potentiometer 6 1RC 1% wire wound non-inductive resistors: one 400 ohm, two 2500 ohm, one 5000 ohm, one 10,000 ohm, one 15,000 ohm. Excellent for building a zero center multimeter with ranges of 1, 10, 100, 1000 volt

COMPLETE BRAND NEW \$7.95



### T9/APQ-2 RADAR TRANSMITTER

80/115 V 400-260-26 VDC. Designed primarily for aircraft operation.  
NEW . . . . . \$42.50

### BC-221 Frequency Meter

Real Value! QUANTITY IS LIMITED—so first come, first served. They are just like new, with original calibration charts. Range 125-20,000 KC with crystal check points in all ranges. Complete with \$119.50 crystal and tubes. . . . .



VISIT PLATT'S RETAIL STORE, TOO!

**Minimum Order \$2.00**  
Immediate Delivery—Send 25% deposit on C.O.D. orders. All shipments F.O.B. N.Y.C. (N.Y.C. residents add sales tax to your remittance.)


## PLATT ELECTRONICS CORP.

DEPT. A, 489 BROOME ST., NEW YORK 13, N. Y.  
PHONES: WO 4-0827 and WO 4-0828

# University LOUDSPEAKERS


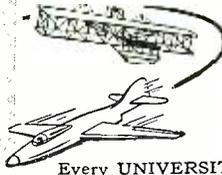
## Quality and Dependability

...designed by  
**PROGRESSIVE  
ENGINEERING!**


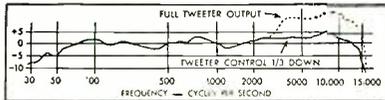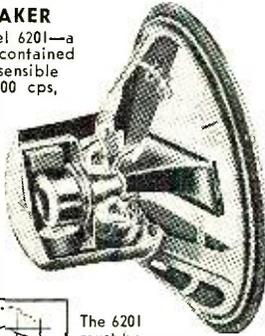
### MODEL 6201 COAXIAL SPEAKER

You'll find no compromise in the model 6201—a true coaxial system, completely self-contained with LQ network and attenuator, at a sensible price. Full range response 45 to 15,000 cps, power capacity 25 watts. Highest quality construction throughout—separate Alnico V tweeter driver, exclusive UNIVERSITY "W" shape Alnico V "woofer" magnet, special cone edge treatment for longer life, minimum distortion; and even the famous UNIVERSITY wide angle "Cobra" tweeter horn for uniform dispersion of the "highs." Variable attenuator adjusts "balance" to personal preference.



The 6201 must be heard to be appreciated

Every UNIVERSITY product is built to traditional standards of quality that have earned a world-wide reputation for absolute dependability. Highest quality materials, skillfully fabricated, result in unsurpassed performance and extra reliability. "Progressive Engineering" assures the latest design improvements in every piece of UNIVERSITY equipment.

Ask for your free copy of the **TECHNOLOG**

Handy technical catalog, published for engineers, installers, service men. Request yours today—write Desk 31



**UNIVERSITY  
LOUDSPEAKERS, INC**

80 10, KENSICO AVE., WHITE PLAINS, N. Y.

## The TURNTABLE is the **HEART** OF YOUR HIGH FIDELITY SYSTEM

You may own the finest pickup, amplifier and speaker that money can buy... yet you'll get poor reproduction if your TURNTABLE has excessive wow, hum or rumble! Rek-O-Kut offers a complete range of 12" Turntables, including models to match your individual amplification system and your individual pocketbook. Not every sound system requires the most expensive Turntable... your Turntable should be chosen to match your other equipment. Each REK-O-KUT Turntable Specification rates the DB Noise Level to enable you to select the appropriate machine to match your other components. Quality and workmanship of every REK-O-KUT Turntable is identical... price differential depends solely on type of materials used.

### MODEL LP-743 3-Speed 12" Turntable

Induction type motor, designed for smooth, vibration-free operation. Instantaneous speed changes without stopping turntable or removing disc. .... \$54.95 Net



### MODELS T-12H & T-43H - 2-Speed 12" Turntables

Recommended for use with ULTRA HIGH FIDELITY Amplifiers and Speaker Systems. The only 12" Turntable that meets N.A.B. specifications for speed regulations and Wow content.

MODELS	MOTOR	DB Noise Level	SPEED	PRICE
T-12 H*	Hysteresis Synchronous	-50DB	78-33 1/3	\$119.95
T-43 H*	Hysteresis Synchronous	-50DB	45-33 1/3	\$119.95
T-12 †	4 Pole induction	-40DB	78-33 1/3	\$84.95
T-43 †	4 Pole induction	-40DB	45-33 1/3	\$84.95

\*Delivery limited to short supply of Hysteresis motors.

## REK-O-KUT CO.

38-05 Queens Blvd., Long Island City, N. Y.

EXPORT DIVISION: 438 Broadway, New York City, U. S. A.  
CANADA: ARCAZ RADIO CORP., LTD., 150 King St. W., Toronto 58, Ontario

## PREMAX

# ANTENNAS



## For Civil Defense

Now that frequencies have been established, local directors are working up their nets, particularly on the 2-meter band. Low cost but thoroughly satisfactory antennas for fixed and mobile stations are available—products of the Premax engineers. Send for Bulletin and prices.

## PREMAX PRODUCTS

DIVISION CHISHOLM-RYDER CO., INC.

5105 Highland Ave., Niagara Falls, N. Y.

logue covering its complete line of PM speakers, electrodynamic speakers, units for TV replacement, auto radio replacement, p.a. applications, intercoms, and outdoor weatherproof speakers.

Complete data is given on the company's full line ranging from 2" to 15" units. Copies of the catalogue are available from the company without obligation.

### GC CATALOGUE

Of interest to radio and television technicians is the new 64-page 1952 catalogue just released by *General Cement Manufacturing Company* of 919 Taylor Avenue, Rockford, Illinois.

Designated catalogue No. 155, this handy new publication lists hundreds of radio and electronic products ranging from adhesives, tools, hardware, cabinets, accessories, etc., to wrenches and wrinkle varnish.

Copies of this new publication will be supplied free on request.

### SERVICING BOOKLET

The *Bendix Radio Division of Bendix Aviation Corporation*, Baltimore 4, Maryland, has begun the distribution of a cartoon booklet for television technicians entitled "Blue Book of TV Servicing."

The booklet contains 40 pages of "do's and don't's" and tips for TV technicians on how to get along with the customers he visits. Each point of servicing conduct has been illustrated by cartoonist Yardley of the "Baltimore Sunpapers" and "Pathfinder" newsmagazine. Printed in two colors, the booklet is of convenient size for easy reading.

### MILO CATALOGUE

*Milo Radio & Electronics Corp.*, 200 Greenwich Street, New York 7, N. Y., has just published a comprehensive 1100 page catalogue listing over 75,000 items in the industrial electronic, radio, television, sound, and broadcast fields.

This hard-cover catalogue deals specifically with items for the industrial field and includes listings of tubes, panel meters, laboratory test instruments, relays, switches, condensers, resistors, transformers, plugs, jacks, connectors, wire, metal chassis and cabinets, dials, knobs, voltage regulators, pilot light indicators, etc.

Distribution of this 1952 catalogue is confined to purchasing agents, chief engineers, and other company officials who make their requests direct to Dept. HK on company letterhead.

### SELENIUM RECTIFIERS

The Rectifier Division of *Sar'kes Tazian, Inc.*, 415 North College Avenue, Bloomington, Indiana, has just issued a comprehensive catalogue covering its line of power selenium rectifiers.

Designated PR1, the publication shows isothermal, frequency, and reverse current vs temperature curves in addition to data which heretofore has not been available in printed form.

**RADIO & TELEVISION NEWS**

# Manufacturers' Literature

Readers are asked to write directly to the manufacturer for the literature. By mentioning RADIO & TELEVISION NEWS, the issue and page, and enclosing the proper amount, when indicated, delay will be prevented.

## MANUAL SUPPLEMENT

A new TV control replacement manual supplement is now being offered to TV technicians by *Clarostat Mfg. Co., Inc.* of Dover, New Hampshire, through its regular jobbers.

The company issued a manual last spring listing standard and exact-duplicate controls available in its line. This new supplement provides a continuation of this listing.

The new supplement has been compiled to aid technicians in stocking and ordering controls. It lists by receiver manufacturer the frequency of use of the various controls. In this way the technician can carry the stock he needs to service the prevailing makes of receivers in his specific area.

## SERVICE NOTES BINDER

RCA tube distributors are now offering dealers and service technicians a three-ring leatherette binder designed for the filing of individual RCA Victor service data booklets.

A "bonus" plan has been devised whereby these binders may be obtained without charge. Details on how these binders may be secured are available from the company's tube distributors.

## SOUND CHART

*Newcomb Audio Products Co.*, 6824 Lexington Avenue, Hollywood 38, California, is currently offering copies of a new wall chart of impedance mismatch and line loss vs. line impedance and line length.

This handy chart will be sent to sound specialists and audio installation engineers without charge. In making requests for this publication please ask for Chart 103.

## MIDGET RELAYS

*Signal Engineering & Mfg. Co.*, 154 W. 14th St., New York, New York, has issued a new four-page bulletin which describes and illustrates its Series 80 line of midget telephone type relays.

The booklet contains information and drawings giving types of covers, characteristics, general specifications, and other pertinent data.

When requesting copies of this booklet, ask for Bulletin MTR-151.


## OXFORD CATALOGUE

*Oxford Electric Corporation*, 3911 South Michigan Avenue, Chicago 15, Illinois, has just published a new cata-

January, 1952

only \$67<sup>50</sup>  
for this

"Challenger"  
tube tester  
by JACKSON

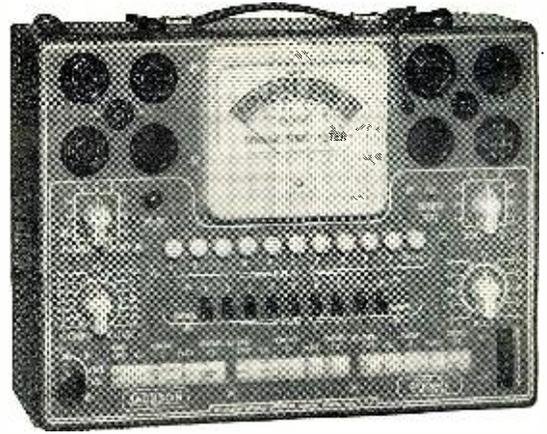

As the name implies, we ask you to compare our "Challenger" instruments with any and all others at anywhere near the price.

In the Model 115 "Challenger" Tube Tester, the famous Jackson *Dynamic*® test principle is employed. Separate voltages are applied to each tube element. Tests can be made under actual use conditions.

A feature of this instrument is the high voltage power supply. It affords more accurate results because of high plate voltages—over 200 v. for some types of tubes.


Spare socket positions are pro-

vided for future use, thus avoiding obsolescence. Push-button and selector switch controls simplify operation. The 4-inch-square meter is easy to read. The instrument gives complete short tests. It is applicable to over 700 types of tubes including TV amplifiers and rectifiers. The built-in roll chart is frequently revised to provide data on new tubes. This service is free for one year.

Finish is attractive Challenger Green with harmonizing knobs, meter cover, and push-buttons. Size, as of all "Challenger" instruments, is 13" x 9½" x 5½". Weight, 11 lbs.


Each of these "Challenger" instruments

\$59<sup>50</sup>

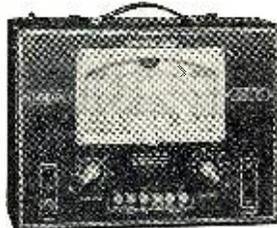

Condenser  
Tester  
Model  
112

Push-button controlled. Provides quick positive range selection for capacity and leakage tests. Shows up all types of faulty condensers, using a new method for detecting leakage. No need to count flashes on the electron ray tube indicator! Test voltages from 20 v. to 500 v. in six steps. Glass-enclosed dial with Jackson "Scale Expander" pointer which doubles effective scale length. Power factor measured on Direct Reading Scale calibrated from 0 to 60%. Ranges from .00001 to 1000 mfd in four steps.

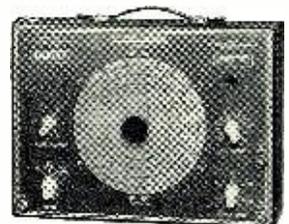

Test  
Oscillator  
Model  
106

Here's a "Challenger" instrument for testing AM and FM radios. It is also used as an auxiliary TV marker generator. Range of fundamental frequencies is 100 kc to 54 mc . . . Harmonics calibrated 54 mc to 216 mc. Two-circuit attenuator controls signal strength. 400 cycle audio modulation, or may be used for straight RF unmodulated signal. Accuracy is ½ of 1% in all ranges. Same finish and dimensions as other "Challenger" instruments. Compare this instrument with any low-priced signal generator or with any so-called kit.

**JACKSON ELECTRICAL INSTRUMENT CO.**

"Service Engineered"  
Test Equipment

DAYTON 2, OHIO

In Canada:  
The Canadian Marconi Co.

# AT LAST! TV RECEPTION UP TO 200 MILES

ON ACTUAL FIELD TESTS WITH

## NEW DX630 CHASSIS

will operate in fringe areas or in localities remote from TV broadcast stations up to 200 miles.

HAS 4 MICROVOLT SENSITIVITY—10 times any other TV receiver. Will pick up distant stations without use of boosters or special antenna arrays—and with less noise. Will operate any tube including 24", greater brilliance, improved keyed AGC circuit, (eliminating flickering and fading). Uses the best materials with a high factor of safety to insure trouble-free operation, STD. RTMA GUARANTEE free replacement of defective parts or tubes for 90 days. Completely factory wired chassis ready to operate with 12" P.M. Speaker.  
Price including excise tax..... **\$147.95**

## TELEVISION PICTURE TUBES

Standard makes, 6 months guarantee, all prices include 10% excise tax. (See ad for prices.)

## TELEVISION CABINETS

We have a large variety of table model, consoles and combination cabinets DESIGNED TO PLEASE the most discriminating tastes. Beautifully finished, mostly handrubbed available in mahogany, walnut, and blond colors. Table model (outside dimensions 23 3/4" x 24" x 24") price in mahogany for all sizes up to 20", including **\$34.95** mask, and 10% excise tax.....  
Extra for glass..... \$2.75

Console cabinet of beautiful design made of the finest veneers and good finish. Size 39" high x 24" wide x 22 3/4" deep finished. In mahogany or walnut. Cut for 630 chassis with 12" speaker will take either 16, 17, or 20" tube. **\$43.95**  
Price including mask and excise tax.  
Extra for glass..... \$2.75

For the various other cabinets in our large selection we will furnish photos and other NECESSARY INFORMATION, ON REQUEST. New Dumont conversion kit—see copy.

## TELEVISION COMPONENTS

Television 630 chassis pan all socket, transformer, etc. holes punched made of sturdy cadmium plated steel. Size—16" x 17" x 3 1/2". **\$3.95**

## TELEVISION PICTURE TUBES

### Standard Brands

SIX-MONTH GUARANTEE

12 1/2" (Black or White).....	\$23.95	Glass 16" Round (Black).....	\$34.50
Glass 14" Rectangular (Blk.).....	\$23.50	Glass 16" Rectangular (Blk.).....	\$34.50
17" Rectangular (Blk.).....	\$31.95		
19" Round (Blk.).....	\$39.95		
20" Rectangular (Blk.).....	\$39.95		
21" Rectangular (Blk.).....	\$42.95		
24" Metal.....	\$69.95		

### New—DuMont True Focus Conversion Kit

Convert your old set for even focus over entire screen!  
DuMont 70" Yoke, Model Y2A1—distributed winding..... \$6.57  
DuMont 70" Flyback Transformer Model H1A1..... 6.57  
DuMont Linearity control—for above units..... .75  
DuMont Width Coil for above units..... .75

## TELEVISION COMPONENT SPECIALS

"Faster Than Hotcakes!"

That's how these original 13-channel RCA Tuners are selling. Uses 3—6J6 tubes. Sold as is, less tubes and dial, only..... **\$3.95**

NEW DEFLECTION YOKE RCA 201D1, with network, only..... **\$1.95**

NEW FOCUS COIL 240 Ohms, RCA type 202D1 only..... **\$1.25**

NEW PM/EM FOCUS COIL, 1200 ohm winding only..... **\$ .89**

All Merchandise Subject to Prior Sale. All Prices Subject to Change without Notice.

WRITE FOR COMPLETE CATALOG N-1

# EDLIE ELECTRONICS INC.

154 Greenwich St. New York 6, New York

the booster input and then compare pictures with and without the booster. When you wish to show a fringe area customer the difference in fringe performance of various receivers, you can simulate fringe conditions right in the shop by using the attenuator pad shown in Figs. 3 and 6. Or if the fringe receiver requires peaking the video i.f. section you can do that in the shop, check the response curve on the oscilloscope and sweep generator and also check the picture with the attenuator inserted in the antenna lead-in. If excessively strong signals are received in a particular location it may be impractical to operate without an antenna because of strong ghosts. Connect the attenuator permanently to the antenna terminal of the set to avoid overloading, or, if other stations come in weaker, use a double-pole, double-throw switch to connect the attenuator into the circuit only when required.

As we stated in the beginning, the items described in this article are but a few of many which can be made by the technician at very little expense and which help to speed up and simplify TV repairs. Of those mentioned here, all can probably find more applications than we can think of and once they are available it is up to the technician to make the fullest use of them. A few minutes invested occasionally in working out a handy gadget or simple service tool will always be repaid by faster and more efficient television servicing. —30—


## TV LINK TO CANADA

**A**UTHORITY to build the U.S. end of the first international television link, between Buffalo, N.Y. and Toronto, Canada, has been granted to the Long Lines Department of the American Telephone and Telegraph Company by the FCC.

Antennas will be added to the Bell System microwave station at Buffalo to beam U.S. network programs across the border to a Toronto-Montreal relay system now under construction by Bell Telephone Company of Canada.

Bell of Canada has a 5 year contract with CBS to provide this service.

—30—

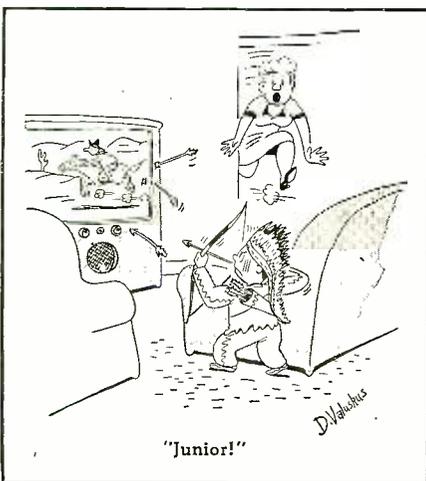

"Junior!"

# WINTER SALE PRICES SLASHED

Don't Buy Tubes until you get our prices. Quantities Limited. Prices Subject to Change Without Notice. Low Prices.

## RADIO & TELEVISION TUBES

These prices apply only on orders for 12 or more tubes. Orders for less than 12, write for quotation.

1B3—\$ .89	6BA6—\$ .72	6X4—\$ .48
1L4— .68	6BA7— .96	12AT6— .58
1R5— .78	6BE6— .72	12AT7— 1.08
1S5— .78	6BG6— 1.18	12AU6— .88
1T4— .78	6BH6— .80	12AU7— .78
1U4— .68	6BQ6— 1.18	12AX7— .88
1U5— .72	6CB6— .80	12BA6— .78
3Q4— .78	6CD6— 2.48	12BE6— .88
3S4— .78	6C4— .66	198G6— 1.78
3V4— .78	654— .72	19T8— 1.08
6AK5— 1.38	6D57— .98	25E06— 1.18
6AL5— .68	6SK7— .88	25L6— .68
6AQ5— .68	6SN7— .78	35C5— .68
6AT6— .58	6T8— 1.08	50C5— .68
6AU6— .68	6V6— .68	117Z3— .58
6AV6— .58	6W4— .68	

## All Other Types at Vast Reductions

Westinghouse Kuprox Rectifier 0.64 Amp. 28 Volts. Reg. \$11.00 ea. Special..... \$1.95  
TUBE SLIDE—2247-55-27-85-31-56-57. No Mixed Ass't. 6 of Any Type..... 2.25

12 BRAND NEW 10" PHONO RECORDS—Ass't. Jazz—Popular. Please specify..... \$1.79  
Single Pole—10 Pos. 2 Gang Switch..... .29c

## FRESH EVEREADY BATTERIES

### IN STOCK FOR PORTABLES, ETC.

'B'-'A' 'B' Batts.....	\$1.75	'A' Batts.....	70c
457.....	1.75	710.....	.39c
467.....	1.58	724.....	.42c
490.....	2.22	728.....	.49c
753.....	3.96	736.....	.60c
756.....	3.68	742.....	.74c
950 Flash Cells.....	4.03	746.....	.63c
		48 for.....	\$3.90

3 Ft. 5 Wire Shielded Cable with Amphenol Connection..... .8 for \$1.00

Signal Corps Phones—2 M. Ohms (8 M. Ohms Imp.)..... \$1.00

2 Ft. Ext. Cord (and Plug)..... 40c

2 MFD—1000 V Upright Bottom Lug Oil Cond..... .89c

## TOBE TUBULAR ELECTROLYTICS

20-20 MFD. 150 V..... .49c 30-30 MFD. 150 V..... .57c  
40-40 MFD. 150 V..... .59c

Low-Loss Short Wave Lock Type Air Trimmer Variable Condensers  
3 PL.—12-15 Mmfd. .12c  
7 PL.—25-30 Mmfd. .15c  
8 PL.—30-35 Mmfd. .16c  
14 PL.—56 Mmfd. .24c

D.P.D.T. SLIDE TOGGLE SWITCH..... 15c

4 PR. WAFER SOCKETS—\$1.49 per C. each..... .3c  
5-6 PRONG WAFER SOCKETS..... \$2.50 per C  
100 ASST. SOCKETS—4-5-6-7..... \$3.50 per C  
1,000 OHM WIRE WOUND POTENTIOMETER..... .15c  
30 HY-FILTER CHOKE SHIELDED..... .3 for \$1.25  
UNSHIELDED..... .3 for 1.00  
2,000 ohm Wire Wound Rheostats..... .24 per doz.  
CARTER WIRE WOUND C.T. VARIABLE 20 OHM RESISTORS..... .85c per doz.

PIEZO CRYSTAL HOLDERS, 12 for \$1.00—\$6.00 per hundred—\$50.00 per 1,000

RCA Band Switches—3 gang, 3 pos. 3 band. 30c 6 gang, 4 pos. 4-5 band. 40c

Trimmer-Padder Ass't.—all isolantite—singles, dual; triples—100 ast. pieces..... \$2.25

Philco push button Rotary Switch Double Pole..... .35c

ATTENTION: Prospectors, Explorers for Hidden Treasures! Construct a U.S. Army Type of Metallic Mine Detector Amplifier. Amplifier unit only (less tubes and batteries) with cables, headphone cord, and jack. Army wiring diagram. Type AN/PRS-1..... \$1.95

RCA Ass't. Mica By-Pass Cond. .001, 100 for..... .95c  
8 or 9 Gang Push Button Switch..... .49c

DRILLED CHASSIS FOR 5-6 tubes 5" x 10" x 1 1/2"..... .25c  
PHONE JACKS—OPEN & CLOSED AUTO..... .15c  
EBY SPEAKER VOL. CONTROL—60 OHMS..... .15c  
SALE—PHONO RECORD ALBUMS—12"—3 comp. 15c; 10"—3 comp.—15c; 4 comp. 20c; 12 comp. 69c

6 Prong Amphenol Sockets..... \$4.00 per C

AMERTRAN FILAMENT TRANSFORMER—6.3 V. 1 Amp. Encased Isolantite Terminal Posts..... \$1.50

VULCAN HEAVY DUTY 100 WATT SOLDERING IRON. Built for U.S.N.—Brand New—Equiv. sells for \$8.50..... OUR PRICE \$2.99

AMERTRAN AUDIO OUTPUT XFORMER—Pri. 10,000 @ 15 MA; Sec. 300, 6:1 Ratio..... \$1.49

AMERTRAN MIXER AUDIO XFORMER—Pri. 600-10,000 Ohms..... \$1.00

156-1 RATIO VERNIER DIALS—4 in., 3/8 in. Hub..... .35c

LINE VOLTAGE NOISE ELIMINATOR—Plugs in Between Radio and Elec. Socket..... .35c

HEARING AID CORDS—Assortment of 12 for..... \$1.00

BY-PASS COND. ASST.—25 Cans. Bakel. Paper, etc..... \$1.00

MINIMUM ORDER \$3.00—NO C.O.D. SHIPMENTS—PLEASE INCLUDE POSTAGE

## NEWARK SURPLUS MATERIALS CO.

Dept. DC  
324 Plane Street NEWARK 1, N. J.

**LOWEST  
PRICES**

# TUBES and PARTS

All TUBES are Guaranteed for one year... individually boxed...  
10% DISCOUNT on orders of 100 tubes or more... all brands

0Z4	59c	6AB7	\$1.15	6J5GT	\$ .54	7A6		12BE6	\$ .65	35B5	72c
0Z4G		6AC5GT		6J6	1.04	7A7	65c	12BF6	.59	35C5	
1A5GT	.65	6AC7	1.04	6J7G	.79	7A8		12BH7	.87	35L6GT	.59
1A7	.79	6AG5	.95	6J8G	1.15	7B4		12C8	1.15	35W4	.45
1B3GT	.95	6AG7	1.15	6K5GT	.87	7B5	.65	12F5GT		35Y4	59c
1B5		6AH6	1.40	6K6GT	.59	7B6	.65	12H6	65c	35Z3	59c
1C7G		6AK5	.87	6K7GT	.79	7B7	.65	12J5GT	.54	35Z4GT	54c
1E7		6AK6	.87	6K8GT	.87	7B8	.65	12K7GT	.79	35Z5GT	.95
1H6		6AL5	72c	6L5G	.95	7C4	1.15	12Q7GT	.65	35Z6G	.79
1H5GT	.65	6AQ5	.65	6L7	.87	7C5		12S87GT	.95	35 51	.79
1H6G	\$1.15	6AQ6	.59	6N6G	1.40	7C6	65c	12SA7GT	.72	41	
1J5GT	.95	6AR5	.54	6N7GT	87c	7C7		12SC7	.79	42	72c
1L4	.29	6AT6	.72	6P5GT	.65	7E6	.79	12SF7GT	72c	43	
1LA4		6AS5	.95	6Q7GT	.95	7E7	.95	12SF7		45	
1LA6	95c	6AU5GT	.65	6R7GT	.65	7F7	.79	12SH7GT	.79	45Z5GT	.59
1LC5		6AU6	59c	6S4	.65	7F8	1.15	12SJ7GT	.65	46	1.04
1LC6		6AV6	1.15	6S7GT	1.15	7G7	.95	12SK7GT	.72	47	
1LD5	.95	6B4G	1.15	6S8GT	.95	7H7	.72	12SL7GT	.87	50A5	.79
1LE3	.95	6B5	.79	6SA7GT	72c	7J7		12SN7GT	.79	50B5	72c
1LH4	.95	6B6G	1.15	6SC7	.79	7K7	95c	12SQ7	.54	50C5	1.04
1LN5	.95	6B8GT	.65	6SD7GT	1.04	7L7		12SQ7GT	.59	50L6GT	.59
1N5GT	.72	6BA6	.87	6SF5	.59	7N7	.79	12SR7GT	.79	70L7GT	1.40
1P5GT		6BA7	.72	6SF5GT	.65	7Q7	.72	12Z3	.95	50X6	.79
1Q5GT	95c	6BC5	.72	6SF7	.72	7R7	.79	14A7	.79	50Y6GT	.59
1R5		6BC7	.79	6SH7GT	.79	7S7		14AF7	.87	50Y7GT	.72
1S5	72c	6BD5GT	1.15	6SJ7	65c	7V7	95c	14B6	.87	71A	.87
1T4		6BE6	.65	6SJ7GT	.72	7W7		14B8	79c	75	
1U4		6BF5	.59	6SK7GT	.87	7X6	.79	14C5	.95	77	72c
1U5	.65	6BF6	1.29	6SL7GT	.79	7X7	.95	14C7	.87	78	
1X2A	.95	6BG6G	72c	6SN7GT	.54	7Y4		14C8	.79	80	.45
2A3	1.15	6BH6	59c	6SQ7	.59	7Z4	65c	14F7	.79	85	.79
2A5	.79	6BJ6	1.15	6SQ7GT	.65	12A7	1.15	14F8	1.15	117L7	
3LF4	.95	6BN6	1.58	6SR7GT	.72	12A8GT	.79	19BG6G	2.15	117N7GT	1.40
3Q4	.79	6BQ6	59c	6SS7	1.15	12AH7GT	.95	19T8	1.04	117P7GT	.54
3Q5GT	.87	6BQ7	.79	6T7G	.72	12AT6	.54	20	1.40	117Z3	.87
3S4		6C4	79c	6T8	.72	12AT7	1.04	24A	.79	807	1.95
3V4	72c	6C5GT	.65	6U5	.65	12AU6	.72	25AC5GT	1.04	813	9.95
5T4	\$1.40	6C6	1.69	6U6GT	.72	12AU7	.65	25BQ6GT	1.15	1294	29c
5U4G	.59	6C8G	.72	6U7G	.65	12AV6	.54	25L6GT	.59	1299	.45
5V4G	.87	6CB6	1.15	6V6GT	.72	12AV7	1.15	25W4GT	.72	1619	.45
5W4	59c	6CD6G	.79	6W4GT	.65	12AW6	.95	25X5	1.04	1629	.29
5W4GT		6D6	1.15	6X4	54c	12AX7	.87	25Z6GT	.79	2050	2.00
5X4G	.65	6D8G	.79	6X5GT	.87	12BA6	.65	32L7GT	1.15	2051	1.15
5Y3GT	.45	6E5	.79	6Y6G	.72	12BA7	.87	35A5	.59	7193	.87
5Y4G	.54	6F5GT	59c	7A4	.79					VT51	29c
5X4G	65c	6F6GT	1.15	7A5	.79					VT52	
5Z3	\$1.15	6F8G	.95								
6A3	.79	6G6G	.59								
6A8GT	.95	6H6	.65								
6AB5/6N5		6H6GT									

**TUBE SPECIALS!** 6AU6 ..... ea. 59c 6BG6G ..... ea. \$1.29  
12AU7 ..... ea. 65c 6CD6G ..... ea. \$1.69

**TUBE KITS**

**BEST BRANDS at BEST PRICES**

3Q4, 1T4, 1R5, 1S5, List Value \$8.00. Tube Kit only	\$2.39
3S4, 1T4, 1S5, 1R5, List Value \$7.80. 4 Tube Kit	\$2.39
1U4, 3S4, 1S5, 1R5, List Value \$7.80. All Four Tubes for	\$2.39
3V4, 1R5, 1S5, 1T4, List Value \$7.80. All for	\$2.39
117Z3, 1U5, 3V4, 1R5, 1T4, AC-DC Portable Kit. All for	\$2.89
12AT6, 12BA6, 12BE6, 35W4, 50B5, 5 Tubes for	\$2.95
50L6GT, 35Z5GT, 12SQ7GT, 12SK7GT, 5 Tubes for	\$3.22

**TWIN LEAD** 300 ohm twin lead 55 Web virgin polyethylene, in either clear or brown, the finest available. 100 ft. \$1850 | 100 ft. \$195  
**6 FOOT LINE CORD** will be scarce — UL approved cord and plug—10 for \$1.95  
Get our special sales bulletins... write TODAY!

**TV PICTURE TUBES**

Six month guarantee

10BP4	\$1295	16JP4	\$2995
12LP4	\$1695	16RP4	\$2995
12LP4A	\$1995	16TP4	\$2995
14PB4	\$2295	17BP4A	\$3195
7JP4	\$1795	19AP4A	\$3995

**FILTER CONDENSERS**

Any standard filter condenser you want—name your own prices and quantity!

**RESISTOR KITS**

Insulated 1/2, 1 and 2 watt assortment of most used values, best brands. 100 for \$3.95  
50 asst.—\$2.25

**RESISTORS**

You pick them, we ship them. Insulated—best U. S. brands.

ANY RESISTANCE In lots of 10

1/2 watt	20% 3 1/2c ea.	1 watt	20% 4 1/2c ea.
	10% 5c ea.		10% 7 1/2c ea.
	5% 9 1/2c ea.		5% 15c ea.
2 watt	20% 10 for 60c		
2 watt	10% 10 for 95c		
2 watt	5% 10 for \$2.15		

TERMS: 20% DEPOSIT with order, balance C. O. D. \$1.00 handling charge for orders less than \$5.00. All shipments F. O. B. Chicago. Our parts and tubes are warranted to be 100% replacements for the prototypes in the listings above. Prices are subject to revision without notice. SATISFACTION GUARANTEED. Illinois residents add 2% sales tax. ORDER TODAY!

**Premier RADIO TUBE CO.** 551 W. Randolph St. Chicago 6, Illinois ANdover 3-1590

(Advertisement)



## Frank J. Moch

president of the  
National Alliance of Television  
and Electronics Service Associa-  
tions.

says:  
"there is no other  
Oscilloscope like the

### Simpson MODEL 476 MIRROSCOPE"

Simpson Model 476 MIRROSCOPE reflects the 5-inch cathode ray tube image on a high grade mirror mounted in the cover allowing the tube to be vertically mounted which reduces bench space requirements to 9" x 8" and brings the viewing surface to eye level. The upright construction permits location of controls and connections for maximum convenience and allows for internal cathode ray tube connections at the front of the panel. The unique construction and superior specifications of the Model 476 make it worthy of leading experts' recommendation for all phases of TV receiver service including observation and diagnosis of Sync signals. For complete information see your Parts Jobber or write: SIMPSON ELECTRIC CO., 5200 W. KINZIE ST., CHICAGO 44, COLUMBUS 1-1221.



## Shirt Pocket Radio

(Continued from page 44)

is required. If the regeneration control is advanced to maximum, this station may be heard clearly all over the room if the headphone is held in the cupped hand. For weak signals and also those at the extreme low frequency end of the broadcast band more care is required in tuning. For best results, first tune the station for best reception without adjusting the regeneration. Next, advance the regeneration control until the detector just oscillates, as will be evidenced by a slight rushing sound. Then back off the regeneration control until the rushing stops. Now retune the station, which will now be at its maximum volume. Using this method, the author has received (in the daytime) station WTMJ in Milwaukee, a distance of 85 miles. Its signal could be called "barely understandable," but nevertheless audible. Station WIND whose transmitter is in Gary, Indiana, a distance of 40 miles, can be heard easily. At night, reception is not limited to locals. The original set has "pulled in" large, clear channel stations from as far as 400 miles away!

It will be noted that the antenna is bi-directional. If the set is rotated until the signal fades completely, then the knobs point either towards or directly away from the station being received. This could conceivably serve as a kind of radio direction finder for a person lost in the woods, provided he were able to tell general directions. For purposes of general reception, the directivity of the antenna bothers us little, as the nulls are very sharp, whereas the peaks are very broad. This means that a given station can be received over about 340 degrees rotation of the set. There will be two ten degree nulls where the station fades out. This is not objectionable, as one may turn a corner while listening, and very seldom hit the ten degree null!!

### Litz Wire Loops

The performance of the receiver, as outlined in this article, is good. However, there is one way that it may be improved, *i.e.*, introduce a larger signal at the input grid! The signal pick-up of a loop antenna is proportional to the area thereof. However the *voltage* across any tuned circuit, loop antennas included, is also proportional to the "Q" of the circuit. "Q" is the ratio of the reactance to the resistance of a coil. To raise the "Q" of the antenna loop, it is only necessary to use a heavy litz wire. By using 35-44 litz wire, the "Q" of the antenna is raised from 75 to 220. The signal delivered by such an antenna will be almost three times that delivered by one wound with #30 solid wire. The author has not specified litz wire for the loop in this article, due to the general unavailability of litz, however, he recommends it highly to those who may

be able to get some. Use 20-44 to 55-44 single silk enameled for best results. If the highest possible performance is desired, the set may be redesigned mechanically so that the "A" cell, switch, and tuning condensers are outside the loop. The "shorted turn" effect of these components will materially affect the "Q" of a loop wound of litz reducing its efficiency as much as 40%. Do not use small litz wires, such as 5-44 or 10-44. They are virtually no better than solid wire and the additional difficulty in handling these sizes is not justified by any notable increase in performance.

-30-

## Service Aids

(Continued from page 51)

shown in Figs. 3 and 6. Basically this is a two-section balanced attenuator giving a total attenuation of approximately 35 db, unshielded, up to about 220 mc. For convenience we have mounted the resistors on an insulating board and added a set of alligator clips in such a manner that they fit all standard TV antenna terminals. *Scotch* tape helps keep the clips in place and prevents them from shorting to the chassis. The input and output impedance of the attenuator is normally about 300 ohms, but by shorting out the two series resistors in each lead, a 50 ohm input or output can be achieved.

The application of this attenuator lies mostly in checking TV receiver sensitivity and fringe area operation. In many instances a technician may get strong signals at his shop, but service receivers in a weak signal area. By connecting this attenuator between the antenna lead-in and the receiver under test, weak signals will be obtained. Occasionally a set will tend to be regenerative under weak signals and bench testing is difficult because strong signals are found at the shop. Using only one side of the antenna is not always permissible because unbalance occurs and in many receivers unbalanced input will greatly alter the response of the r.f. tuner. Using this attenuator reduces the signal to any desired level while maintaining proper balance and impedance match. If the circuit shown in Fig. 3, gives too much attenuation, remove one set of resistors and use only one I-section. On the other hand, if more attenuation is desired, another section can be added.

Other applications of this balanced attenuator network include signal reduction to avoid overloading on one particularly strong station, demonstrating sensitivity characteristics of different receivers, and checking booster operation. When a booster is connected to a receiver having an efficient automatic gain control circuit, little difference will be observed as long as strong signals are received. Often a booster is tagged as weak for that reason. To check its performance under weak signal conditions, connect the attenuator pad between the antenna and





# MAKE MONEY

with the aid of the new

## TRANSVISION CR TUBE TESTER - REACTIVATOR

performs 2 vital functions:

- Tests Picture Tubes
- Renews Brightness of Many Dim Picture Tubes



### It's a TESTER:

Without removing picture tube from set, you apply this precise instrument to:—

- Measure Cathode emission
- Locate shorts between elements
- Locate high resistance shorts or leakage as high as 3 megohms

### It's a REACTIVATOR for dim CR Picture Tubes


Revives dim TV Picture Tubes, without removal of tubes from sets. Works on a great many tubes with low light output, if there's no mechanical defect in tube. 110 V—60 cycles. Portable, weighs only 3 lbs. One or two applications pays for instrument.

**SATISFACTION GUARANTEED**  
or money refunded if you return the instrument in 10 days in good condition. **\$19.95** NET
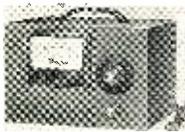
### FIELD STRENGTH METER at NEW LOW PRICE:

**\$59** net

Improves TV Installations; saves half the work. Model FSM-1, complete with tubes, \$59 net.



## SAVE ON PICTURE TUBES

Direct from Factory!

Amazing new LOW PRICES on all sizes Picture Tubes with Transvision's 2 YEAR FACTORY GUARANTEE, pre-rated.

Send for Price List Now!

**FREE:** Sample copy of "TV and Electronics Notes." Or send 50c to cover cost of addressograph plate and mailing for FREE Subscription. Monthly issues are gold mines of info on new devices, conversion, sales, service, etc.

## TRANSVISION, INC.

Dept. RN NEW ROCHELLE, N. Y.


January, 1952

easily integrated with the speaker mounting bracket and no extra fastenings are needed.

Two models are currently available—the Model T-11 with primary taps for 500, 1000, 1500, and 2000 ohms, and secondary windings of 4 and 8 ohms. The Model T-12 has a primary of 45 ohms and a secondary of 4 and 8 ohms. Both models will handle 12 watts.
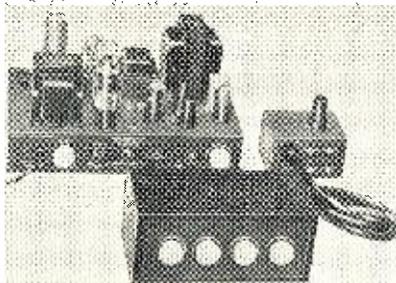
### BOGEN AMPLIFIER

A new high fidelity amplifier and remote control unit have been an-



nounced by David Bogen Company, Inc., 663 Broadway, New York 12, New York.

The Model H010 power amplifier and the Model RXPX remote controller and preamplifier provide quality music reproduction for the serious listener. The H010 is an all-triode amplifier rated at 10 watts output. It delivers its full rated output with less than 1.3% distortion over the entire frequency range from 20 to 20,000 cps.


The remote controller and preamplifier provides full control of function selection, volume, tone, and record equalization at distances up to 25 feet from the amplifier.

Detailed specifications on either or both of these units will be furnished by the company on request.
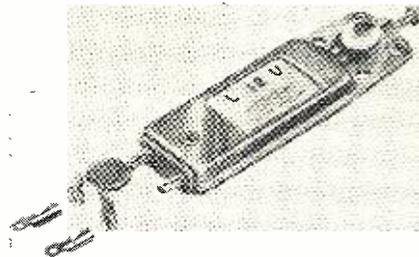
### PICKUP CARTRIDGE

The Astatic Corporation, Conneaut, Ohio, has developed a new phonograph pickup cartridge employing a condenser harness which slips on or off the terminals to change the output from a high of 4 volts to a low of 1.2 volts at 1000 cps.

The L-12-U may be used as a replacement for more than 125 different standard 78 rpm cartridges now in use. Another feature of this dual-output



cartridge is a needle chuck limiting principle which restricts motion of the chuck both radially and lengthwise. This feature helps to prevent dislocation of the chuck and to protect against

(Continued on page 112)


# TRANSVISION

## SAVE UP TO 50% on TV Kits, Sets, Chassis DIRECT from FACTORY

Beautiful TV CONSOLES for  
CUSTOM-BUILDING or for  
CONVERSION


from  
**\$49**

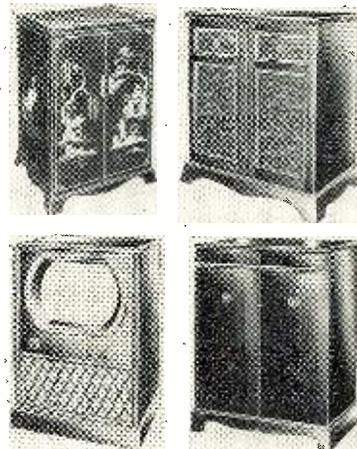Enjoy GIANT SCREEN TV  
now. Send for Cabinet Catalog. Conversion instructions come with every cabinet.



### FEED Up to 5 TV SETS from 1 Antenna with

TRANSVISION'S  
MULTI-SET  
CONNECTORS

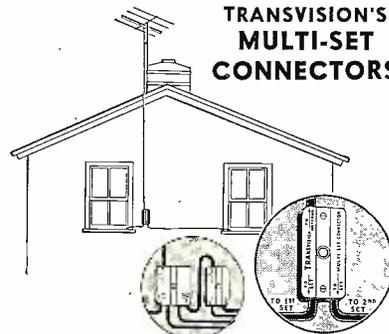

Increase Sales with Multi-Set Connectors. Ideal for homes, garden apartments, TV dealers, bars, etc. Big savings in time and labor. Guaranteed! PRICES: Multi-Set Conn. for 2 sets, \$4.95 list. \* Multi-Set Conn. for 3 or 4 sets, \$7.95 list. \*

\* Dealers, write for discounts

Write for details on amazing Transvision FACTORY AGENT PLAN!

**FREE:** Sample copy of "TV and Electronics Notes." Or send 50c to cover cost of addressograph plate and mailing for FREE Subscription. Monthly issues are gold mines of info on new devices, conversion, sales, service, etc. WRITE FOR IT TODAY!

## TRANSVISION, INC.

Dept. RN NEW ROCHELLE, N. Y.

# COMPARE OUR PRICES!

These are all top standard brands. Many in Original Factory Boxes. All individually boxed.

**FREE!** Introductory offer. One roll, 60 ft. Bull-Dog Friction Tape with each \$10.00 order or more.

## STANDARD BRANDS

024	\$.72	68C5	\$.95	12AUG	\$.90
183	\$.95	68E6	\$.80	12AU7	\$.90
1R5	\$.85	68G6	1.90	12AV6	1.35
155	\$.85	68J6	\$.85	12BA6	1.35
174	\$.90	68N6	1.40	12BB6	1.35
1U4	\$.80	68Q6	1.20	12BE6	1.35
1U5	\$.80	6C4	\$.80	12B7	1.35
3V4	1.05	6CB6	\$.90	12K8	1.00
3Q4	\$.95	6CD6	2.40	12S7	1.00
3Q5	1.10	6H6	\$.85	12SA7	1.80
3V5	1.00	6J5	\$.65	12SB7	1.80
5U4	\$.66	6J6	1.15	12SN7	1.00
5V4	1.10	6K6	\$.80	12SOT	1.75
5Y3	1.50	6S4	\$.80	19B6	2.40
6AB4	\$.95	6SA7	\$.80	25A7	1.80
6AC5	1.15	6SW7	\$.65	25B7	1.80
6AG5	1.06	6SK7	\$.75	32L7	1.28
6AG7	1.25	6SN7	\$.85	35B5	1.90
6AH5	1.00	6T7	\$.70	35L6	1.90
6AK5	1.95	6T8	1.25	35W4	1.60
6AL5	\$.65	6V6GT	\$.80	35Z5	1.65
6AQ5	1.15	6W4	\$.47	50A5	1.00
6AR5	\$.75	6W6	\$.90	50B5	1.00
6AT6	\$.70	6X5	\$.60	50C5	1.00
6AU6	\$.65	6Y6	\$.95	50L6	1.00
6AV6	\$.70	12AT6	1.65	57	1.00
6BA6	\$.75	12AT7	1.10		

Order other types not listed, our prices are lower!

## TELEVISION ANTENNAE

CONICAL 8 ELEMENT—4 elements, 4 reflectors high gain, all channel for general use.	\$2.99
Packed 6 to a carton	\$.50 ea.
Less than 6	\$.35 ea.
DOUBLE BAY CONICAL—with stacking rods, 4 elements, 4 reflectors per bay. Two stacks with 1/4 wave connecting bars. Solves fringe area problems.	\$6.58
Packed 6 to a carton	\$.69 ea.
Less than 6	\$.59 ea.
FOLDED HI-LO	\$2.99
	\$.99 ea.
INDOOR V—Individually cartoned	\$1.99

## ANTENNAE ACCESSORIES

CHIMNEY MOUNTS, Special	\$.99
3 1/2" WALL MOUNT, Special	\$.29
7" WALL MOUNT, Special	\$.89
12" EAVE BRACKET, Special	1.99
EAVE MOUNT (15") Heavyweight	2.25 pr.
EAVE MOUNT (18") Heavyweight	2.95 pr.
EAVE MOUNT (24") Heavyweight	3.50 pr.

## SINGLE SCREW-EYE for TWIN LEAD

3 1/2" . . . . . 2c ea. 7 1/2" . . . . . 5c ea.
(Minimum order 100 to a box)

## FOUR RECEIVER COUPLER

Model AM-20—couples 300 OHM antenna to 2-300 OHM receivers	\$4.50
Model AM-40—couples 300 OHM antenna to 4-72 OHM receivers	5.25
TELEMETRIC ANTENNA SWITCH, will accommodate 2 or 3 separate antennae	\$2.05

## SPECIAL 300 OHM TV WIRE

1st quality 55 mil web, 22 gauge pure polyethelene and 7 Strand pure copper. 1000 ft. spools

**\$17.50** per M ft.

6 FT. TV CORDS, Hanked	28c ea.
10 for	\$2.50
6 FT. LINE CORDS, Hanked	19c ea.
10 for	\$1.75

## Condensers Standard Brands (Special)

RCA 50 x 30 150 wv	.45c
F.P. Type	
40 mfd—175wv	SPECIAL 75c
40 mfd—100wv	60c
20x20—450wv	60c
20 x 25	SPECIAL 60c

## SPEAKERS (Alnico #5) 4" PM

50L6—6K6—3S4—3V4	45c ea.
------------------	---------

## MINIATURE I.F. TRANSFORMER

456KC—comp. w/clip. Input—Output	59c ea.
----------------------------------	---------

## DIAL LAMPS

247 G.E.	\$4.75 per 100 (10 boxes)
1 box	55c

## ALLIANCE 3-SPEED PHONO MOTOR

Complete with turntable (Special)	\$5.49
Volume Control 1/2 meg w/switch (Centralab)	Special 45c

## SELENIUM RECTIFIER (Top Quality)

### Full Wave Bridge Types

Up to 18 v. in/up to 28 v. out.	Up to 30 v. in/up to 14 v. out.
2 amp. . . . . \$2.50	2 amp. . . . . \$ 3.25
4 amp. . . . . 3.75	4 amp. . . . . 5.00
10 amp. . . . . 6.00	10 amp. . . . . 12.00
12 amp. . . . . 7.75	12 amp. . . . . 16.00

Power Supplies Built to Order—"FAST SERVICE"

## SEND FOR COMPLETE CATALOG

TERMS: 10% deposit with order. Balance C.O.D. F.O.B. N.Y.C. Include shipping charges with paid in full orders. Minimum order \$5.00.

## ATLAS TEL-RAD PARTS

153 CHAMBERS ST., DEPT. RN-12, NEW YORK 7, N.Y.  
Phone HANover 2-5813

# WHAT'S New in Radio

For additional information on any of the items described herein, readers are asked to write direct to the manufacturer. By mentioning RADIO & TELEVISION NEWS, the page, and the issue number, delay will be avoided.

## BINAURAL RECORDING

Magnecord, Inc., 360 N. Michigan Avenue, Chicago 1, Illinois, has developed a new binaural tape recorder




control, volume control, and pilot light. A kickproof metal grille protects the speaker. The unit is housed in a sturdy carrying case of solid plywood construction, covered with durable, washable fabricoid material. Total weight is 31 1/2 pounds and the unit is UL approved.

## NYLON RETAINING RING

Cambridge Thermionic Corporation, 463 Concord Avenue, Cambridge 38, Massachusetts, has developed a new nylon-phenolic terminal retaining ring which is said to greatly extend the scope of its ceramic coil forms.

The new rings in no way impair the moisture and fungus resistant qualities of the coil form assemblies but provide new benefits not available heretofore. They are excellent for bifilar windings. The four separate terminals, two on each nylon-phenolic ring, mean secure individual connections for each coil lead.

In applications using single pi wind-

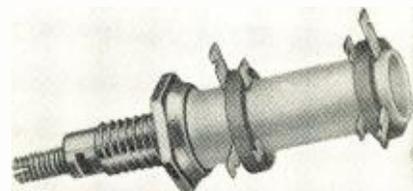

which records the sound through two separate microphones.

In the new system each of the microphones records on a separate side or channel on standard 1/4 inch sound recording tape. Since the two channels are recorded at the same time and reproduced simultaneously through two separate speakers and/or two separate headphones, the effect is that of the listener's ears actually being present at the time the recording was made.

The new amplifier has been designated the Type PT6-BN. When used with the PT63-A binaural mechanical unit, it provides two complete recording and playback channels.

Complete details on this new system are now available from the company.

## DELUXE RECORD PLAYER

A lightweight portable record player has been added to the line of audio equipment being produced by Newcomb Audio Products Company, 6824



Lexington Ave., Hollywood 38, California.

Known as the Model RC-12, the new player features a powerful 5 watt, a.c. amplifier, a Webster changer, and a 6" x 9" Alnico V PM dynamic speaker. The unit plays 33 1/2, 45, or 78 rpm recordings.

The operating panel includes a tone

ings, terminals can be located above or below the winding to shorten wiring to circuit elements. In addition, soldering spaces are doubled, as the shape of the terminals affords two soldering spaces on each to segregate coil terminations from circuit wiring.

All materials and finishes meet government specifications. The new rings are available with the company's LST, LS5, and LS6 coil forms.

## MATCHING TRANSFORMERS

Atlas Sound Corp., 1449 39th Street, Brooklyn 18, New York, has developed a new line of weatherproof matching transformers which is specifically designed to permit the sound technician to match all of the company's "Dual Projector" and "Paging and Talk-Back" speakers to either constant voltage (70 volt line) or constant impedance systems. Transformer taps eliminate the need for complex computations.

These new transformers are mounted in a heavy steel protective housing that prevents mechanical or atmospheric damage. Double rubber grommets and gaskets protect the cable connections entering the transformer housing. The convenient transformer bracket is

# NEW TELEVISION "SLAVE" KIT FOR 16 TO 20 INCH TUBE \$39.95

**COMPLETE 16 TO 20 INCH TELEVISION "SLAVE" KIT**  
**\$39.95**  
 LESS TUBES

Television Slave Kit, Model No. SK-21; for use with 16, 17 or 20 inch rectangular picture tubes, as well as 16 or 19 inch round tubes. It may be connected to your present TV receiver, regardless of screen size, to give you a remote TV slave unit; sometimes referred to as a TV duplicator. You pick up the TV signal at the picture tube grid. The audio is picked up at the high side of the audio gain control. These two connections are all that is necessary on your present set. A two tube cathode follower kit is supplied with the slave kit so that there will be no loading of your present set. The duplicator kit itself is 14 1/2" wide and 21" long. A ready punched chassis and complete hardware kit is furnished. The circuit is a straight forward AC transformer type. The circuit employs the following tubes: (2) 6SN7, horizontal and vertical oscillators, (2) 6AL5 phase detector and DC restorer, 6K6 vertical output, 5Y4 rectifier, 6K6 audio, 6X4 horizontal output, 6V4 damper, 1X2 high voltage rectifier, 12AT7 and video sync. separator, (2) 6AG5 are used in the cathode follower. (No speaker is furnished). This kit is the same essentially as a full TV kit, except that it has no tuner or video. All resistors, tube sockets, power transformer, etc., are furnished along with a schematic diagram and instructions. **WARNING:** Only those who understand TV, should buy this kit; as television is very complicated and should not be attempted unless you know what you are doing. TV Duplicator Kit, Model SK-21, complete less all tubes, Net price \$39.95. Shipping weight 38 lbs. 8" PM speaker, \$2.95 extra. Kit of 12 receiving tubes \$39.95. Shipping weight 18 lbs. 17BP4A, 17" blackface picture tube, \$21.95 extra. 20CP4A, blackface picture tube, \$39.95 extra. (Specify when ordering, which picture tube that you intend using.)

**COMPLETE 17" TO 20" T.V. KIT**


- ★ AC-TRANS-TYPE **\$59.95** LESS TUBES
- ★ CONVENTIONAL CIRCUIT
- ★ READY WIRED 12 CHANNEL T.V. FRONT END
- ★ 70° DEFLECTION
- ★ CERAMIC FLYBACK
- ★ KIT OF TUBES EXCEPT KINE \$16.95
- ★ 17BP4A \$21.95 EXTRA



A complete kit of parts to build an AC transformer operated television chassis for use with a 16, 17 or 20 inch rectangular picture tube. The 12 channel Sarkes Tarzian tuner is ready wired. The 4 tube video IF strip is also wired. Circuit is of the conventional accepted design, with latest ceramic type flyback high voltage supply. Chassis is ready punched. **Warning:** Do not buy this kit unless you understand Television and electronics. It is difficult to wire. We furnish schematic and photos. Kit model WH 20 ship weight 40 lbs., less all tubes \$59.95. Kit of 13 tubes but less picture tube \$16.95 extra. 17 inch 17BP4A \$21.95 extra. 20CP4 inch rect. tube \$39.95 extra.

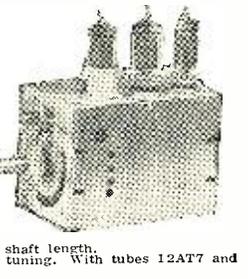**SARKES TARZIAN 3-TUBE T.V. TUNER \$7.95**

This popular Sarkes-Tarzian television front end is widely used today. The 13 channel rotary switch type with individually tuned coils. Price includes a schematic diagram and 3 tubes, 6C4 osc, 6BH6 RF and 6AG5 mixer. Regular factory cost is twice our price. Each tuner and its own tube sockets are wired, ready to hook up to a video and sound IF strip. May be used with either interactor or separate sound IF circuit. Built-in fine frequency control. Ship. weight 3 lbs. Sarkes-Tarzian Type 2 TV tuner with tubes net. \$7.95. Combination deal, Sarkes-Tarzian TV tuner and 205-XX video coil kit, both for \$14.95. Sarkes-Tarzian Type 3—Same as Type 2 but has input IF coil built-in. Tapped for sound IF channel. Net \$9.95. Above tuners offered with either 2 1/2" or 4 1/2" shaft length. 3-tube Sarkes-Tarzian tuner with 2 1/8" shaft but no fine tuning. With tubes 12AT7 and 26AG5. Stock No. TX-3T \$7.95 with tubes.



**CONVERT TO A RECTANGULAR PICTURE**

With each conversion kit you get a plastic mask, 70 degree deflected yoke, 90 day guaranteed back face picture tube, plus our new 771-X 14,000 Volt Universal fly-back and horizontal output transformer that works on any output tube and any single tube rectifier (1B3 or 1X2). A suggested diagram is furnished for use of the transformer with several different output tubes and rectifiers. We think this is the finest and best priced conversion kit in the country. Shipped Truck or Express, only.




Kit No. TCK-14, with 14BP4A 14" rectangular tube, Net price \$27.95  
 Kit No. TCK-16, with 16RP4A 16" rectangular tube, Net price \$29.95  
 Kit No. TCK-17, with 17BP4A 17" rectangular tube, Net price \$29.95  
 Kit No. TCK-20, with 20CP4A 20" rectangular tube, Net price \$49.95

**BUY YOUR WIDE RANGE COAXIAL SPEAKER AT McGEE**

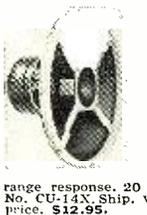**12" COAXIAL PM \$12.95**

A \$32.50 retail value, 20 watt 12" coaxial PM speaker. It is used on radios of the \$300 to \$500 bracket. Hook up like any other speaker. High pass filter is built on speaker. Matches 8 ohm output of radio or amplifier. Wide range response, 20 to 7,500 Cps. Model No. CU-14X. Ship. wt. 9 lbs. Special price, \$12.95.



**15" COAXIAL PM \$19.95**

Only \$19.95 buys a full 15", 20 watt coaxial PM speaker with high pass filter. Hook to any 8 ohm output on radio or amplifier. Respo. 20 to above 17,500 Cps. Good bass response. A lucky purchase makes this price possible. Full 32 ohm magnet in the woofer. 5" tweeter. Model #15-2. Ship. wt. 11 lbs. Sale price, \$19.95.



**100 ASST. RESISTOR KIT**

100 for \$2.49

Ohio Carbon, 100 resistor assortment. You get 50, 1 watt and 50, 1/2 watt sizes, from 100 ohms to 10 meg-ohms. A good assortment when you have around. Made and packaged by Ohio Carbon. Kit may not include 0 or 10 megohm resistors. This is used only to indicate ohms covered. Stock No. OH-100, 100 assorted resistors, \$2.49.




**RCA T.V. FRONT END \$9.95**

Terrific buy on this RCA TV tuner. We have a limited quantity of the famous original 201E1, 13 channel completely wired and tested TV front end tuners. Ready to connect to your TV video IF strip. Offered at a sacrifice. Price was originally \$44.00, now only \$9.95 each, less tubes. You'll save plenty on this item. 3-6J6 tubes are required. Stock No. RCA-13P TV front end tuner, \$9.95 each, two for \$19.00. 6J6 tubes 99¢ each, extra.

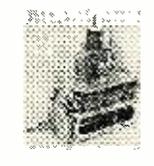**GENERAL INST. T.V. FRONT END Sale Price \$7.95**

All completely wired, brand new and pre-aligned, 13 channel selector incorporating fixed inductance and variable capacitance. Converter output transformer is attached to be coupled direct to separate sound and video I.F.'s. 3-6J6 tubes are required. Built in fine frequency control. Original factory cost over \$20.00. Weight 4 lbs. Stock No. G1-13PX, net \$7.95. Stock No. G1-13PX Same as above only not in new condition. Have been in sets, but guaranteed a good value—less tubes. G. Inst. Tuner #G1-13PX, net \$2.95. Either of the above G.I. tuners are available with either 6 1/4" or 1 1/2" shafts. Specify which shaft you desire, when ordering. 6J6 tubes 99¢ each, extra.




# SENSATIONAL NEW 2-BAND RADIO KIT ONLY \$14.95

**7-TUBE FM-AM TUNER**

MODEL RAL-8

- ★ AC SELF POWERED **\$29.95**
- ★ 3 GANG TUNING
- ★ A COMPLETE KIT


McGee has ready for delivery, this self powered AC, 7 tube FM and AM superhet tuner kit. Build yourself a professional looking tuner that may be connected to any audio amplifier. Receives broadcast 550 to 1650 kc and FM 88 to 108 mc. A 3 gang tuning condenser is used on both FM and AM. This extra stage of TRF makes a smoother working tuner. 2 IF stages on FM and one IF stage on AM (I.F. frequency 456 and 10.7 mc). Lighted slide rule dial with metal escutcheon plate. Our own lab designed and wired an original tuner using these parts. Chassis is ready punched and painted. Everything furnished including 6BA6, FM-AM R.F., 12AT7 mixer, osc., 6BA6 I.F., 6BA6 FM limiter, 6AL5 FM radio detector, 6AT6 AM detector, 1st audio. Plus rectifier and diagrams. Shipping weight 12 lbs. Stock No. RAL-8, net price \$29.95.

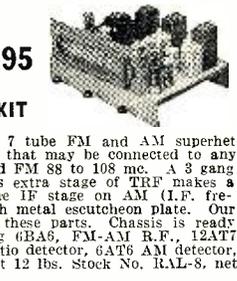

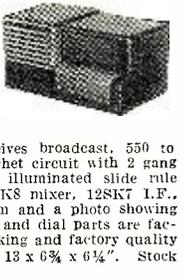**MODEL ME6-2 \$14.95**

**NEW MODEL 6-TUBE, 2-BAND RADIO KIT**  
**A FULL 2-GANG SUPERHET KIT**  
**RECEIVES 550-1600 KC PLUS 6-18 M.C.**

McGee's new 1951, 6 tube; AC-DC 2 band radio kit. Receives broadcast, 550 to 1600 kc and short wave, 6 to 18 mc. A straight forward superhet circuit with 2 gang tuning condenser, 456 kc I.F. transformers, etc. 5" speaker illuminated slide rule dial. Everything furnished, including tubes, 12SK7, R.F., 12K5 mixer, 12SK7 I.F., 12SQ7 detector, 1st audio, 35L6 output, 35Z5 rectifier, diagram and a photo showing view of underside of completely wired chassis. The chassis pan and dial parts are factory production. With this kit, you can build a commercial looking and factory quality 2 band radio, housed in a streamlined plastic cabinet. Size: 13 x 6 3/4 x 6 1/4". Stock No. ME6-2, shipping weight 10 lbs. Net \$14.95.



**SELF POWERED AC**


**Broadcast Tuner Kit, 3-Gang Tuning, Complete Kit, \$12.95**

A self-powered, 3-gang superhet tuner kit with R.F. stage when wired according to our diagram will make a top quality broadcast tuner (550 to 1650 kc), for use with any amplifier. Don't class this with ordinary tuners; this has its own power transformer. This complete kit is furnished with a diagram, photos and tubes. 6AU6 R.F., 6BE6 oscillator R.F., 6AU6 I.F. detector, 6AL5 diode, AVC, plus rectifier. Connect to any audio amplifier. Ideal for use with our S-2020, TH-16 or T-5 amplifier kits. Chassis size, 9 1/2" x 4 1/2" high. Shipping weight, 7 lbs. Broadcast tuner kit Model BT-38X. Net price, \$12.95.

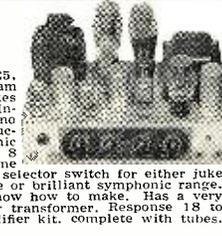**8-TUBE 22 WATT Wide Range Amp.**

Model Tx5 Kit Only \$37.95

A complete kit, including tubes (3-7E5, 2-7F7, 2-6A3, plus rectifier), diagram and photos. All triode circuit makes for minimum harmonic distortion. Inputs for radio tuner any kind of phono pickup (crystal or G.E. variable reluctance) and either crystal or dynamic mike. Output transformer matches 8 ohm voice coil. Twin electronic tone controls, bass and treble with range selector switch for either juke box quality with heavy bass response or brilliant symphonic range. The best quality amplifier kit we know how to make. Has a very wide range output and heavy power. Response 18 to 20,000 Cps. 8 tube all triode amplifier kit, complete with tubes. Weight 25 lbs. Net \$37.95.




**10-TUBE RADIO KIT \$29.95**

**3-GANG TUNING MIKE INPUT 12 WATT HI-FI AUDIO BASS-TREBLE BOOST**

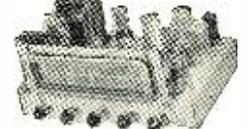**A NEW 1951 ALL-PURPOSE RADIO KIT**

10-Tube Broadcast (550 to 1700 kc) Radio Kit for custom builders. Features 3-gang superhet circuit with A.V.C., high gain IF circuit, 8" slide rule dial. Chassis size 12 1/2" long, 10" front to back, 6 1/2" high. Audio inputs for a crystal or dynamic mike, record changer or player. Tone compensation for standard crystal pick-up or General Electric variable reluctance. Push-pull 6V6 output tubes, shielded high fidelity output transformer matches 8 ohm PM speaker, husky power transformer, 2 tone controls for separate bass and treble boost. A complete kit including tubes 6SK7 R.F., 6SA7 mixer, 6SK7 I.F., 6H6 detector, AVC, 6SQ7 1st audio, 12AX7 phase inverter, 2-6V6 outputs, plus rectifier, diagram and instructions. Shipping weight 18 lbs. Stock No. BK-R10. Net price \$29.95. 10" PM speaker, \$6.95 extra. Crystal mike and desk stand, \$4.95 extra. 12" coaxial speaker \$12.95 extra.




**5-Tube Broadcast SUPERHET RADIO KIT \$12.95**

Model RS-5 tube AC-DC superheterodyne radio kit. Has loop antenna and 2 gang condenser, with lighted slide rule dial and attractive plastic cabinet. Receives broadcast, 550 to 1650 kc. Full size dynamic speaker, matched 456 I.F.'s, automatic volume control. This is a complete radio kit. Everything furnished, including diagram, photos and tubes: 12K8 mixer, 12SK7 I.F., 12SQ7 detector, 1st audio, 50L6 output, 35Z5 rectifier. Shipping weight 7 lbs. Stock No. RS-5. Net price \$12.95.

**Build Your Own \$7.95**

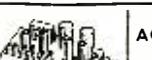**Phono-Mike Broadcaster**

Kit Model DE-6R. With this simple kit, you can build a 3-tube phono oscillator that also has a mike input. Will broadcast over any radio, within your home, (about 75 feet) from 1000 to 1500 kc. Inputs for crystal mike or crystal phono pickup. Fader control fades from mike to record. Ideal for home P.A. system, baby listener and home entertainment. A complete kit of parts including tubes, Kit Model DE-6R. Net price, \$7.95. DE-6RWT, wired and tested. Net price, \$9.95. Crystal mike and desk stand, \$4.95 extra. Concealed microphone unit, only 1 1/2" in diameter and 1 1/2" thick. Specify hidden mike when ordering. Stock No. T-001. Net \$3.95 extra.



**6-TUBE AC-2-BAND KIT \$16.95**

A New 2-band radio chassis kit, features 2-gang tuning, full AC circuit with power transformer, complete with diagram, all parts and tubes. 6SK7 R.F., 6SA7 mixer, 6SK7 AVC, 1st audio, 6V6 output, plus rectifier. Chassis size, 7" deep, 6" high, 12 1/2" long, 7 1/2" slide rule dial. Very ideal for schools, etc. A straight forward superhet circuit complete except for speaker and cabinet. Output transformer included. Ship. weight 8 1/2 lbs. Stock No. AA-61. Shipping weight \$16.95. 6" PM speaker \$2.79 extra, 8" PM \$3.49 extra.



**McGEE RADIO COMPANY** Prices F.O.B. K.C. Send 25¢ deposit with Order, Balance Sent C.O.D. With Parcel Post Orders, Include Postage **TELEPHONE VICTOR 9045, WRITE FOR FLYER 1422 GRAND AVE., KANSAS CITY, MISSOURI**


# ORDER BY MAIL FROM McGEE AND SAVE MONEY!

## New Versatile Espy

### 12-TUBE FM-AM CHASSIS
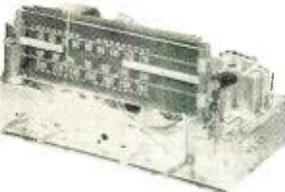
# \$64.50

- ★ BUILT IN PRE-AMPLIFIER FOR G.E. VARIABLE RELUCTANCE PICKUP
- ★ WIDE RANGE AUDIO
- ★ MAY BE USED WITH A CRYSTAL MIKE AS A HOME P. A. SYSTEM



McGee's new 1951 model 12 tube FM/AM chassis. Latest design with phono inputs for all types of record players, crystal or G.E. variable reluctance. Receives standard broadcast and has boost tone control. Long antenna for broadcast and 300 ohm line type antenna, may be stapled in cabinet. Attractive lighted slide rule dial. Chassis size 13 1/2" x 11 1/2" x 9" deep. Shipping weight 20 lbs. Stock No. 7-CX. Made to sell at a higher price. McGee's sale price is \$64.50, less speaker output matches 8 ohms, 7-CX chassis with our 12" coaxial PM, CU-14X, both \$74.50. 7-CX chassis with our 12" coaxial PM, CU-14X and latest model 3 speed record changer with crystal cartridge, all for only \$99.45. Same combination deal as always, except changer has the G.E. variable reluctance turntable cartridge. All for only \$106.65.

## SPEAKER AND BAFFLE SALE

### 8" SPEAKER AND BAFFLE \$4.95

Stock No. 818. Tan leatherette covered, plywood slant type wall baffle, plus an 8" Oxford, 2.15 oz. Airtone V magnet, FM speaker. A real hot McGee special for only \$4.95 each, or \$4.70 each in lots of 3 or more.

### 10" SPEAKER AND BAFFLE \$6.95

Stock No. CA-10. Tan leatherette covered, plywood slant type wall baffle, plus 10" Pennatone, 3.16 oz. Airtone V PM speaker. Only a few hundred to sell at \$6.50 each, or \$6.25 each in lots of 3 or more.

### 12" SPEAKER AND BAFFLE \$6.95

Stock No. CA-12. Tan leatherette covered, plywood slant type wall baffle, plus a 12" speaker. Popular. A terrific McGee value for only \$6.95 each, or \$6.60 each in lots of 3 or more.

## ELECTRONIC RADIO and TV TUBES

- 6 MONTHS' GUARANTEE • INDIVIDUALLY CARTONED
- IN RED AND BLUE DE LUXE VARNISHED CARTONS
- EVERY TUBE SET TESTED FOR YOUR PROTECTION

ORDER 50 ASSORTED—TAKE 10% OFF. Prices as Low as 39¢

024	\$.05	6AV6	\$.04	6SA7GT	\$.05	12BA7	\$.09
1H5GT	\$.05	6BA7	\$.05	6SL7GT	\$.05	12AX4	\$.05
114	\$.05	6BA7	\$.05	6SN7GT	\$.05	12BE6	\$.05
1RS	\$.05	6BC6	\$.05	6V6GT	\$.05	12SA7GT	\$.05
1U4	\$.05	6BG6	\$.05	6W4GT	\$.05	12SQ7GT	\$.05
1U5	\$.05	6BH6	\$.05	6X4	\$.05	12S07GT	\$.05
3A4	\$.05	6BJ6	\$.05	6X5GT	\$.05	25B06GT	\$.05
30A	\$.05	6BQ6GT	\$.05	6X7	\$.05	25L6GT	\$.05
504C	\$.05	6C4	\$.05	6X8GT	\$.05	35C5	\$.05
5Y3GT	\$.05	6CB6	\$.05	12AT6	\$.05	35W4	\$.05
6AB4	\$.05	6CG6	\$.10	12B7	\$.05	3Z5GT	\$.05
6AK5	\$.05	6HG6	\$.05	12AU7	\$.05	50B5	\$.05
6AL5	\$.05	6K6GT	\$.05	12AV7	\$.05	50C5	\$.05
6AQ5	\$.05	6L6GT	\$.05	12AX7	\$.05	50L6GT	\$.05
6AT6	\$.05	6S4	\$.05	12BA6	\$.05	5Y17Z	\$.05
6AU6	\$.05						

## Crosley, G.E., Raytheon, Sylvania, Tung-Sol, etc.

These very low price tubes are made possible by our purchasing from set manufacturers, in bulk quantities and boxing tubes in plain white cartons. Each tube has brand and type stamped on carton. Nothing but nationally advertised brands will be shipped to you. Sylvania, National Union, RCA, Tung-Sol, G.E., Raytheon, Jewel, etc. 6 months' guarantee. All list quality: no throw-outs or seconds. You must be satisfied.

024	\$.05	6K7C	\$.05	7E5	\$.09	144A	\$.09
1B3GT	\$.10	5Y3GT	\$.09	6L7C	\$.05	144T	\$.09
1RS	\$.09	6AG5	\$.09	6S4	\$.05	7H7	\$.09
155	\$.09	6AL5	\$.09	6SE7GT	\$.05	7L7	\$.09
157	\$.09	6AR5	\$.09	6Y4	\$.09	7Y4	\$.17
1X2A	\$.09	6AU6	\$.09	6SH7	\$.09	12A6	\$.09
1F5G	\$.09	6BB6	\$.09	6SH7GT	\$.09	12A8C	\$.09
2A5	\$.09	6B8C	\$.09	6SN7GT	\$.09	12C7GT	\$.09
2A7	\$.09	6BA6	\$.09	6U7C	\$.09	12AV7	\$.10
2K2	\$.09	6B06GT	\$.15	6V6GT	\$.09	12K6	\$.09
3A4	\$.09	6B6GT	\$.09	6W4GT	\$.09	12Q7GT	\$.09
354	\$.09	6CG5GT	\$.09	6Y7C	\$.09	12SH7	\$.09
3V4	\$.09	6J6GT	\$.10	6Z5C	\$.09	12SN7GT	\$.09
5T4	\$.15	6K5GT	\$.09	7B6	\$.09	12S7	\$.09

1.4 VOLT AC-DC SERIES

1RS	\$.09	12SA7GT	\$.07	LOCALS	
155	\$.09	12SK7GT	\$.07		
1T4	\$.09	12SQ7GT	\$.07	1B3GT	\$.10
354	\$.09	12S07GT	\$.07	1X2A	\$.09
3V4	\$.09	12S07GT	\$.07	504C	\$.09
				504GT	\$.09
				50C5	\$.09
				50A5	\$.09
				50L6GT	\$.09

Television Receivers

6SA7	\$.08	7B6	\$.08	785	\$.08
6SH7	\$.08	7H7	\$.08	7H7	\$.08
6SK7	\$.08	82	\$.08	7Y4	\$.17
6SL7	\$.08	65L4	\$.08	12A6	\$.09
6SN7	\$.08	64	\$.08	12A8C	\$.09
6S07	\$.08	65	\$.08	12C7GT	\$.09
6Z5	\$.08	59	\$.08	12SH7	\$.09
7A7	\$.08	59	\$.08	12SN7GT	\$.09

MISC. REC. TYPES

6SA7	\$.08	785	\$.08
6SH7	\$.08	7H7	\$.08
6SK7	\$.08	82	\$.08
6SL7	\$.08	79	\$.08
6SN7	\$.08	64	\$.08
6S07	\$.08	12J17	\$.08
6Z5	\$.08	59	\$.08
7A7	\$.08	59	\$.08

## 50-WATT BOOSTER AMPLIFIER—\$39.95



25-Watt Horn \$28.95

50-Watt Booster \$39.95

2-Mike Pre-Amp. \$10.00 Extra.

### 50-WATT BOOSTER

A sensational value. 50 watt booster amplifier with push-pull parallel 6L6 output tubes. Connect to your present amplifier as input. The booster amplifier has one input jack and with 1 volt input gives 50 watts of audio. Booster has a 6 lb. potted case high fidelity output transformer, matches speaker with 4-8-16 ohm voice coil, also 60 ohm and 250 ohm line. Booster has a 225 mill 2-way variable controls are for master volume control and base boost tone control. Size 8 x 6 1/2 x 1 1/2. Stock No. PA-55X. Shipping weight 26 lbs. Sale price \$39.95 ea.

### 2-MIKE PRE-AMP.

Pre-amplifier plugs in directly to the PA-55X Booster amplifier. It enables use of 2 Crystal or Dynamic Mikes plus one low level input. Furnished with 4 foot cables and plugs for remote control of the 55 watt Booster Amplifier. Small chassis size 3 x 3 1/4 x 4 1/2. Stock No. PR-2X, with tubes 7F7 and 7N7. Net price \$10.00 ea.

### 25-WATT HORN

25-Watt Driver and 3/4-foot air column re-entrant Trumpet. The standard type trumpet and driver you see the most. Drivers are 100% weatherproof, horn is spun aluminum, offered to you at a considerable savings. Stock No. MA-33. Shipping weight 20 lbs. Net price \$28.95.

## 5-0Z4 TUBE & 5 VIB. \$950

### DEAL No. RN-V5



Here's a real hot deal for you fellows that do a lot of auto radio service. 5 standard brand metal 0Z4 tubes and 5 of our famous 4-prong serrated cant vibrators. This vibrator is of the latest design, for long life. Standard diameter ran, short enough to fit all Chrysler auto sets, also fits Motorola, etc. Our 20th Anniversary, big deal No. RN-V5. You can get 5 0Z4 metal tubes and 5 4-prong vibrators, all for \$9.50. Shipping weight 3 lbs.

## 100 Molded Plastic Bypasses \$995



100 molded plastic tubular bypass condensers. All 600 volt. And all by the same nationally known mfr. Regular dealer's net is over two and one-half times our price. You'll chuckle when you look these over. Here's what you get: 10—001, 10—002, 20—005, 20—01, 20—05 and 10—1. Our big deal No. RN-202. 100 plastic tubulars. Shipping weight 2 lbs. Net price, \$9.95.

## 100 600 VOLT TUBULARS \$695



100 top quality 600 volt tubular by-pass condensers. Made this year by a famous condenser factory. Don't confuse these with grab-bag surplus. McGee's deals are guaranteed to please you. Here's what you get: 10—001, 10—002, 20—005, 20—01, 10—02, 20—05 and 10—1 600 volt condensers. Our big deal No. RN-203. Shipping weight 2 lbs. Net price, \$6.95.

## 20 50 x 30 150 V. ELECTROLYTICS \$975



Here's a red hot value. 20 of our F.XV quality replacement electrolytics. The most popular condensers in use today. Takes care of 90% of your AC-DC radio filter needs. Compact construction, 105 production, 1-year guarantee, 50-30 mfd, 150 volt, housed in a cardboard tube with common negative, has long flexible leads. 20th Anniversary, big deal No. RN-204. Sale price \$9.75.

## SELENIUM RECTIFIERS

65 mill Selenium Rectifier, net . . . . .59c each  
100 mill Selenium Rectifier, net . . . . .59c each  
150 mill Selenium Rectifier, net . . . . .79c each  
200 mill Selenium Rectifier, net . . . . .1.19 each  
350 mill Selenium Rectifier, net . . . . .1.79 each

450 mill Selenium Rectifier, net, 1.79 each  
McGee offers you the finest in Selenium rectifiers. All standard 130 volt.

## T.V. BOOSTER REGENCY \$19.10



Regency DB-410 television booster. A real engineered unit, same construction as a d and compact. Six u g tuned, using 1-616 tube as neutralized push-pull amplifier. Dollar for dollar, your best booster buy. \$54x49". For 110 volt AC operation. Weight 6 lbs. Net price \$19.10.

## RED HOT SPEAKER VALUES

McGee has a tremendous stock of 100,000 speakers to fill your needs. Every speaker is fully guaranteed. Order your speakers now.

4 inch, square	1 oz. magnet	\$1.39
5 inch, pincushion	1 oz. magnet	1.39
6 inch, pincushion	1.47 oz. magnet	2.09
4 x 4 inch	1 oz. magnet	1.49
3 x 7 inch, oval	1.47 oz. magnet	2.19
7 inch, pincushion	2.15 oz. magnet	3.19
8 inch, pincushion	2.15 oz. magnet	3.29
6 x 8 inch, oval	2.15 oz. magnet	3.09

## McGee's Super High Fidelity Best Value in U. S. A. OUTPUT TRANS. \$795



Model A-403 High fidelity output transformer. Why pay \$20 or \$30 for an output, when our A-403 is available at \$7.95! Impedance, 6000 ohms plate to plate (for PT 6L6 or 6V6), 10% feedback winding, 4-8-15-250 and 500 ohm secondary. Housed in a potted case. Net weight 6 lbs. Recommended for all amplifiers up to 34 watts, 625.

## GENERAL INSTRUMENT 78 R.P.M. Record Changer SCOOP PRICE \$10.95



General Instrument 78 RPM automatic record changer. Plays 10- or 12-inch records automatically. One of the latest models made. Beautiful golden brown hammer-tone finished base, 12x12 1/2". Equipped with an Astatic L-70 crystal cartridge. Heavily floored turntable and plastic fittings are deep maroon color. This may be our last chance to offer a 78 RPM changer at this price. Comes packed two to a master carton, just like they would be shipped to a set manufacturer. Order 2 changers for an additional saving. Shipping weight for 2 changers, 20 lbs. Stock No. IT-SGL. Net price, \$10.95.

## 10 FP ELECTROLYTICS DEAL RN-10DS \$3.49



10 assorted F.P. aluminum can electrolytics. Popular twist tap mounting. Mostly multiple section banks, 50, 350 and 450 volts. A red hot deal. Shipping weight 3 lbs. Deal #RN-10DS. Net \$3.49.

## 100 KNOBS Set-Screw Type \$3.95



100 bakelite set screw knobs, for radio set replacement. All fit standard 1/4" shaft. Assorted walnut, black and ivory. Enough of each style to give you matched sets. This value worth \$7.50. Shipping weight 2 lbs. Deal No. RN-10K.

## 3-SPEED CHANGERS ON SALE AT McGEE

### WEBSTER CHICAGO 3-SPEED \$24.95

Regular \$47.50 List Only



Webster Chicago Model 100-16 3 speed automatic record changer with crystal cartridge and all speed Sapphire needle. 1 needle plays all records. Base size 12x12 3/4". Shipping weight 14 lbs. This offer good only as long as our stock lasts. A special purchase makes this offer possible. Webster Chicago 3 speed changer, Model 100-16, Sale price \$24.95.

### WEBSTER CHICAGO MODEL 100-2 ONLY \$24.95

For the first time we offer the world famous Webster-Chicago, model 100-2. Features a newly designed spindle that draws the records flat air-cushioned to the turntable. Pickup arm sets down automatically after the last record plays. Plays all records automatically. 33 1/3, 78 and 45 rpm. New balanced tone arm with Electro-Voice Tilt-A-Matic cartridge with dual needles. Ordinarily cost over \$32.00. McGee offers them for only \$26.95 each. Base size 12"x12 3/4". Shipping weight 14 lbs.

### V.M. 3-SPEED MODEL 406 \$22.95

VM model 406, deluxe 3 speed automatic record changer. Plays them all. Intermines records of the same speed. Equipped with a flip over crystal pickup with twin needles. Base size, 12 1/2"x13 1/2". Shipping weight 12 lbs. VM-406. Net price \$22.95.

### GENERAL INSTRUMENT 3-SPEED \$19.95



Another tremendous McGee record changer scoop. Only \$19.95 to sell. General Instrument, 3 speed automatic record changer with standard crystal cartridge and all purpose permanent needle. Brand spanking new. Our first offering of a 3 speed changer at less than \$20.00. We purchased a large quantity and pass our savings on to you. Stock No. GI-3384. Sale price \$19.95 each. Price to the small manufacturer in lots of 48 or more, \$19.50 each.

# McGEE RADIO COMPANY

Prices F.O.B. K.C. Send 25% Deposit with Order, Balance Sent C.O.D. With Parcel Post Orders, Include Postage

TELEPHONE VICTOR 9045. WRITE FOR FLYER 1422 GRAND AVE., KANSAS CITY, MISSOURI

**WANTED! WANTED!**

**MILITARY TEST SETS & EQUIPMENT**

TS-12, 13, 35, 14, 15, 146, 174, 175, 263, 268, etc. APR, ARC, ART, AFS, APA, SCR, BC equipment and parts. Also TUBES, any quantity. WRITE. WIRE OR CALL.



Coaxial Relay K-101 SPTT-24V DC5..... \$ 4.95  
Set of S-138 Cables Connectors for Above..... 1.35  
1000 KC Crystal BT cut..... 3.95  
VS-2 Vacuum Switch..... 1.25  
Sungate Plate Relay 8000 ohm SPTT..... 2.49  
RG-59/U Coaxial Cable-75 ohm..... 22.50  
150' roll..... \$11.95 300' roll..... 1.29  
3" Scope Shield..... 2.95  
2000-0-2000 V @ 800 MA Xformer..... 24.95  
15 HY @ 800 MA Choke..... 6.95  
2 mfd 3000 V Condenser..... 4.25

**TUBES!! BRAND NEW! STANDARD BRANDS! NO SECONDS! COMPARE! TUBES!!**


0A3/VRT5 \$1.69	3C24 \$2.25	217C \$8.95	812H \$6.90	8008 \$7.95	WL616 \$37.50	5V4G \$0.73	6SL7GT \$0.98	12SL7 \$1.05
0C3/VR100 1.29	3C27 4.95	237A/3C27 5.95	814 8.95	8011 1.75	WL619 18.95	3Z3 .89	6SN7GT .98	12SN7 .98
0C3/VR105 1.49	3C31/CIB 3.49	249C 3.95	818 2.95	8012 3.95	WL677 34.50	3Z4 .89	6X4 1.25	12X7 .85
0C3/VR150 1.29	3C45 19.95	250R 12.95	826 1.30	8013 29.95	WL681 22.50	6A4 1.25	6X5 1.25	12X7 .85
1B23 1.25	3C49 6.95	274B 2.95	834 1.98	8020 1.29	WA2 1.55	6A4LA 1.35	6X7 1.10	12X7 .85
1B24 19.95	3DP1 4.95	274A 5.50	838 1.27	8025 5.95	OA4G 1.20	6A6 .92	6X8 1.10	12X7 .85
1B26 3.95	3DP1A 4.95	274B 2.95	841 1.98	9001 1.25	OB1 1.65	6A7 .99	6X9 1.10	12X7 .85
1B27 24.50	3DP1S2A 8.95	276A 9.95	842 1.98	9002 2.25	O24 1.75	6A8 1.05	6X9 1.10	12X7 .85
1B29 2.75	3DP2A 1.98	293A 2.98	843 1.98	9003 3.95	O1A .75	6A7 1.05	6X9 1.10	12X7 .85
1B32 8.95	3E29 14.95	294A 4.95	844 1.98	9004 1.25	O24 1.75	6A7 1.05	6X9 1.10	12X7 .85
1B36 24.95	3FP7 3.95	300B 9.95	845 1.98	9005 2.95	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1B38 3.25	3GP1 4.75	304TH 14.95	846 1.98	9006 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1N21 Xtal 22.50	3H1 7.95	324A 4.95	847 1.98	9007 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1N21A 2.25	4-6SA 14.21	303A 34.95	848 1.98	9008 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1N21B 4.25	4-12SA 26.95	307A/RK75 5.95	849 1.98	9009 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1N22 1.25	4-15SA 12.95	310A 4.95	850 1.98	9010 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1N23 2.25	4AP10 4.95	316A .65	851 1.98	9011 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1N23A 3.25	4B22/EL5B 9.95	323A/B 24.50	852 1.98	9012 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1N23B 1.95	4B21/EL6C 7.95	324A/5C37 8.95	853 1.98	9013 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1N25 5.95	4B25/6CF 8.95	328A 8.95	854 1.98	9014 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1N27 1.69	4B26/2000 8.95	331A 12.95	855 1.98	9015 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1N34A 1.40	4B28 9.95	330B 8.95	856 1.98	9016 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1P23 3.25	4C27 14.95	350B 4.95	857 1.98	9017 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1P24 1.79	4C27/CV92 9.95	368SA 7.95	858 1.98	9018 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1P36 2.95	4C35 34.50	371A 1.49	859 1.98	9019 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
1R2 1.25	4D21 257B 17.95	450TH 47.50	860 1.98	9020 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2A1 11.95	5AP1 3.69	388A 2.75	861 1.98	9021 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C1/RK33 6.9	5AP4 3.69	393A 4.95	862 1.98	9022 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C2/RK33 7.9	5AP7 3.69	394A 8.75	863 1.98	9023 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C2A 4.9	5BP4 5.95	417A 12.95	864 1.98	9024 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C34/RK34 8.9	5CP1 4.95	433A 4.95	865 1.98	9025 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C39 3.25	5E1 12.95	450A 8.95	866 1.98	9026 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C40 12.95	5C22 55.00	446B 4.95	867 1.98	9027 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C43 14.95	5D21 24.50	450TH 47.50	868 1.98	9028 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C44 2.9	5E27 12.95	471B 8.95	869 1.98	9029 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C46 7.50	5GP1 4.95	527 12.75	870 1.98	9030 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C51 6.95	5JP1 24.45	559 1.39	871 1.98	9031 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C52 1.95	5JP2 24.45	575A 13.95	872 1.98	9032 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C24 4.89	5J23 12.95	701A 5.95	873 1.98	9033 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C26 3.66	5J29 9.95	702A 2.95	874 1.98	9034 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C28 2.29	5J30 49.50	703A 7.95	875 1.98	9035 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C21A 9.95	5J32 49.50	704A 1.05	876 1.98	9036 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C22 8.9	5J37 12.95	705A 2.95	877 1.98	9037 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C23 2.50	5G1 3.95	706BY 39.50	878 1.98	9038 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C27 29.50	6AS6 3.69	706CY 39.50	879 1.98	9039 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C30 99.50	6C21 2.95	707 17.95	880 1.98	9040 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C31 2.9	6E1 12.95	708A 3.95	881 1.98	9041 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C32 39.50	6J4 6.95	708B 3.95	882 1.98	9042 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C33 39.50	7BP7 8.95	710A/8011 1.75	883 1.98	9043 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C34 9.95	7DP4 14.95	711A 1.69	884 1.98	9044 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C36 12.75	9J1P 14.95	712A 2.59	885 1.98	9045 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C38 3.95	9J2P 16.95	713B 2.95	886 1.98	9046 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C39 39.50	9J17 14.95	714A 1.69	887 1.98	9047 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C40 39.50	10BP4 22.50	715A 1.69	888 1.98	9048 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C46 29.50	12DP7 16.95	717A 1.69	889 1.98	9049 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C49 39.50	12CP7 16.95	721A 2.59	890 1.98	9050 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C50 39.50	2BP7 16.95	722A 2.59	891 1.98	9051 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C54B 39.50	121P4 22.50	723A 14.95	892 1.98	9052 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C55 97.50	15E 1.19	723A/B 22.50	893 1.98	9053 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C61 8.9	5T1 8.9	724A 2.59	894 1.98	9054 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2C62 49.50	16AP4 42.50	725A 7.95	895 1.98	9055 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2K25/723AB 29.50	16CP4 42.50	726A 6.95	896 1.98	9056 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2K28 36.25	23D4 4.45	726B 6.95	897 1.98	9057 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2K29 24.50	28D7 1.35	750TH 79.50	898 1.98	9058 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
2K33 31.00	35T Special 4.95	800 1.95	899 1.98	9059 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3A1 12.95	35TG 4.95	801A 4.49	900 1.98	9060 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3B23/Elc 2.95	4J Special 3.99	802 4.49	901 1.98	9061 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3B23/RK22 4.85	5A1 5.95	803 4.49	902 1.98	9062 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3B24 8.95	5J1L 6.95	804 9.95	903 1.98	9063 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3B24W 7.95	100R .89	805 4.49	904 1.98	9064 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3B25 4.65	100TH .95	806 29.95	905 1.98	9065 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3B26 3.95	200R 2.98	807 1.98	906 1.98	9066 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3B27 3.95	203A 8.95	808 7.25	907 1.98	9067 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3B28 8.95	204A 69.50	809 2.45	908 1.98	9068 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3B21 20.9	210R 24.95	810 9.95	909 1.98	9069 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3C22 64.50	212E 49.50	812 2.95	910 1.98	9070 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85
3C23 9.95	215A .19		911 1.98	9071 2.25	OB2 1.65	6A7 1.05	6X9 1.10	12X7 .85

**RADAR COMMUNICATIONS—TEST EQUIPMENT**

AN/APA10 Panoramic Adapter..... \$175.00	ARA 300-1500KC Receiver, good..... \$24.95	T53/AP S-Band Freq & Power Meter..... \$35.00
AN/APA11 Pulse Analyzer..... 39.95	R28/ARC-5 Receiver..... 29.95	T510/APN Altimeter Test Set, Ex..... \$35.00
AN/APN-4B Receiver..... 39.95	BC455B 6-9 mcs. Receiver..... 19.95	T511/AP..... 19.95
AN/APR4 Radar Search Receiver..... 375.00	ARR-2 234-258 mcs. Receiver..... 19.95	T512/AP V.S.W.R. Test Set for X-Band..... 19.95
AN/APR5 Radar Search Rec. 1000-31000 mcs..... 375.00	BC-454 3-6 mcs. Rec. w/tubes, New..... 16.95	T513/AP X-Band Sig Gen Pwr & Freq Mtr..... 19.95
AN/APR3 Airborne X-Band Search Radar..... 99.50	TRC-4B X-Mitter..... 29.95	T514/AP SA Band Sig Gen..... 19.95
AN/APS15 X-Band R.F. Head..... 149.50	TYPE O 5-3.7 mcs Xmitter..... 9.95	T515/AP Flux Meter..... \$29.95
AN/AP75 300-1500 mcs Xmitter..... 129.50	AVT-23 300-13,000KC Complete, New..... 59.95	T516/AP Altimeter Test Set..... \$29.95
AN/CR73 Dual Freq Victory Grl..... 19.95	BC-456 Modulator, good..... 2.25	T519/AP Range Calibrator..... 82.00
AVR-15 Alrfvrt Receiver..... 149.50	BC-450 Control Box (3 Rec.) used..... .98	T523/APN Test Set for SCR718 Altimeter..... 1.95
AN/PPN-1 Portable Radar Beacon..... 149.50	BC-442 Relay Unit (Ant) Used..... 1.95	T532/TRC-1 70-100 mcs Sig Gen used to check ANTRAC Equipment.....
BC-221AK Freq. Mtr. with Modulation..... 39.95		T533/AP X-Band Freq. Meter.....
BC-433G Compass Receiver..... 1300.00		T534/AP Synchroscope.....
BC-640B 100-136 mcs ground xmitter..... 29.95		T535/AP X-Band Sig Gen Pwr Mtr Freq Mtr.....
BC-733D Receiver..... 459.50		T536/AP X-Band Power Meter.....
BC-1016 Tape Code Recorder..... 4.95		T545/AP X-Band Sig Gen.....

# the AUDIO AMPLIFIER

## with the Listeners' Seal of Approval

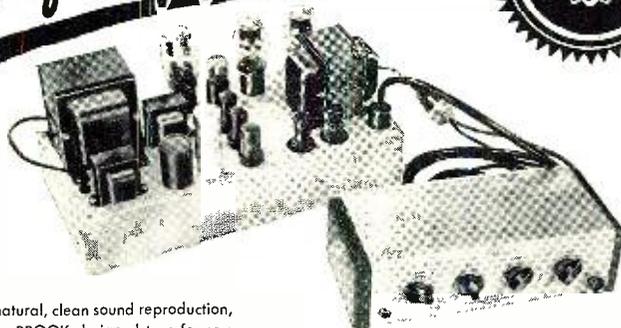

- For the utmost in natural, clean sound reproduction, ALL TRIODES, plus BROOK designed transformers and circuits.
- "Listening fatigue" reduced to a minimum.
- Inputs compensated for any type of phono pickup, TV, FM and AM receiver.
- Attractively designed remote-control pre-amplifier incorporates separate stepped controls for bass and treble.

- High quality, natural and lifelike, at extremely low volume or at full loudness of a band or symphony orchestra.

Our free booklet, "BETTER LISTENING" contains some interesting ideas on what goes into a high quality audio system. Write for it and technical bulletin and detailed distortion analysis.

**Brook Electronics, Inc., • • Dept. RA-2**  
 • • • • 34 DeHart Place, Elizabeth, New Jersey

We explain to the customer that he will save money in the long run because it will not be necessary to remove the radio from the car or dismantle it. He is free to make his own decision—we do not high-pressure him—but his service card is noted "Customer does not desire vibrator."

If a vibrator has laid on the shelf for a long time, points may become oxidized, or if an auto radio has been in storage for a long time, the points of the vibrator may become oxidized and the vibrator will not start. We use a 100 watt bulb in series with a 110 volt a.c. line to start the vibrator and then let it run for a few seconds. This will burn off the oxide and the vibrator will operate satisfactorily in the future. This same outlet is used to test portables when we suspect the oscillator tube of failing to oscillate at low voltage.

You will notice that the photo of the work bench shows two positions complete with polarized six volt battery outlets and speakers. There are two similar positions in the rear. Most of the test equipment sits on a shelf and can be turned to face either direction. You will also note that each position has a d.c. ammeter, 0-15 amp. scale. If you have seen the same make of auto radio day after day, you know, within ½ an amp. how much it should draw. An excessive reading is, of course, an indication of a shorted buffer condenser or bad vibrator, if the condition persists with the rectifier tube removed. If the current draw is below normal with the rectifier removed, and is excessive when the rectifier is inserted, it means either a shorted condenser in the "B-plus" line or a shorted rectifier tube. This helps speed up the diagnosis.

We have made a small vibrator checker. It only contains two sockets, a standard four prong and an offset four prong. These two sockets will take care of 90% of the vibrators in use today. It consists of an ordinary auto radio transformer, rectifier sockets, buffer condenser, and resistive load. The primary input current is read on the bench ammeter. The output is read on an ordinary d.c. voltmeter and the waveform is analyzed on the oscilloscope. This device requires no additional meters. For convenience, we have a jack and plug to plug in the oscilloscope and meter.

When you do a repair for the radio set manufacturer, he furnishes you with a form on which you list the customer's name and address, delivery date, etc. We use the names on these forms for our mailing list, and we have had special postcards printed telling the customers we are the local authorized factory service station for their particular make of auto radio.


Our Service Department is "open"—no back rooms. We are separated from the customer by a glass panel similar to those used in modern drug store prescription departments. We attempt to show the customer our equipment and manner of working.

-30-

RADIO & TELEVISION NEWS

## The Largest Selling LIGHTNING ARRESTER At Any Price!

NO. AT102

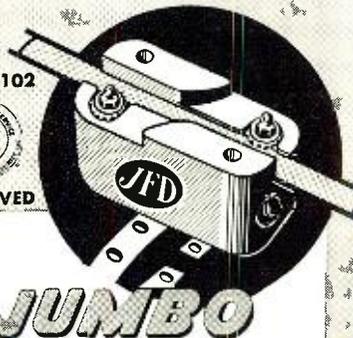

Protects Home and TV Set Against Lightning Hazards

**\$2.25** LIST

U.S. Patent No. D-4664

- Installs anywhere
- No wire stripping, cutting or splicing

(Complete with strap and ground wire.)

**OVER 1,000,000 IN USE TODAY!**

See Your Jobber or Write for Form No. 84



MANUFACTURING CO., Inc.,  
 6105A 16th AVENUE, BROOKLYN 4, N. Y.  
 FIRST in Television Antennas and Accessories



## HEY, MAC!


Send a penny postcard TODAY for our giant bargain catalog already mailed to many thousands of regular customers. Your chance to save big money on TV and radio items for servicemen and builders. Everything in stock! Quick shipment and fair dealing always.

### WEBSTER-CHICAGO 3-SPEED CHANGER


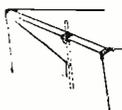
#### Famous Model 100

Plays 7", 10" and 12" records at 33 1/3, 45 and 78 RPM. Brand new and fully guaranteed. Don't wait—buy now at less than 1/2 regular list price! Modernize that old record player while these fine changers are available at our record low price!



#### SUPER V-BEAM

**\$2.95** each

in Lots of 10

Only \$3.25 Each, Singly

Pre-assembled V-Beam for one-man quick-up. High gain and excellent directivity on all channels. Shipped less mast. Wonderful for fringe areas. Approved by TV installation men everywhere. Unbeatable value!

#### BIG SAVING! 300-OHM TWIN-LEAD!

Standard 300-ohm twin-lead recommended for outdoor use. Will withstand severest weather conditions. Buy in quantity and save at our record low price. Per 1000 ft. **\$1.995**

**STAR ELECTRONIC DISTRIBUTORS, INC.**

Dept. [RN-1] -7736 S. Halsted, Chicago 20, Ill.

**Successful Servicing**  
(Continued from page 35)

ponents are subject to vibration and heat at all times, even when the radio is not operating.

The elimination of ignition and motor noise is no longer the tricky problem it was. The new sets have been designed with this in mind. The various car manufacturers have available hints on removing motor noise from their particular models. We use a 250 watt iron and copper braid to ground various parts of the car, when necessary. Tire static is a problem that can be easily eliminated by injecting special anti-static powder into the inner tube of the tire. A special device to do this, and the powder, can be obtained from *General Cement Company* as well as from the tire manufacturers. A good hint is to also inject it into the spare tire. The reason for this is obvious, sooner or later the customer will have a flat and the spare tire will wind up on one of the wheels.

Fading sets are quite a problem. They can be caused by high generator voltage as well as mechanical distortion of the set. Some service shops recommend putting the set in a large carpenter's vise and subjecting it to different stresses and strains while it is playing. A high generator voltage output will cause output tubes to draw excess grid current and because of this, to distort. A quick check for this is to place the auto radio on 8 volts. Adding an extra cell to a 6 volt battery will accomplish this. Placing the set on 6 volts on a bench from now to doomsday will not show it up.

One of the largest sources of trouble in an auto radio is the vibrator. As you no doubt have noticed, the package in which every new vibrator comes has a warning label which reads something like this "Guarantee void unless buffer condenser is checked." We use an oscilloscope across the primary input to auto radio. Since each vibrator in the auto radio draws a pulsating current, the oscilloscope will read or show this pulsation as a voltage drop or rise. In the preface of the *Radiart* "Vibrator Catalog," there is an excellent description of the functions of the vibrator, condenser, etc. In five seconds, by viewing the oscilloscope, you can tell the condition of the vibrator, the buffer condenser, power transformer, and rectifier tube. It only takes a little practice and you can be an expert in interpreting the pattern on the oscilloscope. Of course, this test can be made without dismantling the set. We make it a practice, whenever we find a shorted buffer condenser in an auto radio, to suggest to the customer that the vibrator be replaced even if it is operating normally at present. If the customer operates his auto radio with a shorted buffer condenser, even for a few minutes, the points of the vibrator are taking such a beating that they are bound to fail in the near future.

January, 1952

**GET YOUR** **BIG, NEW 1952**  
**CONCORD Catalog**  
**FREE!**  
*Send for it NOW!*



**ALL-NEW COMPLETE BUYING GUIDE for Every Need!**

FAMOUS PRODUCTS—VAST STOCKS—LOWEST PRICES

**TV • RADIO • ELECTRONICS**

You save time and money—with this bigger, better 1952 Buying Guide! Here is page-after-page full of the latest and greatest values in Television, Radio and Electronics. It brings right to your finger tips one of the world's largest stocks of nationally known guaranteed quality parts and equipment. You find it quick and easy to get whatever you need—at the very lowest prices! Send for your **FREE Concord Catalog** today! Have it handy for quick reference!

*Supplies for Industry, TV and Broadcast Stations, Schools, Servicemen, Hams, Government, Experimenters and Builders*

**CONCORD RADIO**

901 W. JACKSON BLVD. • CHICAGO  
Over 30 Years of Service to the Radio World

CONCORD RADIO CORP., Dept. RA-52

901 W. Jackson Blvd., Chicago 7, Illinois

Rush FREE Big, New 1952 CONCORD Catalog No. 951

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

- HIGH FIDELITY TV & RADIOS
- PHONOS & RECORDERS
- SOUND SYSTEMS
- HAM GEAR
- TEST EQUIPMENT
- ELECTRONIC TUBES
- PARTS, BOOKS, KITS

**FAST DELIVERY**  
Large and varied stocks insure quick shipment on thousands of items.

**HELPFUL SERVICE**  
Our technical experts give personal attention to your problems!

**INDUSTRIAL DIVISION**  
Experienced staff and centralized efficiency speed service on supplies to industry!

**HIGH FIDELITY**  
Complete systems and custom components for finest reproduction!

**EXPORT DIVISION**  
Special Export Division gives prompt service on orders and inquiries.

**POSITIVE SATISFACTION**  
CONCORD'S policy of quality and value assures you of complete satisfaction!

**FREE SEND FOR IT TODAY!**

# BE A RADIO-TELEVISION TECHNICIAN *Train at Home in Spare Time*



J. E. SMITH, President,  
National Radio Institute,  
Washington, D. C.

## There's a Bright Future For You In America's Fast Growing Industry

Do you want good pay, a job with a bright future and security? Would you like to have a profitable shop or store of your own? If so, find out how you can realize your ambition in the fast growing RADIO-TELEVISION industry. Even without Television, the industry is bigger than ever before. 90 million home and auto Radios, 3,100 Broadcasting Stations, expanding use of Aviation and Police Radio, Micro-Wave Relay, Two-Way Radio for buses, taxis, etc. are making opportunities for Servicing and Communications Technicians and FCC Licensed Operators.

### You Learn by Practicing with Kits I Furnish

With both my Servicing Course and my NEW Communications Course I send you many Valuable Kits of Parts. They "bring to life" theory you learn in my

illustrated texts. Some equipment from both courses is shown below and on previous page. All equipment I send is yours to keep. Among equipment you build is a Tester. Use it to make extra money fixing neighbors' sets while training. Special booklets show you how.

### Training Features Television

Both my Servicing and Communications training include up-to-date lessons on TV principles. Throughout the country my graduates are filling jobs, making good money in both Radio and Television. Remember the way to a successful career in Television is through experience in Radio.

### Send NOW for 2 Books FREE— Mail Card

Send the Postage-Free card now for my FREE DOUBLE OFFER. You get Sample Servicing Lesson to show you how you learn at home. Also my 64-page book, "How to Be a Success in Radio-Television." Read what my graduates are doing, earning; see equipment you practice with at home. Mail card now. We pay postage. J. E. SMITH, President, National Radio Institute, Washington 9, D. C. Our 38th Year.

## Read What Successful NRI Graduates Say:



### Radio Operator with ABC

"I was a bookkeeper with a hand-to-mouth salary. Now, a Radio Operator." —N. H. Ward, Ridgefield Park, N. J.



### Can Step Into FM, Television

"When I enrolled with N.R.I., was a laborer. Now I have a position paying over \$10 a day." —R. Ford, Phila., Pa.



### Is Broadcasting Operator

"Now employed at station WHAW as operator. I have also opened my own Radio business." —R. J. Bailey, Weston, W. Va.



### \$10 Week In Spare Time

"Before finishing your course, I learned \$10 a week in Radio servicing in my spare time." —S. J. Petrucci, Miami, Fla.



### \$10 to \$15 Week Spare Time

"4 months after enrolling averaged \$10-\$15 a week spare time servicing Radios. Now have business." —W. B. Weidner, Brooklyn, N. Y.



### Last Job, Now Has Own Shop

"Got laid off. Best thing that ever happened as I opened a Radio shop." —E. T. Slate, Corsicana, Texas.

## Make Extra Money While Learning


Keep your job while training. Learn Radio-Television principles from illustrated lessons. Get Practical Experience experimenting with circuits common to Radio and Television. Many students make \$5, \$10 a week extra fixing neighbors' Radios in spare time while learning. I send you special booklets that start teaching you the day you enroll.



**IMPORTANT!**  
See Other Side

**Extra Pay in Army,  
Navy, Air Force**

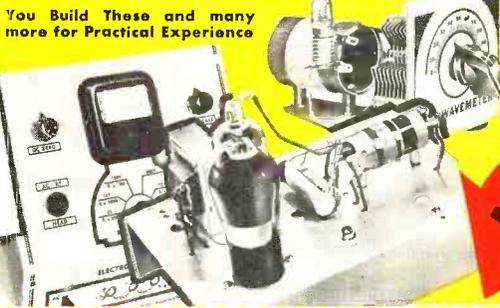Knowing Radio, TV, Electronics can help you get extra rank, extra prestige, more interesting duty at pay up to several times a private's base pay. You are also prepared for good Radio-TV jobs upon leaving service. Mail Coupon NOW.



You Build These and many more for Practical Experience

## MAIL POSTAGE FREE CARD TODAY

### Want Your Own Business?


Let me show you how you can be your own boss. Many N.R.I.-trained men start their own business with capital earned in spare time. Robert Dohmen, New Prague, Minn., whose store is shown at right, says, "Am now tied in with two television outfits and do warranty work for dealers. Often fall back to N. R. I. textbooks for information on installing Television sets."



FIRST CLASS  
Permit No. 20-R  
(Sec. 34.9 PL & R)  
Washington, D. C.

**BUSINESS REPLY CARD**  
No Postage Stamp Necessary If Mailed In The United States

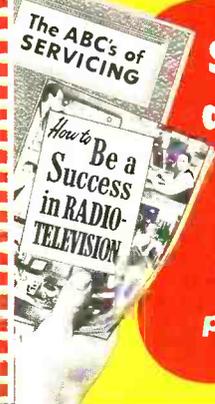4c POSTAGE WILL BE PAID BY  
NATIONAL RADIO INSTITUTE  
16th and U Sts. N. W.  
Washington 9, D. C.



**SAMPLE LESSON  
and 64-PAGE BOOK  
Both FREE**

Cut out and mail  
postage-free card now!

J. E. SMITH  
President,  
National Radio  
Institute,  
Wash., D. C.


# I Will Show You How to Learn RADIO-TELEVISION

## by Practicing at Home in Spare Time


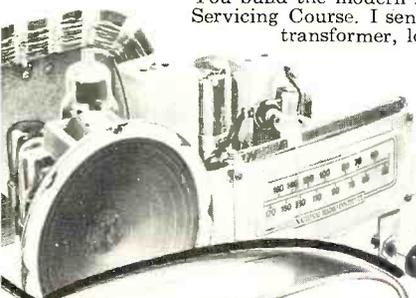
### You Practice **SERVICING** with Equipment I Furnish

You build the modern Radio (at left) as part of my Servicing Course. I send you speaker, tubes, chassis, transformer, loop antenna, everything you need. You use it to make many tests, get practical experience you need to make EXTRA money fixing Radios. I send you many other kits of parts with which you build other circuits common to Radio and Television, some of which are pictured on the next page. All equipment is yours to keep. See and read about them in my FREE 64-PAGE BOOK. Mail card below.



### You Practice **COMMUNICATIONS** with Equipment I Furnish

As part of my Communications Course I send you kits of parts to build the low power broadcasting transmitter shown at the right and many other circuits common to Radio and Television. You use this equipment to get practical experience putting a station "on the air," performing procedures demanded of Broadcast Station operators. I train you for your FCC Commercial Operator's License that puts you in line for good pay in Radio or Television Broadcasting. Mail card below.



**NEW! Advanced Television Practice!**

New, special TV kits furnished to build high-definition SCOPE... RF OSCILLATOR with flyback power supply... complete TV SET... many other units. You see pulse, trapezoidal, saw-tooth wave forms. Get valuable PRACTICAL EXPERIENCE locating and correcting TV troubles. Mail coupon for facts, pictures and prices!

CUT OUT AND MAIL CARD

SEE OTHER SIDE THE TESTED WAY TO BETTER PAY

NOW!

NO POSTAGE NEEDED

## Both FREE

Sample Lesson & 64-Page Book

ACT NOW! Send for my DOUBLE OFFER FREE. This card entitles you to Sample Lesson on Servicing; shows how you learn Radio-Television at home. You'll receive my 64-page Book, "How To Be a Success in Radio-Television." Mail card now! No postage needed. J. E. SMITH, President, National Radio Institute, Washington 9, D.C. Our 38th year.

Mr. J. E. SMITH, President, Dept. 2 AR  
National Radio Institute, Washington 9, D. C.

Mail me Sample Lesson and 64-Page Book, "How to Be a Success in Radio-Television." (No Salesman will call. Please write plainly.)

NAME..... AGE.....  
ADDRESS.....  
CITY..... ZONE..... STATE.....

The ABC's of SERVICING

How to Be a Success in RADIO-TELEVISION

### Television Is Today's Good Job Maker

In 1946 only 6,000 TV sets sold. In 1950 over 5,000,000. By 1954, 25,000,000 TV sets estimated. Over 100 TV Stations now operating. Authorities predict 1,000 TV Stations. This means more jobs, good pay for properly trained men. Mail this Postage-Free card NOW for FREE book and sample lesson.

# FREE

TELLS HOW—

**WE GUARANTEE  
TO TRAIN YOU AND COACH YOU  
AT HOME UNTIL YOU GET  
YOUR FCC LICENSE**

if you have had any practical radio experience—  
amateur, Army, Navy, radio repair, or experimenting



TELLS HOW YOU CAN GET A **FREE TELEVISION ENGINEERING COURSE**

**TELLS HOW— Our Amazingly Effective  
JOB-FINDING Service Helps CIRE Students  
GET BETTER JOBS**

**GETS JOB WITH CAA**

"I have had a half dozen or so offers since I mailed some fifty of the two hundred employment applications your school forwarded me. I accepted a position with the Civil Aeronautics Administration as a Maintenance Technician. Thank you very much for the fine cooperation and help your organization has given me in finding a job in the radio field."

Dale E. Young, 122 Robbins St., Owosso, Mich.

**GETS PUBLIC UTILITIES JOB**

"I have secured the position of Radio Technician with the Toledo Edison Company. I want to thank you once more. The help you gave me was much more than would ordinarily be expected—both in

obtaining my license and in finding employment."  
Norman W. Stokes, Jr., Rt. 11, Box 612, Toledo 7, O.

**GETS DEVELOPMENT ENGINEERING JOB**

"I wish to express my thanks for the Applications-For-Employment you recently prepared for me. I received 3 telephone calls and one letter. As a result I am now employed in a development engineering capacity."

K. E. Fosberg, 26 Soley St., Charlestown, Mass.

**GETS BROADCAST JOB**

"I have accepted a position with KWAD. I secured this position through the help of your Job-Finding Service and I had at least six other offers. I am sincerely under obligation to you."

Fred W. Kincaid, Box 241, Wadena, Minn.

Your FCC Ticket  
Is Recognized  
in All Radio Fields  
as Proof of  
Your Technical Ability

**ACT  
NOW!**

**TELLS HOW— Employers Make JOB OFFERS  
Like These To Our Graduates Every Month**

Telegram from Chief Engineer, Broadcast Station, Pennsylvania: "Immediate opening for engineer. Automobile and First Phone a must. If graduate available, please forward name and address."  
Letter from Chief Engineer, Broadcast Station, Montana: "Immediate opening for Engineer-Announcer. Basic salary \$62.50 . . . real future for

right man."  
Letter from Chief Engineer, Broadcast Station, Tennessee: "Have opening for operators. If you have men, please have them contact us."  
These are just a few examples of the job offers that come to our office periodically. Some licensed radio men filled each of these jobs; it might have been you!

**HERE'S PROOF FCC LICENSES ARE  
OFTEN SECURED IN A FEW HOURS OF STUDY  
WITH OUR COACHING AT HOME IN SPARE TIME**

Name and Address	License	Mrs. of Training
James A. Gram, 11 West Main St., Cuba, New York . . .	1st class telephone	34
Ernest K. Hodson, Box 1001, Caldwell, Idaho . . .	1st class telephone	71
Howard J. Kischessy, Rt. 2, Box 736, El Cajon, Calif. . .	2nd class telephone	49
Ralph I. Nichols, 510 Elm St., Kerrville, Texas . . .	2nd class telephone	34
Elbert L. Risinger, P.O. Box 122, Bodys, Texas . . .	1st class telephone	34
Harry R. Rogers, R.R. 6, Lafayette, Indiana . . .	2nd class telephone	50

Ours is the only  
home study  
course which  
supplies FCC-Type  
Examinations  
with all lessons  
and final tests.

**Mail This Card Now  
NO POSTAGE REQUIRED  
Get All 3 FREE**



I want to know how I can get my FCC ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a sample FCC-type exam and the amazing new booklet, "Money-Making FCC License Information".

I want to know how greater technical knowledge will bring promotion, better pay, security. Send me complete information, free, about CIRE Courses A, B, and C, with coaching and training under personal supervision of Carl E. Smith, E.E., at home in my spare time. (See our ad on next page.)

Be sure to check here if you have FCC Commercial License

Yes  No

Tell me how I can get your FREE Television Course.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_  
ZONE \_\_\_\_\_ STATE \_\_\_\_\_

**CLEVELAND INSTITUTE OF RADIO ELECTRONICS**  
Desk RN-37, 4900 Euclid Building, Cleveland 3, Ohio  
(Address to desk to avoid delay)

SEE OUR AD ON NEXT PAGE



*Where Will You be*  
in **ELECTRONICS**  
SIX MONTHS FROM TODAY



**Study NOW for a Better Job Then!**

**IF YOU Want • A BETTER JOB • BETTER PAY • SECURITY  
ADD TECHNICAL TRAINING TO YOUR PRACTICAL EXPERIENCE**

**These CIRE Courses Are the Solution to Your Problem of Promotion, Better Pay, Security**

**A—Master Course in Radio Communication — 4 courses in 1.**

1. Complete Training and Coaching in the Fundamentals of Radio.
2. Complete Training and Coaching for the FCC Commercial License Examinations.
3. Complete Training and Coaching for the Jobs Which Require an FCC License.
4. Complete Training and Coaching for Broadcast Station Engineering and Operation.

**B—Advanced Course in Radio Communication Engineering**

A genuine college-level radio-engineering course, completely mathematical in treatment. For the advanced radioman with considerable practical experience and training.

**C—Special Television Engineering**

An advanced college-level course for the radioman who has had formal training equivalent to A or B.

**You Will Easily Handle Professional Problems Like These with Carl E. Smith's Coaching-Training**

1. An FM station feeds 3 kw power into an antenna with a power gain of 4 and height of 500 feet. Find the field strength at 25 miles and a height of 30 feet.
2. Design an H pad to match 250 ohms to 600 ohms with 15 db loss.
3. Find the values of reactances to be used in a T network matching a 230 ohm transmission line to an antenna with impedance  $100 + j85$ . Phase shift to be  $-90$  degrees.
4. Design a low-pass m-derived filter to cut off at 1000 cps and have an infinite attenuation at 1200 cps.

**This Famous Broadcast RADIO ENGINEER Personally Supervises Your Training**



CARL E. SMITH, E.E.

Let Carl E. Smith, Nationally Known Radio and Consulting Engineer, through an amazingly complete home-study plan of coaching and training, teach you to handle radio-television-electronic engineering, successfully at home, in your spare time.

**Then Use Our Amazing Free Job-Finding Service to Get the Better Job — Better Pay — Security Your Increased Knowledge Entitles You to Have**

**LOOK AT THE BENEFITS THESE STUDENTS HAVE GOT!**

"Since beginning the course, I have been appointed Director of Engineering of WLOS and WLOS-FM, and feel this course is responsible."  
W. M. Chambers, Radio Station WLOS, Asheville, N. C.

"I should like to thank the Institute for all the good things that have come along my way since I started taking your course. I have received several raises in pay and have been promoted to Assistant Engineer."  
Frank Schoales, Asst. Eng., CHEX, Ontario, Canada.

"After working at WHIZ for two years doing control room engineering, my 1st class ticket has already netted one raise in pay, with more to follow. Thanks for a well planned course and for the School's cooperation."  
John P. Armstrong, 1349 Newman Drive, Zanesville, Ohio.

"I have recently completed your Nelson's Master Course, and have found it to be an excellent course in radio. It is a fine course for beginners in radio, and equally good for anyone already in the radio field desiring a review in basic radio, as well as a wealth of up-to-date material in all phases of radio communication."  
Robert J. Schilling, Chief Engineer, Radio Station WIMS, Michigan City, Ind.

**These Benefits Can Be Yours, Too!**

**CLEVELAND INSTITUTE OF RADIO ELECTRONICS**  
4900 EUCLID BLDG. • CLEVELAND 3, OHIO

Desk RN-37 (Address to Desk to Avoid Delay)

**YOU CAN GET THIS TELEVISION COURSE FREE MAIL POSTCARD TODAY!**

**TEAR OUT AND MAIL THIS CARD NOW!**

Be Sure to Fill Out Reverse Side

**BUSINESS REPLY CARD**  
NO POSTAGE STAMP NECESSARY IF MAILED IN UNITED STATES

2c POSTAGE WILL BE PAID BY

**CLEVELAND INSTITUTE OF RADIO ELECTRONICS**

DESK RN-37

4900 EUCLID BLDG.

FIRST CLASS  
PERMIT NO. 8685  
(SEC. 34.9 P. L. & R.)  
CLEVELAND, OHIO

CLEVELAND 3, OHIO

## Artificial Hangover

(Continued from page 61)

able, the a.c. reactance of all of the power supply elements should be calculated for the lowest frequency that the amplifier will handle. For example, a ten microfarad condenser, a fairly common value in filter circuits, will have an a.c. reactance of approximately 800 ohms at 20 cycles and in the case of output tubes having relatively low impedance plate loads a relatively large voltage may be developed across the condenser at this frequency.

Aside from the advantages of improving the apparent acoustics of the reproducing environment, artificial hangover has a number of other very important applications. One of these is the fact that it can give the effect of very greatly improved "transient" response from conventional loudspeakers. The reason for this is the fact that the conventional loudspeakers may require a definite period of time to build up to maximum peak acoustic output. As a result, transients of very short duration may not be reproduced at all, even though an acoustic environment were present which would allow the listener to hear them if reproduction had been perfect. By introducing additional hangover in the signal *before* it reaches the loudspeaker, transients with very brief initial duration may last long enough to bring the acoustic output from the speaker to the proper level. By making the amount of hangover introduced of the same order as that produced by the worst ringing resonance in the speaker very smooth transient response which should be superior to virtually any mechanical arrangement of loudspeakers may be obtained. However, in the writer's experience, it appears desirable to use this technique on speakers which do not evidence any serious ringing resonances as the improved response tends to make cross modulation due to the resonance more noticeable due to the greater *average* power contained therein. In the case of speakers in which the original transient response falls off gradually at a rate of approximately 6 db per octave in relation to the steady state response, the hangover technique appears to work very well in that a hangover of 100 cycles at ten thousand cps, ten cycles at one thousand cps and one cycle at one hundred cps all represent the same time duration of one one-hundredth second, an interval not too easily recognizable by the ear. Thus the apparent transient response of the speaker can be made to closely simulate the steady state characteristics. Similarly, if hangover is properly introduced, it can considerably reduce the audible effects of serious resonances in the reproducing system by making the audible output more uniform over an appreciable band of frequencies, thereby tending to eliminate "one note thump"

January, 1952

"Workshop DUBL-VEE antennas  
are second to none."

Francisco Laboratories

HYPROD SERVICE FOR HEYER DEVICES  
EQUIPMENT REPAIRED, REMANUFACTURED AND EXCHANGED

3015 GLENDALE BOULEVARD  
LOS ANGELES 24 CALIFORNIA  
39 NORMANDY 6676  
OLYMPIA 0602

20 August 1951

Workshop Associates, Inc.  
135 Crescent Road  
Needham Heights 94, Massachusetts

Gentlemen:

Having originated products in other fields, we can appreciate to the fullest extent a quality product. We have used Workshop DUBL-VEE antennas extensively since they were first introduced to the Southern California market. The results of tests in low signal fringe areas convinced us that the Workshop TV antennas are second to none.


There are many imitators of your products, as you are doubtless aware, but the differences are apparent once the DUBL-VEE is compared in operation against the others. Your engineering department is to be complimented for originating what we believe is one of the finest television antennas on the market.

Yours very truly,

FRANCISCO LABORATORIES

Wallace E. Francisco  
Wallace E. Francisco

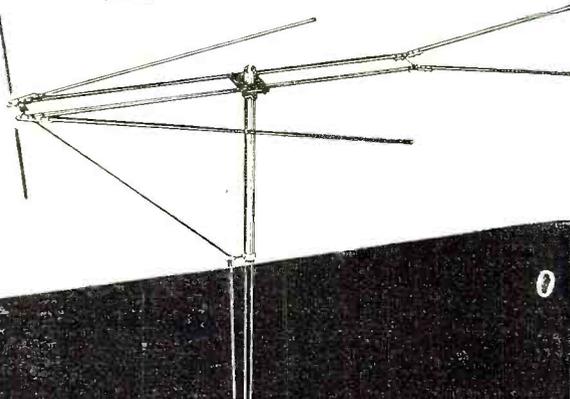"The Workshop-patented DUBL-VEE is tops for all-channel performance. And remember last winter? Rugged DUBL-VEE's stood up best. Specify DUBL-VEE and be sure."



The WORKSHOP ASSOCIATES

DIVISION OF THE GABRIEL COMPANY

Specialists in High-Frequency Antennas  
135 Crescent Road, Needham Heights 94, Massachusetts



The music you love sounds better  
with a

# McIntosh

## World's Most Efficient Amplifier

Unsurpassed for performance and quality — your entire record collection (either tape or disc) will reproduce better with lifelike reality through this new amplifier circuit.

Unequaled for quality reproduction of any sound source, the McIntosh offers **OVER 65% EFFICIENCY; DYNAMIC RANGE OVER 70 db.; FREQUENCY RESPONSE 20-20,000 cps.**

Music lovers agree that McIntosh gives superlative audio reproduction!

50W 2 Amplifier  
50 Watts (Peak: 100)

Reaches audio peaks from 200 to 400 times the average power of speech and music

Less than 1% distortion of peak power

Works perfectly with variable impedance loads

1% intermodulation distortion at peak power

20W 2 Amplifier  
20 Watts (Peak: 40)

AE-2 8-stage Amplifier Equalizer perfectly matches the stable, distortion-free amplifier performance.

Send for Free Catalog

**McINTOSH ENGINEERING LABORATORY, Inc.**  
320 WATER ST. • DEPT. RT-1 • BINGHAMTON, N. Y.

DID YOU GET IT? IF NOT  
SEND NOW FOR B-A's  
136 BIG PAGE  
**FREE CATALOG**

1952  
**RADIO TELEVISION ELECTRONICS**

REPAIRS • SUPPLIES • TESTERS • PARTS  
REPRODUCTION • PLANS • TUBES • INSTRUMENTS  
EXPERIMENTAL • REPAIRS • CATALOGS

# B-A

INCLUDING 21 PAGES OF  
DOLLAR-SAVING BARGAINS!

BURSTEIN-APPLEBEE CO.  
1012-14 McGee St.  
Kansas City 6, Mo.

**FREE**

Send your 1952 catalog to:


Name.....

Address.....

City.....State.....

**BURSTEIN-APPLEBEE CO.**

## Model 200 AM & FM SIGNAL GENERATOR

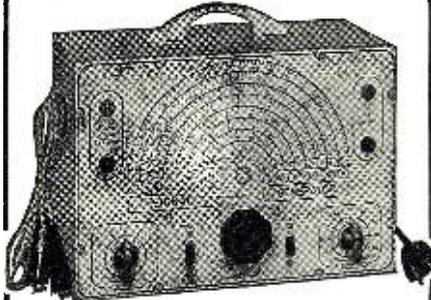

Specifications: • **R. F. FREQUENCY RANGES:** 100 Kilocycles to 150 Megacycles. • **MODULATING FREQUENCY:** 400 Cycles. May be used for modulating the R.F. signal. Also available separately. • **ATTENUATION:** The constant impedance attenuator is isolated from the oscillating circuit by the buffer tube. Output impedance of this model is only 100 ohms. This low impedance reduces losses in the output cable. • **OSCILLATORY CIRCUIT:** Hartley oscillator with cathode follower buffer tube. Frequency stability is assured by modulating the buffer tube. • **ACCURACY:** Use of high-Q permeability tuned coils adjusted against 1/10th of 1% standards assures an accuracy of 1% on all ranges from 100 Kilocycles to 10 Megacycles and an accuracy of 2% on the higher frequencies. • The Model 200 operates on 110 Volts A.C. Comes complete with output cable and operating instructions.

**\$21.85** NET

**Sold on Money-Back-If-Not-Satisfied Guarantee.**


We carry a complete line of test equipment. Write for **FREE Catalog**  
**GENERAL ELECTRONIC DISTRIBUTING CO.**  
Dept. RN-1, 98 Park Place, New York 7, N. Y.

such as is found in the bass regions of some systems. However, as previously noted, care should be taken that serious cross modulation does not take place.

Another factor of definite importance is the fact that hangover can actually multiply the over-all efficiency of amplifiers, speakers, and similar devices by greatly reducing the ratio between the peak and average powers which must be transmitted for a given amount of audibility. In speech or music this ratio is claimed to be as high as four hundred to one on a power basis. This ratio is occasionally used as a justification of very high power audio equipment for home use and would be a correct assumption if no acoustic hangover were introduced either in the original pickup or in the acoustics of the reproducing environment. However, if hangover is present, and as noted earlier it is a very important element in tonal quality, then the ratio of peak-to-average power content will be much lower, with the result that much less peak audio power is required and the attendant problems are diminished. On the basis of limited observation it seems likely that from ten to twenty cycles of linearly decaying hangover will be quite acceptable, with the result that the actual efficiency of an amplifier or loudspeaker may be increased from five to ten times in the case of transients with very short duration. This factor should readily lend itself to applications in which it is desired to obtain the maximum possible signal-to-noise ratio, e.g., the highest average level practical. One possible application of this is the music distribution system, such as the juke box, in which it is desired to have good tonal rendition under conditions of appreciable background noise. An experimental installation by the author resulted in a system with good clean bass response at a level which did not seriously interfere with conversation in the vicinity. Similarly, the previous high intensity peaks which had tended to deafen listeners and produce ear fatigue were eliminated. Of particular interest to some users should be the fact that artificial hangover tends to greatly improve the character and audibility of outdoor reproduction.

For the high quality enthusiast, a number of other benefits may be achieved through use of controlled hangover, principal of which is correcting for some of the distortions that may arise in the elements of the reproducing chain. One of these is in reducing the effects of intermodulation distortion that may be present in a signal by means of demodulation or smoothing out due to the hangover. Likewise, a much greater apparent dynamic range may be produced from a signal which previously contained relatively little hangover, and in a similar manner an apparent increase in signal-to-noise ratio can be obtained when the noise is of sufficiently continuous nature, such as hum, that hangover does
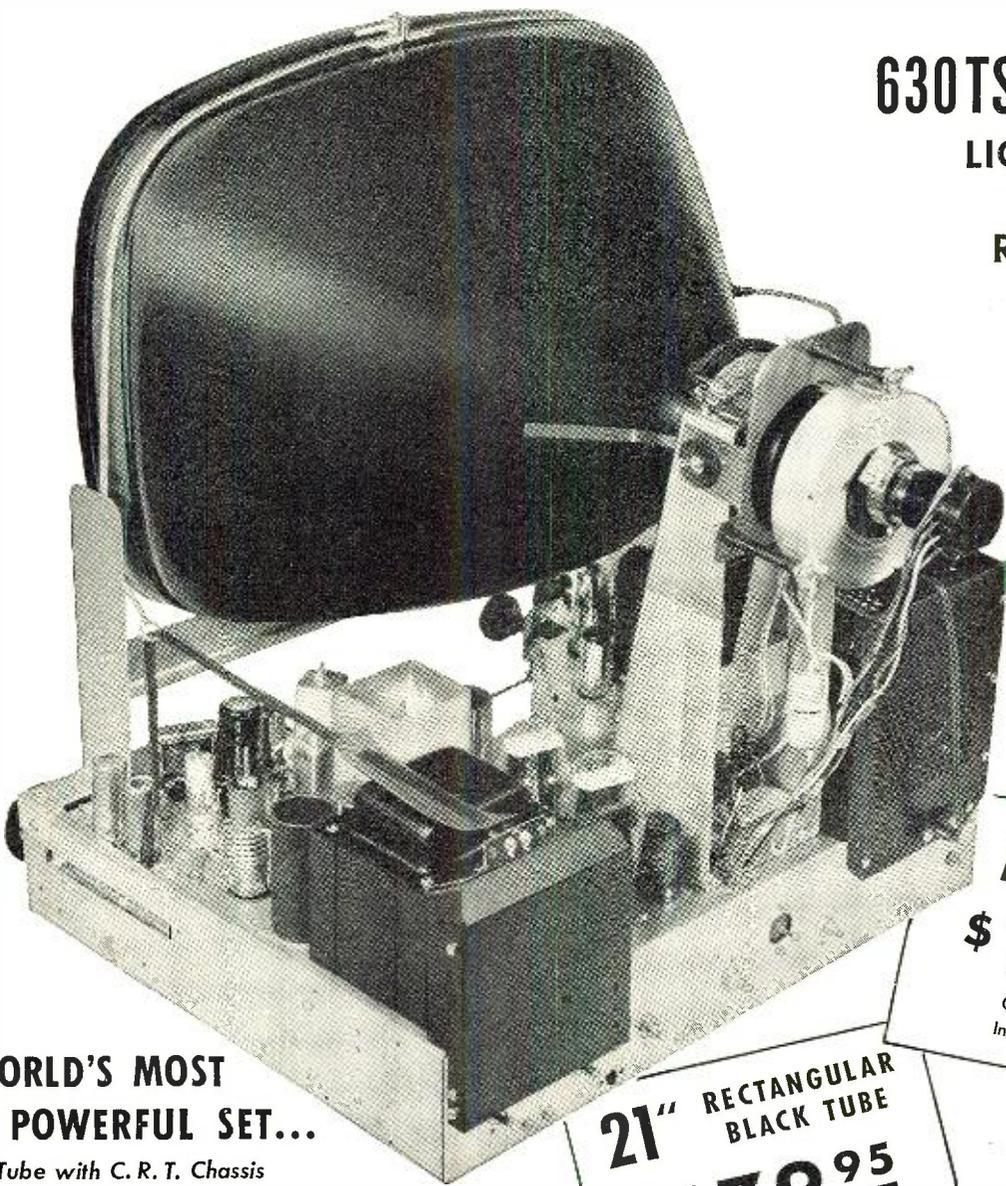
# Now! Get the TV chassis that has everything you want



**630TS CHASSIS**

LICENSED  
BY  
R. C. A.

## WORLD'S MOST POWERFUL SET...

31 Tube with C. R. T. Chassis

- Best for fringe area reception
- Improved keyed A. G. C.
- Full 4 megacycles 14,000 to 16,000 output
- A. F. C. Sync Separator Syncrolok Improved
- 25 Microvolts or better
- Complete chassis with tubes aligned
- Use 70° to 90° deflection yoke coil
- Standard tuner F.M. Radio
- 6-inch 'True-to-Life' speaker

**17" RECTANGULAR  
BLACK TUBE**  
**\$159<sup>95</sup>**  
Complete Chassis  
Including Speaker

**21" RECTANGULAR  
BLACK TUBE**  
**\$179<sup>95</sup>**  
Complete Chassis  
Including Speaker

**NO EXTRA CHARGES**

— R. M. A. guarantee on all parts

**IMMEDIATE DELIVERY**—15% Down—Balance

C.O.D. Remit in full—save C.O.D. charges

(Chassis equipped with 12-inch speaker, \$5.00 additional)

●  
**Export Orders Filled**

**GEM RADIO & TELEVISION CORP.**


900 Passaic Avenue

• East Newark, N. J.

# HARVEY

DELIVERS PROMPTLY...  
EFFICIENTLY... AND  
AT LOWEST PRICES!

## WILLIAMSON HR-15 AMPLIFIER KIT

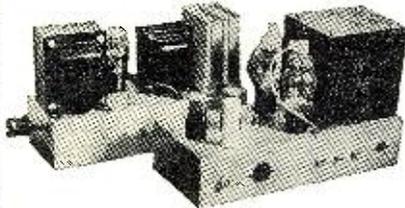

The famous Williamson HR-15 amplifier circuit... now available with the original Partridge transformers built to Williamson's specifications. Build this kit in 3 hours or less, and enjoy sound of a quality you never heard before. The HR-15 is a 2-Chassis power amplifier for use with tuners or other front ends having own volume and tone controls. All American triodes, 2-6SN7GT, 2-807, or 6BG6G in PP output, 5V4G rectifier. Response  $\pm .5$  db, 10-100,000 cycles. Output impedances 1.7 to 109 ohms in 8 steps. Absolute gain 70.8 db. of feedback around 4 stages and the output transformers. Kit is Complete with Tubes, Punched Chassis, Pre-wired Resistor Board, Sockets, Genuine Partridge Output Transformer, and All Necessary Parts. **\$76.50**

**HR-15T** A Williamson Kit with all TRIAD TRANSFORMERS... including power transformer, chokes and specially designed output transformer which is completely sealed in tar.  $\pm 2$  db. 10-100,000 cps. Harmonic Distortion less than .1% - 10 watts output. Output impedances 4-8-16 ohms. **\$69.50**  
Both HR-15 and HR-15T Kits available with KT-66 tubes for \$3.00 extra.

## If it's GOOD... HARVEY has it!

**HARVEY'S** immensely popular **AUDIO-Torium** is a musical paradise for high fidelity sound enthusiasts. Here you can see, hear, enjoy the products of 59 leading manufacturers. And from our working display, we can instantly "custom match," for your direct comparison, any combination of components and equipments... from the least expensive to the "best in the world."

If you would like to receive future HARVEY sound equipment bulletins... or if you want detailed information on specific products... or if you want assistance in planning your own installations, please write to DEPT. RN-1. No obligation, of course.

**NOTE:** In view of the rapidly changing market conditions, all prices shown are subject to change without notice and are net, F.O.B., N.Y.C.

Telephone **hrc** LUxemburg 2-1500

**HARVEY**  
RADIO COMPANY, INC.  
103 West 43rd St., New York 18, N. Y.

not increase its audibility. The same may apply to noise such as needle scratch if it is of a fairly constant nature and the system does not tend to "ring" at any one frequency.

Another interesting advantage of controlled hangover is in correcting for nonlinearity in the reproducing chain. As nonlinearity usually causes weak signals to be suppressed in the presence of strong ones, a low amplitude transient wave train may be damped too rapidly when passing through a nonlinear element. This is very apparent in some cases in which a particular instrument will sound as if it were almost stripped of harmonic content in the reproduction. If the initial portions of the low amplitude wave trains still exist, partial compensation may be achieved by introducing hangover. Another form of nonlinearity may exist in which some portion of the system refuses to pass signals below a certain amplitude. This may be noted in electromechanical devices, such as speakers, pickups, and microphones, as well as in some amplifier circuits. A similar effect is produced by the human ear in the presence of an appreciable noise level. Again the result is that damped wave trains are not produced for their full duration and require the application of additional hangover for naturalness.

In conclusion it should be noted that the artificial hangover system proposed in this article is not the same thing as the conventional "echo" chamber which, though useful in specific applications, is not applicable in the sense in which the phase delay hangover system is used, inasmuch as the phase delay system permits exact relationships to be maintained between the initial transient and the hangover at any frequency, while the echo chamber, or even the best of present day concert halls, may present problems due to phase interference. The advantages of controlled hangover should be appreciated by anyone who likes music whether he be a musician or high fidelity enthusiast with a critical ear, or someone who is simply searching for a pleasing combination of sounds.



# Columbia

GEM OF THE SURPLUS

## HAM WANTED!

Must be intelligent but lazy and interested ONLY in making a lot of money without working for it. If you meet these qualifications, we've got just the deal for you. Round up all your new or used radio gear and sell it to Columbia immediately! We pay mile-high prices! Write us and see!

## PLATE TRANSFORMER

Save \$35.05! Has 1,750 V. on each side of center tap @ 400 mls. This baby lists for \$110.00. Brand new, name brand, and going fast at... ONLY \$24.95

## 4 V. BATTERY PACK

For TBY Walkie-Talkie. New, in original boxes... \$4.95

## PE-103 DYNAMOTOR

With filter base and cords. 6 or 12 V. input; 500 V. output. Excel. cond. Limited quantity... \$24.95

## VHF ARC-5 R-28 RECEIVER

10-tube, superhet with 4-channel xtal controlled freq. range of 100-156 mcs. Makes a dream fixed or mobile unit. Brand new. \$32.50.

## VHF ARC-5 T-23 TRANSMITTER

Companion to above receiver. Uses plate modulation, 1625 osc., 1625 and 832-A triplers; 832-A final. This VHF set can be converted to 6 or 10 meters easy as pie. Excel. cond. \$42.50.

## SPECIAL

Both of above units are terrific for 2 meters, ham, novice, CAP or CD. Special price for the combo: ONLY \$71.95.

INCLUDES FREE GIFT OF CONVERSION BOOK COVERING WORLD OF INFORMATION.

## 5 W. MARINE RADIO TELEPHONE

Jefferson-Travis Emerson Radio Corp. Freq. 2-3 mcs. 2-channel, x-tal control. Complete with mike, speaker, 110 V. charging unit, all tubes and instructions. 6 V. input or will run 8-10 hrs. on own battery pack. BRAND NEW, BOXED (Less xtals & batteries) ONLY \$79.50.

**CIRCUIT BREAKER:** 15 amp 110 VAC. New. \$1.59  
20 amp 110 VAC. New. \$1.79

## PM SPEAKERS 6 OHM ALL BRAND NEW!

4" square ..... \$1.75 8" round ..... \$4.25  
5" round ..... 1.99 10" round ..... 5.95  
6" round ..... 2.49 12" round ..... 7.95  
**TD-1 CHEST SET:** With P-1 button. NEW. Only \$2.95

## BC-728-A PORTABLE RECEIVER

This item is harder to find than square eggs. But YOU asked for 'em so here they are. 4 adjustable push-button controlled frequencies in the 2-6 mc. band. Wonderful for marine, police and ham use. Uses a 2 V. wet cell for power. Can be held in one hand. Complete with tubes, speaker AND NEW BATTERY. Good cond. For our hams ONLY \$28.95.

## ARC-5 OR 274-N TRANSMITTERS

2-1-3 mcs. New ..... \$19.95  
2-4 mcs. Used, excel. cond. .... 14.95  
4-5-3 mcs. Used, good cond. .... 6.95  
2-1-7 mcs. .... 5.50  
7-9-1 mcs. .... 12.50

## ARC-5 OR 274-N RECEIVERS

5-5-1.5 mcs. Brand new ..... \$49.50  
1-5-3 mcs. Brand new ..... 24.50  
6-9-1 mcs. Used ..... 7.95  
6-9-1 mcs. Brand new ..... 11.25  
**28 V. RECEIVER DYNAMOTOR** ..... 1.00  
**14 V. RECEIVER DYNAMOTOR** ..... 9.95  
**RACK FOR DUAL TRANSMITTER** ..... 2.95  
**BC-442-A ANTENNA RELAY** with 50 mmfd. condenser. Excel. cond. .... 3.95

## METERS! OUR BARGAIN SPECIALS!

0-100 VDC movement with 20-0-20 scale.  
2 in. sq. Simpson. Used. .... \$2.25  
0-20 kilovolt DC 3 in. rd. Westinghouse.  
FS equals 1 ma. Use external multiplier.  
Only ..... 4.95  
0-25 MADC 2 in. rd. Weston ..... 2.99  
0-2 amp. RF 2 in. rd. Thermocouple type ..... 2.99  
0-9 amp. RF 2 in. rd. Westinghouse ..... 2.99

All orders F.O.B. Los Angeles. 25% deposit required.  
All items subject to prior sale.

## COLUMBIA ELECTRONIC SALES

522 South San Pedro Street  
LOS ANGELES 13, CALIFORNIA

**Low-Pass Filter**  
(Continued from page 38)


able reluctance cartridge can be used to form a low-pass filter.

One of the most common variable reluctance cartridges in use today is the standard impedance *General Electric* pickup. This unit bears the model number RPX-040 or RPX-041 in the single needle version and RPX-050 in the twin stylus type. The inductance of this pickup is specified as 520 millihenrys. With the value of the inductance and of the "Q" both specified, the capacity and resistance required in the filter become a function of the cut-off frequency alone. Fig. 3 is a graph of the capacity and resistance required to form a low-pass filter of the type described, using a *General Electric* pickup. The frequency plotted on this graph is that at which the response passes through zero decibels in the negative direction as shown on Fig. 2. If it is desired to consider the minus 3 decibel point on the curve of Fig. 2 as the cut-off frequency, then  $f_0$  of Fig. 3 is 77% of this value.

Only one of the three values,  $RC$ , and  $f_0$ , can be chosen at will; the other two are specified by the relations indicated on the graph of Fig. 3. Since the graduation in commercial condenser sizes is very coarse, the most practical procedure is to choose an available value of capacity which gives a cut-off frequency closest to that desired. Then the resistance required for this capacity can generally be obtained with one or two resistors. The resistance used need be within only  $\pm 15\%$  of the value specified on the graph to retain the desired cut-off characteristics in the filter.

One important point which must be

Fig. 3. Graph used to determine capacity and resistance required to form a low-pass filter. See text for all details.

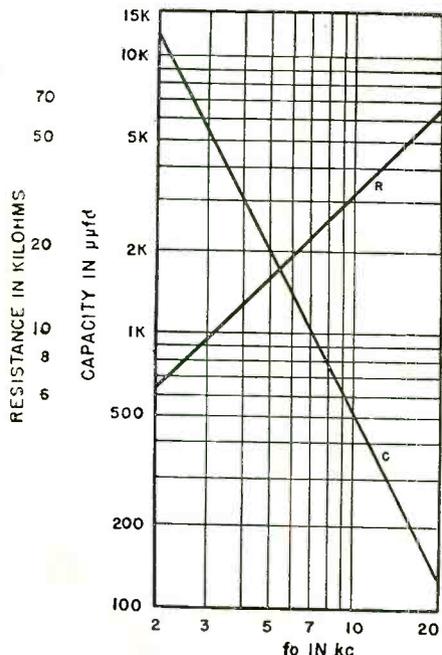

**for OPTIMUM P.A. PERFORMANCE  
at moderate cost!**

Specify

**CHICAGO**

**Public Address Range  
Audio Transformers**

These famous CHICAGO "Sealed-in-Steel" Output Transformers are the choice of many leading makers of high-quality amplifiers. Unmatched for service in the Public Address range, they have a frequency response within 5 from 50 to 10,000 cycles, and will deliver their full rated output over this entire range.

Line and voice coil impedances used in the design of these output units are those recommended by RMA. All have tertiary windings to provide 10% inverse

feedback. Output and matching drivers are fully enclosed in one-piece drawn-steel cases. Available in choice of two dependable constructions: with wire leads—at surprisingly modest cost; with solder lug terminals, at slightly higher cost. Order from your electronic parts distributor. Be sure to ask for CHICAGO P.A. Range Audio Transformers.



**OUTPUT TRANSFORMERS**

Catalog No.	Typical Output Tubes	Class	Impedance Primary-Secondary	Max. D-C in Pri.	Power Level	List Price
PCO-80 PSO-80	P-P 6B4G's, 6L6's P-P 6V6's, 6L6's	A1 AB	Pri: 5,000 ohms CT Sec: 600/150/ * 16/8/4 ohms	120 ma.	20 watts	\$12.10 16.50
PCO-150 PSO-150	P-P 6V6's, 6F6's P-P 6K6's	AB AB†	Pri: 10,000 ohms CT Sec: 600/150/ * 16/8/4 ohms	200 ma.	15 watts	10.45 14.85
PCO-200 PSO-200	P-P 6L6's P-P Parallel 6V6's	B AB†	Pri: 6,000 ohms CT Sec: 600/150/ * 16/8/4 ohms	250 ma.	30 watts	13.75 18.15

**DRIVER TRANSFORMERS**

Catalog No.	Typical Driver Tubes	Primary Impedance	Max. D-C In Pri.	Ratio Pri./1/2 Sec.	List Price
PCD-10 PSD-10	P-P 6N7's, 6A6's, 6J5's, 6C4's, etc.	20,000 ohms CT	10 ma.	3:1	\$5.50 7.95
PCD-25 PSD-25	P-P 6N7's, 6A6's, 6J5's, 6C4's, etc.	20,000 ohms CT	25 ma.	3:1	5.20 7.70
PCD-100 PSD-100	P-P 6B4G's, 45's, 2A3's, 6L6's, etc.	5,000/10,000 ohms CT	100 ma.	5:1	9.35 13.20

\* Has tertiary winding to provide 10% inverse feedback. † For low distortion, use fixed bias.



**Write for "NEW EQUIPMENT" TRANSFORMER Catalog**

The units described above are typical of CHICAGO'S New Equipment Line featuring engineering that sets the transformer trend in circuit design. Get the full facts on the complete line now. Check the features, check the quality. Check the price: see how little more these tougher, better units cost. Write for your free copy of the CHICAGO New Equipment Line Catalog today.

**CHICAGO TRANSFORMER**

DIVISION OF ESSEX WIRE CORPORATION

3501 ADDISON STREET • CHICAGO 18, ILLINOIS





# THE SENSATIONAL ROCKET

## A POWERFUL MAST MOUNTED BOOSTER

Increases signal strength for single channel reception sensationally. Easy to install—low in price—

only \$34.95 list



Send coupon below for this complete descriptive folder that gives full details about the amazing new Rocket Booster.

THE LaPOINTE-PLASCOMOLD CORP.  
Windsor Locks, Connecticut

Send details on the Rocket Booster.

NAME .....

COMPANY .....

ADDRESS .....

CITY..... ZONE..... STATE.....

noted is that the distributed capacity of the shielded lead and the input capacity of the preamplifier must be added to the value of any additional condenser which is used, to obtain the total capacity.

An example will best illustrate the procedure to follow. A low-pass filter is to be designed with a cut-off frequency of about 7 kc. The phonograph uses a G.E. model RPX-050 cartridge and there is 4 feet of shielded phono lead between the cartridge and the preamplifier. The preamplifier is the NPX-003 built by General Electric, using a 6SC7 tube.

The common type of brown cloth-covered phono lead has a distributed capacity of 80  $\mu$ fd. per foot, resulting in 320  $\mu$ fd. of capacity in the cable. The input capacity of a 6SC7, including the Miller effect, is about 60  $\mu$ fd. Thus, there is 380  $\mu$ fd. of capacity already existing at this point. Fig. 3 shows that 995  $\mu$ fd. of capacity is required for a cut-off frequency of 7 kc. Then a 615  $\mu$ fd. condenser would be required. Using a 500  $\mu$ fd. unit would give a total capacity of 880  $\mu$ fd. This together with a 25,000 ohm resistor would then result in a filter with a cut-off frequency of 7.5 kc. and the correct Q.

A tap switch may be used to switch various resistor-condenser pairs across the input of the preamplifier to provide several cut-off frequencies. A continuously variable filter would be rather difficult to build since the resistance and capacity must be varied at the same time and the resistance must be inversely proportional to the square root of the capacity to maintain the proper value of Q.

To obtain the highest cut-off, no additional condenser is used. A resistor of the value specified in Fig. 3 for the shunt capacity of the cable and preamplifier is used alone.

The previous example also indicates why excessive noise results when a high resistance on the order of 50,000 to 100,000 ohms is used at the input of the preamplifier. The Q of the circuit is greater than one and there is a peak in the response, which increases the noise level.

If it is desired to build a record player which has an extended high frequency range, the shunt capacity of the cable and preamplifier must be maintained below the value indicated in Fig. 3 for the range desired. The system used in the example, with 380  $\mu$ fd. of shunt capacity, has a limit of 11.4 kc. when a 33,000 ohm resistor is used alone as the input of the preamplifier. Increasing the resistor would not materially extend the range, but only increase the response at 11.4 kc., as shown in Fig. 2.

The three steps which should be taken to minimize the shunt capacity of the system, if it is desired to extend the high frequency response, are:

1. Minimize the length of cable from pickup to preamplifier.
2. Use a low capacity cable, such as Belden #8401 mike cable, between the turntable and the preamplifier.
3. Use a dual triode preamplifier which obtains its equalization by negative feedback from the second plate to the first cathode. This type of a preamplifier has a low input capacity over the upper audio frequency range.

To Keep Abreast of the Times  
Read **RADIO & TELEVISION NEWS**  
Every Month  
The February Issue Will Be On Sale Feb. 1st 1952

### SAVE UP TO 95% SENSATIONAL SURPLUS VALUES!

#### 274-N & ARC-5 EQUIPMENT

**RECEIVERS**  
BC-946B, 550 to 1500 KC  
New \$35.00  
3-6 MC. Used, Originally \$30.  
NOW \$6.95  
6-9-1 MC. Used... \$8.95  
1.5-3 Megas. New \$34.95

**TRANSMITTERS**  
T-22 ARC-5, 7-9 Megas  
Used Xint. \$14.95  
MD7-ARC5 Modulator Plate and Screen for T23ARC5, with Dynamotor. \$15.00  
T-21 ARC-5, 3-7 MC. New, Orig. \$40. Now... \$8.95  
4-5.3 MC. Used, Orig. \$30.00. Now... \$5.95  
2.1-3 MC. 1W. Orig. \$40. Now... \$6.95  
T-19 ARC-5, 3 to 4 Megas... \$12.95  
R-23 ARC-5, 190 to 550 KC, Loop or Straight wire antenna input... \$18.95



#### VHF SETS

- ARC-5, complete with control boxes. Price on Request.
- ARC-4 with tubes less dynamotor. Xint. condition... \$30.00
- SCR-522, complete. Price on request.

Visors I-152, New... \$2.00  
FL-30 AUDIO FILTERS, Newly mtdg. (quantities avail)... \$17.50  
APN-4 ACCESSORIES, Consists of cables assembled to plugs, antenna switch, FT446 and FT447, New... \$15.95

#### EXPORT INQUIRIES INVITED!

We carry an unusually large stock of Airline Equipment, Test Equipment, Radar Sets, etc. Write for our low prices and complete information. Complete shop facilities for testing, repairing and overhauling.

#### IMPORTANT!

Send 30% deposit. All merchandise and prices subject to prior sale or change at any time.

#### WANTED! BC-611 HANDIE-TALKIES, ART-13

Also Any Surplus Electronic Gear, Test Equip., Parts or Assoc. Equip. Prompt Replies—Top Prices Paid!

R9A/APN-4 Revr. with \$9.95  
4x8 MFD Oil Filter Condenser, New \$2.95  
BC-442 Antenna Relay \$2.95  
BC-1206 Revr. 200-400 Kc. HS-33 Head Sets, Used \$2.95  
Used \$5.75  
L.F. Transformer, 112 KC, Part of MN-28, New \$1.95  
BC-434 Control box for BC-433, New \$6.95  
BD-77 12V. input, 1000V output, New \$19.50  
HS-33 Head Sets, Used \$2.95  
CD-307 cord for above \$1.00

#### NEW STANDARD BRAND CHOKES

SWINGING CHOKES		SMOOTHING CHOKES		CASE	WT.	
HY	MILS	OHMS	PRICE	VOLTAGE		
8-40	175	100	2.75	3KV	Closed 3.5	
8-30	200	80	3.25	3KV	Closed 4.5	
5-25	200	100	4.95	2KV	Closed 5	
5-25	300	90	9.95	5KV	Closed 18	
8-25	300	80	5.95	5KV	Open 8 1/2	
5-25	500	60	12.95	7KV	Closed 28	
8-40	1 amp	50	39.95	10KV	Closed 58	
HY	MILS	OHMS	PRICE	VOLTAGE	CASE	WT.
5	500	600	4.95	2KV	Closed	4
7	150	200	1.25	2KV	Open	2
10	500	60	12.95	7KV	Closed	28
12	300	80	5.95	5KV	Closed	9
12	400	400	6.95	2KV	Open	4.5 lbs.
15	200	120	2.95	3KV	Open	4.5 lbs.
20	300	80	5.95	4000	Closed	9 lbs.
20	400	85	6.95	5KV	Closed	14 lbs.
16 Series	175	96	5.95	2.5K	Closed	15
4 Paral.	161	350	24			
26 Series	200	112	6.95	3.5K	Closed	15
6.25 Par.	400	28				

**V&H RADIO & ELECTRONICS SUPPLY**  
DEPT. 29, 2033-37 W. VENICE BLVD.  
LOS ANGELES 6, CALIFORNIA

**Within the Industry**  
(Continued from page 28)

tative organization. His new offices are in the Pure Oil Building in Chicago . . . **MURRAY WEINSTEIN**, well-known consulting engineer in the electronics industry, is now associated with *Regal Electronic Corp.* of New York . . . **T. Y. HENRY** is the new division manager of *Copperweld Steel Company's* new subsidiary, *Flexo Wire Company* of Oswego, N. Y. . . . **AARON LIPPMAN** has been appointed chairman of the 1952 NEDA Convention. He has long been prominent in NEDA activities and is presently serving as chairman of the board . . . *Jewel Radio Corporation* has named **HERMAN N. LUBET** to the dual post of advertising manager and export manager of the firm . . . **MAURICE HARP** has joined the engineering staff of *Lenkurt Electric Co.*, San Francisco . . . **MARTIN L. SCHER** is the new national sales manager for the *Emerson Radio and Phonograph Corporation* line of radio and TV products.

**C. J. LUTEN** has been appointed editor of "Sylvania News" succeeding Robert A. Penfield as editor-in-chief of the service dealer publication. Mr. Penfield has been promoted to the position of advertising and sales promotion supervisor.

Prior to joining the advertising department of the company in July of last year, Mr. Luten served as assistant director of educational advertising to *The Ronald Press Company* of New York. He formerly edited the houseorgan for the *W. T. Grant Company* and prior to that was a reporter for the *Dallas Times-Herald*.

**PROPOSED CHANGES IN AMATEUR REGULATIONS**

AT THE present time there are four separate proposals before the FCC requesting changes in the Amateur regulations. The first three proposals concern the Amateur frequency band from 7000 to 7300 kc.

A proposal by the ARRL requests that the portion of the band from 7250 to 7300 kc. be opened to permit frequency shift keying (type F-1 emission) for radio printer operation. An additional petition by Robert H. Weitbrecht requests that frequency shift keying be permitted on all amateur frequencies below 27 mc.

A petition filed by the National Amateur Radio Council requests that amplitude modulated telephony (type A-3 emission) be permitted in a 100 kc. segment of the 7000-7300 kc. band.

The ARRL has also petitioned to authorize narrow band frequency or phase modulation in the segments from 3800 to 4000 kc., and 14200 to 14300 kc.

**Real values on hard-to-obtain items**

**Give These Items a Careful Look!**  
**TRANSFORMERS-CHOKES:**

5V, 25A. Pri. 115V, 60 cy. AC. A real rugged job excellent for 304TL—4-250A etc. Limited quantity. Only \$4.50 ea.

2.5V, 10A. 10KV insulation. Suitable for 866, 836, etc. Reduced to \$3.39 ea.

10H, 200 ma choke. Hermetically-sealed steel case. Also has hum-bucking tap. A beautiful item only \$1.98.

10H, 50 ma choke. Strap mounting. Handy for dozens of applications. Reg. 98c, reduced to 65c. Charger or fil. trans. Pri. 110V, 60 cycle. Secondary, 9-10-11-12-13 volts @ 1.2 A. Fully cased. A buy at \$1.49.

Fil. transf. Pri. 110V, 60 cy AC. Sec. 24V @ .6A. . . . . only \$1.95 ea.

Power Transf. 350-0-350 @ 70 ma. 5V @ 3A. 6.3 @ 3A. Pri. 110V, 60 cy, AC. Upright mtg. . . . . \$3.25 ea.

Power transf. Pri. 115V, AC, 60 cy. Sec. 520-0-520 @ 200 ma. . . . . \$5.25 ea.

Power transf. Pri. 115V, 60 cy. AC. Sec. 310-0-310 at 50 ma. Cased, upright mount. . . . . only \$1.95 ea.

Output transf. 50L6 to voice coil. . . . . 79c ea.

Choke, 6 henry, 200 ma. Strap mtg. . . . . only \$1.95 ea.

350-0-350 @ 300 ma. 6.3 @ 4A. 6.3 @ 8A. 5V @ 3A. Pri. 115V, 60 cy. AC. . . . . only \$7.95 ea.

450-0-450 @ 200 ma. Pri. 115V, 60 cy. AC. 5V @ 3A, 6.3 @ 5 amp. In shielded case. Only \$8.90 ea.

920-0-920 or 740-0-740 @ 200 ma. Primary 115 or 230V 60 cy. AC. Upright shielded case. Excellent for 807 RP or mod. Only \$10.80 ea.

Scope HV transf. Pri. 115V, 60 cy. AC. Fully cased and insulated. Use with 2X2 rect. Excellent buy at . . . . . \$4.95 ea.

2X2 fil. transf. HV insulation. Fully cased. Also has 4V @ 14A. winding. True O-R value at . . . . . \$1.49 ea.

Double 30 henry choke. 20 ma. Use for low-level speech filter, etc. Fully cased. Hard to beat at . . . . . \$1.49 ea.

836 hi-vacuum rectifiers. 2 for . . . . . \$1.50

**NEW PHONE PATCH**

Now redesigned into more compact and convenient housing, the #6008 phone patch retains all of its excellent characteristics. Provides you with exactly what you need to patch your phone into transmitter or receiver. Features include hi-impedance input suitable for xtl mike and both hi and low impedance inputs to insure proper match to your particular receiver. Unit is complete . . . "Sure-fire" ready to go to work for you. Only . . . . . \$4.95 ea.

**EE89 REPEATERS**

See previous ads. Only a few left. NEW! Regularly \$9.95 ea. . . . . now \$6.95 ea.

**NEW SPECIALS IN VACUUM TUBES**

- |   |                       |
|---|-----------------------|
| 1N15 . . . \$ .89 net                     | 6L6G . . . \$1.95 net |
| 5Z4 . . . . . .74 net                     | 6L6GA . . . 1.95 net  |
| 6E5 . . . . . .99 net                     | 6SN7 . . . 1.32 net   |
| 6H6 . . . . . .99 net                     | 6SH7GT . . . .69 net  |
| 6K7GT . . . .49 net                       | 12K8 . . . .79 net    |
| 6L6 Metal 2.25 net                        | 12SH7 . . . .65 net   |
| 1636 VHF converter. . . . . 1.00 net      | 25L6GT . . . .74 net  |
| WE-316A. Trans. doorknob. . . . .75 net   |                       |
| WE-388A. Large doorknob. . . . . 1.00 net |                       |
| WE-717A . . . . . 1.00 net                |                       |
| HYTRON. HY-615 . . . . . .30 net          |                       |
| 8012 UHF Triode. . . . . 1.50 net         |                       |
| 2C22/7193 . . . . . .39 net               |                       |
| 3CP1 CR Tube. . . . . 2.50 net            |                       |
| 3F7A CR Tube. . . . . 2.50 net            |                       |

**LOOK! NO HANDS!**

This mike leaves both hands free for mobile QSO's. Fastens to operator by simple snap strap. Adjustable. Double action sw. operates push-to-talk or holds on. BRAND NEW only \$2.00 ea. POSTPAID in U.S.A. and CANADA.



**LOW FREQUENCY CRYSTALS**

FT-241A (Brown) Holders. Channel spacing, 1.388 kcs. All frequencies in kilocycles. . . . . 89c ea.	375	402.777	430.555	458.333	486.111	513.888
	376.388	404.166	431.944	459.722	487.500	515.277
	377.777	405.555	433.333	461.111	488.888	516.666
	379.166	406.944	434.722	462.490	490.277	518.055
	380.555	408.333	436.111	463.877	491.666	519.444
	381.944	409.722	437.5	465.277	493.055	520.833
	383.333	411.111	438.888	466.666	494.444	522.222
	384.722	412.5	440.277	468.055	495.833	523.611
	386.111	413.888	441.666	469.444	497.222	525.000
	387.5	415.277	443.055	470.833	498.611	526.388
	388.888	416.666	444.444	472.222	500.000	527.777
	390.277	418.055	445.833	473.611	501.388	529.166
	391.666	419.444	447.222	475.000	502.777	530.555
	393.055	420.833	448.611	476.388	504.166	531.944
	394.444	422.222	450.000	477.777	505.555	533.333
	395.833	423.611	451.388	479.166	506.944	534.722
	397.222	425.000	452.777	480.555	508.333	536.111
	398.611	426.388	454.166	481.944	509.722	537.5
	400.000	427.777	455.555	483.333	511.111	538.888
	401.388	429.166	456.944	484.722	512.5	540.277

**Power Supply for Any 274-N Receiver**

Just plug it into the rear of your 274-N RECEIVER . . . any model. Complete kit and black metal case, with ALL parts and diagrams. Simple and easy to build in a jiffy. Delivers 24 volts plus B voltage. No wiring changes to be made. Designed especially for the 274-N receiver. All necessary parts for conversion of rest of receiver also included. ONLY \$8.95.



**ANTENNA LOADING COILS**

Part of SCR-284. Form 2 1/4" diam., 4 1/4" long, 32 turns #14 silver plated wire. Form is Pyrex glass, threaded. Excellent as replacement in SCR-284 or for mobile loading. A buy at . . . . . \$9 ea.

**NEW RELAY ITEMS**

Miniature, SP-ST, 6500 ohm coil. (2 ma) Excellent for voice control or models. Only \$1.50 ea. 12V, D.C. 3 pole, ST. Miniature. 1A contacts . . . . .75 ea. 24V, D.C. DP-DT heavy contacts. . . . .75 ea.

**SPEAKERS**

10" PM. Alnico 5 magnet. Only. . . . . \$5.95 ea. 15" with 12,500 ohm field. Use across 300V or higher amplifier power supply. Has one piece molded cone. Made by very well known manufacturer . . . . . \$14.95 ea.

50 watt sockets. Ceramic, transmitting type. Well known make . . . . .74 ea.

**NOVICE XMTR KIT**

Two tube, xtl cont. xmtr. Covers all bands between 20 and 160. Pi-coupler output for operation with any length antenna. 35 Watts input. Uses 6V6 and 6L6.

Kit (less coils, tubes, xtals) . . . . . only \$9.90  
Companion, matching power supply kit (less tube) . . . . . \$9.90  
Wound coil (specify band) . . . . . \$1.05 ea.  
Tube kit for osc. amp. and rect. . . . . \$3.95 set  
(3 tubes) . . . . . \$2.75 ea.  
Crystals (specify frequency) . . . . . \$2.75 ea.

TU-10B Tuning units. This is the hi-freq. tuning unit with the excellent variable condensers as well as loads of micas, coils, worm drive, etc. Only . . . . . \$1.75 ea.

Permeability tuner for BC band. Complete with osc. coil and tuner assembly. Diagram for making 5 or 6 tube set using this tuner. Only . . . . . \$1.25 ea.

**U-V LIGHT SOURCE**

8 watt ultra-violet light source. In kit form including Sylvania black-light tube, (for U-V light in the 3660 Angstrom unit region) ballast, starter, mounting panel, reflector, line cord/plug, hardware, instructions. An invaluable device for schools, labs, service shops, home workshop, etc. Here is a genuine value. Complete kit, (less outer housing) . . . . . \$4.95

**274N/ARC-5 ACCESSORIES**

Mounting rack, holds three receivers. Easily modified for single receiver—NEW. . . . . only \$1.95 ea.  
274N/ARC-5 Spline tuning knobs. . . . . .59 ea.  
Same as above except with deluxe tuning crank . . . . . .89 ea.  
Tuning crank. Fits RU 16-17, BC 433 etc. for manual tuning . . . . . .89 ea.

**CONDENSER TESTER**

One of our best sellers! Useful, versatile laboratory item, in kit form. Simple, and easy to build in less than an hour. Checks condenser leakage and continuity up to 8 megs. Will test any paper, electrolytic, mica or oil capacitor from 50 mf. to 50 mfd. Self-contained power supply and neon bulb indicator with socket and bezel. Drilled metal cabinet. Complete instructions and diagrams included with each kit. Only \$5.00.




**NOTE NEW ADDRESS!**

Minimum order \$2.00. All items subject to prior sale. All prices subject to change without notice. 20% deposit must accompany all orders, balance C.O.D.

**OFFENBACH & REIMUS CO.**

1564 MARKET ST., SAN FRANCISCO, CALIF.

# Become an Electrical Engineer

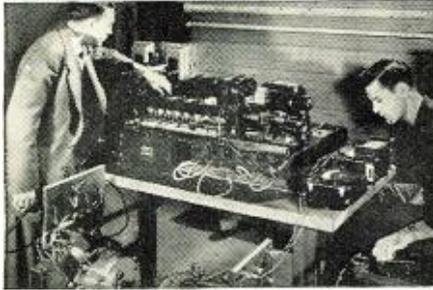

## MAJOR IN ELECTRONICS



- B. S. Degree in 36 Months
- Radio-Television Technician Certificate in 18 Months

Experts predict that by 1954 there will be at least two positions for every engineering and technician graduate. This College offers a tested plan that permits you to enter these vast employment opportunities at an early date. First — you save a valuable year through optional year-round study. Second — you can receive advanced credit for prior training gained in the armed forces, other schools or field experience.

### Enter Both Radio and Television Through This Plan

12 months or one-third of the B. S. degree course (Electronics major) — also brings you the Radio Technician's certificate. An added 6-month course qualifies you for the Radio-TV Technician's Certificate.

### The Proven "UNIT CHASSIS SYSTEM"



of teaching was developed here. It "breaks down" the TV set by stages. You learn every component of all types and makes — and are prepared for future design changes, including the advent of color.

### SPECIAL! Television Clinics

Ambitious Radio and TV Servicemen can enroll now in special one-month spring or summer clinics — to handle latest field service problems. Write for full details.

Over 48,000 former students from all states and 23 overseas countries. Faculty of trained specialists. Modern laboratories and equipment. Nonprofit technical institute and college 49th year.

## MILWAUKEE

SCHOOL OF ENGINEERING  
Founded 1903—Milwaukee, Wis.

Terms open April, July, October, January

FREE — Write for "Occupational Guidance Bulletin," "Your Career" booklet, and Catalog.

Milwaukee School of Engineering  
Dept. RN 152, 1025 N. Milwaukee  
Milwaukee, Wisconsin

Without obligation send Catalog for Electrical Engineering, B. S. Degree, major in  Electronics;  Power;  "Your Career"; Occupational Guidance Bulletin on:  Radio-TV;  Electrical Power;  Welding;  Heating, Refrigeration Air Conditioning;  TV Service Clinic.

Name.....Age.....  
Address.....  
City.....Zone.....State.....  
If veteran, indicate date of discharge.....

## V.T. Keyed Transmitter

(Continued from page 41)

on 160 meters, the 6AC7 stage on 80, the 6AQ5 stage on 40, and the final on 40 or 20 meters, the key should be closed. The positive test lead of a high resistance voltmeter should be grounded to the chassis, and a 2.5 mhy. r.f. choke should be placed in the negative lead to read grid drive to the 6AQ5 and to the 807's. Approximately 40 volts of grid drive should be present on the grid of the 6AQ5 and 60 should be measured on the grids of the 807's. Of course, these figures will vary with different loading and bands but they should not vary greatly. With plate voltage applied to the final, from 55 to 60 volts of drive to the 807's should be obtained with careful adjustment of the preceding stages.

The 47 ohm resistors in the grids of each of the 807's are to prevent parasitics. Also, the chokes, RFC, and RFC, are 47 ohm resistors wound with 7 and 9 turns respectively of #20 s.c.c. enamel.

After preliminary tuning adjustments have been made, say for forty meter output, the oscillator should be heard only faintly with the key up, if it is on 160 meters. Switching the receiver to 80 will increase the volume of the oscillator in the receiver, but still not enough to be bothersome when listening on the transmitting frequency. On 20 and 10, it will not be heard at all. If the oscillator is operating on 80 meters instead of 160, a slight increase in volume will be noticed on 40 and 20, but no signal should be heard on 10 with the key up.

Checks on keying should be made on the 20 and 10 meter bands to determine the keying characteristics. Needless to say, they will be practically perfect on any band with this system. The keying current, measured at the key, should be very close to one tenth of one milliampere. There should be no noticeable chirps whatsoever on 10 meters.

A "fone-c.w." switch is used, as shown in Fig. 2, with W6CXM's modulator as described in the September 1950 issue of RADIO & TELEVISION NEWS. The reader is advised to investigate this compact, useful method of modulation before building a modulator of any kind. The "fone-c.w." switch grounds the speech tube filaments, placing the modulator in operation, connects the 6SQ7 audio output to pin 5 of the 6Y6, and removes the ground from pin 8 of the 6Y6, when it is thrown to the "fone" position. In the c.w. position, it reverses this procedure, connecting the 6Y6 grid to the grids of the 807's through the 2.5 mhy. r.f. choke. For phone operation, the 25,000 ohm, 25 watt screen resistor will have to be adjusted for correct screen voltage.

### REFERENCES

Goodman, Byron: "Improved Break-In Keying," QST, March 1948.

# SURPLUS

## COAXIAL CONNECTORS

83-1AC	\$.42	83-1R	\$.40	83-22AP	\$1.40
83-1AP	1.30	83-1RTY	.50	83-22R	1.68
83-1F	.10	83-1SP	.50	83-22SP	1.15
83-1H	.10	83-1SPN	.50	83-18	1.15
83-1	.80	83-1T	1.30	83-18	1.15

## FULL LINE OF JAN APPROVED COAXIAL CONNECTORS IN STOCK

UHF	B	BNC		
UG-7	UG-27	UG-87	UG-166	UG-245
UG-12	UG-27A	UG-88	UG-167	UG-254
UG-18	UG-29	UG-89	UG-171	UG-255
UG-19	UG-30	UG-98	UG-175	UG-260
UG-21	UG-34	UG-102	UG-176	UG-274
UG-21B	UG-36	UG-103	UG-185	UG-278
UG-22B	UG-37	UG-104	MX-195	UG-276
UG-23	UG-57	UG-106	UG-197	UG-290
UG-24	UG-58	UG-108	UG-200	UG-291
UG-25	UG-86	UG-149	UG-206	UG-306
		UG-156	UG-236	MX-367
M-358	MC-277	PL-259A	PL-325	
M-359	MC-320	PL-274	SO-230	
M-360	PL-258	PL-284	SO-264	
	PL-259	PL-293	TM-201	
93-C	49120	D-163950	ES-685696-5	
93-M	49121A	D-166132	ES-689172-1	

## SOUND POWERED TELEPHONES

U. S. NAVY TYPE M HEAD AND CHEST SETS  
U.S.I. A-260 W.E. D-173013  
A.E. GL832BA0

ANY TYPE—\$14.88 EACH  
TS-10 Type Handsets.....\$8.92 ea.  
RCA SOUND POWERED UNITS—Use as microphone or receiver.....Pair \$4.95

### F. W. BRIDGE SELENIUM RECTIFIERS

AC Volts Input.....18	AC Volts Input.....40
DC Volts Out.....14.5	DC Volts Out.....34
2.3 Amps.....\$ 3.85	0.6 Amps.....\$ 4.60
6.6 Amps.....\$ 4.95	1.2 Amps.....\$ 5.95
13.0.....\$ 7.75	3.0.....\$ 8.95
17.0.....\$ 9.75	6.0.....\$ 15.50
26.....\$ 15.75	9.0.....\$ 17.50
39.....\$ 22.75	12.....\$ 26.95
52.....\$ 35.50	15.....\$ 32.50
70.....\$ 48.50	25.....\$ 42.50
	36.....\$ 55.50

## GENERATORS

• Eclipse-Pioneer type 716-3A (Navy Model NEA-3A) Output—AC 115V 10.4A 800 to 1400 cy. 1g; DC 30 Volts 60 Amps. Brand New.....\$38.50  
• Eclipse-Pioneer type 1235-1A. Output—30 Volts DC 15 Amps. Brand New—Original Packing \$15.50

## CATHODE RAY TUBES

2AP1	\$ 9.75	SAP1	\$ 3.75	78P1	\$ 8.75
2AP5	9.75	SAP4	4.75	78P7	7.95
3AP1	10.25	SBP1	5.75	78P14	14.95
3AP4	10.25	SBP4	5.75	9GP7	12.85
3BP1	7.95	SCP1	4.95	9LP7	9.95
3CP1	2.25	SCP7	5.50	10P4	24.50
3DP1	4.85	FP7	7.75	10P4A	18.50
3DP1A	6.25	SP4	5.75	12DP7	16.50
3EP1	4.95	SP1	26.50	12GP7	16.50
3FP7	2.95	SP2	26.50	12P7	16.50
3GP1	4.95	SP4	26.50	902P1	9.95
3HP7	4.91	SLP1	19.75	905	4.45
4AP10	4.75	SWP1	10.65		

## METERS

3 MA DC 2 1/2" R—Simpson black scale.....\$3.35
500 Microamps, DC—2 1/2" round—Sun.....4.30
1 ma. DC Fan type "A" scale (from equip.).....3.95
500 ma. DC 2 1/2" R—General Electric.....2.95
2 amp. RF 2 1/2" Sq.—Simpson.....4.11
5 amp. DC 4 1/2" R—JST.....3.15
30 DC 2 1/2" R—General Electric.....3.95
3 amp. RF 3 1/2" R—Weston.....6.00

## OIL FILLED CONDENSERS

MFD	VDC	PRICE	MFD	VDC	PRICE
2	400	\$0.55	.25	2000	\$1.50
5-5	400	1.65	.1	2000	1.30
2	600	.69	1	2000	1.95
5	600 R'd	.69	1.1	2000	2.85
2	600 R'd	1.65	.5	3000	15.80
4	600 R'd	1.65	.03	4000	2.40
6	600	1.75	.03	4000	2.95
5	600	1.85	.32	4000	2.95
8-8	600	1.95	.1	5000	1.60
4-4	600	2.50	.1	5000	2.50
4x3	600	2.50	.01-.03	6000	4.88
1	1000	.65	.1	7000 R'd	1.79
2	1000	.95	.1	7500	2.85
2	1000 R'd	.95	.1	7500	12.50
3.5-.5	1000	1.85	.1	12KV	8.95
4	1000	1.95	.05	16KV	4.70
8	1000	2.00	.05	16KV	4.95
8	1000	3.25	.075	18KV	8.95
1	1200	1.85	.25	18KV	19.95
1-1	1500	1.25	10	330VAC	3.95
1.5	1500	1.25	5	440VAC	3.10
4	1500	1.25	8	500VAC	3.25
1-.5	2000	.95	7	660VAC	4.50

## HIGH VOLTAGE TRANSFORMERS

G.E.—Pri. 115V 60 cy  
Sec. 6250V 80 MA—12.5 KV Ins.....\$18.50  
G.E.—Pri. 115V 60 cy. Sec. 6250/3850/2600V 56 MA  
(2.5 KV Ins.....\$18.50  
Raytheon—Pri. 115V 60 cy. Sec. 8500/6450V CT 43  
Ma Hermetically sealed.....\$22.50

## CRYSTAL DIODES

1N21	\$1.19	1N23	\$1.49	1N34	\$0.79
1N21A	1.69	1N23A	3.25	1N34A	.95
1N21B	4.00	1N23B	5.25	1N45	1.94
1N22	1.09	1N27	1.79	1N52	1.05

## SYNCHROS

Size 1, 3, 5, 6, 7 and 8 generators, motors, control transformers, differential generators, and differential motors in stock.

AY-120D	5G	N	C-69405-1
AY-130D	5N	X	C-77610
	6DG	2J1F1	C-78248
	6G	2J1G1	C-78249
SB	7DC	2J1H1	C-78411
SD	7C	C-44968-6	C-79331
SCT	A	C-5679-1	C-78254
SDG	B	C-5676-1	C-78670
SF	M	C-69405-2	C-78863

## ELECTRONIC RESEARCH LABS.

715-R Arch St., Philadelphia 6, Pa.  
Phones—Market 7-6771-2-3

All prices F.O.B. Phila.  
Terms—Net 10 Days to well rated accounts or cash with order. Minimum order—\$3.00.

## Winding Machines

(Continued from page 45)

*Kovar*, a special alloy selected for the job because it has the same coefficient of expansion as has glass. The big problem in assembling the tubular container was, initially, to solder the *Kovar* rings to the open ends of the case. Conventional soldering was slow and costly and caused occasional mechanical damage. Finally, high-frequency soldering equipment was developed that does the job neatly and quickly. The assembled end of the condenser, with a ring of very thin rosin core solder resting on the *Kovar* ring, is simply placed in an open U-shaped induction loop of water-cooled copper coil. Fed by a three-kilowatt r.f. power oscillator working on about three megacycles, this one-inch loop induces a heavy current in the solder and the end of the metal case and, as if by magic, the solder melts and seals the *Kovar* ring to the case.

The pigtail leads pass through tiny *Kovar* bushings in the center of the glass discs. These bushings, as yet unsealed, act as breather holes and permit the condenser unit to be vacuum processed, that is, all air and moisture are withdrawn and any free space inside the container is filled with impregnating compound. The wires are then sealed to the bushing with specks of solder applied with a midget iron, and the condenser is finished except for marking, exhaustive test procedures, and final inspection and packaging prior to shipment.

-30-


Television scientist Dr. Allen B. Du Mont (left) receives a citation from Mayor Morris Pashman of Passaic, New Jersey for "continuous pioneering, development and inspired leadership in the art of television and electronics." Dr. Du Mont received the award on November 14 at special ceremonies marking adoption by the city of the official slogan, "Passaic, Birthplace of Television." The scroll was signed by New Jersey's Governor Alfred E. Driscoll, Thomas E. Prescott, president of the Passaic Chamber of Commerce and Mayor Pashman.



January, 1952

# Put across that PERSONALITY

WITH AN **E-V** MIKE

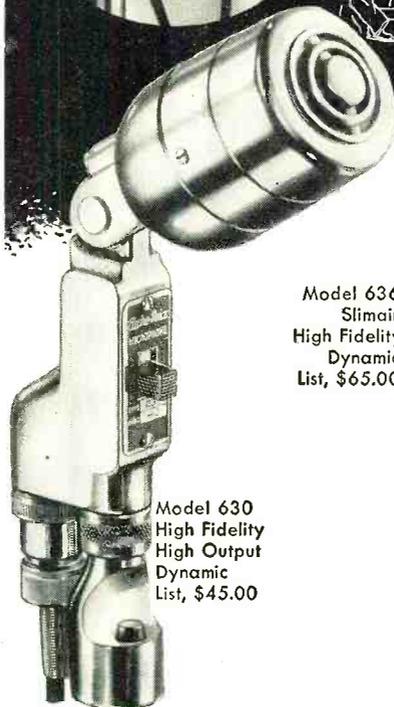

Model 630  
High Fidelity  
High Output  
Dynamic  
List, \$45.00



Model 636  
Slimair  
High Fidelity  
Dynamic  
List, \$65.00



Model 950  
CARDAX  
Crystal  
Cardioid  
with Dual  
Response  
List, \$42.50



Authorized  
Distributors  
Everywhere

### REPRODUCE VOICE AND MUSIC... ACCURATELY!

The microphone makes a difference in the sound you hear! As a radio ham, sound specialist, or home recording fan, you are certain to reproduce the individual quality and personality of speech or song or orchestral music... with a *research-engineered* E-V mike! Send today for illustrated bulletin.


NO FINER CHOICE THAN

## Electro-Voice


410 CARROLL STREET • BUCHANAN, MICHIGAN  
Export: 13 East 40th St., New York 16, N.Y., U.S.A. Cables: Arlab  
MICROPHONES • HI-FI SPEAKERS • TV BOOSTERS • PHONO CARTRIDGES



CARDYNE  
CARDIOID  
DYNAMIC

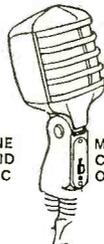

MERCURY  
CRYSTAL  
OR DYNAMIC

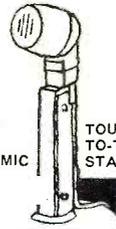

TOUCH-  
TO-TALK  
STAND



MOBIL-MIKE  
CARBON OR  
DYNAMIC



SPHEREX  
CRYSTAL



CENTURY CRYSTAL  
OR DYNAMIC

E-V Pat. Pend.

Crystal microphones licensed under Brush Patents

# USE PHOTOFAC

the world's best Radio-TV service data—it pays for itself every working day



Try **PHOTOFAC!**

**FREE** We'll send you any Photofact Folder listed in the Photofact Cumulative Index\*

**WE'LL PROVE YOU'LL SAVE TIME and EARN MORE WITH PHOTOFAC**

NOW—learn for yourself—at our expense—how PHOTOFAC makes your Radio and TV work quicker, easier, more profitable! Examine an actual PHOTOFAC Folder. Use it. You'll learn first-hand why over 35,000 successful service technicians use PHOTOFAC daily. You'll learn that no other service gives you PHOTOFAC's completeness, accuracy, uniformity, and lowest cost. PHOTOFAC is the only radio and TV service data prepared from laboratory analysis of the actual equipment. Know the facts—get your FREE Folder now. Examine, use, compare—learn why no modern service shop can afford to be without PHOTOFAC!

\*Except those followed by asterisk (\*) or letter A.

**WRITE FOR FREE INDEX**

**PAY AS YOU EARN!** Ask your distributor about this amazing plan. Only \$18.39 puts the entire profit-boosting Photofact library in your shop now!

**NOTE:** Our FREE Folder offer is limited to Service Technicians only. Attach coupon below to your letterhead and mention your jobber's name. If you have no letterhead, send coupon to your jobber. Experimenters and others may obtain the Photofact Folder by remitting amount shown below.

HOWARD W. SAMS & CO., INC.  
2201 E. 46th St., Indianapolis 5, Ind.

- Send FREE Photofact Cumulative Index
- Send Full Easy-Pay Details

I am a Service Technician:

- Send FREE Folder for set model.....

I am an Experimenter: Enclosed \$.....

- Send Folder for set model.....
- TV-\$1.00. Record Changer or Comm. Receiver-75c. AM/FM-50c

Name.....

Address.....

City.....Zone.....State.....

## What's New in Radio

(Continued from page 91)

crystal breakage from rough handling and when changing the needle.

The new unit is furnished with the tiny condenser harness in position on the terminals. Installed in that manner, output is low. Slipping off the condenser raises the output.

The range of the new cartridge is to 5000 cycles. Minimum needle pressure is one ounce and the weight of the cartridge is 19 grams. The housing is of stamped steel.

### HIGH VOLTAGE TUBULARS

Aerovox Corporation of New Bedford, Massachusetts currently has available a new line of universal high voltage tubular ceramic condensers which have been especially designed for service and experimental work.

The Type SI-TV units are of the "Hi-Q" brand and are available in eleven capacitance values from 4.7 to 47  $\mu$ fd. but at a single 6000 volt rating.

These units come packed five to a carton and are currently available from the company's jobbers.

### BEAM POWER AMPLIFIERS

Precision Electronics, Inc., 641-643 Milwaukee Avenue, Chicago 22, Illinois, has published a new brochure describing its line of beam power amplifiers designed and engineered to provide high performance and simple operation with a minimum of maintenance.

Six units are included in the line, a ten watt amplifier (Model G-10); a fifteen watt unit (Model G-15); the Model G-30, a thirty watt amplifier; the G-45, a forty-five watt model; a seventy-five watt unit (Model G-75); and the Model G-30MP, a thirty watt mobile unit.

All of these units are housed in durable cabinets which are suitable for installation in stores, offices, factories, clubs, ballrooms, auditoriums, or outdoor arenas. Catalogue No. 5551, available from the company, carries complete specifications on these amplifiers.

### SHORT-WAVE RECEIVER

The Hallicrafters Company, 4401 W. Fifth Avenue, Chicago 24, Illinois has recently introduced a precision built short-wave home radio set which will retail in the moderate price class.

Tradenamed the "Continental," the set with its short-wave band marked with the names of the most popular foreign stations is housed in a plastic case which comes in five decorators' colors (smoky black, air force blue, dove grey, sandalwood, and forest).

### PLUG BASE

Industrial Devices, Inc., Edgewater, New Jersey is in production on a new plug base that is said to offer many advantages to the manufacturer employing it in assemblies.

The new unit is manufactured for

condensers of the Type CE50 series, fitting a standard medium octal socket. It is suitable for use in condensers made under JAN-C-62 specifications and carries the manufacturer's designation of Model #1800.


The use of nylon gives the unit a toughness which reduces breakage to a minimum while being assembled to metal cans or other related parts. Due to the high strength of this material it has been possible to hollow the unit to a great extent thus making it lighter and creating a savings in material.

### TAPE MECHANISM

Tape Master, Inc., of 13 W. Hubbard Street, Chicago 10, Illinois, has announced the availability of a new tape transport mechanism, the Model TH21, and a matching preamp-bias erase oscillator.

The mechanism operates at a tape speed of 7½ inches-per-second and incorporates both fast forward and fast rewind, single switch control, an oversized motor, and practically vibrationless operation.

The companion preamp unit, Model

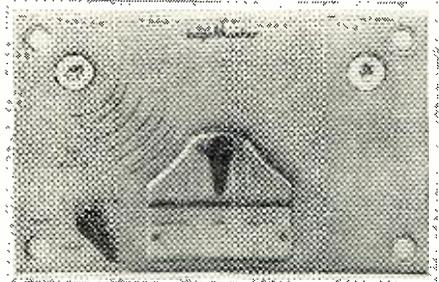

PA-1, is fully wired and incorporates a push-pull bias-erase oscillator-full monitoring, inputs for both radio-phonograph and microphone, outlets for amplifier and headphones, complete master switching, and a neon recording level indicator.

A data sheet giving full details on both of these units is available on request.

### NEW SOLDER

Kester Solder Company, 4201 Wrightwood Avenue, Chicago 39, Illinois is currently in production on a new and highly active resin flux, known as "44" resin.

According to the company, the new product melts, wets the metal, and flows or spreads all in one instantaneous action with such speed that it is impossible to distinguish the separate actions.

The "44" resin is non-corrosive and electrically non-conductive. It conforms with Army-Navy-Air Force specification MIL-S-6872 (AN-S-63) and the U. S. Air Force specification No. 41065-B-Method 31, in addition to Federal specification QQ-S-571b.

Bulletin No. 444 giving complete information on this new product is available on request.

### OUTPUT TRANSFORMERS

Acro Products Co., 369 Shurs Lane, Roxborough, Philadelphia 29, Pa., has recently introduced a new line of out-

# LEARN Practical RADIO AT HOME



COMPLETE ONLY . . .

# \$19<sup>95</sup>

## BUILD 15 RADIOS

ABSOLUTELY NO PREVIOUS TRAINING NEEDED  
EXCELLENT BACKGROUND FOR TELEVISION

### 10-DAY MONEY-BACK GUARANTEE

#### WHAT THE 1952 PROGRESSIVE RADIO "EDU-KIT" OFFERS YOU:

This is a practical home radio course. You learn theory, construction, operation, trouble shooting, code. You build receivers, transmitters, amplifiers, code oscillator, signal tracer.

You start with a simple radio circuit, and gradually advance to more complex circuits. No previous background is required. No instructor is needed. All parts and instructions are included and every single step is clearly explained.

All parts are guaranteed, individually packaged, identified, and explained.

There is nothing extra to buy. You receive all parts, tools and instructions at once. You keep everything, there is absolutely nothing you return to us.

You can easily pay for the kit in a short time by repairing radios. Use the tester and signal tracer for servicing. The signal tracer alone is worth more than the price of the entire kit.

#### USED BY RADIO SCHOOLS AND GOVERNMENT AGENCIES!

Progressive Radio "Edu-Kit" includes tubes, power condensers, mica condensers, electrolytic condensers, variable condensers, selenium rectifiers, chassis, hardware, tie strips, tube sockets, solder, wire, soldering iron, tubing, coils, instruction book, radio trouble-shooting guide, radio tester, television trouble-shooting manual, etc.; in brief, everything you need in a practical radio course.

Order your "Edu-Kit" today, or send for further information.

Postage prepaid on Cash orders—C.O.D. orders accepted in U.S.A.

**PROGRESSIVE ELECTRONICS CO.**  
497 UNION AVE. DEPT. RN-1 BROOKLYN, NEW YORK

## FREE RADIO TESTER & SOLDERING IRON

GET A WELL-PAYING JOB



GO INTO A PROFITABLE BUSINESS AND PLAN FOR A FUTURE




## SENSATIONAL VALUE!

#630 SUPER 30 TUBE CHASSIS  
Mfr. Licensed under R. C. A. Patents

Complete with 20" first quality tube

AND Beautiful hand-rubbed Mahogany Console Cabinet.

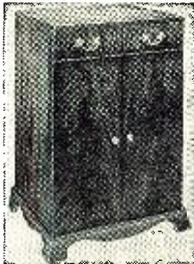COMPLETE PRICE **\$259.95** slightly higher with full doors



the latest 1952 model with all the newest electronic improvements . . .

- peak sensitivity for fringe areas
- synchrolock tuning
- keyed A G C
- 15,000 volts under load
- 12-inch RCA speaker
- can be adapted to color & UHF
- high quality parts

A set—NOT A KIT

Completely wired, Factory Engineered, aligned and tested. RMA Guaranteed

### 1 YEAR GUARANTEE ON TUBE

A half-hour to mount; ready for operation. Saves up to \$150.

Compare this anywhere for high quality—low price!

Write Dept. F for further information. Phone and mail orders filled on receipt of money order for 25% as deposit . . . the balance C.O.D., f.o.b. N. Y.

**NEW ENGLAND TELEVISION CORP.**  
75 CHURCH STREET NEW YORK, N. Y.

## FOR THE "GOLDEN EAR" CROWD

### THE STRAIN-SENSITIVE PHONOGRAPH PICKUP

Here's why this truly faithful reproducer appeals to people gifted with the "Golden Ear" . . . why the STRAIN-SENSITIVE PICKUP developed by the PFANSTIEHL CHEMICAL COMPANY brings out the brilliance of great voices and orchestras . . . the latent music on your records that other pickups leave untouched.

- The STRAIN-SENSITIVE PICKUP is an amplitude transducer with a CONSTANT RESISTANCE of about 250,000 ohms.
- Signal output is at a practically CONSTANT IMPEDANCE LEVEL.
- Excellent Transient Response.
- NO DISTORTION, phase shift or evidence of intermodulation is audible.
- LINEAR RESPONSE, free from peaks or resonances.

Cartridges are available for both standard and micro-groove, and can be had with Famous PFANSTIEHL M47B Precious Metal Alloy or diamond tipped styli.

A special preamplifier is necessary to provide the correct D.C. voltage for the pickup element and to provide the first stages of signal gain. Four styles are ready, or, if you prefer, you can build your own from the circuit in the literature.

Ask your radio supply man, or write today for complete FREE INFORMATION.

**PFANSTIEHL**  
CHEMICAL COMPANY

101 Lake View Avenue, Waukegan, Illinois

LEARN

# Television-Radio Electricity

## REFRIGERATION-ELECTRONICS

IN THE GREAT SHOPS OF **COYNE**

**TRAIN QUICKLY! OLDEST, BEST EQUIPPED SCHOOL** of ITS KIND in U.S.  
*Young and Older Men . . .*

Come to the Great Shops of Coyne in Chicago. Get practical training in TELEVISION-RADIO or ELECTRICITY—vital in Defense Program. Prepare now for a better job or better service rating.

### START NOW—PAY LATER

You can finance most of your tuition, pay for it later in easy monthly payments. Special plan for men of Draft Age. Part time employment service available.

**FREE BOOK** Clip coupon for Big Free Illustrated Book. Indicate below, course that interests you. No salesman will call. ACT NOW.

**COYNE** [SCHOOL] B. W. Cooke, President  
A TECHNICAL TRADE INSTITUTE CHARTERED NOT FOR PROFIT Established 1899 500 S. Paulina, Chicago

ELECTRICITY ★ TELEVISION  
RADIO ★ REFRIGERATION ★ ELECTRONICS

B. W. COOKE, Pres.  
COYNE School  
500 S. Paulina St., Chicago 12, Ill. Dept. 12-85-H

Send FREE BOOK and full details on:  
 TELEVISION-RADIO  ELECTRICITY

NAME.....

ADDRESS.....

CITY..... STATE.....

# HIGH VOLTAGE POWER SUPPLIES

## MODEL PN-30

REVERSIBLE POLARITY Continuously VARIABLE 1-30 KV DC POWER SUPPLY  
A light, compact unit in wide use for insulation testing, precipitators and laboratory research. Polarity reversible from front panel. Current output—2 milliamperes at 20 KV; 250 microamperes at 30 KV. Input—110 V AC 60 cycles. Dimensions 14" x 11" x 12".

## MODEL RG-30

CONTINUOUSLY VARIABLE 15-30 KV REGULATED DC POWER SUPPLY  
A high grade supply which incorporates a voltage tap in the range of 4 to 6 KV for use with SWP4, STP4 and flying spot tubes. Regulations better than .5% at 1 milliamperes. In wide use for theatre and transcription recording systems.  
Dimensions of HV unit—14" x 11" x 12". Separate low voltage DC Supply—14" x 6" x 8".

## MODEL 2040

VARIABLE 20-40 KV RF TYPE DC POWER SUPPLY  
Ideal for TV. Electrostatic paint spraying, insulation testing, etc. Current output—1 milliamperes. Input—110 Volts AC 60 cycles. Dimensions 14" x 11" x 12"—Completely encased.

## MODEL PN-60

REVERSIBLE POLARITY Continuously variable from 20 to 60 KV. Current output—1 milliamperes. Ideal laboratory type unit for insulation testing, precipitation tests, etc. Polarity reversible from front panel. Dimensions: 19 1/2" high x 21" wide x 15" deep.

## MODEL 4575


4 1/2 KV POWER SUPPLY  
Complete Voltage Range—from 1 KV to 7 1/2 KV. Current output—1 milliamperes  
Input—250 Volts DC—50 milliamperes  
Dimensions—5 3/8" x 4 1/2" x 5"

## MODEL LAB-30

CONTINUOUSLY VARIABLE 1 to 30 KV REGULATED DC POWER SUPPLY  
Compact, well built supply with regulations 1/2% at 1 milliamperes. Dimensions: 14" x 21" x 12".

SEND FOR DESCRIPTIVE LITERATURE

## HIGH VOLTAGE RF STEP-UP COILS

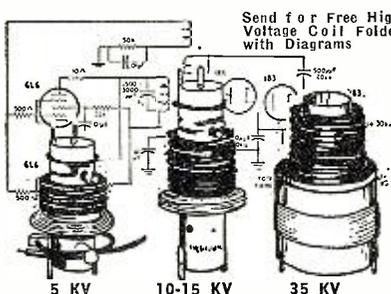

5 KV  
DIMENSIONS:  
Secondary Height . . . 3 1/2"  
Secondary Windings . . . 13 1/4"  
Windings consisting of 4 Pie  
Primary Diameter . . . 2 1/4"  
Secondary Voltage Out-put . . . . . 5 KV  
Secondary Current . . . . . 2 Milliamperes  
Approx. Frequency 175 Kc  
\$3.70 each

10-15 KV  
DIMENSIONS:  
Secondary Height . . . 5 1/4"  
Secondary Windings . . . 13 1/4"  
Windings consisting of 7 Pie  
Diameter . . . . . 2 1/2"  
Secondary Voltage Out-put . . . . . 10-15 KV  
Secondary Current . . . . . 2 Milliamperes  
Approx. Frequency 175 Kc  
\$9.30 each

35 KV  
Dimensions:  
Secondary Height . . . 7"  
Secondary Windings . . . 13 1/4"  
Windings consisting of 10 Pie  
Primary (separate from secondary)  
Height . . . . . 4"  
Diameter . . . . . 4 1/4"  
Secondary Voltage Out-put . . . . . 35 Kilovolts  
Secondary Current . . . . . 5 Milliamperes  
Approx. Frequency 70 Kc  
\$42.00 each  
25 KV—Same as 35 KV  
cept Secondary Ht. . . 6"  
\$36.00 each

STILL AVAILABLE FOR PROJECTION TV  
• High Efficiency SCHMIDT OPTICAL BARRELS for projecting up to 8 x 10 ft. theatre size pictures.  
• Model 2040 Power Supply specially designed for Projection TV

put transformers which have been especially designed for use in "Ultra Linear" amplifier circuits.

These new transformers, in the newly developed circuit arrangement, permit lower distortion and wider bandpass than hitherto available in audio power amplifiers.

These "Acrosound" units provide full rated power throughout the audio spectrum and have frequency response ± 1 db from 10 to 100,000 cps. They have a ratio of shunt inductance to leakage reactance in excess of 15,000 to 1 and feature precision winding of better than .5% accuracy.

Information on "Ultra Linear" circuitry and the new line of transformers to be used in "Ultra Linear" amplifiers is available from the company on request.

-30-

## Spot Radio News (Continued from page 18)

keted along with black and white sets, using standard types of components whose metallic content would be nominal and not enough to interfere seriously with any material-allocation schedules.

## COLOR'S FOREMOST ADVOCATE.

FCC headman Wayne Coy, viewing the stop-production order as a sort of victory for industry, declared in an address before the National Association of Educational Broadcasters in Biloxi, Mississippi, that ". . . Mr. Wilson did not need to address his letters to other manufacturers inasmuch as they, by a common pattern of ridicule and a lack of selling efforts and promotion of color in television, had decided that the American public should not have the opportunity to enjoy color television except on a basis and at a time to be determined by the industry.

"Notwithstanding the stoppage," he said, "it was felt that . . . color cannot longer be kept underground as it has been for many years by the recalcitrance of those who put their private interests ahead of public interest."

THE RADIATION LAW, recently passed, which provides for the control of transmissions to eliminate any possibility of the use of signals for alien aircraft homing, will operate under the guidance of an advisory group of broadcasters who will cooperate with the FCC, designated by the new law as the enforcing agency.

In the new legislation, which became a part of the Communications Act as an amendment, the President will have the authority, in the event there exists war or a threat of war, or a state of public peril or national emergency, to close down ". . . any station for radio communication or any device capable of emitting electromagnetic radiations between 10 kilocycles and 100,000 megacycles which is suitable for use as a navigational aid beyond five miles . . . and see that the equipment is removed,

# SPELLMAN TELEVISION CO., INC. 3029 WEBSTER AVENUE BRONX, N. Y. Kingsbridge 7-0300

## J-A-N TUBES! J-A-N

AT DEALERS COST!! WHILE THEY LAST!!  
New!! (Minimum Order \$25.00) Guaranteed!!

1A5GT . . . . .	.65	6L6GA . . . . .	1.30
1B22 . . . . .	2.75	6Y6G . . . . .	.65
1B24 5y1 . . . . .	13.00	6X4 . . . . .	.75
1L4 . . . . .	.50	6SL7GT . . . . .	.75
1T4 . . . . .	.55	6SN7GT . . . . .	.70
2C26A . . . . .	1.25	6X4 5y1 . . . . .	1.25
2J22 . . . . .	4.50	700A . . . . .	14.50
2J31 . . . . .	17.50	707B . . . . .	11.00
2J32 . . . . .	27.50	714A . . . . .	4.50
2J33 . . . . .	24.50	720BY . . . . .	45.00
2J38 . . . . .	12.50	721A . . . . .	2.25
2J48 . . . . .	19.50	723A/B . . . . .	9.50
2J128A . . . . .	135.00	724B . . . . .	2.00
2X2 . . . . .	.65	725-A . . . . .	6.50
2X11 . . . . .	.49	726-A . . . . .	4.50
3-15 . . . . .	9.55	728-A . . . . .	.45
3B7 1291 . . . . .	.45	829-B . . . . .	10.50
3D6 1299 . . . . .	.45	832-A . . . . .	6.75
3B26 . . . . .	2.75	834-A . . . . .	45.00
3B27 . . . . .	2.75	931-A . . . . .	3.95
3B28 . . . . .	4.95	954 . . . . .	.19
3B29 . . . . .	3.95	955 . . . . .	.45
3HP7 . . . . .	2.75	10Y . . . . .	.35
4J26 . . . . .	99.50	19 . . . . .	.35
5B7 . . . . .	3.95	35 51 . . . . .	.35
5D21 . . . . .	14.50	39/44 . . . . .	.35
5FP7 . . . . .	1.60	VT4C . . . . .	.49
5U4G . . . . .	1.60	VT-52 . . . . .	.45
5Z3 . . . . .	.60	1616 . . . . .	.75
6AC7 . . . . .	.65	1619 . . . . .	.25
6C6 . . . . .	.35	1642 . . . . .	.40
6C86 . . . . .	.59	REL-21 . . . . .	2.00
6H6 . . . . .	.59	9003 . . . . .	1.25
6J5 . . . . .	.40	C6J . . . . .	3.50
6L6 . . . . .	1.60	12SL7GT . . . . .	.70
6L6G . . . . .	1.50	12A6 . . . . .	.35

NEON LAMPS—G.E. Type NE-2 Miniature. With Pig-tails. Starting Volts: A.C.—65, D.C.—90, 1/25W. 3 for 25c. . . . . \$6.75 per 100

BLOWER ASSEMBLY—Size: 4 1/2" Long x 3 1/4" Diam. (approx.). Cast Aluminum Housing. 27 1/2 V.D.C. J. Oster 7000 R.P.M. Motor. . . . . NEW \$4.95

AS97/ART—Ant. System. 54" tapered whip with matching section in shielded base. 52 ohm coax input. . . . . NEW \$1.25 ea.

LEVER SWITCH—W.E. Anti-Capacity Switchboard Type. D.P.D.T. Momentary and Lock. With Red or White Knob. . . . . NEW 75c ea. 3 for \$2.00

DYNAMOTORS (28 V. Input), 2 DA 1-A. Output: 230 V.D.C. @ 100 Ma. . . . . New \$3.95  
# P.E. 86. Output: 250 V.D.C. @ 60 Ma. with Spare Brushes. . . . . NEW \$1.25 ea.

TUNING UNITS—For TCE-1 Transmitters. Contains Tank Condensers, Coils, Dials, etc. Ideal for V.F.O. or 100 watt Xmtr. Freq. Ranges: . . . . .

(A) 3000-4525 KC. . . . . \$5.75 ea.  
(B) 4525-6500 Kc. . . . . \$5.25 ea.  
(C) 6500-9050 Kc. . . . . \$5.75 ea.

VERY GOOD CONDITION  
SEND FOR OUR NEW CATALOG!  
Prices F.O.B. our Whse. Material subject to prior sale. 25% Dep. with all orders. Bal. C.O.D. Foreign Cash with order. Orders without postage are shipped Express Collect.

**FOREST SALES CO., INC.**  
702 Madison Street Euc. 6-1663 Oak Park, Ill.

## SELLS ON DEMONSTRATION DUKANE MAGNETIC TAPE RECORDER



DEALERSHIPS AVAILABLE NOW!  
MAIL COUPON FOR INFORMATION TODAY!

DUKANE CORP. Dept. RTN-12, St. Charles, Ill.

Please send information on the Dukane Magnetic Tape Recorder.

I am interested in a dealership.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

ESTABLISHED AS "OPERADIO" 1922

if necessary, providing just compensation to the owners. Those who violate the law will be subject to stiff penalties." Specifically, the amendment declares that those who are found guilty will "... be punished ... by a fine of not more than \$1,000 or by imprisonment for not more than one year or both, and if a firm, partnership, association of corporation, by fine of not more than \$5,000." Those who violate the law "... with intent to injure the United States, or with intent to secure an advantage to any foreign nation shall upon conviction ... be punished by a fine of not more than \$20,000 or by imprisonment for not more than 20 years, or both."

**THE SHIFTING OF FREQUENCIES**


by broadcasters to confuse enemy aircraft trying to use the signals for homing, proposed in a master plan several months ago to industry, was tried recently during the early morning hours with extremely successful results. In a joint effort of about 400 stations in nineteen states located on the eastern seaboard from Maine to Virginia, and as far west as portions of Illinois and Wisconsin, plus the Eastern Air Defense Force as well as the FCC, the deception plan featured a shift in frequencies in different locales every half minute or so. Direction finders in aircraft trying to glide in on a particular broadcast beam acted quite queerly, since they danced all over the dialplate.

The intriguing plan, which it was said originated in Great Britain, would also call for all elimination of station breaks or call-letter announcements to confuse further any alien aircraft seeking to home in on the beams.

**COMMUNITY TV**, in a new form, using common-carrier microwave links, recently found its way to the desks of the Commission in Washington. In an application filed by *J. E. Belknap and Associates* of Poplar Bluff, Missouri, a request was made for a system which would permit relaying of TV signals between the Memphis and Missouri communities of Kennett and Poplar Bluff, using frequencies of 5925 and 6425 mc.

In this novel approach to the distribution of signals to DX areas, the video programs of WMCT would serve as a feed, with a two-channel pickup chain employed for beaming signals to a point 75 miles northwest to Kennett and from that site to Poplar Bluff, 40 miles away. Other cities en route were indicated as possible signal sharers, with cities as far north as Cairo, Illinois and Paducah, Kentucky suggested as other points to which signals might be focused. Should the plan work out, the signals of KSD-TV may be used in another route scheme, providing service to Mt. Vernon, Benton, DuQuoin, West Frankfort, Johnson City, Marion and Carbondale, Illinois.

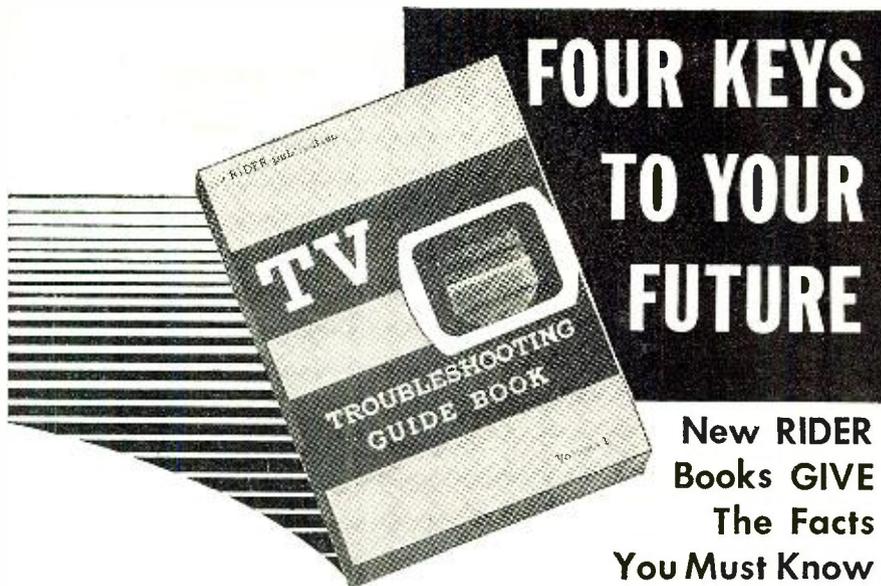The application revealed that distributors of sets would be asked to pay \$5000 upon the installation of 100 chassis, plus \$25 per receiver up to 500



**New RIDER Books GIVE The Facts You Must Know**

**TV TROUBLESHOOTING GUIDE BOOK**

A new, practical, easy-to-use guide book that is the final word on television troubleshooting. It tells how to spot receiver troubles and correct them. Contains actual information right from the manufacturers. Five information-packed chapters, durably bound.

More than 200 pp., 8 1/2" x 11" ..... **\$3.90**

**RECEIVING TUBE SUBSTITUTION GUIDE BOOK**

First Supplement by H. A. Middleton

An indispensable addition to the original book. Illustrating 650 completely new radio-television tube substitutions in numerical sequence with accompanying wiring instructions, original and substitute tube socket illustrations. If you own the original edition, you need this supplement for complete coverage.

48 pp., 8 1/2" x 11" ..... **\$ .99**

**TV AND ELECTRONICS AS A CAREER**

by Ira Kamen and Richard H. Dorf

Here is an interesting, informative book important to your future. Written by top authorities of the industry as an authentic guide to the career possibilities offered by all phases of the electronics industry.

326 pp., 5 1/2" x 8 3/8" ..... **\$4.95**

**BROADCAST OPERATOR'S HANDBOOK**

by H. E. Ennes, Second Edition

A practicing broadcast operator tells veteran and student operators all the procedures of AM and FM studio operating practices. A valuable, easy-to-read book for anyone wishing to make a career of broadcasting or to increase present knowledge if already active in the field.

440 pp., 226 ill. .... **\$5.40**

**Coming Soon... UHF PRINCIPLES, by Allen Lytel... Don't Miss This!**

CLIP AND MAIL THIS COUPON - TODAY!

**JOHN F. RIDER, Publisher, Inc., Dept. RN**  
480 Canal Street • New York 13, N. Y.


Please send me book(s) checked. It is understood, if not satisfied, I may return them within 10 days and receive full refund.

TV TROUBLESHOOTING GUIDE BOOK, \$3.90  
 RECEIVING TUBE SUBSTITUTION GUIDE BOOK, 1st Supp., \$9.99  
 TV AND ELECTRONICS AS A CAREER, \$4.95  
 BROADCAST OPERATOR'S HANDBOOK, \$5.40

Name.....  
 Address.....  
 City.....Zone.....State.....  
 (Please Print)



## Special Purchase FM Radio Chassis

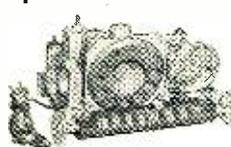

88-108 MC  
Complete with 6 tubes. Built-in Antenna and Speaker. Product of Famous Radio & TV Manufacturer whose name we promised not to mention.

**TUBE LINEUP**  
1-12B7 1-12S8  
2-12BA6 1-35W4  
1-35B5

Regularly \$29.95  
Brand New

**\$16.95**

May also be used as an FM Tuner by picking signal off detector.

## Special Purchase Number Two!

GENERAL INSTRUMENTS 3-SPEED  
AUTOMATIC RECORD CHANGER

... with flip-over dual cartridge. Plays 33 $\frac{1}{2}$ , 45 and 78 RPM records automatically. . . .

Regularly \$34.95  
BRAND NEW **\$19.97**

NOTE: Do not send money for postage on above items—we ship best way—charges collect.

## VARIABLE CONDENSERS

From SCR-522 2 Gang—25 MMF per section . . . . . **\$1.29**


From SCR-522 3 Gang—25 MMF per section . . . . . **\$1.59**



BRAND NEW with CONCENTRIC AIR TRIMMERS
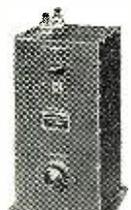
## BC-306A ANTENNA TUNING UNIT

Contains antenna variometer heavy duty 3 pole 5 pos. ceramic switch, velvet vernier dial. Standard off insulators housed in heavy aluminum case only. . . . . **\$1.95**



## LOW FREQ. XTALS-Ft 241A

For SSB, lattice filter, etc. 1/2" spc. 54th or 72nd harmonic channels listed by fundamentals. Fractions omitted.

372 404 435 506	400 462	5910	2030 2442
374 405 436 507	440 463	6370	2045 2532
375 406 437 508	441 464	6450	2105 2545
377 407 438 509	442 466	6470	2125 2557
379 408 481 511	444 468	6497	2145 3202
380 409 483 512	446 469	6522	2155 3215
381 411 484 514	447 470	6547	2220 3237
383 412 485 515	448 472	6610	2258 3250
384 413 487 516	450 474	7350	2280 3222
385 414 488 518	451 475	7480	2282 3510
386 415 490 519	452 476	7580	2290 3520
387 416 491 520	455 477	7810	2300 3550
388 418 492 522	457 479	7930	2305 3570
390 419 493 525	459 480		2320 3580
391 420 494 526	461		2360 3945
392 422 495 530			2390 3955
393 423 496 531			2415 3995
394 424 497 533			2435
395 425 498 537			
396 426 503 538			
397 427 504			
401 431			
402 433			
403 434			

## SCR 522 Xtals

1/2" pins 1/2" spc.

5910	2030 2442
6370	2045 2532
6450	2105 2545
6470	2125 2557
6497	2145 3202
6522	2155 3215
6547	2220 3237
6610	2258 3250
7350	2280 3222
7480	2282 3510
7580	2290 3520
7810	2300 3550
7930	2305 3570
	2320 3580
	2360 3945
	2390 3955
	2415 3995
	2435

99c ea. 10 for \$9.00  
SPECIAL 200 Kc xtals without holders 99c Each 3 for \$2.00

## HAM XTALS-Ft 243 HOLDERS—1/2" pin spc.

4190 6773 7840	1015 5773 6273 6540 7440 7650
5030 6873 7873	1129 5800 6306 6573 7473 7673
5485 6906 7906	2045 5806 6325 6575 7506 7706
6040 6973 7940	3735 5825 6340 6600 7540 7806
6073 7740 7973	5305 5840 6373 6605 7573 8240
6106 7773 8273	5677 5850 6406 6625 7606 8340
6125 7806 8306	5706 5873 6440 6640 7640 8400
6140	5725 5875 6450 6673
6173	5740 5906 6473 6706
6175	5750 5940 6475 6740
6206	5760 5973 6506 7340

Add 20c for each 10 xtals or less for postage and handling.

**TERMS:** All items F. O. B., Washington, D. C. All orders \$30.00 or less, cash with order. Above \$30.00, 25 per cent with order, balance C. O. D. Foreign orders cash with orders, plus exchange rate.



units and then \$10 a set for between 500 and 1000 sets. There would be no further charge for more than 1000 sets. In addition, service charges were proposed; \$1.75 per month for each set up to 500, \$1 for 500 to 1000 chassis and 75 cents thereafter. No rates were established for the distributor-to-consumer charges, nor was any plan offered on the methods which might be used to affect distribution of the community-type pickup receivers.

In judging the virtues of this plan the Commission will be obliged to consider the status of the community systems already installed, which simply pick up signals on a high-gain antenna, amplify them and pipe them to sets in the surrounding country for a fee. Although no transmission is involved and coax serves as the feedline from antenna to each set, the service was said by some to come within the common-carrier scope since fees were paid by the individual set operators. Also to be considered are the possibilities of new stations which might be installed around the proposed receiving sites for the v.h.f. or u.h.f. bands. The remote links might be viewed as a competitive media, restricting the listening appeal of the new stations and thus endangering their economic standing. In view of the allocation angle, it may be necessary for the Commission to ask for a hearing or review their assignment proposals in the southern areas. It may also be necessary to introduce rules which will provide for expanded receiving areas produced either by coax or the microwave type of community TV.

**TWO PROPHECIES**, offered by a pair of government's outstanding specialists during an industry meeting in Washington in the early winter months, disclosed that '52 might not be as blue a year as many forecasted earlier.

In one prediction presented by Curt Plummer, the FCC's Broadcast Bureau Chief, it was indicated that the freeze would definitely be lifted by April and that about 80 stations would shortly thereafter receive their permits to go on the air, with about fifty per cent receiving ultra-high authorization and fifty per cent low-band approval. Industry experts declared that there were enough transmitters in stock, or being made, to permit some of these to go on the air before the close of '52.

The second crystal-gazing statement, issued by Ed Morris, Chief of the Electronics Section of the *National Production Authority*, disclosed that around 4 million television sets would be produced in '52, and production of several hundred thousand sets may be for the new markets created by very-high and ultra-high stations which might go on the air before the end of the year. There should be sufficient material available for the manufacture of these chassis, Morris pointed out; the peak of military requirements occurring early in '52 and leveling off to a plateau stage for the remainder of the year.

## for dependable sound, INDUSTRY relies on ATLAS



DR Double-Reentrant Projectors

**DEPENDABLE QUALITY:**  
The latest electro-acoustic research and engineering—and over 20 years of manufacturing know-how—are behind every ATLAS product.

**DEPENDABLE SERVICE:**  
Coast-to-coast and around the world today—in every Industrial, Marine, Railroad, Military, Educational, Civic, U.S. and Foreign Government application—under every kind of climate and noise condition—ATLAS sound equipment is famous for highest efficiency and durability. That's the proof of ATLAS performance dependability.

**DEPENDABLE DELIVERY:**  
Yes, ATLAS gives our Government highest priority. And yes, we too feel the pinch of material shortages. But our customers will continue to get our usual dependable delivery—because we believe in equitable and dependable distribution to all ATLAS users.

**DEPENDABLE PROFITS:**  
Completeness of line, excellence of product, dependable delivery, right prices—that's the ATLAS combination that means high, steady Industrial Sound profits for You!


JUDGE for yourself, COMPARE ATLAS at your local Jobber today. See why ATLAS is the preferred line for utmost dependability. Write NOW for FREE latest Catalog 551.



Paging & Talk-Back Speakers



ALNICO-V-PLUS Driver Units

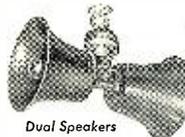

Dual Speakers



FULL-GRIP, VELVET-ACTION Mike Stands

**RADIO ENGINEERING DEGREE IN 27 MONTHS**

Radio engineering is a big field. There's room for you in it—if you're good. Get first-class training at Indiana Tech. Intensive specialized course, including strong basis in mathematics and electrical engineering, advanced radio theory and design, television. Modern laboratory. Low tuition. Also 27-month courses in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. Approved for G.I.'s. Enter March, June, September, December. You can earn part of your expenses right here in Fort Wayne while you are studying.

**INDIANA TECHNICAL COLLEGE**  
912 E. Washington Blvd., Fort Wayne 2, Indiana  
Please send me free information on B.S. Engineering Degree in 27 months as checked.

Radio-Television  Aeronautical  
 Civil  Mechanical  Electrical

Name . . . . .  
Address . . . . .

The January-to-April period will probably be the most critical of the new year and may frighten many, it was said. Those who are able to carry on during this time should find the remaining eight months good ones for business on the domestic front, according to the Washington timetable.

**THE PROGRAM PURGE** campaign, described briefly in these columns in '51 and noted as having flared soon after the Benton measure which suggested a citizens' advisory committee to blue-book programs was proposed in Congress, has resulted in several striking developments, particularly the industry code which many have indicated should solve the problem.

Commenting on the broadcasters' policing plan, FCC chairman Wayne Coy declared that it may work, if it "... is enforced and it is flexible enough to meet changing conditions."

In a blistering attack on the programs as they are still being produced, Coy said: "The obscenity on the TV screens is getting worse. I am not a prude, and there may be a place for off-color jokes, but they are not for the television screen." Noting that people are concerned about what the children see on the screen, Coy added "... The mail at the FCC grows and the protests get louder and louder."

The advisory group, as suggested by the Benton bill, could evaluate program material and see that listeners and viewers are getting their dollar's worth "... out of what the FCC is allocating to broadcasters ..." noted Coy.

In the meanwhile, the *Association of Radio and Television Broadcasters* notified all its members that they should comply with the code which was quite a rigid affair. In a section on acceptability of program material, the code declared that "... profanity, obscenity, smut and vulgarity are forbidden, even when likely to be understood only by part of the audience. From time to time, words which have been acceptable, acquire undesirable meanings and telecasters should be alert to eliminate such words. ... Exhibitions of fortune-telling, astrology, phrenology, palm-reading and numerology are not acceptable. ... Criminality should be presented as undesirable and unsympathetic. The condoning of crime and the treatment or the commission of crime in a frivolous, cynical or callous manner is unacceptable. ... The use of visual or aural effects which would shock or alarm the viewer, and the detailed presentation of brutality or physical agony by sight or sound are not permissible."

If this code, based in part on the code used by the motion-picture industry, is adhered to honestly by all stations, not only by those who belong to the association, the Benton bill and other bureaucratic measures will certainly vanish. But if the self-policing fails, the government will surely begin to patrol the screen. ... L.W.

# NEW for '51

## Automatic Radio

CUSTOM-BUILT AUTO RADIOS

**1949, 1950 and 1951 FORD AUTO RADIOS**




List Price.....\$59<sup>95</sup>

**1949, 1950 and 1951 PLYMOUTH-DODGE RADIOS**



List Price.....\$59<sup>95</sup>

**1949, 1950 and 1951 CHEVROLET RADIOS**

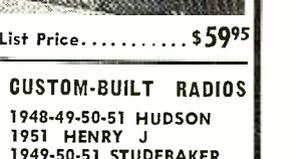


List Price.....\$59<sup>95</sup>

**ATTRACTIVE DISCOUNTS TO DEALERS**

Each radio is a six tube superheterodyne, six volt battery operation. Three gang tuning condenser and tuned RF stage. PM speaker Alnico No. 5 W.T. 10 lbs.—installation in a few minutes.

---

**SPECIAL**

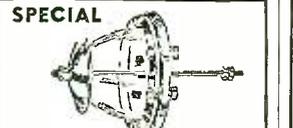

Navy entering type insulator. Porcelain flanged bowl with brass rod and fittings and aluminum shield. Dimensions: 4 3/8" high, 6-5/16" O.D. at base. New. \$4.50 Spare Bowl.....\$5

**MICROWAVE EQUIPMENT**

- 10CM Echo Box Frequency Range 2890Mc-3170Mc. Direct Reading Micrometer Head. Ring Prediction Scale Plus 90% to Minus 90%. Type "N" Input. Resonance Indicator Meter with Accessories and 10CM Directional Coupler and Spares—Brand New.
- 50 Radar 10CM Rotating Antenna 24" Parabola in Turbet 360° Span—Brand New 50-3 Bearing Control.

PRICES UPON REQUEST  
All Sizes of Crystal Electrodes.

---

**TUBES Prices Slashed**

2C34	50.85	523	89
2X2/879	65	6AL5	66
3C24	1.35	6AR5	77
7C4/1203A	75	6AR5	79
10Y	45	6AT6	59
151T	85	6AU6	90
30 SPEC	55	6AU6	69
39/44	40	6AV6	75
45 SPEC	35	6BA6	69
WE 203A	8.80	6BE6	73
316A	65	6B6G	77
WL531	4.25	6B6GT	1.19
713A	1.00	6J5GT	.63
801A	4.65	6J6	1.29
803	4.45	6J7	.85
823	.95	6L7	.95
931A	4.95	6S7GT	.90
864	4.45	6S7GT	.79
CK1005	.48	6U6G	.95
CK1007	1.20	6V6GT	.68
1828	.45	6W4GT	.66
1829	1.35	6X4	.72
2051	1.15	6X5GT	.49
7193	.50	7C6	.80
8011	.45	7A7	.82
9006	.30	12AU6	.59
C5B	9.75	12AT6	.75
CEGT 2	1.35	12AV6	.73
CK70	4.25	12BA6	.79
CRP-72	1.30	12BE6	.89
E-1148	1.35	12SN7	.99
HY-615	.25	12SQ7	.85
RKR-72	1.30	25Z5	.75
AWC-14	1.40	25Z5	.90
5BP4	4.95	35W4	.59
5FP7	1.95	50B5	.96
136C	.85	50C8	.89
136T	.85	50C8GT	.69
5U4G	.57	75	1.15
5W4	.90	85	.85

**LINEAR POTENTIOMETERS WW**

Ohms	Watts	EA	TEN
500	2	\$0.45	\$0.40
1000	2	.50	.45
3000	2	.55	.50
10,000	2	.55	.50
5000	3	.50	.45
15,000 Dual	3	.85	.80
10,000	3	.35	.30
25,000	3	.65	.60
50,000	4	.90	.85
15	25	.95	.90
20	25	.95	.90
25	25	.95	.90
30	25	.95	.90
100	25	.95	.90
200	25	1.20	1.10
500	25	1.20	1.10
1000	25	1.30	1.25
3000	25	1.40	1.35
15,000	25	1.70	1.60
20,000	25	2.00	1.95
150/switch	50 AN 3155-50	2.15	2.00
200/W/switch	50	2.15	2.00
800	50	2.65	2.50
3000	50	2.95	2.75
10,000	50	2.95	2.75
60	60	2.75	2.75
15	75	2.95	2.75
750	150	3.95	3.85
20,000	5	9.50	—
20,000	5 433AC	8.50	—
5000		1.95	—
6000		2.25	—

---

**WIRE AND CABLE**

**CORDAGE**—CO-122-3 Conductor Each AWG #22 Neoprene Jacket—CO-127 Single #14 Braided & Shielded—CO-121 Twisted Pair #16 Shielded SJ.

**ARMOUR**—Dria-23—Fria-4.

**MULTI-CONDUCTOR**—19 Cond. #16 AWG—14 Cond #16 AWG—7 Cond #16-7 Cond #14 AWG.

**COAXIAL**—RG-14/U—RG-22/U—RG-74/U.

**NYLON CORE**—#22 AWG Plastic Insulation.

**RELAYS**

12 VDC DPST Allied Control Box #32.....\$1.75

24 VDC 3 PDT 8 Amp.....1.50

24 VDC Solenoid, Operates 2 Switches.....1.75

40 VDC DPST—SPDT 1000 Ohm 110 VAC DPST 1 Amp Contacts Struth's Dunn CXA 1970.....3.65

110 VAC DPDT 35 Amp Contact Ward Co 25.....3.95

115 VAC DPST Struth's Dunn CXA-2997.....3.65

220 VAC DPDT Struth's Dunn CX212.....4.50

---

**HI-VOLTAGE FILTER CHOKES**

4 HY 4.5 Amp DC 3 Ohms 1230 RMS to ground GE 69G351.....NEW

1.7 HY 2 Amp DC 9000VDC GE Y3464A.....NEW

.25 HY 4 Amp 1.5 Ohm 20,000.....NEW

1 HY 3.2 Amp DC 3.5 Ohm GE 69G450.....NEW

**PRICES ON REQUEST**

**TOGGLE-ROTARY SWITCHES**

Pole	Posi-tion	Sec-tion	Shaft	Price
1	3	1	15/16"	\$0.35
1	3	6	7/8"	.60
*2	4	4	7/8"	.60
2	8	2	2 1/4"	.55

Permit 3A 250 Volt W/Hard-ware.....\$0.35

DPDT Center OFF Throw 1.15

DPDT 10A-250 VAC.....1.25

DPDT 5A 250VAC......95

DPDT C-H AN3023-2......90

---

**TIME DELAY SWITCHES**

1 Minute 115 VAC 60 Cy Enc. in Waterproof Metal Case. New.....\$5.25

3 Micro Switches Make Contact at 40-41-42 Sec. Time Delay 110 VAC Motor. New Thermo Switch 50° to 300° F. 115 VAC @ 6A, 230 VAC @ 200V @ 5-8A, 580V @ 5.25A RMS 4000V.....NEW

Test Relay VPC 365 15VDC Output 250V @ 70MA.....34.95

Synchronous Mallory.....NEW 5.95

Vibrator ATR 2410 24VDC Output 110V 100W.....NEW 2.50

**POWER EQUIPMENT**

Generator Voltage Regulator 115V 400 CY GE.....NEW

20C.....NEW \$29.95

Regulator X-Former 92-138V 60CY Phase Secondary 200V @ 5-8A, 580V @ 5.25A RMS 4000V.....NEW

Test Relay VPC 365 15VDC Output 250V @ 70MA.....34.95

Synchronous Mallory.....NEW 5.95

Vibrator ATR 2410 24VDC Output 110V 100W.....NEW 2.50

---

**TRANSFORMERS**

**PRIMARIES 115V 60CY**

9V @ 750 MA, 6.3C @ 3.9A, 5V @ 0.6A, 2400 V.....\$3.25

6.6V @ 0.6A, 2000V @ 2.60V @ 1.7A, 2700V.....2.75

6.4V @ 10A, 6.3C @ 0.6A.....3.45

660/330 @ .08A CT 5.0/2.5 @ 3A CT.....3.25

350-0.350 @ 120 MA, 5V @ 5A, 6.3V 4A CT 6.3V.....4.25

**ELECTROLYTICS**

2500 MFD 3 VDC \$ .40 \$ .35

500 MFD 12 VDC .90 .85

25 MFD 25 VDC .40 .35

50 MFD 25 VDC .60 .55

1000 MFD 25 VDC 1.25 1.15

150 MFD 50 VDC .50 .45

---

**TERMS:** Minimum order \$5.00—Mail orders promptly filled—All prices F.O.B. Boston, Mass. Send M.O. or check. Shipping charges sent C.O.D. 25% deposit required with all C.O.D. orders.

Prices Subject to Change without Notice

**SEND FOR OUR CATALOGUE**

Inquiries from Dealers, Schools and Industrial Firms Invited

# COMET ELECTRONIC SALES CO.

22 Washington St. • BEacon 2-7863 • Brighton 35, Mass.

117


ANNOUNCING THE SENSATIONAL

# R-J\*

\*Patent Pending

## SPEAKER ENCLOSURE

"Maximum Bass—Minimum Space"

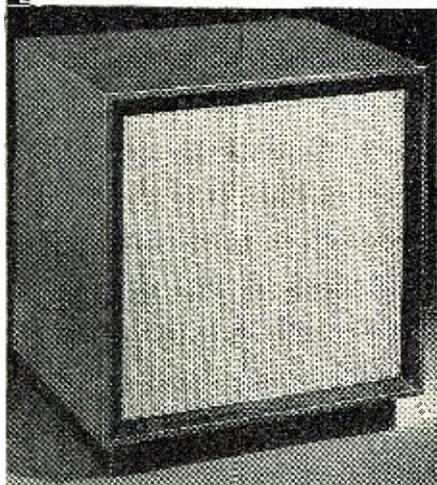

INCREDIBLE, but true—clean fundamentals down to 30 cycles in an enclosure measuring only 20" wide, 16" deep, 22 $\frac{3}{4}$ " high for a 15" speaker. The R-J will outperform ordinary enclosures many times its size. To hear it is to believe it. Visit your parts jobber for a thrilling demonstration.

### Outstanding Features

- Smooth response throughout the range.
- Unique damping and loading assures perfect separation of percussive tones.
- Small, flat sides need no bracing to prevent cabinet resonance and acoustic feedback.

Write for descriptive folder.

**R-J SPEAKERS, INC.**

45-39 VAN DAM ST., L. I. CITY 1, N. Y.

## International Short-Wave

(Continued from page 57)

1215A. (Pearce and O'Sullivan, England)

*Albania*—Tirana, 7.825, noted 1605 with music; news 1615. (Harris, Mass.)

*Algeria*—Radio Algerie, 9.57, Algiers, noted after KWID leaves the air, 1745-1800 sign-off. (Maurice, N. Y.)

*Anglo-Egyptian Sudan*—"Huna Om-durman" noted with fine signal, in clear, opening 2315 on 9.74A; QRM developed and signal faded somewhat by closedown 2145; all-Arabic speech and music. (Fargo, Ga.) The 17.944A outlet noted in South Africa 1130-1300 and 1400-1430, and on Fridays with *English* at 1230-1300. (Ridgeway)

*Angola*—CR6RP, Radio Clube do Cu-anza Sul, Novo Redondo, is operating on 4.932 at 1300-1500, with 200 watts; CR6RK, Radio Clube do Sul de Angola, Lobito, is broadcasting 0600-0730, 1130-1400, and 1500-1700 on 7.180 with 75 watts. (WRH Bulletin)

Radio Clube de Angola, Luanda, 9.64, is heard in "morning" session opening 0115; plays recordings mostly; also is using a 41-m. channel but that one is not being heard at the time this report was made. Radio Clube de Hu-ambo, Nova Lisboa, sent verification; said its transmitter is a 1 kw. job made in Brazil; that hopes to broadcast a French and *English* program shortly; is heard well in South Africa from 1330 to closedown 1530; has music-box interval signal; noted on 9.705 in parallel with 7.11. (Ridgeway, South Africa)

*Argentina*—LRT, 11.840, Tucuman, noted good strength around 1730. (O'Sullivan, England) LRA, 17.720, Buenos Aires, heard in *English* talk 1315-1325. (Sutton, Ohio)

*Australia*—VLM4, 4.9175, Brisbane, signs on 0245; news 0600, good level; VLX4, 4.8975, Perth, also has news 0600. (Saylor, Va.) VLI6, 6.09, Sydney, heard as early as 0230; formerly signed on 0300. (Balbi, Calif.) VLR6, 6.150, Melbourne, noted around 0310 at excellent level in Calif. (Winch)

*Austria*—Radio Sweden says the Blue Danube Network, Salzburg, is now using 6.055, 5.080, and 9.617. Noted by Pearce, England, on 9.617 with news 0115; on 6.065A at 1045 with music, call 1100.

*Radio Wein*, 11.784, Vienna, heard with recordings 0215. (Pearce, England)

*Azores*—Ponta Delgada, 4.845, noted with news in Portuguese now 1730. (Pearce, England) The 11.090 channel noted on winter schedule 1500-1600. (Ferguson, N. C., others)

*Balearic Islands*—Menorca, 7.550, is again reported at 1430 and signing off 1630. (*Short Wave News*, London)

*Bechuanaland*—Mafeking's ZNB operates on measured 8.244 at 1200-1430; good strength in South Africa. (Ridgeway)

*Belgian Congo*—OQ2AB, 11.90, is noted in South Africa at high level; is

RADIO & TELEVISION NEWS

# AMPERITE

Studio Microphones  
at P.A. Prices

Ideal for  
BROADCASTING  
RECORDING  
PUBLIC ADDRESS

"The ultimate in microphone quality," says Evan Rushing, sound engineer of the Hotel New Yorker.

• Shout right into the new Amperite Microphone—or stand 2 feet away—reproduction is always perfect.

• Not affected by any climatic conditions.

• Guaranteed to withstand severe "knocking around."



Models  
RBLG—200 ohms  
RBHG—Hi-imp.  
List \$42.00

"Kontak" Mikes  
Model SKH, list \$12.00  
Model KKH, list \$18.00



Special Offer: Write for Special Introductory Offer, and 4-page illustrated folder

AMPERITE Company, Inc.

561 BROADWAY • NEW YORK 12, N. Y.

Canada: Atlas Radio Corp., Ltd., 540 King St. W., Toronto

# Master Mobile

ANNIVERSARY MODELS  
132-J JUNIOR—140-J JUNIOR



132-J

## \$4.17

NET



140-J

**No. 132-J JUNIOR**—Junior Model of 132 MASTER MOUNT—slightly less in size. Rugged MASTER construction. SPRING: cadmium plated—beautifully finished. Plus a moisture-proof gasket and steel washer. Split Ball permits antenna adjustment to body contour. . . . Built to APPROVED and ACCEPTED MASTER SPECIFICATIONS.

**NEW No. 140-J JUNIOR BUMPER MOUNT.** Same high quality spring construction, workmanship and finish as 132-J JUNIOR.

### NEW MASTER TRIPLE M SILICON-CHROME WHIP ANTENNAS

Fits Master Mounts. Special tempered wire—finest cadmium plated. THE TOP BUY AT THESE PRICES:

Model No.	Overall Length	Net Price
NEW 9 SERIES—with $\frac{3}{8}$ " Threaded Studs		
9-60T	60"	\$2.97
9-72T	72"	3.24
9-84T	84"	3.30
9-86T	86"	3.60
9-96T	96"	3.75

Model No.	Overall Length	Net Price
NEW 8 SERIES—Without Studs		
8-60	60"	\$2.82
8-72	72"	3.08
8-84	84"	3.13
8-86	86"	3.42
8-96	96"	3.56

FOR SALE AT ALL LEADING JOBBERS

Master Mobile Mounts, Inc.

P. O. BOX 1817 • LOS ANGELES 36, CALIFORNIA  
WAREHOUSE AND SHIPPING ADDRESS: 1306 BOND STREET

scheduled Sundays *only* 0800-1000; all-French; plays recordings; calls "Radio Elizabethville"; opens with Westminster chimes at 0800 and National Anthem. (Ridgeway)

In answer to a listener's question recently, OTC, 9.767, Leopoldville, said it does not use native announcers but that *Radio Congo Belge*, also Leopoldville, has both a male and female native announcer for its native programs. (Bellington, N. Y.) OTM, 9.380 (seems back here from 9.400 now), noted with news in French 1400. (Pearce, England)

**Bolivia**—*Radio Illiamani*, La Paz, is operating as CP5 on 5.970 and as CP6 on 9.500 at 0630-0800, 1000-1200, 1630-2200; output for each is 1 kw. (WRH Bulletin)

**British New Guinea**—VLT9, 9.5196, Port Moresby, ends *English* 0200; has short interval of single drum beats, then continues with native commentary. (Russell, Calif.) VLT7, 7.280, noted signing off weekdays 0745, good level in West Virginia.

**Bulgaria**—*Radio Sofia* is currently using 9.705A to North America evenings with its own program at 2000; also relays Moscow's North American (*English*) service at times. (Keltling, N. Y.; Balbi, Calif., others) Is using 6.070 in *English* 1500; in Italian 1515; in French 1530, and in German 1545; seems to have increased power on this channel. (Radio Sweden)

**Burma**—Rangoon now has an *English* session on 9.543 at 2015-2030; during the 0115-0145 period, 6.035 is added, and is also used at 0915-1015 for *English* period. (Radio Sweden) Has been heard on 4.775 in *English* to 1015 sign-off. (Radio Sweden)

**Canada**—CBFY, Montreal, noted mornings recently on measured 11.700 with religious program daily 0815. (Ferguson, N. C.) VED, 7.32A, Edmonton, Alberta, noted with news in progress when tuned 0105. (Bellington, N. Y.) Identifies and signs off 0200. (Russell, Calif.) CBNX, 5.970, St. John's, Newfoundland, 300 watts, is scheduled 0600-2230 now except Sat. when National Hockey League is carried to 2245. (Peddle, Newfoundland)

**Cunary Islands**—EA8AB, measured 7.517, noted from tuning 1704 to sign-off 1800; heavy QRM, fair signal.

**Ceylon**—*Radio Ceylon* is currently operating for India

## Seletron SELENIUM RECTIFIERS

*May be up your alley, too!*

AS THEY ARE FOR  
THE BRUNSWICK-BALKE-  
COLLENDER COMPANY



The new "Tel-E-Foul" photo-electric Foul Indicator produced by The Brunswick-Balke-Collender Company, famous manufacturer of bowling equipment, includes 75 MA SELETRON miniatures in its electronic circuits.


SELETRON Selenium Rectifiers are the choice of an increasing number of manufacturers in diversified fields because they are so thoroughly dependable under all types of grueling conditions. SELETRON is available in the miniature sizes required for radio, TV and other electronic circuits, all the way up to heavy duty power stacks used in a wide range of industrial applications.

Whenever you meet up with a power conversion problem, no doubt SELETRON engineers can be of substantial assistance in recommending the right rectifier for your needs. Write us today!

Illustrated above is the "Tel-E-Foul" control box. When the bowler oversteps the foul line the electronic beam conveys an impulse causing a light to flash above the alley. A 75 MA SELETRON miniature is built into the control box on each bowling lane.

**Seletron**  
SELETRON DIVISION  
**RADIO RECEPTOR COMPANY, INC.**  
Since 1922 in Radio and Electronics

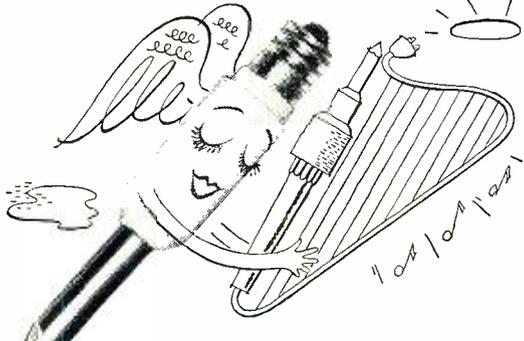
Sales Dept.: 251 W. 19th St., New York 11, N. Y. • Factory: 84 N. 9th St., Brooklyn 11, N. Y.



## Ungar's little Angels

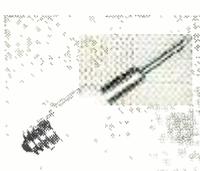**STILL HARPING ON THE SAME SWEET SONG**

From minor repairs to high-speed production soldering, 8 talented muses to remember are Ungar's Little Angels. Each versatile, job-designed tip fits the trim, slim Ungar Pencil to strum a tune in perfect harmony with most soldering requirements. Ask your supplier for the lyrics to this merry melody.




No. 538 1/8" CHISEL TIP, 20 Watts  
For Light Duty Work. Especially recommended for Printed Circuits. Very useful for small joints and hard-to-reach points on radio and TV, electronic assemblies, aircraft instruments, hearing aid assembly and repair.

Write for Catalog No. 400

**Ungar** ELECTRIC TOOLS, INC., Los Angeles 54, Calif.
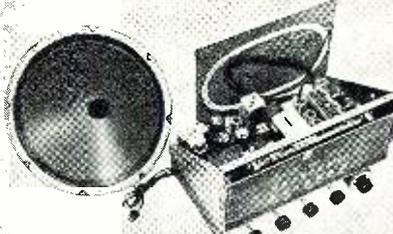
# SAVE

**THAT GOOD LOOKING OLD CONSOLE—  
REPLACE YOUR OBSOLETE RADIO  
with a modern, easily installed  
ESPEY AM/FM CHASSIS  
and your favorite console is "right-up-to-date"**



Rated an excellent instrument by America's foremost electronic engineers. Fully licensed under RCA and Hazeltine patents. The photo shows the Espey Model 511-C, supplied ready to play. Equipped with tubes, antenna, speaker, and all necessary hardware for mounting.

**NEW FEATURES**—Improved Frequency modulation circuit, drift compensated • 12 tubes plus rectifier, and pre-amplifier pick-up tubes • 4 dual purpose tubes • High quality AM-FM reception • Push-pull beam power audio output 10 watts • Switch for easy changing to crystal or variable reluctance pick-ups • Multi-tap audio output transformer supplying 4—8—500 ohms.

Makers of fine radios since 1928.

Write Dept. RN-1 for literature and complete specifications on Model 511-C and others.

**ESPEY**  
MANUFACTURING COMPANY, INC.  
528 EAST 72nd STREET, NEW YORK 21, N. Y.  
TEL. TRafalgar 9-7000

# THERE'S Fun A D Profit IN Magnetic Recording



A complete guide to this fast-growing art

by S. J. Begun  
300 pages, 6 x 9  
130 illustrations  
Price only \$5

## A HOW-TO-DO-IT BOOK FOR REAL RESULTS!

Beginning with the history and theory of the art, this fascinating book, MAGNETIC RECORDING, brings you accurate data on every detail of modern magnetic recording equipment and how to use it for best results. From home entertainment to motion pictures, broadcasting, professional and amateur radio to special applications such as secret communications (speech scrambling) you get the latest, most comprehensive data on all phases of recording by magnetic methods.

## Fundamentals—Components Equipment

Whether you do recording as a hobby or as a business, this great book will prove invaluable. Included are clear explanations of acoustic and magnetic factors, reproducing heads, drive mechanisms, recording media and the methods of recording, reproduction and erasing.

Standard equipment is fully discussed along with instruments needed to evaluate recording performance. Subjects covered include:

- |   |  |
|---|--|
| 1—History of Magnetic Recording             | 6—Magnetic Recording Equipment               |
| 2—Acoustic Factors                          | 7—Applications of Magnetic Recording         |
| 3—Magnetism                                 | 8—Instrumentation and Recording Measurements |
| 4—Theory of Magnetic Recording              | 9—The Magnetic Phonograph                    |
| 5—Components of a Magnetic Recording System | 10—General Glossary                          |

## READ IT 10 DAYS... at our risk!

Dept. RN-12, RINEHART BOOKS, Inc.,  
(Technical Division),  
232 Madison Ave., New York 16, N. Y.

Send MAGNETIC RECORDING for 10-DAY FREE EXAMINATION. If book is O.K. I will then promptly remit \$5.00 in full payment. If not, I will return book postpaid in good condition and owe you nothing.

Name .....

Address .....

City, Zone, State .....

Employers' Name & Address .....

Price outside U. S. A. \$5.50—cash only.  
Money back in 10 days if you return book.

on 15.120, 11.975, and 7.190 at 2045-0230, 0630-1145. (Radio Sweden) Takes BBC news relay 2100.

Noted on 11.975 at 1125; QRA now is Radio Ceylon, Torrington Square, or P. O. Box 582, Colombo 7, Ceylon. (Kroll, N. Y.)

Chile—CE1190, 11.900, Santiago, noted 2325 with closing announcements in Spanish, march, chimes, and then carrier left the air. (Ferguson, N. C.) CE920, 9.200A, Punta Arenas, heard 2120 with weak level, fading. (Bromley, Ontario)

China—When this was compiled, Radio Peking was noted on approximately 10.37 mornings and also evenings (around 1700-2030); news 1700, usually followed by POW messages 1715; the 15.060A outlet is noted in various oriental languages, no English, around 1700-2030 sign-off. Another Chinese outlet on 15.175A is noted to after 2000; this one was measured 15.1756 by Russell, Calif., at 1900.

Peking's 6.100 outlet noted 0400 carrying the news. (Gay, Calif.)

Colombia—Radio Nacional, Bogota, operates weekdays 0955-1400 on 4.955; 1700-2330 on 6.200, 11.680; Sundays 1100-1515, 1800-2315 on 4.955, 6.200, 11.680. HJKH, Bogota, *Emisora Nueva Granada*, is on the air daily 0700-2300 on 6.160, 10 kw.; HJDU, operated by the University of Antioquia, Medellin, is on the air on 4.805 weekdays 1130-1400, 1800-2300. (WRH Bulletin) HJAP, 4.931, Cartagena, *Radio Colonial*, noted signing off 2250; HJAE, 4.9695, Cartagena, heard in Spanish signing off 2340. (Russell, Calif.)

Costa Rica—TIPG, 9.62A, noted identifying as "La Voz de la Victor" 1900. (Bellington, N. Y.) TIRH, 6.1533, San Jose, noted to after 0100. (Russell, Calif.)

Radio Nueva Alma Tica is a new station in San Jose, operating on 6.180 with 3 kw., call is TIGH4; other new Costa Rican stations are "La Voz de Costa Rica" on 9.692, 3 kw.; "La Voz del Hogar," on 9.714, 1 kw. (WRH Bulletin)

Cuba—COCY was recently measured 11.736 at 1020, strong signal. (Ferguson, N. C.) COBL is back on 9.833A again. (Stark, Texas; Machwart, Mich.)

Cyprus—Bellington, N. Y., recently noted Limassol around 2340 tune-in on 6.117A in parallel with 6.167A with Arabic chanting.

Czechoslovakia — CLR4B, 15.320, Prague, noted with news 0715, strong signal; English ended 0743; asked for reports and said letters would be acknowledged Sundays 1400. (Ferguson, N. C.) Prague noted on 6.170 with English 1400-1430 in parallel with 11.875; found on same channels 1600 with English. (Pearce, England) Noted signing on in Czech 2315 on 6.010. (Machwart, Mich.)

Dominican Republic—HISZ, 5.030, is coming in now around 1700. (Saylor, Va.) HI4A, 4.980, Santiago, noted 1715. (Catch, England) HI2A, 9.680, noted recently when XEQQ, Mexico, was very weak on that channel; heard 1646 when

## TUBE BARGAINS

5U4G .....	\$ .65	6AU6 .....	\$ .55
5Y3GT .....	.49	6BC5 .....	.67
5Z4 .....	.90	12AU6 .....	.67
6AL5 .....	.55	12AU7 .....	.82
6AK5 .....	.85	12BE6 .....	.60

All tubes standard brands, guaranteed.  
Write for prices on other types.

## MULTIMETER

5000 ohms per volt, 3" meter, 24 ranges, only 5 7/8" x 3 1/16" x 2 3/8"  
4 DC VOLT RANGES 0/0.3/0.30/1.50  
4 AC VOLT RANGES 0/6/150/300/600  
4 ohms ranges 0/2K/20K/200K/2 meg  
4 AC VOLT RANGES 0/6/30/150/600  
4 OUTPUT RANGES 0/6/30/150/600  
4 RESISTANCE RANGES -6/+10/+8/+24, +22/+38, +34/+50.

Complete with battery test leads & 90 DA test GUARANTEE ...



4" SQ 0-50 UA Meters ..... \$12.95

## OIL CAPACITORS

3mf 330VAC .....	1.95	2mf 2KVDC .....	\$1.95
5mf 330VAC .....	3.95	5mf 2KVDC .....	3.95
14mf 275VAC .....	3.95	2mf 3KVDC .....	5.50
2mf 600VDC .....	.99	3mf 4KVDC .....	8.95
8xmf 600VDC .....	2.75	4mf 4KVDC .....	10.50
50mf 600VDC .....	9.95	2mf 5KVDC .....	12.50
2mf 1KVDC .....	1.25	2mf 6KVDC .....	14.95
4mf 1KVDC .....	5.95	1mf 7.5KVDC .....	23.99
16mf 1.5KVDC .....	7.95	2mf 12.5KVDC .....	59.50

## CO-AXIAL RELAYS

Allied Control Type RA, SPDT, 6 VDC. Uses Standard Co-Ax Connectors.....\$5.95

NEW STEEL TABLE RACK CABINETS, 8 3/4" H x 19" W x 13" D, Black Crackle Finish, Hinged Top with Lock, 2" opening in rear for cable connections. Shipped via Ry. Xpr. ....\$5.95

## CHOKES

6 HY 70 MA, 215 Ohm .....	5.95
8 HY 90 MA, 100 Ohm, Cased .....	.99
7 HY 125 MA, Cased .....	1.49
.28 HY 130 MA, 57 Ohm, Cased .....	.85
10 HY 150 MA, 140 Ohm .....	1.69
4 HY 200 MA, Cased .....	3.15
4 HY 200 MA, 140 Ohm, Cased .....	5.10
5 HY 250 MA, 15 Ohm, Cased .....	1.95
5 HY 250 MA, 65 Ohm, Cased .....	3.49
1 HY 300 MA, 120 Ohm, SW, CH, Cased .....	6.50
3 HY 300 MA, Cased, 85 Ohms .....	5.00
4 HY 300 MA, 30 Ohm, Cased, Herm. Seal. ....	5.50
5 HY 500 MA, Cased .....	5.95
7 HY 700 MA, 15 Ohm, Cased .....	11.50
3 HY 800 MA, SW, CH, Cased .....	7.95
3 HY 950 MA, 23 Ohm, Cased .....	11.50
7 HY 1 AMP, Cased .....	29.50
16 HY 1 AMP SW, 45 Ohm .....	37.50
8 HY 1.5 A, Cased .....	42.50

## 115V FILAMENT TRANSFORMERS 60 CY

2 VCT 10A, 10 KV Insulation, Cased .....	\$4.50
1 VCT 3A, 2.5 V @ 6A, Cased .....	3.45
1 VCT 3A, 2.5 V Insulation .....	2.95
1 V @ 3A, 6.3 VCT @ 3.5A .....	2.95
1 VCT 12A, 2.5 KV Insulation .....	5.95
1 VCT 20A, 2.5 KV Insulation .....	6.95
1 VCT 1A, 2.5 KV Insulation .....	.99
3 VCT 3A, 2.5 KV Insulation .....	2.95
1 V @ 4A, 6.3 V @ 4A, Cased .....	2.95
1 V @ 6A, 5V 3A .....	2.95
1 VCT @ 6A, 2.5 KV Insulation .....	2.75
1 VCT 10A, Cased, 10A .....	3.95
10 VCT 10A, 2.5 KV Insulation .....	6.00
24 V 1A, 2 KV Insulation .....	3.95
32 V 1A .....	1.95

## 115V POWER TRANSFORMERS 60 CY

68 to 83 V Half Wave, 1.5A .....	\$1.25
300 V 20 MA (Half Wave) .....	\$1.25 ea. / 2 / 2.00
415 VCT 145 MA, 6.3 V 3A, 5V 3A .....	2.95
8 V @ VCT 10A, 6.3 V 3A, 5 V 3A .....	3.25
100 VCT 90 MA, 6.3 V 3A, 5 V 3A .....	3.50
140 VCT 185 MA, 6.3 V 4A, 5 V 2A .....	3.25
200 VCT 200 MA, 6.3 V 3A, 5 V 2A .....	3.25
800 VCT 300 MA, 6.3 V 10A, 5 V 6A, 5 V 2A .....	4.50
750-600-0-600-750 VDC, 225 MA .....	3.25
3500 VCT 350 MA, Cased .....	25.50
5400, 5800, 6200 VCT 110 MA .....	25.50
2500 VDC 1A, Pr. 230 V 3ph 60 Cy .....	12.50

## COMPONENT BARGAINS

1N29B crystals, 54, 55, 1N24 diodes .....	\$0.49
866A \$1.50, 872A \$2.95, 304TL .....	9.95
TS-13 Handset \$4.95, National type N dial .....	3.75
Dual 10 Amp, 115 V, 60 Cy, circuit breaker .....	2.95
1 screw terminal strip, 6/32 (Screw) .....	10 / 2.0
Barrier Strip, Yellow Bakelite, 6 term .....	10 / 1.50
Millen terminal strip 37104 .....	10 / .40
1 pin min. water socket .....	10 / .85
1 pin min. molded sock, base shield .....	10 / 1.75
Octal sock, 8 mica filled .....	18 / 1.00
plug stentite socket .....	18 / 1.75
4 pron. MIP 6 socket .....	10 / .85
1 pin min stentite sock, base shield .....	10 / 2.50
1CA Phono Plug & Jack #2383-2385 .....	10 / 1.50
1 Panel Bearing .....	10 / 1.50
1 rubber line cord & mold, plug .....	10 / 1.99
1 green 110V Pilot Light assembly .....	.75
SPST 6A 125V, H & H Handle Togg. Sw .....	.35
C-H Luminous tip bat handle Aircraft Togg. Sw .....	.35
SPST 5A 125V .....	.25
SPST as above, momentary only .....	.25
SPDT as above, neutral center .....	.49
SPST Rotary Switch, wafer type .....	2 / 2.0
6 pos., Ceramic Rotary Switch .....	.59
TRC 2000 ohm 50W WW Res .....	.49
Rheostat—50 ohm 25W, 100 ohm 25W .....	.75
1000 Carbon Pot .....	.35
Millen Flex. coil (39002) .....	10 / 1.50
PL-55 plugs 50c, PL-68 plugs .....	.75
JK3 Jack (455) 1B, JK35 (PL-68) .....	10 / .49
1 digit counter dials, 1/4" shafts .....	1.25
2 cell penlite bulbs (#222), 3V .....	.65
Grant of Wheat 3V bulb 10c, GE #57, 12V .....	.25
Mazda S-6 115V 6W bulb .....	.10
3000MF 3V electrolytic capacitor .....	.49
TREATITE plate Caps—807 17c, 866 .....	.21
Johnson 210 sock, 65c, 211 sock .....	.35
AN/PRS-1 mine detector .....	39.50
HI-Imped Phone, 2K ohm DC less H-Band .....	.59

## POLY-TECH

919 Dawson St., New York 59, N. Y.  
Tel. Murray Hill 6-2650

man identified as "La Vox de Reelection." (Machwart, Mich.)

**Dutch New Guinea**—Hollandia, 7.125A, noted 0415 with Dutch news, music; good level in Australia. (Sanderson)

**Ecuador**—HC1T2, Salinas, Radiodifusora Costa, is on 6.230 with 300 watts. (WRH Bulletin)

**El Salvador**—YSO, 7.3144, San Salvador, noted in Spanish 2015, music. (Russell, Calif.) YSR, 6.050, San Salvador, broadcasts 1100-0100; YSUA is on 6.250 daily 0700-0000. The short-wave transmitter of Radiodifusora Nacional, San Salvador, is off the air due to damage by fire. (WRH Bulletin)

**Fernando Po**—Construction of the "super-powered" Radio Atlantica has been delayed indefinitely. However, by this time an "improved" transmitter may be on the air; has been operating with low power on 7.200. QRA is P. O. Box 195, Santa Isabel, Spanish Guinea, West Africa.

**Fiji**—A short-wave transmitter is being built at Suva with power of 500 watts; expected to be ready early this year. (Patrick via ISWC, London)

**France**—Paris noted on 5.945A at 1500-1745 sign-off; used both French and Portuguese. (Saylor, Va.) Paris, 6.145, still has German 0130-0145; has Portuguese-French session now 0300-0315 on 6.145 and 7.240. (Bellington, N. Y.) Noted on 11.845 at 2315-2330 sign-off. (Niblack, Indiana) Heard in French on 9.560 at 0030 to after 0100. (Crandall, N. Y.) New Paris schedule for English broadcasts ("The French Have a Word For It") is 0315-0330 on 7.240, 6.145; 1345-1400 on 7.280, 6.200; Sat. and Sun. 0800-0900 on 7.240. (Pearce, England)

**French Equatorial Africa**—Radio Brazzaville, 11.970, noted signing on in French 1000. (Ferguson, N. C.) Noted in English 1745-1800. (Sams, Oregon; Suarez, Md.)

**French West Africa**—Radio Dakar, 15.346, noted 1515 with news in French. (Pearce, England)

**Germany**—Radio Sweden says Radio Free Europe is currently using 6.020, 6.095, 6.130, 9.607 (Lisbon), and 11.735. AFN, 5.470, noted around 1430. Deutschlandsender Berlin, 6.115 and 7.150, heard with music 0215. (Pearce, England)


**Gold Coast**—Accra is scheduled weekdays 0100-0125, 0458-0815, 0943-1300, 1300-1615; Sundays 0100-0815, 0915-1615 (with relays from BBC only); frequencies are 4.915, 6.049. Gold Coast time is 5½ hours ahead of EST from January 1 to August 31. (WRH Bulletin)

**Greece**—Radio Athens, 9.607, noted in English 2046, fair level in N. Y. (Hoffman) Noted on this channel 1430 with English broadcast. (Pearce, England)

**Greenland**—Anmagssalik, 7.575, is heard 1630 and closing 1858; identifies with "God Aften her Gronlands Radio." Also reported testing on 12.300, 15.402. (Short Wave News, London)

**Guatemala**—TGNA officials are considering the possibility of using a fre-
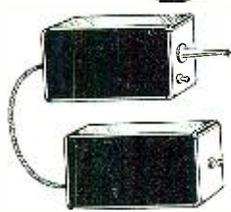
# JUST ARRIVED— 160-80 METER MOBILE RECEIVERS



**HOTTEST ITEM OF THE YEAR!**

MOBILE RECEIVER which will operate in your boat or car from 6 Volts D.C. and will cover the 160 METER BAND, Ship to Shore and Police Bands. Frequency Range 1600 KC. to 2500 KC. Can be used on a fixed frequency only or by slugging will cover its complete frequency range. Comes in 2 separate units; Receiver and External 6 Volt Vibrator Power Supply Unit. The equipment is used, but is in excellent condition complete with tubes.

**PRICE FOR COMPLETE UNIT WITH POWER SUPPLY... \$24.95**

Separate } RECEIVER ..... \$22.50  
Unit } 6 VOLT POWER SUPPLY ..... 7.95

## COAXIAL CABLE


52 OHM Transmission Cable. Made to J.A.N. Specification. 1F549. Same as RG-8U. All unused, on Reels of approximately 1,000 Ft.

100 Ft. .... 9c per Ft.  
1,000 Ft. .... 8c per Ft.  
10,000 Ft. .... 7c per Ft.

## ARC-4 TRANSCEIVER

100-156 MCS. Complete with all tubes and 12 Volt Dynamotor. For Planes or Mobile. 2 Meters. in excellent condition. .... **\$39.95**

## ARC 5 EQUIPMENT:

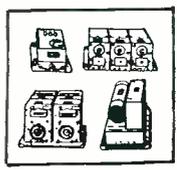

**TRANSMITTERS**  
3 to 4 MCS... \$14.95  
4 to 5.3 MCS... 8.95  
5.3 to 7 MCS... 7.95  
All above complete with all tubes and crystal. In excellent condition.  
T-23 ARC-5 VHF TRANSMITTER—100-156 MCS Chassis. Less Tubes and Crystals. Each **\$12.95**



## PROP PITCH MOTORS

For your Beam Antenna: 20 Volt to 32 Volt. A.C. or D.C. 1/4 H.P. Motor; 1 1/4 RPM Gear Reduction; 7000 to 1. ALL BRAND NEW. Each **\$13.95**



## FL-8 FILTER

Range or Voice for 1020 cycles Audio. Switch mounted on Filter. Excellent for C.W. .... **\$12.25**

## SCR-522 TRANSCEIVER

100-156 MCS—HOTTEST 2 METER BUY OF THE YEAR. VHF MOBILE or FIXED. Complete with all Tubes and 24 Volt Supply. Excellent Cond. .... **\$62.50**

## BC 375 TUNING UNITS

**FREQUENCY RANGES AVAILABLE**  
200 KC-500 KC; 1500 KC-3000 KC; 3000 KC-4500 KC; 4500 KC-8200 KC; 8200 KC-7700 KC; 7700 KC-10000 KC; 10000 KC-12500 KC. With Vernier Dial and many parts which alone are worth 5 times our Low Price of... **\$2.95** per unit

**CAPACITORS • FIXED OIL FILLED**

Solar, Pyranol, C.D., Etc.	
2 MFD. 400 V. D.C.	\$0.79
1 MFD. 600 V. D.C.	.75
4 MFD. 600 V. D.C.	1.25
8 MFD. 600 V. D.C.	1.95
10 MFD. 600 V. D.C.	2.25
1 MFD. 1000 V. D.C.	1.00
2 MFD. 1000 V. D.C.	1.25
4 MFD. 1000 V. D.C.	1.75
1 MFD. 1500 V. D.C.	1.50
2 MFD. 2000 V. D.C.	1.95
3 MFD. 2000 V. D.C.	3.50
4 MFD. 2000 V. D.C.	3.95
2 MFD. 4000 V. D.C.	5.95

**CAPACITORS TRANSMITTING VARIABLE**

K 1 MMFD. to 75 MMFD.	
3/4" Spacing	\$1.95
*D 12 MMFD. to 125 MMFD. 3000 V. Peak	\$3.50
J 28 MMFD. to 110 MMFD. 5000 V. Peak	\$3.95
*F 12 MMFD. to 150 MMFD. 3000 V. Peak	\$3.50
A 7 MMFD. to 80 MMFD. 1500 V. Peak	\$1.00
3 With Nonlinear Vernier Dial.	\$1.00
All New. Hammerlund, Cardwell, Etc.	

**12 VOLT STORAGE BATTERY**

Aircraft Type, 12 Volt, 34 Amp. HR. Made by Exide. Completely enclosed with removable top. Dry Charged. All Brand New. .... **\$14.95**

**WALKIE TALKIE BATTERIES**

BA 37-1 1/2 V-A	\$0.50
BA 38-103 1/2 -B	1.29
Both for	1.50

**TUBES**

8025	\$4.95	8020	\$2.95
3FP7	1.95	6SL7	1.25
5BP4	1.25	6V6	1.25
6S47	1.00	6B8	.75
12SR7	.90	83V	1.25
6AK5	1.20	6SH7	.50
6AK3	1.50	7193	.50
6AC7	1.50	6SN7	1.25
4E27	12.95		

**304TL** ..... **\$7.95**

Pre Amp. for Direction Finder. Contains two tubes. Specify 12 V. D.C. or 24 V. D.C. Excellent Condition. .... Each **\$19.95**


# TAPE

**CANNED FRICTION TAPE, 3/4", 82 1/2 Ft., 6 Rolls to Can, \$1.25 per Can.**

**INDIVIDUAL BOXES**  
RUBBER TAPE, 3/4", 15 Ft., 15c Roll. SCOTCH TAPE, 1", 50 Yds., 35c Can. FRICTION TAPE, 3/4", 82 1/2 Ft., 15c Roll. MICA TAPE, ..... 25c Can.

All Mail Orders Promptly Filled, F.O.B. San Francisco. All California Orders—Add 3% Sales Tax. Do not send postage stamps. Write for our free booklet listing our stock and prices on Radio, Electronics, Hardware, Motors, Wire, Meters, Batteries, Aluminum Sheets, etc. 20% Dep. on all C.O.D. orders. All items subject to prior sale.

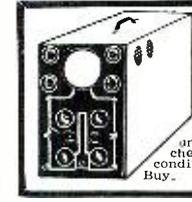**STANDARD SURPLUS** 1230 Market St., San Francisco 3, Cal. Telephone HEMlock 1-3106



## 3" TRIUMPH OSCILLOSCOPE

Complete Test Scope, with built-in Wobbulator, so as to be used on TV or FM servicing. Operates from 110 to 60 V. A.C. Limited Supply. All these units have been carefully checked and are in excellent condition. Buy. **SPECIAL \$34.95 Ea.**

## REVERSIBLE MOTOR

1/40 H.P. Ball-bearing 3450 R.P.M. in Blast-proof case. Needs only a capacitor for starting. All Brand New. 110 V., 60 Cy. Special **\$3.95**

## TANK PERISCOPES

Type M9 Contains 2 glass prisms, one at each end of the periscope. Use them for looking over crowds, at parades, ball games, races, etc., or use prisms separately for optical work. Low Priced. All Brand New. .... **\$1.95**

## SOUND POWERED HEAD AND CHEST SET

Use same way as Hand Set except you have freedom of hands. No Batteries or Power source required for operation. Excellent Condition. Pair **\$11.95**

## SOUND POWERED HAND SETS

TS-10 type — Various manufacturers. No batteries needed for operation. Use in pairs with wire. Audible up to 10 miles. Ideal for TV antenna installations, etc. Excellent condition. Pair **\$17.95**

## GO-9 TRANSMITTER

All brand New. 100 Watts CW, or MCW. emission. Operates from 110 V., 800 Cycle, easily converted to 60 Cycle operation. Low frequency range, 300 KC. to 600 KC. High frequency 3,000 KC. to 18,000 KC. using an E.C.O. We furnish complete conversion data with each transmitter. Complete with schematics. .... **\$59.95**

## 2 VOLT VIBRATORS

VBA Synchronous Type. Used in all portable radios having 2 Volt wet cell supply. All new. .... **\$1.50**

## JEEP GENERATORS

12 Volt DC Output @ 60 Amp. Complete with Voltage Regulator and Ammeter. Ideal for boats, Trucks or Mobile Radio use. Excellent condition. .... **\$39.95**

## MIDGET SELSYNS

AY type operates from 6-12 Volts 60 Cyel. Use as both transmitter and receiver. These compact little units draw almost no current and work fine for all remote position indicating applications. OD 2 1/4 x 2 1/4 x 2". All New (Approx. Wt. 1 lb.). Each **\$2.50**

# Be precise! Buy **PRECISE** you'll save with these top quality kits

The New **PRECISE** Vacuum Tube Voltmeter with the famous PRECISE Reflex Circuit for increased stability and greater accuracy.

By comparison, your best value! 1% Ceramic resistors; Etched panel; Amphenol connectors; Separate 5 V., AC scale; Tubes: 6AL5, 6X5, 6SN7; True zero adjust; 4 1/2" Meter; Three-color rapid construction book explains each step. Complete with btry. & test lead.

Ranges: +DC: 0-5-25-250-500-1000 V.  
-DC: 0-5-25-250-500-1000 V.  
AC: 0-5-25-250-500-1000 V.  
Ohms: Rx1, Rx10, Rx100, Rx1,000, Rx1,000,000 ohms.  
DB: From -20 to +55 DB.

**PRECISE Kit Model \$2598\***  
909-K Factory Wired, Model 909. \$44.98\*

NO OTHER PROBE OFFERS SO MUCH... all PRECISE exclusives... make it the most practical, foolproof and sturdy High Voltage Probe in the industry today.

Multiple insulation; Mechanically shockproof construction; Interchangeable tips; Swivel lead connection; Interchangeable resistors; Triple flash guards; Sturdy, non-porous shell construction.

**PRECISE DeLuxe V.T.V.M.**... Build it horizontally or vertically to fit your own bench requirements. Large 7 1/2" meter for better visibility—greater accuracy.

All the unusual features and ranges of the **PRECISE Model 909 V.T.V.M.** in a DeLuxe version. Complete with btry. & test lead.

**PRECISE Kit Model \$3898\***  
907-K Factory Wired, Model 907 \$57.98\*

New R.F. PROBE Lowest Price in the field! Leads in Value!

Time-tested circuit; Special non-porous case; Uses germanium crystal rectifier up thru 250 meg. Probe handle terminated in an amphenol connector—other end of shielded cable available in either amphenol, phone plug or phone tip type fitting at no added charge.

All instruments carry the **PRECISE** Guarantee, components protected by the RMA Warranty. Write for FREE Catalog N-1. SEE THE COMPLETE PRECISE LINE AT YOUR JOBBER NOW! \*Prices slightly higher in the West. EXPORT DEPT.: 15 Moore St., New York, N. Y., Cable "Minthorne."

**PRECISE Model 912 \$425\***  
(Wired only)



**PRECISE PRECISE DEVELOPMENT CORP.**  
An Engineered Product Oceanside, L. I., New York

**\* HEAT DISSIPATING CONNECTORS**

**Vacuum Tube Accessories by Eimac — Now Available!**

Type HR heat dissipating connectors are designed to provide an efficient method of heat transfer from tube elements and seals to the air. Also facilitate electrical connection to plate or grid leads of most popular transmitting tube types. Machined from solid dural rod, come complete with necessary machine screws for use.

**\* Write for new Eimac Catalogue Summary showing Eimac tubes and other accessories.**

**Eitel - McCullough, Inc.**  
San Bruno, California

**SPECIAL! HANDY KIT**

FOR **EXPERIMENTAL WORK**

EL-MENCO CMI5 Capacitor Kit consisting of 5 each of 46 capacities of miniature silvered mica ranging from 1 mmf. to 510 mmf.

Actual Size 9/32" x 1/2" x 3/16" For Television, Radio and other Electronic Applications.

2 - 420 mmf. cap. at 500v DCA.  
2 - 535 mmf. cap. at 300v DCA.  
Temperature Coefficient ±50 parts per million per degree C for most capacity values. 6-dot color coded.

**DON'T GET CAUGHT SHORT . . . Always Have The Correct Capacity On Hand!**

THESE MINIATURES FIT INTO THE SMALLEST AREA CAPACITOR SIZE (9/32" x 1/2" x 3/16").

Packed in moisture-proof transparent cellophane envelope, properly identified for permanent use.

**ARCO ELECTRONICS INC.**  
103 Lafayette St., N. Y. 13, N. Y.

quency in the Tropical Band (between 3-4 megacycles) for Spanish transmissions—to effect less spread of the signal to outside areas as well as because of less congestion on that band; has been using approximately 5.952; has received quite favorable reports on reception on the new 11.85 channel—used for *English* daily 2200-2230 (extended to 2300 on Wednesdays when last 30 minutes is Mail Bag session) in parallel with 9.668; several alterations and adjustments have had to be made to the new 11.85 transmitter. TGNA appreciates reports and will verify all correct ones. (Russell, Calif.)

**Haiti**—4VEH in verifying for Bel- lington, N. Y., sent this schedule for its 9.710 outlet—*English* daily except Sun- day 0600-0630, 0730-0815; Spanish 0630-0730; Sunday schedule is 0630-0700 Spanish; 0700-0830 *English*; 1730-1830 Spanish; 1830-1915 *English*; 1915-2000 Creole; 2000-2030 Spanish; 2030-2100 *English*. Power is still 800 watts and a station official said "it looks like it will be quite some time before we can get on 10 kw." QRA is Box 1, Cap-Haitien, Haiti.

When this was compiled, 4VRW was "on the move" again; noted on 9.870, 9.878, then on 9.96, and still later on 9.24. (Oskey, N. J.; Stark, Texas; Bel- lington, N. Y.)

**Holland**—Hilversum now uses 6.025 in parallel with 9.59 to North America weekdays 2130-2210; for "Happy Sta- tion Programs" Sundays 2130-2300.

**Honduras**—HROW, 6.660, Tegucigal- pa, noted with good signal around 2200 and later. (Ferguson, N. C.) HRN, 5.870, Tegucigalpa, noted signing off 2230 recently. (Stark, Texas)

**Hong Kong**—ZBW3, 9.524, noted 0700 with news. (Machwart, Mich.)

**Hungary**—Saylor, Va., reports Buda- pest noted signing on 1800 recently on 6.023A; caused QRM to ELBC, 6.025, Monrovia, Liberia.

Budapest is using 6.247A in parallel with 7.220 and 9.833A (has dropped 11.910) for *English* programs to North America evenings (EST); takes some relays from Moscow.

**India**—AIR's External Services schedule received airmail is—*To East and South-East Asia and Australia and New Zealand*—1930-2000, 15.290, 11.850; 2030-2200, 15.160; 17.740; 0200-0330, 21.510, 17.830; 0600-0815; 17.740, 15.190; 0830-0945, 17.740, 15.290. *To Middle East, Central Europe, United Kingdom, Burma, and Philippines*—0200-0330, 21.510, 17.830; 0230-0330, 17.740, 15.190; 0600-0700, 17.740, 15.190; 0830-0945, 17- 740, 15.290. *To China, Japan* (Sat. and Sun. only)—0530-0600, 17.705, 15.160. *To East and South Africa, Mauritius*— 2300-0015, 17.740, 15.160; 1045-1215, 15.290, 11.710. *To West Indies*—1830- 1930, 15.290, 11.850, 9.575, 7.170. *To Burma*—1945-1955, 11.710, 9.720; 0615- 0700, 21.660, 15.160. *To China*—0430- 0545 (to only 0530 Sat., Sun.), 17.705, 15.160. *To Indonesia*—1745-1800, 11.790, 9.720; 0700-0730, 21.660, 15.160. *To East and South-East Asia*—1930-2000, 15.290, 11.850; 2030-2200, 17.740, 15.160; 0200- 0330, 21.510, 17.830; 0600-0815, 17.740,

15.190; 0830-0945, 17.740, 15.290. *To Fiji*—0200-0330, 21.510, 17.830. *To West Pakistan*—2245-2300, 11.850, 9.590, 7.120, 6.150; 0945-1000, 5.970, 4.940. *To Afghanistan*—2215-2230, 9.620, 7.225; 0030-0130 (Fri. only), 9.565, 7.225; 0845-0930, 4.940; 1130-1230, 9.720, 5.990, 4.940, 3.435. *To Persia, Afghanistan*—1230-1330, 9.720, 7.155, 5.990, 4.940. *To Saudi-Arabia, Egypt, Lebanon, Syria, North Africa, Jordan, Sudan*—2230-2315, 15.210, 11.760; 0000-0045, 17.760, 15.210; 1230-1430, 9.550, 7.125. *To East and South Africa, Mauritius*—2300-0010, 17.740, 15.160; 1045-1215, 15.290, 11.710. *To Europe*—1400-1500, 9.720, 7.170; 0230-0330, 17.740, 15.190. *English* news is at 1400-1410, 9.720, 7.170; 1930-1945, 11.850, 15.290; 2315-2330, 17.740, 15.160; 0300-0310, 17.740, 15.190; 0830-0840, 17.740, 15.290; 1045-1100, 17.740, 15.290.

*Indo-China (Vietnam)*—"The Voice of Vietnam" in Saigon is broadcasting on three channels now—9.620, 12 kw., 6.180, 1 kw., at 1800-1900, 2300-2400, 0500-0830 in Vietnamese; 0830-0900 in *English*; on 7.090, 12 kw., at 1800-1900, 2300-2400, 0500-0830 in various languages; in French at 1800-1830, 2330-2400, 0615-0730; in *English* at 0800-0830. *Radio Hue, 7.205*, Hue, is scheduled now 1830-1900, 2130-2230, 2300-2345, and 0200-0300, 0500-0730; news in French 2330-2345. (*WRH Bulletin*) Noted on 7.0912 with news 0845. (Russell, Calif.)

*Radio France-Asie, 9.754*, Saigon, is noted at good level from 0900 to close-down 1030 or 1033; all-French programs, woman announcer; not in parallel with 11.83 which has *English* and bi-lingual programs at 0900-1030 close-down. (Ridgeway, South Africa)

*Iran*—Teheran, 15.100, still noted with short newscast 1500. (Pearce, England)

*Iraq*—Baghdad, 11.724, noted with news 1415, good signal at that time (since *Radio Pakistan* leaves 11.726 at 1415); QRM is "terrific" prior to 1415; also has QRM from Hilversum on 11.73. (Ridgeway, South Africa) Normal closedown is 1500. (Radio Australia) Noted in Arabic 0100. (Bellington, N. Y.)

*Israel*—Tel-Aviv, 9.010A, still noted in *English* to 1700A sign-off. (Alcock, Ky.)

*Italy*—At the time this was compiled, Rome was making several frequency changes. Heard signing on 0300 on 9.575, 11.81. And on 7.11 with Portuguese at 1615. (Bellington, N. Y.) Noted calling Great Britain-Ireland in *English* 1350-1435 on 6.010, 9.575. (Pearce, England)

*Italian Somaliland*—*Short Wave News*, London, says an experimental station is operating from Mogodishu on 7.420 at 1200-1300; all programs are in Italian and consist of Italian music, songs, and news; opens and closes with announcement "Transmette Mogodishu. . ."

*Jamaica*—*Radio Jamaica*, 3.360, noted signing off 2301 with "God Save the King." (Machwart, Mich.)

*Japan*—JO8G, 6.0053, Tokyo, noted around 0115. (Russell, Calif.) AFRS,

High-Fidelity • TV • Radio  
Phonographs • P.A. • Parts  
Test Equipment • Tools • Books  
Ham Gear • Electronic Tubes



31st year

# New Lafayette e Catalog NOW READY!

IMMEDIATE  
SHIPMENTS

☆  
COMPLETE STOCKS

☆  
TECHNICAL SERVICE

☆  
30-DAY MONEY BACK  
GUARANTEE



A practical encyclopedia used by economy-minded servicemen, hams and technicians throughout the world because they know they have a complete "one-source" guide. For quality equipment, for hard-to-get items, for nationally-advertised merchandise, for low prices, it's Lafayette.

*Lafayette*

DIV. RADIO, WIRE, TELEVISION, INC.

**RADIO &  
TELEVISION**

**RUSH THIS COUPON AT ONCE**

VISIT LAFAYETTE  
SHOPPING CENTERS  
at

100 Sixth Ave.  
New York 13, N. Y.

•  
110 Federal St.  
Boston 10, Mass.

•  
24 Central Ave.  
Newark 2, N. J.

•  
542 E. Fordham Rd.  
Bronx 58, N. Y.

Lafayette Radio, Dept. RA  
100 Sixth Avenue  
New York 13, N. Y.

**FREE!**



*I need the 1952 catalog. Please rush!*

Name.....

Address.....


City..... Zone..... State.....

PASTE ON POSTCARD

# TRIAD

## High-Fidelity Output Transformers
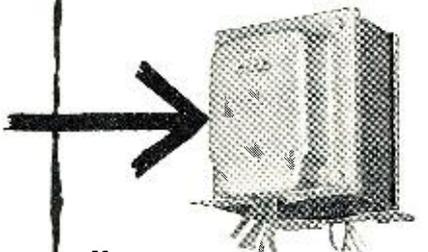
### Give you Highest Performance at LOW COST!



HIGHEST PERFORMANCE is assured when using Triad high-fidelity output transformers through the use of highest quality core material and interleaved windings of low resistance. LOW COST is maintained by use of mass produced die-stamped cases and flexible leads. Coils have a frequency response within 1 db from 30-15,000 cycles; deliver full-rated output within 3 db over entire frequency range. These transformers, having high open circuit inductance and low leakage reactance, may be used in feedback circuits having as much as 30 db of neg. feedback.

#### Compare these Specifications and Prices

Type No.	Primary Impedance	Secondary Impedance	Output Watts	List Price
S-31A	8000 C.T.	4-8-16	15	10.50
S-32A	8000 C.T.	500/250/125	15	11.00
S-33A	3000 C.T.	4-8-16	15	10.50
S-35A	5000 C.T.	4-8-16	18	11.50
S-36A	5000 C.T.	500/250/125	20	12.00
S-38A	9000 C.T.	4-8-16	25	15.20
S-39A	9000 C.T.	500/250/125	25	16.00
S-40A	2500 C.T.	4-8-16	30	15.20
S-42A	4500 C.T.	4-8-16	50	21.25
S-45Z	4000/2000/4-8 1000/500		10	5.80
S-46A	2000/1000/4-8-16 500/250		20	12.95

These Triad High-Fidelity Output Transformers afford a standard of performance second only to Triad's "HS" Series.

Write for Catalog  
TR-51

**TRIAD**  
TRANSFORMER MFG. CO.

2256 Sepulveda Blvd.  
Los Angeles 64, Calif.

Tokyo, noted on 9.605, 11.825 at 0150 with music. (Bellington, N. Y.) "Voice of the United Nations Command," Tokyo, heard opening 0655 on 6.015 in *English*; announced 7.257 and 9.505 as parallel; runs to 1000 sign-off. (Rosenauer, Calif.) BCOF, 6.105, Kure, sent interesting card; said 1470 kc., 200 watts, and s.w. 6.105, 1 kw., operate daily 1630-0900. (Dary, Kans.)

*Kenya Colony*—Nairobi, 4.855, has local news 1315. (Pearce, England)

*Korea (South)*—HLKA, 7.934, has been heard at fair strength around 0630 lately. (Radio Australia)

*Labrador*—VONW, Northwest River, shares 3.480 with a new station at Nain, Labrador, on irregular schedule; low-powered. (Peddle, Newfoundland)

*Lebanon*—Saylor, Va., reports Beirut noted on 15.600 with a French program at 1335; fair level. Ridgeway, South Africa, notes the 8.036A channel ending *English* period 1100. *English* session begins 1100, says Pearce, England. This outlet is heard in Mass. at 1550 with news in French, signing off 1600, according to Harris.

*Malaya*—BFEB, 9.690, Singapore, noted signing off 0615. (Ferguson, Va.)

*Martinique*—Radio Martinique, Fort-de-France, radiates on 9.700 weekdays 0530-0630, 1115-1345 (Sat. to 1430), 1730-2015 (Sat. 1700-2100); Sundays 0630-0800, 1115-1430, 1700-2015; news in French 0600, 1200, 1900 (relayed from Paris). (WRH Bulletin)

*Mauritius*—Ridgeway, South Africa, flashes that V3USE, Forest Side, is back on its old channel of 15.053A after having tried 11.84 and 12.12 for a short time. It still has QRM although sometimes is good level and in the clear in South Africa. Schedule is weekdays 2200-0015, 0300-0430, and 0930-1230; French news 1045; signs off with "God Save the King"; has French announcements but uses some BBC-transcribed programs for its English-speaking audience.

*Mexico*—Widely reported of late is XWKW, "Radio Morelia," measured by Russell, Calif., on 6.3017; signs off 2330. Heard from before 1800 by Stark, Texas.

XESC, Mexico City, seems to be operating now near its original frequency of (announced) 15.205; was measured 15.206 at 1005 recently. (Ferguson, N. C.) Had been as high as 15.220A at times.

*Monaco*—Monte Carlo noted signing off 1745 on 6.035 in French. (Rodger, Scotland)


*Mozambique*—CR7AA, 11.764, Lourenco Marques, noted starting 2300 in *English*; poor to fair signal; announces "For happy listening from 6 in the morning 'till 11 at night." (Niblack, Indiana) Lourenco Marques is noted by a British listener on 15.270 to 1500 closedown. (Radio Sweden) Heard on 4.920A at 1030-1045 in *English*; weak level. Rosenauer, Calif.) This outlet noted in England 1245 with commercial program. (O'Sullivan)

*New Caledonia*—Noumea, 6.035, noted in French news 0345. (Saylor, Va.)

*Norway*—LLM, 15.175, Oslo, noted



### New Series "G" Amplifiers

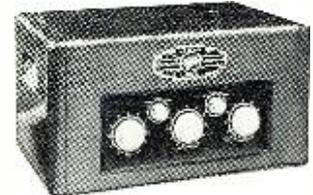

CATALOG NO. 5551

## PRECISION ELECTRONICS INC.

643 MILWAUKEE AVENUE CHICAGO 22 ILLINOIS

### SURPLUS BARGAINS

RELAYS, 24 VDC, P. R. Mallory, 150 and 90 ohms. breaks one contact makes one. 25c ea., 5 for \$1.00.

RELAYS, 24 VDC, P. R. Mallory, 150 and .5 ohms, breaks one makes three, 25c ea., 5 for \$1.00.

RHEOSTATS, 100 ohms, 10 watt, screwdriver shaft, 8c ea., 15 for \$1.00.

MICRO SWITCHES, Type AHG 200, encased, normally open, 35c ea., 3 for \$1.00.

SOLENOIDS, 24 Volts, Cannon Elec. Mfr., plunger travel 3/4", strong pull, wt. 1 lb., 5 for \$1.00.

3 WAY SWITCHES, H&H, for under panel mounting, rotary, pointer knob, 10c ea., 12 for \$1.00.

I. F. TRANSFORMER ASS'Y, 5 m. e., 2nd limiter wired, ceramic base, used on receiver R-190, \$1.25 each.

TOGGLE SWITCH GUARDS, Cutler & Hammer, prevents accidental tripping of switch. 6 for 25c.

CARTRIDGE FUSE CUTOUTS, porcelain base, 30c ea.

ELECTRICAL COTTON SLEEVING, colors of red, blue, black, green, yellow, 5/32", 1 lb. 500 ft. spool \$1.00, 5 lb. 2,500 ft. spool, red or white, \$4.00 spool.

MAGNET WIRE, Formvar, No. 17, 85 ft. 8 oz. coil, 30c.

MAGNET WIRE, paper covered enamel:

No. 19, 165 ft. 13 oz. coil, 45c.

No. 19, 130 ft. 10 oz. coil, 35c.

No. 18, 130 ft. 12 oz. coil, 35c.

No. 17, 85 ft. 8 oz. coil, 25c.

STEEL TOOL OR PARTS CHESTS, new Navy surplus, sturdy spot weld constr., with side handles and hasp, painted grey, approx. wt. ea. 14 lbs., in following sizes:

18"x12"x9" ..... \$4.50

18"x12"x6" with partition ..... \$4.25

16"x12"x6" with partition ..... \$4.00

18"x 9"x6" with partition ..... \$3.75

12"x12"x6" with partition ..... \$3.50

Include sufficient postage, excess will be refunded.

### STUART SALES

6402 Pittsburgh Ave.

Detroit 10, Michigan

0600-0700, 0800-0900, replacing LKV, 15.170; latter is still used afternoons but normally is covered by TGWA. (Legge, N. Y., via NNRC)

**Pakistan**—The news from *Radio Pakistan* is now being heard 0730 over 7.096A, 7.147A, and 15.620. (Stark, Texas; Boord) *Radio Pakistan* was recently measured on 11.673 at 0850; announced in *English* 0915 and continued with Burmese program. (Ferguson, N. C.) Open 0830 to Burma.

Dacca, 15.620, noted with news 0210-0220; Karachi, 7.010, 11.726, noted with *English* at dictation speed 1210-1230; on 11.675 with news 1015-1030. (Pearce, England)

**Panama**—HO50, 6.045, Panama City, noted 2330 with orchestral selections; giving slogan of "Transmitte Radio Programs Continental" at 0000, with sign-off 0002 after anthem. On another occasion was heard to after 0200. (Russell, Calif.) HOQQ, Panama City. *Radio Nacional*, is on 6.140 daily 0700-2200; all-Spanish programs but gives some announcements in English also. (*WRH Bulletin*)

**Paraguay**—*Radio Nacional de Paraguay*, 6.270, noted to after 2030; listed ZPA, 6.275. (Stark, Texas)

**Peru**—*Radio Nacional del Peru*, 9.560, noted to after 2215; calls given are OAX4A, OAX4T, and OAX4Z. Has bad QRM before 2200; OAX4Z, 5.880A, is in parallel; another night both 5.880A and 9.560 were noted going after 2300. (Stark, Texas) The measured 9.5607 outlet is "supposed" to be the new 50 (Continued on page 146)

### WORTH PUTTING ON YOUR WINDOW

A STEP forward towards a better understanding of the serviceman by the consumer was a recent national advertisement by Sprague Products Company. Entitled, "Are Servicemen Gyps?", the ad reflects the anxiety of many consumers towards their local TV servicemen.

In this advertising message to the consumer, Harry Kalker, President of Sprague Products Company, completely belittles the arguments often made against servicemen. Mr. Kalker points out that the people who complain about high priced servicemen are the same ones who accept the excessive charges placed on them by the garageman, the medical specialist and the lawyer. The ad fully states the case of the reputable television technician in the following quote:

"Servicemen are not fly-by-night businessmen. Ninety-nine out of 100 radio-television servicemen run their businesses properly. The other one per cent—the gyps—can usually be spotted a mile away. Nine times out of ten, they are the shops that feature 'bargain' prices and ridiculously liberal service contracts. And their victims are generally set owners who expect to beat the game by 'getting something for nothing.'"

Giant window size reprints of their advertising message will be sent to you upon request by Sprague Products Company, North Adams, Massachusetts. Enclose ten cents to cover handling and postage.

## Our New Year's Resolution to You . . . HIGHEST QUALITY AT LOWEST PRICES!

Make Steve-El your headquarters for everything in electronics . . . and save big money!

### Brand New Standard Brand Tubes

Individually Boxed and Guaranteed

0Z4	.59	6BN6	1.32	7J7	1.19
1A3	.89	6BQ6	1.44	7K7	1.19
1A6	.89	6C4	.72	7L7	1.19
1A7	.98	6C5	.79	7N7	.99
1B3	1.02	6C6	.85	7Q7	.89
1B5 255	1.09	6C86	.86	7T7	1.19
1H5	.89	6CD6	2.49	7Y4	.86
1J6	.74	6D6	1.09	7Z4	.84
1L4	.79	6D8	1.39	12A5	.79
1LA4	1.12	6F6	.88	12A8	.86
1LA6	1.12	6F8	1.49	12A15	.86
1LC5	1.12	6H6	.56	12AT6	.65
1LC6	1.12	6J5	.79	12AT7	1.09
1LN5	1.12	6J6	1.09	12AUG	.89
1M5	.87	6J7	.81	12AUF	.96
1N5	.87	6K6	.66	12AV6	.79
1R5	.82	6K7	.74	12AV7	1.24
1S5	.79	6L5	1.39	12AX7	.99
1T4	.83	6L6GA	1.69	12BA6	.79
1U4	.79	6L7	1.19	12BE6	.79
1U5	.78	6M7	1.19	12H5	.89
1V2	.69	6Q7	.88	12J5	.79
1X2A	.96	6S4	.76	12Q7	.79
2A4G	.84	6SA7	.76	12SA7	.77
2A5	.84	6SF7	.99	12SJ7	.78
2A4	.89	6S07	.89	12SK7	.77
3Q4	.89	6S17	.89	12SL7	1.09
3Q5	1.02	6SJ7	.76	12SN7	1.09
3S4	.88	6SK7	.79	12SQ7	.68
3V4	.99	6SL7	1.19	14A7	1.03
5U4	.65	6SN7	.89	14B6	1.03
5V4	1.10	6SR7	.86	14B8	1.03
5W4	.83	6SQ7	.72	14N7	1.05
5Y3	.47	6T8	1.19	14R7	1.02
5Y4	.75	6V6	1.69	14W7	1.09
5Z3	.89	6V6GT	.86	19T8	1.34
5Z4	1.12	6W4	.66	25A6	1.09
6A3	1.59	6W6	.89	25B06	1.49
6B7	1.49	6X7	.74	25L6	.58
6AC7	1.21	6X5	.74	25W4	.85
6AF6	1.18	6Y6	.96	25Z6	.74
6AC5	.86	7A4	.89	32L7	1.49
6AC7	1.59	7A5	.99	35L6	.86
6AH5	1.49	7A6	.86	35W4	.59
6AK5	1.49	7A7	.86	35Y4	.58
6AL5	.68	7AD7	1.92	35Z5	.57
6AQ5	.72	7AF7	.89	47	1.34
6AR5	.67	7AG7	1.05	50A5	.96
6AS5	.99	7B5	1.05	50B5	.86
6AT5	5.39	7B6	.89	50C5	.86
6AT6	.68	7B8	.99	50L6	.72
6AUS	1.59	7C4	.79	50Y6	.99
6AU6	.76	7C5	.89	56	.66
6AV6	.67	7C6	.99	70L7	1.69
6BA6	.69	7E5	.99	77	.89
6BA7	1.16	7E6	.99	80	.79
6BC5	.86	7F5	.99	11L6	.79
6BE6	.82	7F7	.99	11Z73	.78
6BG6	1.76	7G7	1.21	20S1	1.22
6BH6	.86	7H7	.96	11N7	1.79

### ALL-AMERICAN 5-TUBE KIT

50L6, 35Z5, 12SA7, 12SQ7, 12SK7  
Standard Brands only \$3.60 complete

### TV PICTURE TUBES

All black faced—Non glare SHELDON, ZETKA, and other famous makes. All Guaranteed.

10BP4A	\$21.95	17BP4	\$22.90
12LP4A	22.95	17HP4	24.95
14BP4	21.95	19AP4	32.95
16HP4	28.95	19CP4	32.95
16KP4	28.95	19DP4	29.50
16GP4	30.95	20CP4	32.95
16LP4	32.95	24AP4	65.50

### SPECIAL MONEY-SAVING BONUS FOR QUANTITY PURCHASES

5% off on 25 tubes or more  
10% off on 100 tubes or more

#### MODEL IT5



#### TV & FM BOOSTER

Dimensions:  
Height 5 1/2" —Width 7 3/4" —Depth 7"

Simple To Operate  
All 12 TV Channels  
One Knob Control  
Easy To Install  
Continuous Tuning

- Improves TV reception in weak signal area
- Permits use of indoor antenna in many locations
- Reduces noise and "snow" effects
- Reduces electrical and diathermy interference
- Minimizes "Ghosts"

**\$15.95**

LIST PRICE \$32.95

### FREE—WRITE FOR OUR NEW BARGAIN CATALOG

Terms: 20% cash with order, balance C.O.D. Prices F.O.B. N. Y. City warehouse. Min. order \$5. (Allow for postage.) Prices in this ad supersede all others published.

### STEVE-EL ELECTRONICS CORP.

Dept. N-1, 61 Reade St., N. Y. 7, N. Y., COrtlandt 7-0086

Visit Our New Store

World's Finest

## TELEVISION RECEIVER

\$141<sup>50</sup> Less C.R.T.



### The Famous 630 TV CHASSIS

The New and Improved Super Famous "630" T.V. Chassis. Is a 30 tube high quality television receiver (including 3 rectifiers) manufactured under license by the Radio Corporation of America. The "630" Television Chassis is universally recognized by leading electronic engineers as the highest standard of television excellence. This chassis is the standard by which all other T.V. chassis are measured.

Standard R.M.A. Guarantee! FREE replacement on all defective tubes and parts.

**FEATURES:** 1. Full channel coverage. 2. Discriminator-type FM sound system. 3. Improved picture brilliance. 4. AFC horizontal hold. 5. Keyed AGC. 6. Stabilized vertical hold. 7. 3 stage sync. separator and clipper. 8. Automatic brightness control. 9. 4Mc band width. 10. Highest quality parts used. All tubes standard nationally. 11. Finest for Fringe area reception.

Focus: Adapted for all Cathode Ray tube sizes and types.

Sweep Deflection: For 16", 17", 19", 20", 24" tubes. Perfect for Fringe Area Reception—Will work where most sets fail to operate.

With HiGain standard coil tuner and R.C.A. Hi-Fi 12" Speaker. Complete with knobs and hardware. Complete with Fed. Taxes Paid. Less **\$141.50**  
Cathode Ray Tube . . . . .

**630 DX Chassis**—Extra power for fringe areas. Can be operated without booster or complicated antenna. Complete with Fed. Taxes Paid. Less **\$151.50**  
Cathode Ray Tube . . . . .

Mounting Brackets for above chassis. . . . . \$4.95



### NATIONALLY ADVERTISED AUTOMATIC RECORD CHANGER

Series 100

Made by well known mfr. and only introduced on the market a few months ago as one of their latest models. Plays 12, 10 or 7 inch records at 33 1/2, 45 or 78 R.P.M. New spindle carefully lowers unplayed record stack. Balanced arm assures light needle pressure and long wear. Needle-tip (included) for standard or micro-groove records. Inside-out records played without any adjustment. Pickup arm comes to rest position after last record has played. Complete factory packed and sealed record changers, normally listing at \$47.50. LIMITED QUANTITIES. . . . . **\$24.79**

# NOW YOU'LL Really Know How to Use 'Scopes!



Don't let the oscilloscope "stump" you! Learn to use it fully on all sorts of jobs—and watch your efficiency soar!

## MODERN OSCILLOSCOPES AND THEIR USES

BY JACOB H. RUITER, JR.  
of Allen B. DuMont Laboratories, Inc.  
326 pages, 370 illustrations, \$6.00

Here at last is a book that makes it easy for you to become expert in the many uses of the greatest, most versatile service instrument of all—the oscilloscope! It contains no involved mathematics. First, the author explains oscilloscopes fully—then gets right down to earth in telling exactly how to use them on AM, FM and TV service work . . . from locating receiver troubles to aligning and adjusting the most complicated circuits.

### HOW THEY WORK

Expert knowledge of oscilloscopes helps you work faster, far more accurately and more profitably on all sorts of service and laboratory jobs. Basic subjects covered include: 1—Introduction to Oscilloscopes; 2—History of the Oscillograph; 3—Development of the Cathode Ray Tube; 4—Principles of Cathode Ray Tube Operation; 5—Details of the Modern Cathode Ray Tube; 6—The General-Purpose Oscilloscope; 7—Power-Supply Circuits; 8—Amplifiers, Attenuators and Positioning Circuits; 9—Time-Base Circuits.

### HOW TO USE THEM ON THE JOB

Each operation is carefully explained including the making of connections, adjustment of circuit components, setting the oscilloscope controls and analyzing patterns. About 400 illustrations including dozens of pattern photos make things doubly clear. Here are the specific how-to-do-it subjects covered: 10—Operation; 11—Interpretation of Basic Patterns; 12—Auxiliary Equipment; 13—Typical Applications in Electronics; 14—Servicing A-M Receivers; 15—Servicing F-M Receivers; 16—Television Receiver Servicing; 17—Use of the Radio Transmitter; 18—Using the Oscilloscope in Teaching; 19—Additional Industrial Uses; 20—Photographing Cathode Ray Tube Patterns; (a) Glossary.

Send coupon today!

READ IT 10 DAYS . . . at our risk!

Dept. RN-12, RINEHART BOOKS, Inc.,  
Technical Division,  
232 Madison Ave., New York 16, N. Y.

Send MODERN OSCILLOSCOPES AND THEIR USES for 10-DAY FREE EXAMINATION. If book is satisfactory, I will then send you \$6.00 promptly in full payment. If not, I will return book postpaid in good condition and owe you nothing.

Name .....

Address .....

City, Zone, State .....

Employers' Name and Address .....

Price outside U. S. A. \$6.50, cash only.  
Money back if you return book within 10 days.

126

## Beat-Frequency V.F.O.

(Continued from page 49)

dial. The dial can contain scales for each harmonically related amateur band and, providing good trimming and tuning condensers are used, can be relied upon for repeat performance. If good frequency standards are available, the unit may be accurately calibrated and employed as a secondary standard thereafter.

The normal output of the v.f.o. was designed to be equal to that of the average crystal oscillator. Where higher output may be desired there is no reason why a cathode follower of higher output cannot be employed. Since the output impedance of a follower is about  $1/G_m$ , there is also no reason why the output impedance cannot be changed if desired. The output power of a cathode follower operating class A is substantially 25 per-cent of the d.c. plate input power. Since operation is potential up to the grid of the cathode follower, there are no reactions due to sudden changes in loading such as keying and hence the r.f. regulation of the unit is excellent.

The unit is keyed by simultaneously breaking the cathode circuits of both the adder and cathode follower. Impedance match to the cathode follower is obtained by proper coupling of the small coil attached to the far end of the 300 ohm line to the input tank of the amplifier or multiplier to be used in the following stages of the transmitter.

In normal operation of the station, the oscillators are allowed to run continuously as the power consumed is negligible. The plate voltage of the oscillators only is regulated at 150 volts through use of a 0D3/VR150, as indicated in Fig. 2. Only the simplest kind of power supply is necessary or one supplying unregulated, 300 volts d.c. plate and 6.3 volts a.c. heater supply. With the unit continually warmed up, there is no question about its being instantly available for break-in service at the desired frequency.

In the model described, the panel size was  $1\frac{1}{2}$  inches long by 6 inches high. The chassis was 9 inches wide, 6 inches deep, and 2 inches high. Two cans, each 6 inches long, 4 inches high, and  $2\frac{3}{4}$  deep, were used for the oscillators and adding stage. Cans and chassis were constructed from 3/32 inch aluminum.

The design of this model does not necessarily have to be followed religiously. Now that the circuits have been proven, conventional chassis construction could be used. The oscillator and adder coils could be mounted in individual cans similar to those used for i.f. transformers with the trimmers mounted in the top of each can. The tuning condensers could be mounted above chassis as in conventional receiver design. Tubes could be spaced sufficiently from the coil cans to prevent undue heating of the cans. —30—

## STAN-BURN E-PARKS

CONDENSER SPECIALS BY PASS—ALL GUAR- ANTEED	SPEAKER SPECIALS ALL GUARANTEED
20x20-150 Stan Burn. \$0.41	4" P.M. .... \$1.64
50x30-150 Stan Burn. .49	5" P.M. .... 1.75
20x150 Stan Burn. .32	6" P.M. .... 2.41
8-450 Stan Burn. .41	8" P.M. .... 3.41
16-450 Stan Burn. .49	12" P.M. .... 6.33
4 Prong Vibrators each \$3.29	4x6 P.M. .... 2.19
Lots of 12 or more. 1.19	6x9 ..... 3.73
Standard TV Tuners. \$18.95	5x7 ..... 3.43
	10" P.M. .... 5.48

### NEW for '51 AUTOMATIC RADIOS



\$59.95  
List Price

Each auto radio is specifically designed to fit all 1949, 1950 and 1951 cars for Ford, Plymouth, Dodge, Chevrolet, Hudson, Henry J and Studebaker. All incorporate the same outstanding features: Six-tube superheterodyne. Six-volt storage battery operation. Two dual-purpose tubes. Eight-tube performance. Installation in a few minutes. Three-gang tuning condenser and tuned R.F. stage for extreme sensitivity. Permanent magnetic dynamic speaker with Powerful Alnico No. 5 magnet. Low battery drain. Weight 10 lbs.

### ATTRACTIVE DISCOUNTS TO DEALERS

CHASSIS 630 K3B Video Product. . . . \$139.50

### CATHODE RAY TUBE SPECIALS

71P4 ..... \$15.00	16RP4A ..... 26.00
10BP4 ..... 14.95	17BP4A ..... 27.00
12LP4 ..... 19.95	20CP4 ..... 39.95
12LP4A ..... 19.95	19AP4A ..... 47.95
14BP4 ..... 19.95	19DP4A ..... 47.95
16DP4A ..... 26.00	24AP4A ..... 73.00
16BP4 ..... 33.00	Single ion traps. .... .39
16AP4A ..... 39.00	Double ion traps. .... .58

### RAM TRANSFORMERS

RCA type for 16" to 24"	X032 ..... \$3.85
G.E. type for 16" to 24"	X045 ..... \$3.85

These are very special prices while they last!

### 70° DEFLECTION YOKES

Todd wired replacement for RCA, G.E., etc. Special \$3.85

### ANTENNAS

Conical, less mast, 10 element	..... \$ 2.98
Circle X, less mast	..... 2.98
Double V, less mast	..... 2.98
Chinney Masts—1-12	..... .95
12 or more	..... .89
100 ft. roll strapping	..... 2.98
Mast standoffs	..... 1.93
10 ft. masts, each	..... 1.58
12 or more, each	..... 1.49
55 mil. 300 ohm wire white or black, 1000 ft.	19.97

AUTHORIZED DISTRIBUTORS for: General Electric, Kenrad, Tung-Sol, National Union Jewel, De Wald, Regal, Automatic and Satchel Carlson.

We carry a complete line of popular makes of Radio and TV tubes, at 50% discount. Also many other special purpose and transmitting types, and all electronic parts and equipment at lowest prices. Send us a list of your requests for quantities and prices.

Terms: 20% with order. Balance C.O.D. All prices FOB, NEW YORK Warehouse. Minimum order \$5.00.

Write for our latest price list to Dept. RN-1

**STAN-BURN RADIO and ELECTRONICS CO.**  
(C.B.S. THEATRE BLDG.)  
1697 BROADWAY • NEW YORK 19, N.Y.

## F. C. C. COMMERCIAL RADIO OPERATORS LICENSE

Critical Shortage of Licensed Operators Exists!!

A wonderful future is yours with an F. C. C. commercial radio telephone or telegraph operators' license leading to well-salaried jobs in aviation, broadcasting, transportation and civil service. Sensational new simplified HOME STUDY COURSE teaches you in shortest possible time at lowest possible cost. NO OTHER COURSE LIKE IT! Proven valuable during World War II in speedily training thousands of men; eliminates tedious schooling, exam papers, poring over books. Each page of text directly related to official F. C. C. exam questions, thus assuring you of all theory requirements.

The entire up to date course, nothing else to buy, containing 230 pages of complete material, diagrams, etc., yours for only \$9.95. Send check or money order; or pay postman \$9.95 upon receipt plus C.O.D. charges. COMPLETE SATISFACTION OR MONEY REFUNDED WITHIN 10 DAYS.

**STREAMLINED SELF STUDY COURSES**  
509 5th Avenue, Dept. B, New York City

RADIO & TELEVISION NEWS

## Crystal Diodes

(Continued from page 65)

result is substantially the same. The voltage *versus* frequency characteristic for an FM discriminator is shown in Fig. 7. The total voltage output of a discriminator varies in a positive and negative direction depending upon the deviation of the i.f. signal above or below the mean frequency. The greater the frequency deviation the greater the voltage developed.

The output voltage is the algebraic sum of the voltages developed across the load resistors of the two diodes. It should be apparent from the curve shown that if the straight portion of the discriminator voltage frequency curve covers a wider range of frequencies than those generated by the transmitter, the audio output will be reduced from the maximum value of which the receiver is capable. This must be so because at its "center" frequency the discriminator produces zero output voltage. On either side of this center frequency there is developed a voltage of a polarity and magnitude that depends upon the direction and amount of frequency shift from the center frequency.

Therefore, the voltage output of a discriminator varies in precisely the same fashion as the audio voltage which modulates the carrier. The greater the voltage developed across the diode load the louder the sound coming from the speaker. When there is no modulation on the FM carrier there is no deviation of frequency and consequently no audio voltage is developed; hence, no sound comes from the speaker.

But there is an important point to be made in connection with a discriminator detector. The output voltage of a discriminator may vary directly with change in input voltage. The curves marked A and B in Fig. 7 indicate this fact. This is why a limiter circuit is important. It holds the input level at constant amplitude and does not permit the discriminator to receive signals that are amplitude modulated. The reason why amplitude modulated signals might appear at the discriminator in an FM circuit was discussed before in connection with the limiter, where it was shown that since the response curve is not perfectly flat topped, there is some variation in the signal level which is, in effect, amplitude modulation of an FM signal wave.

The method of conversion of frequency changes into audio voltage is graphically illustrated as a function of the linear portion of the discriminator characteristic, shown in Fig. 8.

The circuit of Fig. 9 is a simple discriminator detector circuit. The better the matching of the diodes the better the performance of this type circuit; but note the remarks in the caption. This circuit will operate over the entire range of commonly encountered i.f. frequencies from the 4.5 mc. used with intercarrier sound to the 44 mc.

## DYNAMOTORS:



**DYNAMOTOR And BLOWER**  
9 Volts DC input, output 450 Volts 60 MA., 4500 RPM. At 6 Volts DC input, output 260 Volts 65 MA., 3000 RPM.  
Price .....\$4.95

INPUT:	OUTPUT:	STOCK No.:	PRICE:
12 V. DC	220 V. 70 MA.	DM-24	\$6.95
12 V. DC	220 V. 100 MA.	DM-18	4.95
12 or 24 V. DC	440 V. 200 MA. & 220 V. 100 MA.	D-104	9.95
14 V. DC	375 V. 150 MA.	DM-375	8.95
14 V. DC	330 V. 135 MA.	DM-330	7.95
14 V. DC	500 V. 500 MA.	PE-50	14.95
12 or 24 V. DC	275 V. 110 MA.	USA/0516	3.95

Tell Us Your Dynamotor, Inverter, & Motor Needs!

## TRANSFORMERS AND CHOKES:

### TRANSFORMERS

110 VOLT 60 CYCLE PRIMARIES	Sec. 6.3 V. 1 Amp. ....	\$1.25
	Sec. 24 V. 1/2 Amp. ....	1.50
	Sec. 24 V. 1 Amp. ....	1.95

### CHOKES

H-115 8 Henries 500 MA Filter, 5000 V. Ins.	\$10.95
H-121 13 Hy. 250 MA Filter, 1500 V. Ins.	4.95
H-422 4-12 Hy. Swinging, 300MA, 2500V. Ins.	4.95

## WHIP ANTENNA EQUIPMENT MAST BASE—INSULATED



**MP-132 BASE**—as illustrated at left, 1" heavy coil spring, 2" insulator. Overall length: 11 1/2". Weight: 2 3/4 lbs. Price .....\$3.95

**MAST SECTIONS FOR ABOVE BASE**—Tubular steel, copper coated, painted, in 3 foot sections, screw-in type. MS-53 can be used to make any length, with MS-52-51-50-49 for taper. Price for any section.....50c Ea.

## BC-223 TRANSMITTER

30 Watt Transmitter with Crystal or MO control on four pre-selected channels. CW, MCW cover frequency range 2000-5200 KC by use of plug-in coils. Complete with tubes and choice of one Tuning Unit (listed below). Less Mtg. Prices: NEW: \$32.50. USED (Gov't Reconditioned).....\$26.50

CABLE—Trans. to Power Supply.....\$2.00  
TUNING UNITS: TU-17—2000-3000 KC. TU-18—3000-4500 KC. TU-25—3500-5250 KC. \$3.50 EACH  
Spare VIBRATOR & TUBE KIT f/PE-125BX.....\$ 5.95

PE-125BX POWER SUPPLY f/BC-223—12/24 Volt input; output 475 Volts 150 MA. NEW: 14.95

SPARE TUBE KIT in metal box. f/BC-223 5.95

OPERATING MANUAL for BC-223AX.....2.50

SHOCK MOUNTING for PE-125.....1.50

PT-173 MOUNTING for BC-223.....2.50

BC-223 TRANSMITTER—Incomplete, for parts. No front panel or meters. Price—As is:.....\$4.95

## GUY CABLE

Regular Aircraft Control Cable, 3/8"—7x7—40 Strands galvanized weatherproof, 920 lb. Test. Ideal for television or radio mast guying. Non preformed. Prices: 2 3/4c per Ft.—1000 Ft. or more: 2 1/2c per Ft.

## BLOWERS:

115 Volt 60 cycle BLOWER (pictured), approx. 100 CFM Dis. 2 1/4" intake; 2" outlet. Quiet running. Motor size: 2 1/2" x 3 3/4". NEW—not Gov't surplus. Order No. RN-520.....\$7.99



**DUAL BLOWER**—Same as RN-520 above, except has blower assembly on each side of motor. Order No. RN-800.....\$12.95

SEND IN YOUR ORDER TODAY!  
Address Dept. RN • Minimum Order \$2.00  
Prices F.O.B., Lima • 25% Deposit on C.O.D. Orders

# FAIR RADIO SALES

132 SOUTH MAIN ST.  
LIMA, OHIO

## AUDIO (Sound) ENGINEERING COURSE Home Study Training

BIG PAY JOBS open in Television, Radio, Electronics, Disc Recording and Motion Pictures. Recognized and Approved Training. Write for complete details. TODAY!

HOLLYWOOD TECHNICAL INSTITUTE  
3359 Cahuenga Blvd., Dept. B. K.  
Hollywood 28, California

## 6-VOLT POWER SUPPLY

VIBRATOR TYPE—6 Volt DC input; output 230 Volt DC 50 MA. filtered w/tube. Size: 6 1/2"x4"x5 1/2"  
Price .....\$6.95

VIBRATOR TYPE—6 Volt DC input; output 230 Volt DC 50 MA.—not filtered—w/tube. Ideal for Command Receiver operation as receiver is filtered internally. Size: 4 1/2"x4 1/4"x3 1/2"  
.....\$4.95

## METERS:

0-150 Volt, 400 cycle, 2 1/2" Rd. ....\$3.95

0-5 Amp. AC, 3" Rd., 0-75A Scale..... 3.95

0-5 Milliamp DC, 2 1/2" Sq., 0-5 Scale..... 3.95

0-1 Milliamp DC, 2 1/2" Rd., 0-150 Scale..... 3.95

0-500 Microamp, 2 1/2" Rd., 0-15 & 0-600 DC Volt Scale..... 3.95

TUNING METER 1-70B Reverse Scale, Weston #606 for Compass Control Boxes..... 3.95

## AERIAL WIRE


Aerial Wire—Phosphorous Bronze #16 Stranded, 200 lb. test. Weather-proof. 150 feet on Reel. RT-3 with Clips ...\$1.50

## WIRE—HEAVY DUTY RUBBER COVERED

2/#16—20 Ft. Length.....\$1.25  
2/#12—10 Ft. Length..... 1.00  
1/#6—Shielded, 15 Ft. .... 1.50  
1/#6—Shielded, 7 1/2 Ft. .... .75  
1/#8—Shielded, 8 Ft. .... 1.00  
1/#8—Cotton covered—Per Foot......06  
500 Ft. #20 Cotton covered stranded and tinned, in 9 1/2 Ft. lengths, 500 Ft. (Ass't. colors).....\$3.95
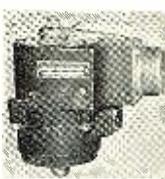
## 3/4 RPM ANTENNA ROTATOR MOTOR

High torque, reversible motor—operates directly from 110 Volt 60 cycle by use of condenser. Light weight, quiet running, ruggedly built, positive stop, easily mounted. Normally operates from 110 Volt 400 cycle. Complete—with instructions. NEW.....\$4.95



10 MFD 400 Volt Cond., \$1.00. SPDT Switch: 35c

## What'll You Have?

BC-230 Transmitter, with Tubes.....\$ 4.95

R-1/ARR-1 Receiver f/conversion to 220 MC. 4.95

AN-104A Antenna—100-150 MC..... 2.00

AN-117 Whip Steel, 6 Ft..... 1.50

AN-109A Whip Steel, 5 Ft. w/Base..... 1.50

AT-37A/APT Stub—113-150 MC..... 5.95

AS-27/ARN-5 Ram's Horn, 110 MC. USED: 5.95

FL-8 Filter, 1020 cycle Audio Filter. USED: 1.50

Leg & Seat Assembly for 11and Generators... 3.50

CD-501 Cord for GN-45 Generator..... 2.00

C-87/ART-13 Control Box f/ART-13 Trans.: NEW: \$6.95 USED: 4.95

CD-318 Cord f/Throat or Lip Mikes..... .59

CD-307 Cords 65" w/PL-55 & JK-26..... .99

CD-604 Cord w/C-410 Trans. & PL-54 Plug... .89

Head & Chest Set w/Plug for EE-S... USED: 2.95

Microphone & Headset, Dynamic type f/MARK II: NEW: \$2.95 USED: 1.95

TUNING UNITS for BC-375-191: TU-5, 7, 8, 9, 10, or 26.....Each: 3.95

TA-12B Transmitter w/Tubes..... USED: 29.50

RA-10 CA or DA Receiver w/Tubes... USED: 17.95

BC-605 Amplifier..NEW: \$ 5.95 USED: 3.95

BC-347 Amplifier w/Tube..NEW: 2.95 USED: 1.95

BC-709 Amplifier..NEW: 4.95 USED: 3.95

BC-434 Control Box..NEW: 8.95 USED: 5.95

BC-732 Localizer Control Box..NEW: \$2.95 USED: 1.95

MC-211 Right Angle Adapter f/MC-215..... .50

MC-215 Tuning Shaft for 274 N—96"..... 2.00

MC-124 Tuning Shaft f/Radio Compass—12 ft. .... 3.95

FA-10 Fairlead..... 1.00

BC-455 Comm. Receiver, 6-9.1 MC... USED: 7.95

BC-457 Comm. Transmitter, 4-5.3 MC. USED: 5.95

BC-458 Comm. Transmitter, 5.3-7 MC. USED: 5.95

**Examine FREE**



**Prentice-Hall  
ELECTRONICS &  
UHF LIBRARY**

Edited by **W. L. EVERITT**

5 VOLUMES 1662 ILLUSTRATIONS

**Pay Easy Installments If You Keep Set**

Turn to this new, up-to-date Library with complete confidence, for dependable facts on any phase of modern electronic theory and practice. These volumes, by outstanding authorities, give you thorough guidance—clearly written, logically arranged, profusely illustrated.

**Electronic Fundamentals and Applications**

By **Prof. John D. Ryder, Univ. of Illinois**

Complete, logical, easy-to-follow treatment of (a) physical principles underlying electron tubes, (b) characteristics of vacuum tubes, (c) all basic tube circuits. Includes: Electron Ballistics. Cathode-Ray Tubes. Emission of Electrons. Space Charge in Vacuum Tubes. Diode Rectifiers. Triodes. Multi-Element Tubes. Small-Signal Amplifier Circuits. Audio-Frequency Amplifiers. Radio-Frequency Amplifiers. Oscillator Circuits. Modulation Systems. Wave-Shaping Circuits. Gaseous Conduction. Gas Diodes. Gas Control Tubes and Circuits. Photoelectric Cells. Solid-State Electronics.

**Electromagnetic Waves and Radiating Systems**

By **Prof. Edward C. Jordan, Univ. of Illinois**

Covers entire field of electromagnetic engineering. Includes propagation as well as radiation and transmission. Full treatment of UHF transmission lines, wave guides, antennas, slot antennas, radiation and diffraction, ground-wave and sky-wave propagation.

**Ultra High Frequency Engineering**

By **Thomas L. Martin, Univ. of New Mexico**

Theory and technique of ALL the new fields of electronic engineering: Radar, Telemetering, Electronic computing, Facsimile, Television, Blind landing systems, Pulse-time modulation, Ionosphere measurements . . . and the others.

**Networks, Lines and Fields**

By **Prof. John D. Ryder, Univ. of Illinois**

Network transformations and theorems. Resonance. Impedance transformation and coupled circuits. Filters. General transmission line. High-frequency line. Equations of the electromagnetic field. Radiation. Transmission and reflection of plane waves at boundaries. Guided waves between parallel planes. Wave guides.

**Elements of Television Systems**

By **George E. Anner, New York University**

Complete basic theory, plus current practice, covering: Closed TV Systems. Commercial Telecasting Systems. Color TV Systems. Gives clear exposition of all phases of picture transmission, including the new technique of dot interlace.

**SEND NO MONEY—EXAMINE FREE**

Just mail coupon below to get complete 5-Volume Set on 10 DAYS' FREE TRIAL. If not completely satisfactory, return in ten days and owe nothing. Or keep the set and pay only \$5.35 down and \$8 a month for five months until full price of \$45.35 is paid. Decide for yourself—without risk or obligation—just mail coupon to examine Library ten days free.

**PRENTICE-HALL, Inc., Dept. M-RN-152  
70 Fifth Avenue, New York 11, N. Y.**

Send me the Prentice-Hall, **ELECTRONICS & UHF LIBRARY** (5 Volumes) for ten days' free examination. If fully satisfied in ten days I will send you \$5.35 plus few cents postage and then \$8 a month for five months until full price of \$45.35 is paid. Or I will return the Library in ten days and owe nothing.

Name .....

Address .....

City and State .....

i.f. The crystals and associated resistors and condensers may be mounted under the chassis or they may be enclosed in a small shield can. In some instances, by careful layout and design, it is possible to include the diode crystals, resistors, and condensers in the FM discriminator shield can. Such location is important in preventing feedback. This makes a most compact assembly although it does present servicing difficulties.

The circuit shown in Fig. 10 is desirable from the standpoint that crystal matching is not necessary. The 220,000 ohm resistors in parallel with standard stock type 1N48 diodes keep the circuit balanced irrespective of the back resistance of the crystals. The other circuit values are typical of those found in a discriminator circuit. The reverse resistance of a crystal diode is subject to minor variations with changes in ambient temperature, humidity, and impressed voltage. While in general applications the small changes in back resistance are of little consequence they are significant in an FM detector because demodulation depends upon close balance between the two parts of the circuit. The better the balance the higher the degree of linearity and the greater the AM suppression for the discriminator.

The sound circuit of a television receiver is the same as that found in a typical FM receiver. Detection of the i.f. signal is accomplished by a discriminator or a ratio detector circuit. Both types of circuit require two diodes and balanced conditions for optimum operation. Germanium diodes have been successfully substituted for vacuum tube diodes in a discriminator circuit; probably the most widely used discriminator is the Foster-Seeley type. The chief circuit difference for crys-

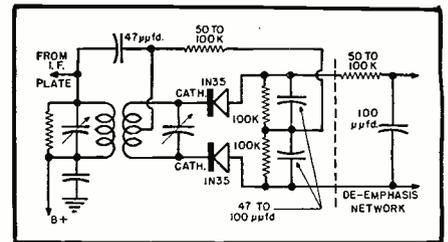


Fig. 9. FM discriminator circuit using germanium diode crystals. The IN35 duo-diode, consisting of carefully matched crystals, is highly satisfactory for this circuit. IN35's are matched in forward resistance only and since this resistance is small compared to 100,000 ohm load, balance is unimportant. The necessary balance is in back resistance which is not very much greater than 100,000 ohms. This is one reason why shunting resistors are suggested in Fig. 10. Use of shunting resistors will permit the use of less expensive IN34 type crystals. The 100,000 ohm resistors and 47 µµfd. condensers should be low tolerance matched components for ideal balance of two parts of circuit. The de-emphasis circuit network is shown only to indicate parts values.

tals as compared to the vacuum tube is the use of shunting resistors with the crystals to maintain fairly uniform balance between both halves of the circuit with respect to the back resistance characteristics.

**Ratio Detector Circuits**

A discriminator detector requires one and preferably two limiter stages because of discriminator sensitivity to amplitude as well as to frequency variations. For effective limiting there must be good amplification of the i.f. signal before it reaches the limiter in order that all signals have a level sufficiently high to operate the limiter at saturation. Since a ratio detector does not respond appreciably to amplitude

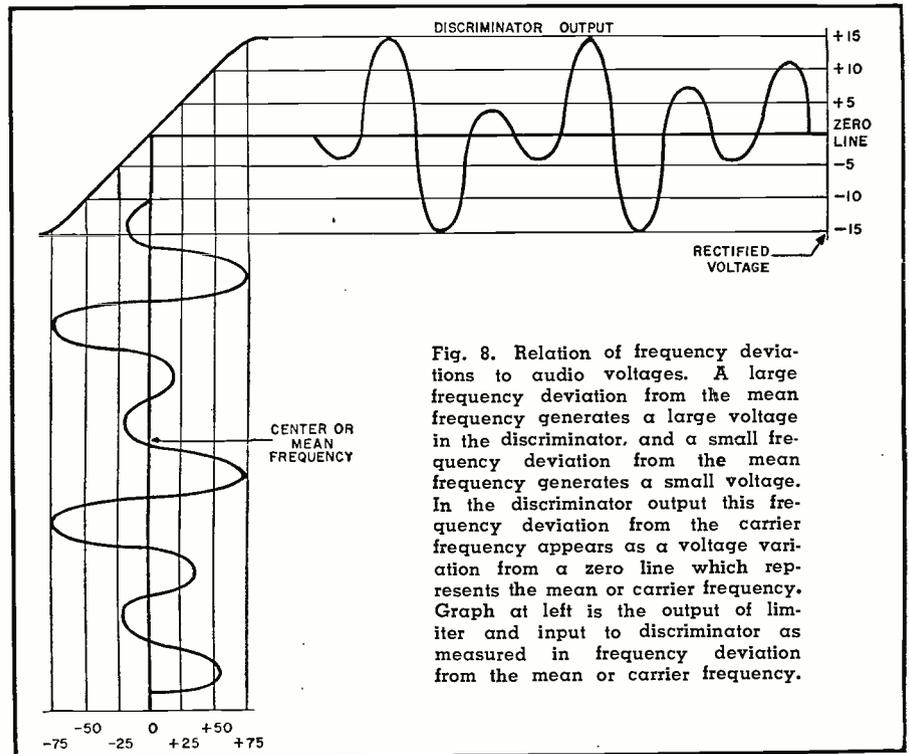


Fig. 8. Relation of frequency deviations to audio voltages. A large frequency deviation from the mean frequency generates a large voltage in the discriminator, and a small frequency deviation from the mean frequency generates a small voltage. In the discriminator output this frequency deviation from the carrier frequency appears as a voltage variation from a zero line which represents the mean or carrier frequency. Graph at left is the output of limiter and input to discriminator as measured in frequency deviation from the mean or carrier frequency.

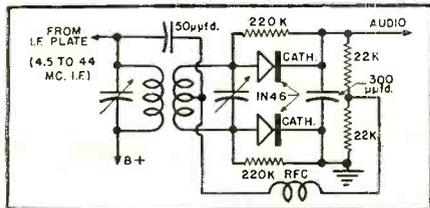


Fig. 10. Frequency discriminator circuit. This circuit performs as well as that shown in Fig. 9 but eliminates the need for using matched diodes by using 220,000 ohm resistors in parallel with IN48 type diode crystals. Circuit is thus balanced regardless of back resistance of diodes. Other component values are typical of those found in a discriminator circuit.

variations in it, from that point of view, superior to a discriminator type detector.

The chief advantage of a ratio detector is that for a weak carrier, on modulation, the voltage ratio is the same as for a strong carrier, on modulation; therefore, the ratio detector is not responsive to carrier changes, and hence relatively insensitive to either sudden or dynamic changes in amplitude of the applied signal. Because a ratio detector is responsive to slow changes in carrier, a.v.c. may be desirable. The audio output deriving from frequency modulation of the applied signal results from the change in the ratio of the two diode voltages which makes the circuit responsive mainly to variations in signal frequency and not to dynamic changes in signal amplitude.

With a ratio detector circuit, balance between the halves of the system is more critical than for a discriminator type circuit. The ratio detector provides AM suppression as well as FM detection and its operation depends, to a great extent, on the balance between the halves of the system. The back resistance of crystals is not uniform and changes with temperature and voltage level; the situation is complicated by the fact that the changes are not likely to be the same in both diodes, nor to occur at the same time.


It is therefore more difficult to design a ratio detector system using germanium diodes, but it is not impossible. Variations of the ratio detector circuit have been designed to minimize any detrimental and undesirable effects of the back resistance characteristics of the crystals. Although these circuits do not achieve all the good inherent in the ratio detector system, they do approach the operating quality of conventional vacuum tube circuits.

The ratio detector has excellent inherent noise and AM reduction characteristics, and the conventional circuit using a 6AL5 is economical. But it is not possible to simplify the conventional ratio detector circuit just by inserting germanium diode crystals as substitutions for the separate halves of the 6AL5. The dynamic characteristics of a crystal are somewhat different from those of a vacuum tube diode.

However, experimental work with

# Sam's Surplus Sells For Less
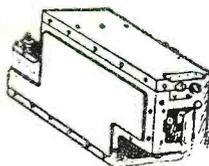
## COMMAND AND/OR ARC5 TRANSMITTERS and RECEIVERS



BC-142 Antenna Relay, less Vac.	USED \$1.95
BC-450 3 Receiver Control.	USED \$1.49
3-6 MC Receiver.	USED \$ 6.95
	NEW 17.95
6-9.1 Receiver.	USED \$ 6.95
	NEW 12.95
Triple Receiver Rack.	USED NEW \$1.95

V.H.F. ARC5 Transmitter or Receiver, Complete w/tubes.	\$24.95
2.1-3 MC Transmitter with tubes	14.95
4-5.3 MC Transmitter with tubes	6.95
5.3-7 MC Transmitter with tubes	6.95
7-9.1 MC Transmitter with tubes	9.95
3-4 MC Transmitter with tubes	18.95
28V Receiver Command Dynamotors.	\$0.97

### MODULATORS

BC-156 with Tubes, less dyn.	2.95
MD-7/ARC5 Plate Modulator.	8.95
MD-7 Modulator Dynamotor, 28V	2.95

BC-433 Receiver—with tubes.	\$24.95
MN-26C Compass Receiver.	24.95
MN-26Y Compass Receiver.	24.95
BC-1206 Receiver 200-400 kc.	5.95
BC-357 Marker Beacon Rec. W.O. Tube	5.95



BC-223 TRANSMITTER, 30 watt Ideal for Ship-to-Shore or Ham Rig. Crystal or MO control on four pre-selected channels. 2000 to 5250 KC. Use of 3 plug-in coils. Five tubes: 2-801, and 3-36, and TU 17-18-25 tuning units.	TRANSMITTER—\$39.95. Tubes—\$3.75.
TUNING UNITS—\$2.25. AMP METER. No. 50-60. New—\$1.29.	

### CIVIL AIR DEFENSE or 2 METERS

ARC-4. W/tubes. Good, used.	\$29.95
522 Transmitter-Receiver, W/tubes. Good, used.	69.50
MODULATION TRANSFORMER, BC-375. New	2.49

BC-375 Trans. 100 Watt Voice, CW, MCW, freq. range 200 kc to 12 mc. uses Plug-in Tuning Units listed complete with tubes.	\$29.95
less Tuning Units.	
TUNING UNITS for BC-375 or 191 Trans:	
TU-7 4500-6200 kc	\$2.49
TU-8 6200-7700 kc	2.49
TU-9 7700-10000	2.49
TU-10 10000-12500	2.49
TU-22 & TU-26 200-500 kc	each 4.50
FT-151 Shock Mounting for BC-375 or 191.	2.95
BC-306 Antenna Loading.	1.95

GP-7 NAVY TRANSMITTER: 100 watt master os. Can use on any freq. from 350-9050 kc. by using proper plug-in. With 1 tuning unit	\$13.33
---	---------

### LOOP ANTENNAS

DU-1 Has 2 tube amplifier.	New \$25.95
MM-20-E	New 7.95
LP-21 A	New 16.95
ROTATABLE LOOP UNIT—Type MN-20E. 3" diameter—used with MN-26 Compass and RA 10 DB. By Bendix.	Only \$7.95
FL8 Filters—A's, B's, C's.	New 1.95
FL5 Filters	New .95
Hand Keys—J-38	New 1.19
TSC TRANSMITTER & RECEIVER with 12V Power Supply and Cables. Good—used	179.50
Heinemann Circuit Breakers,	
115 V., 20 amp.	1.39
115 V., 5 amp.	.97
Prop Pitch Motors—with Transformer	19.95
Prop Pitch Transformer, only.	New 6.95
RT-7APN-1 Transceiver, tubes & dyn. used	9.95

Cash with order. Prices subject to change without notice. California Orders Please Include 3 1/2% Sales Tax. Please Include Approximate Postage—Excess will be refunded. What Have You in Surplus? Submit

**ESEGE SALES COMPANY INC.**

1306 BOND STREET, at PICO LOS ANGELES 15, CALIFORNIA

### "S" METER



"S" METER—SAM'S SPECIAL. Illuminated face (supplied with miniature lamp). Full scale reading of 5 ma. A standard value for most "S" Meter Circuits. Dia. across face—2 3/4". Black bakelite face. Reverse-set pointer. New \$2.49

VIBRATORS — MALLORY. For use on 12 V battery. New \$0.97

HEADSET ADAPTER, MC-385-C. High to low imp. For Headset HS-33 or HS-38. New \$1.95

### TRANSFORMERS

12V 24V 2am 110V primary.	\$2.95
ARC-4 2 Meter Transceiver, tubes—good, used	\$29.95
BC-134 Control.	Used—\$1.95 New 2.95
Code Practice Tapes for TG-10 15 rolls.	New 7.95
BC-906 Absorption Type Freq. Meter Range 150-225 mc. 0-500 DC Microm. Used—\$11.50 New 14.95	
Field Phones E-E 8's. Used \$19.95 pr.	New \$34.50 pr.
Mobile Relay, SP-ST. Leach 6 V or 12 V	New 1.49

### CRYSTALS

\$150.000	\$1.19 ea.
8036.25	3 for \$2.95
8001.43	

### DYNAMOTORS

PE-103 NEW, ORIG. CASE	\$29.95
PE-103 N E W, Less Base—Dynamotor	19.95
DM-32A Input 28V. Output 250 DC. .06 amps. Used.	1.95
DA-1A Input 28V @ 1.6 amps. Output 230 DC @ .1 amp.	Used 5.95
PE-73 29V @ 20 amps. output 1000V @ 350 amps.	New 8.95
PE-77 14V @ 40 amps output 1000V @ 350 amps.	New 19.95
SPEC. 27V @ 400V 7.50 mil 750V 350 mil.	New 12.95
PE-91 or SCR—522 24V. Used—\$5.95. New 14.95	
PE-94 Dynamotor only	4.95
DM-34 12V @ 2.8 amps. Output 220V @ 160 amps	New 9.95
SPEC. 0V @ 450V output @ 80 ma. New 5.95	
SPEC. 12V @ 320V output @ 80 ma. New 4.95	
SPEC. 6V @ 250V output @ 80 ma. New 6.95	
SPEC. 12V @ 440V output @ 200 ma	New 8.95
ARC-1 DY-9/ARC-1	Used 11.50
ARC-1 Dy-10-12V	Special 9.50
14 Volt Input—425 Volt Output at 163 mils. Starting Filter and Relays in base	Like New 3.95
683 FM Receiver 26 to 39 mc FM Receiver with tubes—used—\$29.95. New 39.50	
RJ-42B Antenna Reel Ass. Less wire.	New 9.95

### OIL CONDENSERS

Standard Makes—New

2 mfd	600V	\$0.49
4 mfd	600V	1.39
1 mfd	1000V	.69
3 mfd	4000V	7.95
.5 mfd	2500V	1.49
10 mfd	600V	1.95
2 mfd	2500V	3.95
2 mfd	4000V	5.95
2 mfd 5000V	\$ 8.95	2 mfd 7500V 29.95
T-30 Throat Mikes.	Used—3 for \$0.50	
CD-307 Head Set Extension Cord.	1.19	

### HEAD SETS

HS-30	New \$1.95
HS-23	Used—\$1.95; New 2.95
Matching Transformer for HS-30	.69
BC-348 Mounting Base.	2.49
RG-7U Coax Cable, 97.5 ohms foot	.08
MIKE CHEST SET "F-1" button.	New 2.95

### DECK INSULATORS

Bowl & Flange type. Heavy galv. metal flange—10 1/4" dia. Porc. bowl set in rubber gaskets. Top bell—7 3/4" dia. Brass feed through rod L insul. dist. between top bell and flange—6 1/2".	New \$2.95
--	------------



EVERYTHING you buy from KEY is fully guaranteed. If you are not satisfied you may return your purchase for credit or refund as you prefer. No questions asked. All merchandise offered subject to prior sale. Minimum order \$2.00. All prices are F.O.B. Baltimore, Maryland. Shipment will be made by Railway Express Collect unless otherwise specified. Include 25% with all COD orders.

### AUDIO OUTPUT TRANSFORMERS

900 V. Insulation 50-60 ma primaries. Secondaries match 3.2 ohms nominal.

Stock No.	Primary Impedance	Price Ea.
987	2,000 ohms	\$0.49
775	2,400 ohms; with bucking winding	.69
247	2,500 ohms	.49
178	2,900 ohms; with bucking winding	.69
656	5,000 ohms	.49
876	8,000 ohms	.49
876	8,000 ohms	.49

### I. F. TRANSFORMERS All in shield cans

Stock No.	I.F.	Description	Price Ea.
540	10.7 Mc.	3/4x1 1/4x2 3/4; terminals	\$0.45
877	455 Kc.	1 1/4x1 1/4x2 3/4; Magnette core; leads	.40
577	455 Kc.	1 3/4x1 3/4x2 1/2; leads	.30
419	10.7 Mc.	1 7/8x1 7/8x2 7/8; 3rd I.F.; 455kc Lim; terminals	.55
218	455 Kc.	1 1/4x1 1/4x2 3/4; leads	.30
180	455 Kc.	1 1/4x1 1/4x2 3/4; 3 leads	.30
345	455 Kc.	1 1/4x1 1/4x2 3/4; series tuned pri. leads	.30
207	455 Kc.	1 3/4x1 3/4x4; 1st I.F.; leads	.30
206	455 Kc.	1 3/4x1 3/4x4; 2nd I.F.; leads	.30
723	455 Kc.	3/4x3/4x1 3/4; powd. iron core; terminals	.35
538	10.7 Mc.	1 1/4x1 1/4x2 3/4; Discriminator	.45

### HORIZONTAL OUTPUT (FLYBACK) TRANSFORMER. Equivalent to RCA 21T3 .269 ea.

#### OIL-FILLED CAPACITORS

Capacity	Voltage	Price ea.
2 mfd	1,000 V.D.C.	\$1.49
3.5 mfd	220 V.A.C.	.69
4 mfd	3,000 V.D.C.	5.95
6 mfd	1,000 V.D.C.	3.29
7 mfd	220 V.A.C.	1.39
7 mfd	600 V.D.C.	2.69
8 mfd	1,000 V.D.C.	3.69
8 mfd	330 V.A.C.	2.75
10 mfd	1,000 V.D.C.	3.89
12 mfd	600 V.D.C.	3.50
16 mfd	330 V.A.C.	3.98

#### PAPER CAPACITORS, TYPE TTR

.005 mfd. .01 mfd. .02 mfd

10 for \$0.49

100 for 3.85

1,000 for 29.00

### BLOWERS, A. G. REDMOND TYPE L

Approx. 100 cfm . . . . . \$7.50 ea.

### POWER TRANSFORMERS, 117 V., 50/60 C. Primaries

Stock No. Description Price

\*1159 Sec #1-650 V.C.T. @ 150A; Sec #2-6.3V @ 2.1A; Sec #3-3.5V @ 3A Jefferson . . . \$4.95

\*1160 Sec #1-1450 V.C.T. @ 100A; Sec #2-6.3V @ 1.2A; Sec #3-5V @ 3A Jefferson . . . 5.95

192 Sec #1 700 V.C.T. @ 900A; Sec #2-6.3 @ 4A; Sec #3-5V @ 3A SNC . . . 3.89

### HIGH VOLTAGE TRANSFORMER, 117V 50/60 C. Primary

\*1158 Pri-117V, 50/60C; Sec 4000V @ .025A Jefferson . . . 8.95

\*1157 Sec #1 4V @ 16.0A; Sec #2.5V @ 1.75A Jefferson . . . 5.75

239 Sec #1 5V @ 3.25A; Sec # 5V @ 3.25A can deliver 5V @ 6.5A; 10V.C.T. @ 3.25A SNC . . . 2.50

### FILTER CHOKE

\*1161 Dual 30 henry, .020A Jefferson . . . . . 1.00

\* Current ratings for these items are conservative. They are Government equipment and are underrated. High-voltage insulation.

### TANK CIRCUIT, 150-200 Mc. Uses 2-826's

In Metal Shield Box, complete w/tubes. \$7.95 ea.

### CONTROL STRIP, ANTENNA LINE, Uses 2-9006.

1-9002. Has 6VAC DPST relay. Complete w/tubes and relay . . . . . 2.50 ea.

### KNOB ASSORTMENT . . . . . 20 for \$1.00

SARKIS TARTAN TUNERS, Uses 1-6C4, 2-6AG5. Good condition. As is, less tubes 2.98 ea.

### PANEL LAMPS

Type 47 . . . . . 10 for \$0.55

Type 44 . . . . . 10 for .45

100 for 3.95

### RECEIVER LOOP ANTENNA ASSORTMENT, 10 for \$2.39

AC LINE CORDS, MOULDED RUBBER PLUGS ASSORTED . . . . . 10 for 1.95

### ATTENTION INDUSTRIAL USERS!!!!

We have large stocks of the following items:  
Amphenol Connectors  
Allen Bradley Potentiometers  
T & B "Sta-Kon" Terminals  
Tube Sockets  
High-vacuum and Gas-filled Condensers  
Compression Type Trimmer Capacitors  
Magnet Wire  
AMP Terminals  
Bundy Hytugs  
Fiberglass Yarn  
We invite your inquiries. We will reply the same day your query is received.

## Key Electronics Division


1801 N. LONGWOOD ST. BALTIMORE 16, MARYLAND

Something worth thinking about—

ARE DAILY ADJUSTMENTS ADDING YOUR OPERATING COSTS?

There's a big factor showing up in the tape recording world . . . it's the tragedy of High Maintenance Costs. Many radio stations are confronted with the daily ritual of recorder checking and adjusting. Added to the time cost of such inspections is the cost of frequent parts replacements and loss of program time.

In contrast, Ampex users find their equipment will operate continuously eighteen hours a day with but infrequent inspection. Upkeep and replacements are almost nil; heads have remarkably long life. Ampex performance is constant over long periods of continuous operation. Long life with low maintenance is assured in each Ampex recorder by high manufacturing standards and complete test of each machine before shipment. It all adds up to one sure fact—Ampex quickly pays for itself out of savings from lower operating costs and added dependability.

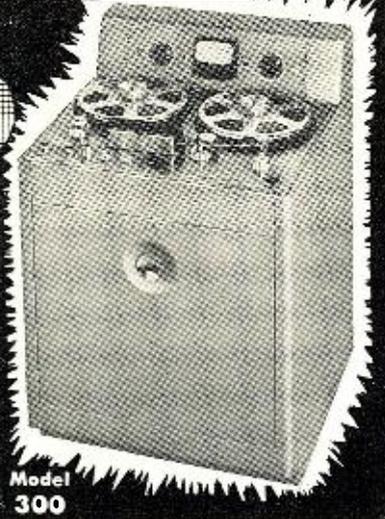

### Complete Specifications on Request

Shown is the time proven Model 300 Console. Throughout the field of professional audio recording this machine is the recognized leader.

STANDARD OF THE GREAT RADIO SHOWS

AMPEX ELECTRIC CORP.  
Redwood City, California  
Dealers in Principal Cities

# AMPEX

## Magnetic Tape Recorders

the ratio detector circuit has facilitated the development of a crystal diode ratio detector circuit that provides performance data approximately equivalent to that obtainable from a vacuum tube. The crystal diode circuit has excellent physical advantages over the vacuum tube diode with respect to savings in weight, power, and space, making possible the development of battery-operated, portable-type FM receivers.

The ratio detector circuit depends critically upon close balance between the two individual parts of the circuit in order to obtain a high degree of linearity and to provide the amount of AM suppression desirable in an FM receiver. The modified form of ratio detector circuit here presented will yield results comparable to those achievable by a vacuum tube circuit, assuming that both units are properly designed and equally well constructed.

The combined load circuit shown in Fig. 11, has a time constant long with respect to the period of any AM components present and causes the sum of the diode output voltages to remain constant as far as AM components are concerned. Since the sum of the diode voltages is thus fixed by the long time constant load circuit, the ratio detector is not responsive to the dynamic changes in the amplitude of the signal.

The audio output due to frequency modulation of the applied signal results from a change in the magnitude of the two diode voltages, the net effect of which is to make the circuit responsive only to variations in signal frequency and not to dynamic changes in signal amplitude. Thus AM components due to noise and multipath transmission effects are largely suppressed in the ratio detector.

To obtain maximum suppression of amplitude variations in the output of the ratio detector, it is essential that the two halves of the circuit be balanced and remain so throughout the entire dynamic range of the input signal. This requires close tolerances in the resistance and capacitance values and careful design of the input transformer primary, secondary, and tertiary windings, as well as close matching of the diode characteristics. The close matching of the diode characteristics is most critical; for this reason it is generally necessary to supplement the ratio detector with some means of AM reduction before the ratio detector stage. In this one respect crystals have some superiority over vacuum tube diodes. Additional details on this point will be given later.

Many attempts to substitute crystal diodes for vacuum tubes in the conventional ratio detector circuit have been unsuccessful, in that little or no AM reduction was obtained, and the circuit itself proved to be unstable both with respect to symmetry of detector characteristic and permanency of alignment. However, with suitable modification of the basic circuit arrangement the undesirable effects of the variations in the back resistance

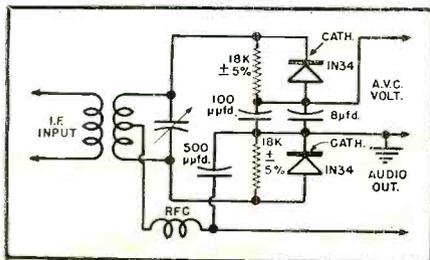


Fig. 11. Crystal diode shunt ratio detector.

of the crystal can be largely eliminated, and a germanium diode ratio detector exhibiting the characteristics of the vacuum tube diode circuit can be designed.

Modifications from the conventional type ratio detector circuit are relatively minor, as can be gathered from a consideration of the modified shunt ratio detector circuit shown in Fig. 11. The load resistors for the crystals are shunt rather than series connected. Electronically, the shunt circuit is equivalent to the series circuit in that, for given values of load resistance and signal voltage, the rectification efficiency is essentially the same for both.

Shunt connection of the crystal diodes makes possible the use of resistances in parallel with the crystals, each of which is of much lower value than the back resistance of the crystal across which it is connected; these resistances have the effect of swamping out the crystal back resistances. This detector circuit is relatively insensitive to changes in crystal back resistance and tends to reduce static and dynamic imbalance between the halves of the circuit. By virtue of their high conductance, crystals tend to provide somewhat improved circuit efficiency over vacuum tube diodes. Low shunting resistors, however, reduce efficiency as compared to vacuum tubes. Diode balance or AM suppression can only be obtained at the expense of output.

There are numerous advantages to be gained by using crystal diodes to replace the vacuum tubes in this type of circuit:

1. **Compactness**—The entire assembly can be built into the same shield can as a plug-in device if one is willing to use the *Vector* socket technique. The associated condensers and resistors, in addition to the two germanium diodes, occupy so little space that there is plenty of room to make a complete package unit of the entire ratio detector circuit.

2. **Filament Elimination**—The elimination of heater requirements materially reduces hum difficulties, particularly with series heater circuits, where the potential difference between cathode and heater of a detector tube may be quite large.

3. **Parts Elimination**—This makes for economy in the number of component parts, such as the socket and a smaller size filament transformer, which result in a substantial saving of space and reduction of weight.

4. **Imbalance Elimination**—There is complete elimination of imbalance re-

# NOW..THE 1952 IMPROVED "630" with the NEW CASCODE TUNER..

4 Microvolt Sensitivity

BRINGS IN RECEPTION UP TO 200 MILES

... This amazing new Super DX-2 handles all tubes from 10" to 24" will bring in better reception up to 200 miles without the use of boosters and will work where other sets have failed. The NEW STANDARD COIL CASCODE tuner gives you greater sensitivity with less snow. This tuner utilizes the newly developed 6BK7 tube with the gold plated grid... is fully shielded against radiation and has a newly designed converter circuit. Has new improved Mark Hyback with 3 stage sync separator; 5 hour minimum control; 15 KV output; heat run at factory. Moulded plastic cone-densers; synco lock; improved new Ferrite core with coil for greater range of width. Armstrong FM sound system; improved linearity adjustment and second horizontal linearity control. Factory wired, aligned and tested before shipment. Phone connection and switch on chassis. Complete with RCA Hi-Fi 12" Speaker. DIRECTLY ADAPTABLE FOR COLOR AND UHF STATIONS.

**\$149<sup>95</sup>**

Complete with Fed. Tax Less TV Tube


CHASSIS MTG. BRACKETS ...\$4.95

RMA GUAR.

Mfr. Lic. by RCA.

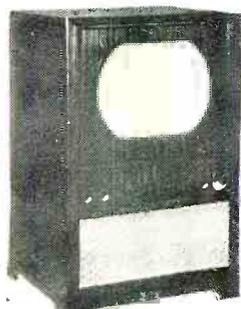
## PRICE SMASHING VALUES IN TV CABINETS FOR THE 630 CHASSIS

Beautiful, richly finished, hand rubbed mahogany cabinets to suit every taste. They are designed to house the "630" chassis, 12" speaker and up to 20" TV tube. The combination cabinets will hold only a 20" TV tube, radio and Webster record changer, with ample record space. All cabinets are equipped with mask and mounting brackets. The perfect chassis deserves a perfect cabinet. It will be a focal point of beauty in your home. Other models in stock. When ordering chassis and cabinet, no chassis mounting brackets needed. Send for FREE circular.



"ECONOMY"

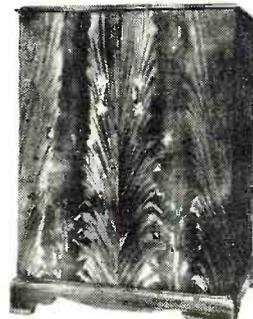
38x22 1/2x22 1/2-16" & 17" tube...\$49.95  
41x25x23-16" to 20" tube...\$9.95  
43x28x25-24" tube...\$74.95  
Blonde \$10 additional.



"STRATFORD"

40x28 1/2x23 1/2. Genuine crotch Mahogany doors...\$84.95

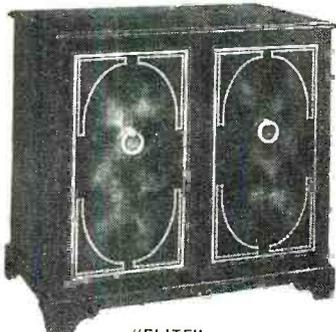SEND POSTCARD TO BE PUT ON FREE MAILING LIST



"ELITE"

Combination-39x40x23 1/2. Red antique gen. leather. Gold leaf hand tooling...\$139.95  
In lined oak, gold colored leather...\$149.95

## TV TUBE EXTRA

Standard Brands Factory New—1st Quality

12 1/2" Round	\$22.95
14" Rectangular	23.95
16" Rectangular	29.95
17" Rectangular	32.95
20" Rectangular	39.95
24" Round, metal	69.95
Ring & sleeve for 24"	7.50

All tubes carry full 1 YEAR Manufacturer's guarantee

## ESPEY FM-AM RADIO

12 TUBES Push Pull Out Put **\$6995**

300 OHM TV WIRE 1000 ft. spool **\$17.95**

100 ft. spool **\$2.00**

RECORD CHANGER NATIONALLY ADVERTISED 3 SPEED

Series = 100 **\$2995**

## SPECIAL VALUES

- STANDARD COIL TUNER...\$22.95
- TV MASKS—16 & 17"—\$4.95; 20"—\$7.95; 24"—\$14.95
- REGENCY BOOSTER MODEL DB410...19.11
- BELL AMPLIFIER, extended control...54.95

We carry a complete line of 630 component parts. We have a full line of RADIO TUBES. FROM 40% TO 60% OFF LIST.

All merchandise is brand new, factory fresh & fully guaranteed. Mail & phone orders filled upon receipt of certified check or money order for \$25 as deposit on TV chassis, 20% on other items. Balance C.O.D., F.O.B. N. Y. Prices subject to change without notice. No Fed. taxes to buy. Prices lower than OPS Retail.

**AIREX RADIO CORP.**

171 WASHINGTON ST., N. Y. C. 7, N. Y. PHONE WOrth 2-4029

## For GREATER TV ENJOYMENT...

Install a MOSLEY 3-WAY ANTENNA SWITCH



Cat. No. F-20 List \$3.75



Cat. No. F-10 List \$3.75

Here's convenience! MOSLEY TV Antenna Switches give instant, easy selection of any one of three antennas. Special rotary type switch, making silver-to-silver contact, assures low-loss, constant impedance.

Cat. No. F-10 is Flush Mounted Switch and Lead-in Socket combination for neat, concealed-in-wall installation in standard electrical box. Cat. No. F-20 is enclosed in attractive plastic case for mounting on wall or back of set. Both models available in brown or ivory.

MOSLEY Low-Loss TV Antenna Accessories Provide BETTER TV PICTURES Through More Efficient Installation!

At leading Radio Parts Jobbers everywhere

**MOSLEY ELECTRONICS** 2125 Lackland Road Overland, Missouri

# SAVE UP TO 53% ON COMPLETE ANTENNA KITS

Why search for parts. We put everything you need for a perfect installation in one kit. No forgotten parts. No wrong sizes. By prepacking these kits, we save handling costs. These savings are passed on to you. That's why you buy at such sensational prices, many below wholesale cost. All kits guaranteed to satisfy you or your money back.

## Rocket 5 Element YAGI KITS

Excellent Pictures in Fringe Areas

HIGH GAIN. Clearer, sharper, steadier pictures. PERFECT PICTURES IN FRINGE AREAS. Minimum interference from ghosts and noise due to a directive pattern. Five elements include one folded dipole, three directors, and one reflector. MATCHES 300 OHMS IMPEDANCE. Molded insulator provides additional strength. Exclusive design mast clamp prevents antenna turning or canting under any conditions. STURDY, TROUBLE-FREE CONSTRUCTION. No return calls. No broken elements. Stands the test of severe weather. Elements of heavy aluminum-clamped top and bottom. QUICK RIG. Completely pre-assembled. Just swing elements into line and tighten wing nuts. Simple to quick and easy. Available for any channel, high or low band.

### FRINGE AREA YAGI KIT

For people over 30 miles from station

2 Yagi Antenna for Channels 7, 8, 9, 10, 11, 12, 13 \$19.00

1 Pair Stacking Bars (Tie Rods) 2.00

1 5-foot Mast Standoffs (Swaged) 4.50

75 Feet 300 Ohm Twin Lead @ 1/2 foot 3.75

60 Feet Galvanized Guy Wire @ 1/2 foot .90

3 No. 4 Guy Wire Screw Eyes @ 5c each .15

2 Mast Standoffs @ 5c each .10

1 Guy Ring for Guy Wire @ 1/2 foot .15

3 Screw Eye Insulators @ 6c each .18

1 Mounting Base .45

1 Lightning Arrestor .125

1 Instruction Sheet .15

1 Instruction Sheet .15

Channels 7 to 13 Total Value \$19.13

Channels 7, 8, 9, 10, 11, 12, 13 Kits, You Pay \$ 9.25

Channels 4, 5, 6 Kits, You Pay \$ 14.25

Channels 2 or 3 Kits, You Pay \$ 17.25

Channels 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13 Kits, You Pay \$ 25.25

EACH CHANNEL requires a DIFFERENT Yagi antenna. When ordering, specify exact channel number desired. Any merchandise listed above may be purchased separately at prices shown.

SOLD ONLY BY MAIL BY NATIONAL ELECTRONICS.

## Rocket DIRECTRONIC MOTORLESS TV ANTENNA

360°

Electronically Switched Beam

• No Motors

• No Roof Orientation

• No Electric Power

• No Ghosts

The Directronic 18 element, 360° antenna is the finest for ultrafringe or metropolitan reception. The HI-PAC molded insulator is a material of extreme tensile strength not affected by weather or temperature, either mechanically or electrically. Included in the AX-599 "Service-men's Array" are:

18 hi-tensile aluminum alloy elements

1 set of connecting stubs (3)

Universal U Clamps for masts to 1 1/2" Diameter Beam Selector

75 feet of Tri-X Cable

1 stacked array per carton

AX-56 Directronic, 6 element Single \$ 9.05

AX-56B Directronic, 12 element Stacked \$ 14.25

AX-59 Directronic, 9 element Single \$ 9.95

All above antenna prices include Tri-X Cable and Switch

SOLD ONLY BY MAIL BY NATIONAL ELECTRONICS

## Rocket All Channel CONICAL KITS

This sturdy, all-aluminum constructed TV antenna is designed for broad-band reception on all TV channels, plus FM, High Gain, 4 to 1 front to back ratio. For use with 72-150-300 ohm lines. Low inception angle.

METROPOLITAN KIT F-44 No. 1 \$8.95

FRINGE AREA KIT F-44X No. 2 \$13.95

Rocket Conical Kits contain same accessories as Yagi Kits above.

Any merchandise listed above may be purchased separately at prices shown.

SOLD ONLY BY MAIL BY NATIONAL ELECTRONICS. Prices subject to change without notice. All prices F.O.B. Cleveland—Do not remit more than complete purchase price. Pay shipping charges on receipt of goods. 25% on C.O.D. orders, please. Money back guarantee.

For Faster Service, Address Desk RN-1

# National Electronics OF CLEVELAND

THE HOUSE OF TV VALUES

Delco Building • Cleveland 3, Ohio

sulting from contact potential effects in diode elements. Contact potential may upset static balance between the halves of the circuit.

In FM detector circuits that are properly balanced maximum AM suppression occurs at that frequency corresponding to the crossover of the detector characteristic. A crystal circuit is somewhat more susceptible to residual amplitude modulation than a 6AL5 duo-diode circuit.

The load resistance in a crystal type ratio detector circuit has some effect upon circuit sensitivity as well as upon AM reduction. Sensitivity as used here indicates the ratio of the d.c. voltage across the holding condenser to the r.f. voltage across the secondary of the input transformer.

On the basis of experimental curves showing circuit performance with load resistances varying from 5000 to 50,000 ohms, it has been found that the circuit is most stable when the load resistance is kept small with respect to the back resistance of the crystals. Values from 15,000 to 20,000 ohms are a nice compromise among the variety of factors which obtain.

In some respects a crystal circuit is superior to a vacuum tube circuit for AM suppression, but for an off-tune signal, background noise is quite likely to be greater. On the other hand, a crystal circuit is simpler to align than a vacuum tube circuit, by virtue of elimination of contact potential imbalance effects.

A ratio detector circuit may be adjusted for virtually any pair of crystals, but the AM reduction will vary from pair to pair, because of the degree of variability in the dynamic forward characteristics. With random selection of crystals an AM reduction factor of about 0.025 is possible, while with careful selection of crystals matched for similar forward dynamic characteristics the AM reduction factor is better than 0.010.

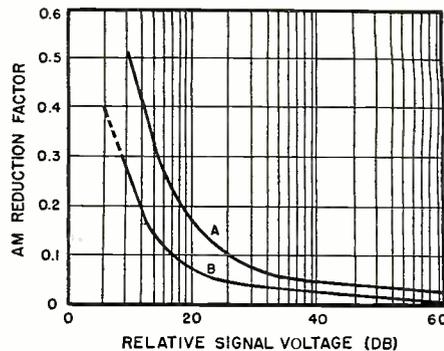


Fig. 12. Effect of single crystal diode dynamic limiter on AM reduction factor for shunt crystal diode ratio detector. (A) Crystal diode ratio detector only. (B) Crystal diode ratio detector and dynamic limiter.


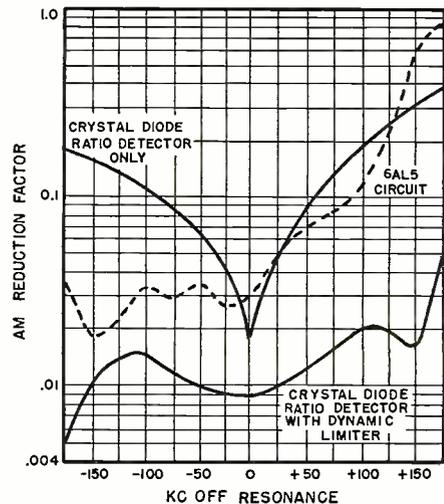


Fig. 13. The effect of a single diode dynamic limiter on the AM reduction factor over entire band of operating frequencies.

Fig. 14. Dynamic limiter and ratio detector with (A) single and (B) double diodes.

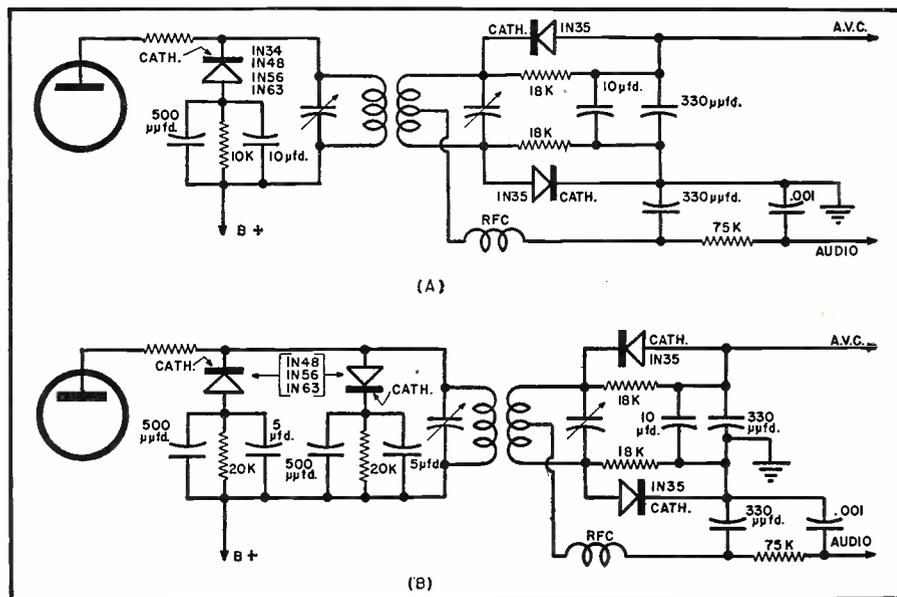

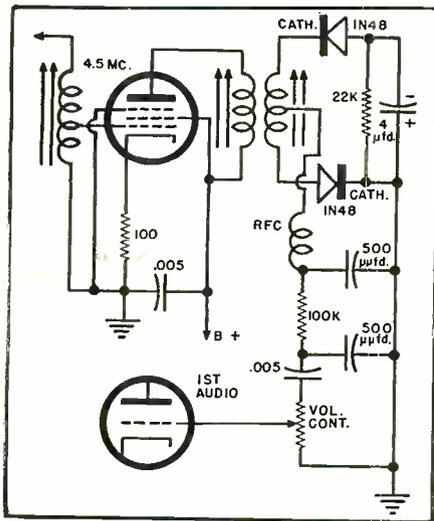


Fig. 15. One manufacturer's commercial adaptation of a ratio detector circuit.

stantial degree of AM suppression in itself a dynamic limiter tends to minimize the necessity for AM suppression by the ratio detector.

In such a combination germanium diode circuit crystal selection may be eliminated in the ratio detector stage. This is because a dynamic limiter extends AM suppression to lower input signal levels and over a wider frequency deviation range from the mean signal frequency. Fig. 12 and Fig. 13 show the AM reduction factor as a function of signal level both with and without the dynamic limiter.

In summary, then, a crystal diode shunt type ratio detector combined with a crystal diode dynamic limiter will provide an audio output comparable to that obtainable with the conventional duo-diode tube ratio detector of the 6AL5 type. A suggested circuit is shown in Fig. 14.

Fig. 15 shows a commercial application of the 1N48 to a good ratio detector circuit.

(To be continued)

## NEW RADIO-RELAY PLANNED

**T**HE Long Lines Department of the American Telephone and Telegraph Company has revealed plans for a radio-relay system to operate between Pittsburgh, Pa. and St. Louis, Missouri.

An existing relay system which now connects Columbus, Dayton, and Indianapolis would make up the central section of the proposed route. When completed, the system, including the Columbus-Indianapolis section, will represent an investment of about 9 million dollars.

The new system would be the second east-west microwave route across the midwest. It will augment cable and wire facilities and will tie-in to the coast-to-coast microwave highway at Pittsburgh.

The new relay system is to have a total of 24 microwave stations. Expected to be ready in mid-1953, the new route will provide, initially, hundreds of telephone message circuits. When fully developed it will provide over a thousand message circuits and several television channels.

-30-

January, 1952

greatest adventure of our time!

Despite 101 days of salt spray and even total immersion, a National transmitter and receiver kept the world-famed Kon-Tiki Expedition in touch with the world! Now the same rugged dependability is yours in the amazing SW-54, the "Mighty Midget" broadcast and shortwave receiver (540 kcs. to 30 mcs.). Measures only 11" x 7" x 7". Write for details and name of nearest supplier!



## LAST OF THE HI WATTERS!

**150-WATT GENERAL ELECTRIC BC-375-E RADIO TRANSMITTER**

Voice & Code to 1,000 miles and more! Includes 5 tuning units, 3 plugs, aut. tuning unit, dynamotor, tubes, etc., ready to use. U. S. Govt. surplus. Tropicalized. Use in boats, trucks, at airports, on farms. MANY OTHER USES. Price upon request.

Converted to Crystal Control, 1 tuning unit. . . \$225.00


**POWER SUPPLY UNIT**, in 115 V. A.C.; out 24-28 V. D-C, 30 A., for BC-375-E, \$150.00; 230 V. model available.

## OTHER GOV'T SURPLUS SPECIALS

- ANTENNA KNIFE-SWITCH SW-225.** Square D Co. #1513-DAY-44, 3-pole, 2 pos., on pore, posts 2 1/2" high; base 7 1/2"x8"x1/4". Sig. C. #328223. NEW, bxd. ea. \$1.95
  - HEADSET ADAPTER MC-385-C.** Matches hi to low imp., for HS-33 or HS-38. Has jack for PL-55. Sig. C. #4AK985C. NEW cond., bxd. . . . . ea. 65c
  - CONTROL UNIT RM-23.** Permits patching 6 radio receivers to 5 phone channels. P/o KC-76, -168. Sig. C. #2C679-23. NEW cond. . . . . ea. \$29.95
  - CONTROL UNIT RM-25.** Permits intercom. P/o SCR-561, -572, -642. Sig. C. #2C679-25. NEW. ea. \$49.95
  - DYNAMOTOR PE-94.** In 28 V. D-C; out 14.5 V. D-C, 4.2 A., 300 V. D-C, 260 ma., and neg. bias, 150 V. D-C, 10 ma. P/o SCR-522. Sig. C. #3H1894C. Good used cond. F.O.B. Kingman, Ariz. . . . . ea. \$6.95
  - WRITING STANDS MC-308-B.** Holds tape for writing. P/o Facsimile Eqpt. RC-58. Sig. C. #6M2200B. NEW cond., ideal for memos., skeds, etc. . . . . ea. \$1.98
  - CORD CD-605.** 2 tinsel conductors, 6 1/2 ft. long; eye-lets, spades. Sig. C. #3E1603-6.3. NEW. . . . . ea. 13c
  - CONNECTORS:** 4106-P, w/AN-3054-24 (Rumson Co.) AN-3108-36-9S (Amphenol). . . . . ea. \$5.95
  - AN-3102-22-10P (Amphenol). . . . . ea. .49
  - RSK-82-23C-34" Plug, w/RSK-82-31SL Socket (Cannon) . . . . . set 1.49
- Many more types available, including UG.

Minimum sale \$2.00; subject to prior sale; F.O.B. N.Y.C.; 20% with order, balance C.O.D. Prompt shipment.

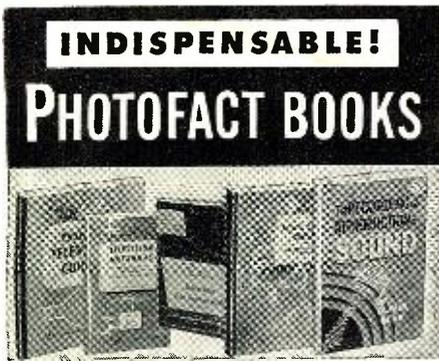**COMPONENTS SUPPLY CO.** 161 Washington St. Dept. RN—New York 6, N. Y. BEekman 3-8717



**Photofact Television Course.** Covers TV principles, operation and practice. 216 pages; profusely illustrated; 8 1/2 x 11". Order **TV-1**.....Only **\$3.00**

**Television Antennas. New 2nd edition.** Describes all TV antenna types; tells how to select, install, solve troubles. Saves time; helps you earn more. 200 pages; illustrated. Order **TAG-1**.....Only **\$2.00**

**Television Tube Location Guide. Volume 2.** Accurate diagrams show position and function of all tubes in hundreds of TV sets; helps you diagnose trouble without removing chassis. 224 pages; pocket-size. Order **TGL-2**. Only **\$2.00**

**Television Tube Location Guide. Vol. 1.** Over 200 pages of TV receiver tube position diagrams on hundreds of models. Order **TGL-1**.....Only **\$1.50**

**Making Money in TV Servicing.** Tested proved methods of operating a profitable TV service business. Covers all important phases. Authoritative, valuable guide to success. Over 130 pages. Order **MM-1**.....Only **\$1.25**

**Servicing TV in the Customer's Home.** Shows how to diagnose trouble using capacitor probe and VTVM. Short-cut methods help save time, earn more on outside service calls. Order **TC-1**.....Only **\$1.50**

**1949-1950 Record Changer Manual. Vol. 3.** Covers 44 models made in 1949, including multi-speed changers and wire and tape recorders. Original data based on actual analysis of equipment. 286 pages; 8 1/2 x 11"; paper-bound. Order **CM-3**.....Only **\$3.00**

**1948-1949 Changer Manual. Vol. 2.** Covers 45 models made in 1948-49. Paper bound. Order **CM-2**. Only **\$4.95**

**1947-1948 Changer Manual. Vol. 1.** Covers 40 post-war models up to 1948. Order **CM-1**.....Only **\$3.95**

**Recording & Reproduction of Sound.** A complete authoritative treatment of all phases of recording and amplification. 6 x 9". Order **RR-1**.....Only **\$5.00**



**Audio Amplifiers. Vol. 3.** Clear, uniform, accurate data on 50 important audio amplifiers, plus full coverage of 22 FM and AM tuners, produced during 1950. 362 pages, 8 1/2 x 11". Order **AA-3**.....Only **\$3.95**

**Audio Amplifiers. Vol. 2.** A complete analysis of 104 well-known audio amplifiers and 12 tuners made 1949-50. 368 pages, 8 1/2 x 11". Order **AA-2**.....Only **\$3.95**

**Audio Amplifiers. Vol. 1.** 102 amplifiers and FM tuners made through 1948. 352 p. Order **AA-1**.....Only **\$3.95**

**Auto Radio Manual.** Complete service data on more than 100 post-war auto radio models. Covers over 24 mfrs. 350 pages, 8 1/2 x 11". Order **AR-1**.....Only **\$4.95**

**Communications Receiver Manual.** Complete analysis of 50 popular communications models. 246 pages, 8 1/2 x 11". Order **CR-1**.....Only **\$3.00**

**Radio Receiver Tube Placement Guide.** Accurate diagrams show where to replace each tube in 5500 radio models, covering 1938-1947 receivers. 192 pages, pocket-size. Order **TP-1**.....Only **\$1.25**

**Dial Cord Stringing Guide. Vol. 2.** Covers receivers made from 1947 through 1949. Shows you the one right way to string a dial cord in thousands of models. Pocket-size. Order **DC-2**.....Only **\$1.00**

**Dial Cord Guide. Vol. 1.** Covers sets produced 1938 through 1946. Order **DC-1**.....Only **\$1.00**

Order from your Parts Jobber or write direct to  
**HOWARD W. SAMS & CO., INC.**, 2201 E. 46th St., Indianapolis 5, Indiana  
**HOWARD W. SAMS & CO., INC.**

**Mac's Service Shop**  
(Continued from page 62)

forming other jobs of mechanical manipulation in very restricted quarters. When working on live receivers, it is a good idea to slip a length of spaghetti over the shanks so that you will not short out anything."

"And don't forget to mumble 'This may hurt a little' before you start using them on a set," Barney advised. "But how about the automobile mechanics? Did they watch you too closely for you to steal any of their stuff?"

"Borrow' is the word," Mac corrected with a pained expression; "and I did get some tools and ideas at the garage. Notice these three additions to our pliers department: that big, loose-jawed pair is known as water-pump pliers, and they are just the stuff for grabbing hold of a can-type electrolytic and holding it solidly while you unscrew the big mounting nut. For that matter, they are also fine for starting those nuts or for acting as a wrench on any outside nuts for which we do not ordinarily have an end-wrench. The pliers with the short powerful jaws are called battery pliers, and they are fine for any job where you need some extra leverage. The tiny little pliers are ignition pliers, and they have a dozen uses around the shop. For example, they can be used for loosening or tightening the nuts that hold speaker spiders, for loosening speaker mounting nuts when the bolts are so long that our spintite wrenches will not reach them, or for doing any job where you need to grip something firmly in a space where there is no room for ordinary pliers."

Before continuing, Mac opened a box sitting beneath the bench and revealed a brightly-painted little bench-grinder. "I was shamed into buying this," he said with a grin. "The other night Homer Frank, my favorite garage mechanic, was loafing here while I turned out a few sets. He got to prowling around in the tools and nearly had a fit when he saw our collection of drills, punches, chisels, and screwdrivers, which he insisted was the sorriest lot he had ever seen outside of a toy tool chest! Then he *did* have a fit when he wanted to sharpen them and I told him we had no electric grinder.

"Homer declared that tools ought not be sold to a man who was too tight to buy equipment to maintain them. He said the emery wheel in his garage got more of a workout than any other power tool in the shop. He pointed out that if we had a grinder here we could keep our chisels sharp, our punches punching, our screwdriver bits square, and our bits so they would cut. He kept insisting that he could punch a hole quicker using a nail for a drill than I could using some of the bits we have in our collection. After listening to about twenty minutes of that kind of talk I promised to buy a grinder just

\*\*\*\*\*  
**WANTED WE NEED YOUR**  
**Surplus Electronic Equipment!**  
**WE PAY TOP \$\$\$ FOR:**  
 Radio Receivers | An Connectors  
 Transmitters | Clamps  
 ARC-1 | Plugs  
 ARC-3 | Cords  
 ART-13 | Relays  
 Control Boxes | Telephone Materials  
 Indicators | WE BUY ANYTHING!!  
**WRITE, WIRE, TODAY!**  
 TELL US WHAT YOU HAVE  
**TALLEN COMPANY, INC.**  
 Dept. RN, 159 Carlton Ave.  
 Brooklyn 5, N. Y.  
 \*\*\*\*\*

**CASH IN ON FRINGE AREA SALES**  
*with the sensational*

**DAVIS SUPER RHOMBIC ANTENNA**

- Eliminates ghosts!
- Eliminates costly stacked arrays!
- Gives all-channel coverage with gain of over 12 DB!
- Features exclusive 15-degree tilt to take advantage of horizontal wave lengths.
- Extensively lab and field tested. Constructed with aluminum alloy elements that out-perform copper wire rhombics.
- Space tapered elements construction gives automatic match to all commonly used lead-ins without matching transformer.
- Super-sensitive 12-degree directivity for maximum distance (DX) reception and ghost elimination.
- Pre-assembled, lightweight construction cuts installation time to minutes!

**TO: DAVIS ELECTRONICS** 1-1  
 3047 W. Olympic Blvd., Los Angeles 6, California  
 Sir: Rush information to me as checked below:  
 Send free technical data on Super Rhombic Antenna.  
 Send name and address of nearest jobber.  
 Name \_\_\_\_\_  
 Street \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_

to shut him up; but I've got a sneaking suspicion he was right to a certain extent."

"Well, it certainly does me a lot of good to know that you were on the receiving end of a currying for once," Barney commented. "My only regret is that I was not here to listen to him pour it on."

"Never mind that," Mac told him. "The point I want you to keep in mind is that we can speed up our own work a lot if we will keep our eyes open for tools and techniques employed in other lines of service work that can be used to advantage in our shop."

"Hm-m-m-m," Barney said, thoughtfully stroking his chin, "you have something there; and I'm going to look into another form of repair and maintenance shop this very noon-hour."

"And where would that be?" Mac asked suspiciously.

"At that beauty shop on the next corner," Barney explained. "There's the cutest little redhead working in there who has been giving me the eye every day when I go to lunch; so today I'll just drop in and casually ask—"

Before he could finish the sentence Mac grabbed up the cardboard box in which the grinder had been and crushed it down over the boy's ears.

-30-

### CIVIL DEFENSE FILM

General Electric Company recently previewed a new film which evaluates the need for a good, efficient communications system in times of emergency.

Produced by the March of Time for G-E, the new film has been entitled, "A Voice Shall Be Heard".

Emphasizing the use of two-way radio in the community, the film graphically illustrates the operation of a centrally-controlled communications set-up and its coordination of mobile units. It first evaluates the part two-way radio plays in peacetime and then considers its requirements in an Atomic War. The film points out the need for this type of communication to be used when all other types of communications are inoperative.

The film unfolds the story of Syracuse under an atomic attack and portrayed the effectiveness of its civil defense measures. The destruction of Syracuse is depicted in such a manner that the viewer is able to foresee the possibility of this destruction in his own community.

The company is making this film available for local showings through many of its local offices. All that is required is that organizations contact the nearest office to schedule a showing of this film.

The following General Electric offices will be handling the film: 113 South Salina Street, Syracuse, New York, c/o H. M. Wales; 187 Spring Street, Atlanta 3, Georgia, c/o J. W. Bryant; 2511-13 Book Tower, Detroit 26, Michigan, c/o R. L. Casselberry; 106 W. Fourteenth St., Kansas City 6, Mo., c/o C. G. Turner; 901 Ross Avenue, Dallas 2, Texas, c/o J. W. Rondel; and 235 Montgomery St., San Francisco 6, California, c/o L. R. Sheeley.

-30-

ELECTRIC  
SOLDERING  
IRON

# ROSE Co's SENSATIONAL

## FREE GIFT OFFER

### FREE! This Superior Electric SOLDERING IRON. What every serviceman needs! Yours absolutely FREE!

### TUBES VERY LOWEST PRICES

Receiving-Transmitting-TV

RMA GUARANTEED—STANDARD BRANDS

0Z4 . . . . . \$ .59	6B07 . . . . . \$2.29	12BE6 . . . . . \$ .79
1A5 . . . . . \$ .89	6C4 . . . . . \$ .79	12BH7 . . . . . \$ 1.19
1A7 . . . . . \$ 1.09	6CB6 . . . . . \$ .89	12BY7 . . . . . \$ 1.19
1B3 . . . . . \$ 1.19	6CD6 . . . . . \$ 2.69	12BZ7 . . . . . \$ 1.09
1H5 . . . . . \$ .79	6D6 . . . . . \$ 1.09	12S47 . . . . . \$ .89
1LN5 . . . . . \$ 1.19	6J5 . . . . . \$ .69	12S47 . . . . . \$ .79
1R5 . . . . . \$ .99	6J6 . . . . . \$ 1.29	12S17 . . . . . \$ 1.19
1T4 . . . . . \$ .99	6K6 . . . . . \$ .79	12S7 . . . . . \$ .99
1U4 . . . . . \$ .89	6L6 . . . . . \$ 1.79	12S07 . . . . . \$ .69
1V2 . . . . . \$ .69	6Q7 . . . . . \$ .99	14A7 . . . . . \$ 1.09
1X2A . . . . . \$ 1.19	654 . . . . . \$ .79	14B6 . . . . . \$ 1.09
3Q5 . . . . . \$ 1.19	658 . . . . . \$ 1.29	14Q7 . . . . . \$ 1.09
5U4 . . . . . \$ .79	65A7 . . . . . \$ .79	19B6G . . . . . \$ 2.99
5V4 . . . . . \$ 1.39	65K7 . . . . . \$ .79	19J6 . . . . . \$ 1.59
5Y3 . . . . . \$ .49	65L7 . . . . . \$ 1.19	19T8 . . . . . \$ 1.39
6A6 . . . . . \$ 1.19	65Q7 . . . . . \$ .69	25B06 . . . . . \$ 1.49
6AB4 . . . . . \$ .89	6T8 . . . . . \$ 1.39	25L6 . . . . . \$ .79
6AC7 . . . . . \$ 1.39	6V6 . . . . . \$ .89	25W4 . . . . . \$ .89
6AG5 . . . . . \$ 1.19	6W4 . . . . . \$ .79	35A5 . . . . . \$ .89
6AH6 . . . . . \$ 1.89	6W6 . . . . . \$ .99	35B5 . . . . . \$ .99
6AK5 . . . . . \$ 1.89	6X4 . . . . . \$ .69	35C5 . . . . . \$ .99
6AL5 . . . . . \$ .79	7C4 . . . . . \$ .89	35L6 . . . . . \$ .79
6AQ5 . . . . . \$ .89	7C5 . . . . . \$ .89	35W4 . . . . . \$ .59
6AT6 . . . . . \$ .69	7F8 . . . . . \$ 1.59	35Y4 . . . . . \$ .89
6AUS . . . . . \$ 1.29	12AL5 . . . . . \$ .89	35Z5 . . . . . \$ .59
6AU6 . . . . . \$ .79	12AT6 . . . . . \$ .69	39/44 . . . . . \$ .49
6AV5 . . . . . \$ 1.29	12AT7 . . . . . \$ 1.29	50A5 . . . . . \$ 1.09
6BA6 . . . . . \$ .79	12AU6 . . . . . \$ .89	50B5 . . . . . \$ .89
6BC5 . . . . . \$ .89	12AU7 . . . . . \$ 1.19	50C5 . . . . . \$ .89
6BE6 . . . . . \$ .89	12AV6 . . . . . \$ .69	50L6 . . . . . \$ .89
6BG6 . . . . . \$ 1.99	12AV7 . . . . . \$ 1.29	50Y6 . . . . . \$ .89
6BH6 . . . . . \$ .99	12AW6 . . . . . \$ 1.29	80 . . . . . \$ .59
6BJ6 . . . . . \$ .89	12AX4 . . . . . \$ 1.09	117L7 . . . . . \$ 1.89
6BL7 . . . . . \$ 1.39	12AX7 . . . . . \$ 1.19	117Z3 . . . . . \$ .69
6BN6 . . . . . \$ 1.29	12AY7 . . . . . \$ 3.69	117Z6 . . . . . \$ 1.19
6BQ6 . . . . . \$ 1.49	12BA6 . . . . . \$ .79	807 . . . . . \$ 1.79



\* Nickel Chrome Wire Heating Element  
\* Handsomely Plated Shaft  
\* Replaceable Tips  
\* U.L. & C.S.A. Approved

For a limited time, The ROSE Co. is offering, absolutely FREE, this wonderful new Soldering Iron to its customers. With each order of \$25 you get FREE this 75 Watt Electric Soldering Iron. A \$50 order brings you a 100 Watt Soldering Iron or two (2) 75 Watt Irons. A 75 Watt Iron for each \$25 order. Be sure to mention when you write with your order. Act quickly—order NOW! GET THIS SUPERIOR ELECTRIC SOLDERING IRON NOW . . . ABSOLUTELY FREE. We're sorry that this offer does not include TV Chassis, Picture Tubes, or complete radios.

### TV PICTURE TUBES

Full Year's Guarantee—Not Pro-Rated—Black Face—Brand New—Standard Brands—Sealed Cartons.

10BP4 . . . \$24.95	16GP4 . . . \$31.95	19AP4A . . \$37.95
12LP4 . . . \$24.95	16HP4 . . . \$33.95	20CP4 . . . \$37.95
14BP4 . . . \$24.95	17BP4 . . . \$29.95	24BP4 . . . \$69.95

### SPEAKERS

All Alnico V—  
Every one a Buy!

4" P.M. . . \$1.59 ea.  
5" P.M. . . 1.69 ea.  
6" P.M. . . 1.89 ea.  
8" P.M. . . 2.95 ea.  
4"x6" P.M. . . 1.79 ea.  
6" G2 ohm with output . . . 3.75 ea.  
4"x6" 1500 ohm with output . . 3.49 ea.

DEDUCT 5% from price of any Speaker in lots of 10 or more. May be assorted. ORDER NOW before cabinet freeze advances prices!

### GENUINE MOLDED CONDENSERS


Fresh Stock—All Mineral Oil Filled—100% Centigrade—Meets Jan. 291 Tests. ALL 600 VOLTS.

Cap. Per 100	Per 100
.001 . . . \$ .79	\$ 6.90
.002 . . . . .	.79 6.90
.005 . . . . .	.79 6.90
.01 . . . . .	.89 7.90
.02 . . . . .	.99 8.90
.1 . . . . .	1.09 9.90
.1 . . . . .	1.25 11.50

May be asst. for 100 lot prices!
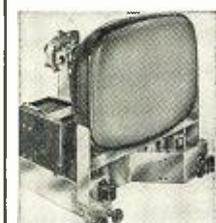
### The Great 630 SUPER CHASSIS

Bargain Priced for Terrific Savings!  
30 Tubes—RCA Lic.—For 16" to 24" Picture Tubes



- High efficiency high voltage circuit
- Keyed AGC
- Automatic brightness control
- Special extra-high gain standard coil tuner
- Directly adaptable for color
- 12" Quality speaker
- Factory wired, aligned & tested
- Complete, ready to play
- Including hardware & knobs

**\$144.50**  
(less CRT)

630DX Chassis, 3 times normal reception of regular chassis. Needs no complicated antenna or booster.  
Reduced to **\$159.50** (less CRT)  
FREE OFFER: Schematic diagram FREE with any chassis ordered!

### Rose Saves You Plenty!

### ELECTROLYTIC CONDENSERS

All Guaranteed Fresh Stock!

	Each	Lots of 10	Lots of 100
20x20—150 V. . . . .	\$ .39	\$3.70	\$34.95
40x40—150 V. . . . .	.45	4.30	39.95
50x30—150 V. . . . .	.45	4.30	39.95
50x50—150 V. . . . .	.49	4.50	41.95
40x40x20—150 V. . . . .	.69	6.70	59.95
50x30x20—150 V. . . . .	.69	6.70	59.95
50x50—150 V. (200-25 V.)	.79	7.70	69.95
35—25 V. . . . .	.19	1.50	13.50
25—50 V. . . . .	.19	1.50	13.50
20—250 V. . . . .	.29	2.59	23.95
8—120 V. . . . .	.39	3.69	32.50
10—450 V. . . . .	.39	3.69	32.50
16—450 V. . . . .	.59	5.69	49.50

Order Now! Save Now!  
May be asst. for 100 lot prices!

NOW AVAILABLE . . . FREE! Write for new catalog including complete listings of tubes, parts, accessories for radio and TV and special test equipment catalog for instruments and kits!  
MINIMUM ORDER: \$5.00. 25% deposit with order, balance C.O.D. Include postage with order. All merchandise subject to prior sale, F.O.B. New York, N. Y.  
ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE



# THE ROSE COMPANY

102 Park Place Dept. R-1 New York 7, N. Y. CORtland 7-6195

### WANTED!

ALL TYPES AIRCRAFT, RADAR, RADIO SETS, COMPONENTS, DYNAMOTORS AND ASSOCIATED EQUIPMENT. Such as ART-13, BC-611, Test Equipment, Etc.

WE PAY TOP DOLLAR!  
WEST REGION ELECTRONICS  
1437 South Norton Ave., Los Angeles 19, California

### RADIO COURSES

- RADIO OPERATING • CODE
  - RADIO SERVICING • ELECTRONICS
  - F.M. TELEVISION
  - PREPARATION FOR CIVILIAN, MARITIME, ARMY AND NAVY LICENCE REQUIREMENTS.
- Write for Catalog T.S.

Y.M.C.A. TRADE & TECH. SCHOOL 15 W. 63 ST., N. Y. 23 INdicott 2-8117

### WANTED

Highest prices paid for surplus equipment parts and tubes. Offer us your surplus test equipment. PE 104 Power Units; IN 106 Insulators; Hand Generators GN 45; BC 610 Coils; Tuning Units; Transformers; Antenna Loading Coils BC 939-A; Frequency Meters BC 221; Rectifier RA 34 & Receivers BC 312, BC 342 and BC 348.

RADCOM ENGINEERING COMPANY  
8 Livingston Street Newark 3, N. J.

# PEAK FOR VALUE!

## CARTER MOBILE DYNAMOTOR

6 Volt DC Input, 400 Volts at 375 MA. Output. Model No. 4037AS. 7" Long, 4" Wide, 3 1/2" High, 1.0 lbs. (List Price \$70.00) **\$24.95**

**SENSITIVE RELAY**  
D'Arsonval moving coil type, mounted in meter case. Adj. 700 microamps to 1 ma. Made by Triplet. ea. **\$5.75**

**6 VOLT DC RELAY**  
Small Size. Ideal for Mobile Use, SPDT **\$0.99**

## PANEL METERS

NEW GOV'T SURPLUS STANDARD BRANDS  
\*Special Sale

**2" METERS**

0-1 MA ..... \$3.95  
0-2 MA ..... 2.25  
0-5 MA ..... 1.75  
0-30 MA ..... 2.75  
0-50 MA ..... 2.75  
0-100 MA ..... 2.45  
0-200 MA ..... 2.95  
0-300 MA ..... 2.95  
0-10 MA AC ..... 2.95  
0-2 AMP RF ..... 2.95  
0-50 AMP AC ..... 3.25  
0-30 AMP DC ..... 2.95

**3" METERS**

0-1 MA ..... 3.95  
0-1 MA ..... 4.95  
0-2 MA ..... 4.50  
0-50 AMP AC ..... 5.95  
0-2.5 AMP RF ..... 5.95  
0-100 VDC (1 MA) ..... 5.95  
0-250 VDC (1 MA) ..... 5.95  
0-250 VDC (1 MA) ..... 5.95  
0-750 VDC (1 MA) ..... 7.95  
0-4 KW DC (1 MA) ..... 7.95  
0-150 VAC ..... 6.95  
0-300 VAC ..... 6.95

**FILTER CHOKES**

10 Hy 175 MA ..... \$2.25  
10 Hy 250 MA ..... 3.95  
10 Hy 350 MA ..... 3.95  
6 Hy 500 MA ..... 4.95  
6 Hy 400 MA (Rusty) 2.95

**PIGTAIL MICAS**

MMF: 5, 20, 50, 60, 100, 250, 300, 400, 500, 750, 800, 1000, 2000, 3000, 4000, 5000, 6000  
10000 ..... \$0.09 ea.

**Silver Mica Capacitors**

MMF: 10, 50, 60, 340, 750, 780, 1000, \$0.12 ea.

**Non-Inductive Resistors**

Ohms: 500, 2000, 12,500  
100 watts ..... \$0.75

**FILAMENT TRANSFORMER**

6.3 Volts at 10 Amps plus 2.5 Volts CT at 12 Amps. 3500 Volt insulation. Primary 115 Volt, 60 Cy. Fully shielded. \$2.99 ea.

**BAKELITE CASSED MICAS**

MFD	VDC	Price	MFD	VDC	Price	MFD	VDC	Price
.001	600	\$1.18	.001	1500	\$0.65	.001	5 KV	\$1.60
.002	600	.24	.033	1500	.75	.002	5 KV	1.60
.01	600	.26	.02	2 KV	.90	.003	5 KV	1.90
.02	600	.26	.005	2500	.45	.005	5 KV	2.50
.01	1 KV	.45	.004	2500	.50	.001	6 KV	2.50
.002	1200	.35	.0001	5 KV	.70	.002	6 KV	2.90

**WIRE WOUND RESISTORS**

5 watt ohms: 25-50-84-200-2500 ..... \$0.09 ea.  
10 watt ohms: 25-40-125-250-2K-4K ..... .15 ea.  
20 watt ohms: 150-300-750-1K-1.5K ..... .20 ea.  
2.5K-2.7K-10K-20K ..... .20 ea.  
30 watt ohms: 100-250-500-18K ..... .22 ea.  
100 watt ohms: 100-3750-1500-2K, 10K, 15K, 20K, 100K ..... .59 ea.

**POWER SUPPLY KIT**

1-UTC Power Transformer 700 VCT @ 60 ma, 5V 2A, 6.3 @ 1.2A  
2-UTC 60 ma chokes. Transformer and chokes fully cased, transf. & 2 chokes. SPECIAL \$3.95

**ADJUSTABLE SLIDER RESISTORS**

20 Watt: 1.5 Ohms ..... \$0.25  
50 Watt: 500 Ohms ..... .42  
75 Watt: 100, 150, 200 Ohms ..... .39  
100 Watt: 50, 3750 ..... .69

**MISCELLANEOUS BARGAINS**

Ceramics .0005 mfd ..... 7 for \$0.49  
Ceramics .0002 mfd ..... 7 for .49  
.05 600V Oil Tubular ..... 2 for .99  
10K, 15K Pots ..... 4 for .99  
Air Padder 50 W/M/A APC50 ..... .39  
.01 MFD, Molded Paper Cond. .... 20 for .39

## PEAK ELECTRONICS CO.

188 WASHINGTON ST., NEW YORK 7, N. Y.  
Phone COrtlandt 7-6443-4

## Audio Simplified

(Continued from page 56)

from the equivalent circuit of Fig. 4B. The circuit at middle frequencies is used for this calculation, and the gain at high and low frequencies obtained from the frequency response curve. The formula used for this calculation is:

$$Gain = -\mu \frac{R_L}{R_p + R_L}$$

where  $R_L = (R_p R_C) / (R_B + R_C)$  is the total resistive load in the plate circuit, and the negative sign indicates that there is a 180° change of phase in a single tube amplifier. For pentodes a more convenient simplified formula is that

$$Gain = -G_m R_L$$

which is approximate but fairly accurate, because of the high plate resistance of pentodes.

(b) The output impedance of the tube is important when matching to attenuators, equalizers, transmission lines, and various other types of networks. It can be determined from the equivalent circuit of Fig. 3. The grid resistor generally does not exist in such circuits, and the tube circuit is considered to consist of the circuit elements up to this point, as shown in Fig. 3A. The output impedance at middle frequencies therefore appears as a resistance equal to the parallel combination of the plate load resistor and the tube plate resistance  $(R_p R_B) / (R_p + R_B)$  in series through the coupling condenser, as shown in Fig. 3B.

(c) Frequency response can be predicted from the equivalent circuits at high and low frequencies shown in Fig. 4B, together with the curves of Fig. 4C. The coupling condenser and the following grid resistor give the low frequency response, while the total shunt capacity and the load resistance give the high frequency response. In determining the high frequency response, it is essential to take the Miller effect of the following tube into account.

(d) Harmonic distortion can be measured from the plate current characteristics of the tube as given in the tube handbook and from the load line. Considering the set of curves shown in Fig. 1A, it can be seen that if +1 volt is added to the grid voltage to change the bias to -1 volt, the voltage at the plate decreases by 35 volts, while if -1 volt is added to the grid voltage to change the bias to -3 volts, the voltage at the plate increases by 35 volts. Therefore for a +1 volt peak grid swing this amplifier is very linear and shows little distortion. However, when +2 volts is added to the grid voltage to change the bias to 0 volts, the plate voltage decreases by 70 volts, while it only increases by 55 volts when -2 volts is added to the grid voltage to change the bias to -4 volts. Therefore, for a +2 volt peak grid swing the amplifier is not linear, and harmonic distortion is introduced into the output

## For Highest Quality and Profits— it's STANDARD WOOD AUDIO & TV CUSTOM CABINETS

**Model RX Bass Reflex Speaker Cabinets** (top): for 15" & 12" speakers. Approximately 10,000 cubic inch capacity. Wider frequency & angle distribution; higher power-handling capacity. Lumite grille; no sag or stain. **Model RP Radio-Phono Cabinets** (middle): perfect companions to Model RX. Top panel for all FM-AM tuners, middle pull-out drawer for all record changers (positions interchangeable); bottom compartment for amplifiers. **Series RP3 Radio-Phono Combination Cabinets** (bottom): compartments for record changer, radio chassis, record storage and 15" or 12" speaker. 36" h, 34" w, 19" d. **All Above Models:** sturdy 3/4" stock, latest acoustic design; rich authentic furniture styling in lustrous Mahogany, Cordovan Mahogany, Walnut, Ebony, Blonde, or Unfinished.



*Beautiful TV CABINETS*  
For Custom-Built Sets or Conversions

**Series 503 TV Cabinets** accommodate all 630 Radio Crafts men & similar chassis, all round & rectangular tubes. Complete with all mountings for tube & yoke. Fidelity-styled in Period, Traditional & Modern; hand-rubbed to high lustre in Mahogany, Walnut, Ebony or Blonde. 40" h, 24" w, 24" d. **Series 505 TV Combination Cabinets** have identical features plus separate compartments for all FM-AM radio chassis, record changers & record storage. 40" h, 40" w, 24" d.

Write NOW for literature and prices.

**STANDARD WOOD PRODUCTS CORP.**

43-02 38th St., L.I.C. 4, New York

## Immediate Delivery of SCARCE RADIO-TV TUBES

**TUBES BOUGHT, SOLD and TRADED**

Send Your Want and Trade List!

Complete Line of TELEVISION PICTURE TUBES

Radio and TV service men, experimenters, amateurs - we have many types of scarce tubes ready for immediate shipment. Don't use make-shifts or spend valuable time looking for tube sources. Try Electro FIRST... and get the tubes you need without delay. Get complete list and Electro's low prices. It's FREE... write today!

**ELECTRO-SALES** 425 W. Randolph St. Chicago 6, Ill.

RADIO & TELEVISION NEWS

signal. This is illustrated graphically in Fig. 6. The maximum signal which can be applied to the grid of the amplifier is that voltage which will still produce linear changes in plate voltage as measured on the plate characteristic curves.

These formulas and curves contain sufficient information for the design of the voltage amplifier stage and for predicting accurately what will be its performance under practical operating conditions.

The complete voltage amplifier consists of a number of amplifier stages designed according to the procedure outlined before, and combined in such a manner as to meet the requirements of the system. In general, these requirements will be: (1) over-all gain, (2) input and output impedance, (3) frequency response, (4) input and output voltages, and (5) distortion. From the specific requirements of the system which is under consideration, it is possible to decide upon a good general tube lineup, choose the specific tube types to be used, the voltage gain of each stage, and the specific values of the circuit components to be used. The actual practical procedures involved in this process can best be illustrated by demonstrating their application to one or two typical amplifier designs.

### Practical Circuits

As the simplest example of a voltage amplifier design, consider the requirements of a voltage amplifier to be used with a standard type of crystal phonograph pickup or a radio tuner. The input voltage to this amplifier will be in the neighborhood of 1 volt, and the output voltage should be at least 10 to 15 volts. Allowing for a reserve amplification of two or three times this amount so that the volume control will not have to be set full up, the required amplification has to be of the order of 30 to 50 times. The volume control is generally placed at the input of this amplifier to prevent overloading with high-level signals. This type of amplifier is used in most radio receivers, therefore a number of important points are illustrated in considering its design features.

The voltage amplifier circuit used in most radio receivers usually consists of a high-gain triode, such as the 6SQ7, in a circuit similar to that shown in Fig. 5A. The amplifier meets the requirements of gain, distortion, and output voltage but it cannot have good response at the higher audio frequencies. The reason for this can be readily understood by considering the Miller effect of the tube, especially when the volume control is set near the middle of its range. Specifically, for a tube gain of 40 the input capacity of the tube is about 85  $\mu\text{fd.}$  or higher; therefore with a 1.0 megohm volume control set halfway up, the response can be as much as 7 to 19 db down at 10,000 cps. The manufacturers of commercial radio receivers may consider this frequency response satisfactory for AM reception, but it is certainly not ac-

# Now

## BLONDER-TONGUE BRINGS YOU FOR THE FIRST TIME IN TV HISTORY

An ALL-CHANNEL MASTER ANTENNA SYSTEM that YOU can install—in a matter of minutes—that is guaranteed to out-perform any other system.

...AND AT THE LOWEST COST!



Distribution Amplifier  
8 TV Outlets at Lowest Cost




Model #DA8-1-M  
\$87.50

Model #DA8-1-M Distribution Amplifier

Full electronic isolation (min. 35db. between outlets). Amplifies as it distributes... Variable Gain Control... No signal loss. Automatic All-Channel transmission. Ordinary screw terminals assure faster, simpler installation.



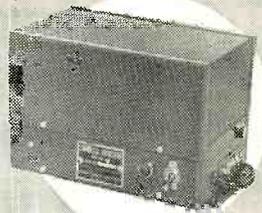MODEL #DA2-1-M  
List Price \$39.50  
Distribution Amplifier  
2 TV-Set Outlets



Model #CA-1-M. List Price \$77.50. Commercial Antensifier (30 Times Gain). Use As Pre-Amplifier, Line Amplifier or de-luxe Booster.

Combine these B-T units to serve up to 2,000 TV sets from 1 antenna.



Literature on Request write Dept. E1  
Mt. Vernon, N.Y.

Model #HA-2-M  
HOME ANTENSIFIER — Fully automatic, all-channel TV booster. 16 times gain. In metal cabinet. 57.50



**RADIO and TELEVISION ELECTRONICS**  
Thorough training for men and women in all Technical phases  
New Classes (Day & Eve.) Start 1st of March, June, Sept. and Dec.  
Free Placement Service For Graduates  
For Free Catalog write Dept. RN-52  
RCA INSTITUTES, INC.  
A Service of Radio Corporation of America  
350 West 4th St., New York 14, N. Y.

**PEN-OSCIL-LITE**  
Extremely convenient test oscillator for all radio servicing; alignment • Small as a pen • Self powered • Range from 700 cycles audio to over 600 megacycles u.h.f. • Output from zero to 125 v. • Low in cost • Used by Signal Corps  
• Write for information.  
**GENERAL TEST EQUIPMENT**  
38 Argyle Buffalo 22, N. Y.

**MARK THESE VALUES!** TOP STANDARD BRANDS ONLY—100% GUARANTEED  
RCA—GE—SYLVANIA—HYTRON—PHILCO—KENRAD—NU—TUNGSO—WESTINGHOUSE—WESTERN ELECTRIC

6SN7 ..... 79c	5U4 ..... 59c	6AL5 ..... 59c	12AU7 ..... 84c
0Z4 .. \$ .64	6AB4 .. \$ .89	6BE6 .. \$ .77	6CD6 .. \$2.25
1B3 .. .89	6AC7 .. 1.16	6BG6 .. 1.89	6J6 .. .98
1L4 .. .73	6AC5 .. .85	6B06 .. 1.29	6K6 .. .64
1R5 .. .79	6AH6 .. 1.48	6CB6 .. .78	6N7 .. .98
1S5 .. .78	6AK5 .. 1.37	6E6 .. .57	6D6 .. \$2.25
1X2A .. .95	6AU6 .. .64	6S17 .. \$ .79	6W4 .. \$ .65
5V4C .. 1.09	6BA6 .. .67	6SK7 .. .79	7F8 .. 1.49
5Y3 .. .46	6BC5 .. .78	6SL7 .. .99	12AT7 .. 1.05
		6T8 .. 1.09	12BA6 .. .77

1000 Kc. CRYSTALS—Laboratory Precision 1.35  
Cut. New. Uncased.....Each

WRITE FOR YOUR FREE BARGAIN LIST NOW.

**MARK electronics** 1888 Randall Ave. New York 72, N. Y.

# NOW! BECOME EXPERT AT RADIO-TELEVISION IN 4 EASY STEPS!



Complete Self-Training Course in RADIO and TV by Famous Experts — Takes You BY SIMPLE STEPS From Basic Theory to Problems of Repair, Installation, Color TV, etc.

NOW you can do ANY Radio-TV installation, service, or repair job like an expert; operate field-testing equipment; understand problems of TV, FM-AM transmission, etc. Step into a good-paying job—or start your own service business. Train yourself AT HOME . . . IN SPARE TIME . . . with the McGraw-Hill Basic Course in Radio and TV.

2296 Pages—  
1611 Illustrations

The men who wrote this complete 4-volume course are among the outstanding radio and TV instructors in America today. Every detail is clearly explained in over TWO THOUSAND PAGES of step-by-step instruction and over SIXTEEN HUNDRED "how-to-do-it" illustrations, cross-section diagrams, etc. The review questions and answers "nail down" everything you learn. At-a-glance "trouble-shooting" charts show how to diagnose instantly any radio or TV breakdown . . . and how to repair it expertly and quickly. The course will pay for itself many times over. It can qualify a beginner for FCC's 1st-Class License test, gives an experienced technician more confidence, shows him new tricks.

### SEND NO MONEY

Mail coupon below to examine complete four-volume course FREE for 10 days. No obligation. Or you may examine individual books FREE for 10 days by checking the proper boxes in coupon. Don't delay. Mail coupon at once!

### PARTIAL CONTENTS ESSENTIALS OF RADIO.

800 pages, 433 illus. Circuit Analysis • Vacuum Tubes • Circuits: Detector • Amplifier • Tube Oscillator • Power Supply • Transmitting, Receiving • Etc. ELEMENTS OF RADIO SERVICING, 475 pages, 375 illus. Multimeters • AC Power Supply • Speakers • Antennas • Auto Radios • Push-Pull Output Stage

BASIC TELEVISION, 592 pages, 415 illus. Scanning • Synchronizing • Video Signal • Brightness Control • Reinsertion • Picture • FM Alignment • Picture Tubes • VHF and UHF transmission • Reception

TELEVISION SERVICING, 429 pages, 388 illus. Antennas • Transmission Lines • Test-pattern and Picture Analysis • Localizing Reception Troubles • Interference Remedies • Deflection Circuits • AND MUCH MORE!

### FREE 10-DAY TRIAL COUPON

McGraw-Hill Book Co., Inc., Dept. RTN-1-52  
327 West 41st St., New York 18, N. Y.

Send me for 10 day free examination the Basic Course in Radio and TV, 4 Vols. (Regular retail price is \$23.75; Special Course Price only \$19.95 in easy installments.) If not satisfied with Course, I will return it, pay nothing. Otherwise, I'll send \$1.95 plus delivery then and only \$3.00 in monthly installments.

If you wish to examine any of these books individually, check below the ones you wish us to send you for 10 Days' FREE EXAMINATION:

- Essentials of Radio, \$6.50  
 Elements of Radio Servicing, \$4.75  
 Basic Television, \$6.50  
 Television Servicing, \$6.00

For any book I keep, I'll send \$2.00 plus delivery in 10 days, balance in easy monthly installments.

Name .....  
Address .....  
City ..... Zone ..... State .....  
Position ..... RTN-1-52  
Company .....

WE PAY FOR DELIVERY if you send first payment of \$1.95 when ordering Course or full price when ordering individual books (prices above). Same return privilege.

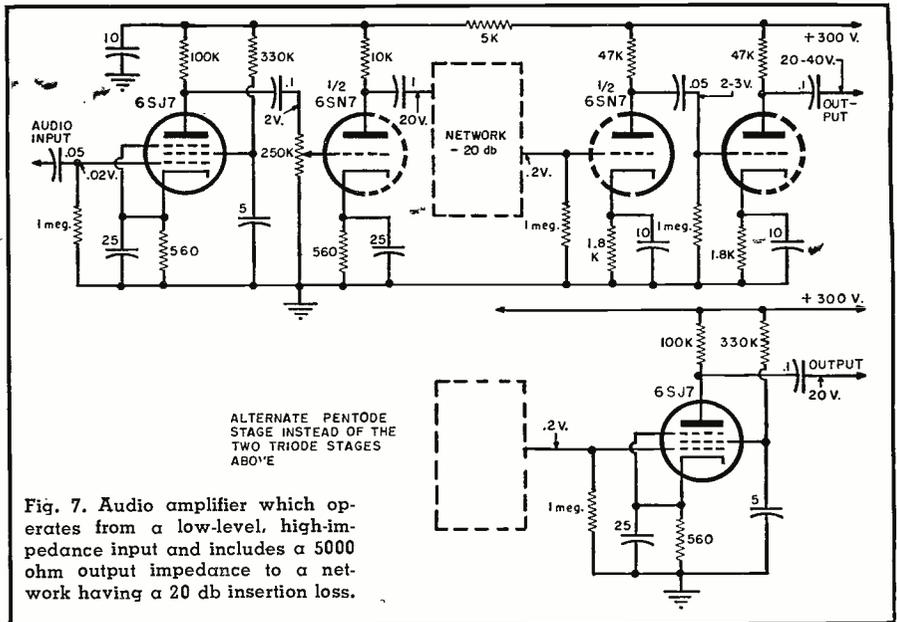


Fig. 7. Audio amplifier which operates from a low-level, high-impedance input and includes a 5000 ohm output impedance to a network having a 20 db insertion loss.


ceptable for high-quality sound reproduction.

A good frequency response in this voltage amplifier can be achieved by using a pentode instead of the high-gain triode stage. A typical pentode voltage amplifier which can be used for this purpose is shown in Fig. 5B. It is a standard pentode amplifier, designed from the tube plate current characteristics as described in this article, and has quite satisfactory gain, output voltage, distortion and frequency response characteristics.

In many applications, a more elaborate voltage amplifier than this is required. Often there may be additional gain and impedance matching require-

ments which must be met. The schematic of such an amplifier, which illustrates the methods of design to meet specific gain and impedance requirements, is shown in Fig. 7. This particular amplifier is designed to give full voltage output to the driver with an input of 0.02 volt at high impedance, and includes sufficient gain to compensate for a 20 db insertion loss network (such as a tone control or mixer circuit), which is fed from a 5000 ohm impedance. The first stage is a pentode, which has an amplification of 100 and whose output feeds into a 0.25 megohm volume control. Because of the Miller effect, the tube after the volume control is a low-gain triode. With

Fig. 8. Circuit of push-pull voltage amplifier with input and output transformers, which has extremely good characteristics suitable for broadcast applications.

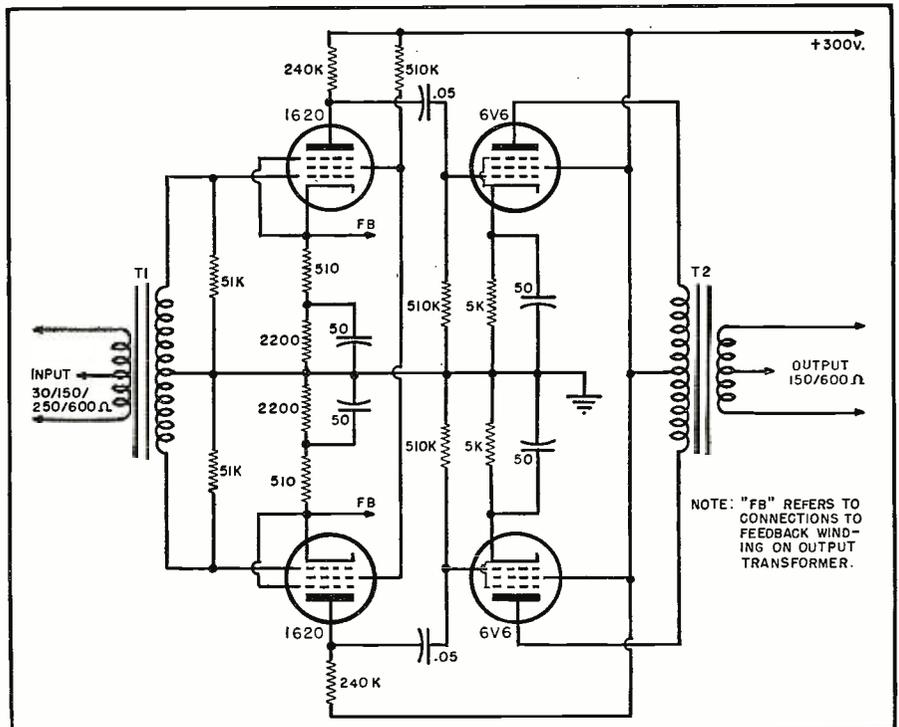

NOTE: "FB" REFERS TO CONNECTIONS TO FEEDBACK WINDING ON OUTPUT TRANSFORMER.

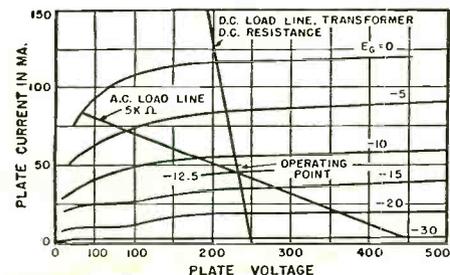


Fig. 9. Curves showing different load lines for d.c. and for a.c. signal when using a transformer in the plate circuit and method for determining operating conditions.

the 6J5 (or one-half 6SN7) and the circuit constants as shown, the input capacity of the tube is about 45  $\mu$ fd., which does not greatly affect the frequency response at any setting of the volume control. From the equivalent circuit, since the plate resistance of the tube is about 7000 ohms, the source impedance which is presented to the network is about 5000 ohms through the 1  $\mu$ fd. coupling condenser. The output of this arbitrary network can then be amplified again either by a two-stage triode amplifier or by a single pentode, as shown in the diagram. The two triodes will have up to 6 db more gain, but either arrangement will have enough gain and supply adequate voltage to the driver. The approximate signal voltage levels at the various points in the circuit are indicated on the schematic diagram.

Some reproducing systems may require voltage amplifiers which are coupled through input and output transformers. The schematic in Fig. 8 shows the circuit of an amplifier of this type which has extremely good frequency response, noise and distortion characteristics, and which has been widely used for broadcast applications. This particular unit is a two-stage push-pull amplifier with a fixed gain of 50 db with various input and output impedances available. The amplifier stages are designed according to the principles described in this article, and illustrate an important point in the design of transformer-coupled stages. It should be noted that the impedance of a transformer is different for direct-current and for alternating-current signals, therefore the static operating point is determined by the d.c. resistance of the winding, while the signal gain is determined by the a.c. impedance reflected into the transformer primary. This is illustrated in the set of curves of Fig. 9. The amplifier shown in Fig. 8 and on page 54 has a frequency response of  $\pm 1$  db from 30-15,000 cycles, and has a 1 watt output at less than 0.5% distortion and up to 8 watts with slightly higher distortion. An amplifier with these characteristics can be extremely useful in setting up a sound reproducing system.

The next article in this series will discuss the application of negative feedback to amplifiers, cathode followers, the design of driver amplifiers and their coupling to the power amplifier. (To be continued)

# ARROW "The Home of Values!"

## CATHODE RAY TUBES

3FP7 --- 1.95	4AP10 --- \$ .95
5FP7 --- 1.95	5GP1 --- 3.95
5BP4 --- 3.95	5CP1 --- 4.95
16JP4 -----	\$19.95
16DP4 -----	19.95

Tubes—304TH.....	\$8.95
304TL.....	8.95
830B.....	2.95

## MISCELLANEOUS SPECIALS!

	Used	New
RA 10 DA Receiver.....	\$17.50	\$24.95
BC 442 Less Condenser.....	1.49	1.95
APS 13 UHF Antenna, Pair.....	.....	.98
I-97 Bias Meter.....	3.95	4.95
RL 42 Antenna Gearbox Motor and Reel.....	4.95	7.50
Circuit Breaker 40 Amps.....	.....	.59
I 82 F Five Inch 360 degree compass indicator and Selsyn receiver.....	4.95	.....
A-81-2 Transmitters Selsyn for I82 indicator (both I82F & Trans. Selsyn for \$7.00).....	2.45	.....
PE-101 Dynamotor.....	2.75	.....
Model 507, Thermal-converter Weston Type D, range 12 amp.....	.59	.....
BC-1023 Marker Beacon Receiver, complete with tubes, shock mount and instruction manual.....	9.95	.....
BC-924 27-38 MC. FM Transmitter, complete with tubes.....	19.95	.....
BC-684 27-38 MC. FM Transmitter, less dynamotor.....	19.95	.....
BC-610 10 meter modification kit.....	3.95	.....
SCR-183 complete 12 volt set with all coils, tubes, dynamotor and control units.....	49.50	.....
ARB Control Box.....	1.95	.....
ARR 2 Control Box.....	.89	.....
BC 1206C Receiver, new.....	7.95	.....
BC-375, transmitter only.....	19.95	.....
TA-12, transmitter.....	22.50	.....
110 volt, 60 cycle motor.....	7.95	.....
A27 Phantom antenna.....	1.95	.....
PE 206 Inverter.....	4.95	.....
Scott Hi-Fi output transformer.....	1.49	.....
PE-218 Inverter.....	19.95	.....
BC-604, as is.....	7.95	.....
SCR-522, transceiver, less tubes.....	39.50	.....

## MONTHLY SPECIAL!

### LP 21A/ADF LOOP

Automatic loop in used condition but complete in water-proof housing with Sel-syn and drive motors..... **\$6.95** ea.

## CONDENSERS

1 mfd.—800 VDC..... 19c each  
6 for \$1.00

## I. D. 6B/APN4 LORAN INDICATOR SCOPE

less tubes, like new..... **\$39.95**  
ONLY

Shipments FOB warehouse. 20% Deposit on orders. Minimum order \$5.00. Illinois residents, add regular sales tax to remittance. Prices subject to change without notice.

# ARROW SALES, Inc. Dept. N, 1712-14 S. Michigan Ave., Chicago 16, Ill.

## MIKES and HEADSETS

HS 23 High Impedance Headset.....	new \$4.95
HS 30 Miniature Headset.....	new 1.50
.....	used .75
CD-307 Ext. cord for HS 23-33.....	like new .95
J41 Key.....	new .98
T-32 Desk Stand microphone. Good used cond.....	\$2.95
Throat Mike—T 30—New.....	98c
Lip Mike—Navy Type—New.....	98c
Extension Cord and Switch Assembly for lip and throat Mikes—New.....	98c
CW 49505 High impedance headset complete with leather headband and rubber cushions. Used.....	98c
RS-38, Microphone.....	new 6.95

## VIBRATORS

2 Volt—7 Prong Synchronous.....	69c 10 for \$6.00
6 Volt—4 Prong Non-synchronous.....	98c 10 for 9.00

## SCR 508 EQUIPMENT

BC 603 Receiver L/dyn.....	\$24.95	Exc. Used
BC 604 Transmitter L/dyn.....	12.95	Exc. Used
BC 605 Amplifier L/dyn.....	4.95	New
BC 606 Control Box.....	.95	Exc. Used
FT 237 Mounting.....	9.95	Exc. Used
MP 48 Mast Base.....	2.95	Exc. Used
DM 34, Dynamotor.....	10.95	Exc. Used
DM 35, Dynamotor.....	14.95	Exc. Used
DM 36, Dynamotor.....	10.95	Exc. Used
DM 37, Dynamotor.....	14.95	Exc. Used
TM 11-600 Tech. Manual.....	1.95	.....
Crystals, Set of 80.....	19.95	.....

## COMMAND (SCR 274 N) EQUIPMENT

	Used	New
ATA 2-3 mc transmitter.....	\$17.50	.....
BC-452.....	4.95	.....
BC-454.....	\$9.95	.....
BC-455 6-9 mc receiver.....	7.95	.....
BC-457 4-5.3 mc transmitter.....	6.95	14.95
BC-458.....	6.95	.....
T-19 ARC 5, 3-4 mc transmitter.....	10.95	.....
T-21 ARC 5, 5.3-7 mc transmitter.....	7.95	11.95
T-23 ARC 5, 100-156 mc xmt.....	49.50	.....
BC-496, 2 position Rec. Control Box.....	1.95	.....
MC-215 Mechanical Drive Shaft, per length.....	2.45	.....
BC-450 3 Receiver Remote Control.....	1.95	.....
BC-451 Transmitter Control Box.....	.69	1.50
BC-442 Antenna Relay, complete.....	2.95	.....
3 Receiver Rack.....	1.95	.....

BC 770 Keyer P/O RC 100, new less tubes..... **\$4.95**

## SCR 625 Famous Army Mine-Detector

For Prospectors, Miners, Oil Companies, Plumbers, etc.

This unit is being offered now at a considerable reduction in price. Recently advertised at \$79.50 it is now available in the same brand new wrappings in suitcase style carrying case (less batteries) at

**\$59.50** WHILE THEY LAST! Used, like new, \$39.50

## ASB 7 EQUIPMENT

CPR-46 ACJ Receiver—509 to 556 mc, new with tubes.....	\$29.50
CAY-52 ACV Transmitter, new with tubes.....	7.95
CJP-55 AER Scope, new with tubes.....	19.95
CJP-20 AEBX Power unit, new with tubes.....	4.95
..... used with tubes.....	3.95
CJP-14 AAV Antenna switching unit, new complete.....	4.95


## ELECTRONIC CIRCUIT KIT

Form your own electronic circuits with amazing kit. Contains resistor and carrier pigments, insulator and instructions—complete. Experiment, develop, miniaturize.

Prepaid—\$5.50. \$5.50 plus C.O.D.

ALDEN ELECTRO CO. 6760 Stony Island Ave. Chicago 49, Ill.

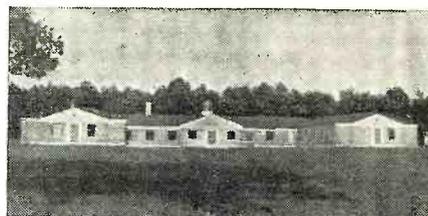Another Outstanding Jobber  
**OLYMPIC ELECTRONICS SUPPLY**  
1440 W. OLYMPIC BLVD.  
LOS ANGELES 15, CALIF.  
has all 17 KITS & INSTRUMENTS in stock!  
**EICO**  
22K VTVM KIT \$25.95  
5% higher on West Coast See EICO ad on Page 30




## RADIO ENGINEERING TELEVISION ELECTRONICS

Thorough training in all phases of radio and electronics, open to high school and junior college graduates. Old established school specializing in Radio training exclusively. Modern laboratories and courses. Enrollments limited. Approved veteran training.

VALPARAISO TECHNICAL INSTITUTE  
Dept. RD Valparaiso, Ind.
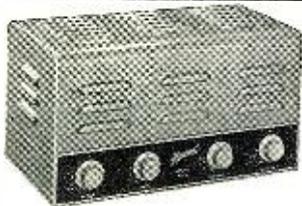
# Newcomb Packs More Quality Features In New Low Cost "E" Series Amplifiers

No other low-priced amplifiers offer so much quality as is found in the Newcomb "E" Series 10, 17, 25 and 50 watt models which include phono-tops, mobile and portable assemblies



Low cost has been achieved through simplification of design stressing all essential requirements but avoiding frills. There has been no sacrifice in quality of materials or craftsmanship in the making of these fine utility amplifiers.

**MODEL E-25**, illustrated, is unquestionably the standout 25-30 watt amplifier in the low-priced field, designed to fill the majority of everyday needs.

It has inputs for two high impedance microphones and a phonograph, with provision for easy conversion of mike inputs to low impedance. New individual bass and treble tone controls offer wide range of adjustment for varying conditions and feature bass emphasis for phonograph without emphasizing voice bass. Finest molded type coupling condensers give protection from heat and moisture. Etched metal panel is lighted for night use, operating knobs are large and skirted for easy handling.

### SPECIFICATIONS

Power output: 25 watts design center rating, 30 watts maximum, at less than 5% distortion. Frequency response:  $\pm 2$  db, 40 to 15,000 cycles. Inputs (3): 2 mike (2 meg.) gain 117 db, and 1 phono ( $\frac{1}{2}$  meg.) gain 77 db. Output impedances: 4, 8, 16, 500 ohms. Tubes (6): 1-6SJ7, 1-6SC7, 1-6J5, 2-6L6G, 1-5Z4. Power consumption: 90 watts at 117 volts, 60 cycles A.C. Shipping weight: 19 lbs.

Check catalog wanted  
and mail coupon ✓

**NEWCOMB AUDIO PRODUCTS CO.**  
Dept. F, 6824 Lexington Ave., Hollywood 38, Calif.

- LOW COST E SERIES**
- DELUXE H SERIES**
- CUSTOM K SERIES**

Name \_\_\_\_\_

Address \_\_\_\_\_

Firm \_\_\_\_\_

## High-Gain Amplifier (Continued from page 59)

model. This equalizing circuit, designed for use with tape operating at a speed of  $7\frac{1}{2}$  inches per second, is a bridged-T network, and its action is to suppress the middle frequencies, or, conversely, to boost the high and low end of the audio spectrum. The high boost is taken care of by the condenser  $C_{20}$  which has little reactance to the higher frequencies and hence conducts them directly to the grid of the following tube. Some of the middle frequencies are shunted to ground through the network  $R_{26}$  and  $C_{21}$ , but the value of  $C_{21}$  is such that it has high reactance to the very low frequencies and hence, they too, are amplified. The insertion of this equalizer does result in some loss of gain, but as previously stated, the amplifier has ample gain to take care of this loss nicely. If the builder wishes to use this circuit, it is inserted at the points X, Y, and Z on the schematic. It may be noted at this time, that this equalizer enhances the tone quality of the output of some types of phono pickups, and it seems to suppress the scratch frequencies to some extent, so it may be desirable to use it even if tape playback is not to be used. One other point should be mentioned regarding tape playback with this amplifier. Condenser  $C_1$  is not needed in the circuit except for reproducing tape recordings. Its purpose is to form a resonant circuit with the playback head, giving a sharp high frequency boost, particularly at those frequencies which need boosting on tape playback. Its action does not have much effect on a crystal or dynamic microphone, so it is not necessary to switch it out of the circuit when a mike is used.


$V_2$  is a second 12SL7 which is used as a phase inverter. It will be noted that  $R_{13}$ , the bias resistor for this stage, is unbypassed. This can be bypassed if it is necessary for hum reduction, but somewhat better results can be expected from the phase inverter if this resistor is left unbypassed. Also, in connection with the phase inverter circuit, it should be noted that resistors  $R_{17}$  and  $R_{18}$  form a voltage divider which supplies the proper voltage to grid No. 2 of the phase inverter tube. Since the voltage delivered from the junction of  $R_{17}$  and  $R_{18}$  is dependent on the relative values of these resistors as well as upon the gain of the 12SL7, and since tubes and particularly resistors vary considerably, somewhat better results can be obtained from the phase inverter if the final value of  $R_{18}$  is chosen by measurements taken from the grids of the output tubes than if a nominal value of resistor is chosen. The measurements can very easily be made if a vacuum tube voltmeter or an oscilloscope is available. With a steady signal supplied to the amplifier, such as a tone from an audio oscillator, a voltage reading is taken at the grid of  $V_3$ , using either the vacuum tube voltmeter or


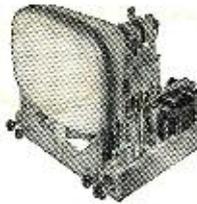
## NEWEST 30-TUBE 630 TV CHASSIS

Takes All Size Picture Tubes  
to 20"

Specifically made for fringe area reception. This chassis succeeds in rendering clear pictures where others fail! New AGC, 15 KV output, new high-voltage system, 3-stage sync separator and clipper. Armstrong FM sound system, complete with RCA 12" speaker



4-MICROVOLT SENSITIVITY.

Factory aligned, ready-to-play, less CR tube, with STANDARD TUNER..... **\$149.95**

With Dumont Tuner..... **\$154.95**  
TUBE MOUNTING BRACKETS..... **4.95**

### TV TUBE SPECIAL

14" rect..... **\$23.94** 17" rect..... **\$28.95**  
16" rd/rect... **27.95** 20" rect... **39.95**

Brand New—Fully RTMA Guaranteed

### POWER TRANSFORMERS

ALL PRIMARIES 115V—50 TO 60 CYCLES

Sec: 820v, 280 mils, 6.3v @ 5 amps; 3v @ 3 amps; 5v @ 3 amps; 2.5v c.t. @ 5 amps, upright mt. .... **\$6.95**

RCA—Sec. 750v c.t. @ 225 mils; 6.3v @ 3 amps; 6.3v @ 1.2 amps; 5v @ 3 amps, half shell mt. .... **\$6.95**

PHILCO—Sec. 650v c.t. @ 150 mils; 6.3v @ 1.5 amps; 6.3v @ .3 amps; 5v @ 3 amps; half shell mt. .... **\$3.95**

MAGNAVOX—Sec. 800v c.t. @ 120 mils; 6.3v @ 4 amps; 5v @ 3 amps; half shell mt. .... **\$3.49**


UTC—Sec. 700v c.t. @ 75 mils; 6.3v c.t. @ 3 amps; 5v @ 3 amps; 2.5v c.t. @ 8 amps; half shell mt. .... **\$2.95**

STANCOR—Sec. 900v c.t. @ 325 mils; 6.3v @ 5.5 amps; 6.3v @ 4.5 amps; 5v @ 6 amps; upright mt. .... **\$10.95**
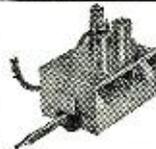
## STANDARD Turret Type FRONT END **\$18<sup>95</sup>**

TYPE TV 201: 21.25 sound, for 630 chassis, etc.

TYPE TV 303: for all inter-carrier systems.



### FILTER CHOKES

Hy. @ Ma.	Ohms D. C.	D. C. Channel	Mounting	Price
10 75	350	C. Channel	Sealed	\$0.50
10 75	400	D. C. Herm.	Sealed	.70
17 75	420	D. C. Herm.	Sealed	.89
10 75	200	D. C. Channel		.78
10 75	200	D. C. Channel		.69
2 100	350	D. C. Herm.	Sealed	1.09
10 75	460	D. C. Herm.	Sealed	1.79
15 110	400	D. C. Upright		1.39
8 100	130	D. C. Channel		1.19
10 150	200	D. C. Cased Channel		1.39
8 150	25	D. C. Channel		1.29
8 150	25	D. C. Cased		1.39
10 200	25	D. C. Upright		2.25
2.5 200	60	D. C. Channel		1.25
15 200	25	D. C. Upright		2.05
8 200	95	D. C. Channel		2.30
12 200	95	D. C. Cased		8.95

TERMS: 20% cash with order, balance C.O.D. unless rated. Prices F.O.B. our warehouse in N. Y. C. Minimum order \$3. NOTE: Due to conditions beyond our control, prices are subject to change.

Phone WOrth 4-3270

**ACORN ELECTRONICS CORP.**  
76 Vesey St., Dept. N-1, New York 7, N. Y.

# Prepare Now! RADIO ENGINEERING

## B.S. DEGREE IN 27 MONTHS

Complete Radio Engineering course incl. Telev., U.H.F., and P.M. BS Degree Courses also in Mech., Civil, Elect., Chem. and Aero Eng.; Bus. Adm., Acct. Extensive campus, modern buildings, well equipped labs. Low cost. Prep courses. Personalized instruction. Heavy demand for graduates. Placement service. Founded in 1884. Prepare now for the civil and military opportunities ahead. Enter Jan., March, June, Sept. Write for Catalog.

**TRI-STATE COLLEGE**  
1612 COLLEGE AVE. ANGOLA, INDIANA

the oscilloscope. Then a similar reading is taken at the grid of  $V_4$ . If the voltage at  $V_4$  is lower than that of  $V_3$ , the value of  $R_{18}$  should be increased. Conversely, if the reading at the grid of  $V_4$  is higher than that at the grid of  $V_3$ , the value of  $R_{18}$  should be decreased. With a little experimenting, a very precise voltage balance can be achieved between the grids of the output tubes. However, if the builder does not have the necessary test equipment at his disposal, the values of the resistors given in the parts list will give good results.

At first glance it may appear that no inverse feedback is used in this amplifier. However, it will be noted that the cathode resistor,  $R_{20}$ , of the output tubes is unbypassed. This results in a small amount of degeneration which helps somewhat to reduce any hum and distortion which may be present. If a greater degree of feedback is desired, a  $\frac{1}{2}$  megohm resistor can be connected from the plate of  $V_3$  to the plate of  $V_2$ . However, this may necessitate a change in the value of  $R_{18}$ . The results obtained with the amplifier, as indicated in the schematic, were such that no additional feedback was deemed necessary, especially in view of the losses which would result.

50L6's were chosen for the output tubes because of their high power sensitivity and relatively high power output at low plate voltage. It will be noted that the maximum ratings for these tubes are indicated in tube manuals as 200 volts on the plate and 125 volts on the screen. The power supply previously described supplies very nearly the maximum voltage at full load and the proper screen voltage is obtained by using dropping resistor  $R_{21}$ . The output of these tubes at the maximum voltage ratings is in the neighborhood of 8 watts.

One precaution should always be taken with any equipment in which one side of the power line is connected to the chassis, *i.e.*, be sure that the chassis is not connected to the "hot" side of the power line. One method of assuring that the chassis will be connected to the ground side of the line is to use a chassis ground, actually connecting the chassis to a cold water pipe or other ground connection, and then to use just a single wire in the power cord, connected to just *one* of the prongs of the power plug. In this way, if the plug is inserted incorrectly, the set will be inoperative, but in no way will it be possible to make the chassis "hot." If this method is inconvenient, a small neon test lamp can be used to indicate whether or not the chassis is connected to the high side of the power line.

Operation of the completed amplifier should pose no special problems. The builder will find that within its power limits, this amplifier will perform as well as many higher-priced units.


#### REFERENCE

Fleming, Lawrence: "Controlling Hum in Audio Amplifiers," RADIO & TELEVISION NEWS, Nov. 1950.
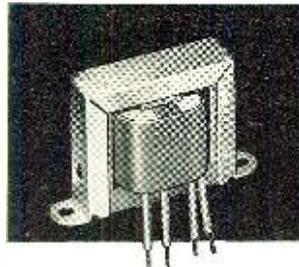
# NEW! STANCOR




Here are three of the newest additions to the most complete transformer replacement line in the industry.



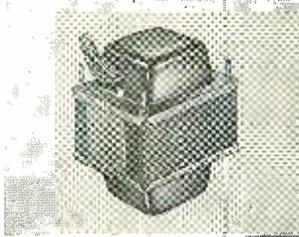
#### A-8124, VERTICAL BLOCKING-OSCILLATOR TRANSFORMER

A three winding transformer for replacement in Dumont models RA-103, RA-103D, RA-104A, RA-105, RA-105B, RA-108 and RA-110A. See Stancor Bulletin 384.

For use with picture tubes up to 24". Equivalent to RCA 202D2. See Stancor Bulletin 383.



#### FC-11, FOCUS COIL.

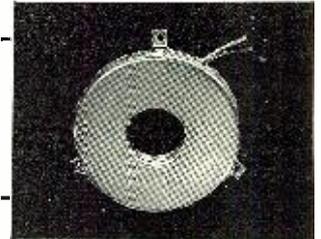

#### P-8163, TV POWER TRANSFORMER

Equivalent to RCA 75508 (971316-1), used in 28 RCA models. See Stancor Bulletin 388 for a complete list.

Your Stancor distributor has data sheets on these new Stancor TV transformers. Ask him for the latest Stancor Bulletins.

Other new Stancor TV components include **DY-8**, **DY-9**, and **DY-10**, 70° deflection yokes with ferrite cores, nylon coil bobbins and anti-astigmatic focusing (resulting from "cosine" distributed windings) for tubes up to 24". **A-8131**, an air core "flyback" for direct drive circuits, to be used with **DY-10**.

**STANCOR TV TRANSFORMER CATALOG AND REPLACEMENT GUIDE** lists transformer replacements for over 1500 TV models and chassis. Available FREE from your Stancor Distributor.



## STANDARD TRANSFORMER CORPORATION

3584 ELSTON AVENUE, CHICAGO 18, ILLINOIS

### Advance with ELECTRONICS CITY

You need firm grasp of fundamentals to keep pace with these complex, fast-growing fields. In thorough 2-year course learn electricity, electronics, physics, mathematics, drafting, etc. Other engineering and technical courses. Coed. Day, evening. 44th year. Write for Catalog.

FRANKLIN TECHNICAL INSTITUTE  
46 Berkeley Street Boston 16, Mass.

**BARGAIN HUNTING?** **RADIO SERVICEMEN!**  
Write for SENSATIONAL CATALOG  
**HENSHAW RADIO SUPPLY**  
3619 TROOST KANSAS CITY, MO.

### No Experience Needed To PRINT YOUR OWN POST CARDS


The GEM STENCIL DUPLICATOR saves money... gets results quickly! Hundreds of uses for every type of business and organization. We ship the GEM complete with all supplies, Guide Board for accurate printing and 60-page Book of Ideas at the special low price of only **\$8.50** (a \$15.00 value)

**FREE TRIAL OFFER**

Use the GEM FREE at our expense! SEND NO MONEY. Write and complete GEM outfit will be sent you postpaid. After ten days, send us only **\$8.50** or return the GEM. You must be satisfied! WRITE TODAY.

**BOND EQUIPMENT CO. Dept. 52**  
6633 Enright • St. Louis 5, Mo.

# Cash in on TV Service Profits!

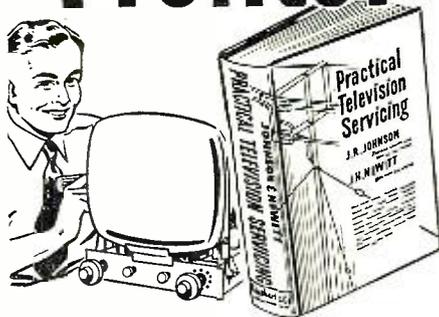

## PRACTICAL TELEVISION SERVICING

By J. R. Johnson and J. H. Newitt  
375 Pages, 230 Illustrations, \$4.00

Good training for television service doesn't need to cost you a lot of money! This great book at only \$4.00 is a complete guide that tells you step by step just what to do, what mistakes to avoid, what tools, parts and equipment to use—in short, how to handle every phase of television receiver servicing promptly, efficiently and profitably.

### LEARN FAST! ... LEARN RIGHT!

The authors of PRACTICAL TELEVISION SERVICING actually operated a TV service shop to get the specific, how-to-do-it information they now pass along to you in easily understood form. In addition to a clear explanation of how television work differs from radio, they show exactly how to perform all operations in trouble-shooting, diagnosing and remedying television troubles. You don't bother with needless theory. They show you exactly how to do the work!

Dozens of actual TV servicing case histories, service hints and common TV receiver troubles make the book literally worth its weight in gold.

**Subjects include:** TV System Fundamentals; R-F, I-F and Detector Sections; Video Amplifiers; Cathode Ray Tubes; Synchronizing and Sweep Circuits; Power Supplies; Antenna & Wave Propagation; TV Receiver Installation; Test Equipment and Alignment; Wiring and Repair Techniques; Color Television; Receiver Layout Diagrams—and dozens more. In addition there are countless tips on such things as getting better fringe area reception; improving picture linearity; checking video response with a square wave; getting signals over a mountain and numerous others.

Read PRACTICAL TELEVISION SERVICING on our 10-day examination offer! Send coupon today!

### READ IT 10 DAYS • at Our Risk!

Dept. RN-12, RINEHART BOOKS, Inc.,  
Technical Division,  
232 Madison Avenue, New York 16, N. Y.

Send PRACTICAL TELEVISION SERVICING for 10-DAY FREE EXAMINATION. If book is O.K. I will then promptly remit \$4.00 in full payment. If not, I will return book postpaid in good condition and owe you nothing.

Name .....

Address .....

City, Zone, State.....

Employers' Name & Address.....

Price outside U. S. A., \$4.50—cash only.  
Money back in 10 days if you return book.

# RADIO-TV Service Industry News

AS REPORTED BY THE  
TELEVISION TECHNICIANS LECTURE BUREAU

**N**OW that the 1951 Holiday Season is over, the sixty-four dollar question is how quickly, where, and how much will the service industry benefit from the lifting of the TV station construction freeze which has been freely predicted to happen in January?

### Fall Service Business Disappointing

The Fall upswing of service business in practically all TV areas did not reach the levels that had been hoped for. Each year the Fall rise in installation and service volume in TV areas has been less pronounced than the previous year. This indicates that the "boom type" of business is definitely a thing of the past in those areas.

Hopes for a boom converting receivers for color TV died with the freeze clamped on color by the WPB. The result is that most progressive service businessmen are critically reviewing their entire operating plans to determine what type of service selling programs they need to maintain an adequate volume of business under these new norms. And u.h.f. does not promise too much in the way of increased service volume in major TV areas.

A "task force" of the Radio-Television Manufacturers Association has been making a study of the television

industry to determine the effect on the national economy and the mobilization program of the lifting or continuing of the TV "freeze" on station construction. Its purpose is to determine the effect on materials and manpower if the freeze is lifted and the effect on the television industry if construction of additional TV stations is not permitted.

There has been some concern that the lifting of the freeze would start a rush to get many new television stations on the air and create a demand for steel, copper, and other materials. However, many industry representatives believe there are sufficient transmitters now under construction or already completed and held in warehouses to satisfy the demand through 1952.

Also, there has been considerable concern in the industry that if the Federal Communications Commission does not lift the "freeze," the electronic industry may suffer from a period of depression and unemployment in spite of heavy military electronic contracts. This is further evidenced in statements previously quoted in this department to the effect that even at its peak the defense program will be using only about twenty per-cent of the productive capacity of the electronics industry.

A capacity crowd jams St. Joseph's auditorium to hear Edward M. Noll of the Lecture Bureau speak on u.h.f. television and the alignment of TV front ends. The lecture, which included a demonstration of the correct procedure for aligning TV front ends, was sponsored by Albert Steinberg & Co., Philadelphia parts distributing company.






# WE CHALLENGE COMPARISON! The **Phillips DX-er** HAS NO EQUAL

The only Rhombic Type antenna actually field tested and proven in extreme fringe areas to have higher gain than any other type of television antenna on the market today.

**NON-RESONANT...T4 DB GAIN  
SEE AND HEAR THE DIFFERENCE**

FOR HIGH AND LOW BANDS (2-13)


## MODEL 102P

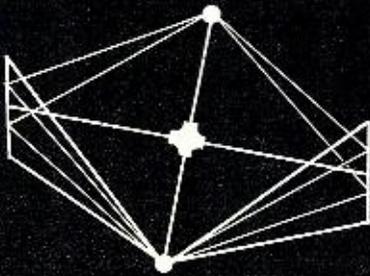

**HIGH GAIN • DIRECTIONAL  
COMPLETE COVERAGE 2-13  
PRE-ASSEMBLED • WIND RESISTANT  
LIGHTWEIGHT • QUICK ASSEMBLY**

HIGH BAND ONLY (7-13)

## MODEL 104P

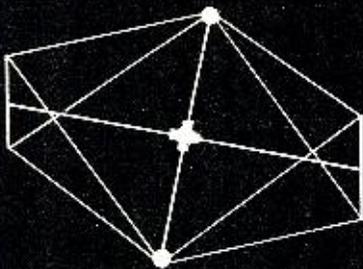

WRITE DIRECT OR CONTACT YOUR JOBBER TODAY FOR LITERATURE AND INFORMATION ON THE PHILLIPS DX-er RHOMBIC ANTENNA.

**Roger-Phillips  
RESEARCH LABORATORIES**

717-RD North Lake Avenue, Pasadena 6, Calif.

ing cost of living and you end up with today's average consumer who is a critical buyer.

Sure, there will be a good spot market for television receivers in each new area that opens coupled with the need for the associated installation, adjustment, and service. But service businessmen in new TV areas should expand their businesses cautiously. Adequate finances should be available to make the necessary capital investments for the business of installing and servicing TV receivers. Many TV service contractors in the early TV areas went broke simply because they were badly under-financed and attempted to finance the necessary trucks, test equipment, parts, tubes and supplies stocks, etc., out of income. This looked easy when they were getting all of the installation and service contracts they could handle. But when payrolls and general operating expenses had to be met month after month in servicing those contracts for twelve months they found there just wasn't enough income to go around. The seeds of success or failure are usually sown during the first six months of a TV service business' operation so it is vitally important to get started on a sound business basis.

An interesting article on "Financing a Service Business" is available to readers of this department. You may obtain a copy by writing to Service News Editor, RADIO & TELEVISION NEWS, 366 Madison Ave., New York 17, N. Y.

The most serious problem in new TV areas will be the lack of trained, competent, installation and service technicians. This is already a very serious problem in all present television areas so there is little hope for drawing experienced television service technicians from those sections to work in the new TV areas. This shortage of qualified personnel will be a serious obstacle to the growth of independent service businesses that must depend on the local labor pool for skilled TV technicians.

The RTMA program which will start with service training programs for technicians in the nation's trade and vocational schools, is one that should be actively and aggressively supported by all segments of the television industry and particularly by independent service business operators. This program, which is being developed under the direction of E. W. Merriam, former service manager of the *Allen B. DuMont Laboratories, Inc.*, and now service manager for RTMA, is especially designed to expand the pool of trained technicians available for field service work. It is of special importance to independent service businessmen whose businesses are not large enough to support internal technician training programs of their own.

### U.H.F. in Major TV Areas

It is highly questionable whether u.h.f. will cause any appreciable increase in service business volume in areas that are now being served by two or more stations. If manufactur-

## WHY WILL YOU CHOOSE YOUR TAPE RECORDER?

Q. Higher Fidelity and Smoother Performance?

**A. THEN BUY TWIN-TRAX!\***

Q. Longer Continuous Playing Time?

**A. THEN BUY TWIN-TRAX!\***

Q. Professional Specifications at Popular Price?

**A. THEN BUY TWIN-TRAX!\***

Q. Wider Selection of Models?

**A. THEN BUY TWIN-TRAX!\***

No matter which of these features you consider most important. You'll find them all—and many other exclusive features—in our Twin-Trax Recorders. Send today for your free copy of our Catalog #5272. \*Reg. U. S. Pat. Off.

**AMPLIFIER CORP. OF AMERICA**  
398 Broadway, New York 13, N. Y.

## DIAGRAMS OF "SURPLUS" EQUIPMENT

We can furnish schematics of many surplus electronic items not included in our "Surplus Radio Conversion Manuals." Send stamp for list.

### FOREIGN RECEIVER SCHEMATICS

We can obtain schematics (but no other data) on most foreign-made receivers at \$2.00 each (including air mail from Europe to you). No list available, but \$1.65 refunded if we cannot furnish promptly.

EDITORS AND ENGINEERS, LTD.

Box 689

Santa Barbara, Calif.

## PANEL METERS

LARGE STOCK • GUARANTEED ACCURACY

GRUEN 3" Rd. 0-100 Microamp DC	\$ 9.95
SIMPSON 2" Rd. 0-300 Microamps DC	7.95
MARION 2" Sq. 0-1 MH. DC	4.95
DALE 2" Sq. 0-1 Mil. DC	4.95
WESTON 2" Rd. 0-2 MH. DC	5.95
GE 2" Sq. 0-15 Mil. DC	6.95
TRIPLETT 2" Rd. (0-200 Mil.-0-2 Amp.) Dual	3.95
WESTON Ltd. 2" Sq. 0-300 Mil. RF	4.45
SIMPSON 2" Rd. 0-2 Amp. RF	4.95
SIMPSON 2" Rd. 0-3 Amp. RF	4.95
SUN 2" Rd. 0-300 VDC-1000 ohm/V.	4.95
SIMPSON 3" Sq. DB-10	9.95
WESTON 4" Rd. 5 Amp. AC-1% Acc.	12.95
WESTON 4" Rd. 250 Amp. AC 1% Acc. w/en. current xform.	17.95
GE 2" Rd. 30 Amp. DC	4.95

### LAB TEST EQUIPMENT—NEW—USED

### COMPLETE STANDARDS LAB

WE ARE SPECIALISTS IN ALL PHASES OF METERS & MEASUREMENT REQUIREMENTS

### AMERICAN ELECTRONICS

29 S. Park Avenue, Rockville Center, L. I., N. Y.  
RO 6-0207

## PICTURE TUBE REACTIVATOR



Reactivates dim picture tube without its removal from cabinet. A real money maker for servicemen or contractors! Supply limited. Reactivator. **\$27.50 net**

F. O. B. New York—1/4 with order, balance C. O. D.  
**ELECTRONIC VISION PROJECTION CO.**  
3492 Kingsland Avenue Bronx, N. Y. C.

**KAAR  
RADIOPAK**

**THE MOBILE  
RADIOTELEPHONE**

KAAR ENGINEERING CO.  
PALO ALTO, CALIFORNIA

**RADIO & TELEVISION NEWS**

ers' claims about the ease and simplicity of adding u.h.f. channel reception to their current model receivers are valid, there will be very little additional income available from u.h.f. conversions. An outdoor antenna may be necessary on some sets that are now receiving v.h.f. satisfactorily with indoor or built-in antennas but the customer himself will probably have to be sold on whether the programs he would receive on u.h.f. are enough better than his v.h.f. programs to justify the outlay for the conversion and antenna installation.

The pattern of service in major TV areas seems to be pointing toward a necessity for service-selling programs that will keep the consumer conscious of the fact that his set needs maintenance attention for top picture quality just as the automobile owner has been sold on car maintenance as an insurance for dependable service and for avoiding expensive overhaul jobs. The TV set owner is using an instrument about which he knows practically nothing and it is a service industry responsibility to keep him informed about what he should have done in the way of maintenance to get the most pleasure and satisfaction out of that instrument.

Another thing that is being called constantly to the attention of editors of this department is the general lack of interest or courtesy when a set owner phones the average TV service shop about service on his receiver. Since we have heard these complaints from set owners in practically every major center in the country it must be a universal failing of the independent servicing industry.

Your business phone is one of your most important service sales tools. When a customer calls you for service you can either make him a strong booster for your business or you can lose him completely as a customer—in a hurry. Your customer is your boss and even though he may act a little exasperated when he phones in for service he is not going to like you if you answer him in kind. Remember always that a "soft answer turneth away wrath," apply it in all of your dealings with your customers and you will do a good job of building customer good-will for yourself and for your business.

### Parts Warranty Sales Vex Service Industry

The most exasperating and expensive problem that TV receiver manufacturers have put in the laps of the service industry has been that of the sale of 12-month parts warranty contracts tied-in with the purchase price of the receivers. Executives of the various service associations such as TISA of Chicago and TCA in Philadelphia have pounded on this subject for months trying to bring about an abatement of the practices which they say are brought about by the 12-month parts warranty sales.

The National Radio & Appliance

January, 1952


SEE LEO FIRST FOR . . .

# hallicrafters

I can SAVE you money . . . Liberal Trade-ins



Leo I. Meyerson  
WØGFQ

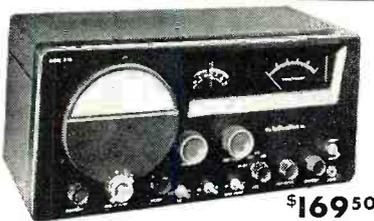

\$169.50

### New S-76 RECEIVER

Extra selectivity with double superheterodyne circuit. One RF, two conversion and 3 IF stages. Range 550-1550 Kc, 1.7-34 Mc in four bands. 8 tubes plus voltage regulator and rectifier. Complete with tubes, less speaker.

R-46 SPEAKER \$19.95



\$199.50

### SX-71 RECEIVER

Double Conversion sharp selectivity, plus built-in NBFM at moderate cost. 11 tubes plus voltage regulator and rectifier. Low down payment.

R-46 Speaker \$19.95

NAME YOUR TERMS • LOW DOWN PAYMENTS • PERSONALIZED SERVICE

## HALLICRAFTERS RECEIVERS AVAILABLE FOR IMMEDIATE SHIPMENT

S-38B . . . . .	\$49.50	S-72 Portable . . . . .	\$109.95
S-40B . . . . .	\$99.95	SX-62 . . . . .	\$289.50
S-81 . . . . .	\$49.50	S-78A . . . . .	\$89.50
S-82 . . . . .	\$49.50	S-76 . . . . .	\$169.50
		R-46 Speaker . . . . .	\$19.95

### Famous WRL RADIO REFERENCE MAP 25c



CU on 10-20 & 75 Meters

### NEW LOG BOOK 25c

For mobile or fixed station. Spiral binding. Full column log listing all FCC required info. Will accommodate 1,525 stations. "Q" signals, phonetic alphabet, amateur international prefixes.



PHONE 7795

WRITE—WIRE



## JUST OFF THE PRESS!

### WRL 1952 CATALOG

Send for your copy today. Contains everything new in radio and television. Jam-packed with bargains. Leo I. Meyerson, WØGFQ



FREE

WORLD RADIO LABORATORIES RN-1

744 West Broadway

Council Bluffs, Iowa

Please send me:

- Radio Map
- New Catalog
- Used Equipment List
- SR-75 Info
- SX-71 Info
- New Log Book

Name . . . . .

Address . . . . .

City . . . . . State . . . . .

## BMC TRANSCRIPTION PLAYER



16" Synchronous

Model TP16E \$126.00

Model TP16D \$84.00

Model TP12H \$58.50

(F.O.B. Port Chester, N. Y.)

Export: Rocks International Corporation.

13 East 40th Street New York 16, N. Y.

### FOR HIGH FIDELITY RECORD REPRODUCTION

Meets the rigid demands of Army-Navy requirements, even Navy salt-spray test. Used by U.S. Signal Corps all around the world. Standard equipment in Veterans' Hospitals, and most radio stations, transcription services, etc., for realistic reproduction of transcription records up to 16 inches, 78 and 33 1/8 r.p.m.

Descriptive Bulletin HS3-1, upon request.

Available Through Authorized Jobbers.

# RADIO-MUSIC CORPORATION

PORT CHESTER • NEW YORK

**FREE** GET YOURS NOW!

JUST OFF THE PRESS!  
Value-Packed, JANUARY  
**F.Y.I. BULLETIN**

Published Monthly To  
Keep You Up-To-Date On  
• Latest & Greatest Values!  
• Newest Equipment & Designs!  
**WRITE TODAY! FYI Dept.**

Snyder's Powerful 5 Element  
**YAGI TELEVISION ARRAYS**



Channels  
3—HY3  
4—HY4  
5—HY5  
6—HY6

Channels  
7—RY7  
8—RY8  
9—RY9  
10—RY10  
11—RY11  
12—RY12  
13—RY13


**\$7.95**      **\$4.95**

**For Fringe & Ultra Fringe**

Highly directional and closely tuned to each channel. Cuts interference and noise to a minimum. Five elements; one folded dipole, three directors and one reflector. Individual array for each channel. Specify model desired.

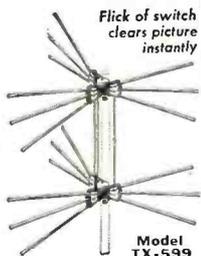**360° MOTORLESS TV AERIAL**

Same Clear Pix As Motor Rotating Aerial Systems. Costing Triple This Price FOR ULTRA FRINGE Only **\$1895**



Flick of switch clears picture instantly

COMPLETE with three 3½ ft. masts, 75 ft. 3 cond. cable, beam selector sw., guy ring, mtg. base & U clamp.

Electronically beams in complete 360° rotation to give clear picture on all channels. You choose direction with Directronic selector switch mounted on or near TV set. Complete double-stacked arrays with 18 hi-tensil double-alloy aluminum elements.

**TV ANTENNA ACCESSORIES**

- STEEL EXTENSION POLES. Weather treated.
- 10 ft. long, 1¼" dia. .... \$2.19
- 5 ft. long, 1¼" dia. Crimped End. .... 1.35
- 3½ ft. long, 1¼" dia. Crimped End. .... 1.19
- CHIMNEY MOUNT BRACKETS. Complete with strap CM-1. .... 1.59
- HEAVY DUTY MAST BRACKETS WB-2. Adj. to 18" from wall. .... 3.75
- ANTENNA SWIVEL BASE. Aluminum. Fits 1¼" O.D. mast section. .... .45

**CLOSEOUT!**

Reg. \$29.95 Famous Make FM RADIO CHASSIS



May Also Be Used as FM Tuner

- 6 Tubes • Built-in Ant.
- 4" PM Speaker • AC-DC
- 88 to 108 mc.

**\$16.95** Because of a slight change in design we were able to buy a closeout from one of America's best known set makers. YOU SAVE \$13.

**WHOLESALE RADIO PARTS CO., Inc.**  
311 W. Baltimore St.  
**BALTIMORE 1, MD.**

Dealers Association through the efforts of its president, Mort Farr of Upper Darby, Pa., has done much to bring the dangers and inequities of this practice to the attention of responsible manufacturers. It is now generally felt that steps will soon be taken to correct this situation that has been so costly to servicing contractors and dealers.

**Plus Service Income**

There is not a home in which you are called to service a radio or television receiver that does not need some other products or accessories that you handle regularly. Such items will add to your "per call" income—and profit. A few of these are:

- (1) Dry batteries for portable radios and flashlights
- (2) Phonograph needles
- (3) Phono replacement cartridges
- (4) Wire and tape for home recorders

Usually when you mention batteries for flashlights you receive an appreciative response from the customer because they find the batteries are usually dead when they occasionally try to use the flashlight that is kept for emergencies. This is also true of battery-operated portable radios, thousands of which rest on closet shelves while someone in the family tries to remember to get some batteries.

More than nine million battery-operated portables have been sold since the end of the war and current sales are at the rate of about two million sets per year. This represents a tremendous market for batteries and one which the service shop operator can handle profitably and which can be helpful in getting other service business.

**International Short-Wave**

(Continued from page 125)

kw. rig that tested some months ago. Verified from Philips Peruana, Box 1841, Lima, Peru. (Russell, Calif.)

Lima, 15.105, *Radio El Sol*, noted around 1815; identifies plainly 1830 with slogan. (Russell, Calif.)

*Philippines*—Russell, Calif., flashes that he has picked up the new 25-m. outlet, DZH9, of the Far East Broadcasting Co., Manila, on 11.850A, in parallel with other outlets of this broadcaster on regular schedule. Russell says DZH7 has apparently moved from measured 9.7345 to measured 9.7286.

DHY2, 6.14, signs off around 0959; announces also for DYRC, 1040 kc. (Gay, Calif.) *Radio Free Asia*, 6.110, Manila, still noted signing off 1000. (Dale, Calif.)

*Poland*—*Radio Warsaw* still noted signing off *English* program 0100 on 7.205. (Hoffman, N. Y.) Excellent on this channel opening in *English* 1700. (Mast, N. Y.)

*Portugal*—*Radio Sweden* says Lisbon can be heard mornings (EST) over 11.960 but changes to 11.995A at 1230. Measured by Ferguson, N. C., as 11.960 at 0945. Pearce, England, reports Lis-

**BE SURE**

REPLACE WITH

*Adjust-A-Cone*  
**QUAM SPEAKERS**



with the ADJUSTABLE VOICE COIL

You can be sure when you sell Quam Adjust-A-Cone Speakers. They are designed right for top performance—they are built right for trouble-free service and they are backed by more than a quarter century of speaker building experience.

Always sell the speaker that is first in original equipment—first in the replacement field. It costs no more and provides more satisfaction.

Also makers of Quam Focalizer Unit and Ion Traps  
**WRITE FOR CATALOG**

**QUAM-NICHOLS COMPANY**

522 E. 33rd Place, CHICAGO 16, ILL.

MAKERS OF QUALITY SPEAKERS FOR 27 YEARS, UNDER THE SAME MANAGEMENT

LEARN DAY and EVENING CLASSES  
**TELEVISION**  
ELECTRONICS-RADIO  
Modern Laboratory Instruction in

- SERVICING
- BROADCAST OPERATING
- ELECTRONIC and TV ENGINEERING

**G.I. APPROVED**

WRITE FOR ILLUSTRATED CATALOG  
**ELECTRONICS INSTITUTE, Inc.**  
21 HENRY, DETROIT 1, MICH.

**RADIO & TELEVISION NEWS**

bon on 11.995 to 1530 and 1600-1800 (parallel 9.745); on 11.962 at 1030; he also notes Lisbon on 15.130 at 1015 with music.

*Radio Free Europe* relay from Lisbon noted on 9.605A with interval melody on chimes when tuned 1903, then left the air. (Bellington, N. Y.) Heard in Czech 1145 and at 1200 gave call "Radio Volna Sobotna Europa"; noted another day signing on 1100. (Pearce, England)

*Portuguese Guinea*—Bissau, 5.84A, is still signing off 1800 with "A Portuguesa." Has usual heterodyne QRM. (Bellington, N. Y.)

*Portuguese India*—Radio Goa, 9.610, has an *English* broadcast at 100 called "Catholic Hour," which features devotions to the Sacred Heart conducted by Jesuit Fathers and directed by priests from the "Legion of John Bosco." (*Short Wave News*, London)

*Sao Tome*—CR5SB, 17.677, noted recently 0702 in Portuguese; signal faded greatly by 0720. (Ferguson, N. C.) This one is scheduled 0700-0800 on Sundays and Thursdays only.

*Saudi-Arabia*—Djeddah, 11.952, noted with Arabic program 1200-1350; sometimes closes 1330 or 1315; calls "Houna Mecca" pronounced ("Mukka"); has interval signal on flute playing 8 notes—before opening at 1200. (Ridgeway, South Africa) Also heard on 11.85 (jammed) and 5.975 at that time. (Pearce, England) Still signs on 2300 and runs to approximately 2345 daily, heard on 5.975A, 11.85, 11.95. (Bellington, N. Y.)


*Sierra Leone*—At present there is no regular broadcasting from this country but experimental broadcasts are carried out irregularly from Freetown over a 300 watt transmitter operating on 9.630. (*WRH Bulletin*)

*Southern Rhodesia*—Salisbury, 3.320, noted with organ recordings 1325, call 1330. (Pearce, England) Salisbury is definitely back on 9.50 now that *Springbok Radio*, Johannesburg, South Africa, is using 9.60 at 0300 to approximately 0700. (Ridgeway, South Africa)

*Spain*—Madrid, measured 15.627, noted opening program in Spanish to Canary Islands 1146, ending 1157. (Ferguson, N. C.)

*Sweden*—According to a *WRH Bulletin*, from January 15 the new 100 kw. transmitters at Horby will be on the air on this schedule—1900-2145 on 6.065 to USA (East Coast); 2200-2245 on 9.535 to East Africa; 2300-2345 on 9.620 to India, Indonesia, and on 9.535 to USA (West Coast); 0000-0100 on 9.535 to South Africa; 0600-0645 on 21.580 to South America; 0700-0745 on 11.880 to USA (East Coast); 0800-0845 on 9.535 to Far East, Pacific; 0900-1100 on 9.535 to India, Indonesia; 1200-1245 on 9.535 to East Africa; 1300-1345 on 9.535 to South Africa; 1600-1700 on 9.535 to USA (West Coast) and 1800-2100 on 6.095 to South America. Uni-directional transmissions to Europe (relay of Swedish Home Service) will be radiated at 0000-0400 on 6.065; 0400-1200 on 11.705; 1200-1800 on 6.065, and 1400-1545 on 6.095.

January, 1952

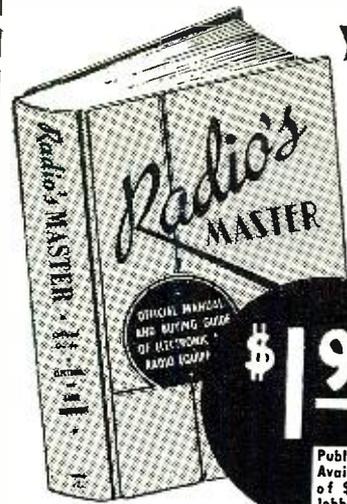

You'll find it  
**FASTER**  
in the  
**MASTER**

No More  
Files of  
Small  
Catalogs and  
Loose  
Literature



Publisher's price \$6.50.  
Available at special price  
of \$1.95 thru Parts  
Jobbers who absorb part  
of cost for privilege of  
printing ad on cover.

Industry's OFFICIAL  
Buying Guide of Radio-  
Electronic-Television  
parts and equipment.

When you **BUY--SELL--SPECIFY**  
you must have the **MASTER**

- 1100 Pages
- Hard Cover
- Fully Indexed
- Over 75,000 Items
- Over 7000 illustrations
- Weight—5 lbs.
- Size—8¼ x 10¾"
- Serving the Industry 16 years

This single volume replaces all other small catalogs

Over 90% of the products manufactured in the Radio-Electronic-Television Parts and Equipment Industry are catalogued in this BIG 1100 page MASTER Buying Guide. Complete descriptions, with specifications and illustrations are written and compiled by each manufacturer covering such products as: tubes, instruments, TV parts, transformers, capacitors, resistors, test equipment, relays, coils and antenna equipment. Also, recording and PA systems, intercoms, tools, hardware, switches and thousands of associated products. IT'S YOUR "RADIO BIBLE"—SAVES YOU TIME AND MONEY.

**BE MASTER-Minded—GET your copy NOW**

**UNITED CATALOG PUBLISHERS, INC.**  
110 Lafayette St., New York 13, N. Y.

**NEW — 16th Edition available  
from local Parts Distributor at  
the special \$1.95 price.**

It **COUNTS**  
and **CARRIES**  
your **TUBES**



Television  
tube caddy

Specially designed for the television serviceman. Makes work easier and quicker—and YOU more efficient.

You take **INVENTORY AT A GLANCE**—and always have the right tube with you.

Thin, easy-to-carry leatherette cabinet, 20½"x14"x9" deep. Holds up to 249 tubes, or less with space for **TOOLS and METER**, Clips in cover for price list or mirror.

\$13.50  
Net to  
Dealer—  
Higher on  
West Coast

Ask your parts jobber how it  
can **PAY FOR ITSELF**  
in 3 WEEKS,  
or write

Also  
TV Cabinets,  
Wall Baffles

**ARGOS PRODUCTS CO.**  
310 MAIN STREET • GENOA, ILLINOIS



**MANUFACTURERS!  
EXPORTERS!  
PURCHASING AGENTS!**  
• HONESTY • INTEGRITY  
• QUALITY OF  
PRODUCT

- Radio and Receiving Tubes
- Transmitting & Special Purpose Tubes
- Radio and Electronics Parts and Equipment
- All Types of Electrical Wire, Magnet Wire, and Cable

Write — Wire — Phone  
For Your Special Needs

We are also bonafide  
General Purchasing Agents.  
**CAN WE HELP YOU?**  
References: Dun & Bradstreet.

*Electronic Expeditors*

225 N. Wabash Ave., Dept. R, Chicago 1, Ill.  
Phone ANdover 3-0841

BRANCH OFFICES


257 S. Spring St., Los Angeles 12, Cal. MA 6-2004  
507 Fifth Ave., New York 17, New York MU 7-0084

# STEEL TOWERS and MASTS

## Tubing - Roof Mounts - Guy Rings

### PRODUCTS

#### for T-V and ELECTRONICS

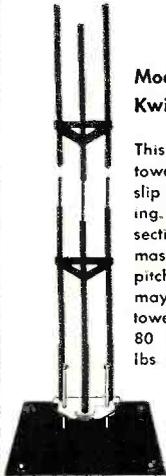

**Model 100 -  
Kwick Climb Tower**

This light weight tubular steel tower comes in 10' sections with slip joints that require no bolting. Safe and easy to climb. Top section has sleeves for up to 2 1/4" mast. Base adaptable to any pitch roof. Additional sections may be added to 100 feet 30' tower complete with base weighs 80 lbs. Additional sections 22 lbs each.

MODELS 130 and 140, 30 foot and 40 foot Manually Telescoping Masts. Priced for that inexpensive installation.




**Model 115 -  
Krank Up Mast**

27' telescoping crank up mast complete with all hardware. Cranks to any positive position from 10' to 27'. Made of sturdy 2", 1 1/2" and 1 1/4" tubing Easily installed.

**Model 125 -  
Krank Up Mast**

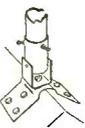47' telescoping crank up mast complete with all hardware. Same as Model 115 in construction Will telescope to any positive position from 20' to 47'. Weight 45 lbs. A locking device on both of the above models removes all the strain from the cable.



### ROOF MOUNTS

**Model A-5 - Apex Roof Mount**  
A sturdily constructed Roof Mount with 4-way swivel. Fully adaptable to any type of mounting. Will take up to 2 1/4 inch tubing.

### ALSO

MODEL S, Rotary 4-way T-V mast base mount  
MODEL P, 2-way swivel T-V mast base mount  
RUGGEDLY CONSTRUCTED MOUNTS - LOW PRICED

**QUALITY PRODUCTS SOLD THRU  
RECOGNIZED JOBBERS**

**JOBBERS and DISTRIBUTORS  
WRITE FOR PRICES AND LITERATURE**

**JONTZ MANUFACTURING CO.**  
1101 E. MCKINLEY AVE.  
MISHAWAKA, INDIANA

Switzerland—Winter schedules of Berne are (to April 30)—*To North America*—2030-2215, HER3, 6.165, HE13, 7.210, HER4, 9.535, HEU3, 9.665, HER5, 11.865; 2215-2300, HER3, 6.165, HI3, 7.210, HER4, 9.535, HEU3, 9.665, and HER5, 11.865. *To South Africa*—0945-1130, HER6, 15.305. *To Eastern Australia and New Zealand*—0215-0400, HER5, 11.865, HER6, 15.305, HER7, 17.784. *To Western Australia and the Far East*—0400-0445, HER5, 11.865, HER6, 15.305, HER7, 17.784. *To South-East Asia and Japan*—To Feb. 29, 0745-0930, HER5, 11.865, HER6, 15.305, HER7, 17.784; from March 1-April 30, 0745-0930, HEU3, 9.665, HER5, 11.865, HER7, 17.784. *To India and Pakistan*—To Feb. 29, 0945-1130, HER5, 11.865, HEU3, 9.665; from March 1-April 30, 0945-1130, HER5, 11.865, HER7, 17.784. *To The Middle East*—HEU3, 9.665, HER2, 6.055. *To Spain and Portugal*—1545-1600 in Portuguese, 1600-1715 in Spanish, HER2, 6.055, HEU3, 9.665. *To Latin America*—In Portuguese 1800-1830, in Spanish 1830-2000, HE13, 7.210, HEU3, 9.665, HER4, 9.535, HER5, 11.865, HE15, 11.715. *To Europe*—0015-0115, 0500-0830, 1000-1730, HER3, 6.165, HER4, 9.535. *To South Africa*—0015-0140, HER6, 15.305; 0500-0730, HER8, 21.520; 1130-1730, HER6, 15.305.

*United Nations Radio*, 6.672, noted with news 1330; news in French 1345. (Pearce, England)

*Taiwan*—When this was compiled, Taipei, 7.133A and 11.730A, had changed time of *English* news from 0630 to 0730 (winter schedule). (Rosenauer, Calif.) Also noted by Stark, Texas, and by your editor in West Virginia.

The *N.Z. DX Times* reports a new station of the Chinese Broadcasting Corporation heard on 10.425 at 0600; call is either BED26 or BED36. Frequency varies greatly.


"The Voice of Free China," Taipei, is now on the air daily with a program directed to Europe 1400-1600 over BED4, 11.800; at 1400 in Russian; 1420 *English*; 1450 French; 1520 Arabic, and 1540 Mandarin. (*WRH Bulletin*) *Radio Australia* reports the 11.800 outlet noted 1500 and with identification in *English* 1700 followed by a program of Chinese music; signal strength and quality vary from poor to good.

The 15.235 outlet noted 0005 with native music. (Winch, Calif.) The *English* transmission on 6.095 now is 0630-0700 but does not appear to be daily. (Rosenauer, Calif.) BED26, 10.080A, noted 0545 with Chinese news and popular music; BED32, 7.010, noted 0645 with Chinese-*English* lesson; BEC22 (?), 9.775, heard 0430 with Chinese news. (Sanderson, Australia)

*Tangiers*—At the time this was compiled, Pearce, England, flashed that he had not heard Pan-American Radio on 7.525 lately; moved?

*Radio Africa* noted on 7.125 at 1630 with call in *English*. (Pearce, England)

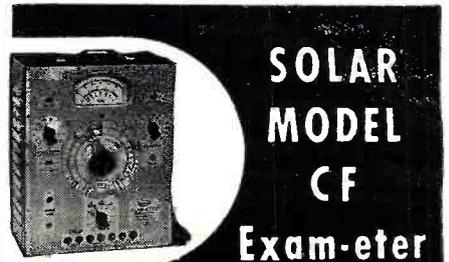*Thailand*—Bangkok, 11.910, noted 0510 with news and weather reports; on 6.240 at 0600 with news, music. (Sanderson, Australia)



# SOLAR MODEL CF Exam-eter

The most complete of all capacitor analyzers, Solar's famous Model CF is a sturdily constructed, reliable instrument designed to simplify electronic servicing.

- Has exclusive patented Quick-Check circuit for qualitative tests and intermittent checks without unsoldering capacitors
- Capacitance bridge—10 mmf to 2000 mf in 4 ranges
- Power factor—0 to 50 percent
- Insulation resistance—3 to 10,000 megohms
- Electrolytic leakage current reads directly on 4 1/2" meter
- Built-in d-c power supply continuously adjustable from 0-550 volts for electrolytic tests under rated voltage
- 100 ohms to 7.0 megohm A-C resistance bridge
- 0-600 volt, D-C vacuum-tube voltmeter
- 10-50 volt A-C vacuum-tube voltmeter
- Quality Components for Long, Trouble-free Service • 115 V. 50-60cy
- Complete with test leads
- Instruction manual

Ready to operate Price: **\$69.95** F. O. B. N. Y.  
20% deposit with order. Balance C.O.D. Jobbers—Write for discounts.

**ARCEE ELECTRONICS CO.**  
96 WARREN ST., N. Y. 7, N. Y.—Dept. A

# SHOCKED

- By a "hot" ac-de chassis? Not if you use Our #409 Isolation Transformer. Prim. 117v 60 cy. Sec. 117v or 145v plus 6.3v tap. Shielded. 2 1/4 x 2 1/2 x 3" high. 40W. \$ 2.45
- \*250 watt output xfmr 6000 ohms PP to 8 ohms W.E. KS9496 from "Beachmaster"... 14.95
  - \*Time Delay Relay adjustable 10 sec. to 2 minutes. Cramer TD2-120S, 115v 60 cy. .... 12.95
  - \*Link mobile xmr w/6v dynamotor 30-42mc nbfm w/tubes Model 25UFM used, good... 59.50
  - \*PP 6K6, 6V6 to 8 or 3.2 ohm xfmr ..... .95
  - \*Single 6V6 to 3.2 ohm heavy duty ..... .79
  - \*Choke 4H 70ma. 70 ohms 69c, 2H 70ma. 100~ .49
  - \*Grid wire, shielded, 1 cond., per 100 ft. .... 2.25
  - \*Fil xfmr 6.3 v. @ 1.3 A. .... .99
  - \*.5mfd 400v bathtub cond. side term. .... .29
  - \*Silver trimmers TS2A 1.5-7, 7-45, 3-12, 4-30
  - \*Silver micas .0001, .00015, .001, .0005, .33mmfd ..... .69
  - \*SloBlo 3AG fuses 1/4, 1/2, 3/4, 10 amps. .... .08
  - \*Variable 100mmfd Bud MC1875 @ \$1.10, 15mmfd ..... .49
  - \*AN3106-10s-2s. PL259AJAN, PL68, JK33 & 84, 83-1H
  - \*Micas, Bathtubs, Oils, Fuses, Sockets, Mini-shields

INQUIRIES INVITED... YOUR SURPLUS BOUGHT  
**EMPIRE ELECTRONICS COMPANY**  
Box 41, Midwood Station, Brooklyn 30, N. Y.  
CLoverdale 2-2411, BRyant 9-1220, 1221

# SPEAKER RECONING

Complete line Cones, Spiders, Rings and Voice Coils. Custom Built Voice Coils. Low prices. Write for Parts List and Reconing information.

**WESTERN ELECTRONICS CO.**  
3164 West Colfax Denver 4, Colo.

# BRAND NEW TUBES

1B23 ... \$ 8.95	YOUR SURPLUS WANTED!	829B ... \$12.50
1B24 ... 8.50	We Pay Highest Prices!	832A ... 9.95
1N2 ... 1.25		836 ... 3.75
1N23 ... 1.49		837 ... 1.49
1N23A ... 2.75		838 ... 2.95
1N23B ... 4.50		860 ... 4.00
3B24 ... 4.50		861 ... 1.63
3E29 ... 14.50		872A ... 2.75
4E27 ... 17.50	726B ... \$25.00	884 ... 1.75
5B4 ... 4.50	807 ... 1.59	931A ... 5.95
5D25 ... 19.95	808 ... 2.95	991 ... .39
6AN5 ... 5.95	809 ... 2.95	993 ... .90
6J4 ... 6.95	810 ... 9.95	1616 ... 1.50
250R ... 8.95	813 ... 8.50	1624 ... .45
3047L ... 9.95	829 ... 9.95	1625 ... .39
307A ... 4.95		1631 ... .89
703A ... 4.95	Vacuum Capacitors	2050 ... 1.75
715B ... 8.95	50-15 ... \$ 5.95	2051 ... 1.50
717A ... 1.59	12-20 ... 6.50	8012 ... 2.50
723A/B ... 14.50	50-32 ... 12.50	8025 ... 4.95

Complete Line of Transmitting & Receiving Tubes.  
**J. S. H. SALES CO.**  
Dept. R-8, 7552 Melrose Ave., Los Angeles 46, Calif.

**RADIO & TELEVISION NEWS**

Trans-Jordan — "The Hashemite Jordan Broadcasting Station," Ramallah, is operating on 7.030 with 500 watts 0045-0130, 0600-0730, 1000-1500; English 0600-0630, 1000-1100. (Bluman, Israel, via *WRH Bulletin*)

Trinidad — VP4RD, 9.625, Port-of-Spain, noted at fair level 1930-2000 and later; announces "This is Radio Trinidad," severe QRM from XEBT, Mexico. (Hoogerheide, Wisc.)

Turkey—Radio Ankara has English now daily for British Isles-Europe 1600-1645 over TAP, 9.465, and TAS, 7.285; noted signing on in Italian 1415 on these channels recently. (Pearce, England) I recently noted TAU, 15.160, in English at 0835; seemed to be calling Germany with a special broadcast.

Uruguay—Radio El Espectador lists its schedule on 11.835 as 0600-2200. (Radio Sweden)

USI—The Indonesian on 11.080 appears to be parallel mornings with Makassar, Celebes, on 9.550. (Stark, Texas) The 11.080 outlet noted around 0800. (Dilg, Calif.) The Indonesian on 7.165A has been identified by Graham Hutchins, DX Editor of *Radio Australia* as an Indonesian Air Force station located at or near Djakarta; for a while was heard regularly mornings but had not been noted for some days (by either Stark, Texas, or Dilg, Calif.) when this was written.

Djakarta, 4.94, noted with French program 1045, strong signal, woman announcer; fades 1115; possibly YDP? (Ridgeway, South Africa) Rosenauer, Calif., reports Djakarta heard recently in parallel over 6.045 and 7.270 at 0900-0930, best on 6.045.

YDC, 15.15, still noted signing on 1400 with English for Europe. (Pearce, England)

"The Voice of Indonesia," Djakarta, has an English language program for South Asia 0930-1030 on 15.150, 11.770, 4.915. (Radio Sweden) YDF, 6.045, Djakarta, noted in native program when tuned 0547; fair level with slight heterodyne QRM. (Bellington, N. Y.)

USSR—Khabarovsk is noted on 6.07 at 0301 in language; fair level in Calif. (Winch) Moscow noted opening 0102 on 6.000 in French session; parallel on 7.34. (Bellington, N. Y.) *Radio Tashkent*, 6.825, noted with English 1000 and 1115-1130. (Pearce, England) A Soviet outlet is noted around 0300-0500 on approximately 15.400. (Osburn, Alaska)

Vatican—HVJ has English news 1000 on 15.120, 11.740, 9.646. (*Short Wave News*, London)

Venezuela—Caracas, 4.9227, noted in native program 2200. (Russell, Calif.)

Yugoslavia—Radio Belgrade, 6.100, heard with call "Radio Yugoslavia" 1630, followed by news in what sounds like Russian; terrific jamming, still noted 1650. (Pearce, England)

### Press Time Flashes


The Yugoslav Emigrant Radio Station (clandestine) seems to be scheduled 0030-0050A on 6.887 and 7.444 (listed) and in second period 0115-0200; during first session only a man talks,

January, 1952

# SURPLUS JANUARY BARGAIN SPECIALS

**ALL NEW**  
30 amp plug fuse, house type  
**A WONDERFUL BUY.....100 for \$3.00**

15 amp 3AG fuses.....100 for	\$2.00
50 amp 5AG type HBR.....100 for	2.95
40 amp 5AG type HBR.....100 for	2.95
40 amp 4AG type.....100 for	2.95
35 amp 4AG type.....100 for	2.95
20 amp 4AG type.....100 for	2.95
15 amp 4AG type.....100 for	2.95
10 amp 4AG type.....100 for	2.95
1 amp 4AG type.....100 for	2.95
4 amp 3AG type.....100 for	2.00
1 amp 3AG type.....100 for	2.00
1/2 amp 3AG type.....100 for	2.00
275 amp HBR type.....100 for	2.95
70 amp HBR type.....100 for	2.95
70 amp ACL type.....100 for	2.95

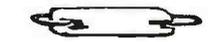

### ANTENNA INSULATORS

A specially designed insulator that provides great tensile strength.....10 for 60c

Open circuit jacks.....10 for	\$1.50
JK 26 and PL 54.....per set	49c
3 AG fuse post.....25c each	
4 AG fuse post.....25c each	
3 AG type HJM.....25c each	
30 ft. hook-up wire.....10c	

1250 ft. of 2 cond. twisted stranded wire.....\$3.95  
2 MFD 600 volt oil condensers, round can.....89c EACH

**LUMINOUS PAINT KIT.....79c EACH**  
For Dusting, Painting or Mixing  
To Suit Your Requirements  
**GLOWS IN THE DARK**



### MUELLER CLIP JUMPER

A complete jumper, ready to use. Two No. 21-A clips and 14" of insulated wire. Packed 10 in a box. 19c each.....Lots of 10 \$1.50

3HK4970—3 Regulator; Carbon Pile; 80V A.C.; Leland #B2475 (76 carbon discs 0.1968" ID; 0.1968" thk; 0.432" OD; solenoid contained in base; 2 5/16" diameter by 1 5/16" high; mounted by a strap fastened around solenoid portion; overall dimension 2.469" diameter by 3 3/4" high.....EACH **\$3.95**

J41A Telegraph Keys.....	\$0.89 each
J5A Telegraph Keys.....	.95 each
J38 Telegraph Keys.....	1.25 each

### DUAL VARIABLE MIDGET CONDENSER, 35 mmfd. per section.....\$1.49

50 watt Birnback tube sockets.....95c each  
3" round Weston meters; Model 476. 0 to 150 volts A.C.....\$5.95 each  
Removed from new surplus equipment.

PL 68 covers only, NEW.....5c each  
6 ft. cord with PL 35 plug.....59c

Head phones, high impedance (Used, Good condition).....\$1.69

250 ft. rolls phosphorus bronze ship-type antenna wire. Seven strands #18.....\$6.95 roll

2 MFD 4000 volt D.C., G.E. 23 F 47 Prynol. \$7.95

90 MFD 120 volt A.C., 3 phase G.E. 26 F 685 Prynol.....\$7.95

Edwards Lungen Buzzers, Type O, #15, 12 volt. Works on 6 V D.C. NEW.....69c each

**VERTICAL ANTENNA MASTKIT** fully adjustable to 35 ft. Easy to setup for Fringe Area FM, Television or Rotary Mast Beam.....\$12.95

6AK5, new, boxed.....\$1.19



**DRY AIR PUMPS.....\$4.95**  
Hand Pump CPL-10198-12 with 30 lb. Shalloss Gauge. Tank for silica gel, 2 bottles of gel, air hose, shut-off valve. Used for drying coax lines, instruments, etc. NEW. INDIVIDUALLY BOXED.

Write for Our Bargain Bulletin

1759 E. Colorado St. **DOW RADIO, INC.** Pasadena 4, Calif.  
\$2.00 min. order PHONE: 5ycamore 3-1196 25% deposit with orders  
Send full remittance to save C.O.D. charges. All merchandise fully guaranteed. Subject to prior sale.

**EVERY RADIOMAN Can Use These SERVICE HINTS!**  
Valuable Manual Yours—FREE!

Every page of "How to Simplify Radio Repairs" is packed with on-the-bench, practical ideas. Contains photos, charts, diagrams—no fluff—no vague theory. In plain every-day language it gives you priceless suggestions—new servicing ideas. You'll use and benefit from the experience of experts. Partial list of contents: How to Localize Trouble; How to Service Amplifiers; How to Test for Distortion; How to Test Audio Circuits; How to Test Speakers; How to Find Faults in Oscillators; How to Test Radio Parts—and it's all yours—FREE! No obligation.

**FEILER** SEND COUPON OR PENNY POSTCARD FOR YOUR FREE COPY TODAY!

FEILER ENGINEERING CO., Dept. 1H2  
8026 N. Monticello Ave., Skokie, Ill.  
(Suburb of Chicago)

Please RUSH my FREE copy of "How to Simplify Radio Repairs."  
Name.....  
Address.....  
City..... Zone..... State.....

**JUST PLUG IN AND TALK!**


Your Cost **\$29.95** ea. NET  
10% Cash with Order

Almo presents amazing new Vocation. No wires. No installation. Just plug in and talk. Use in any AC or DC outlet. Handsome durable gray crackle finish cabinets. Size 6 3/4 x 5 3/4 x 4 3/4. Weight 3 1/2 lbs. Power supply: 105-120 volts, 25-60 cycles. AC or DC. Frequency: 175 KC. AF output: 1.5 watts. Power consumption: 23 watts. 3 Position Switch: Stand-by, talk, and fixed talk. Volume control with On-Off switch.

**ALMO RADIO CO.**  
509 ARCH ST. & 6205 MARKET ST.  
Philadelphia, Pa.  
6th & ORANGE STS. • Wilmington, Del.  
4401 VENTNOR AVE. • Atlantic City, N. J.  
1133 HADDON AVE. • Camden, N. J.

**ARMY — NAVY  
AIR FORCE — MARINES  
SERVICEMEN — TECHNICIANS**

**Here's Help!**

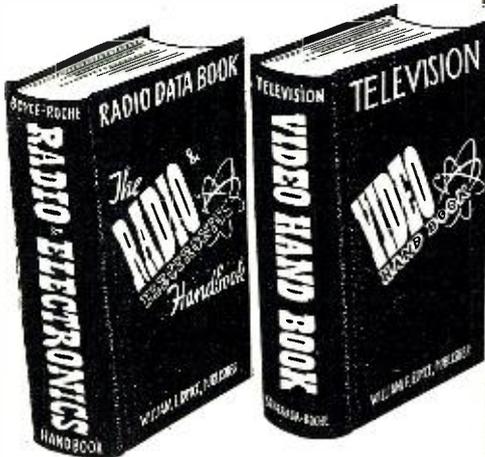

**Now! IN 1800 PAGES**

THE BASIC KNOWLEDGE AND DATA OF  
**RADIO & TELEVISION**  
DIGESTED INTO 32 SECTIONS . . . IN A  
COMPLETE, QUICK-TO-FIND, EASY-TO-READ  
HANDBOOK FORM.

You can plan every operation in TV—Radio and Electronics with the Library Set. These handbooks are your lifelong tools—use them every day on the board, at the bench, or in the field—for construction, production, servicing, installation or operation—for adjusting, trouble-shooting, measuring and testing. Your invaluable aid in service, research, development, design, manufacturing and maintenance. With all data and servicing procedures, these handy books work better, faster and easier. In addition, you get complete coverage of everything you need in TV, Radio and Electronics—in practical form—everything presented in plain talk, all terms explained; schematics, working diagrams and pictures all clearly illustrated for your quick and easy reference.

These books are works of complete authority prepared by the well known engineers, Joseph J. Roche and Morton Scheraga, under the direction of William F. Boyce, famous for the preparation of hundreds of handbooks and manuals for the U. S. Signal Corps, U. S. Navy, U. S. Air Force, Western Electric Co., General Electric Co., Bell Laboratories, National Radio Co., and many others.

These Handbooks are endorsed by leading schools for instruction and reference. The armed services make them available to their technicians in libraries, schools, and in the field. Engineers, Draftsmen, Laboratory and Production men in every industry have purchased over 50,000 of these books for use in their work.

500 Radio jobbers keep them constantly in stock for the convenience of their service and industrial customers. These are the most commonly used books in Radio and TV.

Whether you use these Handbooks for general reference, scientific instruction or education, one thing is certain; the practical help, the daily usefulness you will derive from them will prove to be worth many times their price.

Contents are too long and complete to describe here, so see the books at your Radio Jobber, your bookstore, or

**SEND FOR TEN DAY  
FREE TRIAL EXAMINATION**

**RADIO ELECTRONICS HANDBOOK.....\$7.00**  
**VIDEO HANDBOOK.....7.00**

**SPECIAL OFFER! SAVE \$2.00**

**The LIBRARY SET.....\$12.00**

**BOYCE ROCHE BOOK CO.**  
Caldwell 11, New Jersey

Send ( ) Library Set (2 books) @ \$12.00  
( ) Radio Electronics Handbook @ \$7.00  
( ) Video Handbook @ \$7.00

In ten days I will send price plus postage, or I will return books postpaid.  
(Offer good in U.S.A. and to men in Armed Services overseas only.)

Name.....

Address.....

Employed by.....

Save postage—we pay postage and packing if you send money NOW. Money back on same return privilege.

presumably in a Slavonic tongue; in second period both a man and woman are heard; cannot find on 9.14 at that time. Also noted on 6.887 afternoons or later. (Bellington, N. Y.; Harris, Mass.; Machwart, Mich.) Bellington also has noted the 6.887 outlet in parallel with one on 6.28 at 1745.

Radio America, 9,405, Lima, Peru, announces *English for every day* at 1200 and *Sundays* at 2100. (Stark, Texas)

Nepal Radio, 7,100, Kathmandu, Nepal, verified for Dilg, Calif. Gave schedule of 2150-2320, 0320-0450, 0820-0950; *English* news is 0845-0850. Station opened last April. Hopes to expand. Said Kathmandu time is 10 minutes ahead of Indian Standard Time which makes it 10 hours and 45 minutes ahead of EST.

Bellington reports Greenland on approximately 7.580 from around 1730 to 1845 when closes with Danish Anthem; man announcer.

Radio Sweden says Hamburg, Germany, has two new transmitters on 17.815 and 17.815, respectively, in parallel with 7.290, 11.795.

Pakistan has changed its time—West Pakistan (Karachi) is now 9½ hours ahead of EST, while East Pakistan (Dacca) is 11 hours ahead of EST. (WRH Bulletin)

RIAS, 6,005, Berlin, Germany, is heard regularly in England with powerful signal; often features dance music around 1330; QRA is RIAS, Berlin-Schoneberg, Kufsteiner Strasse 69, Berlin, Germany. Radio Andorra, 5,990, noted around 0700 with Latin-American music, announcements in French and Spanish. Radio Mediterraneo, 7,037, Valencia, Spain, heard with strong signal prior to closedown 1830. (Catch, England)

The English transmissions from Lourenco Marques, Mozambique, are now 2300-0200 on 11.762, 4.911; 0200-0500 on 11.762, 7.305; 0500-0800 on 11.762, 9.732, 7.305; 0800-1200 on 11.762, 7.305; 1200-1600 on 4.911, 3.490. (WRH Bulletin)

The Swiss Broadcasting Corporation by this time should have a DX session in English in its various transmissions (probably on the first Tuesday and/or Wednesday of each month); I hope to have details soon.

Australian DX-ers Calling is now Sundays 0030 on 15.200, 21.540; repeated 0902 on 9.580, 11.810, 15.320; no longer heard 0200.

"The Voice of Free China" at Taipei, Taiwan, is now radiating these Overseas Services—2300-0200 to USA on 15.235 (BED3) and 11.735 (BED6), English to 0000, Chinese slow-speed news from 0100; 0530-1100 on 7.130A (BED7) and 11.735 (BED6), to 0800 to Japan, Korea, and South East Asia, with news 0730, news in French 0740-0750, and from 0800 to Chinese mainland; from 1100 to 1230 has dictation news in Chinese to China and South East Asia on 6.095 (BED9), 7.130A (BED7), and 11.735 (BED6). (WRH Bulletin)

WRH says Radio Free Europe is now operating on six s.w. channels—6.020,

## TUBE SPECIALS

VR-150	...	\$0.95	6SJ7	.....	\$0.75
1L4	.....	.65	6SJ7Y	....	.90
1LH4	.....	.98	6V6GT	...	.65
1R4	.....	.95	6Y6G	.....	.85
1R5	.....	.75	394-A	....	3.98
1S5	.....	.75	717-A	....	1.05
1T4	.....	.75	807	.....	1.45
3S4	.....	.75	CK1005	...	.57
5D21	....	21.50	1619	.....	.45
5GP1	.....	3.95	1624	.....	1.35

## ARCBY ELECTRONICS

103 West Liberty, Louisville, Ky.

## WHOLESALE PHOTO SUPPLIES

KODAK • ANSCO • GRAFLEX • Others  
Radio Service Shops Coast to Coast  
Increase Profits with Photo Supplies

You can add big photo equipment sales to your gross almost over night. Gamera's fast wholesale service on any quantity, low inventory investment, and low space requirements make it easy to capitalize on photo equipment sales. WRITE FOR CATALOG AND DETAILS NOW.

**GAMERMAN**

DEPT. R-1  
3808 EASTERN AVE.  
BALTIMORE 24, MD.

## ON-THE-SPOT BATTERY RECORDER

WALKIE-RECORDALL 8 lb. miniature BATTERY RECORDER-PLAYBACK  
Continuous, permanent, accurate, indexed recording at only 5¢ per hr. Instantaneous, permanent playback. Picks up sound up to 60 ft. Records conferences, lectures, dictation, 2-way phone & sales talks; while walking, riding or flying. Records in closed briefcase with "hidden mike"! Write for Detailed Literature.

**MILES REPRODUCER CO., INC.**  
812 BROADWAY Dept RN-2 NEW YORK 3, N. Y.

## VARIAC COMBINATION

G.R. Co. 200C 5 to 7½ Amp.  
115 VAC input 0-135 VAC output

## WESTINGHOUSE BA-33

0-150 VAC iron vane 2" R. panel meter these have been removed from new equipment. Guaranteed like new while they last. Both for.....\$20.95

**McCONNELL'S** 3834 Germantown Ave. Phila., Penna. RA 5-6033



Please send me FREE Jenselector. Picks the proper replacement needle.

Name.....

Address.....

City..... State.....

Jensen Industries, Inc., 336 S. Wood St., Chicago 12

**RADIO & TELEVISION NEWS**

6.095 at 2300-1900; 6.130, 7.165, 7.300 at 1000-1900 and 9.607 at 1200-1900.

Paris noted on 21.740 to 1045 sign-off; on 11.700 at 1615 in French. (Leary, Ind.)

Radio Peking now has news 0400 instead of former 0430. (Alcock, Ky.) Confirmed by Cushen, N. Z., who lists frequencies at that time as 6.100, 10.260, 11.690, 15.060, 15.170 (these vary somewhat). (Radio Australia)

The Indonesian Air Force station, 7.163A, believed located at or near Djakarta, now signs off 0630 instead of former 0845. (Rosenauer, Calif.) Confirmed by Cushen, N. Z. (Radio Australia)

Dilig, Calif., hears Thailand on 7.105A, in dual with Bangkok, 6.240, around 0900 in native.

Russell, Calif., notes AFRS, Tokyo, on measured 9.6054 and 11.825 with news 0100.

Ridgeway, South Africa, flashes that Salisbury, 9.50, Southern Rhodesia, now closes 1315 on 9.60 after which continues on 3.320; Luanda, Angola, on 9.64 at 1300 parallel with 7.148; Radio Tananarive, 7.37 and 9.695, Madagascar, with Malgache programs, opening 0905 after interval signal of Malgache guitar.

Ferguson, N. C., recently noted Lisbon on 15.020 with a program for Chile to after 2017; Indo-China on 9.740 around 0530 to after 0630; HJCCQ, 11.680, Bogota, Colombia, opening 0700; Baghdad's listed 11.724 measured on 11.726 at 2257; Moscow 1233 with news on 15.360.

Gerran, N. Y., reports YVQI, 3.450, Barcelona, Venezuela, at 2116 through heavy QRM; YNHB, 6.550, Managua, Nicaragua, around 2048 with music; YNDG, 7.660, at 2100 in clear with music; AIR on 11.85 with news 1930 (is parallel on 15.29); Paris, 9.680, signing on 1900 with "La Marseillaise."

Bellington, New York, flashes that he recently heard Athens on 7.300 with news 0000; that Greenland is again audible on 7.575 around 1746 tune-in to after 1800, mostly music, and that Lagos, Nigeria, 7.255, is sometimes audible around 0001.


Short Wave News, London, says Radio Eirrean hopes to start broadcasting over the new high-powered station within six months now that the new Government "has given the green light. Vatican Radio will probably be one of the first users of the new station."

An attractive QSL card has been received from the new Spanish station at Cadiz, "Radio Juventud, Escuela No. 17 del Frente de Juventudes," which translates "Radio Youth, School No. 17 of the Youth Front." The frequency is 7.200 and the QRA is "Radio Juventud." Buenos Aires 4, Cadiz, Spain. (Short Wave News, London) This one noted signing off 1800A. (Bellington, N. Y.)

Canada's International Service schedules are — European Service — 0850-1130, CKNC, CKCX; 1130-1330, CKNC, CKCS; 1330-1345, CKCS; 1345-1400, CKCS, CHOL; 1400-1420, CHOL; 1420-1545, CHOL, CKLO; 1545-1600,

# THE JUN OR SUPER-METER
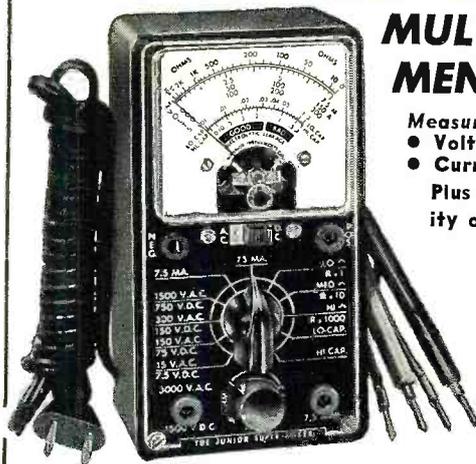
## THE MOST COMPLETE AND COMPACT MULTI-SERVICE INSTRUMENT EVER DESIGNED!



- Measures:
- Resistance
  - Inductance
  - Voltage
  - Capacity
  - Current
  - Reactance
  - Decibels

Plus Good-Bad scale for checking the quality of electrolytic condensers.

### Specifications:

D.C. Volts: 0-7.5/75/150/750/1500 Volts.  
A.C. Volts: 0-15/150/300/1500/3000 Volts

### Resistance:

0-10,000/100,000 ohms. 0-10 Megohms.  
D.C. Current: 0-7.5/75 Ma. 0-7.5 amperes.  
Capacity: .001 Mfd.—.2 Mfd..1 Mfd.—20 Mfd.  
Electrolytic Leakage: Reads quality of electrolytics at 150 Volt test potential.

Decibels: -10 Db. to +18 Db. +10 Db. to +38 Db. +38 Db. to +58 Db.

Reactance: 15 ohms—25 K ohms 15 K ohms—2.5 Megohms.

Inductance: .5 Henry—50 Henries 30 Henries—10 K Henries.

Handsome round cornered molded bakelite case 3 1/8" x 5 7/8" x 2 1/4" complete with all test leads and instructions.

**\$21.40**


## SOLD ON EASY PAYMENTS AT THE NET CASH PRICE

No interest or carrying charges added. Simply remit \$5.40 with order, pay balance \$4.00 per month for four months.

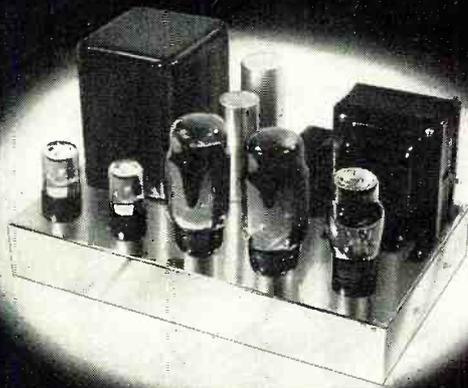**MOSS ELECTRONIC DIST. CO., INC.**

Dept. B-7, 38 Murray St., New York 7, N.Y.

MEET THE FINEST audio amplifier ever built, at any price. Its name: the Craftsmen 500, with the famous Williamson all-triode circuit. We had to invent a new word to describe its 99.99%\* distortion-free performance. The word is ULTRA-FIDELITY. Hear the "500" and you'll know why.



### C500 Amplifier Features

- Freq. response:  $\pm 0.1$  db., 20 cps to 20,000 cps;  $\pm 2$  db., 5 cps to 100,000 cps.
- Power response: 12 watts  $\pm 2$  db., 10 cps to 50,000 cps.
- Total H Distortion: Less than 0.1% at 10 watts, at mid-freq.
- \*0.01% at av. listening level below 1 watt.

• Tube complement: (2) 6SN7GTA; (2) KT66 power output; 5Y4G rectifier.

for information, write

THE RADIO **craftsmen** INCORPORATED

Dept. R-1, 4401 N. Ravenswood Ave., Chicago 40, Ill.

# Specified by Manufacturers\* for Servicing 2-Way Mobile Radios



**Leading Manufacturers Say . . .** "It's the only one to withstand continuous high overloads, so we specify the Model "B" for servicing." Exclusive application of selenium rectifiers, aided by conduction cooling, doubles rectifier power rating, dissipates over 3 times the heat with lowest cost per ampere output. 1 to 20 amperes continuous duty with peak instantaneous rating of 35 amperes. Operates 2 auto radios with push-button solenoids simultaneously. **Net \$49.80.**

**Other Uses**—Phone circuits, relays, instruments, low voltage devices. Battery charging and electroplating. \* Names on request.

**Model "BJ" Low Cost Power Supply**  
6 Volts DC 1 to 12.5 Amperes Net **\$37.50**



Model "S"

**Converts Battery Radios to All-Electric**  
Plugs into AC outlet. Hum-free reception from any 1½ volt 4-6 tube battery radio. Uses less than ¼ the power of cheapest AC radio. Fits battery space. Guaranteed 3 years.



Many Others Available  
**FREE BULLETIN**  
ON BATTERY ELIMINATORS

**ELECTRO PRODUCTS LABORATORIES**  
4501-NP Ravenswood Ave., Chicago 40, Ill.

Name \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_  
In Canada: Atlas Radio Corp., Ltd., Toronto

CKLO; 1600-1830, CKLO, CKRZ. *Australasian Service*—2300-2335 (except Sat., Sun.), commentaries from the United Nations, CHOL, CKLO; 0340-0450 (Sun., Wed. only), English sessions, CHOL, CKLO. *Caribbean and Latin American Service*—1850-2240, CHOL, CKLO; English 2105-2135. Channels are CKNC, 17.82; CKCS, 15.32; KKCX, 15.19; CHOL, 11.72; CKLO, 9.63; CKRZ, 6.06.

The Malayan Station on 6.135, reported by Rosenauer, Calif., earlier as probably Kuala Lumpur, has been identified by Graham Hutchins, *Radio Australia*, as *Radio Malaya*, Singapore; noted mornings.

Bangkok, 6.240, has *English-Thai* session 0500-0625 now; around 0624 gives preview of next day's program. (Radio Australia)

DYH4, 6.055, Dumagete City, Philippines, noted in Calif. 0800-0830 sign-off in *English*; fair. (Rosenauer)

Rome, 17.800, noted 1445-1500 in *English* for South Africa. (Alcock, Ky.)

Teheran has informed Harris, Mass., it operates with 20 kw. on 15.100 with German 1330; *English* 1345 and 1500; 1400 Persian program for Iranians abroad; 1445 French; 1515 in Russian; signs 1530 with Iranian National Anthem; *English* may not be daily according to schedule furnished.

OAX4Z, 5.8873 (measured), Peru, noted signing off 2345 after anthem. (Russell, Calif.)

PRF6, 4.895, Manaus, Brazil, noted 2346-0325 and later; announces "Radio Bare, en Manaus, Amazonas, Brasil." Noted another night leaving the air 0100. HI1Z, 6.112, Trujillo, Dominican Republic, noted signing off after anthem 2301. HC2FB, Guayaquil, Ecuador, noted on *new* channel of 6.118 after HI1Z leaves the air, signs 0058. (Machwart, Mich.)

Copenhagen is now scheduled to North America daily 2030-2130, 2200-2300 on 9.520.

ZM2AP, Apia, Western Samoa, operated by the New Zealand Broadcasting Service, should be testing soon on 3.410 and 6.040; schedule should be 0030-0330 (Mon. 0100-0230), 1500-1600. (Cushen, N. Z.)


*Radio Pakistan*, 11.675, has good signal opening 0830 with program for Burma. (Ferguson, N. C.; Boord) Carriers news 1015.

*Radio Dalat*, Indo-China, is broadcasting a daily program in Vietnamese on 7.265, 1 kw., at 0515-0630; a program in French is on the air each Saturday 0630-0700. *Radio Hanoi* operates on 6.165, 1 kw., at 1830-1930, 2300-0030, 0500-0830 in Vietnamese, French, *English*, and Chinese; news in French 1805-1820, 2345-2400, 0730-0755; news in *English* 0530-0545. (WRH Bulletin)

### Acknowledgement

Thanks for all the splendid reports during 1951, fellows! May 1952 bring you much worth-while DX! Send reports to Kenneth R. Boord, 948 Stewartstown Road, Morgantown, West Virginia, USA. . . . . KRB

**BOTH BOOKS FREE**

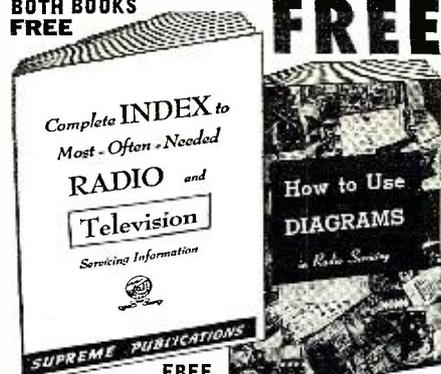

**FREE** to every reader of RADIO & TV NEWS. No strings, nothing to buy. "How to Use Diagrams" gives hints, suggestions, short cuts on the use of diagrams in radio servicing. The 25-page INDEX will tell you just what models or television manuals. If you need a circuit at any time, the INDEX will tell you where to get it. Get both books in 2-in-1 volume FREE; just send stamp for postage. 3727 W. 13th St. CHICAGO 23, ILL.



**Reconditioned LIKE-NEW EE-8 Phones, per pair. \$36.50**

**GRADE I—Unused, excellent condition.**  
Mile reels (wt. 160 lbs.) . . . . . \$22.50  
Half-mile reels (wt. 80 lbs.) . . . . . 12.50  
500 ft. reels (wt. approx. 15 lbs.) . . . . . 4.95

**W-130—Lightweight Assault Wire—2 Conductor. Excellent inter-com wire. Unused, excellent condition. 10,500 ft. reels. 57.50**  
Approx. 3,800 ft. reels. . . . . 19.50

Send for **FREE FOLDER**  
All prices F.O.B. Sacramento. No C.O.D. (Calif. residents add 3% for sales tax.) Prices subject to change without notice. Send check or money order.

LORIS SALES, P. O. Box 1896 M-1, Sacramento, Calif.

### SCHEMATICS—CONVERSIONS FOR SURPLUS GEAR

**NEW LIST! MANY ADDITIONS!**  
Send stamped, self addressed envelope for List B. Add 25c for chart explaining AN nomenclature.

R. E. BOX 1220  
GOODHEART BEVERLY HILLS, CAL.

### DIAMOND NEEDLES \$10.50 plus postage

Our main business is the manufacture of diamond styli for broadcasting stations and high fidelity sound equipment. As a service to the general public we offer to retip your present replaceable needle with a genuine, unconditionally guaranteed broadcast quality diamond tip for either LP or Standard records.

Send us your replaceable needle (or complete cartridge except Pickering) together with check or money order for \$10.50 plus 25c for shipping.

### THE TRANSCRIBER CO.

176 Green Street Boston 30, Mass.



**HIGH SPEED WITHOUT NERVOUS TENSION**  
REVEALING BOOK shows how "crack" operators develop high speed and proficiency. Learn code for Amateur or Commercial Radiotelegraph License, or improve your sending and receiving

with the Candler System which develops radiotelegraph experts and code champions.

**CANDLER SYSTEM CO. FREE BOOK!**  
Box 928, Dept. 2-A, Denver, Colo.

# Technical BOOKS

**"TELEVISION INTERFERENCE"** by Philip S. Rand, et al. Published by the Laboratory of Advanced Research, Remington Rand, South Norwalk, Conn. 80 pages. Will be sent to any ham without charge upon postcard request to the company.

This paper bound booklet contains seventeen articles on the subject of TVI reprinted from several well-known technical magazines in the radio field.

The articles cover a variety of topics ranging from curing r.f. heater television interference, to "TVI-proofing" the 10 meter transmitter, and other pertinent information.

Most of the articles contained in this reprint were originally prepared by Mr. Rand although one of the articles was authored by George Grammer and another by A. David Middleton. All of the material is of vital interest to the ham and we would like to suggest that amateurs get their requests in early for copies of this booklet.

Reprints from RADIO & TELEVISION NEWS, Modern Plastics, QST, Electrical Manufacturing, CQ, and Electronics have been included.

\* \* \*

**"HIGH FREQUENCY TRANSMISSION LINES"** by Willis Jackson. Published by John Wiley & Sons, Inc., New York. 149 pages. Price \$1.75.

This small handbook contains much practical information of interest to those working with the high frequencies.

In six concise chapters the author covers such topics as the applications of transmission lines at very high frequencies, the basic equations for transmission lines propagating in the principal mode, the propagation characteristics of lines, the behavior of terminated lines, resonant lines, and impedance transformation and the use of the circle diagram technique. Two appendices provide data on the construction of a Cartesian grid diagram and on the construction of the polar form of diagram. A supplementary bibliography completes the work.

Treatment of the subject is largely mathematical so a working knowledge of advanced algebra and calculus is a "must". The author's style is lucid and if the reader can hurdle the barrier of the formulas, he should derive considerable benefit from this text.

## PHOTO CREDITS

Page	Credit
31 (left), 32 (right)	Baltimore & Ohio
32 (top), 33 (right)	Bendix Radio Division
32 (left)	Missouri Pacific
33 (top)	Maryland & Pennsylvania R. R.
33 (lower left)	Toledo Terminal Railroad
34, 35	Globe Radio & Sound Service
45	Pyramid Electric Co.
54	Langevin Manufacturing Corp.
57	Radio Tokyo
63	General Electric Company
66, 67	Republic Studios, Hollywood
68	Cinema Engineering Co.
78	Brach Manufacturing Corp.
100	U. S. Army
111	Allen B. Du Mont

Let MILTON S. KIVER Help You Prepare For U.H.F.-TV And...

# TELEVISION SERVICING

Easy to TRAIN AT HOME This Practical Way!


Men with the right training in Television Servicing are in big demand... pull down big pay. T.C.I. TRAINS YOU RIGHT with easy-to-follow technical training designed by servicemen, for servicemen! You learn practical, professional type Television Servicing without leaving your present job. Included are money-making extras such as set conversion, master antenna installation, U.H.F.-TV and field servicing short cuts. You can start earning Television money after the first few lessons. You learn to test, trouble shoot and repair all types of TV sets the Proven, Practical way!

HERE'S HOW YOU GET EXPERIENCE!

You train on your own large screen modern television receiver, furnished as part of your course. This set is yours to keep! As an optional feature you can get two weeks of actual field experience out on service jobs and on the repair bench for Chicago's largest independent servicing organization. You learn Television Servicing by actually doing Television Servicing... you get the practical know-how you need to qualify for BIG MONEY in this fast-growing field! Age is no barrier. Many TCI students are over 40!

ACT NOW! Fill out and mail coupon for FREE Catalog and SAMPLE LESSON. Write TODAY!

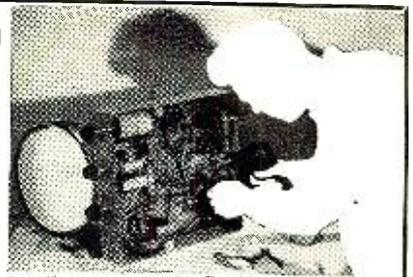**TELEVISION COMMUNICATIONS INSTITUTE**  
205 W. Wacker Dr., Dept. 1-S, Chicago 6, Ill.



**YOU GET** and keep modern large screen Television receiver.  
**YOU DO** actual testing, servicing, trouble shooting and repairing

**NEW! TV BROADCASTING TRAINING**  
2,000 New TV stations will need video engineers, cameramen, microphone engineers, etc. Train at home for these big pay studio jobs! Easy non-mathematical training covers all phases of TV Broadcasting. Write for facts!

**MAIL NOW FOR FREE BOOKLET**

MILTON S. KIVER, President  
TELEVISION COMMUNICATIONS INSTITUTE  
205 W. Wacker Dr., Dept. 1-S, Chicago 6, Ill.  
Rush full facts on the course checked below. I am not obligated. Salesman will not call.

( ) TV Servicing ( ) TV Broadcasting

Name..... Age.....  
Address.....  
City..... Zone..... State.....  
( ) BEGINNERS check here for information on Pre-Tel Radio Course.

## TRANSFORMERS—CHOKES—COMPONENTS

NEW STOCK—LOW PRICES!!

115V-60 CYCLE PRIMARIES		GE Cat. Section	
7475689*	8.3-10.0A .....	747068*	7.4; 6.3; 5.0; 2.5-1.4KVA.
7479609*	11.0-0099KVA ...	7477914*	1500VCT-15MA; 2.5V-1.75A
7475689*	11.0-005KVA ...	7477932*	6.3V-0.6A .....
7478435*	6.3CT-6.3CT; 12.6-12.6A ..	676700*	100MA; 6.3-2.0A; 12.6-12.6A; 7.5-2.0A .....
7475698*	6.3CT-126KVA ..	676700*	2.5VCT-.025KVA..
208/230 V-60 CYCLE PRIMARIES			
7479614*	8.3V-20.0A .....	7477795*	1100VCT-200MA..
7480435*	25.0V-2.0A .....	7479675*	3X10VCT-1225KVA .....
7475682*	6.3V-1.0A .....	7475626*	6.3VCT; 6.3V; 5.0V (3.0 A each)
7477712*	22.6-1.4A .....	7476465*	Marked 60 cycle Vertical sweep
7477947*	24.0-1.0A .....	7476420*	M a r k e d 60 cycle Horizontal Sweep .....
7478454*	5.0-24.0A .....	7470613*	115 / 230 V; 2.5V-2.5A .....
7475625*	2.5VCT-10.0A ..	7467115*	80V P H I 17.6V-.1A .....
7475625*	1550VCT-300MA..		
CHOKES—REACTORS			
7478426*	8 HENRY-.075A ..	7471937*	10 HENRY-.4A ...
7471985*	20 HENRY-.050A..		1.35

\* G.E. Cased. ° Open Frame Construction.

## MISCELLANEOUS PARTS EQUIPMENT—ALL BRAND NEW

Input Xformer—WED171088—H'S'LD .....	\$ 1.25
Output Xformer—WKS88615—H'S'LD .....	1.25
CHUKE-RAYTH—U7862-17.5 HEN-20MA-CSD .....	.99
PULSE Xform.—P.O. AN/APS13 901736-501 .....	1.00
BLOCK OSC. Xform.—P.O. AN/APS13 901737-501 .....	1.95
FL. Xform.—WE D161917-115-60 SEC. 6.3V; 2.5V; HV Insul. H'S'LD .....	2.95
SET Input—Interstage—Output Xform. Mid by THORD for G.E. Streamline Series T50044; T50996F; 49232B Set of 3 (no specs) .....	10.00
KOOLOHM—120KT-10K ohms-120W-W/all mtg hdwe and insul.—Ind. packed .....	1.00
25 Watt RHEOSTATS—Most sizes—famous makes .....	.69
BATHTUB ELECT.—20MFD-50VDC S.T. ....	1.4
HV COND.—C.D.—1.0MFD-1KV .....	.25
XTAL DIODE—IN22 Ind. boxed—new .....	1.00
PYRANOL—.03-7500VDC orig. pack. ....	1.60
PYRANOL—.15-4KVDC—Orig. pack. ....	1.75
SMALL CHANNEL Cond.—1-1KV GE .....	.50
HV Condenser—.001-7500VDC AERO orig. pack. ....	74.95

(Above listing available in Quantities)

TERMS: F.O.B., N.Y.—25% Deposit—Bal. C.O.D.  
Rated Firms: Net 10 days.

## GREENWICH SALES

59 CORTLANDT ST., NEW YORK 7, N. Y. Dlgby 9-3813

**NOW... quickly, easily**  
cut **SQUARE** and **OBLONG** openings in radio chassis

**WITH THE GREENLEE No. 731 SQUARE RADIO CHASSIS PUNCH**

Now, in 1½ minutes or less you can do hole-cutting jobs that might take an hour with old "drilling and filing" methods. Simply insert GREENLEE Punch and turn with an ordinary wrench... a square or oblong opening is cut immediately. An indispensable, timesaving tool that pays for itself in a hurry.



In sizes ½", ¾" and 1"  
**GREENLEE**

Write today for facts and prices on this handy Punch. Greenlee Tool Co., 1881 Columbia Ave., Rockford, Ill.

# QUALITY TESTED TUBES

New and guaranteed in stock now; many others not listed—complete line of receiving tubes at low prices. Submit your requirements on any types for our quotation. Call us on Westinghouse and other types of industrial and special-purpose tubes.

0A2	1.00	6C4	.65	12AY7	\$2.75
0B2	1.10	6CB6	.70	12BA7	.90
0Z4	.65	6CB6	.85	12BH7	.70
1B3GT	.85	6CD6G	1.75	12BE6	1.00
1N21	.80	6F7	.98	12BH7	.70
1N21B	3.50	6F8G	.98	12SH7	.95
1N23	1.45	6H6	.75	12SJ7	.75
1N23A	2.50	6J5GT	.55	12SK7	.75
1N23B	1.75	6J6	.70	12SL7	.75
1N34	.68	6I7	.95	12SO7	.75
1R5	.65	6K6GT	.79	25BQ6GT	.98
1U4	.65	6K7	.75	25L6GT	.65
2B7	.75	6K8	.80	35C5	.60
3A4	.85	6L7	.98	35Z5GT	.60
3A5	1.10	6R8	.90	50C5	.60
3A6	.55	6SA7	.75	60L6GT	.60
3Q4	.55	6T8	.80		
354	.90	6S6GT	.98	304TL	11.50
5F7	1.95	6SH7	.70	304TH	11.50
5U4G	.59	6SK7	.75	717-A	.98
5V4G	1.05	65L7GT	.75	807	1.65
5X4G	.85	65N7GT	.70	813	7.75
5Z3	.98	65Q7	.70	813	7.75
6AC7	.95	6B6	1.25	872-A	2.25
6AG5	.85	6U4GT	.80	955	.45
6AH6	1.50	6V6GT	.60	956	.37
6AJ5	1.95	6V6M	1.50	1616	.75
6AK5	1.25	6W4GT	.50	1624	1.40
6AK6	1.30	6X4	.45	1625	.40
6AL5	.55	6Y6GT	.45	1626	.40
6AU5	.65	6Y6	.75	1629	.30
6AV6	.55	7H7	.80	5866	3.95
6B4G	1.25	12A6	.75	5910	.75
6BA6	.70	12C8	.85	9004	.44
6BE6	.70	12AT7	1.00	9005	1.50
6BG6G	1.20	12AU7	.75	9006	.44
6BQ6GT	.90	12AV6	.55	VR-105	1.25

• CARTER, 6 Volt Dynamotors Brand New—400 VDC @ 375 ma. List Price \$71.40. Your Cost—Special .....\$28.00

• TV "Cheater" Cord—6 Ft. Complete. U.I. App'd. Reg. net 59c. Special.....39c

• ART-1—75 meter DeLuxe Mobile AM XMTR. Complete. New @ .....\$25.00

• AR-11—Complete, Ultra-compact XMTR-RCVR. Write for Details.

• Speco Signal-Tracer Kit. Complete with 3 tubes, steel case, all parts, cabinets, easy instructions, less batteries. Only .....\$9.45

• 300 ohm quality Twinlead. Pure Poly. 55 Ga. #20 wire. All tinned strands. New, 1,000 Ft. Roll .....\$20.00

• RG 59/U—73 ohm CO-AX Cable. New, 1,000 Ft. Roll .....\$55.00

## ELECTROLYTIC CONDENSERS

All Guaranteed Fresh Stock		Lots of 10		Lots of 100	
20x20—150 V.	39	53.70	534.95	39	39.95
40x40—150 V.	44	4.30	41.95	44	41.95
50x50—150 V.	49	4.50	41.95	49	59.95
40x40x20—150 V.	69	6.70	59.95	69	59.95
50x30x20—150 V.	79	7.70	69.95	79	69.95
50x50—150V. (200-25V.)	39	3.69	32.50	39	32.50

• PM Speakers—New, Boxed.

Imported English Hi-Fi Speakers	
3".....\$1.60	5".....\$2.15
4".....1.65	6".....3.50
5".....1.75	8".....4.50
6".....1.89	10".....5.50
12".....5.95 (RCA)	

• New, Selenium Rectifier Transformers

PRI: 110V, 60 cycle in. } 4 Amps...\$ 7.75  
SEC: 18, 24, and 36 } 12 Amps... 14.75  
Volts } 24 Amps... 33.75

Designed for Bridge or Center-Tap use—Not Surplus.

• 110 V. PRI.—36 V. @ 50 Amp. SEC. \$39.95  
• 110 V. PRI.—5 V. @ 190 Amp. SEC. 85.00

## Selenium Rectifier Specials

110 V., 1/2 Wave.... 65 ma....only \$9c each  
110 V., 1/2 Wave....450 ma....only \$1.65 each

## SELENIUM RECTIFIERS—FULL-WAVE BRIDGE TYPES

Current (cont.)	18/14 Volts	36/28 Volts	54/40 Volts	130/100 Volts
1 Amp.	\$2.40	\$1.98	\$6.95	\$10.50
2 Amps.	4.85	3.00	9.00	
4 Amps.	5.65	9.00		
6 Amps.	5.95	14.00		48.00
10 Amps.	5.95	20.50		58.00
12 Amps.	13.25	25.00		
20 Amps.	14.00	25.00		
24 Amps.	19.00	30.00		
30 Amps.	25.50	35.00		

All our Rectifiers are new & Guaranteed one year. We manufacture special types of rectifiers and rectifier supplies to your specs. . . . FAST DELIVERY.



136 Liberty Street, N. Y. 6, N. Y. Rector 2-2563  
Terms: 25% with order, balance C.O.D.—Send a few cents for postage—All merchandise guaranteed, F.O.B. N.Y.C.

# Classified

Rate 50c per word. Minimum 10 words

## RADIO ENGINEERING

RADIO Engineering Broadcasting, Aviation and Police Radio, Servicing, Marine Operating and Electronics taught thoroughly. Expenses low. Write for catalog. Valparaiso Technical Institute, Dept. N, Valparaiso, Ind.

## SALE

TOWERS: 100-foot galvanized steel, bolted, sectional, 12-foot square base, pyramidal. Ideal for long distance TV and FM antenna mounting. Penn Albert Hotel, Greensburg, Pa.

RADIOTONE RA16 portable dual speed 16" recorder, amplifier, tuner, speaker. Recordings air, microphone, instrument. 90-130LPI reconditioned, \$225.00. W. Harmon, 1301S 19th, Birmingham, Alabama.

DIAGRAMS Radio, Record Changers, Recorders, 75c; Television with Service Data, \$1.25 up. State manufacturer and model number. Kramer's Radio Service, Dept. N8, 36 Columbus Ave., New York 23, N. Y.

HOTTEST surplus list in the country. Electronics-Hydraulics, Aircraft-Gadgets. Dick Rose, Everett, Wash.

RECORD changer parts for leading makes. We ship everywhere. Friend's Wholesale Distributors, 106 N. 6th St., Philadelphia 6, Pa.

COLOSSAL bargain in radio parts, over 150 assorted radio parts including resistors, condensers, controls, coils, etc. All new, \$75.00 value, guaranteed satisfaction or money refunded, postpaid in U.S.A., \$3.00. Write for catalog. Buyers' Syndicate, 30 N. Taylor St., Springfield 3, Mass.

HEARING aids, used. Zeniths, less accessories, \$7. One-piece Nationals, \$10. One-piece overhauled, with accessories, \$20.00. Shelby Instrument, 321 W. 7th St., Long Beach, Calif.

TUBES, surplus, bought-sold. Free list. Betz, 73 Columbia Ave., Yonkers, N. Y.

53 OHM Coax, 300 ohm twin, reasonable. Inquire: Harry Van Dick, Little Falls, N. J.

LONG distance TV and FM antennas. Yagi beams, stacks, etc. Wholesale Supply Co., Dept. H, Lunenburg, Mass.

## WANTED

AN/APR-4, other "APR-," "ARR-," "TS-," "IE-," ARC-1, ARC-3, ART-13, everything surplus; Tubes, Manuals, Laboratory equipment. Describe, price in first letter. Littell, Farhills Box 26, Dayton 9, Ohio.

WANTED: The following sets, parts or equipment associated with: BC-611 handie-talkies; ARC-1; ARC-3; ARN-7; BC-342, 312; R-89B/ARN-5; T-47, 47A/ART-13 & dynamotor; F-21/ARA-9 audio filter; RT-7A/APN-1; APN-2; APN-9; BC-348; MG-149; BC-733D; BC-966A; DM-32A; BC-453B; CRT-3; SCR-522; plus all types test equipment. Top Dollar paid. Write: Robert Sanett, 4668 Dockweiler, Los Angeles, Calif.

## CORRESPONDENCE COURSE

USED Correspondence Courses and Books sold and rented. Money back guarantee. Catalog free. (Courses bought.) Lee Mountain, Pisgah, Ala.

RADIO Servicing Course shows latest short cut methods. Lessons easy to follow. Only \$3.00, postpaid in U.S.A. Buyers Syndicate, 30 Taylor St., Springfield, Mass.

## MISCELLANEOUS


SPEAKERS repaired, wholesale prices, guaranteed workmanship. Amprite Speaker Service, 70 Vesey St., New York City 7.

USED correspondence courses and educational books bought, sold, rented; catalog free. Educational Exchange, Summerville, Ga.



**SOUND POWERED PHONES** RCA-MI-2454  
Complete with 24' of Rubber Covered Wire.  
**NEW EXPORT PACKED**  
Shipping weight 6 lbs.  
**\$9.95 per set**  
**2 for \$19.50**  
EACH SET GUARANTEED  
Brand New Gov't. Cost, \$42.00  
INCLUDE POSTAGE WITH ORDER  
**McCONNELL'S**  
3834 Germantown Ave.  
Phila., Pa. RA 5-6033

# RADIO Surplus Buys

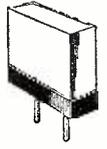


**500 KC CRYSTALS**  
500 KC Crystals in FT 241-A holders with 1/2" pin spc.  
**ONLY LIMITED QUANTITY AVAILABLE**  
**\$1.95 ea.**

## PROMOTE YOUR SALES AND SERVICE

Install Neon in Your Car or Truck  
**BRAND NEW NEON G.E. TRANSFORMER**  
6 Volt DC input; 6000 Volt AC, 10 mills output.  
**BRAND NEW .....ea. \$9.95**  
Above transformer will also operate blacklite in your auto . . . 12" 8 watt Blacklite Tube (with holder).....ea. **\$2.50**

## TUNER FROM NAVY "BN" EQUIPMENT

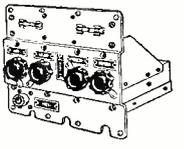

Simply modified into 2-meter converter for car or communications receiver. Uses 1-616, 1-6SH7, 1-9006, 1-6J5 (Not Furnished). Slus is tuned from 157 to 187 Megacycles. Includes schematic diagram for "BN" equipment.  
Now—A New LOW Price.....**\$4.95**

ALL EQUIPMENT F.O.B. PASADENA UNLESS OTHERWISE SPECIFIED. PLEASE ENCLOSE FULL AMOUNT WITH ORDER

## C & H SALES CO.

BOX 356-JT, East Pasadena Station, Pasadena 8, Calif.

See Your Dealer FOR THESE Outstanding Books

- RADIO HANDBOOK
- ANTENNA MANUAL
- BETTER TV RECEPTION
- SURPLUS RADIO CONVERSION MANUAL
- WORLD'S RADIO TUBES
- RADIO-TV QUESTIONS AND ANSWERS

OR WRITE TO:  
Editors and Engineers  
1302 KENWOOD ROAD, SANTA BARBARA, CALIFORNIA

# EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.



**ENDORSED BY THOUSANDS!**  
The Instructograph Code Teacher literally takes the place of an operator instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

## INSTRUCTOGRAPH COMPANY

4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS

Another Outstanding Jobber  
**THE LUKKO SALES CORP.**  
5024 IRVING PARK RD, CHICAGO 41, ILL.  
has all 17 KITS & INSTRUMENTS in stock!  
**EICO**  
415K 5' SCOPE KIT \$44.95 See EICO ad on Page 30

## RADIO & TELEVISION NEWS

# INDEX OF Advertisers

While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.

NAME	PAGE
Acorn Electronics Corp.	140
Airex Radio Corp.	131
Alden Electro Company	139
Allied Radio Corporation	9, 100
Almo Radio Company	149
Alvaradio Supply Co.	156
American Electronics	144
American Television & Radio Co.	16
Amperite Company, Inc.	118
Ampex Electric Corporation	130
Amplifier Corporation of America	144
Arch Electronics Co.	148
Arcee Electronics Co.	148
Arco Electronics, Inc.	122
Argos Products	147
Arrow Sales, Inc.	139
Ashe Radio Co., Walter	24
Atlas Sound Corp.	116
Atlas Tel-Rad Company	90
Barry Electronics	154
Bell Telephone Laboratories, Inc.	14
Belmont Radio Corp.	6
Blonder Tongue Laboratories	137
Bond Equipment Company	141
Boyce-Roche Book Co.	140
Brook Electronics, Inc.	86
Burstein-Applebee Company	104
C & H Sales	154
Candler System Co.	152
Capitol Radio Engineering Institute	29
Channel Master Corporation	12
Chicago Transformer Company	107
Cleveland Institute of Radio Electronics	101, 102
Collins Audio Products	27
Columbia Electronic Sales	106
Comet Electronic Sales Co.	117
Communications Equipment Company	7
Component Supply Company	133
Concord Radio Corporation	85
Coyne Electrical School	113
DeForest's Training Inc.	5
Davis Electronics	134
Dow Radio Inc.	149
DuKane Corp.	114
Dumont Electric Corp.	143
Allen B. Dumont Laboratories	3rd Cover
Editors & Engineers, Ltd.	144, 154
Edlie Electronics, Inc.	96
Eitel-McCullough, Inc.	122
Electronic Expeditors, Inc.	147
Electronic Instrument Co., Inc.	30, 127, 139, 154, 156
Electronic Vision Projection Co.	144
Electronics Institute, Inc.	146
Electro Products Laboratories	152
Electro Sales, Inc.	136
Electro Voice Inc.	111
Empire Electronics	148
Esgee Sales	129
Esvey Manufacturing Company, Inc.	119
Fair Radio Sales	127
Feller Engineering Co.	149
Forest Sales Co., Inc.	114
Franklin Technical Institute	141
G. L. Electronics	143, 152
Gamerman's	150
Garrad Sales	143
Gem Radio & Television Corp.	105
General Electric Company	7
General Electronics Dist. Corp.	104
General Test Equipment	137
Gonsert Company	156
Greenlee Tool Co.	153
Greenwich Sales Company	153
Hallierafters Company, The	81
Harvey Radio Company, Inc.	106
Heath Company	70 thru 77
Henshaw Radio Supply	141
Hiekk Electrical Instrument Co.	78
Hollywood Technical Institute	127
Hytron Radio & Electronics Co.	15
Indiana Technical College	116
Instructograph Co.	154
J.F.D. Manufacturing Company, Inc.	86
J S H Sales Company	148
Jackson Electrical Instrument Co.	97
Jensen Industries, Inc.	150
Jontz Mfg. Co.	148
Kaar Engineering Company	144
Key Electronics Division	130
Knepper Aircraft Service	80
Lafayette Radio Corporation	123
La-Pointe Plasmomold Corporation	108
Leotronic Research Labs.	110
Leotone Radio Corp.	80
Loris Sales	152

# OAK RIDGE CRT TESTER



## "CATHETTE"

is the **ONLY CRT Tester\***

that checks **ALL** the following:

- HIGH VOLTAGE BREAKDOWN
- BEAM CURRENT MEASUREMENT
- ELECTRON GUN CONDUCTANCE
- SHORTS BETWEEN ANY ELEMENTS

Ask to see this **INDISPENSABLE** new tool at your nearest jobber. You'll agree that it's a **MUST** for every TV Serviceman today! MODEL 106 "CATHETTE" CRT Tester, net **\$29<sup>95</sup>**

\* Pat. Applied for.

### Check these additional features:

#### MODEL 108 POWER SUPPLY

(Pocket Size, same as above), used in conjunction with Cathette CRT Tester, permits testing of Picture Tubes in carton! net. **\$19.95**

- Checks gas between elements in Electron Gun
- Checks gas between High Voltage Anode and Electron Gun
- Checks conductance between Cathode, Control Grid, and Screen Grid
- Checks filament continuity
- Checks high voltage on Anode
- Checks Screen to Control Grid voltage from set
- Checks Control Grid to Cathode voltage from set
- Checks leakage
- Tests and positions Ion Trap
- Checks brightness control voltage
- Easy-to-read calibrated DC Voltage scales (0-500V, 0-15KV)
- Easy-to-read tube test scales
- Supplied with duo-decal plug and socket. (Special adaptors available as accessories)
- Pocket size: 5/2 x 3/8 x 2/4". Shpg. wt. 3 lbs.



Send NOW for your copy of our complete new catalog, illustrating and describing the above equipment, as well as all other OAK RIDGE TV Test Instruments.

Cable Address: "UNIONTEX" N. Y.

## OAK RIDGE PRODUCTS

37-01 Vernon Blvd. Long Island City I, N. Y.

Mfg. Division of VIDEO TELEVISION, INC.

OAK RIDGE PRODUCTS, Dept. N  
37-01 Vernon Blvd., Long Island City I, N. Y.

Please send your complete new OAK RIDGE Catalog at once, to:

Name .....

Address .....

City..... State.....

## PHOTOCON SALES

1062 N. Allen Ave. Sycamore 4-7156  
Pasadena 7, Calif. RYan 1-8271

### WRITE FOR OUR LATEST SURPLUS SALES CATALOGUE

WE WILL BUY YOUR NEW OR CLEAN USED ELECTRONIC SURPLUS: ARC-1, ARC-3, BC-224, BC-348, BC-312, BC-342, ATC, ART-13, APS-13, BC-221, LM's, TS-12, TS-13, TS-23, TS-84, TS-35, IE-19A, I-222, SCR-522, TS-100, or any BC, I, IE, TS, APR.

#### WRITE FOR PRICES:

APR4, APR5A, APR7, TS-34, 804CS2, APA-38, BC-348, ART-13, TS-12, APN-9, ARC-1, BC-610, TCS.

DuMont 208 5" Oscilloscope	EXCELLENT	\$225.00
804B General Radio Signal Generator 8-330 mc.	EXCELLENT	350.00
APN-1 Altimeter Indicator 0-1 ma. shunt, 250° dial	NEW	2.95
LM & BC-221 Frequency Meter with cal. book, crystal, and tubes	EXCELLENT	99.50
SCR-625 Mine Detector	NEW	69.50
AN/APN4B Complete	EXCELLENT	150.00
PE-218 Inverter 400N	NEW	29.50
PE-206 Inverter 800N	NEW	12.50
Weston Model 545 Tachometer Meter	NEW	17.50
HS-33 600 ohm Headsets	USED	3.50
400 cycle Inverters—G.E. 5D21N10A Input 24V. DC. Output 115V. AC. 400 cycles 485 V.A.	NEW	24.50
DuMont 241 Oscilloscope	EXCELLENT	300.00
G.E. Oscilloscope CRO5Y	EXCELLENT	225.00

TS-148/UP, Large quantity BC-348's, TS-12, TS-13, TS-100, ID59/APA-11 Indicator. Write for Prices.

Receiver-Indicator R-65/APN9 complete	\$400.00
Drafting Machine single scale 16" Fulcrum less scale. Exc.	35.00
CRT-3 Two-Channel Gibson Girl. NEW	75.00
DuMont 224 Oscilloscope less front cover	125.00
304TL Tubes	6.50
889R Tubes	100.00


NOTE: One of the largest and most complete electronic surplus stocks in the country. We have thousands of tubes, capacitors, plugs, accessories, transmitters-receivers, test equipment, etc. Send us your requirements.

TERMS: Prices F.O.B. Pasadena, California. 25% on all C.O.D. orders. Californians add 3% Sales Tax. Prices subject to change without notice.

# TEVCO
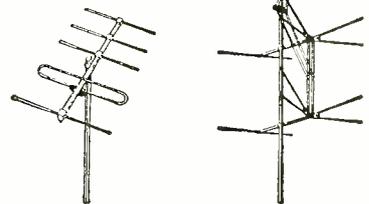
### SINGLE REFLECTOR CONICALS

- 1259—Single Bay 3/8" elements. 3.19
- 1256—Single Bay 1/2" elements. 3.89
- 1254—Double Bay 3/8" elements. 6.68
- 1258—Double Bay 1/2" elements. 7.89
- 1257—Four Bay 3/8" elements. 14.89
- 1253—Four Bay 1/2" elements. 17.19



### FIVE ELEMENT YAGI BEAMS

- 2002 to 2006—any lo channel. 8.69
- 2007 to 2013—any hi channel. 3.19

- 1236—Single Bay Twin-V. 3.76
- 1237—Double Bay Twin-V. 7.49
- 1231—Four Bay Conical. 16.99
- 1230—Double Bay Conical. 7.89
- 1243—Swift Rig Folded Hi Folded Low. 3.89
- 1240—Single section conical—lots of 6. 1.69
- 1244—Swift Rig Folded Hi Straight Low. 3.49
- 2113—Deluxe Indoor Antenna. 1.99
- 1860—Chimney Mount. Dozen Lots 1.19
- 1905—3/2" Mast Snap-On Standoff. Per 100 3.60
- 1873—3/2" Mast Standoff Insulator. Per 100 5.50
- 1872—4" Nail-In Insulator. Lots of 50 .02
- 1870—3/2" Wood Screw-Eye Insulator. Lots of 50 .02
- 1229—Single Bay Conical. 3.75
- 1861—5 Ft. 1/4" Diam. Galv. Steel Mast. .82


Send for quantity prices and complete list

### TELEVISION SUPPLY CO.

Box 13 Greenpoint Station Brooklyn, N. Y.

# 3

New  
Custom-Built  
Deluxe  
TV Chassis

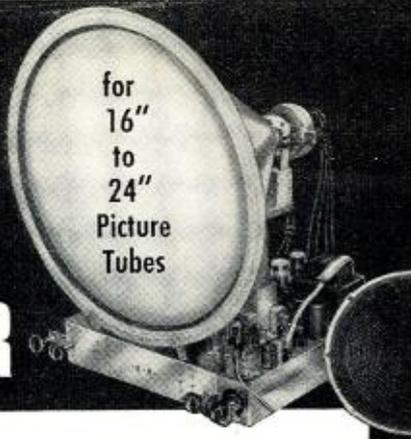

for  
16"  
to  
24"  
Picture  
Tubes

by **TECH-MASTER**

**MODEL 2430**—Designed specifically for all picture tubes requiring from 65 to 70 degrees horizontal deflection, (such as 24AP4, 20CP4, 19AP4, etc.) Supplied with quality PM speaker, and Universal Picture Tube Mounting Brackets & Phono Jack. \$189.50

**MODEL 2431P**—Similar to model 2430, but with Push-Pull Audio, True Fidelity Output and Universal Picture Tube Mounting Brackets. \$199.95

**MODEL 2431C**—Basically same as Model 2430 but with Continuous Tuner, Push-Pull Audio, True Fidelity Output and Universal Picture Tube Mounting Brackets. Allows complete coverage of both TV and F.M. bands. \$199.95

The new **Gold Medal Series** incorporates all the latest Tech-Master features which have made this improved 630 type chassis the standard by which custom-built TV is measured... performance and service are assured because Tech-Master design and construction are as fine as human hands and brains can produce. All chassis are supplied completely wired, aligned and tested with all tubes (less picture tube).

**LOOK** for your Tech-Master registration and guarantee card attached to each chassis... it is your assurance that you are buying a genuine Tech-Master receiver.

See the Gold Medal Series and other quality Tech-Master products at your favorite Radio Parts Jobber or write direct to Tech-Master Products Co. Dept. RN-1, for complete descriptive literature.



**TECH-MASTER PRODUCTS CO.**  
443-445 Broadway • New York 13, N. Y.

McConnell's	150, 154
Meete Radio Company	88, 89
McGraw-Hill Book Co., Inc.	138
McIntosh Engineering Company	104
Mallory & Co., P. R.	4th Cover
Mark Electronics	137
Master Mobile Mounts, Inc.	118
Midwest Radio & Television Corp.	17
Miles Reproducer Company, Inc.	150
Milwaukee School of Engineering	110
Mosley Electronics	131
Moss Electronics	151
National Co., Inc.	133
National Electronics	132
National Radio Institute	83, 84
National Schools	11
Newark Surplus Materials	96
Newcomb Audio Products	140
New England Television Corp.	113
Niagara Radio Supply Corporation	69
Northwestern Vocational Institute	143

Oak Ridge Products Company	155
Offenbach & Reimus Company	109
Olson Radio Warehouse	92, 93

Peak Electronics Company	136
Penn Boiler & Burner Mfg. Company	28
Pfanziehl Chemical Company	113
Photocon Sales	155
Pickering and Company, Inc.	30
Platt Electronics	99
Poly-Tech Company	120
Precise Development Company	122
Precision Electronics, Inc.	124
Premax Products	98
Premier Radio Tube Co.	95
Prentice-Hall, Inc.	128
Progressive Electronics Company	113
Pyramid Electric Company	26

Quam Nichols Company	146
----------------------	-----

RCA Institutes, Inc.	19, 137
R-J Speakers, Inc.	118
Radcom Engineering Co.	135
Radio Corporation of America	23, 2nd Cover
Radio Craftsmen, Inc., The	151
Radio Ham Shack, Inc.	87
Radio-Music Corp.	145
Radio Receptor Co., Inc.	119
Raytheon Manufacturing Company	140
Rek-O-Kut Co., Inc.	98
Relay Sales	22
Rider, Publishers Inc., John F.	115
Rinehart Books, Inc.	120, 126, 142
Rogers-Phillips Research Labs.	141
Rose Company, The	135

Sams & Company, Howard W.	112, 134
Simpson Electric Co.	94
Snyder Manufacturing Company	82
Spellman Television Co., Inc.	114
Sprague Products Co.	18
Sprayberry Academy of Radio	25
Stan Burn Radio & Electronics	126
Standard Surplus	121
Standard Transformer	141
Standard Wood Products Corp.	136
Star Electronic Distr., Inc.	86
Steve-El Electronics	135
Streamlined Self Study Courses	123
Stuart Sales	124
Sun Radio of Washington, D. C.	116
Supreme Publications	152
Sylvania Electric Products	20, 21

Tab	157, 158
Tallen Company	134
Tech-Master Products Co.	156
Television Communications Institute	153
Television Supply Company	155
Transcriber Company	152
Transvision, Inc.	91
Triad Transformer Mfg. Co.	124
Trio Manufacturing Co.	3
Triplet Electrical Instrument Co.	13
Tri-State College	140

Ungar Electric Tools Company, Inc.	119
United Catalogue Publishers, Inc.	147
University Loudspeakers, Inc.	98

V & H Radio & Electronics	108
Valparaiso Technical Institute	139
Weller Electric Company	8
West Region Electronics	135
Western Electronics Co.	148
Wholesale Radio Parts, Inc.	146
Workshop Associates, Inc.	103
World Radio Laboratories, Inc.	145

YMCA Trade & Technical School	135
-------------------------------	-----

Another Outstanding Jobber  
**LIFETIME ELECTRONICS**  
1501 ADAMS STREET • TOLEDO, OHIO  
has all 17 KITS & INSTRUMENTS in stock!  
**EICO**  
221K VTVM KIT \$23.95 See EICO ad on Page 30

## WE PAY CASH!

**GET TOP DOLLARS**

for your spare

**PARTS & EQUIPMENT**

We Especially Need all types AIR-CRAFT, RADIO and TEST EQUIPMENT and component parts.

**HAVE YOU THESE ITEMS?**

- ARC-1      • Any TS, I or IE EQUIP.
- ARC-3
- R5A/ARN7
- BC-348
- ALL TYPES AIRCRAFT INSTRUMENTS
- ART-13
- TS-34

Send us a complete list of your equipment, its present condition and your asking price. We'll shoot back a prompt reply and help you convert your equipment to real ready cash in a jiffy! No red tape!

**ALVARADIO SUPPLY CO.**

Dept. A-20, 341 S. Vermont  
Los Angeles 5, Cal.  
DUnkirk 8-2211

*The Original!*  
**LOW LOSS OPEN WIRE LINE**  
(lowest loss lead-line mfd.)

**"GONSET LINE"**

- 1/2 THE LOSS OF NEW MOLDED RIBBON
- 0.5 DB LOSS PER 100 FT. AT 200 M.C.
- POLYSTYRENE SPACERS

*Ideal for*

- TELEVISION
- AMATEUR
- COMMERCIAL
- FRINGE AREAS
- LONG RUNS
- BEACH AREAS

send for latest bulletin

**GONSET CO., BURBANK, CALIF.**  
72 E. TUJUNGA AVE.



