

CALDWELL-CLEMENTS'

Formerly
TELEVISION RETAILING

TECHNICIAN

TELEVISION • ELECTRONIC • RADIO • AUDIO • SERVICE

November • 1953



In This Issue: Tracking Down TVI
Vertical Circuit Problems • Color TV
Servicing Phono Motors • CIRCUIT DIGESTS


NO. 1 CHOICE

of **ALL** Fixed Composition Resistors by almost

3 to 1*

**Not Claims! Not Predictions! But Plain Facts!
Unbiased, authoritative, independent surveys (made
regularly since 1930) show IRC BT RESISTORS to
be the Service Technicians' choice by a continually
increasing margin. Today, BT RESISTORS are
preferred over the total of all other brands combined!*

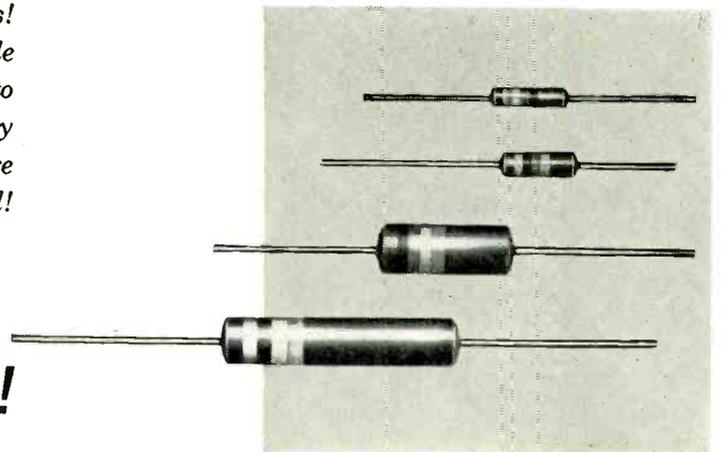**Ask for IRC BT's...
Most Service Technicians Do!**



INTERNATIONAL RESISTANCE COMPANY

425 N. Broad Street, Philadelphia 8, Pa.

Wherever the Circuit Says ~~~

In Canada: International Resistance Co., Ltd., Toronto, Licensee

TECHNICIAN*

(Formerly the TECHNICIAN SECTION of "TELEVISION RETAILING")

TELEVISION • ELECTRONIC • RADIO • AUDIO • SERVICE

M. CLEMENTS O. H. CALDWELL
Publisher Editorial Director
 SOL HELLER, *Managing Editor*
 SIDNEY C. SILVER, *Associate Editor*
 A. P. MASSON, *Associate Editor*
 ANN O'ROURKE, *Assistant Editor*
 J. L. STOUTENBURGH, *Consulting Editor*
 CHARLES F. DREYER, *Art Director*
 ELMER KETTERER, *Circuit-Digest Production*
 GEORGE PUGLICI, *Circuit Diagrams*

BUSINESS DEPARTMENT

M. H. NEWTON, *Business Manager*
 H. A. REED, *General Sales Manager*
 HAROLD PRINCE, *Sales Promotion Mgr.*
 DIXON SCOTT, *District Manager*
 LEE GRAVES, *District Manager*
 CHARLES S. ROEVER, *District Manager*
 N. McALLISTER, *Asst. Business Manager*
 MARTHA USDIN, *Production Manager*
 KATHLEEN CAFARO, *Reader Service*
 480 Lexington Ave., New York 17, N. Y.
 Telephone Plaza 9-7880
 S. M. GASKINS, *Western Manager*
 JOHN D. LUPTON, *District Manager*
 201 N. Wells St., Chicago 6, Ill.
 Telephone RAndolph 6-9225
 CHRIS DUNKLE & ASSOCIATES
California Representative
 3257 W. 6th Street, Los Angeles 5, Calif.
 Telephone DUnkirk 7-6149
 1355 Market Street, San Francisco
 Telephone KLondike 2-2311, Ext. 579
 WARREN S. BROWN, *Circulation Manager*
 M. GROENING, *Asst. Circulation Manager*
 JOHN J. BORCHI, *Controller*
 W. W. SWIGERT, *Credit Manager*

CIRCULATION

This issue: 44,000. Guaranteed circulation
 by January 1954:

50,000

—serving the industry's largest group of
 service technicians, service managers and
 installation specialists.

TECHNICIAN, November 1953, Vol. 58, No. 5.
 50 cents a copy. Published monthly by Caldwell-
 Clements, Inc., Publication Office, Emmett St.,
 Bristol, Conn. Editorial, Advertising and Ex-
 ecutive Offices, 480 Lexington Ave., New York
 17, N. Y. Application for acceptance as second-
 class matter pending at Bristol, Conn. M.
 Clements, President; Orestes H. Caldwell, Treas-
 urer. Subscription rates: United States and Can-
 ada, \$4.00 for one year; \$6.00 for two years;
 \$8.00 for three years. Pan-American and Foreign
 countries: \$7.00 for one year; \$10.00 for two
 years; \$14.00 for three years. Printed in U.S.A.

Copyright by
 Caldwell-Clements, Inc., 1953

NOVEMBER, 1953

Front Cover—"What Next?"

| | |
|--|-----------------------|
| Free Tube Checking—Good Business or Bad? | 25 |
| "Tuning in the Picture" | 26 |
| Tracking Down TVI to Its Source | James A. McRoberts 28 |
| Preventing Tube Damage | John H. Wyman 31 |
| Television Antenna Mounting Problems | Philip Thier 32 |
| Troubleshooting Vertical Deflection Circuits | M. M. Gershuny 34 |
| Vertical Circuit Troubles | 37 |
| Color vs Black & White TV Receivers | Peter W. Orne 38 |
| Servicing Phono Motors and Drive Assemblies | Harry Mileaf 42 |
| Shop on Wheels Pays Off in Sunny Florida | Carroll B. Shaw 44 |
| Color-TV Progress Report | 45 |
| New Audio Gear | 46 |
| Antennas and Accessories | 47 |
| Is Your Number in the Book? | 48 |
| Shop Equipment and Instruments | 52 |
| "Tough Dog" Corner | 54 |
| Circuit Digest Cumulative Index | 69 |

*CIRCUIT DIGESTS (See page 73 and the following sheets)

ARVIN: Chassis TE 359
 CBS-COLUMBIA: Chassis 750-3
 CROSLY: Chassis 411, 411-1
 SYLVANIA: Chassis 1-518-1, -2, -3
 TRUETONE: Chassis 21T2A
 WESTINGHOUSE: Chassis V-2243-1

DEPARTMENTS

| | | | |
|---------------------------------|--------|--|----|
| Letters to the Editors | 12 | News of the Trade | 56 |
| Shop Hints | 50 | Service Ass'n. Reports | 60 |
| New Products | 52, 58 | News of the Reps | 63 |
| Calendar of Coming Events | 56 | Manufacturers' Catalogs & Bulletins .. | 67 |

CALDWELL-CLEMENTS, Inc.


Publication Office, Bristol, Conn.

Editorial/Business Offices 480 Lexington Ave., New York 17, N. Y., Tel. Plaza 9-7880
 Publishers also of MART and TELE-TECH & ELECTRONIC INDUSTRIES


*Reg. U. S. Patent Office

FALCON


Introduces -

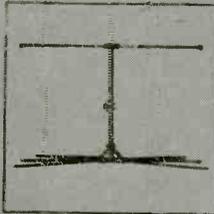


Channels 2-13, peaked for low channels (2 thru 6)

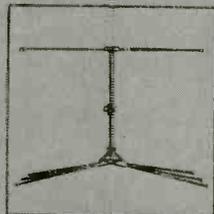


Channels 2-13, normal position, peaked for all VHF channels (2 thru 13)

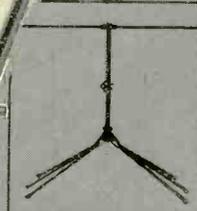

Channels 2-13, peaked for high channels (7 thru 13)

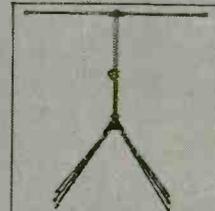

Channels 2-83, peaked for UHF channels

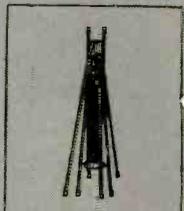

Falcon "VARI-CON" folded for packing

Model VC-1



Model VC-2



Model VC-4

Stack them for added gain.

FALCON

easiest of all antennas to assemble merely open like an umbrella and tighten wing nuts


There is **NO ASSEMBLY** problem with a FALCON "VARI-CON". It takes longer to explain the operation than to accomplish it! Your FALCON "VARI-CON" comes folded into one compact unit. You need only swing the reflector into position and tighten the wing nuts. Move the sliding sleeve to the calibrated channel setting you desire and tighten. The butterfly springs snap the elements into position and lock them securely. The FALCON "VARI-CON" is ready to install, ready to provide peak performance. *Changing the channel peaking of the "VARI-CON" is just as simple and easy as making the original setting. No tools are needed for either operation.*

THE HEART OF THE "VARI-CON"

Above is a view of the new mechanism which enables anyone to adjust the peaking of the FALCON "VARI-CON" to any range of channels desired. The sliding sleeve, on the calibrated boom, automatically fans out the elements to their correct position.

A simple, trouble-proof, snap-action spring in the

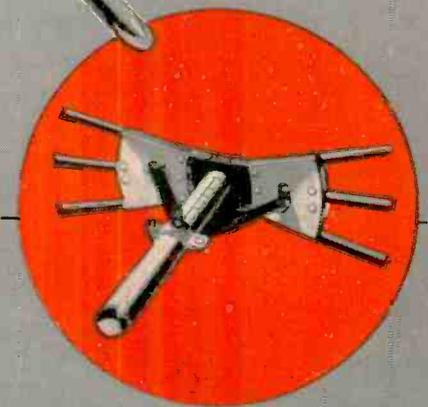butterfly keeps the elements solidly in place. The insulated hinge assembly is extremely strong, durable and weather-resistant and has an extra long leakage path. Weight has been kept to a minimum, strength at a maximum in order to assure long life and freedom from wind and weather damage. A heavily plated mast clamp is supplied.



Calibrated sleeve for quick peaking of antenna.

the "VARI-CON"

(The conical that's variable)

Provides all Channel Performance...

Yet can be Peaked for Increased Gain on any Channel Range

The FALCON "VARI-CON" was designed for today, tomorrow and years to come. Its unusual construction permits setting the "VARI-CON" for all-channel performance peaked to provide the additional gain needed on special channels. In addition, the variable patterns obtainable are of great value in ghost elimination.

There is no guess work; no tedious assembly; no field strength equipment needed to peak the "VARI-CON" for high-gain, sharp pattern performance in your area. It's as simple and easy as opening an umbrella. Here's all you do: Unpack the "VARI-CON"—Slide the adjusting sleeve to the calibrated marking on the boom for the best reception of channels in your area—Fan out the reflector elements—Tighten the locking wing nuts. The "VARI-CON" is

automatically peaked WHERE YOU WANT IT and ready to install. It is the only conical that enables you to provide a custom-made installation resulting in higher gain and increased customer satisfaction.

The NEW FALCON "VARI-CON" is ruggedly constructed. Heavy-duty heads will not crack or break. The steel spring snap-action butterfly assemblies are unbreakable. Full length, 48 inch, elements are used. One of the most capable engineering staffs in the industry has worked out every last detail of this truly remarkable TV antenna. To the high gain all-channel performance and excellent line match of the conical, FALCON engineers have added the "plus" feature—adjustable, calibrated channel range peaking!

FALCON

The new "VARI-CON" is one of the most significant additions to antenna design. Watch for the other new FALCON antennas which will be announced in the near future! Each will represent the most advanced, most efficient antenna design of its type.

WRITE FOR ILLUSTRATED FOLDER AND PRICES



FALCON ELECTRONICS COMPANY • 2003 CEDAR ST. • QUINCY, ILLINOIS



NATIONAL ADVERTISING TO BACK NEW FALCON "VARI-CON"


To stimulate sales on all levels, FALCON is conducting one of the most aggressive advertising campaigns in the industry. Full two-page color spreads are appearing regularly in many of the nation's top trade and consumer publications.

WE'LL TELL THE WORLD!

ONLY *Regency*
HAS **5** WAY
CONVERSION!

We'll tell them not to take chances with 2-way Conversion... that the Regency Quintuplet Converter, unlike *all* others, is designed to utilize any of 5 VHF channels in converting to UHF; other converters work only on 2 channels. Insure your customers against image interference, obsolescence! Sell them REGENCY'S Quintuplet Converter! ... and at \$49.95 list, there's greater profit for you!

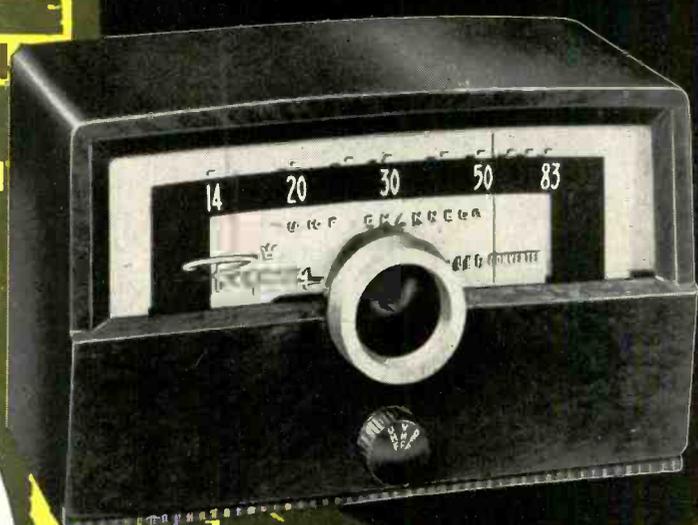
Yes, you'd better be ready for a big turnover this fall, because REGENCY'S promotional program is directing more traffic than ever *your* way!



Makers of VHF Boosters, FM Boosters, UHF Converters, Professional High Fidelity Equipment and Remote Control for Television.

Regency DIVISION OF I. D. E. A. INC.

Burton Browne Advertising

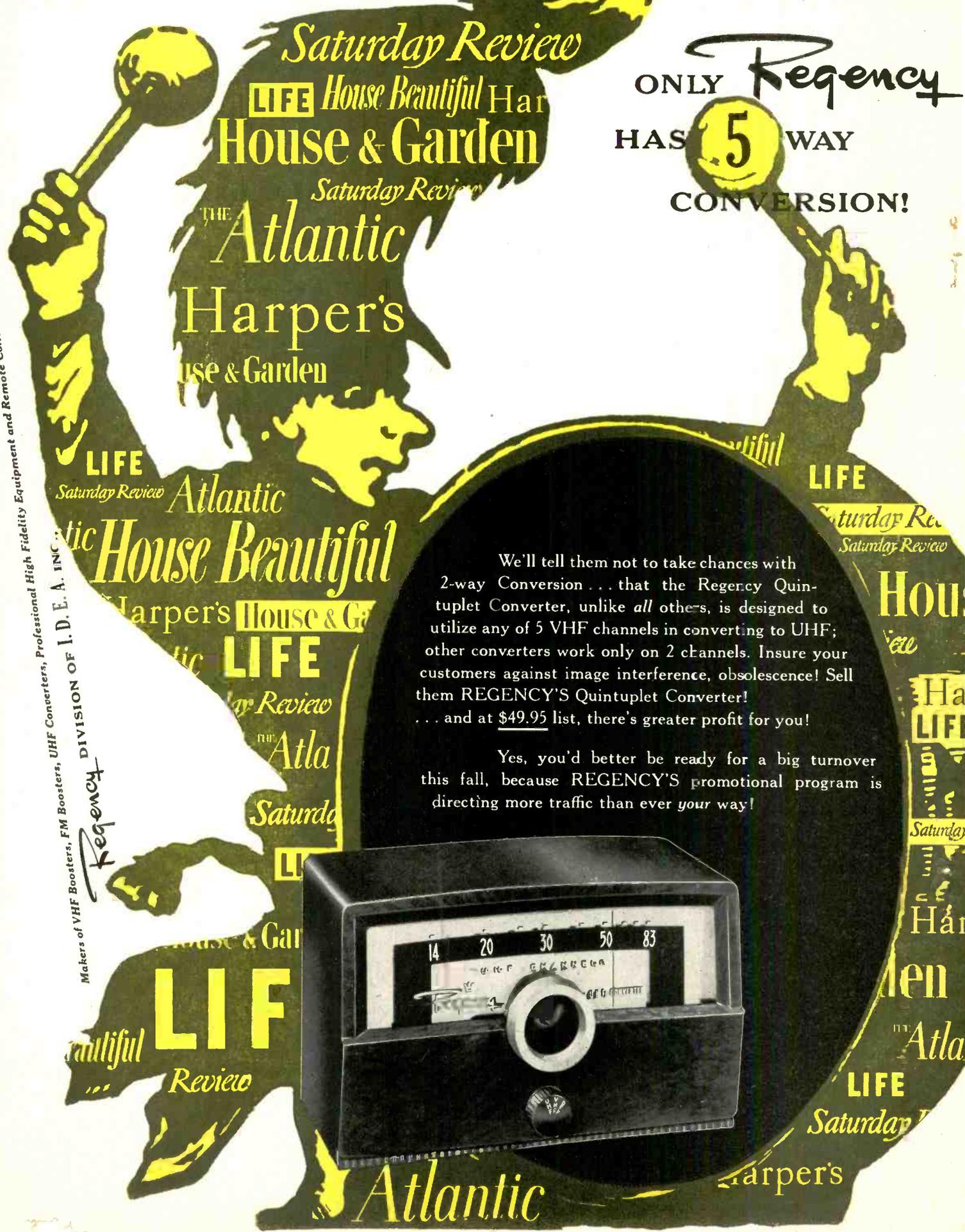

EVERYTHING IN

TV


ANTENNAS AND
ACCESSORIES

Now available from Your

Admiral DISTRIBUTOR

Admiral is first with the best and the mostest! Your Admiral distributor now carries the most complete and up-to-the-minute line of TV antennas and accessories. See him for high-gain UHF antennas of the most advanced design . . . rotators . . . all-weather transmission line . . . mast and tower equipment for every type of installation.

For your convenience every item is fully described and priced in the Admiral Catalog. Just a letter or phone call gets you everything needed, down to the last screw-eye and insulator, to make the most suitable antenna installation under all conditions. No need to waste time shopping around. Quick, close-to-home service. Admiral prices are lowest. And every item conforms to Admiral's high quality standards. Order your needs from your Admiral distributor.

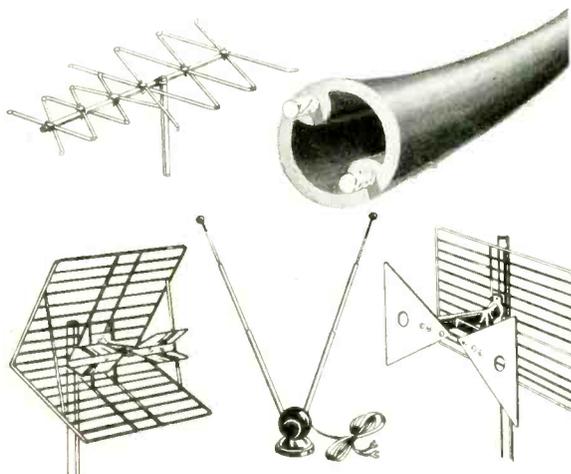


FREE! GET THIS
CATALOG FROM
YOUR *Admiral* DISTRIBUTOR

Admiral Corporation

Accessories and Equipment Division, Chicago 47, Illinois

TRIO

proudly announces

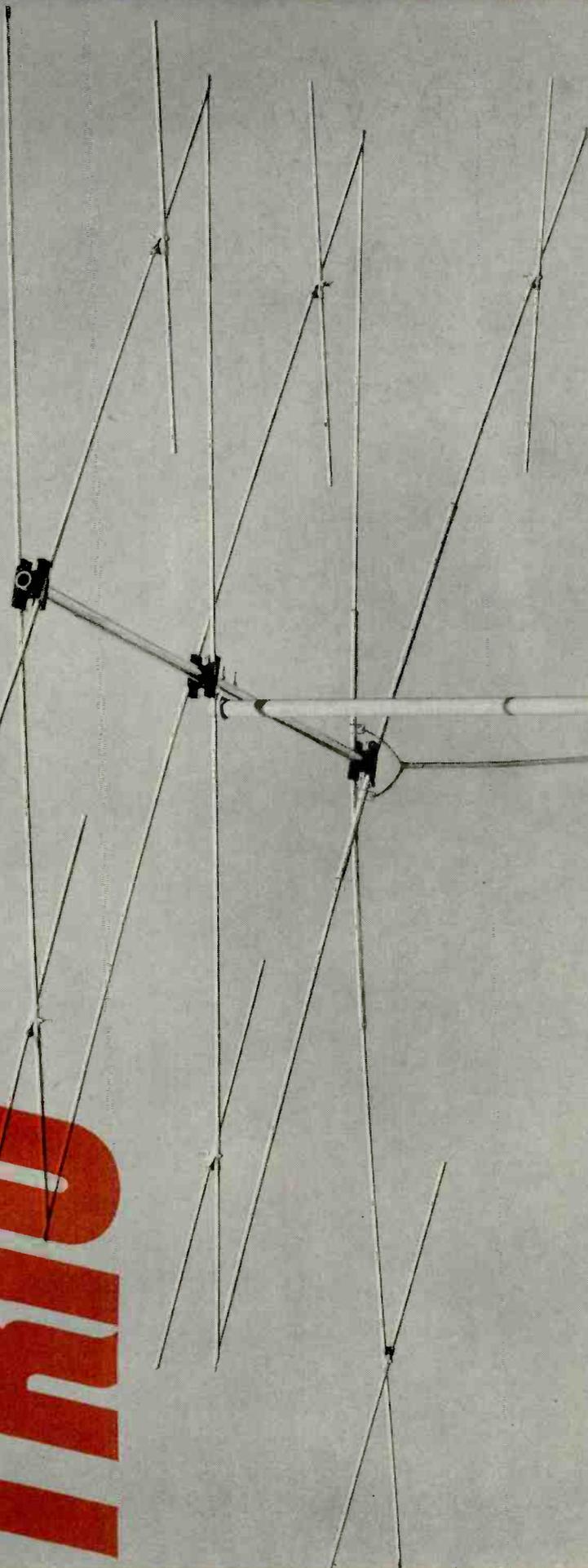

The New ZIG-ZAG

"TWIN-SIX"


(A significant addition to the Zig-Zag line)

... the greatest advance ever made in **ALL-CHANNEL** antenna design!


Not content to bring out just another all-channel antenna, TRIO studied and tested every other model available. Months of research produced the "Twin-Six", a Zig-Zag that provides all of the desirable features indicated above. Quantitative ratings for antennas are practically meaningless because of some exaggerated claims. For this reason, the "Twin-Six" is announced without the usual gain charts. The new "Twin-Six", however, equals and, in most cases, greatly exceeds the gains of these antennas on every channel. For instance, the "Twin-Six" showed a 2 to 6 db higher gain than a competitive antenna which is advertised as having a 12 db gain.

MINUTE-UP ASSEMBLY

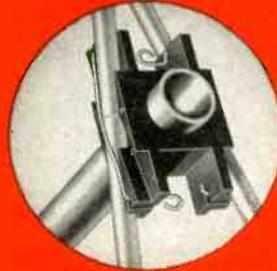There's no antenna easier to assemble. Shipped with all hardware mounted on the boom. Complete assembly consists of matching elements to color coded insulators and snapping on spring clips. Improper assembly impossible.



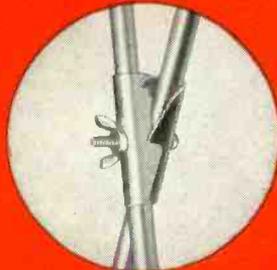Insulators come mounted on boom and are so designed that "shorting-out" is impossible. Antenna elements mounted merely by snapping on the spring clips.



Pre-assembled high channel elements are swung into position and quickly locked by mating brackets.

NEW ZIG-ZAG "TWIN-SIX" OFFERS:

Measurable Higher Gain On All VHF Channels Than Any Other Single Bay All-Channel Antenna

PLUS

1. One Horizontal Bay Does It All!
2. Single Lead-In Operation!
3. Easy-Up, One Minute Assembly!
4. Rugged Construction Throughout — No Droop, No Sag! Light Weight — Attractive Appearance!
5. UHF Reception For All Primary Areas!
6. Low Standing Wave Ratio!
7. Built and Backed by TRIO — A Name You Can Trust!
8. Competitively Priced!



TRIO

MANUFACTURING CO. GRIGGSVILLE, ILL.



Team the new Zig-Zag "Twin-Six" with the dependable TRIO rotator for the maximum in TV enjoyment!



CHANNEL MASTER

introduces a

basically *new type*
of VHF antenna

the **CHAMPION***

the highest gain
all-channel VHF antenna
ever developed!

Featuring the unique new "Tri-Pole"

TRIPLE-POWERED DIPOLE

The "Tri-Pole" is a new antenna system in which the Low Band folded dipole also functions as three folded dipoles tied together in phase on the High Band. This is the heart of the Champion, the secret of its phenomenal performance on all 12 VHF channels.

the **CHAMPION** is the most sensitive all-channel VHF antenna ever designed!

Stacked **CHAMPION** provides:
11-13 D B High Band gain
6½-7½ D B Low Band gain

Here is a totally NEW kind of antenna, completely different — in principal and performance — from any VHF antenna you've ever seen! Since the lifting of the TV freeze means a gradual disappearance of the single-channel VHF area, the VHF antenna of the future will be a *multi-channel* antenna. Prepare now for outstanding reception on *all* VHF channels — present and future — with Channel Master's super-sensitive **CHAMPION**! Outperforms every all-channel VHF antenna made today — and many Yagis, too!


COMPARE these features with the antenna you are now using:

- Folded dipoles throughout — give close to 300 ohms impedance across the entire band.
- Screen-type reflector provides high uniform gain on every channel, 2 through 13. *Not* frequency sensitive — this reflector provides more than twice as much extra gain as straight bar reflectors.
- Phase-correcting harness is built-in and fully assembled; the only wiring you do is to attach the lead-in.
- All-aluminum construction . . . lightweight, durable, non-corrosive.

MARVEL OF PRE-ASSEMBLY

assembles faster than a
5-element yagi!

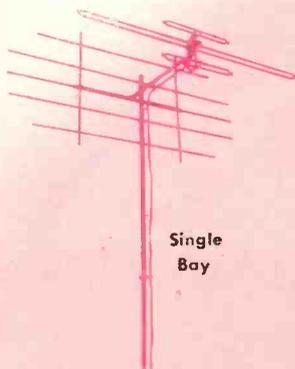Collapsed "Pop-Up" screen opens instantly — no loose rods, elements or hardware. "Tri-Pole" assembly features automatic Spring Lock Action — all dipoles snap permanently into place without wing nuts or any other hardware.




Single
Bay

It's a **CHAMPION** in any area!

- 1-bay—local areas
- 2-bay—secondary and fringe areas
- 4-bay—super-fringe areas


Copyright 1953, Channel Master Corporation

THIS ANTENNA...

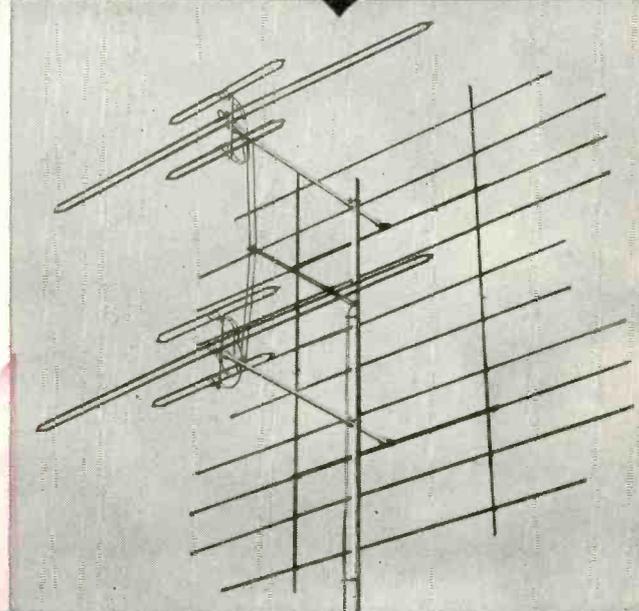


OUT-PERFORMS:


this ...

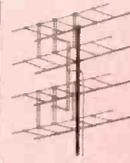


this ...

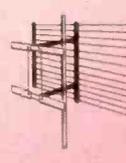

this ...



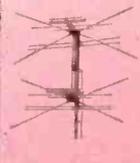


or this ...

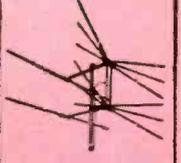

The 2-Bay **CHAMPION** actually
gives you the performance of:

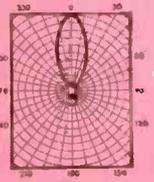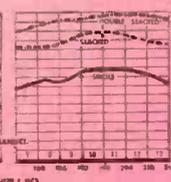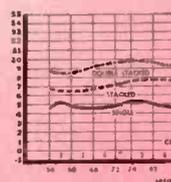- Separate 5-element Yagis for every Low Band channel!
- Separate 10-element Yagis for every High Band channel!



channel
10

| Model No. | | List Price |
|---------------------------|---------------|------------|
| 325 | Single Bay | \$20.83 |
| 325-2 | 2-Bay | \$42.36 |
| 325-4 | 4-Bay | \$83.89 |
| Separate Stacking Harness | | |
| 325-3 | 2-Bay Harness | \$ 2.08 |
| 325-5 | 4-Bay Harness | \$ 4.15 |


Send for complete technical literature.

CHANNEL MASTER CORP.

GREENVILLE, S. C.



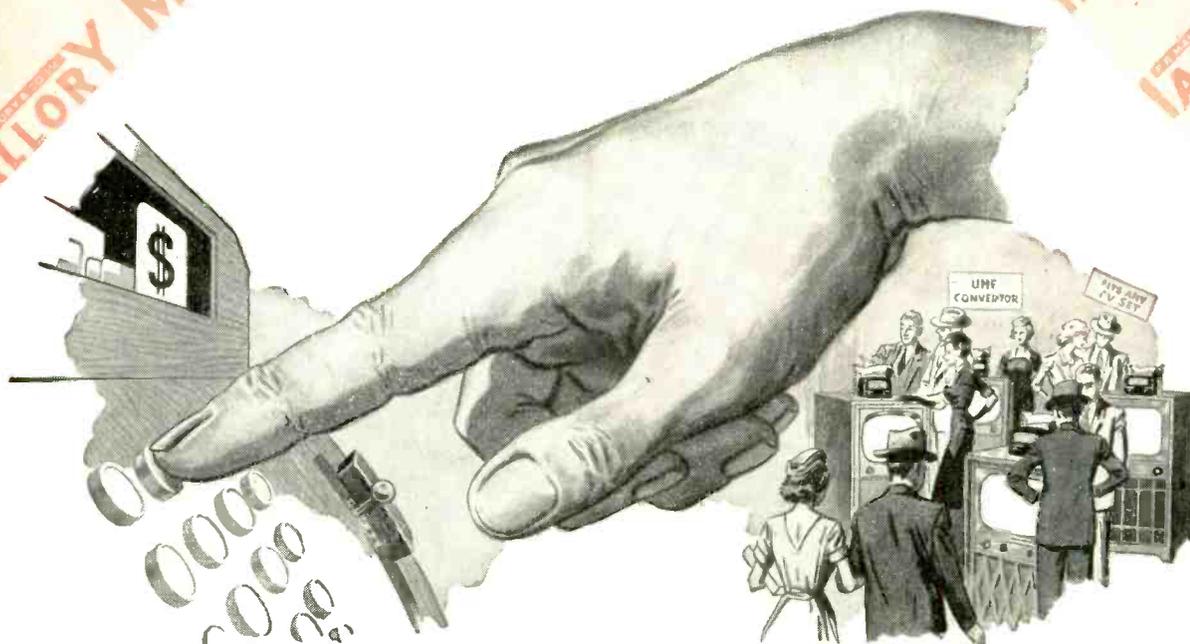Depend on Mallory
for
Approved Precision Quality




The MALLORY CONVERTER

Can Be Your Best Profit Maker in the New UHF Market

When UHF goes on the air in your area, thousands of sets will need converting. The Mallory UHF Converter can become your fastest moving item almost overnight. Be sure you are ready to take advantage of the opportunity... get your full share of the market.

- The Mallory Converter adds *all* UHF channels to any TV set without sacrificing reception of a single VHF channel.
- The Mallory Converter has outsold all other makes in every area where UHF is already on the air.
- A preselector in the Mallory Converter protects against image interference, interference at the IF frequency and oscillator radiation. It insures better selectivity.
- The attractive deep maroon plastic cabinet is smaller than most portable radios.
- The customer has nothing more to buy, no adjustments to make... even if he moves to another broadcast area.

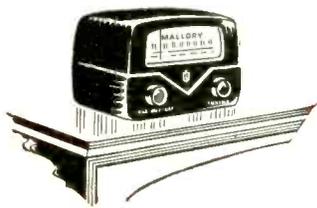

YOUR MALLORY DISTRIBUTOR has complete details on the Converter. It has been an outstanding profit maker in other areas. It can be for you.

Installation is easy too. Simply connect the antenna leads and power lines from the Converter to the set... right in the customer's home.

P. R. MALLORY & CO. INC.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA



5881

6AX4
GT



**TUNG-SOL DESIGNED
AND DEVELOPED**

6U8



**ACCEPTED
BY THE ELECTRONICS INDUSTRY**

You may have detailed information on these and other types upon request.
TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers,
Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.
TUNG-SOL ELECTRIC INC., Newark 4, New Jersey
Sales Offices: Atlanta, Chicago, Columbus, Culver City (Los Angeles), Dallas, Denver, Detroit, Newark, Seattle



6AU4
GT

5687



LETTERS

To the Editors

BBB Headaches

EDITORS, TECHNICIAN:

A day never passes without some customer blasting me for "robbing" him, and I'm sick and tired trying to explain my bills. The same goes for every other service man here.

Only the manufacturers, with big advertising budgets behind them, can tell set-owners the facts. But why do only a handful of them help us? While they're at it, the manufacturers should also educate the Better Business Bureaus. Every week I get some BBB man in my shop giving me a hard time about some customer who has "reported" me for overcharging! The BBB man knows no more about repairing a TV set than the customer, and yet *he* tells *me* to watch my step!

Why should the little guy take such an unfair beating?
Ohio

L.K.

Chock-full

EDITORS, TECHNICIAN:

" . . . May I congratulate you on your first issue of TECHNICIAN and laud you for your continuation of the "Circuit Digests", which all of our members feel are one of the best additions to a serviceman's library, and fulfill a great need. If all other issues are as chock-full of knowledge as the first, you will never have to worry about subscriptions."

H. F. MACFARLAND
Executive Secretary

Long Island Electronic
Technicians Association
Williston Park, N. Y.

Agreement On Charges

EDITORS, TECHNICIAN:

I wish there was industry-wide agreement on fair service charges for at least the most common jobs such as is done in the automobile business. The next step would be for the entire industry to get out some literature to educate the public to the cost of equipment and training, as well as all the other business costs of the electronic service technician.

Connecticut

F.F.

Poor Business Men

EDITORS, TECHNICIAN:

It's your own fault, fellows! The fact is that electronic technicians are such poor businessmen that they allow so-called wholesale parts houses to sell to anyone who walks in the door; some even advertise wholesale prices in the classified newspaper columns.

8106 Liberty Ave.
Parma 29, Ohio

ELMER FISCHER



the **W W** CLIPPER VHF all channel antenna

Not Just Claims But Unquestioned
Proof Of

- **PERFORMANCE** — an engineering accomplishment providing an outstanding antenna designed for increased sensitivity and higher gain in both primary and fringe areas.
- **ACCEPTANCE** — a phenomenal customer acceptance resulting from WW's superb performance characteristics — thousands in use throughout the U.S.
- **SALES** — performance, design, workmanship . . . outstanding selling points to create unprecedented sales demand. Get your share now!

Specifically engineered and designed for true and complete all-channel VHF reception.



CHECK THESE FEATURES

High Uniform Gain — One Major Forward Lobe — Narrow Beam Reduces Ghosts and Noise Pickup — High Signal to Noise Ratio — Good Front-to-Back Ratio Eliminates Co-Channel Interference — Perfect 300 Ohm Match — Light, Rigid, Quickly and Easily Installed to All Heights — Low Wind Resistance.

ALSO MANUFACTURERS OF

Models 10 and 20 UHF Fans — Models 30 & 40 Colinear Fans — Model UH 6 element UHF Yagi — Model HT High Band VHF Antenna — K series Original Hairpin, Combination Yagi Antenna.

Performance charts for the W-W Clipper

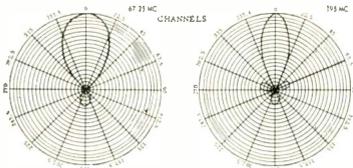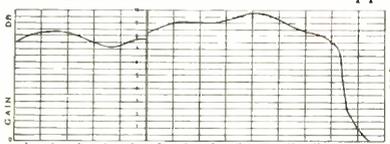

Wells and Winegard
television accessory mfgs.
DEPT. T BURLINGTON, IOWA

Says Licensing Is the Bunk

EDITORS, TECHNICIAN:

Before I'll let anybody "brand" me with a license, I'll sell my tools and close the front door! My dictionary defines licensing as *permission given by law to do something*. Thus, the implication that to do something *without* a license is illegal!

Things are bad enough in the TV repair business without adding more fuel to the fire. No, sir—there won't be any dog tag around my neck!
Newark, N. J. Burned Up

He's FOR Licensing

EDITORS, TECHNICIAN:

This may sound crazy, coming from a repair man, but I think a uniform license system should be made a 48-state law! If one could be effectively passed, it would weed out the crooks, amateurs and poorly trained, leaving only those men who could be trusted by the public.

By tests given once or twice a year, I think this could be done. I don't know how they could test a man's honesty, but there should be a way. Any step along these lines would help the men (including myself) who are both competent and honest.
New York City "Jimmy"

His Men "Steal" the Show!

EDITORS, TECHNICIAN:

The biggest headache in my shop (and in others, I'm sure) comes from the "extra curricular activities" of some of my men. It's bad enough knowing they "wildcat" after store hours (and at cut-prices) but they use MY PARTS to do it!

My city is fairly big, so it's not a matter of simply firing the culprits. They are the best men available—and they know it! I pay better than average wages for this area, and even give the men every Wednesday afternoon off. Still the chiseling goes on.

Can any of your readers give me a solution? Frankly, I'm just about licked, otherwise.
New York State O.P.G.

Give 'Em 'Facts of Life'

EDITORS, TECHNICIAN:

When is something going to be done about educating the public to the facts of TV life? I mean about understanding why we charge for our labor as well as for parts?
Pennsylvania C.K.

"Terrific!"

EDITORS, TECHNICIAN:

I have just received the new September TECHNICIAN. May I congratulate you and your staff on a very fine achievement. This issue is "terrific". It has everything the service technician wants in a magazine.

7 St. James Place SIDNEY KEITZ
New York 30, N. Y.

**INTERNATIONAL
RECTIFIER
CORPORATION**

EL SEGUNDO
CALIFORNIA

DIRECT
REPLACEMENT

RADIO Selenium TV Rectifiers

UNIVERSAL
MOUNTING

WIDER
RANGE

Write for
Bulletin JRP-1

**INTERNATIONAL RECTIFIER
CORPORATION**

1521 E. Grand Ave., El Segundo, Calif • Phone: ORegon 8-6281
CHICAGO: 205 W. Wacker Drive • Phone: Franklin 2-3889
NEW YORK: 501 Madison Avenue • Phone: Plaza 5-8665

HICKOK

MODEL 605A



Large
5"
Meter

TECHNICAL DESCRIPTION

Enthusiastically accepted everywhere, this fine instrument is specifically designed to meet the technician's need for a smaller size, lower cost portable tube and set tester. The 605A is built with HICKOK Dynamic Mutual Conductance circuits with a 3-range micromho scale of 0-3000, 6000, 15,000. Tests all tubes normally encountered in all phases of communications and electronics. Provides the HICKOK Tube Gas Test. New bias fuse prevents accidental damage to bias potentiometer. Operating voltages, including DC grid bias, are applied to the control grid and large 5" meter shows AC component in plate current. This HICKOK test is the same test used by tube manufacturers in their own laboratories.

See your nearest parts jobber and ask for a demonstration of this lighter, smaller, handier Tube & Set Tester. (Also available as Model 600A without multimeter.)

THE HICKOK ELECTRICAL INSTRUMENT CO.

10523 DUPONT AVENUE • CLEVELAND 8, OHIO

Complete TUBE TESTER AND SET ANALYZER

INCLUDES: High Sensitivity MULTIMETER

The Model 605A, in addition to being a complete and highly accurate tube tester, also contains a handy 20,000 ohm per volt DC multimeter to measure . . .

Volts: AC-DC; 0-10, 100, 500, 1000

Sensitivity: 20,000 ohms per volt DC; 1,000 ohms per volt AC

Resistance: 0.1 ohm to 100 megohms, (center scale 25, 2500, 500,000 ohms)


Inductance: to 70 henries through use of conversion chart furnished

Capacitance: Microfarads; 50, 5, as low as .0001

Current: DC; 10, 100, 500 M.A.

Built with minimum number of jacks. Ranges are selected with a rotary master switch.

ONLY FOR THOSE WHO WANT THE BEST

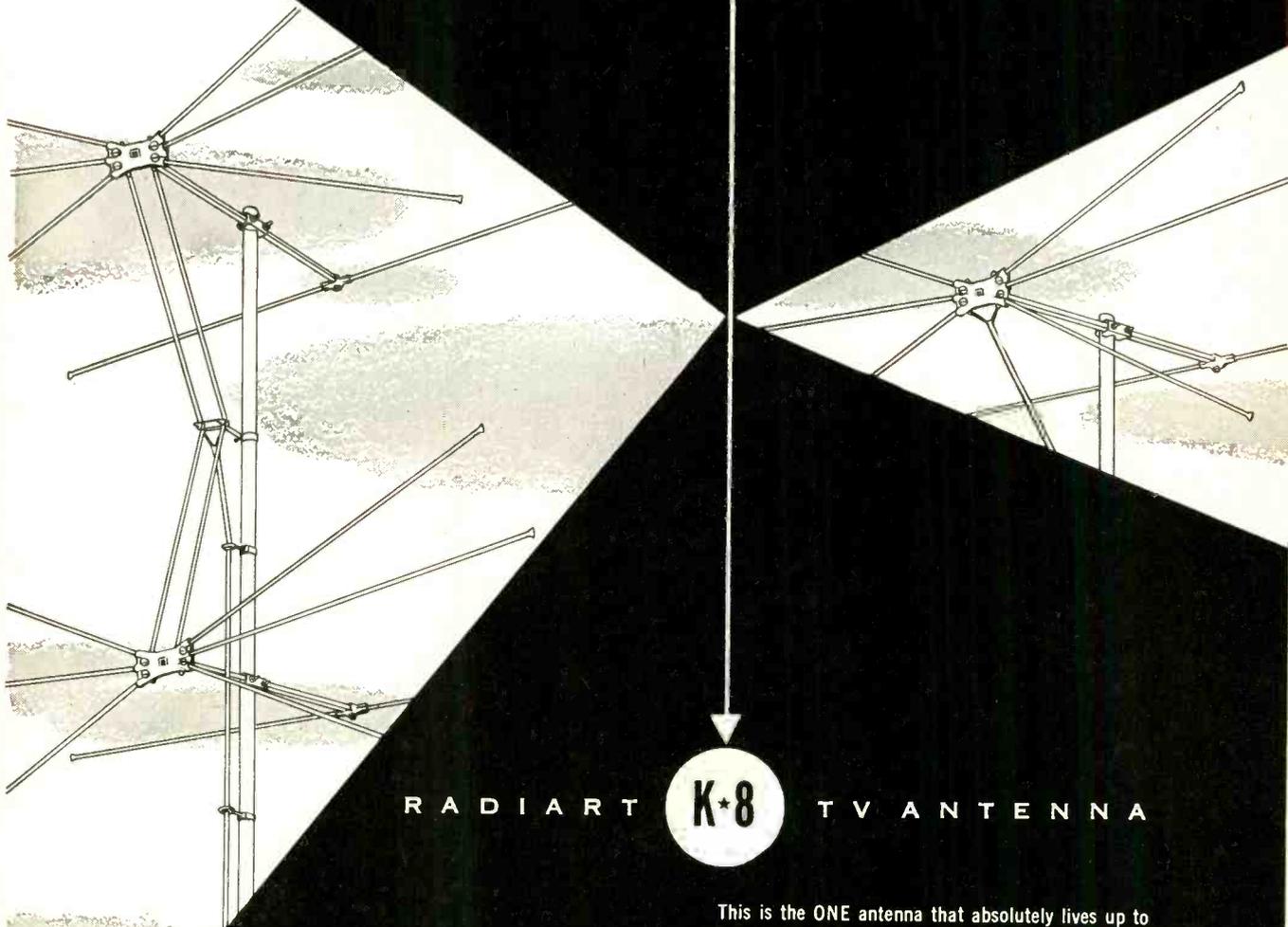

RADIART **K-8** TV ANTENNA

This is the ONE antenna that absolutely lives up to and completely merits the superlatives and all claims made for other type antennas! Here's why:

- Field tested for two years — proving its ability to get all VHF channels exceedingly well.
- Superior construction throughout featuring ½" seamless aluminum elements.
- Exclusive, patented, quick-rig, cam action locking device for positive speedy assembly.
- Extra heavy moulded plastic insulators with precision machined brackets as well as costly die cast fixtures.
- Double stacked array eliminates fringe area reception problems.



THE **RADIART** CORP.
CLEVELAND 13, OHIO

VIBRATORS • TV ANTENNAS • AUTO AERIALS • ROTORS • POWER SUPPLIES

Again proving
tube-design
leadership...

40% OF 1952'S NEW RECEIVING TUBES WERE G-E DEVELOPMENTS... TWICE ANY OTHER MAKE

FOURTEEN out of thirty-five registered *new* receiving-tube designs—40%—were G-E, in the last calendar year, 1952. As still further proof of leadership... new G-E types numbered more than twice those of any other manufacturer!

Outstanding research and development by General Electric have given to the TV-radio industry its newest, most advanced tubes. You can be sure, when servicing latest-model receivers, that G-E tubes are available for every need—that G-E leadership

in tube development brings you the finest obtainable product. Every working day, you will receive extra dividends in superior performance and reliability.

You can expect more new and improved tubes from General Electric in the months ahead—types that will make your work easier and cut call-backs. Keep in touch with your G-E tube distributor for forthcoming new-tube announcements, each with a profit message for you! Tube Dept., General Electric Co., Schenectady 5, N.Y.

SHOWN BELOW: a few of the many new G-E tubes that are making money for service dealers.



You can put your confidence in—

GENERAL  ELECTRIC

161-1A8

NEW

Model RM-15 ROOF MOUNT


AGAIN South River has the serviceman in mind! With the new South River Roof Mount Model RM-15 his job is a quick, easy, efficient operation. A unique "walk-up drop-lock" feature permits ONE MAN roof-mounting for single mast installations. This mount allows fast, simple installation from a horizontal position. After the antenna and mast are "walked-up" to the vertical position, the mast holder DROPS into a special notch and LOCKS securely. The serviceman is then free to guy the mast.

Made of heavy-gauge metal, heavily plated for rust resistance and embossed at all critical points for extra strength and rigidity, the 5 1/2" long mast socket accommodates masts measuring up to 1 1/2" O. D.


The mast is secured in the mounting socket with 2 rugged hex screws, eliminating the danger of the installation vibrating loose. Two "in line" holes in mounting base permit bolting directly into heavy roof cross member.

FROM

South River

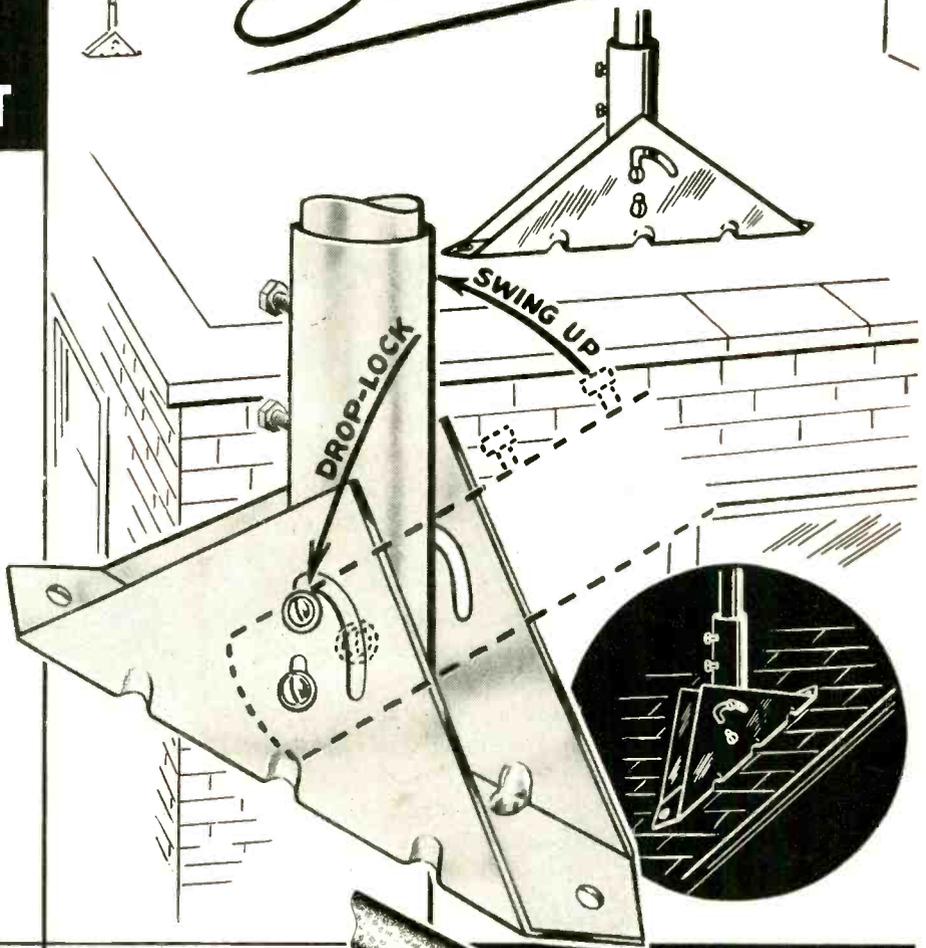

Rust-Proof

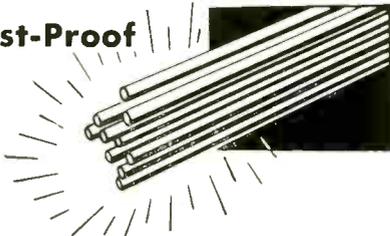

ALUMINUM TUBING

Only South River is able to offer the industry this super-strength product extruded especially for us. The new aluminum tubing is fabricated of 63S-T6, a special structural alloy designed for maximum strength. Aluminum itself is bright and non-rusting, affording a lasting finish. Made with a .054 wall by 1-1/4" dia., in 10' lengths, the tubing is supplied 25 to a bundle.

Stronger, Tight-Twist GUY WIRE

Do the best installation job... use South River's new hot-dip galvanized guy wire, carefully drawn with a tighter, stronger twist for extra durability under stress—providing tensile strength up to 70,000 lbs. per square inch. Produced in either 18 gauge or GENUINE 20 gauge, both available in either 4 or 6 strands, this vital product comes to you in 1,000' lengths on metal spool, or in continuous loops of 50' and 100' lengths.



Exclusive STEEL TUBING

Hot-Dip Galvanized Inside and Outside!

South River presents another FIRST in the industry... 18 gauge steel tubing, hot-dip galvanized INSIDE AND OUTSIDE... affording maximum utility and long life because of complete, all-over protection. It greatly increases the resistance of steel to the extreme atmospheric corrosion of shore and industrial areas. Hot-dip galvanizing is the only experience-proven rust resistant finish known. The tubing is available in 5' and 10' lengths, 10 to a bundle, is 1-1/4" dia., and is supplied with either plain or swaged end for mast extension.

South River's INSIDE AND OUTSIDE hot-dip galvanized steel tubing is another step forward in combating rust and corrosion. Your use of this product will prove that you keep abreast of important, new developments, for increased customer satisfaction.

South River

METAL PRODUCTS CO., INC., South River, New Jersey

Write for
Complete Catalog

PIONEER MANUFACTURER AND OUTSTANDING PRODUCER OF THE FINEST LINE OF ANTENNA MOUNTINGS

In Canada—A.T.R. Armstrong Co., Toronto

PHILCO TEST EQUIPMENT SPECIFICALLY DESIGNED FOR THE SERVICEMAN


AGAIN PHILCO LEADS THE INDUSTRY

Serviceman's needs seen as Philco's Engineering Goal


This new Philco VHF to UHF adapter pioneers a whole new approach to service problems and at the same time is the most economical and practical unit ever offered. Servicemen are taking full advantage of the introductory demonstrations of this amazing piece of equipment now offered by Philco distributors coast to coast.

The First and Only VHF to UHF Signal Generator Adapter

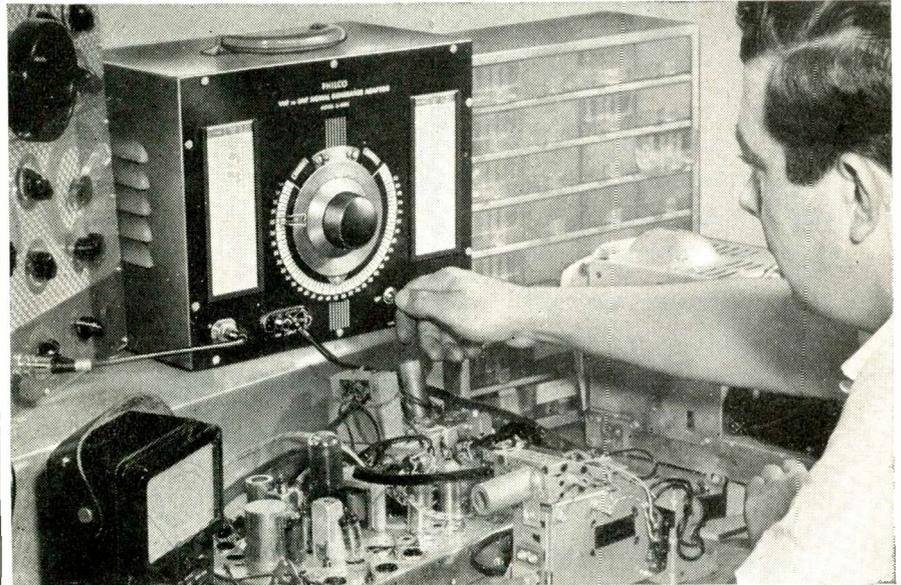Continuing its engineering program designed to provide the serviceman with the best possible test equipment Philco Corporation now offers at a fraction of the usual cost an exclusive highly specialized adapter unit for converting the output of VHF TV servicing test equipment to UHF.



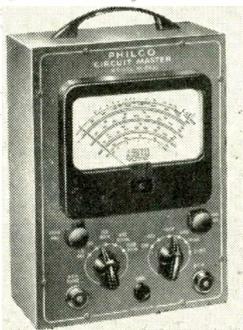Under the trained eye of a Philco Serviceman the amazing model G-8000 VHF to UHF signal generator adapter is shown in action.




One of the Finest Vacuum Tube Voltmeters ever Designed

Facing up to the task of measuring high impedance circuits where loading effect must be kept to a minimum Philco has again designed a unit which meets the most rigid engineering specifications. All reports indicate this unit is unexcelled for complete and accurate measurements.

Practical Portable 3-inch Television Oscilloscope

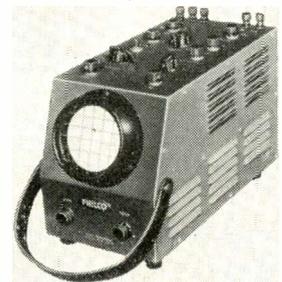The tremendous growth of television requires the most practical and versatile types of equipment to answer service needs. Philco has such equipment, particularly in its 3" scope which is 2½ times smaller than other 3" units, making it adaptable to either bench use or field servicing. High sensitivity and wide response make it ideal for TV work.



"Philco Test Equipment Specifically designed for the serviceman!" That's the theme of Philco's engineering program. A program which you, the serviceman, can depend upon to supply the very finest in service test equipment. Discover how easy it is to own a complete Philco Test Equipment Laboratory. Your Philco Distributor is eager to serve you by offering his new special payment plan to best accommodate your needs. Fill out the attached coupon as shown and mail to Philco Accessory Div.

PHILCO CORPORATION

Accessory Division
Allegheny Ave. & "A" St., Phila. 34, Pa.

I am interested in the Philco Test Equipment shown here. Please send me details of your SPECIAL PURCHASE PLAN for obtaining these units.

Please send FREE copy of your new booklet on Philco Test Equipment.

NAME

ADDRESS

CITY STATE

IMPACT IN UHF

FINCO

series 500

Great UHF ANTENNAS

Engineered To Give
HIGHEST GAIN and
NARROWEST PATTERNS
 to solve difficult "GHOST"
 problems in the **FRINGE**
AREA AND IN CLOSE
TO THE STATION

IMPACT

Through Advertising

LOCAL NEWSPAPERS

LIFE

FARM MAGAZINES

RADIO

TELEVISION

FINCO IS A NAME
 YOUR CUSTOMERS
 KNOW BECAUSE OF
 THIS POWERFUL
 NATIONAL ADVERTISING
 PROGRAM!


**THE
 FINNEY COMPANY**

Dept. T311—4612 St. Clair Ave., Cleveland 3, Ohio


This great series once again reaffirms Finco leadership! Model 502 is a 2-bay unit of the colateral* type with a "snap-out" screen for instantaneous installation. Model 504 is the 4-bay version, highly effective in super fringe areas where ultra high gain is consistently required. Both models feature high front to back ratio and excellent impedance match to 300 OHM line for low signal fringe areas. Completely preassembled — corrosion proof aluminum throughout (including screen) — one antenna, one transmission line!

Both Units available in 3 models which peak on channel ranges shown below and maintain high gain on balance of frequencies:

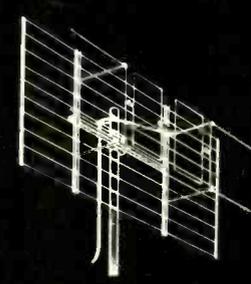- # 502A — channels 14-32
- # 502B — channels 29-55
- # 502C — channels 53-83



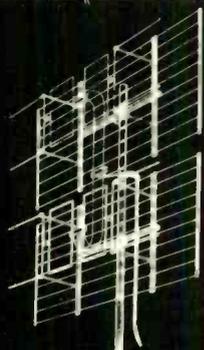- # 504A — channels 14-32
- # 504B — channels 29-55
- # 504C — channels 53-83




Patent No. 2,566,287
 *Reg. U.S. Pat. Off.

PROOF!




When measurement standards* are uniform
AMPHENOL antennas provide the best
 electrical characteristics

* All AMPHENOL VHF antenna measurements made
 in accordance with proposed RETMA standards.

LOW BAND

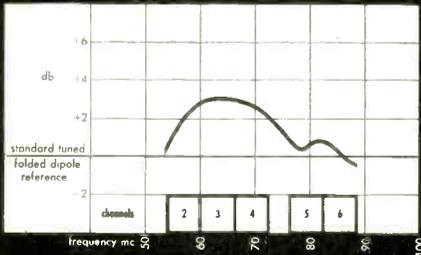

HIGH BAND

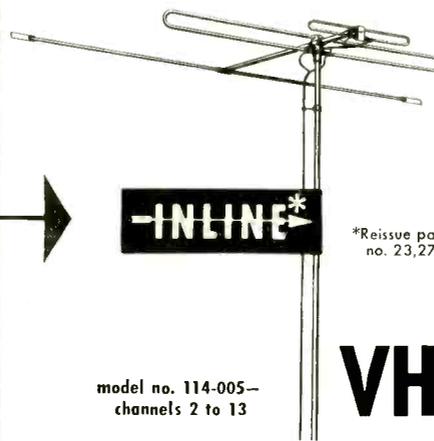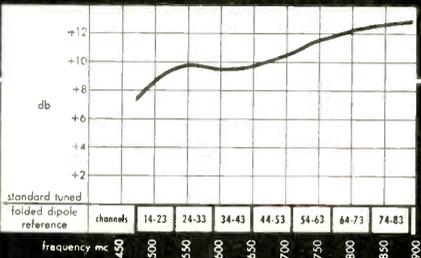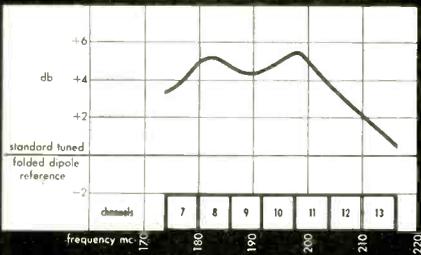


-INLINE*

*Reissue patent
 no. 23,273


model no. 114-005—
 channels 2 to 13

VHF

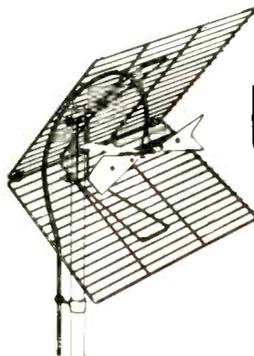

UHF

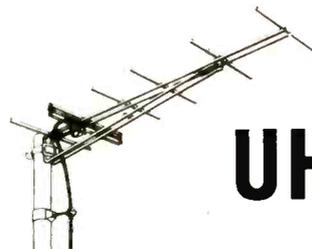Corner Reflector—model no. 114-058
 for channels 14 to 83




UHF

Yagi—model no. 114-054 (24-30)
 for channels 24 to 30
 (models available for all channel groups)

Advertisements claiming 40 db gain for gilded coat hangers will be a thing of the past with the adoption of proposed RETMA antenna measurement standards. By this move, all antenna manufacturers will measure the performance of their antennas by the same methods.

The adoption of uniform standards will not affect AMPHENOL literature, however, as all AMPHENOL antenna measurements are, and have been, made in accordance with these proposed standards. The gain charts to the left represent **reliable** indices to the characteristics of three representative AMPHENOL antennas—give **proof** of top performance.

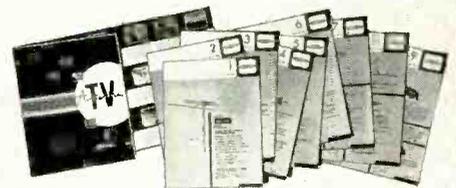The superb **electrical performance** of AMPHENOL antennas plus the famous AMPHENOL **craftsmanship construction** has made these antennas the first choice of dealers, servicemen and installers all over the nation. They have found the AMPHENOL line to be the **quality** line on both top **electrical performance** and **durable construction**.



For complete information on every AMPHENOL antenna, be sure and get your copy of the free "TV Antenna Folio" which contains antenna and accessories catalog sheets with full electrical data. See your AMPHENOL distributor.



AMERICAN PHENOLIC CORPORATION

chicago 50, illinois

Decide on DuMont

on the basis of...



Microscopic look at the cathode surface reveals soft, even texture, necessary for efficient tube performance

Product Superiority

*not too wet, not too dry—
not too light or heavy...*

THE CATHODE plays an important role as source of electron energy in the picture tube. Moisture content and texture of the cathode coating must meet rigid standards to insure maximum picture tube life.

At Du Mont, exclusive processes are used for applying the cathode substance. The soft even texture achieved (see illustration) packs the effective emitting area (in circle) with extra electron power.

The resulting brighter performance over maximum tube life tells you why Du Mont is the right replacement for any set.



*Trade-mark

REPLACEMENT SALES, CATHODE-RAY TUBE DIVISION • ALLEN B. DUMONT LABORATORIES, INC., CLIFTON, N.J.



GUARANTEED PERFORMANCE

MONEY BACK GUARANTEED TO RECEIVE *All* UHF and *All* VHF STATIONS IN *All* DIRECTIONS FOR 60 MILES WITHOUT A ROTORMOTOR OF ANY KIND!!

**SO NEW! SO DIFFERENT!
IT'S PATENTED!**

- # 2,585,670
- # 2,609,503
- # 2,625,655
- # 2,644,091

OTHERS PENDING

WORLD'S MOST POWERFUL UHF - VHF TELEVISION ANTENNA

While antenna reception is guaranteed for 60 miles, perfect pictures have been consistently received as far as 160 miles from stations.

NEW POLYMICALENE 4 CONDUCTOR TRANSMISSION LINE

- Low Loss External - Air Dielectric
- Matched Impedance
- Eliminates End Sealing
- Eliminates Condensation
- Up to 50% Less Loss Than Tubular When Wet
- Easily Spiraled
- No Breaking or Shorting
- Patents Pending - T. M. Reg.



All NEW DESIGN FOR '54

- LOW-LOSS SWITCH
- LOW-LOSS PHENOLIC INSULATORS
- USES NEW 4-CONDUCTOR MATCHED IMPEDANCE LINE
- ONLY 10 INCH SPACING BETWEEN ANTENNA BAYS



The 9 position selector switch electronically rotates the antenna in a stationary position.

LIST PRICE

\$36⁷⁵

SEE YOUR LOCAL JOBBER.

PRICE INCLUDES

Complete stacked array • 4 stacking bars • 9 position switch • Switch-to-set coupler • 2 - 7 1/2" stand offs • Individually boxed in mailable carton

Money Back Guarantee IN EVERY AREA WITH STATIONS IN ALL DIRECTIONS

The new All Channel Model Super 60 is guaranteed to bring in, immediately on installation, every UHF and every VHF station within 60 miles in any direction, giving clearer and sharper pictures than any antenna or combination of antennas with or without rotor motors. If, immediately on installation, it fails to do this we agree to refund to the jobber to whom we sold and shipped it, his full purchase price.

ALL CHANNEL ANTENNA CORP.

70-07 Queens Blvd., Woodside 77, N. Y.

Hickory 6-2304

TECHNICIAN

CALDWELL-CLEMENTS, INC., 480 LEXINGTON AVENUE, NEW YORK 17, N. Y.

FREE TUBE CHECKING — GOOD BUSINESS or BAD?

"TUBES CHECKED FREE." Does this sign appear in your window? If so, how much good is it doing you?

Do you know how much it costs, in labor time alone, to test each tube? Don't say it's a matter of seconds. Try timing it yourself. You have to warm up the checker and adjust it for line voltage. You have to set it up separately for each tube, more than once for multi-section tubes—and there are more of these today than ever before. You have to wait for each tube to heat. Added all together, two to three minutes is a reasonable estimate of time required to test each tube.

Let's suppose your shop man is doing the job. If his salary is in the range of \$70 to \$80 per week, he averages \$2 per hour or more than three cents a minute, or about eight cents for each tube he tests. If you do the checking yourself, this cost is still higher. You still haven't counted time lost in talking to the customer or in breaking off another job and picking up the threads again; the cost of your tube checker plus its maintenance and depreciation; or any of the other overhead factors, like rent, electricity, paperwork, and insurance, that hang over every move you make.

Cost—12 to 14 Cents Per Tube

If you check an average of only 25 tubes a day—five customers with five tubes each will do it—your labor-cost factor alone is \$2. Another dollar a day for other expenses is a conservative figure for this service. In addition, your tube checker itself (initial cost spread out over its useful life plus maintenance and depreciation) can easily account for 50 cents more. At this rate, tube testing will cost you \$18 to \$20 every week, or about 12 to 14 cents a tube.

But this is advertising, you say; you're buying good will. Good will from whom? You're playing to the fix-it-yourself crowd, the something-for-nothing bunch. The customer who marches in with a box full of tubes will solicit additional advice—also at no charge. He wants to know what he can next do to fix his set without paying you an honest fee for legitimate service.

Set Servicing More Profitable

Good will? Let's take cases. You've checked a bag of tubes for a customer whose TV set produces weak pix and sound. The local oscillator shows low emission and two IF tubes are on the borderline. You sell three new tubes. Actually you make less profit this way than you would have made on them if the set had wound up on your bench. Yet it turns out that the original oscillator was functioning anyhow and the IF tubes were also getting by. But there's an open grid-return resistor in the video amplifier that keeps on blocking signal after the new tubes are in.

Another case. Your checker shows a horizontal output tube is burned out. You sell a replacement. Half an hour later, your customer is back and in an unhappy mood. The same short circuit that finished off the original tube has just ruined your replacement. You can't get an exchange for this defect. Who bears the cost? Remember good will! If you satisfy your customer with a refund, how do you recover this loss?

Make a Minimum Charge

If you're against price cutting on your sales or other services, don't contradict your stand on this practice. A nominal testing charge, say 15 or 20 cents per tube, will do little more than protect you against loss of time and money. But it will guarantee you the minimum charge you have earned for a service performed. In addition, since it provides no escape from the minimum charge, it will put on your bench more of the sets that belong there. Your tube checker is a respectable instrument but, like your meter or scope, it is not the answer to all receiver defects by itself.

Finally, a charge for tube testing has the effect of saying to the set owner, "We are responsible people who do a skilled job, and we charge for it. We stand behind our work. We're not giving you pie in the sky; we're marketing our service."

Don't sell yourself short.

Tuning In the

NO DEPRESSION IN SIGHT, but good general business through first half of '54 seems to be the combined "best guess" of business soothsayers at this writing. The combined index of wholesale prices is expected to be steady to lower from now to 1954 mid-year. This will bring about a lower level of personal income by July. But chance of any real depression like 1929 is guarded against by these comparisons with 24 years ago.

Income is 198% higher.

Gross national product is 248% higher.

Total net private debt is only 75% higher.

Hourly earnings are 224% higher.

The cost of living is only 55% higher.

Dow-Jones industrial stock averages are 15% lower.

19% OF SETS SERVICELESS! Survey of New Brunswick, N. J., by Cunningham & Walsh, shows that this city of 38,768 people, 40 miles from New York City, has 71% saturation of TV sets. While replacement sales doubled last year, they still amounted to only 21% of total sets sold. When people do buy a second set, the purchase is actually replacement for smaller-screen set; the owner generally just "hangs on" to old set. Only 4½% of TV homes have two sets. High-cost-of-maintenance myth appears to be exploded by this latest survey of "Videotown." Some 19% of owners have "never had their sets repaired"; of sets purchased before 1951, there are still 4% which have "never been repaired." Average annual TV repair bill is \$11, except for those few who have had to replace picture tube.

DRASTIC OVERHAUL OR REPLACEMENT work needs to be done on more than half of the outdoor antenna systems in use. Such services are required to insure better reception or for safety reasons. At an average service charge of \$15 per system, the total is a tidy sum—a large potential to shoot at.



THE DOCTOR, THE PLUMBER, and the TV serviceman now have one common aspect in that they charge for a home call whether or not a service is performed, a prominent manufacturer points out. The physician cannot be substituted for, the plumber cannot be delayed, but the TV serviceman can not only be substituted by an amateur or part-time worker, but can be delayed indefinitely until the set is completely useless.

MOVIE OF TV SERVICEMAN in action, showing his usefulness and value to the public, is planned by Service Committee of the Radio-Electronic-TV Mfrs. Assn. A script costing \$2500 is now being prepared. Black-white film is expected to cost \$15,000 to complete; if in Technicolor \$22,500 to \$25,000. Prints of the 15-minute film will cost \$25 each, and will be rented for \$3.50 per showing or \$12 per TV program.

IN THE RED-HOT PRICE-CUTTING BELTS, chiseling customers want that "something off" in cold cash when they buy sets these days. Chiseling dealers who offer to throw in antenna installations and free service contracts are finding that such inducements have lost their one-time luring power. Result: Technicians in such areas are running into plenty of "new work" from chiseling customers, and brother, they've got to watch their step—the servicers, we mean—in coming out of such deals with a profit.

ABOUT HALF OF THE WHOLESALE-RETAIL parts houses in New York City will give dealers a break on Hi Fi equipment in cases where the latter provide letterhead or business card. The "breaks" given are considerably better than those offered the man who walks in off the street.



THE FINE LINE OF HONESTY—Where does it end and dishonesty begin, many service firm employers are asking themselves as they notice the disappearance of tubes and parts from their shelves and stockrooms. They know where the components are going but what can they do about it? Shall they accuse their day-time employes of working on their own after hours and using the bosses' materials for private profit?

MANY EYES ON RETMA'S TRAINING COURSE. The pilot program being developed in New York City will, if successful, be extended to other parts of the country, in an attempt to up-grade the quality of television servicing. Among the 85 candidates applying for admission for the NYC course starting this Fall, were servicemen working long hours at the bench, ready to give up the shreds of spare time they had left, in an effort to improve their technical ability. Eligibles who are accepted will be given the opportunity to work on late-model receivers of many different makes, and become familiar with a wide variety of test equipment.

Picture

PUBLIC PLACES, SUCH AS BARS are away behind homes in putting up with poor TV reception, almost always due to the operation of obsolete sets. Technicians who have plenty of headaches with out-of-date projection receivers, peanut-size screen jobs and other "trouble-makers" will be doing themselves and their customers a favor in cases where they sell 'em a new TV set.



MY "TOUGH DOG CORNER" is right in the home of a certain dog-owning customer of mine, writes a Georgia technician. "Kids don't bother me a bit, but this lousy canine gives me the jitters. He barks at me all the time I'm working, chews up the lead-in wire, and flies at me every time I make a move. To make matters worse, he's big as a lion, and about as ferocious, too. The people in the house say he's gentle as a kitten. I wonder!"

PLENTY TECHNICIANS ARE GRIPING THESE DAYS about "back-door" servicing by distributors, claiming that many of the set wholesalers go all-out in repairing consumers' receivers, and some in selling parts. Distributors have gripes, too, in this situation. Some of the big firms claim they don't want such consumer business but are usually forced into it by folk who claim they can't get proper service from their neighborhood repairman.

AND MUCH OF THE SERVICE WORK performed by distributors for consumers comes about as a result of letter-writing to factories by disgruntled users. Some manufacturers don't answer such complaints, but others do, sometimes recommending, in extreme cases, that the owners go to the distributor. Slews of griping mail pours into TV manufacturing plants. You'd be surprised how much!


TWO SOLUTIONS TO THE PROBLEM: 1. Get to know your distributor. And if you think he's taking away any of your bread and butter, tell him so and perhaps you can straighten out the situation. 2. Handle the "headache" customers with kid gloves. Try to put the "Tough Dog" receivers in good working condition, and be willing to go to the mat with your own customers to prevent them from going over your head with their complaints.

HAM INTERFERENCE IN TV RECEIVERS using "strips" to bring in UHF channel may pose a real problem for set owners, manufacturers, servicemen and hams. Under the dual conversion system used in strip tuning,

the second harmonic as well as the fundamental frequency of the oscillator is employed to produce the first and second intermediate frequencies, respectively. The first intermediate-frequency, unfortunately, falls within the 144-148 MC amateur band. Since there are circuits in the front end that tune to the 150 MC frequency region (in tuners using strips), ham band signals in this part of the spectrum are accepted, and interfere with reception. Many amateurs have been staying off the air, to avoid ruining their neighbors' TV reception. Officials of the American Radio Relay League have announced, however, that their members cannot be expected to stay off the air because of design faults for which TV set manufacturers are responsible. If a serviceman is called in on a TVI complaint of the kind just described, he has a choice of one of two courses of action: 1—Acquaint the customer with the facts, and let it go at that. 2—Try lining the inside of the cabinet with a shield of some sort.

CONTROL OF PARTS STOCK vitally important. Millions of dollars' worth of new components go down the drain in service departments, in dealer stores, and in factories and distributor establishments. Loss occurs when employes take new parts out of stock, fail to use them, or just simply chuck 'em out. Huge sums are lost, too, when servicers "forget" to charge out components taken from shelves and bins. An efficiently operated accounting system is a must for every profit-minded operator.

WHAT WE ARE WORKING FOR

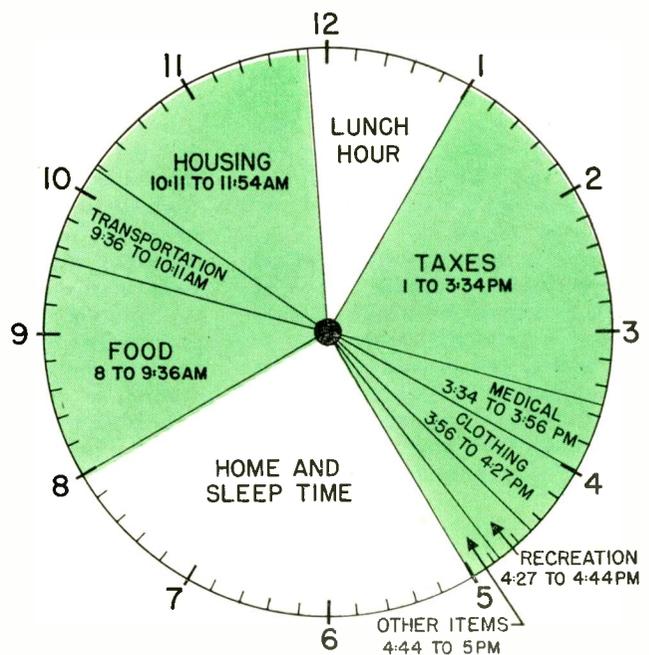

This clock diagram shows just how many minutes each day it takes you to earn the money for your family's food, housing, clothing, doctor bills and TAXES—if you work eight hours a day for an income around \$4500 a year. Both direct and indirect taxes are included, as computed by Tax Foundation, 30 Rockefeller Plaza, New York City.

Tracking Down TVI

How to Troubleshoot External and Internal

By JAMES A. McROBERTS

• When interference is present in a set, the serviceman must determine whether the symptoms are internally or externally caused. Some technicians are apt to dismiss what is apparently a case of external interference with a statement like:

"Local interference is the cause of those lines, Mr. Smith. I'm afraid we can do nothing for you."

Have you heard this approach before? Contrast it with the following: "We're not certain where you're

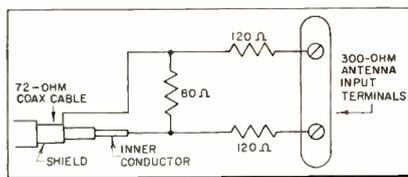


Fig. 1—Suggested matching network for connecting probe to receiver's antenna input.

symptoms originate, Mr. Smith. Suppose we leave this Superbo set with you for a few days—if the interference symptoms appear on this set too, we'll know for sure that the trouble is *outside* the set, and we can then go on to locate its source. If the symptoms *don't* appear on the Superbo, on the other hand, the trouble is probably originating *inside* your set. When our final test verifies this, we'll haul the set into the shop for repair."

Not only is this a practical method for determining whether the TVI present is originating inside or outside the customer's receiver—it is also a way of *demonstrating* this fact to the customer; and, in cases where an improperly designed set is responsible for TVI pickup, the demonstration may help sell a new set.

Still another pleasant feature of this lend-a-set technique may be mentioned: considerable time is saved by having the customer monitor the symptoms, without pay.

When it has been determined—by the lend-a-set method or some other technique—that the source of the TVI is external to the set, the possible routes of entry of the undesired signal should be considered. Determination of the route of entry will indicate whether the transmission line and antenna system, or the power line, must be signal-traced for the source of TVI, or whether direct pickup of the TVI via the chassis must be investigated.

While a cure may be effected during the course of such signal-tracing, TVI cures are not the subject of this article, which concerns itself primarily with TVI localization tests.

Tests to determine the TVI route of entry may be made by the technician; the customer (suitably guided by the technician, of course) may, in some cases, also make the tests.

The first check might logically be one to determine whether the TVI is entering via the power line. To make this test, install a commercial power-line filter between the set and the electric outlet. It is desirable to attach suitable plugs to the filter, so that it may be connected, not to the receiver line cord, but to the point where the line cord connects to the receiver proper. When an external ground connection is provided at the filter, a wire should be run between it and a good ground, to get maximum effectiveness from the filter.

If the symptoms of interference are now eliminated or greatly re-

duced, entry of the TVI via the power line is indicated. If the TVI is diminished to some extent—but not greatly—by the filter, signal tracing may start at the power line, using techniques to be described later; it should be kept in mind, though, that additional points of entry may be involved.

The check just described should be made before any of the others to be listed, to eliminate the possibility of TVI getting into the set *indirectly* (via radiation), from the line cord, as well as *directly* from the line cord, through the receiver's AC input terminals.

To determine whether the TVI is entering by way of the antenna system, disconnect the transmission line from the receiver's antenna-input terminals. If the intensity of the TVI symptoms is diminished, the interference is entering via this path. (The station signal will, of course, be attenuated when the antenna is disconnected.)

Sources, Tests, Remedies


If the TVI route of entry is the antenna-transmission line system, several possibilities must be considered:

1. *The frequency of the interfering signal is the same as that of the desired signal.* If this is the case, the TVI cannot be eliminated by filtering and trapping methods (such as those described in succeeding steps) without also eliminating or attenuating the desired signal. Sometimes re-orienting the antenna, re-routing the transmission line, or using a shielded lead-in will eliminate the symptoms. At other times, it may be

Fig. 2—Length of the probe may be between 6 and 100 feet (see text). Basic probe for tracking down television interference.



Fig. 3—TVI probe with a wire added to increase its pickup.

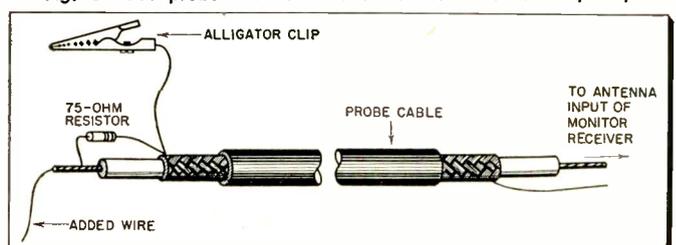

to Its Source

Interference, Using a Probe and a TV Receiver.

necessary to trace the unwanted signal to its source (which is usually nearby) and apply control measures at the latter point.

2. *The interference is present on all station channels.* This symptom indicates that the frequency of the offending TVI lies within the IF band of the receiver. To check whether this is the case, install at the antenna terminals a commercial trap that is tunable over the TV intermediate-frequency bandpass. If the TVI is reduced or eliminated by appropriate tuning of the trap, a cure as well as a localization of the trouble has been effected. If the interference is attenuated, but remains troublesome, signal tracing of the transmission-line antenna system will be necessary.

3. *The interference is due to some harmonic of an undesired signal.* A commercial trap at the antenna terminals will eliminate or attenuate this kind of TVI. Obviously, the trap must cover the frequency range of the possible interfering signals. The offending frequency will be some subharmonic ($\frac{1}{2}$, $\frac{1}{3}$, $\frac{1}{4}$, etc.) of the frequency of the channel(s) on which the symptoms appear.

4. *The interference falls within the image-frequency band of the receiver, and is produced by a signal source operating outside the band of VHF TV channels.* Ordinarily, the undesired image will be separated from the station signal by a frequency of twice the receiver video IF. In cases where the oscillator operates below, rather than above the incoming signal, however, this will not be true. The set's schematic and service data should be checked, to determine what conversion system is actually being used. Try a suitable trap at the antenna input,

to remedy this kind of TVI.

A relatively powerful, closely-situated source of TVI may cause unwanted signals to be picked up directly, by chassis wiring or other chassis components. This means of entry can be checked by moving the receiver from place to place about the room and observing whether the TVI intensity changes. Often, movement of the technician, or other people in the room, will produce this same intensity variation, eliminating the need for moving the receiver.

Troubleshooting Clues

Manipulation of a metal sheet (such as the mirror used in making raster adjustments) in the vicinity of the set, can provide clues to the origin of the interfering signal. This is so because the interfering signals travel in relatively straight lines. The ability of the metal sheet to reduce TVI, when positioned between the receiver and the TVI source, suggests chassis shielding as a possible cure for the trouble.

It is not at all unusual for some portion of the interference to be entering by all of the three routes previously mentioned: via the power source, the antenna-transmission line system, and direct chassis pickup. In this event, the tracing procedures to be described will start with that source of entry which seems responsible for most of the TVI; but the other routes will be kept in mind for subsequent investigation.

With respect to the tracing procedure itself, equipment is required which will pick up the interference and monitor its intensity, as we

probe various locations. This equipment comprises, in most cases, a set which can tune in the interference (the customer's set, for example) and a shielded probe which permits only a small amount of the pickup energy to enter the set used as a monitor device. A 72-ohm coax cable is well suited for use as a probe; this type of shielded unit is desirable because we want the probe to pick up a minimum of interference signal.

We attach one end of the probe cable to the monitoring set *directly*, if the set has a 72-ohm antenna input; if a 300-ohm input is present, a matching pad (Fig. 1) is inserted between the probe and the receiver. The pad may be either a commercial or home-made unit (same type as the ones used for matching signal generators to antenna inputs).

To make the probe proper, simply remove some (about a half-inch) of the outer coaxial shield from one end of the coaxial cable (see Fig. 2). To the shield (at the end from which the half-inch section has been removed) attach a short length of lead, preferably shield braid; terminate the free end of this lead in a clip, as illustrated in Fig. 2.

Probe Length

The length of this elementary probe should be a minimum of one hundred feet, to be suitable for most cases of external interference; a minimum length of six feet is suggested for troubleshooting internal TVI (interference originating in set). The cable end opposite the clip-terminated one is connected to the input of a set which can pick up and display the TVI.

The end of the probe forms one

Fig. 4—Probe used with series condenser (C-1) in checking the power line for TVI. Additional connection of probe shield to line through C-2 will increase TVI pickup. C-2 may be .1 mfd.

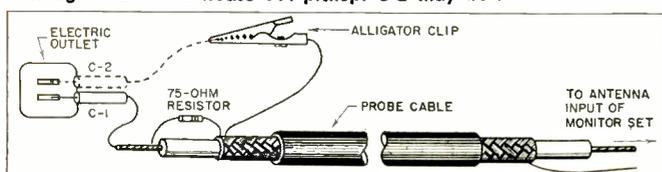


Fig. 5—How an exploring coil is connected to the probe.

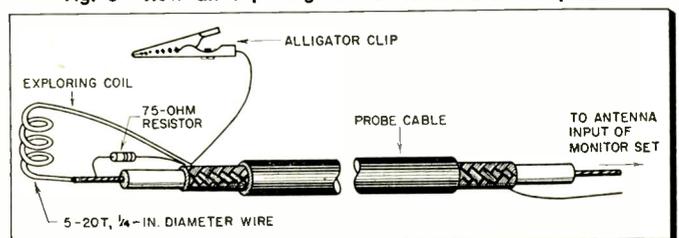


plate of a condenser, the metallic parts of the circuit near it comprise the other plate. Capacitive coupling is thus used to transfer the TVI from the circuit (or several circuits) being tested, to the probe.

The signal pickup of the probe may be insufficient at some stages of the test procedure. To increase it, attach a wire to the probe (see Fig. 3). The longer the wire, the greater the TVI pickup will become. The 70-ohm resistor connected between shield and inner conductor terminates the cable; this termination increases the probe pickup by preventing loss due to mismatching. You may remove this resistor if you choose, to decrease the sensitivity of the probe's TVI pickup.

If the addition of a piece of wire provides insufficient pickup of the TVI, connect the inner conductor directly to the circuit under test, through a condenser.

Such a hook-up, for use in power line tests, is illustrated in Fig. 4. Pickup may be increased by the connection of the shield to the grounded part of the circuit directly, or through a series condenser; the dotted lines in Fig. 4 illustrate the latter set-up.

In exploring a magnetic (interference) field, such as the one set up by oscillation in a TV front end, a coil may be of service as an accessory unit. Such an exploring coil is connected between the inner conductor and the shield of the probe, in parallel with the 70-ohm terminating resistor (see Fig. 5). The more turns on the exploring coil, the greater the pickup; you can use this fact as a guide in determining the number of turns to wind.

You may wish to pick up a signal that, you have discovered, is entering the chassis by way of the antenna, say by way of another antenna on the roof. A dipole (possibly an indoor type) could be attached to the probe terminals, as shown in

THE SERVICEMAN

SPEAKS—

“It is something that has been needed for a long time and you surely deserve credit for being the first to bring it to the service field. It contains a wealth of information for the serviceman.”

G. H. Doty,
Doty Radio Sales and Service
Dayton, Ohio

—and he's raving about

**TECHNICIAN'S
CIRCUIT DIGESTS!**

Fig. 6, to form a signal-collecting unit. The dipole may be mounted on a pole for ease of manipulation, as well as to keep it away from your body, and prevent you from affecting the pickup appreciably. The 70-ohm resistor is omitted in this application, as the antenna furnishes the match to the transmission line.

Localizing TVI

To elaborate on some procedures mentioned previously: the process of localizing TVI necessitates the determination of whether the interference is of internal or external origin, as step number one. If external, we trace the route by which it has entered the set, said route including the circuits contributing the TVI—for example, power line to basement to landlord's oil burner, when the latter is the source of trouble.

The maximum intensity of TVI pickup is always sought; when the area of maximum interference is located, it should be a simple matter to

identify the TVI source.

To make the technique entirely valid, some additional precautions are necessary with respect to the monitoring receiver. To avoid misleading indications, it is essential that TVI enter the latter set *only through its connecting probe and cable*. Entry from the AC source can be prevented by inserting a good commercial filter between the receiver and its power outlet. To avoid pickup along the length of the power line cord, the filter is inserted as close to the monitor receiver as possible. An extension cord can be used from the filter to the outlet.

If the TVI is radiating directly into the affected chassis, it may have the same action on the monitor receiver. To prevent this, the latter is physically separated from the set under examination as much as possible. The entire monitoring set may have to be shielded in addition. If the, monitor continues to pick up TVI after both these measures are applied (with no coupling present between the monitor and the set under test), the interference is so strong that it can generally be tracked to its (nearby) source without the use of the tracing techniques described here.


If internal TVI seems present, we move our probe about the chassis to locate the point of maximum intensity; this procedure discovers the circuit(s) which generate or transmit the TVI. (Example: parasitic oscillation of the horizontal amplifier and its B-feeds, the latter feed-lines acting as transmitters.)

Stage Gain

A word of caution is necessary concerning the troubleshooting of internal TVI. The factor of stage gain must be considered in such cases. For example, once interference is present in the audio or video systems, it is likely to be stronger, after amplification, at some point following the point of entry. In a case like this, tracing would have to proceed back, not to the area of maximum TVI intensity, but to the point of entry of the undesired signals in the circuit section that has been invaded. This is the point preceding which no TVI can be picked up.

The probe described here, together with its accessories, is useful for tracing other types of signals besides TVI. It may be used in conjunction with an oscilloscope to locate the cause of hum, video or sweep signal pickup by audio stages, or sweep signal pickup by video stages.

Fig. 6—Using a dipole in conjunction with the probe to pick up TVI signals.

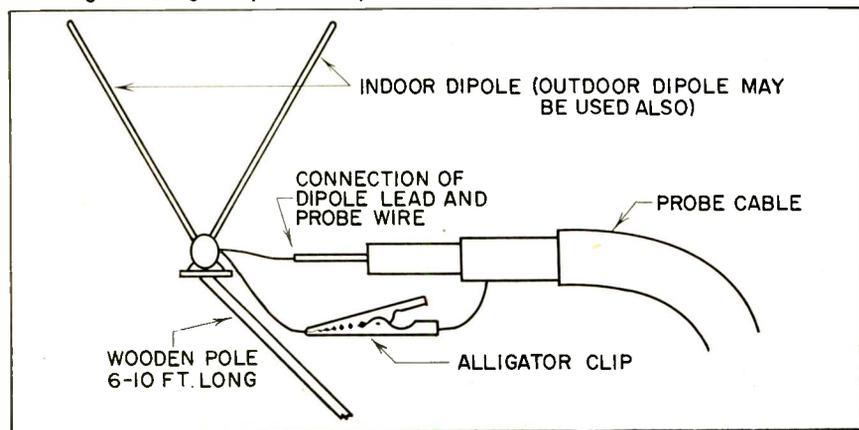

Preventing Tube Damage

Data to Help You Locate the Cause of Some Premature Tube Burn-Outs

MOST OF THIS MATERIAL WAS WRITTEN AND ILLUSTRATED BY JOHN H. WYMAN.

• Many technicians perhaps do not realize that there is current flow in the control grid circuit of all tubes. Normally this current is on the order of a few microamperes. It is caused chiefly by residual gas, and/or emission from the first grid. In some closely-spaced high Gm triodes and some beam tubes, tube ventilation is inadequate; under these circumstances, grid current may rise as high as four or five microamperes. If this current flows through a one-meg grid resistor,

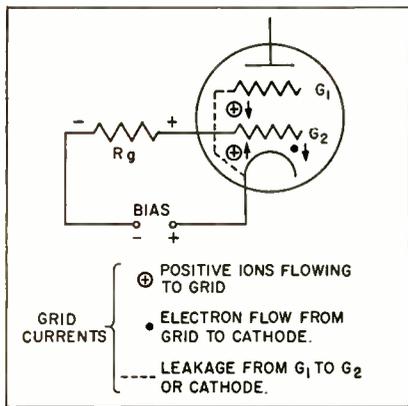


Fig. 1—Gas, leakage between elements (G_1 and G_2) and grid emission, may be responsible for lowering the tube bias to the point where cathode emission is destroyed.

four or five volts may be developed across the resistor (see Fig. 1). The polarity of this voltage is such that the tube bias is reduced, and the plate current consequently increased. This action can be cumulative, resulting in the quick destruction of the tube.

The moral of all this is, check the control grid-to-ground voltage when a premature failure of cathode emission in a tube is encountered, following up by a resistance check of the grid resistor, if an excessive positive voltage is present. Grid resistors over 100,000 ohms in value are particularly eligible candidates for the suspicious eye.

Inadequate cooling in the vicinity of the tube may also be a source of trouble. Check to see that the back of the receiver is some distance from the wall, and that vent holes are not obstructed, to remedy as well as prevent tube damage due to this factor.

Rectifier Limiting Resistors

Servicemen are sometimes uncertain about the function of the small resistor used in series with the rectifier plate in some radio receivers (see Fig. 2A). The technician may find one of these units burned out, and look around for a replacement; unable to locate one in the shop, he connects the rectifier plate to its source voltage, omitting the resistor. The set works fine—why bother getting another resistor?

The answer is, the resistor is a protective one, and promotes longer tube life. Most rectifiers can safely pass a certain peak plate current; if this current is exceeded, rapid deterioration of the tube cathode is apt to result.

In a power supply, the peak current value (see Fig. 2B, C) is determined by the values of load resistance, input capacitance and the impedance of the tube and transformer (or tube and power line generator, in the case of a transformer-


less set). During each cycle, as C starts to charge, the impedance to current flow is practically zero; the rectifier impedance (and that of the transformer, when present) is the only factor limiting tube current flow. Since this impedance is very low, the tube will pass current up to the limit of the emission available from its cathode—an undesirable state of affairs that doesn't do the tube any good.

The insertion of a limiting resistor in series with the rectifier plate (in series with *each* plate, in case of a transformer-powered set) reduces peak current to a safe value. In the case of a transformerless set, the resistance may be in the vicinity of 40 ohms. When a power transformer is present, the limiting resistor value is between 100 and 150 ohms. Limiting resistors, incidentally, are seldom used in sets using power transformers. They are, however, almost always or always used in selenium rectifier circuits; the value of such a resistor in this application may be as low as 7.5 ohms.

Summary


Two important points are worth noting, in summing up: 1—Replace any limiting resistor found to be defective, to insure a normal life span for the rectifier present; 2—Avoid turning equipment on right after it has been turned off; the "hot switching surge" that takes place when the cathode is still hot and "rarin' to go," while the condenser has partly discharged (permitting a larger current to flow through it and the tube), is not healthy for the rectifier.

Fig. 2—A) Half-wave rectifier circuit with series limiting resistor. B) Instantaneous peak current with limiting resistor absent. C) Instantaneous peak current with limiting resistor present. Note that while the current peaks are considerably reduced, the average current is not appreciably affected.

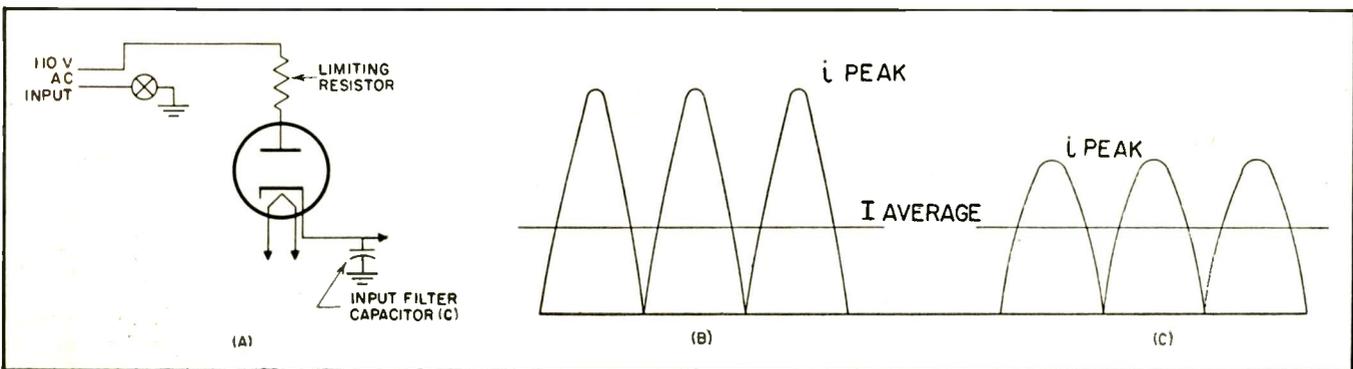

Television Antenna

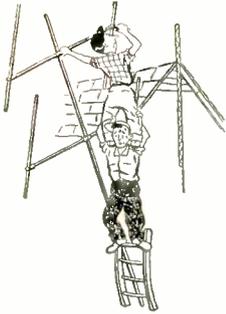Wind Pressure Considerations. Setting Up Guy Wires.



By PHILIP THIER

• The major consideration in any antenna installation is, of course, keeping the antenna up in the air. A fallen antenna may be responsible for a considerable amount of property damage, as well as personal injury. Mounting problems are thus important, particularly in the case of tower-mounted antennas. Since antennas of this type are widely used in fringe areas, a careful examination of the problems associated with their installation may be helpful. These problems and their solutions also apply to the smaller rooftop antennas.

In a fringe area, a tower may be thirty to fifty feet high; a ten-foot mast on an apartment-house roof on the other hand, is about seventy-five feet above ground. Wind pressures on each antenna will be of similar magnitude; the main difference between the two types of installation will generally lie in the type of base mounting used.

Standards have been set up with respect to expected maximum wind pressures without specifying any antenna type. The National Bureau of Standards has set the maximum anticipated wind pressure at nine pounds per square foot. The Radio-Electronic-Manufacturers Association has more than doubled this value, choosing 20 pounds per square foot as their maximum. One apparent reason for the choice of the higher figure by RETMA is to make mandatory the use of at least a 100% safety factor. If the antenna installer wants to allow a safety factor above the RETMA value, more power to him. The importance of safe, secure installations cannot be stressed too strongly.

A wind pressure of even 20 pounds per square foot may not seem like a great load. Consider, however, that this force is acting on the end of a lever. As can be seen from Fig. 1, the base mount must be strong enough to resist the rotational force moment (or torque) created. Let us

assume that the overall area of the antenna assembly exposed in any one direction is one square foot. At the base of a thirty-foot mast, the 20-pound per square foot wind pressure produces a torque of 600 foot-pounds. If this mast is set in a steel plate on a concrete base, the minimum safe stud-type expansion bolt diameter is $\frac{3}{4}$ in.


A relatively small rooftop antenna mount is subjected to forces of 200 foot-pounds or more. The safe bolt diameter in such cases is $\frac{1}{2}$ in.

On an apartment house roof-top, the brick and mortar in the safety wall may become waterlogged and soft from many years of exposure to the elements. In these cases, it has been found necessary to drill clear through the safety wall, using steel plates on each side for reinforcements. The antenna mast is mounted to a steel plate.

Try to avoid any such installation if possible; should one be unavoidable, however, make doubly sure that the steel reinforcing plates are large enough to give secure purchase on the roof. From an inspection of Fig. 1C, it can be seen that tensile stresses in the mast itself must be taken into consideration. A good, solid base is not worth much if the mast above it bends or snaps. The wind pressure acting on the antenna will create forces that tend to bend the mast. Compression on one side and tension on the other combine to produce stresses in the mast material. When these stresses exceed the maximum safe limit for the metal used in the mast, it will shear; the entire structure then collapses. It therefore becomes very important to choose a mast made of the proper material. Our opinion, based on long experience, is that the best metals for the job are 24ST aluminum or a good grade of steel.

Another important consideration in antenna construction is the use of guy wires. After the antenna has been mounted, it may be strong enough to withstand wind pressure without shearing but it may, unless held in place securely, tend to sway continually. Constant bending, however slight, will weaken the metal and eventually result in breakage. Guy wires placed from the mast to a

Fig. 1—A) Diagram showing basic antenna elements and direction of wind. B) Antenna and force acting on it are comparable to lever and fulcrum. C) Mast may be compared to a crowbar ripping bolts out of a housing.

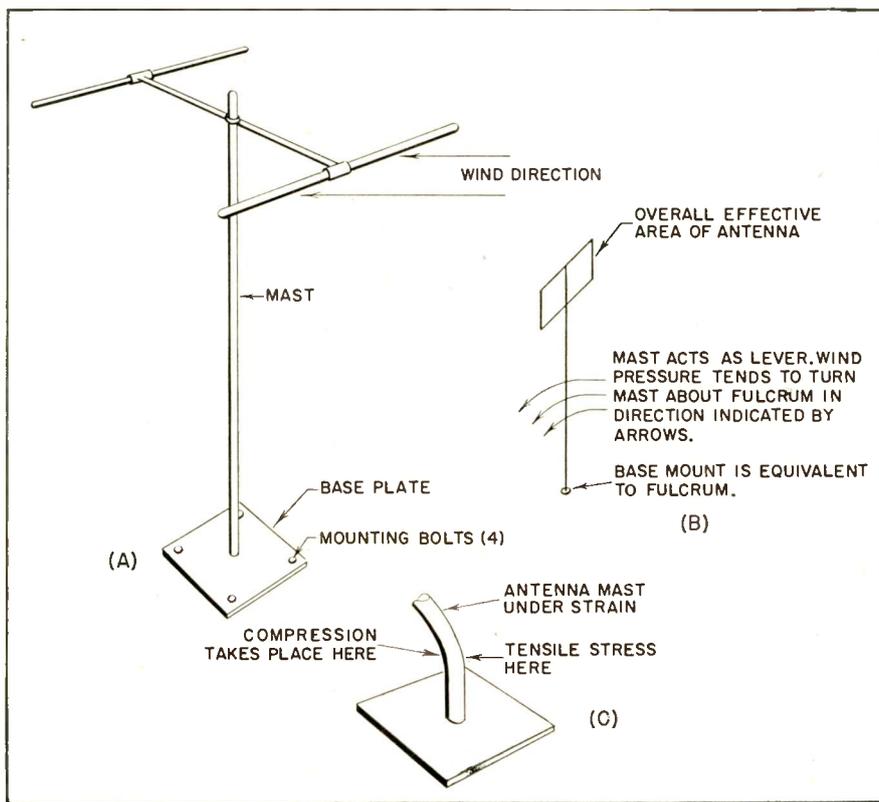

Mounting Problems

Minimizing Corrosion. Corking Mast Ends

secure anchor post increase the overall strength and stability of the tower or mast. Six-foot masts on the top of an apartment house have been known to vibrate enough to shatter the bricks to which they were mounted, and collapse. An easily installed set of guy wires would have prevented the vibration, thereby saving the antenna and possibly the technician's reputation.

In the case of large masts, or in areas where high winds are common, guy wires are absolutely essential. At times as many as four sets of guys are needed to support an extra tall tower. Guy wires should be attached to the mast and to the anchor posts in such a way that the angle between each wire and the ground at the anchor post will be from 30 to 60 degrees (see Fig. 2A). An angle of 45 degrees is considered the most efficient, but variations of plus or minus 15 degrees can be tolerated. The choice of angle depends on space limitations. The 60-degree angle uses least space, and the 30-degree angle most space, from the antenna base.

If three guy wires are used, place them at angles of 120 degrees apart (Fig. 2 B); four wires are placed at right angles to each other.

To facilitate guying placement calculations, Fig. 2A shows only one of the set of wires actually used for

each support angle. Note that the wire going to the top of the mast makes a 60-degree angle with the ground. If space permits, the wires may be anchored further from the base, as indicated by the dotted lines in Fig. 2A. Shorter masts, such as the ten-foot lengths commonly used, can be adequately supported by only one set of guys placed at the top of the mast. Guy wires are fastened to the mast by guy rings or clamps, as shown in Fig. 3.

Guy-Wire Insulators

Place insulators in the guy wire, to break it into independent lengths which are not equal to, or any integral multiple of, the length of any single element in the antenna. This will prevent the guy wire itself from resonating at the frequencies for which the antenna is cut, thus eliminating the possibility of the guy wire re-radiating incoming signals and causing multiple images (ghosts) in the receiver.

Corrosion will greatly reduce the tensile strength of any metal. To prevent or minimize corrosion, it has been found advisable to clean each mast and paint it with at least two coats of aluminized radiator paint. Then, after installation, the mast is coated with grease. The same

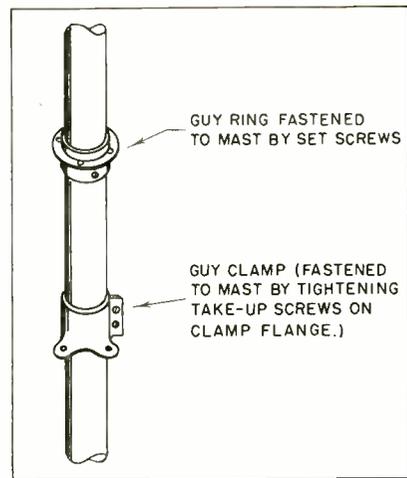


Fig. 3—Methods of fastening guy wires to mast, using either a guy ring or guy clamp.


paint and grease treatment will protect the rest of the antenna structure against the ravages of nature. The paint serves to protect the metal from corrosion and the grease helps to prevent the formation of ice. Ice loading on the antenna structure can increase tensile stresses and torque forces by two or three hundred percent. Since ice formation increases the overall antenna area, wind pressure effects increase by a like amount.

The mast and the antenna elements are usually tubular (hollow rod). The open ends of the units should be plugged with cork or rubber stoppers. Certain commercially-available masts are made of rolled-plate metal, which has been mechanically seamed to form a tube. These may be less expensive than the seamless-type mast, but they are much weaker, in the opinion of the writer.

To illustrate the desirability of closing off the mast ends, particularly when a seamed mast is being used, the following case history is presented. A seamed-tube mast was installed on an apartment-house roof in New York City. The mast top was not plugged, but the bottom was flush against the rooftop. Rainwater filled the mast and then froze. The expanding ice burst the mast asunder and the entire antenna collapsed.

In our next article, matching problems in antenna installations will be dealt with.

Fig. 2—A) Three sets of guy wires should be attached to an antenna when a large mast is to be reinforced. The solid-line wires illustrate the positioning of one wire in each set, when roof space is limited. Dotted lines illustrate guy-wire set-up when more roof space is available. Suggested angles for heights of $1/3 H$, $3/5 H$ and H are shown. B) Diagram indicating spacing of anchor bolts, when a group of 3 guy wires is connected to the mast. C) A 2x4 board nailed under the walls of a pitched roof maintains 120-degree spacing between guy wires.

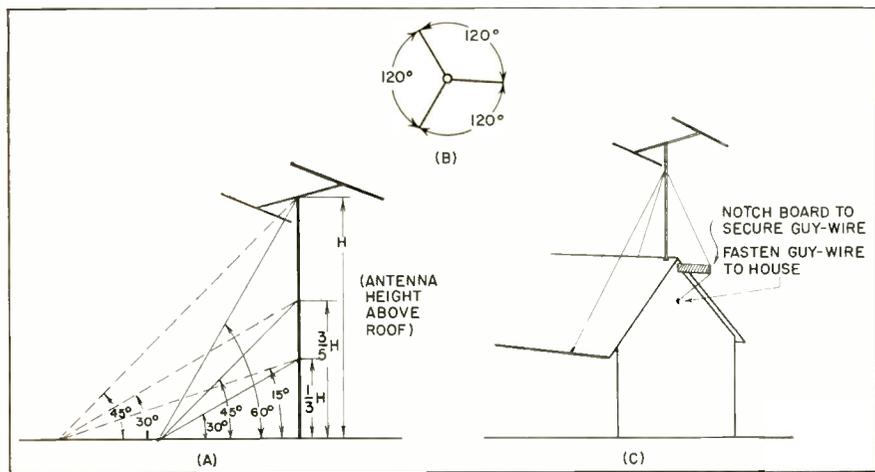

Troubleshooting Vertical

Fast Checks for Defective Tubes, Vertical Output Transformer,

By M. M. GERSHUNY

• The vertical deflection circuits of a television set are probably the simplest circuits to service in the receiver. There are usually only two stages involved, both of which are relatively uncomplicated. An understanding of some simple facts about these circuits should enable the technician to service them with a minimum waste of time and parts.

Possible symptoms produced by defects in vertical deflection systems may be classified as follows: 1. Complete loss of vertical deflection; 2. Insufficient height; 3. Foldover; 4. Loss of synchronization; 5. Distortion (non-linearity).

Although it is entirely possible that a single defect may cause more than one of the above symptoms to appear, it has been the writer's experience in the majority of cases that one symptom alone has generally had to be dealt with.

The vertical circuit shown in Fig. 1 is typical of many television sets in use today. Another circuit in common use is illustrated in Fig. 2. The troubleshooting suggestions for these circuits may be easily adapted to other similar ones.

Let us consider the first possibility, complete loss of vertical deflection. This problem involves two approaches. One is the procedure of the serviceman in the customer's house, carrying a minimum of test

equipment and parts. The other is that of the benchman who has a wide assortment of equipment and parts readily available.

The usual procedure in the customer's house is to check the tubes in the vertical circuits by substitution. Most cases of vertical trouble are due to defective tubes. In checking this circuit, it is desirable to replace both oscillator and amplifier tubes at the same time; if the trouble disappears, replace the old tubes *one at a time*. In this way, if both tubes happen to be defective, they will be quickly found.

Should the tube substitution test prove inconclusive, the next logical procedure would be a check of the height and vertical linearity controls. (Some servicemen might prefer to check the setting of these controls *before* substituting tubes—Ed.) Each of these controls should be turned from one extreme to the other, while the CRT screen is observed, to determine whether the control action is normal. It is not too uncommon to find that a defect in one of these controls is responsible for a loss of vertical deflection. The same is true, of course, of the vertical hold control. If one of the controls is found to be defective, an emergency repair can sometimes be made in the customer's home.

It will be found that, in most sets, potentiometers are used for vertical controls. Usually one side of the pot

will be tied to the variable arm, or left unconnected. If the wire on one end of the defective pot is transferred to the unused terminal, the circuit will frequently work quite satisfactorily. If the serviceman has an ohmmeter with him, this need not be a matter of guesswork.

Defective New Tubes

If the foregoing procedures do not bring desired results, the next logical procedure is to "pull" the chassis to the shop for repair. Once the chassis is set up on the bench, the experienced benchman will usually check the tubes again. All too often, the new tubes in the service kit are found to be defective.


While checking the tubes, the technician can also test the output transformer and yoke by rocking the output tube in its socket. If the disturbance makes the bright line on the CRT jump up and down (total loss of vertical deflection is assumed), these components are probably in good condition. If not, they should be first on your list of suspects.

The amplifier stage can be rapidly checked by placing a finger on its control grid. (Applying a 60-cycle hum signal through a .1 mfd condenser would be a safer procedure—Ed.) The easiest way to do this is to hold a long, thin screw-driver by the handle, placing one finger on the blade; the tip of the blade is then touched to the grid pin. The AC voltage picked up by your body is thus applied to the vertical amplifier; if the amplifier is functioning properly, some deflection will now be seen on the screen of the CRT. This will isolate the trouble to the oscillator, which can now be checked with a vacuum-tube voltmeter.

The typical vertical oscillator has comparatively few components, which simplifies the technician's job. Since the tube, vertical hold control and height control have already been tested, only a few components remain to be checked.

If the preliminary test indicates trouble in the vertical output circuit, simple voltage checks at the plate and cathode of the output tube will speedily indicate the source of the de-

Fig. 1—Typical vertical circuit using blocking oscillator. R-1 is height, R-2 hold control.

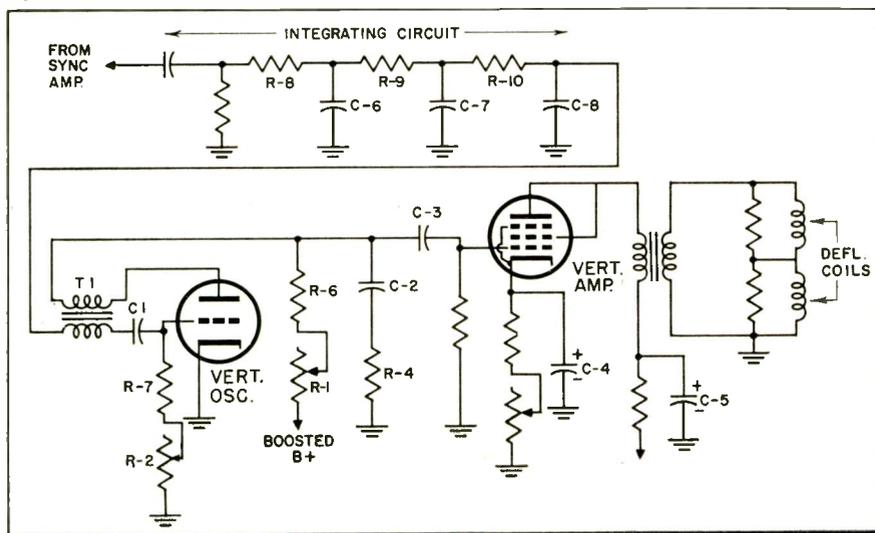

Deflection Circuits

Yoke, and other Components. Troubles, Tests.

fect in most cases. On the rare occasions that, by the process of elimination, the yoke becomes suspect, the writer has found that the best check is to substitute another yoke. If one of the correct inductance is not available at the moment, any unit can be used, provided that it is kept in the circuit only long enough to verify the diagnosis.

The problem of insufficient height has plagued the serviceman since the onset of television. This trouble has two variations. One is the condition in which, with height and linearity controls fully advanced, the picture does not fill the screen. The other is the less obvious but equally annoying condition of being able to fill the screen, but only by severely distorting the picture. (The writer has noticed that the average person is much more disturbed by vertical than horizontal distortion.)

Tube Substitutions

The approach to this problem can be split up into field and shop techniques. The field technician is limited, in the average service operation, to tube substitution. In addition to replacing the oscillator and amplifier tubes, the low-voltage rectifier tube or tubes should be replaced. If the set uses selenium rectifiers, these should be checked in the shop.

In some cases, where the amount of picture shrinkage is small, and ordinary substitution does not help, substitution of a different tube type may be worth trying. Types 6V6 or

6W6 have been successfully used in place of a 6K6 vertical amplifier to give just the extra bit of deflection needed. In circuits using a 6SN7 vertical amplifier, a 6BL7 has been used with good results.

This practice is desirable only in the field, in cases when the customer does not want to stand the expense of a shop repair. The set owner should, incidentally, be made aware of what has been done, and why. Over several years, the writer has never seen any ill effect resulting from this type of substitution. We must confess having encountered a small minority of cases where the method did not work.

If the problem proves too much for the outside serviceman, the benchman comes into the picture. He can simplify his problem by first inspecting a picture, or, preferably, a test pattern. The benchman will find that either the height control or the vertical linearity control will lack sufficient range to bring the picture into good linearity at the proper size. If the height control is found wanting, the trouble is most likely in the oscillator or the grid circuit of the output tube. If the vertical linearity control does not have enough range, the trouble is in the cathode or plate circuit of the amplifier.

A trouble commonly encountered is a leaky coupling capacitor (C-3, Fig. 1; C-71, Fig. 2). This defect usually causes a compression at the bottom of the picture, and possibly a short foldover. One very confusing problem can be caused by a defective C-1 (Fig. 1). The writer has seen cases where, with C-1 partially

shorted, the vertical sweep frequency went up to over 400 cycles per second. In addition to severe loss of height, the resulting jumble on the screen resembled a loss of horizontal sync. Only close inspection of the raster, showing uneven spacing of scanning lines, especially the oddly-rambling vertical retrace lines, gave a hint of the real trouble.


Vertical Amp. Tests

The output circuit of the vertical amplifier is best checked by substituting parts. The author does not recommend substituting parts from junked sets for test purposes. If the vertical output transformer is not a good impedance match between the amplifier and the yoke, adequate height may not be attained. In the case of permanent replacement, it is a false economy to use any but an exact replacement part.

In many cases, where the height is almost, but not quite satisfactory, replacement of the vertical amplifier's plate decoupling and cathode bypass condensers (after a bridging test) will bring it up to par.

Among the easiest symptoms to recognize are some of those produced by a defective yoke. When we have loss of height due to yoke trouble, a trapezoidal raster will almost always be seen. When one side of the raster is noticeably different

Fig. 2—Vertical deflection circuit using multivibrator as oscillator. Numbers at various circuit points refer to wave forms that appear at these points. Pertinent wave forms are illustrated in Fig. 4, on following page. Circuit is from an Emerson 120168-D television chassis.

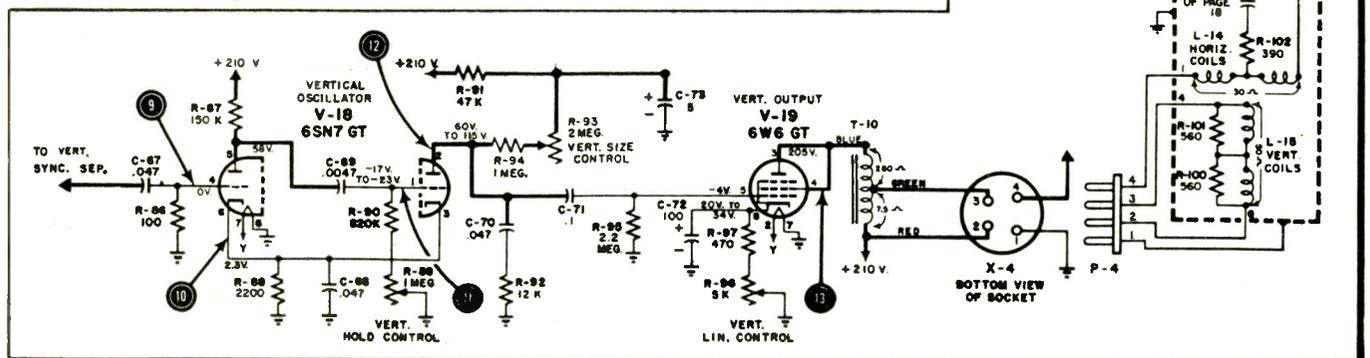

in size from the other, look no further; replace the yoke. (It would seem wise to check components in parallel with yoke windings, before condemning the yoke—Ed.)

Vertical foldover is caused by distortion in the vertical sawtooth wave applied to the deflection coils, or by a slow vertical retrace. In the first case there will be foldover at the bottom of the picture; in the second, a foldover will appear at the top. Bottom foldover can usually be cleared by replacing tubes. Sometimes, an improperly-adjusted vertical linearity control will introduce foldover; the condition is, of course, eliminated by proper control adjustment.

When vertical foldover seems present, the settings of all vertical controls should be carefully checked. Sometimes, when the vertical oscillator locks in at an incorrect frequency, the picture looks as though it has a bad vertical foldover.

Next to the tubes, the most common cause of foldover, in our experience, is a leaky coupling capacitor. Even when leakage in C-3 (Fig. 1) is so slight that a resistance of several megohms is measured across it, an annoying foldover at the bottom of the picture is apt to be produced. The best way to check this capacitor is to disconnect it at the grid of the output tube and measure for DC voltage between the open side of the capacitor and ground. With a good capacitor, the meter may fluctuate around some low reading, no higher than about three volts. A bad capacitor will cause an appreciably larger reading. A leak in the charge-discharge capacitor (C-2, Fig. 1; C-70, Fig. 2) can cause a severe compression at the bottom of the picture, resembling a foldover. This condenser may be checked in the same manner as the coupling capacitor.

Foldover at the top of the picture is relatively rare. It may be caused by an increase in the value of the peaking resistor (R-4, Fig. 1; R-92, Fig. 2), or a bad output transformer or yoke. Unfortunately many customers prefer to live with this condition rather than pay for its cure.

When the all-too-frequent complaint, "The picture jumps," is heard, the experienced technician goes to the customer's house prepared for anything, from fixing the antenna to suggesting new glasses for the customer. There is probably no other television defect with as many possible causes as unstable vertical hold. To mention just a few, this condition can be caused by electrical interference, incorrect antenna orientation, improper adjustment of the fine tuning control, and video IF misalignment. We will discuss only defects in the vertical circuits which may be the cause of this condition.

Vertical Amp. Tests

Under the normal operating conditions, in the case of most television sets, the vertical sync pulses are separated from the horizontal ones by a low-pass filter—the integrating circuit. These pulses are fed to the vertical oscillator, and lock it into synchronization with the corresponding oscillator at the transmitter. The normal or free-running frequency of the vertical oscillator should be somewhat less than sixty cps for optimum control by the sync pulse. The oscillator's free-running frequency is adjusted by the vertical hold control. The height control also has some effect on frequency; it should be possible to compensate for this effect by re-setting the hold control.

There are three possible conditions pointing to a defect in the vertical hold circuit. One would be the condition in which the vertical oscillator is not locked in. The hold control can be adjusted to approximately sixty cps, but the picture continues to drift up or down. A second condition would be where the vertical hold setting does not bring the oscillator close enough to sixty cycles to permit it to lock in. In this case, the picture can frequently be locked at a multiple of sixty cycles, or even at thirty cycles, depending on whether the frequency is too high or too low. The third problem exists when the vertical oscillator frequency drifts, requiring readjustment of the hold control; eventually,

the drift in frequency is too great for hold control re-setting to correct, and condition two results.

It should be immediately apparent that the vertical sync pulse is not reaching the oscillator in the first condition described. If the picture is not out of horizontal sync at the same time, then the likeliest place for the pulse to be lost is the integrator. Since the fault is a sync rather than a vertical circuit defect, we will not discuss it further.

For condition two—oscillator too far out of range—the oscillator grid components (C-1, R-7 and R-2 in Fig. 1; C-69, R-90 and R-89 in Fig. 2) are the ones to check, since they control the oscillator frequency. The technician should note whether the picture is rolling up or down. If the picture rolls *up*, the oscillator frequency is *less* than sixty cycles. If it rolls *down*, the frequency is *above* sixty cycles.

An increase in the time constant of C-1, R-7, and R-2 would make the oscillator frequency too low. This is commonly caused by an increase in the value of the resistor in series with the hold control (R-7, Fig. 1). Conversely, an increase in oscillator frequency would be caused by a *decrease* in the time constant just mentioned. This could very well be due to a loss in the capacitance of C-1 (Fig. 1).

Condition number three (drift) can usually be cured by replacing both C-1 and R-7 (Fig. 1). We have seen cases where a defect in the hold control was responsible for drift; this is, however, very unusual.

Distortion in the vertical direction is relatively rare. It can be caused by a defective vertical amplifier tube, or an open coupling capacitor. Strong hum in the B supply can cause apparent stretching and compression of the picture in the vertical direction. If the transmitter is powered from a different source than the receiver, the stretched and compressed areas will slide up or down, causing an effect like trick mirrors at a carnival. The open capacitor can be found, of course, by successively bridging the different electrolytics in the B supply.

Fig. 3—Normal waveforms and their amplitudes in a typical vertical circuit using a blocking oscillator. A—Grid of vertical oscillator (135v p-p) B—Plate of vertical oscillator (105v p-p) C—Grid of vertical output tube (105v p-p) D—Plate of vertical output tube (900v p-p) E—Cathode of vertical output tube (1v p-p). (Courtesy, RCA)


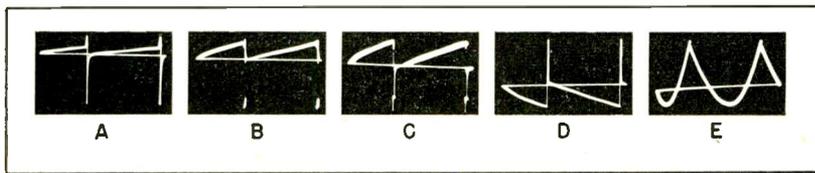


Fig. 4—Waveforms and their amplitudes in the circuit of Fig. 2 (preceding page). Numbers under the waveforms refer to the circuit points in Fig. 2 at which the waveforms were obtained.

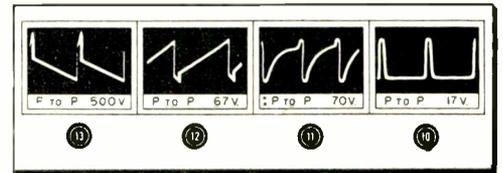

Vertical Circuit Troubles

Common Defects, and How They Affect the Test Pattern

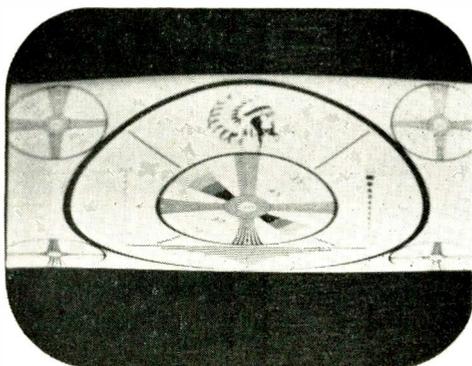


Fig. 1—Loss of height, vertical linearity poor. Possible sources of the trouble include: Low emission in the vertical sweep amplifier tube; insufficient signal input to this amplifier; defective sweep output transformer; insufficient B-voltage feed to the vertical amplifier; loss of capacitance in the vertical amplifier cathode bypass condenser.

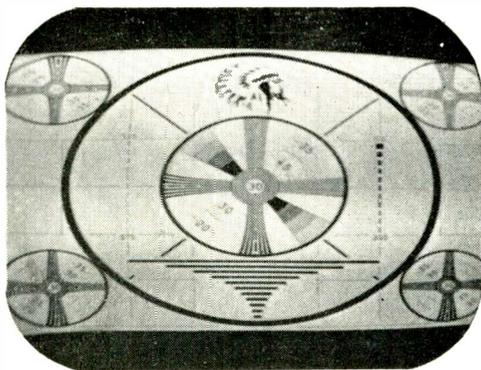


Fig. 2—Insufficient picture height, vertical linearity approximately normal. Possible sources of trouble: Loss of emission in the vertical oscillator or sweep amplifier; increase in value of oscillator (multi-vibrator) plate resistor; defective vertical output transformer; improper plate or grid voltages on output tube; loss of capacitance in the vertical amplifier cathode bypass condenser.

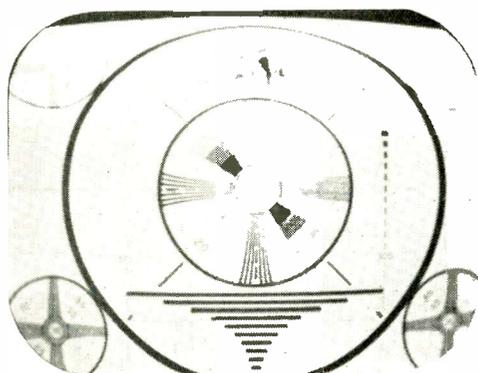


Fig. 3—Poor vertical linearity; height can be adjusted satisfactorily. Possible sources of trouble: Improper setting or defect in linearity control potentiometer or other linearity circuit components; vertical amplifier tube may require replacement; loss of capacitance or leakage in the cathode bypass condenser of the vertical amplifier.

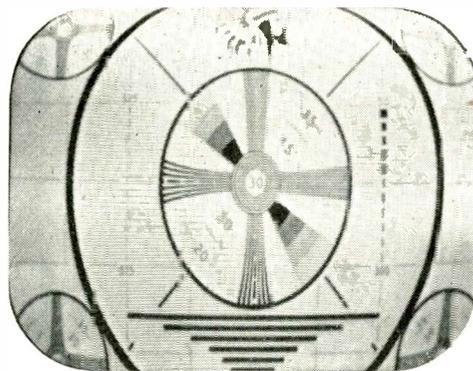


Fig. 4—Excessive height. Usually caused by excessive "drive" at grid of vertical amplifier. Check for decrease in value of charge resistor in plate circuit of vertical oscillator; reduced capacitance in charging capacitor; defective height control.

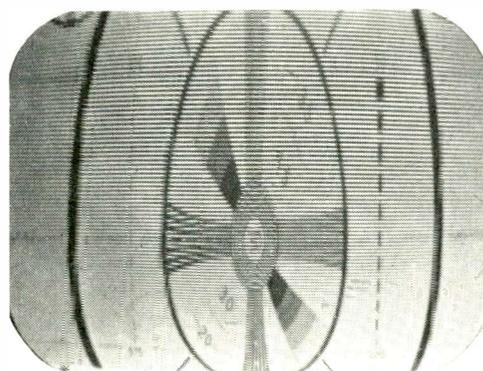


Fig. 5—Excessive height, vertical linearity poor, foldover at bottom of raster. Possible sources of trouble include: Leakage in the coupling capacitor between the vertical oscillator plate and amplifier grid; loss of capacitance in the oscillator's charging capacitor.

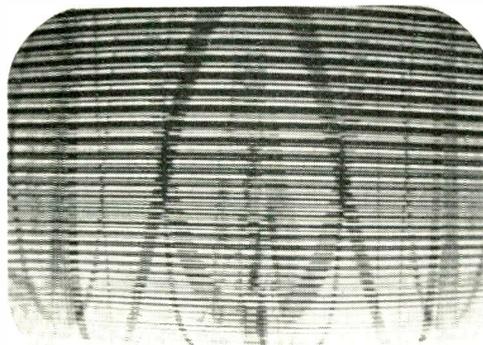


Fig. 6—Excessive height. Sweep is so great that the horizontal scanning lines are pulled apart. Severe leakage in the coupling condenser between vertical oscillator and amplifier may cause this.

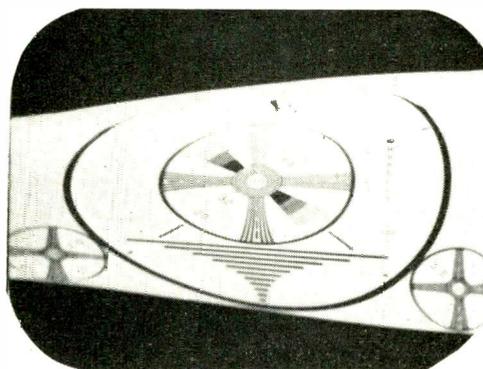


Fig. 7—Vertical keystone effect. Possible trouble sources: Change in value of a shunt resistor across one of the vertical yoke coils; shorted turns in vertical yoke. (Photos on this page courtesy GE; captions based on GE text.)

Color vs BLACK & WHITE

Block Diagram of First Color Set. Similarities and Differences

BY PETER W. ORNE

• In this article we will consider the block diagram of the NTSC color television receiver and discuss the functions and purposes of the new circuits. Future articles will consider these circuits in greater detail. It might be added that the receiver under discussion is the equivalent of the famous RCA 630 black and white chassis. Like the 630 chassis, this receiver is designed to take as much advantage as possible of the capabilities of the system. It should be kept in mind that present-day monochrome receivers do not follow the 630 design, and it is likely that there will be many short-cuts introduced in later color receivers. This prototype is expensive and good, its main purpose aimed at getting customer acceptance of color.

Comparing Figs. 1a and 1b, the sectional block diagrams of a monochrome and an NTSC color receiver, respectively, we find a num-

ber of similarities. Note that all the sections used in the monochrome receiver are also necessary in the color receiver. It should be understood that the sections are *not* the same in circuitry; the fact that they serve the same functions, however, is important to remember for servicing. This is so because symptoms produced by defects in various sections of the color receiver will be similar to those produced by comparable faults in the corresponding sections of a black and white set.

Service Predictions

The reader will note that the color receiver has a number of sections that have no parallel in the black and white set. Furthermore, the sound signal is taken off at a different point, in a way similar to the one used in older split-sound receivers.

It may be interesting to give service-wise consideration to some


of the familiar-looking color TV sections, and try to predict the symptoms that would be produced by a dead stage in these sections. We will do this from time to time as we proceed.

Since the front end of the color receiver is very similar to that of the black and white set, a dead stage in either set's tuner section will tend to eliminate or severely attenuate picture and sound, without affecting the raster. Trouble in the video IF section of each set will similarly tend to produce corresponding sets of symptoms.

The color receiver's IF system is somewhat different from the one present in the black and white set. Color information is transmitted interleaved with the high video frequencies; the frequency response of the color receiver's video IF stages should therefore be the full 4.2 mc transmitted, if a good color picture is to be reproduced.

The color receiver's video detec-

Fig. 1—A) Sectional block diagram of monochrome receiver. B) Page opposite—Block diagram of NTSC color receiver. Note the similar blocks.

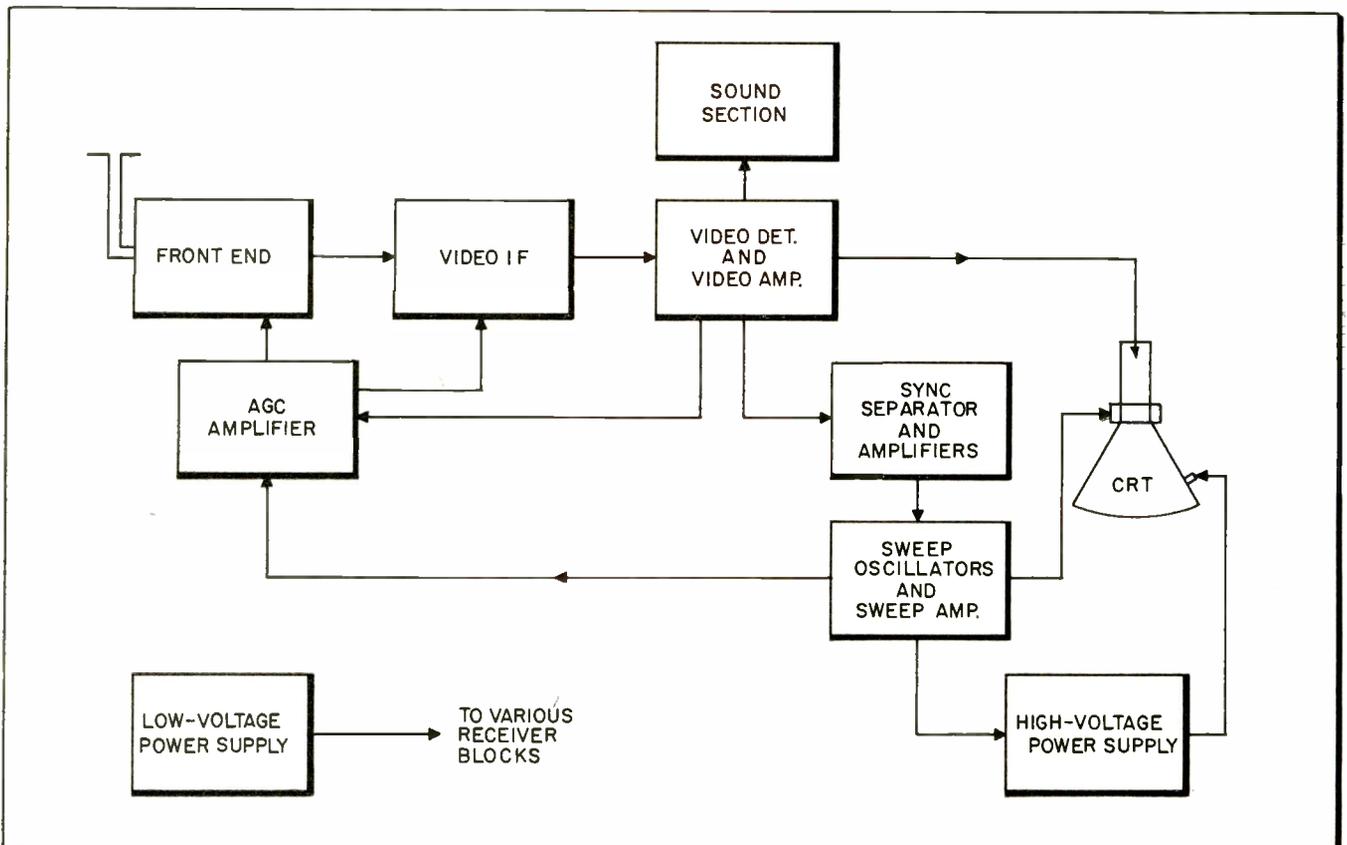

TV Receiver Circuits

Between Monochrome and Color Chassis. Sectional Troubles

tor should be as linear as possible. This necessitates a relatively large output from the IF section. As a result of these considerations, the IF system in the color receiver contains five stages, compared to the corresponding three or four stages in a monochrome set.

The wide frequency response of the video IF stages in the color receiver necessitates the incorporation of a very efficient sound trap. The trap is needed to eliminate the 920 kc beat that tends to be produced in the video detector by the heterodyning of the sound carrier and the color subcarrier.

To prevent such a beat note from producing an interference pattern on the screen, there must be very little or no sound signal present in the video detector. The sound signal is, consequently, taken off at some

point in the video IF section (rather than at the video detector or amplifier) and fed to the sound stages. A sound rejection trap is present in the last video IF stage, to insure against the presence of an appreciable sound signal in the video detector.

Sound Section


We should point out that it is not the sound signal alone that is taken off in the video IF section; a portion of the sound and video signal is removed, for application to the sound section. This is done to permit the advantages of intercarrier operation to be obtained—i.e., good tuning, better stability, etc.

Two detectors are required in the sound section. The first one operates like the video detector in a black-

and-white intercarrier set, converting the high-frequency sound IF signals down to 4.5 mc. The other detector removes the modulation from the sound IF signals. From this point on, the sound stages in the color and black and white receivers are practically identical.

We may point out that, in the intercarrier set, the symptoms *no picture, no sound, good raster* indicate the presence of trouble in the front end, or the video IF, video detector, or video amplifier stages. In the color receiver, on the other hand, the same set of symptoms points to trouble in the front end or video IF section only, since neither the video detector or amplifier affect the sound.

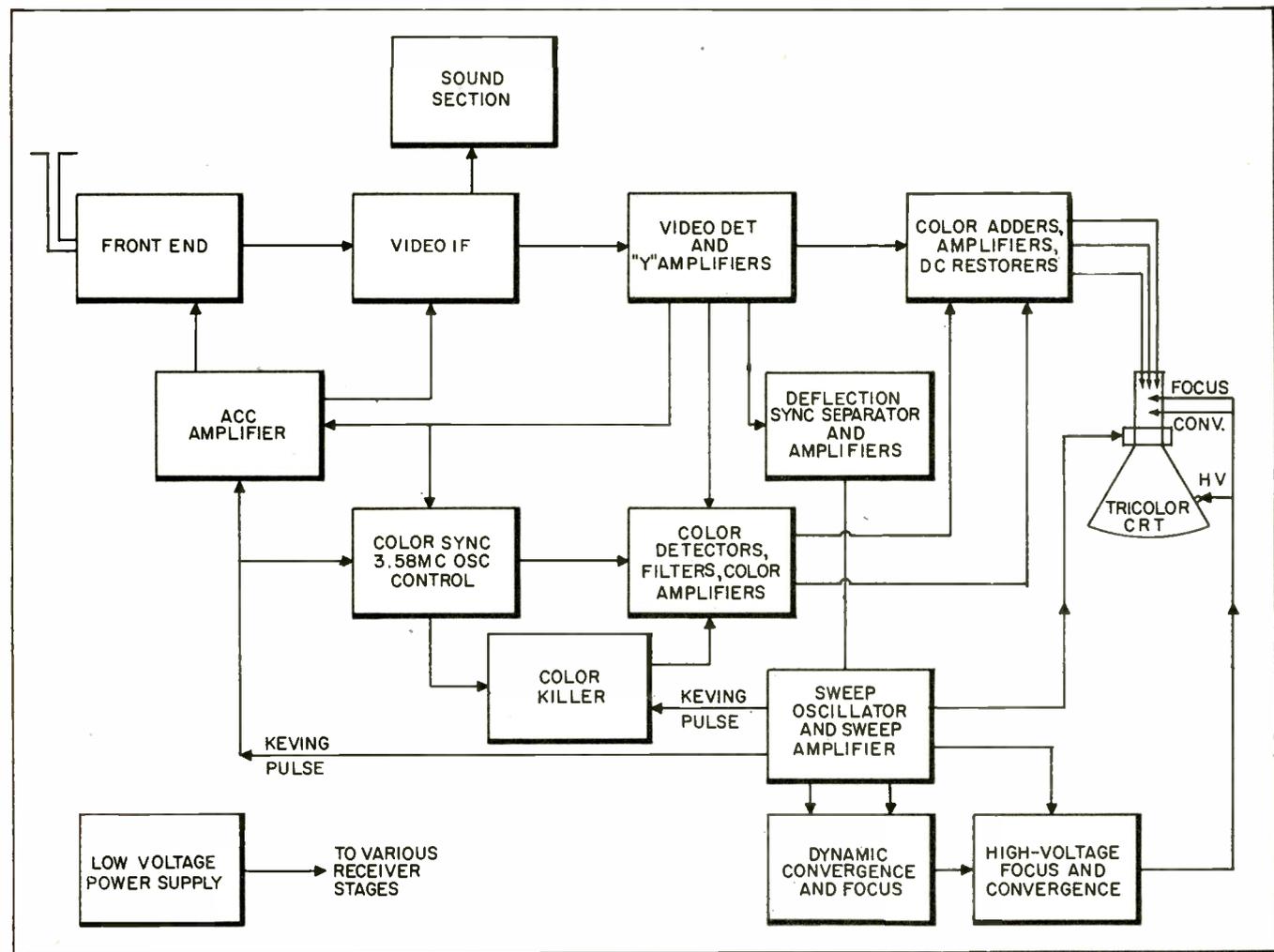The video detector and "Y" amplifiers correspond to the video detector and video amplifier sections in the monochrome receiver. The



"Y" signal is the luminance information of the color signal—that is, it contains information regarding the brightness of each pictorial unit. This "Y" signal is, incidentally, the only one of the several video signals present in the color transmission that a monochrome set will also respond to, and is equivalent to a monochrome video signal.

The only difference between the video amplifiers in the color set, and the ones used in the monochrome receiver, lies in the better linearity of the color set's video amplifier. By linearity we are not, of course, referring to deflection linearity, but the faithfulness with which the output signal reproduces the input one. Any non-linearity (i.e., any deviation from Class A amplifier operation) will tend to cause cross-talk or interaction between chrominance or color information, and "Y" or monochrome signals. This cross-talk or cross-modulation will severely affect the reproduction of color on the CRT screen. Whereas in a monochrome receiver, video amplifier non-linearity that causes cross-talk (between video and

sound signals, or between different video signals) tends to introduce an almost unnoticeable fine interference pattern, in the color receiver the picture is far more visibly affected, since the colors deteriorate. More than one video amplifier is necessary in the color receiver, because of signal losses in various circuits.

From the video amplifier, signal is fed to the sync separator, which is the exact equivalent of the corresponding sync stage in the monochrome receiver. Just as in the monochrome receiver, many different sync circuits may be present. Symptoms such as picture rolling, tearing, or both will have similar sources in both the monochrome and color receiver.

The *Deflection Sync Separator and Amplifiers* block corresponds to the *Sync Separator and Amplifiers* block in the black and white receiver. The word *deflection* is used in front of *Sync Separator* to differentiate this sync section from the color sync section.

The sweep sections of the color and monochrome receivers are very

much alike. The vertical oscillator and amplifier, and the horizontal oscillator stages, are or can be identical. The horizontal output stage is similar in both receivers; in the color receiver, however, better linearity is demanded of this stage. This is so because the necessary convergence of the three electron beams exciting the red, blue and green phosphors cannot be obtained over the length of a horizontal line if the linearity is not good; improper color reproduction will be produced in such a case. This business of convergence will be treated in detail a bit later. Because of the more stringent linearity requirements, components in the sweep section such as the yoke, vertical and horizontal output transformers, and width coil differ in design from corresponding units in black and white sets.

Keying Pulses


Keying pulses are derived from the horizontal sweep section which are used in a number of circuits in the color receiver. The keyed AGC system, which uses one of these pulses, employs it in the same manner as the corresponding system in a monochrome set. The keying pulse applied to the block labeled *Color Killer* will be discussed later.

We can take a breath at this point and consider some familiar symptoms that will be produced in a color receiver by failure in some of the sections we have been discussing. An inoperative vertical sweep stage will produce a horizontal line; a defective horizontal sweep will eliminate the raster (since a kickback type high-voltage power supply is used in the color receiver); an improperly-functioning AGC system will tend to introduce buzz and poor or no syncing of the picture (as well as contrast troubles, negative pix, etc.).

Considerable differences are present in the color receiver's kickback high-voltage power supply (as compared to the monochrome set's HVPS). The regulation of the color receiver's HVPS must be very good—i.e., the high voltage must remain constant or unchanging. This is so because the cathode-ray tube requires a constant high voltage to provide correct coloring and brightness to the picture. This constancy must be maintained in the presence of, or in spite of, brightness level changes.

In the monochrome receiver, a change in brightness tends to cause a change in picture size. The high voltage rises when the brightness is reduced (due to reduced loading on

Fig. 2—RCA tricolor three-gun kinescope. A part of the metal shell is cut open to show the internal assembly of the phosphor-dot plate and shadow mask. The gun mounting supports and connecting wires have been omitted. For a more accurate sketch of the shadow mask, see Fig 3.

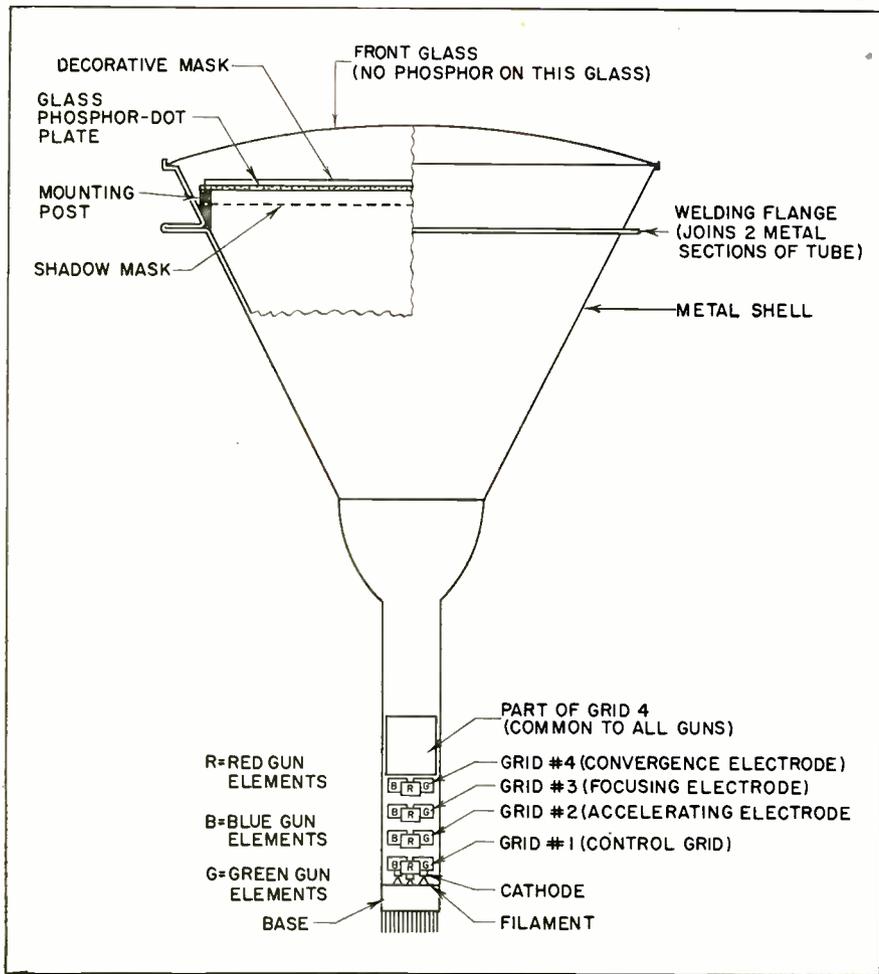

ne HVPS), causing the picture to shrink. The reverse happens when the brightness goes up. While such effects are hardly noticeable in a monochrome set, they affect a color picture very seriously. This is so because the correct rendition in color of one pictorial unit depends on the impingement on the CRT screen of three correctly-oriented electron beams. If the raster size changes, the points struck by the beams change as well, and proper color reproduction thus fails to result. The color receiver's focus must, consequently, be a focused one.

High Voltage Focus and Convergence section supplies the tri-cathode-ray tube with the correct voltage required for correct beam operation. The 2nd anode voltage is about 20 kv; focus voltage, approximately, to chassis) to form a correctly-sized spot on the screen. The convergence electrode (which is at a potential of approximately to chassis) focuses the three color beams concentric to one point on the screen. The focus electrode draws appreciable current, a single hv rectifier is not sufficient to supply its current as well as those of the hv section; a separate rectifier is used before the focus circuit. The low-voltage power supply in a color receiver differs from the one employed in the monochrome set in that it delivers a higher output voltage and more current. The higher voltage is required mainly to provide a more linear sweep system. (The greater the voltage applied to a sweep amplifier plate, the

less is the plate current required for the same watts output. A smaller plate current means that the tube will operate on a smaller part of its Eg- I_p characteristic, avoiding the extreme or non-linear part of this characteristic. A more linear output is thus possible.) The larger current-handling ability of the low-voltage power supply is needed because of the greater number of tubes used in the color receiver. An inoperative low-voltage supply will, of course, result in no raster and sound in the color receiver.

Color Tube

To understand the functions of color receiver sections that have no equivalent in the monochrome set, some understanding of the color CRT is necessary. Many different types of color tubes are currently being experimented with. The only one that will be discussed here is the RCA tricolor kinescope, since the NTSC receiver is really built around this CRT. Fig. 2 shows some constructional features of the tube.

The tube contains three electron guns, one for each "primary" color: red, green, and blue. In the front of the tube there is a flat glass plate on which an orderly arrangement of red, green, and blue phosphor dots is deposited. Three dots—one of each color—form a triangle; about 195,000 such triangles cover the viewing area in the tube.

The latter is a 16-inch metal-shell round tube; its viewing area is about 11½ by 8½ inches. Behind the phosphor-dot plate there is a shadow mask with as many holes as there are dot triangles. The

shadow mask is so arranged with respect to the three guns and the phosphor dots that the beam from each gun can only strike a phosphor dot of its own color. This precision set-up indicates why a high degree of accuracy is required in the yoke, and the high voltage and focus supplies; any variation in the focusing or direction of the beam may cause it to hit the wrong color spot. To avoid stray magnetic fields from affecting the beams, a magnetic shield is placed around the tube's metal cone.


We may point out, in passing, that an improper yoke adjustment may produce not only neck shadow, or a tilted picture, but also improper color reproduction. The last-named fault is due to the fact that the yoke determines the starting point from which the beams are reflected; a change in the starting point may cause the beams to hit the wrong-color phosphor dots.

The construction of the tricolor CRT is the reason for the presence of the section in Fig. 1b labeled *Dynamic Convergence and Focus*.

The need for and function of this section may be explained as follows: Because of the flatness of the color dot plate, the distance from each gun to the center of the plate is shorter than the distance to the edges. Now, a focus voltage that assures proper focus at the center will not provide it at the ends of the plate, under such conditions. An additional potential must therefore be introduced, to provide suitable compensation.

The principle is similar to the one (Continued on page 62)

Fig. 3—Detailed sketch showing how the beam from each gun can only hit a phosphor dot of its own color when the tube has been properly adjusted. High adjustment accuracy is obviously vital. X, Y, and Z indicate points where deflection begins for each beam.

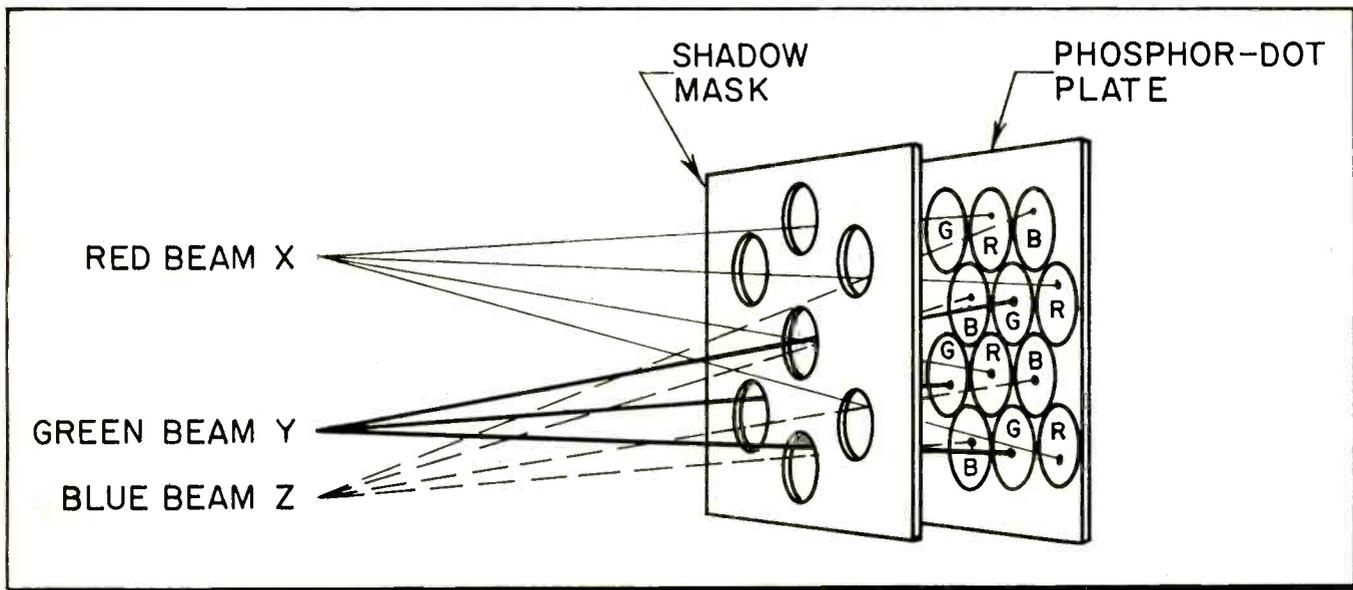

Servicing Phono Motors

Wow, Rumble, and Scraping Problems in

By HARRY MILEAF

• In a preceding article, we discussed the overall Hi Fi system. This piece will confine itself to one element in that system: the record player.

The record player is primarily a mechanical device. It is more important to prevent the introduction of noise and distortion at the record player than in any other part of the overall audio system. This is so because distortion or noise developed at the player passes through the entire system and is greatly amplified; more so than the distortion or noise that is developed at any other point in the audio system. The chief troubles that develop at the player are wow, rumble, and scraping.

The basic parts of the record player are: 1—The motor. 2—The drive assembly. 3—The turntable. 4—The pickup arm and cartridge. The last-named units will be discussed in another article.

The Motor. Noise and distortion can be developed by the motor in many ways. If the armature (see Fig. 1) is not seated properly in a vertical position, it will rub against the field poles. If it is only slightly off the vertical plane, it may merely cause a scraping sound to be audible. If the armature is too far off, however, and there is too much pressure applied to it by the field poles, the speed of the armature will decrease, possibly causing wow;

or the armature may not turn at all.

Ordinarily, this condition is brought about when the screws holding the bearing bracket have worked loose. The trouble can easily be remedied by shifting the position of the bearing bracket (while rotating the armature) until the armature rotates freely. Hold the bearing bracket in this position and tighten the bracket screws, to complete the repair.

If the bearing portion of the bearing bracket wears too much, the armature will tend to vibrate from side to side, introducing excessive noise. A worn bearing can easily be located by inspection. The only remedy for the condition is replacement of the bearing bracket.

Armature Vibration

Armature vibration can also occur in the vertical direction. This condition is brought about by worn, bent or broken washers (see Fig. 1). The purpose of the washers is to hold the armature firmly in position and prevent it from bobbing up and down. If any of these washers are bent, broken, or missing, the armature will tend to vibrate and cause noise. The washers referred to usually snap into grooves that are cut around the armature shaft. On some motors, the armature is held in place by the front and rear of the armature itself; there are usually a number of "shim" washers between the armature and the bearing

bracket, to hold the armature in position as firmly as possible.

Phono motors require lubrication periodically, not only to prevent unnecessary wear on the armature and bearings, but to keep the armature as free-running as possible. If there is a lack of lubrication at the bearings, the armature shaft will tend to bind. The extra pressure exerted due to the lack of lubrication tends to slow down the motor and may cause wow. A light grease should be used for lubricating purposes; oil splatters and is easily lost. A heavy grease tends to slow down the motor, and should not be used for this reason.


The phono motor may develop a high resistance in its windings, or a low magnetic field, causing it to slow down. The only remedy for such a condition is to replace the motor. Use only a direct factory replacement. This is necessary because the diameter of the motor drive shaft helps determine the speed of rotation of the turntable.

The Drive Assembly. The drive assembly is generally the most troublesome section of the record player. The purpose of the drive assembly is to couple the motor drive shaft to the turntable, and keep the turntable rotating at a proper, constant speed. Never apply oil or grease to the drive assembly. This unit depends on friction for its proper operation; the application of a lubricant will cause slipping, and may result in the turntable not rotating at all. Fig. 2 illustrates a basic one-speed drive assembly.

The drive wheel has a rubber tire that is the coupling surface between the motor drive shaft and the rim of the turntable. This rubber tire develops various defects that affect the operation of the record player. In its normal condition, the tire provides friction and is perfectly round. If either one of these characteristics changes, noise, or wow due to slipping, may result.

The rubber tire is so constructed that it provides good traction at the rim of the turntable. If the outer edge of the rubber tire becomes excessively smooth, it will slip and cause the turntable to rotate at a slower speed, or possibly not at all. After the rubber tire is in use for a

Fig. 1—Shaded 4-pole squirrel-cage phonograph motor. If this assembly is not properly seated in the vertical direction, correct turntable speed will not be obtainable.

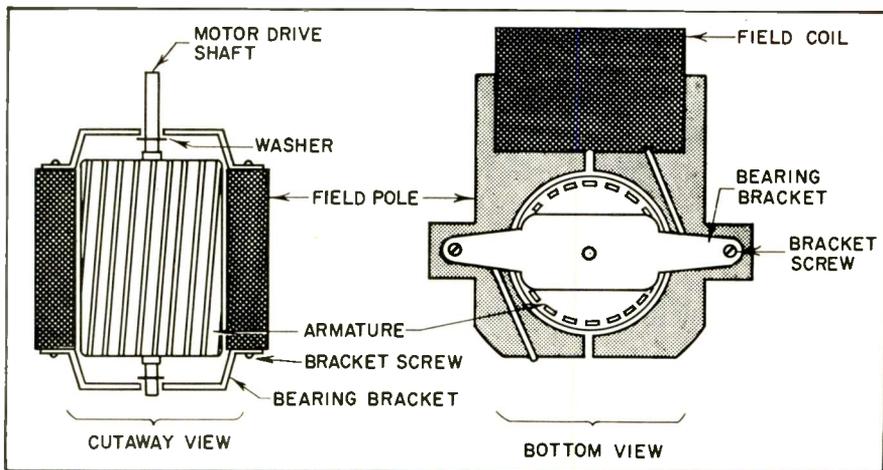

and Drive Assemblies

Single-Speed and Three-Speed Record Players.

while, it may wear irregularly and develop flats or indentations (see Fig. 3A). This condition will cause a thump or rumble whenever the tire comes in contact with the motor drive shaft and the turntable. Fig. 3B shows how the rubber tire may be removed from the drive wheel.

If the drive wheel binds on the drive wheel shaft, it will cause the turntable to rotate slowly or not at all. Lubricating the drive wheel shaft will ordinarily prevent this. Care must be taken, when applying the lubricant, to prevent the latter from coming in contact with the drive wheel rubber surface.

Slipping may also be caused by a weak drive wheel spring. The purpose of the spring is to pull the drive wheel tightly against the turntable rim. A weak spring will cause the drive wheel to slip, resulting in the turntable rotating slowly or not at all.

The purpose of the cotter pin is to prevent the drive wheel from rising. If the cotter pin is missing, the drive wheel will be pushed up, causing it to rub against the underside of the turntable.

A 3-speed record player system is shown in Fig. 4. The basic difference between a 3-speed and 1-speed player lies in the use of three idler wheels in the 3-speed unit (one for each speed). When the control arm is moved to the speed position desired, the idler wheel for that speed is moved between the motor drive shaft and the drive wheel. The three-speed record player is subject to the same troubles as the single-speed unit. The lower section of the idler wheels are rubber-rimmed, and develop the same defects drive wheels do.

The Turntable. The turntable has definite requirements to fulfill, to provide adequate operation. It must be flat, parallel to the mounting board and able to rotate freely; it should also grip the record being played.

If the turntable is warped, the record being played will wobble, causing the pickup needle to skip and jump grooves.

If the turntable is not parallel to the mounting board, it will prob-

ably come in contact with the mounting board, resulting in scraping. This turntable scraping is usually the result of the spindle not being prop-

erly seated in a vertical position. A simple bend-adjustment can easily remedy the condition.

The turntable center-hole can

Fig. 2—Single-speed drive assembly. The drive wheel makes contact with the turntable rim.

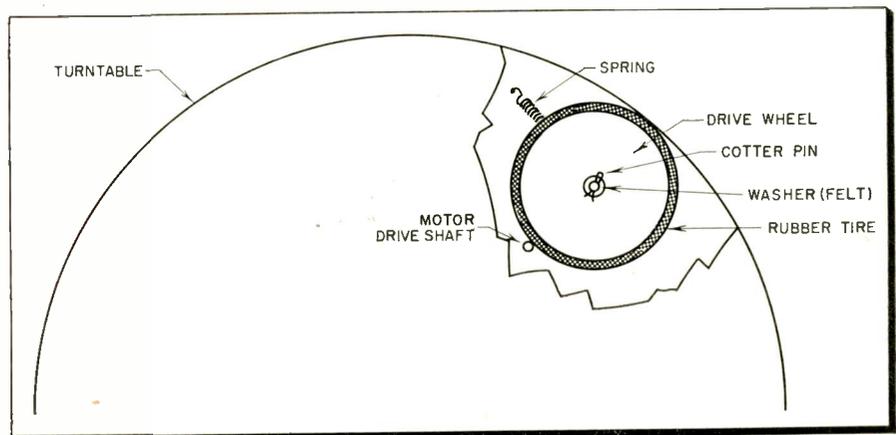


Fig. 3A—Flat and indentation on drive-wheel tire. B—Removing tire from drive wheel.


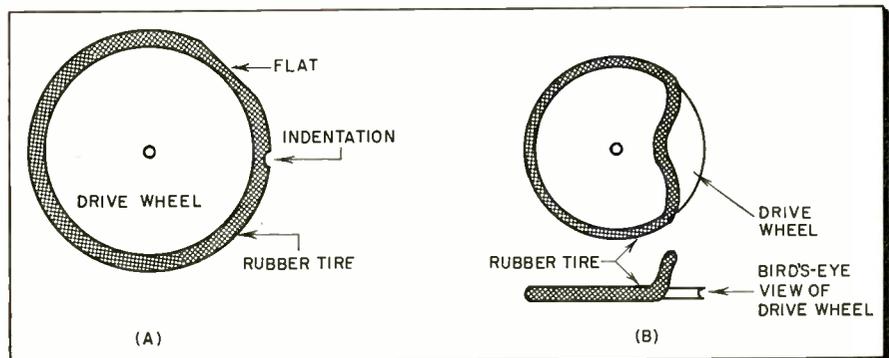


Fig. 4—Three-speed drive assembly showing separate idlers mounted on selector lever.

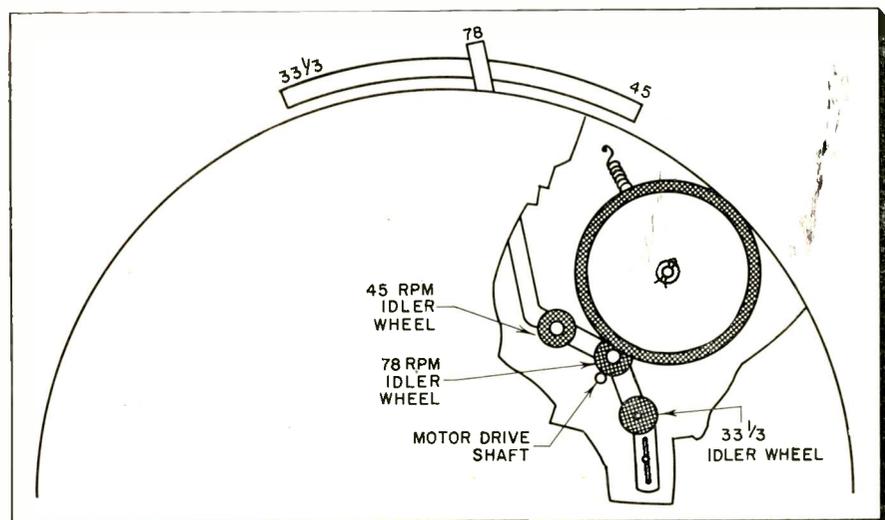

become enlarged due to wear, causing the turntable to rest too loosely on its support; the turntable will tend to slant and scrape the mounting board in consequence. If the spindle wears excessively, a similar condition will be produced.

In some cases, the turntable may show a tendency to bind on the

spindle, causing it to slow down or jam. Applying grease to the bearing portion of the spindle will solve the problem in most instances. If it does not, the spindle or the center-hole of the turntable should be smoothed down with emery cloth.

The turntable must "grip" the record, so that the latter turns at

the exact same speed as the turntable. If there isn't enough grip, the weight of the pickup arm will cause the record to slip, producing wow. This grip is brought about by the flock (furry substance) that is sprayed over the top of the turntable. If the flock wears off, the turntable should be re-flocked or replaced.

Sometimes mechanical noises, referred to as rumble, are too slight to be heard at their point of origin; when transferred to the pickup cartridge and amplified, however, they become annoyingly noticeable at the speaker. The presence of rumble may be checked for as follows: 1—Set the record player in operation. 2—Place the pickup arm on the run-off grooves of the record. 3—Turn up the volume only so far that the surface noise of the record is barely noticeable. 4—No rumble should now be heard.

It is important to note that the size of the various parts of the record player helps determine the speed of rotation of the turntable. Because of this fact, the identical replacement parts supplied by the player manufacturer should be used.

Service's Advice to Mfrs.

1. Use self-tapping screws or similar units in mounting transformers, large resistors, and other items that are very likely to burn out. Do not use rivets to fasten such items to the chassis.

2. Do not place parts in such positions that it is necessary to disconnect several components to get at the defective one.

3. Do not use filter capacitors, or other components that have more than three separate sections enclosed in one envelope.

4. In the case of condensers intended for use in semi-tropical states, by all means use plastic moulded paper capacitors in place of the wax-sealed cardboard tubular variety.

5. If you manufacture a set whose components are unlikely to be stocked by distributors in most TV cities of the country, use major components (such as power and other transformers, focus units, yokes, etc.) that are generally available at local distributors. In your service information, present cross-references indicating the "substitute" part that may be purchased, when the original replacement is unavailable.

6. Do not use an unplated steel chassis if you expect your television set to last a few years in a damp climate.

Little Stories of Servicemen's Success

Shop-on-Wheels Pays Off in Florida



"Eight years ago I got tired of fighting frozen radiators, sleet, snow and cold, and fled to the sunny sands of Florida. We had no TV here then, but everyone had a radio. Not having too much money, I purchased a house-car trailer, sixteen feet long for \$50 down and \$50 a month. I proceeded to set up a Radio Shop-on-Wheels, all repairs made right at the customer's home. Of course, the repair work was done in the trailer, where I had a bench, test equipment and power supplied by a 150-ft. extension, which was on a reel and plugged into the customer's line," begins a letter to **TECHNICIAN** from Carroll S. Shaw, 5814 Hallendale Beach Blvd., Hollywood, Fla. He continues:

"Being the father of four children, I had to make money. My plan was ridiculed by all competition, the argument being you can't make money unless you pull the set into the shop.

Expansion a Mistake

"All work was secured by a direct house-to-house canvass. This only lasted about two months, after which time my recommended business became so great that I did no more canvassing. Then I started to expand. I bought another trailer and hired a service-man to run it. This was mistake No. 1. I could go out in the trailer and clear from \$100 to \$300 a week, but the employed man usually turned in only about \$30 a week. I changed men three or four times. It always worked out the same—no business from the hired man—while the trailer I ran still paid off beautifully.

"A customer would call up and complain—the set you fixed doesn't work—and after looking through the files, I would find no card on that job. Upon investigation I found the service-man had fixed this set and many more and

put the money in his pocket—thus no business. I solved this problem by hiring older men, men over fifty with no radio experience but with sales experience. They solicited the business in the same trailers and brought it into the shop. The shop-man fixed it. I priced the job, and the trailer operator took it back.

"This operation worked out very good. I finally sold the whole business, which at that time was comprised of two stores, five trucks and trailers, three shop-men and one secretary.

Back to One-Man Operation

"A year ago I moved from Miami, Fla., to Hollywood, Fla., a small town of some 10,000 population, and in less than six months of operating a complete Shop-on-Wheels, with my wife taking the phone calls and my doing all my own repair work, I had to start turning down business. I now have more than I can do. I get very good prices for my work.

"I believe I have the most honest operation in the country. If the customer wishes, I have a nice soft seat in the truck so he or she can sit and watch me repair the set. Ninety-eight percent of all work is done on the job. I rarely pick up a set.

"Today I do not take on many new customers, because I cannot handle them. My customers are so happy with the speed of the service and so confident in the honesty of this operation that they rarely ever question the price on any job I am called in on.

"All work is C.O.D. I sell no sets. I specialize in service. I have whipped the big overhead problem. My only expense is phone and truck maintenance.

"My twin boys, aged 15, help on Saturdays and after school, putting up aerials and repairing AC-DC sets. TV Service, believe me, can be a very lucrative business."

COLOR SHORTS

THIRTEEN DIFFERENT color-TV receivers built independently by as many competitive manufacturers, gave a 100% performance on the new NTSC color-TV standard signal at New York, October 15th. The two-hour test demonstrated that color TV is here as a practical workable service, as soon as approved by the FCC commissioners who, with 500 other industry leaders, watched the presentation. FCC members revealed themselves as greatly impressed, indicating that official approval will come quickly, and that color-TV will soon be a commercial reality.

COOPERATING in the October 15th demonstration besides the CBS, DuMont and NBC broadcasting stations, were Admiral, CBS-Columbia, Crosley, Emerson, GE, Hallicrafters, Hazeltine, Motorola, Philco, RCA, Sylvania, Westinghouse and Zenith.

NTSC CHAIRMAN BAKER said: "Let me emphasize that the equipment at the studios and at the transmitters, and even more important, the receivers which you see in front of you, represent individual designs of individual companies. There has been no pooling of apparatus know-how—instead, there has been only the strongest possible incentive for the development of competitive individual apparatus designs. And that incentive will continue and reach new heights, should the Commission proceed to the adoption of these proposed standards. The Commission will not, of course, by such action be approving or disapproving particular apparatus; just as

the NTSC today is not indorsing or withholding indorsement of individual apparatus. The apparatus is here in order to establish that the companies in this industry are capable of originating and transmitting successfully the signal described by the NTSC in this pending proposal; and similarly, that the companies in the industry can successfully develop receivers capable of receiving this color transmission in color, and, furthermore, without making any changes whatsoever, of receiving a monochrome transmission in monochrome. Finally, there are receivers, similarly representing designs of individual manufacturers, which are here for the purpose of demonstrating that the color transmissions under the proposed standards result in satisfactory monochrome pictures on existing monochrome receivers."


"THESE TV STANDARDS" Dr. Baker continued, "are the culmination of over a million engineering man-hours, and therefore cannot be evaluated on the basis of a single 70-minute showing." "All of us associated with this demonstration," Dr. Baker said, "have confidence in the basic soundness of the proposed technical transmission standards."

FCC REPS at the Oct. 15 demonstration included Chairman Rosel Hyde and Commissioners Frieda B. Henock, Edward M. Webster, Robert E. Lee, John C. Doerfer, George E. Sterling, Robert T. Bartley. Other staff members attending were: Curtis B. Plummer, chief BC bureau; Arthur Scheiner, rules and stand-

ards division; Sol Schildhouse, acting chief, Division of Operations; Hart S. Copperthwaite, chief of the Technical Branch, TV Facilities Division; Edward W. Chopin, chief labor division, office of chief engineer; William C. Boese, chief of Technical Research Division, office of chief engineer; Wilar Roberts, Labor Division; Warren E. Baker, general counsel, and George O. Gillingham, Chief of Information for the FCC.

MUCH INTEREST was shown in the new CBS-Hytron structural modification of the RCA-Goldsmith mask-type color tube, greatly reducing picture-tube weight and cost. Despite earlier difficulties, the CBS tube worked very well on the NBC color signal, and industry observers heretofore skeptical of color-TV's immediacy, opined that the CBS tube might soon bring 21-inch color sets to a \$400 price level, instead of the \$800 price heretofore generally predicted.

DU MONT'S color-TV equipment used in presenting the UHF color demonstrations was developed by the company's Research Division under the supervision of Dr. Thomas T. Goldsmith, Jr., director of research. To present the UHF color signals during the demonstration, two DuMont Universal color scanners were used to reproduce pictures from the selected color slides. Operating on the principle of flying spot scanners, the color scanners pick up the pictures in green, red and blue channels, feeding them to a color encoder. This unit scrambles the channels into a combined signal containing the necessary color brightness and the proper chrominance, or color content. The combined signal is then fed to the DuMont UHF transmitter and broadcast. The antenna is located on top of the building at 515 Madison Ave.

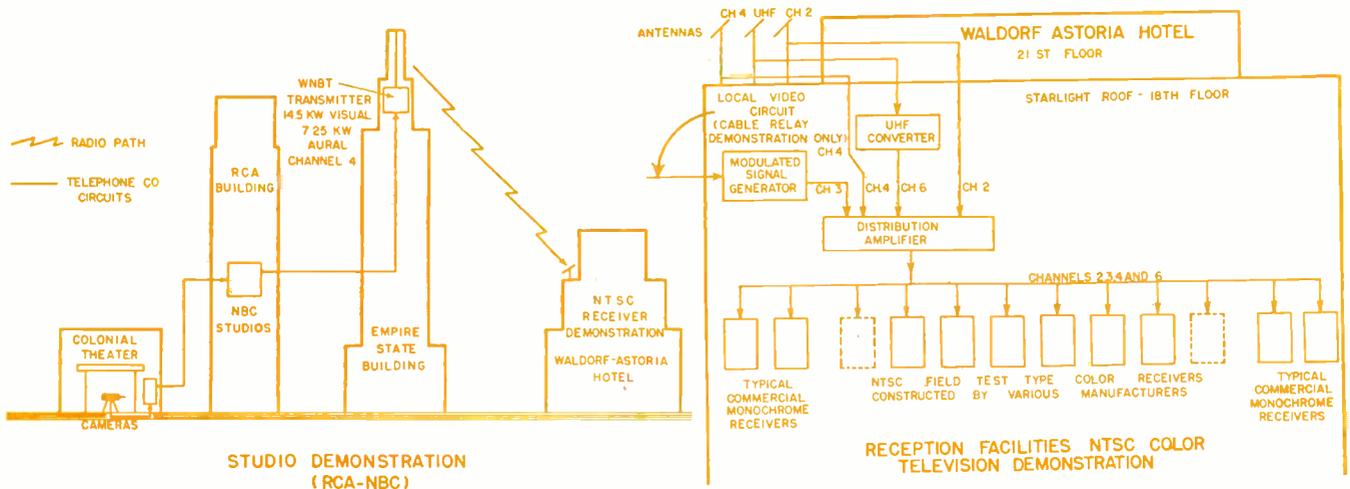

How color signal was transmitted through Empire State tower to color receivers in Waldorf

New Audio Gear

Hi Fi Amplifiers Microphones, Loudspeakers and Housings

Regency HI FI ENSEMBLE


Regency model 1000 Hi Fi ensemble, designed for decorative appearance, need not be housed in a cabinet. It consists of three moisture-protected units: a preamp-equalizer, power amplifier, and power supply. A built-in variable crossover network for correct matching to loudspeaker systems is said to be an innovation. Other features: One low- and two high-impedance inputs



with independent level adjustments; low noise input level; flat response beyond the limits of audibility. Controls include compensated loudness, gain, tone, and a six-position cross-over switch for different recordings. The tone controls are separate bass and treble stepped adjustments. The ensemble sells for \$995, Regency Division (I.D.E.A.), 7900 Pendleton Pike, Indianapolis 26, Indiana.—TECHNICIAN

Insuline SPEAKER GRILLS

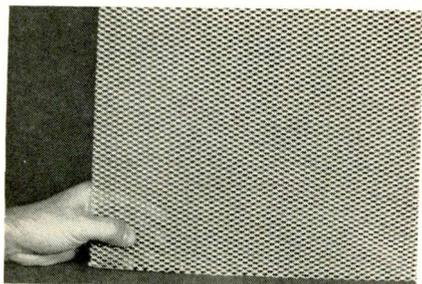Aluminum mesh grills, intended to protect the loud speakers of custom-built sound installations. Finished in non-tarnishing gold color. Available in three sheet sizes: the



No. 3947, 12-in. x 18-in., at \$2.35; the No. 3948, 18-in. x 24-in., at \$4.65; the No. 3949, 24-in. x 36-in., at \$9.35. Insuline Corp. of America, 3602 35th Ave., Long Island City 1, N.Y.—TECHNICIAN

Approved HI FI TUNER

Model V12 is a 12-tube Hi Fi AM-FM tuner, RF stage is used on both AM and FM; 456 kc IF stages and crystal detector are used on AM; 2-stage 10.7 mc IF strip and double limiter and discriminator stages used on FM. Printed circuit capacitors, temperature compensated where necessary, are used. Common slide rule tuning with separate RF and IF channels on AM and FM; neon-lamp channel indicators present. AM-FM selector switch. Common cathode follower output for FM and AM tuning range. Net price, \$85.00. Approved Electronic Instrument Co., 928 Broadway, New York 10, N.Y.—TECHNICIAN

Fold-A-Flex SPEAKER HOUSING

The Fold-A-Flex speaker cabinet incorporates within its construction, characteristics common to three of




the most popular loudspeaker cabinet types. It is possible by simple mechanical means to change the enclosure into 1) infinite baffle, 2) bass reflex, 3) folded horn. Choice of the enclosure type is determined by the listener, on the basis of room acoustics and his particular listening preferences. The Fold-A-Flex will incorporate the Stephens TRUSONIC 206AX coaxial speaker. The three-in-one cabinet contains three ports with variable openings which, in different combinations, embody the three basic cabinet types in common use. Stephens Manufacturing Co., Culver City, Calif.—TECHNICIAN

Bell AMPLIFIER

Bell amplifier, model 3717-MB, is intended for mobile use and has a built-in 78 RPM rim-drive phono with crystal pickup and separate volume control. Microphone input also has separate volume control. A stand-by switch saves power while keeping filaments hot. Operates on either 115 V AC or 6 V DC; cables for both types of connection are supplied. Where a complete range of turntable speeds is necessary, the deluxe model, 3717-MB3, is available. This model has a three-speed motor and turnover-type pickup for 33 $\frac{1}{3}$, 45, and 78 RPM records. Bell Sound Systems, Inc., 555 Marion Rd., Columbus 7, Ohio.—TECHNICIAN.

Atlas MIKE STAND

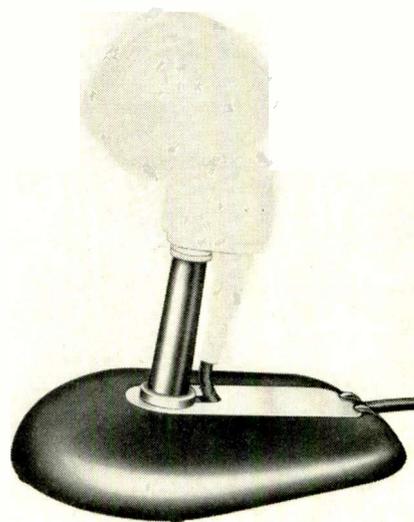The Atlas model DS-10 desk stand for all types and styles of microphones incorporates a new rear cable exit feature. The microphone cable is concealed in a slot below the center section of chromium trim and is directed out at the rear of the base. All parts are die cast and finished in gun metal enamel and chro-




mium. Atlas also has a new swivel, Model SW-1, for microphone positioning. It moves through 360° and can be used on any desk or floor stand. Unit is locked in any position by a turn of the locking knob. The parts are die cast and chrome finished. Atlas Sound Corp. 1451—39 St. Brooklyn 18, N.Y.—TECHNICIAN.

Antennas and Accessories

UHF-VHF Antennas, Boosters, Converters, Installation Aids

Channel Master VHF ANTENNA

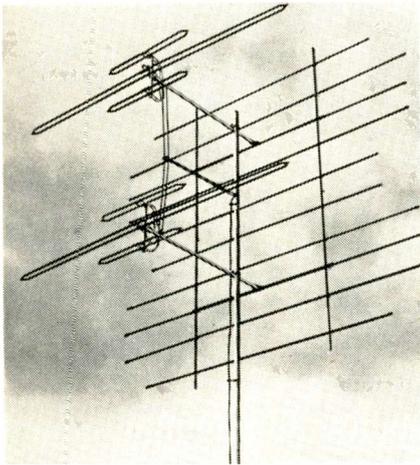The "Champion" provides reception on all VHF channels, equal to or exceeding that obtainable with many single-channel antennas, ac-



ording to the manufacturer. A reflecting screen is claimed to increase sensitivity without introducing frequency discrimination. The manufacturer states that, in addition to high sensitivity and sharp directivity, this broad-band system maintains a match close to 300 ohms. The antenna takes into account the fact that the high portion of the VHF band (channels 7 to 13) is approximately the third harmonic of the low portion of the VHF band (Channels 2 to 6). The antenna's design is accordingly based on a dipole cut for sensitivity on the low band, which is made to act as three dipoles, in the same phase, on the high band. This is achieved by addition of other elements and a phasing and matching harness. Factory pre-assembly facilitates rapid installation. The antenna is made in 1-, 2-, and 4-bay versions. List prices: model No. 325 (1-bay), \$20.83; model No. 325-2 (2-bay), \$43.36; model No. 325-4 (4-bay), \$88.68. Channel Master Corp., Ellenville, N.Y.—TECHNICIAN

RMS BROAD-BAND YAGIS


Six 10-element broad-band models cover the VHF band as follows: model STY1024 covers channels 2-3-4; STY1025, 2-3-4-5; STY1026, 2-3-4-5-6; STY1036, 3-4-5-6; STY-1046, 4-5-6; STY10713, 7 through 13. No hardware bag is needed for in-

stallation. The elements swing out and are tightened. RMS, 2016 Bronxdale Ave., New York 62, N.Y.—TECHNICIAN

JFD UHF-VHF ANTENNA

A rhombic section for UHF pickup, mounted in front of a conical section for VHF channels, is combined to provide all-channel coverage with a single antenna. Jetomic models JeT454 (single-bay) and JeT454S (two-bay array) are factory pre-assembled, and use simple quarter-wave copper jumpers for UHF-VHF matching in place of couplers or cross-over networks. List prices: JeT454, \$16.50; JeT454S, \$34.50. JFD Manufacturing Co., 6101 16th Ave., Brooklyn 4, N.Y.—TECHNICIAN

iE LIGHTNING ARRESTOR

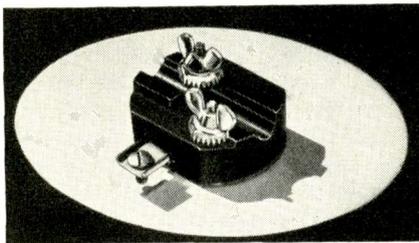

A lightning arrester designed to carry all common types of transmission lines, including the tubular, small oval, large oval, open line, 300 ohm and Anaconda line, is claimed by the manufacturer. Positive contact is made by long piercing teeth which bite into the insulation, to shunt lightning and static charges to the ground. Insulation need not be stripped. Impedance of line is not disturbed. The iE arrester is readily adaptable for indoor or outdoor installation; may be used on walls, windows, masts or pipes. Model No. 4000 lists at \$1.25; No. 4005, with stainless steel strap for pipe mounting, lists at \$1.50. iE Mfg. Co., 325 N. Hayne Street, Chicago, Ill.—TECHNICIAN

Bogen UHF CONVERTER

Unusually high gain is claimed for model UCT-1 UHF converter. This is achieved by reduction of the noise figure to only 13 db. Installed by connection to the antenna input of a standard VHF receiver, the unit provides reception on all 70 UHF channels and feeds through either

Channel 5 or 6 on the standard receiver. Changeover from UHF to VHF is accomplished by a simple switch which, when in the VHF position, bypasses the converter without attenuating signals. List price, \$42.50. David Bogen Company, 29 Ninth Avenue, New York 14, N.Y.—TECHNICIAN


Saxton TRANSMISSION LINES

Open-wire UHF transmission lines, available in a choice of 300- or 450-ohm types. Either plain or formvar covered, the wire comes in spools of 100, 250, 500, or 1000 feet. Also available for this wire: stand-off insulators, window straps, rotor straps, and a device to permit the wire to be used in places where sharp turns are necessary. Saxton Products, Inc., 2101 Grand Concourse, New York 53, N.Y.—TECHNICIAN

ITI UHF BOOSTER

Model IT-133 UHF Autobooster is a continuously tunable amplifier covering the entire UHF band. Featuring a 6AJ4 low-noise triode, the booster provides high usable gain with low noise, according to the manufacturer. Industrial Television, Inc., 369 Lexington Avenue, Clifton, N.J.—TECHNICIAN

Tescon VHF-UHF CROSSOVER

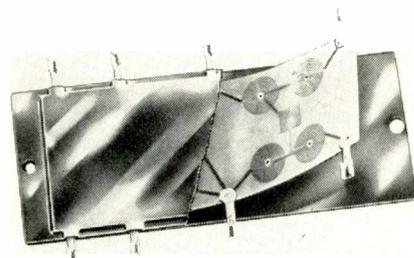

Triple-tie cross-over filter, model UV-3, employs a printed circuit to eliminate the need for two down leads when both a UHF and VHF antenna are in operation. Use of one down-lead eliminates interaction between the UHF and VHF systems, in addition to simplifying the installation job. Impregnation before encasement to make the unit moisture-proof and fungus-proof also eliminates possibility of drift or shorting of components. TV Products Co., Springfield Gardens, N.Y.—TECHNICIAN

Is YOUR Number in the Book?

Many TV Technicians Find Classified Telephone Ads Helpful

There are two things that usually happen when a home-owner's TV set breaks down. If he's like most people, his initial act is to howl like a wounded bear as he rushes to tinker with the ailing receiver.

After a "thorough examination," (he really knows little about the set but feels he might as well twist a few knobs) the now thoroughly frustrated owner takes step number two—the locating of a service man who will respond to his frantic plea for help—within a minimum of sixty seconds!

Seriously though, a TV set's failure is almost a critical one today because it forms such a major part of a family's entertainment. Even the slightest loss of use is now likened to the automobile which conks out just as the long-planned picnic trip gets underway.

But let's get back to our unhappy set-owner who's now in dire need of a competent and quick TV repair man.

There are probably several TV shops in his town, perhaps dozens if he lives in a larger city. He's seen a few of them many times but at this particular moment can't recall the name of a single one. Or, maybe he

does know the name but *doesn't* have the telephone number!

Far-fetched? Not at all. Similar situations have confronted all of us, probably more times than we'd care to admit.

One solution to our mythical friend's problem is for him to consult the "Yellow Pages" of his local "Redbook" Classified Telephone Directory, a volume usually as close at hand as the telephone itself.

In it the set-owner will find TV service firms listed alphabetically, under a bold-faced heading which immediately identifies their line of work. In many cases, the trade-names of sets a shop specializes in are also listed. Thus, the harried customer gets his man!

Always identifiable by its well-known "Yellow Pages," whether in a separate volume or bound as part of a regular telephone book, a classified directory is declared to provide its advertisers with the most inexpensive advertising medium available. Continuous surveys made by the telephone companies and by prominent manufacturing concerns bear out this statement.

What Servicemen Say

TECHNICIAN, too, has interviewed servicemen on the relative merits of classified directory advertising. Spot-checking has revealed answers which are much the same as those obtained by commercial survey organizations.

One technician, who had particularly good results from his medium-sized ad, said he simply couldn't afford *not* to be in the book! Still another service man stated that he had dropped his former method of advertising to "concentrate solely on the telephone book kind." To be sure, many of those interviewed said they used the "Yellow Pages" only because their competitors did. Almost all queried, however, felt that the directory was a good source of business, particularly for the emergency repair calls they received.

One major TV manufacturer conducted its own national survey to determine the value of classified directory advertising as it affected sales and service shops. Here are some of the facts that survey disclosed:

51% of all telephone subscribers (your potential customers) use the directories one or more times in any given week; 90% use them one or more times a year. This means nine out of ten subscribers in *every* community *actually* use their directories as buying sources! And, as the telephone companies point out, these people are in a "buying frame of mind" when they look you up!

The Cost Factor

Based upon the circulation of directories in his area, a serviceman's one-line listing can cost him as little as fifty cents a month. Larger listings (more than one line) and display ads are proportionally higher but still less expensive than any other form of advertising, it is claimed.

There are some 15 kinds of listing and display-type ads from which to choose, and should an advertiser wish to illustrate his, free art service and advice are available.

It has been said that no matter what size space an advertiser uses, his name in the "Yellow Pages" insures "the maximum return on all of his present sales efforts, for rather than compete with other advertising, the directory supplements it."

Here's what that means. Suppose a service man runs a small newspaper ad. Those interested will clip it out. But suppose they later lose it. Probably they've remembered the name of the shop but not the telephone number. Where do they find it?—the classified telephone directory. Similar situations can also apply to billboards, cards, circulars, envelope stuffers and other mass forms of promotion: seen today, forgotten tomorrow.

Remember, too, you *don't* have to be an artist, copywriter or engraver to create an effective ad. The directory representative in your area is skilled in this work and it's part of his job to help with such problems.

Those who produce them feel the classified telephone directories occupy a unique position in the advertising field. Like the "straight line" in mathematics, the directory, they say, represents the shortest distance between two points—"the customer and the cash register!"



DISCOVER WHAT

GOLD


AND 2 INCHES OF AIR

DO FOR

2

NEW


WALSCO ANTENNAS

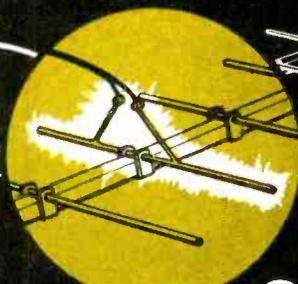

AMAZING
3 YEAR
GUARANTEE

● NEW WALSCO GOLD DIPOLE YAGI (UHF)

No less than *24 kt. gold* plating on the receiving dipole of this great, new, 10 element Yagi. Why *gold*? Because *gold* resists corrosion better than any other metal... and *gold* is an excellent conductor. Like the most powerful *radar* antennas, the *Walcco Gold Dipole Yagi* guarantees *permanent* high gain in any location, under all weather conditions. It's custom-made for each location. The *only* Yagi that carries a *3 year* unconditional guarantee! And it costs no more than conventional Yagis.

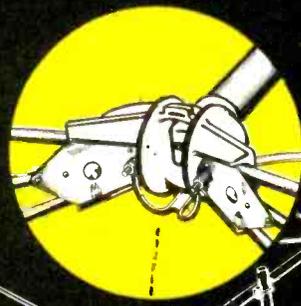

● NEW WALSCO IMPERIAL CONICAL (VHF)

Here's the first radical improvement in Conicals. A new insulator which utilizes "barrier discs" and *2 inches of air space* between the terminals prevents "shorts." Soot deposits, dirt, moisture, salt etc., *cannot* affect the insulator. This great, new *Conical* will therefore maintain high gain performance under any and all weather conditions. Front-end hardware is *stainless steel* to prevent corrosion losses permanently. Takes only *2 minutes* to assemble because there's no loose hardware. Nothing compares to the *Walcco Conical* at any price... and it's backed by the *only 3 year* unconditional guarantee!

Write for complete information

WALSCO ELECTRONICS CORPORATION

3602 Crenshaw Boulevard, Los Angeles 16, California

Shop Hints to Speed Servicing

Tips for Home and Bench Service Contributed by Readers

Intermittent Tube Filaments

My method of locating intermittent tube filaments cuts down most of the time usually required to "nail" this type of trouble. When an intermittently-open tube filament seems to be present, it can be easily located by shunting a $\frac{1}{4}$ -watt, 125-volt neon lamp across the heater pins. When the filament opens for even an instant, the neon lamp lights up. I usually place the set on the bench, with the neon lamp hooked to a tube socket, while I work on another set. If the neon lamp doesn't glow after a reasonable time, I move the lamp to the next socket, continuing this procedure until the open filament is found. On AC-DC sets, a flickering pilot lamp will often indicate the presence of this type of trouble. 50L6's have been found to be frequent offenders.—*Joseph Amorose, Richmond, Va.*

Removing Frozen Yokes

Now and then the TV serviceman is plagued by the necessity of removing a "frozen" yoke. If solvent applied around the neck of the picture tube fails to loosen the yoke, many manufacturers recommend the application of a suitable ac voltage (25 to 50 volts) to the yoke's horizontal windings. To reduce the line voltage, a variable voltage transformer is often recommended. The use of this device may be impractical for at least two reasons: less expensive transformers of this type do not permit a sufficiently gradual variation of voltage output in the desired range, introducing the danger of yoke damage; and many service shops do not have such a transformer available at all. The following

method requires an accessory that can be assembled easily and inexpensively:

Arrange three light-bulb sockets, an outlet and a line cord in the manner shown. Attach one end of a line-cord wire, to the other end of which a male plug has been connected, to the horizontal section of the yoke. (First disconnect the yoke from the circuit, of course.) Insert this male plug into the socket on the test device. By screwing various sizes of electric bulbs into the three parallel sockets, enough heat will be generated in the yoke so that it can be slipped off.

Use the smallest wattage (highest resistance) bulbs that will do the trick. Application of some vaseline or similar lubricant to the portion of the CRT neck over which the yoke must slide may prove helpful. Remove the yoke with a gentle, rocking motion.

Note that the light-bulb sockets are electrically in parallel with each other, but in series with the yoke and the ac line. Using higher wattage bulbs or placing bulbs in parallel reduces the resistance in series with the yoke. This increases current and voltage in the yoke's windings.—*B. O. Rüs, Little River, Miami, Fla.*

Keeping Resistors Handy

A neat, space-saving way for keeping an assortment of resistors handy to the service bench is to stretch a length of a discarded coiled heater element between two hooks above the bench. Bend a hook on the end of one lead on each resistor, and hook the resistors along the coil. The color code will show readily and, if the resistors are arranged in the

order of their value, a desired one may be selected quickly.—*S. Sandler, Providence, R.I.*

Faulty CRT Prongs

I frequently find poor connections on the pins of picture tubes, especially filament pins. Inserting a piece of fine wire in the pin when resoldering establishes better contact, eliminating this trouble completely.—*Richard P. Thull, Rutland, Vermont.*

Auto Radio Noise

Before attempting to troubleshoot an auto radio afflicted with undue static, open up the drain hole in the bottom of the aerial (with which some antennae are equipped) and let the water out. The drain holes in some of these aerials become clogged, and allow water to accumulate in the tube, with noisy reception resulting in consequence.—*Harvey Muller, Danboro, Pennsylvania.*


Overheated Resistors

Dual triodes used as TV RF amplifiers, such as the 6BK7, 6BQ7, and 6BZ7, often develop intermittent shorts. When such a defective tube is replaced, go a little further: check the voltage-dropping resistors to the tube. Frequently the tube short results in overheating of these resistors, causing an increase in their resistance value and a subsequent loss of gain. Turn the set on and let the resistors warm up for a while before measuring their value. Replacing the resistors that have changed in value will restore the set to its original sensitivity.—*Patrick E. McGee, Raritan, Ill.*

Replacing Socket Lugs

Undoubtedly many of your readers, at one time or another, have broken a lug in a molded socket. Instead of replacing the socket, they have tried to replace the lug, only to have the socket (in a tuner, of course) also break. To remove the broken lug from the socket, solder a short length of No. 12 or No. 14 wire to the top side of the broken lug and simply pull the wire out. The broken lug will come out with it, and a replacement may be readily slipped in.—*Thomas A. Donaldson, Smyrna, Delaware.*

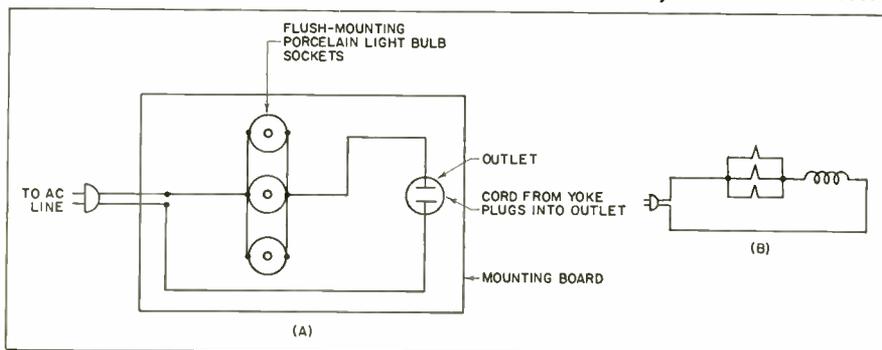Set-up for removing frozen yokes. Porcelain sockets can be readily mounted on a board.



ONLY JFD OFFERS YOU A *FULL YEAR "GOLD SHIELD" GUARANTEE AGAINST RUST!*

Every screw, nut, bolt, washer and bracket in JFD's new "Gold Shield" UHF antennas is "Bronzidite" plated! Only these spectacular performing antennas carry a full year's guarantee against damaging rust. Safeguard your antenna installation and your reputation . . . depend on the new JFD "Gold Shield" gold-colored UHF antennas.

See them at your jobber or write for brochure #29.



JFD

Model UHF400-GOLDEN MAXI-COR \$14.95 list

JFD MFG. CO., BROOKLYN 4, N.Y.
World's largest manufacturer of TV antennas and accessories

Model UHF411-GOLDEN BRIDGE

\$11.75 list

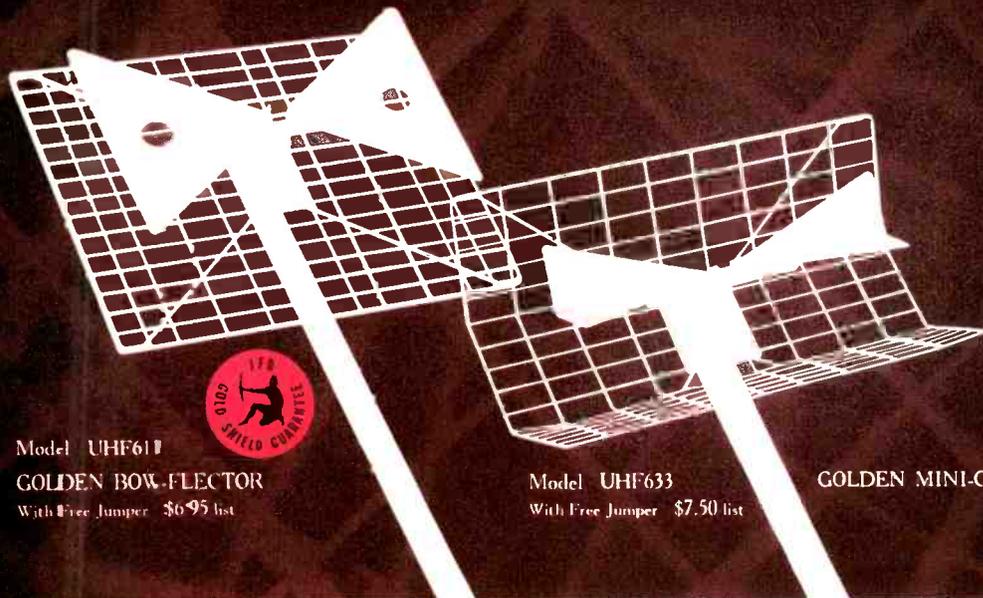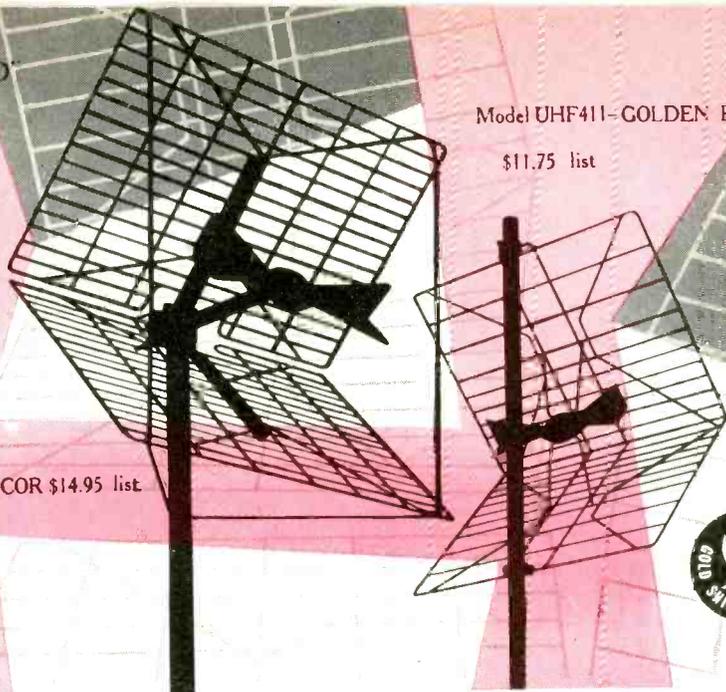

Model UHF611
GOLDEN BOW-FLECTOR
With Free Jumper \$6.95 list


Model UHF633
With Free Jumper \$7.50 list

GOLDEN MINI-COR



JFD introduces something **NEW** in UHF antenna design. Now you can offer gold-colored antennas with a *full year* guarantee against the ruinous rust and corrosion that impairs the UHF picture. JFD "Gold Shield" UHF antennas deliver the **POWER** needed for brilliant reception, plus the exclusive "Bronzidite" Army-Navy "spec" plating that means more profit for you—without call-backs—See them at your jobber or write for Bulletin No. 225.

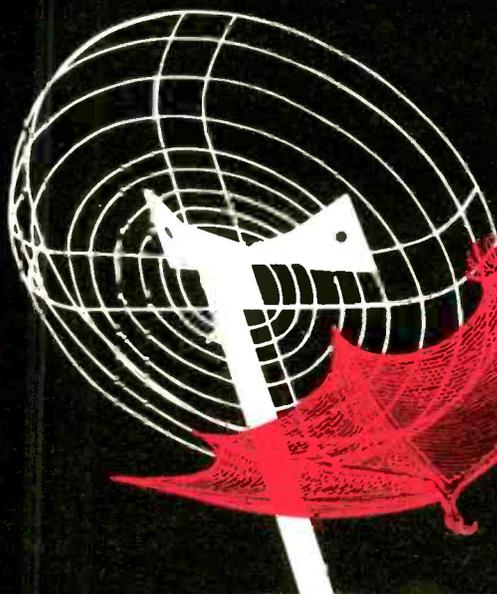JFD MFG. CO., BROOKLYN 4, N. Y.
World's largest manufacturer of TV antennas and accessories



The JFD Golden "Para-Bow" delivers the performance of two antennas because it actually is two sensitive antenna designs combined into one powerful array: the radar parabola and the time-tested bowtie. Guaranteed for a full year against rust with **BRONZIDITE**, the "Gold Shield" gold colored Para-Bow is the finest UHF antenna you can offer your customers. It's completely preassembled, too. **UHF900—\$14.95 LIST.** Write for bulletin 231.

SENSITIVE AS RADAR


JFD MANUFACTURING COMPANY, Brooklyn 4, N.Y.
World's largest manufacturer of TV antennas and accessories



Shop Equipment and Instruments

Crest MIDGET BAR GENERATOR

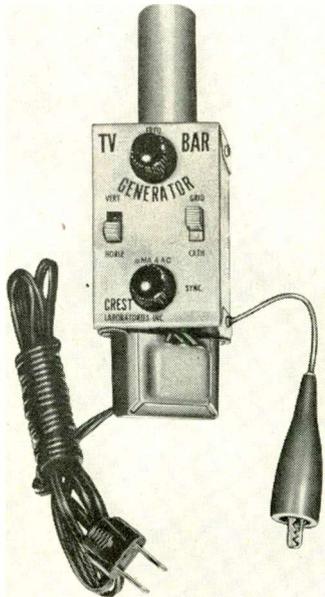Model MA4-AC is a self-powered, pocket-size bar generator, usable with all TV sets. Plugged into any AC wall outlet, it is immediately



ready for use. The number of vertical or horizontal bars is adjustable. Dealer net, \$14.85. Crest Laboratories, Rockaway Beach, N.Y.—TECHNICIAN

Precise OSCILLOSCOPE

The model No. 308 oscilloscope, using an 8½-inch 8CPI cathode-ray tube, is available either in kit or assembled form. A switch-controlled synchronizing circuit is intended for "difficult-to-sync" applications. Other features: voltage regulation, and a high accelerating potential. Kit form, \$129.50; assembled, \$229.50. Precise Development Corp., 999 Long Beach Road, Oceanside, N.Y.—TECHNICIAN

Centralab CALCULATOR

Centralab's color-code calculator for capacitors and resistors has seven rotating wheels from which capacitance or resistance, tolerance, and temperature co-efficient can be read directly. The calculator covers RETMA color code specifications on normal and extended-range tubular ceramic capacitors, and radial or axial lead resistors. It is on sale at Centralab distributors.

Triplet TUBE TESTER

Mutual conductance tube tester, Triplet model 3423, tests tubes by applying a high-frequency signal to the grid and measuring the signal component in the output. Tubes with widely varying characteristics can be checked without overloading or otherwise damaging the tube. Flexible switching arrangement; roll chart for testing. The Triplet Electrical Instrument Co., Bluffton, Ohio—TECHNICIAN.

CBS PIN STRAIGHTENER

The CBS-Hytron twin pin straightener is designed to accommodate all types of miniature tubes. Made of wear-resistant steel dies, it consists of one 7-pin and one



9-pin straightener, mounted back to back. The compact device may be carried in the tool box or in a pocket. CBS-Hytron, Danvers, Mass.—TECHNICIAN

EMC SIGNAL GENERATOR

Model 700 is a generator with several types of output. It may be used as a bar generator for TV adjustment with a variable number of bars available for horizontal or vertical adjustments; a square-wave generator to 20 KC, or a Wien bridge AF oscillator with sine wave output from 18 CPS to 300 KC. A Colpitts RF oscillator produces output signals ranging from 300 KC to 108 MC on fundamentals—up to 216 MC on second harmonics. The instrument is priced at \$55.90. Electronic Measurements Corp., 280 Lafayette St., New York, N. Y.—TECHNICIAN.

Industrial HV METER


Model No. 520 Hi-Volt, designed for television and other high-voltage DC supplies, has a range up to 30,000 volts. Instead of a conventional meter movement, a glow lamp indicator that is burnout-proof, according to the manufacturer, is present. A knob is turned until the neon lamp extinguishes; then voltage is read directly off the dial. In use, the meter's test-clip lead is grounded; the insulated test prod is touched to the high-voltage terminal. List price: \$11.00. Industrial Devices, Inc., Edgewater, N.J.—TECHNICIAN

Raytheon TELE-JAR ROTOR

Raytheon's Tele-jar Rotor is a shop aid for servicemen. It has 48 plastic, unbreakable jars for storing miniature tubes, crystal diodes, panel lamps, resistors, small condensers, insulators and hardware. The jars are held on eight shelves mounted on a ferris wheel rack. They can be set on a bench or wall-mounted. Raytheon Mfg. Co., Receiving Tube Div., 55 Chapel St., Newton 58, Mass.—TECHNICIAN.

Tele-Matic TVI ANALYZER

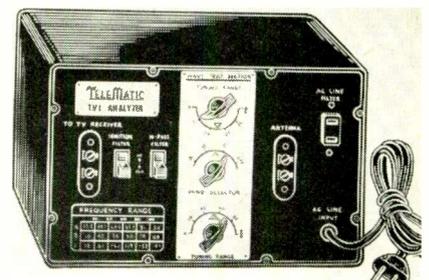The TVI Analyzer, designed to identify TV interfering signals, contains a hi-pass and ignition filter section, an AC line-filter section, and a full range of calibrated wave traps. The desired wave trap is selected by a rotary switch; tuning is accomplished with 2 calibrated selector



knobs. The wave traps and filters can be used either singly or in any combination, as required. The unit is housed in a compact steel case measuring 5½ by 7-in. Net price to servicemen is \$19.95. Tele-Matic Industries, Inc., 1 Joralemon St., Brooklyn 1, N.Y.—TECHNICIAN.



Why didn't someone do this before?




A **Leader** FIRST!

Only Superotor®

has the Quick Detachable Drive Unit




“TERRIFIC!” say TV servicemen — and you’ll echo their words when you see the amazing new Superotor. Imagine — a drive unit as easy to replace as a light bulb! Strictly a one-man job! No fussin’, no cussin’, — no need to dismount the antenna — no need to interrupt TV viewing while the drive unit is being serviced. Great? Yes! — and this is just one of FIVE major advances that put Superotor years ahead of anything on the market. No wonder the big switch is to Superotor!

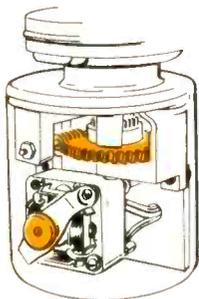


- Double Lock Stop Prevents Drift & Coast

A **Leader** FIRST!

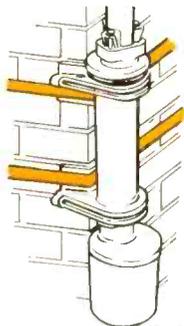

- Built-in Chimney Mount Design

A **Leader** FIRST!

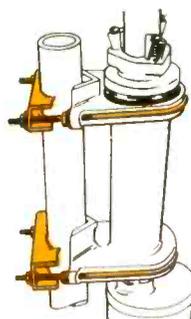

- Steel Reinforced Construction

A **Leader** FIRST!

VP* Tuning

*Vernier Precision

A **Leader** FIRST!

Patent Applied for Copyright



2925 EAST 55th ST., CLEVELAND 27, OHIO

... LEADING THE WAY TO BETTER PRODUCTS

"Tough Dog" Corner

Difficult Service Jobs Described by Readers

Flicker on UHF

A complaint of flickering—on UHF stations only—occurred on a set that used a single antenna for UHF and VHF reception. Since a converter was being used for UHF, I tried another converter. The set still flickered. Suspecting the antenna or lead-in might be the cause of the flicker, on UHF, I hooked up an indoor antenna, and left the lead-in from the outside antenna lying on the floor near the set. The receiver still flickered. With the indoor aerial connected, I picked up the lead-in from the outdoor antenna, curled it up, and placed it as far away from the set as possible. Result: the flickering was greatly reduced.

I checked the outside antenna on the roof, as well as the lead-in to the apartment, and everything appeared all right. While on the roof I noticed another antenna. It was a double corner-reflector, providing much too high a gain for that signal area. I also noticed that it used no stand-offs. The only anchoring was by means of a house brick placed on the transmission line just before the line went over the side of the roof. The slightest breeze would move the lead-in, which would then rub against a vent pipe in one place. Deciding to be a good Samaritan, I pulled the wire away from the vent pipe and fastened it down with a stand-off.

I did not have to wait long for a reward for my good deed. On returning to my customer's apartment, I found the picture had stopped flickering. Apparently the flapping line not only varied the signal strength of the antenna to which it was connected, but also that of nearby antennas, including the one belonging to my customer.—*F. Mattioli, Madison, Wisconsin.*

Audio Fault Kills Pix

Here is a Tough Dog whose cause you would never suspect unless you were thoroughly familiar with the circuit, which was a Du Mont RA 164-5 chassis. These were the symptoms: when the set was turned on, picture and sound would come in for about five seconds and then go completely out, leaving just the raster.

After the routine of substituting front-end and IF amplifier tubes, I decided to take IF amplifier voltage measurements, starting with the control grids (AGC voltage). This negative voltage was definitely much higher than normal, no doubt cutting off the tubes. I was so sure that the fault was in the AGC circuit that I focused all my attention on tracking down the trouble there (see Fig. 1). That was where I made my mistake, although my meter showed a below-normal B-plus voltage between cathode of the AGC amplifier, V-218, and ground.

I finally realized that the AGC cathode voltage came from the same source as the voltage for the cathode of the audio output tube, V-211. Then I started looking for the trouble in the audio amplifier. On the grid of the audio output tube, V-211, I got a reading of 60 volts positive although the normal reading given was +115 v. The next logical step—a resistance check of the .02 mfd coupling capacitor—showed leakage in this component. I replaced it. Picture and sound were restored. (Heavy plate current flow in V-211, caused by its positive biasing, was producing increased drops in B supply resistors, and thus lowering the voltage available at the +135 v terminal, to which the cathode of the AGC amplifier was connected.—Ed.)
—*John L. Mancini, Winthrop, Mass.*

Cracked 1B3

This defect baffled a number of TV servicemen before it was remedied. The set happened to be a Philco using a conventional high-voltage flyback supply, with 6SN7, 6BG6, 6W4, and 1B3 tubes.

When I was called in to service the receiver, the woman of the house complained that the set would go dead after playing one hour. Everything was normal when I examined the set. On my return one hour later, I found the set dead. There was no picture or raster. Careful visual inspection in time showed a thin crack in the glass shell of the 1B3 tube. In order to see this, a watchmaker's eye-piece was used. The tube was replaced and the problem was solved. As these cracks cannot always be seen by the naked eye, they are difficult to locate. The crack permitted air to enter and cut off the tube after one hour of playing.—*Gelman's TV, Philadelphia, Penna.*

Times Have Changed Dep't.

Service manager (to boy applying for a job as TV apprentice): "Are you willing to work long hours?"


Boy (eagerly): "Yes, I am."

Service manager: "And will you accept a very low starting salary?"


Boy: "I will."

Service Manager: "Then I'm sorry—we can't use you. We're looking for an intelligent lad, not a fool!"

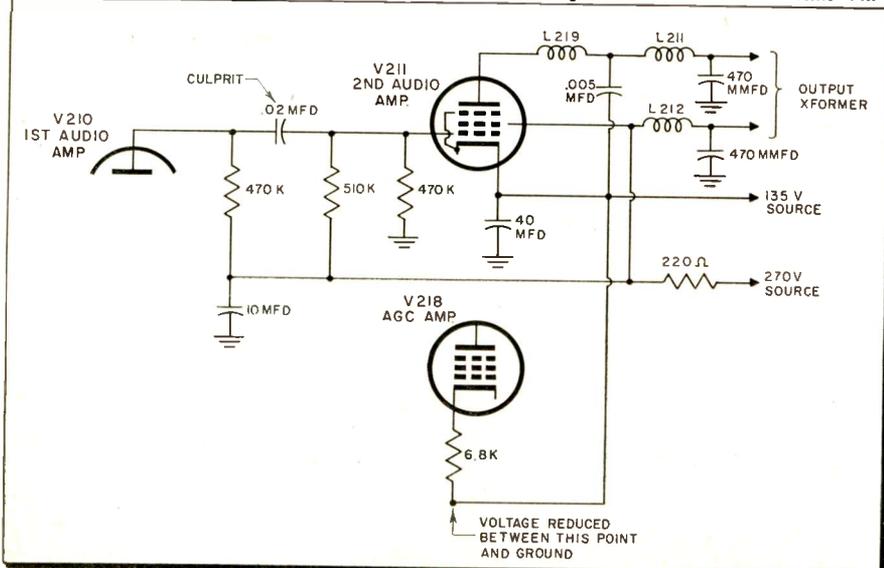Schematic of section of Du Mont RA 164-5 chassis in which leaky audio coupling condenser killed pix and sound by reducing the 135v source voltage. (See "Audio Fault Kills Pix")



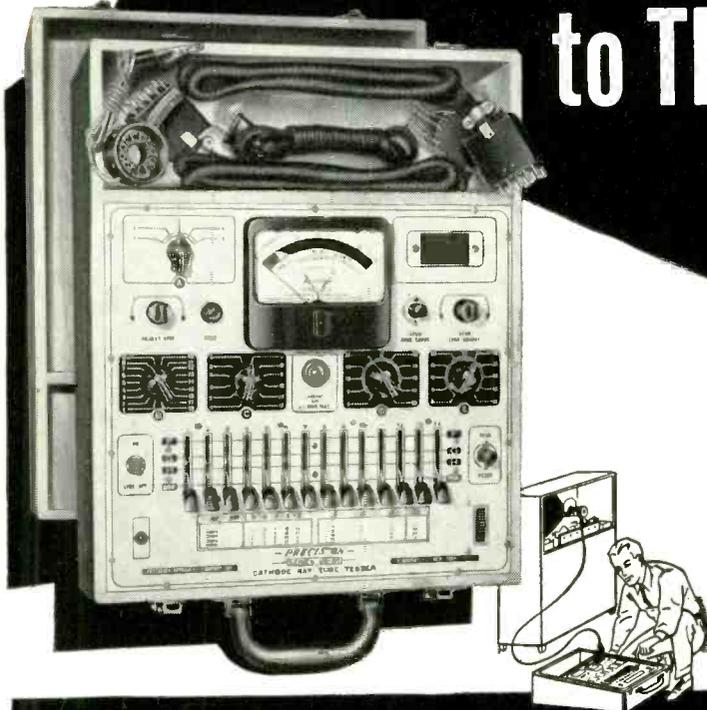It takes a CR TUBE TESTER to TEST a CR TUBE...



...because CR tubes are electrically and physically different from all other types of electron tubes! Some of the more obvious differences include:

- PICTURE PRODUCING BEAM CURRENT
- EXTREMELY LOW ANODE CURRENTS
- DIFFERENT, MULTIPLE OPERATING VOLTAGES
- HIGH LEAKAGE and SHORT CHECK LIMITS
- MORE and DIFFERENT TUBE ELEMENTS
- ELECTROSTATIC FOCUS ELEMENT
- ELECTROSTATIC DEFLECTION PLATES
- ELECTROMAGNETICALLY FOCUSED GUN
- ELECTROMAGNETICALLY DEFLECTED BEAM
- ETC., ETC., ETC.

YES, IT TAKES A CR TUBE TESTER TO TEST A CR TUBE...
AND THE **PRECISION CR-30**
WAS SPECIALLY DEVELOPED FOR THIS VERY IMPORTANT PURPOSE!


TESTS ALL TV PICTURE TUBES Magnetic & Electrostatic
Oscilloscope & Industrial Types
...FOR BEAM CURRENT INTENSITY (Proportionate Picture Brightness)

Stop Guess-Checking with CABLE ADAPTERS!

- Receiving tube checkers were made for testing receiving tubes and NO CABLE ADAPTER can adapt them to do the job of the CR-30.
- CABLE ADAPTERS only check for filament continuity, a degree of inter-element short and a so-called emission test.
- CABLE ADAPTERS do not test for the all-important, picture producing beam current.

You can't afford to guess when you test the most expensive component of a TV set.
Be sure with PRECISION Model CR-30!

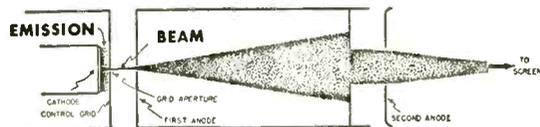IT IS THE ELECTRON BEAM (and NOT total cathode emission) which traces the pictures on the face of the CR tube.



Cathode emission can be high, and yet Beam Current (and picture brightness) unacceptably low. The CR-30 will reject such tubes because it is a Beam Current tester. Conversely, cathode emission can be low and yet Beam Current (and picture brightness) perfectly acceptable. The CR-30 will pass such tubes because it is a Beam Current Tester.

The CR-30 incorporates additional special test facilities necessary for overall performance evaluation of the CR tube as will permit positive answer to the question "Is it the Picture Tube or the TV Set?" And the CR-30 gives the answer in but a fraction of the time required to test the other 2 dozen or so tubes in the set.

SERIES CR-30: In hardwood, tapered, portable case, with hinged, removable cover. 17¼" x 13¾" x 6¾". Complete with standard picture tube cable, universal CR tube test cable and detailed instruction manual. Shipping weight: 22 lbs.

NET PRICE \$104.75



PRECISION APPARATUS COMPANY, INC.

92-27 HORACE HARDING BLVD., ELMHURST 13, N. Y.

Export Division: 458 Broadway, New York 13, U.S.A. • Cables—Morhanex
In Canada: Atlas Radio Corp., Ltd., 560 King Street, W., Toronto 2B

NEWS of the TRADE

Calendar of Coming Events

- Nov. 13-14: IRE Annual Electronics Conference, Hotel President, Kansas City, Mo.
- Nov. 17-19: RETMA, Palmer House, Chicago.



At the NATESA banquet in Chicago. Left to right, Bert Lewis, Rochester, N. Y.; William Briza, Omaha, Neb.; Milton Klarsfeld, Albany, N. Y.; Fred Colton, Columbus, Ohio; Frank J. Moch, Chicago (President); John Cecich, Chicago (Convention Chairman); Vincent Lutz, St. Louis; Jack McDowell, Kansas City; Harold Rhodes, Paterson, N. J., and John Hemak, Minneapolis, Minn. (Treasurer).

NATESA Plans Industry-Relations Program for '54

The National Alliance of Television & Electronic Service Associations plan a comprehensive three-point industry relations program for the coming year, Frank J. Moch, president announced at the close of the fourth annual TV-Radio Service Industry Convention and Show held at the Morrison Hotel, Chicago, October 9, 10 and 11. The convention brought delegates from thirty-eight states and Canada to view the thirty-two manufacturers' displays and to attend the seminars, color-television symposium and discussion groups and the gala annual NATESA banquet.

All present officers of NATESA were re-elected for the 1954 term and one additional office was filled. Four new affiliate groups joined NATESA. Officers re-elected included Frank J. Moch, Chicago, President; John Hemak, Minneapolis, Treasurer; J. B. McDowell, Kansas City, Kansas, Secretary-General; Bertram Lewis, Rochester, New York, Eastern Vice President; Fred Colton, Columbus, East Central Vice President; Harold (Dusty) Rhodes, Paterson, N.J., Eastern Secretary; Francis Fingado, Denver, Western Vice President; Vincent Lutz, St. Louis, West Central Vice President and W. A. Rosenberg, Wichita, Kansas, West Central Secretary. C. N. Burns, Memphis, was elected East Central Secretary.

The three-point program outlined by NATESA includes an integrated public relations and customer relations program in cooperation with the regional and local affiliates which will include promotional and advertising material; an expansion program and a manufacturer-relations program which was described by President Moch as presaging closer liaison between suppliers and

service groups, and a training program. This latter will include a speakers bureau, lectures, films and training sessions in cooperation with manufacturers.

New affiliates of NATESA announced at the Convention include the Utah Association of Radio and Television Servicemen; the Rhode Island Radiomen's Business Association; the Radio and Television Service Association of Western New York and the Associated Television Service Companies of Cincinnati.

Two companies were nominated for the NATESA Friends of Service Management Award—the Radio Corporation of America and Howard W. Sams & Co., Inc.; and two others were given continuing awards—General Electric Company and Sylvania. Formal awards to RCA and Sams will be made in these companies' plants at a later date.

The fifth annual NATESA TV-Radio-Electronic Service Industry Convention will be held in Chicago in mid-September, 1954, President Moch announced.

Technician Is Custodian of TV's Good Will

"Without in any way detracting from the importance of the other segments of the industry, the distributors and dealers, I believe it is fair to say that the prosperity of all four groups depends upon the proficiency and the honesty of the manufacturer and the service technician," said James D. Secrest, executive vice-president Radio-Electronic-TV Mfrs. Assn., speaking before a servicemen's audience at Fort Worth, Texas.

"The distributor and the dealer are highly important from the sales point of view, but it is the manufacturer and the serviceman who are responsible for the customer's satisfaction and consequently, in the final analysis, for industry stability.

"The manufacturer certainly has the initial and major responsibility. If he does not make a product that is properly engineered, manufactured, and inspected, everybody concerned with the selling and servicing of that receiver will suffer the consequences. If he produces a good set, everyone's job is made easier all down the line.

"The serviceman, given a satisfactory product, is probably more often responsible than the manufacturer for the consumer's satisfaction or complaints. In all instances he is closer to the set owner than the manufacturer and therefore in a better position to create good or ill-will for the product and the industry," declared Mr. Secrest in closing.



At left, John Cecich, chairman of the NATESA convention committee gives address of welcome. Center, Frank Hoffman receives attendance award from President Frank J. Moch, right.


now . . . new beauty

for the

housetops

DAVE CHAPMAN, S. I. D.

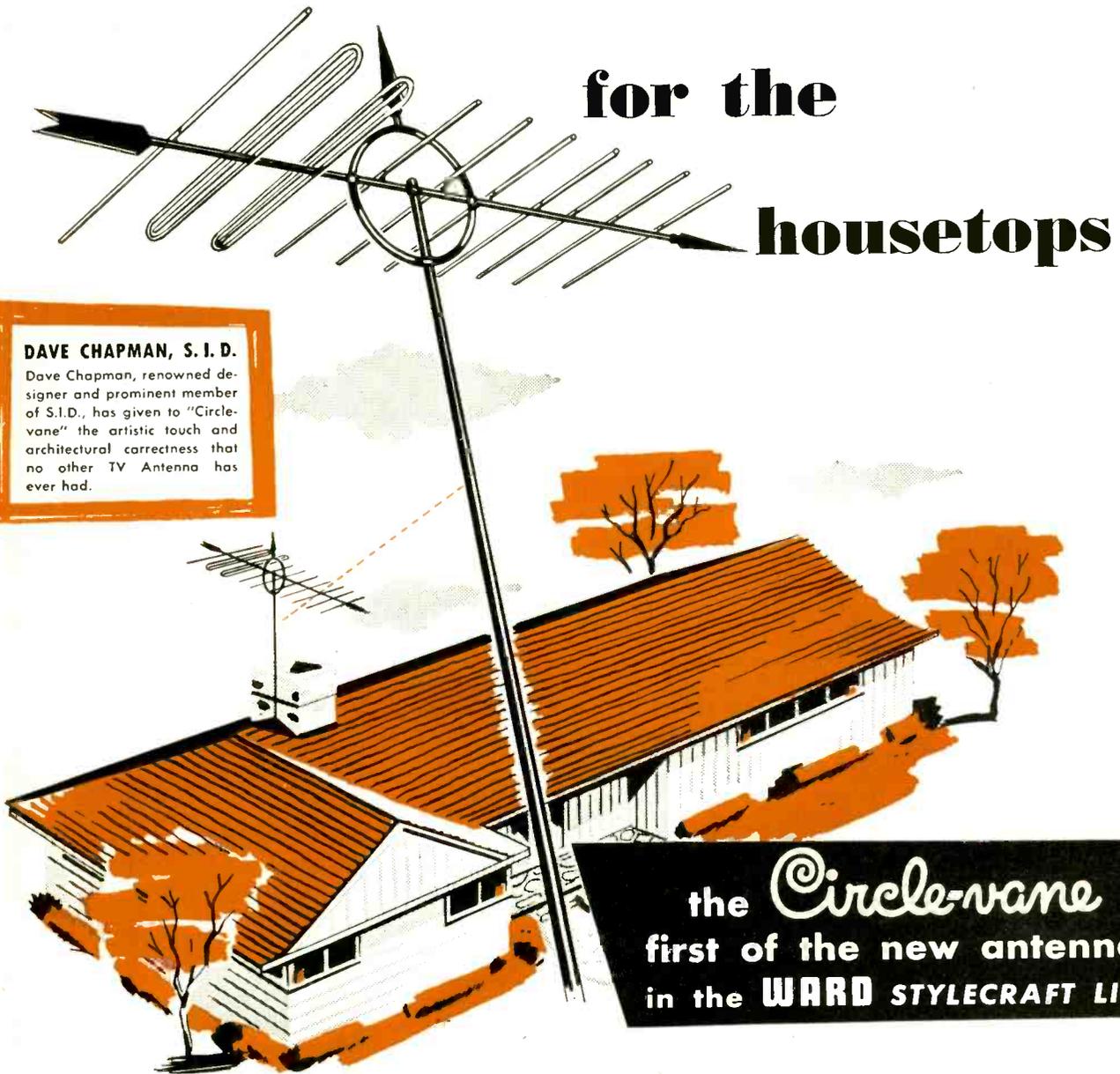Dave Chapman, renowned designer and prominent member of S.I.D., has given to "Circle-vane" the artistic touch and architectural correctness that no other TV Antenna has ever had.



the *Circle-vane*
first of the new antennas
in the **WARD STYLECRAFT LINE**

Antennas, styled to the modern tempo . . . cleverly patterned to enrich the appearance of any house . . . expertly engineered to give finer pictures . . . skillfully designed by the famous Dave Chapman, (S.I.D.) . . . these new Ward Circle-vane Antennas complement the home and add dignified charm and beauty. Everybody, dealers and owners alike, have been waiting for "something new" in antennas — The new, finer Ward Circle-vane supplies the answer. The Ward Circle-vane is constructed of aluminum elements with a cross-arm of durable Permatube . . . Comes completely pre-assembled.

Be first with this Ward FIRST in your territory. Order today.

THE WARD PRODUCTS CORP.
DIVISION OF THE GABRIEL COMPANY




1148 Euclid Avenue, Cleveland 15, Ohio • In Canada: Atlas Radio-Co., Ltd., Toronto, Ont.

For the Technician

Useful Products for Sales and Service

Rex UHF CONVERTERS

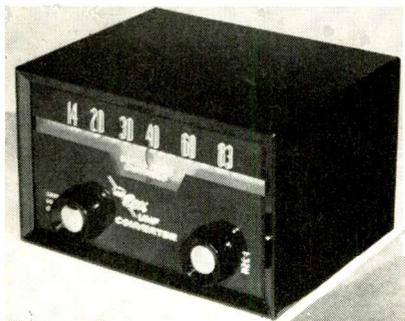
Designed for stability and high signal-to-noise ratio, models UC-1 and UC-2 both feature a silver printed-circuit tuner. Quiet, efficient performance, easy connection to standard receivers, and unimpaired reception of existing VHF channels are claimed for these converters.



The units normally convert to Channel 5 or 6, but can be used on Channel 4 without adjustment. Model UC-2 is intended for use in metropolitan areas up to 15 miles from the transmitter. List prices: model UC-1, \$39.50; model UC-2, \$29.50. Rex Electronics Corp., 1351 DeLoss Street, Indianapolis 2, Indiana.—TECHNICIAN


South River MAST MOUNT

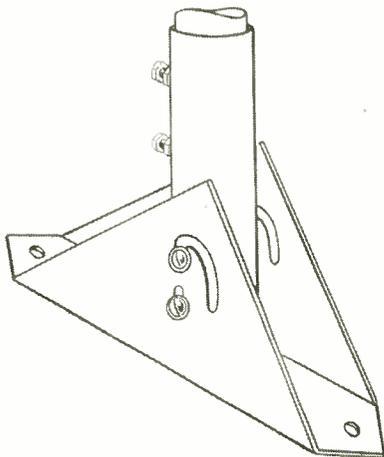For use on either a flat or pitched roof, model RM-15 is claimed to simplify one-man installation techniques while assuring vertical posi-



tioning of the mast. Mast and antenna are set in the base, then "walked up" to the vertical position and locked. South River Metal Products, South River, N.J.—TECHNICIAN


Telco UHF ANTENNA

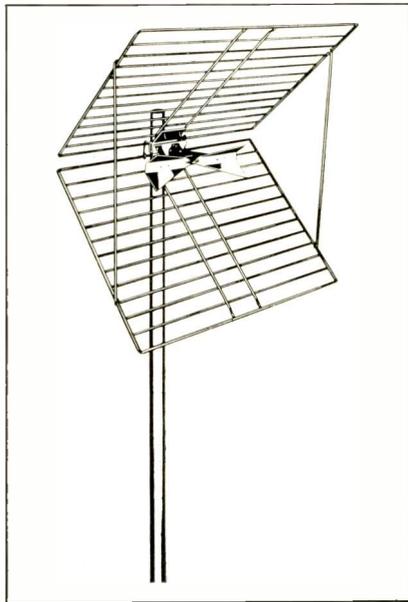

Rapid three-step installation is claimed for model 8984 UHF corner reflector antenna. Pre-assembled at the factory, the antenna is plated to prevent corrosion and comes with a vibration-proof mast bracket. Television Hardware Mfg. Co., Div. General Cement Mfg. Co., 904 Taylor Street, Rockford, Ill.—TECHNICIAN

Alliance TENNA-ROTORS

The model U-83 Tenna-Rotor provides automatic rotation to any pre-selected stop position; model T-10, the manually operated unit, features a control bar across the top of the rectangular control case. Other improvements over older models made by the same manufacturer include a die-cast housing on rotator, faster rotation, new magnetic brake, more accessible terminal block and guy wire attachment on clamp plate. Both models are priced at \$44.95. Alliance Mfg. Co., Alliance, Ohio—TECHNICIAN.

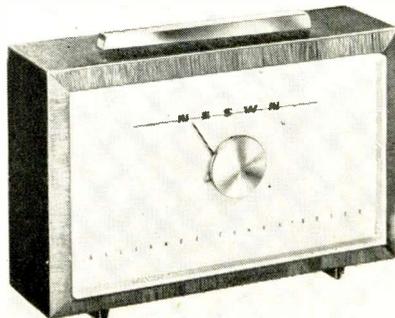

Vineta TV TURNTABLES


The Vineta model 14 turntable is of welded wrought-iron with ball-bearing rotor. Adjustable for any TV set up to 32" wide; will support up



to ½ ton. Legs are 22" high. List price, \$14.95. The same manufacturer makes a model P-104 with table-top in natural mahogany finish, and a model P-106 with limed oak table-top finish. Both list at \$24.75. Vineta Mfg. Co., 2738 No. Sheffield Ave., Chicago 14, Ill.—TECHNICIAN.

M-S TV TOWERS

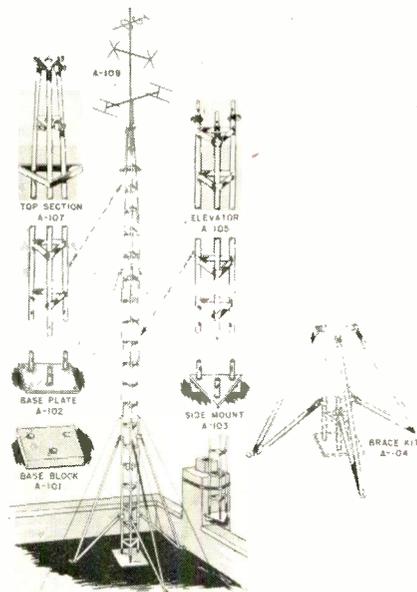Mechanical Steel Tubing Corporation's line of TV towers and telescoping masts includes 10-foot elevator sections which can be used to erect towers from 70 to 150 feet in



height; also telescoping masts which can go up to 50 feet, and a one-piece 20-foot "Economy Jiffy Tower." Mechanical Steel Tubing Corp., 1801 Eighth Ave., Brooklyn 15, N.Y.—

Sprague Capacitor Guide

Intended to supplement the *Sprague TV Capacitor Replacement Manual*, this brown and yellow card, *Supplement C-45*, shows listings of Sprague Twist-Lok electrolytics being used in almost every 1953 model TV set. Available from Sprague distributors.

CBS Substitution Chart

This TV picture tube substitution chart lists all magnetically-deflected tubes, regardless of make. Physical and electrical differences are given so that the technician may decide which tube may be substituted for another, with a minimum number of alterations to the receiver. May be obtained from CBS-Hytron distributors or CBS-Hytron, Danvers, Mass.

Weller Guns as Xmas Gifts

A complete package of Christmas sales helps is available to distributors and dealers by Weller Electric Corporation, Easton, Pa. Weller experience over several years has shown their soldering gun to be a hot Christmas item among Servicemen and Mechanics.

A special 3-dimensional counter display promotes the guns as gifts and shows them off to best advantage. Side panels illustrate the great number of jobs that can be done with Weller Guns.


Hi-Fi Speakers from England Are Marketed by Beam

Beam Instruments Corp., 350 Fifth Ave., New York, N. Y., has announced a complete new line of full-range high-fidelity loudspeakers, manufactured especially for the American audio market by the Whitely Electrical Radio Co. in England, and sold in the U.S. under the brand name Beam "Stentorian." The line includes "Duplex" twin-concentric speakers with crossover networks which are offered in 10 and 12-in. models. Also available is a complete range of high-frequency tweeters, woofers, and single-cone direct-radiator type loudspeakers. All the speakers in the line incorporate a low frequency cone of a new design. A new method of cone processing is said to bring low frequency response down to about 20 cycles, without loss of sensitivity.

Also exhibited by Beam was a new development by Whitely, a Quadruplex wide-range speaker system, the first integrated design employing four independent driving mechanisms on a common axis.



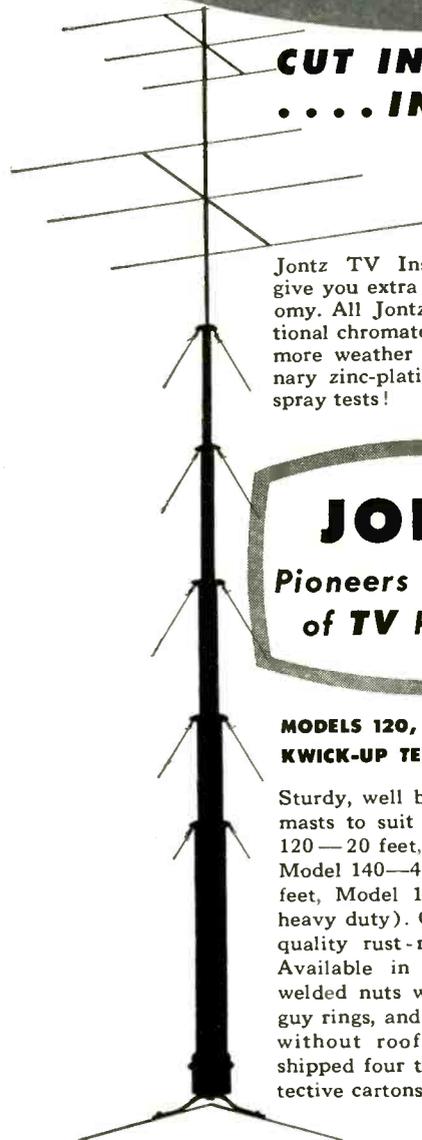**CUT INSTALLATION COSTS
... INCREASE PROFITS**



Jontz TV Installation Accessories give you extra quality, greater economy. All Jontz masts have an additional chromate coating . . . six times more weather protection than ordinary zinc-plating, as proved in salt spray tests!

JONTZ
Pioneers in the field
of TV Reception

**MODELS 120, 130, 140, 150, 150A
KWICK-UP TELESCOPIC MAST**


Sturdy, well built, good-looking TV masts to suit any location . . . Model 120—20 feet, Model 130—30 feet, Model 140—40 feet, Model 150—50 feet, Model 150A—50 feet (extra heavy duty). Constructed of highest quality rust-resistant steel tubing. Available in complete package of welded nuts with set bolts, six-way guy rings, and cotter keys . . . with or without roof mounts. All masts shipped four to a set in special protective cartons.

Your inquiries will receive prompt attention.

Write us for details today!


QUALITY CONSTRUCTION

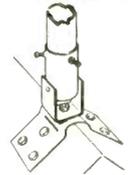Jontz masts are made of highest quality electric weld steel tubing, with heavy zinc galvanized coating . . . your assurance of tubular strength and durability.



APEX MOUNT, MODEL A-S

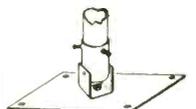4-way swivel mount for any type of installation. Fully adaptable to flat surface, peak roof, or corner mounting.



ROTARY MOUNT, MODEL S

4-way rotary base mount. Fits along roof peak for safe, easy installation.



GUY RINGS BY JONTZ

The answer to your guy ring needs. Handy Jontz guy rings may be used with either 3 or 4 guy wires . . . your choice of 5 I. D.'s.



QUALITY



ECONOMY

MANUFACTURED BY

JONTZ MANUFACTURING CO.

1101 East McKinley, Mishawaka, Indiana, Mishawaka 5-5178

SERVICE ASS'N REPORTS

LBRT Is Active in Southern California

Covering all of southern California, the Long Beach Radio Technicians Assn. is one of the most energetic groups in the country. It is also the oldest and largest, according to Harry E. Ward, general chairman, public relations division. The Long Beach chapter holds dinner meetings twice monthly, while all chapter presidents and secretaries meet monthly for general discussions on common problems.

Current officers of the Long Beach group are Joseph Martin, president; Fred Abrams, vice-president; Merlyn Cochems, secretary; Clarence Spencer, treasurer.

RTSA of Buffalo, N. Y.

Instituted in November, 1951, the Radio Television Service Assn. of Buffalo (N.Y.) is one of many organizations rapidly gaining recognition. Meetings are held on the first Monday of each month at the Hotel Lafayette in Buffalo. Dues are \$12 a year plus a \$5 initiation fee. Present officers of the group are Ferdinand J. Lynn, president; Clarence Thielke, vice-president; John G. Wick, secretary; William Harrington, treasurer; William Wagner, sergeant-at-arms. Wick is a member of a prominent Buffalo law firm.

NETSDA at Trenton, N. J.

The National Electronic Technician And Service Dealers Assoc. (NETSDA) met in Trenton, N. J. Sunday October 4th in the Stacy-Trent Hotel. President Roger Haines of Haddonfield, N. J., presided. Among the items of business conducted were: Plans for the proposed Eastern Conference which is scheduled for Philadelphia, Pa. in early February, dates to be announced. Samuel Brenner, President of PRSMA, associating with the newly formed Philadelphia Council, was appointed Chairman of the Conference arrangements for NETSDA. Max Leibowitz, President of the New York State Federation was appointed co-chairman. NETSDA went on record endorsing a TV lecture course for the coming year, which is promoted by many leading manufacturers for NETSDA members.

It was decided by the delegates, that under their charter, three meetings per year will be held. The first

Sundays in February, May and October were selected as regular meeting dates for the organization. The next meeting will be held in Philadelphia, Pa., Sunday, February 7. John Wheaton, 464 Sagamore Avenue, East Williston, Long Island, N. Y. is corresponding secretary, and L. J. Helk, 67 S. Main St., Carbondale, Pa., is in charge of publicity.

Ten Ways to Kill an Association

1. Don't go to meetings.
2. If you do go, go late.
3. If the weather doesn't suit you, don't think of going.
4. If you do attend a meeting, find fault with the work of the officers and members.
5. Never accept office, as it is far easier to criticize than to do things.
6. Get sore if you are not appointed on a committee, but if you are, never attend the committee meetings.
7. If asked by the president to give your opinion on some matter, tell him you have nothing to say.
8. After the meeting tell everyone how things should have been done.
9. Do nothing more than absolutely necessary, but when other members use their ability to help matters along, howl out that the organization is run by a clique.
10. Hold back your dues, or don't pay at all.

—J. Henderson Stock,
Mechanicsburg, Pa.
in NATESA Scope

Texas Town Prepares for UHF

Wholesale Electronic Supply, of Dallas, Tex., has opened its first branch store at 203 S. High, Longview, Tex., under the management of Tom W. Fickling, who had previously traveled the east Texas area since the be-



ginning of the business in November, 1950. The branch is to serve a 100-mile radius of Longview, traveling one other salesman, Charles Renner. Renner will be ably backed up by the experience of Bob Townsend, who has also been with the firm since its inception, except for a year in Korea. As Longview is to have a UHF station in the near future, the firm will house a large stock of TV and radio supplies in its warehouse.

Radio Institute Alumni

The Buffalo (N.Y.) Radio Institute Alumni, an organization of electronic technicians, held its first meeting in February of 1952 in that city's Downtown Branch Y.M.C.A. Membership now exceeds 100. Meetings are held the first Monday of each month, except in July and August.

Since its inception, the BRIA has played host to GE, Philco, Motorola, Sylvania and other companies who have sponsored service clinics and demonstrations at meetings. The organization also provides free service literature and pamphlets for members, according to Philip Oebler, corresponding secretary.

Current officers, in addition to Oebler, are Albert Licata, president; Peter Stasio, vice-president; Edward McGuire, treasurer; David Stephens, sergeant-at-arms.

More Letters From Our Mailbox

Distributor Competition

EDITORS, TECHNICIAN:

How is the ordinary technician to compete with service shops owned and operated by TV manufacturers' distributors? These shops purchase replacement parts at jobber prices and have the prestige of the manufacturers' names. It's a tough struggle against that kind of competition.

10380 W. Chicago MALCOLM R. WRIGHT
Detroit, Mich.

Sets Shipped with Schematics

EDITORS, TECHNICIAN:

I went through the September issue of Technician with a great deal of interest, even down to reading the "Letters to the Editors" column. Mr. J. R. D. wants to know why major television manufacturers do not include schematics with their television sets as do mail-order houses like Sears Roebuck. I would like to advise J. R. D. that every one of our television sets for the past few years has packed with it a complete schematic diagram for whatever chassis is used in the receiver. In addition to this our chassis are clearly stamped with run numbers and model numbers, and they also include a tag which lists the various tests that the set has been subjected to before it left the factory. This tag when returned to us properly filled out enables us to pinpoint whatever problems may be arising in the field and immediately be able to correct the condition.

Lots of success with your new magazine.

Admiral SIDNEY KAPLAN
Distributors Service Manager
New York City Radio & Television

"TUBES TESTED FREE"

Here's What NATESA and President Frank J. Moch Have to Say About This Practice

How many times a day have you found it necessary to ask one of your shop technicians (of which there is great shortage) to drop everything to test a 'bushelbasket' of tubes, which you are expected to test free. In radio days this was not a serious problem since the average set contained only 5 to 12 tubes, most only five. These tubes generally were simple single section tubes. In TV, however, 20 to 30 tubes, many of which are multi-section types, require multiple tests.

Let us analyze this free testing idea. Even with the most efficient technician and the best tester each tube will require a minimum of 2½ minutes per tube. Since good technicians normally used in the shop are paid anywhere from \$2 to \$2.50 per hour simple arithmetic will show that his cost to you per minute is about 4.1 cents, further it is obvious that the cost per tube is 10.25 cents. Consider also that whenever you pull your man off a job he loses time getting back on the track of his mental processes. The tester costs you anywhere from \$80 to \$250. Its life is about 5 years meaning that the cost to you per day is about \$1.00. Thus it is obvious that the actual cost to test a tube runs about 13 cents per tube.

Don't "Absorb" This Cost!

Don't make the serious mistake of thinking that you should absorb this cost since you are making a mark-up on the possible sale of replacement tubes. Actually this mark-up covers the normal costs of handling the tube such as rental of space, insurance, breakage, shrinkage, billing expense, etc. and your profit on your investment. Another factor to consider is that you are not buying good will in testing tubes since most people who bring tubes in for test are 'chislers' who are trying to 'do' a service company out of a service job. After all service is your business and any actions which reduce the possible volume of service are contrary to your best interests. Yet another thing to consider is that after you have tested the tubes you will in all probability be 'pumped' for advice on how to correct the trouble.

You Sell Knowledge

Never forget that you sell knowledge and that therefore you would have to be a class A fool to give it away. Yet another problem faces you; certainly you have sold tubes across the counter only to have the buyer insert them into the wrong socket, one of higher voltage, ruining the tube, and then demanding that you exchange the tube. Your parts jobber justifiably, will not honor such burnt out tubes.

As a summary, tube testing cannot


and should not be done without a charge since definite costs and risks are attendant upon such activities. It is suggested that a charge of 10c or 15c per tube be made to cover these hazards. In any case where the charge is challenged the above facts are sufficient to handle any reasonable person. There is no reasonable reason why you should deprive yourself of income from service and in addition pay for the privilege of doing so.—Natesa Scope

Du Mont Teletron Service

Expansion to new and larger quarters at 760 Bloomfield Avenue, Clifton, N.J. for the teletron service department of Allen B. Du Mont Laboratories, Inc., cathode-ray tube division, has been announced by B. C. Scales, sales manager of the division.

The department coordinates the servicing and adjustments of Du Mont's television picture tubes with distributors and other television receiver manufacturers.

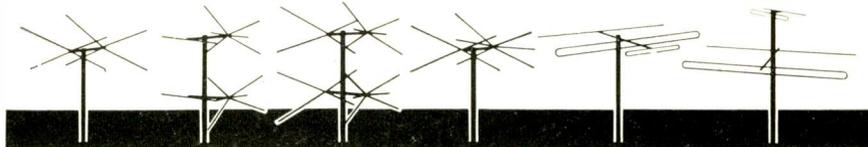The department, under the supervision of Robert G. Scott, sales engineering manager, is moving from 750 Bloomfield Avenue.



CTC-001 Conical with interchangeable elements. 2 or 3 element dipole with conical or hori. reflector. Single or stacked.
 CTS-002 Stacked conical with high frequency element. Also available in Single Bay, No. CTC-002.
 CTS-003 All-Wave, High-Gain stacked conical. High signal-to-noise ratio. Available: Single Bay, No. CTC-003.
 CTC-004 Single 3-element dipole with conical reflector. Also available in Stacked Array, No. CTC-004.
 CIL-001 Inline, Quick folded dipole for all channels. Max. signal strength. Also in kit, CIL-001-C.
 CHL-001 Quick Rig HI-Low folded dipole. All channels. Maximum signal strength. Also in kit, CHL-001-C.

Do it right the first time

with

CASS ANTENNAS

and

TV-RADIO HARDWARE

CASS TV-FM INDOOR

Model CIA-001 for use with all modern TV receivers, giving good reception in most cases where outdoor antennas cannot be used.

CUH-002 SINGLE WITH REFLECTORS

(Can be stacked (not shown) CUH-002)

In addition to bringing you a thoroughly engineered line of antennas for normal outdoor and indoor use, CASS gives you great flexibility and adaptability in meeting difficult situations arising from location, multi-directional signal sources, interference, erection, etc.

This means satisfaction to the customer and full profit to you because, in most cases, it enables you to

MEET ALL CONDITIONS
 SPEED UP INSTALLATIONS
 PROVIDE BETTER RECEPTION

KEEP DOWN INVENTORIES
 AVOID PRICE COMPETITION
 SAFEGUARD YOUR PROFITS

CASS antennas are available in Regular or Thrift lines and are priced to net you real profits because you fix your own markup.

Write for complete details

Some choice territories open for representatives

CASS MACHINE COMPANY Electronics Division

NOTED FOR FINE MACHINE PRODUCTS FOR 15 YEARS

691 Antoinette

TRinity 1-9010

Detroit 2, Michigan

Color vs Black & White (Continued from page 41)

used in dynamic focus in monochrome sets, in which an AC current derived from the horizontal sweep section is suitably modified and added to the focus current. In the color receiver, suitable amounts of horizontal and vertical sweep voltages, appropriately modified in waveshape, are applied to the focus and convergence electrodes; these additional voltages assure correct and uniform focus over the whole screen. Any defect in this section of

the color receiver will tend to cause blurring and/or incorrect coloring in some portion of the picture.

The three guns of the tricolor kinescope must be supplied with signals of the proper color. This job is taken care of by the color adders. These stages add the right amount of "Y" signal to the detected color information, in the proper phase, thus providing the correct color for each gun. The color amplifiers in this section build up the color signals to

levels required by the CRT for proper operation. The DC restorers function in the same way that they do in the monochrome sets. Individual DC restorers, as well as individual amplifiers, are required for each color. Since the colors in this part of the receiver (color adder, DC restorer, color amplifier section) are separate from each other, any (single) trouble in a stage will affect one color alone, providing a clue to the faster localization of the circuit at fault. For example, if the picture contains no reds, then suspicion is narrowed down to the red adder, the red amplifier, the red DC restorer, and the red gun of the CRT.


Since the color receiver is intended to receive black and white transmissions as well as color programs, receiver stages that process color signals must be disabled, to prevent them from giving black and white signals an undesired going-over. The color killer has this watch-dog type function. It performs this function by biasing an amplifier tube to cut-off when no color sync burst is received. The resultant action of this tube prevents the black and white signal from reaching the color detectors.

Defects in Color Killer

There are basic symptoms that defective operation of the color killer may introduce: 1—If the monochrome signal is permitted to get to the color detectors, the picture will probably have a meaningless, constantly-shifting coloring. 2—If the color signal is cut off from the color detectors, it will be reproduced as a black and white picture. Which basic symptom will manifest itself depends on what component goes bad.

The keying pulse applied to the color killer prevents it from being triggered by the wrong signals, and improves its performance in the presence of noise.

The blocks labeled *Color Detector*, *Filters*, and *Color Amplifiers* and *Color Sync*, 3.58 MC and *Control* will be discussed in the article to follow. For the present, it will suffice to point out that the color detectors (also called *decoders*) remove or detect color information from the carrier-modulated signal applied to them; the color amplifiers amplify the (unseparated) colors; and the filters remove cross-talk and spurious signals. The color sync section keeps the color detectors working in proper phase with respect to the transmitted color sync signal.

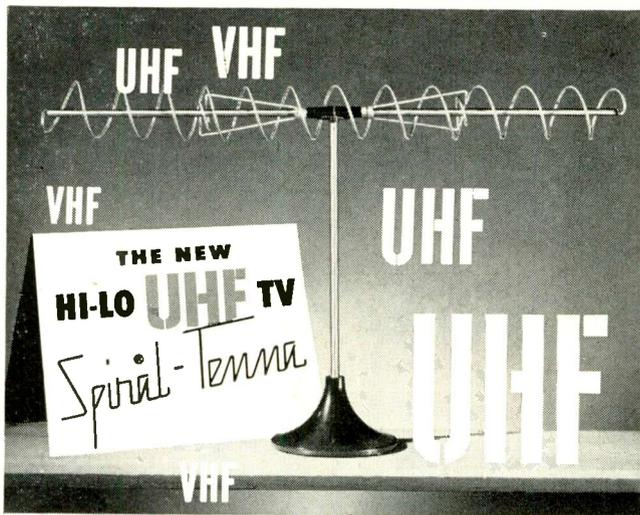

Peak Performance for Indoor UHF and VHF Television Reception

Model 202 U-V

Now — the nationally advertised, consumer accepted HI-LO TV Indoor Spiral-Tenna is applicable for both VHF and UHF with our exclusive UHF antenna adapter from channels [2-83]. But, you still get the volume by selling at the same low, low price.

The Hi-Lo UHF antenna adapter is available separately for all previous HI-LO antennas. List Price \$2.00.

Sold by recognized jobbers

U. S. Patent No. 2,495,579 Canadian patents 1951 — other patents pending

ORDER HI-LO UHF-VHF TV Spiral-Tenna TODAY!

Hi-Lo TV ANTENNA CORP.
3540 N. Ravenswood • Chicago 13, Illinois

at the same
low list price!

\$9⁹⁵
LIST PRICE

CLOSING DATES FOR

TECHNICIAN
TELEVISION • ELECTRONIC • RADIO • AUDIO • SERVICE

1st of preceding month for all ads requiring proofs, composition, foundry work, key changes, etc.

10th of preceding month for complete plates only—no setting.

10th of month—Publication Date. Cancellations not accepted after 1st of preceding month.

CALDWELL-CLEMENTS, INC., 480 LEXINGTON AVENUE, NEW YORK 17

REP NEWS

Perlmuth-Colman Moves to Larger Quarters

The firm of Perlmuth-Colman & Associates, who are celebrating their thirtieth year in the manufacturer's representative business in the California-Arizona territory, announce their removal to new and enlarged quarters at 2419 South Grand Avenue, Los Angeles 7, Calif. These new facilities include modern offices, as well as conference and sales rooms and larger warehouse space, which will enable them to offer fast efficient service to their principals and customers.

Rohn Reps

Rohn Manufacturing Company, 116 Limestone Bellevue, Peoria, Ill., announces the following appointments as sales representatives for the Rohn tower and accessories line: W. B. Golliver, 1003 Grandview Ave., Boulder, Colo. Territory: New Mexico, Colorado, Utah, Wyoming. The Branum Co., 123 Manufacturing St., Dallas, Texas Territory: Texas, Oklahoma, Louisiana, Arkansas. Arthur Hess, 62-07 68th Ave.,

Brooklyn 27, N.Y. Territory: Upper State New York. Sam Karns Company, 36 Oak Avenue, Tuckahoe, N.Y., Territory: Metropolitan New York, Northern New Jersey.

Interested distributors are invited to contact these representatives.

Plastic Capacitors Names Rep


Plastic Capacitors, Inc., Chicago, has appointed the Conrad R. Strassner Co., 1865 N. Western Ave., Los Angeles, as its exclusive representative in California, Arizona, Nevada and New Mexico. Plastic Capacitors specializes in the development and production of capacitors.

Atlas Sound's New Rep at Minneapolis

Robert C. Reinhardt, president of Atlas Sound Corp., 1451-39th St., Brooklyn 18, N.Y., manufacturers of the complete Atlas line of public-address loudspeakers and microphone stands and accessories, has confirmed the appointment of Clark R. Gibb as sales rep for the territory of Minnesota, Western Wisconsin and North and South Dakota.

Well-known for his technical and merchandising experience, Mr. Gibb will have his business headquarters at 312-16th Avenue, S.E., Minneapolis 14, Minn.

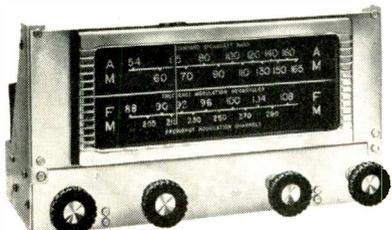Why Count Profits in Small Change? WHEN YOU CAN STACK IT IN \$\$\$



FAMOUS MAKE HI-FI AMPLIFIER WITH AM-FM TUNER 30 - 15,000 CPS

LATEST MODEL

THE LOWEST PRICED QUALITY AM-FM HI-FI AMPLIFIER ON THE MARKET!

Features

- Complete self-contained AM-FM Tuner and Hi-Fidelity Amplifier
- Push-Pull Audio Output—10 Watts Undistorted
- Equipped with large output transformer tapped for 3-2 and 8 ohms
- Full Range Bass & Treble Control
- FM Band 88 to 108 MC Hi-Sensitivity
- Built-in FM & Hi-Gain Ferrite Antenna Input for AM
- Large illuminated slide-rule dial
- Tuner and chassis completely shock mounted
- Provision for Phonograph Input
- Provision for operating additional Audio Amplifier
- Separate Power Socket
- All hardware and instructions for mounting
- Nine Tubes 1-6BE6, 1-6CB6, 2-6AU6, 1-12AX7, 1-6AL5, 2-6V6, 1-5Y3
- Operates on AC 117 volts, 60 cycles
- Size 12 1/2" wide, 5 1/2" deep, 7 1/2" high; Weight: 11 lbs.


REMEMBER!! AN AM-FM TUNER WITH 10 WATT HI-FI AMPLIFIER NEVER BEFORE SOLD AT THIS PRICE . . . \$52.00 FOB, OUR WAREHOUSE. FAMOUS MANUFACTURER'S NAME OMITTED BECAUSE OF SPECIAL PRICE! MONEY BACK GUARANTEE!! SEND 25% WITH COD'S!!

WIRE WRITE PHONE QUANTITIES LIMITED

S & R ELECTRONICS, Inc.

Tel. COrtland 7-4710 • 136 Liberty St. • New York 6, N.Y.

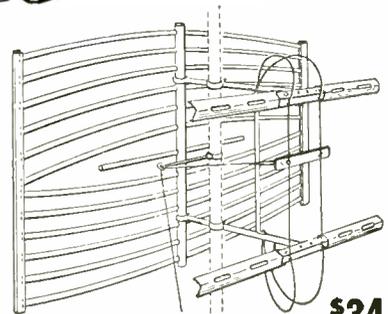Dealers and TV Service Organizations selling DAVIS SUPER-VISION ALL-CHANNEL TELEVISION ANTENNAS do count their PROFITS IN DOLLARS



\$34.95

DAVIS SUPER-VISION

Trade Mark Reg.

SOLD TO YOU WITH A MONEY-BACK GUARANTEE

DON'T WAIT! . . . Get the "BIG DOLLAR PROFIT FACTS" from our Jobber's Salesman in your area. We will get him in touch with you. USE THE COUPON.

BUILT BY AMERICA'S FASTEST GROWING ANTENNA MANUFACTURER

Copyright 1953

DAVIS ELECTRONICS TR-4
BOX 1247, Burbank, California

SIRS: RUSH INFORMATION TO ME AS CHECKED:

Send Complete Information and Technical Data on New SUPER-VISION ANTENNA.

Send Name and Address of NEAREST JOBBER.

Name _____

Street _____

City _____ State _____

TWO REASONS for the TV Servicing Industry's Greatest Publishing

SUCCESS

1 **GIANT-SIZE EDITORIAL SERVICE!** Yes, **TECHNICIAN's** editorial is *giant-size in quality* (thanks to the largest and most experienced staff in the field) . . . *giant-size in quantity* (giving the reader far, far more helpful service and installation features than any other magazine in the field). That's why **TECHNICIAN** is winning increasing leadership in trade paper surveys to the nation's TV servicemen.

COMPARE —

| PUBLICATION | NUMBER EDITORIAL PAGES SEPTEMBER, 1953 | TECHNICIAN'S EDITORIAL SPACE IS GREATER BY— |
|--------------------|---|---|
| TECHNICIAN | 77.6 | |
| Service | 53.8 | 44 % |
| Service Dealer | 40.0 | 94 % |
| Service Management | 25.6 | 203 % |

(TECHNICIAN is not compared with the television newstand magazines in the field, because they dilute their editorial with features for students, experimenters, and amateurs.)

The editorial pages in **TECHNICIAN** include the famous **CIRCUIT DIGEST** feature that gives schematics and service data on large quantities of TV sets currently reaching the market. Exclusive with **TECHNICIAN**, it's the most costly editorial feature ever prepared by any trade paper. Servicemen from coast to coast have acclaimed **CIRCUIT DIGESTS** in thousands of voluntary testimonials!

Remember—**TECHNICIAN** is the magazine now being credited with upgrading the editorial content of all service publications—and that benefits not only the readers, but the advertisers, too!

2 **AD ACCEPTANCE POLICY PROTECTS MANUFACTURERS!** Advertising quoting cut-prices is accepted only if the advertiser can show the manufacturer's consent. Otherwise, the advertiser must choose between the mention of the brand name or the price—but may not use both. **TECHNICIAN** protects the manufacturer's equity in his nationally advertised products.

FIRST! FIRST! FIRST! FIRST! FIRST!

First in servicemen's preference! **First** in number of editorial pages! **FIRST** in upgrading editorial to advertisers' benefit! **First** in circulation! **First** in economy! **First** in price-protection for manufacturers! **First** in experience!

No matter how you look at it, **TECHNICIAN** is the *first* publication in the TV-service field. Make it *first* on your media schedule, too.

FIND OUT FOR YOURSELF

Prove to yourself—at our expense—that the nation's servicemen *prefer* **TECHNICIAN**. Here's how: Pick any group of servicemen listed in the yellow pages of any phone directory. (They must have a phone.) Ask them by mail what television service publication is most helpful in their work. Tabulate the answers. We'll underwrite your costs, provided you let us use the results. Why not accept our challenge and write us for details today?

TECHNICIAN • CALDWELL-CLEMENTS, INC. • 480 Lexington Avenue • New York 17, N. Y.

Magne-Pulse RECORDER

The Magne-Pulse recorder is capable of detecting and indicating the presence of intermittent troubles in radio and TV receiver circuits; unit sounds a buzzer and lights a lamp when an intermittent defect occurs. The instrument contains three VTVM circuits which may be used to monitor three different voltages simultaneously. When the defect causes a voltage deviation from normal, the associated VTVM circuit detects the deviation and causes the appropriate lamp to light and the buzzer to operate. The lighting and buzzing continue even if the voltage returns to normal. A manual reset is provided to turn the warning signals off. AC or DC voltages may be monitored. Magne-Pulse Corp., 140 Nassau St., New York 38, N. Y.—TECHNICIAN.

Acrolite PLASTIC SPRAY

Acrolite's new plastic protective coating is a heavy-duty acrylic plastic made to insulate, waterproof, and stop rust and tarnish. It will eliminate TV "highlights" and corona, and prevent antennas from rusting, according to the manufacturer. A single can (12 oz.) retails for \$1.79. Acrolite International, Hillside, N.J.—TECHNICIAN.



"Better make sure first that it's equipped with a Jensen needle."

SERVICE MANAGERS— WHAT IS YOUR TUBE E.Q.* RATING?

CHECK ONE

- 1.—Are you buying all your tubes at over 60% off list? . . . (YES)—(NO)
- 2.—Are you receiving first grade, standard brand tubes instead of rewashed and rebranded tubes (YES)—(NO)
- 3.—Are your recalls because of inferior tube failures down to nil (YES)—(NO)

If your answer is YES to all three, you are "ON THE BALL." If NOT well—it's time to wake up and look around.

In either case you can increase your E.Q.* rating by taking advantage of our new direct sales to service department. Inaugurated to insure prompt delivery of top grade individually boxed standard brand tubes far below market prices.

*E.Q. Efficiency Quota

COMPARE THESE PRICES WITH YOUR PRESENT INVOICES.

| TYPE | PRICE | TYPE | PRICE | TYPE | PRICE | TYPE | PRICE |
|-------|-------|--------|-------|-------|-------|---------|-------|
| OZ4 | .52 | 6BC5 | .75 | 6U8 | .99 | 12SK7 | .66 |
| 1B3GT | .89 | 6BE6 | .65 | 6V6GT | .65 | 12SN7GT | .79 |
| 1X2 | .89 | 6BG6G | 1.85 | 6W4GT | .62 | 12SQ7 | .57 |
| 5U4G | .59 | 6BQ6ET | 1.29 | 6W6GT | .79 | 19BG6GT | 2.15 |
| 5V4G | .95 | 6CB6 | .70 | 6X5GT | .54 | 25BQ6GT | 1.35 |
| 5Y3GT | .46 | 6CD6G | 1.85 | 6X8 | .89 | 25L6GT | .64 |
| 6AC7 | 1.10 | 6J5 | .55 | 12AT6 | .54 | 25W4GT | .67 |
| 6AG5 | .75 | 6J6 | .80 | 12AT7 | .94 | 35L6GT | .67 |
| 6AK5 | .89 | 6K6GT | .61 | 12AU7 | .74 | 35W4 | .47 |
| 6AL5 | .59 | 6S4 | .60 | 12AV7 | .94 | 35Z5GT | .46 |
| 6AQ5 | .63 | 6SA7 | .66 | 12AX7 | .73 | 50A5 | .81 |
| 6AT6 | .50 | 6SK7 | .63 | 12BA6 | .67 | 50B5 | .65 |
| 6AU6 | .61 | 6SN7GT | .75 | 12BE6 | .68 | 50C5 | .68 |
| 6AV6 | .50 | 6SQ7 | .63 | 12BH7 | .89 | 50L6GT | .64 |
| 6BA6 | .62 | 6T8 | .89 | 12SA7 | .67 | | |


Over 400 other types equally low priced, consult us for your special purpose tubes. All our tubes are standard brand, first quality and carry standard RMA guarantee.

WRITE — WIRE — PHONE — IMMEDIATELY — TODAY

S&R ELECTRONICS, INC.

Telephone COrlandt 7-4710 136 Liberty Street • New York 6, N. Y.

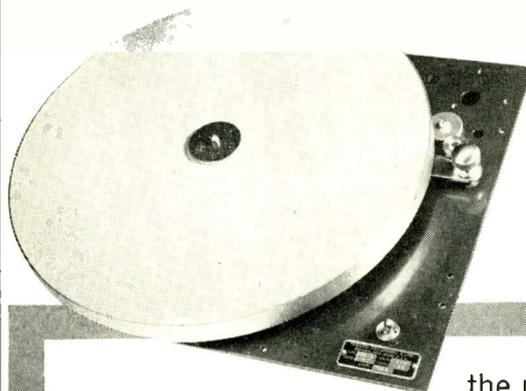TERMS—Cash with order or 25% deposit—balance COD. Net 10 days to rated accounts. All prices are Net FOB, our warehouse.



sell this one
for **PROFIT**
and
CUSTOMER
SATISFACTION

the precision engineered

PRESTO 15-G

turntable

designed and manufactured by the world's largest producer of professional tape and disc recording equipment.

- Heavy, cast aluminum 12" table
- Precision, constant speed motor
- Instant 3-speed selection
- Quiet, rumble-free performance

Retails at \$53.50 (chassis only)

Write for dealer arrangements and attractive counter display





First Again!

to bring you the alignment tool you've been asking for!

X-57

PLASTIC "Long Slim" TELEVISION SET ALIGNMENT TOOL

Made of New . . . Super-tough X-57 Plastic

Steel-like Strength . . . yet highly flexible

Extra Slim . . . only 1/8" in diameter

All Insulated . . . high di-electric

Stronger . . . More Durable than ordinary fibre alignment tools

Blade

| Number | Length | List |
|--------|--------|--------|
| 8987 | 7" | \$1.00 |
| 8988 | 12" | 1.50 |
| 8989 | 16" | 2.00 |

SUPER-TOUGH TIP

WRITE FOR YOUR COPY OF THE NEW G-C No. 156 CATALOG

GENERAL CEMENT MFG. CO.
904 TAYLOR STREET
ROCKFORD • ILLINOIS

NEW BOOKS

TELEVISION FUNDAMENTALS. By **Kenneth Fowler and Harold B. Lippert.** McGraw-Hill Book Co., Inc., 330 West 42nd Street, New York 36, N. Y. 524 pages, \$7.

Television Fundamentals presents, on a fairly simple level, the basic principles needed by the radio technician to install and service TV sets. The first 12 chapters deal with the theory of operation of the various TV receiver sections. Chapter 13 discusses receiving antennas and their installation; Chapter 14, test equipment and alignment; Chapter 15, servicing; Chapter 16, troubleshooting by picture analysis.

HOW TO USE SIGNAL AND SWEEP GENERATORS. By **J. Richard Johnson.** John F. Rider Publisher, Inc., 480 Canal Street, New York 13, N.Y. 144 pages, paper binding. \$2.10.

This book is beamed at radio and TV technicians, as well as students and experimenters. It discusses the various types of signal and sweep generators available; their basic operating principles; controls and adjustments present; set-up and adjustment of generators for various

applications; and generator maintenance. Only basic knowledge of radio theory needed to understand the book.

STATEMENT REQUIRED BY THE ACT OF AUGUST 24, 1912, AS AMENDED BY THE ACTS OF MARCH 3, 1933, AND JULY 2, 1946 (Title 39, United States Code, Section 233) SHOWING THE OWNERSHIP, MANAGEMENT, AND CIRCULATION OF

TECHNICIAN published monthly at Bristol, Conn., for October 1, 1953.

1. The names and addresses of the publisher, editor, managing editor, and business manager are: Publisher, M. Clements, Rumson, N. J. Editor, Orestes H. Caldwell, Catrock Road and Bible St., Cos Cob, Conn. Managing Editor, Sol Heller, 124 W. 93rd St., New York 25, N. Y. Business Manager, M. H. Newton, 583 W. 215th St., New York, N. Y.

2. The owner is (if owned by a corporation its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding one per cent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given.) Caldwell-Clements, Inc., 480 Lexington Avenue, New York 17, N. Y.; M. Clements, Rumson, N. J.; O. H. Caldwell, Catrock Rd. and Bible St., Cos Cob, Conn.

3. The known bondholders, mortgagees, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.) None.


4. Paragraphs 2 and 3 include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting; also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner.

(Signed) ORESTES H. CALDWELL
Sworn to and subscribed before me this 29th day of September, 1953.

ALICE H. POND
Notary Public, State of New York
No. 03-8406175
Qualified in Bronx County
Cert. filed with N.Y. Co. Clerk
Commission expires March 30, 1954

It's proven—

THE FRETARAY IS HERE TO STAY

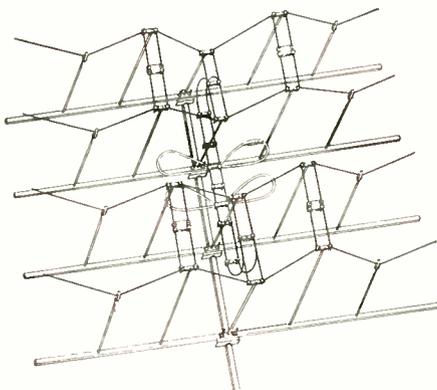

The Fretaray has and will continue to set the pace in the antenna industry. One antenna, one lead in for all channels UHF and VHF. Let the Fretaray's past performance speak for itself by letting it sell itself.

THE FINEST IN HIGH GAIN ALL CHANNEL ANTENNAS, IN THE PAST, PRESENT AND FUTURE



INCORPORATED

406 N. Craig St., Pgh. 13, Pa.

Patents Pending

OF COURSE IT'S

AEROVOX

FOR ALL TYPES
OF MICAS!



Yes sir, it's still the most complete line. Including types that meet JAN specs. Pick just the right mica capacitor from over two dozen different types.

Postage-stamp or tiny wafer types; high-voltage heavy-duty types in different terminals and mountings; silver micas; porcelain-cased types; etc. Choice of tolerances.

Don't fumble, fuss or fume! Let Aerovox micas fit your particular needs.

Ask your distributor for Aerovox mica capacitors — the outstanding selection of types.



FOR RADIO-ELECTRONIC & INDUSTRIAL APPLICATIONS
AEROVOX CORPORATION
NEW BEDFORD, MASS., U. S. A.

In Canada: AEROVOX CANADA LTD., Hamilton, Ont.
Export: 41 E. 42nd St., New York 17, N. Y.

MFRS' Catalogs & Bulletins

Admiral Antenna Catalog

The accessories division of Admiral Corp. published October 15, a 20-page, two-color catalog listing antennas, masts and towers, tables and bases, multiple installation equipment, transmission line and hardware. Raymond W. Peterson, manager of the division, said the catalogs are being offered with distributors' imprints.

"Our department's sales have increased over 300% over 1952 and many distributors are discovering that accessory sales are easy to get, easy to handle, and profitable."

Vee-D-X Antenna Booklet

A 30-page illustrated booklet describing the entire Vee-D-X line of UHF and VHF antennas and accessories is now available. Thirty-six different products, including the company's antenna rotator, are described in this wallet-sized guide. For a copy, write to LaPointe Electronics Inc., Rockville, Conn.

Capehart Serv-U-Facts

Capehart's new Serv-U-Fact booklet presents schematic and alignment data, tube location guide, waveforms and voltage readings on current Capehart receivers. This material appears on loose-leaf charts bound into a sturdy easel-type binder. Adequate room is provided for insertion of new charts. The large, readily-removed schematics will no doubt be appreciated by servicemen. Net price of Serv-U-Facts is \$3. Copies may be obtained from Capehart distributors or the Capehart-Farnsworth Co.'s service department in Fort Wayne, Ind.


Vidaire Bulletins

Two bulletins published by the Vidaire Electronics Mfg. Co., and titled *Better Sound for Your Pictures* and *TV Interference and Its Remedies*, are available. The first one describes methods of improving sound quality in TV receivers; the second is devoted to TVI causes and cures. Write Vidaire Sales Office, 6 E. 39th St., New York, N. Y., for a copy.

Delco Electronic Catalog


Bulletin 6A-100 is a 63-page catalog listing the complete line of Delco electronic parts, including tubes, vibrators and TV components. Available from United Motors Service Div. of General Motors Corp., GM Bldg., Detroit 2, Mich.

TV Voltage Trouble?

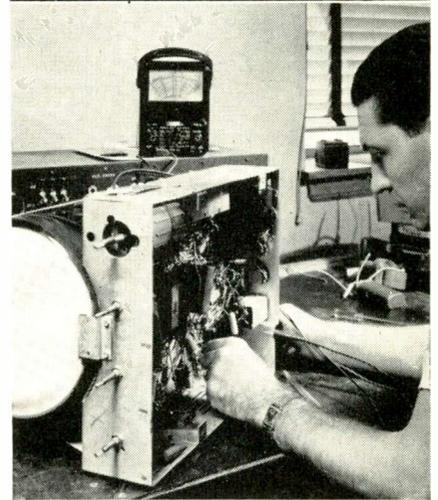

TeleVolt AUTOMATICALLY corrects fluctuating line voltage


Low voltage causes poor television reception. If your customers' line voltage is bad, supply the television manufacturers' specified voltage by plugging in a SOLA TeleVolt Constant Voltage Transformer between the set and wall outlet. It will also protect costly components against damaging high voltage surges. The TeleVolt is a patented voltage regulator that automatically stabilizes voltage within $\pm 3\%$ with line fluctuations as great as $\pm 15\%$; it is not a voltage booster.

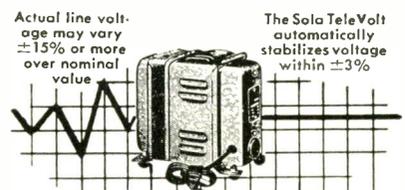

Write today for Bulletin AE-CV-175
or see your electronic distributor

SOLA Tele Volt
Automatic Constant Voltage
TRANSFORMERS


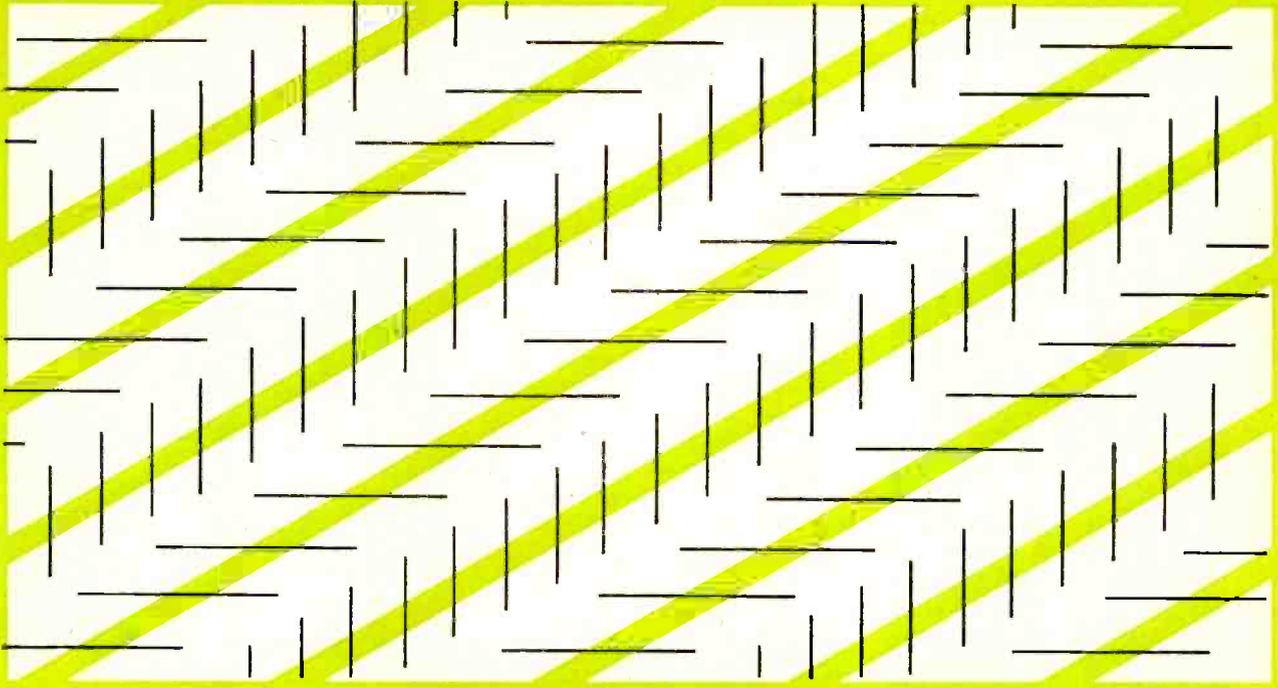
SOLA ELECTRIC CO.
4633 W. 16th St. Chicago 50, Ill.



THINGS ARE **NOT** AS THEY SEEM...

The long lines are strictly parallel—that they appear otherwise is an optical illusion.

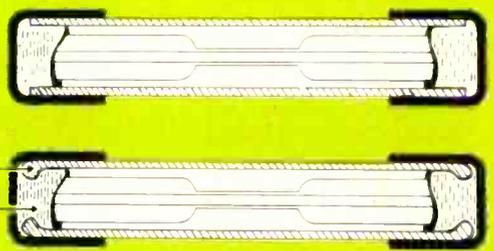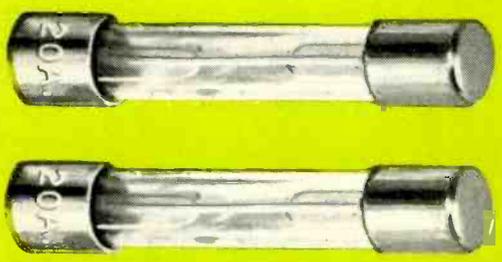This fuse merely has the metal caps cemented to the glass.



The difference between these two fuses is no illusion...

This Littelfuse has the caps locked to glass like this. The ends of the glass are formed^A. The solder which is bonded in a separate operation to the cap reflows through the small aperture and spreads out to form a permanent collar-button lock^B between cap and glass—impervious to moisture and vibration. The exclusive Littelfuse feature eliminates fuse failure due to loose caps.

LITTELFUSE

DES PLAINES, ILLINOIS

Littelfuse leads all other fuse manufacturers in design patents on fuses. Lock-cap assembly patent no. 1922642


ALL "CIRCUIT DIGESTS" TO DATE

Including Current Issue. CIRCUIT DIGEST NOS. 95 to 100 will be found in this issue of TECHNICIAN.

| All Units Are TV Receivers Unless Otherwise Noted | Circuit Digest No. | Circuit Digest No. | Circuit Digest No. |
|---|---------------------------|--|---------------------------|
| ADMIRAL | Circuit Digest No. | DU MONT | |
| Chassis 2242: Models 520M15, 520M16, 520M17. Chassis 22A2A: Models 520M11, 520M12. Chassis 22M1: Models 121M10, 121M11A, 121M12A, 121M11, 121M12, 121K15A 221K16A, 121K17A, 121K15, 121K16, 121K17, 121K45A, 221K46A, 221K47A, 221K45, 221K46, 221K47. Chassis 22Y1: Models 321M25A, 321M26A, 321M27A, 321M25, 321M26, 321M27, 421M15A, 421M16A, 421M15, 421M16, 421M35, 421M36, 421M37, 521M15A, 521M16A, 521M17A, 521M15, 521M16, 521M17 1 | 1 | Chassis RA-164: Model Clinton. Chassis RA- 165: Models Beverly, Ridgewood, Shelburne, Milford, Wakefield 3 Chassis RA-166/167, 170/171: Models 17T350, 21T327, 21T328, 21T329, 21T359, 21T366, 21T376, 21T377, 21T378 | 3 |
| Chassis 19B1: Model 17DX10, 17DX11. Chassis 19C1: Model 121DX12, 121DX16, 221DX15, 221DX16, 221DX17, 221DX26, 221DX38. Chassis 19F1A: Model 121DX11. Chassis 19H1: Model 222DX15 15 | 15 | EMERSON | |
| ANDREA | | Chassis 120166-D: Models 721D, 728D 10 Chassis 120168-D: Models 716F, 717F, 719F, 727D. Chassis 120169-B: Models 711F, 712F, 720D, 732B, 734B 31 Chassis 120174-B: Models 752A, 755A, 784A; Chassis 120198-D: Models 753F, 785C, 785E 91 | 10 31 91 |
| Chassis VM21: Models T-VM21, C-VM21, 2C- VM21, CO-VM21 44 | 44 | ESPEY | |
| ARVIN | | 513-C AM-FM Tuner 70 | 70 |
| Chassis TE331: Models 6175TM, 6179TM 13 Chassis 337-341: Models 7210, 7212, 7214, 7216, 7218, 7219 45 TV Dual Tuner, used in Chassis TE 330,332, 340, 341 75 Chassis TE 359: 9200 series 100 | 13 45 75 100 | FADA | |
| BENDIX | | The "Imperial" Series: Models 17T6, 17T9, 17C2, 17C4 25 Models U2100C, U2150C, U2100T, UDL2100T, UH21T 83 | 25 83 |
| Chassis T14: Models 21K3, 21KD, 21T3, 21X3, OAK3 20 Chassis T17: Models KS21C, TS21C. Chassis T17-1: Model TS17C 50 | 20 50 | GENERAL ELECTRIC | |
| CAPEHART | | "Stratopower" chassis: Models 17C125, 20C107, 21T1, 21C208, 21C204, 21C201, 21C202, 21C214, 21C206 4 UHF-Tuner Model UHF-103 52 "F" Chassis: Models 17C127, 21T14, 21C115, 21C116, 21C117, 21C119, 21C120, 21C121, 17T15, 21T10, 21T12, 21T4 84 | 4 52 84 |
| Chassis CX-36, RF-1P chassis coded R-3, De- flection chassis coded D-4: Models 1T172M, 2C172M, 3C212M, 32212B, 4H212M, B, 5F212M, 6F212M, B, 7F212M, 8F212B, 9F212M, 12F272M, 10W212M, 11W212M 17 Chassis CX-37: Models 1T172MA, 1T172BA, 3C212MA, 3C212MG, 3C212BA, 4H212MA, 4H212BA, 5F212MA, 6F212B, 7F212MA, 8F212- BA, 9F212MA, 11W212MA, 12C13M, 2F213F, 3C213M, 4T213M, 4T213B, 5H213M, 8F213B 37 | 17 37 | GRANCO | |
| CBS-COLUMBIA | | UHF Converter Model CTU 74 | 74 |
| Chassis 817: Model 17T18, 17M18, 17C18. Chassis 820: Model 20T18, 20M18, 20M28 14 Chassis 1027: Models 27C11, 27C21 77 Chassis 750-3: Models 17MO6, 22CO6, 22C38 95 | 14 77 95 | HALLICRAFTERS | |
| COLUMBIA RECORDS | | Chassis A1200D, K1200D or W1200D: Models 1010P, 1012P. Chassis D1200D, L1200D or X1200D: Models 1021P, 1026P. Chassis F1200D: Model 1013C. Chassis G1200D: Models 1022C, 1027C. Chassis U1200D: Model 1056C. Chassis T1200D: Models 1051P, 1055C, 1056C, 1060C, 1061C. Chassis P1200D: Model 1052P. Chassis R1200D: Models 1053P, 1054P. Chassis P1200D: Models 1057C, 1062C, 1063C. Chassis Z1200D: Model 1057U 21 | 21 |
| 360 Phono Amplifier 43 | 43 | HOW TO FIND MONTH in which any CIRCUIT DIGEST APPEARED | |
| CROSLEY | | <i>Circuit Digest Numbers</i> | |
| Chassis 380: Models EU17COM, EU-17TOB, EU-17TOM. Chassis 381: Models EU-21CDB, EU-21CDM, EU-21CDN, EU-21COBa, EU-21- COMa 2 VHF Chassis 392: Models EU-COMUa, 21COBUa, 21CDMU, 21CDBU, 21CDNU (Chassis 392 is very similar to the 380—refer to Circuit Digest No. 2) Chassis 388: Models EU-30COMU, 30COBU 33 Chassis 393: Models EU-21TOLU, EU-21- TOLBU. Chassis 394: Models EU-21COLU, EU-21COLBU 46 Chassis 402: Models F-17TOLH, F-17TOLBH; Chassis 403: Models F-21TOLH, F-21TOLBH; Chassis 404: Models F-21COLH, F-21COLBH, F-21CDLH, F-21CDLBH; Chassis 402-1: Mod- els F-17TOLU, F-17TOLBU; Chassis 403-1: Models F-21TOLU, F-21TOLBU; Chassis 404-1: Models F-21COLU, F-21COLBU, F-21CDLU, F-21CDLBU 82 Chassis 411: Models F-24COLH, F-24COLBH; Chassis 411-1: Models F-24COLU, F-24COLBU 96 | 2 33 46 82 96 | 1- 8 Sept. 1952 9- 16 Oct. 1952 17- 24 Nov. 1952 25- 30 Dec. 1952 31- 36 Jan. 1953 37- 43 Feb. 1953 44- 49 Mar. 1953 50- 58 Apr. 1953 59- 64 May 1953 65- 70 June 1953 71- 76 July 1953 77- 81 Aug. 1953 82- 88 Sept. 1953 89- 94 Oct. 1953 95-100 Nov. 1953 | |
| DE WALD | | Note: Months prior to September, 1953, refer to issues of Television Retailing [predecessor of TECHNICIAN] | |
| Models ET-14OR, DT-163R, DT-163A, ET-170, ET-171, ET-172, ET-191, DT-190D 69 | 69 | HOFFMAN | |
| EMERSON | | Chassis A1300D: Model 1075 38 Model TW-1000 World-Wide 8-Band Portable Radio 49 | 38 49 |
| JACKSON | | Chassis 213: Models 21M903, 21B904, 21P905 32 Chassis 403-24: Models 24M725, 24B726, 24P727 92 | 32 92 |
| MAGNAVOX | | Model J, K-105 Series: CT331, 332, 333, 334, 335, 336, 337, 338, 339, 340, 341, 342, 343, 344, 345, 346, 347, 348, 349 23 UHF Converter Tuner Model 700359 53 107 Series: Chassis CT 358 65 UHF Converter Tuner 595461 (700359 Re- vised) 80 | 23 53 65 80 |
| MALLORY | | TV-101 UHF Converter 58 | 58 |
| MOTOROLA | | Chassis TS-292: Models 21C1, 21C1B, 21F2, 21F2B, 21F3, 21F3B, 21K4, 21K4A, 21K4B, 21K4W, 21K5, 21K5B, 21K6, 21K7. Chassis TS-324: Models 21T4A, 21T4EA, 21T5A, 21T5BA 9 Models TC-101, TC-101B UHF Converters 59 Auto Radio Mopar Models 610T 72 | 9 72 |
| MUNTZ | | Chassis 17B1 or 17B2: Models 2053A, 2054-A, 2055-A, 2056-A. Chassis 17B2: Model 2055-B. Chassis 17B3 or 17B4: Models 2457-A, 2461-A. Chassis 17B5 or 17B6: Models 2158-A, 2159-A, 2162-A 39 | 39 |
| OLYMPIC | | Chassis TK: Models 17T40, 17T48, 17C44, 17K41, 17K42, 17K50. Chassis TL: Models 20T46, 20T47, 20C45, 20C52, 20C53, 20D49, 20K43, 20K51 30 Chassis TMTN: Models 17T56, 17C57, 17K55, 21T58, 21T69, 21T70, 21T74, 21C65, 21C68, 21C72, 21C73, 21D60, 21D64, 21K61, 21K62, 21K63 68 | 30 68 |
| PACKARD-BELL | | Chassis 2720: Models 2721, 2722. Chassis 2710: Models 2723, 2724 60 | 60 |
| PHILCO | | RF Chassis 91, Deflection chassis J-1 used in 1953 Code 126: Models 2269, 2270, 2271, 2273, 1853, 1853L, 2127, 2266, 2268, 2285, 2286, 2287 5 RF Chassis 81, Deflection Chassis H-1: Models 1824, 1825, 1826, 1852, 1852L, 2125, 2125L, 2152, 2152L, 2226, 2227, 2262, 2272, 2272L 22 R-F chassis 97, Deflection chassis J-7: Model 2750 47 All-Speed Record Changer: Model M-24 29 R-F Chassis R-201, Deflection Chassis D-201: Models 4308, 4110, 4108, 3104, 4008 89 | 5 22 47 29 89 |
| RADIO CRAFTSMEN | | AM-FM Tuner C-800 28 | 28 |

(Continued on page 70)

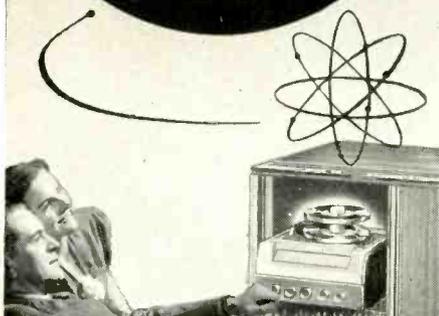These outstanding **SHURE** PICKUP CARTRIDGES provide maximum fidelity of RCA 45 r.p.m. records



"DIRECT DRIVE" CRYSTAL (W31AR)
High output (2.1 volts!) "Direct Drive" cartridge specifically designed for use with all fine-groove records. Universal mounting bracket provides quick, easy installation in RCA-type 45 r.p.m. changers. (Fits 1/2" and 3/8" mounting centers.) Has easy-to-replace needle. For maximum quality, highest output, and low cost, specify Model W31AR at the low list price of only \$6.50.



"DIRECT DRIVE" CERAMIC (WC31AR)
Same as Model W31AR, except for ceramic element and .65 volts output. Highly recommended in areas where heat and humidity make use of conventional crystal cartridges impractical. List price \$6.50



"VERTICAL DRIVE" (W21F)* High-fidelity cartridge. Provides superlative reproduction for 33 1/2 and 45 r.p.m. records. Extended frequency response (50 to 10,000 c.p.s.). Low tracking pressure (only 6 grams) and high needle compliance guarantee faithful tracking and longer record life. Uses quiet tracking Shure "Muted Stylus" needle, scientifically designed for maximum performance and long life. List price \$7.75

*Cartridge with .453 Mount for Oak Changer



SHURE BROTHERS, Inc.

Microphones and Acoustic Devices
225 W. HURON ST. • CHICAGO 10, ILLINOIS
Cable Address: SHUREMICRO

Circuit Digest Index

(Continued from page 69)

Circuit Digest No.

RAYTHEON

Chassis 17T1: Model M1733A, C1735A, C1736A.
Chassis 17T2: Model M-1734A. Chassis 21T1:
Model M-2107A, C-2108A, C-2110A, C-2111A.
Chassis 21T2: Model C-2109A **16**
UHF Tuner **54**
Chassis 21T8: Models UM-2133, UM-2134, UM-
2135, UM-2136, UM-2139, UM-2141, UM-2142,
UM-2144, UM-2145 **94**

RCA VICTOR

Chassis KCS72: Models 17T200, 17T201, 17T202,
17T211, 17T220 **6**
Chassis KCS78 or KCS78B: Models 17-T-301,
17-T-301U, 17-T-302, 17-T-302U, 17-T-310,
17-T-310U **48**
UHF Selector Chassis KCS70: Model U70 **42**
UHF Selector Model U2: Chassis KCS79 **55**
Chassis KCS81: Models 21-D-305, 21-D-317,
21-D-326, 21-D-327, 21-D-328, 21-D-329, 21-D-
330: Chassis KCS81B: Models 21-D-305U, 21-D-
317U, 21-D-326U, 21-D-327U, 21-D-328U, 21-D-
329U, 21-D-330U **67**
Chassis KCS83C: Models 21-S-354, 21-S-362:
Chassis KCS83D: Models 21-S-354U, 21-S-362U
90

REGENCY

UHF Converter Model RC-600 **73**

SENTINEL

Chassis 118: Models 454, 1U-454, 455, 1U-455,
456, 1U-456, 457, 1U-457 **18**
Models 1U-532, 1U-552, 1U-554 **85**

SHERATON

Chassis 250XL: Models T1750, T2150, T1755,
T2120, T2155, C2125 **81**

SPARTAN

Chassis 25D213: Models 5342, 5343, 5382, 5383,
5384, 5386, 5390, 5391 **24**
Chassis 27D213: Models 5342A, 5343A, 5384A,
5386A, 5382A, 5383A, 10352, 10353 **40**
Chassis 29U213: Models 22312, 22313, 23322,
23323 **71**

STANDARD COIL

Tuner Models TV-1532, TV-2232 **86**

STEWART-WARNER

Chassis 9210: Models 9210-C, 21T-9210A,
21C-9210C **34**

STROMBERG-CARLSON

Chassis 421 series: Models 421 TX, 421 CM,
421 CDM **19**
521 Series: Models 521T, 521TO, 521CM,
521CDM, 521C5M, 521C50, 521C5Dec **66**

SYLVANIA

Chassis 1-508-1, 1-508-2: Models 172K, KU,
M & MU; 175B, BU, L, LU, M & MU; 176B,
BU, L, LU, M & MU; 177B, BU, M & MU;
178B, BU, M & MU **12**
Chassis 1-504-1, 1-504-2: Models 105B, 105BU,
105M, 105MU. Chassis 1-510-1, 1-510-2: Models
120B, 120BU, 120M, 120MU, 126B, 126BU,
126L, 126LU, 126M, 126MU **35**
Chassis 1-509-1, 1-509-2: Models 187B, BU,
M, MU **41**
UHF Converter Models C31M, C32M, C33M
87
Chassis 1-518-1, -2, -3: Models 175-18, 372,
373, 375, 376, 377 **97**

TRAV-LER

Chassis 36A2: Models 217-32, 217-33, 220-35,
221-36 **27**

TRUETONE

Model 2D1344A **61**
Chassis 21T2A: Model 2D1326A **98**

MONTGOMERY WARD

Manual 4107A: Model 25WG-3056A **36**
Auto Radio, Model 35BR-6796A

WEBSTER-CHICAGO

Webeor Model 210 Tape Recorder **62**

WESTINGHOUSE

Chassis V-2207-1: Model H-706T16. Chassis
V-2220-1: Model H-708T20 **11**
Model H-803 all channel UHF Tuner **56**
Chassis V-2208-1: Model H-716T17 **63**
Chassis Assembly V-2233-4: Models H-
746K21, H-747K21 **78**
Chassis V-2243-1: Models H-770T21, H-771T21,
H-772K21, H-773K21, H-774K21, H-775K21,
H-776T21 **99**

ZENITH

Chassis 19K22: Models K1812E, K1812R. Chas-
sis 19K20: Models K1815E, K1815R, K1820E,
K1820R, K1846E, K1846R, K1850E, K1850R,
K1880R. Chassis 19K23: Models K2229R,
K2258R, K2286R, K2288E. Chassis 21K20:
Models K2230E, K2230R, K2240R, K2240E,
K2260R, K2263E, K2266, K2266R, K2267E,
K2268R, K2270H, K2270R, K2287R, K2290R,
K2291E **7**

VHF-UHF Turret Tuner **57**

Portable Radio Chassis 5L42: Model L507 **79**
Chassis 22L20: Models L2571R, L2572R,
L2573E, L2574R, L2575E, L2592R, L2593H,
L2876E, L2876R, L2878R, L2879E, L2894HU **88**

BASIC ALIGNMENT DATA

8

Copyright 1953 by Caldwell-Clements, Inc.

WIRE WARNING!

WHY

pay more for questionable quality* tubular TV lead-in wire?
*subject to patent infringement.

LOOK **JSC**

for highest quality license-labeled* Tubular TV Wire...
*JSC Tubular Wire is manufactured under license of Amphenol Pat. 2543696.

DEMAND **JSC**


the most for your wire dollar... get BOTH Quality**! AND Low Price**!
**JSC—Highest in Quality... Lowest in Price

JSC NEW Twin Tubular TV Lead-in Wire...

The best low loss, low cost 300 ohm lead-in for UHF and VHF television.

Rain, snow, dirt or salt deposits do not materially affect impedance and electrical efficiency.
JSC tubular construction contains and protects the concentrated field of energy and reduces to a minimum high ratio signal losses.

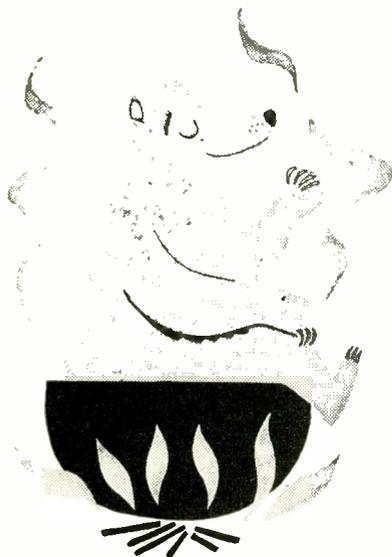Always Look for Orange and Blue Disc of Quality



C-D's new Cub

outlasts other
molded tubulars
in humidity tests!



- Government humidity tests show C-D's to be 3 to 6 times better!
- A better all-around tubular designed specifically for radio and TV service replacement needs!
- Compare its new sleek looks!
- -- and be sure to ask about the new "Cub-Kit".

This time try C-D's NEW CUB! For your nearest C-D distributor see the Yellow Pages of your Telephone Directory. Write for catalog to Dept. RT113, Cornell-Dubilier Electric Corporation, South Plainfield, New Jersey.

CONSISTENTLY DEPENDABLE
CORNELL-DUBILIER
CAPACITORS



There are more C-D capacitors in use today than any other make.


PLANTS IN SO. PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASS.; PROVIDENCE AND HOPE VALLEY, R. I.; INDIANAPOLIS, INDI.; SANFORD AND FOUQUAY SPRINGS, N. C. SUBSIDIARY: RADIART CORP., CLEVELAND, OHIO

INDEX TO ADVERTISERS NOVEMBER, 1953

| | |
|--|---------|
| Admiral Corp. | 5 |
| Aerovox Corp. | 67 |
| All Channel Antenna Corp. | 24 |
| American Phenolic Corp. | 22 |
| American Television & Radio Co. | 72 |
| | |
| Caldwell-Clements, Inc. | 64 |
| Cass Machine Co. | 61 |
| Channel Master Corp. | 8, 9 |
| Cornell-Dubilier Electric Corp. | 71 |
| | |
| Davis Electronics | 63 |
| DuMont Laboratories, Inc., Allen B. . | 23 |
| | |
| Falcon Electronics Co. | 2, 3 |
| Finney Co. | 20, 21 |
| Fretco Inc. | 66 |
| | |
| General Cement Manufacturing Co. . | 66 |
| General Electric Co. | 17 |
| | |
| Hickok Electrical Instrument Co. | 14 |
| Hi-Lo TV Antenna Corp. | 62 |
| | |
| IE Manufacturing | 71 |
| International Rectifier Corp. | 13 |
| International Resistance Co. ... | Cover 2 |
| | |
| JFD Manufacturing Co. | 51 |
| Jensen Industries, Inc. | 65 |
| Jersey Specialty Co. | 70 |
| Jontz Manufacturing Co. | 59 |
| | |
| Leader Electronics Inc. | 53 |
| Littelfuse Inc. | 68 |
| | |
| Mallory & Co., Inc., P. R. | 10 |
| | |
| Philco Corp. | 19 |
| Precision Apparatus Co., Inc. | 55 |
| Presto Recording Corp. | 65 |
| | |
| Radiart Corp. | 16 |
| Radio Corp. of America | Cover 4 |
| Radio Merchandise Sales, Inc. | 72 |
| Raytheon Manufacturing Co. | 15 |
| Regency Division, I.D.E.A., Inc. | 4 |
| | |
| S & R Electronics, Inc. | 63, 65 |
| Shure Brothers, Inc. | 70 |
| Sola Electric Co. | 67 |
| South River Metal Prods. Co., Inc. ... | 18 |
| Sprague Products Co. | Cover 3 |
| | |
| Trio Manufacturing Co. | 6, 7 |
| Tung-Sol Electric Inc. | 11 |
| | |
| Walsco Electronics Corp. | 49 |
| Ward Products Corp. | 57 |
| Wells & Winegard | 12 |

While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.

NEW!

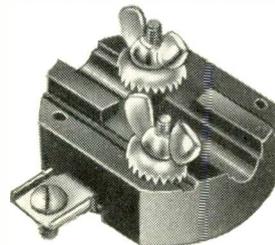

LIGHTNING ARRESTOR




Open Line




Tubular Round

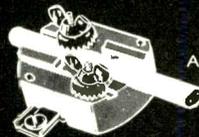
HOLDS EVERY COMMON TYPE OF TRANSMISSION LINE



Anaconda Foam

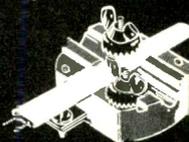

300 Ohm

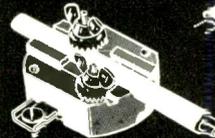

Anaconda

Now! No stripping of insulation, no straps or ears to break off, no signal loss—and no "misses." This new Lightning Arrestor by iE reduces your installation problems—and inventory, too! Easily installed indoors or outdoors.

Model 4000 for walls and window, etc. List \$1.25
Model 4005 with stainless steel strap for pipe mounting. List \$1.50



Write for details & new iE catalog.

325 N. HOYNE AVE.
CHICAGO 12, ILL.

Attention!! • EXECUTIVES
 • SALESMEN • PUBLIC OFFICIALS
 • POLICEMEN • FIREMEN • OUTDOOR MEN
 REPORTERS • FIELD INSPECTORS • DOCTORS • LAWYERS, ETC.

DICTATE IN YOUR CAR



with **ATR**

INVERTERS

for changing your battery current to
A.C. Household CURRENT
Anywhere . . .

in your own car!!

ATR INVERTERS . . . especially designed for operating standard 110 volt A.C. Tape Recorders, Wire Recorders, Dictating Machines and Electric Razors **IN YOUR CAR.**



\$25.55
 AND UP

EASY TO INSTALL
EASY TO OPERATE

A VALUABLE TIME SAVER FOR:

- **TRAVELLING SALESMEN**—Dictate reports in your own car. Send your dictated reports in daily to your home office or sales manager.
- **FIELD INSPECTORS & INVESTIGATORS**—Dictate your field inspection reports in the field—on the spot. Give the complete story factually and completely. Include your clients recordings also.
- **DOCTORS**—Dictate and record your house calls on the completion of your call while everything is fresh in your mind. Have these records for transcription by your office girl.
- **LAWYERS**—Record evidence in the field at your client's premises. Obtain factual and complete witness reports, etc.
- **EXECUTIVES**—Dictate in your car all business matters while on trips for pleasure or business.
- **PUBLIC OFFICIALS**—Dictate complete field reports in your car. Obtain recorded opinions and expressions of Mr. Public in the field. Dictate your business reports while traveling.
- **POLICE SQUAD CARS**—Dictate accident reports right on the scene complete and factual. Include witness recordings at the same time. Have the complete story available by dictation.
- **FIRE TRUCKS**—Dictate your fire reports factually and complete on the scene and include witness reports. Have the complete story.
- **AMBULANCES**—Dictate complete reports of your ambulance run. Include witness recordings, etc.
- **ADVERTISING AGENCIES**—Use AC operated animated or illuminated displays in or on the car.
- **FISHERMEN & HUNTERS**—Use your electric razor on camping trips operating in your car. Also small home radios and other electrical or electronic items.
- **CAMPERS**—Make your camping and outing trips more exciting using mix-masters, tape recorders, or wire recorders operating from your car battery.
- **WAREHOUSE & MATERIAL HANDLERS**—Dictate your inventory and material handling reports on the scene, in the warehouse, yard, or wherever you may be.

There is an **ATR INVERTER** for most applications for inverting D.C. Voltages (ranging from 6 volts D.C. to 220 volts D.C.) to 110 volts A.C. . . . Specially Designed for operating A.C. Radios, Tape Recorders, Wire Recorders, Dictating Machines, Electric Razors, Record-Changers, Television Sets, Amplifiers, Address Systems, Radio Test Equipment and most small electrical and electronic devices FROM D.C. VOLTAGES IN AUTOMOBILES, BUSES, TRUCKS, SHIPS, TRAINS, PLANES AND IN D.C. DISTRICTS.

Additional information available upon request.

FREE!! ATR INVERTER!


. . . given away every 30 days to lucky registrant of preceding month. Mail a postcard as your registration request today!

| TYPE | Input DC Volts | AC Output 40 Cycles | Output Inter- mittent | Wattage Contin- uous | List Price | RECOMMENDED APPLICATIONS |
|----------|----------------|---------------------|--------------------------|-------------------------|------------|--|
| 6-LIF | 6 | 110 volts | 40 | 35 | \$25.55 | For operating small flea-power AC motors, electric razors, small radios and small portable dictating machines having wattage consumption less than 35 watts. |
| 12-LIF | 12 | 110 volts | 50 | 35 | 25.55 | |
| 6-RSD | 6 | 110 volts | 85 | 75 | 39.25 | Recommended for operating small AC motors, Radio Sets, PA Systems, Amplifiers, and Radio Test Equipment having input wattage consumption within continuous output wattage ratings indicated. |
| 12-RSD | 12 | 110 volts | 125 | 100 | 39.25 | |
| 6-ISQ-F | 6 | 110 volts | 85 | 75 | 49.95 | Especially recommended for operating dictating machines, wire recorders, tape recorders, and small AC motors and electronic or electrical apparatus having input wattage consumption within continuous output wattage ratings indicated. |
| 12-ISQ-F | 12 | 110 volts | 125 | 100 | 49.95 | |
| 6T-HSG | 6 | 110 volts | 175 | 150 | 96.45 | For operating large tape recorders, wire recorders, PA Systems, amplifiers, and small TV sets having input wattage consumption within the continuous output wattage ratings indicated. |
| 12T-HSG | 12 | 110 volts | 250 | 200 | 96.45 | |

See your jobber or write factory ✓ **NEW MODELS** ✓ **NEW DESIGNS** ✓ **NEW LITERATURE**
 "A" Battery Eliminators, DC-AC Inverters, Auto Radio Vibrators

ATR **AMERICAN TELEVISION & RADIO Co.**
 Quality Products Since 1931
 SAINT PAUL 1, MINNESOTA—U. S. A.

NEW RMS "PRE-FAB"

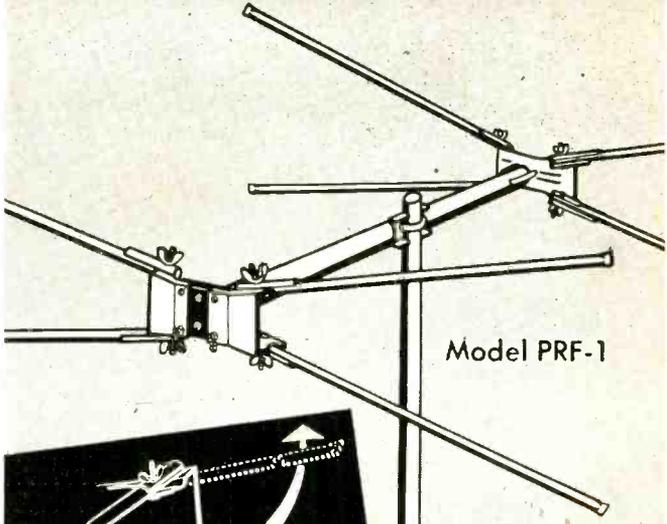

Model PRF-1




SWING OUT - INSTALL . . . THAT'S ALL!

the lowest priced — most rugged completely
PREASSEMBLED CONICAL
 on the market!

This is not an economy model . . . it is virtually a deluxe 4-front-4-back conical being massed produced by RMS in such vast quantities that costs are lowered . . . not quality!

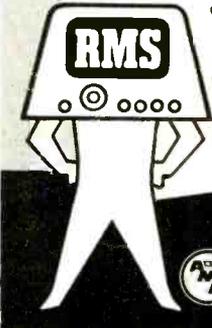- Rugged brackets hold elements securely—are triple-thick plated.
- 3/8" aluminum elements with pinched ends.
- Standard 36" aluminum crossarm dowel-reinforced at both ends and at the U-bolt.
- Tenna-Tek for signal terminal protection with each antenna.
- Six to the carton. Available in stacked and 4-bay.



AVAILABLE ALSO WITH STEEL CROSSARM
 See your local RMS Jobber


In Canada, MJS TV Accessories Co.
 Mexico: Industrias Comerciales

RMS. NEW YORK 62, N. Y.

NOTE:
UNLESS OTHERWISE NOTED:
1. ALL CAPACITORS MARKED LESS THAN 1, IN MF.
2. ALL CAPACITORS MARKED MORE THAN 1, IN MMF.
3. ALL CAPACITORS RATED 600V.
4. ALL RESISTORS IN OHMS.

5. ALL VOLTAGES MEASURED WITH VTVM FROM SOCKET TERMINALS TO GROUND WITH LINE VOLTAGES OF 117VAC AND ANTENNA TERMINALS SHORTED.
6. ALL RESISTANCE VALUES OF TRANSFORMER WINDINGS APPROXIMATE.

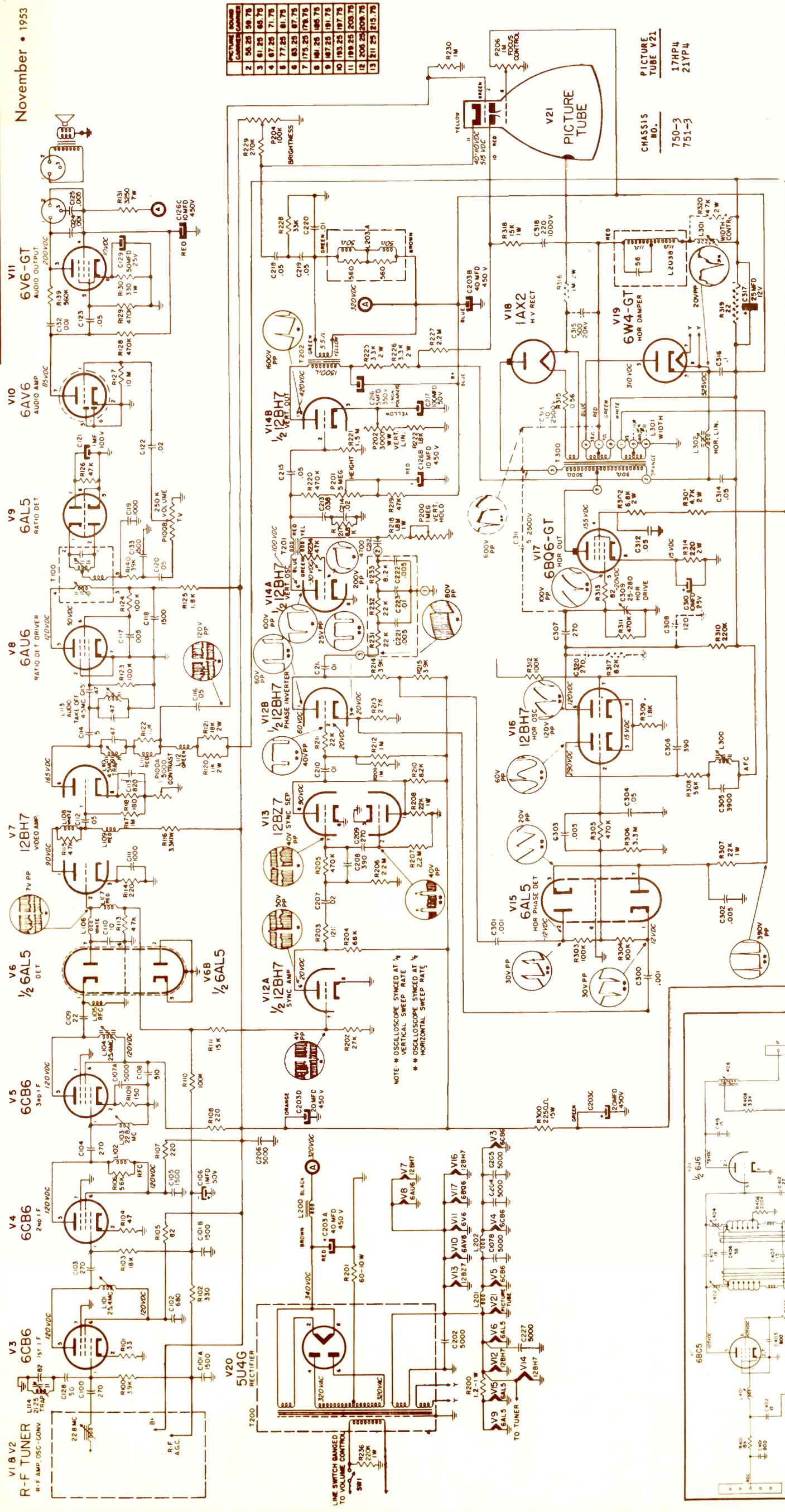7. IN CHASSIS DESIGNATED 750-3, C311, C313, C315 AND R316 ARE OMITTED. R319 IS 47 OHM, AND L301 (WIDTH CONTROL) IS SERIES CONNECTED IN LOW SIDE OF YOKE HORIZONTAL WINDING SHUNTED BY R 20.



CHASSIS NO. 750-3
751-3

PICTURE TUBE V21
17HP4
21TP4

Chassis 750-3:
Models 17M06, 22C06, 22C38

CBS-COLUMBIA

Chassis 750-3

Technician

CIRCUIT DIGEST

95

5 - The Brightness control should now be reduced (ccw) to a point where the raster is slightly above normal brilliance.

DEFLECTION YOKE, ION TRAP AND FOCUS ADJUSTMENT
Following is the proper procedure for adjusting the Deflection Yoke, Ion Trap and Focus.

HORIZONTAL OSCILLATOR ALIGNMENT
If the horizontal hold control fails to maintain sync, the horizontal oscillator should be reset. To reset this screwdriver adjustment, set the horizontal hold control in the center of its range and sync the picture with the horizontal A.F.C. adjustment screw. Check the hold control on various channels and alter the screw adjustment as required to provide sync on all channels.

6 - With Brightness and Contrast controls at normal positions, adjust the Focus control (rear of chassis) for well-defined scanning lines.

HEIGHT, WIDTH AND LINEARITY
To adjust the overall size and linearity of the picture it is almost mandatory that a test pattern transmitted from a local station be used. It should also be remembered that in areas where more than one station is being received, that pictures transmitted from different stations will vary slightly in size. The smallest uncut picture should be made to fill the area outlined by the mask.



1 - The Deflection Yoke should be moved as far forward as possible on the neck of the CRT.

2 - The Brightness control should be turned to maximum (clockwise) and the Contrast control should be turned to minimum (counterclockwise).

3 - The Ion Trap should be rotated and at the same time moved forward and backward to find the position which produces the brightest raster on screen.

4 - The Deflection Yoke should be rotated so that the top and bottom edges of the raster are parallel to the top of the chassis.

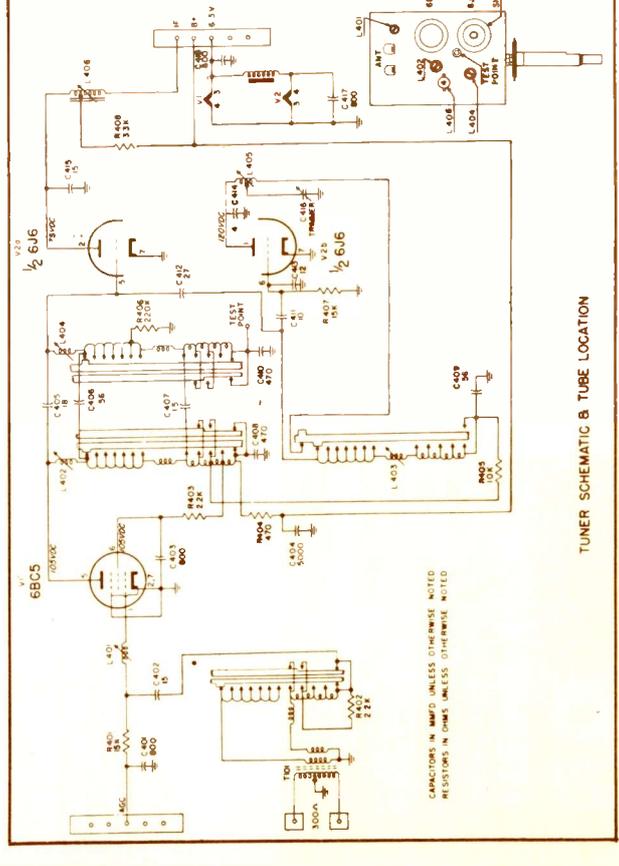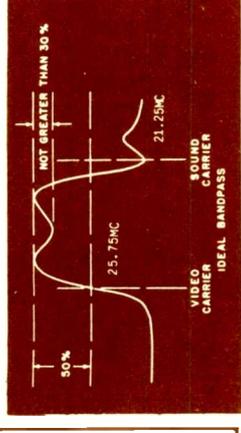11 198.25 203.75
12 205.25 209.75
13 211.25 215.75



TELEVISION ALIGNMENT PROCEDURE

Aligning a television receiver is an exacting procedure and involves the use of bench space, test equipment and skilled personnel at the service shop, as well as the cost of making two trips to the customer's home. Before deciding that the serviceman should check these very common sources of trouble:

- 1 - The antenna and installation.
- 2 - Front panel and rear chassis controls, including picture tube adjustments.
- 3 - Reception on all available channels.
- 4 - Tube failures. Substitute from your kit of known good replacements.
- 5 - Visual inspection of underside of chassis for obvious faults, such as loose connections, etc.

TEST EQUIPMENT REQUIRED FOR ALIGNMENT

The equipment specified below is desirable, but in cases where this equipment is not available, it is possible to align the receiver by use of a 20 to 30 mc. modulated r-f signal generator, using the picture and speaker as indication of alignment.

- 1 - Signal Generator with an output variable between 100 and 100,000 microvolts, and crystal controlled or crystal-calibrated at the following frequencies:
 - a - 4.5 megacycles
 - b - 22.8 megacycles
 - c - 25.4 megacycles
 - d - 21.25 megacycles
- 2 - DC Vacuum Tube Voltmeter with 5 volt and 10 volt scales.
- 3 - A pair of balanced (± 1%) 100K carbon resistors.

TEST EQUIPMENT REQUIRED FOR SWEEP ALIGNMENT CHECK

- 1 - R-F sweep generator with frequencies ranging from 40 to 220 megacycles, having sweep width of approximately 10 megacycles, and having adjustable output to approximately 0.1 volt.

- 2 - Crystal-controlled or crystal-calibrated meters for the picture and sound carrier of each channel.
- 3 - Cathode Ray Oscilloscope with good low frequency response.

I.F. ALIGNMENT PROCEDURE

- 1 - Connect "high" lead of signal generator to the test point located on the top of the R-F tuner unit (Refer to the R-F tuner location diagram located on inside of cabinet). Connect ground to chassis.
- 2 - Connect DC VTVM lead (through 10K isolating resistor) to 4.7K diode load resistor (R113); ground to chassis. Set VTVM to 5 volt scale, negative polarity.
- 3 - Set I.F. generator to 25.4 megacycles with sufficient output to read approximately 3 volts on the VTVM.
- 4 - Carefully adjust L101 and L104 (see tube and tuner location) for maximum deflection on VTVM. Adjust sweep generator output to keep meter reading approximately 3 volts.
- 5 - Set I.F. signal generator to 22.8 megacycles with sufficient output to read approximately 3 volts on the VTVM.
- 6 - Carefully adjust L406, L103 (see tube and tuner location) for maximum deflection on VTVM. Adjust signal generator output to keep meter reading approximately 3 volts.
- 7 - Set I.F. signal generator to 21.25 megacycles, set VTVM to 10 volt scale (negative polarity), and adjust signal generator output for convenient deflection on VTVM.
- 8 - Adjust L114 for minimum deflection on VTVM.

SWEEP ALIGNMENT CHECK

- 1 - Connect R-F sweep generator to antenna terminals (antenna impedance 300 ohms).
- 2 - Calibrate oscilloscope for convenient 5 volts peak-to-peak vertical deflection (5 volts peak-to-peak is approximately 1/4 of the peak-to-peak voltage of the 6.3V A.C. filament).
- 3 - Connect vertical input of oscilloscope (through 10K isolating resistor) to 4.7 diode load resistor (R113); ground to chassis. Connect horizontal input of oscilloscope to "scope" terminals of R-F generator; adjust for convenient horizontal sweep.

VIDEO AMPLIFIER TAP

- 1 - Connect 4.5 mc signal generator "high" lead to picture tube grid; ground to chassis.
- 2 - Connect DC V.T.V.M. to pin 7 of 6AL5 (V9) r-f detector, 10 volt scale, negative polarity.
- 3 - Adjust L110 for minimum deflection on V.T.V.M. When necessary, the video amplifier 4.5 mc trap (L110) should be adjusted as follows:

- 1 - Connect 4.5 mc signal generator "high" lead to picture tube grid; ground to chassis.
- 2 - Connect DC V.T.V.M. to pin 7 of 6AL5 (V9) r-f detector, 10 volt scale, negative polarity.
- 3 - Adjust L110 for minimum deflection on V.T.V.M.

R-F OSCILLATOR

- 1 - Connect 4.5 mc signal generator "high" lead to picture tube grid; ground to chassis.
- 2 - Connect DC V.T.V.M. to pin 7 of 6AL5 (V9) r-f detector, 10 volt scale, negative polarity.
- 3 - Adjust L110 for minimum deflection on V.T.V.M.

FINE TUNING

- 1 - If all channels are not within range of FINE TUNING control, adjust two screws located in front of r-f tuner unit for adjustment of either low or high band. CAUTION: Do not touch adjustments on top of r-f tuner unit, other than converter plate coil, L404, during IF Alignment.

PARTS LIST

| LOC. | CHASSIS* | PART NO. | DESCRIPTION | LOC. | CHASSIS* | PART NO. | DESCRIPTION |
|------|----------|------------|--------------------------|------|----------|------------|----------------------------|
| C100 | C100 | PE191-133 | Mica, 270mfd 500V 110% | R100 | R100 | PE231-1143 | Carbon, 3900 Ohm 1/2W 110% |
| C101 | C101 | PE191-147 | Ceramic, Shielded Dual | R101 | R101 | PE231-1147 | Carbon, 100 Ohm 1/2W 110% |
| C102 | C102 | PE355-334 | 350V 100mfd 1000mfd | R102 | R102 | PE231-1149 | Carbon, 100 Ohm 1/2W 110% |
| C103 | C103 | PE190-133 | Mica, 270mfd 500V 110% | R103 | R103 | PE231-1151 | Carbon, 100 Ohm 1/2W 110% |
| C104 | C104 | PE190-133 | Mica, 270mfd 500V 110% | R104 | R104 | PE231-1153 | Carbon, 100 Ohm 1/2W 110% |
| C105 | C105 | PE191-148 | Ceramic, Single Disc | R105 | R105 | PE231-1155 | Carbon, 100 Ohm 1/2W 110% |
| C106 | C106 | PE190-140 | Mica, 5000mfd 50V Dual | R106 | R106 | PE231-1157 | Carbon, 100 Ohm 1/2W 110% |
| C107 | C107 | PE190-151 | Mica, 22mfd 500V 110% | R107 | R107 | PE231-1159 | Carbon, 100 Ohm 1/2W 110% |
| C108 | C108 | PE190-101 | Ceramic Tubular 10mfd | R108 | R108 | PE231-1161 | Carbon, 100 Ohm 1/2W 110% |
| C109 | C109 | PE355-101 | 500V 120% (Unun.) | R109 | R109 | PE231-1163 | Carbon, 100 Ohm 1/2W 110% |
| C110 | C110 | PE355-101 | 500V 120% (Unun.) | R110 | R110 | PE231-1165 | Carbon, 100 Ohm 1/2W 110% |
| C111 | C111 | PE355-136 | Ceramic Tubular 1000mfd | R111 | R111 | PE231-1167 | Carbon, 100 Ohm 1/2W 110% |
| C112 | C112 | PE190-160 | Mica, 270mfd 500V 110% | R112 | R112 | PE231-1169 | Carbon, 100 Ohm 1/2W 110% |
| C113 | C113 | PE190-133 | Mica, 270mfd 500V 110% | R113 | R113 | PE231-1171 | Carbon, 100 Ohm 1/2W 110% |
| C114 | C114 | PE355-100 | 350V 110% (Unun.) | R114 | R114 | PE231-1173 | Carbon, 100 Ohm 1/2W 110% |
| C115 | C115 | PE355-133 | Ceramic Tubular 47mfd | R115 | R115 | PE231-1175 | Carbon, 100 Ohm 1/2W 110% |
| C116 | C116 | PE191-160 | Mica, 5000mfd 50V Dual | R116 | R116 | PE231-1177 | Carbon, 100 Ohm 1/2W 110% |
| C117 | C117 | PE190-151 | Mica, 22mfd 500V 110% | R117 | R117 | PE231-1179 | Carbon, 100 Ohm 1/2W 110% |
| C118 | C118 | PE191-148 | Ceramic Single Disc | R118 | R118 | PE231-1181 | Carbon, 100 Ohm 1/2W 110% |
| C119 | C119 | PE355-336 | 350V 120% (Unun.) | R119 | R119 | PE231-1183 | Carbon, 100 Ohm 1/2W 110% |
| C120 | C120 | PE190-160 | Mica, 5000mfd 50V Dual | R120 | R120 | PE231-1185 | Carbon, 100 Ohm 1/2W 110% |
| C121 | C121 | PE46201-81 | Electrolytic, 1mfd 100V | R121 | R121 | PE231-1187 | Carbon, 100 Ohm 1/2W 110% |
| C122 | C122 | PE190-156 | Paper, 0.01mfd 600V 120% | R122 | R122 | PE231-1189 | Carbon, 100 Ohm 1/2W 110% |
| C123 | C123 | PE190-145 | Paper, 0.01mfd 600V 120% | R123 | R123 | PE231-1191 | Carbon, 100 Ohm 1/2W 110% |
| C124 | C124 | PE190-145 | Paper, 0.01mfd 600V 120% | R124 | R124 | PE231-1193 | Carbon, 100 Ohm 1/2W 110% |
| C125 | C125 | PE190-151 | Paper, 0.05mfd 600V 120% | R125 | R125 | PE231-1195 | Carbon, 100 Ohm 1/2W 110% |
| C126 | C126 | PE190-151 | Paper, 0.05mfd 600V 120% | R126 | R126 | PE231-1197 | Carbon, 100 Ohm 1/2W 110% |
| C127 | C127 | PE190-145 | Paper, 0.01mfd 600V 120% | R127 | R127 | PE231-1199 | Carbon, 100 Ohm 1/2W 110% |
| C128 | C128 | PE355-100 | 350V 110% (Unun.) | R128 | R128 | PE231-1201 | Carbon, 100 Ohm 1/2W 110% |
| C129 | C129 | PE355-100 | 350V 110% (Unun.) | R129 | R129 | PE231-1203 | Carbon, 100 Ohm 1/2W 110% |
| C130 | C130 | PE355-133 | Ceramic Tubular 47mfd | R130 | R130 | PE231-1205 | Carbon, 100 Ohm 1/2W 110% |
| C131 | C131 | PE191-160 | Mica, 5000mfd 50V Dual | R131 | R131 | PE231-1207 | Carbon, 100 Ohm 1/2W 110% |
| C132 | C132 | PE190-151 | Mica, 22mfd 500V 110% | R132 | R132 | PE231-1209 | Carbon, 100 Ohm 1/2W 110% |
| C133 | C133 | PE191-148 | Ceramic Single Disc | R133 | R133 | PE231-1211 | Carbon, 100 Ohm 1/2W 110% |
| C134 | C134 | PE191-148 | Ceramic Single Disc | R134 | R134 | PE231-1213 | Carbon, 100 Ohm 1/2W 110% |
| C135 | C135 | PE355-336 | 350V 120% (Unun.) | R135 | R135 | PE231-1215 | Carbon, 100 Ohm 1/2W 110% |
| C136 | C136 | PE190-160 | Mica, 5000mfd 50V Dual | R136 | R136 | PE231-1217 | Carbon, 100 Ohm 1/2W 110% |
| C137 | C137 | PE190-151 | Mica, 22mfd 500V 110% | R137 | R137 | PE231-1219 | Carbon, 100 Ohm 1/2W 110% |
| C138 | C138 | PE191-148 | Ceramic Single Disc | R138 | R138 | PE231-1221 | Carbon, 100 Ohm 1/2W 110% |
| C139 | C139 | PE191-148 | Ceramic Single Disc | R139 | R139 | PE231-1223 | Carbon, 100 Ohm 1/2W 110% |
| C140 | C140 | PE191-148 | Ceramic Single Disc | R140 | R140 | PE231-1225 | Carbon, 100 Ohm 1/2W 110% |
| C141 | C141 | PE355-136 | 350V 120% (Unun.) | R141 | R141 | PE231-1227 | Carbon, 100 Ohm 1/2W 110% |
| C142 | C142 | PE190-160 | Mica, 5000mfd 50V Dual | R142 | R142 | PE231-1229 | Carbon, 100 Ohm 1/2W 110% |
| C143 | C143 | PE190-151 | Mica, 22mfd 500V 110% | R143 | R143 | PE231-1231 | Carbon, 100 Ohm 1/2W 110% |
| C144 | C144 | PE191-148 | Ceramic Single Disc | R144 | R144 | PE231-1233 | Carbon, 100 Ohm 1/2W 110% |
| C145 | C145 | PE191-148 | Ceramic Single Disc | R145 | R145 | PE231-1235 | Carbon, 100 Ohm 1/2W 110% |
| C146 | C146 | PE355-336 | 350V 120% (Unun.) | R146 | R146 | PE231-1237 | Carbon, 100 Ohm 1/2W 110% |
| C147 | C147 | PE190-160 | Mica, 5000mfd 50V Dual | R147 | R147 | PE231-1239 | Carbon, 100 Ohm 1/2W 110% |
| C148 | C148 | PE190-151 | Mica, 22mfd 500V 110% | R148 | R148 | PE231-1241 | Carbon, 100 Ohm 1/2W 110% |
| C149 | C149 | PE191-148 | Ceramic Single Disc | R149 | R149 | PE231-1243 | Carbon, 100 Ohm 1/2W 110% |
| C150 | C150 | PE191-148 | Ceramic Single Disc | R150 | R150 | PE231-1245 | Carbon, 100 Ohm 1/2W 110% |
| C151 | C151 | PE355-336 | 350V 120% (Unun.) | R151 | R151 | PE231-1247 | Carbon, 100 Ohm 1/2W 110% |
| C152 | C152 | PE190-160 | Mica, 5000mfd 50V Dual | R152 | R152 | PE231-1249 | Carbon, 100 Ohm 1/2W 110% |
| C153 | C153 | PE190-151 | Mica, 22mfd 500V 110% | R153 | R153 | PE231-1251 | Carbon, 100 Ohm 1/2W 110% |
| C154 | C154 | PE191-148 | Ceramic Single Disc | R154 | R154 | PE231-1253 | Carbon, 100 Ohm 1/2W 110% |
| C155 | C155 | PE191-148 | Ceramic Single Disc | R155 | R155 | PE231-1255 | Carbon, 100 Ohm 1/2W 110% |
| C156 | C156 | PE355-336 | 350V 120% (Unun.) | R156 | R156 | PE231-1257 | Carbon, 100 Ohm 1/2W 110% |
| C157 | C157 | PE190-160 | Mica, 5000mfd 50V Dual | R157 | R157 | PE231-1259 | Carbon, 100 Ohm 1/2W 110% |
| C158 | C158 | PE190-151 | Mica, 22mfd 500V 110% | R158 | R158 | PE231-1261 | Carbon, 100 Ohm 1/2W 110% |
| C159 | C159 | PE191-148 | Ceramic Single Disc | R159 | R159 | PE231-1263 | Carbon, 100 Ohm 1/2W 110% |
| C160 | C160 | PE191-148 | Ceramic Single Disc | R160 | R160 | PE231-1265 | Carbon, 100 Ohm 1/2W 110% |
| C161 | C161 | PE355-336 | 350V 120% (Unun.) | R161 | R161 | PE231-1267 | Carbon, 100 Ohm 1/2W 110% |
| C162 | C162 | PE190-160 | Mica, 5000mfd 50V Dual | R162 | R162 | PE231-1269 | Carbon, 100 Ohm 1/2W 110% |
| C163 | C163 | PE190-151 | Mica, 22mfd 500V 110% | R163 | R163 | PE231-1271 | Carbon, 100 Ohm 1/2W 110% |
| C164 | C164 | PE191-148 | Ceramic Single Disc | R164 | R164 | PE231-1273 | Carbon, 100 Ohm 1/2W 110% |
| C165 | C165 | PE191-148 | Ceramic Single Disc | R165 | R165 | PE231-1275 | Carbon, 100 Ohm 1/2W 110% |
| C166 | C166 | PE355-336 | 350V 120% (Unun.) | R166 | R166 | PE231-1277 | Carbon, 100 Ohm 1/2W 110% |
| C167 | C167 | PE190-160 | Mica, 5000mfd 50V Dual | R167 | R167 | PE231-1279 | Carbon, 100 Ohm 1/2W 110% |
| C168 | C168 | PE190-151 | Mica, 22mfd 500V 110% | R168 | R168 | PE231-1281 | Carbon, 100 Ohm 1/2W 110% |
| C169 | C169 | PE191-148 | Ceramic Single Disc | R169 | R169 | PE231-1283 | Carbon, 100 Ohm 1/2W 110% |
| C170 | C170 | PE191-148 | Ceramic Single Disc | R170 | R170 | PE231-1285 | Carbon, 100 Ohm 1/2W 110% |
| C171 | C171 | PE355-336 | 350V 120% (Unun.) | R171 | R171 | PE231-1287 | Carbon, 100 Ohm 1/2W 110% |
| C172 | C172 | PE190-160 | Mica, 5000mfd 50V Dual | R172 | R172 | PE231-1289 | Carbon, 100 Ohm 1/2W 110% |
| C173 | C173 | PE190-151 | Mica, 22mfd 500V 110% | R173 | R173 | PE231-1291 | Carbon, 100 Ohm 1/2W 110% |
| C174 | C174 | PE191-148 | Ceramic Single Disc | R174 | R174 | PE231-1293 | Carbon, 100 Ohm 1/2W 110% |
| C175 | C175 | PE191-148 | Ceramic Single Disc | R175 | R175 | PE231-1295 | Carbon, 100 Ohm 1/2W 110% |
| C176 | C176 | PE355-336 | 350V 120% (Unun.) | R176 | R176 | PE231-1297 | Carbon, 100 Ohm 1/2W 110% |
| C177 | C177 | PE190-160 | Mica, 5000mfd 50V Dual | R177 | R177 | PE231-1299 | Carbon, 100 Ohm 1/2W 110% |
| C178 | C178 | PE190-151 | Mica, 22mfd 500V 110% | R178 | R178 | PE231-1301 | Carbon, 100 Ohm 1/2W 110% |
| C179 | C179 | PE191-148 | Ceramic Single Disc | R179 | R179 | PE231-1303 | Carbon, 100 Ohm 1/2W 110% |
| C180 | C180 | PE191-148 | Ceramic Single Disc | R180 | R180 | PE231-1305 | Carbon, 100 Ohm 1/2W 110% |
| C181 | C181 | PE355-336 | 350V 120% (Unun.) | R181 | R181 | PE231-1307 | Carbon, 100 Ohm 1/2W 110% |
| C182 | C182 | PE190-160 | Mica, 5000mfd 50V Dual | R182 | R182 | PE231-1309 | Carbon, 100 Ohm 1/2W 110% |
| C183 | C183 | PE190-151 | Mica, 22mfd 500V 110% | R183 | R183 | PE231-1311 | Carbon, 100 Ohm 1/2W 110% |
| C184 | C184 | PE191-148 | Ceramic Single Disc | R184 | R184 | PE231-1313 | Carbon, 100 Ohm 1/2W 110% |
| C185 | C185 | PE191-148 | Ceramic Single Disc | R185 | R185 | PE231-1315 | Carbon, 100 Ohm 1/2W 110% |
| C186 | C186 | PE355-336 | 350V 120% (Unun.) | R186 | R186 | PE231-1317 | Carbon, 100 Ohm 1/2W 110% |
| C187 | C187 | PE190-160 | Mica, 5000mfd 50V Dual | R187 | R187 | PE231-1319 | Carbon, 100 Ohm 1/2W 110% |
| C188 | C188 | PE190-151 | Mica, 22mfd 500V 110% | | | | |

ADJUSTMENTS

LOCAL-DISTANCE (AGC) SWITCH:

The LOCAL-DISTANCE SWITCH can be set to prevent the receiver from overloading in strong signal areas or to reduce "snow" in the picture in weak signal areas. In strong signal areas, the "LOCAL" (counter-clockwise) position of the switch must be used. The second and third positions "SUBBAND" and "DISTANCE" are to be used in medium to weak signal areas. Use the position with which the best picture is obtained with a minimum of overloading of the receiver when the CONTRAST control is advanced.

NOISE GATE CONTROL:

This control makes it possible to obtain improved picture stability in the presence of electrical interference (noise) when the LOCAL-DISTANCE SWITCH is in the "SUBBAND" or "DISTANCE" position. When the control is turned completely counter-clockwise, it is out of the circuit and has no effect. Adjust the control by turning it clockwise until the picture is stable. The limiting factor of this adjustment is the buzz or noise that may be introduced, if the control is turned too far in the clockwise direction.

VHF OSCILLATOR ADJUSTMENT USING A TELEVISION SIGNAL:

Do not make any adjustments on the two oscillator adjusting screws unless the FINE TUNING control/range is insufficient to properly tune-in the station. The adjusting screws are accessible through holes in the front of the chassis after the tuning knobs are removed. To make the adjustment, proceed as follows:

1. Turn the receiver on and allow a warm-up period of approximately five minutes.
2. For stations on channel 13 to channel 7, set the Station Selector Switch to the highest channel received and adjust the Contrast and Volume control for normal sound and picture. Set the Fine Tuning Control in the center of its range.
3. Using a small non-metallic screwdriver, adjust the slotted head brass screw located above and to the right of shaft and above the fiber disc for the clearest and sharpest detail in the picture. This adjustment will be effective on all channels between 13 and 7. If other stations are operating in this range, it may be necessary to compromise slightly on the high channel adjustment so the other channels may be properly tuned-in.
4. For stations on channel 6 and below, set the station Selector Switch to the channel received closest to channel 6 and adjust the Contrast and Volume control for normal sound and picture. Set the Fine Tuning Control in the center of its range.
5. Using a small non-metallic screwdriver, adjust the slotted head brass screw located below the shaft for the clearest and sharpest detail in the picture. This adjustment will effect all channels between 6 and 2.

HORIZONTAL HOLD ADJUSTMENT

1. Tune in a local television signal and adjust contrast control for normal picture.
2. Connect electronic voltmeter between TP-3 (green lead) and chassis.
3. Short TP-5 (orange lead) to chassis and adjust electronic voltmeter to zero.
4. Remove short from TP-5. Do not change zero on electronic voltmeter.
5. Connect a 0.1 mfd. 600 volt capacitor between TP-4 (red lead) and chassis.
6. Adjust Horizontal Hold control for zero reading on the meter.
7. Remove the 0.1 mfd. capacitor from TP-4 and chassis. Do not disturb setting of horizontal hold control.
8. Adjust Horizontal Stabilizer coil (L114) for zero reading on the meter.
9. Remove electronic voltmeter from TP-3.
10. Check horizontal pull-in range. The pull-in range should be approximately 50% of the control rotation.


I. F. ALIGNMENT

All lead connections from the signal generator and voltmeter must be shielded. Keep the exposed ends and ground leads as short as possible (about one inch). Always locate the ground lead connections as close as possible to their respective "hot" leads in the television receiver chassis. The voltmeter, signal generator output, and contrast control must be kept low enough to prevent overloading the television receiver circuits.

CAUTION: One side of the chassis is connected to the power line. Therefore, test equipment should not be connected to the receiver unless an isolation transformer is used between the power line and the receiver. DO NOT GROUND THE RECEIVER CHASSIS UNLESS AN ISOLATION TRANSFORMER IS USED.

1. To Check I. F. Alignment on Oscilloscope:

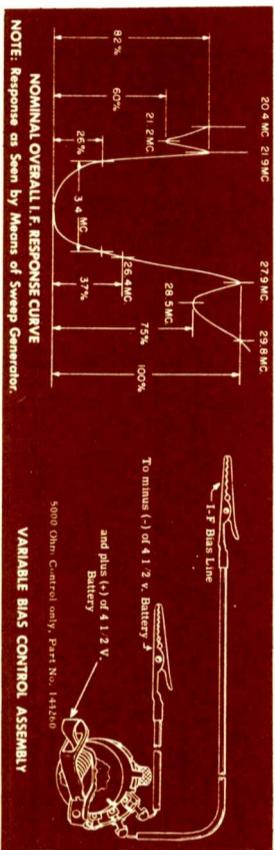1. Lift the shield of the Oscillator-Mixer tube V2 sufficiently to clear the set screw. Connect signal generator "hot" lead to the grounded tube shield and generator ground lead to the tuner chassis.
2. Connect high side of oscilloscope to high side of contrast control, and the low side to chassis.
3. Apply -3.0 volts D.C. bias to I. F. Bias line (see sketch "Variable Bias Control"). Contrast control should be set in the maximum counter-clockwise position.
4. With the generator sweep set at zero, connect an electronic voltmeter between top of detector load and chassis. Adjust the I. F. Tuner of the generator to obtain a reading of 2 volts D.C. on the meter.
5. Set generator to sweep from 20 mc. to 30 mc.
6. Connect marker generator to sweep generator output leads and adjust to provide markers that appear in the curve. See nominal response curve.
7. Observe curve and position of markers (see nominal response curve). Slight deviation in shape from the nominal response curve is permissible, but if any great deviation is noted, it will be necessary to realign the I. F. Amplifier.
8. Alignment I. F. and Tune Assembly (with electronic voltmeter):
 - a. Connect -3.5 volts D.C. bias supply to I. F. Bias line.
 - b. Connect signal generator "hot" lead through a 1000 mfd. capacitor to TP-1 (wire protruding from tuner directly adjacent to the oscillator mixer tube V2) and the ground lead to the R. F. Tuner case.
 - c. Connect high side of Electronic Voltmeter to top of detector load resistor, R118 and low side to chassis; zero the meter.
 - d. Set signal generator to 24.4 mc. and adjust top of T101 for maximum D.C. meter indication on voltmeter. Adjust signal generator amplitude to make this peak indication 2 volts D.C., approximately.
 - e. Note: When aligning bottom of L103 and bottom of L101 the first null obtained when tuning the core into the trap winding is the proper alignment null.
 - f. Remove the signal generator and electronic voltmeter.
 - g. Repeat steps "j" and "k".
 - h. Check sensitivity. The input, to obtain 2 volts D.C. output with zero bias, should not exceed 650 microvolts at 24.4 mc. with generator properly terminated and generator fed into grid of first I. F. Amplifier.
 - i. Remove the signal generator and electronic voltmeter.
 - j. Note: When aligning bottom of L103 and bottom of L101 the first null obtained when tuning the core into the trap winding is the proper alignment null.
 - k. Set signal generator to 25.5 mc. Connect the 100 ohm resistor and the 1000 mfd. series capacitor from TP-2 (wire protruding from the tuner through the insulated spigot between the brass adjusting screw) on the R. F. Tuner to the tuner case and adjust L101 for maximum D.C. meter indication, adjusting amplitude of signal generator to make this maximum indication approximately 2 volts D.C. Remove the 100 ohm resistor and the 1000 mfd. capacitor.
 - l. Repeat steps "j" and "k".
 - m. Check sensitivity. The input, to obtain 2 volts D.C. output with zero bias, should not exceed 650 microvolts at 24.4 mc. with generator properly terminated and generator fed into grid of first I. F. Amplifier.
 - n. Remove the signal generator and electronic voltmeter.



SOUND ALIGNMENT

1. Connect crystal controlled 4.5 mc. 400 cycle amplitude modulated signal, modulated 30% or greater, between grid of video amplifier and chassis.
2. Connect high side of scope through detector probe to the picture tube cathode (pin 11). Connect low side of scope to chassis. Adjust 4.5 mc. trap, L109, for minimum 400 cycle deflection on scope.
3. Connect electronic voltmeter to lug 2 of ratio detector, V104, and adjust 4.5 mc. sound take-off (L112) and bottom of ratio transformer (T102) for peak reading on a voltmeter. Adjust input to make this peak reading 4 volts.
4. Adjust input to obtain 12 volts output. Transfer electronic voltmeter to junction of R129 and C128 (reference schematic Wiring Diagram). Adjust top of T102 for zero balance on electronic voltmeter.
5. Recheck steps 2, 3 and 4 above.
6. Remove input signal, scope and electronic voltmeter.

UHF ALIGNMENT






ALIGNMENT NOTES:

CAUTION: This UHF converter unit is used with a VHF receiver that has one side of the chassis connected to the power line. DO NOT CONNECT TEST EQUIPMENT TO ANY PART OF THE RECEIVER OR GROUND THE CHASSIS UNLESS AN ISOLATION TRANSFORMER IS USED BETWEEN THE POWER LINE AND RECEIVER.

1. Remove the UHF Converter from the VHF receiver chassis.
2. Disengage the toggle coupling from the switch throw arm on the front of the UHF chassis.
3. Turn the UHF tuning control clockwise until the pin located on the rear of the drive pulley is free from the toggle coupling.
4. Loosen the two set screws in switch throw arm collar and remove from switch shaft.
5. Turn the switch clockwise to the UHF position; contact blade on switch rotor must contact and center on the two switch fingers with the red wires attached. Leave switch in this position while aligning.
6. Connect the output leads of the UHF converter to the R. F. Input terminals of the VHF Tuner.
7. Connect the B- and filament leads of the tuner to their respective points from which they were removed on the VHF receiver. Connect UHF Converter chassis to B- (VHF receiver chassis).
8. Keep all leads as short as possible. One way of accomplishing this is to mount the UHF Converter at right angles to the TV chassis with one mounting screw. Most of the leads on the UHF Converter will then be of sufficient length and no additional length need be added.
9. Set VHF Tuner to Channel 6.
10. Alignment should be followed in the order shown.

OSCILLATOR ALIGNMENT:

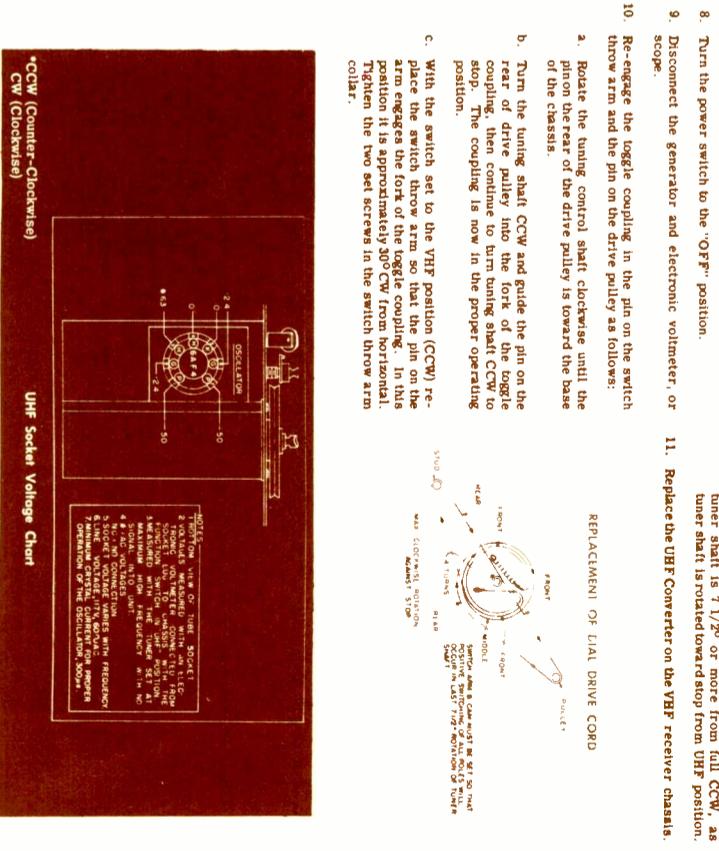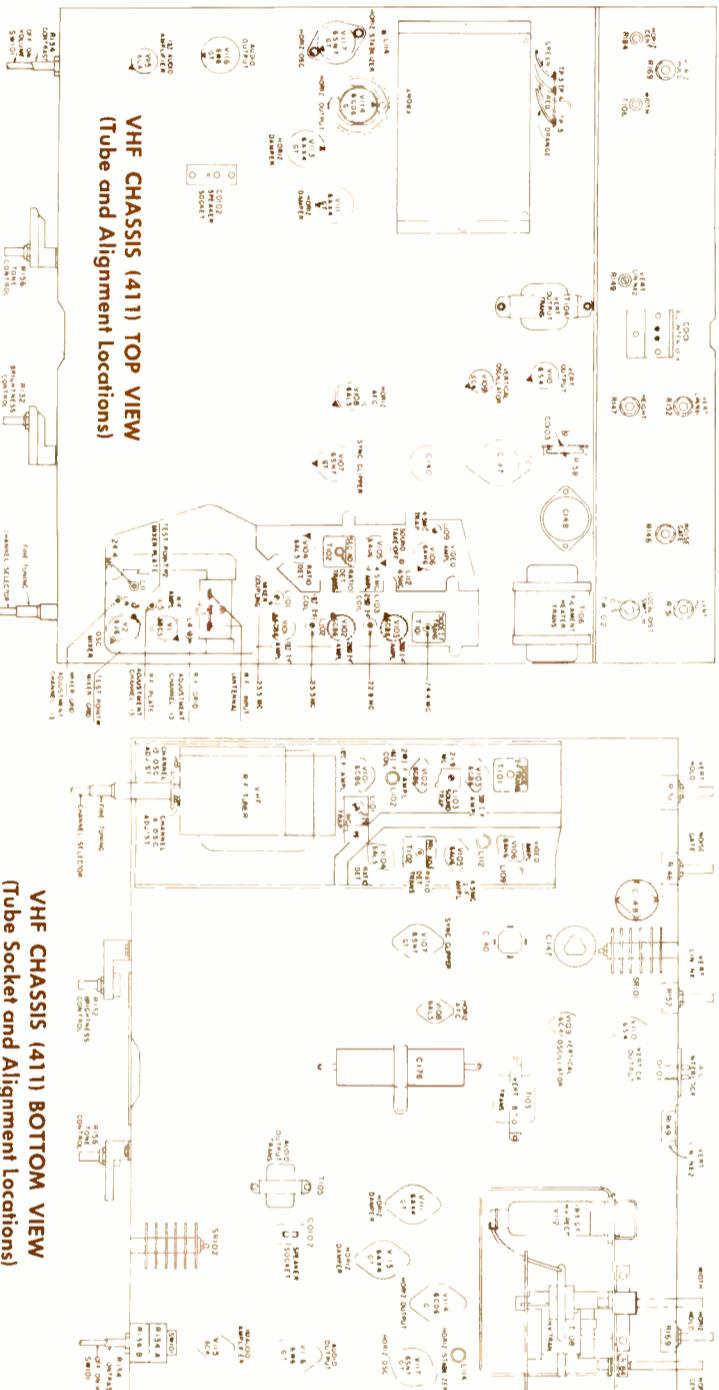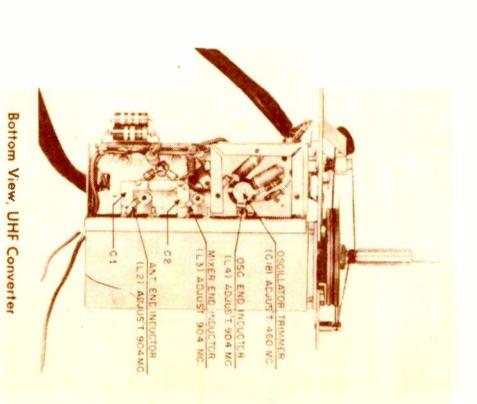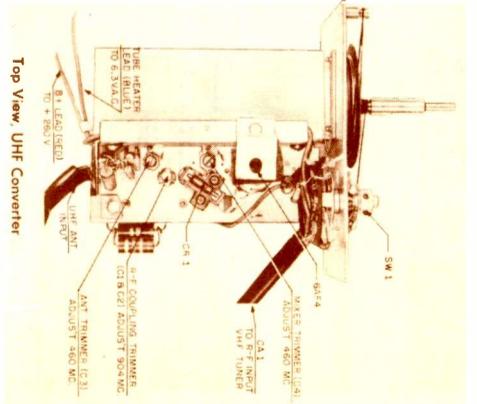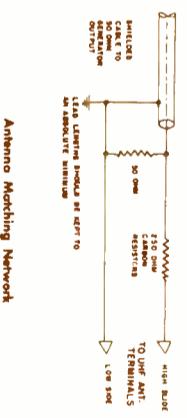1. Connect an electronic voltmeter or scope across the second detector load resistor.
2. Turn on the power.
3. Apply a 460 mc. (amplitude modulated when scope is used) signal to the UHF antenna terminals through the antenna matching network (see Antenna Matching Network Sketch).
4. Repeat steps 2 through 5 until maximum reading is obtained.
5. Turn the tuner shaft to maximum CW position and adjust the antenna and mixer trimmers, C3 and C4 for maximum meter reading (or scope indication).
6. Repeat signal generator to 904 mc.
7. Rotate the tuner shaft to maximum CW position and adjust the antenna and mixer trimmers, L2 and L3, for maximum reading on meter or scope, by forming larger or smaller loop.
8. Repeat steps 2 through 5 until maximum reading is obtained.
9. Turn the tuner shaft to maximum CW position and adjust the coupling trimmer, C1 and C2 for peak reading at 904 MC.
10. Turn the power switch to the "OFF" position.
11. Replace the UHF Converter on the VHF receiver chassis.



(Continued from reverse side)

2. Repeat steps "2", "4", and "5" of "Horizontal Hold Adjustment".
3. Adjust the Phasing screw on bottom of Horizontal Discriminator Transformer T62 until equal blanking is observed on both sides of the picture. It will be necessary to turn the Picture (Contrast) control to minimum, readjust the Brightness control and move the picture to the left and to the right with the centering lever to see the blanking.
4. Repeat steps "3" and "4" of "Horizontal Hold Adjustment".
5. Repeat phasing as in step "3". It is important that both "free running" and phasing are correct.
6. Remove the short from across R264 and readjust the Horizontal Drive control as in step "2" of "Horizontal Hold Adjustment".
7. Turn the adjustment screw in Ringing coil L69 until equal blanking is again visible on both edges of the picture.
8. Repeat steps "3", "4", and "5" of "Horizontal Hold Adjustment".




UHF TUNER ALIGNMENT

PRELIMINARY INSTRUCTIONS

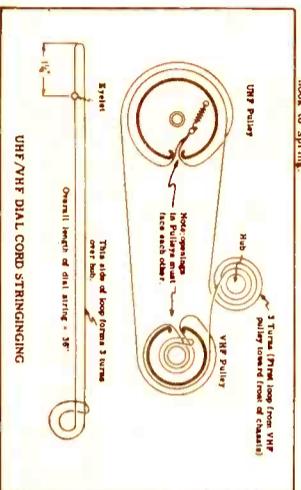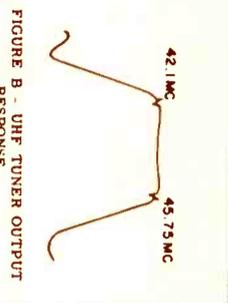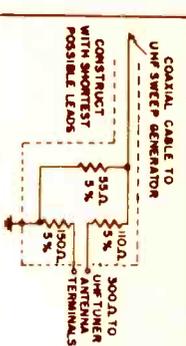1. Allow receiver to warm up for fifteen minutes before performing UHF alignment.
2. Check Video IF response as outlined in "Video IF Alignment". It is particularly important that the respective band pass circuit be aligned for correct response as shown in step 2 of "Video IF Alignment". Leave detector circuit connected for use in UHF tuner alignment.
3. When the Video IF band pass adjustments have been checked, switch to "UHF" position and proceed with alignment as indicated in the following paragraphs.

OUTPUT CIRCUIT ALIGNMENT

Apply 45.25 MC sweep (10 MC sweep width) into test point on UHF tuner. Apply 42.1 MC and 45.75 MC markers as shown in "UHF Tuner Alignment Setup" and adjust T25 on UHF tuner for response curve shown in accompanying Figure B.



1. With accurately calibrated UHF signal generator tuned to 896 MC, feed into antenna terminals of UHF tuner, connect DC VTVM across Video Detector Load resistor, R152 - 3.3K.
2. Turn UHF tuning knob to extreme high frequency end of dial. At this point UHF tuning capacitor plates are fully unmeshed.
3. Adjust C28 (See UHF Tuner Layout drawing) for Maximum reading on VTVM.

PRESLECTOR ALIGNMENT





1. Inject 42.1 MC and 45.75 MC markers as shown in "UHF Tuner Alignment Setup".
2. Apply UHF sweep signal to UHF antenna terminals through a properly terminated output cable (matched to 300 Ohms) or through the matching pad shown in Figure A.
3. Tune UHF sweep generator and UHF tuner simultaneously across entire tuning range from 464 MC to 896 MC and observe response curve.
4. Adjust trimmers C37, C38 and C39 for best compromise on dip and tilt; if necessary, additional adjustment may be accomplished by bending the rotor plates slightly. Overall response curve should appear as in Figure B.
5. Disconnect test equipment, remove 330 Ohm resistor and reconnect T55 into circuit.

NOTE: DO NOT attempt to correct for tilted response curve by adjusting band pass circuit (L8, L33 and L54). Readjustment of these circuits will adversely affect VHF reception of receiver.

DIAL CORD STRINGING

1. In replacing the dial drive cord, position the eyelet in the UHF tuner as shown in the following order: See UHF Dial Cord Stringing drawing.
1. Loop around shaft of VHF pulley.
2. Loops around UHF pulley in each direction.
3. Three turns around hub on anti-blankish gear.
4. Loops around UHF pulley in each direction.
5. Leads to spring through opening in UHF pulley and back to spring.



OSCILLATOR ALIGNMENT

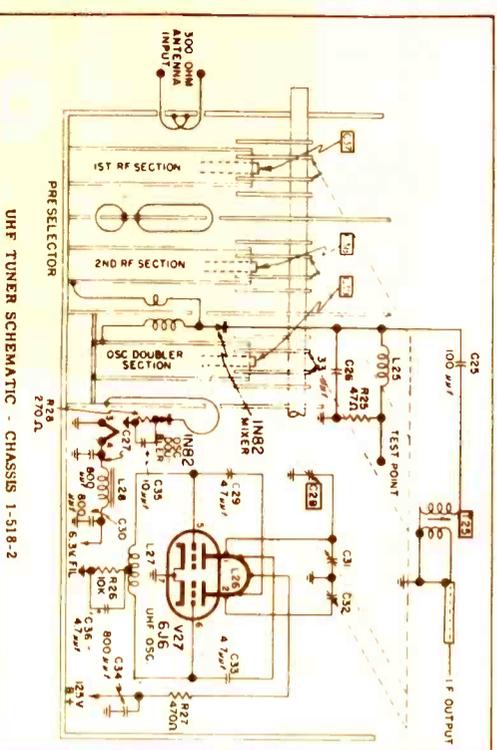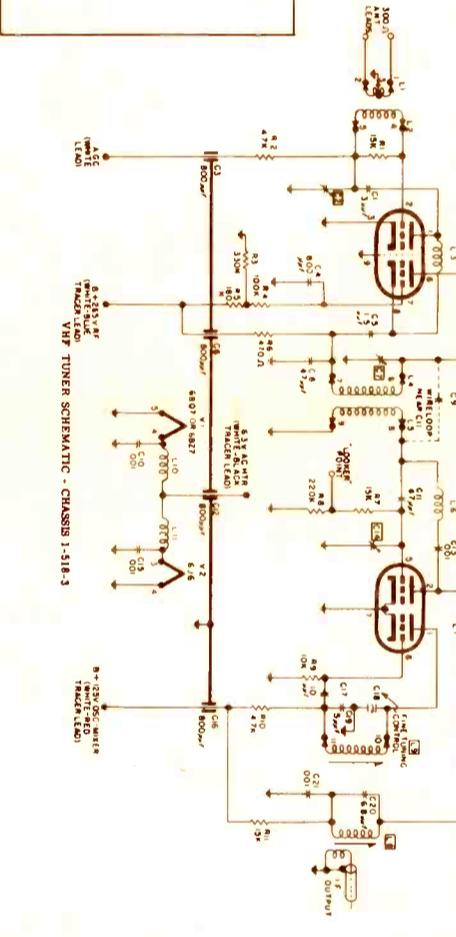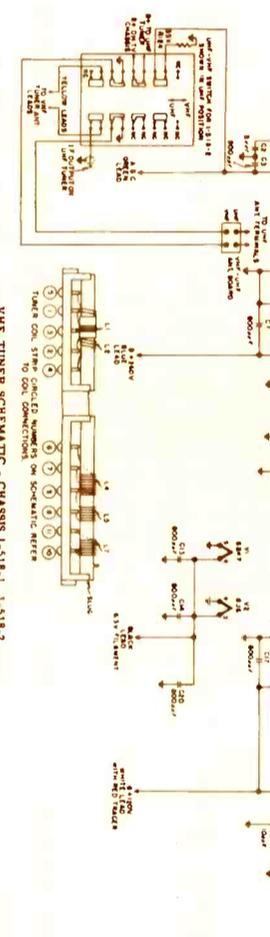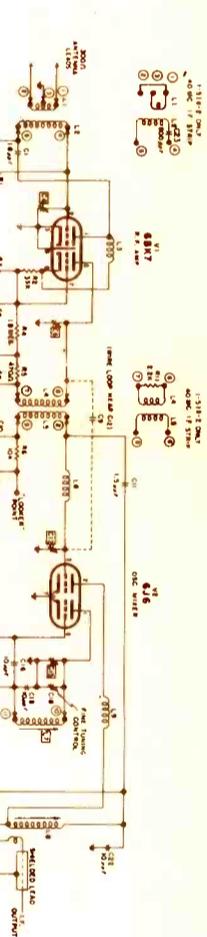

The drawings on this page illustrate the wave forms at various positions within the receiver. The wave forms are not theoretical but exact copies of that shown by an oscilloscope and were taken under normal operating conditions, with a transmitted signal and the picture in sync at all times.

When checking the wave forms, connect the ground lead from the oscilloscope to the top chassis plate and the hot lead to the position indicated. The wave shapes may vary somewhat depending on the strength of the signal, the picture information being transmitted and the adjustments of the various controls.

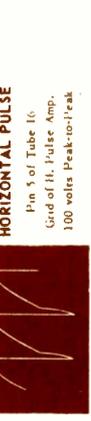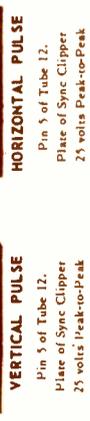Under each wave form is the schematic reference, position taken at, peak-to-peak voltage and the type of wave form indicated (Vertical—60 cycles and Horizontal—15,750 cycles).




BUILT-IN VHF TV ANTENNA

The new Built-in VHF Television Antenna incorporated in your receiver eliminates the need of an outside VHF antenna in most locations. In areas too distant for normal reception with a built-in antenna, provision is made for outside antenna connections. If any other type of antenna is used with the set, disconnect the transmission line from the built-in antenna to the antenna terminals. When connections are made, check to see that the antenna terminal screws are moderately tight.

The antenna is mounted inside the cabinet and is operated by the use of a knob at the top of the back of the cabinet. Since the antenna is fastened to the cabinet, it may be necessary to orient the cabinet to obtain the best reception. It is desirable that either the front or the back of the cabinet face the transmitting station. If however, "ghosts" or multiple images appear, the cabinet may be rotated slightly to minimize this condition. In some cases it may be necessary to face the back or the front of the cabinet toward a window to obtain a television picture. This may be due to walls, water pipes, or a steel structure in your location preventing television reception.

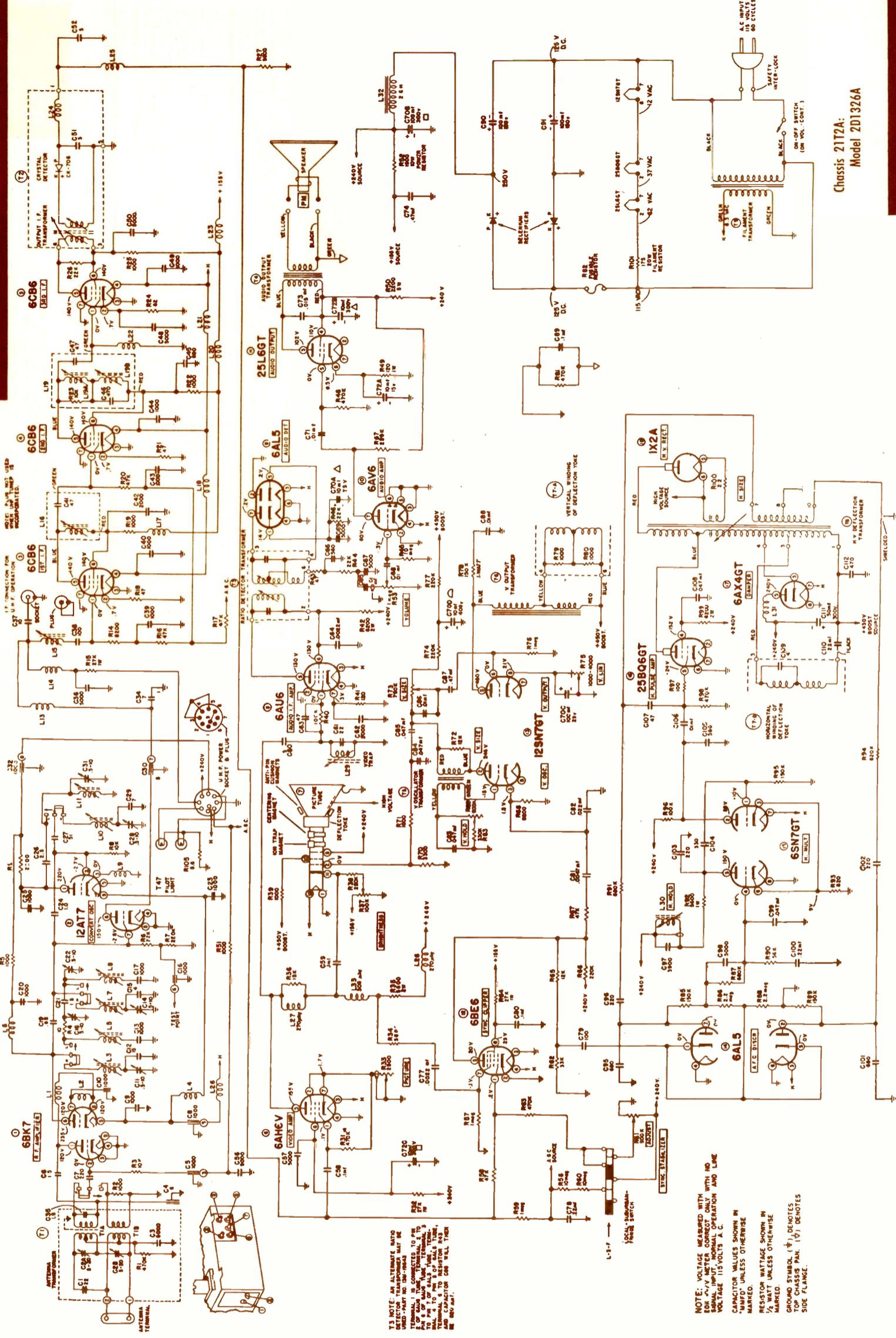VHF ANTENNA KNOB—The antenna tuning knob for the built-in VHF antenna should be used as a fine tuning control and should be adjusted until the best picture is obtained. In order to eliminate "Body Effect" when adjusting the antenna, stand in front and reach over the top of the set. Do not at any time force the knob in either direction if it becomes difficult to turn.



TRUETONE
Chassis 21T2A
Model ZD1326A

Horizontal Hold Control (L-30):
The horizontal hold control is located on the rear flange of the chassis and should be adjusted in the following manner.
Set the picture control to its normal operating position. Turn the thumb screw clockwise until it reaches its stop. Turn two complete turns counter-clockwise. The thumb screw is a vernier adjustment and will then be in the center of its range.
Turn the iron core with a small screwdriver or adjusting tool until the picture is steady (no horizontal movement). Set the core to the middle of its range.
After the iron core has been properly adjusted the thumb screw should then be used as a vernier adjustment to control synchronization, when necessary.

Centering Magnet (Figure 3):
The centering magnet should be rotated and the control adjusted until the picture is properly framed keeping in mind that the effect of the control is governed by the position of rotation. If the control is above or below the neck of the picture tube, the picture will be moved up or down. To the left or right of the neck of the picture tube, the picture will be moved either to the left or right.

Anti-Pin Cushion Magnet - 21" only (Figure 3B):
Adjust cushioning until an edge of the raster is visible. Loosen the positioning screws and slide the magnet backward or forward until the edge of the raster is vertically straight. If keyframing is noticed adjust magnets in vertical plane.

High Voltage Power Supply:
In the process of inspection, repairs, changing of tubes or transformers, or for any other reason where it is necessary to work within the high voltage power supply, the following should be closely observed:
1. Terminals on the 1X2A socket must be dressed toward the inside of the cone ring and be free of sharp protrusions.
2. Its presence useful, that is, properly centered and about 1/8 inch below the socket terminals.
3. All leads must be dressed as far away as possible from the transformer winding. Excess lead length should be transferred to the top side of the chassis.
When replacement of the H.V. deflection transformer is necessary, be sure to closely follow the precautions listed above. The transformer can easily be replaced with the chassis in the cabinet by the following procedure:
1. Remove two (2) hex head screws on either side of the H. Size control.
2. Overpage the H.V. lead holder ring. (back side of shield can)
3. Remove 250Kohm plate cap.
4. Remove shield can by pushing back side of shield can toward front and lifting up.

Sync Stabilizer Adjust Control (R-41):
The control varies the operational characteristics of the sync clipper stage to obtain the optimum operation point for the least effect of noise interrupting synchronization. The control should be adjusted for a steady picture.

DIAL CORD REPLACEMENT

DIAL CORD STRINGING: Two separate dial cords are used and can be restringed separately if replacement is necessary.

POINTER PULLEY STRINGING: Follow the above diagram (front view) and start by attaching the dial cord to the tension spring; route to pointer pulley and make 2 1/2 clockwise turns around pulley; wrap dial string under pointer lug as shown in rear diagram. Route under tuning 2 1/2 clockwise turns around driven pulley assembly, make 2 1/2 clockwise turns around driven pulley; make 2 1/2 clockwise turns around the driven pulley lug as shown in the diagram and connect to other end of tension spring. Tension spring must be in location shown when tuning shaft is rotated to extreme clockwise position.


MECHANICAL TRACKING: If for any reason the stop washers do not correspond to the stop position of the tuner, loosen the two (2) drive pulley allen head set screws and reposition. Turn both the tuning shaft and tuner shaft to the extreme clockwise position. Turn tuner shaft back 1/6 turn counter-clockwise. Tighten allen head set screws.

POINTER POSITIONING: If when a station is properly tuned in and the pointer is off calibration, reposition the pointers as follows:

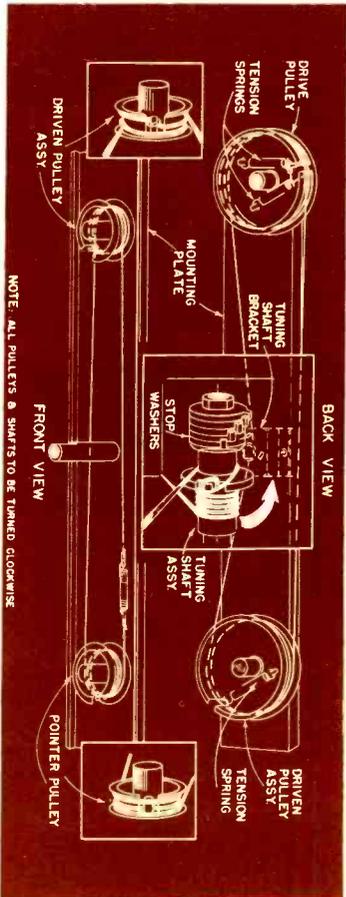1. Remove the on-off volume and tuning knobs (pull straight out)
 2. Remove two outside escutcheon screws and one small screw in center (in tuning knob recess), then remove escutcheon.
 3. Remove pointer indicator and reposition.
- DRIVE PULLEY STRINGING:** Drive pulley restringing requires removal of the mounting plate assembly. To remove the mounting plate assembly follow the simple instructions below:
1. Remove two (2) star knobs
 2. Remove two (2) drive pulley allen head set screws.
 3. Loosen three (3) spacer screws.
 4. Remove two (2) drive pulley allen head set screws.
 5. Pull assembly straight out.

To restring the drive pulley turn the tuning shaft completely clockwise. Follow the top back-view diagram (this view is for 60° reference only) and make 2 1/2 clockwise turns around the dial cord to the tension spring shown at the extreme left on the drive pulley. Route the cord through the opening in the pulley and make a 1/2 counter-clockwise turn around the pulley and four under the tuning shaft. Make 5 counter-clockwise turns around tuning shaft between counter-clockwise turns around the tuning shaft. Continue in the clockwise direction and make 1/2 turn around the counter-clockwise direction and make 1/2 turn around the tuning shaft between the lugged washer and stop washers. Route to the large driven pulley and then route to the drive pulley. Make two (2) complete counter-clockwise turns around the tension spring and second tension spring as shown. Add another tension spring in the driven pulley assembly as shown on the right side.

Replace mounting plate assembly and follow directions for mechanical tracking.



COIL DC RESISTANCE CHART

The DC resistance readings shown in the chart below have been taken with an ohmmeter directly across the coil being measured. The coils not listed in the chart have a DC resistance reading of less than one ohm. A tolerance of ± 5% is permissible.

| COILS | RESISTANCE IN OHMS | COILS | RESISTANCE IN OHMS |
|-------|--------------------|-------------------------------|--------------------|
| L17 | 1.5 | T4 PRI. | 170 |
| L20 | 1.5 | T5 PRI. | 960 |
| L22 | 2.2 | SEC. | 160 |
| L23 | 2 | T6 PRI. | 1100 |
| L24 | 2 | SEC. | 6.6 |
| L25 | 2 | T7A | 68 |
| L27 | 8 | B | 12.5 |
| L28 | 8 | T8 2510Q6 plate to 1X2A plate | 180 |
| L29 | 1.5 | 2510Q6 plate to term 4 | 9.5 |
| L30 | 80 | 2510Q6 plate to term 3 | 17.5 |
| L31 | 2.3 | 2510Q6 plate to term 1 | 25.5 |
| L32 | 72 | term 7 to term 8 | 2.6 |
| L33 | 8.5 | term 7 to term 10 | 5.4 |
| L34 | 2.3 | | 7 |
| | | | 4.7 |

UHF TUNER SERVICE DATA

To determine whether the oscillator section is functioning, a convenient check point has been provided where the oscillator grid current can be measured. To measure the oscillator grid current, place a Simpson Model 260 across the 20 microampere (K2). See Figure 4. A reading of 10 to 20 microamperes (K2) should be obtained if the oscillator is functioning normally.

Both the oscillator and crystal detector can easily be checked by measuring the oscillator injection current. Place a Simpson Model 260 Multimeter (or equivalent) on the 100 microamp scale across the 22 ohm resistor (R10) at the terminal indicated in Figure 5A or 5B depending on the version of the tuner. A reading of 5 to 40 microamperes should be obtained if both the oscillator and crystal are functioning normally.

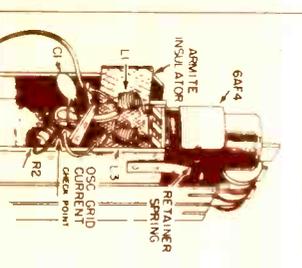


Figure 4

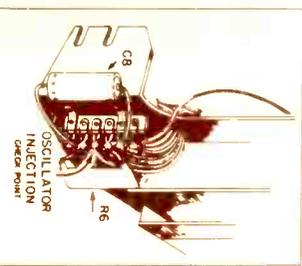


Figure 5A
Early Version

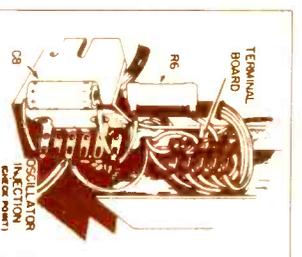


Figure 5B
Later Version

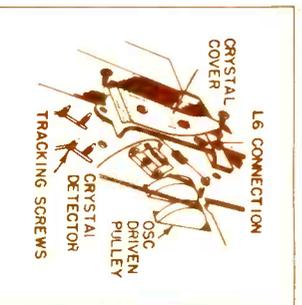


Figure 6. Top Chassis View.

CRYSTAL DETECTOR: If replacement of the CK-710 Crystal Detector is necessary, the picture tube must be removed along with the crystal cover (refer to figure 6). The crystal is soldered into place and should be carefully resoldered after replacement. Care must be taken to ensure that the crystal is soldered into place. Grasp each crystal lead with a pliers when soldering into place.



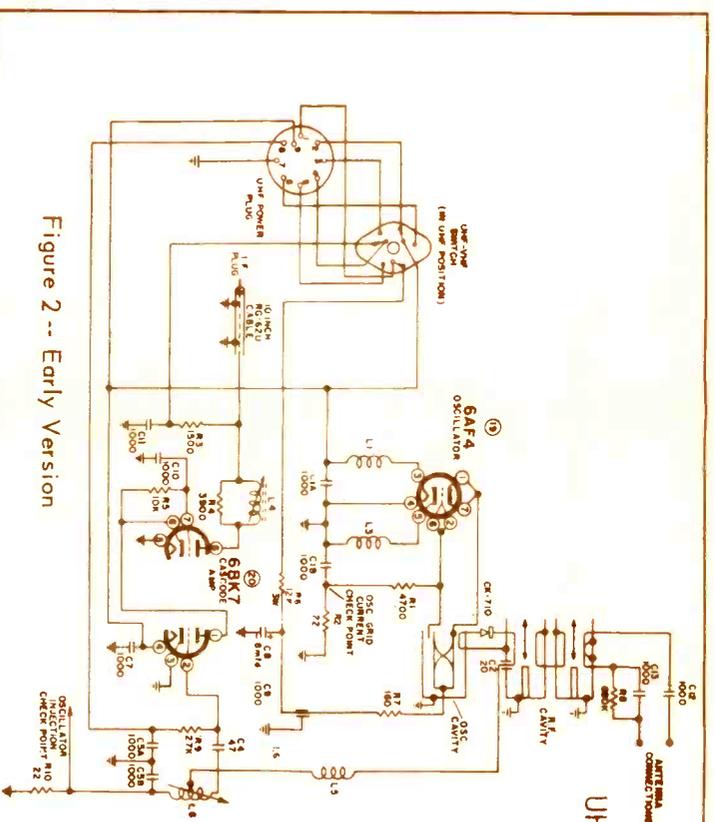


Figure 2 -- Early Version

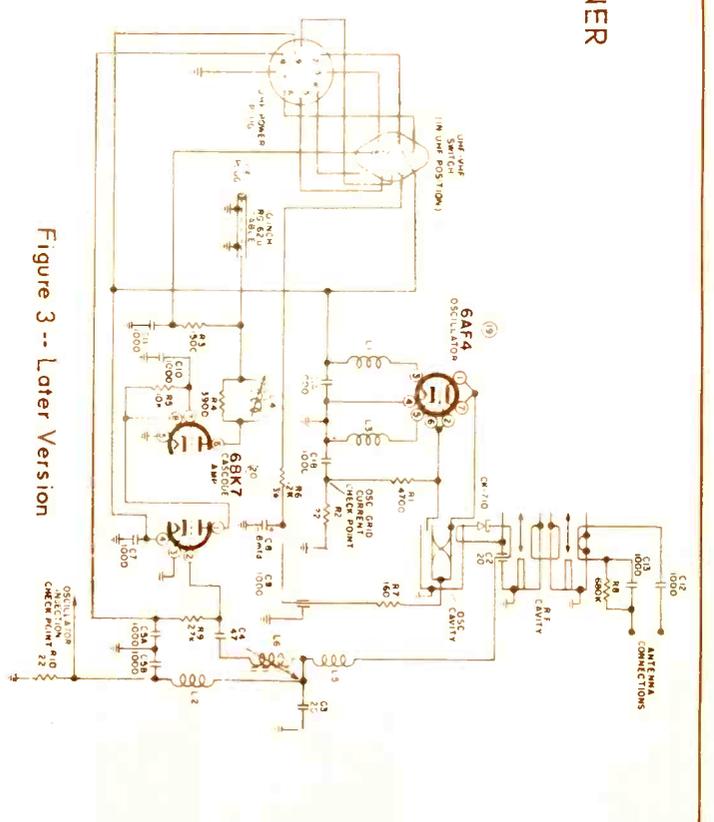

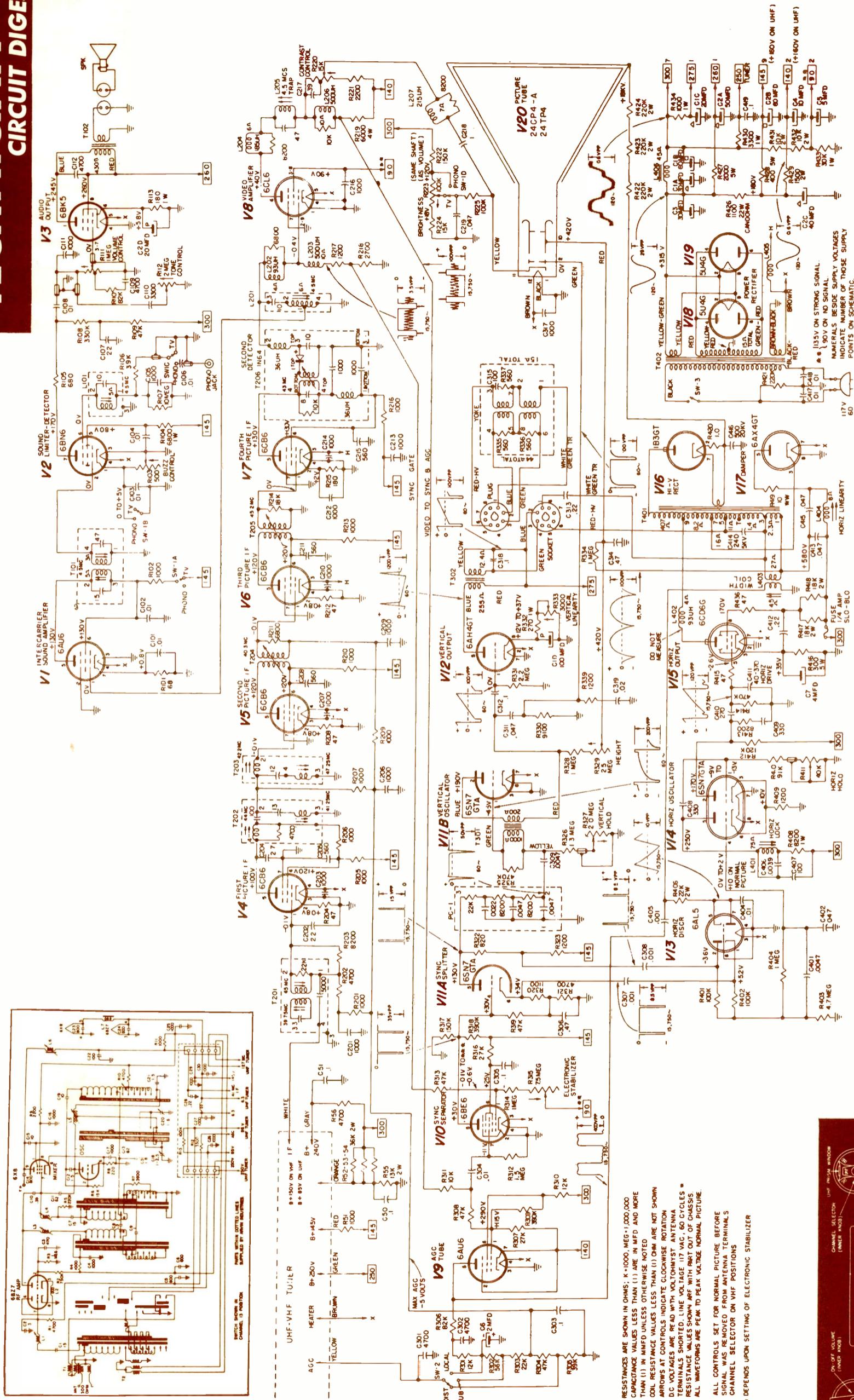

ARVIN
Chassis TE 359
Technician
CIRCUIT DIGEST
100


Chassis TE359:
9200 series

OPERATING THE TELEVISION CONTROLS (UHF) ON (UHF-VHF MODELS)
UHF operation is identical to (VHF) operation as outlined above, with the exception of step 3 and 4 which differ as follows:

3. Rotate the CHANNEL SELECTOR to UHF position-prism window UP.
4. Rotate the FINE TUNING until the dial pointer in the prism window is approximately at the desired channel number. Adjust the FINE TUNING for best picture definition--the second will automatically be best at this point due to "synchro-sound tuning."

NOTE: In its normal tuning position the FINE TUNING control moves the UHF dial pointer very slowly for accurate tuning. By PUSHING FIRMLY IN on the Fine Tuning Knob a direct drive will be engaged. This will allow very rapid movement of the UHF dial over the complete UHF band when the FINE TUNING is turned. When the dial pointer is in the vicinity of the desired channel number, the FINE TUNING should be released into its normal "geared-down" position for careful tuning of the station.

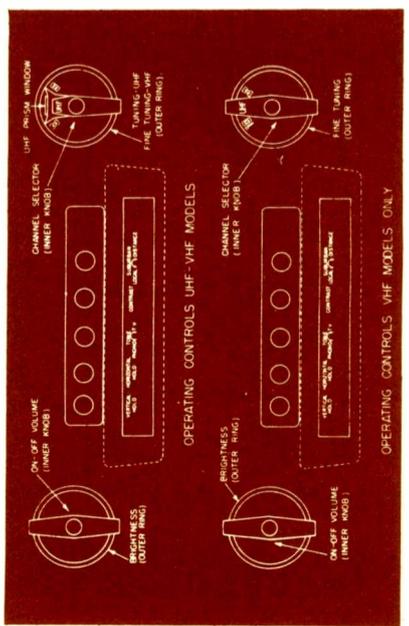1. RESISTANCES ARE SHOWN IN OHMS; K=1000, MEG=1,000,000
 2. CAPACITANCE VALUES LESS THAN (1) ARE IN PFD AND MORE THAN (1) IN MFD UNLESS OTHERWISE NOTED
 3. COIL RESISTANCE VALUES LESS THAN (1) OHM ARE NOT SHOWN
 4. ARROWS AT CONTROLS INDICATE CLOCKWISE ROTATION
 5. DC VOLTAGES ARE READ WITH VOLTAHMMYST ANTENNA TERMINALS SHORTED. LINE VOLTAGE 117 VAC, 60 CYCLES
 6. RESISTANCE VALUES SHOWN ARE WITH PRNT OUT OF CHASSIS
 7. ALL WAVEFORMS ARE PEAK TO PEAK NORMAL PICTURE
- ▶ ALL CONTROLS SET FOR NORMAL PICTURE BEFORE SIGNAL WAS REMOVED FROM ANTENNA TERMINALS CHANNEL SELECTOR ON VHF POSITIONS
- *** DEPENDS UPON SETTING OF ELECTRONIC STABILIZER



capacitor replacements

FOR SETS OF THE MONTH

CBS-COLUMBIA CHASSIS 750-3

| Symbol No. | Rating Mf @ WVDC | CBS-Col. Part No. | Sprague Replacement |
|------------|---------------------|----------------------|------------------------|
| C106 | 1 @ 50 | PA20138 | TVA-1300 |
| C129 | 50 @ 25 | PA20182 | TVA-1206 |
| C203 | 40+40+20+20 @ 450 | PA20144 | { TVA-2740 TVA-2730 |
| C216 | 5 @ 350NP | PA20174 | *TVA1504 |
| C310 | 10 @ 25 | PA20137 | TVA-1204 |
| C317 | 25 @ 12 | PA20147 | TVA-1205 |

* Use two units in series with reversed polarity.

CROSLEY CHASSIS 411, 411-1

| Symbol No. | Rating Mf @ WVDC | Crosley Part No. | Sprague Replacement |
|------------|-------------------------------|---------------------|------------------------|
| C125 | 5 @ 50 | 154103 | TVA-1303 |
| C140 | 10 @ 300/200+200 +30 @ 150 | 155910 | TVL-4559 |
| C142 | 10 @ 50 | 154104 | TVA-1304 |
| C147 | 200 @ 150 | 155911 | TVL-1431 |
| C148 | 200+5 @ 150 | 155426 | TVL-2444 |
| C164 | 10 @ 10 | 156054 | TVA-1204 |
| C176 | 20 @ 600 | 156021 | TVA-1906 |

SYLVANIA CHASSIS 1-518-1, -2, -3

| Symbol No. | Rating Mf @ WVDC | Sylvania Part No. | Sprague Replacement |
|------------|---------------------------------|----------------------|------------------------|
| C109 | 2 @ 50 | 161-1001 | TVA-1301 |
| C113 | 20+10 @ 400/20 @ 100/25 @ 25 | 161-4006 | R-1303 |
| C126 | 2 @ 50 | 161-1001 | TVA-1301 |
| C175 | 80+40 @ 400 | 161-2004 | TVL-2675 |
| C176 | 80+40 @ 200/100 @ 50 | 161-3012 | **TVA-4700 |
| C215 | 10 @ 500 | 161-1010 | TVA-1802 |
| C266 | 10 @ 450 | 161-1013 | TVA-1705 |

** Omit 10 Mf. Section.

Sprague makes more capacitors . . . in more types . . . in more ratings . . . than any other capacitor manufacturer. Send 10c for 44-page TV Replacement Capacitor Manual to Sprague Products Co., 65 Marshall St., North Adams, Mass., or get it FREE from your Sprague distributor.

TRUETONE MODEL 2D1326A (Chassis 21T2A)

| Symbol No. | Rating Mf @ WVDC | Truetone Part No. | Sprague Replacement |
|------------|----------------------------------|----------------------|------------------------|
| C70 | 100+10 @ 300/10 @ 75/100 @ 25 | 8C-20808 | TVL-4638 |
| C72 | 10+10 @ 300/10 @ 15 | 8C-20954 | TVL-3580 |
| C90 | 100 @ 150 | 8C-20709 | TVL-1423 |
| C91 | 100 @ 150 | 8C-20684 | TVL-1423 |
| C111 | 50 @ 300 | 8C-21274 | TVA-1613 |

WESTINGHOUSE CHASSIS V-2243-1

| Symbol No. | Rating Mf @ WVDC | Westing- house Part No. | Sprague Replacement |
|----------------------------------|----------------------------|-------------------------------|------------------------|
| C213B C409B C410B C411B | 30+10 @ 450/150+20 @ 50 | V-11535-1 | { TVL-3753 TVA-1306 |
| C216A C436A C502A C503A | 40+40 @ 450/30+30 @ 350 | V-9891-1 | TVL-4720 |
| C320 | 10 @ 450 | V-10293-1 | TVA-1705 |

ARVIN CHASSIS TE359

| Symbol No. | Rating Mf @ WVDC | Arvin Part No. | Sprague Replacement |
|------------|----------------------------------|-------------------|------------------------|
| C1 | 30 @ 400/60+20 @ 350/100 @ 50 | 22422-20 | R-1457 |
| C2 | 50 @ 400/60+40 @ 350/20 @ 25 | 22422-21 | { TVL-4707 TVA-1712 |
| C3 | 30 @ 400 | 22422-22 | TVA-1720 |
| C4 | 10 @ 350 | 41429 | TVA-1604 |
| C5 | 5 @ 250 | 40002 | TVA-1501 |
| C6 | 2 @ 150 | 41534 | TVA-1701 |
| C7 | 4 @ 150 | 25453 | TVA-1402 |

DON'T BE VAGUE...INSIST ON

SPRAGUE

(Distributors' Div. of the Sprague Electric Co.)

Have you hung up

your shingle?

IT PAYS TO KEEP GOOD COMPANY . . .
and it's good business to advertise the
good company you keep.


Thousands of dealers and servicemen
are using the sales-magic in the RCA name
to instill confidence in their customers.
Identifying *your* name with RCA pays off
in dollars and cents.

And it's so easy to do . . . because RCA's
new Dealer Identification Program pro-
vides you with a handsome "shingle" with
your name on it, that you'll be proud to
display in your shop. When a customer
sees this Dealer Identification Plaque he
knows you are using the best tube products
available.

So, we ask . . . "Have you hung up *your*
shingle yet?" If not, be sure to see your
RCA Tube Distributor today and learn
how *you* can qualify for a Registered
Dealer Plaque at no extra cost.

Unlock the door to bigger profits

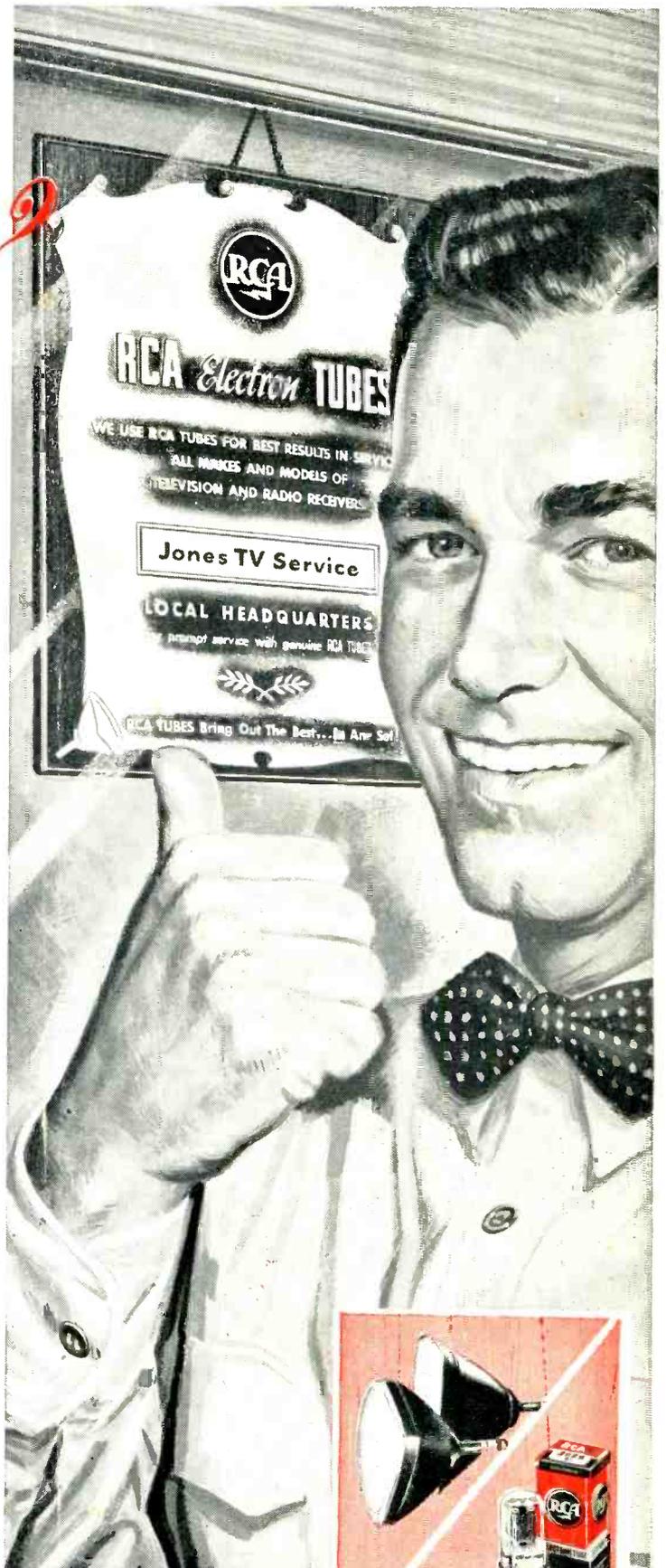Here's *your* key to better business . . . RCA's
dynamic Dealer Identification Program. Ask
your *RCA Tube Distributor* for your copy of the
colorful, 16-page booklet
"A Magic Pass-Key to
Customer Confidence."
It tells you how — for
the first time—you can
become a Registered
Dealer . . . and get
extra sales benefits.



RADIO CORPORATION of AMERICA
ELECTRON TUBES

HARRISON, N. J.