

# TECHNICIAN

## Circuit Digests

1954

August • 1954

### Growth of Service Test Equipment Over Past Three Decades

CALDWELL-CLEMENTS, INC.


1920's

Aerovox Wireless Corp.  
Alden Mfg. Co.  
Dubilier Condenser Corp.  
General Instrument Corp.  
Hoyt Electrical Inst. Works  
International Resistance Co.  
Jefferson Elec. Mfg. Co.  
Muter Co., Leslie F.  
Radio Corp. of America  
Raytheon Mfg. Co.  
Sprague Specialties Co.  
Sterling Mfg. Co.  
Sylvania Products Co.  
Thordarson Electric Mfg. Co.  
Westinghouse Elec. & Mfg. Co.  
Weston Electrical Instrument Corp.



Aerovox Corp.  
American Electronic Mfg.  
Approved Electronic Instrument Corp.  
Barker and Williamson  
Beam Instruments Corp.  
Browning Laboratories, Inc.  
Clarostat Mfg. Co.  
Cornell-Dubilier Elec. Corp.  
Crest Laboratories, Inc.  
DuMont Laboratories, Inc., Allen B.  
Electronic Instrument Co.  
Electronic Measurements Corp.  
Ecco Electronics, Inc.  
Feiler Engineering & Mfg. Co.  
General Electric Co.  
General Test Equipment Co.  
Granco Products, Inc.  
Heath Co.  
Hewlett-Packard Co.  
Hickok Electrical Instrument Co.  
Hoyt Electrical Instrument Works  
Hycon Mfg. Co.  
Industrial Instruments, Inc.  
Jackson Electrical Instrument Co.  
J-B-T Instruments  
Jerrold Electronics Corp.  
Kay Electric Co.  
Lampkin Laboratories  
Linear Equipment Labs  
Magne-Pulse Corp.  
Mallory & Co. Inc., P. R.  
Marion Electrical Instrument Co.  
Millen Mfg. Co.  
Miller Instruments, Inc.  
National Union Electric Corp.  
Ohmite Mfg. Co.  
Philco Corp., Accessory Div.  
Precise Development Corp.  
Precise Measurements Co.  
Precision Apparatus Co.  
Precision Electronics, Inc.  
Radio City Products Co.  
Radio Corp. of America, Tube Div.  
Radio Kits, Inc.  
Radio Merchandise Sales, Inc.  
Radion Corp.  
Service Instruments Co.  
Simpson Electric Co.  
Special Products Co.  
Sprague Products Co.  
Sterling Mfg. Co.  
Superior Instrument Co.  
Supreme, Inc.  
Sylvania Electric Products, Inc.  
Tektronix, Inc.  
Texas Instruments, Inc.  
Triplett Electrical Instrument Co.  
Vidair Electronics Mfg. Co.  
Waterman Products Co.  
Weston Electrical Instrument Co.  
Weston Labs.
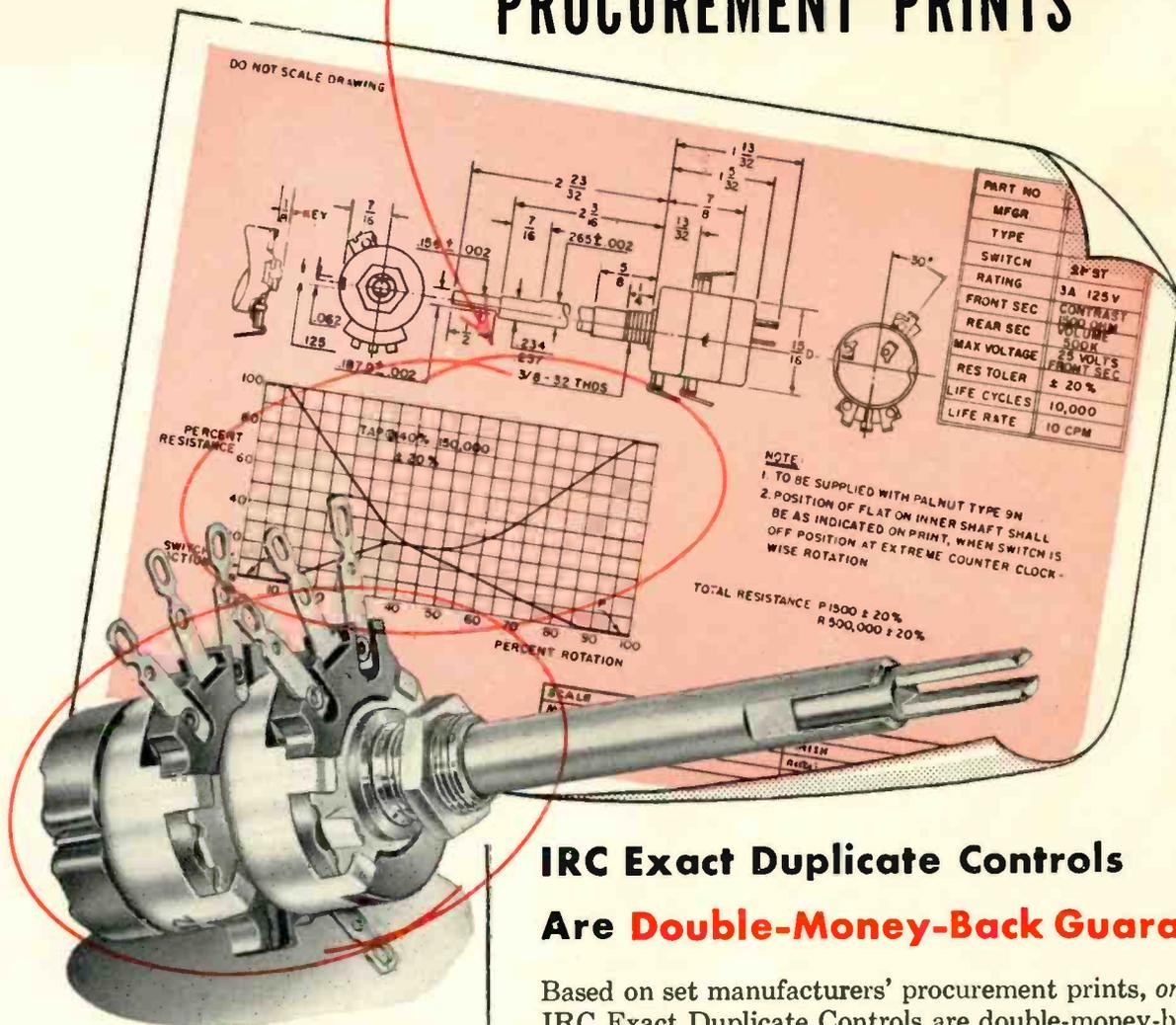
# ASSURED ELECTRICAL ACCURACY BASED ON MANUFACTURERS' PROCUREMENT PRINTS



**ONLY IRC GUARANTEES  
ACCURATE ELECTRICAL OPERATION  
AND SATISFACTORY MECHANICAL FIT  
OR DOUBLE-YOUR-MONEY-BACK**

Electrical specifications of this typical manufacturer's procurement print are exactly duplicated by IRC's QJ-412 control (shown). CONCENTRIKIT assembly includes P1-206 and R1-223 shafts with B17-109 and B13-133X Base Elements and 76-1 Switch.



Whenever the Circuit Says 

## IRC Exact Duplicate Controls Are **Double-Money-Back** Guaranteed

Based on set manufacturers' procurement prints, *only* IRC Exact Duplicate Controls are double-money-back guaranteed for accurate electrical operation. This firm guarantee applies to both IRC factory-assembled Exact Duplicates and universal CONCENTRIKIT equivalents.

Set manufacturers' electrical specifications are closely followed.

Resistance values are carefully selected to match.

Tapers are watched carefully; IRC doesn't arbitrarily substitute tapers to obtain wide coverage.

For exact duplicate controls of guaranteed accuracy, specify IRC. Most Service Technicians do.

## INTERNATIONAL RESISTANCE CO.

425 N. Broad Street, Philadelphia 8, Pa.

In Canada: International Resistance Co., Ltd., Toronto, Licensee

# TECHNICIAN & Circuit Digests

TELEVISION • ELECTRONIC • RADIO • AUDIO • SERVICE

M. CLEMENTS      O. H. CALDWELL  
Publisher          Editorial Consultant

SOL HELLER, *Managing Editor*  
SIDNEY C. SILVER, *Associate Editor*  
J. L. STOUTENBURGH, *Consulting Editor*  
ALBERT J. FORMAN, *Consulting Editor*  
DR. A. F. MURRAY, *Contributing Editor*  
ANN O'ROURKE, *Assistant Editor*  
CHARLES F. DREYER, *Art Director*  
ELMER KETTERER, *Circuit-Digest Production*  
GEORGE PUGLICI, *Circuit Diagrams*

## BUSINESS DEPARTMENT

M. H. NEWTON, *Business Manager*  
H. A. REED, *General Sales Manager*  
P. J. CARNESE, *Sales Promotion Manager*  
DIXON SCOTT, *District Manager*  
LEE GRAVES, *District Manager*  
CHARLES S. ROEVER, *District Manager*  
N. McALLISTER, *Asst. Business Manager*  
MARTHA USDIN, *Production Manager*  
KATHLEEN CAFARO, *Reader Service*  
M. GROENING, *Asst. Circulation Manager*  
JOHN J. BORGHI, *Controller*  
W. W. SWIGERT, *Credit Manager*  
480 Lexington Ave., New York 17, N. Y.  
Telephone PLaza 9-7880  
S. M. GASKINS, *Western Manager*  
JOHN D. LUPTON, *District Manager*  
201 N. Wells St., Chicago 6, Ill.  
Telephone RAndolph 6-9225  
CHRIS DUNKLE & ASSOCIATES  
*California Representative*  
3257 W. 6th Street, Los Angeles 5, Calif.  
Telephone DUmkirk 7-6149  
1355 Market Street, San Francisco  
Telephone KLondike 2-2311, Ext. 579

## CIRCULATION

This issue 50,000, which includes 45,114 professional servicemen and service managers of retail stores, 2,006 parts distributors, plus manufacturers and miscellaneous.

TECHNICIAN & CIRCUITS DIGESTS, August 1954, Vol. 60, No. 2. \$5.00 a copy. Published monthly by Caldwell-Clements Inc., Publication Office, Emmett St. Bristol, Conn. Editorial, Advertising and Executive Offices, 480 Lexington Ave., New York 17, N. Y. Entered as second class matter at the Post Office at Bristol, Conn. June 10, 1954. M. Clements, President; M. H. Newton, Assistant to President; John J. Borghi, Vice President and Secretary; M. B. Clements, Treasurer. Subscription rates: United States and Canada, \$4.00 for one year; \$6.00 for two years; \$8.00 for three years. Pan-American and foreign countries: \$7.00 for one year; \$10.00 for two years; \$14.00 for three years. Printed in U.S.A.

Copyright by  
Caldwell-Clements, Inc., 1954

AUGUST, 1954

TECHNICIAN'S Test Equipment "Spec Charts" provide some much-needed data on five types of service instruments. You'll find these charts very helpful as a "purchaser's guide."

Open Letter to Test Equipment Mfrs. ....	13
"Tuning in the Picture" .....	14
Using the Oscilloscope for TV Receiver Servicing James A. McRoberts	16
Setting Up A Successful Public Address Sound System Arthur H. Smith	18
Making the Most of Your Test Equipment ..... Maury Goldberg	21
Why You Need "High Fidelity" .....	22
Louisiana Technicians Fight "Gyp" Competitors Charles R. Maduell, Jr.	24
Auto Radio Service Notes .....	26
Shop Hints .....	28
Color Shorts .....	30
Test Equipment "Spec" Charts .....	34
New Antennas .....	40
"Tough Dog" Corner .....	42
New Tubes & Accessories .....	44
New Test Instruments .....	46
Industry Keyhole .....	47
New Shop Equipment .....	50
Transmission Line Review ..... Edward Abbo	54
New CBS and RCA Large-Screen Color Tubes .....	61
Circuit Digests* .....	65

## DEPARTMENTS

Letters to the Editors .....	10	Technician's Lighter Side .....	51
Calendar of Coming Events .....	15	Manufacturers' Catalogs & Bulletins	52
Service Association Reports .....	32	New Books .....	53
New Products .....	40	News of the Industry .....	62
News of the Reps .....	62		

## CALDWELL-CLEMENTS, INC.

Publication Office, Bristol, Conn.

Editorial/Business Offices 480 Lexington Ave., New York 17, N. Y., Tel. Plaza 9-7880  
Publishers also of MART and TELE-TECH & ELECTRONIC INDUSTRIES

\*Reg. U. S. Patent Office

# Naturally

I'm building my Electronics  
On **DELCO** and

**UNITED MOTORS SERVICE**

DIVISIONS OF GENERAL MOTORS CORPORATION

It pays to deal with names you know—names that through years of service have won national respect for dependability and business integrity. Through these great names you can build a better electronics business on a solid foundation that offers many exclusive advantages to the industry.

**ONE SOURCE**

- Delco offers special application parts as well as complete coverage of the most important universal parts groups.

**ONE POLICY**

- A single sales policy for all electronics parts eliminates the confusion of dealing with many manufacturers.

**ONE BILLING OPERATION**

- Means fewer records to keep, fewer purchase orders; cuts bookkeeping time and costs to a minimum.

**READY-MADE MARKET**

- In addition to universal replacement parts, Delco is the sole source for original equipment replacement parts on all Delco radios.

**TECHNICAL ASSISTANCE**

- Current bulletins and field schools play an important part in keeping the industry well posted on new developments.

**DISTRIBUTION**


- United Motors Service maintains 21 strategically located warehouses to assure ample supply of all parts.

**QUALITY**

- You are assured of uniformity of parts, built to high standards of production and to exacting specifications.



**SPEAKERS**

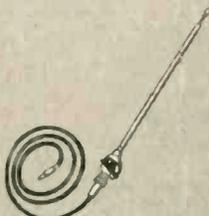


**AUTO RADIO AERIALS**



**VIBRATORS**




**CONTROLS**

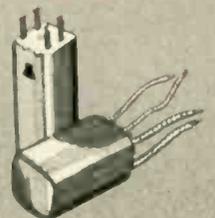

**COILS**


# Business

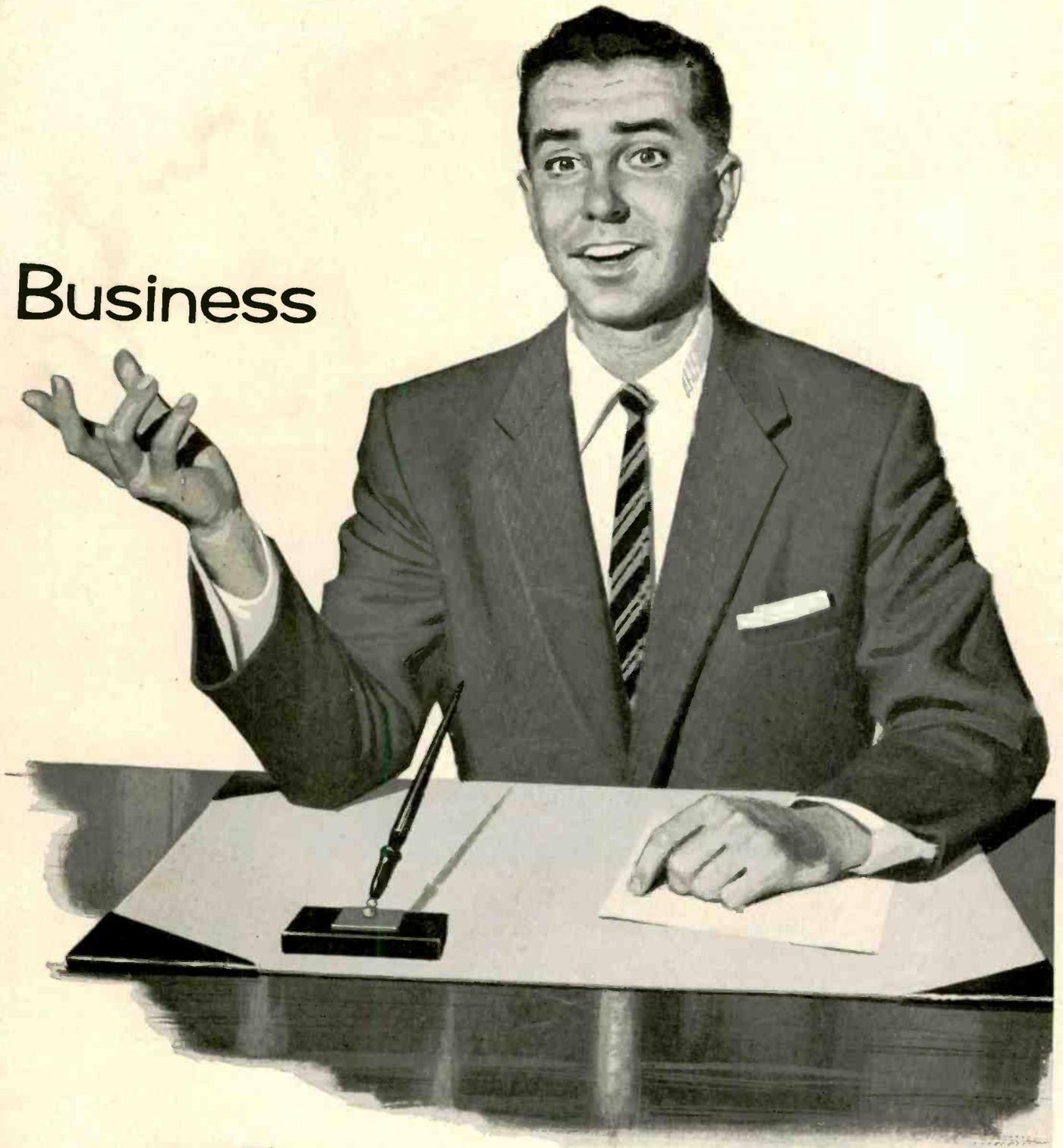


A GENERAL MOTORS PRODUCT   A UNITED MOTORS LINE



CAPACITORS

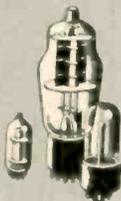


RECEIVING TUBES

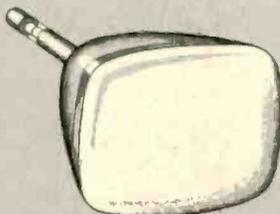

PICTURE TUBES



CONDENSERS

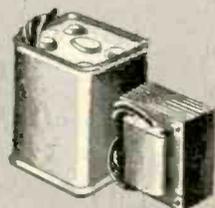

TRANSFORMERS



*Duette*

# Treasure Chest

**F**IRST to give you the real high fidelity of a two-way speaker system in a small package—the Jensen "Duette" won your acclaim.

Now the Jensen Duette "Treasure Chest" model is an elegant compliment to your decor whether traditional or modern. The handsome versatile chest design is available in either selected mahogany or blonde oak veneer with genuine matching hardwood trim.

The "Treasure Chest" Duette fits on your book shelf or in a small table area. Measures only 11" by 23¼" by 10". The "Treasure Chest" may be made into a graceful free-standing piece by the addition of modern wrought iron legs—available separately.

Duette "Treasure Chest" gives the full performance of the true two-way system with its special 8-inch woofer and compression driver tweeter in an unusually compact scientifically designed acoustic enclosure. Ideal for

small space hi-fi system, excellent as an improvement addition for true hi-fi from existing radio, TV, phonograph or tape recorder. Capable of adequate bass reproduction even at low listening levels. Clean, smooth response with the unmistakable presence of the true two-way reproducer.


The Jensen "Treasure Chest" Duette in either blonde oak or mahogany is an extraordinary value at **\$76<sup>50</sup> net.**

ST-862 Wrought iron leg set, \$4.25

Also see the "Duette DU-201" in Dupont Fabrikoid finish at a new low price **\$62<sup>50</sup> net.**

And the "Duette Portable" in black leatherette carrying case at only **\$77<sup>50</sup> net.**

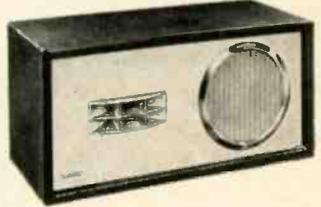*Jensen has been the world's quality standard in loudspeakers for more than a quarter of a century.*



**DUETTE DU-201**



**DUETTE PORTABLE**

# Jensen MANUFACTURING COMPANY

Division of The Muter Company  
6601 South Laramie Avenue • Chicago 38, Illinois  
In Canada: COPPER WIRE PRODUCTS, LTD., Licensee

*"Wish someone had thought of the vertical chassis before"*

CHARLES W. RHODES

*"Back-breaking chassis tugging belongs to the past"*

L. B. HALLBERG

*"Another wonderful feature—easier circuit tracing"*

ROY R. THOMPSON

# CROSLEY SUPER-V IS A SERVICE MAN'S DREAM


*—read these letters*

"The Super-V is not only a low-priced set, but a set that can be maintained at a low price, which is equally important. I only wish that someone had thought of the vertical-chassis arrangement for a TV set before. To me, there is nothing more annoying than fishing around blindly trying to get a miniature tube back into its socket on a conventional chassis."

Charles W. Rhodes, Electronic Service Mgr.  
Robert L. Rice & Co., Portland, Oregon

"By removing the cabinet back, every tube is right in front of one's eyes. No more groping and twisting to relocate tube-socket pins. Back-breaking tugging of the chassis belongs to the past. If a repair or check of chassis components is necessary, a few screws are removed and the cabinet lifts off like a bonnet. The separate diagram showing the actual filament wiring makes the search for an open filament a matter of seconds."

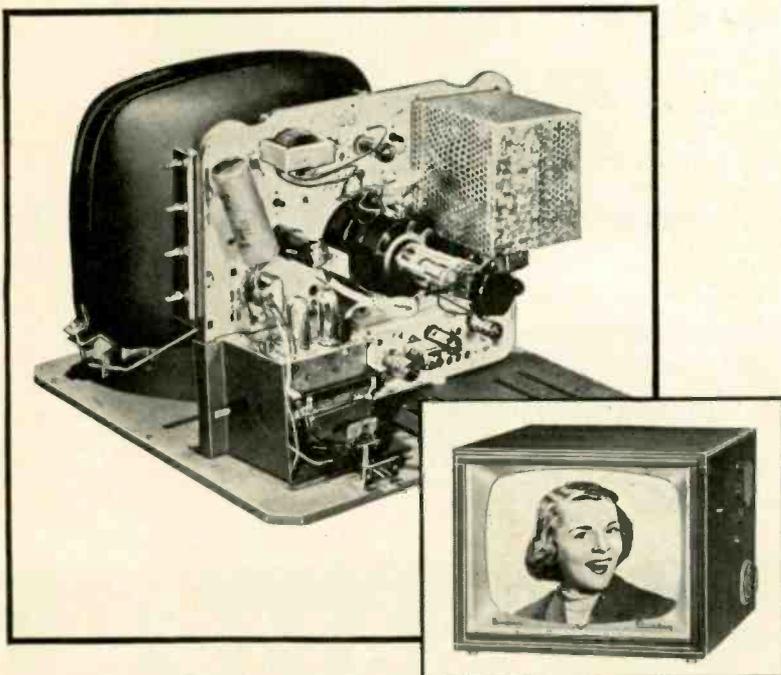L. B. Hallberg, Manager, Service Dept.  
Hardware Products Co., Sterling, Ill.



"The Crosley Super-V is a service man's dream; the new vertical plane chassis allows the changing of any tubes in a very few minutes. When service of a more complicated nature is required, the entire cabinet can be removed by loosening 6 screws; this leaves the entire chassis accessible for service. Another wonderful feature is that the picture-tube chassis and bracket are incorporated in one common mounting board along with the points wired on terminal strips for easier circuit tracing."

Roy R. Thompson, General Service Manager  
Saginaw Distributors, Inc., Saginaw, Mich.

Crosley  
Division



Cincinnati  
25, Ohio

# SCIENTIFICALLY DESIGNED ...


**FOR BETTER TV RECEPTION**

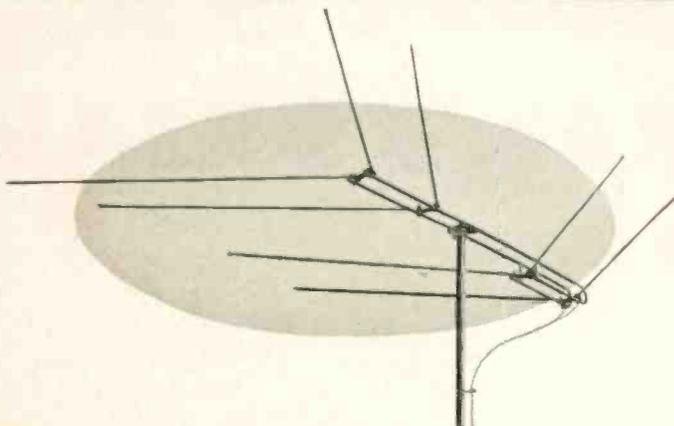**... BETTER PICTURE QUALITY**





Scientifically designed to give top performance, Philco television antennas are products of extensive research into receiver requirements in all types of locations. Field tested electrical and mechanical designs provide

proper gain, directivity, bandwidth and impedance... long life and ease of installation. Now a wide choice of Philco television antennas give you better picture quality... build complete customer satisfaction... more sales for you!




**PHILCO TWO-BAY SUPER CONICAL ALL-CHANNEL ANTENNA:** Strong signal pickup on VHF channels 2 through 13, UHF channels 14 through 83... ideal reception in fringe areas... all-aluminum: Part No. 45-3096-2. Fringe area single bay design: Part No. 45-3096.

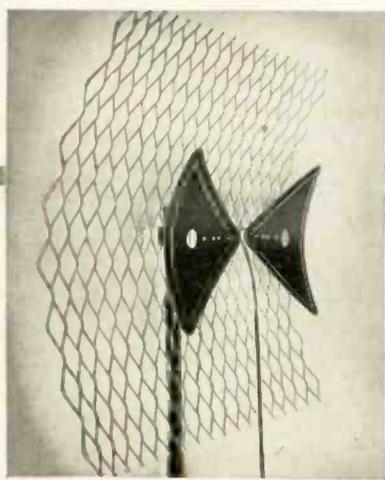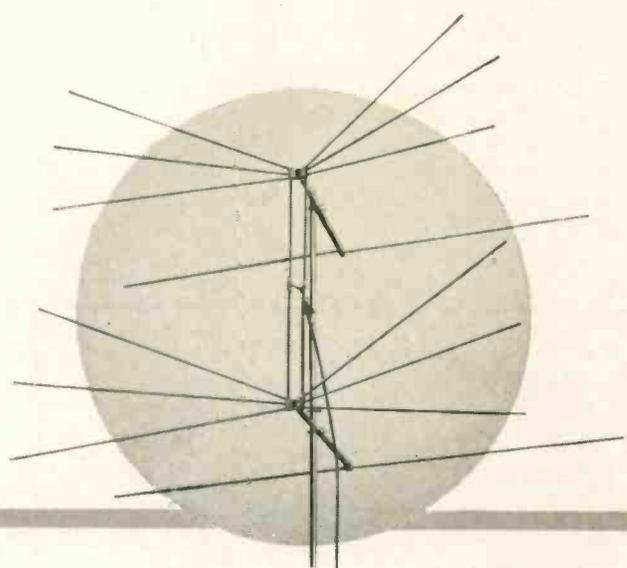**PHILCO ALL-CHANNEL UHF-VHF TROMBONE ANTENNA:** The ideal antenna for areas having both UHF and VHF stations. The Philco Trombone can be stacked for VHF fringe area use. Completely pre-assembled at the factory... all-aluminum construction with dowelled elements: Part No. 45-1880.



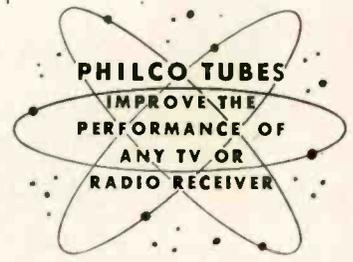**PHILCO PARAFLECTOR ALL-CHANNEL UHF ANTENNA:** Pre-assembled, all-aluminum... 8 db to 10 db gain... outstanding fringe area performance... immediate mounting on existing masts: Part No. 45-3071. Bow Tie, Part No. 45-3069 and Bow Tie with reflector, Part No. 45-3070 provide top quality pictures in many UHF areas.





# PHILCO CORPORATION

# PHILCO

... SUPER PERFORMANCE

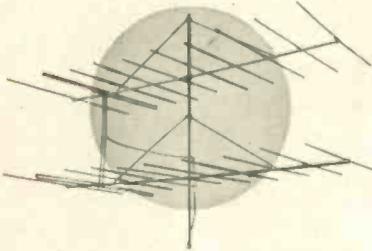
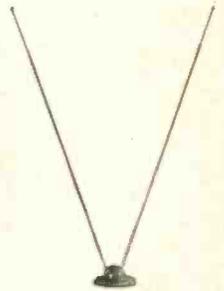
## TV ANTENNAS

**PHILCO VHF "V" ANTENNA:** Adequate reception on all VHF channels in most localities . . . heavy chrome plated three-section brass tubing . . . weighted plastic base holds antenna fully extended in any direction: Part No. AD-2643. Also available with aluminum tubing "V": Part No. AD-2643-1.





**PHILCO TWO-BAY VHF LOW BAND YAGI ANTENNA:** 10 elements . . . all-aluminum . . . factory pre-assembled. Top performance on channels 2 through 6 . . . 13 db to 15 db gain on various channels. Single bay Part No. 45-3112-2 through 6. Stacked version uses stack-harness Part No. 45-3267.

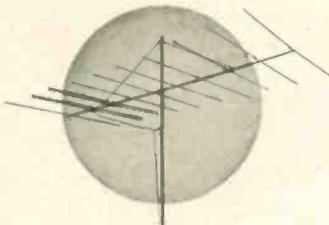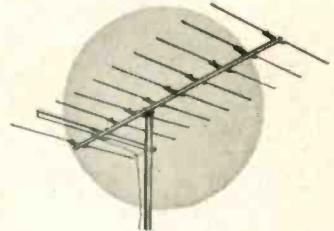**PHILCO HIGH BAND VHF YAGI ANTENNA:** Pre-assembled, all-aluminum, 10 elements . . . high gain in fringe areas on channels 7, 8, 9, 10, 11, 12, or 13 . . . 10 db to 12 db gain on various channels . . . eliminates co-channel station interference: Part No. 45-3112-7 through 13.



**PHILCO BROAD BAND VHF YAGI ANTENNAS:** All-aluminum, factory assembled for quick installation . . . high gain plus adequate band width. Three broad band models cover channels 2 to 6 . . . 4, 5, 6 . . . or 7 through 13: Basic Part No. 45-3112.

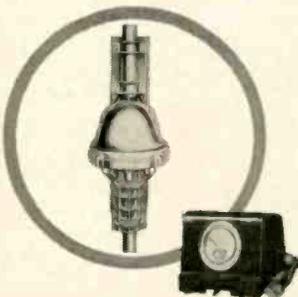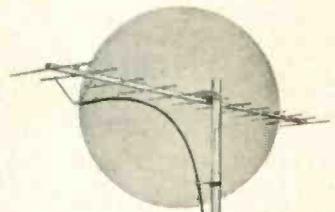
**PHILCO GOLDEN YAGI UHF ANTENNA:** Designed for 300 ohm operation . . . all steel construction . . . 11 db to 12 db gain on various channels . . . "Cronak" coated components resist salt air . . . humidity . . . six models cover entire UHF spectrum: Basic Part No. 45-1996.


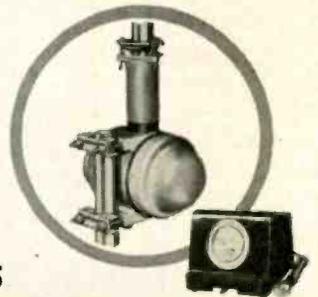
### ← PHILCO HEAVY DUTY ANTENNA ROTORS: →

**PHILCO MODEL P-4:** Supports antenna installations weighing up to 150 pounds . . . completely weather sealed . . . factory lubricated for life . . . uses 4-wire rotor cable . . . modern direction meter control cabinet: Part No. 45-1974.

**PHILCO MODEL P-11:** Easily handles two-bay arrays . . . mounts on masts up to 1 5/8" in diameter . . . accurate direction control . . . heavy duty motor . . . streamlined design . . . uses 4-wire rotor cable . . . modern direction meter control cabinet: Part No. 45-1994.




A complete line of powerful Philco TV antenna rotors as low as **\$39.95**

## ACCESSORY DIVISION

'A' AND ALLEGHENY AVE. • PHILADELPHIA 34, PA.

*Sensationally  
New!*

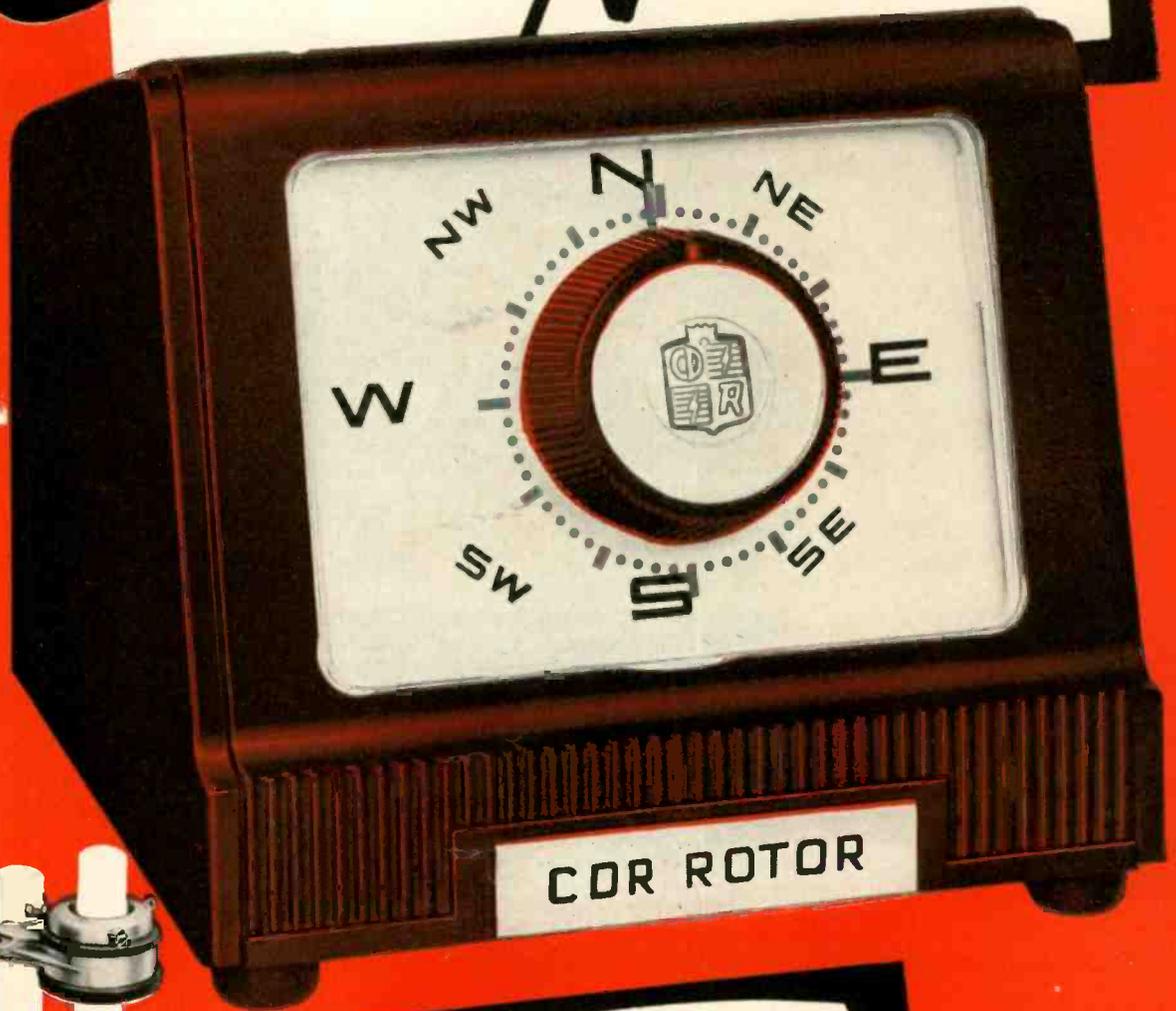

*Pre-Sold* to consumers in every leading TV market area with saturation TV spot announcements as well as newspaper advertisements. These further helps — animated point-of-sale display... newspaper mats ... envelope enclosures... window streamers.

Models AR-1 and AR-2

# CDR AUTOMATIC ROTOR

*40% sharper tuning*  
than any other  
**AUTOMATIC ROTOR**

They said it couldn't be done — never thought it possible — but **HERE IT IS!** The AR-1 and AR-2... the sharpest tuning **AUTOMATIC ROTORS** in the world. Superior construction and quality manufacture are featured in these as in the other **CDR ROTORS**, plus a handsome **NEW MODERN DESIGN CABINET** styled along lines for gracious, contemporary living. An added feature is a **MECHANICAL BRAKE THAT IS RELEASED MAGNETICALLY!** Here, truly, is the ultimate in rotors — handsome design, accurate, pinpoint, automatic performance easier to set and adjust — and **CDR dependability!**

### Model AR-2

... complete, **AUTOMATIC** rotor with **THRUST BEARING**... and handsome modern design plastic cabinet, uses 4 wire cable..... **47.95**

### Model AR-1

... same as AR-2, without thrust bearing..... **44.95**

### Model TR-2

*The heavy-duty rotor with plastic cabinet featuring "Compass Control", illuminated "perfect pattern" dial, uses 8 wire cable.....* **44.95**

### Model TR-4

*The heavy-duty rotor complete with handsome, modern design cabinet with meter control dial, uses 4 wire cable.....* **48.95**

### Model TR-11

*The same as the TR-12 without thrust bearing, complete with meter control dial cabinet, uses 4 wire cable* **39.95**

### Model TR-12

*A special combination value consisting of complete rotor including thrust bearing. Handsome modern cabinet with meter control dial, uses 4 wire cable* **42.95**



**CORNELL-DUBILIER**

SOUTH PLAINFIELD, N. J.



THE **RADIART** CORPORATION

CLEVELAND 13, OHIO

# DEALERS...

LIVE LIKE  
KINGS ON

 **CROWN'S**

NEW

## PFP PLAN




### WHAT IT IS—

It's a sensational new plan that increases your profits and makes it doubly attractive for you to promote and sell the famous Crown Antenna Rotator. Win wonderful, nationally advertised prizes for yourself, your wife and family, on Crown's new and exclusive "Points for Profit" Plan.
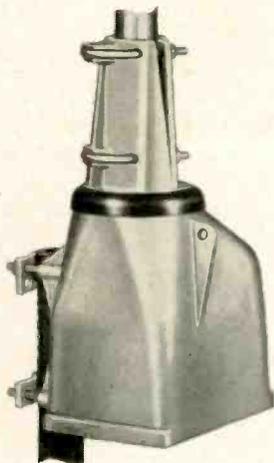
### HERE'S HOW IT WORKS—

For twelve months only, Crown will award you with 36 prize winning points for the sale of each Crown Antenna Rotator. Prize points may be accumulated during this period enabling you to win any of the more than 500 valuable prizes featured in Crown's "P.F.P." catalog. Wonderful, easy-to-win, prizes are awaiting you—Start participating in this sensational prize winning program by purchasing a Crown Antenna Rotator from your distributor, today—He has complete "P.F.P." details ready for you now!



Remember—when you sell Crown you are selling a high quality rotator, at a competitive price, with the highest profit in the antenna rotator field. Last year only 1.06% of units sold required service.

## SELL with confidence

sell  **CROWN**

 **CROWN** CONTROLS Co., Inc.

NEW BREMEN,  
OHIO

SUBSIDIARY—CROWN CONTROLS MFG., LTD., 1166 LAKESHORE RD., LONG BRANCH, ONT.

## LETTERS

To the Editors

### Stripped-Set Headache

EDITORS, TECHNICIAN:

Your editorial last month ("Stripped TV Sets Spell Trouble") was okay, but you overlooked some important angles. I know a lot of manufacturers have backed the independent servicer by keeping factory service to a minimum, running ad campaigns for the public that give us a pat on the back and even hold free training lectures for us—but doesn't this help them, too?

Take a look at the problem. You can buy one of these stripped sets for less than \$150. Since it needs more servicing, you could shell out with \$50 during the first year in repair bills. That's more than a third of the original cost. No wonder the public squawks. How would you like to pay \$700 during the first year in repair bills on a new car that cost you \$2000? The technician, trapped between the original cost and the fee he must charge if his family is to keep on eating, is on the spot.

Looking at it this way, the manufacturer is lucky to get out of the servicing end of the business. He's steering clear of a low-profit or no-profit operation. Free training and favorable ads don't take all the curse off the situation, either. Why can't the set makers take some of the dough they sink into these programs and put it back into their sets? It might do us all more good that way. Or else, why don't they underwrite some of the first-year servicing costs on these stripped chassis?

Most manufacturers are still on the ball as far as protecting their brand names with good quality is concerned. To the few who are creating the problem, I say this: "You need us as much as we need you. Let's get together on this problem for our mutual benefit."

E. BROWN

Detroit, Mich.

### Suggestion

EDITORS, TECHNICIAN:

Just one suggestion. Would it be possible to run some articles on tape recorders, both servicing and fundamentals? With several . . . concerns readying pre-recorded tapes, I believe we will need any hints and information we can get.

DONALD RINGLER

Washington, D. C.

• We won't let you down. Watch future issues.—Ed

### ATTENTION ANTENNA MANUFACTURERS

If you have not received your Antenna Specifications questionnaire, to be used in compiling an up-to-date Antenna TV "Spec" Chart in the September issue, please notify this office immediately.

Mr. Service Dealer:

**THIS RAYTHEON AD IS YOUR AD**

**LIFE**

**"DOCTOR"**  
(of Sound and Sight)

Your **RADIO AND TELEVISION SERVICE DEALERS** might be called *eye and ear specialists*, because theirs is the exacting job of curing the ills of the instruments that supply you with looking and listening pleasure. To accomplish the tremendous task of keeping America's millions upon millions of television and radio sets in top condition, requires many trained technicians of expensive up-to-the-minute equipment, and a wealth of experience and know-how.

America is fortunate indeed to have tens-of-thousands of conscientious TV-Radio technicians from coast to coast, doing the miraculous job of keeping up with this complex and fast growing industry. Raytheon salutes them all and is especially proud of those who are **RAYTHEON Bonded ELECTRONIC TECHNICIANS**. During the past ten years more than 35,000 Registered Bond Certificates have been issued by Raytheon to qualified service dealers all over the country. In spite of the fact that these dealers have handled many millions of jobs *less than fifty complaints* have been received.

Facts such as these justify confidence in your TV and Radio Service Dealer. Make doubly sure of satisfaction by taking a moment to look up the Raytheon Bonded Electronic Technician near you. Find him through his shop identification or in the yellow pages of your telephone directory.

**RAYTHEON**  
NEWTON MASS. CHICAGO ILL. ATLANTA GA. LOS ANGELES CALIF.

**RAYTHEON MANUFACTURING COMPANY**, Receiving and Cathode Ray Tube Operations

RECEIVING AND RADIO TUBES, INDUSTRIAL AND POWER TUBES, TELEVISION SETS, ROOM AIR CLEANERS, SEMICONDUCTOR PRODUCTS, DIODE EQUIPMENT, ELECTRONIC COMPONENTS, ELECTRONIC EQUIPMENT, ELECTRONIC COPIERS, ELECTRONIC INSTRUMENTS, ELECTRONIC PUBLISHERS, INDUSTRIAL EQUIPMENT, ELECTRONIC MACHINE TOOLS, AND ELECTRONIC TUBES, SOLES, RAYX AND COMMERCIAL TUBES FOR THE UNITED STATES GOVERNMENT

**Look for this seal, here's what it stands for:**

1. GUARANTEES ALL RAYTHEON AND TELEVISION BOND PARTS UNDER FULL PAYMENT
2. Use only parts of recognized quality
3. Charge not more than list price for parts
4. Test customers' tubes as accurately as possible
5. Keep labor charges at a reasonable level
6. Perform only such work as is necessary
7. Maintain proper equipment for good repair work
8. Maintain the highest quality service

**RAYTHEON**  
**Bonded**  
**ELECTRONIC TECHNICIANS**

**EGC**

SEPT. 13, 1954

More than twenty-six million people will read about you and the good work you are doing, in the September 13th issue of LIFE Magazine. We at Raytheon are publishing this advertisement because we believe you deserve a public pat on the back for the successful way you have met every challenge of the Radio and Television Service industry. We

are telling you about it in advance so that you can take full advantage of its appearance to help increase your volume and profit. It's our way of saying thank you for using and recommending *Raytheon Quality Radio and Television Tubes*.



**RAYTHEON MANUFACTURING COMPANY**

Receiving and Cathode Ray Tube Operations  
Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

RAYTHEON MAKES ALL THESE:

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • SEMICONDUCTOR DIODES AND TRANSISTORS • NUCLEONIC TUBES • MICROWAVE TUBES

# The BACKSTOP


**STOPS co-channel and adjacent-channel interference caused by rear signal pick-up!**

- Highest front-to-back ratio ever built into an antenna!
- No rear pick-up; eliminates "venetian blinds"!
- Largest screen area: 70 square feet!
- Very high all-channel gain. Incorporates basic Champion design, including Tri-Pole, with additional elements!
- Completely preassembled!


Table of Front-to-Back Ratios (Relative Voltage)

Channels	Front-to-Back Ratios
2	9:1
3	10:1
4	11:1
5	20:1
6	18:1

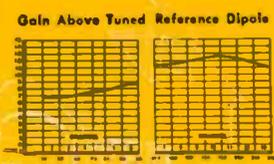Only Low Band channels shown, since co-channel interference is not encountered on High Band channels.



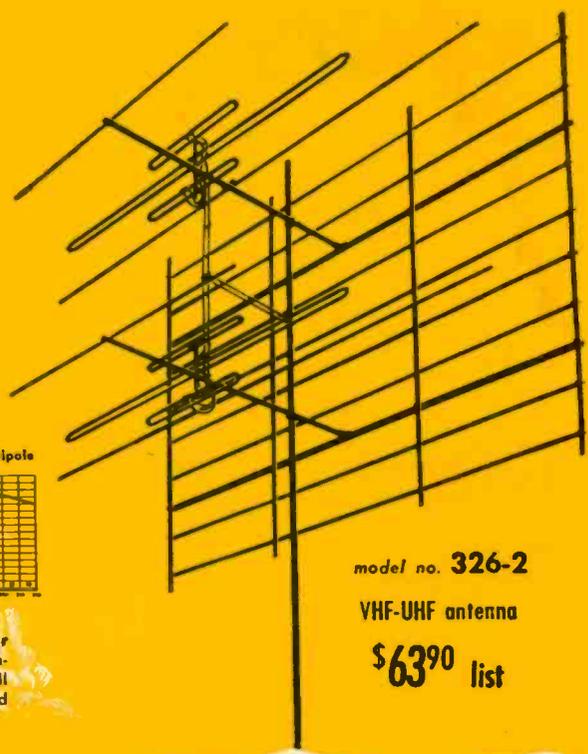**IMPORTANT** . . . don't be misled by polar patterns representing relative POWER. Remember, power is the square of voltage. All Channel Master polar patterns are presented in relative VOLTAGE.



model no. 326-2  
VHF-UHF antenna  
**\$63<sup>90</sup>** list

## 2 radical new antennas by CHANNEL MASTER

The most beautiful antenna ever made! The only indoor antenna featuring powerful outdoor design principles — Bow-Tie and Screen.

*Wonder Bow*

\* VHF-UHF indoor antenna


### DESIGNED FOR POWER!

On **UHF**: For primary and secondary areas. In many cases, performance is equal to actual outdoor installations. Good directivity on all channels.  
On **VHF**: Ideal in areas of strong VHF signals.

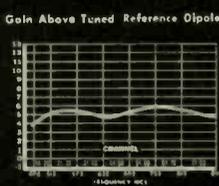
### STYLED FOR BEAUTY!

Designed by a well-known industrial designer, the WONDER BOW is proof that indoor antennas can be beautiful as well as powerful. Wins customer approval on beauty alone!

The first gain figures ever to be published for an indoor antenna!



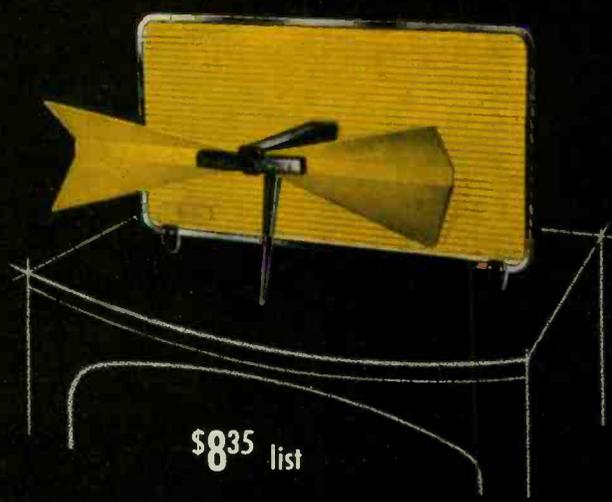**Gold and black**  
model no. 416  
**Silver and black**  
model no. 417



**\$835** list



**CHANNEL MASTER CORP.** ELLEVILLE, N. Y.  
The World's Largest Manufacturer of TV Antennas

Write for complete technical literature.  
Copyright 1954, Channel Master Corp.

\*Pat. No. D-171560

# TECHNICIAN & Circuit Digests

CALDWELL-CLEMENTS, INC., 480 LEXINGTON AVENUE, NEW YORK 17, N. Y.

## Open Letter to Test Equipment Mfrs.

*Accurate, Complete "Specs" Should Be Made Available to Technicians*

No serviceman will quarrel with the statement that properly designed test equipment is a must in the TV-radio repair shop. An instrument of good quality can, when properly used, greatly speed up service work and boost service revenue. An instrument with significant design faults, on the other hand, particularly faults (or limitations) poorly comprehended by the user, can make a difficult service job of a relatively simple one, and cause appreciable losses of time and money.

Let's get down to cases. The signal output of some sweep generators is quite non-linear. If the user isn't familiar with the non-linearity introduced by his instrument, some alignment jobs may prove quite troublesome. The non-linearity present may vary with the output setting of the generator, further complicating the job of interpreting response curves.

In quite a few oscilloscopes, the vertical attenuator control is not frequency-compensated. Measurement of horizontal sweep signals at one vertical amp. setting may not provide the same amplitude indication that it will at another setting. Furthermore, composite video signal waveshapes change considerably with vertical gain setting in these scopes. Confusion and delay may result if the technician is unfamiliar with the true source of these conditions.

### Case in Point

A TECHNICIAN reader wrote us some time ago, telling about a service job that had taken him quite some time to perform. The waveforms of the horizontal sync pulses in some stages were considerably smaller than those cited by the set manufacturer. The technician accordingly assumed that trouble in one of these stages was present. It took him several hours before he deduced that the limited frequency response of his (newly-

purchased) scope was responsible for the reduced amplitude of the waveforms, and not the set itself.

Other cases could be described, illustrating important design limitations in test equipment. Does this mean that the equipment is necessarily bad or useless? Not at all. *The technician's attention should, however, be called to the limitations of the instrument he is purchasing, or planning to purchase, if he is to employ it efficiently.* This is a point of ethics frequently overlooked by some test equipment manufacturers.

### Improper "Specs" Listing

Linked with this "oversight" is the provision of inaccurate or misleading "specs", as well as the omission of "embarrassing" characteristics that reflect no credit on the instrument.

An example of an inaccurate specification is the statement that the output of a signal generator is continuously variable between, say, 0 and 500 millivolts, whereas in actuality, the output of the instrument cannot be reduced to zero volts at all.

An instance of the misleading "spec" is a statement that voltmeter accuracy is within, say, 3% of full-scale deflection at one specified range. The actual percentage of error at the low section of the range may be very much greater, but many technicians are apt to overlook this.

What is obviously needed is some system of 1—Standardizing specifications and 2—Insuring adherence to these "specs." All "specs" needed for correctly evaluating the merits of an instrument should be presented, not merely some of the more favorable ones. And these "specs" should be accurate, not "doctored up" to meet the more favorable "specs" of a competitor.

When the test equipment manufacturers fill this tall order, they will, we feel, go a long way toward picking up more business from the serviceman.

# Tuning In the

**NEW 19-IN. COLOR TUBE, CBS 205**, is in mass production right now with output of about 40,000 expected this year. Capehart, CBS, Motorola, Westinghouse and others will use it in their sets. Motorola has already announced a color receiver using this crt for THIS FALL, to sell at \$895. "205" refers to number of square inches on the tube's viewing area.

**GROWING NUMBER OF WOULD-BE "experts"** calling in technicians to work on Hi-Fi gear bought by the former with the notion that assembly and set-up is a cinch. At present the high-fidelity sales market is suffering a seasonal lull, with component volume lagging. Some high-class stores are moving fair quantities of complete instruments, and are doing fairly well with custom work.

**TV SET SALES HAVE BEEN** holding up well, with dealers fighting hard for a share of the business. As a matter of fact, the market is much better than most expected it to be, but most of the sales are in low-end new models or "distressed" larger units offered at fantastically low prices. Competition in TV is terrific in all markets. . . . Radios are slow in many localities, though portables and clocks are moving fairly well. . . . Recorders are steady and are expected to show a big increase over last year. . . . Phonos have been moving in the low and medium price brackets, with large deluxe units dragging.

**THERE ARE STILL "SNOWY REGIONS"** in many parts of the country, but one hears less and less about "fringe areas" these days because of the great improvements in antennas, towers and other reception accessories, plus increased skill and knowledge on the part of the nation's technicians. Some repairers we know of travel fifty miles and more to service one fringe set. What's your record distance? Let's hear from you for publication in **TECHNICIAN**.


**STRANGER THAN FICTION.** In a hard-boiled district of New York City, a technician was called in to service a receiver. The customer claimed (over the phone) that it had never worked since it was fixed, and refused to pay for the repair. As the technician placed his tool kit inside the front door hall, the woman kicked the box farther inside the house and slammed the door in the technician's face. The case was subsequently settled in court to the woman's satisfaction. Hm. . . . Easterner who used to run a small radio repair shop, is now a big-shot engineer for a national network, but he still has to personally repair the TV sets, Hi-Fi equipment and other electronic gear in his boss' home. Seems the latter is so sold on the guy's ability that he won't let anyone but the ex-servicer do the work.

**BUSINESS SO-SO AS SUMMER CONTINUES**, though a sharp pickup is foreseen in September when the trek back from vacationland commences. Repair shops in many thickly-populated Summer resorts have been very busy, but conditions have been spotty in most of the big cities, with heavy competition in such cities as New York and Chicago, where some high-pressure outfits are spending up to \$500 a week in advertising. Prices for service are holding up well in most independent shops. Trend noticed in some of the older TV cities: An increase in number of folk who are seeking "minimum" repairs, and who are unwilling to spend money for other needed work in cases where picture and sound are still present.

**TRENDS OF THE TIMES:** Numbers of discount-houses setting up service departments to counteract competitive claims that such outfits have no maintenance or installation facilities to offer. . . . Slight increase in number of firms advertising service on time-payment bases. . . . Large 24-hour, seven-days-a-week firm doing 60 percent of its volume on holidays and "after hours." . . . Most shop owners interviewed by **TECHNICIAN** editors say they do not plan to charge more for working on color-TV sets when the latter really hit the home market.

**PORTABLE RADIO SALES** are sharply up for the 1st quarter of this year as compared to a similar period last year. Though the trend is nationwide, heaviest demand is in northeast area of the country. New England technicians, please note! Don't overlook a good bet.

**TV MEMORY MIRROR:** Remember the pre-age split-sound sets, many still in use, that required at least half-a-dozen knob adjustments when switched from one channel to another? Contrast, fine tuning, horizontal hold, brightness and other controls had to be carefully adjusted each time. Not a hard job, if you happened to be an octopus. . . . And how about those clumsy magnifiers, oil-filled and others, that used to mar the appearance of 7- and 10-in. sets to produce a bigger picture? Remember the time, in the not-too-distant past, when conversions to a larger pix tube were a good source of income? Plummeting prices on large-screen sets have just about killed this sideline.

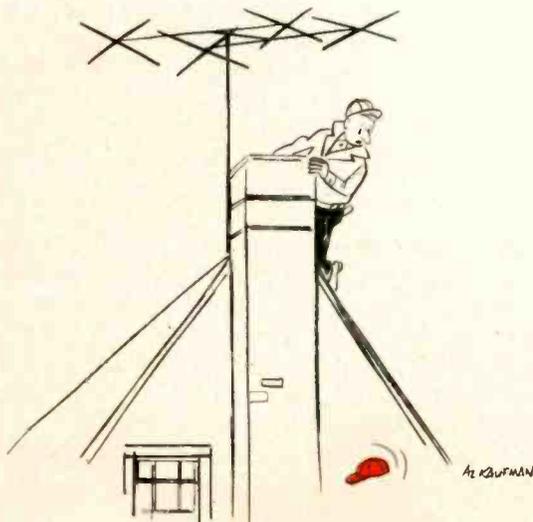

"Gesundheit!"

# Picture .....



"Think it over—my repairs free or—kerplow!"

**COLOR-TV IS CERTAINLY ON THE WAY**, according to RCA Victor's former exec. VP, Jos. B. Elliott. He says the industry should be able to sell several hundred thousand sets in 1955; about one and three-quarter million in '56, and five million in '58.

**INCREASE IN BOTCHED UP SETS** repaired by would-be servicers in the home noted in several industrial centers. Although most technicians dislike working on these "worked-over" receivers, and many express their displeasure to the owners, one Chicago firm accepts such repairs with a smile. "If we're willing to take this kind of work we might as well be courteous about it," says the owner.

**OPPORTUNITIES MANY OVERLOOK.** Just about every customer needs phono needles, and just about every technician who visits the home can sell 'em—and make money, too. . . . "Are all your radios working satisfactorily?" is the stock question the owner of a small shop and his two men ask each time a TV repair call is made. And it pays off handsomely. . . . A New York technician, servicing a television set in a doctor's office was asked by the latter if he could repair a piece of electronic medical equipment. He tackled the job, put the unit back into good working condition, and now has several other doctors on his customer list.

**TV MANUFACTURERS' WARRANTIES** are moving in two directions at the same time. Some mfrs are in favor of dropping 1-yr. warranties on pix tubes, claiming that present crt prices and quality are so favorable that these items no longer represent a big-cost replacement headache. On the other hand, GE has just extended its standard 90-day warranty on TV sets to cover labor charges, as well as parts replacement.

**GARAGE-DOOR OPENER**, recently introduced, will be marketed via TV-radio distribution channels. Even if you don't do selling, this kind of item can be a good "added line" for servicing.

**THE JOB-SECURITY FACTOR** should improve steadily. To judge by current population trends, the deck will be stacked in the worker's favor by 1963. In an anticipated (increased) population of 177 million, there will be a big percentage increase in the over- and under-age groups, leaving fewer workers in "acceptable" age brackets to furnish goods and services for more people.

**TAPE DUPLICATING SYSTEM**, announced by Ampex, will give still another shot in the arm to the growing field of pre-recorded tapes. By copying tapes at speeds several times normal playback speed, 2500 hours of tape playing time can be duplicated in a single 8-hr. working day. This includes simultaneous copying of both tracks on a dual-track recording. On modern stamping presses, disc recordings are usually produced at a rate of less than 1500 hours of music per 8-hr. day.

**BIGGEST BOTTLENECK IN COLOR TV** may not be the size of the crt so much as the non-interchangeability of pix tube types already developed. Most set makers are afraid to sink big dough into a circuit design that may become obsolete if the crt used in it is eventually abandoned. Sufficient standardization to allow interchangeability of tube types is one answer. Is this a problem for another "all-industry" committee? Technician-dealers and distributors also have a stake in this problem: Who has the warehouse space—or the money—to stock replacements for at least half a dozen varieties of crt?

**LOOKING FOR WORK?** Makers of master antenna systems, which are doing well, report a shortage of trained personnel for installing and maintaining these rigs. Also, Jerrold of Philadelphia announces a new licensing plan for people interested in selling or installing their master systems. The same mfr is setting up a school in Philadelphia, open to the entire industry, for training personnel in installation, maintenance and operation techniques.

**THOUGH A FEW TV SET MAKERS** have said off the record that they may revise a few receiver prices upward this Fall, most are looking forward to a knock-down-drag-out fight to the finish with leader models. "Price-wise, we haven't seen anything yet," a prominent sales executive told a **TECHNICIAN** editor.

## CALENDAR OF COMING EVENTS

- Aug. 25-27: Western Electronic Show & Convention, Pan-Pacific Auditorium, Los Angeles (show) Ambassador Hotel, Los Angeles (convention hq.)
- Aug. 27-29: TV Service Clinic, Sponsored by the Texas Electronics Association, Adolphus Hotel, Dallas, Texas
- Sept. 24-26: Fifth Annual TV-Radio Service Industry Convention and Exhibitions, Morrison Hotel, Chicago, Ill.
- Sept. 30-Oct. 2: High Fidelity Show, Washington Athletic Club, International Sight and Sound Exposition, Palmer House, Chicago, Ill.
- Oct. 4-6: Tenth Annual National Electronics Conference, Hotel Sherman, Chicago, Ill.
- Oct. 8-20: Radio-Electronics-Television Mfrs. Assoc. Radio Fall Meeting, Hotel Syracuse, Syracuse, N.Y.
- Oct. 13-16: The Audio Fair, Sponsored by Audio Engineering Society, Hotel New Yorker, New York.


# Using the Oscilloscope

## Scope Requirements; Eliminating Stray Pickup; Non-Linearity;

• In the performance of routine TV service operations, such as waveform inspection and alignment, a reasonably good oscilloscope is a "must" requirement. Economically, many readers cannot afford the best, so this article will discuss measures by means of which an inexpensive scope's usefulness may be extended (until a really good scope can be procured). Auxiliary equipment that may be used for this purpose will also be described.

**Response Needed.** Probably the most critical duty of a scope is the display of waveforms associated with the horizontal frequency of 15,750 cycles per second. Contrary

Fig. 1—Distortion of horizontal sync pulse on a laboratory scope (A); on an inexpensive scope (B); excessive distortion on inexpensive scope due to loss of high frequencies (C).

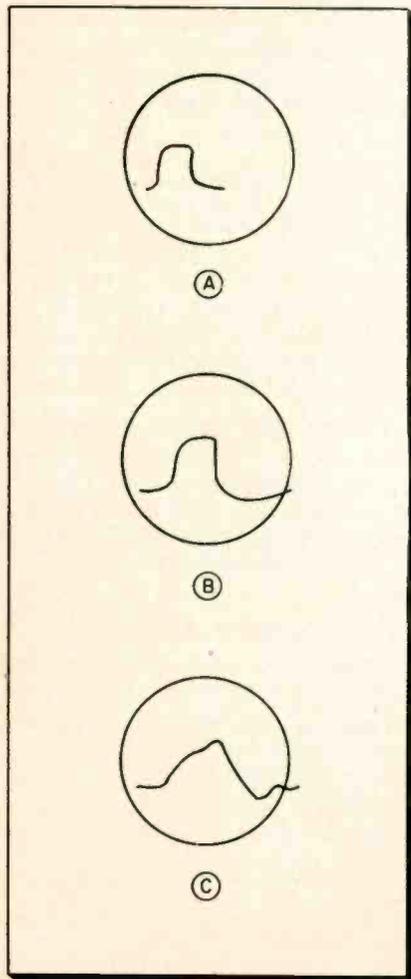

BY JAMES A. McROBERTS

to the general run of opinion, the vertical amplifier must be faithful far beyond the tenth harmonic of this frequency, if small portions of a single cycle—such as the retrace of a horizontal pulse—are to be accurately displayed. Ideally, the vertical amplifier should pass, without discrimination, frequencies 500 times as high as the horizontal sync pulse. Scopes of such a high-frequency response are, of course, prohibitive in price for the average technician, and not really needed for ordinary service work. A hundred times the horizontal frequency is a more practical requirement—i.e., a response extending to 1.5 or 2.0 megacycles.

Inexpensive scopes with a "usable" high-frequency response of only 150 kc may be employed. One very simple way to get the most out of such a scope is to note carefully how it reproduces horizontal waveforms on some TV receiver in good operating condition. Take particular note of—i.e., memorize—the distortion present, so you will know how much distortion is normal with a scope of this kind.

To illustrate: a horizontal sync pulse observed on an excellent scope is shown in Fig. 1A; its appearance on an inexpensive scope is illustrated in 1B. If a waveform seen on the inexpensive scope is ex-

cessively distorted (Fig. 1C), trouble in the receiver is indicated.


**Eliminating Stray Pickup.** Stray pickup by the vertical amplifier and its leads are perhaps the most annoying things that the serviceman encounters in a scope. He can readily do something about such pickup. The input circuit to the vertical amplifier should be shielded inside the scope. A microphone connector may be substituted for the customary binding post input. A microphone cable (Fig. 2) may be used as a shielded input lead; the input is thus shielded as far as the end of the microphone cable. Another length of microphone cable, complete with connectors, is handy as a spare or as an extension.

Probes—discussed later—may be terminated in a connector to match the cable, thus shielding the entire input system as far as possible.

Shielding of the vertical amplifier and the input cables not only prevents stray pickup (such as hum); it also prevents radiation of the signal on the cable to other parts of the receiver under test. Such radiation can cause regeneration and/or spurious modulation.

**Scope Non-Linearity.** The horizontal sweep may not be linear in inexpensive scopes. This non-linearity may be of the kind illustrated in Fig. 3A, which occurs towards the end of the sweep. The resultant dis-

Fig. 2—Single-contact microphone cable, with connector for coaxial (shielded) input, may be used for attaching scope vertical input to circuit under test. Set-up eliminates hum pickup.

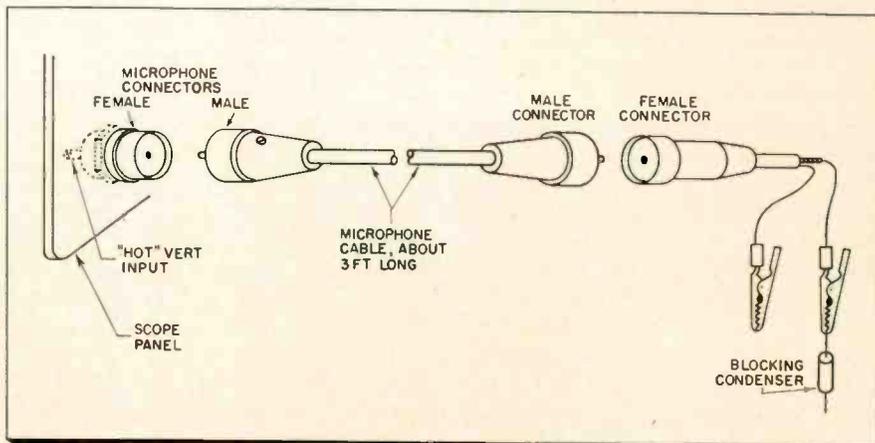

# for TV Receiver Servicing

## Isolation & Filtering; Low-Capacitance and Detector Probes

ortion produced in a sine-wave signal is shown in Fig. 3B. Now, ordinarily, two or more waveform cycles are observed simultaneously. To remove the non-linear part of the display, simply expand the sweep by suitable rotation of the horizontal gain control; then move the right-hand cycle entirely off the screen by setting the horizontal positioning control so that only the one or two cycles at the left are visible. Fig. 4 shows such a display with the "unused" portion dotted.

In alignment operations, the non-linearity just described is not too important. The technician should look at alignment curves obtained on several sets in good working order, to familiarize himself with the response distortion introduced by his scope.

**Filters and Isolation Resistors.** Shielding the leads is not all that is required to make the input to the scope vertical amplifier satisfactory. Filter networks are also needed, to prevent upsetting the circuit under test, and to provide a more usable response curve in alignment. Intelligent use of filters is very important in oscilloscope work.

Alignment curves are frequently fuzzy and hazy, due to the presence of excessive high-frequency signal content, where only the relatively low frequencies are required. A high-pass filter can change a fuzzy curve (Fig. 5A) into a cleaner, far more usable one (Fig. 5B). The simple addition of a 0.001 to 0.01 mfd condenser across the scope vertical input terminals is enough for this magic transformation, although a more elaborate filter is preferable. (The more elaborate filter will do a better job of removing higher-frequency audio components as well as radio-frequency signals, from a sweep-generated response curve. Only 60 or 120 cycle components and their first ten harmonics are needed, for correct reproduction of the response curve.)

Fig. 5C shows the schematic of such a filter. R-1, a 10k resistor, isolates the scope from the circuit under test; 500 mmfd condenser C-1 serves as an r-f bypass. Fur-

ther r-f filtration is provided by R-2, another 10k resistor. C-2's primary function is to bypass the higher audio (noise) frequencies, eliminating the fuzz that tends to develop in the alignment curve when the set is brought into alignment. C-2 has a value of 0.05 mfd in many such applications.

The entire filter should, preferably, be mounted in an i-f transformer can, with a female microphone connector (panel-mount) provided on the end of the can, to match the coaxial microphone input cable shown in Fig. 2. The lead length extending from isolation resistor R-1 beyond the shielding enclosure should be minimum.

**Low-Capacitance Probes.** An isolation resistor tends to prevent interaction of the scope vertical input with the circuit under test (i.e., loading or detuning). Interaction is further minimized by use of a low-capacitance probe. A typical low C probe is schematically illustrated in Fig. 6. Note that a series-connected low capacitance is capable of reducing the capacitive loading of a tuned circuit by the probe. The 47 mmfd capacitor in Fig. 6 is in series with the capacitance of the probe; the series combination represents the capacitive load shunting the circuit under test. The 47 mmfd series condenser also prevents or blocks the passage of direct current. (Although most scopes have a series blocking condenser, addition of another one prevents damage that may be caused by a short-circuit at the terminals of the scope binding post.)

Use low-capacitance probes for viewing the waveforms in horizontal oscillator and discriminator-ratio detector circuits, where the capacitance of the probe leads will upset the circuit if a larger-capacitance probe is employed. A resistor (1 or 2K) may be used in series with the end of the probe, if desired, to further isolate the circuits and reduce the shunting capacitance present.

**Detector Probes.** To view the modulation of radio or intermedi-  
(Continued on page 58)

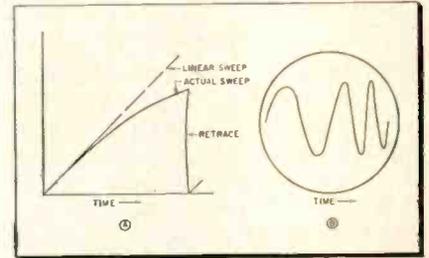


Fig. 3A—Non-linear sweep. B—Effect of non-linearity shown in (A) on a sine-wave signal.


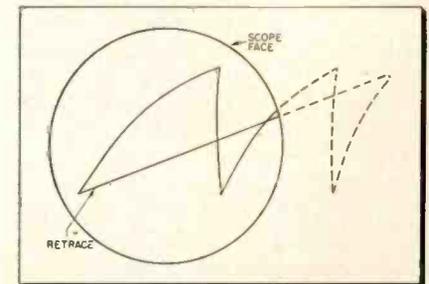


Fig. 4—Display adjusted so that only the left-hand or most linear part of the signal is left on the screen for inspection purposes.

Fig. 5A—Fuzzy response curve. C—Filter designed to remove the fuzz shown in (A). B—Response curve with fuzz content eliminated.

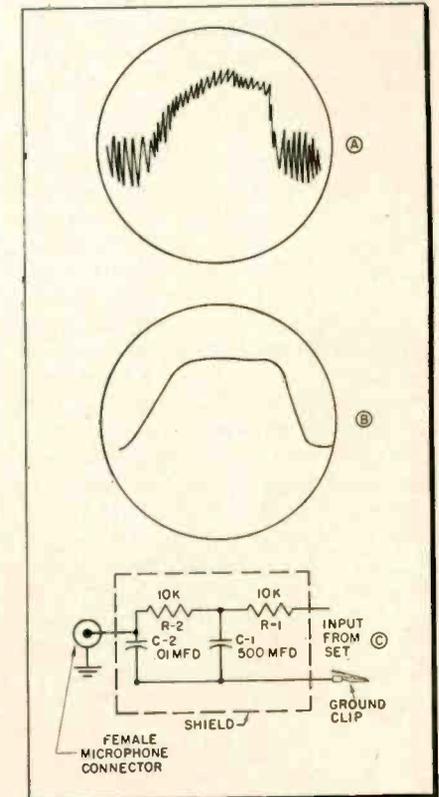

# Setting Up A Successful

## Factors Entering into an Indoor or Outdoor Installation.

BY ARTHUR H. SMITH

• The successful outcome of a well planned, properly installed public address system is gratifying to both the purchaser and the technician. Some installations, however, do not turn out successfully. Unusual conditions may arise—in some cases weeks after an installation is completed, in others as the system is in the process of being set up—that impair its operation.

A great deal of troubleshooting, replacement and re-arrangement can be avoided if certain basic installation fundamentals, about to be described, are observed.

Public address systems vary greatly in requirements, ranging as they do from small units, intended for audiences in quiet rooms or auditoriums, to large complex installations at stadiums, theaters or racetracks, where the public address system is required to have sufficient reserve power to override the noise levels that exist at these sites. Other installations include paging and music amplifiers at industrial plants, schools, hospitals, bus depots, restaurants and night clubs.

In some installations, fixed requirements must be met; i.e., the audience and activity are about the same at all times. Other installations may have varying requirements during the day or evening, due to fluctuations in the number of listeners, changes in surrounding noise levels, and other variables.

The success or failure of your system depends on satisfying these varying requirements adequately. The technician who fails the first time in an installation of this type may fail again, unless he is equipped with basic installation information.


When called upon to install a public address system, your first logical step would be to go to the location where the installation is to be made. Look the place over yourself. Do not depend on descriptions of the place. Spend as much time as you can asking questions, the an-

*Arthur Smith is a design engineer who operated a p.a. business for ten years.*

Amplifier Power	Speakers Needed for Indoor Installation	Speakers Needed for Outdoor Installation
6 to 8 w	Two 8-in. speakers	One 12-in. speaker
15 to 18 w	Two 12-in. speakers	One trumpet
25 to 30 w	Four 12-in. speakers	Two trumpets
45 to 50 w	Six 12-in. speakers	Three trumpets
60 to 70 w	Eight 12-in. speakers	Four trumpets

Fig. 1—Number and size of speakers required with an amplifier of specified power output.

Fig. 2—Placement of four speakers in oblong room, for most effective use of the dispersion angle.

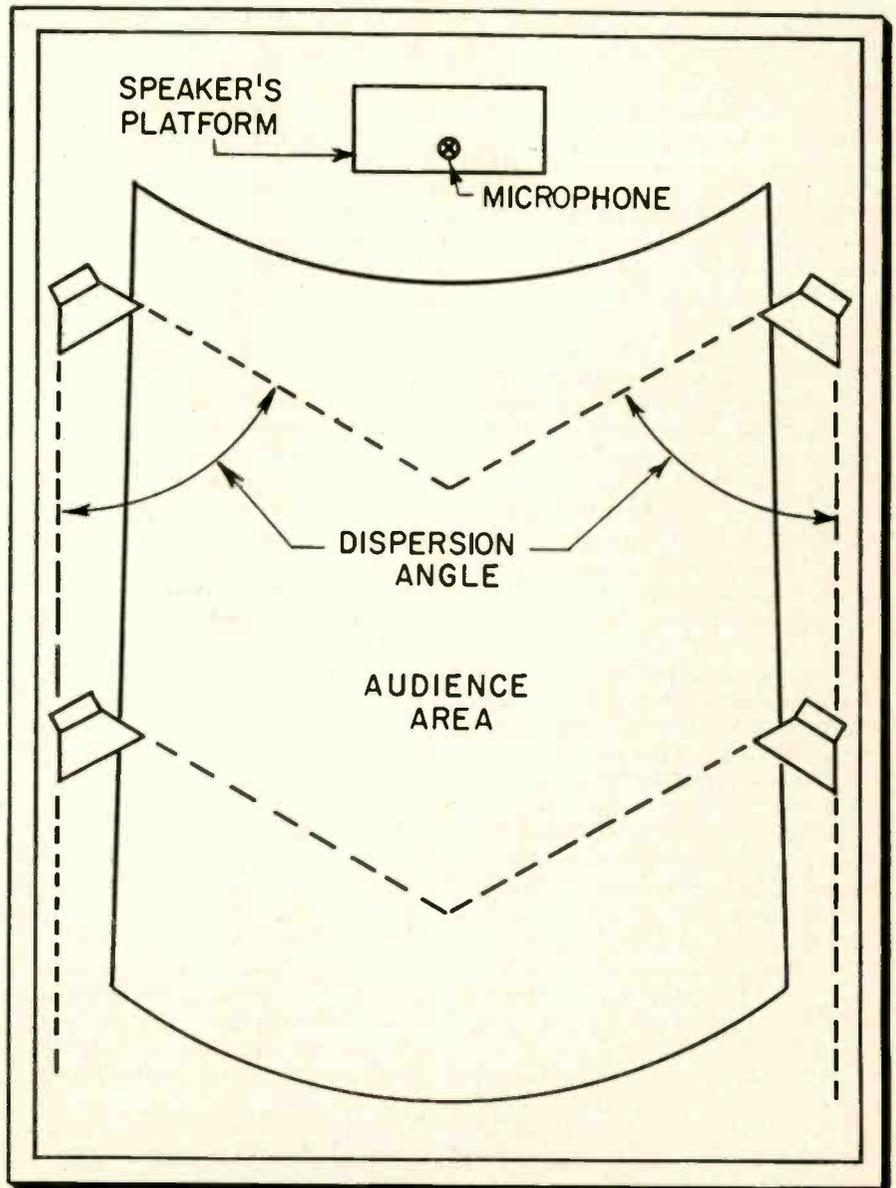

# Public Address Sound System

## Meeting Requirements. Speaker Considerations

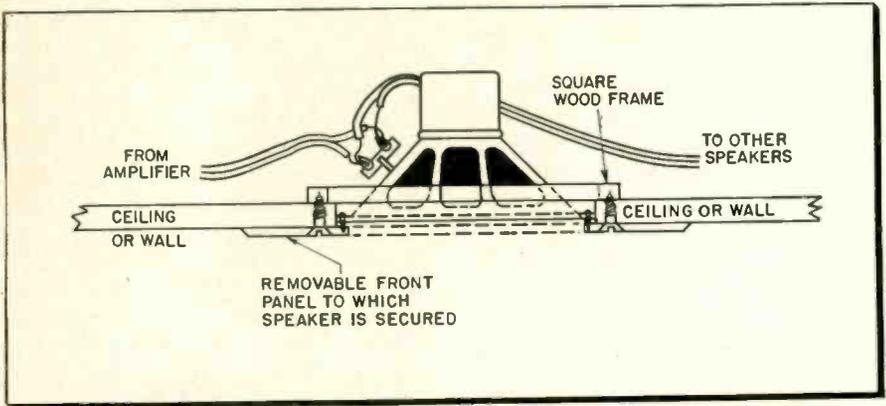


Fig. 3—Method of connecting ceiling or wall speakers to permit access to speakers and cables.

swers to which may be needed. Whatever the case may be, determine whether the requirements will be the same during the use of the system, or if they will vary.

Public address installations may be divided into indoor and outdoor systems. An indoor system, once established, can be relied upon to distribute sound faithfully under all conditions for which it was designed. The outdoor system, however, cannot be set up and forgotten about quite so easily.

Because of the usual absence of walls, ceilings and floors in an outdoor installation, sound distribution is dependent wholly upon the air mass that surrounds the audience. The lack of reflecting surfaces prevents re-distribution of the sound, which is literally lost to infinity due to the excessive damping effect of air in open space. Prevailing winds may carry the amplified sounds to or away from the audience, little or no control being possible. To cope with such conditions, at least in part, something of a brute-force technique, employing highly-directive trumpets, is used.

The following formula is based on indoor factory installations, which require adequate reserve power to override peak production noise. This formula is applicable to all other types of installation, since it provides for a good margin of reserve power. Multiply the number of people to be served by a constant index of .008, to obtain the amplifier power required.

Example:  $4000 \times .008 = 32$  watts. In the case of a comparable outdoor installation, 10 watts should be added to the power requirement.

Now that the proper amount of power has been determined, the next consideration will be the number and types of speakers or trumpets to be employed. The table shown in Fig. 1 may be used in this connection. Good-quality twelve-inch speakers, with adequate handling capacities of fifteen to twenty-five watts, and trumpets using 25-watt driver units, are ideal for the installations referred to.

We have now determined the power required, and the number and types of speakers. The next consideration is speaker placement. You will want to achieve maximum sound coverage by utilizing efficiently the speakers available.

In a square or oblong room having straight walls, speakers should be mounted 10 to 12 feet from the floor. When a seated audience is anticipated, speakers should face the audience at a 45-degree angle from the wall. This will make the most effective use of the dispersion angle of the speakers (see Fig. 2).


Where the audience is expected to move about, two kinds of speaker placement can be used. The speakers can be placed flat against the wall, so that they radiate energy at an angle of 45 degrees from the wall. The speakers can also be placed in the corners of the room. The dispersion angle is more effectively used in the latter case. If the

room is oblong, two or more speakers may be required to fill in possible dead spots along the long wall. The best type of placement is that in which the speakers are concealed in walls and ceilings. This will be discussed shortly.

Rooms of other than square or oblong construction may pose some problems. Alcoves, dividing walls, booths, balconies and side rooms should not generally be served by speakers in the main-room area. It may be advisable or necessary to use two eight-inch speakers in place of one twelve-inch unit, installing the two in obvious or possible dead spots. It is advisable to install suitable pads in such speakers, in order that a balanced level can be maintained, in relation to the sound level in the main room.

In permanent installations, when

Fig. 4—Ceiling support channel. The heavy-gauge steel unit shown comes in 24 and 48-in. spans. (Courtesy Lowell Mfg. Co.)

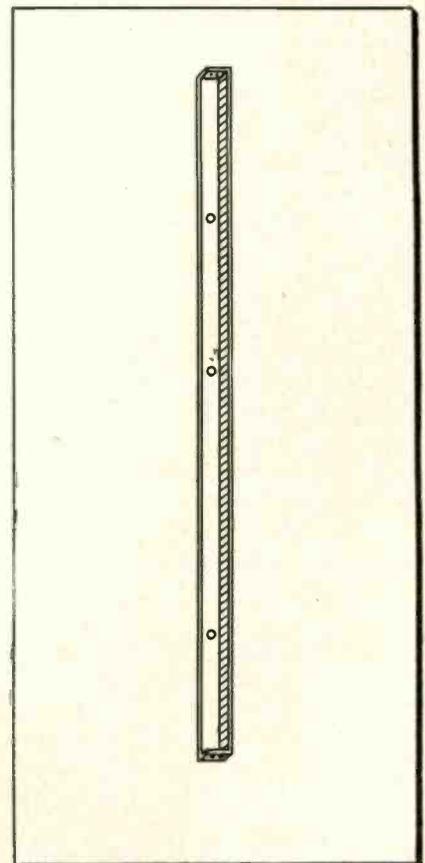

it is architecturally possible, or in new room construction, speakers may be installed recessed into the ceiling or wall. Access to the speakers and connecting cables should be provided by the use of mounting rings or plates, in the event future servicing is needed. Also provide accessible tie points for the cables between speakers, in order that continuity and resistance checks may readily be made. In the event of shorted or open cables, new cables can be pulled through by means of the old cable.

Removable ceiling or wall panels can be made up as shown in Fig. 3. Such panels will make speakers and cables in permanent installations accessible.

Steel support channels may be used for ceiling or wall installations (see Fig. 4). The channels used by the author come in either 24 or 48-in. lengths, and are made to conform to standard construction

specifications (refer to Fig. 5).

In installations where requirements vary, and speakers may need to be moved to different positions from time to time, speakers mounted in wood cabinet baffles should prove satisfactory. The cables in this case may be laid in mouldings, or supported by means of slip rings spaced about the room, or securely strapped or stapled to the walls.

The outdoor installation usually uses trumpets which have a dispersion angle of 90 degrees. Position these trumpets as judiciously as possible, to make optimum use of the dispersion angle. Two trumpets are usually mounted near the speakers' or musicians' platform, while others are set up in trees, on poles or on suitable tripods, to cover the remaining area.

Up to this point, we have decided on the power requirement of the amplifier, and installed the speakers

and cables. The next consideration will be the quality and input requirements of the system. For ordinary speech, ballyhoo and carnival service, an ordinary amplifier with no special features may be chosen. Where the system calls for music distribution or orchestral service, however, a good quality amplifier with several input channels should be selected. Good frequency response down to 15 cycles and up to and above 15,000 cycles, with low distortion, is mandatory.

Amplifiers with tone correctors and controlled feedback circuits will make it possible for you to make corrections in the acoustics, and counteract the effect of resonance points that may exist in the room in which the system is used. No matter what the installation, before you decide to purchase the amplifier, set up and review specifications and ratings. Make sure that the service for which you intend using the equipment is suited to it.

The amplifier should be equipped with good-quality, oversized components (preferably oil-filled condensers), and should have adequate ventilation. In many cases, public address systems are very much abused. They are put to long periods of operation at full power output. Failures have frequently been attributed to systems accidentally being left on overnight, or for the duration of a week-end. Ruggedness of the amplifier is therefore important.


Input requirements dictate the quality of the microphone and other accessories. These units should match amplifier "specs." Choose a mike cable that will be adequate for all possible needs. It is customary to provide several cables of 10, 25 and 50-foot lengths, with suitable connectors to join all cables if necessary.

### Speaker Considerations

In connecting your speakers together, consideration must be given to impedance matching and phase relations. It is most advisable to install speakers in parallel or series-parallel. A large group of speakers should never be wired in series. Due to high transient voltages that may develop in a series wiring set-up, arc-over at the air gap of the voice coils may occur, possibly causing serious damage to the speakers. Furthermore, if a coil open-circuits, the entire system will be inoperative. If for some reason series operation must be used, the speaker

(Continued on page 48)

Fig. 5—How steel support channels for sound systems are used in various types of ceiling. Units shown were designed for special kinds of speaker enclosures. (Courtesy Lowell Mfg. Co.)

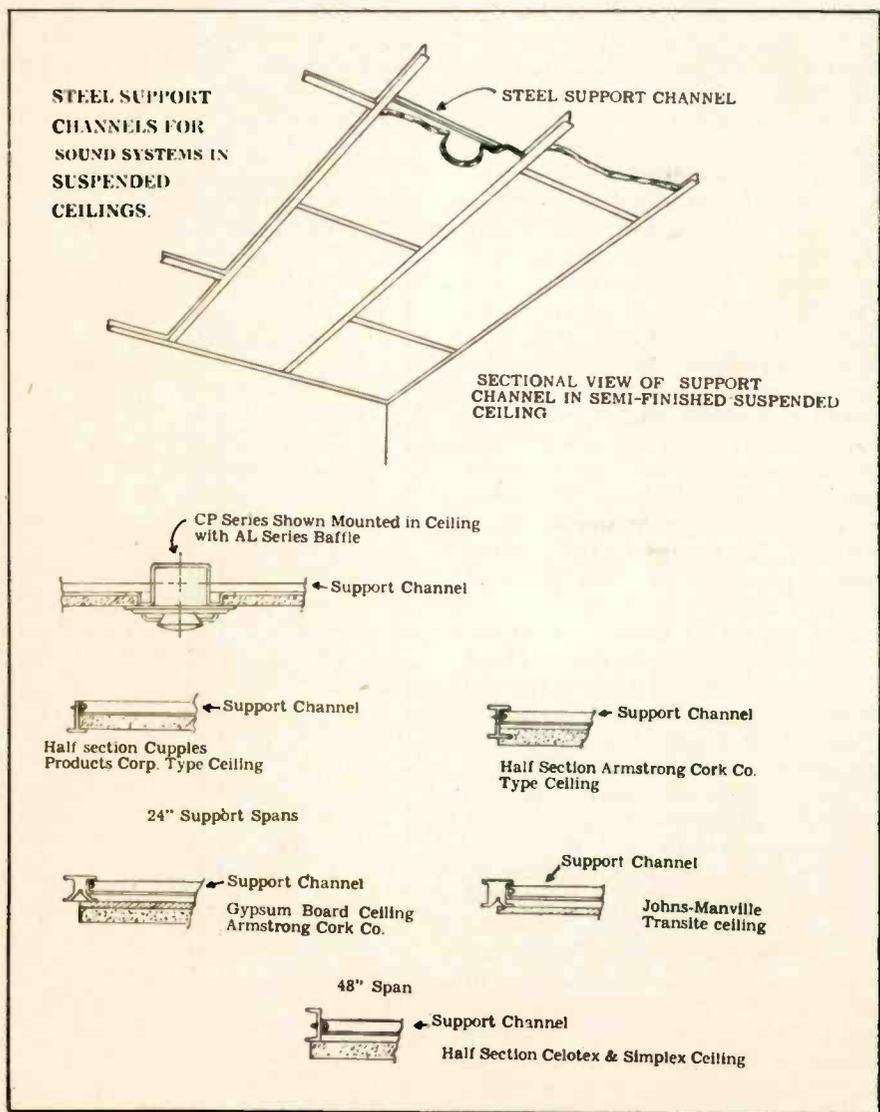

## Making the Most of

# Your Test Equipment

## Adjusting Oscillator Padders with a Sweep Generator and Scope; Calibrating a Signal Generator; Enlarger for 3-in. Scope

By MAURY GOLDBERG

**Adjusting Oscillator Padders.** Due to cost considerations, low-priced receivers seldom contain series oscillator padders for tracking at the low-frequency end of the dial. Because of the relative broadness of response of the single-tuned circuit between the antenna and the mixer grid (usually the loop itself), minor discrepancies in the tracking of the oscillator and mixer tuned circuits can usually be tolerated. Only a low-capacity shunt trimmer, ordinarily mounted on the tuning gang, is used to track the circuit at the high-frequency end of the dial.

In better-grade communication sets, home receivers and Hi-Fi tuners, some form of series padder is usually incorporated to give closer tracking at the low-frequency end of the band. Some receivers dispense with the capacitor padder shown in Fig. 1A and use a pow-

dered iron slug instead, as shown in Fig. 1B. In the usual adjustment of a padder or slug, a station—say around 600 kc on the broadcast band—is tuned in; the dial is then “rocked,” while various settings of the slug, or padder capacitor, whichever is used, are made. The adjustment position providing maximum response is assumed to be the correct one; after it is obtained, the shunt trimmer is adjusted near the high-frequency end of the dial. The same procedure is then repeated as a re-check.

This is a relatively slow and somewhat unsatisfactory process, and can be speeded up and improved upon by using the following procedure: Clip the output lead from a sweep generator to the insulation on the “high” side of the antenna or loop wiring (see Fig. 2A). The input cable from a scope is then connected across the set's detector load resistor. With a center sweep frequency of about 600 kc, and a sweep width of .5 mc or less, a pattern such as the one shown in Fig. 2B will be observed. The receiver dial is set at a point near 600 kc, at which no station is received, for this test. It is immaterial whether the scope's internal horizontal sweep or the sweep from the generator is used, since the height indication alone is of interest, not the exact shape of the response curve.

The padder or slug is adjusted for maximum curve height. The response curve will slide to right or left along the baseline during the process, showing that the frequency of the tuned circuit is being varied. The small pip near the main response is the 455 kc i-f signal. Advantage can be taken of its presence by adjusting the i-f trimmers for maximum pip output at this time. If the main response curve is off to one side of the screen, adjust the


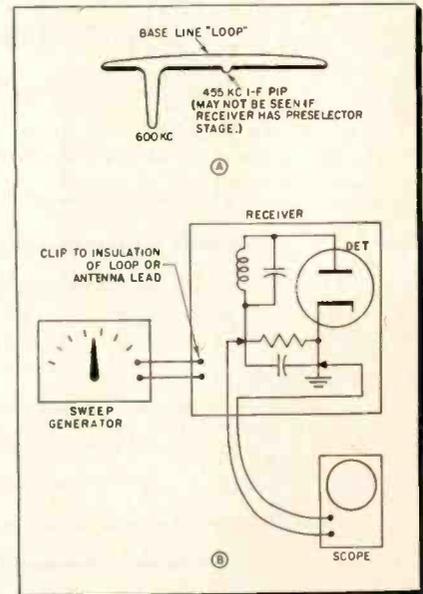


Fig. 2A—Connection of sweep generator and oscilloscope for oscillator alignment at the low-frequency end of the band. B—Response obtained on scope. To minimize “looping” of the base line, reverse line plug to the sweep generator, scope or the radio.

phasing control on the generator, or reset the center frequency slightly, to bring the curve closer towards the center of the screen.


The method of adjustment just described is of value even when no series padder or slug adjustment is incorporated in the circuit. By pressing against one of the outer oscillator section rotor plates with an insulated rod, the height of the pattern will change. The same is true if one of the rotor plates of the mixer section is pressed inward slightly. If the output *decreases* in BOTH cases, the adjustment is correct as is. If the output *increases* when the oscillator rotor plate is pressed, bend the MIXER rotor plate *outward* slightly, until proper correction is obtained. If the output *increases* when the mixer plate is pressed, bend the OSCILLATOR plate *outward* to compensate.

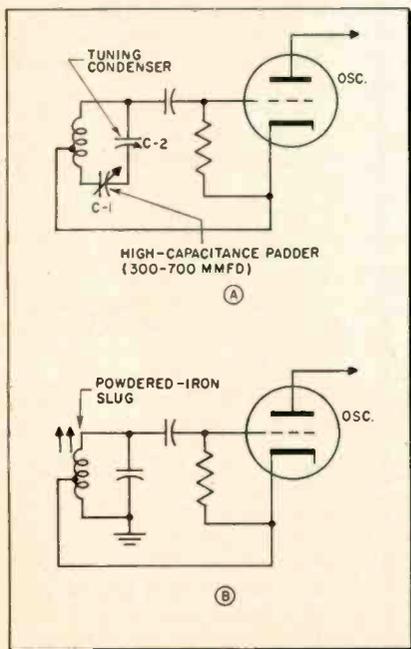This method is just the opposite (Continued on page 56)


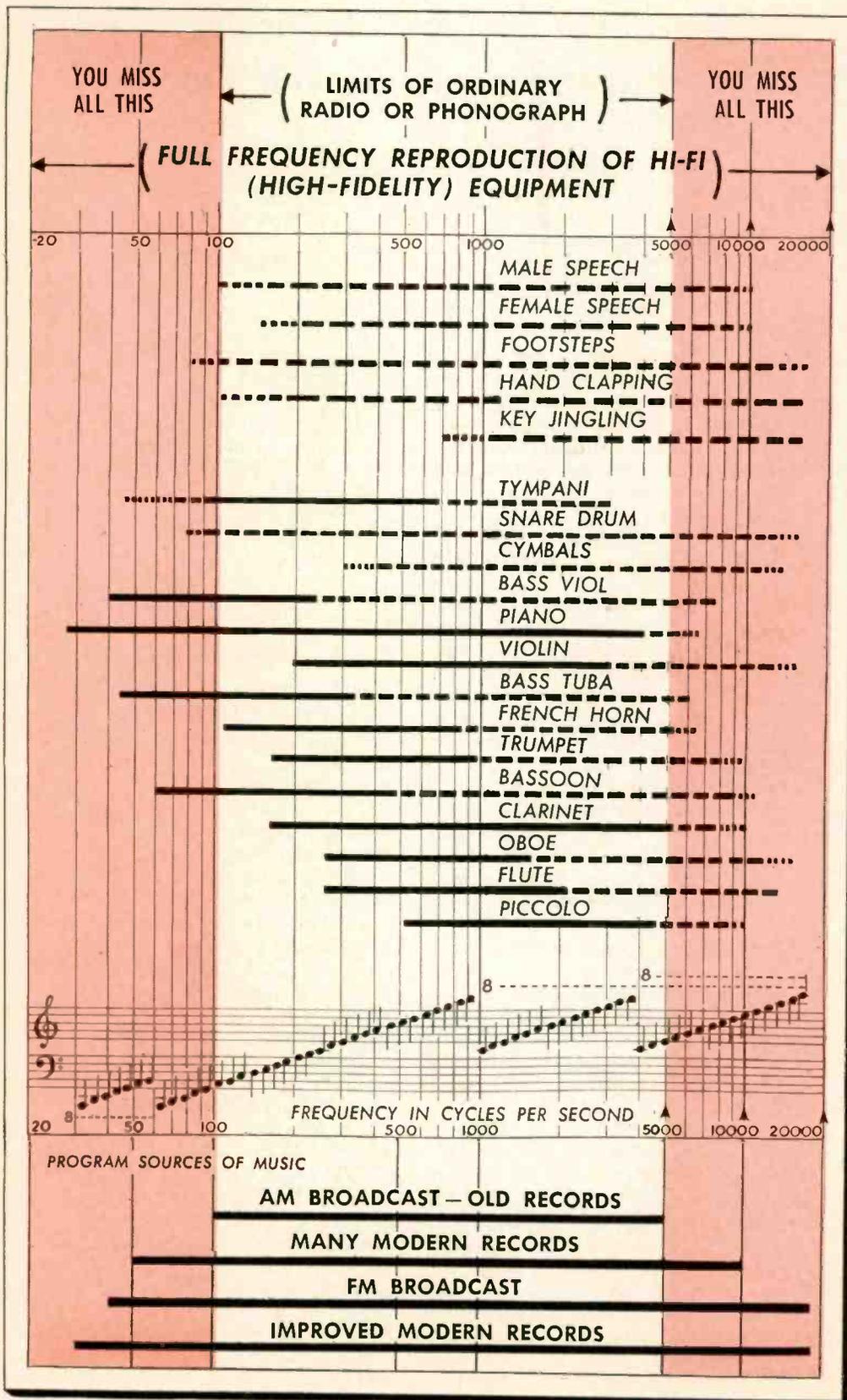
# WHY You Need "HIGH FIDELITY"

To Enjoy the Full Value of Great Music and Fine Instruments



HIGH FIDELITY, in broad terms, refers to the re-creation of sound so that it resembles closely the original expression of that sound.

In the technical sense, many factors contribute to this life-like realism. One of the most important of these is the range of frequencies that is faithfully reproduced. The chart at the left shows that some musical instruments can produce tones lower than 30 CPS. The piano's lowest A vibrates to 27.5 CPS. Other instruments, like the organ, extend even lower than this.

At the high end of the frequency scale, the hearing varies from person to person. For many people, this limit goes beyond 15,000 CPS. We should note that, aside from harmonics, 5,000 CPS is about the highest fundamental tone an instrument can produce.

Now, no instrument produces a "pure" tone, which is uninteresting. Distinctive instrumental color lies in the harmonics, or overtones. These help make the piano sound like a piano, the trumpet sound like a trumpet. (Each instrument's range of fundamentals is shown as a solid line on the graph; the broken-line extensions indicate harmonics.)

As shown toward the bottom of the chart, old-type 78 RPM records and AM broadcasts rarely exceeded 5,000 CPS. When they did, accompanying background noise in the upper frequencies masked high-frequency musical sounds. Hi Fi reproducers, which faithfully recreated noise and distortion, did not find favor when they first appeared on the market. In fact, response was often limited deliberately to eliminate noise.

In the years after World War II, a rapid sequence of developments changed the listening climate. The advent of fine-groove plastic records, the opening of the present FM band and the refinement of magnetic recorders made possible source materials that were wide in range but low in noise and distortion. Some of these sources are indicated at the bottom of the chart.

Today, the limited range of the conventional radio or phonograph, shown at the top, is not acceptable to the Hi Fi lover. Room-filling deep tones cannot be "felt." The tinkle of the triangle, the in-the-room crash of the cymbals and the brilliance of the violins come through as a combination of muddy sounds. But a high-fidelity system brings all these living sounds into the home with their original clarity and color.

# YOU Can Sell Hi-Fi

## There's Room for the Small Dealer in this Growing Field

Interest in Hi-Fi is growing steadily. More and more people in all parts of the country are purchasing record-players, tape-recorders, FM tuners and related equipment that has the Hi-Fi ticket on it. There's gold in them thar hills, but you've got to know how to mine it.

The first job that should be performed if you're going to sell Hi-Fi to the public is to fan the latent interest of potential customers to sales temperature. Many people who have heard about Hi-Fi, and have developed some degree of interest in it, can have that interest stimulated to the point where it leads to a purchase. Here are some of the ways you can go about achieving this desirable result:

*Get up an effective window display.* For instance, obtain an old phono somewhere—the kind that is readily identified as old—and set it up beside a late-model record player. A small sign in front of each unit can give the frequency response of the machine, and list other characteristics that make for interesting comparisons. The language used should, of course, be as non-technical as possible.

You might, on another placard, state that records will be played on each machine at such-and-such an

hour in the evening, giving listeners a chance to hear how much progress has been achieved in the field of record reproduction.

Demonstration and test records of various types might also be played on both machines, and the response in each case made visible to the audience on a scope. One of the better orators in the shop could handle whatever spiel is necessary.

*Literature can be made available in the store,* acquainting people with what Hi-Fi is all about. You don't have to write this stuff yourself. Plenty of Hi-Fi manufacturers have brochures available that are beamed at the layman. You can cut out portions of these booklets that you think do a good job, get permission to reproduce and distribute them under your store's imprint, adding a short sales message at the end, if you wish.

If you aren't shy, you might tell lodge secretaries and officials of similar organizations that you would be willing to deliver a talk on Hi-Fi to their membership. By delivering several such lectures, you can build up quite a reputation as a Hi-Fi expert, and profit from the business that results.

All of the preceding presupposes that you have acquired a good fundamental background on Hi-Fi, and have really made yourself an expert.

One of the fundamental problems the technician-dealer entering this field faces is the problem of how to meet the competition of cut-rate

houses that sell at or near wholesale to both technicians and laymen. Meeting the prices of these houses is, of course, out of the question for the small independent. What he can do however, is offer customers something the cut-rate house cannot readily duplicate, i.e., a sincere interest in the customer's problems; simple, intelligible, accurate answers to questions posed by the customer; honesty about merchandise offered for sale; and last, but certainly not least, good service, within or outside the guaranty period.

Many customers don't know enough to buy intelligently from the cut-rate houses; they need guidance, and will pay your price if you can give it to them. Hi-Fi customers are basically more interested in quality than in price. If you can lead them by the hand through the claims and counter-claims that are currently befuddling the field, and steer them to a really good instrument or custom installation, your selling job will be made much simpler.

It will pay you to educate customers or potential customers with respect to acceptable hum level, distortion, frequency response, etc. Demonstrations to small groups of potential customers, audibly illustrating these characteristics, should prove very effective.

There's room for the independent technician-dealer on the Hi-Fi bandwagon . . . but he must "know his stuff" . . . and he'll have to educate his customers. . . .

### Webster INTERCOMS

The RF and WC Com-ette intercom systems are designed for low-cost installation. The RF Com-ette series is designed to work on ac or dc and requires no interconnecting wires between units. The WC series is a wired system, also operates on 115-volt ac or dc, and includes 50 feet of interstation wire. Sound Sales Div., Webster Electric Co., 1900 Clark St., Racine, Wisc.—TECHNICIAN

### Pentron TAPE RECORDER

Featured in model TV-4 are dual-speed, dual-track operation at 7½ and 3¾ in. speeds; editing key for

deletion of material while playing back tape. Four jacks include mike input, radio input, output to speaker and output to amplifier. Response (7½ in.): 50-9500 cps. List price including mike, reel of tape and extra reel, \$189.50. Pentron Corp., 777 S. Tripp Ave., Chicago 24, Ill.—TECHNICIAN

### Duotone SPEAKER SYSTEMS

The complete line of Ticonal magnet speakers, in new cabinets designed for Hi-Fi performance, feature improved cone design in the speaker for extended flat response. Duotone, Keyport, N. J.—TECHNICIAN

### Masco INTERCOMS

The Econofone has been introduced to provide economical multiple-station intercom operation. The master is designed to handle up to 5 remotes which can originate or receive calls. An easy modification changes the Econofone into an all-master system; up to 6 masters may then be used with up to 3 separate pairs of conversations or a conference of any group of stations. Remotes have talk-listen switch. Master has volume control with off-on switch, talk-listen switch, pilot light and 5 station-selector switches. Mark Simpson Mfg. Co., L. I. City, N.Y.—TECHNICIAN

# Louisiana Technicians

## New Orleans Association Proposes Licensing

BY CHARLES R. MADUELL, JR.

A few days ago, while the author was at the parts counter of a local distributor, he was approached by a casual acquaintance with the statement, "Aren't you a member of the Radio and Electronic Technician's Association?" When I stated that I was a member, he said that we RETA people were a very foolish bunch. Here we were charging at the rate of \$5.00 for a service call, plus the legal or suggested list price for tubes; he was getting only \$3.00 for a service call, but making all the gravy.

Upon further conversation, it was learned that he sometimes charged as much as \$6.00 for a type 5U4 tube. We learned that this "gyp artist" does not have any test equipment, and would not know how to use it if he did. When he finds that the television set needs more extensive repairs than the simple replacing of one or more tubes, he simply takes the set to a local distributor for that make, has it repaired there, and charges the customer twice the price the distributor charged him. And so, with no investment, no equipment, and no knowledge, he makes money on TV repairs. He considers me and the other members of the RETA

The honest technician-dealer is severely handicapped in competing against the "gyp" serviceman. Louisiana technicians feel that the licensing measure they are proposing will untie their hands.



The new bill is intended to help laymen who feel lost when it comes to choosing a technician.

poor business men and rather stupid, because with all our knowledge, all our expensive instruments, and our large investment, we get only the hard jobs, which anyone knows do not pay for themselves, while the back-yard "tube-changer" makes all the money on the simple, paying jobs.

### Other Cases

On checking with the other members of RETA, I found they all had similar stories to tell. The records of the Better Business Bureau of New Orleans was full of the doings of the "gypts." Here are two picked from the lot:

A former customer (says the technician-dealer who is telling the story) called us on the phone to request service on her TV set. Our price of \$5.00 for a service call was too high, according to her. She could get the job done for \$3, she said. However, it was a Saturday, and the \$3.00 man had gone fishing. She would gladly pay the extra \$2 if we would come right out to repair her set.

Our serviceman returned from the customer's house with the story that all the set needed was a fuse and a 6AU5 tube. He charged her

\$0.30 for the fuse, \$3.20 for the tube, and \$5.00 for the service call, a total of \$8.50.

The statement was made to him, "Gee, that tube has certainly dropped in price, hasn't it?" Our serviceman replied that tubes had gone up, not down. At this point, the customer brought out a ticket (the kind used to make out cash bills in small drug and grocery stores, with no name on the top); the bill showed that she had paid \$7.80 for the same tube the last time it had gone bad, plus \$3.00 for the service call. She thought she was getting by cheaply. The sharp tactics here are obvious to any serviceman—the profit on the "\$3.00 call" is obtained by the simple expedient of overcharging on parts, or replacing unneeded parts.

Another case that comes from the files of RETA members: A set came to the XYZ shop for repairs, and it

Charles R. Maduell, Jr. is a college graduate with a degree in physics who has been doing service work on radio, television, electro-medical and industrial electronic equipment since 1940. Maduell is one of the authors of the bill described in his article. He is also a member of the Board of Directors of the Radio and Electronic Technicians Association of New Orleans (RETA).

# Fight "Gyp" Competitors

## to Eliminate Some of the Evils in the Trade

was determined that it had a defective horizontal output transformer. When so informed, the customer stated that he believed this unit was replaced during a former repair job, but that he would check to make sure. About two days later, the bill for this former job was shown to the author. It read as follows:

Two condensers, at \$0.50 each	\$1.00
Replaced horizontal circuit	\$9.50
Replaced vertical circuit	\$9.50
Labor	\$9.50
<hr/>	
Total	\$29.50

What is wrong with this bill is rather obvious.

We have seen several others of a similar nature. One bill listed "replacement of the modulated rectifier" (whatever that is), "repaired chassis front" (body and fender work?) "put picture back in picture tube," etc.

### Legitimate Operators

In New Orleans there are approximately 250 television service shops operating legitimately. By the term "operating legitimately" is meant that there is a store facing on a street or alley, along with the presence of a small stock of parts, some test equipment, and the proper state and city Sales Tax registrations and licenses (business licenses, not technical ones). On a rough estimate, there are over 500 others who are in the "television repair business," operating from their "back-yard." This number includes those who are in legitimate jobs during the day, and become servicemen at night; some of these men are in the trade.

The situation is by no means found only in television. In the electro-medical field, for example, we ran into several instances where a crystal-controlled diathermy had the wrong crystal in it; or non-FCC-approved diathermy units were still being used, units which the salesmen had sold on the basis that the "FCC will not do anything unless they find out you have it."

About two years ago the Radio


and Electronic Technician's Association was re-organized to combat these unethical practices. As an organization going about the matter without legal assistance, we met with one failure after another. Finally, the subject of licensing was brought up, and we had several meetings to see if we could develop a workable law. The plan was to find a law that would not "play politics" in the sense that a group of lawyers, or politicians who knew nothing of the technical side of the thing, would be the administrators of the law.

The Legislature of the State of Louisiana has been considering a

Registration Law for Electronic Technicians that RETA formulated. While the law was designed with a number of purposes in mind, it was chiefly intended to improve customer-technician relations, and to lift the technician from the status of a "laborer" to that of a professional.

The licensing bill proposed by RETA was recently voted down 43 to 26 in the Louisiana House of Reps. RETA will not, however, let its proposal die. Re-introduction of the bill (after modification) is planned when the State Legislature meets again. RETA may alternatively try to get the bill passed as a New Orleans city law.

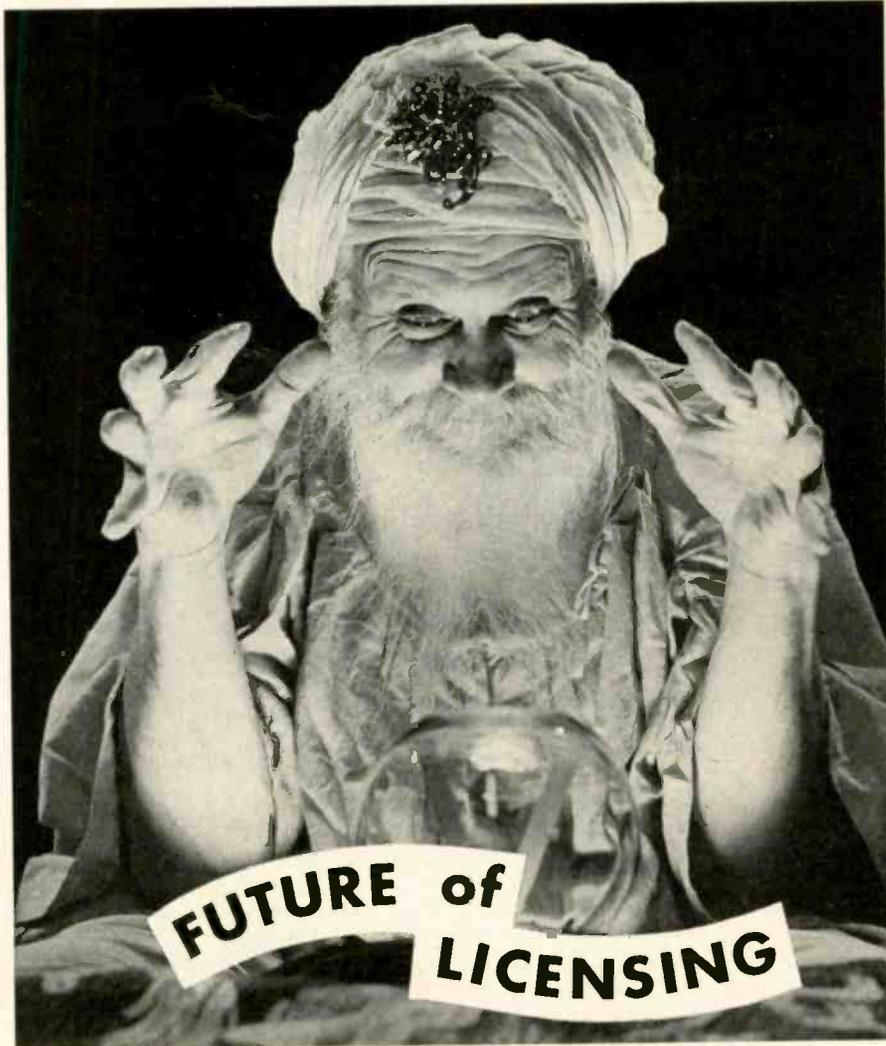Will licensing solve some of the serviceman's problems? Louisiana technicians feel it will, if the technicians themselves, rather than politicians and bureaucrats, administer the bill.




# Auto Radio Service Notes

## Suggestions from Readers on Antenna Installation and Repairs, Interference and Static Elimination
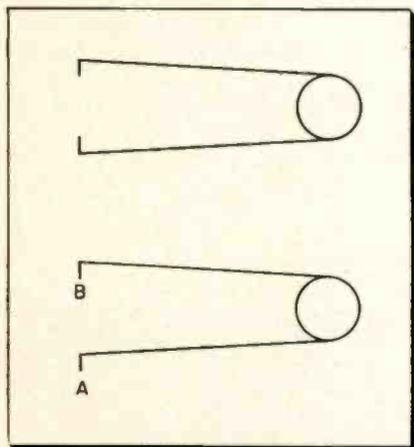
### Handy Tool for Trim Nuts

Many of the trim nuts on auto radio antennas have only two drilled holes providing for tightening. The use of pliers for this job invariably results in marring of the car's finish. To avoid such unpleasantness, we make up two instantly adjustable



wrenches from large steel safety pins, like those used by laundrymen. These tools will accommodate the trim nuts in general use.

Cut off both prongs of the snap end even with the catch. File them down enough to fit the holes in the nuts, and bend them as shown. By poking points A and B down into the two holes in the trim nut, then swinging the tool like an open end or spanner wrench, keeping the handle elevated, the surface finish surrounding the nut will not be scratched.—*Harry J. Miller, Sarasota, Fla.*

### Auto Radio Power Supply

Repairing auto radios was a problem for me, until I licked it. I had no 6 v dc power supply and did not intend to purchase one, since I do not repair many auto radios. What I do now is remove the vibrator and rectifier tube from the auto radio being serviced. Then I feed 6.3 v ac to the input of the set, and apply a B+ voltage to the rectifier output. The two sets of voltages are obtained from a variable voltage supply I have built for experimental purposes (but they might as readily come from other sources available in

the technician's shop).


When the trouble lies in the power supply (as indicated by normal operation of the set when hooked up as just described), resistance checks will generally locate the defect.—*Richard D. Peressini, Fairview, N.J.*

(A pm speaker will have to be substituted, if the set uses an em type.—Ed.)
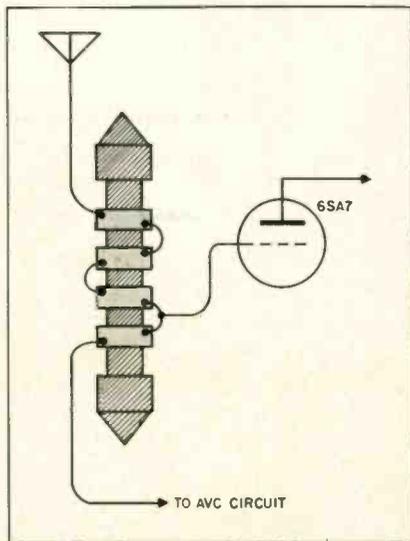
### Substitute Antenna Coil

On numerous occasions, a bad antenna coil is discovered in an auto radio. The motorist wants the set fixed in a hurry. An exact replacement may not be on hand, nor easily available. On such occasions, I have found the conventional radio-frequency choke coil a highly efficient and satisfactory "universal" substitute.

To cite an example: a Chevrolet auto radio, model 985538, was found to have a defective antenna coil. A 2.5 mh radio-frequency choke with 4 pies on it was connected in its place, as shown in the sketch below.



The grid of the 6SA7 tube was connected between the first and second "pie," (counting from bottom). The lead at the top end of the uppermost "pie" went to the antenna. The remaining (bottom) lead was connected to the AVC circuit, as shown. After completion of the repair, the set was given a thorough test. It performed perfectly.

The rfc coil illustrated permits a measure of adjustment on the individual receiver, since the number of pies placed in the circuit may be varied. The unit thus becomes a good "universal" type antenna coil to keep on hand.—*Joseph Amorose, Richmond, Va.*

### Simpler Antenna Installation

A short cut to the installation of radio antennas on 1952 and 1953 Ford cars (as well as Plymouths) may be described as follows: After drilling the hole for the erection of the aerial, lift the hood and poke the aerial down into the space between the V-shaped metal splash pan and the fender. Poke the aerial up through the hole, then drop the rubber grommet plastic cap, metal cap and holding nut down over the aerial. Now the aerial can be held with one hand, while a wrench is used to tighten the hold-down nut that locks the assembly.

Some technicians drill the hole, insert the aerial from the top, then spend a lot of time poking around the innards and splash pan under the hood, to get the locking assembly over the bottom of the aerial. They are thus forced many times to remove the splash pan, whereas my method avoids this time-wasting procedure.—*Harvey Muller, Danboro, Pa.*

### Obscure Static Source

An elusive noise on a car radio was finally traced to static electricity in the car. Seems like the rear end collects the static charge because it is insulated, save through the universal joints, which do not make a good ground; static generated in this area is picked up by the antenna. The trouble was eliminated with the aid of a 20-inch web-type battery ground strap. The terminal end of the strap was attached to the front "U"-bolt of the left rear spring; the surface of the frame above the bolt was well cleaned, and the other end of the strap fastened in place with a sheet metal screw.—*Stanley Clark Service, East Bradenton, Fla.*

## **We Shut Our Order Book!**

In spite of frequent increases in plant capacity, we have often had to refuse orders from set manufacturers for Mallory FP Capacitors. If we hadn't, we would not have had enough to meet demands from servicemen all over the country. That's...

*Proof Positive of  
Mallory Capacitor Dependability*


### **Shut your door—**

on complaints and loss of time and money that call-backs cause you. Always use Mallory Capacitors on your service jobs.

**The Mallory FP Capacitor Line is complete.** There is a rating for every set. Mallory FP's are the only Fabricated Plate Capacitors on the replacement market. And they cost no more than ordinary capacitors.

Always order Mallory Plascaps® for your plastic tubular capacitor needs. Improved moisture-proofing puts an end to shorts, and leads are permanently secured.

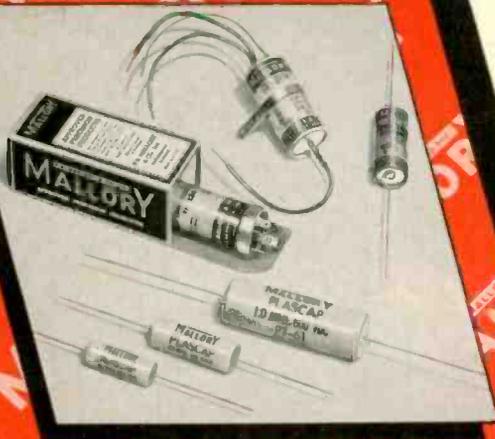Prove to yourself — as many manufacturers and thousands of servicemen have — **YOU CAN ALWAYS DEPEND ON MALLORY CAPACITORS.**



P. R. MALLORY & CO. Inc.  
**MALLORY**

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS  
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES  
**APPROVED PRECISION PRODUCTS**


**P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA**

# Shop Hints to Speed Servicing

Tips for Home and Bench Service Contributed by Readers
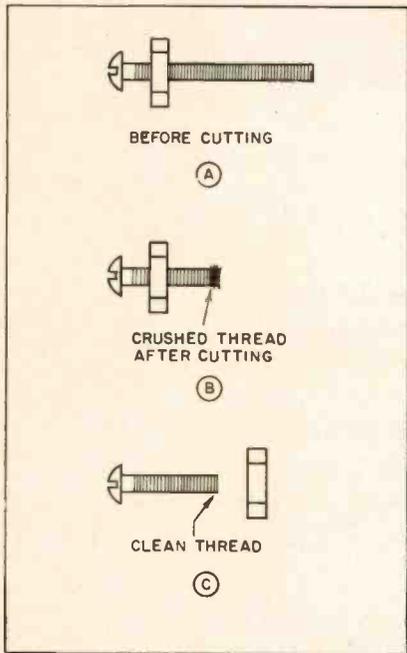
## Tip on Cutting Screws

When a hacksaw is used to reduce the length of a screw to the size desired for a particular job, the starting thread left after cutting is frequently so badly jammed that a nut cannot be threaded on. To pre-




vent this, thread a nut of the right size on the screw *before* cutting, as shown in A. After cutting, when the starting thread has been crushed by the hacksaw blade (see B), the nut is simply threaded off the screw. In coming off, the nut will clean the thread, as shown in C.—M. G. Goldberg, St. Paul, Minn.

## Battery Care For Self-Charging Portables

On G.E. self-charging portables, I have had complaints to the effect that the battery becomes prematurely discharged, and possibly ruined. I have found that customers have a habit of pulling the plug out to shut off the set, instead of first turning the switch to the "off" position. When the receiver is left "on" or in the "charge" position while it is not plugged in, the relatively small leakage current through the set's dry-disc rectifiers tends to discharge the battery. Turning the switch to the "off" position when the receiver is not in use will prevent this.—S. Sandler, Providence R. I.
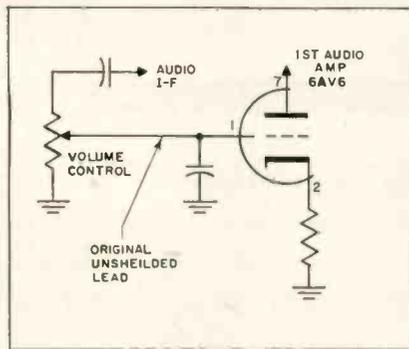
## Buzz Elimination

We had a complaint of excessive buzz on an Admiral 19F1 chassis. Examination showed the buzz to be present on off-channel settings of the tuner, as well as when a signal was being received. The buzz, which was not sync clatter, became more marked with maximum settings of the volume control. Don't waste your



time checking the sync or other circuits; the trouble is in the audio. The trouble spot is an unshielded lead going from the tap on the volume control to the grid (pin 1) of the 1st audio amplifier, 6AV6. We replaced this lead with a length of coaxial cable, which was grounded at both ends of the shield; however, ordinary shielded audio wire can be used.—Paul Leichter, Philadelphia, Penna.

## Horizontal Jitter

Sparton Chassis 27D213: A jelly-like jitter of the picture in a side-wise direction was evident on strong audio signals, following the replacement of condenser C-73 in the audio output stage. This symptom was particularly evident when the volume control was turned up. The two sections of C-73 are respectively the screen and cathode bypass condensers for the 6V6 sound output tube, V-15. The trouble arose be-

## SHOP HINTS WANTED

TECHNICIAN will pay \$5 for acceptable shop hints. We are particularly interested in hints that tell how a technician located a hard-to-find trouble in a TV set, radio, record-changer or similar unit; or how he traced a conventional defect to its source more rapidly than usual by using a shortcut. Unacceptable items will be returned to the contributor. Send your ideas to "Shop Hints Editor, TECHNICIAN, Caldwell-Clements, Inc., 480 Lexington Ave., New York 17, New York."

cause the ground terminal for this tube was too near the 6AL5 horizontal phase detector, V-25. Apparently the ground currents of the audio tube mingled with the ground currents of the phase detector.


A heavy piece of shielding braid was connected to each of the grounding lugs and returned to the chassis near the cathode resistor ground of V-15, the sound output tube. This extra grounding minimized the audio ground loop and eliminated the symptom.—James A. McRoberts, Brooklyn, N. Y.

## Screwdriver Improvement

Considerable burring of all types of Phillips-head screws often results from slippage of the Phillips-head screwdrivers. The slippage may be decreased considerably by filing down the tips of the no. 1 and no. 2 screwdrivers about  $\frac{1}{32}$  in. This measure will insure better traction in the screw heads.—A. Ringel, Culver City, California.
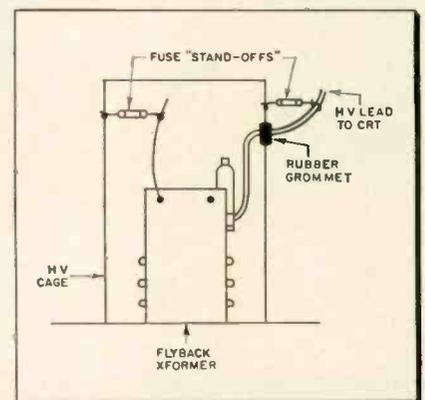
## Unique HV Standoff

Don't throw those burned-out pigtail fuses away! When trying to dress leads inside high voltage cages, and in similar applications when it is desired to keep leads fixed in desired positions, the burned-out pigtail



fuses can be used as anchors. Since the fuse is blown, the glass envelope provides effective high voltage insulation. As with cellulose tape, the applications for these fuse "stand-offs" are only limited by the technician's ingenuity. The pigtailed are used for tying purposes. Some possibilities are illustrated. B. O. Riis, Little River, Miami, Fla.

# CONQUERORS of CANYONS!


## Federal's

QUALITY-CONTROLLED

# BIG 5
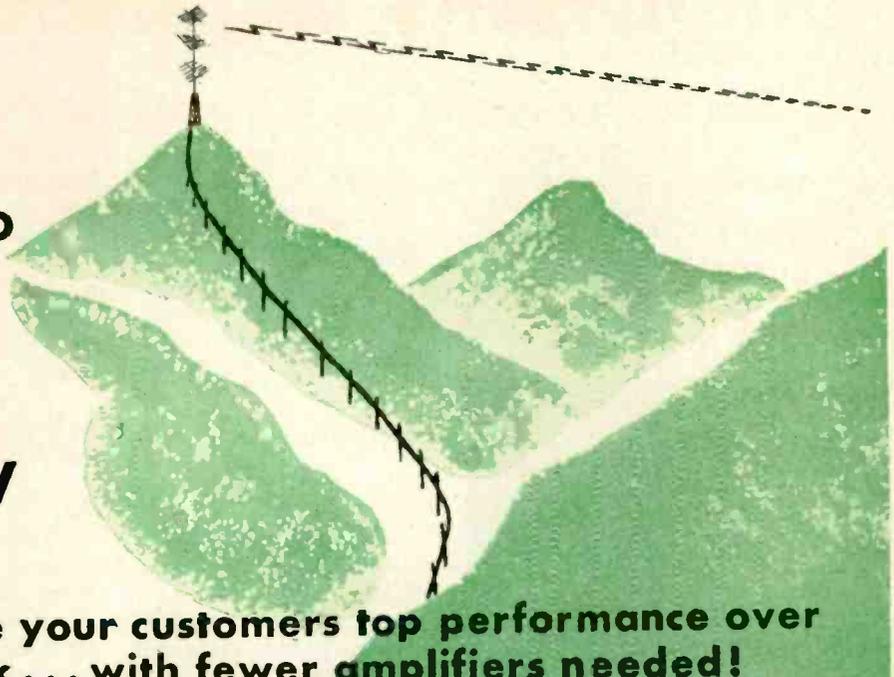
## COMMUNITY TV LEAD-INS

Engineered to give your customers top performance over the longest link... with fewer amplifiers needed!



K-14—Primary Lead-in



RG-11/U—Secondary Lead-in



RG-59/U—Tap-off Lead-in

NON-RADIATING LEAD-INS



K-125—Alternates for RG-11/U



K-126—Alternates for RG-59/U

# SWEEP-TESTED

TO ORDER—backed by notarized proof!

Federal's K-14—the primary lead-in famous for lowest line loss, long cable runs and fewer amplifiers—and Federal's RG-11/U and RG-59/U are the coaxials you can specify with utmost confidence... for Community TV Distribution Systems in any area... for any amplifier system.

When profit-eating signal leakage occurs the answer is Federal's K-125 and K-126 (non-radiating alternates for RG-11/J and RG-59/U).

All five are made to Federal's high standards of quality—and that means dependable, all-weather transmission... anywhere!

ORDER SWEEP TESTING—BE DOUBLY SURE!

Upon request, Federal will sweep test K-14, RG-11/U and K-125... check attenuation from 50 mc up to 220 mc... for VHF channels 2 to 13. A notarized statement certifies that the test has been made... that attenuation does not vary over .5 db from the nominal values throughout the spectrum. There is a small additional charge for this valuable service.

Be doubly sure you're getting today's finest lead-ins for Community TV... specify Federal's "Big 5"... backed by sweep testing!

Principal Characteristics of Federal's "Big 5" of Community TV

TYPE	ZO Impedance Ohms	Capacitance per ft. micro-micro farads	DB per 100 Feet				Jacket OD Mils	Weight per 1000 Ft. (lbs.)
			50Mc	100Mc	200Mc	400Mc		
K-14	71	21	.57	.90	1.42	2.3	885	392
RG-11/U	75	20	1.5	2.15	3.2	4.7	415	89
RG-59/U	73	22	2.7	4.0	5.7	8.5	250	36
K-125 (5P-75)	75	20	1.5	2.15	3.2	4.7	470	127
K-126 (5P-76)	73	22	2.7	4.0	5.7	8.5	325	79

America's leading producer of solid dielectric cables



## Federal Telephone and Radio Company

A Division of INTERNATIONAL TELEPHONE AND TELEGRAPH CORPORATION  
COMPONENTS DIVISION 100 KINGSLAND ROAD CLIFTON, N. J.

In Canada: Federal Electric Manufacturing Company, Ltd., Montreal, P. Q.  
Export Distributors: International Standard Electric Corp., 67 Broad St., N. Y.

WRITE DEPT. D-254  
for complete data on  
Federal's "Big 5" of  
Community TV and  
Certified  
Sweep Testing

# COLOR SHORTS

**NEW DEFLECTION YOKE FOR 19-IN. TUBES** provides improved convergence characteristics according to the manufacturer, General Instrument Corp. The product of research in an optical laboratory especially set up for such design, the yoke is suitable for use with the three current types of 3-gun tubes;



the planar mask type, the monconvergence shadow-mask type, and the type in which the color phosphors are applied directly to the curved face. The complete yoke with plastic case removed is being held by Edgar Messing, General Instrument exec.

**21-IN. SETS FOR ABOUT \$500 IN '55:** That's the prediction of Barney Balaban, prexy of Paramount Pictures. Paramount is 50-percent owner of Chromatic TV Labs, developers of the single-gun Lawrence color crt (Chromatron). The prediction is based on the use of the Chromatron . . . Chromatic has issued a full data-specification sheet on development type PDF 21-3, the rectangular glass-shell version of their single-gun tube. Diagonal of the viewing area is about 18 in.

**INTEREST AMONG TECHNICIANS** in color TV remains high in Kansas, Missouri and Southern Illinois, reports the Hoffman Sales Corp. of Missouri, as evidenced by the success of the six color schools in this area now being conducted by this outfit. As an example, David Doss, Hoffman gen. mgr., points to an attendance of 300 during the first week of the St. Louis training program, which corresponded with the opening of the vacation season. Second-week attendance was 400. Program will run for 10 weeks, each class is for a 3-hour period.

**ANDREA'S 19-IN. COLOR SET** will be ready for sale this fall, according to F. A. D. Andrea, the firm's prexy. Production on the 15-in. set, announced in April *Color Shorts*, has been dropped. "Developments in the television field," says Andrea, "have confirmed my early convictions to the effect that a small screen would not sell and is not a practical investment . . . I sincerely believe that this larger picture is the ideal size to start with."

**CLOSED-CIRCUIT TV SYSTEMS** for educational and industrial applications can now operate in full color. As a result of a recent patent license agreement with CBS, GE is now making such equipment. The color system used is not similar to the present commercial one approved by the FCC. Instead it is based on the old field-sequential system formerly given FCC approval. GE says this technique was chosen after comparative field tests because it provides superior color reproduction, makes possible better image detail and offers the user lower initial-equipment and operating costs . . . GE has also shipped complete color slide origination equipment to KING-TV, Channel 5, Seattle, Wash., will also ship color film origination equipment. KING-TV will begin regular color programming by early fall.

**DU MONT NETWORK** begins color telecasts this fall. Programs will originate from WABD, Channel 5, Du Mont's New York outlet. Dr. Du Mont feels that development of economical large-screen color pix tubes is breaking the log-jam in color TV. Receivers under this brand name, using the 19-in. Chroma-Sync Teletron, are expected to be available this fall.

**TESTING REQUIREMENTS** and test procedures for color-TV took up all of the June issue of the *Technician's Timesaver*, monthly test-equipment publication of Simpson Electric Co. Typical response curves and test set-ups are illustrated for color sets. Use of the Chromatic Probe and Chromatic Amplifier in adapting existing test instruments for color service is also illustrated.

**CBS VERSION OF THE 3-GUN TUBE**, designated 15HP22, is the subject of a 4-page data and application folder released by that manufacturer. As we go to press, CBS also announces a 19-in. version of their 3-gun design. This larger crt is being designated Colortron 205.

**MOTOROLA MOBILE LAB** is touring the country to check color TV performance and reception conditions under a wide variety of local conditions. These "on-location" checks are being conducted, says the manufacturer, because it is impossible to simulate interference,



snow and fringe problems, together with their effects on color reception, in the fixed-installation engineering department. The mobile lab truck, in addition to \$20,000 worth of elaborate testing gear, carries a full staff of engineers and technicians.

**BIGGER PIX, LOWER PRICE:** More news from Motorola comes in the form of an announcement of 3 color receivers, all using the CBS 19-in. color tube and each selling below \$1000—or below previously announced prices for sets using 15-in. pix tubes. Basic price for one of these sets is \$895.

Paul L. Galvin, Motorola prexy, in making the announcement also predicted his company would sell 25,000 of these color sets this fall. However, he still expects his monochrome receivers to outsell the new color models by a ratio of about 25 to 1.

Decision to market color now, after a wait-and-see period, was prompted by availability of larger crt, increase in color TV programming, and ability to market at a reasonable price.

after  
you  
leave . . .



**ASTRON**

**capacitors**

**build your reputation**

**C**onsumer satisfaction means repeat business. That's why smart servicemen install **ASTRON BLUE POINT®** capacitors and **SAFETY MARGIN\*** electrolytics.

They know **ASTRON** capacitors are worthy of their trust.


Exclusive **ASTRON**-developed material treatments, electrolytes, tough element-proof shells and contamination free assembly . . . stop call-backs, insure consumer satisfaction.

Servicemen install **ASTRON** capacitors because they know that more and more TV & Radio manufacturers use them in original equipment.

More and more manufacturers are using them because of their surprisingly long life and utmost dependability!

Try something new . . . start installing **ASTRON CAPACITORS** today . . . they work for you long after you leave the call.

\*TRADEMARK

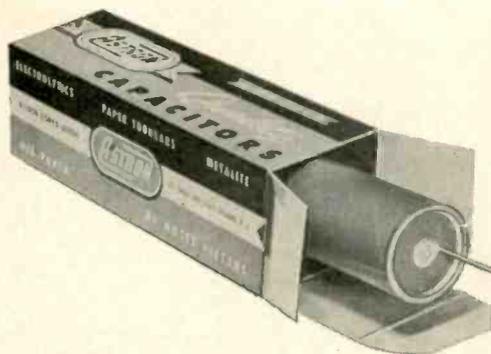

**ASTRON**  
CORPORATION

255 GRANT AVENUE, E. NEWARK, N. J.



Export Division: Radio International Corp. 13 E. 40 St., New York, N. Y.  
In Canada: Charles W. Pointon 6 Alcino Ave., Toronto 10, Ontario

# SERVICE ASSOCIATION REPORTS

## LIETA Code of Ethics

New members of the Long Island Electronic Technicians Association, 88 Fourth Street, Oceanside, N.Y., subscribe to the group's Code of Ethics when they sign their applications. Some points covered in the code: employment of qualified personnel, with no students working as master technicians; avoidance of trick advertising; 90-day guarantee on repairs to customers, including itemized bill; use of replacement parts of suitable quality.

*LIETA News*, published monthly, now includes a page for the ladies. Contributions are by members of the Ladies' Auxiliary, made up of wives and daughters of regular members.

## RTTG Uses TECH'N Piece

The Radio & Television Technician's Guild, 315 North 24th Street, Gadsden, Alabama, has been granted permission to reproduce *TECHNICIAN's* March editorial, *So Much for So Little*, as an ad in the local paper, *The Gadsden Times*. The organization feels such use of the editorial will help the local serviceman. The request came from Guy Brooks, RTTG Secy. President of the Guild is F. F. Hall.

## NATESA Organizing Guide

Having trouble getting a service association rolling in your area? National Alliance of Television & Electronic Service Associations, 5908 S. Troy St., Chicago 29, Ill., will send you a copy of its booklet, *Here's How*, which lists a dozen steps to establishing a local association. A sample constitution and examples of promotional material and other forms actually used by some groups are included. The booklet stresses the need for local organizations, as well as nation-wide affiliation and representation in this nation-wide industry. NATESA, however, does not accept member-

ship from individual technicians, as such, but only from operators of service businesses, whether they are one-man set-ups or larger.

Membership in NATESA, by a local group, is \$25 per year. Associate membership for individual service companies operating in areas where a local association does not exist is permitted. Such individual membership has been reduced from \$10 to \$5 a year.

## Welcome to ESA

The recently formed Electronic Service Association, 1763 E. Seven Mile Road, Detroit 3, Mich., is looking for members. The organization is open to "anyone engaged full time in the servicing of radio, television and electronic equipment," according to R. Aronson, Chairman of the Publicity Committee. Educational meetings and service clinics are being planned for the future. Prexy is Ralph L. Carew; corresponding secy. is T. T. Czarnecki.

## TSDA Elections

Installed at the June dinner and meeting of the Television Service Dealers Association of Philadelphia, 6021 Ogontz Ave., Philadelphia, Penna., were the new officers elected to serve for 1954-55. They were Charles Kneell (president), Edward Strychowski (vice president), Harrison Neel (treasurer) and Martin Benoff (secretary).

TSDA has approved a bill to be proposed to the city council, for the purpose of controlling bait advertising. Drafted by the association's legal counsellors, the proposed ordinance would put the squeeze on phoney ads by unethical service operators.

## RTSA Subscribes

The Radio & TV Service Association, 9302 Dartmouth Avenue, Tampa 4, Florida, has sent in a group of subscriptions to *TECHNI-*

*CIAN*. The accompanying letter says, in part: "The object of our organization is to better acquaint the general public with TV and to inform all servicemen in this area with up-to-date service information. We feel assured that a subscription to *TECHNICIAN* is one of the better ways of acquainting our servicemen with the latest, up-to-date information." The letter is signed by Ray Murphy, secy.

Other RTSA officers are L. W. Van Slyck, pres.; Benny Diaz, vice pres.; and Charles Stump, treas. Meetings are held the 2nd and 4th Tuesday evenings of each month.

## TSE Doings

According to *The Supreme Effort*, organ of Television Service Engineers, 307 Shukert Building, Kansas City, Mo., chronic absenteeism from meetings will be a cause for suspension of membership. This ruling was incorporated in the new by-laws. Such rules, which have been adopted by other associations, seem to be part of a trend to establish healthy active groups rather than paper organizations. . . . TSE will run free want ads in its paper for qualified technicians who are seeking employment.

An item in *The Supreme Effort* lauds "Sol Heller, managing editor of Caldwell-Clements great magazine, *TECHNICIAN*," for the work "he and his staff are doing to better the position and lighten the load of the service man and shop owner. . . . (*TECHNICIAN*) really fills the bill. For instance there is in the June copy several suggestions as to how to combat the summer slump. . . . not hairbrain schemes or get-rich-quick ideas, but solid business-builders."

The business-builder material was prepared by J. L. Stoutenburgh, consulting editor.

## RTGLI Ad Policy

*The Guild*, monthly organ of the Radio Television Guild of Long Island, Box 87, Bethpage, N.Y., accepts ads only from those wholesalers and jobbers who observe a code of fair practices that excludes cut-price sales direct to the public. One-third of a page in the June issue was left blank except for this brief notice inserted in the larger area of white paper: "But for his over-the-counter sales, this space could have been occupied by another distributor."

## WILL YOU HELP US?

. . . By giving us the name of the technical association to which you belong? We'd like this information as part of an editorial survey which we're conducting.

Service Association: .....

Address .....

Manager or Recording Secretary's Name: .....

Phone: .....

Your Name: .....

Your Address: .....


Mail to: Associations Editor, *TECHNICIAN*,  
480 Lexington Avenue, N.Y.C. 17, N.Y.



**SYLVANIA**  
*Aluminized  
 Picture Tubes*  
**ARE PACKED  
 WITH PROFITS!**

**Make old sets like new... have more satisfied customers!**

**SIZE?**

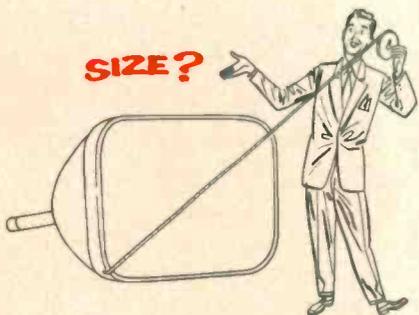


Interested in new sales records? You'll be heading in that direction when you replace old picture tubes with new Sylvania Aluminized Tubes.

Sylvania Aluminized Picture Tubes give terrific performance. They make old sets better and brighter than new by providing whiter whites—blacker blacks... a 6-times better picture contrast.

Sylvania Aluminized Picture Tubes are now available in most sizes for all popular TV sets. In other words, with Sylvania Aluminized Picture Tubes, you give your customers the best possible buy *and* the best possible service, including a full one-year warranty.

Remember, millions of set owners see and hear about Sylvania Picture Tubes on the nation-wide weekly television show "Beat The Clock." They know that they are famous for quality and dependability. For full details about aluminized tube replacement, write for Sylvania's "Aluminized Picture Tube Replacement Guide." Address: Dept. 4R-4208, Sylvania NOW!

**COST?**

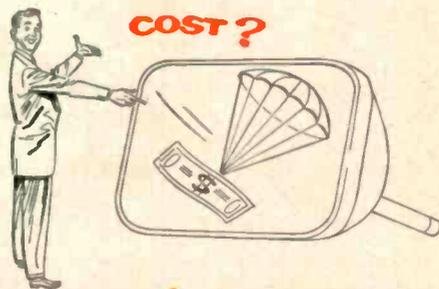

**PERFORMANCE?**



**SYLVANIA**

Sylvania Electric Products Inc.  1740 Broadway, New York 19, N. Y.

In Canada: Sylvania Electric (Canada) Ltd.  
 University Tower Building, St. Catherine Street, Montreal, P. Q.

**LIGHTING • RADIO • ELECTRONICS • TELEVISION**

# Test Equipment "Spec" Chart

## Data on Scopes, VTVM's Generators & Tube Checkers

(Specifications on other types of test equipment will appear in forthcoming issues.)

### OSCILLOSCOPES

MANUFACTURER	MODEL	FREQUENCY RESPONSE, VERT. AMPLIFIER	FREQUENCY RESPONSE, HORIZ. AMPLIFIER	DEFLECTION SENSITIVITY, VERT. AMP.	DEFLECTION SENSITIVITY, HOR. AMP.	SWEEP FREQUENCIES	INPUT IMPEDANCE, VERT. AMP.	INPUT IMPEDANCE, HORIZ. AMP.	CRT DIAMETER	PRICE
ALLEN B. DU MONT LABORATORIES, INC. 760 BLOOMFIELD AVE., CLIFTON, N.J.	274-A	UNIFORM WITHIN 10% FROM 20 CPS TO 50,000 CPS, DOWN NOT MORE THAN 50% AT 200 KC	UNIFORM WITHIN 10% FROM 20 CPS TO 30,000 CPS	.7 V/IN., PEAK-TO-PEAK TO-PEAK PER IN., $\pm 18\%$	.7 PEAK-TO-PEAK V/IN. (DIRECT: 51 P.P. V/IN., $\pm 18\%$ )	8 CPS TO 30,000 CPS	1 MEG, 40 MMFD. (DIRECT: 4.7 MEG, 50 MMFD)	1 MEG PARALLELED BY 40 MMFD. (DIRECT: 4.7 MEG PARALLELED BY 50 MMFD.)	5 IN.	\$150.00
ELECTRONIC INSTRUMENT CO., INC., 84 WITHERS STREET, (BROOKLYN 11, N.Y.)	292 *	UNIFORM WITHIN 30% FROM 5 TO 100,000 CPS	FLAT $\pm 0$ DB, 10 CPS TO 1 MC	.4 RMS V/IN. (DIRECT: 20 RMS V/IN.)	.36 RMS V/IN. (DIRECT: 3 RMS V/IN., $\pm 15\%$ )	8 CPS TO 30,000 CPS	1 MEG, 70 MMFD (DIRECT: 4.7 MEG, 25 MMFD)	1 MEG PARALLELED BY 70 MMFD. (DIRECT: 4.7 MEG PARALLELED BY 25 MMFD)	3 IN.	\$130.00
ELECTRONIC MEASUREMENTS CORP., 280 LAFAYETTE STREET, N. Y. 12, N.Y.	470-K	FLAT $\pm 2$ DB, 10 CPS TO 1 MC	FLAT $\pm 0$ DB, 10 CPS TO 200 KC, -4 DB AT 500 KC	10 RMS MV/IN.	.3 RMS V/IN.	15 CPS TO 100,000 CPS	3 MEG SHUNTED BY 35 MMFD	1 MEG SHUNTED BY 40 MMFD	7 IN.	IN KIT FORM, \$ 79.95, WIRED, \$129.50
ELECTRONIC MEASUREMENTS CORP., 280 LAFAYETTE STREET, N. Y. 12, N.Y.	425	5 CPS TO 500 KC, USABLE TO 2.5 MC	5 CPS TO 500 KC	.05 TO .1 RMS V/IN.	.05 TO .15 RMS V/IN.	15 CPS TO 75 KC	1 MEG	1 MEG	5 IN.	IN KIT FORM, \$ 44.95, WIRED, \$ 79.95
ELECTRONIC MEASUREMENTS CORP., 280 LAFAYETTE STREET, N. Y. 12, N.Y.	600	USEFUL TO 5 MC	USEFUL TO 1 MC	.02 RMS V/IN.	3 RMS V/IN.	15 CPS TO MORE THAN 75 KC	1 MEG, 35 MMFD ON 600 V POSITION	5 MEG, 40 MMFD	5 IN.	\$ 99.50
FELER ENGINEERING & MFG. CO., 8026 N. MONTICELLO AVE., SOKKIE, ILLINOIS	T5-7	USEFUL RESPONSE, 20 CPS TO .75 MC, UNIFORM WITHIN 20% TO 100 KC	USEFUL TO 1 MC	5 RMS V/IN. (DIRECT: 18 RMS V/IN.)	.5 V RMS/IN. (DIRECT: 18 V RMS/IN.)	10 CPS TO 32,000 CPS	1 MEG, 50 MMFD (DIRECT: 5 MEG, 60 MMFD)	1 MEG, 50 MMFD (DIRECT: 5 MEG, 50 MMFD)	5 IN.	IN KIT FORM, \$ 49.50, WIRED, \$ 98.50
GENERAL ELECTRIC, ELECTRONICS DIVISION, SYRACUSE, N.Y.	ST-2A *	PROBE AND AC: $\pm 0$ TO 20% FROM 20 CPS TO 500 KC, $\pm 0$ TO 50% FROM 20 CPS TO 1 MC, DC $\pm 0$ , -20% FROM 0 TO 500 KC	0 TO 100 KC AT FULL GAIN SETTING; -20% FROM 20 CPS TO 100 KC AT ANY GAIN SETTING	AC INPUT: .015 RMS V/IN. DC INPUT: 2 RMS V/IN. PROBE: 2 RMS V/IN.	.4 RMS V/IN.	10 CPS TO 100 KC	AC INPUT: 1 MEG, 36 MMFD. DC INPUT: 1 MEG, 80 MMFD AT MAX. GAIN SETTING. PROBE: 1 MEG, 10 MMFD.	10 MEG, 35 MMFD	5 IN.	\$327.50
HEATH COMPANY, BENTON HARBOR, MICH.	0-9	$\pm 2$ DB, 10 CPS TO 2 MC, $\pm 6$ DB, 5 CPS TO 3 MC	$\pm 6$ DB, 10 CPS TO 500 KC	.025 V/IN. AT 1 KC	.6 V/IN./AT 1 KC	10 CPS TO 50,000 CPS	47 MMFD SHUNTING 2 MEG AT X1 POSITION, 35 MMFD SHUNTING 2 MEG, AT X10-100 POS.	25 MMFD SHUNTING 1 MEG	5 IN.	\$ 59.50
HICKOK ELECTRICAL INSTRUMENT CO., 10514 DUPONT AVE. CLEVELAND 8, OHIO	665	.5 CPS TO 700 KC, WITHIN 3 DB	0-250 KC	.02 RMS V/IN.	.03 RMS V/IN.	18 CS TO 50 KC	1.5 MMFD, 2.2 MEG.	52 MMFD, .1 MEG	5 IN.	\$129.50
HYCON MFG. CO., 2961 EAST COLORADO ST., PASADENA 8, CALIF.	670 *	DC TO 600 KC, WITHIN 3 DB, USEFUL BEYOND 5 MC	0-250 KC	.015 RMS V/IN. (DIRECT: 12 RMS V/IN.)	.07 RMS V/IN. (DIRECT: 13 RMS V/IN.)	3 CPS TO 50 KC	2.2 MEG, 30 MMFD. (DIRECT: 3.3 MEG)	1 MEG, 35 MMFD. (DIRECT: 3.3 MEG)	5 IN.	\$244.00
JACKSON ELECTRICAL INSTRUMENT CO., DAYTON 2, OHIO	CRO-2	FLAT WITHIN 1 DB FROM 20 CPS THROUGH 4.5 MC	FLAT WITHIN 1 DB FROM 20 CPS THROUGH 4.5 MC	NARROW-BAND: .01 V P.P. PER INCH; WIDE-BAND: 0.1 V P.P. PER INCH		15 CPS TO 100 KC			3 IN.	\$260.00
PHILCO CORP., ACCESSORY DIVISION, PHILADELPHIA, PA	8202	10 CPS TO 1 MC WITHIN 6 DB	10 CPS TO 300 KC	.01 RMS V/IN.	.3 RMS V/IN.	TO 100 KC			5 IN.	\$225.00
	8200 *	0-750 KC WITHIN 2 DB; 0-1 MC, WITHIN 6 DB	20 CPS TO 80 KC WITHIN 2 DB, 10 CPS TO 125 KC WITHIN 6 DB	WITH DIRECT CABLE: .05 V RMS/IN. WITH LOW-CAP. PROBE: .5 RMS V/IN.	.5 RMS V/IN.	15 CPS TO 30,000 CPS	WITH LOW-CAP. PROBE: 1 MEG SHUNTED BY 10 MMFD.	WITH OUT CABLES: 1 MEG SHUNTED BY 25 MMFD, WITH LOW-CAP. PROBE: 1 MEG SHUNTED BY 10 MMFD	5 IN.	\$159.95
	8200 *					TO 100 KC			3 IN.	\$149.50



VTVM'S (CONT'D)

MANUFACTURER	MODEL	METER SIZE	VOLTAGE RANGES (HV, P-P, SEE FOOTNOTE)	RESISTANCE RANGES	FREQUENCY RESPONSE (HF, SEE FOOTNOTE)	DB RANGES	INPUT IMPEDANCE (MEOGHAS)	NOTES	PRICE
HICKOK ELECTRICAL INSTRUMENT CO., 10514 DUPONT AVE., CLEVELAND 8, OHIO	209A	9 IN.	AC/DC: #0-3, 12, 30, 120, 300, 1200 V. P-P	7 RANGES 0.1 OHM TO 10,000 MEGS	HF(N): 200 MC		AC: 12 DC: 15	MEASURES CAPACITANCE, 0-1000 MFD IN 7 RANGES; INDUCTANCE, 50 MH-100HY AUDIO TONE FOR CONTINUITY CHECKS	\$ 132.50
	225	9 IN.	AC/DC: #0-1.5, 3, 12, 30, 120, 300, 1200 V. P-P	0.2 OHMS TO 100 MEGS	40 CPS TO 3.5 MC		10		\$ 89.50
	215	5 IN.	SAME AS MODEL 225	7 RANGES 0.2 OHMS TO 1000 MEGS	40 CPS TO 3.5 MC		10 WITH PROBE, 30		\$ 67.50
HYCON MANUFACTURING CO., 2961 E. COLORADO ST., PASADENA 8, CALIF.	612	4.5 IN.	AC/DC: #0-3, 10, 100, 300, 1000 V. HV: 30 KV	5 RANGES TO 10 MEGS	HF(X): 50 MC		10	BUILT-IN TUBE CHECKER	\$ 135.00
JACKSON ELECTRICAL INSTRUMENT CO., DAYTON 2, OHIO	614	5.5 IN.	SAME AS MODEL 612	SAME AS MODEL 612	HF(X): 50 MC		10		\$ 85.00
JACKSON ELECTRICAL INSTRUMENT CO., DAYTON 2, OHIO	709	7 IN.	AC/DC: #0-1, 5, 10, 50, 100, 500, 1000 V. HV: 30 KV, P-P	7 RANGES TO 1000 MEGS	TO 4.5 MC		11		\$ 95.00
MEASUREMENTS CORP., BOONTON, N.J.	67		5 RANGES, AC P-P ONLY 0.0005 TO 300 V		5 CPS TO 100 KC		1		
PHILCO CORP., ACCESSORY DIV., "A" & ALLEGHENY AVE., PHILA. 24, PA.	M-8100		AC/DC: #0-1.5, 15, 150, 450, 1500 V. HV: 22.5 KV. P-P	5 RANGES TO 1000 MEGS	HF(X):	-20 TO +65	AC: 5 DC: 10	VOLTAGE REGULATED	\$ 64.95
PRECISE DEVELOPMENT CORP., OCEANSIDE, N.Y.	9071W*	7.5 IN.	AC/DC: #0-5, 25, 250, 500, 1000 V. HV: 30 KV	5 RANGES 0.2 OHMS TO 1000 MEGS	HF(X): 250 MC	-20 TO +55	DC: 25		\$ 49.95
PRECISION APPARATUS CO., INC., 92-27 HORACE HARDING BLVD., ELMHURST 6, N.Y.	909W*	4.5 IN.	SAME AS MODEL 9071W	SAME AS MODEL 9071W	HF(X): 250 MC	-20 TO +55	DC: 25	MODEL 907 SAME WITH 7.5 IN. METER	\$ 37.50
RADIO CITY PRODUCTS CO., INC., 152 W. 25 ST., NEW YORK 1, N.Y.	EV-10A	7 IN.	AC/DC: #0-3, 12, 60, 120, 300, 1200 V. HV: 60 KV	8 RANGES TO 10,000 MEGS	HF(X):	8 RANGES -20 TO +77	DC: 11	8 CURRENT RANGES, DC: 0-0.5, 1.5, 5, 0-1.2, 6, 30, 120, 600, 1200 MA; 0-1.2 AMPS	\$ 99.75
	657	8.5 IN.	AC/DC: #0-1.5, 3, 6, 30, 150, 600, 1500, 6000 V. HV: 30 KV. P-P	7 RANGES TO 1000 MEGS	30 CPS TO 3 MC	-20 TO +62	25	SAME CURRENT RANGES AS MODEL EV-10A	\$ 69.95
	655		AC/DC: #0-1.5, 15, 50, 150, 500, 1500 V. HV: 30 KV. P-P	7 RANGES TO 1000 MEGS				MEASURES CAPACITANCE, 1 MMFD TO 1000 MFD, IN 6 RANGES	\$ 59.50
	345		AC/DC: #0-5, 25, 100, 250, 1000 V. HV: 30 KV	5 RANGES TO 1000 MEGS					\$ 47.50
RADIO CORP. OF AMERICA, TEST EQUIP., HARRISON, N.J. (RCA)	WV-87A	8.5 IN.	AC/DC: #0-1.5, 5, 15, 50, 150, 500, 1500 V. P-P	7 RANGES TO 1000 MEGS	30 CPS TO 3 MC		AC: 1.5 DC: 11	9 CURRENT RANGES, DC: 0-0.5, 1.5, 5, 1.5, 50, 150, 500 MA; 0-1.5, 1.5 AMPS	\$ 112.50
	WV-97A		SAME AS MODEL WV-87A	SAME AS MODEL WV-87A	SAME AS MODEL WV-87A		SAME AS WV-87A		\$ 67.50
	WV-77A		AC/DC: #0-3, 12, 60, 300, 1200 V	5 RANGES, TO 1000 MEGS			AC: 2 DC: 11		\$ 47.50
SIMPSON ELECTRIC CO., 5200 W. KINZIE ST., CHICAGO 44, ILL.	303		AC/DC: #0-1.2, 12, 60, 300, 1200 V	5 RANGES TO 1000 MEGS	5 RANGES 25 CPS TO 100 KC	5 RANGES -20 TO +63	AC: 0.275 DC: 10	6 CURRENT RANGES, DC: 0-10 AMPS. MODEL 302 SIMILAR, WITH RF PROBE	\$ 68.00
SYLVANIA ELECTRIC PRODUCTS, INC., 254 RANO ST., BUFFALO, N.Y.	301	7 IN.	AC/DC: #6 RANGES, 0-1000 V. HV: 30 KV. P-P	6 RANGES TO 1000 MEGS	HF(X): 100 MC	6 RANGES -20 TO +61.4	AC: 2.7 DC: 17		\$ 109.50
	221Z	4.5 IN.	AC/DC: #0-3, 10, 30, 100, 300, 1000 V. HV: 30 KV	SAME AS MODEL 301	HF(N): 300 MC		301	7 CURRENT RANGES, DC: 0-10 AMPS	\$ 99.50
TRIPLITT ELECTRICAL INSTRUMENT CO., BLUFFTON, OHIO	631	5.5 IN.	DC: #0-1.2, 6, 30, 120 V					VTVM IS COMBINED WITH VOLT OHM-MILLIAMMETER WHICH MEASURES AC/DC: #0-1200 V; DC: 0-12 AMPS; DB: -30 TO +56. OHMS: 0-150 MEGS	\$ 59.50
WESTON ELECTRICAL INSTRUMENT CORP., 614 FREUNGHUYSEN, NEWARK 5, N.J.	650	5.5 IN.	AC/DC: #0-1, 5, 10, 50, 100, 500 V. DC TO 1000 V. HV: 50 KV. P-P	6 RANGES TO 1000 MEGS	HF(N): 110 MC		AC: 1.4 DC: 11		\$ 69.50
	982		AC/DC: #0-1.6, 8, 40, 160, 400, 800, 1600 V. P-P	7 RANGES TO 1000 MEGS	HF(X)		AC: 2.8 DC: 10		\$ 69.50

\*AC VOLTAGES ARE ROOT-MEAN-SQUARE  
 HF: HIGH FREQUENCY RANGE EXTENDED WITH PROBE. (N): PROBE IN-CLUDED IN PRICE; (X) PROBE AVAILABLE AT EXTRA COST.  
 #AC VOLTAGES ARE ROOT-MEAN-SQUARE  
 P-P PEAK-TO-PEAK (AS WELL AS RMS) VOLTAGES MAY BE MEASURED.  
 HF: HIGH VOLTAGE THAT CAN BE MEASURED WITH PROBE. (PROBE AVAILABLE AT EXTRA COST.)  
 P-P PEAK-TO-PEAK (AS WELL AS RMS) VOLTAGES MAY BE MEASURED.  
 \$ KIT FORM.

SIGNAL GENERATORS

MANUFACTURER	MODEL	FREQUENCY RANGE	INTERNAL MODULATION	EXTERNAL MODULATION	OTHER FEATURES	PRICE
APPROVED ELECTRONIC INSTRUMENT CORP., 142 LIBERTY ST., NEW YORK 6, N.Y.	A-200K	100 KC-25 MC (FUNDAMENTALS); 18-75 MC (HARMONICS)	440 CPS	40-30,000 CPS	CATHODE FOLLOWER OUTPUT. MODULATION % VARIABLE, 0-100%. KIT FORM.	\$ 250.00
CLOUGH-BREngle CO., 6014 BROADWAY, CHICAGO 40, ILL.	*299-A	100 KC-32 MC	400 CPS	50-10,000 CPS	ACCURACY 1% ON HIGH BAND (10 MC-32 MC), 1/2% ON OTHERS. BUILT-IN VTVM. MODULATION % VARIABLE, 0-80%. OUTPUT VARIABLE FROM 0.1 TO MORE THAN 1 V.	(315K) \$39.95 (315W) \$59.95
ELECTRONIC INSTRUMENT CO., INC., 84 WITHERS ST., BROOKLYN 11, N.Y.	*315	75 KC-50 MC (FUNDAMENTALS); 30-150 MC (HARMONICS)	400 CPS	YES	ACCURACY WITHIN 1%. OUTPUT OVER 0.1 V. KIT FORM (315K) OR FACTORY WIRED (315W).	(320K) \$19.95 (320W) \$23.95
ELECTRONIC MEASUREMENTS CORP., 280 LAFAYETTE ST., NEW YORK 12, N.Y.	*320	150 KC-34 MC (FUNDAMENTALS); 22 MC-102 MC (HARMONICS)	400 CPS	YES	R-F OUTPUT OVER 0.1 V. AUDIO OUTPUT 1 1/2-2 V. KIT FORM (320K) OR FACTORY WIRED (320W)	(KIT) \$19.75 (WIRED) \$26.75
GENERAL ELECTRIC, ELECTRONICS DIV., ELECTRONICS PARK, SYRACUSE, N.Y.	500	150 KC-36 MC (FUNDAMENTALS); OVER 100 MC ON HARMONICS	400 CPS	YES	MODULATION % VARIABLE. SQUARE-WAVE OUTPUT TO 20 KC. R-F ACCURACY 1 1/2%. CRYSTAL MARKER AND AMPLITUDE CONTROL.	\$ 55.95
	700	18 CPS-108 MC (FUNDAMENTALS); UP TO 216 MC ON HARMONICS	18 CPS-300 KC		CRYSTAL CONTROLLED R-F CARRIERS, 5 SWITCH SELECTED. CRYSTAL ACCURACY 0.02%.	\$ 439.50
	ST-5A	TV PICTURE CARRIERS, CHANNELS 2-13; VARIABLE I-F CARRIER: 20-50 MC			I-F ACCURACY 0.5%. DIAL READABILITY TO 0.1 MC.	

MANUFACTURER	MODEL	FREQUENCY RANGE	SWEEP WIDTH RANGE	MARKER FACILITIES	OTHER FEATURES	PRICE
HEATH CO., BENTON HARBOR, MICH.	SG-8	160 KC-110 MC (FUNDAMENTALS); 110 MC-220 MC (CALIBRATED HARMONICS)	400 CPS	YES	CATHODE FOLLOWER OUTPUT. R-F OUTPUT OVER 0.1 V. A-F OUTPUT 2-3 V. KIT FORM.	\$ 19.50
HICKOK ELECTRICAL INSTRUMENT CO., 10514 DUPONT AVE., CLEVELAND 8, OHIO	LG-1	100 KC-30 MC (FUNDAMENTALS)	400 CPS	60-10,000 CPS	BUILT-IN METER CALIBRATED IN OUTPUT VOLTAGE AND % MODULATION. OUTPUT FROM 1 MICROVOLT TO 0.1 V. EXTERNAL MODULATING SOURCE MAY BE METRED. CRYSTAL CONTROLLED. VARIABLE A-F OUTPUT 0-15,000 CPS. VARIABLE FM SIGNALS.	\$ 39.50 KIT FORM. \$195.00
INDUSTRIAL TELEVISION, INC., 369 LEXINGTON AVE., CLIFTON, N.J.	*288X	110 KC-110 MC (AM), 110 KC-160 MC (FM), ALL FUNDAMENTALS	60 CPS OR 400 CPS (FM), 400 CPS (AM)		CRYSTAL ACCURACY. SELECTOR FOR 3 CRYSTALS (2.5 MC CRYSTAL SUPPLIED). CALIBRATED CHANNEL MARKERS FOR PIV AND SOUND, 0.05% ACCURACY. BUILT-IN INDICATOR TUBE FOR ZERO-BEAT CALIBRATION.	\$129.50
KAY ELECTRIC CO., 14 MAPLE AVE., PINE BROOK, N.J.	*680	53-89 MC, 174-217 MC, ALL FUNDAMENTALS TO 868 MC ON HARMONICS	400 CPS (ON SOUND CARRIERS)	FROM VHF SOURCE	CONVERTS INPUT SIGNAL (ANY VHF SOURCE) TO OUTPUT ON ANY UHF CHANNEL. CONVERTS VHF TEST EQUIPMENT FOR UHF USE.	\$149.50
PHILCO CORP., ACCESSORY DIV., "A" & ALLEGANY AVES., PHILA. 34, PENNA.	IT-130R	OUTPUT (CONTINUOUS) 470-890 MC (CHANNELS 14-83). INPUT (SWITCH-SELECTED) 50-90 MC, 170-220 MC (CHANNELS 2-13)			SOUND CARRIER ACCURACY TO 0.01%. SEPARATION BET. PIV AND SOUND CARRIER, 4.5 MC WITHIN ±500 CPS. MAXIMUM OUTPUT: SOUND CARRIER, 0.1 V; PIV CARRIER, 0.045 V. 4.5 MC OUTPUT, 0.1 V OR LESS (VARIABLE).	\$350.00
PRECISION APPARATUS CO., INC., 92-27 HORACE HARDING BLVD., ELMHURST, N.Y.	*DUAL-MEGA-MARKER, SR.	R-F SOUND AND PIV TV FREQUENCIES, CHANNELS 2-13	400 CPS OR 60 CPS OR 400 CPS	YES	CATHODE FOLLOWER OUTPUT. KIT FORM (610KA), KIT WITH ASSEMBLED R-F HEAD (610KA); OR WIRED (610W).	(610K) \$23.95 (610KA) \$28.95 (610W) \$39.95
RADIO CORP. OF AMERICA, HARRISON, N.J.	G8000	OUTPUT (CONTINUOUS) 470-890 MC (CHANNELS 14-83). INPUT (FIXED) 60 MC	20-20,000 CPS	YES	CRYSTAL MARKER WITH SEPARATE AMPLITUDE CONTROL. MODULATION % VARIABLE. CATHODE FOLLOWER OUTPUT. KIT FORM (630KA); KIT WITH ASSEMBLED R-F HEAD (630KA); OR WIRED (630W).	(630K) \$33.95 (630KA) \$38.95 (630W) \$53.95
RODACE CITY PRODS., 152 W. 25 ST., NEW YORK 1, N.Y.	610	300 KC-110 MC (FUNDAMENTALS); 60 MC-330 MC (HARMONICS)	400 CPS	YES	MODULATION VARIABLE 0-100%. SEPARATE AUDIO OUTPUT. INDIVIDUALLY CALIBRATED. BUILT-IN AVC-AGC SUBSTITUTION VOLTAGE.	\$ 78.50
SYLVANIA ELECTRIC PRODUCTS, INC., 254 RANO ST., BUFFALO, N.Y.	630	SAME AS 610; ALSO, SEPARATE A-F OUTPUT, 20-20,000 CPS	400 CPS	YES	ACCURACY WITHIN 1% OF CALIBRATION ADJUSTMENT. MODULATION VARIABLE 0-80%.	\$ 67.50
TELEONIC INDUSTRIES, 44 S. RURAL ST., INDIANAPOLIS, IND.	E-200C	88 KC-60 MC (FUNDAMENTALS); TO 240 MC ON HARMONICS	400 CPS	YES	ACCURACY WITHIN 0.5%. MAY BE USED AS BAR OR CROSS-HATCH GENERATOR.	\$ 79.50
TRIPLETT ELECTRICAL INSTR. CO., BLUFFTON, OHIO	*706A	150 KC-55 MC (FUNDAMENTALS); TO 220 MC ON HARMONICS	400 CPS	UP TO 10 MC	OUTPUT 0.1 V OR MORE. CRYSTAL CALIBRATED. ONE TWO OR THREE SIMULTANEOUS MARKERS. % CHECK POINTS, 2.5 MC APART, FOR CRYSTAL CALIBRATION.	\$242.50
WESTON ELECTRICAL INSTR., 614 FREILINGHUYSEN AVE., NEWARK 5, N.J.	*750	9-220 MC (FUNDAMENTALS); TO 900 MC ON HARMONICS	360 CPS AND 141.75 KC	YES	SEPARATE AUDIO OUTPUT, MORE THAN 1 V.	\$ 42.95
	WR-89A	19-260 MC (FUNDAMENTALS)	4.5 MC, 600 CPS, 100-150 KC	YES	DIAL CALIBRATION WITHIN 1% ACCURACY. CRYSTAL CONTROLLED. MAXIMUM FUNDAMENTAL OUTPUT, 0.1 V. SEPARATE CRYSTAL OUTPUT.	\$129.50
	660-A	100 KC-60 MC (FUNDAMENTALS); 60 MC-220 MC (HARMONICS)	400 CPS	YES	MAXIMUM OUTPUT, 1 V. BETTER THAN ± 0.25% ACCURACY	\$100.00
	501	15-120 MC (FUNDAMENTALS); 120 MC-240 MC (HARMONICS)	400 CPS	40-15,000 CPS	MODULATION % VARIABLE. INTERNAL OR EXTERNAL SEPARATE VARIABLE AUDIO OUTPUT, 400 CPS, 0-10 V.	\$ 79.50
	MO-1	420-930 MC	1000 CPS		MAXIMUM R-F OUTPUT, 0.5 V. ACCURACY WITHIN 1% (HAND-DRAWN SCALE). SEPARATE AUDIO OUTPUT, 1000 CPS, 0-20 V.	\$169.50
	*3432	165 KC-40 MC (FUNDAMENTALS); 36-120 MC (HARMONICS)	400 CPS, 300 KC, 4.5 MC		CRYSTAL CALIBRATED (1.5 MC AND 4.5 MC CRYSTALS). DUAL VIDEO AND SOUND MARKERS AVAILABLE. MARKER OUTPUT CONVENTIONAL PIP OR FOR INTENSITY MODULATION OF SCOPE. BAR PATTERN OUTPUT FOR TV LINEARITY CHECKS.	\$199.50
	*3436	470-900 MC (FUNDAMENTALS)				

## SWEEP GENERATORS

MANUFACTURER	MODEL	FREQUENCY RANGE	SWEEP WIDTH RANGE	MARKER FACILITIES	OTHER FEATURES	PRICE
APPROVED ELECTRICAL INSTR. CORP., 142 LIBERTY ST., NEW YORK 6, N.Y.	A-400	0-227 MC	0-12 MC	2-40 MC (FUNDAMENTALS); 40-80 MC (HARMONICS)	CRYSTAL CONTROLLED. UNSWEPT R-F OUTPUT AVAILABLE. PHASING CONTROL. MARKER ACCURACY TO 0.5% OR BETTER.	(360K) \$34.95 (360) \$49.95 \$395.00
ELECTRONIC INSTRUMENT CO., INC., 84 WITHERS ST., BROOKLYN 11, N.Y.	360	500 KC-228 MC	0-30 MC	BUILT-IN OSCILLATOR REQUIRES EXTERNAL CRYSTAL	MARKER AMPLITUDE CONTROL PHASING CONTROL KIT (360K) OR WIRED (360) FORM.	
GENERAL ELECTRIC CO., ELECTRONICS DIV., ELECTRONICS PARK, SYRACUSE 1, N.Y.	ST-4A	4-110 MC, 170-220 MC	500 KC-15 MC	19-60 MC (FUNDAMENTALS); 57-180 MC (HARMONICS); ALSO EXTERNAL	LINEAR SWEEP. PHASING CONTROL. RANGE GREATER THAN 360 DEGREES. SWITCH FOR RETURN SWEEP BLANKING. OUTPUT VOLTAGE 0.1 V, 4-110 MC; 0.5 V, 170-220 MC.	\$ 44.50
HEATH CO., BENTON HARBOR, MICH.	TS-3	4-220 MC	0-15 MC MINIMUM, 0-50 MC MAXIMUM, DEPEND-ING ON FREQUENCY.	EXTERNAL	LINEAR SWEEP. PHASING CONTROL. RANGE APPROX. 170 DEGREES. VARIABLE BIAS VOLTAGE OUTPUT. OUTPUT UP TO 0.3 V.	\$265.00
HICKOK ELECTRICAL INSTRUMENT CO., 10514 DUPONT AVE., CLEVELAND 8, OHIO	695	0-50 MC (HETERODYNED OUTPUT), 50-90 MC (FUNDAMENTALS), 170-220 MC (FUNDAMENTALS)	±20% OF CENTER FREQUENCY UP TO 250 MC; ±10% ABOVE 250 MC		OUTPUT UP TO 2 V. ACCURACY OF MARKER DIAL CALIBRATION, 0.1%.	\$330.00
HYCON MFG. CO., 2961 E. COLORADO ST., PASADENA 8, CALIF.	610	19 MC-900 MC	0-18 MC	19-50 MC, 60-90 MC, 160-220 MC, 450-900 MC		\$245.00
JACKSON ELECTRICAL INSTR. CO., DAYTON 2, OHIO	TVG-2	2-108 MC, 174-216 MC	0-30 MC	FUNDAMENTALS; 4-8 MC, 16-29 MC, 27-54 MC. HARMONICS: 8-16 MC, 54-216	PHASING CONTROL. RETURN TRACE BLANKING CONTROL. 400 CPS MODULATION. MODULATION OF R-F OUTPUT BY EXTERNAL VIDEO SIGNAL. OUTPUT UP TO 0.25 V. TRIPLE MARKERS AVAILABLE.	\$465.00
KAY ELECTRIC CO., PINE BROOK, N.J.	*MEGA-SWEEP (CAT. #100-A)	50 KC-1000 MC	0-30 MC	MC. ALSO EXTERNAL	LINEAR SWEEP. SWEEP RATE ADJUSTABLE 50-100 CPS. SAW TOOTH SWEEP OUTPUT FOR SYNCHRONIZING OSCILLOSCOPE. OUTPUT, 0.1 V.	

\*OTHER MODELS AVAILABLE.

## SWEEP GENERATORS (CONT'D)

MANUFACTURER	MODEL	FREQUENCY RANGE	SWEEP WIDTH RANGE	MARKER FACILITIES	OTHER FEATURES	PRICE
PHILCO CORP., ACCESSORY DIV., "A" & ALLEGHANY AVES., PHILA. 34, PENNA.	7008	4-120 MC. 145-260 MC	0-15 MC	3.2-250 MC	LINEAR SWEEP. COMBINATION UNIT INCLUDES OSCILLOSCOPE. OUTPUT, 0.5 V.	\$466.00
PRECISION APPARATUS CO., INC., 92-27 HORACE HARDING BLVD., ELMHURST, N.Y.	G8002	470-890 MC	TO 25 MC AT LOW END; TO 30 MC AT HIGH END.	ACCOMMODATES 4.5-WITCH- 0.1 MC (NARROW BAND), 0.15 MC (WIDE BAND).	LINEAR SWEEP. PHASING CONTROL RANGE 140 DEGREES. RETURN TRACE BLANKING SWITCH. MINIMUM OUTPUT, 1 V (PEAK-TO-PEAK).	\$289.50
RADIO CORP. OF AMERICA, HARRISON, N.J.	WR-59C	2-240 MC (FUNDAMENTALS), 240-480 MC (HARMONICS).	0-12 MC OR BETTER	SELECTED EXT. CRYSTALS.	PHASING CONTROL. RETURN TRACE BLANKING. 2-MC & 4.5-MC CRYSTALS IN- CLUDED. CRYSTAL CALIBRATED.	\$139.75
SIMPSON ELECTRIC CO., 5200 W. KINZIE ST., CHICAGO 44, ILL.	479	300 KC-50 MC. SWITCH SELECTION OF VHF CHANNELS: 34-88 MC; 174-216 MC.	0-15 MC	3.3-250 MC, INPJT FOR CRYSTAL	LINEAR OUTPUT. PHASING CONTROL RANGE, 160 DEGREES. RETURN TRACE BLANKING CONTROL.	\$274.50
SYLVANIA ELECTRIC PRODUCTS, INC., 234 RANO ST., BUFFALO, N.Y.	500	2-230 MC	0-600 KC (FM) 0-15 MC (IV)	400-930 MC	PHASING CONTROL. RETURN TRACE BLANKING CONTROL. 400 CPS MODULATION OF R-F GENERATOR AVAILABLE AT 30%. ACCURACY 0.1% WHEN CALIBRATED WITH 5-MC CRYSTAL. DIAL ALSO MARKED IN HARMONICS FOR UHF USE.	\$325.00
TELEON INDUSTRIES, 444 S. RURAL ST., INDIANAPOLIS, IND.	*SM-2	375-950 MC	0-75 MC		LINEAR SWEEP. PHASING CONTROL. MAXIMUM OUTPUT 0.1 V. SWEEP OUTPUT FOR SYNCHRONIZING OSCILLOSCOPE.	\$139.50
TRIPLETT ELECTRICAL INSTR. CO., BLUFFTON, OHIO	3434-A	0-240 MC	0-12 MC	FUNDAMENTALS: 3.5-4.9 MC 19.5-48.6 MC; HARMONICS: UP TO 241 MC. ALSO EXTER- NAL	PHASING CONTROL. MARKER AMPLITUDE CONTROL. 600 CPS MODULATION AVAIL- ABLE FOR R-F GENERATOR SECTION, OR AS SEPARATE AUDIO. SWEEP OUTPUT FOR SYNCHRONIZING OSCILLOSCOPE. OUTPUT OVER 1 V. CHOICE OF ABSORPTION OR PIP-TYPE MARKERS. DIAL MARKERS AVAILABLE.	\$450.00
WESTON ELECTRICAL INSTR., 614 FREILINGHUYSEN AVE., NEWARK 5, N.J.	3435	0-240 MC	0-12 MC	EXTERNAL	PHASING CONTROL. SWEEP OUTPUT FOR SYNCHRONIZING OSCILLOSCOPE.	\$114.50
	984	13-POSITIONS, PRE-SET. ONE POSITION (VARIABLE TO 50 MC) FOR I-F; OTHER POSITIONS FOR 12 VHF CHANNELS & 2 FOR FM.	0-10 MC		LINEAR SWEEP. PHASING CONTROL RANGE, 165 DEGREES. OUTPUT TO 0.1 V. RETURN TRACE BLANKING SWITCH.	\$199.50

\*OTHER MODELS AVAILABLE.

## TUBE CHECKERS

MANUFACTURER	MODEL	COUNTER OR PORTABLE MODEL	DOES TESTER CHECK DYNAMIC MUTUAL CONDUCTANCE	SPECIAL FEATURES	NOTES	PRICE
AMERICAN SCIENTIFIC DEVELOPMENT CO., 334-336 S. MAIN ST., FT. ATKINSON, WIS.	TV-20	PORTABLE	YES	GAS DETECTION CIRCUIT		\$124.50
ELECTRONIC INSTRUMENT CO., INC., 84 WITHERS ST., BROOKLYN 11, N.Y.	625	PORTABLE	NO	SPARE BLANK SOCKET PROVIDED FOR FUTURE TUBE TYPES	KIT WITH COUNTER DISPLAY CASE, \$44.95; FACTORY-WIRED, \$19.95	\$ 24.90
ELECTRONIC MEASUREMENTS CORP., 280 LAFAYETTE ST., N. Y. 12, N.Y.	208	PORTABLE	NO	MATCHES AND CHECKS H1-F1 TUBES SUCH AS 1614, KT66 AND 5881		\$ 83.50
HEATH COMPANY, MICHIGAN BENTON HARBOR,	206*	PORTABLE	YES	TESTS TUBES FOR GAS, NOISE	AVAILABLE WITH SLOPING COUNTER CASE AT \$79.50	\$ 29.50
HICKOK ELECTRICAL INSTRUMENT CO., 10514 DUPONT AVE., CLEVELAND 8, OHIO	TC-2*	COUNTER	NO	SPARE BLANK SOCKET PROVIDED FOR FUTURE TUBE TYPES	PORTABLE MODEL, \$34.50	\$164.00
JACKSON ELECTRICAL INSTRUMENT CO., DAYTON, OHIO	600A	PORTABLE	YES	CONTAINS BIAS POTENTIOMETER	MODEL 605A OFFERS SAME FEATURES, BUT CONTAINS MULTIMETER IN ADDITION. UNIT MEASURES CAPACITANCE-INDUCTANCE. PRICE, \$189.50	\$185.80
	533AC*	COUNTER	YES	TESTS TUBES FOR NOISE, GAS, LIFE EXPECTANCY	AVAILABLE IN PORTABLE MODEL, SAME PRICE	\$ 79.50
	715	PORTABLE	YES	PROVIDES C-R TUBE TEST; SPARE SOCKETS, CIRCUITS FOR FUTURE USE		\$104.50
PHILCO CORP., ACCESSORY DIV., PHILA, PA.	468	PORTABLE	YES	TESTS TUBES FOR LIFE EXPECTANCY; PROVIDES SIM- PLIFIED OPERATION VIA "SEQUENCE SWITCH"		\$187.50
PRECISION APPARATUS CO., INC., 92-27 HORACE HARDING BLVD., ELMHURST, N.Y.	7052	COUNTER	YES	TESTS TUBES FOR LIFE EXPECTANCY	WITH MULTIMETER, \$139.50	\$189.50
RADIO CITY PRODUCTS CO., INC., 152 WEST 25TH ST., N. Y. 1, N.Y.	9100	PORTABLE	YES	TESTS TUBES FOR LIFE EXPECTANCY	WITH MULTIMETER, \$107.00	\$ 76.75
SIMPSON ELECTRIC CO., 5200 W. KINZIE ST., CHICAGO 44, ILL.	SERIES 10-12P SERIES 612*	PORTABLE	NO	HIGH SPEED ROLLER CHART, EXTRACTOR FUSE POST	COMBINATION PORTABLE-COUNTER MODEL, \$79.50	\$ 99.95
SUPERIOR INSTRUMENTS CO., 2435-41 WHITE PLAINS RD., N. Y. 67, N.Y.	324	PORTABLE	NO	PROVIDES NOISE AND CONDENSER TESTS		\$ 135.00
SYLVANIA ELECTRIC PRODUCTS, INC., 254 RANO ST., BUFFALO, N.Y.	808A*	PORTABLE	NO	PROVIDES OHMMETER, C-R TUBE REACTIVATOR, VIVIM. TESTS CRT FOR SHORTS, LEAKS		\$ 47.50
TRIPLETT ELECTRICAL INSTRUMENT CO., BLUFFTON, OHIO	1000	PORTABLE	TESTS DYNAMIC PLATE CON- DUCTANCE, WHICH IS RELATED TO MUTUAL CONDUCTANCE	TESTS OHMMETER, C-R TUBE REACTIVATOR, VIVIM. TESTS CRT FOR SHORTS, LEAKS	COUNTER-TYPE TESTER 219 HAS SAME CHARACTER- ISTICS AND PRICE AS THE 220	\$114.50
WESTON ELECTRICAL INSTR. CORP., 614 FREILINGHUYSEN AVE., NEWARK, N.J.	TV-11	PORTABLE	NO	CHECKS CONDENSER LEAKAGE		\$ 79.50
	220	PORTABLE	YES	NEW SETTINGS REGULARLY PUBLISHED IN "SYLVANIA NEWS" CAN BE READILY RECORDED ON ROLLER CHART	TESTS TUBES USED IN RADIO-TV, INDUSTRIAL PRODUC- TION, THEATER, P.A. SYSTEMS & COMMUNICATIONS	\$199.50
	3413-A	PORTABLE	NO	PROVIDES ADAPTER FOR TESTING C-R TUBES		\$199.50
	3423	PORTABLE	TESTS PROPORTIONAL MUTUAL CONDUCTANCE	H-F SIGNAL IS APPLIED TO GRID OF TUBE, OUTPUT SIGNAL IS MEASURED	TESTS VOLTAGE REGULATOR AND SUBMINIATURE TYPE TUBES	\$199.50
	981	PORTABLE	TESTS PROPORTIONAL MUTUAL CONDUCTANCE	PROVIDES METER MEASUREMENT OF HIGH LEAKAGE RESISTANCE BETWEEN TUBE ELEMENTS		\$199.50

\*OTHER MODELS AVAILABLE.

A new  
dimension  
in price and  
performance

**WALSCO**

**Scotty**

**377**

LIST

GUARANTEED FOR 1 YEAR

**Greatest Antenna  
Value in America**


The new "Scotty" has every quality feature necessary for crystal-clear reception in metropolitan and suburban areas. Good gain and directivity on all VHF channels. Used effectively for UHF, or as a combination antenna. Tested and approved for color reception.

**COMPARE**

<b>WALSCO "Scotty"</b>	<b>3.77</b>
Antenna B	7.50
Antenna C	4.86
Antenna D	5.40
Antenna E	4.60


Place your order today

Easily  
stacked for  
semi-fringe  
reception

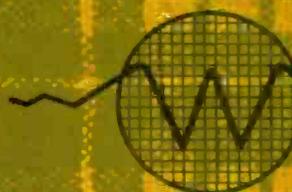 **Walseo**  
ELECTRONICS CORPORATION

3602 Crenshaw Boulevard, Los Angeles 36, California

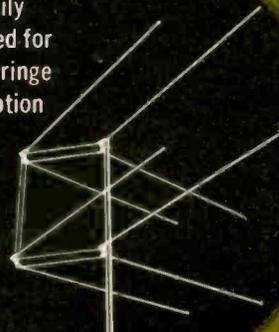Exclusive Distributor:  
E. J. AD AURICENA, Inc., 89 Broad St., New York 4, N.Y.




# New Antennas

## TV Types & Installation Items; Converters & Connectors
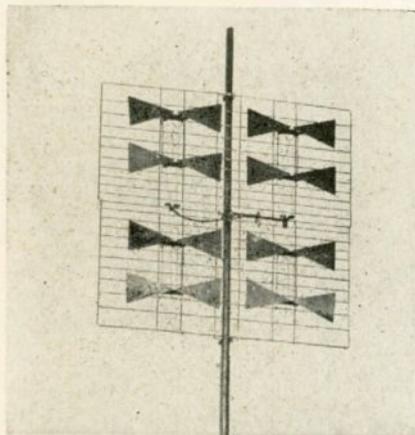
### Channel Master UHF ANTENNA

The Twin Multi-Bow, model 410-8, is an 8-bow bow tie with screen. The large screen contributes to the




antenna's gain, said to range from 12½ to 16½ db. It also provides high front-to-back ratio. List price, \$20.83. Channel Master Corp., Ellenville, N. Y.—TECHNICIAN

### Danforth VHF ANTENNA

The Mountie, model 38, is a yagi-type 5-element antenna made with rugged boom and elements for durability. Field tests 110 miles from transmitters are said to show good performance on all 12 VHF channels. Danforth Mfg. Co., Monmouth, Ill.—TECHNICIAN
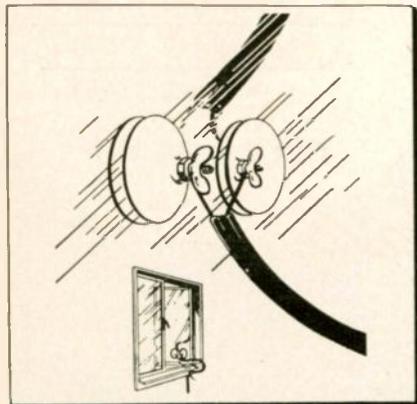
### Walsco WINDOW CONNECTOR

Window-Thru bushing allows servicemen to bring antenna wires into a home without drilling holes. The durable bushing attaches to




any window in a few minutes, is effective for VHF and UHF. Weatherproof capacitor discs attach to the window pane; windows can be

opened and closed without breaking wires. Packaged with window-pane cement and instructions. List price, 99 cents. Walsco Electronics Corp., 3602 Crenshaw Blvd., Los Angeles 36, Calif.—TECHNICIAN
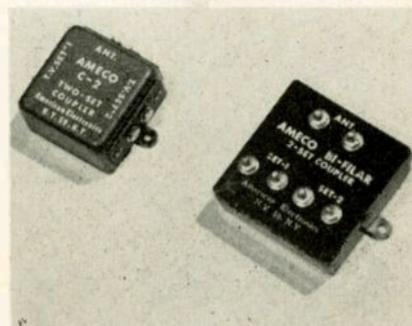
### Ameco ANTENNA COUPLERS

Two 2-set couplers operate 2 receivers from 1 antenna while retaining impedance match and avoiding mutual interference. Model C-2, \$1.84 list; model C-2B (bi-filar wound for low insertion loss), \$3.30 list.

Two antenna crossover networks permit joining UHF and VHF antennas to a single transmission line. One model is for 2 antennas (1 UHF, 1 VHF); another model is for



3 antennas (1 UHF, 1 VHF low-band, 1 VHF high-band). Model UV-2 (double-tie), \$3.25 list; model UV-3 (triple-tie), \$3.85 list.

Also available: "Thru-Window" coupler for passing antenna signal into house without drilling holes. List price, \$1.48. American Electronics Co., 1203 Bryant Ave., New York 59, N. Y.—TECHNICIAN

### GI HIDDEN UHF CONVERTER

The Tuck-A-Way, a low-cost all-channel UHF converter, can be installed behind, on either side or on top of the TV set. Dial and switch are positioned on top, making them accessible in any position. Continuous tuning covers channels 14-83. General Instrument Corp., 829 Newark Ave., Elizabeth 3, N.J.—TECHNICIAN


### Granco UHF CONVERTER

Model LCU-A features high-ratio finger-tip tuning, slide-rule tuning dial, two-cavity coaxial tuner to cover the UHF band continuously with a low noise figure, stability and

signal amplification. Offered at \$29.95 list (mahogany) and \$32.95 (blond). Granco Products Inc., 36-17 20 Avenue, L. I. City 5, N.Y.—TECHNICIAN
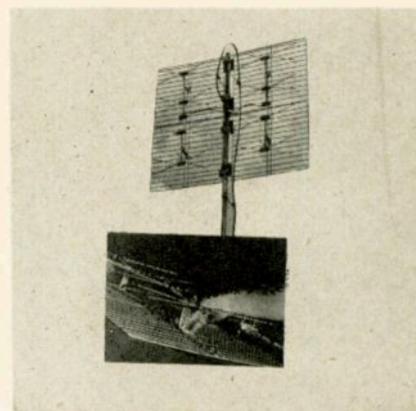
### JFD UHF ANTENNA


This new high-gain 8-bow antenna with screen features an ad-



justable calibrated slide for peaking of any one or any group of UHF channels. The pre-assembled unit is said to have a sharp directivity pattern with 18 db of back rejection. Model UHF-308 lists for \$25.95. JFD Mfg. Co., 6101 16th Ave., Brooklyn 4, N. Y.—TECHNICIAN
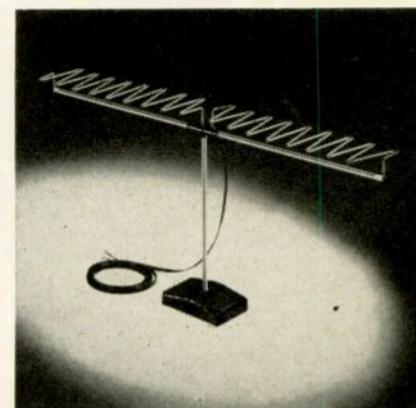
### Peerless INDOOR ANTENNA

The Diron Golden Wand is designed for operation on all VHF and FM channels without individual adjustment for different frequencies, includes 12 ft. of 300-ohm twin lead.



Available in gold finish, model DV11G, or black, model DV11B. List price, \$9.95. Peerless Products Industries, 812 Pulaski Rd., Chicago 51, Ill.—TECHNICIAN



Once again  
we're taking television  
out of the  
knothole class...

From a knothole—to a box seat . . . That was Du Mont's big contribution to black and white television . . . Now, again, Du Mont leads the way in practical, big-screen color television.

Out of Du Mont cathode-ray tube research comes the dramatic Chroma-sync Teletron . . . a bigger-screen, shorter-length, lower-cost color picture tube featuring electrostatic "Mono-Convergence".

**DU MONT<sup>®</sup>**  
**CHROMA-SYNC**

*Teletrons\**

**FEATURING**  
**"MONO-CONVERGENCE"**


**ALLEN B. DU MONT LABORATORIES, INC.**

\*T.M.

Cathode-ray Tube Division • 750 Bloomfield Avenue • Clifton, N.J.


# "Tough Dog" Corner
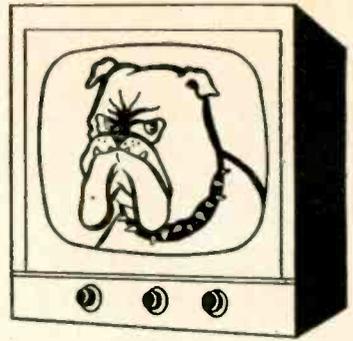
## Difficult Service Jobs Described by Readers


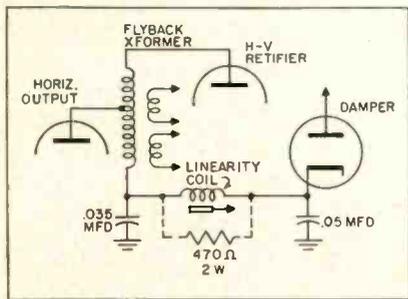
### Double Trouble

This set came into our shop with the customer's complaint that it would break out every so often into a double picture horizontally. When the set broke down in the shop after a half hour wait, I noticed an effect similar to that of a ghost. However, with no video present, the same effect could be seen on the raster. There appeared to be two rasters present, one displaced from the other by about one inch. With video present, the horizontal hold control showed normal action. What made matters tough was that, when an effort was made to troubleshoot, the



set snapped back to normal. Introduction of a probe apparently disturbed the fault. There was then another long wait for the set to break down again.

The next time the set broke down, I used hand capacity near the horizontal oscillator circuit. The set again returned to normal. After considerable probing, it was found that the most sensitive area was in the vicinity of the horizontal linearity coil. The two capacitors connected to this coil (0.035 mfd and 0.05 mfd) were checked on a condenser bridge and found to be good. This left the coil itself, which we felt must be setting up some kind of parasitic oscillation. A 470-ohm, 2-watt resistor was shunted across the coil to load it down. The set then operated normally for a long test period; then was delivered to the customer. There have been no call-backs.—*Joseph F. Valenti, Bronx, N. Y.*

### B & W Pix OK, No Color

Here is an early Tough-Dog case on a color TV receiver. After we received our first RCA CT100 color set, we enjoyed beautiful color reception

for about a month. Then one day we turned the set on (during a color program) to get a beautiful monochrome picture, but no color. Frantically we began to change tubes in the color section of the receiver, but to no avail. Before we could progress any further, the 15-minute color broadcast was over. During subsequent color programs, we checked voltages and undertook other troubleshooting, but could find no defect.

When we finally got in our color bar generator, we hooked it up to the set and, to our surprise, got excellent results. We saw the full range of color bars, as specified in the instruction manual. The set's hue control had normal range. After a few days of thinking it over, the right idea finally popped up. The day before the defect was first noted, there had been some moving around of sets and antenna wires in the showroom where the color receiver was located. The belief that the difficulty was due to trouble in the antenna system was supported by the presence of colored snow off channel.

The next time a color program was on, the trouble was located. It turned out to be a trap in our master antenna system which was tuned to eliminate Channel-5 interference from Channel 4, a problem which is common in our area. In the process of moving around, someone had nailed the trap to the wall. This apparently detuned the trap enough to kill the color subcarrier for Channel 4 without noticeably affecting monochrome video signal. When the trap was removed, color came back perfectly.—*Donald E. Tucker, Washington, D.C.*


### \$ For Your "Tough Dog Story"

Have you tangled with a difficult or obscure service problem recently? Write it up, telling us how you licked it, and send it to "Tough Dog" Editor, **TECHNICIAN**, Caldwell-Clements, Inc., 480 Lexington Ave., New York 17, N.Y. \$10 will be paid for usable material. Unacceptable items will be returned to the contributor.
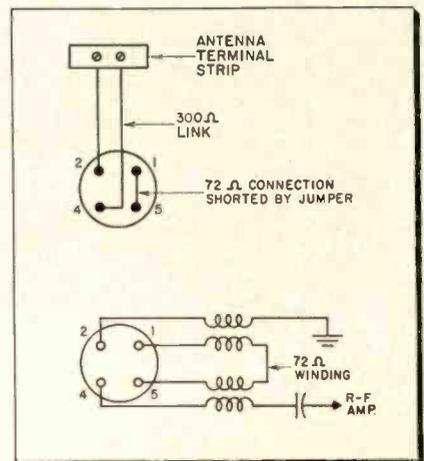
### Open Winding, Weak RF

The favorite expression customers use is, "There must just be a wire loose in the set." How right they were on this one!

An RCA 6-T-53 came in with a very snowy and indistinct picture. Used with rabbit ears, it was unusually sensitive as to position of the aerial. A complete check of tubes and voltages showed nothing abnormal. On our outside antenna in the shop, Syracuse (some 50 miles away) came in very poorly; the local station showed an excellent picture. The trouble seemed to be in the front end, but where?



The antenna matching unit shows provision for both 72-ohm and 300-ohm lines. You will note on the diagram that the winding for a 72-ohm input, connected between points 1 and 5, is shorted out when the 300-ohm input is used. However—and here is the sticker—both coils are wound together to make up the bifilar matching transformer. With one side of the 72-ohm coil open, even though this side was shorted out by the jumper on the connector, the wrong impedance was reflected back into the 300-ohm winding. Hence, a mismatch was created.

When this one little open wire was connected—bango—normal reception returned.—*Stanley T. Curtis, Utica, New York*

# NOW AT LAST...

## A Reliable, General-Purpose 5" OSCILLOSCOPE

Priced  
at Only \$127.50



### The NEW **PRECISION** MODEL **ES-520**

The new ES-520 is **PRECISION**-engineered in response to long and growing demand for a reliable, factory-made, general purpose 'scope at a price within reach of all to whom initial investment is of extreme importance.

The ES-520 conforms to every **PRECISION** standard of quality, workmanship and performance. It is a completely factory-engineered, factory-wired and factory-calibrated instrument . . . ready to go to work for you the moment you take it out of its carton!

#### SPECIFICATIONS

- ★ Push-Pull vertical drive. 20 millivolts per inch sensitivity.
- ★ 3-Step, frequency-compensated, vertical input attenuator.
- ★ Vertical frequency response 20 cycles to 500 KC within 2 DB
- ★ 1 volt, peak-to-peak, built-in vertical voltage calibrator.
- ★ Excellent vertical square wave response from 20 cycles to 50 KC.
- ★ Push-pull horizontal drive. 50 millivolts per inch sensitivity.
- ★ 'H' frequency response 20 cps to 200 KC within 3 DB (at full gain).
- ★ Internal linear sweep 10 cycles to 30 KC. Neg. and pos. sweep synch.
- ★ Tube Complement: 12AU7 'V' cathode follower and amplifier, 6C4 phase-splitter, 12AZ7 push-pull 'V' drive. 6AB4 'H' amplifier, 12AZ7 push-pull 'H' drive. 12AU7 sweep oscillator. 6X4 rectifier, 1V2 high potential rectifier, NE-51 calibration regulator, 5U1 CR tube.
- ★ Built-in 60 cycle sine-sweep phasing control.
- ★ Beam modulation input terminal at front of panel.
- ★ All 4 deflection plates directly accessible at rear.
- ★ Filter-type, removable, calibrated graph-screen.
- ★ Etched, anodized, heavy gauge aluminum panel.

**SERIES ES-520:** In black ripple finished, rugged steel cabinet, 8¼ x 14½ x 16½". Complete with all tubes, including 5U1 CR tube. Comprehensive instruction manual. Code: Quest. Shipping weight: 30 lbs. Net Price: \$127.50.

...and STILL THE LEADER IN ITS FIELD  
for performance, versatility and value —

the popular **PRECISION**

**ES-500A**

HIGH SENSITIVITY  
WIDE-RANGE  
5" OSCILLOSCOPE



The famous ES-500A incorporates advanced engineering features and refinements so necessary to meet the more critical needs of modern electronic circuit analysis, AM, FM and TV.

**SERIES ES-500A:** in louvered, black ripple-finished, heavy gauge steel case, 8¼ x 14½ x 18". Complete with removable light shield, calibrating mask and detailed instruction manual. Net Price: \$173.70



**PRECISION Apparatus Company, Inc.**

92-27 HORACE HARDING BLVD., ELMHURST 6, N. Y.


Export Division: 458 Broadway, New York 13, U.S.A. Cables: Morhanex  
Canada: Atlas Radio Corp., Ltd., 560 King Street W., Toronto 2B

# New Tubes & Accessories

## CRTs, TV Types, Tester, Carton & Ventilated Shield
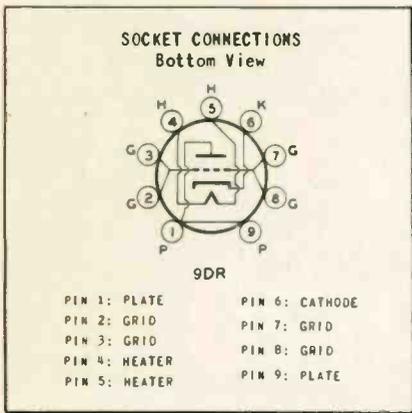
### RCA UHF TRIODE

Medium-mu triode of the 9-pin, short-bulb miniature type, the 6BC4, is designed for use as r-f amplifier in cathode-drive circuits



of UHF tuners. Features high gain, low noise and good isolation within the tube between input and load circuits. Tube Department, Radio Corp. of America, Harrison, N. J.—TECHNICIAN

### GE TUBE CARTON

Newly designed container completely suspends the tube within its carton. An inner cardboard sleeve, built into the box, improves cushioning and protection. Container



now being used for all GE tubes. General Electric, Electronics Park, Syracuse, N. Y.—TECHNICIAN

### Sheldon ALUMINIZED CRTs

New 10-, 12- and 20-in. aluminumized pix tubes complete the manufacturer's line of aluminum crt's from 10-in. to 27-in. sizes. Added types include 10BP4C, 10BP4D, 12ZP4, 12ZP4A, 20CP4B and

20CP4D. The last 2 are said to be only ones in that size available in aluminized versions. Sheldon Electric Co., Irvington 11, N. J.—TECHNICIAN

### CBS HEAVY-DUTY TUBES

Three ruggedized horizontal-output tubes, 6CU6, 12CU6, and 25CU6, are high-rated equivalents of the 6BQ6-GT, 12BQ6-GT, and 25BQ6-GT. Electrical characteristics and socket-pin arrangements follow those of the prototypes, but the new tubes are said to provide longer life, withstand higher pulse voltages and momentary overloads. CBS-Hytron, Danvers, Mass.—TECHNICIAN

### Sylvania 21ATP4

New 21-in. rectangular glass-shell crt features filter glass spherical faceplate, aluminized screen, electrostatic focus, magnetic deflection and external conductive coating. Shorter neck length (20% in.) is due to use of 90-degree deflection angle. Picture area: 263 sq. in. Typical voltages: 2nd-anode—16 kv; grid no. 2—300 v. Picture Tube Div., Sylvania Electric Products, Inc., Seneca Falls, N. Y.—TECHNICIAN

### Precise TRANSISTOR KIT


Kit model T1 includes equipment (transistors, transformers, coils, etc.) necessary for the purchaser to acquire basic transistor knowledge through experimental and practical use. Audio one-stage amplifiers, transformer-coupled amplifiers and other circuits are covered in the instruction book, along with the physics of transistors and applications. Price, \$17.95. Precise Development Corp., Oceanside, L. I., N. Y.—TECHNICIAN

### Raytheon 17AVP4

Four lbs. lighter than conventional 17-in. monochrome crt's and 3/8 in. shorter due to use of 90-degree deflection angle, type 17AVP4 is designed for use in new-type compact TV designs. Uses electrostatic focus, magnetic deflection. Typical 2nd-anode voltage, 12 kv. Receiving Tube Div., Raytheon Mfg. Co., 55 Chapel St., Newton 58, Mass.—TECHNICIAN
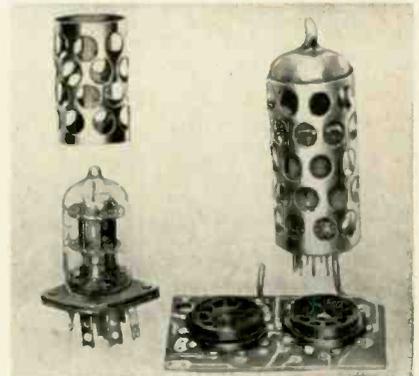
### Methode VENTED TUBE SHIELD

Ventilator shields improve "hot" tube performance by dissipating heat; are easily handled and com-



pression fitted to ground terminals on laminated or printed circuit sockets. Available in lengths of 1 11/16 in. or 2 1/16 in. with one standard diameter to fit either 7- or 9-pin tubes; tin or black oxide finish. Methode Mfg. Corp., 2021 W. Churchill St., Chicago Ill.—TECHNICIAN

### AMS CRT TESTER


Portable cathode-ray tube tester, model 101, is said to provide positive indication within 90 seconds for continuity and emission. Three neon indicators and a meter provide facilities for testing of open connections, shorted elements, leakage, cathode



emission and indication of gaseous tubes. Tests can be made with crt in carton, TV set, cabinet or on the bench. Weight: 5 1/2 lbs. Authorized Manufacturers Service Co., 919 Wyckoff Avenue, Brooklyn, New York—TECHNICIAN

# Great Antennas by **FINCO**<sup>®</sup>

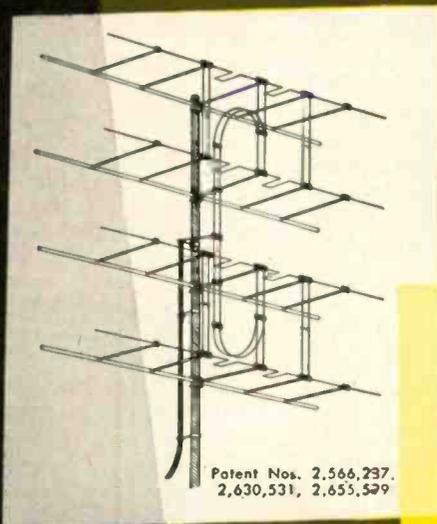
**DESIGNERS AND PATENT HOLDERS OF THE WORLD'S MOST ADVANCED ANTENNA PRINCIPLES . . . . .**



Patent Nos. 2,566,237,  
2,630,531, 2,655,529
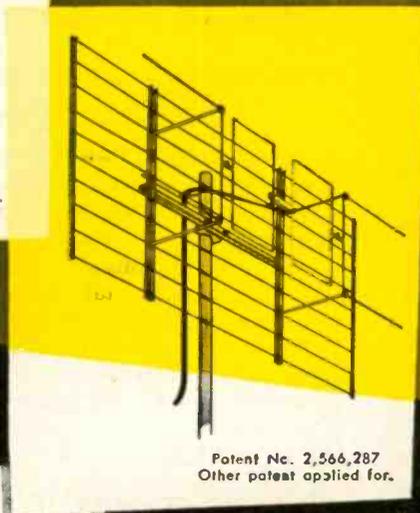
## **FINCO 400-A UHF-VHF**

The acknowledged leader in the fringe area market — Perfect pictures, all channels 2 to 83, up to 150 miles and MORE from station. Protected by exclusive electronic and mechanical patents.



Patent No. 2,566,287  
Other patent applied for.

## **FINCO 500 Series UHF**

Consistently out-performs all others on entire UHF band — in close to the station and in the super-fringe. Very high gain and narrow pattern for complete elimination of ghosts.

**The FINNEY COMPANY**

### **THE FINNEY COMPANY**

Dept. T-84 • 4612 St. Clair Avenue • Cleveland 3, Ohio

WRITE FOR COMPLETE INFORMATION ON THESE VERY PROFITABLE ANTENNAS

- information on the 400-A
- information on the new "500" series UHF antennas
- information on advertising program

NAME .....

COMPANY NAME .....

ADDRESS .....

CITY ..... ZONE ..... STATE .....

**LIFE**

**RADIO • TV**

**NEWSPAPER • FARM PAPERS**

OFFERING YOU THE MOST POWERFUL NATIONAL ADVERTISING PROGRAM IN THE INDUSTRY... a program in which you can participate at no cost! A program that has been so very successful with jobbers and dealers and servicemen all over the nation!

Copyright, The Finney Company, 1953

# New Test Instruments

## Meters & Other Circuit Testers; Instrument Accessories

### IDL RESISTANCE CHECKER

Meterless operation is featured in model R-10 Signa-Glow, which uses null-indicating pilot bulbs incorporated in a Wheatstone bridge circuit to measure resistances from 5 ohms to 50 meg. Requiring no calibration or re-calibration, the instrument operates from normal ac line current. A 3-position multiplier switch provides following ranges: Scale reading x.01, x1 and x100. Manufacturer states the tester is more durable, more accurate and



faster to use, because it requires no adjustments, than conventional meters. Industrial Development Laboratories, 17 Pollock Ave., Jersey City 5, N.J.—TECHNICIAN

### Sylvania VTVM

The 302 Polymeter offers a sub-miniature vacuum tube r-f probe, peak-to-peak scale, 7-in. meter movement, lighted scale, a patented linearity circuit, input impedance of 17 megohms, shielded ac and r-f leads, and screw-on connectors. Changes in control arrangement speed switching. These changes include a new selector switch sequence and range switches. Reads peak-to-peak or dc from 200 millivolts to 2,800 volts, ac from 50 mv to 1,000 v, r-f from 100 mv to 300 v (10kc to 300 mc), resistance from .5 ohms to 1,000 megohms and db from -20 to +61.4. The dc range may be extended to 30 kv by using the Type 225 multiplier probe. List price, \$129.50. Sylvania Electric Products, Inc., 1221 West Third Street, Williamsport, Penna.—TECHNICIAN

### Precision V-O-M

20,000 ohms per volt on dc, 5,000 ohms per volt on ac are features of model 120. 44 self-contained ranges include an extra-low resistance range (2-ohm center scale); an extra-low voltage range (1.2 v full scale) on both ac and dc; and an extended low dc current range (0-60 microamperes). Direct ac or dc voltage readings to 6,000 v; dc current to 12 amp; resistance to 20 meg. Price, including batteries, test leads and manual: \$39.95 net. Precision Apparatus Co., 92-27 Horace Harding Blvd., Elmhurst, Long Island, N. Y.—TECHNICIAN

### RCP V-O-M

Model 480 AC-DC Multitester has 1000 ohms-per-volt sensitivity for all dc measurements. Operating features include circuit and range selection by means of both selector switch and jacks, providing protection against burnout and misuse. Meter movement is built to withstand overloads. Radio City Products Co., Inc., Easton, Penna.—TECHNICIAN

### Simpson COLOR ADAPTERS

New color adapter cable (Chromatic Probe) and booster amplifier are available for alignment and adjustment of color TV sets. They are externally used accessories for either the model 480 Genescope or model 479 AM-FM signal generator. These accessories quickly convert monochrome sweep marker systems to chromatic systems. Price of chromatic probe is \$9.95; booster amplifier is \$24.95. Simpson Electric Co., 5200 W. Kinzie St., Chicago 44, Ill.—TECHNICIAN

### EICO PEAK-TO-PEAK VTVM

Model 232 peak-to-peak vtm includes the new dual-purpose ac-dc Uni-Probe. A half-turn of probe tip selects dc or ac-ohms. Features: stable push-pull bridge circuit, unaffected by voltage variation; reads peak-to-peak voltage of complex and sine waveforms, reads rms voltage of sine waves, dc voltage and resistance; center-scale zero adjustment for alignment. Specifications: dc or ac, to 1500 v in 7 ranges ( $\pm 3\%$  accuracy); peak-to-peak, to

4200 v in 7 ranges. Response from 30 cps to 3 mc (to 250 mc with r-f probe),  $\pm 5\%$ . Resistance to 1000 meg in 7 ranges, accuracy  $\pm 3\%$ . Model 232-K, kit, sells for \$29.95; factory wired, \$49.95. EICO, 84 Withers St., Brooklyn, N. Y.—TECHNICIAN

### Crest SCOPE CRT BOOSTER

Designed to improve the emission of weak cathode-ray tubes used in test oscilloscopes, this rejuvenator is of open frame construction, and may be mounted to the scope either internally or externally. Crest Laboratories, Inc., 84-11 Rockaway Beach Blvd., Rockaway Beach 93, N.Y.—TECHNICIAN

### Eby MULTIPLE TESTER

Pocket-size tester, model A1000, is said to combine functions of several instruments. Some uses: low or high ac or dc voltage measurements, signal tracer, audio oscillator, condenser checker, age substitution



voltage supply, continuity checker. Complete with instructions, \$5.95. Eby Sales Co., 130 Lafayette St., New York 13, N. Y.—TECHNICIAN

### Scala 2-WAY PROBE

As a direct probe, the Scala BZ-5 is designed for general troubleshooting. A flip of the switch converts it into a resistive isolating probe for visual alignment. The latter arrangement (low-pass filter) sharpens up alignment markers and cleans up noisy response curves. Scala Radio Co., 2814 19th St., San Francisco, Calif.—TECHNICIAN

# Industry Keyhole

**RADIO RECEPTER CO.** has changed the name of one of its divisions. The Seletron & Germanium Div. is now being called the Semi-Conductor Div. . . . **GRANCO PRODUCTS**, of Long Island City, N. Y., mfrs of UHF converters, have opened a new plant annex right beside the original building. Production facilities are now more than doubled. Move was made necessary by brisk sale in converters and recent entry into the test-equipment field with announcement of a UHF signal-gain generator . . . **RIDER BOOK-DISPLAY RACK** is part of a stepped-up sales campaign in paperbacks for technical readers. The rotating floor-stand merchandiser holds up to 500 books (66 titles), keeps all titles in full view for easy selection.


**TWO HEADS:** Brush Electronics Co., 3405 Perkins Ave., Cleveland 14, Ohio, announces 2 new magnetic heads, one for record and one for reproduce, designed to meet specs of Cinemascope applications. Details from Dept. RT-3 . . . **CORNELL-DUBILIER ELECTRIC CORP.** has new vice prexy. Recent board of directors meeting elected Leslie A. Johnson to that post, also apptd. him as mgr. of new plant in Sanford, N. C. . . . **BENDIX AVIATION CORP.** will make all radios used in 1955 models of Lincoln and Mercury autos. Shipment of the 8-tube sets begins in early fall.

**HAZARD E. REEVES**, prexy of Reeves Soundcraft and Cinerama, is in Europe studying latest continental developments in audio and choosing new sites for Cinerama theatres. Reeves Soundcraft got an Academy Award this spring for developing a magnetic recording system for motion pix use . . . **CBS-COLUMBIA** has a new publications mgr. for its Service Dept. Joseph Roche, who holds the post, held a similar position with Du Mont, is co-author of the Video Handbook and the Radio Data Book . . . **GENERAL CEMENT MFG. CO.**, 919 Taylor Ave., Rockford, Ill., has a new serve-yourself counter display for its tools. Display holds a dozen of each of 49 most popular alignment tools.

**A VARIABLE AUDIO TIME DELAY**, introduced by Kay Electric Co., Pine Brook, N. J., has a variety of applications. The Echo-Vox, as it is called, can be used to time speakers in auditoriums and other large areas so that objectionable echoes are eliminated. On the other hand, the unit can be used to introduce or enhance a desired echo effect . . . **AEROVOX CORP.** of New Bedford, Mass., has put Stanley W. Horrocks in charge of its new Special Products Div. Initial products of the division will be printed wiring and a line of ceramic power and transmitting capacitors.

across the spectrum...

it's TACO that gets 'em!

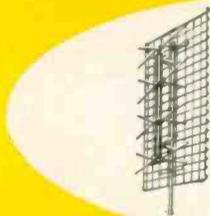


**CAT. NO. 3006C Four-stacked bow-tie**—Receives all UHF channels. Exceptional gain. Fine directivity. Available in many models from single bow-tie to array of 12.



**CAT. NO. 3C15 Grid yagi**—Finest UHF antenna made. Available as single, double or four-stacked array. Excellent front-to-back ratio.


83  
UHF  
14

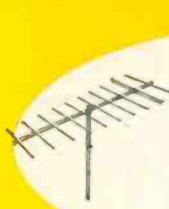

**CAT. NO. 1850 Silver Streak high-band**—Optimum gain and signal-to-noise ratio on any single high-band VHF channel. Recommended for weakest signal areas.




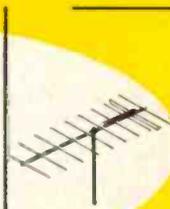**CAT. NO. 1350 5-element yagi high-band**—The best buy among medium-price antennas. Provides excellent gain and directivity on any single high band channel.



**CAT. NO. 1860 Bazooka-Tuned high-band**—Provides yagi gain and directivity throughout entire VHF high band. Bazooka element assures perfect impedance match on all channels.

13  
VHF  
7

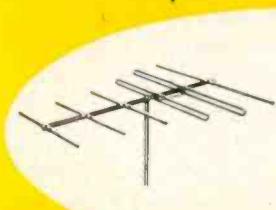


**CAT. NO. 644 Twin-driven FM**—Ideal for fringe areas. Receives entire UHF band with highest signal-to-noise ratio. Sharp directivity. Single or stacked.




**CAT. NO. 6245T Omni-directional**—Perfect circular gain pattern. Receives FM from all directions without mechanical rotating. Single or stacked.

FM

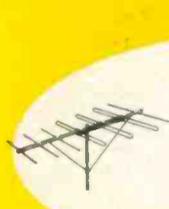

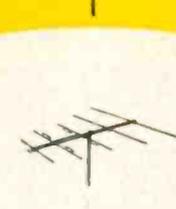**CAT. NO. 1840 Triple-driven yagi**—Single channel yagi characteristics throughout the low-band. Provides maximum signal pickup and gain.



**CAT. NO. 1880 Broad band Trapper**—The most revolutionary TV antenna ever offered. Peak performance on channels 2 through 13. Also UHF in prime service areas.



**CAT. NO. 1325 5-element yagi**—For those installations where price is a "must." Yagi gain and characteristics in a medium priced antenna.

6  
VHF  
2

FOR COMPLETE INFORMATION ON THESE AND OTHER TACO ANTENNAS, ASK FOR YOUR COPY OF THE TACO LOCALIZED CATALOG...

TECHNICAL APPLIANCE CORPORATION, SHERBURNE, N. Y.

In Canada: Hackbusch Electronics, Ltd., Toronto 4, Ont.

# Setting Up Public Address Sound System

(Continued from page 20)

frames should be electrically insulated from those of adjoining speakers; that is to say, no metallic mounting brackets which are common to all speakers should be employed.

Shown in Fig. 6A are typical speaker connections used when matching to a low-impedance tap of the amplifier output transformer. The top circuit represents a simple paging system. The 16-ohm source impedance is properly matched by the 16 ohm impedance presented by the speaker.


The second-from-the-top circuit is for two (or more) loudspeakers in

parallel. When the individual impedances of each speaker connected in parallel is the same, the total impedance is equal to the impedance of any one speaker, divided by the number of speakers. In B, this total

$$\text{or load impedance} = \frac{16}{2} = 8 \text{ ohms.}$$

The next sketch shows two or more speakers in series. The total impedance presented by several speakers in series is obtained by simply adding the individual impedances. In this case, the net or load impedance = 8 ohms + 8 ohms = 16 ohms.

Fig. 6A—Speaker matching to output transformer. B—Correct and incorrect speaker phasing.

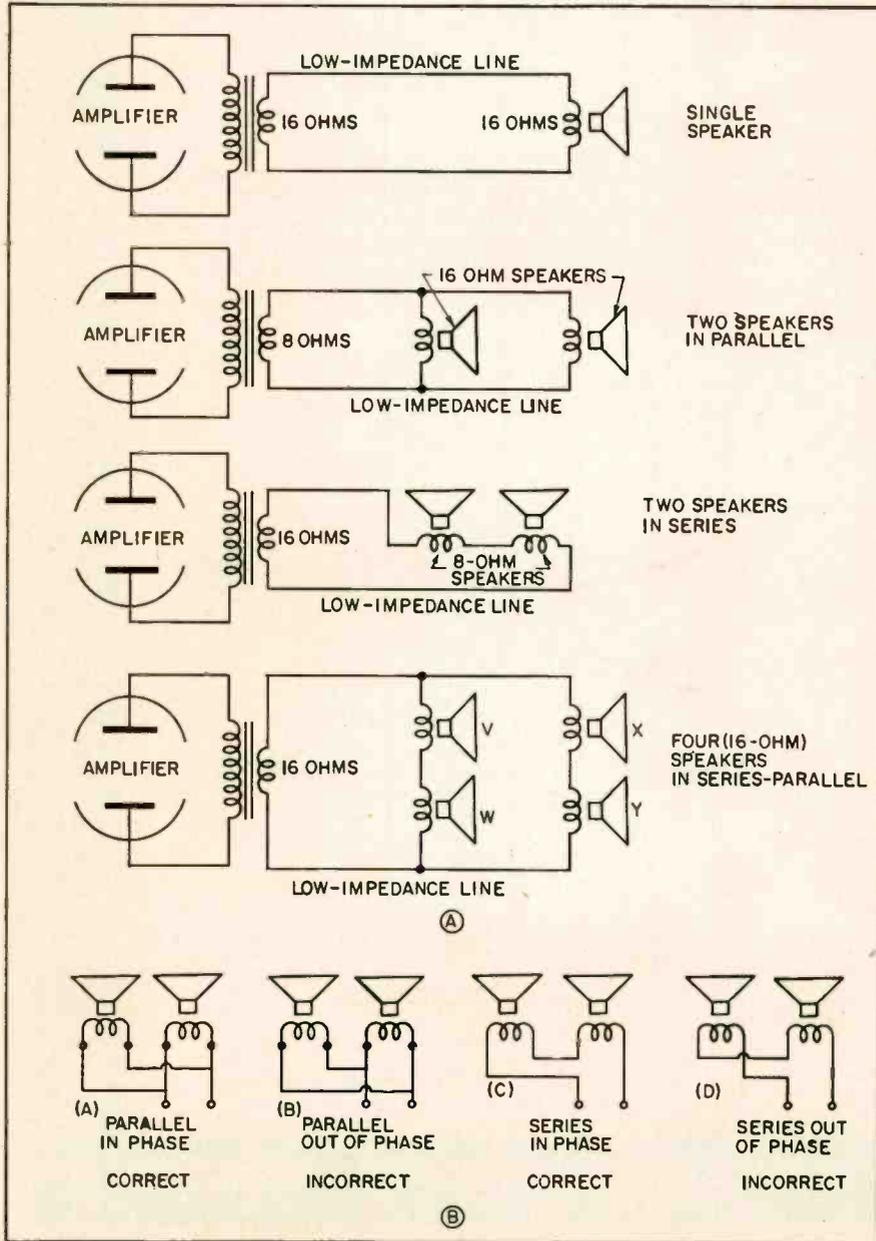

The last sketch shows four speakers in series-parallel. The 32 ohm impedance produced by the series connection of speakers V and W, is in parallel with the 32-ohm impedance of speakers X and Y in series. The overall load therefore equals 16 ohms, and properly matches the 16-ohm secondary of the output transformer.

When two parallel-connected speakers are not of equal impedance, divide the produce of their impedances by the sum of their impedances, to determine the net impedance they will offer. The impedance of a 4 and 16-ohm speaker in parallel would be:

$$\frac{4 \times 16}{4 + 16} = 3.2 \text{ ohms}$$

Where more than two speakers of differing impedance are connected in parallel, add the reciprocals of the individual impedances, and then take the reciprocal of their sum, to obtain the net impedance. The impedance of a 4, 8 and 16-ohm speaker connected in parallel would be worked out as follows:


The sum of the reciprocals of the individual impedances equals  $\frac{1}{4} + \frac{1}{8} + \frac{1}{16} = \frac{7}{16}$ . The reciprocal of this equals  $\frac{16}{7}$ , which equals 2.2 ohms.

## Speaker Phasing

Phasing is concerned with the utilization of two or more loudspeakers in such a way that the sound from any one speaker does not cancel the sound of any other speakers (and create a dead area between both). This is an important consideration where speakers face the same direction. The connection to the voice coil, whether in series or parallel, must be so made that at any one instant, all diaphragms move in or out in unison. For parallel operation, the like terminals of each unit must be connected together; if the speakers are wired in series, two unlike terminals must be used as a junction. Fig. 6B illustrates these connections.

When the time to test out your system arrives, place all necessary microphones where needed and connect them to the amplifier. Determine the control settings and mike placement at which feed-back occurs with each microphone, making a note of this as a reference for you and other operators of the system. Make whatever corrections are required in output and tone control settings and microphone placement. Get comments from various people to help you in determining the success of your installation.

(Continued on page 59)

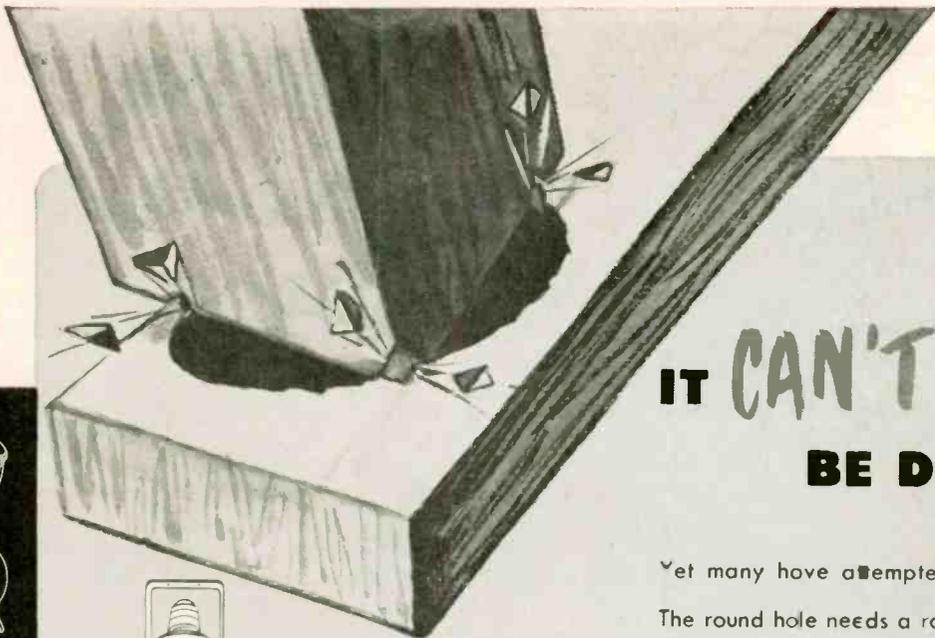


# IT CAN'T BE DONE!

Yet many have attempted to try it.


The round hole needs a round peg—custom-fit to meet the need. In the choice of a speaker, just as in the choice of the peg, the point of application should be the governing factor.

So why waste loudspeaker capacity and amplifier power using the wrong speaker for the job? University makes available over 50 different models of speakers, each designed to meet a particular requirement most efficiently. University loudspeakers are *application engineered* to provide optimum performance with maximum economy—technically and cost-wise.

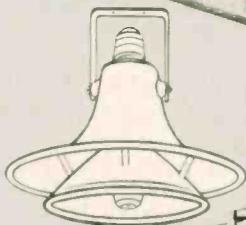
Whether the need is for music or voice, or both—for either indoor or outdoor use: whether in a fixed position in a factory or for mobile use on a vehicle, boat, train or airplane... there's a University speaker that can do the job best. *Don't spend more for more than you need...* CHECK UNIVERSITY FIRST!



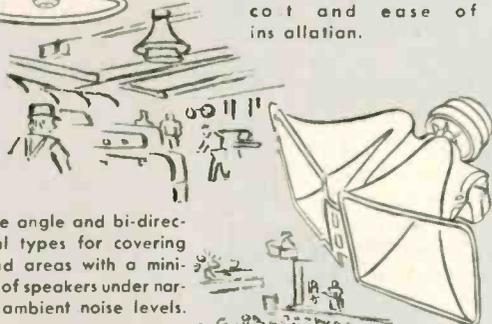Racial type projectors and paging speakers with 360° dispersion for maximum coverage at lowest cost and ease of installation.



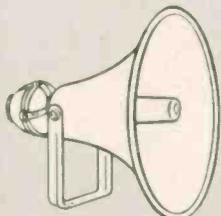Wide angle and bi-directional types for covering broad areas with a minimum of speakers under normal ambient noise levels.




Reflex trumpets in various sizes for incomparable efficiency, distance and noise penetration.



**FREE**—Illustrated copy of the University Technilog • Complete up-to-date manual of sound theory, application and installation requirements • SEND for your copy today.



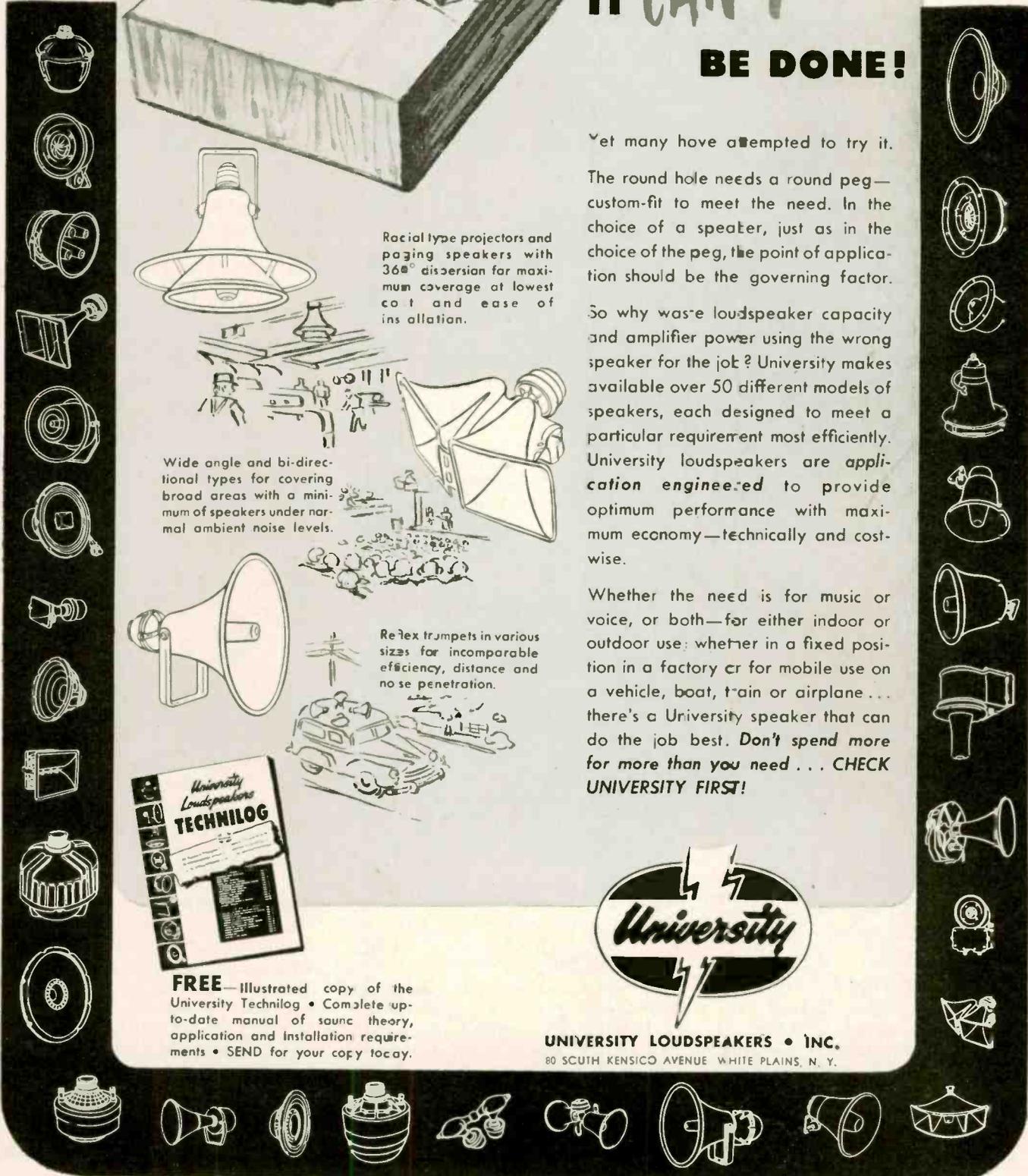UNIVERSITY LOUDSPEAKERS • INC.  
80 SOUTH KENSICO AVENUE WHITE PLAINS, N. Y.



# New Shop Equipment


## Replacement Components; Units for Sales and Service

### Wen **SOLDERING GUN**

Model 199 features light weight, (1½ lbs.), speed (working-hot in 2½ seconds), long reach and long-life tips. Fully guaranteed. Price, \$7.95. Wen Products, Inc., 5808 Northwest Hwy., Chicago 31, Ill.—TECHNICIAN
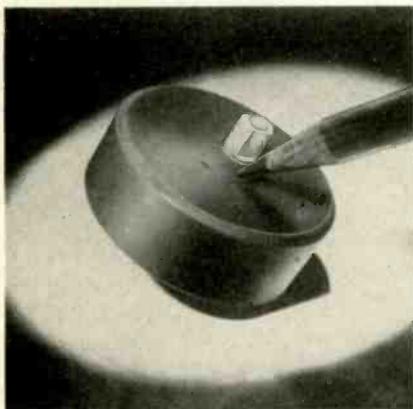
### Aerovox **CAPACITORS**

Permanently sealed Cartwheel capacitors were developed to meet the requirements of color-TV, are available in ratings up to 30 kv, and



can operate under high humidity or high temperatures. Available in a choice of sizes, voltages and capacitances, as well as several terminal styles, Hi-Q Div., Aerovox Corp., Olean, N. Y.—TECHNICIAN

### Mueller **SERVICE MIRROR**

Mounted on floor stand and using a 3-section telescoping mast, this TV mirror can be adjusted to any height from 13 to 32 in. The mirror (7 in. by 7 in.) swivels on a ball-and-socket joint, can be adjusted to any angle. When collapsed, the light-weight assembly can be carried in tool kit. Complete unit priced at \$7.95. Mueller Mfg. Co., 230 Tuscan Rd., Maplewood, N. J.—TECHNICIAN

### Astron **CAPACITORS**

Blue Point molded plastic paper capacitors are designed for continuous high-temperature operation without derating. For use where combination of small size, stability and moisture resistance are prime factors. Astron Corporation, 255 Grant Ave., East Newark, N. J.—TECHNICIAN

### Phalo **POWER-SUPPLY PLUG**

Molded directly to the cable, this power-supply plug is ready for connection with any standard octal radio socket. The need for mechanical fitting of plug to cable is eliminated. Units available to meet any application where from 1 to 11 pins are required, with or without the phasing pin keyed for easy seating in the socket. Phalo Plastics Corp., 25 Foster St., Worcester 8, Mass.—TECHNICIAN

### Teflon **SPAGHETTI**

High-temperature spaghetti tubing of high dielectric strength is available in a wide range of sizes in white, black, brown, red, blue and yellow. The tubing maintains full electrical insulating characteristics even when flexed or bent during assembly and installation, will not melt, burn or decompose while soldering a joint next to it. This tubing offers resistance to water absorption, tending to repel water. Supplied on reels in lengths of 100, 200, 500 and 1,000 feet. Polymer Corp. of Penna., Reading, Penna.—TECHNICIAN

### CBS **TUBE CADDY**

The DeLuxe Caddy incorporates several improvements over the earlier version. These include: scuff-proof vinyl plastic covering; metal corner reinforcements; more space for GT tubes (caddy holds 68 GT tubes, 210 tubes in all); 1-in. deeper tool compartments; roomier door pocket for flashlight, manuals, etc.; a 10 x 12-in. test mirror mounted inside cover; finger-notched carrying handle and non-marring rubber feet. Available from CBS-Hytron distributors. CBS-Hytron, Danvers, Mass.—TECHNICIAN

### Ersin **SOLDER**

Five-core solder in tin-lead mixtures of 60-40, 50-50 and 40-60 are available in Service Paks, mounted on wooden spools. Activated rosin core wets metals rapidly, results in easy tinning. Packs are 50 cents each. British Industries Corp. (Multicore Sales Corp.), 164 Duane St., New York 13, N. Y.—TECHNICIAN

### Hunter **SLUG RETRIEVERS**

Retrieving tools for tuner slugs are now available in 3 lengths—12, 16 and 20 in. The longer shafts, for use in sets on which the tuning units are mounted toward the back, incorporate the same non-magnetized holding mechanism as that of the standard TV-12. To operate, the technician slips the blade of the retriever into the tuning slot and engages the head of the slug, then gives slight forward press on the handle, which causes the tip of the retriever to grip the slug. The serviceman then rotates the slug back into place. The retriever is disengaged by a backward pull on the handle. Hunter Tool Co., 6608 So. Gretna Ave., Whittier, Calif.—TECHNICIAN

### Vidaire **TEST SOCKET**

The Adap-Test has dual sockets with 20 in. of lead extensions to bring socket voltages into the open on inaccessible tubes. Test points are numbered for identification.



Available in 3 models: AT-1 for octal tubes, AT-2 for 7-pin miniatures, AT-3 for 9-pin miniatures. Vidaire Electronics Mfg. Co., 576 W. Merrick Rd., Lynbrook, N. Y.—TECHNICIAN

### Stancor **FLYBACKS**

Said to be exact duplicates, physically and electrically, that do not require chassis or circuit alterations are flyback A-8239, replacement for Motorola part nos. 24K79-2753 and 24K701099, having application in over 100 Motorola models and chassis; and A-8240 replacement for Muntz part no. TO-0036. Stancor Div. of Chicago Standard Transformer Corp., Addison and Elston, Chicago 18, Ill.—TECHNICIAN

## Technician's Lighter Side

with Sol Heller

**HANDS ACROSS THE SEA.** An elderly technician who was visiting London went window shopping with a young English TV serviceman with whom he had made friends. During the course of their stroll, the Englishman pointed to a 7-inch TV set that had been reduced for clearance.

"Blimey, they're only asking 8 pounds for that set," marveled the Britisher. "Why, it's worth 12 pounds easy."

"Twelve pounds?" cried the American incredulously. "Son, I don't know much about your money system, but I wouldn't give you three ounces for that piece of junk."

**QUARREL THAT LAUNDRY AWAY.** Experiments at Pennsylvania State College indicate that intense inaudible sound waves can be used to wash clothes. If they could only make intense audible sound waves do the job, our laundry problems would be over. We'd just get the dirty linen out every time a quarrel with our better half was incubating, then let nature take its course.

**THIS OFFER EXPIRES IN SIXTY DAYS.** A portable power megaphone has been named "Little Bull." We offer the manufacturer, for free, a fine slogan for his product: "A Little Bull Goes A Long Way."

**NIGHTMARE OF THE FUTURE.** Whatever happened to that \$2 pocket radio that was rumored to be just around the corner early last year? Sounded like a wonderful idea—for everybody except the serviceman, that is. Can't you just hear the customer's howl of anguish when shown his repair bill: "10¢ for a new tube? That's robbery, man!"

**BIG BUSINESS.** A man who had bought a 21-inch TV set for \$2.95, in one of those crazy sales that department stores run from time to time to stimulate traffic, came back to the TV-radio department the next day.

"You having a special sale on antennas soon?" he demanded. "My wife and I will go as high as \$1.50 for a good outdoor unit."

**GETTING MORE MILES TO THE DOLLAR.** "How many miles would 2,836,173 one-dollar bills reach if they were placed end to end?" Motorola recently asked its employees, in a guessing contest. Winning guess was 279.65 miles. Which brings me to my point: If two million-odd dollars can cover 279 miles, why can't one dollar extend to a good meal at my favorite restaurant, seeing that it's only six blocks from my house?

# 3 SHURE CRYSTAL PICKUP CARTRIDGES replace the 192

cartridges you are most likely to encounter  
in your service work!



MODEL RK-54  
Replacement Kit  
List Price \$22.55

- 
- 
- TECHNICAL DATA AND REPLACEMENT CHART IS ENCLOSED.
- Lists 192 Crystal Cartridges manufactured by
- five leading cartridge manufacturers.

**Lowest investment for broadest coverage!** The RK-54 is beyond all doubt the *most practical* Replacement Kit on the market! Proof? Simply this—you get the broadest coverage at the lowest investment—only \$22.55 list! Think of it—3 Crystal Cartridges replace 192 of those specific Cartridges most likely to be in need of replacement! Two of the Cartridges consistently have been "best sellers" in the Shure line—as established by actual sales to Servicemen! The Cartridges are: Model W22AB, 3-Speed, 2-Needle Cartridge—Model W26B, All-Purpose, Single-Needle Cartridge—Model W78, 78 RPM, Dual-Volt, Dual-Weight Cartridge. Model W78 is the new, versatile Cartridge that replaces 149 other Cartridges! This Cartridge alone will become a sensation overnight! Order a Replacement Kit from your Distributor today—once you have worked with this practical kit you will find that these three Cartridges are dependable replacements—will make your service work faster, easier and more profitable!



**TRANSPARENT PLASTIC BOX IS FREE!**  
This Handy Box is 5" long, 3½" wide,  
1¼" deep.

**SHURE** — The Mark of Quality

## MFRS' Catalogs & Bulletins

**CLEAR BEAM ANTENNAS & ACCESSORIES:** Full listing of Clear Beam and Tempo antennas, telescoping masts and other accessories. Clear Beam Antenna Corp., 100 Prospect Ave., Burbank, Calif.

**INT'L RECTIFIER DIODES:** Ratings and specifications on germanium diodes are listed in *Bulletin GD-1A*, 4 pp. International Rectifier Corp., 1521 E. Grand Ave., El Segundo, Calif.

**SNYDER AUTO ANTENNAS:** Full-color catalog describes the complete line of cowl, fender, rear and deck mount auto radio aeriels including the Snyder-Matic, whose 3 sections can be raised or lowered by a finger-tip dash control. Free antenna display materials are also listed. Dick Morris, Snyder Mfg. Co., Philadelphia 40, Penna.

**WARD ANTENNAS:** Separate removable catalog sheets in a folio-type cover keep this catalog, the *Ward Antenna Rama*, up to date by the later insertion of new sheets. Full information on more than 25 models. Free on request. Ward Products Corp., Div. of the Gabriel Co., 1148 Euclid Ave., Cleveland, Ohio.

**COMMERCIAL PRODUCTS ANTENNA HARDWARE:** 14 types of stand-offs (in 60 sizes), in addition to guy-wire clamps, turnbuckles, U bolts, eyebolts, rings and guy hooks are described in the mfr's latest catalog. Commercial Products, 417 Main St., Toledo 5, Ohio.

**AEROVOX CAPACITORS:** Hi-Q ceramic condensers, including new Cartwheel types, are described with full electrical and physical specifications in *Hi-Q Ceramic Capacitor Catalog*; 24 pp; illustrated. Hi-Q Div., Aerovox Corp., New Bedford, Mass.

**EICO INSTRUMENT KITS:** Useful as a condensed catalog or mailing piece, a new 6-page brochure, *Form DMC-554*, gives highlight specs and descriptions of the 38 kits and 42 wired instruments in the EICO line. Electronic Instr. Co., Inc., 84 Withers St., Brooklyn 11, N. Y.

**RHEIN SOUND SYSTEMS:** An amplifier selection chart, designed to aid in the choice of equipment for specific requirements and listing the manufacturer's 27 amplifiers, is featured in this 4-page folder. Notes on applications are included. Available from distributors or write to Rhein Sound Systems, Inc., 2 Coburn Ave., Orlando, Fla.

**HALLDORSON TRANSFORMERS:** Expanded line of transformers, with emphasis on TV components, is described and illustrated in *Catalog No. 22*. Chart of audio amplifier tubes vs. output transformers is included. Halldorson Transformer Co., 4500 Ravenswood Ave., Chicago 40, Ill.


**JAVEX ELECTRONIC ACCESSORIES:** Installation accessories, wall outlets, connectors, feed-through bushings, h-v indicators and display materials are listed in *Catalog 254*, 8 pp. Javex, P. O. Box 646, Redlands, Calif.

**GEN'L CEMENT TOOLS:** Thirty-six TV tools and five tool kits are included in a listing of special-purpose alignment tools, bench kits and display materials. *Brochure no. 3545*, 4 pp., is available from General Cement Mfg. Co., 919 Taylor Ave., Rockford, Ill.

**BOGEN SOUND SYSTEMS:** Indoor and outdoor PA systems, fixed and mobile, as well as complete sound systems and accessories such as mikes and baffles are listed in *Catalog PA554*, 20 pp. Includes a section on selection of systems for specific requirements. Write to David Bogen Co., Inc., 29 Ninth Ave., New York 14, N. Y.
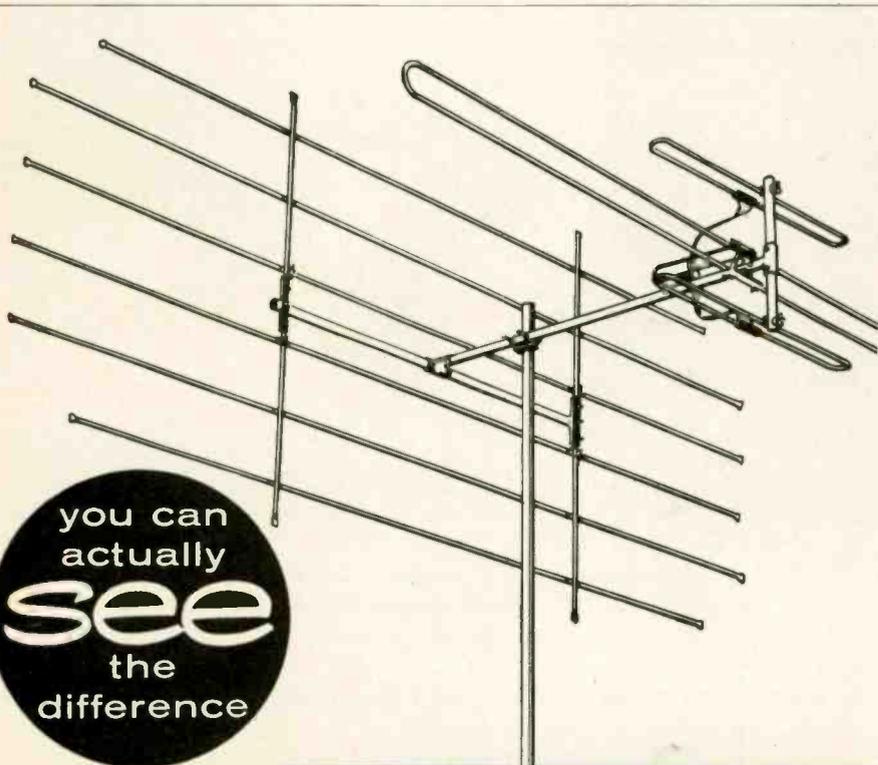
### CORRECTION

**ALPHA SOLDERS:** Seven solder fluxes and 6 types of bar solder, described on p. 42 (New Products), July *TECHNICIAN*, are made by Alpha Metals, Inc. For information on these products, address inquiries to that manufacturer at the following corrected address: 56 Water St., Jersey City, N. J.



you can actually **see** the difference

with the

**C-D Skyhawk**  
**ULTAMATIC**  
All Channel TV Antenna

NOW... C-D designs the finest TV Antenna... the first antenna with which you can actually SEE the difference! Perfectly synchronized for monochrome and COLOR TV. The most uniform gain response that does not vary more than 3 D.B. on any channel across the band. Other features include low voltage standing wave ratio... higher front-to-back ratio... speedy assembly... aluminum screen reflector... dipole and boom of heavy gauge, seamless tubing.



Consistently Dependable  
**CORNELL-DUBILIER**  
SOUTH PLAINFIELD, N. J.



CAPACITORS · ANTENNAS · ROTORS · VIBRATORS · CONVERTERS

## NEW BOOKS

**ELECTRONICS.** By George Corcoran and Henry Price. Published by John Wiley & Sons, Inc., 440 Fourth Ave., New York 16, N. Y. 459 pages; \$7.00, hard cover.

All types of vacuum tubes and such equivalents as germanium diodes and transistors are considered, together with the various classes of linear and non-linear operation and circuit applications. Although treatment is basic, a substantial math background is necessary. The text will be most useful to the lab man and the advanced technician who wishes to expand his background.

**TECHNICIAN'S GUIDE TO TV PICTURE TUBES.** By Ira Remer. Published by John F. Rider Publisher, Inc., 480 Canal St., New York 13, N. Y. 154 pages; \$2.40, paperbound.

Care, handling, replacement, maintenance and repair of crt's are covered in this service technician's guide. Basic parts of the tube, associated accessories and adjustments, and physical and electrical characteristics are presented without complex technical data or formulas. Tube data are in the form of several pages of charts. An appendix describes the 3-gun color tube.

**FUNDAMENTALS OF TRANSISTORS.** By Leonard Krugman. Published by John F. Rider Publisher, Inc., 480 Canal St., New York 13, N.Y. 144 pages; \$2.70, paperbound.

With the growing use of transistors in electronic equipment, this book's explanation of how these semiconductors operate should be of timely interest to technicians. From basic semiconductor physics, the text goes through the mechanism of operation, and into an analysis of the unit with grounded base, emitter, and collector, respectively. The book also covers transistor amplifier, oscillator and high frequency applications. Common transistor symbols are presented in the appendix.

**HOW TO LOCATE AND ELIMINATE RADIO & TV INTERFERENCE.** By Fred D. Rowe. Published by John F. Rider Publisher, Inc., 480 Canal St., New York 13, N.Y. 128 pages; \$1.80, paperbound.

The various sources of radio and TV interference are discussed, along with a number of methods for locating and eliminating such interference. Subjects included are antennas, locating equipment, appliances, power lines, TVI suppression in transmitters, and TV receivers.

**TELEVISION SIMPLIFIED, 4TH EDITION.** By Milton S. Kiver. Published by D. Van Nostrand Company, Inc., 250 4th Avenue, New York 3, N. Y. 544 pages; \$6.75, hard cover.

This enlarged revised edition contains many new illustrations and schematic diagrams, plus two additional chapters

on UHF and color TV. Up-to-date material has also been added on cascade and other TV tuners, keyed agc systems and d-c video amplifiers.

**HIGHLIGHTS OF COLOR TELEVISION.** By John R. Locke, Jr. Published by John F. Rider Publisher, Inc., 480 Canal Street, New York 13, N. Y. 48 pages; \$0.99, paperbound.

General review, covering colorimetry, NTSC color signal, color transmitters and receivers, the 3-gun shadow-mask tube, and some details of the associated receiver. Basic principles and processes are described with the aid of block diagrams and other drawings.

### TeleTest FLYBACK CHECKER

Yokes, width coils and linearity coils, as well as flybacks, may be tested for shorted turns or continuity without the use of a duplicate reference unit on the TeleTest Flyback Checker. The use of normal receiver operating voltages, rather than 100-120 volts, is said to show up faults that might be obscured by a reduced-voltage test. Positive check of condition on good units as well as bad ones is said to be possible. Priced at \$44.95. TeleTest Instruments Corp., 31-01 Linden Pl., Flushing, N.Y.—TECHNICIAN



## The Complete Line of Quality Phonomotors




Model 55  
3-speed, 2-pole motor



Model D55  
3-speed, 4-pole motor



Model DR  
2-speed, 4-pole motor

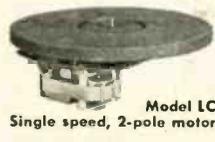

Model LC  
Single speed, 2-pole motor



Model RM4  
Single speed,  
4-pole motor



Model D-10  
4-pole motor widely used  
for tape recorders

- FOR PORTABLE PHONOS
- FOR HI-FI UNITS
- FOR COMBINATIONS
- FOR RECORD CHANGERS
- FOR TAPE RECORDERS
- FOR REPLACEMENT USE
- FOR EVERY PHONO APPLICATION

Whatever your phonomotor or tape recorder requirements, you'll find the *exact* answer in the famous *Smooth Power* line of single-speed, dual-speed and three-speed motors. Illustrated at the left are just a few of the many different types from which to choose.

Each of these advanced design motors incorporates General Industries' exclusive engineering and construction features which assure trouble-free performance and long-lasting dependability.


Complete information, including dimensions, specifications and quantity quotations, furnished promptly upon request. Write to:

**THE GENERAL INDUSTRIES CO.**  
DEPARTMENT MD • ELYRIA, OHIO


# TUNG-SOL TUBE QUALITY PAYS OFF IN SALES!




Black and White Picture Tubes

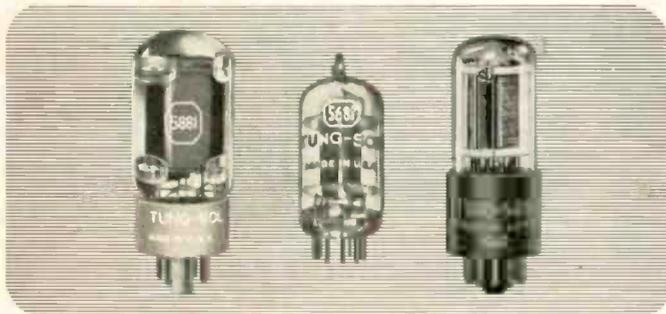

Special Purpose Tubes

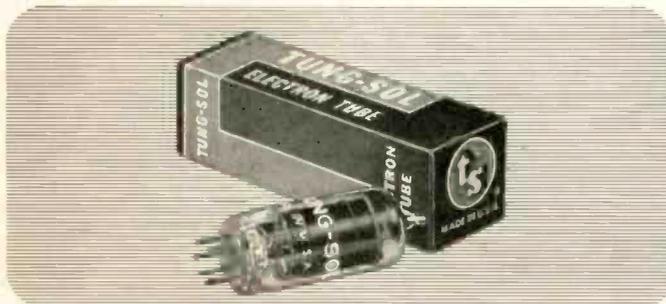

Radio and TV Receiving Tubes

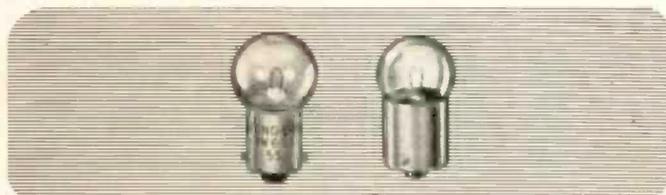

Dial Lamps

The performance quality of Tung-Sol Tubes will keep customers convinced that you're the best serviceman in the business. Tung-Sol Tubes meet highest set manufacturers' specs—protect you against call-backs. Tell your supplier you'd rather have Tung-Sol

TUNG-SOL ELECTRIC INC., Newark 4, N. J.

Sales Offices: Atlanta, Chicago, Columbus, Culver City (Los Angeles), Dallas, Denver, Detroit, Newark, Seattle

**TUNG-SOL**® *dependable*  
ELECTRON TUBES

# Transmission

By EDWARD ABBO

Saxton Products, Inc.

The choice of a proper feed or transmission line is important, if optimum reception is to be achieved. This is particularly true in special-purpose antenna setups (such as community installations) and in fringe installations, where choice of the proper transmission line very often spells the difference between poor, adequate or good reception.

Several types of transmission lines are in popular use. Most widely-used is 300-ohm twin-lead transmission wire. In strong signal areas, twin-lead is normally satis-

TRANSMISSION LINE LOSSES (IN DB PER 100 FEET)

Type of Line	Loss at 100 MC		Loss at 500 MC		Loss at 1000 MC	
	Wet	Dry	Wet	Dry	Wet	Dry
300-Ohm Open Wire	1.20	0.40	2.30	.86	1.9	1.8
300-Ohm Tubular	2.8	1.1	6.8	3.1	10.2	4.8
300-Ohm Flat	7.6	1.5	20.0	3.2	30.0	5.0
RG-59U	—	3.8	—	9.4	—	14.2
RG-11U	—	1.8	—	5.0	—	7.6

factory, primarily because of its relatively low cost, and because it is easy to handle. In noisier, weak-signal areas, however, and where the feed-line is quite long, twin-lead becomes inadequate for the following reasons:

1. The dielectric loss (loss across the polyethylene insulation compound) increases greatly as the frequency goes up.
2. The loss becomes even greater in wet weather, or in sea-coast areas which are normally damp.
3. The line material dries out, tends to break or crack, and changes its characteristics after a period of time, thereby requiring fairly frequent replacement.
4. The signal loss becomes prohibitive as the feed-line is lengthened.
5. Because of its flexibility, the line tends to whip about in windy weather, with consequent loss of picture stability, unless adequately anchored.

Coaxial cable is also used quite extensively. There are many different types of coaxial cable. Two types have become more or less standard with the average serviceman. These are identified by the type numbers RG59U and RG11U.

RG59U is most frequently used because it is thinner and easier to handle, and also because it sells for a lot less than the sturdier and more efficient RG11U. RG11U is more commonly used in community installations, and in urban areas for multiple apartment house master antenna installations.

Coaxial cable has an impedance of 72 ohms, and generally speaking, has its largest field of application in areas where noise impulses are prevalent. Its life span is considerably longer than that of twin-lead; in addition, its tough outer jacket is much more resistant to the weather and the elements. Coaxial cable also shields out and rejects noise impulses, and has a much better loss characteristic.

Briefly, coaxial cable (particularly RG11U) is much more expensive than twin lead; it is more difficult to handle, and its impedance (72 ohms) requires special matching equipment in almost all cases, since 300 ohms is the standard input impedance for most television receivers.

In the last two years, two other types of feed line have

# Line Review


become fairly popular: 300-ohm tubular wire, and more recently both 450-ohm and 300-ohm open-line wire.

300-ohm tubular wire is now being used extensively because it is more weather resistant than the flat 300-ohm lead; its loss characteristics are considerably better, it is less affected by the elements, and it is sufficiently inflexible so that it does not tend to whip around or be affected by high winds.

It has most of the advantages of coaxial cable, besides being much less expensive; it does not, however, have the shielding effect of coaxial cable.

Open-line transmission wire has only recently started coming into its own. Its basic disadvantages are now in great measure being overcome. It was only made in 450-ohm types until recently, thereby negating many of its inherent advantages. Matching stubs were required to change its characteristic impedance to 300-ohms. In its 450-ohm form, it was very unwieldy to handle, due to the large spacing between the wires. These drawbacks, coupled with the fact that there was very little hardware available to extend its application, made its use rather limited. And since its use was limited, and volume sales low, the comparative cost of the line was quite high. Recently, however, improvements in fabricating machinery have made volume production of 300-ohm open-line transmission wire feasible.

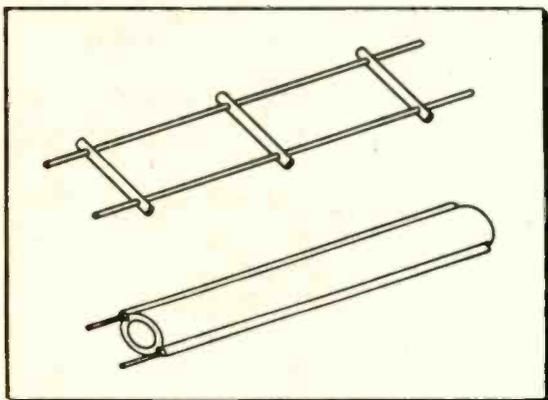(Two disadvantages of open-wire line, when it is used for UHF reception, are: 1—There is appreciable increase




450-ohm open-wire vs 300-ohm tubular line. courtesy Du Mont

in signal loss when the line becomes wet. 2—If the line is run close to a wall or similar object unit, signal losses through absorption are significantly increased. A third disadvantage of the line on both UHF and VHF lies in the fact that its relative inflexibility presents the serviceman with mechanical installation problems—Ed.)

300-ohm transmission wire has some important advantages. For instance, it requires no special matching. It is easy to handle and manipulate (note our preceding comment—Ed). In common with all open-line wire, it has the best loss characteristic of any type of commercial transmission wire. It is least affected by changes in weather. Its price also has rapidly approached that of ordinary flat twin lead, the least expensive of all the transmission lines.

The basic difficulty at the moment is a lack of adequate hardware to facilitate its use. With the increasing popularity and obvious advantages of open-wire line, however, this handicap may be overcome soon. The line is now available in copper-coated steel, pure copper, and (for salt-sea areas) in a variation of these, with a covering of Formvar.
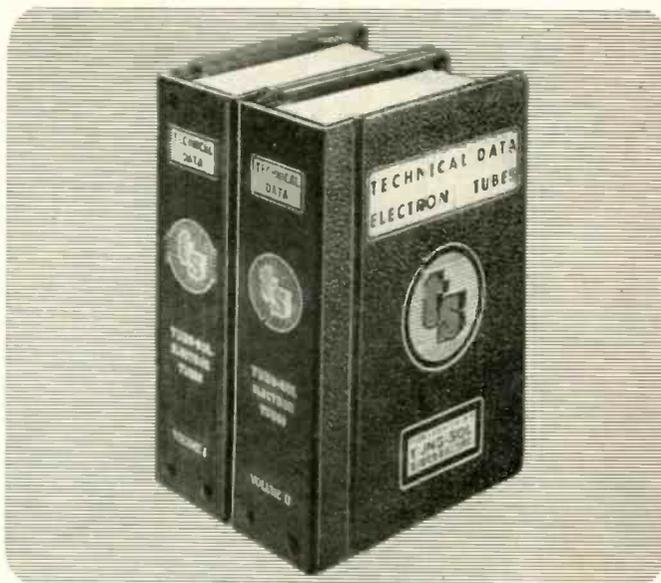
## TUNG-SOL TECHNICAL DATA PAYS OFF IN SERVICE!



T-58 700 pages—600 tube types



NEW! 1954 Edition! T-70 160 pages of data on CR tubes, receiving and special tubes, dial lamps



T-31 300 blueprint base diagrams for 1100 tube types

Here's the most practical set of tube reference books in the industry—all the information you need for everyday jobs! They're easy to read—easy to use (always lie flat when open.) You'll get work done faster with Tung-Sol Technical Data Books. Ask your tube supplier about them.



TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

# TUNG-SOL® *easy reference* TECHNICAL DATA

# Making the Most of Your Test Equipment

(Continued from page 21)

of the one usually recommended, but is preferred for this reason: there is no possibility of plates shorting, as exists when the plates are bent inward; furthermore, there is always more room for outward bending than for inward compression.


**Calibrating Signal Generator.** To properly align sound-stages tuned

to 4.5 mc, an accurately calibrated signal generator is necessary. If a 4.5 mc crystal calibrator is available, accurate setting of the i-f presents no problem; if an AM signal generator is being used for marking purposes, however, it should initially be calibrated at this frequency, and re-checked every month or so.

The simplest method of doing this

is to clip the output lead from the generator to the insulation on the grid wire of the last sound i-f stage of a TV receiver; a TV station is then tuned in. With the signal generator output turned up fairly high, and the modulation OFF, move the generator dial slowly back and forth from the 4.5 mc point on the scale, and set it at the zero-beat point. The generator signal will now be beating against the 4.5 mc sound signal developed in the video detector and fed to the sound i-f stages. Mark this setting on the signal generator dial as the 4.5 mc point, regardless of the actual scale reading at this point.

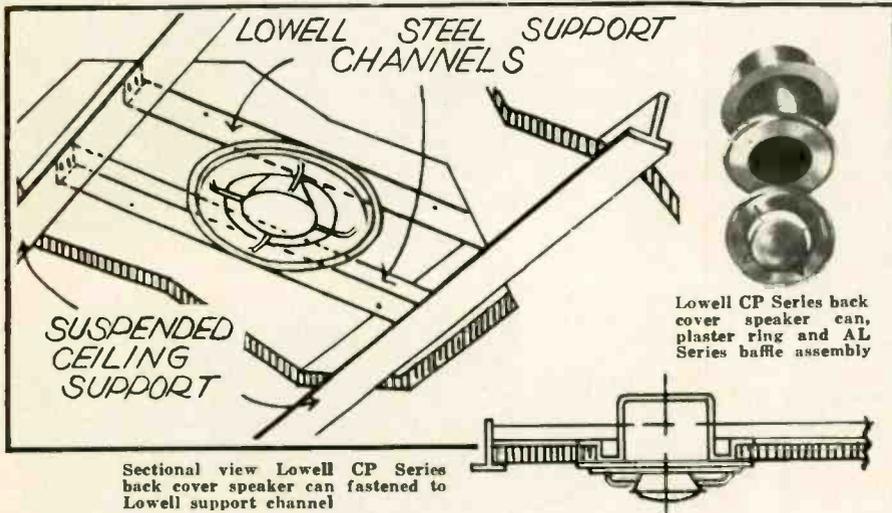The zero-beating is best done during a station break, when no sound modulation is present; if the process is performed at other times, the beat frequency will vary with the modulation, causing it to sound "hashy." With a little practice, however, the zero-beating can be per-



Sectional view Lowell CP Series back cover speaker can fastened to Lowell support channel

## Specify LOWELL Steel Support Channels for Easier, Stronger installations of LOWELL Speaker Baffles in Suspended Ceilings!

Use in Both New and Existing Ceilings! Available for 24" and 48" Spans.

Lowell steel support channels provide a new, easy way to install sound system speakers in suspended ceilings. In new ceiling construction simply secure Lowell support channels between ceiling supports at desired locations for Lowell Protective Back Cover Speaker Enclosures before ceiling material is applied. Where ceiling has already been installed, cut hole for slip fit of Protective Enclosure, or remove ceiling panel for size of hole. Lowell Steel Support Channels may be used with all standard types of suspended ceiling construction and materials.

Model SS24 Steel Supports (24" span) ..... List \$1.85 ea.

Model SS48 Steel Supports (48" span) ..... List \$2.65 ea.  
(Min. quantity, 1/2 doz.)

WRITE FOR COMPLETE SPECIFICATIONS AND INSTALLATION INFORMATION TO

## LOWELL MANUFACTURING COMPANY

3030 Laclède Station Rd., • St. Louis 17, Mo.

IN CANADA: ATLAS RADIO CORP., 560 KING ST., WEST, TORONTO, ONT.

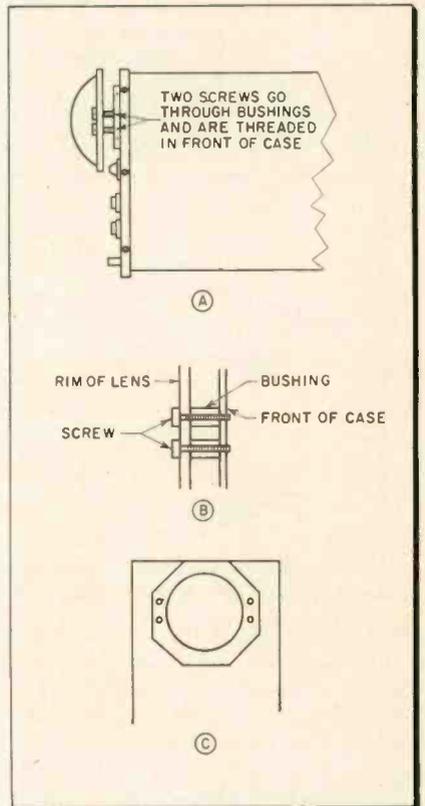


Fig. 3A—Side view of enlarger mounting. B—Mounting detail. C—Front view of unit.

formed fairly accurately even under modulation conditions, since the general over-all sound does vary as the dial is moved.

If a scope is used for observing the zero beat setting, connect it across the volume control, or the discriminator output.

By zero beat we mean, of course, the generator setting at which no audible or visible output occurs; output will, of course, be visible or

Eliminates Small Catalogs and Loose Literature

### Faster, Easier, more PROFITABLE Operation

**Get into the MASTER habit!**

Brings you the product data of the industry in one handy book—all products vital to your daily sales and service operations. In the customer's home, across the counter or on the bench, you'll value the MASTER'S thoroughly complete descriptions, specs, illustrations and prices... all systematically organized in 18 big sections. Over 1300 pages of unabridged catalog data direct from the manufacturers. Keeps you abreast of all latest electronic products. Increase your sales and speed-up your buying—the MASTER way.

As **\$1.95** at your parts distributor. Publisher's price **\$6.50**.

Get your MASTER now from leading parts distributors or write to:  
United Catalog Publishers, Inc., 110 Lafayette St., N. Y. 13

OFFICIAL BUYING GUIDE OF ELECTRONICS-TV-RADIO INDUSTRY

- 1370 pages
- 8" x 11"—5 lbs.
- Over 8,000 illus.

Just a few of the more than 85,000 items included:

Tubes—Transmitters  
Test Equip.—Receivers  
Transformers  
Capacitors—Antennas  
Resistors—Wire & Cable  
Coils & Relays  
Recording & PA  
Hardware & Tools

audible at settings directly above or below this one, if it is the true zero beat point.

**Enlarger for 3-in. Scope.** Technicians who have only an older type 3-in. scope, and who wish to enlarge the viewed pattern on the face of the tube until such time as they can afford a larger and more modern instrument, may be interested in a simple method of bridging the gap between the two. This method consists of securing an enlarging lens (like the one used on the 3-in. Pilot TV receivers a number of years ago) and mounting it in front of the present tube. Fig. 3 shows how one of these lenses was mounted on a 3-in. RCA scope to provide a screen of approximately 4 in. If light reflections from overhead are bothersome, a piece of cardboard shield may be used to form a hood over the lens.

**Walsco Markets  
Low-Cost Antenna**

In ordinary metropolitan and suburban areas, an elaborate array or expensively designed antenna is not necessary to get a good TV picture. With this fact in mind, Walsco Electronics has announced the "Scotty" antenna, designed to produce good results on VHF at distances of 20 or 30 miles from the transmitter, and selling at \$3.77.



"Scotchman" shows Scotty to Walsco proxy Walter C. Schott and sales mgr. Bob Mueller.

Since its angle may be adjusted, the antenna can also be used for UHF or UHF-VHF applications. Made of reinforced aluminum, the receptor carries a 1-year unconditional guarantee. It may also be stacked for semi-fringe use. Further information from Walsco Electronics Corp., 3602 Crenshaw Blvd., Los Angeles, Calif.

See Test Equipment "Spec" Charts beginning on pg. 34

# KESTER

Since the most important single step in Radio-Television Servicing is soldering... it's just plain good sense to use the best — KESTER SOLDER... Key Name in Solder for More Than 50 Years.

**KESTER SOLDER COMPANY**  
264 Wrightwood Avenue • Chicago 39, Illinois  
Newark 5, New Jersey • Brantford, Canada

# SOLDER

THE NEW  
MODEL  
670-A

## SUPER METER

A COMBINATION VOLT-OHM MILLIAMMETER PLUS CAPACITY REACTANCE  
INDUCTANCE AND DECIBEL MEASUREMENTS



- SPECIFICATIONS:**  
**D.C. VOLTS:** 0 to 7.5/15/75/150/750/1,500/7,500 Volts  
**A.C. VOLTS:** 0 to 15/30/150/300/1,500/3,000 Volts  
**OUTPUT VOLTS:** 0 to 15/30/150/300/1,500/3,000 Volts  
**D.C. CURRENT:** 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes  
**RESISTANCE:** 0 to 1,000/100,000 Ohms 0 to 10 Megohms.  
**CAPACITY:** .001 to 1Mfd. 1 to 50 Mfd. (Quality test for electrolytics)  
**REACTANCE:** 50 to 2,500 Ohms 2,500 Ohms to 2.5 Megohms.  
**INDUCTANCE:** .15 to 7 Henries 7 to 7,000 Henries  
**DECIBELS:** -6 to +18 +14 to +38 +34 to +58

**ADDED FEATURE:**

The Model 670-A includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

The Model 670-A comes housed in a rugged crackle-finished steel cabinet complete with test leads and operating instructions. Measures 6 1/4" x 9 1/2" x 4 1/2"

**\$28<sup>40</sup>**

**SHIPPED ON APPROVAL  
NO MONEY WITH ORDER — NO C. O. D.**

Try it for 10 days before you buy. If completely satisfied send \$7.40 and pay balance at rate of \$3.50 per month for 6 months—**No Interest or Carrying Charges Added.** If not completely satisfied, return to us, no explanation necessary.

**MOSS ELECTRONIC DIST. CO., INC.**  
 Dept. D-58, 3849 Tenth Ave., New York 34, N. Y.  
 Please rush one Model 670-A, I agree to pay \$7.40 within 10 days after receipt and \$3.50 per month thereafter.  
 NAME .....  
 ADDRESS .....  
 CITY ..... ZONE ..... STATE .....

# Using the Oscilloscope for TV Servicing

(Continued from page 17)

ate-frequency signals on the scope, a detector must be employed to rectify the modulated signal and remove the radio-frequency carrier. Tubes can be used, but the overwhelming preference is for the simple diode crystal, such as a type 1N64 germanium diode. The entire device can be housed in a commercial-type crystal probe; or else a

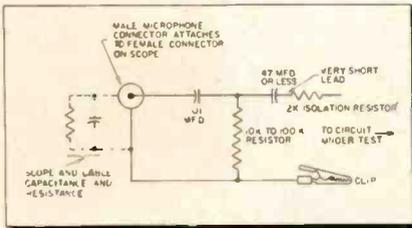


Fig. 6—Schematic of low-capacitance probe.

brass cylinder may be used as the outer casing (the small tube in electric light fixtures makes an excellent casing). A connector may be mounted at one end of this cylinder, to match the microphone coaxial cable arrangement previously mentioned.


A typical shunt diode detector circuit with its filter is shown as Fig. 7A; in 7B, another arrangement which uses a series diode for detection is shown. Either of these setups is entirely satisfactory. The isolating condenser should never be

omitted, and may be used in conjunction with an isolating resistor of about 4.7k, if desired.

The ends of any isolating resistor or condenser attached to the circuit should be extremely short, since r-f circuits are invariably tuned, and even the shortest possible lead will detune the circuit to which it is applied considerably. The detuning results in a loss of amplitude, which must be taken into account in interpreting the waveshapes obtained with the crystal probe across a tuned r-f or i-f circuit.

**Using Tuned Circuit with Detector Probe.** A tuned circuit may be employed in conjunction with a detector probe. The tuned circuit comprises a coil (which may be slug-tuned) and a condenser across it (which may be the self-capacitance of the coil). The parallel combination is connected between the probe point and the ground connection of the detector probe. The coil is placed near the tuned (or even untuned) circuit whose waveform is to be observed on the scope. The probe resonant circuit is tuned to the frequency of the circuit under test.

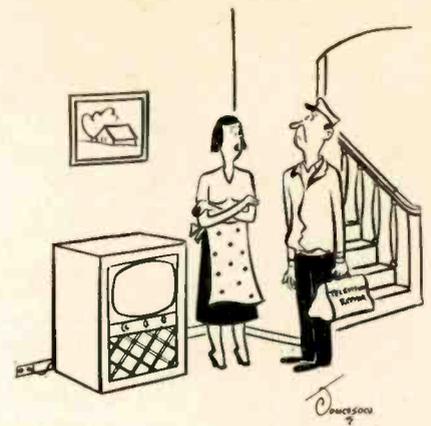The advantage of the arrangement just described lies in the fact that the coupling can be made relatively weak, with the result that



the circuit under test will not be appreciably upset. The coil can be an i-f coil of the same frequency as the one in the circuit under test. No shunting capacitance will be needed in most instances, since the capacitance of the probe and the coil will generally be large enough to provide proper resonance.


Too close coupling between the probe circuit and the circuit under test is to be avoided, since the tuned probe will act as a trap under such conditions.

**Scope Calibration.** In the absence of a scope grid, calibration may be achieved as follows:


The vertical deflection produced by some known peak-to-peak voltage is marked on the tube face. Since a 5-inch tube is the most common type employed, obtain about 4 inches of vertical test signal deflection. Divide this height into 10 equal parts, and mark each division on the scope face with a grease pencil, or else use a Crayola wax crayon.

Use the shop's tube tester as the source of the calibrating voltage. Do not use the test signal from the scope heater supply, since you do not know exactly what its voltage is at any instant. With a tube tester, you can set the line voltage to deliver a metered amount of filament or heater voltage to the filament terminals of some tube socket on the tube-tester face; these terminals may then be connected to the scope's vertical input for calibration purposes.

Fig. 7A—Shunt crystal detector probe. B—Series-type crystal detector probe. Both are used for detecting i-f or r-f modulated signals. C—Pictorial sketch of shunt xtal probe.

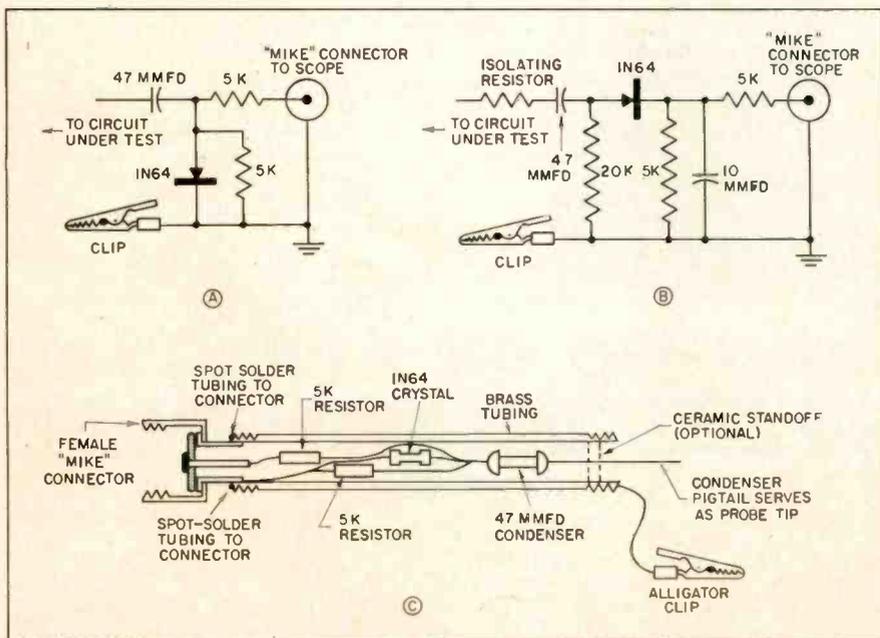

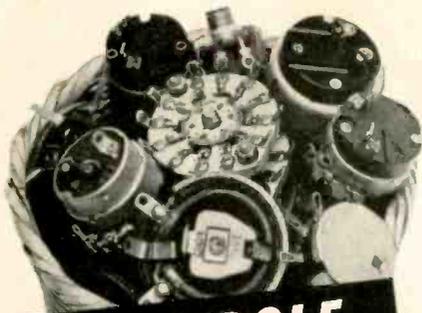Technical new products on pgs. 40, 44, 46, 50, 60



**QUIETROLE**  
 Reg. U. S. Pat. Off.  
 The ORIGINAL  
 NON-INFLAMMABLE  
 NON-CONDUCTIVE  
 LUBRICANT CLEANER



CONTROLS & SWITCHES like new by the BASKETFUL for only a few PENNIES . . . that's what QUIETROLE can do for you, and only QUIETROLE will give that long lasting smooth, quiet operation . . . even new controls last longer and operate quieter when treated with QUIETROLE . . . the original and most reliable product of its kind.

**THE CHOICE OF BETTER SERVICEMEN "EVERYWHERE"**  
 Supplied in 2, 4, and 8 oz. sizes. Ask for it at your distributor.



manufactured by  
**QUIETROLE**  
 COMPANY  
 Spartanburg, South Carolina

## THE NEW ELECTRONIC "SIGN LANGUAGE"



### Graphical Symbols for Electronic Diagrams

First publication of a pictorial summary of the new standards showing symbols of special interest to radio-TV-electronic technicians. These symbols will shortly be used in all circuit schematics by the electronic industries.

Reprints of symbols are available to all servicemen in "wall chart size" (approx. 15" x 21"), @ 15¢ each, cash and/or stamps. Order from

**TECHNICIAN**  
 & Circuit Digests

480 Lexington Ave., New York 17, N. Y.

## P. A. Sound System

(Continued from page 48)

tion. Have the purchaser of your system appoint someone (if he won't do it himself) to operate the unit. Explain the various applications and limitations of the system.

A p.a. system in most cases becomes an important instrument in conducting your client's business. In case of failure or trouble, your client may be out of business, with possible loss of customer prestige. Providing spare fuses and tubes for your customer is a thoughtful act that will, in the end, bring in more revenue than the service income possibly lost by such a procedure.

Show the customer (or his representative) the location of the power plug and the fuse-holder, and describe how he can gain access to and replace the tubes. Discuss the proper manner to handle and store microphones. Every possible bit of consideration and help you can give your client in maintaining his public address system will promote reliable and consistent functioning of his setup. This will enhance your reputation, and stimulate new p.a. business for you via word-of-mouth recommendations.

## New Product Briefs

**SUPERIOR SUPER METER:** New twist in this v-o-m is a built-in isolation transformer to insure automatic protection when used for servicing transformerless receivers. Net price is \$28.40. Superior Instruments Co., 2435 White Plains Rd., New York 67, N. Y.—TECHNICIAN


**JACKSON WIDE-BAND SCOPE:** Flat within 1 db from 20 cps through 4.5 mc, this scope is useful for general TV servicing, and particularly for color. Increased sensitivity may be obtained by reducing bandwidth to 100 kc for low-frequency work. Incorporates retrace blanking, intensity modulation input, calibrating voltage. Jackson Electrical Instr. Co., 18 S. Patterson Blvd., Dayton, Ohio.—TECHNICIAN

**DALTON PORTABLE JIG SAW:** Model D-500, useful for rough-in work, is a portable electric jig saw that can cut straight lines, curves or designs in wood, plastics, metal and rubber. Pistol grip. Built-in compressor acts as cooling unit, blows sawdust away from guide lines. Kapner Hardware, Inc., 2248 2nd Ave., New York 29, N. Y.—TECHNICIAN

**E-V HI-FI MIKE:** Cardioid microphone 666, with high front-back ratio, has response from 30 to 15,000 cps. Light, slim design. Electro-Voice, Inc., Buchanan, Mich.—TECHNICIAN

## New Approach to Practical Tube Testing

INDISPENSABLE ON EVERY SERVICE CALL

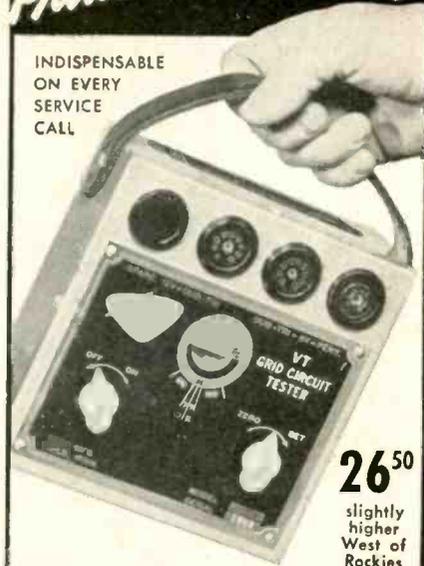

**26<sup>50</sup>**  
 slightly higher West of Rockies

MODEL GCT-3 STORES IN TELEVISION SERVICEMAN'S TUBE CADDY!

PORTABLE

**SECO** GRID CIRCUIT TUBE TESTER

MAKE THIS 4-WAY CHECK:

(without using a selector switch)

1. Control Grid Emission (Exclusivel)
2. Grid to Cathode Shorts
3. Gaseous Condition in Tube
4. Cathode to Heater Shorts

TRACK DOWN TROUBLES LIKE THESE:

- Poor picture contrast
- Vertical jitter or bounce
- Grainy picture
- Sync buzz in the sound
- Twisting, bending or pulling of the picture
- All symptoms caused by sync pulse compression

The SECO TUBE TESTER was developed to detect "positive grid condition" in RF and IF tubes in critical TV circuits in the AGC chain . . . a vital check which no other tester can provide. Video and Sync tubes can also be checked.

Thousands of technicians have proclaimed the SECO TESTER an indispensable servicing aid!

- Simple, quick, reliable
- Tremendous time saver
- Eliminates substitution checking
- Spots tube troubles early
- Aid to better service
- Increases customer confidence
- Increases tube sales

YOUR DISTRIBUTOR HAS IT OR WRITE:



5015 Penn Ave. S. • WH. 1827  
 Minneapolis, Minnesota

# ALLIANCE first with **AUTOMATIC GARAGE DOOR OPERATOR**

THAT'S PRICED **LOW** FOR THE MASS MARKET



**\$179<sup>95</sup>**

**OFF-SEASON PROFITS FOR TV DEALERS**



THE ELECTRONIC

## LIFT-*Alliance*-DOR

**OPENS • CLOSSES • LOCKS GARAGE DOORS**

*Automatically.* A RADIO-CONTROLLED "NATURAL"  
FOR RADIO AND TV SERVICE DEALERS AND INSTALLERS!

**More than 15,000,000 homes are prospects!**

Fast—Easy Installation—Alliance Lift-A-Dor Is a Packaged,  
Quality, Low Priced Unit. Fits Nearly All Overhead Doors  
—Takes Only Ordinary Tools and 'Know How' To Install.

**AVOID SEASONAL SLUMPS WITH THE  
ELECTRONIC ALLIANCE LIFT-A-DOR!**

**AMAZING LOW PRICE!**

The first dependable fool proof garage door operator, fully guaranteed at a price all can afford! A real convenience—a protective necessity that saves work—simply push a button!

### TV DEMONSTRATIONS!

Alliance TV spots like those making Alliance Tenna-Rotor famous, will show and demonstrate Lift-A-Dor to millions of TV viewers.

Newspapers—magazines—point-of-sale displays pre-sell!


### WRITE THE FACTORY FOR FACTS!

A radio impulse transmitter in car, operated by push-button on dash is pre-tuned to receiver in garage which raises or lowers door automatically—locks, unlocks and turns on light. Installation takes no digging—no outdoor wiring, no special tools. Write for catalog and complete information.

**THE ALLIANCE MANUFACTURING CO. • ALLIANCE, OHIO**

*Makers of the Famous Alliance Tenna-Rotor*

# YOU CAN WIN A NEW FORD!

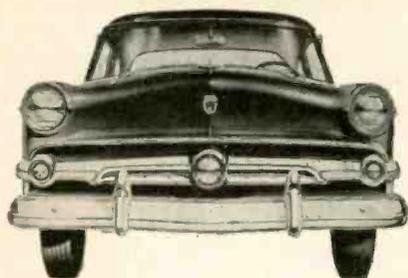

Nothing to buy! Nothing to sell!

Just Illustrate and Explain  
a New Application for  
International Rectifier Corporation  
Selenium Diodes

## 50 PRIZES

### Grand Prize


New Ford V-8 Mainliner Tudor Sedan  
and 49 other  
valuable prizes

**INTERNATIONAL RECTIFIER CORPORATION'S Selenium Diode Application Contest is open to everyone!** Here's all you have to do—pick up an official entry blank from your favorite parts distributor. Illustrate and explain a new practical application for International Rectifier Selenium Diodes. Have the entry blank countersigned by your distributor's salesman and then forward it to us before January 1, 1955. Rules and regulations for this contest are included in the entry blank along with helpful hints on selenium diode applications.

**JUDGES**—Dr. Lee de Forest—United Engineering Labs., Los Angeles, California. J. T. Cataldo, F. W. Parrish—International Rectifier Corp.

### SAMPLE ENTRY

—APPLICATION—

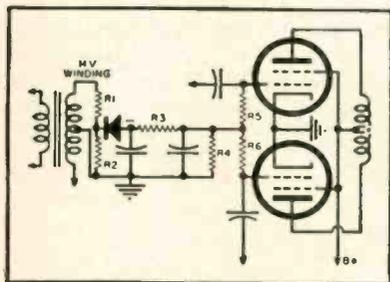

—EXPLANATION—

Typical application for providing fixed bias for push-pull stage of an audio system using International Rectifier Corp. Selenium Diode in conjunction with a voltage divider and filter network... etc.,... etc.

**DON'T DELAY! ENTRY BLANKS ARE AVAILABLE FROM YOUR PARTS DISTRIBUTOR**

CONTEST ENDS JANUARY 15, 1955

**INTERNATIONAL RECTIFIER CORP.  
EL SEGUNDO, CALIFORNIA**

## CBS, RCA Color CRT's

### CBS Colortron 205

The CBS-Hytron Colortron 205 (RETMA type 19VP22) offers viewers 205 sq. in. of picture area on a 19-in. round tube with a glass envelope. This new 3-gun shadow-mask design is electrostatically focused; instead of using an electrostatic convergence system, it incorporates an electromagnetic one.

The deflection angle is 62 degrees; typical 2nd-anode voltage is 25 kv. As in the earlier CBS color tube, phosphor dots are deposited directly on the spherical glass faceplate.

Magnetic convergence is accomplished as follows: 3 pairs of pole pieces are mounted in the tube above the anode and spaced 120 degrees apart. 3 external electromagnets, mounted on the tube neck, create magnetic fields which are induced into the pole pieces to provide dynamic convergence control of each of the 3 electron beams. To compensate for slight variations in manufacturing, small dc fields may also be induced in these pole pieces.

The electromagnets provide adjustment for each of the 3 beams. In case additional adjustment is needed to achieve convergence, an external positioning magnet is provided for one beam, the blue one.

Introductory price of the tube to set makers is \$175.

### RCA 21-in. Tube

A new and improved 21-in. tri-color kinescope with a picture area of 250 sq. in. has been developed by RCA, and will be demonstrated on Sept. 15. The tube has a round metal envelope, is relatively shorter than those produced previously, and is 25% lighter than 19-in. glass color tubes. A filter glass face-plate and new gun provide improved picture contrast.

The most significant improvement is the new RCA curved shadow mask and mounting system, which make possible simplified mechanical mounting in the tube, and greater beam power input during operation without objectionable mask distortion. The phosphor dots are on the face-plate. The manufacturer reports accurate and stable registration, and absence of color impurity around the picture edges.

Introductory price of the tube to equipment manufacturers is \$175.

# SERVICING'S EASY WITH RIDER BOOKS!

## RETMA EXPERTS TELL ALL ABOUT TV SERVICING!

### ADVANCED TELEVISION SERVICING TECHNIQUES

written by the RETMA (Radio Electronic Television Manufacturers' Association) Pilot Training School Teaching Staff.

A completely NEW approach to books for TV service technicians. Written by experts who are teaching every day. The contents have been tried and proven to be the finest ever written. Completely practical. A step-by-step approach to how to service every section of a TV receiver with every kind of test equipment—by resistance measurement, by voltage measurement, by means of the scope. It explains the uses of test equipment of all kinds in connection with TV receiver servicing, such as sweep generators—signal generators—vacuum tube voltmeters—scopes—ohmmeters!

This is not a theory book! It is a book which every technician can use on the bench—and every student in a TV school can use, because it tells what to do and how to do it!



Never a book like this. Words alone can't describe it —you have to see it to believe it! Approx. 175 (8 1/2" x 11") pages. Soft Cover. \$3.60 in Canada, all prices approximately 10% higher.

Write for complete 32 page  
**NEW RIDER CATALOG**

### COMPLETE EXPLANATION COLOR TV TERMS AND DEFINITIONS!



### COLOR TV DICTIONARY

by  
J. R. Johnson

This is more than a dictionary! Over 50 illustrations. Of vital concern to everyone—engineers, service technicians, students, amateurs—interested in color television. Approx. 72 (5 1/2" x 8 1/2") pp. Paper cover.

\$1.25 in Canada, all prices approximately 10% higher. Write for complete 32 page RIDER catalog

### RADIO-TV THEORY REVIEW SERIES



### R-C & R-L TIME CONSTANT

edited by A. Schure, Ph.D., Ed.D. This is the first in a new series of books to help the student or technician brush-up on difficult subjects. Supplements courses on technical institute level. 48 (5 1/2" x 8 1/2") pp. Paper cover. \$ .90 in Canada,

Write for complete 32 page RIDER catalog all prices approximately 10% higher


Buy these books now from your jobber... bookstore. If not available from these sources, write to:

**JOHN F. RIDER PUBLISHER, 480 Canal St., INC. New York 13, N. Y.**

## News of the Industry
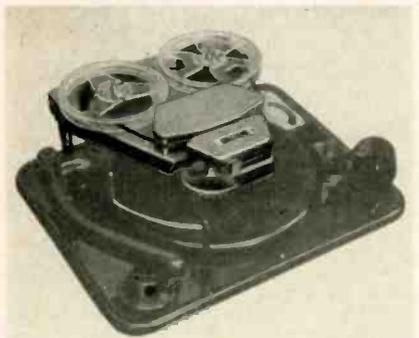
### Low-Priced Tape Playback

Owners of record players can convert these devices to handle pre-recorded tapes with a new non-recording playback-only unit announced by Bell Sound Systems, 555 Marion Rd., Columbus 7, Ohio. The tape player, which is attached to the turntable of any 78-rpm manual record player and may also be mounted on many automatic chang-



ers, is available in 2 models. Frequency response for model 375 (3¾ in. per sec.) goes from 50 to 6500 cps; response for model 750 (7½ ips) ranges from 50 to 10,000 cps. Either unit accommodates 5-in. reels with dual-track tapes and feeds its output directly into equipment designed for standard magnetic phono cartridges. Where a magnetic input is not part of the equipment, the model 2246 pre-amp may be used. The units are only 10 in. square, sell for \$29.95 each.

### Muzak Switches to Tape

Pioneer in the field of functional background music, the Muzak Corp. is converting its operation from one using discs to one relying on tapes. The change-over should be completed this summer. Heart of the new system is a new tape player that accommodates 4800-ft. reels. Subsonic signals recorded on the tape automatically key the following functions: starting, stopping, pre-selection of specialized music, rewinding and changing of tracks. Two such machines used in tandem can go on playing indefinitely. Muzak is now engaged in transcribing its complete disc library of 7,000 pieces to tape.

### RETMA Activities

At a meeting of the RETMA Service Committee, chairman Harold Schulman noted that the cost of servicing will become more important as selling prices of sets are reduced. Technical training, he noted,

is important in the development of an overall improvement in servicing. In addition to making widely available the complete RETMA course for training advanced service technicians, the organization has conducted its first teacher training course at the New York Trade School in July. Thirty teachers in trade and vocational schools attended. Also being considered is a program of community cooperation which will serve to identify technically competent technicians.

### JFD Opens New Lab

Atop the building occupied by JFD Mfg. Co., 6101 16th Ave., Brooklyn, N.Y., is a new penthouse-laboratory built to test antennas under actual use conditions. Headed by chief engineer Doug Carpenter the lab houses a polar recorder, generators, field-strength meters, a transmitter and other equipment for testing antennas. Lining the edges of the roof are experimental antenna designs undergoing try-outs.

### Du Mont Hits Big Networks

Two networks enjoy a virtual stranglehold on TV broadcasting, said Dr. Allen B. Du Mont in a statement filed with the Senate subcommittee holding hearings on UHF problems. FCC stoppage of new-station construction in 1948 left the nation with a large number of operating stations affiliated with either of the two big chains. The freeze, which lasted more than 3 years, gave these networks a head start that has put smaller competing companies at a disadvantage, Du Mont stated.

### NEDA Activities

The 1954 Battery Index, published by the National Electronic Distributors Association, 228 N. La Salle St., Chicago 1, Ill., is available free in single copies, at \$5.75 per hundred in larger quantities. The index uses a single code for identifying batteries of all makes regardless of the manufacturer's numbering system. NEDA is now organizing a meeting with representatives of all manufacturers to check the index. The overall plan is to make certain that batteries now listed as being electrically interchangeable are also physically interchangeable.

Parts and equipment distributors attended a NEDA seminar held in Seattle, Wash., on July 24, 1954. Topics discussed were the impact of color TV on distributors, cost of operation in today's economy and proper selection and training of sales personnel.

## News of the Reps

"THE REPRESENTATIVES" have a new slate of national officers, elected at the annual delegates meeting in New York. New execs, together with chapter affiliations, are: Wally B. Swank, prexy (Empire State); Dean A. Lewis, 1st vice-prexy (California); Ross C. Merchant, 2nd v-p (Wolverine); John J. Kopple, 3rd v-p (New York); David M. Lee, secy. (Pacific Northwest); and Harry Halinton, treas. (Chicagoland) . . . The organization now has 649 members, including 12 in foreign countries . . . **CHICAGOLAND CHAPTER** has also installed new officers: Roy J. Magnuson, prexy; Karl D. Engle, v-p; Helen K. Beebe, secy; and Joe K. Rose, treas.

**GEORGE PETTIT CO.**, 349 N. Ashland Ave., River Forest, Ill., was appointed jobber sales rep for United Catalog Publishers in Illinois, Indiana and Wisconsin.

**EDWIN DURHAM SCHANE, JR.**, Atlanta, Ga., has been added to the staff of the Morris F. Taylor Co., Inc., mfrs' representatives, as a dealer contact man in the southeast.

**GENE PIETY**, 2030 Home Rule St., Honolulu, Hawaii, now represents the Halldorson Transformer Co. in Hawaii.

**M. F. KLICPERA CO.** will represent the Thordarson-Meissner Co. in Oklahoma, Arkansas, Louisiana and Texas . . . The same manufacturer will be represented by the **HYDE SALES CO.** in Montana, Idaho, Wyoming, Utah, Western Nebraska, Colorado and New Mexico.

**FLOYD FAUCETT & SON**, 2380 Sewell Rd., S. W., Atlanta, Ga., will represent Tricraft Products Co. in Virginia, N. & S. Carolina, Georgia, Florida, Alabama, Mississippi and Tennessee.

**BURTON F. HOMSHER**, 2018 Jessie Ave., Fort Wayne, Ind., will cover Indiana and Kentucky for Commercial Products of Toledo, Ohio . . . **WILLIAM B. MOOZA**, National Sales Development Co., 7 E. 42nd St., N. Y. C., will represent the same manufacturer in New England . . . **BARSTOW & DORAN**, 1406 S. Grand Ave., Los Angeles, Calif., will represent C-P in S. California, Arizona and Hawaii.

**PAUL KURTZ CO.**, Detroit, Mich., will contact distributor and industrial accounts in Michigan for the Insuline Corp. of America, Manchester, N. H.

**MARSHANK SALES CO.**, 672 S. Lafayette Pk. Place, Los Angeles, has added 2 sales engineers to its staff. They are **WILLIAM HOOPER** and **E. R. CHAMPION**. Marshank covers southern California, Arizona and southern Nevada.

The  
**ASD**  
Model TV-20



**TELEVISION  
Tube Tester**


- no roll chart
- practically no set-up
- 20 connected sockets

write for details or  
see your distributor

**AMERICAN SCIENTIFIC DEVELOPMENT CO.**  
334-336 S. MAIN ST.  
FT. ATKINSON WISCONSIN

★★★ **INTRODUCTORY OFFER** ★★★

**K.M.S. RADIO, PHONO, and T.V. CRADLE**

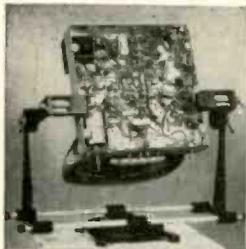

offer good until  
midnight Sep-  
tember 1, 1954  
only

**\$19.95**

Regular price  
there-after  
**\$24.95**

10 day money back guarantee

Introducing the new K.M.S. RADIO, PHONO,  
AND TV CRADLE, never before equalled with  
its rigid, aluminum construction. Its features:

- adjustable to any width chassis
- turntable permits turning chassis without lifting
- friction "L" clamps adjustable for over and under servicing
- portable aluminum construction
- small enough to fit on service bench where instrument leads will reach

25% deposit with order—balance C.O.D.  
shipped f.o.b. Adrian, Michigan  
**JOBBERS INVITED**

Please allow 4 to 6 weeks for delivery

**KEN MILLER SALES**

627 E. Maumee Street  
Adrian, Michigan  
Phone 1475


**ADVERTISERS INDEX**

**AUGUST, 1954**

Alliance Manufacturing Co. ....	60
American Scientific Development Co. ....	63
Astron Corp. ....	31
Caldwell-Clements, Inc. ....	59
Channel Master Corp. ....	12
Cornell-Dubiller Electric Corp. ....	52
Crosley Div., Avco Manufacturing Corp. ....	5
Crown Controls Co., Inc. ....	10
Du Mont Laboratories, Inc., Allen B. ....	41
Federal Telephone & Radia Co. ....	29
Finney Co. ....	45
General Industries Co. ....	53
International Rectifier Corp. ....	61
International Resistance Co. ....	Cover 2
Jensen Manufacturing Co. ....	4
Kester Solder Co. ....	57
Lowell Manufacturing Co. ....	56
Mallory & Co., Inc., P. R. ....	27
Miller Sales, Ken ....	63
Moss Electronic Distributing Co., Inc. ....	57
Philco Corp. ....	6, 7
Precision Apparatus Co., Inc. ....	43
Quietrole Co. ....	59
Radiart Corp. ....	8, 9
Radio Corp. of America ....	Cover 4
Raytheon Manufacturing Co. ....	11
Rider Publisher, Inc., John F. ....	61
Seco Manufacturing Co. ....	59
Shure Brothers, Inc. ....	51
Sprague Products Co. ....	Cover 3
Sylvania Electric Products, Inc. ....	33
Technical Appliance Corp. ....	47
Triad Transformer Corp. ....	63
Triplett Electrical Instrument Co. ....	64
Tung-Sol Electric Inc. ....	54, 55
United Catalog Publishers, Inc. ....	56
United Motors Service Div. of General Motors Corp. ....	2, 3
University Loudspeakers, Inc. ....	49
Walsco Electronics Corp. ....	39

While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.

**FOR THE FINEST  
SOUND SYSTEMS**

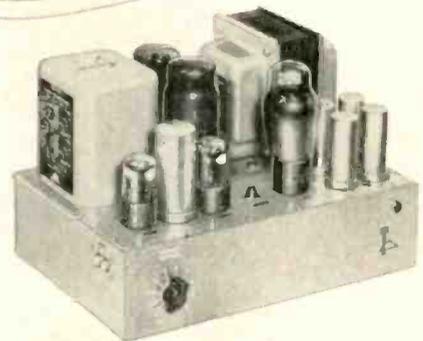

**TRIAD**  
*High Fidelity  
Amplifier Kits*

A home music system which will meet true high fidelity standards must necessarily be composed of the very finest components—pickups, turntables, amplifiers, speakers, enclosures.

In this group of components Triad offers High Fidelity Amplifier Kits—built by men with a brilliant background in producing America's finest transformers. Engineered to produce maximum frequency range with minimum distortion, these "do-it-yourself" kits afford obvious economies over complete units—which permits upgrading of other components in the system.

Triad High Fidelity Amplifier Kits include all necessary transformers and chokes, punched sectional aluminum chassis and complete assembly instructions.

In quality and performance they are fitting companions to the finest sound system components available today.

**HF-3 Kit:** Preamplifier. Adequate gain to drive an HF-40 or HF-18 from any commercial pickup or microphone. D.C. filament supply. Complete record compensation and new tone control circuits. List Price—\$32.80.

**HF-12 Kit:** 10-watt power amplifier. Replaces HF-10. Built-in preamp to accommodate all crystal and magnetic cartridges. Complete record compensation and new tone control circuits. Output Impedances 4-8-16 ohms or 125-250-500 ohms. List Prices from—\$50.40.

**HF-18 Kit:** "Williamson" type all-triode amplifier. Full power output of 16.2 watts for triode operation or 20 watts for pentode operation from 12 to 60,000 cycles. Frequency response within 0.2 db from 7 to 80 kc. Output Impedances 4-8-16 ohms or 125-250-500 ohms. List prices from—\$63.65.

**HF-40 Kit:** Features a full 40-watt amplifier from 20 to 40,000 cycles, using regulated screen voltage and fixed bias on two 6146 output tubes. Output Impedances 4-8-16 ohms or 125-250-500 ohms. List from—\$78.35.



Write for  
Catalog  
TR54K



4055 Redwood Ave. • Venice, Calif.




## PAUL H. WENDELL

EDITOR AND PUBLISHER OF

## SERVICE MANAGEMENT

WRITES ABOUT

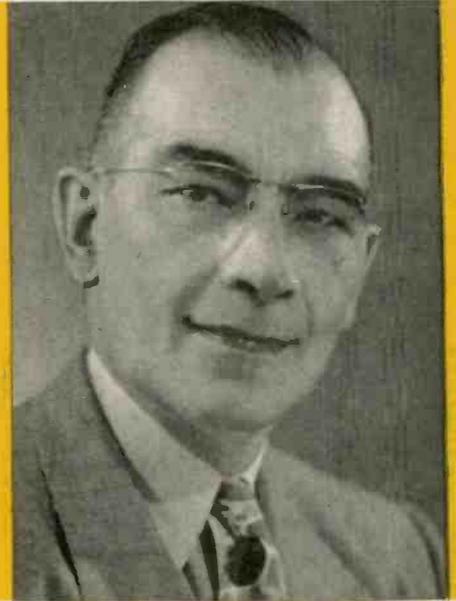


# THE MARK of the PROFESSIONAL

“... **I**n the television service shop of today an observer can quickly spot the expert professional technician by observing his *modus operandi* or manner of working. The tools of his profession are scopes, signal generators, tube testers and vacuum tube voltmeters. They are there at his fingertips—not for use on occasional jobs, but for consistent use on all jobs.”

Reprints of Mr. Wendell's complete article "The Mark of the Professional" are available at no cost from your parts jobber or from Triplett Electrical Instrument Co., Bluffton, Ohio.

## TEST EQUIPMENT STANDARDS ARE SET BY

TRIPLETT

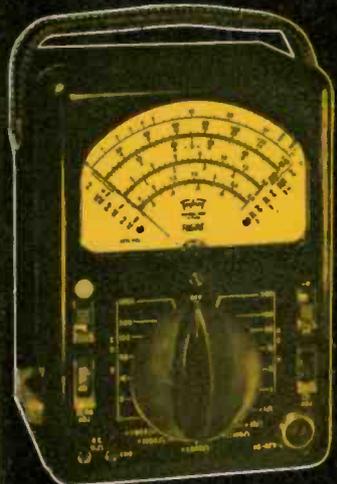

Model 650. Vacuum Tube Voltmeter \$69.50 net. One probe ACV and RF peak to peak measurements. One selector switch all ranges.



Model 3413-A. Tube Tester \$79.50 net. The only tester in its price range to get at each tube pin and make an open and short check.



Model 3436 UHF Marker-Signal Generator \$169.50 net. For calibrating front ends and converters—all that is needed in *one* instrument.



Model 3441 Oscilloscope \$199.50. Peak-to-Peak Voltmeter. Exclusive reversible clarity simplifies wave form reading.

# capacitor replacements

## FOR SETS OF THE MONTH

### DUMONT CHASSIS RA-312, 313

Symbol No.	Rating MF @ WVDC	DuMont Part No.	Sprague Replacement
C286	80+40+10+4 @ 350	03151425	{ TVL-3792 TVA-1601
C287	10 @ 450/80+10 @ 350/ 10 @ 50	03151426	{ TVL-4675 TVA-1705
C288	5 @ 100	03138362	TVA-1402
N201	Integrator Plate	88000631	V-1

### RCA CHASSIS KCS88J, KCS88K, KCS88L, KCS88M, KCS88VA

Symbol No.	Rating MF @ WVDC	RCA Part No.	Sprague Replacement
C114	100 @ 250	79314	TVL-1535
C132	80 @ 400/80 @ 200	79147	<sup>1</sup> TVL-3764
C134	100 @ 400/30 @ 50	79146	<sup>2</sup> TVL-3672

#### NOTES

- <sup>1</sup> Parallel 40 MF sections  
<sup>2</sup> Parallel 10 MF and 20 MF sections

### RAYTHEON CHASSIS 17T18, 21T19

Symbol No.	Rating MF @ WVDC	Raytheon Part No.	Sprague Replacement
C219	25 @ 450/100+10 @ 300/ 60 @ 50	8C-23689	{ TVL-3574 TVA-1711
C504	150 @ 150	8C-22463	TVL-1430
C505	150 @ 150	8C-22464	TVL-1430
C305	Integrator Plate	17A-22376	V-1

### ADMIRAL CHASSIS 21A3Z

Symbol No.	Rating MF @ WVDC	Admiral Part No.	Sprague Replacement
C204	4 @ 50	67A4-9	TVA-1303
C411	20 @ 300	67A4-18	TVA-1608
C501	100+60 @ 350/20 @ 200	67D15-105	<sup>1</sup> { TVL-3640 TVA-1613
C503	40 @ 300	67A4-19	TVA-1611
C504	80+10 @ 200/20 @ 50	67D15-106	<sup>2</sup> TVL-4579
M401	Integrator Plate	63C6-9	V-1

#### NOTES

- <sup>1</sup> Parallel 60 MF and 40 MF sections  
<sup>2</sup> Parallel 40 MF sections

### MAJESTIC CHASSIS 115, 116

Symbol No.	Rating MF @ WVDC	Majestic Part No.	Sprague Replacement				
C36A C58A C92A C141A	40+40+4+4 @ 450	C-5.435-3	{ TVL-3785 TVA-1702				
C70C C73C C89C C95C			40+40+4+4 @ 450	C-5.435-3	{ TVL-3785 TVA-1702		
C72G C139G					100+25 @ 50	C-5.429-2	{ TVA-1310 TVA-1306
C93B C94B C106B							40+40+8 @ 450
C63, C64, C65 R65, R66, R67	Integrator Plate	B10.101			V-1		
C138, R129, R130	Triode Coupling	B10.103	T-1				

## SPRAGUE "T-C" RULE



Use this handy pocket-size Sprague Temperature Coefficient Rule to find quickly the values of stock N750 and NPO type ceramic capacitors to connect in parallel to equal a capacitor of desired intermediate temperature coefficient of the required capacitance.

## COLOR CODE CHARTS

Complete charts for color codes on all types of ceramic capacitors are on the back face of this rule.

Get your Sprague "T-C" Rules now from your Sprague distributor, or directly from Sprague Products Company, 65 Marshall Street, North Adams, Massachusetts. They're only 15¢ each.

Sprague makes more capacitors . . . in more types . . . in more ratings . . . than any other capacitor manufacturer. Send 10c for 48-page TV Replacement Capacitor Manual to Sprague Products Co., 65 Marshall St., North Adams, Mass., or get it FREE from your Sprague distributor.

**DON'T BE VAGUE...INSIST ON**

# SPRAGUE

(Distributors' Div. of the Sprague Electric Co.)


# They look alike...




...but what a difference!

## These RCA types today give you . . .


LONGER LIFE

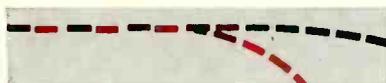

SUPERIOR PERFORMANCE

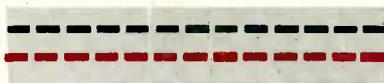

AT NO EXTRA COST

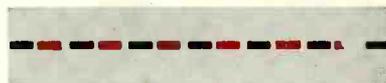

Here are 3 more examples of how regular RCA receiving tubes are constantly being improved to meet the changing requirements of radio and television applications. These RCA types provide you with the superior performance usually claimed for higher priced specialty designed types.

**RCA-6J6** features pure tungsten heaters for improved life . . . uses a special cathode material to help maintain characteristics throughout the life of the tube. Each tube mount is adjusted to provide increased uni-

formity of characteristics of each triode unit.

**RCA-6CB6** uses a No. 2 grid of improved design, resulting in lower grid operating temperature and longer tube life. Special controls on materials and processing improve uniformity of plate cutoff and reduce variations in characteristics when heater voltage fluctuates.

**RCA-6AU6** uses a double helical heater, resulting in an extremely low hum level. Inverted pinched cathode reduces possible motion of tube ele-

ments thus minimizing microphonics.

The superior performance of *regular* RCA receiving tubes—at *regular* prices—eliminates unnecessary call-backs, assures you of greater customer satisfaction, results in increased profits for you.

✓ ✓ ✓

When you sell a receiving tube, your reputation and profit depend on its *performance* and *reliability*. So, you can't afford to buy anything less than the best in receiving tubes . . . and the best are RCA.



**RADIO CORPORATION of AMERICA**  
ELECTRON TUBES

HARRISON, N. J.