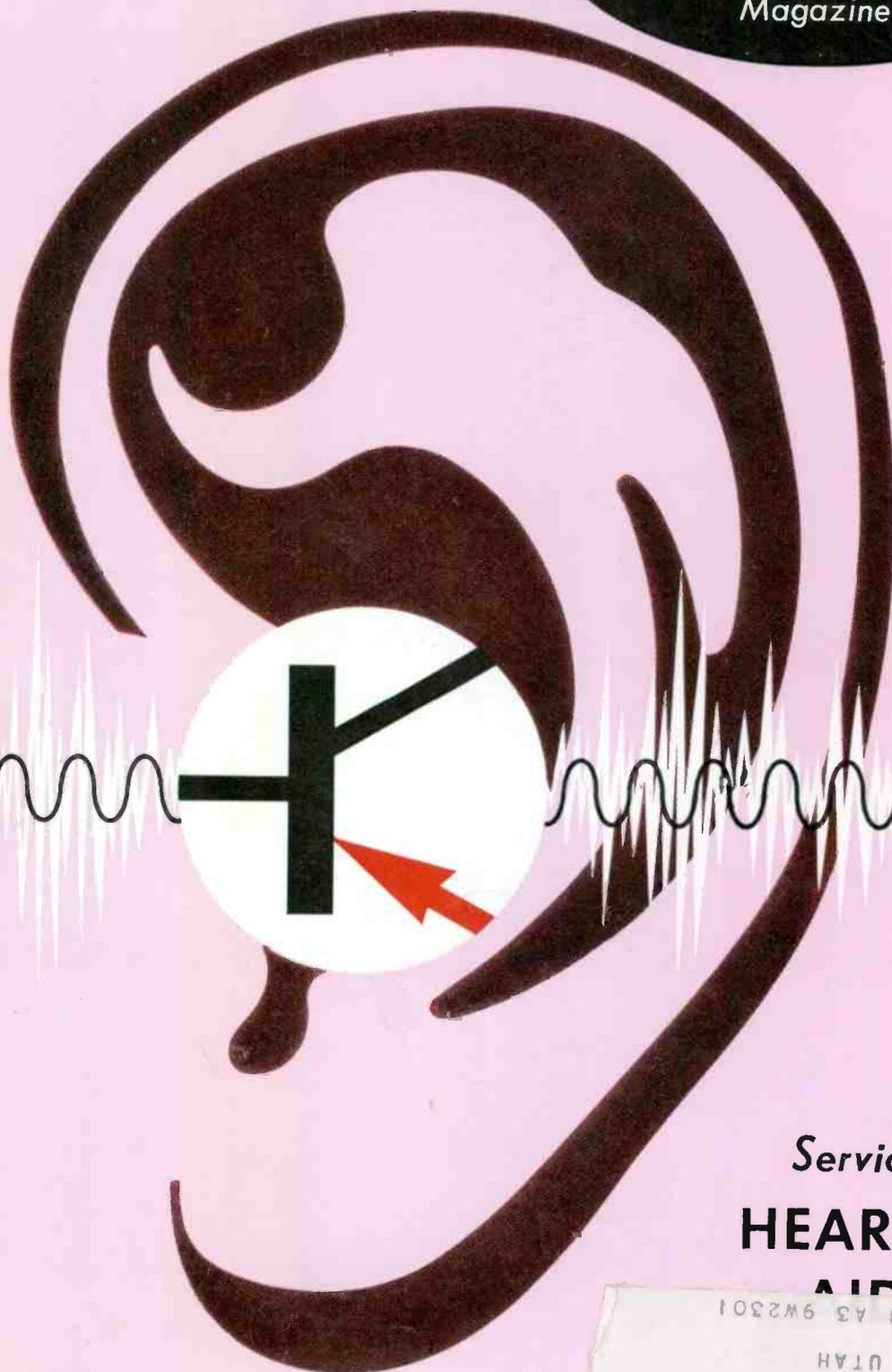


ELECTRONIC TECHNICIAN

Including
SERVICE
Magazine



Servicing
**HEARING
AIDS**

60¢
February • 1961

111-61N AS 9W2301
JOSEPH UTAH
BOX 42
WALDO M OWENS

Make your profit picture
"BRIGHT AND WIDE"



with Sylvania 6DQ6A and 6BQ6GTA

New improvements provide long life, high output, excellent high voltage cutoff.

Tube performance and life can mean the difference between a bright and dismal profit picture. Let's look at some of the proved-in-the-set Sylvania features:

Plate current capabilities have been increased. Plate to screen current ratio has been improved. A special screen-grid coating provides excellent heat dissipation eliminating interelement shorts without causing cathode "poisoning"—a major cause of short tube life. Tests for voltage breakdown, heater and tube life add up to extra quality assurance. The famous Sylvania "Automount" construction is used for the 6DQ6A.

Result: Sylvania 6BQ6GTA and 6DQ6A

- Deliver the horizontal output essential to full picture width.
- Increase picture tube light output.
- Offer extra-long life in TV set.

Here's a servicing plus: tapered pins provide easy insertion in hard-to-get-at sockets.

Make your servicing profits brighter . . . right now. Specify Sylvania 6BQ6GTA and 6DQ6A on your next tube order.

Electronic Tubes Division, Sylvania Electric Products Inc., Dept. 212
1740 Broadway, New York 19, N. Y.



SYLVANIA

Subsidiary of **GENERAL TELEPHONE & ELECTRONICS**



ELECTRONIC TECHNICIAN

Including
SERVICE
Magazine

World's Largest Electronic Trade Circulation

ALBERT J. FORMAN *Editor*
ARTHUR P. SALSBERG *Managing Editor*
JACK HOBBS *Technical Editor*
B. V. SPINETTA *Assistant Editor*
HARVEY WETZLER *Assistant Editor*
ROBERT TALL *Washington Editor*
C. F. DREYER *Art Director*
M. FARRIS *Editorial Assistant*



Address all mail to
480 Lexington Ave., New York 17, N. Y.
Telephone YUkon 6-4242

HOWARD A. REED *Publisher*

BUSINESS DEPARTMENT

R. L. KIPP *Eastern Sales Manager*
N. McALLISTER *Production Manager*
M. RUBIN *Circulation Manager*
M. KANE *Accounting Manager*
A. MOYLAN *Accounting Supervisor*

P. H. DEMPERS JR. *Regional Manager*
10 E. Huron St., Chicago 11, Ill.
Telephone MIchigan 2-4245

CHRIS DUNKLE & ASSOCIATES
California Representative
740 S. Western Ave., Los Angeles 5, Calif.
Telephone DUmkirk 7-6149
420 Market St., San Francisco 11, Calif.
Telephone SUtter 1-8854

BERNIE EDSTROM *Regional Manager*
15605 Madison Ave., Cleveland 7, Ohio
Telephone LAkewood 1-7900

JOHN R. KIMBALL & CO.
Mountain States
420 Market St., San Francisco 11, Calif.
Telephone DOuglas 2-9183



ELECTRONIC TECHNICIAN & Circuit Digests, including Service, February 1961. Vol. 73, No. 2. \$.60 a copy. Published monthly by Electronic Technician, Inc. Publication Office, Concord, N. H. Editorial, advertising and executive offices, 480 Lexington Avenue, New York 17. Telephone YUkon 6-4242.

Entered as Second-class matter at the post-office at Concord, N. H., October 19, 1960. Subscription rates: United States and Canada, \$5.00 for one year; \$8.00 for two years; \$10.00 for three years. Pan American and foreign countries: \$9.00 for one year; \$14.00 for two years; \$18.00 for three years. Copyright 1961 by Electronic Technician, Inc., New York. H. Reed, President, A. Forman, Executive Vice-President. Title registered in U. S. Patent Office. Reproduction or reprinting prohibited except by written authorization of publisher. Printed in U.S.A. by Rumford Press, Concord, N. H.

February, 1961

FRONT COVER Since transistorized hearing aids are essentially miniature transistor amplifiers, experienced service techs should not encounter great repair difficulties. Though many replacement parts are available from regular electronic distributors, some special parts must be ordered from specialty distributors or manufacturers. Circuit operation, servicing, and special parts sources are discussed in the article starting on page 30.



FEATURES and ARTICLES

"Tuning in the Picture"	14
Improving TV Set Serviceability; Those Long Warranties (Editorials) ..	27
TV Manufacturers Technical Digest	28
Servicing Transistorized Hearing Aids	L. G. Sands 30
"Tough Dog" Corner	M. F. McWilliams, Elmer Woods 33
Misconceptions in TV Servicing	Wayne Lemons 34
Electronics in Photography	Lee Craig 36
Get Ready for Stereo Multiplexing	Alan Andrews 38
Shop Hints	Jack Darr, R. R. Fitzmaurice, H. J. Miller, G. F. Stillwell 41
Hand-Wired Chassis Soldering Problems	George Kravitz 42
Free Literature	46

DEPARTMENTS


Editor's Memo	2	Reps. & Dists.	18
Letters to the Editor	6	Catalogs & Bulletins	20
Calendar of Coming Events	15	Audio Newsletter	24
News of the Industry	16	Association News	48
New Books	62		

CIRCUIT DIGESTS

Preceding Back Cover

IN THIS ISSUE

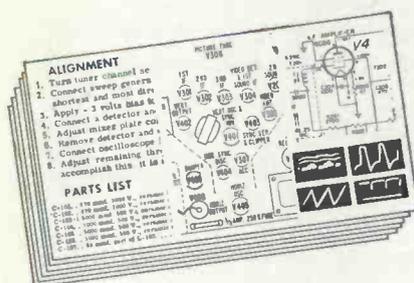- (16 pp. latest schematics & data)
- ELECTROHOME: TV Model "Selkirk"
- EMERSON: Air Purifier Ionizer Model EP-40
- GENERAL ELECTRIC: Transistor Radio Models CT110, CP775
- MONTGOMERY WARD: TV Models WG-4225A, WG4325A
- MOTOROLA: TV Chassis TS-5T5 & WTS-435
- RCA: Reverberation Amplifier Chassis RS-194A
- ZENITH: TV Chassis 16F23, 16F23Q



JUST RIGHT

for Profit-Minded Service Technicians



\$335.00

JACKSON 600

for wide band or high sensitivity operation

Your profit potential goes up when you're equipped with a new Jackson 600 Oscilloscope. You can do all these jobs:

- Peak to peak voltage measurements
- Square Wave Testing from 10 cycles to 200 KC
- Modulation Checks
- Transformer Ringing
- Low Frequency Measurements
- Checking Audio and Video Distortion low frequency and high frequency response... phase shift.

This is a fine quality instrument "service-engineered" by Jackson to best suit the needs of the really active radio and TV Service Technician.

SPECIFICATIONS:

Linear Sweep:

10 cycles to 100 KC

Sensitivity:

20 mv/inch

Wide Band

Vertical Amplifier:
Flat within 1 db from
less than 10 cycles
to 4.9 MC.

Ask your electronic distributor to demonstrate a Jackson 600 or write for Bulletin 106.



ELECTRICAL INSTRUMENT COMPANY

124 McDonough St., Dayton, Ohio

In Canada: The Canadian Marconi Co.

For more data, circle 2-2-1 on coupon, p. 46

Editor's Memo



As long as you know you are right, it pays to stick to your guns, even when the majority says you are wrong.

Some of the greatest successes were the very people who were dissenters by nature, and perhaps even a bit cantankerous. People who see the significance of new trends and new ideas and act effectively, are way out ahead.

We have been talking with a TV-appliance dealer who is also in communications service. When he started his business back in the '30s, many people told him that it would never come to much. Perhaps these very people are among those who heap envious praise and follow behind him today.

When you see an opportunity which demands only moderate risk, grab it. Trying to mimic a competitor who is trying at the same time to mimic you, is no avenue for success.

The more initiative an employee shows, the more responsibility will come his way. That's what supervisory people are really paid for—responsibility. Of course, before a man can be a top-notch manager, he should have a solid background of practical experience. That way he will know what to expect from the people working under him.

Among the responsibilities assumed by growth-minded firms is to have faith in its own aspirations, and to fight for them boldly. It's amazing how the doubters and detractors become your boosters... once you've proved yourself.


An interesting story is told about a famous fighter of yesteryear.

Some fifty-odd years ago, when "Gentleman" Jim Corbett had turned to entertaining after a notable prize fighting career, and made a greater financial success of the stage than the ring had ever afforded, he used to tell this story.


"When I first started to fight, and the chances for success looked very remote, Dad would admonish me to quit the ring and find a steady job so that I could settle down. He used to say, 'Son, remember this, a rolling stone gathers no moss.'

"On the night I won the championship, Dad was seated at ringside. As soon as the fight was over, he jumped into the ring. He was beaming. He grabbed me and slapped me on the back. 'My boy,' he said, 'tis just like I always told you. It's the roving bee that gets the honey.'"

Al Forman

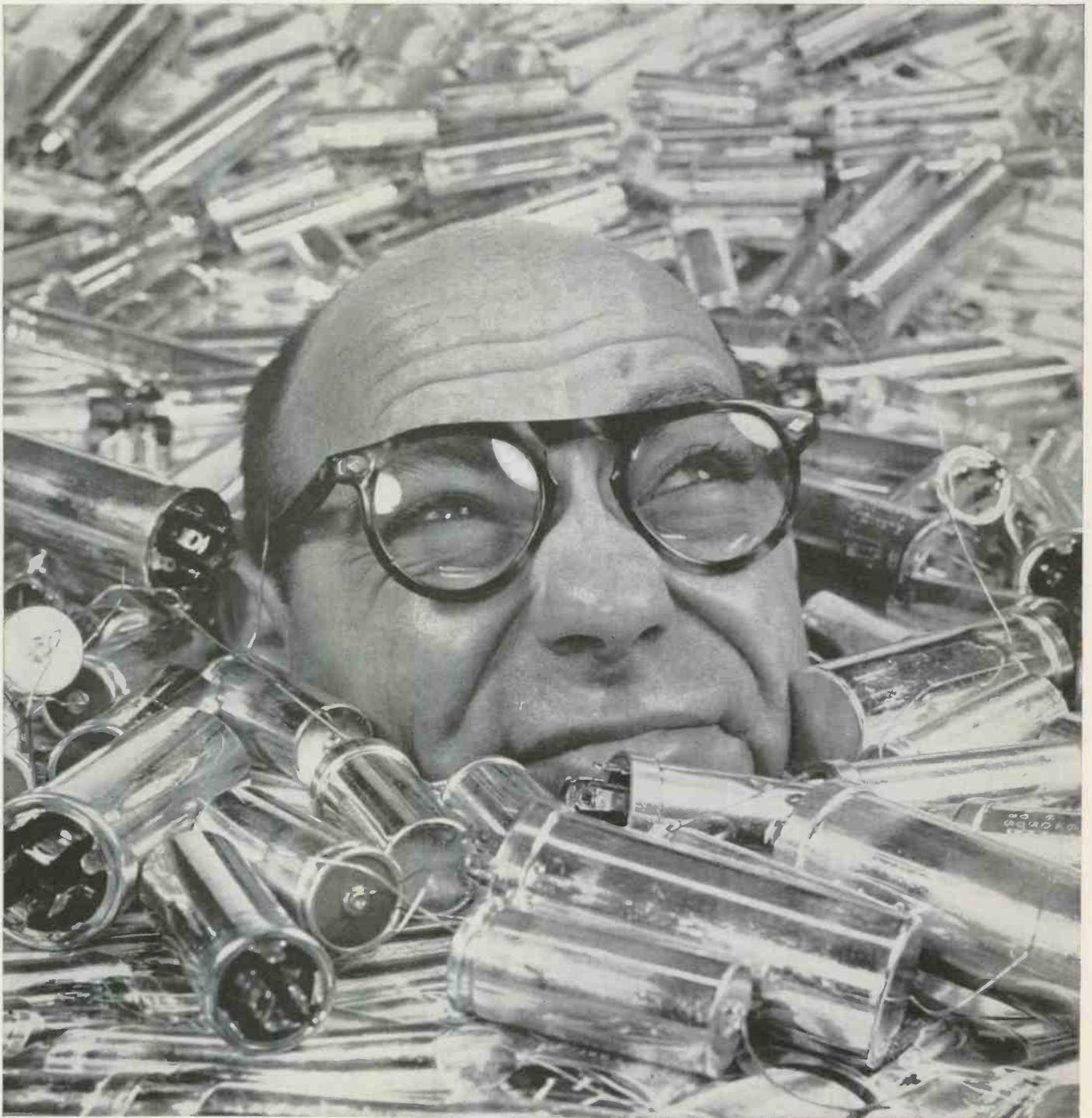

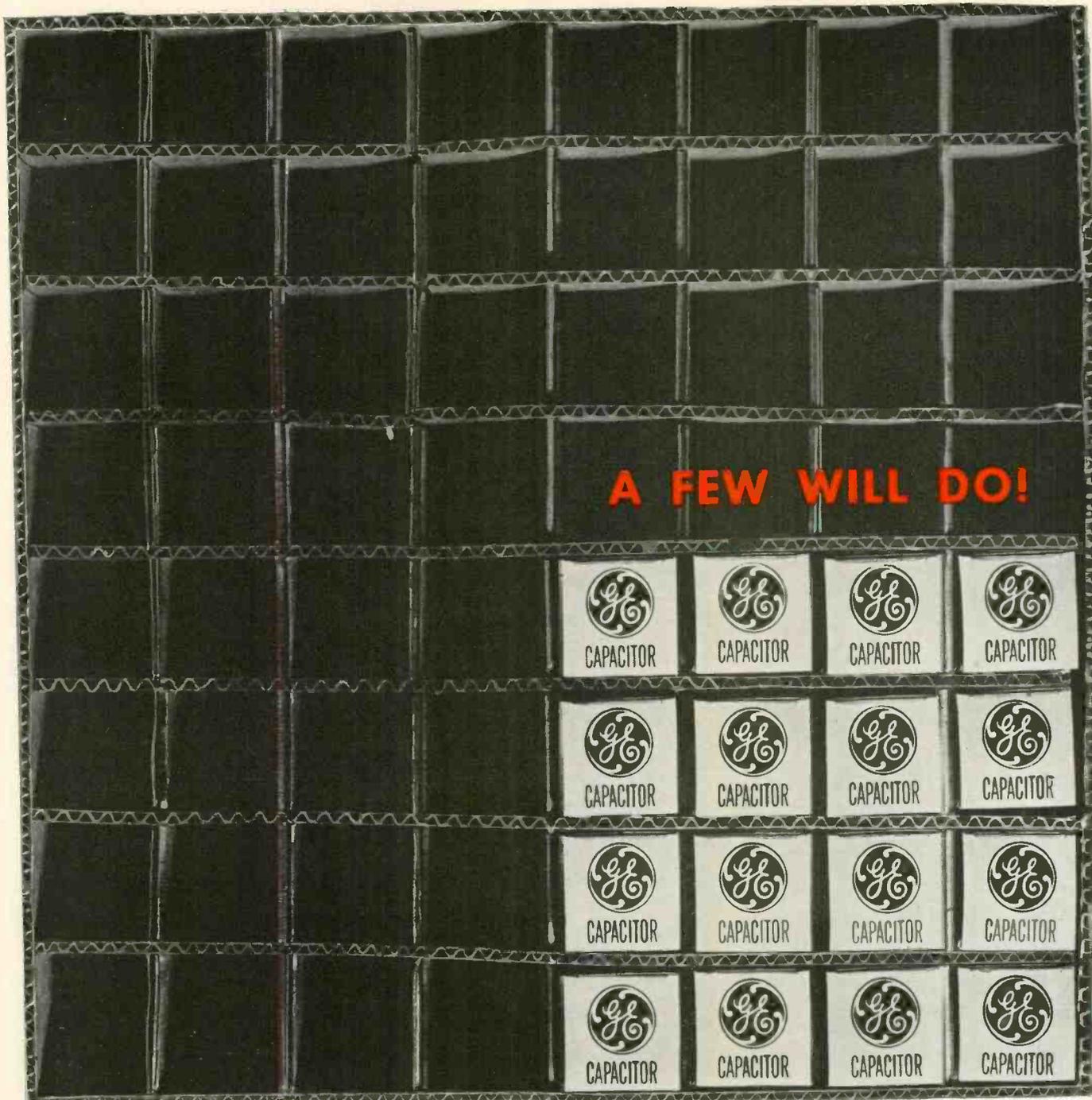GENERAL ELECTRIC TAKES
THE **CONFUSION** OUT OF THE
CAPACITOR BUSINESS!



A FEW WILL DO!





New G-E Capacitor line includes Tubulars, Twist-Prong and Miniature Electrolytic and Paper-Mylar® types

General Electric's new line of Service-Designed Capacitors slashes from 1,200 to just 295 the total number of types necessary to make all aluminum electrolytic capacitor replacements! In fact, you will be able to meet 70% of your replacement needs with just 20 types!

General Electric, long a leading manufacturer of original equipment capacitors, has cut the number of types needed for replacement by eliminating the needless duplication and overlapping of many present ratings. Through its new extended-range concept, similar to the one servicemen are already using in replacing rectifiers, G-E has taken the confusion out of making capacitor replacements!

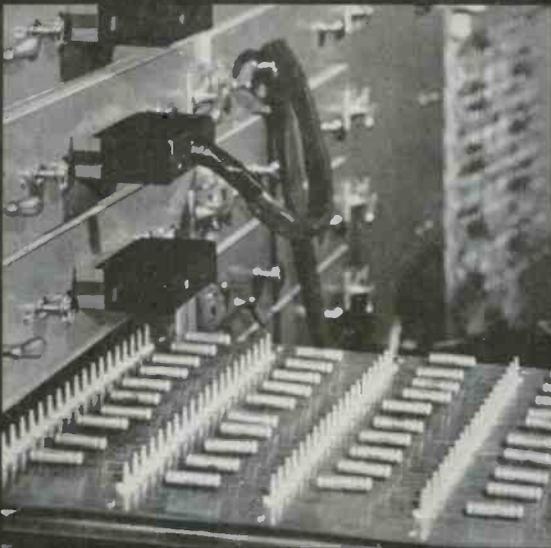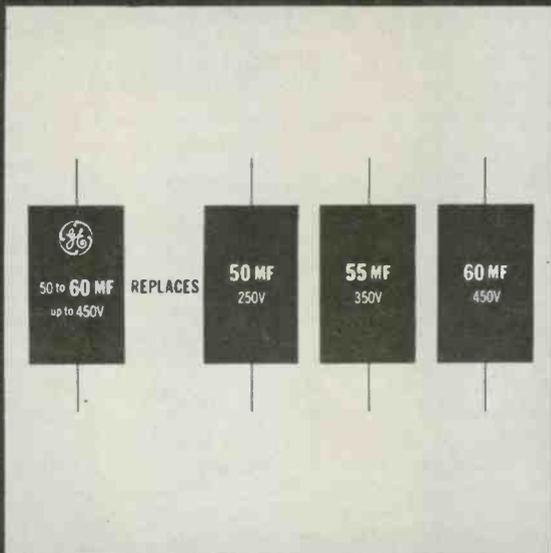Whether you stock capacitors yourself or order them as needed from your distributor, you will be able to simplify your purchasing and increase your profits on every capacitor replacement you make—because General Electric capacitors are Service-Designed with *you* in mind!



NEW G-E SERVICE-DESIGNED CAPACITORS

1. CUT NUMBER OF TYPES BY 75%! You can meet all your needs with fewer types because every G-E capacitor meets not just one, but a range of capacitance and voltage requirements. One G-E capacitor rated "50-60 mfd up to 450 V," for example, will replace any capacitor rated 50, 55 or 60 mfd at *any* voltage up to and including 450 V.

2. MEET MOST NEEDS WITH SMALL STOCK! For the first time it's possible to meet most replacement needs with a small number of units. The 14 tubular types in this Stock-Saver Kit, for example, will meet 9 out of 10 tubular electrolytic replacement needs! And you can buy this kit now from your G-E capacitor distributor at a greatly reduced introductory price!

3. LAST LONGER ON SHELF AND IN SERVICE! Because all G-E Alumalytic[®] capacitors are made with 99.99% pure aluminum foil, their lower-leakage currents reduce

the chances that you'll ever get a "dud" from your distributor! G-E leadership in advanced-design capacitors for critical military applications brings you unmatched quality.

4. FREE 100%-COMPLETE REPLACEMENT GUIDE! The most complete catalog and replacement guide ever published shows you in a flash which G-E capacitor replaces *any* capacitor used in *any* radio or TV set in the past ten years! For your free copy, see your G-E capacitor distributor or write General Electric Company, Electronic Components Division, Owensboro, Kentucky.

Progress Is Our Most Important Product

GENERAL  ELECTRIC

For more data, circle 2-5-1 on coupon, p. 46

from **EICO**... a completely new
CITIZENS BAND TRANSCEIVER

that meets
FCC regulations*



Model 750: 117 VAC
Kit \$59.95 Wired \$89.95
Model 761: 117 VAC & 6 VDC { Kit \$69.95
Model 762: 117 VAC & 12 VDC { Wired \$89.95
incl. mtg. bracket (Pat. Pend.)

*EICO premounts, prewires, pretunes, and seals the ENTIRE transmitter oscillator circuit to conform with FCC regulations (Section 19.71 sub-division d). EICO thus gives you the transceiver in kit form that you can build and put on the air without the supervision of a Commercial Radio-Telephone Licensee!

Highly sensitive, selective SUPERHET (not regenerative) receiver with 5½ dual function tubes and RF stage. Continuous tuning over all 23 bands. Exclusive Super-Hush® noise limiter. AVC. 3" x 5" PM speaker. Detachable ceramic mike. 5-Watt crystal-controlled transmitter. Variable "pi" network matches most popular antennas. 12-position Posi-Lock® mounting bracket. 7 tubes and 1 crystal (extra xtals \$3.95 each). Covers up to 20 miles. License available to any citizen over 18—no exams or special skills required, application form supplied free. Antennas optional.

YOU PROFIT WITH EICO

Everything in top-quality
TEST EQUIPMENT for Shop
and Field—at savings of 50%.



COLOR & Mono DC-5MC
Lab & TV 5" Oscilloscope #480
Kit \$79.95, Wired \$129.50
5" Push-Pull Oscilloscope #425
Kit \$44.95, Wired \$79.95



Peak-to-Peak VTVM #232 & UNI-PROBE®
Kit \$29.95, Wired \$49.95
*U. S. Pat. No. 2,790,051
Vacuum Tube Voltmeter #221
Kit \$25.95, Wired \$39.95

More typical EICO values: Signal Generators from \$19.95, Tube Testers from \$34.95, Sweep Generators from \$34.95, Power Supplies from \$19.95, VOMs from \$12.90.

Everything in CUSTOM HI-FI:
finest quality at 1/3 the cost.



FM Tuner HFT90
Kit \$39.95, Wired \$65.95
Cover \$3.95, Includes FET.
AM Tuner HFT94
Kit \$39.95, Wired \$65.95
Includes Metal Cover and FET.
FM/AM Tuner HFT92
Kit \$59.95, Wired \$94.95
Includes Metal Cover and FET.



Stereo Dual Amplifier-Preamp HF81
Kit \$69.95, Wired \$109.95
Includes Metal Cover.
Stereo Dual Amplifier AF4
Kit \$38.95, Wired \$64.95
Includes Metal Cover.

Write for free catalog ET-2 and name of nearest distributor.
Most EICO distributors offer budget terms.



3300 N. Blvd., L.I.C. 1, N. Y.
Add 5% in the West

For more data, circle 2-6-1 on coupon, p. 46

LETTERS
To the Editor

Is Tele-Vue For You?

Editor, ELECTRONIC TECHNICIAN:

In reply to Mr. Joseph Obiecunas' Dec. letter asking how good Tele-Vue Trouble-Shooter charts are, we have used these charts for about a month. Briefly, they break down into a series of symptoms concerning such common difficulties as snowy picture, loss of sync on strong station, loss of sync period, picture pull, etc., etc. They list a series of checks to make, starting with the most obvious and progressing to the more complicated. Each chart also contains a typical portion of a schematic of the circuit most likely to be affected by the trouble concerned. Each chart also has a picture showing the screen as a picture would appear when this difficulty is present.

I would say, from a technician's viewpoint, that they are helpful, but they are not a substitute for a good background of technical knowledge. They do not in short, say, replace this condenser or that resistor, but rather take this resistance check or that voltage check, or make this alignment. I personally believe they are worth the money.

STANLEY J. PEPERA,
Service Manager

Video TV & Appliance
Saginaw, Mich.

... The system is decidedly worthwhile. I have a set of 50 cards and convenient holder and the day it arrived, I was working on a real "dog". I had spent an hour, and the card found the trouble in less than 10 minutes.

JOHN B. DOWDEN

Glen Cove, N. Y.

... Tele-Vue Trouble-Shooter is a series of antiquated and certainly over priced charts. There are others on the market that are more informative and less expensive.

MONAHAN TV

Bayonne, N. J.

... I like my Tele-Vue.

WALTER BERTUCCELLY

Bert's Radio & TV Repair
Linden, N. J.

... It is ok as far as it goes.

W. H. HOLLEY

Atkinson, N. C.

... I have a set that he can have for half price It would be like a gift for me to get that. There is nothing that takes the place of experience.

FRANK LONG

Frank's TV Service
Vancouver, Wash.

... Mr. Obiecunas need have no qualms as to the worthiness of this troubleshooting method.

HAROLD H. RADINZ

Green Bay, Wisc.

... I have been using it for some time now and keep it handy at the workbench. It refreshes your memory and gives you over a dozen things to do to solve some tough problems. I find it most helpful.

RUSSELL G. MARSHALL

Chicago, Ill.

(Continued on page 10)

TUBES GET THERE FASTER



Shipping parts or entire sound units? Remember, speedy shipment of delicate goods is a specialty of Greyhound Package Express. Shipments going hundreds of miles can arrive *the same day they're sent!* Whatever the destination of your shipment, chances are, a Greyhound is going there anyway... *right to the center of town.* Greyhound travels *over a million miles a day!* No other public transportation goes to so many places—so often.

You can ship anytime. Your packages go on regular Greyhound passenger buses. Greyhound Package Express operates twenty-four hours a day... seven days a week... *including weekends and holidays.* What's more, you can send C.O.D., Collect, Prepaid... or open a charge account.

CALL YOUR LOCAL GREYHOUND BUS TERMINAL TODAY...OR MAIL THIS CONVENIENT COUPON TO:

GREYHOUND PACKAGE EXPRESS
Dept. B-17, 140 S. Dearborn St., Chicago 3, Illinois

Gentlemen: Please send us complete information on Greyhound Package Express service... including rates and routes. We understand that our company assumes no cost or obligation.

NAME _____ TITLE _____
COMPANY _____
ADDRESS _____ PHONE _____
CITY _____ ZONE _____ STATE _____


IT'S THERE IN HOURS...AND COSTS YOU LESS!

For more data, circle 2-7-1 on coupon, p. 46

The growth of the entire Electronic Service Business
is reflected in famous

PHILCO Industry Firsts

Just Plug in and Play!

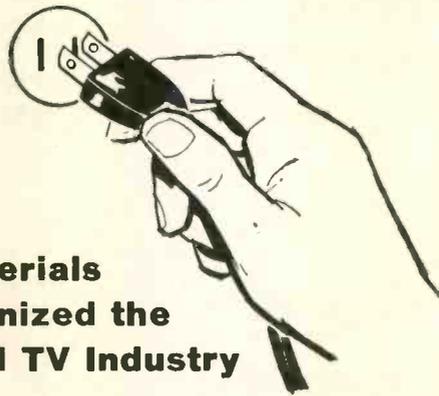

**Philco
Built-In Aerials
Revolutionized the
Radio and TV Industry**

In 1949, Philco introduced the first built-in aerial for television. Overnight, it took the aerial off the roof and the roof off of TV sales, and came just 10 years after Philco's famous built-in aerial for radio. These developments opened up vast new markets, with increased profit opportunities for you. Similarly, the proven reliability of Philco parts, tubes and accessories protects your profits, and builds good will.

For all your servicing needs, look to **PHILCO**
THE FIRST NAME IN ELECTRONICS... THE LAST WORD IN **QUALITY**



SEE YOUR PHILCO DISTRIBUTOR

PHILCO Accessory Division

WORLD-WIDE DISTRIBUTION

Service Parts • Power-Packed Batteries • Universal Components • Long-Life Tubes • Heavy-Duty Rotors • Star-Bright 20/20 Picture Tubes • Long-Distance Antennas • Appliance Parts • Laundry Parts • Universal Parts and Accessories

PHILCO




Famous for Quality the World Over

DON'T MISS THESE

FREE BONUS OFFERS

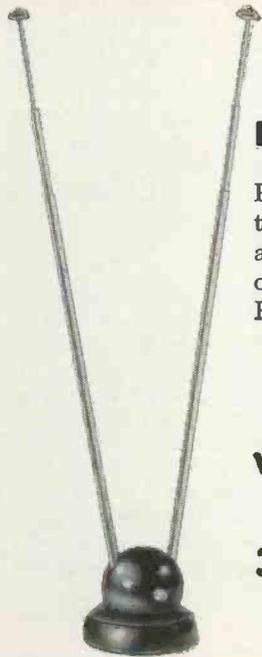with your purchases of quality-first
PHILCO® receiving tubes



DELUXE INDOOR ANTENNA

Philco 3-section telescoping antenna on non-tilting base. Every antenna you get on this bonus offer means extra profits for you. Part No. 426-0014.

FREE
with your purchase
of just
15 PHILCO TUBES



DELUXE ROTARY SWITCH ANTENNA

A real Philco profit-maker for you! 3 brass elements; 6-position switch. Non-tipping, heavy, cast iron base. Part No. 426-0019.

FREE
with your purchase
of just
25 PHILCO TUBES

\$350 NET VALUE TRACE KIT

Revolutionary Philco development simplifies transistor radio servicing—pinpoints faults in 3 easy steps. Kit includes 9 panels for current Philco models.

FREE
with your purchase
of just
**35
PHILCO
TUBES**



PHILCO \$7950 NET VALUE TUBE TESTER

Philco Model 9200. Checks emission, leakage, and continuity. Includes 10-position selector for checking all tube types, pin straightener, and handy roll chart. Made in U.S.A.

FREE
with your purchase
of just
**500
PHILCO TUBES**



LIMITED TIME ONLY

SEE YOUR **PHILCO**® DISTRIBUTOR

Biggest Soldering Gun Value on the market!

MODEL 8100B

**NEW
DESIGN**
and new
low price from


Weller

...and
it's
only **\$644**
LIST PRICE



Check these advanced features:

- ✓ New Long-Life Wellertip—Utilizes copper for superior heat transfer, plus iron-plating for rigidity and long life. Copper conducts heat 5 times faster than steel, permits operation at lower temperature, prevents damage to components. Long reach for easier use in difficult places.
- ✓ 100 watts—single heat
- ✓ Tip heats instantly when trigger is pulled—no waiting
- ✓ Prefocused spotlight illuminates work, eliminates shadows
- ✓ New compact, streamlined design with rugged housing
- ✓ Perfect balance for greatest soldering accuracy
- ✓ Guaranteed for 1 year—UL approved

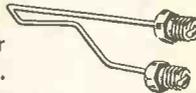

On sale now at your Electronic Parts Distributor

Send for Weller Gun Bulletin

WELLER ELECTRIC CORP. 601 Stone's Crossing Rd.
Easton, Pa.

For more data, circle 2-10-1 on coupon, p. 46

(Continued from page 6)

Readers React

Editor, *ELECTRONIC TECHNICIAN*:

In your letters to the editor column, Dec. issue, one R. M. Thorson wrote "After 10 years in this business, I know almost everything there is to know." He shattered a long cherished illusion of mine, namely that I am just as bright as the next guy, and may even have a slight edge. Yet I have been in the TV business for over 12 years, and was in radio before that, and I still can't claim to know "almost everything there is to know" in this business! Certainly an ego-shattering letter.

Incidentally, your mag is my favorite of the "big 3" electronic mags to which I subscribe and I very enthusiastically welcome your new TV Manufacturers Digest section. It cannot help but be of great value and a natural tie-in with your Circuit Digests. Congratulations.

LES HUCKINS

Les Huckins TV Service
South Gate, Calif.

... Congratulations are in order to Mr. Thorson. It is indeed heartwarming to read that it is possible to learn all there is to know after a mere 10 years in this business. Obviously, you have the Einstein of the electronics industry on your mailing lists. I suggest he procure an accurate meter and place the leads between the plate of his Intelligence Quotient and the grid of his Modesty Amplifier and he will undoubtedly arrive at the conclusion of a direct short.

BUD WILSON

Canton, Ohio

... I find letters to the editor interesting, informative, and sometimes humorous, such as the letter by R. M. Thorson of Palo Alto. I presume it was written in that vein.

E. S. TANTON

Prince Edward Island, Canada

License S.O.S.

Editor, *ELECTRONIC TECHNICIAN*:

This letter is an S.O.S. to all servicemen in the state of New York. As you know, petitions have been circulated for licensing, but the response so far has been spotty. The bill to license has been introduced. It is the moment when success or failure hangs in the balance. A sponsor has been obtained from the Assembly, The Honorable William E. Adams of Kenmore. But he needs your help. I urge each serviceman to see his State Senator and Assemblyman personally. This bill is fair, it discriminates against no one and will raise the standards of our industry.

DOUGLAS COOK

Douglas Electric & Heating Co.
Kenmore, N. Y.


(Continued on page 12)

FIRST CHOICE WITH SERVICE TECHNICIANS . . . EVERYWHERE!

THERE IS ONLY ONE

MINIATURIZED
ELMENCO

DIPPED MYLAR* - PAPER
CAPACITOR

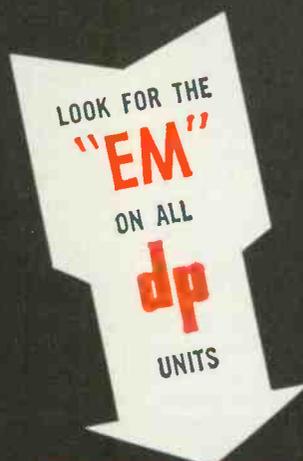

ASK FOR ELMENCO

*don't accept
substitutes
or
imitations!*

- OPERATES AT 125°C. WITHOUT DERATING
- STANDARD TOLERANCE $\pm 10\%$
- MISSILE RELIABILITY
- COMPLETELY MOISTURE PROOF
- UP TO 50% SMALLER THAN OTHER TYPES

* Dupont Reg. Trademark



**OVER 54,000,000
SOLD IN LESS
THAN 2 YEARS**

IS PROOF POSITIVE
OF THE UNIVERSAL
ACCEPTANCE OF
ELMENCO dp
DIPPED MYLAR-PAPER
CAPACITORS



ARCO electronics inc.

Community Drive, Great Neck, New York • Branches: Dallas 7, Los Angeles 35

Available at every REPUTABLE distributor throughout the country!

Now being used in millions of television sets, radios, phonographs, electronic circuitry and military applications.

Write for Catalog dp 110.

(Continued from page 10)

Speedy Distributor

Editor, ELECTRONIC TECHNICIAN:

How's this for fast service. Hal Havens Appliance Co., Hamilton, Texas, in connection with their "Going Out FOR Business Sale" called us for a picture tube and some TV parts. The call was received at 1:34 PM and at 2:52 PM we had delivered the parts and picture tube 120 air miles distant. We were happy to cooperate and help out this good service dealer.

LYLE HAMMER

Electronic Headquarters
Austin, Texas

Current Vs. Electron Flow

Editor, ELECTRONIC TECHNICIAN:

I am plagued with the harassing question on the subject of current flow. What is the difference between Conventional Current flow and Electronic Current flow?

RICHARD MAHLMEISTER

Dayton, Ohio

● It doesn't make much difference whether one talks about Conventional Current flow (plus to minus) or Electronic Current flow (minus to plus). It's a question of semantics. Conventional Current flow came first, thanks to power generation. It may very well be obsolete in view of the more proper application of electron flow in electronic circuits.—Ed

Helpful "Tough Dog"

Editor, ELECTRONIC TECHNICIAN:

The "Tough Dog" article of Mr. Fred J. Will on the motorboating Philco portable radio, Model E676, really helped me out of a spot. I just happened to have one of these on the bench with the same problem when I read the article in Dec. issue. I really enjoy your publication and the Circuit Digests have many times paid for the cost of my subscription. Keep up the good work!

W. L. BUSH

Bills Radio-TV Service
Kent, Ohio



"Lady, the knobs are fake."

lowest cost
master antenna system
ever developed

NEW BLONDER-TONGUE TRANSISTOR 4-SET BOOSTER—MODEL IT-3

All the gain you need from one antenna for 4 TV or FM sets!

This new transistor-operated 4-set booster provides higher gain and lower noise than any comparable vacuum tube unit. There are no tubes to replace, lower power drain and negligible heat — all contributing to lower cost, longer maintenance-free operation than any unit on the market. List price of model IT-3, \$32.50.

SUPERB 1, 2, 3 or 4 SET PERFORMANCE

- 1 SET—B-T 'straight thru' circuit provides full gain without isolation losses (Gain: 9 to 14 db, TV; 8 to 12 db, FM).
- 2, 3 OR 4 SETS—splitting circuit provides gain and inter-set isolation necessary to provide top performance on 2, 3 or 4 sets. Gain two sets—each set 4 to 8 db; Gain three sets—each set 3 to 4 db; Gain four sets—each set 2 to 3 db.

Sold through distributors. For details write: Dept. ET-2
engineered and manufactured by


BLONDER-TONGUE
9 Alling St., Newark, N. J.

Canadian Div.: Benco Television Assoc. Ltd., Toronto, Ont. • Export: Morhan Export Corp., N. Y. 13
home TV accessories • UHF converters • master TV systems • industrial TV systems • FM/AM radios

For more data, circle 2-12-1 on coupon, p. 46

Latest issue of **TUNG-SOL TIPS**

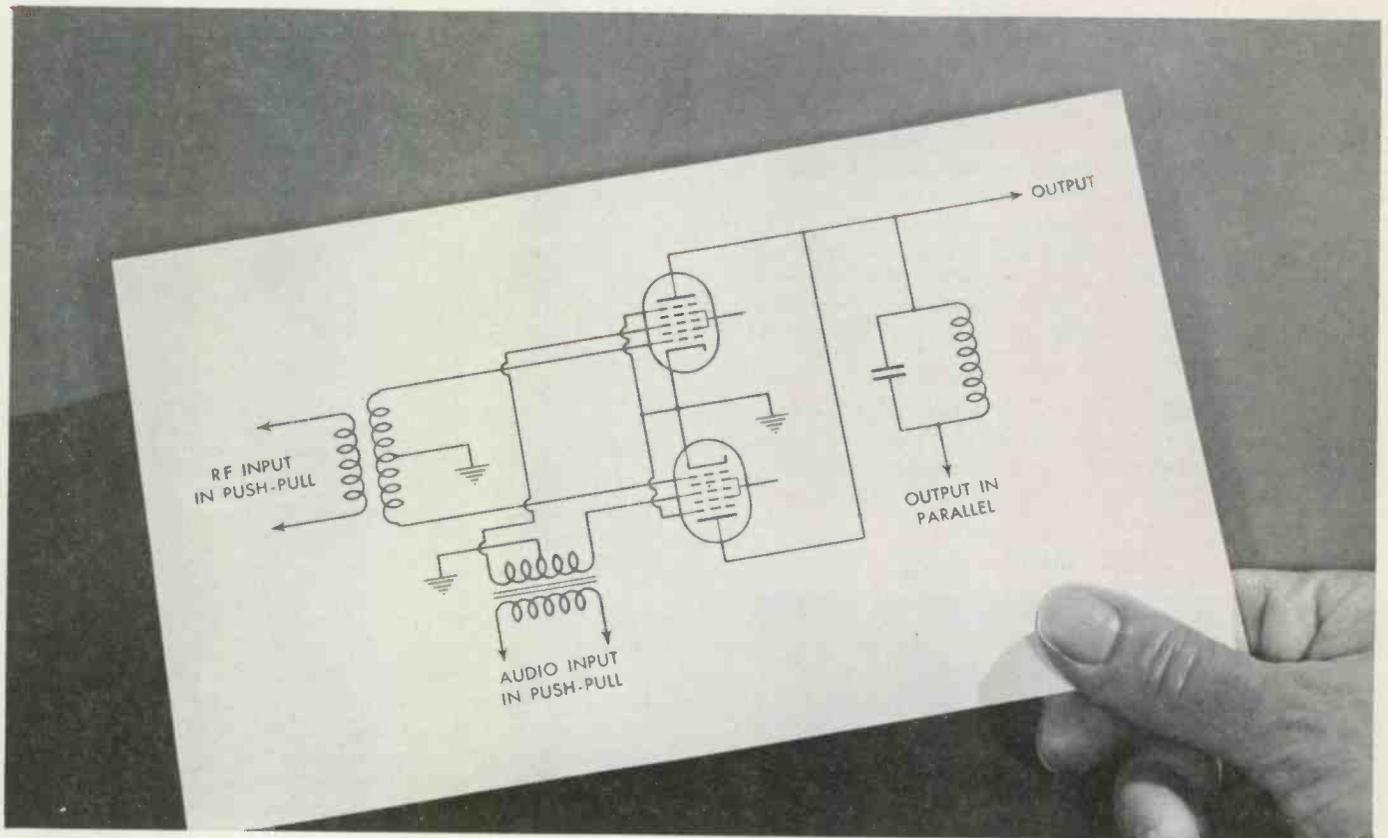tells you what you should know about
SINGLE SIDE BAND



The two-tube balance modulator circuit is an important element in single side band transmission. It's discussed in the latest issue of Tung-Sol Tips.

MONTH after month Tung-Sol has been delivering to the industrial serviceman one important issue of *Tung-Sol Tips* after another. Specially written for the service dealer who wants to devote his talents to servicing industrial equipment, every issue of *Tips* is crammed full of vital information to help him in his work. This latest issue is no exception.

Issue #14 offers in down-to-earth, on-the-job terms a full-scale treatment of single side band transmission. It discusses its advantages over conventional AM signals — and these advantages are considerable. You'll discover how the elimination of the carrier signal and one-side band are accomplished without any reduction of signal quality and intelligence. You'll be introduced to a whole series of typical modulator circuits which are used to suppress the carrier. In addition, there's a thorough

explanation of the filtering and phasing methods for eliminating sidebands.

So, if you're a serviceman who still hasn't signed up to get his issues of *Tung-Sol Tips* free every month, now is the time to do it. You won't want to miss this issue and the important issues planned for the future. All you have to do is drop in to see your local Tung-Sol distributor and ask him to put you on the *Tung-Sol Tips* mailing list. Or write directly. Tung-Sol Electric Inc., Newark 4, N. J.

ts TUNG-SOL®

Sales Offices: Atlanta, Ga.; Columbus, Ohio; Culver City, Calif.; Dallas, Texas; Denver, Colo.; Detroit, Mich.; Irvington, N. J.; Melrose Park, Ill.; Newark, N. J.; Philadelphia, Pa.; Seattle, Wash. Canada: Abbey Electronics, Toronto, Ont.

For more data, circle 2-13-1 on coupon, p. 46

Tuning In the


BUSINESS FORECAST. According to L. Berkley Davis, General Electric vp, 1961 electronic component sales will continue at high volume despite a leveling effect during the first half of the year. Factory sales of tubes should total \$827 million, and semiconductors \$626 million. This includes 385 million receiving tubes (down 4% to \$340 million), power tube sales \$300 million (up 4%), 11 million TV picture tubes unchanged at \$205 million, and industrial-military crt's. The semiconductor figure includes 180 million transistors (up 38% to \$360 million), and rectifiers \$136 million (up 16%). According to GE's Hershner Cross, distributor TV set sales should be equal to 1960, down 5% from 1959.

COLOR TV set sales by RCA were up 30% in 1960, reports Chairman David Sarnoff. Profit on color receivers was measured in seven figures, holding out hope for a stronger, growing market.

BIG GUN



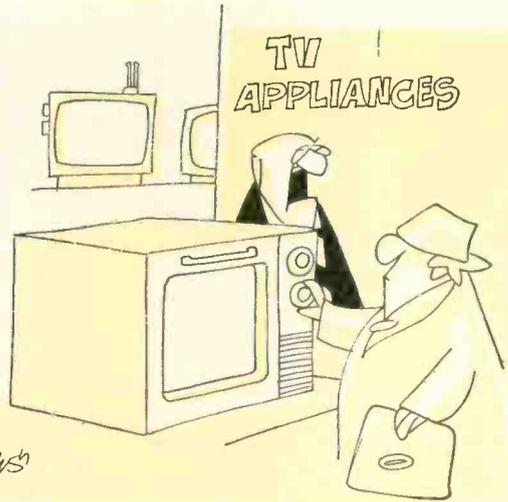This giant cathode ray gun, similar to those found in TV picture tubes, is a tool for studying electron beams. Developed by Westinghouse advisory engineer Dr. Hilary Moss, the gun is used to learn how closely beams can be focused to give images of the greatest density.




"There's no picture madam because that's an electric oven."

CONSENT ORDER (7820) approved by the FTC forbids United Electronics Labs., Inc., 3947 Park Dr., Louisville, Ky. to sell its correspondence and residence course in electronics through false employment offers, exaggerated earnings claims, and other deception. The complaint charged that the real purpose of United's "Men Wanted" advertisements is to obtain purchasers for its course and not to offer jobs, as implied. It further alleged that starting salaries for electronic technicians trained by United often are less than the \$90 to \$160 weekly claimed by United's salesmen. The respondents' agreement to discontinue the challenged practices is for settlement purposes only and does not constitute an admission that they have violated the law.

MARCH 20-23 are the dates for the 1961 IRE International Convention at New York's Waldorf-Astoria and Coliseum. More than 70,000 technical people from 40 countries are expected to attend, making it the world's largest technical meeting. There will be 850 exhibitors at the Coliseum displaying \$15 million of the latest electronic equipment.

KING-SIZE RADIO HUM has been detected by MIT scientists. The world-girdling air space between the earth's surface and the lower ionosphere acts as a resonant cavity resonating at 7.8 cps. The giant cavity is excited by electrical discharges during thunderstorms.

Picture

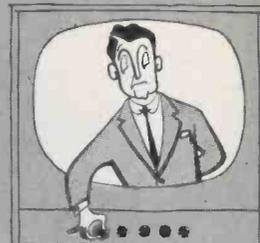

MOST SERVICE DEALERS have mixed feelings when the few gyms in the trade are brought to justice. It's satisfying to see shady operators get their just reward, but we feel a bit uneasy that some portion of the public may not understand that crooks are a tiny minority—as they are in most businesses. These somber thoughts were brought to mind by the arrest of two Los Angeles brothers for padding repair bills. New sets in perfect condition, except for one faulty tube, were set up. The culprits replaced new tubes with used ones . . . and charged over \$40 in the bargain.

“OPERATION SNOWBALL,” a 12-month industry-wide TV set sales promotion program launched in January by Corning, emphasizes the benefits in new sets resulting from technological advances. Objectives are to expand the TV market, encourage more trade-ins, and stimulate demand for higher priced sets. Co-operating companies will underwrite promotions for small and large dealers.

NEW SERVICE POLICY announced by Philco guarantees service labor, as well as parts, on TV repairs during the standard 90-day warranty period. More than 30,000 independent factory authorized service technicians are said to be available to carry out the new service policy. Service costs paid for by Philco are included in the list price of the product. For 17" and 19" portables, “carry-in” service is \$1.75; “in-the-home” costs for portables and consoles are covered for \$4.00. A similar warranty policy has been in effect for radios.

OCTOPHONE is the name of an electronic reader which converts printed letters into musical sounds, thereby eliminating the need for Braille or special tape recordings for the blind. The English development uses a light beam to scan a printed page, producing a pitch that varies with the shape of the letters.

REMOTE-CONTROL TV supervises building of a road near the New York City approach to the George Washington Bridge. A closed-circuit TV camera, mounted on a five-story building's roof, transmits closeup shots of construction activities to a monitor screen in the project manager's office. He keeps the job running smoothly by communicating with his men through a two-way radio.


CALENDAR OF COMING EVENTS

- Feb. 26- Mar. 1: Pacific Electronic Trade Show, Great Western Exhibit Center, Los Angeles, Calif.
- Mar. 20-23: IRE International Convention, The Coliseum and Waldorf-Astoria Hotel, New York, N. Y.
- Apr. 4-9: 1961 Los Angeles High Fidelity Music Show, Ambassador Hotel, Los Angeles, Calif.
- Apr. 7-9: NATESA Spring Directors Meeting, Albuquerque, New Mexico
- Apr. 19-21: 13 Annual Southwestern IRE Conference & Electronics Show, SWIRECO, New Memorial Coliseum and Baker Hotel, Dallas, Texas
- Apr. 26-28: 7th Region Technical Conference & Trade Show, Westward Ho Hotel, Phoenix, Ariz.
- May 22-24: 1961 Electronic Parts Distributors Show, Conrad Hilton Hotel, Chicago, Ill.

U.S. WEATHER BUREAU has put into operation an electronic computer-plotter which draws a complete weather map of the Northern Hemisphere in less than three minutes. Data on magnetic tape is fed to a digital-to-analog converter, which in turn instructs the Weather Plotter's mechanical hands to draw contours or isobars automatically. Information is gathered from 500 weather observation stations by teletype.

MICROMINIATURE CIRCUITS that are swallowed or injected into the body to aid disease diagnosis is envisioned by Dr. Edward Witting, deputy director of Army research. The circuits could be used to telemeter physiological data to the examining physician.

UNDERSEA TV

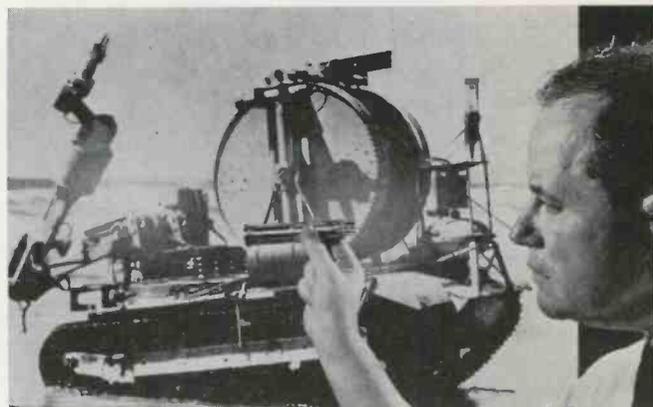

With this RCA vidicon tube, the Navy's new tank-like vehicle (in background) can see as it crawls along the ocean floor. Signals from the nautical TV cameras are transmitted to a land station via a special cable from the large reel. The vehicle is called RUM for Remote Underwater Manipulator. It was developed by U. of Cal.

News of the Industry

SYLVANIA announces production of its two billionth electronic receiving tube at Emporium, Pa.

EMPIRE STATE reports its appointment as an authorized service station for EICO.

SOUTH RIVER METAL PRODUCTS Sales Mgr., Marty Roth, reigns to take a position with another electronic company.

WESTINGHOUSE has named ARIBERT A. BOMBE as sales rep for the Electronic Tube Div. in N.D., S.D., Minn., Wisc., Mich., and No. Ohio.

DELCO RADIO opens a distributors program for its semiconductor products with the appointment of TED HAYES as Mgr. of Distributor Sales.

ZENITH has announced more than one million TV receivers were produced and sold during 1960, the company's second successive million-plus TV set year.

CBS ELECTRONICS announces two appointments to new posts: HERBERT L. REICHERT, Mgr., Dealer Products Sales; and JOHN H. HAUSER, Gen. Mgr., Distributor Sales.


TEXTRON has elected GEORGE H. METTLER as a Vice Pres., to coordinate and assist in development of international business. MB ELECTRONICS, div. of Textron, appoints CHARLES D. BROWN as Pres.

PHILCO International Div. has reached an agreement with JOHN M. OTTER CO., N.Y., N.J. and Philadelphia distributor of domestic Philco Products, to test market the British Philco home electronics in that area.

MALLORY announces Grand Prize winners (all expense jet trip to Montego Bay, Jamaica) of the "Cool Deal" Contest as follows: VERN W. MAXWELL of Cantrall, Ill.; and WOODBUR D. RYAN, salesman for Bruce Electronics, Springfield, Mass.

UNITED CATALOG reports a series of free sales aids available to distributors of THE RADIO-ELECTRONIC MASTER, including a 2-color counter card, sales messages for imprinting on letterhead at no charge, free use of industrial mailing list in distributors' territory. The 1961 edition of the MASTER is the silver anniversary issue cataloging in 1600 pgs. over 175,000 electronic items manufactured by more than 330 companies.

2

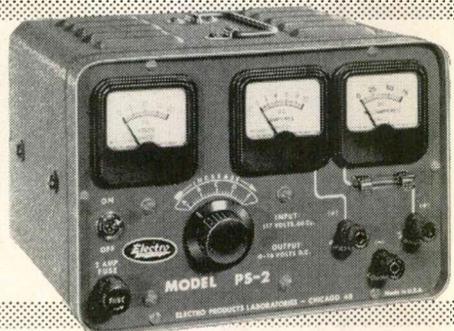

MODEL PS-2
2 OUTPUT RANGES
\$49.95 net

-IN-1 DC POWER SUPPLY

1... use it for operating ALL TYPES of auto radios
(transistor, hybrid and tube)

2... use it for operating personal portable radios
(transistor)

...also operates experimental transistor circuits, relays; use it for electroplating, laboratory work.

- Transistor protection with separately fused milliammeter.
- Longer life with EPL patented conduction cooling.

2 OUTPUT RANGES

VOLTS	CURRENT	RIPPLE
0-16	5 amps.	0.5%
0-20	75 ma.	0.15%

Compare With Others At Your Distributor... Send For Literature!

ELECTRO PRODUCTS LABORATORIES 4501-V Ravenswood, Chicago


Canada: Atlas Radio Corporation Ltd., Toronto

0156

BEST FILTERING, REGULATION

For more data, circle 2-16-1 on coupon, p. 46

NEW

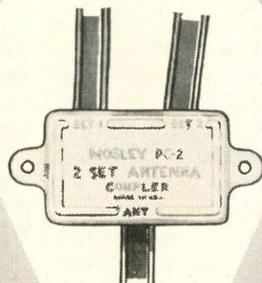

Masley PC-2

TWO SET COUPLER

Masley Electronics, Inc.

4610 N. Lindbergh Blvd. - Bridgeton, Missouri

For more data, circle 2-16-2 on coupon, p. 46

FOR TWO SET TV-FM OPERATION

You'll enjoy using the PC-2 two set coupler because your work and time will command a better price. The more efficient installations result in satisfied customers... fewer callbacks!

FEATURES INCLUDE:

- * Printed Circuit Design!
- * Low Forward Loss!
- * High Inter-set Isolation!
- * Call-Back Proof Connections!
- * Compact - Neat!
- * May be installed outdoors in semi-protected area!

Profit Wise TV Servicemen Choose Masley.

PC-2, Dealer Net, \$1.36
(Suggested List \$2.26)

Another "Premium Quality"
Masley TV Accessory.

Order from your Authorized Masley
Distributor or write.

What type
of TV Lead-in
Cable do you
need?

Your
Belden Jobber
has it!

Convenient lengths
in coils and
spools



WELDOHM . . . two and a half times the flexing life and one and a half times the breaking strength of ordinary lead-in. Resists pulling, whipping, twisting. 300 Ohm. No. 8230.



PERMOHM* . . . for use under conditions of extreme salt spray, industrial contamination, rain, and snow. Gives stronger, clearer signals. 300 Ohm. No. 8285.



STANDARD 300-OHM LINE . . . offers low losses at high frequencies. Also ideal for use with FM receiving antennas. No. 8225.



DECORATOR CABLE . . . this new 300-ohm lead-in cable is of ivory color — blends into any interior decorating arrangement. No. 8226.



CELLULINE* . . . excellent resistance to sun, abrasion, and wind. Installation easy . . . no end-sealing necessary. Gives strong UHF and VHF TV pictures. 300 Ohm. No. 8275.

Belden


WIREMAKER FOR INDUSTRY
SINCE 1902 — CHICAGO

Cord Sets and Portable Cordage •
Electrical Household Cords • Magnet
Wire • Lead Wire • Automotive Wire
and Cable • Welding Cable

WELDOHM, PERMOHM, CELLULINE
are Belden Trademarks
Reg. U.S. Pat. Off.

*Belden Patents U. S. 2782251 and 2814666

8-1-1

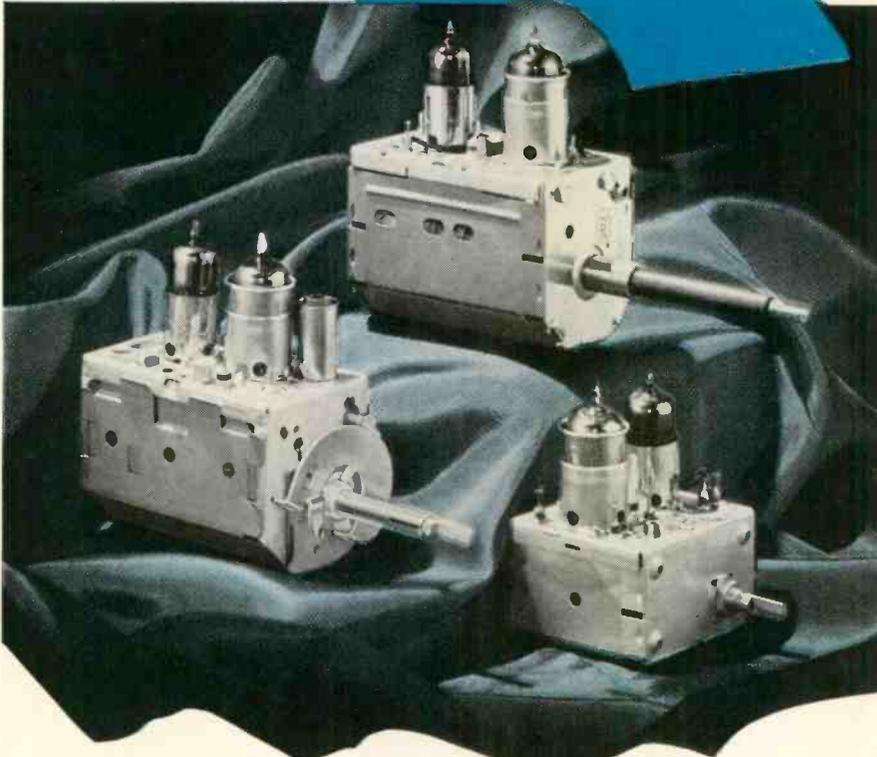

SILVER SEALED
(switch-type)

HOT ROD
(turret-type)

HI FI
(FM) Tuner

Throughout the industry, the trouble-free TARZIAN TUNERS are winning praise for meritorious achievement.

No other commercial unit possesses so many of the desirable features found in the TARZIAN TUNER which is recognized as "the world's finest tuner for the world's finest sets."

Today, TARZIAN is the only commercial manufacturer offering the HOT ROD (turret-type) and SILVER SEALED (switch-type) . . . as well as the Hi Fi FM Tuner. All with built-in HIGH QUALITY . . . DEPENDABILITY . . . and EXCELLENT PERFORMANCE at LOW COST.



For more information, write to: Sales Department, Tuner Division

SARKES TARZIAN INC

east hillside drive • bloomington, indiana

Manufacturers of TV and FM Tuners • Closed Circuit TV Systems
• Broadcast Equipment • Air Trimmers • Magnetic Tape • Semiconductors

For more data, circle 2-18-1 on coupon, p. 46

Reps & Distributors

ERA's nine National Committees met on Feb. 1 to lead off the 2nd annual Electronic Representatives Assoc. Convention in the Los Angeles Ambassador Hotel.

ELECTRONIC ENTERPRISES, INC. is the new name announced by the firm which has operated as MILWAUKEE ELECTRONIC EXPEDITORS, INC., Milwaukee, Wisc.

ELECTRONIC PUBLISHING has announced publication of Catalog No. 102 for **MERQUIP ELECTRONICS, INC.**, Chicago, Ill., containing 196 pages of product and price information for 99 manufacturers.

SENCORE announces **PEOPLES RADIO & TV SUPPLY CO.**, Roanoke, Va., sponsored a SENCORE Clinic with more than 50 TV technicians attending. An educational film was shown featuring the new Mighty Mite Tube Checker, the TC-109.

MARK MOBILE reports the appointment of three reps for its line of Heli-Whip and Beacon antennas: **ATHANS SALES CO.**, Dallas, Tex.; **DIXIE ELECTRONIC ASSOC.**, Madison (Nashville), Tenn.; and **WES ALDERSON CO.**, Los Angeles, Calif.

ARCO ELECTRONICS announces Western industrial distributors to handle the new line of HST DIV. transformers, to which Arco holds exclusive distribution rights to jobbers and distributors in the U.S. and Canada: **RADIO SPECIALTIES & APPLIANCE CORP.**, Phoenix, Ariz.; **BRILL ELECTRONICS**, Oakland, Calif.; **PACIFIC WHOLESALE CO.**, San Francisco; **HOLLYWOOD RADIO & ELECTRONICS**, Hollywood; **R. V. WEATHERFORD CO.**, Glendale, Calif.; **SHANKS & WRIGHT**, San Diego; **SHELLEY RADIO CO.**, Los Angeles; **DENVER ELECTRONIC SUPPLY CO.**, Denver, Colo.; **CARTER SUPPLY CO.**, Ogden, Utah; and **C & G ELECTRONICS CO.**, Seattle, Wash.



For more data, circle 2-19-1 on coupon, p. 46 ➔


CHANNEL MASTER

**harps
on one
theme:
PERFORMANCE!**



To make the most, feature the best — sky-high quality products by Channel Master. Channel Master moves the goods because it delivers the goods. It's the brand that gives you those heaven-sent little "extras". Top quality and top performance for your customers — maximum volume and profits—you get the best of both. Just follow your "growth line" — Channel Master.

**CHANNEL MASTER
SUPER 10 T-W ANTENNA**

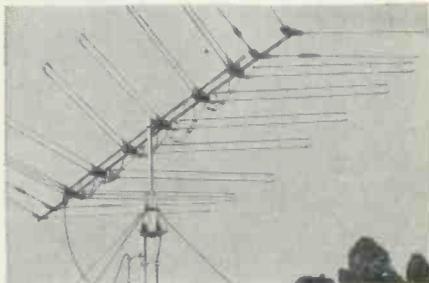

The most powerful super-fringe antenna yet developed. Based on Channel Master's unique Traveling Wave principle, it has 10 elements and offers up to **78% more power** for picture-poor homes.

**CHANNEL MASTER
TENN-A-LINER ROTATORS**



The only automatic rotator that can be aimed within **one degree** of the required direction. Unsurpassed accuracy, plus great repeatability and easier, quieter operation.

**CHANNEL MASTER
PREMIUM QUALITY TUBES**



America's fastest growing line! Longer-lasting, uniformly dependable, with minimum call-backs. No other tube make offers greater opportunity for profits than these fully proved performers.



CHANNEL MASTER works wonders in sight and sound
ELLENVILLE, N. Y.

The Family Gathers

to wait for **Centralab**® push-push
(or push-pull) **CONTROLS**



PHOTO: BETTMAN ARCHIVE



ail, hail, the gang's all here

They'd be inside if the TV set were working . . . but a push-push control went bloo-ey.

Luckily for them, though, CENTRALAB has replacement units . . . the only push-push units on the market, plus a complete line of 35 push-pulls. Four different types—Adashaft, Universal Shaft, Fastatch or dual concentrics, and Twin types for stereo.

Push-push and push-pull controls are now being used in over 78% of the TV, radio and hi-fi sets coming out of the factories. Find the CENTRALAB replacement you need at your distributors, so the folks can get back inside to see what Wyatt Earp is up to.



Centralab®

B-6101

THE ELECTRONICS DIVISION OF GLOBE UNION INC.
902B EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN
CENTRALAB CANADA LIMITED—AJAX, ONTARIO

**ELECTRONIC SWITCHES • VARIABLE RESISTORS • CERAMIC CAPACITORS
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS**

For more data, circle 2-20-1 on coupon, p. 46

Catalogs & Bulletins

TECHNICAL BOOKS: 38-page, 1961 catalog of technical books and business books is available. The Macmillan Co., 60 Fifth Ave., New York 11, N. Y.

For more data, circle 2-20-2 on coupon, p. 46

FLASH-TEST: Circular covers combination continuity-tester and flashlight. Tests all types of fuses and appliances plus regular spotlight coverage. Selcin Corp., Box 88, Medford 55, Mass.

For more data, circle 2-20-3 on coupon, p. 46

FUSE KIT: Literature describes a general purpose kit. Contains assortment of 60 fuses of the 16 most popular types and substitution chart packed in plastic box. Sightmaster Corp., 50 Aleppo St., Providence, R. I.

For more data, circle 2-20-4 on coupon, p. 46

ANTENNAS: Literature describes model HK-1 home TV/FM System Kit, featuring new type indoor antenna that provides reception on up to four TV or FM sets. Blonder-Tongue Labs., 9 Alling St., Newark 2, N. J.

For more data, circle 2-20-5 on coupon, p. 46

MICROPHONES: 6-pg color brochure covers Vega-Mile wireless microphone system and also carries specs of the complete line of the firm's accessories. Illustrates suggested applications. Vega Electronics Corp., Cupertino, Calif.

For more data, circle 2-20-6 on coupon, p. 46

TRANSISTORS: "The 2N741 Mesa Transistor as a Power Oscillator and Class C Amplifier," is the title of Application Note AN 124. Circuit schematics, performance curves, and illustrations included. Technical Information Center, Motorola Semiconductor Products Inc., 5005 E. McDowell Rd., Phoenix, Ariz.

For more data, circle 2-20-7 on coupon, p. 46

EQUIPMENT FOR TV SYSTEMS: Available are 10 two-color specification sheets covering electronic and electrical equipment for closed-circuit and community TV systems. The series cover modulators, amplifiers, preamplifiers, converters, all-weather housings, plus accessories. Ameco Div., Antennavision, Inc., P. O. Box 11326, Phoenix, Ariz.

For more data, circle 2-20-8 on coupon, p. 46

TUBES: Two new Application Notes are: AN-189, "New 100-Milliamper Tubes for 120-volt Series-Heater-String Home Radio Receivers"; and AN-190, "AC/DC Stereo Amplifiers Using Output Tubes having 100-Milliamper Heaters." For copies, write on your letterhead to RCA Commercial Engineering, Electron Tube Div., Harrison, N. J.



Prove how CBS design for Total Reliability CUTS BACK YOUR CALLBACKS

Are callbacks stealing away your profits? CBS Total Reliability tubes can keep them in your pocket. Take the CBS 5U4GB, for example.

This improved CBS tube has been specifically engineered with advanced features for utmost dependability. And its extra quality and longer life will build customer confidence—important for your continued success.

Now you can prove this to yourself right on the job—at CBS Electronics' expense. For a limited time only, you get a free trial CBS 5U4GB when you buy nine. You get a full "10-pack" *but you pay for only 9 tubes*. Order now from your CBS Electronics distributor. Offer expires March 15.


CBS ELECTRONICS

Danvers, Massachusetts

A Division of Columbia Broadcasting System, Inc.

Receiving, industrial and picture tubes • transistors and diodes • audio components • and phonographs

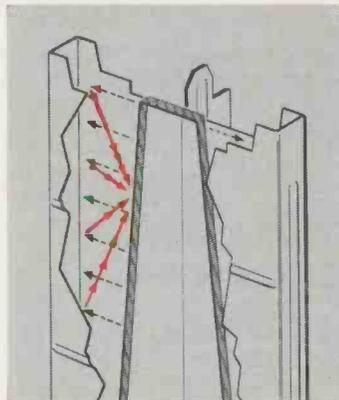
How design for Total Reliability prevents filament failure in the improved CBS 5U4GB



In ordinary rectifier tubes, filaments burn out when they overheat from a rise in reverse current. CBS eliminates this "back emission" in the 5U4GB with larger plates of non-emissive material that permit cooler operation and longer tube life.


CBS proved this by submitting the 5U4GB to dynamic "blast" tests that brutally cycled the tube between 4 and 6.8 volts with 800 volts plate potential. Meter readings showed "back emission" to be barely measurable—less than one ma.

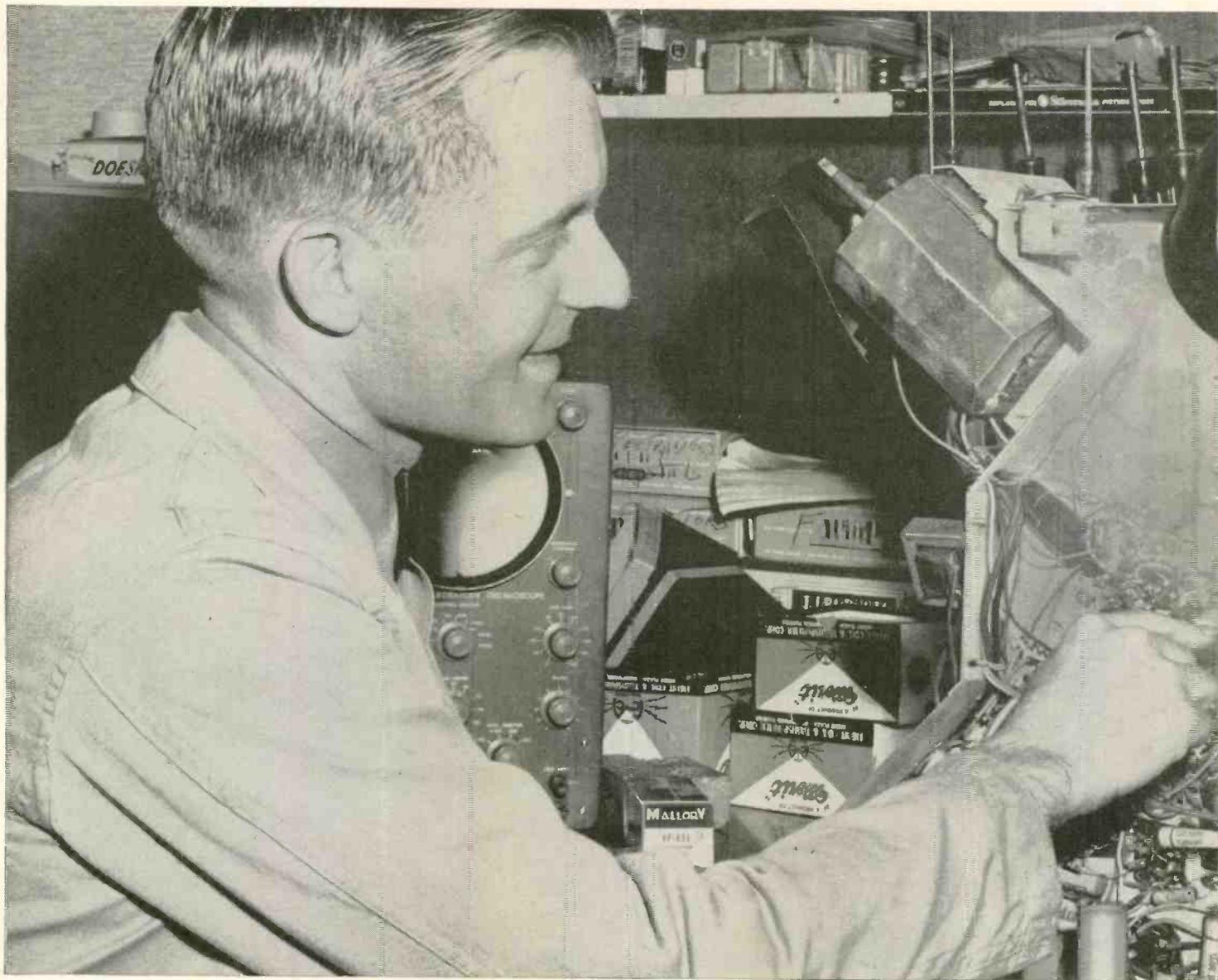For more data, circle 2-21-1 on coupon, p. 46



Roger Hefner owns and operates Hefner Television & Radio Service in Lima, Ohio. He attended DeVry School in Chicago, worked with a major radio-TV manufacturer, then went into business for himself. Roger now has two technicians helping him with sales and service on home and auto radio, TV and hi-fi.

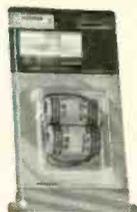Stop call-backs with these quality Mallory components



TC TUBULAR ELECTROLYTICS

Economical filter capacitors. Hermetically sealed. Also special TCX type for -55°C . Twin-pack keeps leads free from kinks.



FP ELECTROLYTICS

Original 85°C capacitor, now better than ever. Etched cathode gives hum-free performance. Chassis or printed circuit mounting.



STA-LOC® CONTROLS

End searching and waiting. Your distributor can custom-build, in just 30 seconds, any of over 38,000 single or dual controls.



GOLD LABEL® VIBRATORS

Quietest ever made . . . for the best in auto radio servicing. Buttonless contact design gives longest trouble-free service.

Radio-TV Serviceman Roger Hefner tells how:

“Mallory quality components protect my reputation for quality service”

“My service reputation is founded on quality—in products and in workmanship—and I’ll never jeopardize it by using cheap ‘specials’ that are sold as ‘just as good’. In replacement components, only the best will do. This means Mallory—and no substitutes!”




In ceramic capacitor replacement, Roger Hefner, like thousands of other technicians, has found Mallory RMC Discaps® tops for customer satisfaction. Long the quality standard in original equipment, Discaps have the built-in quality that ends call-backs . . . provides the margin between just *service* and genuine *quality service*. On handy 3 x 5" file card five-packs. Whatever your need, see your Mallory distributor—for highest quality components . . . widest selection . . . sensible prices.

© Trademark Radio Materials Company, a Mallory division.

Distributor Division, Indianapolis 6, Indiana


P.R. MALLORY & CO. Inc.
MALLORY

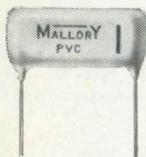

MALLORY PVC CAPACITORS

New, blue Mylar* coupling and by-pass capacitors. Dunk 'em, bend 'em, overload 'em, overheat 'em . . . they can take it.

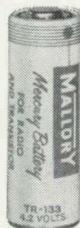*Reg. Trademark E. I. du Pont de Nemours & Co., Inc.



MALLORY MERCURY BATTERIES

Tops for transistor radios. Steady power, up to 3 times longer service . . . they “live” for years when idle. Guaranteed leakproof.



GEMS

Rugged, moistureproof tubular capacitors, unmatched in filter, buffer, by-pass and coupling service. Handy five-pack keeps stock clean, leads kink-free.

For more data, circle 2-23-1 on coupon, p. 46

★ **EARN MORE MONEY**

★ **BUILD A BETTER FUTURE**

NOW you can learn 2-way radio servicing at home from Motorola

NOW, for the first time, a home study course devoted exclusively to 2-way FM radio servicing.

The MOTOROLA TRAINING INSTITUTE trains you for a professional career with unlimited potential. The booming 2-way radio market should triple in the next 10 years. Qualified servicemen are urgently needed!

The Motorola Training Institute course covers everything in 2-way radio from basic principles to system analysis and troubleshooting the latest transistorized equipment.

Course Includes:

- 38 STUDY LESSONS WITH COMPLETE SECTION ON TRANSISTORS
- 9 UP-TO-DATE TEXTS
- MORE THAN 20 TECHNICAL ARTICLES

HERE'S WHAT STUDENTS SAY ABOUT THE MOTOROLA TRAINING INSTITUTE COURSE

"The section on transistors alone is more than worth the price of the full course." (K. F.—Illinois)

"Although I have an FCC license and some experience as a technician, I did not have a good working knowledge of the squelch circuit. Now, through my Motorola Training Institute training, I am able to do a decent troubleshooting job." (P. C.—Indiana)

"Personally, I think any technician that does not sign up for this course is missing a good opportunity to ease his servicing problems." (N. V.—New Jersey)

Write Today for
Complete Information


**NO OBLIGATION AND
NO SALESMAN WILL CALL**



NEW TECHNICIANS: Learn in just a few months what could take years. Course prepared by experienced faculty and highly skilled technicians. Easy-to-grasp lessons—reference library—individualized instruction.



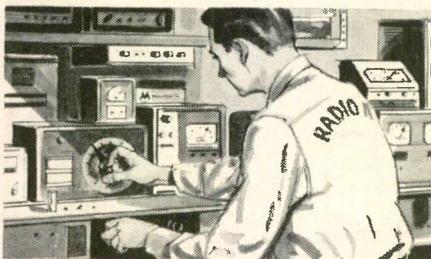TV-RADIO SERVICE MANAGERS: Here's a great growth opportunity for you and your technicians. The Motorola Training Institute home study course teaches your technicians the right way to do 2-way radio servicing and enables you to expand your range of services.



EXPERIENCED TECHNICIANS: Learn advanced servicing techniques and technological improvements. Get new information and know how on all the new transistorized equipment. An excellent "brush-up" course.

MOTOROLA
TRAINING INSTITUTE

4501 Augusta Blvd., Chicago 51, Ill.

Please send me complete information on the MOTOROLA TRAINING INSTITUTE No. A-165.

(please print)

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

For more data, circle 2-24-1 on coupon, p. 46



FEDERATED INDUSTRIES announces its new "MAX-FLX" auto radio speaker line with as much as 33 1/3% more field strength with the same magnet weight.

UNITED AUDIO introduces the Dual-1006 Custom turntable/changer, superseding previous model. It trips and tracks as low as 1 1/2 grams. \$79.95.

BELL SOUND introduces its first bookshelf stereo speaker, having 2-way speaker system featuring 8" woofer, 3 1/2" tweeter, walnut veneer cabinet; \$60.00 each.

ALLIED RADIO introduces the Knight KN-150 Hi-Fi FM Tuner with Dynamic Sideband Regulation. IM distortion is below 0.25% at signal levels over 10 μ v. \$119.95.

ROBINS INDUSTRIES reports new products: Model 5Q17-105 M/M quarter-track stereo record/playback tape head, @ \$30; Model SD-4 4-speed strobe disc, @ 50¢.

NESHAMINY reports introduction of a speaker installation kit, JAN KIT Model 41, for built-in installations. The JansZen electrostatic two-element mid/high range driver and Model 350 woofer are both mounted on a single panel board. Price is \$99.95.


POLAR ELECTRONICS announces an all-transistor stereo preamplifier-amplifier unit offering 15 watts/channel with frequency range of 20-20,000 cps. The unit features complete circuit encapsulation and is guaranteed for 30 months. \$96.50.

LAFAYETTE announces a 4-speed turntable with integrated 12" tone arm @ \$49.50. Turntable features a 4-pole motor, 3 lb 12" aluminum table, speed control varies each speed \pm 7%. Technical specs: noise and rumble —50 db, wow and flutter less than 0.2%.

BENJAMIN ELECTRONIC SOUND introduces a new magnetic phono cartridge, Model ST-310D, for stereo records only. Called the "Studio," it is used by European broadcast studios. Features include: 0.52 mil diamond stylus, 20-20,000 cps frequency response, 3 to 5 grams tracking force. Priced at \$45.00.



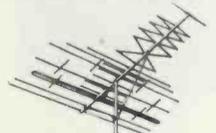
The Businessman in the Serviceman suit knows 1,400,000 new houses* mean unlimited opportunities in new antenna installations. He intends to get his share of this profitable business. His antenna brand? . . . JFD, of course—for performance that delights his customers and confirms their confidence in his technical ability.



HI-FI HELIX



HI-FI BANSHEE

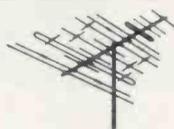

HI-FI FIREBALL

THE BRAND THAT PUTS YOU

JFD

IN COMMAND OF THE MARKET

JFD ELECTRONICS CORPORATION
BROOKLYN 4, NEW YORK


*Source - American Builder

For more data, circle 2-25-1 on coupon, p. 46




TVL TWIST-LOK® CAPACITORS

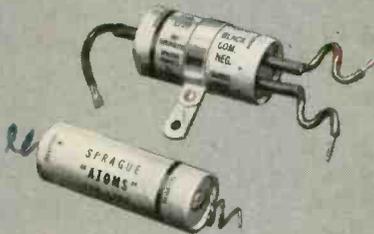These 'lytics take on the toughest TV and radio duty, give maximum trouble-free service, *without HUMMM!* They are dependable at extremely high and low temperatures. Cathodes are etched to meet the needs of high ripple currents, high surge voltages.




TVA ATOM® CAPACITORS

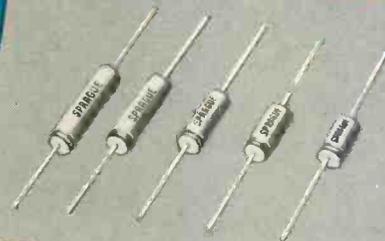Atom tubulars are service favorites because they fit anywhere, work anywhere. They're the *only* small size 85 C (185 F) capacitors in ratings up to 450 WVDC. They have low leakage current, long shelf life, and withstand high ripple currents, high surge voltages.



TE LITTL-LYTIC® CAPACITORS

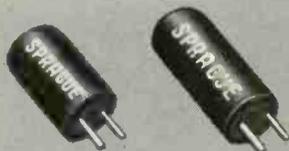The very best ultra-miniature replacements for transistor circuits, offering unusual reliability through all-welded construction. No pressure joints to cause "open" or intermittent circuits. Long shelf life—extremely important in sets used only part of the year.



VL VERTI-LYTIC* CAPACITORS

These single-ended molded tubulars are the ideal replacement for units of this type found on printed wiring boards. Keyed terminals assure fast manual mounting and correct polarity. Resin end fill protects against drying of electrolyte or entrance of external moisture.



PCL PRINT-LOK® CAPACITORS

The printed circuit version of the Twist-Lok. Universal base replaces any of the printed circuit 'lytics in use today. No makeshift mounting adapters to damage capacitor or add extra height . . . no possibility of high resistance contacts.

EVERY 'LYTIC YOU NEED...

- every value
- every rating
- every style

Shown here are the more popular of Sprague's big family of Electrolytic Capacitors, the broadest in the industry. Other types include Metal-encased Screwbase; Plastic-encased High-MF; Metal-encased Octal-base; Ultra-low leakage Photoflash. All are listed and described in Sprague's NEW Catalog C-613A. Get your copy from any Sprague distributor, or write Sprague Products Company, 65 Marshall Street, North Adams, Massachusetts.

*TRADEMARK

SPRAGUE®

THE MARK OF RELIABILITY

WORLD'S LARGEST CAPACITOR MANUFACTURER

ELECTRONIC TECHNICIAN

Including
SERVICE
Magazine

Improving TV Set Serviceability

We have been pleased to note the improvement being made in TV receiver designs. Those portables (some of which are barely toteable) have become more compact. The laminated or bonded faceplate in place of the separate safety glass should improve accessibility, simplify dust removal, and provide greater flexibility in the set's physical design.

Most heartening are the improvements to make sets more serviceable. Along with thousands of service technicians across the country, we complained about early printed circuits which were

not as reliable in performance or easy to service as they should have been. Current models use tracing patterns which simplify the trouble shooter's job in locating defective components.

We hope set designers will not slacken their pace in designing greater serviceability into TV receivers. On some sets, certain controls are either inaccessible or nonexistent. On others you have to remove the entire chassis before you can take out the safety plate. Happily, such shortcomings are not typical of most sets.

There's progress in serviceability.

Those Long Warranties

A TV set buyer has a right to expect proper performance for a reasonable time. Warranties should continue to assure free replacement of defective parts.

However, the very nature of TV sets demands periodic maintenance. To set out a warranty that is unreasonably long—five years, for example—confuses the consumer and places an excessive burden on the service dealer. Warranties should protect against unexpected failures, not normal long-term wear. A five-year warranty incorrectly implies to the consumer that failure should not be expected before that time. The set performing well after five years without service is a rarity among rarities.

As a sales gimmick, unreasonably long warranties can backfire. Competitors will be pushed into matching or surpassing existing warranty periods. Ten-year warranties, anyone? It could happen, saddling the industry with an unnecessary, obnox-

ious burden.

We are pleased to see the January 1961 report by *Consumers Union* inform consumers about the difficulties such a guarantee encourages:

"The Admiral set is worth a brief discussion. The five-year guarantee of its particular printed-circuit board should ease the serviceman's fear of the sort of hairline cracks that drove him to despair when they appeared in the boards of many of the early printed-circuit sets. However, the unusual Admiral guarantee is somewhat less of a help than it purports to be: The many parts on the board are only guaranteed for the usual 90 days. To replace the board under the guarantee, the serviceman will have to transfer all of the parts from the old board to the new one, a time-consuming and costly process."

We hope that set manufacturers will give the same careful thought to service warranties as they have been giving to serviceable designs.

TV MANUFACTURERS

ELECTROHOME (Canadian)

Vertical lines in the background may appear slightly curved due to power supply hum affecting the picture's horizontal linearity.

To correct this condition install a ceramic capacitor whose correct value may vary from 2K to 4.7K $\mu\mu\text{f}$ (3000 $\mu\mu\text{f}$ is correct for most sets) from B+ to the junction of R407 and C408. This capacitor may be conveniently connected across pins one and two on the yoke socket. Future production runs will include this modification.

GENERAL ELECTRIC

Chassis M4, M5, early M6—Interference Bars

Some of these chassis may display an interference pattern resembling two hum bars when receiving extremely weak signals. This condition will not be apparent on normal or strong signal operations.

Interference has been traced to the re-radiation of the r-f signal from the receiver's power supply. To eliminate this effect, disconnect the grounded end of capacitor C405 connected to pin 4 of the low-voltage rectifier (5U4GB) and connect it to pin 2. This change has been incorporated in recent M6 chassis.


Chassis M5, U4—Remote Control Tube Replacement

When it becomes necessary to replace the 6EA8 tube in wireless remote receivers, replace the defective tube with a 6GH8 tube. The 6GH8 tube is an improved tube to replace the 6EA8 when gain is a factor. (However, direct replacement is recommended for *this* application only, not for replacement as a chassis tuner tube).

MAGNAVOX

Chassis 33 Series—Vertical Sync Stability

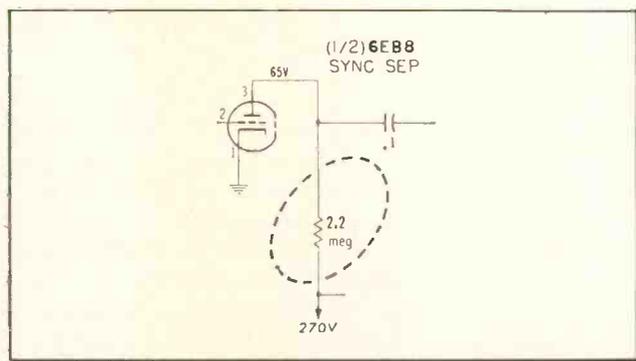To improve vertical sync stability, the plate load resistor in the sync separator circuit ($\frac{1}{2}$ 6EB8 tube) has been changed. The original value of R39, 2.2 meg,



A critical vertical hold control condition in excessive noise areas on some Magnavox series 34 TV chassis, can be corrected by reducing the value of a plate resistor in the sync separator ($\frac{1}{2}$ 6EB8 tube) from 2.2 megs to 1.8 megs.


has been changed to 1 meg. This modification is being incorporated in current production.

MOTOROLA

Chassis TS-435 Code A-01, CS-B—Production Changes

(See ET Circuit Digest #528 10/59 and #551 2/60)

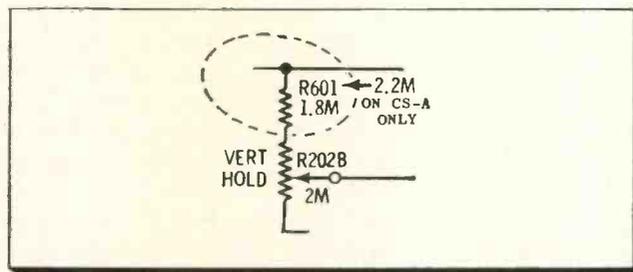To prevent damage to the filament string in the



To recenter the vertical hold control's lock-in position on a Motorola TS-435 TV chassis, change the value of the resistor in series with the control from 2.2 megs to 1.8 megs.

event the CRT arcs, the following production change was made: *Code A-01*—A 0.01 μf , 1400V capacitor (C508) was added to prevent other component breakdown if the CRT should arc. The capacitor is connected between B+ boost and ground. Physically, this is between pin #1 (ground) of the 8GN8 vertical


TECHNICAL DIGEST

oscillator tube and the boost connection of C505. *Code CS-B*—To center up the vertical hold control, a 1.8 meg resistor is used in series with the control, replacing a 2.2 meg resistor (R601).

PACKARD BELL

Chassis V8-7, V8-9—Christmas Tree Effect

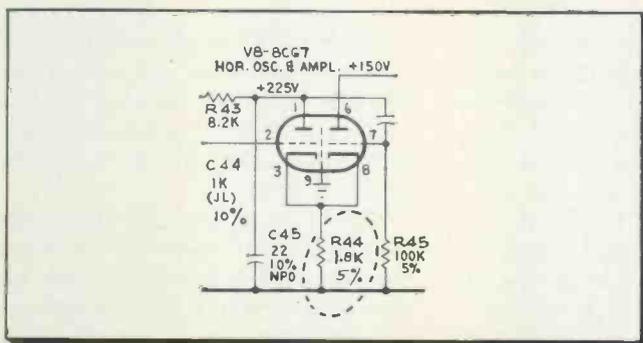To overcome a horizontal lock-out condition, appearing as a Christmas tree effect, change the hori-



To eliminate a "Christmas Tree" effect in some Packard Bell V8-7 & -9 TV chassis, the circled 8CG7 horizontal oscillator's cathode resistor has been changed from 2200 ohms to 1800 ohms.


zontal oscillator tube's (8CG7) cathode resistor from 2200 ohms to 1800 ohms ($\pm 5\%$, $\frac{1}{2}W$). Sets stamped 2962 or higher incorporate this change.

RCA

VC-18, -24 Series—FM Dial String Revision

It was found that mechanical vibrations reaching the FM tuner drive were being transmitted to the tuner's oscillator core. This resulted in a "howl" on FM reception.

To eliminate this condition, the FM tuner string arrangement has been revised. The string now makes a bend at the eyelet where it leaves the tuner and is passed over the top of the pulley, rather than under it, and then continues to the underside of the tuning drum shaft. If this change is made in an earlier production run tuner it will be necessary to reposition the FM tuner string drive collar for correct alignment.

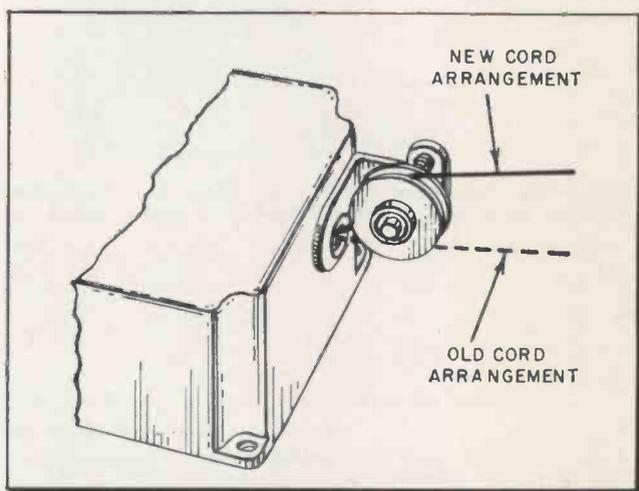


The RCA FM tuner dial string modification illustrated here, eliminates mechanically-induced reception howl.

ZENITH

New Turret Tuner—Oscillator Slug Alignment

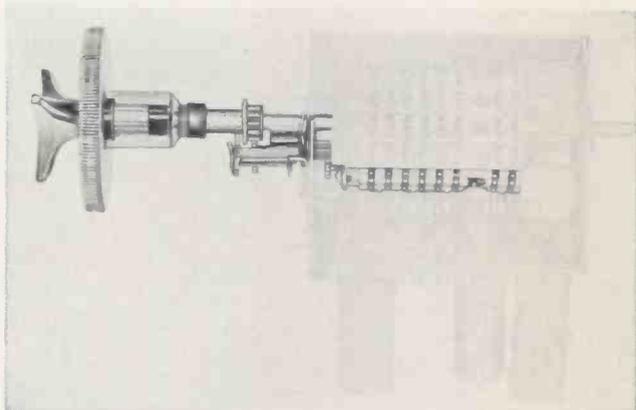The *Gold Video Guard* tuner employs a channel selector knob with a mechanism that permits front panel adjustment of each channel's oscillator slug



Zenith's turret tuner uses the front panel selector knob to adjust each channel's oscillator slug. The "fine tuner" engages each slug through a shaft gear arrangement when rotated.

without disturbing alignment to the other channels. Rotating the tuning knob causes a nylon gear to engage the oscillator adjustment screw of the channel being viewed.

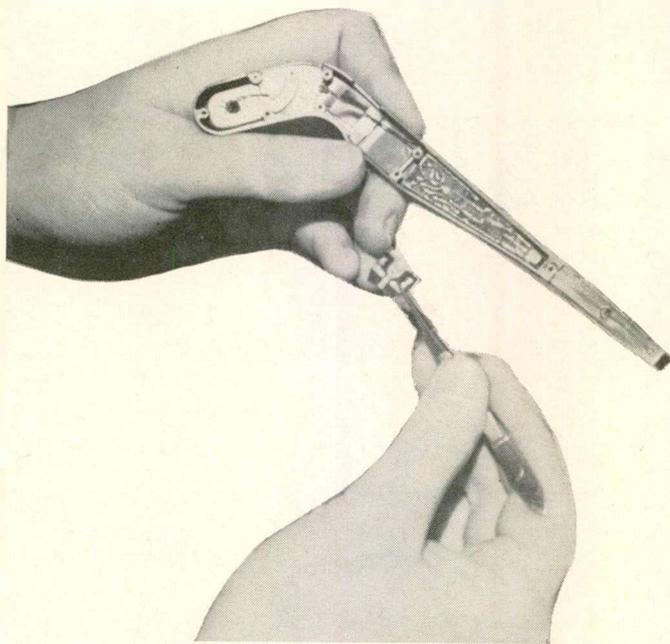


Fig. 1—The "eyeglasses" hearing aid shown here incorporates an electronic amplifier and volume control in its temple frame.

Servicing Transistorized Hearing Aids

- *How They Work*
- *Repair Methods*
- *Obtaining Parts*

LEO G. SANDS

• The public spends around \$60,000,000 for 300,000 new hearing aids every year. Many different types are available, such as the eyeglass temple-type shown in Fig. 1. No figures have been published on how much is spent for servicing hearing aids. But, it is a significant number, you can be sure.

The standard price charged by hearing aid repair specialists for repair and overhaul of a transistor hearing aid is \$12.50 and \$7.50 for tube type aids. These prices include parts, but no batteries. The repair jobs are seldom performed by a hearing aid dealer. Instead, the dealer often ships ailing hearing aids to one of the few specialized shops where this kind of work is done, or to its manufacturer.

Many hearing aid dealers specialize in the sale of new hearing aids and confine servicing to replacement of cords, batteries and ear pieces. He chooses to send hearing aids to a distant city for repairs because none of the electronics service shops in his town has asked him to farm out his repair business to them.

There is nothing mysterious about a hearing aid. It is a very simple PA ("private" address) sys-

tem consisting of a microphone, an amplifier and an earphone or bone conduction transducer. To see how really simple a hearing aid is, let's examine the circuit of one of the popular makes, a Zenith model 50R, shown schematically in Fig. 2.


The microphone output signal is fed directly to the base of Q1 and to the emitter through C1. Bias is developed across R3 and is augmented by the voltage fed to the base from the junction of the voltage divider R1-R2. The signal developed across R3 is fed directly to the base of Q2, functioning as a common emitter amplifier. The signal developed across R5 is applied through C3 to

the base of Q3 whose output signal is developed across R9 and is fed through C4 to the base of Q4. The varying collector current (output) of Q4 passes through the coil of the 400-ohm earphone.

The circuit is conventional except for the manner in which volume is controlled. Fig. 3A shows how the third-stage circuit looks when the volume control is set for minimum gain. Q3 is essentially out of the circuit. The signal voltage developed across R5 is also developed across R6 and R9 which form a 50:1 voltage divider. Hence, there is a 34 db loss through the third stage.

When the volume control is set to

Fig. 2—Schematic diagram of a Zenith Model 50R Hearing Aid.

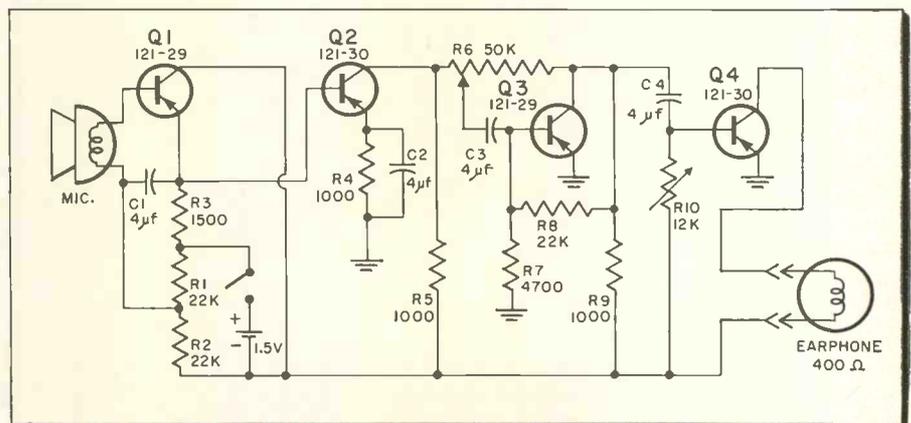

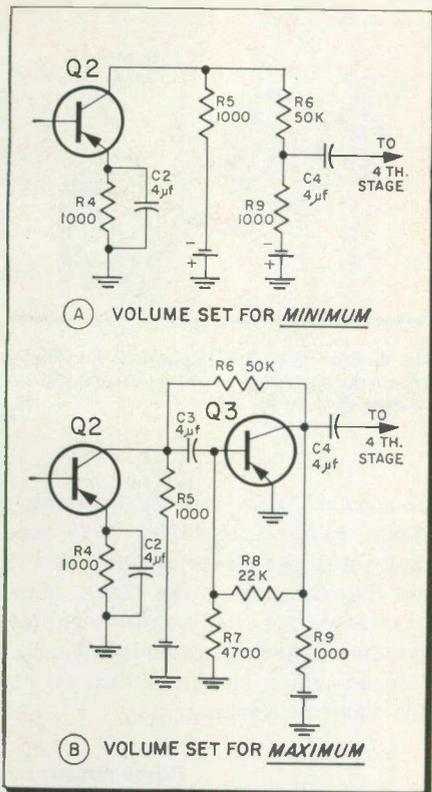


Fig. 3—Equivalent circuits of Zenith Model 50R when volume is set for minimum sound (A) and maximum sound (B). See text!

its maximum gain position, the circuit is as shown in Fig. 3B. The transistor Q3 is now in the circuit. The signal voltage developed across R5 is applied to the base of Q3 through C4 and is developed across R7. But, also appearing across R7 is an out-of-phase feedback voltage from the collector of Q3 whose value is determined by the ratio of R7 and R8 as well as the gain of Q3. In addition, the output signal developed across R9 is fed back through R6 to the input of Q3. The magnitude of this feedback voltage is determined by the gain of the transistor as well as the ratio of R6 to R5, which is 50:1. The feedback through R8 is the same at all frequencies while the feedback through R6, which must pass through C4, has less effect as frequency decreases because of the rising reactance of C4.

R7 and R8 also bias the base of Q3 at the desired d-c value. R10 in the input circuit of Q4 affects gain as well as bias.

It should now be obvious that there is nothing complex about a hearing aid amplifier. But, let's look at another circuit. Fig. 4 is a schematic of the Conny model T2 hearing aid which also employs a four-stage transistor amplifier. All

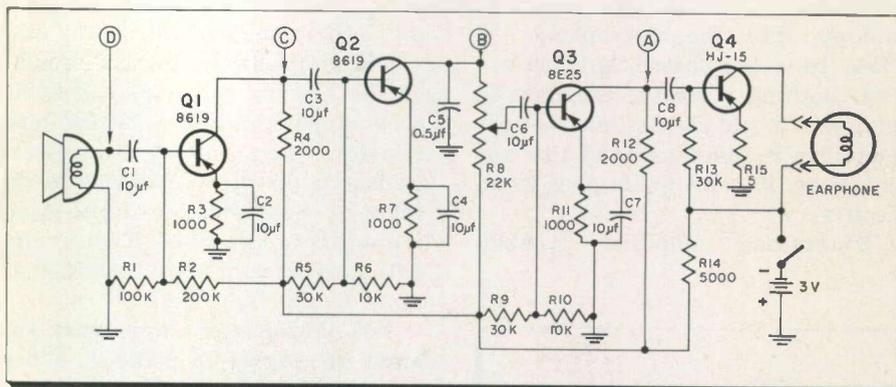


Fig. 4—Conny Model T-2 Hearing Aid that uses a conventionally-wired volume control circuit.


stages employ the grounded emitter connection. In the fourth stage, feedback is provided by leaving R15 unbypassed and by the loop, consisting of R16 and C8, from the collector back to the base. Power is derived from a pair of 1.5-volt penlight cells. Fig. 5 illustrates the unit pictorially.

Troubleshooting

What can go wrong with a hearing aid? The most common trouble is a dead battery. The easiest way to find out, of course, is to replace the battery. Earphone cords are a common source of trouble. Earphones and microphones can also go bad. These troubles can be remedied without requiring any skill in electronics.

To determine if it is the amplifier, earphone or its cord that is defective, simply remove the earphone plug from the amplifier output jack. Connect a d-c voltmeter in place of the earphone plug, turn the hearing aid on and talk into the microphone. There should be voltage and its reading should increase as you talk closely into the microphone. Or, connect a d-c milliammeter through a 200 to 450 ohm resistor to the output terminals. When talking into the microphone, the current reading should increase because of the action of the class B amplifier. If the amplifier is equipped with an output transformer, use an a-c voltmeter or VTVM. It should read zero when no sound is picked up. Output voltage should exist and vary when

Fig. 5—Pictorial view of a Conny T-2 Hearing Aid, showing major components.

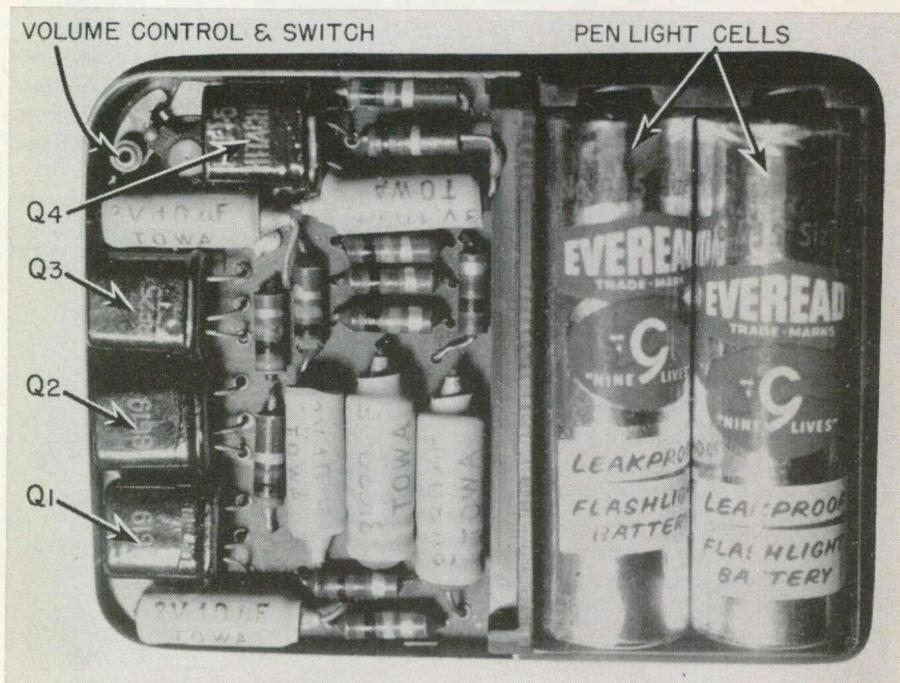

talking into the microphone. If these tests are passed, but you can hear nothing when the earphone is plugged in, you can assume that the amplifier is functional and that the earphone, its cord or its plug is defective.

Diagnosing amplifier troubles

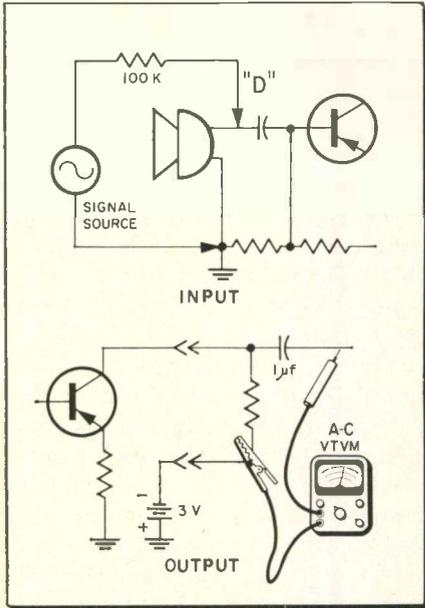


Fig. 6—Practical test set-up for checking the overall gain and frequency response of a transistorized hearing aid.

requires skill, but not a great deal. In the first place, it is a simple electronic audio amplifier. But, because of its compactness, good eyesight and careful workmanship are required. What can go wrong with a hearing aid amplifier? Resistors can change in value, capacitors can open, short or become leaky, and transistors can go bad.

The first step is to make a visual inspection, looking for goo running out of capacitors, dirt, corrosion and broken connections. Don't expect to find scorched resistors since the voltages are so low that current flow through resistors is extremely small.

Once it has been determined that the transistors and battery are good, signal tracing is the next step. With a hearing aid earphone or an ordinary radio headset connected to the output jack, you're ready to proceed. You need an audio signal source. If you're using an audio signal generator, be sure to ground the signal generator case. Also, connect the signal generator's grounded out-

put lead to the ground bus or case (if it is grounded to the circuit) of the hearing aid. Apply a 1000-cycle signal through a 100,000-ohm resistor, using one of the resistor leads as a probe, successively to the input of each amplifier stage, starting with the last stage. Typical signal injection points are identified as A, B, C and D in Fig. 4.

You should hear a tone when you apply the signal to point A. When you apply the signal to points B, C & D, the tone should get progressively louder. Be sure the hearing aid volume control is turned up and keep reducing the output of the signal generator as you progress toward the head end of the amplifier. If you do get tone when you apply a signal at point B, but you get none when feeding signal to point C, you have trouble in the second stage. When you apply signal to point A, you might hear the tone through the microphone, functioning as a loudspeaker.

You can measure overall gain and frequency response by applying a signal to point D and measuring a-c output voltage across a dummy load as shown schematically in Fig. 6. Monitoring an output section with headphones is shown in Fig. 7.

Hearing aids, like other electronic devices, last longer and work better if given periodic preventive maintenance. Cleanliness is most important. Amplifiers worn close to the human body are subjected to heat and moisture. Leaky batteries can contaminate parts. Earphones are apt to become clogged with wax. A simple way to clean amplifiers and earphones is to dunk them into a cleaning solution, using an ultrasonic cleaning system. In a matter

Fig. 7—Monitoring a hearing aid's output with headphones. The phones are shunted across a resistor through a 1 μ f capacitor.

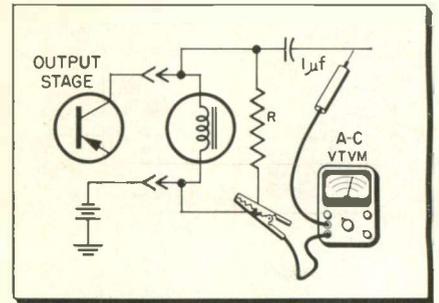
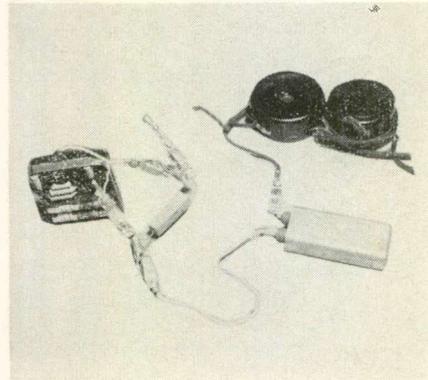


Fig. 8—Test set-up for finding the impedance of a headset, using an a-c meter to indicate voltage drop at R.

of seconds, they will be amazingly clean. Remove batteries first, and make sure the cleaning solution will not dissolve any of the parts. Manufacturers of ultrasonic cleaning systems generally provide information on which cleaning fluid to use for various applications.


Parts Problems

It may be difficult to get parts or information from some hearing aid manufacturers who want to restrict all servicing to themselves or their dealers. If you run into unmarked or unknown transistor types, you can quickly determine which lead is base, collector and emitter if you have an in-circuit transistor tester. Merely try the test leads in various combinations. When you find the right combination, the tester gives an indication, if the transistor is operative. You can also determine if it is PNP or NPN and its beta.

To determine the impedance of an earphone, measure the a-c voltage across it as shown in Fig. 8, trying various values of R. When the voltage is twice as great with R disconnected than it is with R connected, the impedance of the earphone is approximately equal to the value of R.

The resistors and capacitors used in hearing aids are usually standard types available at radio parts jobbers. Volume controls and transformers may be special. Microphones and earphones are usually available from firms specializing in these miniaturized devices. Cords, plugs and other accessories are available from such firms as those listed in the Chart I.

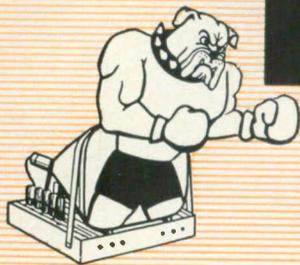To get into the hearing aid am-
(Continued on page 50)



"Tough Dog" TV

Corner



Difficult Service Jobs Described by Readers

Sync Capacitor Weakens Video

An Admiral 21F1 chassis nearly stumped me. The set was brought in with no high voltage due to a shorted 500 $\mu\mu\text{f}$ 20 kv hi voltage capacitor. After replacing same I was faced with a weak pix; the sound appeared normal. The contrast control was operative and when fully clockwise the picture showed re-

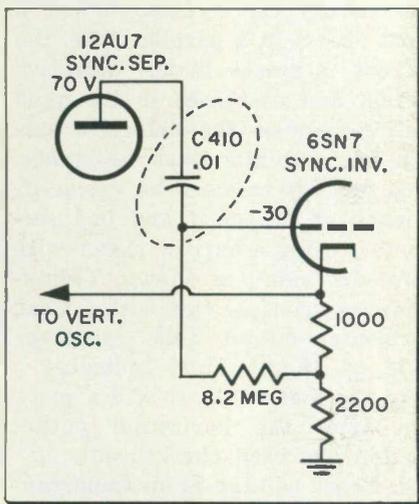


Fig. 1—Intermittent loss of horizontal sync and weak video in an Admiral 21F1 TV set was caused by a leaky sync capacitor.

trace lines. Sync would lock for about ten minutes and then intermittently fall out. It locked in vertically, though.

I used an analyst to check r-f and i-f circuits and could get the pattern to come through fine, with good contrast. However, the horizontal sync still lost hold every now and then. Since my analyst has a variable r-f and i-f signal control, it seems all I was doing was forcing a signal through the set. Still suspecting i-f trouble I measured all voltages: plate, screen, cathode, and

grid bias. All measured normal. The video amplifier voltages were checked and rechecked. Resorting to an age box, I still found no improvement in the contrast.

The thought occurred to me that perhaps I should tackle the sync problem. I began with the 12AU7 (sync separator tube section) shown in Fig. 1. Plate voltage was just a mite low, but continuing on the grid of the 6SN7 sync inverter I read a positive voltage instead of the -30 I was expecting.

I changed the coupling capacitor (already had replaced tubes), and I turned the set on to check the horizontal sync. Much to my surprise, not only did it lock in and hold, but the pix came on with normal contrast too.—*Elmer Woods, Los Angeles, Calif.*

Filament Globar Kills Oscillator

My customer's complaint on his Sylvania Model 21T-103M was: no sound (though audio noise was apparent), picture on low frequency channels (4 and 5) and no picture


on the high frequency band (Channel 9) at any time. After approximately twenty minutes operation, channels 4 and 5 would disappear.

At the shop I double checked by substituting the r-f and oscillator mixer tubes (5X8 and 6AK5) and still didn't receive a picture. Troubleshooting by checking and substituting tuner parts proved a failure. I did notice that it took the set quite a while to warm up when first turned on.

I decided to change the global resistor (shown in Fig. 2) in the series filament string and to my astonishment the set returned to normal operation. The trouble was low filament voltage on the 5X8 and 6AK5 tubes. Since I had full raster and audio noise, I did not suspect low filament voltage.—*M. F. McWilliams, Drummond, Okla.*

• High frequency oscillator circuits are particularly sensitive to voltage inadequacies. Therefore, it's not surprising to find a slightly lower filament voltage affecting tuner oscillator operation before the horizontal oscillator or other circuit sections. A low-voltage rectifier with deficient output could conceivably also kill the tuner oscillator without influencing width.—*Ed.*

Fig. 2—A defective globar resistor used in Sylvania's 21T-103M chassis killed the tuner's oscillator tube.

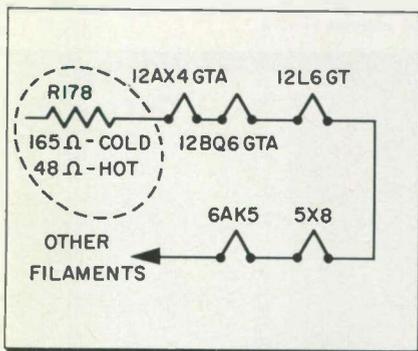

TOUGH DOGS WANTED

\$10 for acceptable items. Use drawings to illustrate whenever necessary. A rough sketch will do. Photos are desirable. Unacceptable items will be returned if accompanied by a stamped envelope. Send your choice entries to "Tough Dogs" Editor, ELECTRONIC TECHNICIAN, 480 Lexington Ave., New York 17, N. Y.

Misconceptions In TV Servicing

Five Commonly Accepted TV Repair "Facts" Are Disproved

WAYNE LEMONS

• Everyday, it seems, we read or hear some fallacy concerning some facet of TV service. These fallacies are picked up by technicians and are told and retold until they permeate the thinking of the service industry—but as someone has said, "if fifty million people say a fallacy is true, it's still a fallacy."

Certain errors have crept into our thinking over the years—with no one more guilty than myself, for at one time or another I would have sworn that all these misconceptions were true!

Let's take a look at some of the more common fallacies and then present evidence to prove that, truly, each is a misconception.

1. A bright vertical line can only occur on sets with a r-f high voltage power supply.

You've probably read this statement somewhere, but the technician who has had vertical line troubles (no horizontal deflection) with a flyback supply knows better. See Fig. 1. The cause may be: open yoke or an open yoke coupling capacitor. Many sets will still develop high voltage without the yoke connected; most auto-former types will! Direct drive sets often produce *excessive* high voltage with the yoke or linearity coil shorted! It follows then that if high voltage is present but there is no sweep energy in the yoke, a vertical line could be present on the picture tube.

2. Vertical output grid will be negative if receiving vertical drive.

This statement is accepted universally by technicians. The facts are: there is no negative drive un-

less the height (shown in Fig. 2) or linearity is misadjusted. Many vertical output stages are class A amplifiers and they *normally* draw no grid current, since they function on the linear portion of the curve. Thus, no vertical output stage will overheat because of the lack of drive! Unlike horizontal circuits, which rely on stored damper current to produce part of the sweep, vertical output stages must pro-


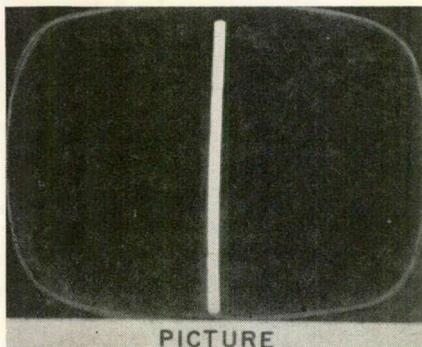


Fig. 1—*Misconception:* Bright vertical line can only occur with a r-f high voltage power supply. *Fact:* This can also happen in a flyback circuit.

Fig. 2—*Misconception:* Vertical output grid has a negative voltage if receiving vertical drive. *Fact:* When height or linearity controls are misadjusted, the grid will indicate a negative voltage. However, at normal control settings, grid voltage is zero.

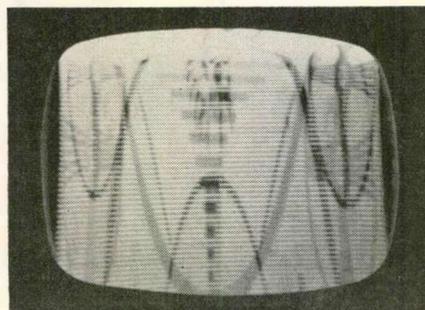

duce a linear sweep through the entire sweep cycle—just like audio amplifiers.

3. A shorted or partially shorted yoke will cause horizontal "keystoning" (trapezoidal raster).

This is true of series-connected yokes (Fig. 3A), except when used in direct drive sets. Many modern sets, though, use parallel yokes. That is, the horizontal yoke windings are connected in parallel (Fig. 3B) across the flyback. When a short occurs in a parallel yoke, the current increases in the defective section and decreases in the good section because the defective section now exhibits least resistance. This tends to balance the sweep efficiency of the good and bad sections, causing a narrow raster with *paralleled* sides, as shown. Technicians may confuse this with a weak horizontal output tube symptom. Rule of thumb then indicates a yoke check if width is still a problem after the horizontal output section has been checked out.

4. Boost voltage is an important measurement in horizontal circuit troubleshooting.

This fallacy is widespread among many TV technicians. You can nearly always start an argument with other technicians by simply saying that it is a misconception. To win the argument—simply ask the disputant to list what troubles he can determine by measuring boost. He'll fumble a bit, for all a boost measurement can do, except in extremely rare instances, is to indicate there is some (undetermined) amount of sweep energy or there is none. However, he already knows this or wouldn't be checking this circuit!

(Continued on page 60)


Shure PHONO CARTRIDGES

Models M7-N21D and M3-N21D stereo phono cartridges have been added to the M7D and M3D series. Equipped with N21D tubular stylus. Tracking force, 2 grams. Claimed for these new units is greater compliance and cleaner high-end frequency response. Also available is the M232 (12") and M236 (16") independent tone arms with either of the new cartridges installed and with the arm balanced and set at the proper tracking force. M7-N21D, \$36.75; M3-N21D, \$47.25; M232 arm with M7-N21D, \$66.70; M236 arm with M7-N21D, \$68.70; M232 arm with M3-N21D, \$77.20; and M236 arm with M3-N21D, \$79.20. M7D and M3D cartridges will continue to sell at \$24 and \$45, respectively. Shure Brothers, Inc., 222 Hartrey Ave., Evanston, Ill.

For more data, circle 2-35-2 on coupon, p. 46

EICO STEREO AMPLIFIERS

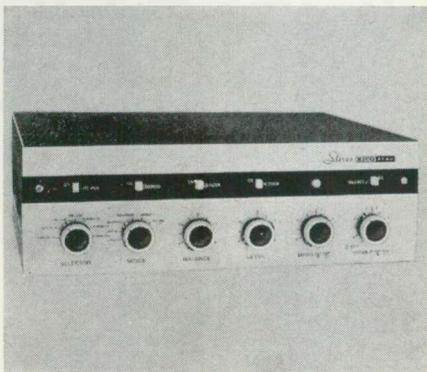Two stereo integrated amplifiers, built to handle any stereo program source, are: model ST70, contains 2 35-watt power amplifiers, frequency response, $\pm \frac{1}{2}$ db 10-50,000 cps, harmonic distortion, less than 1% from 25 to 20,000 cps; model ST40, fre-



quency response $\pm \frac{1}{2}$ db 12-25,000 cps, harmonic distortion, less than 1% 40-20,000 cps. ST70: kit, \$94.95, wired, \$144.95. ST40: kit, \$79.95, wired, \$124.95. Prices include metal cover Eico Electronic Instrument Co., 33-00 Northern Blvd., Long Island City 1, N. Y.

For more data, circle 2-35-3 on coupon, p. 46


RCA TRANSISTOR

Announced is a new "drift-field" power type transistor which makes it possible, economically to transistorize high-fidelity and public address systems, auto radios, jukeboxes and intercoms. It is a p-n-p germanium type for use in both Class A and B audio amplifiers; has an alloyed emitter, diffused collector and graded base; and delivers high audio power for monaural and stereo sound equipment when operated either from a car battery or standard house current. RCA Semiconductor and Materials Div., Somerville, N. J.

Mallory VIBRATOR

Type 1619 vibrator, developed for a photoflash application, employs a molded polyethylene case and is 20% to 30% lighter than a similar unit packaged in metal. The cylindrical case resists deformation at temperatures up to 150°F. Three leads extend through an epoxy-sealed hole in one end of the case. It is non-synchronous, has a frequency of 115 ± 7 cps and a maximum load of 3 amperes. Can be supplied in 3, 6, 12, 24 or 32v ratings. Mallory Electromagnetic Div., P. R. Mallory & Co., Inc., Du Quoin, Ill.

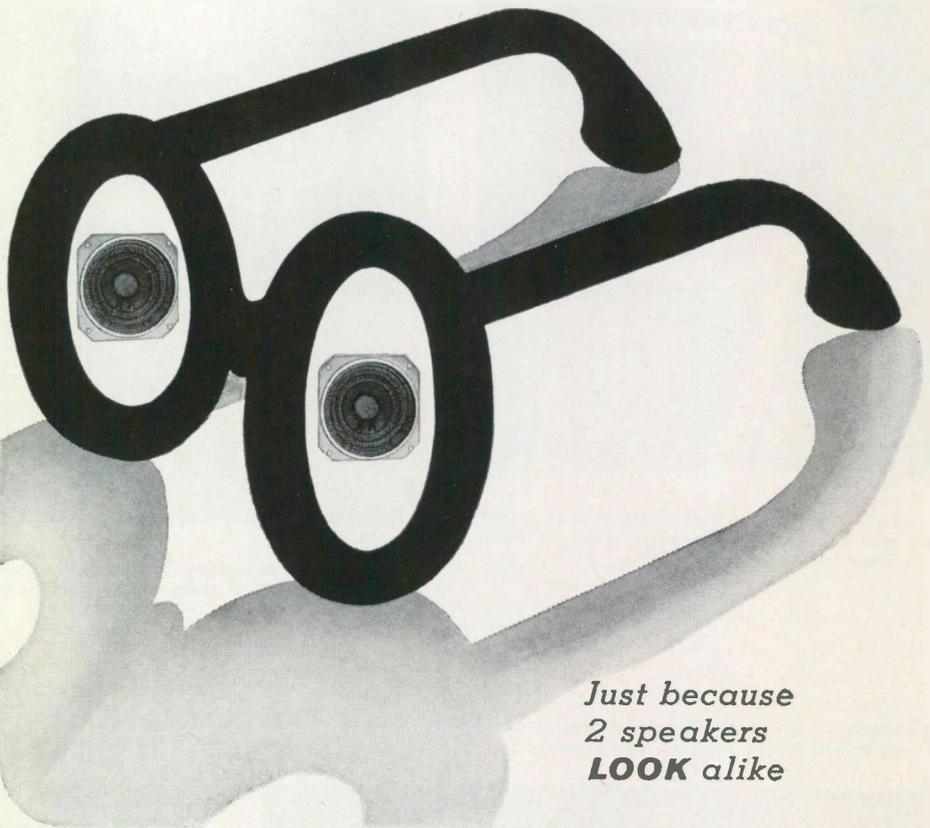For more data, circle 2-35-4 on coupon, p. 46



Just because
2 speakers
LOOK alike

doesn't mean they'll SOUND alike...
or that they'll give the same
trouble-free performance.


ask for **QUAM**

The NO CALL-BACK speaker with the exclusive Adjust-a-Cone Suspension
Completely manufactured in the United States of America

QUAM-NICHOLS COMPANY
226 East Marquette Road • Chicago 37, Illinois

For more data, circle 2-35-1 on coupon, p. 46

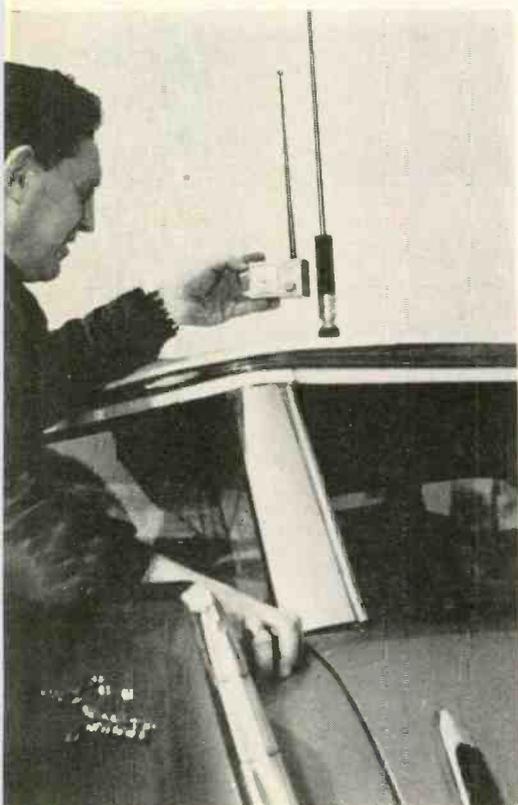When out on assignments, photographer uses mobile telephone to keep in constant touch with clients and his office. Control head of transmitter can be seen to left of the auto's air conditioner.



Technician Cooper holds field strength meter near base-loaded antenna to check out transmitter in Jacques' "wagon."



Local electronic technician, Bob Cooper, who keeps Saphier's equipment in top condition, peaks up one of the police radio monitors in photographer's station wagon.

Ultrasonic high speed film developing is one of the research projects undertaken during Saphier's spare time.



Saphier pushes button in dark room and electronic "computer" controls exposure when making photographic enlargements.



Electronics In Photography

*Photographer Employs Electronic Flash,
2-Way Radio, Ultrasonics
For Increased Efficiency*

LEE CRAIG

• Electronics helps Jacques Saphier to live up to his slogan "Have Camera—Will Travel—Anywhere—Right Now!" This 20th century professional photographer uses electronic devices in his darkroom, while taking pictures, and when on the road.

In order to receive assignments from United Press International and his many clients, he makes it easy for them to reach him. To contact Jacques Saphier, a client merely dials his telephone number. If his secretary is in, she answers the call. If not, a telephone answering service takes the call. Whichever got the call dials "operator" and asks for the mobile service operator who in turn dials Jacques' mobile telephone number.

If he is in his station wagon, the message is relayed to him via the mobile radiotelephone. But, if he is out of his car shooting pictures, the lighted "call" lamp on the telephone control head alerts him to check in with his office immediately.

Not satisfied with this arrangement, he is going a step further. A modified Link transmitter has been installed in his station wagon. When in operation, it will transmit a tone modulated radio signal

which will actuate the selective decoder in his Pagemaster pocket radio receiver. The Pagemaster will issue a beep, which will alert him to run out to his car to answer the telephone.

The 30-watt transmitter operates on 27.255 mc. It transmits for one second when it is actuated by the closure of the contacts of a relay connected to his mobile telephone. This relay is energized when the mobile telephone bell rings. Its contacts control a relay in the transmitter which puts it on the air. A time delay circuit automatically turns off the transmitter after one second.

The Pagemaster receiver, which Jacques plans to carry in his pocket at all times, is tuned to 27.255 mc and responds only to a specific tone.

This telephone bell extension will permit Jacques to know at all times when his mobile telephone is called. It has been tested manually, but is not yet in automatic operation. While already licensed as a class C Citizens Radio station, Jacques has appealed to the FCC to grant him a waiver of the rules to permit remote control of a Citizens radio station.

Besides the mobile telephone and the bell-extender transmitter, Jacques' station wagon is equipped



Photographer Jacques Saphier using a portable Citizens band transmitter-receiver while covering an out-door event. He uses photoelectric and "strobe" flash equipment on cameras.

with a class D Citizens Radio and an AM auto radio, plus HF and VHF fixed-tuned receivers. The HF receiver monitors a 25-50 mc band police radio channel; the VHF receiver monitors a 152-174 mc band police radio channel. Since he is the official photographer for the two police departments whose radio signals he monitors, Jacques has permission to do so.

While taking pictures he uses electronic flash equipment including photocell controlled slave units.

In his darkroom, Jacques employs an electronic computer which automatically controls the exposure time of his enlarger. A photocell looks at the projected image and feeds a signal to the computer which tells the computer how much light is available. As a result—perfect pictures every time.

Jacques also uses an ultrasonic cleaning system for cleaning darkroom tools, film holders and camera parts. The ultrasonic agitation frees them from developer, hypo and dirt.

Recently, Jacques has been experimenting with ultrasonic high speed film developing. The developer is placed in one of the ultrasonic cleaning tanks, hypo in another. By agitating the developer

(Continued on page 56)

Get Ready For Stereo Multiplexing

*A Prime Contender
For FCC-Approved
Stereo Broadcasting
Is Analyzed*

ALAN ANDREWS

• Ever since the advent of stereo sound production, *broadcasting* in stereo has been more desirable to many stereo equipment owners. Early attempts along this line utilized two stations, either AM and FM, or else FM and TV. This system had obvious disadvantages. It required two stations, a costly procedure, and at the receiving end two receivers are needed.

More plausible systems were de-


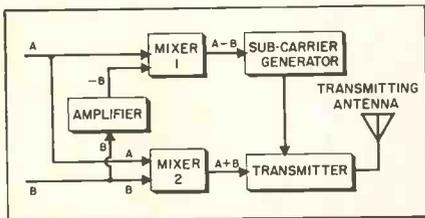


Fig. 1—Block diagram of the mixing circuits employed at a stereo multiplexing broadcasting station, showing the $A + B$ and $A - B$ type Crosby FM-FM transmission system.

Fig. 2—Shown here is a block diagram of an FM receiver multiplex converter.

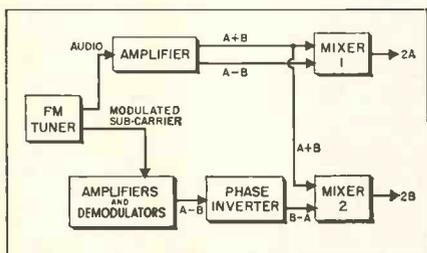

vised whereby stations could broadcast both stereo signals on the same carrier. One of the stereo signals modulated the carrier directly, the other signal was used to modulate a subcarrier which then modulated the main carrier. The general term multiplex is used to describe any communications system where more than one signal is transmitted on the same carrier. Accordingly, stereo broadcasting is often called a stereo multiplex system.

The subcarrier method produces adequate stereo when the proper equipment is available at the receiving end. But there is one primary disadvantage. To receive a broadcast in proper perspective the listener is obliged to be equipped for stereo. The listener, having only a conventional FM tuner, hears only part of the music; usually either the left or the right side of the orchestra. Therefore these systems are not compatible, which is a definite disadvantage.

A compatible stereo multiplex system produces stereo when the proper equipment is available, but also produces a complete output from monophonic equipment. This is comparable to our system of compatible color TV whereby the owner of a black and white receiver can see an acceptable picture even though the broadcast may be in color.

The National Stereophonic Radio Committee has evaluated numerous stereo multiplex system proposals in their efforts to recommend a stand-

ard to the F.C.C. One of the tests employed by the Committee included test-tape field tests using various taped musical selections. Some of these selections and test results are indicated in Chart I.

Among the stereo multiplex systems under FCC consideration is the Crosby system, using FM-FM transmission. (Several manufacturers have already produced stereo receiving equipment based on this system.) This is a compatible system, combining two signals so the combined form produces an acceptable output from a conventional FM receiver. Two separate signals are also available for use in stereo.

Transmission & Reception

A block diagram of the mixing circuits used at the transmitting station is shown in Fig. 1. Two stereo signals, A and B, are amplified and applied to mixer 1. This signal modulates the transmitter in the usual manner, and is the signal received by conventional FM receivers. B signal is amplified to produce an output labeled $-B$. Phase is inverted due to the normal reversal of phase between grid and plate of an amplifier. The $-B$ signal is then applied, along with signal A, to mixer 1 which produces the difference signal, labeled $A - B$. This signal modulates a 50 kc generator which is producing the subcarrier. The modulated subcarrier modulates the main carrier in the transmitter.

separation between the two signals after modulation.

Converter Operation

Filtered signals are simplified by stages V1B and V2A, the latter acting as a limiter, as in conventional FM demodulator circuits. Instead of using a discriminator or ratio detector, the limiter is followed by a different type of circuit, known as pulse or counter detection.

The method converts subcarrier signals into pulses, then controls tube conduction with these pulses. Conduction variations form an audio output equivalent to the frequency changes of the subcarrier signal. In Fig. 3, a triggered multivibrator,

using tubes V2B and V3A, produces the pulses. A cathode-coupled multivibrator is used, and component values are chosen to produce consistently shaped square waves at any frequency between 25 and 75 kc. Amplitude variations are eliminated by the limiter stage V2A, preceding the multivibrator.

In the grid circuit of the counter, V3B, the square waves are differentiated, subsequently applied to the counter as sharp pulses. Positive voltage is applied to the V3B cathode through a voltage divider. This voltage keeps the counter stage cut-off except when input pulses are applied to its grid. The same voltage divider places positive voltage on the grid of V3A, maintaining con-

duction. It holds V2B at cut-off, except when a subcarrier signal initiates a new cycle of multivibrator action. This prevents the multivibrator from operating at its own frequency and distorting the signal.

Positive differentiated pulses cause conduction of the counter stage at a rate determined by the frequency changes of the subcarrier signal. Each of the counter input pulses has the same amplitude and time duration, but the time between them varies. For the low-frequency components the pulses are spaced farther apart in time than for higher frequency components. Consequently, the average conduction of the tube is less for the

(Continued on page 58)

CHART I

Test Tape
Some NSRC Selections For Stereo Broadcast Field Tests

Selection	Suggested Condition To Be Tested	Prominent Resultant Spatial Changes For Center Listener	Excerpt	Album Title	Composer, Orchestra, Conductor, Artists, Etc.	Label	Max Sound Level "C" Scale (slow)
Pathetique	No separation of low freqs.	Tympani on left shifts to center	3rd movement last 2 mins.	Pathetique Symphony No. 6 in B Minor	Tchaikovski Boston Symphony Pierre Monteux	RCA-Victor GCS-5	86 db
A Foggy Day	No separation of low freqs. No separation of high freqs.	String bass on right shifts to center Also Brushes on left shift to center	1st 2 mins.	Donny Brook with Donegan (Disc)	Dorothy Donegan 3 Piece Jazz Combination	Capitol ST1226	87 db (82 used)
Arab Dance	No separation of low freqs. No separation of high freqs. Reduced sep. all freqs.	Broad image of bass and percussion shifts to center Tambourines, right shift to center Side instruments shift toward center	1st 2 mins.	Stereo Adventures in Exotic Lands	Tchaikovski Paris Theater Orchestra, Henri Gaste	Bel Canto ST 11	85 db
Classical Symphony	No separation of high freqs.	Violin section, left shifts to center	1st movement 1st 2 mins.	Classical Symphony	Prokofiev, Netherlands Phil. Orchestra, Walter Goehr	Concert Hall	85 db
You're An Old Smoothie	Reduced sep. all freqs.	Side voices shift toward center	1st 2 mins.	It's The Talk Of The Town	Ray Conniff Singers	Columbia GCB-47	83 db
2nd Piano Concerto	Reduced sep. all freqs. Delay in one channel	Piano, slight left, and Orchestra, left shift toward center Piano shifts to undelayed side	1st movement 1st 2 mins.	Rachmaninoff, 2nd Piano Concerto	Rachmaninoff, Rubenstein, Chicago Symphony	RCA-Victor ECS-19	88 db (86 used)
Surrey with The Fringe on Top	Reduced sep. all freqs. Add channels for mono	Side instruments shift to center Cymbal sounds unsteady. Example of Stereo-Mono not compatible	1st 2 mins.	Straight Down the Middle	Sauter-Finegan Orchestra	RCA-Victor CPS 113	87 db (82 used)

SHOP HINTS



Tips for Home and Bench Service

Pseudo Color-Bar From Video Analyst

If you get a picture like the one shown in Fig. 1 when you turn a B&K Video Analyst on, don't think you've got a color-bar pattern. It isn't! If you'll look inside the Analyst, you'll probably find you have a vertical deflection problem.

Mine turned out to be the vertical

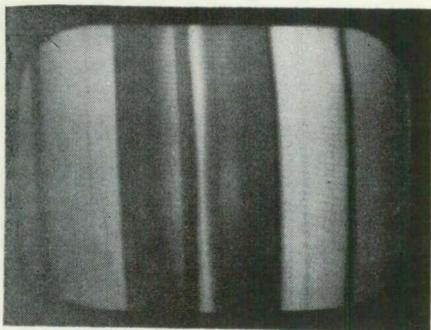


Fig. 1—What appears to be a color-bar pattern may indicate vertical deflection trouble in B&K Video Analysts.

output transformer: this is a standard 8:1 auto-transformer in case you want to replace it yourself without waiting for the part from the factory. Be sure to recheck your vertical linearity with a test pattern before putting the instrument back in the case; this test is described fully in the instrument's instruction book.—*Jack Darr, Mena, Arkansas.*

Solder Tool Tip Removal

By shooting a little graphite into the recess of a soldering iron before installing a new tip, the tip will remove readily when replacement time comes.—*Harry J. Miller, Sarasota, Florida.*

Volume Control Signal Pickup

Not long ago, I had a run of sound trouble on RCA 21CS7815, 21CT-7835, 21CD7895 Series color TV sets. The interfering signal could be heard with the volume control in the normal listening position or, in some cases, with the volume control turned completely counter-clockwise.

I found that the signal pick-up was due to the long leads from the volume control. In all cases (five instances) this interference was remedied by connecting a $470\mu\text{mf}$ capacitor between the grid and cathode of the first audio amplifier tube, shown in Fig. 2.

Keep the leads as short as possible, and do not attempt to use any ground point other than the cathode terminal of the tube socket, as this is *not* chassis ground.—*R. R. Fitzmaurice, Dunedin, Florida.*

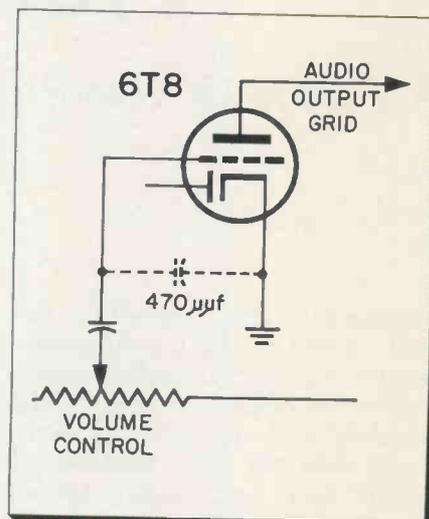


Fig. 2—Reader eliminates audio interference in RCA 21CS7815 color sets by installing a $470\mu\text{mf}$ capacitor between grid and cathode of the first audio amplifier.

Recorder Extension Feet

Tape recorder, changer and amplifier performance can be improved by providing extension feet to afford better ventilation and absorb vibration. Such extensions can be devised in seconds by using sections of garden hose, as shown in Fig. 3. Make these sections at least one-inch long and fit them over the existing plastic feet of the unit. In most cases it will be necessary to cut out one end of the hose section so that it will fit over the plastic foot.

After the correct height is assured, the inside of the hose can be smeared with a bit of white glue to make a permanent installation. Elevating the base of a recorder in this way assures improved air circulation and often reduces the mechanism noise.—*Glen F. Stillwell, Manhattan Beach, Calif.*

Fig. 3—Installing leg extensions made of garden hose can improve chassis ventilation and reduce motor noise.



Hand-Wired Chassis Soldering Problems

A Variety Of Non-Printed Circuit Solder Jobs Still Face Technicians

GEORGE KRAVITZ

• Although many radio-TV, and other electronic equipment manufacturers employ printed circuitry, hand-wired equipment is still very much in evidence. In fact, hand-wired units are being produced in rather large quantities. Consequently, proper application of modern soldering techniques to hand-wired equipment is still necessary and highly important.

Skilled electronic technicians already know that the ability to solder, unsolder, and re-solder properly is a prerequisite to becoming a successful technician. Manufacturers' production and quality control engineers, as well as assembly line inspectors, are all thoroughly aware of this fact.

Only an infinitesimal amount of "heavy handed" soldering passes present day original equipment manufacturers' test and inspection sections. The discriminate and observant technician, however, sees many examples of poor soldering in hand-wired circuitry that was accomplished by prior repair jobs. For example, cold solder joints, excessive flux, balls and splatters of solder clinging or floating around various sections of an equipment chassis. Heavy handed soldering leaves a shoddy, sloppy trail of overheated and damaged resistors, diodes, burned capacitor ends, broken terminals, and shorted termi-

nal strip tie points. And, what technician has never seen at least one broken tube socket terminal which has been "tack soldered" back into place—hanging by a thread of solder?

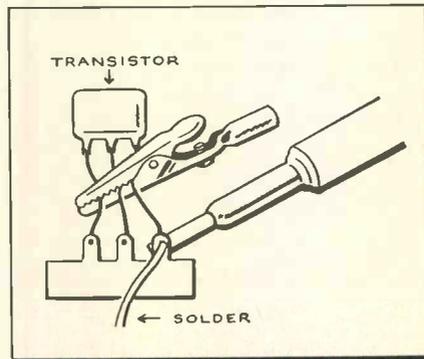


Fig. 1—When soldering-in a transistor, diode or small wattage resistor, an alligator clip is placed on the lead being soldered. Clip is a heat sink to dissipate excess heat which may damage component.

Soldering Fundamentals

Before digging into some of the fine points of removing and replacing hand-wired components, it may be helpful to review a few of the simple elementary rules which are automatically observed by all skilled technicians. Attention should also be directed briefly to some of the soldering pitfalls to be avoided.


A good soldering job that won't return to haunt us at the most inopportune moments must have the

following minimum requirements:

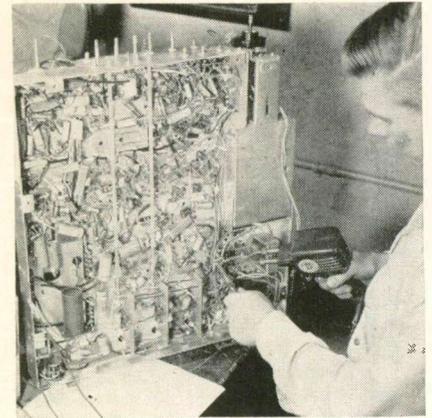1. A clean, thoroughly deoxidized surface.
2. Joint electrically and mechanically secure before soldering.
3. A 50/50 tin-lead or higher tin content, pure rosin cored solder.
4. Iron tip (gun or regular type), to be perfectly clean and brightly tinned.

Clean surfaces are obtained by scraping with a knife, file, sand paper, etc., and pre-tinning surfaces with rosin cored solder. A thoroughly secure joint, tie, or wrap, is one that will conduct electrically and cannot be disturbed by normal pulling or vibration—before it is soldered. The best way to keep a soldering iron tip clean while working is to wipe it frequently with a thoroughly wet cotton cloth or commercially available cleaning pad.

All other requirements being fulfilled, perhaps the outstanding technique involved in obtaining a good solder job is proper application of heat and solder. The joint to be soldered should be heated at one side with a flat surface of the iron tip, and the solder applied to the joint at the top or opposite side, as shown in Figs. # 1 & 2. When the joint is hot enough to cause the solder to flow freely, the iron should be removed. This temperature is about 125° to 150°F above the melting point of the particular solder being used. If more solder is required on the joint (this is seldom necessary



except in special cases), the process should be repeated. If a joint is properly heated, and solder applied directly to the joint, solder will flow into every crevice (through capillary action) and the highly desirable true alloyed joint will result.

In addition to the sad practice of carrying solder to a joint on an iron's tip (usually resulting in a cold solder joint), is the error of overheating. When a joint is overheated, solder runs off like water from a duck's back, or a greased surface. This is primarily true because the rosin flux is partly carbonized and cannot act to completely deoxidize the joint's surfaces.

No technician would think of using a two pound sledge hammer to drive an insulated twin-lead tack, or a tack hammer to drive a PK nail in cement. It is startling, however, to observe the number of technicians who do just this with soldering irons. The proper iron should be selected for a particular job. For example, a thin terminal strip lug carrying two #24 tinned leads can be heated and soldered with a 100 watt iron, properly manipulated. On the other hand, 200 to 250 watts are necessary to heat a chassis ground point for a heater transformer's center tap or comparable type grounded lead.

Another improper practice is holding a component or component lead while soldering. The slightest vibration or movement of a component lead before the solder cools, regardless of its apparent mechanical security to a tie point, can result in a bad solder joint. When cooled, this joint will appear dull, granulated or chalky. Do not hold the component or lead, even with long nose pliers. If a heat sink is required, snap an alligator clip or other type sink next to the joint to be soldered, as shown in Fig. 1. All component leads should be made self-supporting before attempting to solder.

One particularly helpful technique revealed by the experts, is a silver solder tinned soldering iron tip, regular or gun type. This silver solder tipped iron gives excellent heat transfer, lasts longer and develops scale infrequently. A solder pot and torch to heat the pot is necessary for doing this tinning job. The recently cleaned iron tip, at its

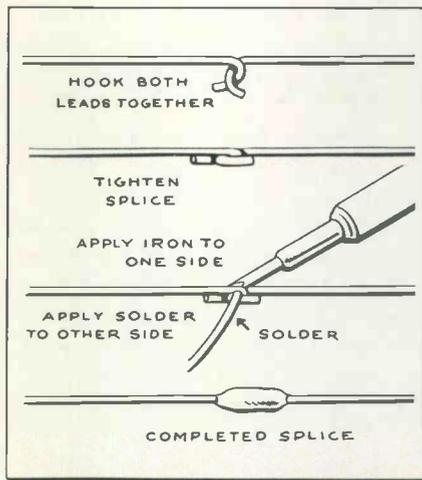


Fig. 2—The hook-splice is frequently helpful when replacing components which have been cut from a crowded terminal tie point.

normal temperature, is dipped momentarily into the molten silver solder one or more times.

Component Replacement

Component replacements in hand-wired chassis sometimes present a problem when three or more component leads are tied to one terminal point. We have all seen examples of "stacked up" components—with the defective part at the very bottom of the stack. There are several approaches to this situation. (A) Remove one lead on all components so they can be moved about, (B) pry and worm-out the defective part, (C) cut out the defective component leaving enough lead to allow splicing-in the new component. The latter method is frequently the most satisfactory.

A practical and widely used splice for component replacement under these conditions, is illustrated step-by-step in Fig. 2. Ends of the old component leads should be scraped and pre-tinned before the hooks are made. The two hooks should then be squeezed together tightly with long nose pliers and then soldered. Solder should not be piled up on the joint (except when soldering certain high voltage leads and terminal points), and the wire outlines of the two hooks should show plainly through the solder. Generally speaking, all finished joints should show approximately two-thirds of the wire thickness standing out from the solder—with one third being covered by solder.

If it is necessary to remove a wire or component lead from a lug, a slotted "soldering aid" type tool is helpful. Heat the lug properly and unwind the lead carefully with minimum pressure on the lug, using the soldering tool. Slotted soldering tiplets can also be used to perform the same task. Attempting to unsolder and remove wires from small thin lugs, for example, miniature tube socket contacts and similar tie points, is not recommended. If absolutely necessary to do so, great care should be exercised or the technician may find it necessary to completely replace a socket or other component.

When soldering leads to closely spaced multiple lug terminal strips, the technician should take precautions to prevent solder flowing to an adjacent lug. If soldering is properly done, however, this problem seldom arises. In the event too much solder is on a joint, for whatever cause, excess solder can be

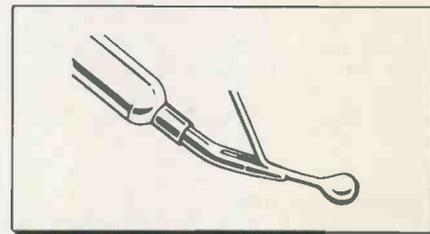


Fig. 3—An offset slotted iron triplet can be used to draw off excess solder from a terminal point. Solder flows into triplet notch.

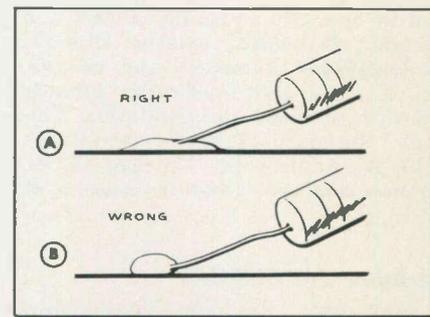


Fig. 4 (A)—A properly made chassis joint has a cohesive contour. (B) "Blob" type will not be electro-mechanically secure.

easily removed with an offset soldering triplet, as shown in Fig. 3.

Ground Connections

Mechanical ground connections made with bolt, washer and nut, or self tapping screws, are frequently

unsatisfactory because of inadequate lead-to-chassis contact. Soldering direct to a chassis is not an easy job. If a punch-out chassis terminal point or a hole is not available for hooking the lead into, the task must be carefully performed if future trouble is to be avoided. Perhaps the largest percentage of hand-wired repair and original equipment solder faults arise in chassis-ground connections—with or without punch-out terminals. In any event, proper cleaning and

heating are prime considerations. To solder directly against a white metal or plated chassis, proceed as follows:

First clean the area carefully with a sharp instrument, file or sandpaper. A thoroughly bright roughened area is desirable. Use a high-wattage gun (about 250 watt) or heavy duty iron and tin the scraped area, applying solder directly to the area and not to the iron. Remove the heating tool and freshly tin about one inch of the

lead end. Curl one turn of the component lead in a circle about $\frac{1}{4}$ inch in diameter. Spring and shape the circle and component lead so that the circular area fits flat and tightly against the tinned area. Apply the iron flat against the tinned area, touching and tangent to the component lead circle. Feed solder to the inner area of the circle until the joint appears as shown in Fig. 4.

If the lead is sufficiently long or there is no danger of overheating a component, the iron may be placed flat over half or more of the circle and solder fed to the inner circle as before. A heat sink can be attached to the component lead if desired. When the proper amount of solder appears at the joint the iron is removed and the joint allowed to cool without vibration or other disturbance. If the joint appears in the vertical plane, place the iron below, feed solder from the top. Capillary and alloying action will insure a good joint and excess solder that may be drained away by the iron will not interfere.

If there is any doubt about a solder joint, test it with a hooked tool by pulling the lead back and forth near the solder joint. A chassis joint can also be tested with a sharp pointed instrument (ice pick) or screw driver. Try to wedge the point between joint and chassis. A properly alloyed joint cannot be dislodged.

One additional caution regarding overheating. Not only can crystal diodes be damaged but $\frac{1}{2}$ watt or even larger carbon resistors can change value considerably if overheated. A 5% tolerance gold-stripe resistor can be made completely useless for its particular application by overheating its lead.


When a technician observes all the basic rules of good soldering and has a full line of proper irons, tips and specialized tools, the so-called problems of soldering quietly disappear.

Illustration credit: Ungar Electric Tools, Inc., Los Angeles, Calif.

Centralab CONTROLS

Five new exact replacement auto radio controls, for use in 1959 Delco auto radios are: Part No. BD-59, replacement for original part No. 7273993 used in 1959 Buicks; CD-59-A and CD-59-B, replacements for original part No. 7273302-1221260 and 7273367-1221268 used in 1959 Chevrolets; OD-59, replacement for original part No. 7272855, used in 1959 Oldsmobiles; and POD-59, replacement for original part No. 7273623, used in 1959 Pontiacs. Centralab Div., Globe-Union Inc., 900 E. Keefe Ave., Milwaukee 1, Wis.

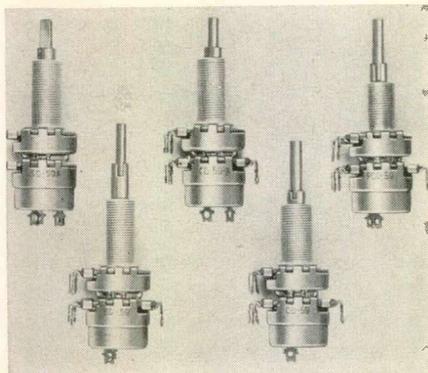
For more data, circle 2-44-1 on coupon, p. 46



STANCOR YOKES

3 new exact replacement deflection yokes are: DY-41A, for RCA Part Nos. 76616, 77625, 77697, 79510, 79868, used in almost 250 models and chassis; DY-42A, for RCA 103830 and Sylvania 100-0031, 100-0032, 100-0033, used in 10 RCA models and chassis and in over 200 Sylvania models and chassis; DY-46A, replaces Olympic CL-26215 in 14 models and chassis. All 3 units have networks already wired in to speed up installation. Chicago Standard Transformer Corp., 3501 W. Addison St., Chicago 18, Ill.

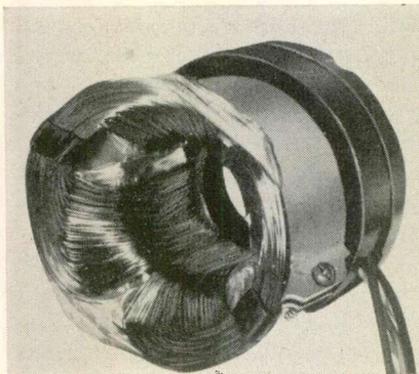
For more data, circle 2-44-2 on coupon, p. 46



Sprague CAPACITORS

Announced are two specially-selected assortments of Isofarad capacitors. TK-22, shown, contains 11 capacitors in the 7 most-frequently-used ratings. TK-8 includes 17 capacitors in the 7 most popular ratings. Packaged in crystal-clear, hinged-lid, compartmented plastic cases; each compartment identified by catalog number and rating. Designed for color TV synchroguide circuits, horizontal and vertical oscillators, etc. Sampler assortment TK-22, \$5.88. TK-8, \$9.18. Sprague Electric Co., North Adams, Mass.

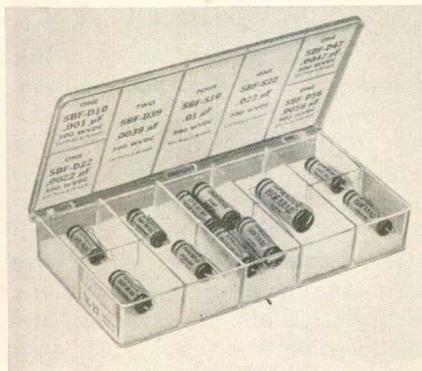For more data, circle 2-44-3 on coupon, p. 46




MOVING?

If you plan to change your address, please notify us at least 8 weeks prior to moving in order to assure uninterrupted service. Write to Circulation Dept., ELECTRONIC TECHNICIAN, 480 Lexington Ave., New York 17, N. Y., stating both your present and future addresses.

First real VOM advance in 20 years

SET IT!

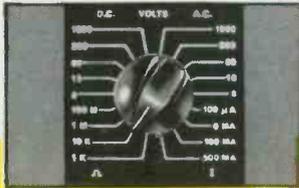


SEE IT!



READ IT!

DIRECTLY—ACCURATELY
WITHOUT MULTIPLYING

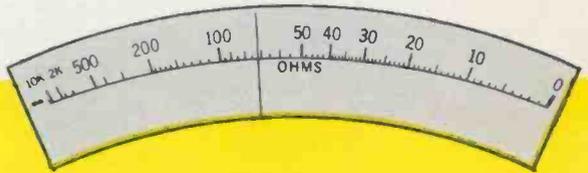

ALL-NEW

B&K

V O Matic 360

AUTOMATIC VOLT-OHM-MILLIAMMETER

- Individual Full-Size Scale for Each Range
- Range Switch Automatically Sets Correct Scale
- Only One Scale Visible at Any Time
- No Multiplying . . . No False Readings
- Meter Protected Against Extreme Overload
- Mirrored-Scale for Precise Readings



EASIEST—FASTEST—ERROR-FREE READINGS

Once you set the range switch properly, *it is impossible to read the wrong scale.* Readings are easiest, fastest of all—so easy the meter “practically reads itself.” Eliminates reading difficulties, errors, and calculations.

All scales, including the ohms scale, are *direct reading.* You do not have to multiply. Saves time and trouble. Gives you the right answer immediately. Ohms-adjust control includes switch that automatically shorts out test leads for “zero” set.

Every scale in the V O Matic 360 is the same full size . . . and only one scale is visible at any one time, automatically. Supplemental ranges are also provided on separate external overlay meter scales.

This new-type automatic VOM is another innovation by B&K that gives you features you’ve always wanted. Outdates all others.

Includes convenient stand to hold “360” for correct viewing in 4 positions.

Net, **\$59⁹⁵**

Ask Your B&K Distributor for Demonstration or Write for Catalog AP17-T

- Ranges:** DC Volts — 0 - 3, 15, 60, 300, 1000, 6000 (20,000 Ω/v)
 AC Volts — 0 - 3, 15, 60, 300, 1000, 6000 (5,000 Ω/v)
 AF (Output)— 0 - 3, 15, 60, 300 volts
 DC Current — 0 - 100 μ a, 5 ma, 100 ma, 500 ma, 10 amps
 Resistance — 0 - 1000 ohms (3 Ω center)
 0 - 10,000 ohms (50 Ω center)
 0 - 1 megohm (4 k Ω center)
 0 - 100 megohms (150 k Ω center)

- Supplemental Ranges:** 18 separate external overlay meter scales for:
 DC Volts— 0 - 250 mv Capacitance—100 mmfd to 4 mfd
 Audio Power Output—up to 56 watts DB (decibels)
 Peak-to-Peak AC (sine) Volts— 0 - 170, 850

- Polarity Reversing Switch and Automatic Ohms-Adjust Control**
Frequency Response AC: 5 - 500,000 cps
Burn-Out Proof Meter: Protected against overload and burn-out
Complete with 1½-volt and 9-volt batteries and test leads



B & K MANUFACTURING CO.
 1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.
 Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
 Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

FREE LITERATURE

To receive the literature below without charge, simply circle the numbers on the coupon.

Cut out and mail to ELECTRONIC TECHNICIAN, 480 Lexington Ave., New York 17, N. Y.

1 Sound Equipment: Components and complete systems for users of public address and allied equipment are covered in a 16-page catalog, No. 307C. Illustrations, descriptions, specifications, and prices included. Bogen-Presto.

For more data, circle 2-46-1 on coupon

2 Home Study Courses: Among several up-to-date electronic courses recently announced are Semiconductors, Hi-Fi & Sound Systems, Radiotelephone License, and Industrial Electronics. International Correspondence Schools.

For more data, circle 2-46-2 on coupon

3 Electronic Components: Transformers, coils, chokes, yokes, inductors, etc., are covered in 32-page catalog 6001. Cross-referenced parts number index included. Merit Coil & Transformer Corp.

For more data, circle 2-46-3 on coupon

4 Components: A 151-page catalog contains complete listings of the firm's universal-type components with specifications. Includes cross reference charts and

prices of major parts used in firm's TV receivers, radios, and record changers as far back as 1949. Motorola Inc.

For more data, circle 2-46-4 on coupon

5 Tube-Checker Kits: Literature covers model T-61C and T61F self-service tube-checker kits. Designed for fast, easy, operation; and reported to provide high accuracy and dependability. Paco Electronics.

For more data, circle 2-46-5 on coupon

6 CB Transceiver: Literature covers model CB1200, combined crystal controlled transmitter and continuous tuning superheterodyne receiver, for use in 11 meter class "D" citizens band. Shell Electronics Mfg. Corp.

For more data, circle 2-46-6 on coupon

7 Antenna Mounting Accessories: Colorful, well-illustrated, 20-page catalog No. 60 and accompanying 16-page price list cover a complete line of antenna mounting accessories. South River Metal Products Co.

For more data, circle 2-46-7 on coupon

8 Antennas & Accessories: Catalog FR-61-B provides 16 well-illustrated pages of information on antennas, mounts, suppressors, mikes, etc. Telco Electronics Mfg. Co.

For more data, circle 2-46-8 on coupon

9 Background Music: Special program for TV-electronic service dealers details how to get into lucrative background music business with only small investment. Deal directly with manufacturer. Attractive brochure, data and application form describe tape system and contract terms. Musi-Pak, Inc.

For more data, circle 2-46-9 on coupon

10 Scope Carrier: Covered in catalog is a scope carrier designed to mobilize your work. Folds to fit into trunk or car. Top: level, and 22° angle. Capacity: 350 lbs. Chrome finish. 4" wheels. Many Models. Technibilt Corp.

For more data, circle 2-50-2 on coupon

CUT HERE

Use this coupon, or your letterhead, before March 20, 1961

Please send me literature of companies whose code numbers I have circled below (includes editorial and advertised items):

Note: Code 2-3-1 means February issue, Page 3, 1st item on page.

2-2-1	2-20-3	2-44-1	2-49-1	2-54-4	2-61-1
2-5-1	2-20-4	2-44-2	2-50-1	2-55-1	2-61-2
2-6-1	2-20-5	2-44-3	2-50-2	2-56-1	2-61-3
2-7-1	2-20-6	2-45-1	2-51-1	2-56-2	2-61-4
2-8-1	2-20-7	2-46-1	2-51-2	2-56-3	2-61-5
2-10-1	2-20-8	2-46-2	2-52-1	2-57-1	2-61-6
2-11-1	2-21-1	2-46-3	2-52-2	2-57-3	2-62-1
2-12-1	2-23-1	2-46-4	2-52-3	2-57-4	2-62-2
2-13-1	2-24-1	2-46-5	2-52-4	2-58-1	2-62-2
2-16-1	2-25-1	2-46-6	2-52-4	2-58-2	2-62-3
2-16-2	2-26-1	2-46-7	2-52-5	2-59-1	2-63-1
2-18-1	2-35-1	2-46-8	2-53-1	2-59-2	2-63-2
2-19-1	2-35-2	2-46-9	2-54-1	2-60-1	2-64-1
2-20-1	2-35-3	2-47-1	2-54-2	2-60-2	2-64-1
2-20-2	2-35-4	2-48-1	2-54-3	2-60-3	2-C3-1

Name Position

Firm Address

City Zone State

Note: If you have given your residence address above, please enter your company name and address on this line:

NEW

TESTS All TV and Radio Tubes
—both old and new

TESTS the Nuvistors

TESTS the new 10-pin tubes

TESTS the new 12-pin Compactrons

TESTS voltage regulators, thyratrons,
auto radio hybrid tubes,
European hi-fi tubes, and
most industrial types.



Model 600 DYNA-QUIK

only \$69⁹⁵
NET

8½" x 11" x 4½"
Handsome, sturdy
leatherette-covered
carrying case

NEW TUBE INFORMATION SERVICE

available every 3
months for all B&K
Dyna-Quik Tube Testers



for the first time, a
B & K QUALITY
TUBE TESTER
at this
amazing low cost!

Checks for all shorts, grid
emission, leakage, and gas

Checks each section of multi-
section tubes separately

Checks tube capability under
simulated load conditions

Rejects bad tubes
—not good tubes

For the man who wants the performance and reliability of a B&K professional-quality tester at minimum cost . . . there's nothing like the new "600". No other tube tester in this price range is so complete and up-to-date. Tests the newest tube types, as well as the old. It's fast . . . it's accurate . . . it's easy to use. Quickly reveals tube condition. Saves customers. Sells more tube replacements. Stops call-backs. Steps up servicing profit . . . day after day. Pays for itself over and over again.

Exclusive adjustable grid emission test. Sensitivity to over 100 megohms. Phosphor bronze socket contacts. Complete tube listing in handy reference index. Extremely compact.

B & K MANUFACTURING CO.

1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.

Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

For more data, circle 2-47-1 on coupon, p. 46



Illinois

TESA, Chicago, reports the following officers were unanimously elected: Pres., Nick Donato; 1st V. P., Marshall Ruehrdanz; 2nd V. P., Al Enzulis; 3rd V. P., John Cahill; Secy., Angelo Chrysogelos; Treas., Joseph Issak; Sgt. at Arms,

Bill Hamada; Ch'man of B'd., Frank Moch.

Indiana

TVB, Elkhart, elected the following officers: Pres., Willis Roberts; V. P., Dale Dinkledine; Sec'y., Arden Gaerte; Treas., Hubert McAllister.

License Fund Faltering

IESA, Indianapolis, urges members to contribute towards their Licensing Fund, introduced at an October meeting, advising that all have not fulfilled their "one service

call per quarter" pledge. Contributions to TESA-Kansas City to check the "license war" is also urged.

Missouri

TESA, Columbia, advises the following officers have been elected: Pres., Benton Linder; N. E., V. P., Ken Cleaton; S. E. V. P., Fred Reichman; N.W.V.P., William Ragen; S. W. V. P., Albert Hawn; Sec'y., Marion Crane; Treas., Carl Adcock.

New York

TSA, Albany, elected the following officers for 1961: Pres., Warren Baker; V. P., Robert Cooper; Sec'y., Roger Wells; Treas., Henry Szypulski.

License Bill Outlined

ESFETA, Albany, reports a special meeting of the License Committee was held with legal counsel to review their proposed license bill. Here is a brief outline of the proposed bill:

- (1) Any TV technician now engaged in TV repair is eligible under a grandfather clause.
- (2) Anyone over 16 years of age may apply for an apprentice license.
- (3) License fee will be \$25 for techs and \$10 for apprentices.
- (4) Seven men will comprise the license board: four licensed technicians, one TV manufacturer's service manager, one electronics teacher (appointed by the State Board of Education), and one individual (with no interest in the TV service industry) to represent consumers.


North Carolina

NCFEA, Mt. Airy, has elected the following officers: Pres., Glenn Thacker; V.P., Sparky Vogler; Sec'y., Mack Wood; Treas., Vic Goad.

Pennsylvania

"Pay TV" Stand

FRTSA, Harrisburg, has elected the following officers: Pres., Wayne Prather; Rec. Sec'y., Clarence Eck; Cor. Sec'y., Leon J. Helk; Treas., L. B. Smith. The Federation's stand regarding "Pay Television or Subscription TV" had been misquoted in the press as opposing the new media. FRTSA advises they do not oppose Subscription TV, but *would* oppose any monopolistic service practices by any and all interests that would tend to make the new system a "captive" one.

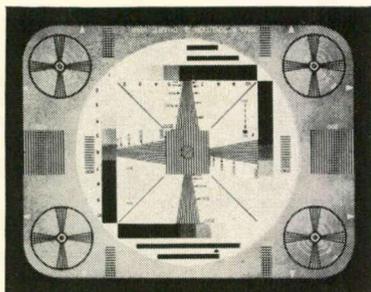

TV TIPS FROM TRIAD

NO. 11 IN A SERIES

"—and then this character with the calibrated eyeballs looked at the next chassis coming down the line, saw it was an inch and a half narrow, reached into the 39 mickey mouse tray for a 4 KV disc, hung it on the damper plate and cathode and sure enough the scan spread out and covered the CRT and the picture became brighter," said Joe, as he reported on his trip to the local TV chassis factory.

"Were all the sets an inch and a half narrow?" asked Ray the outside man.

"No, the one before was almost OK, and a later job was too wide," answered Joe, "and all the scan adjuster did was to clip the collar on the yoke cable and spread the leads a little and the pattern narrowed down to normal."

"Why didn't he adjust the width control, or drive or something?" asked Ray.

"No drive, no width, no lin, no capacity links, no nothing, on that 'Special,'" said Joe with a laugh.

"As long as the line voltage holds optimum, and all tubes and parts are normal, or better, the set may work OK," commented Bill, the Senior PTM, "but the point the serviceman has to watch is to maintain the capacitive balance when he services the set. Changing the flyback, even with an original replacement, will almost always call for change of the 'width calibrating' capacitor because flyback distributed capacitance varies slightly, lead dress may be disturbed, and the only way the width-high voltage relationship can be controlled is by adjustment of the shunt capacity. Don't forget that this capacitor may not be as obvious as in the case Joe mentions; it may be in the AGC circuit, across taps on the flyback, it may be the capacitive divider for the yoke center tap return, may be developed in the yoke cable, or be hidden out in the yoke itself. If the center tap of the yoke is returned to a center tap on the flyback, a capacitor across the 'hot' yoke winding will be as much a width calibrator as an anti-ringing network."

* * *

MORAL: Width and high voltage must be correct when you finish a sweep service problem. If you care to investigate further read page 5, col. 3, and page 7, col. 2 of PTM #2. If you don't have your copy ask your Triad Distributor or write direct to Renewal Division, Triad Transformer Corporation, 4055 Redwood Avenue, Venice, Calif.

For more data, circle 2-48-1 on coupon, p. 46

DOUBLES YOUR EFFECTIVE MANPOWER



Fix "Tough Dogs" Fast!

Save Half Your Time!

Step Up Your Profit!

B&K NEW
MODEL 1076

TELEVISION ANALYST

for Black & White and Color



Check all circuits—Pinpoint any TV trouble...in minutes

**By Easy Point-to-Point Signal Injection,
You See the Trouble on the TV Screen and
Correct it—Twice as Fast and Easy!**

There's no longer any need to "lose your shirt" (and customers)—and worry about the lost hours you never recover—on "tough dogs" or even intermittents. The remarkable B&K Analyst enables you to inject your own TV signal at any point and watch the resulting test pattern on the picture tube itself. Makes it quick and easy to isolate, pinpoint, and correct TV trouble in any stage throughout the video, audio, r.f., i.f., sync, and sweep sections of black & white and color television sets—including intermittents. Makes external scope or wave-form interpretation unnecessary. Most useful instrument in TV servicing! Its basic technique has been proved by thousands of successful servicemen the world over.

The Analyst enables any serviceman to cut servicing time in half, service more TV sets in less time, really satisfy more customers, and make more money.

Model 1076. Net, \$29995

Available on Budget Terms. As low as \$30.00 down.

See Your B&K Distributor or Write for Bulletin AP17-T

Combines all the features of both
the Model 1075 and Model A107

- | | |
|--|--------------------------------------|
| COMPLETE R.F. and I.F. | HI-VOLT INDICATOR |
| VIDEO TEST PATTERN | YOKE and HI-VOLTAGE TRANSFORMER TEST |
| COMPOSITE SYNC | Also Now Provides: |
| FM MODULATED AUDIO | SWITCH-TYPE TUNER |
| COLOR PATTERNS | NEGATIVE BIAS SUPPLY |
| HORIZONTAL and VERTICAL PLATE and GRID DRIVE | AGC KEYING PULSE |
| B+ BOOST INDICATOR | PICTURE TUBE MODULATION |



B & K MANUFACTURING CO.
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

For more data, circle 2-49-1 on coupon, p. 46



TWO-WAY RADIO

communications equipment

VHF-FM FOR:	VHF-AM FOR:	VHF
MOBILE	AIRPORT VEHICLES	ANTENNAS
AIRCRAFT	GROUND STATIONS	REMOTE CONTROLS
MARINE	POINT-TO-POINT	ACCESSORIES
MOTORCYCLE		
PORTABLE		
BASE		



NEW! "680 BASECOM"

FOR VHF-FM TWO WAY
MOBILE RADIO

the new 680 series offers
**HIGH PERFORMANCE at
MODERATE COST with
LOW MAINTENANCE!**



"680" FEATURES AND OPTIONS:

- ★ **PROVEN PERFORMANCE**... all the outstanding features of the popular "580" series, plus the following.
- ★ **HIGH POWER**... 100 watts output 25 to 50 mc, 75 watts 144 to 174 mc, both base and mobile.
- ★ **STONE SQUELCH**... two way tone squelch compatible with other systems to EIA standards.
- ★ Meets all FCC and OCDM requirements.
- ★ **SIMULTANEOUS RECEPTION**... dual front end receiver for monitoring two frequencies anywhere in the band.
- ★ **TRANSMITTER FILAMENT SWITCH**... reduces battery drain when on "stand-by"
- ★ **MONITORS REMOTE CONTROL**... base station monitors remote transmissions. Intercom provided. All functions available at remote position.

"680 FLEETCOM"

COMBINATION

- MOBILE CONTROL HEAD
- SPEAKER
- TRANSISTOR POWER SUPPLY



DESIGNERS AND MANUFACTURERS OF RADIO COMMUNICATIONS EQUIPMENT

COMMUNICATIONS COMPANY, Inc.

FOUNDED 1938

CORAL GABLES, MIAMI 34, FLORIDA

For more data, circle 2-50-1 on coupon, p. 46



SCOPE CARRIER

Mobile-izes your work!
Folds, fits trunk of car
Top: Level, and 22° angle
CAPACITY: 350 pounds
Chrome finish — 4" wheels

Thousands in use!
Many models — \$38.50 up

Write for catalog now!

TECHNIBILT
CORPORATION
GLENDALE 1, CALIF.

For more data, circle 2-50-2 on coupon, p. 46

Hearing Aids

(Continued from page 32)

plifier repair business, you must establish sources of supply for cords, plugs and other special parts. Some hearing aid manufacturers will furnish service manuals. Some will not. See Chart II for a list of major

CHART I

Parts & Accessories Suppliers

A. J. Schneider, Reading, Mass.

ADCO Distributors, 631 15th St., Denver 2, Colo.

All-Makes Hearing Aid Exchange, Mellie Esperson Bldg., Houston 2, Tex.

Danavox, c/o Rye Sound Co., 145 Elm St., Mamaroneck, N. Y.

Hal-Hen Co., 3614 11th St., Long Island City 6, N. Y.


Hearing Mart, 84 Ellis St., San Francisco, Calif.

Mears Radio Hearing Device Corp., 145 Elm St., Mamaroneck, N. Y.

Shelby Instrument Co., 1701 Magnolia Ave., Long Beach, Calif.

hearing aid manufacturers). If you're going to do farmed-out work for hearing aid dealers, they should be able to help you get parts and servicing information.

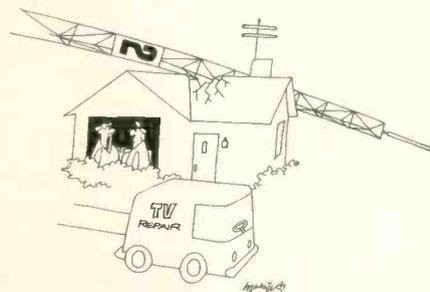The standard price, \$12.50, is fair compensation for a repair job, including parts. Seldom will you find more than one defective part or transistor. Cords, plugs, earphones and batteries are extra, since they are expected to require frequent replacement. •



"The picture's fine but I can't get channel 2."

CHART II

Hearing Aid Manufacturers & Distributors

Acousticon International, 95-25
149th St., Jamaica, N. Y.

Audio Company of America, 401
W. Jackson St., Phoenix, Ariz.

Audiovox, 123 Worcester St.,
Boston 18, Mass.

Beltone Hearing Aid Co., 2900
W. 36th St., Chicago, Ill.

Dahlberg Co., (Motorola), Gold-
en Valley, Minneapolis 27,
Minn.

Danavox, c/o Rye Sound Co.,
145 Elm St., Mamaroneck,
N. Y.

Gem Earphone Co., 89 E. Jericho
Trnpke, Mineola, N. Y.

Hal-Hen Co., 36-14 11th St.,
Long Island City 6, N. Y.

Kendall Laboratories, Inc., 440
E. Las Olas Blvd., Ft. Lauder-
dale, Fla.

Lafayette Radio, 165-08 Liberty
Ave., Jamaica 33, N. Y.

Maico Electronics, Inc., 21 No.
Third St., Minneapolis, Minn.

Muller-Ernesti, Hamburg-
Wandsbek, Germany

Nichols & Clark, Inc., Hathorne,
Mass.

Otarion Listener Corp., Ossin-
ing, N. Y.

Paravox, Inc., 2056 E. Fourth
St., Cleveland 15, Ohio

Qualitone Co., Linden Hills Sta-
tion, Minneapolis, Minn.

Radioear Corp., Valley Brook
Rd., Canonsburg, Penna.

Sears, Roebuck & Co., Chicago,
Ill.

Sonotone Corp., Elmsford, N. Y.

Superior Hearing Aid Co., 411
W. 7th St., Los Angeles 14,
Calif.

Telex, Telex Park, St. Paul,
Minn.

Tonemaster Mfg. Co., 128 S.
Monroe, Peoria, Ill.

Trans-Audio Corp., 45 Bromfield
St., Boston 8, Mass.


Vicon Instrument Co., Vicon
Bldg., Colorado Springs, Colo.

Zenith Radio Corp., 5801 W.
Dickens Ave., Chicago 39, Ill.

CBS TOOL

"Kwik-Klip," for quick and easy TV antenna lead replacement, provides simple, one-hand, clip-on operation. Its use eliminates the bother of removing rusted or corroded nuts and bolts to replace the antenna lead-in; and avoids unnecessary danger when working on roof tops. Its use is also reported to improve reception and restore the original signal strength in many older installations. CBS Electronics, Danvers, Mass.

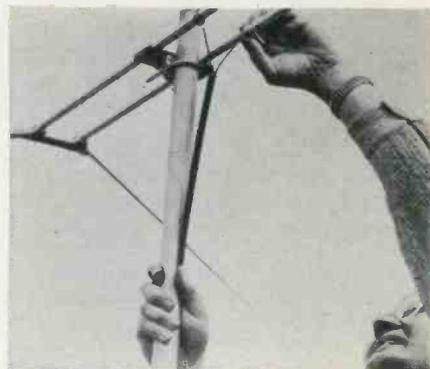For more data, circle 2-51-2 on coupon, p. 46



NOW TEST ALL TUBES



with Models 500, 550, or 650 DYNA-QUIK

SIMPLY BY ADDING THIS

NEW MODEL 610 TEST PANEL



TESTS
OVER 1600
TUBE TYPES

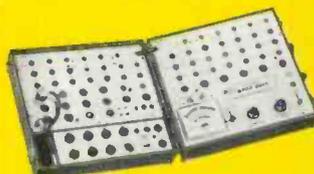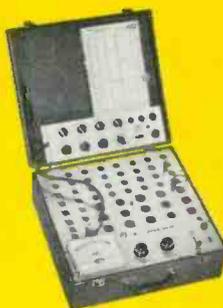

Photos above show how easily the new Model 610 Test Panel fits into the B&K Models 550 and 650 Dyna-Quik Tube Testers.

TESTS OLD AND NEW TUBE TYPES

Measures Genuine Dynamic Mutual Conductance

Also Tests Thyratrons, Voltage Regulators,
Auto Radio Hybrid Tubes, Battery Radio Tubes,
European Hi-Fi Tubes, and most Industrial Types

Merely by adding the new "610" to your Dyna-Quik, you have all the advantages of fast, multiple-socket testing, *plus freedom from obsolescence*. Makes your B&K Model 500, 550, or 650 Tube Tester *more useful and more valuable than ever!* Enables you to test all present plus future TV, radio and other tube types for all shorts—gives highly sensitive grid emission and gas test—checks for leakage and life—*with laboratory accuracy*.

Speeds complete tube test, sells more tubes on-the-spot, saves call-backs, insures your professional reputation, and brings more servicing profit. *It pays to invest in B&K professional equipment.*

Net, \$4995

NEW TUBE INFORMATION SERVICE

Get test data on new tubes even before you encounter them in the field. Subscribe now to New Tube Information Service for owners of B&K tube testers. Issued every 3 months, at \$2.50 per year.



B & K MANUFACTURING CO.

1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.


Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

For more data, circle 2-51-1 on coupon, p. 46

Ungar WIRE STRIPPER

New thermo wire stripping clips strip wire insulation while soldering without changing tools. It can be used with any of the Ungar #4000 series soldering tips or heating units by slipping it on the barrel. Severs all rubber and plastic insulation from 8 to 24 gauge wire and will not cut, nick or score the strands. Available in types #7951, #7952, and #7953 the wire stripper affords the user a choice of v-shaped, notched or circular cutting edges. \$.75 per unit. Ungar Electric Tools, 4101 Redwood Ave., Los Angeles 66, Calif.

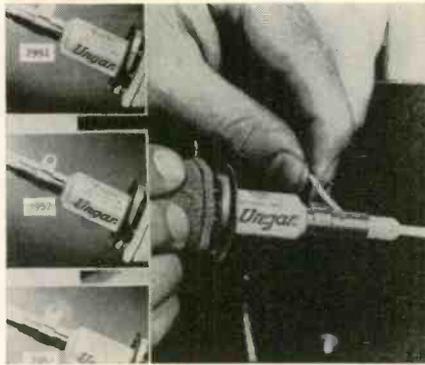For more data, circle 2-52-3 on coupon, p. 46



Sylvania TUBES

Announced are the following receiving tubes: 12FX8, 9-pin miniature triode and heptode used in super-heterodyne receivers as a triode r-f amplifier and frequency converter; 1N2A, filamentary half-wave diode for use in high voltage rectifier applications including TV; 60FX5, 7-pin miniature power pentode for the audio output stages of radio, phonograph, and TV; 2FQ5, semi-remote cutoff triode for use as a VHF r-f amplifier; and 13EM7, double triode with dissimilar sections, section 1 is used as a vertical deflection oscillator, section 2 as a vertical deflection amplifier in TV receivers. Sylvania Electric Products, Inc., 730 Third Ave., New York 17, N. Y.

For more data, circle 2-52-4 on coupon, p. 46



TV TUNER OVERHAUL

ALL MAKES ONE PRICE
\$9.95

VHF TUNERS • UHF TUNERS • UV Combinations*

Castle overhaul charge includes all labor and minor parts and written 90 day warranty. Tubes and major parts are extra at net prices. Tuner to be overhauled should be shipped complete; include tubes, shield cover and any damaged parts. Write down model number and state complaint. Pack well and insure.

Castle, pioneers of TV Tuner overhauling, assure the best service available. Remember, Castle has a decade of experience and overhauling tuners is our only business.

*UV combination tuner must be of one piece construction. Separate UHF and VHF tuners must be dismantled and the defective unit only sent in.

SAME DAY SERVICE!

On Popular Types
48 Hours most others

Castle

TV TUNER SERVICE, INC.

5710 N. Western Ave. • Chicago 45, Illinois
In Canada: 136 Main Street • Toronto 13, Ontario

For more data, circle 2-52-1 on coupon, p. 46


Sencore SUBSTITUTION UNIT

The Big 20, model PR11 has 20 power resistors for fast, on-the-spot substitution of all power resistors. Covers all the values encountered in radio, TV, and Hi-Fi circuitry. Each power resistor can be substituted in circuits that dissipate up to 20 watts



and for all values between 2.5 and 15,000 ohms. It will also substitute for fuse resistors. Each resistor in the unit is reported to withstand up to four times the fuse resistors operating current without burning out. \$12.75. Sencore-Service Instruments Co., Addison, Ill.

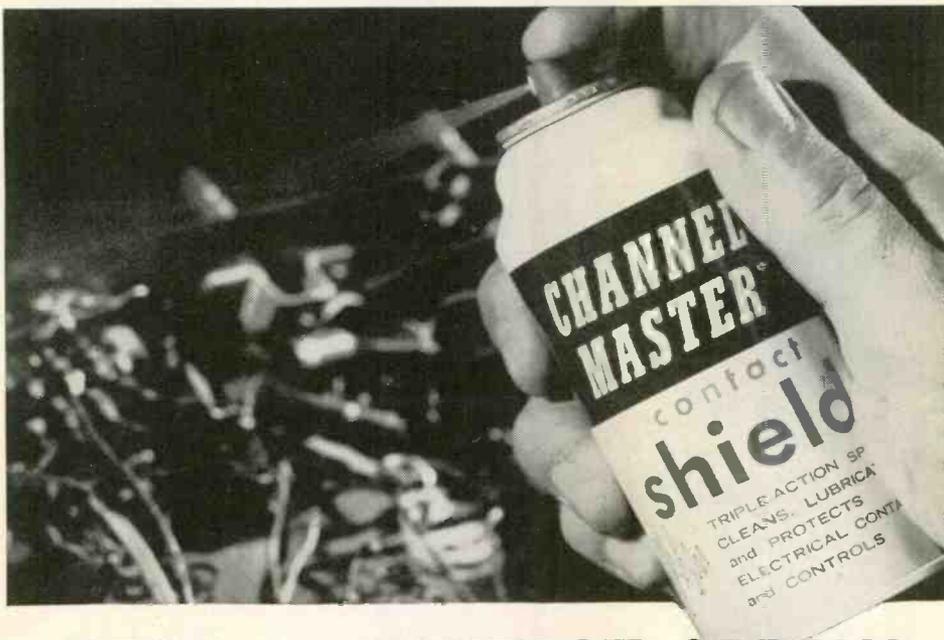For more data, circle 2-52-5 on coupon, p. 46



BEST OF ALL CONTACT SPRAYS

As reported by independent product-testing laboratory

Triple-action Contact Shield cleans, lubricates, and protects electrical controls and switches in seconds. Most effective, safest product of its kind as proved by laboratory tests.

CHANNEL MASTER works wonders in sight and sound

Ellenville, New York


For more data, circle 2-52-2 on coupon, p. 46

RCA TEST INSTRUMENT

WR-64A color-bar/dot/crosshatch generator combines the functions of two test units in one compact, easy-to-use instrument. It provides color-bar signals for checking, adjusting, and troubleshooting color-TV circuits, and dot- and crosshatch-pattern signals for adjusting convergence in color receivers. It may also be used for adjusting linearity and overscan in both color and black-and-white receivers. Has only three control knobs and only one output cable which connects to the antenna-input terminals of the receiver. RCA Electron Tube Div., Harrison, N. J.

BUSS FUSES

PLUS
CLIPS-
BLOCKS-
& HOLDERS

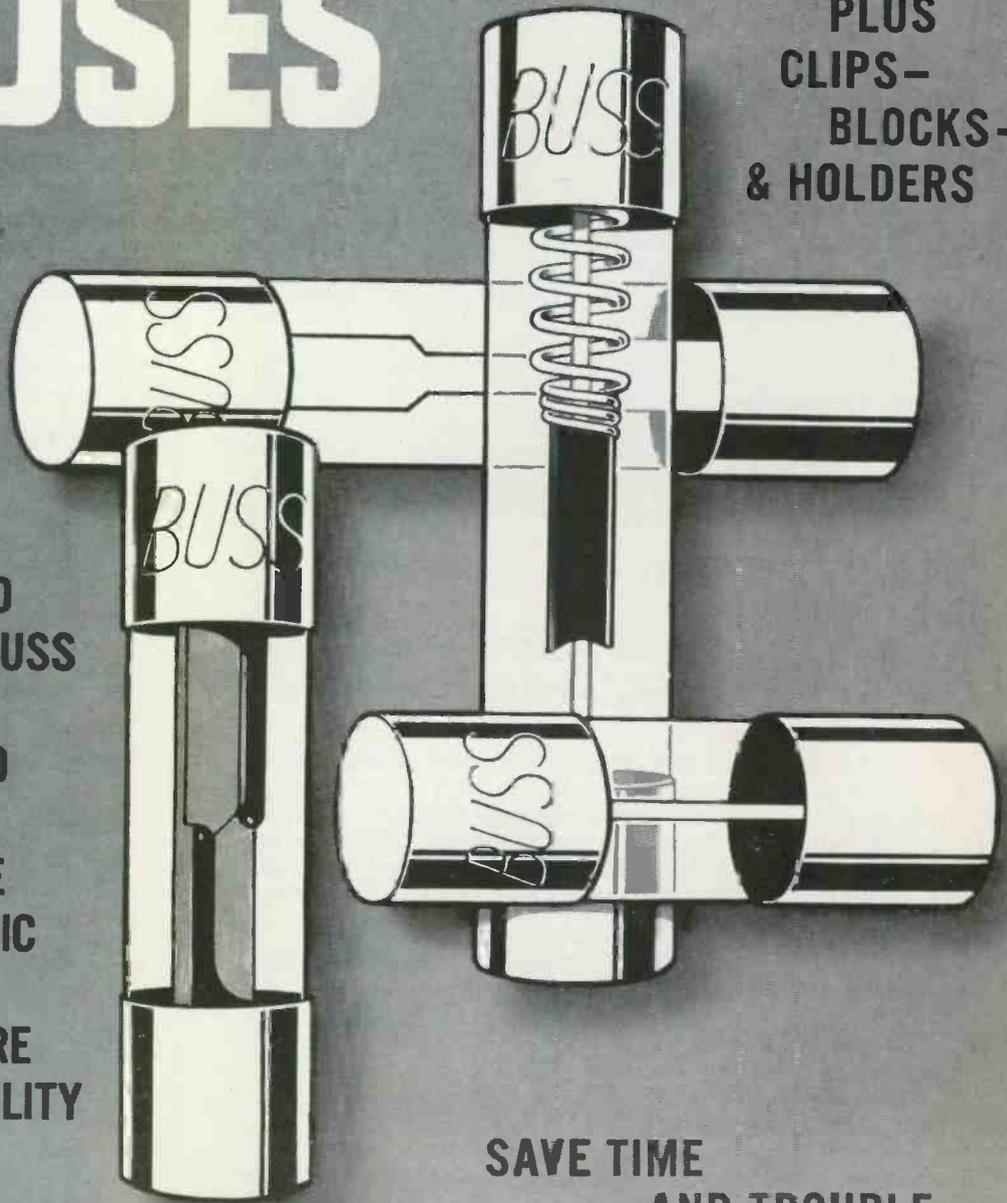

EACH AND
EVERY BUSS
FUSE IS
TESTED
IN A
SENSITIVE
ELECTRONIC
DEVICE
TO ASSURE
DEPENDABILITY


SAVE TIME
AND TROUBLE...

by standardizing on BUSS fuses. There's a right fuse for every need in the complete line. Write for the BUSS bulletin on small dimension fuses (Form SFB) to get full data for your files.

Bussmann Mfg. Division McGraw-Edison Co.
University at Jefferson, St. Louis 7, Mo.

For more data, circle 2-53-1 on coupon, p. 46


Listen!

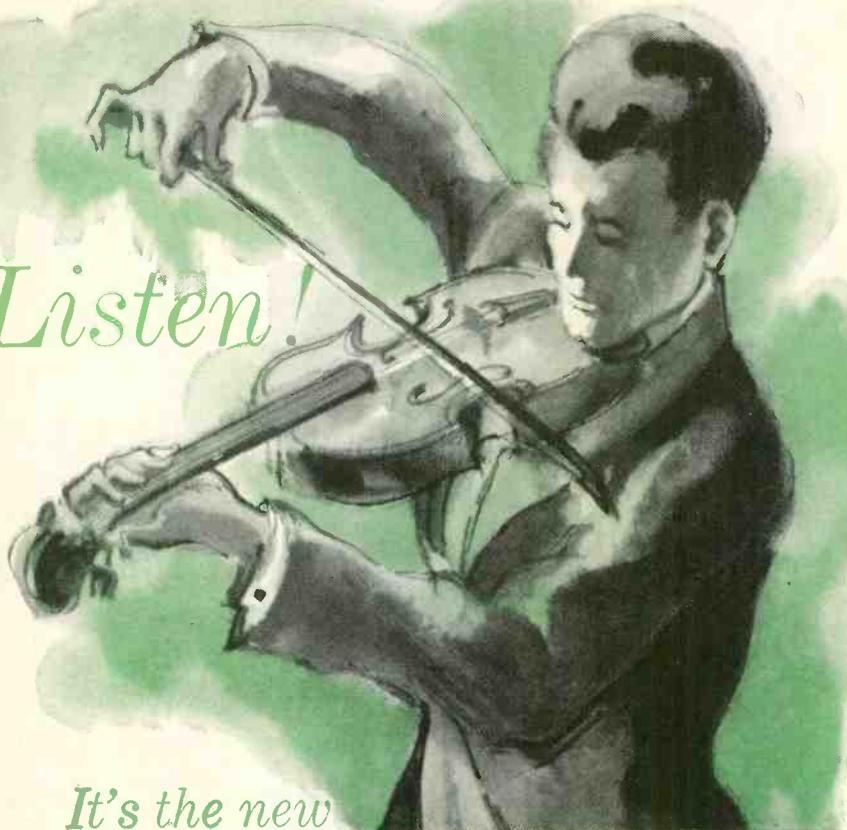

It's the new
Sonotone Ceramic "Velocitone"

No stereo cartridge—not even the finest magnetic in the world—outperforms it!

- Listen!.. with any magnetic you sell today—at any price. Then replace it *directly* in any component system with Sonotone's new "VELOCITONE" STEREO CERAMIC CARTRIDGE ASSEMBLY. Listen again! We challenge you to tell the difference. Experts have tried...in dozens of A-B listening tests. And, in every single one, Sonotone's "VELOCITONE" performed as well as or better than the world's best magnetic.
- Listen!.. perfectly flat response in the extreme highs and lows (better than many of the largest-selling magnetics).
- Listen!.. excellent channel separation—sharp, crisp definition.
- Listen!.. highest compliance—considerably superior tracking ability.
- Listen!.. absolutely no magnetic hum—quick, easy, *direct* attachment to any magnetic inputs.
- Listen!.. remarkable performance characteristics unexcelled anywhere. (Write Sonotone Corporation for specifications.) Now listen to the price. Only \$23.50...about one-half the price of a good stereo magnetic cartridge. Stock and sell Sonotone's "VELOCITONE"... the stereo ceramic cartridge system that cannot be outperformed by any magnetic—regardless of price.

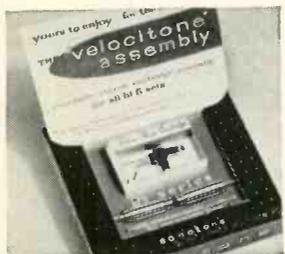


Sonotone®
CORP.

ELECTRONIC APPLICATIONS DIVISION, ELMSFORD, N. Y., Dept. C9-21
IN CANADA, CONTACT ATLAS RADIO CORP., LTD., TORONTO
LEADING MAKERS OF CARTRIDGES • SPEAKERS • TAPE HEADS • MIKES • ELECTRONIC TUBES • BATTERIES

For more data, circle 2-54-1 on coupon, p. 46

Xcelite TOOL HOLSTER

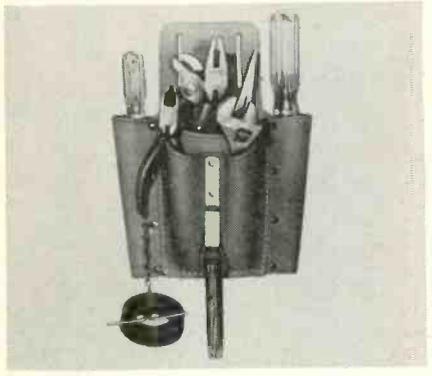Announced is a new saddle leather hip holster featuring an electrical tape holder, knife clip, and 5 tool pockets. It is designed to carry a variety of wrenches, screwdrivers, pli-



ers, and other tools used by the electronic technician. Has a comfortable, hip-contoured back, hot-waxed stitching, brass riveting, and pliable belt slots. Xcelite, Inc., Thorne Ave. & Bank St., Orchard Park, N. Y.
For more data, circle 2-54-2 on coupon, p. 46

Utah AUTO RADIO SPEAKER

Model SP410E replacement auto radio speaker may be used in the following 1961 automobiles: Buick, Cadillac, Chevrolet (except Corvair), Studebaker (except Lark), Pontiac, and Oldsmobile. 4" x 10". Features a 2.15 oz. Alnico V magnet. Delivers 8 watt power handling. Utah Radio & Electronic Corp., Huntington, Ind.
For more data, circle 2-54-3 on coupon, p. 46

PACO POWER SUPPLY KIT

Model B-12 features fully-variable and regulated d-c plate voltages from 0-400v, at 150 ma maximum. Also provides bias voltages from 0-150v at 2 ma and three 3-ampere a-c filament outputs: 2 at 6.3v, plus an exclusive 12v filament output. It has high stabil-



ity, with an output variation of less than 1/3 of 1% (or .3v, whichever is greater), from zero load to full load. Less than 0.4% or 0.5v output variation for ±10v line voltage variation from 117v a-c input. Kit, \$69.95. Wired \$99.95. Paco Electronics Co., 70-31 84th St., Glendale 27, L. I., N. Y.
For more data, circle 2-54-4 on coupon, p. 46




there are drivers



and there are drivers!

Which is by way of saying: If you want your full share of the public address business in your territory, *don't use a boy for a man's job!* University's complete line of man-sized loudspeaker drivers is designed to meet every application requirement of both voice and music. Features like these tell you why University drivers are the standard of the industry: ▶ One-piece linen base phenolic diaphragms for exceptionally uniform over-all frequency response ▶ Rim-centered palate assembly for shock- and vibration-proof mechanism ▶ Individually precision-wound tropicalized voice coils ▶ Conservatively rated continuous-duty power handling capacity at maximum conversion efficiencies mean lower dollar-per-watt costs for the user ▶ Completely weatherproof construction and acrylic finishes for lifetime protection ▶ Models with built-in transformers provide highest degree of versatility of application and flexibility of operation ▶ Important conveniences of field-replaceable diaphragm assemblies, phase-coded terminals, standard threads for interchanging trumpets. ▶ *With drivers like these you're off to a good start.* Now team them up with trumpets from University's all-inclusive line — wide-angle, directional, radial — *and you're ahead all the way.* For complete details on University public address speakers and accessories, write Desk Z-2, University Loudspeakers, Inc., White Plains, N. Y.

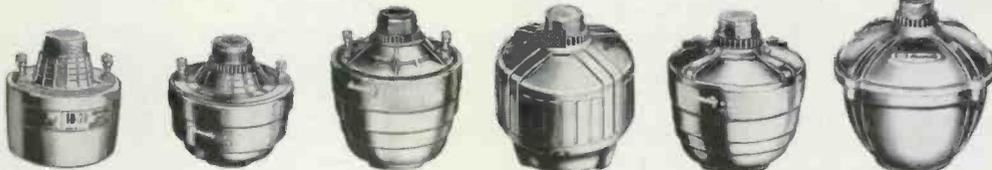CHOOSE FROM THESE SIX DELUXE ID MODELS—FROM 20 TO 60 WATTS



ID-20, 20 watts ID-30, 30 watts ID-40, 40 watts ID-40T, 40 watts ID-60, 60 watts ID-60T, 60 watts

OR FROM THE WORLD FAMOUS STANDARD LINE OF UNIVERSITY DRIVERS

For more data, circle 2-55-1 on coupon, p. 46



ATR

PRODUCTS FOR MODERN LIVING



ATR UNIVERSAL INVERTERS

A. C. Household Electricity Anywhere . . . in your own car!

- Tape Recorders • TV Sets
- Dictating Machines • Radios
- Public Address Systems

• Electric Shavers • Record Players • Food Mixers • and Emergency Lighting. . . . NET

6U-RHG (6 V.) 125 to 150 W. Shp. Wt. 27 lbs. \$66.34

12U-RHG (12 V.) 150 to 175 W. Shp. Wt. 27 lbs. \$66.34

Auto Plug-in Home-type Portable



ATR BATTERY CHARGERS

NO INSTALLATION . . . PLUG INTO CIGARETTE LIGHTER RECEPTACLE!

Keeps car battery fully charged in your own garage! Needed more now than ever before—makes motor starting easy! Operates directly from standard 110 volts A.C. current.

612CA4 (4 amp.) 6/12 V. Shp. Wt. 6 lbs. NET \$19.46

612CA6 (6 amp.) 6/12 V. Shp. Wt. 8 lbs. NET \$22.46

612CA10 (10 amp.) 6/12 V. Shp. Wt. 10 lbs. NET \$27.71



ATR SHAV-PAKS

Keep Clean-Shaved! Plugs into Cigarette Lighter Receptacle. Keep in Glove Compartment. Operates Standard A.C.

- ELECTRIC SHAVERS
- Small Timing Devices . . . In CARS, Buses, Trucks, Boats, or Planes.

6-SPB (6 V.) 15 W. Shp. Wt. 2½ lbs. NET \$7.97

12-SPB (12 V.) 15 W. Shp. Wt. 2½ lbs. NET \$7.97

ATR ELECTRONIC TUBE PROTECTORS


Will Double or triple the life of all types of electronic tubes, including TV picture tube.

Automatic in operation, for use with any electronic equipment having input wattage of 100 to 300 watts. Fuse protected, enclosed in metal case for rugged construction and long life.



MODEL 250 (Wall Model) 115 V. A. C. Shp. Wt. 1 lb.

DEALER NET \$2.63

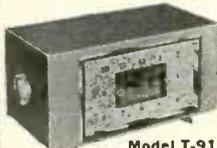

Model T-91

ATR MODERN TABLE RADIOS

Trim, modern clock radio in ebony or ivory plastic. Powerful 5 tubes including rectifier AM radio chassis with built-in "Magna-Plate" antenna. Full-toned 4" PM speaker. Popular features include: Musical Alarm—radio turns on automatically at any pre-set time; Sleep Selector—lulls user to sleep; Automatic Appliance Timer—outlet on back of radio times any electric appliance automatically (up to 1100 watts). Cabinet 10½ in. wide, 5 in. high, 5¼ in. deep. Wt. approx. 8 lbs.

Clock Specifications:

- Genuine Telechron Movement.
- Self-Starting . . . Never Needs Winding, Oiling, or Regulating.
- Simplified Clock Controls for Radio and Sleep Switch.
- 1100 Watt Controlled Outlet.
- Automatic Buzzer Alarm.
- Gold-Plated Bezel and Numerals on Large Bone-White Dial. UL Approved.

ATR HAND WIRED—NO PRINTED CIRCUITRY "TILT-A-STAND" RADIO

MOUNT ON THE WALL—UNDER A SHELF—OR SET ON A TABLE. PERFECT for every room in YOUR home.

Power-packed 5 tubes including rectifier chassis. Built-in loop antenna. Automatic volume control. Full 4" Alnico 5 speaker. Distinctive Roman numerals on dial. Size: 9½" W x 4" D x 5¾" H. AC/DC. U.L. approved. Beautiful bakelite cabinet—Resists heat. Shipping Weight 5½ lbs.



Model T-87

Model T-91 Clock Radio, Black NET \$22.45

Model T-91 Clock Radio, Ivory NET 23.15

Model T-87 (Tilt-A-Stand), Black NET 17.47

Model T-87 (Tilt-A-Stand), Red NET 18.10

SEE YOUR ELECTRONIC PARTS DISTRIBUTOR WRITE FACTORY FOR FREE LITERATURE . . .

ATR AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA—U. S. A.

For more data, circle 2-56-1 on coupon, p. 46

Shell STEREO AMP/PREAMP

The Manhasset model 2020P consists of 2 identical 20-watt amplifiers equipped with fully equalized preamplifiers. Power output, 20-watts/channel; peak, 80 watts. IM distortion, 60 cps—6 kc (4 to 1) less than 2% at rated output. Harmonic distortion, 30



cps to 10 kc less than 1%. Frequency response, ±1 db 30—20,000 cps at rated output; ±1 db 30—50 kc at 2 watts. Other features include binaural output jack and exclusive dynamic input balance controls. \$129.95. Shell Electronics Mfg. Corp., 112 State St., Westbury, N. Y.

For more data, circle 2-56-3 on coupon, p. 46

Photography

(Continued from page 37)

ultrasonically, better "wetting" action is obtained, and developing time is reduced. But, Jacques warns that he is still experimenting and no firm conclusions have been made as to the practicability of ultrasonic developing.

Jacques leans heavily on Bob Cooper, of Bob's TV of Paramus, N. J. for keeping his electronic gear in good shape. Bob is also kept busy installing new electronic gadgets whenever Jacques finds a new one that will help him in his work.

Jacques became exposed to electronic apparatus when he was an executive of Peerless Camera Stores in New York. After being injured in an automobile accident, which kept him from working for a year, he decided to go into business for himself. To make his business profitable, he relies heavily on electronics to gain top efficiency. •

SO SAFE!



won't damage glass tubing
let alone wire or cable!

ARROW STAPLE GUNS can't damage wire or cable because driving blade automatically stops staple at right height! That's why Arrow Staple Guns are proved safer on jobs all over the country. And Arrow staples have tremendous holding power because they're rosin-coated, have diverging points that lock into wood.

T-25 (shown) for wires up to ¼" in diameter. (Hi-Fi wire, radiant heating, bell, thermostat, telephone, inter-com, etc.) tapered striking edge gets into tight corners. Uses ¾", ⅝", and ⅜" staples. List \$15
T-25B For burglar alarm wiring. Drives staples flush . . . List \$15
T-75 For non-metallic sheathed cable, Romex cable or any other object (such as copper tubing) up to ½" in diameter. Uses ⅝", ⅜", and ⅜" Arrow staples List \$15

ARROW FASTENER COMPANY, INC.
1 Junius St., Brooklyn 12, N. Y.

For more data, circle 2-56-2 on coupon, p. 46

Scott AMPLIFIER KIT

LK-72, dual channel, 35 watts/channel, amplifier is packed in a "Kit-Pak" container that opens to a worktable. Wires, pre-cut and pre-strapped. Mechanical parts, pre-riveted to the chassis. Other parts, mounted on "Part-Charts." Instruction book, full-




color, easy-to-follow. IHFM power band, extends down to 20 cps. Total harmonic distortion, 1 kc, is less than 0.4% at full power. Amplifier hum level, better than 70 db below full power output. \$149.95, east of the Rockies; slightly higher West coast. H. H. Scott, Inc., 111 Powdermill Rd., Maynard, Mass.

For more data, circle 2-57-3 on coupon, p. 46

Sherwood AMPLIFIER/PREAMP

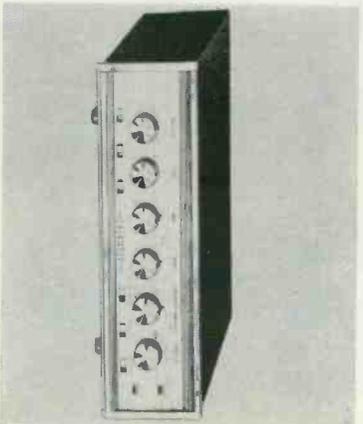Model S-5000 II, 80 watt music power stereo amplifier/preamplifier provides either stereophonic or monophonic hi-fi system operation with only one set of basic controls. Features: 10 two-channel controls; stereo normal/reverse switch; phase inversion switch; dual amplifier mono-




phonic operation with either set of input sources; presence-rise switch, phono channel hum and noise 60 db below rated output and phono sensitivity of 1.8 mv. Also included, at no extra cost, is a third channel output, \$199.50. Sherwood Electronic Labs., 4300 N. California Ave., Chicago 18, Ill.

For more data, circle 2-57-4 on coupon, p. 46

ELECTRONIC TECHNICIAN • February, 1961

ATLAS "Job Rated" P. A. SPEAKERS

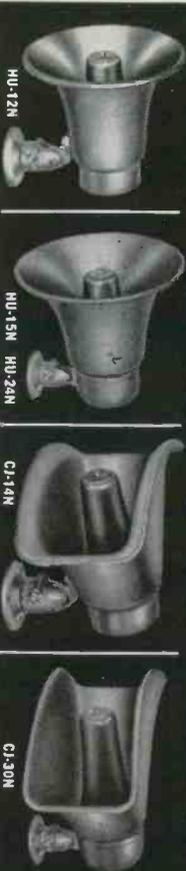

There is an Atlas Speaker Ideally Suited for Every Job

All Atlas P. A. speakers are highly efficient especially in the voice frequency range, providing the extra "punch" needed to override high level background noise. Most are 100% weatherproof; aluminum and diecast parts are treated with corrosion inhibitors, then finished in "stone hard" baked enamel. The CJ Cobra-Jector horns are constructed of nonresonant, indestructible fiberglass, and HU and TP speaker horns of aluminum, finished in gun-metal grey. The HU and TP speakers are particularly designed for efficient talkback operations. The peaked characteristics within the voice frequencies increase the sensitivity of these speakers as pickup devices.

All HU and CJ speakers are equipped with versatile "Versalock" . . . This rugged, reliable mounting bracket, completely adjustable both horizontally and vertically, provides positive locking in any position.

The DU-12 and DC-5, Atlas' renowned DeCor projectors, are styled to harmonize with any decor, modern or traditional. Send for free catalog to Dept. ET-2

Model	HU-12N	HU-15N	HU-24N	CI-14N	CI-30N	CI-44	TP-15N	TP-24N	DU-12	DC-5
POWER*	7.5 w	25 w	25 w	7.5 w	25 w	25 w	25 w	25 w	7.5 w	6 w
IMPEDANCE**	8 ohm	8 ohm	8 ohm	8 ohm	16 ohms	8 ohm	8 ohm	8 ohm	8 ohm	120-
FREQUENCY	350-	250-	200-	400-	150-	250-	200-	400-	120-	700-
C.P.S.	10,000	10,000	10,000	10,000	9000	10,000	10,000	10,000	10,000	7000
LENGTH OVERALL	7 1/4 in.	8 3/4 in.	12 in.	8 in.	1 1/4 in.	23" x 13"	16 1/2 in.	23 in.	14 in.	14 in.
BELL DIAMETER	7 1/2 in.	9 3/4 in.	11 1/4 in.	9 1/2" x 5 1/2"	14" x 6"	19 in.	9 3/4 in.	11 1/4 in.	7 in.	7 in.
NET PRICE	\$16.20	\$20.10	\$22.35	\$18.00	\$24.50	\$43.50	\$31.20	\$34.50	\$19.50	\$13.20

*Input range limited to frequencies above horn cutoff **All models available in 45 ohms at slightly higher prices



ATLAS SOUND CORP.
1449 39th Street
Brooklyn 18, N. Y.
In Canada:
Atlas Radio Corp., Ltd.,
Toronto, Ontario

For more data, circle 2-57-1 on coupon, p. 46

Superior's New Model 85—a DYNAMIC Type TRANS-CONDUCTANCE TUBE TESTER



● THE "FREE-POINT" LEVER TYPE ELEMENT SWITCH ASSEMBLY marked according to RETMA marking, permits application of test voltages to any of the elements of a tube.

● NEW IMPROVED TYPE METER with sealed air-tightening chamber provides accurate, vibration-less readings.

● FREE FIVE (5) YEAR CHART DATA SERVICE. The chart provided with Model 85 includes easy-to-read, up-to-date subsequence charts which will be mailed to all Model 85 purchasers at no charge for a period of five years after date of purchase.

Revised up-to-date subsequence charts will be mailed to all Model 85 purchasers at no charge for a period of five years after date of purchase.

**SHIPPED ON APPROVAL
NO MONEY WITH ORDER — NO C.O.D.**

Try it for 10 days before you buy. If completely satisfied send \$12.50 and pay balance at rate of \$8.00 per month for 5 months.

— No Interest or Finance Charges Added. If not completely satisfied, return to us, no explanation necessary.

● EMPLOYERS latest improved TRANS-CONDUCTANCE circuit. Tests tubes under "dynamic" (simulated) operating conditions. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured as a function of tube quality. The meter in which the tube is tested is a method of simulating the manner in which tubes are used in radio receivers, TV receivers, amplifiers and other circuits. Amplifiers, TV receivers, amplifiers and other circuits.

● SYMBOL REFERENCES: For the first time ever in tube-conductance tube tester Model 85 employs difficult-to-remember letters previously used. Repeated time studies proved to us that use of these scientifically selected symbols speeded up the element switching step. As the tube manufacturer's increase the release of new tube types, this time-saving feature becomes more necessary and advantageous.

● SPRING RETURN SAFETY SWITCH guards Model 85 against burn-out if tube under test is "shorted."

● AN ULTRA-SENSITIVE CIRCUIT is used to detect all tube elements.


Model 85 comes complete, housed in a handsome portable cabinet with slip-on cover. Only

\$52.50

MOSS ELECTRONIC, INC.
Dept. D-967, 3849 Tenth Ave., New York 34, N. Y.
Please rush one Model 85. I agree to pay \$12.50 within 10 days after receipt and \$8.00 per month thereafter. Otherwise I may return, cancelling all further obligation.

NAME _____
ADDRESS _____
CITY _____ STATE _____
ZONE _____
All prices net, F.O.B. N.Y.C.

CUSTOMER SERVICE ENGINEERS

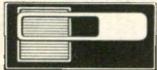

OUTSTANDING CAREER OPPORTUNITIES

Continued expansion of the PHILCO COMPUTER DIVISION has created a number of positions for persons with a minimum of 2 years of data processing equipment maintenance and/or installation experience.

Successful candidates will undergo advanced computer training in the PHILCO 2000 System at our Willow Grove, Pa. plant.

ASSIGNMENTS AVAILABLE IN MAJOR CITIES THROUGHOUT U.S.A.

Contact
Mr. John Felos
Professional Employment Manager

**COMPUTER DIVISION
WILLOW GROVE, PA.**

PHILCO
 Famous for Quality the World Over[®]

For more data, circle 2-58-1 on coupon, p. 46
58

Stereo Multiplexing

(Continued from page 40)


low frequencies. The conduction are averaged out by the pi-network integrator circuit connected between the plate of V3B and the grid of V4A. This removes the subcarrier frequencies, leaving only the audio voltage variations to be applied to the phase inverter stage. Here the A - B signal is amplified, the actual signal input to the stage being determined by the setting of the dimension (sometimes called "difference" or "stereo") control.

V4A, the inverter stage, is a split-load amplifier with equal plate and cathode resistances giving both polarities of output, with equal amplitudes. The A - B signal is applied to the grid, producing A - B at the cathode and B - A at the plate. The two signals are applied to the mixing circuits along with the A + B signal from amplifier stage V4B.

The A + B signal is demodulated in the FM tuner and applied to the converter as audio, so needs no further demodulation.

A double-pole switch is included here because, at the present time, the type of stereo multiplex has not been selected by the FCC which may be compatible or non-compatible. In a non-compatible system one stereo signal is transmitted directly on the main carrier; the other on a subcarrier which modulates the main carrier, with no combining of signals. With the switch of the converter being described in the ORD (ordinary) position the demodulated main carrier is connected from V4B to one of the outputs. The demodulated subcarrier can be obtained from the grid circuit of V4A and applied to the other output jack. For use on the Crosby multiplex system, the switch is set to the COM (compatible) position.

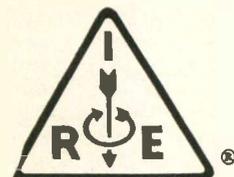There are two controls on the converter, as shown in Fig. 3: the volume control and the dimension control. The dimension control sets the amplitude of A - B signal which is applied as input to the V4A stage.



For that

NEW IDEA

visit the

IRE SHOW

March 20-23, 1961

New York

Coliseum and Waldorf-Astoria Hotel

Members \$1.00, Non-members \$3.00

Age limit—over 18

For more data, circle 2-58-2 on coupon, p. 46

ELECTRONIC TECHNICIAN • February, 1961

In doing this it also sets the amplitudes of the A - B and B - A signals applied to the mixing circuits.

The volume control sets the amplitude of A + B signal which is applied to V4B and to the mixing networks.

In order to achieve proper balance these two controls should be set properly in relation to the rest of the system. First, turn the dimension control all the way down, then raise the volume to the desired level. Both speakers will then be producing sound but it will be a monaural output. The volume controls of the audio amplifiers should then be adjusted so that the sound seems to be coming from a point midway between the two speakers. After this the dimension control should be advanced to provide proper stereo effect.

Installation

Some FM tuners manufactured during the last few years are equipped with multiplex outputs, brought out to terminals at the rear of the chassis. In the overall tuner

circuit this connection normally connects to an audio signal point, just ahead of the deemphasis network. When this connection is available it can be connected to the multiplex input of a converter. Normal audio output should be connected to the other input terminals of a converter.

If a multiplex output connection is not already provided on the tuner it can be installed. The correct connections for both ratio detector and discriminator circuits are shown in Fig. 4. In each case, connection is made at the input of the deemphasis network to keep its response from unduly attenuating the modulated subcarrier. For the ratio detector no circuit changes are required, as shown in Fig. 4A. Simply make a connection at the point shown, connecting a small capacitor (about 0.002 μ f) in series with the lead.

In all probability no circuit changes will be required with a discriminator circuit. However, as shown in Fig. 4B, the capacitor marked C, shunts the output and could attenuate a portion of the subcarrier signal, especially if the ca-

pacitor is large. Sometimes it may be necessary to either remove this capacitor completely, or replace it with a smaller value. For each of these circuit arrangements, the leads carrying the subcarrier signal can be connected to a phono jack or screw-type terminal permanently installed at the back of the tuner.

As stereo multiplex gains in popularity more manufacturers will enter the field. This will offer radio and TV technicians additional sales, installation and servicing opportunities. •

TRU-VAC 1-YEAR GUARANTEED RADIO and TV TUBES

35
EACH
\$33
Per 100 TUBES

Factory Used or Factory Second Tubes! TRU-VAC will replace FREE any tube that becomes defective in use within 1 year from date of purchase!
ALL TUBES INDIVIDUALLY BOXED, CODE DATED & BRANDED "TRU-VAC"

Partial Listing Only... Thousands More Tubes in Stock!

SPECIAL!

6SN7GT.....30¢	6W4GT.....30¢
0Z4	5T6
1A7GT	5U4
1B1GT	5U8
1H5GT	5V4G
1R5	5V6GT
1S5	5X8
1T4	5Y3
1U4	6AB4
1U5	6AF4
1V2	6AH4GT
1X2	6AH6
2AF4	6AK5
2BN4	6AL5
2C Y5	6AR5
3AL5	6AN8
3BC5	6AQ5
3BN6	6A Q6
3BZ6	6A Q7
3CB6	6AR5
3B4	6AS5
3V4	6AT6
4B Q7A	6AU4GT
4B58	6AUSGT
4BZ7	6AU8
4CB6	6AV5GT
5AN8	6AV6
5AT8	6AW6
5AV8	6AX5GT
5AZ4	6B5
5CG8	6B6
5R4	6B6E
	6B6G
	6B6H
	6B6J
	6B6K
	6B6L
	6B6M
	6B6N
	6B6O
	6B6P
	6B6Q
	6B6R
	6B6S
	6B6T
	6B6U
	6B6V
	6B6W
	6B6X
	6B6Y
	6B6Z
	6B7
	6B7A
	6B7B
	6B7C
	6B7D
	6B7E
	6B7F
	6B7G
	6B7H
	6B7I
	6B7J
	6B7K
	6B7L
	6B7M
	6B7N
	6B7O
	6B7P
	6B7Q
	6B7R
	6B7S
	6B7T
	6B7U
	6B7V
	6B7W
	6B7X
	6B7Y
	6B7Z
	6B8
	6B8A
	6B8B
	6B8C
	6B8D
	6B8E
	6B8F
	6B8G
	6B8H
	6B8I
	6B8J
	6B8K
	6B8L
	6B8M
	6B8N
	6B8O
	6B8P
	6B8Q
	6B8R
	6B8S
	6B8T
	6B8U
	6B8V
	6B8W
	6B8X
	6B8Y
	6B8Z
	6B9
	6B9A
	6B9B
	6B9C
	6B9D
	6B9E
	6B9F
	6B9G
	6B9H
	6B9I
	6B9J
	6B9K
	6B9L
	6B9M
	6B9N
	6B9O
	6B9P
	6B9Q
	6B9R
	6B9S
	6B9T
	6B9U
	6B9V
	6B9W
	6B9X
	6B9Y
	6B9Z
	6C
	6C1
	6C2
	6C3
	6C100

SPECIAL! TO READERS OF TECHNICIAN ONLY! 1c SALE ON TRU-VAC

1 YR. QUAR. TUBES IN BELOW LIST ONLY * 2 TUBES FOR PRICE OF 1 PLUS 1c * 35c EACH 33c EACH PER 100 TUBES Buy all you want for 35c each get extra tubes for 1c each. Buy 100 tubes for \$35; get 100 extra tubes for \$1!

Pick Any Types Mix If You Wish
6AC7 6SA7
6AG5 7A7
6AU6 7CL
6AX4GT 7MT
6BA6 12AU7
6CG7 12BF6
6K6GT 12CN5

1c Sale

Tru-Vac pays your postage - on orders of \$5 or more in U.S.A. & territories. Send approximate postage on Canadian and foreign orders. Orders less than \$5 require 25¢ handling charge. Send 25% on C.O.D.'s.

TRU-VAC

Harrison Avenue • Box 107 • Harrison, N. J. Humboldt 4-9770

NEW FROM H. H. SCOTT


Leader in Audio Design and Engineering

6 SUPERB STEREO COMPONENTS PLUS A RADICALLY DIFFERENT FM TUNER KIT

3 NEW WIDE-BAND TUNERS! The new 310D Broadcast Monitor Tuner at \$184.95*, the 314 FM Tuner at \$114.95, and the 330D AM-FM Stereo tuner at \$209.95. All have H. H. Scott's unique silver-plated front end, all are multiplex adaptable.

3 NEW AMPLIFIERS! H. H. Scott now has an amplifier in every important price range. The new 222B (30 Watts) is only \$114.95*, the 299B (50 Watts) is \$209.95, and the 272 (88 Watts) is \$269.95.

NEW WIDE-BAND FM TUNER KIT! A laboratory tuner kit that meets high H. H. Scott standards! The pre-aligned silver-plated front end is the same used in all H. H. Scott tuners. All wires are cut, stripped and tinned... all parts mounted on special Kit-Pack® cover to facilitate assembly. TUNER IS ALIGNED BY USING THE METER ON THE KIT ITSELF! Using this procedure, tuner will work as well as factory aligned units. Only \$89.95*

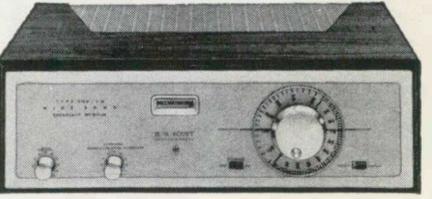

310D Broadcast Monitor FM Wide-Band Tuner

H. H. SCOTT
H. H. Scott Inc., Dept. 140-02
111 Powdermill Rd., Maynard, Mass.

Rush me complete information on your new line. Be sure to include complete details on your new Wide-Band FM Tuner Kit.

Name _____
Address _____
City _____ State _____
Export:
Telesco International, 36 W. 40th St., NYC
*All prices slightly higher west of Rockies. Subject to change without notice. Accessory cases extra.

For more data, circle 2-59-2 on coupon, p. 46



MAD?

...because you had to call back?

Why waste time with cold solder joints...risk your reputation?

Be sure, use ERSIN Multicore 5-core solder—makes a fast-holding perfect solder joint every time!

World's Finest
ERSIN Multicore
FIVE-CORE SOLDER



Sold only by Radio Parts Distributors.
MULTICORE SALES DIVISION BRITISH INDUSTRIES CORP., Port Washington, N. Y.

For more data, circle 2-60-1 on coupon, p. 46

the business-like approach

to SERVICE CHARGES and RECORD KEEPING

For customer's prices on every replacement part, plus flat rate and hourly service charge data, regional and national. Dave Rice's OFFICIAL PRICING DIGEST, listing over 63,000 items. \$2.50.



AVAILABLE FROM YOUR DISTRIBUTOR

If you want to operate on a professional level, Dave Rice's OFFICIAL ORDER BOOKS give you triplicate forms for order, invoice, and office records...spaces for tubes, parts, serial numbers, labor and tax charges, signatures, etc. 75c per book, \$6.50 for dust-proof box of 10.



Dave Rice's
OFFICIAL ORDER BOOK

ELECTRONIC PUBLISHING COMPANY, INC.
180 N. WACKER DRIVE • CHICAGO 6, ILL.

For more data, circle 2-60-2 on coupon, p. 46

Misconceptions

(Continued from page 34)

Almost any trouble in the sweep circuit will affect the boost voltage, but just how will it affect it? No one really knows. Therefore, boost measurement will not help you localize a single defective part! We once read a story, though, that said low boost indicated trouble in the yoke . . . I've often wondered how! Now, of course, boost voltage can be used to indicate sweep energy, or the return of sweep energy


after you make the repair; but then, so will an arc drawn by a screwdriver!

5. A "milky" picture when the brightness is turned up is always caused by defective CRT.


Though it's true that the picture tube is the most common offender in this respect, just ask an embarrassed technician that installed a new tube and still had the same trouble. He'll testify that the picture tube is not the only cause of a milky picture.

In many RCA models, as well as others using the high level con-

Fig. 3—Misconception: A shorted yoke will cause a trapezoid pattern. Fact: This is true in some series-wired yoke circuits (A). In parallel wired circuits (B), a short results in reduced parallel sides.

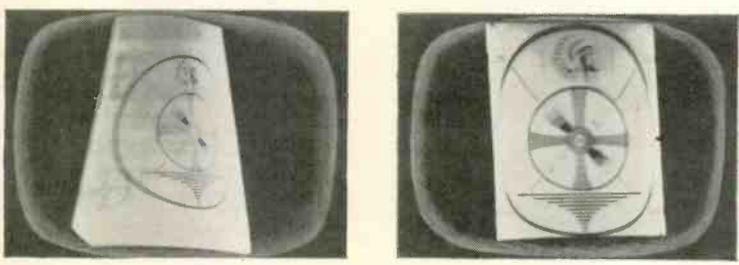


(A)

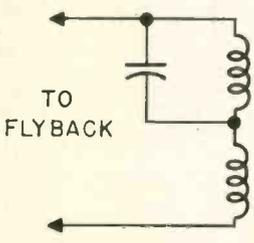

TO FLYBACK

SERIES CONNECTED DEFLECTION YOKE

(B)

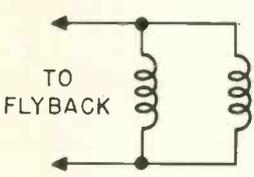

TO FLYBACK

PARALLEL CONNECTED YOKE. NO BALANCING CAPACITOR IS NEEDED WITH THIS CONNECTION. (G.E. U4 Series)

TAP-A-LINE

THE HANDIEST THING SINCE ELECTRICITY

FROM 6 INCHES TO 10 FEET LONG



Tap-A-Line — mounted on or behind work benches, in the lab, on test tables, in lamp or appliance stores — provides multiple taps from a single power source. Safe — concealed conductors — tight positive contacts — easy to install in any position. Sold by Electrical, Electronic and Hardware Jobbers and Dealers

Tap-A-Line Mfg. Co.

P. O. Box 563
Pompano Beach, Fla.



For more data, circle 2-60-3 on coupon, p. 46

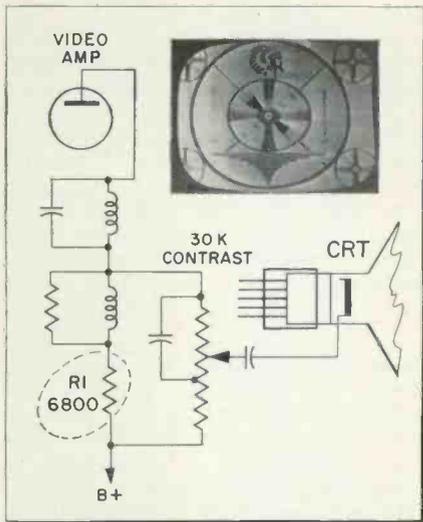


Fig. 4—Misconception: A "milky" picture when the brightness control is turned up is always caused by a defective CRT. Fact: Many TV chassis using the illustrated circuit have been known to cause a milky CRT if the plate load resistor opens.

trast control circuit, shown in Fig. 4, an open video plate load resistor R1 will produce a symptom resembling a defective picture tube. Note that with resistor R1 open, plate voltage is still supplied to the video amplifier tube through the much higher resistance of the contrast control. This keeps the video amplifier working, but the frequency response is very poor.

Though presenting only five common misconceptions that might throw you for a loop, there are no doubt many more. But these will serve to emphasize why service technicians should analyze circuits before jumping to an incorrect conclusion. •

Illustration Credit: John F. Rider Publisher, Inc., New York, N. Y.

Amperex DIODE

Announced is subminiature type 1N3182 voltage variable capacitor silicon diode, for automatic frequency control applications in TV and FM tuners. Specifically designed and manufactured exclusively for automatic frequency control applications. Features a high Q (typical 60) and maintains a precise oscillator frequency. All-glass construction. Maximum series resistance, 3 ohms. Average capacitance, 30 μ f. Inverse voltage, 4v. Amperex Electronic Corp., Semiconductor & Special Purpose Tube Div., 230 Duffy Ave., Hicksville, L. I., N. Y.

Atlas ROTOR WIRE

A new heavy duty rotor wire, Atlas 4-C, is the latest addition to a group of rugged fringe area type wires. The new cable is reported to be heavily insulated and to contain 18 gauge copper in each conductor. Additional stranding, added for flexibility, brings the total in all four conductors to 164 strands. Jersey Specialty Co., Burgess Place, Mountain View, N. J.


For more data, circle 2-61-4 on coupon, p. 46

Raytheon TUBES


Announced are five new entertainment tubes. Audio receiving tubes: 7-pin 7543, replacement for 6AU6 and providing a low-hum, non-microphonic operation; and the 9-pin 14GT8, a duplex diode, a high- μ triode, designed for use as an FM detector and AF voltage amplifier. Video tubes: 9-pin 6GN8, a miniature triode pentode with the triode section designed for use as a voltage amplifier or synchronizing separator and the pentode section designed for video amplifier service; 8-pin 10EG7 octal-based, double-triode with dissimilar sections, one designed as an oscillator and the other as an amplifier in the TV receiver's vertical deflection circuit; and 7-pin 2ER5 miniature, remote-cutoff, frame-grid tetrode for VHF TV tuners. Raytheon Co., Westwood, Mass.

For more data, circle 2-61-6 on coupon, p. 46

Picture-Tube Repair Tool

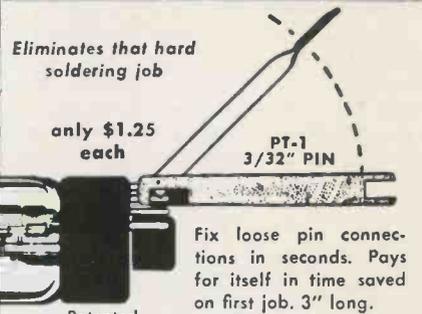

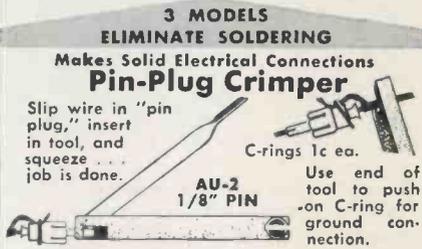Eliminates that hard soldering job
only \$1.25 each
PT-1 3/32" PIN
Fix loose pin connections in seconds. Pays for itself in time saved on first job. 3" long.



3 MODELS ELIMINATE SOLDERING
Makes Solid Electrical Connections
Pin-Plug Crimper
Slip wire in "pin plug," insert in tool, and squeeze... job is done.
C-rings 1c ea.
Use end of tool to push on C-ring for ground connection.

Ant. plugs, hi-fi, multiple plugs, public address, radio and TV tubes, radar, speakers, and loop connections. Many, many more uses.
Madel LC-3 for 5/32" pin diameter
At your parts distributor or write us Dept. 25

BERNS Mfg. Co. 9853 Chalmers, Dept. 25 Detroit 13, Mich.

For more data, circle 2-61-1 on coupon, p. 46

BUY WHAT YOU NEED!



NEW Walsco KOIL-PIK

EXACT REPLACEMENT TRANSFORMERS
SAVE TIME IN SELECTION

NEW WALSCO KOIL-PIK TRANSFORMERS save you time and money because they're so easy to select—44 exact replacements that are clearly identified and protectively packaged.

- EXACT REPLACEMENTS FOR
- IF & RF Coils & Transformers
 - TV Sound Discriminators
 - Miniature IF Transformers
 - Portable Radio & Auto Capacitors
 - Printed Circuit Capacitors

SEND FOR FREE CATALOG!

Walsco ELECTRONICS
WALSCO ELECTRONICS MFG. CO.
Division of Textron Electronics, Inc.
West Plant: Los Angeles 18, California
Main Plant: Rockford, Illinois, U.S.A.

For more data, circle 2-61-2 on coupon, p. 46

LOWEST PRICED ELECTRONIC ASSORTMENTS IN AMERICA!
RADIO-TV PARTS BY THE POUND IN NEW... **JUMBO PAKS!**

SPECIAL TRUCK-LOADS of manufacturers' over-runs at a fraction of their original cost!	ONE POUND PRECISION RESISTORS WORTH \$100	ONE POUND DISC CONDENSERS WORTH \$50	ONE POUND CERAMIC CONDENSERS WORTH \$85	\$3 ⁰⁰ per pound
	ONE POUND DISCS & CERAMICS WORTH \$75	ONE POUND Discs, Ceramics PRECISIONS WORTH \$70	BUY 4 GET THE 5 TH PAK FREE!	


HOW TO ORDER: Include check or M.O. with sufficient postage; excess returned. C.O.D. orders, 25% down; rated, net 30 days. INCLUDE POSTAL ZONE in address.

LEKTRON 242 Everett Ave. CHELSEA 50, MASS.

For more data, circle 2-61-3 on coupon, p. 46
ELECTRONIC TECHNICIAN • February, 1961

James VIBRATOR

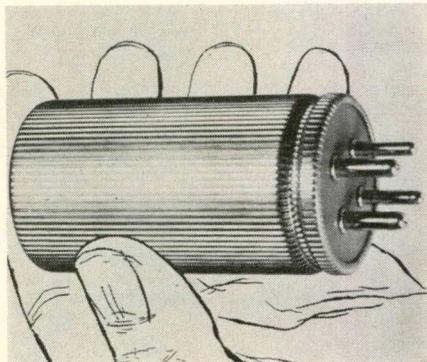Announced are 3 models in a line of vibrators, designed specifically for citizens band radio equipment. Features include double lead wires having twice normal current capacity and oversize contacts giving 71% more contact area. Model CB-40, 6v, 4




prong, receive current 5 amps. max., transmit current 10 amps. max. \$4.95. CB-41, 12v, 4 prong, receive current 3 amps. max., transmit current 6 amps. max. \$5.15. CB-42, 12v, 3 prong, receive current 3 amps. max., transmit current 6 amps. max. \$5.15. James Electronics, Inc., 4050 N. Rockwell St., Chicago 18, Ill.

For more data, circle 2-62-3 on coupon, p. 46

MAIL COUPON TODAY!

Find out how you can get this book

free!

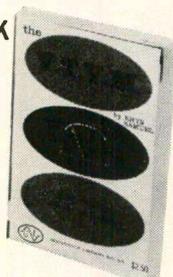

the V.T.V.M. by Rhys Samuel published at \$2.50—contains a wealth of information on how the V.T.V.M. works . . . how to use it. Send for particulars on how to get this valuable book.

Mail to Dept. ET-2
General Techniques, Inc.
Manufacturers of Quality Electronic Kits
1270 Broadway, New York City 1, N. Y.

NAME _____

ADDRESS _____

CITY _____ ZONE _____

STATE _____

New Books

REPAIRING TRANSISTOR RADIOS. By Sol Libes. Published by John F. Rider Publisher, Inc. 168 pages, soft cover. \$3.50.

Transistor theory, how it operates in radio circuits and servicing procedures are thoroughly discussed in this fine book. Each stage of a radio is covered, with a service chart that indicates "Trouble," "Possible Cause," and "What To Look For" following each discussion. AM, FM, and Auto radios receive excellent coverage. A chapter each is devoted to "Troubleshooting Techniques," and "Tools & Test Equipment." Also, an appendix offers a transistor interchangeability chart. Admirably written and illustrated, the guide should further a technician's knowledge of transistor radio repair techniques.

TELEVISION TUBE LOCATION GUIDE, Vol. 10. Published by Howard W. Sams & Co., Inc. 98 pages, soft cover. \$1.25.

This handy guide for caddy or bench is the tenth volume in a series of TV chassis tube layout diagrams. 74 tube location charts with keyed tube pins are accompanied by a listing of failure symptoms and the tubes that could cause these failures. Series-string filament circuits, fuseohm resistor values, and control locations for individual TV receivers are also helpful aids for the service technician. Previous volumes, 8, 9, and 10 are indexed.

TELEVISION ANALYZING SIMPLIFIED. By Milton S. Kiver. Published by B&K Manufacturing Co., Chicago, Ill. 134 pages, soft cover. \$1.00.

This second edition (revised) of a manual published in 1958 employs the publisher's commercially-available analyst to troubleshoot TV receivers. In substance, the text is an applications manual for their instrument. However, the practical TV circuit

analysis and signal injection techniques presented here can serve well as a general guide for the use of all signal injection instruments. The author's shirt-sleeve method of troubleshooting each section of a receiver should certainly help owners of an analyst reduce their service time. Additionally, non-owners of analyst-type equipment can, for only one dollar, expose themselves to the use of this type equipment.

SOUND MERCHANDISING TECHNIQUES. By Walton N. Hershfield. Published by Sound Publishing Co., 299 Madison Ave., New York City. 66 pages, soft cover. \$3.00.

Originally published as a series of articles in a periodical, this collection of sound equipment material has been expanded to include sales and advertising methods. Public address, intercom, and interphone equipment is presented, with a view towards merchandising, which includes a non-technical discussion of equipment. Detailed applications are also presented, such as installations in: schools, airports, churches, offices and other prime selling areas. Recommended reading as a good selling guide in an expanding field.

SERVICING TRANSISTOR TV RECEIVERS. By Milton S. Kiver and Charles R. Gray. Published by Howard W. Sams & Co. 272 pages, soft cover. \$4.50.

Following on the heels of recently introduced transistorized television receivers, this book offers a detailed description of transistors, basic circuits, and how they are applied in modern transistorized TV sets. A chapter is devoted to transistor circuit operation of each section of a TV chassis: tuners, video amps, detectors, etc. A final chapter discusses service techniques, though practical repair methods are limited. Numerous circuit diagrams accompany the text. Recommended to readers wishing a better understanding of a transistor's role in TV.

PHONE
ED 9-9653

\$7.50

plus parts,
C.O.D. and postage charges

Precision Tuner Service

ALL TYPES T.V. TUNERS REPAIRED AND ALIGNED TO FACTORY SPECIFICATIONS ON CRYSTAL-CONTROLLED SWEEP GENERATORS
24-HOUR SERVICE ON MOST TUNERS
UHF - VHF COMBINATIONS — \$13.50

See your local distributor or send to:

P.O. Box 272, 601 N. College
BLOOMINGTON, INDIANA

State make and model. Send
all parts, tubes and shields.

For more data, circle 2-62-1 on coupon, p. 46

For more data, circle 2-62-2 on coupon, p. 46

INDEX TO ADVERTISERS

February 1961

American Telephone and Telegraph Co.	56
Agency: Cunningham and Walsh, Inc.	
Arco Electronics, Inc.	11
Agency: Sternfield-Godley, Inc.	
Arrow Fastener Co., Inc.	56
Agency: Thematic Advertising Productions, Inc.	
Atlas Sound Corp.	57
Agency: Zam and Kirshner, Inc.	
B & K Manufacturing Co.	45, 47, 49, 51
Agency: Henry H. Teplitz Advertising	
Belden Manufacturing Co.	17
Agency: Fensholt Advertising Agency	
Berns Manufacturing Co.	61
Blonder-Tongue Laboratories, Inc.	12
Agency: Gilbert & Felix, Inc.	
British Industries	60
Agency: Irving Greene Advertising	
Bussmann Manufacturing Co.	53
Agency: Henderson Advertising Co.	
Castle Television Tuner Service	52
Agency: R. N. Johnson Advertising	
CBS Electronics	21
Agency: Donahue and Coe, Inc.	
Centralab Division, Globe-Union Inc.	20
Agency: Stral Advertising Co.	
Channel Master Corp.	19, 52
Agency: Duso Advertising, Inc.	
Clarostat Manufacturing Co.	Cover III
Agency: Lescarboursa Advertising, Inc.	
Communications Co., Inc.	50
Agency: Baxter & Crim, Inc.	
Delco Radio Division	64
Agency: Campbell-Ewald Co.	
EICO	6
Agency: Zam & Kirshner, Inc.	
Electronic Publishing Co., Inc.	60
Agency: Stral Advertising Co.	
Electro Products Laboratories	16
Agency: Robertson, Buckley & Gotsch, Inc.	
General Electric Co.	3, 4, 5
Agency: Gardner Advertising Co., Inc.	
General Techniques, Inc.	62
Agency: Irving Greene Advertising	
Greyhound Corp.	7
Agency: Grey Advertising, Inc.	
Institute of Radio Engineers	58
Agency: Raymond Schoonover Advertising	
Jackson Electrical Instrument Co.	2
Agency: Parker Advertising Co.	
JFD Electronics Corp.	25
Agency: Delphi Advertising Inc.	

Lektron	61
Agency: Marketronics Advertising	
Mallory & Co., Inc., P. R.	22, 23
Agency: Aitkin-Kynett Co.	
Mosley Electronics, Inc.	16
Agency: The Biddle Co.	
Moss Electronic, Inc.	57
Agency: Bass & Co.	
Motorola Training Institute	24
Agency: Kolb & Abraham Inc.	
Multicore Sales Corp.	60
Agency: Irving Greene Advertising	
Philco Computer Division	58
Agency: Maxwell Associates, Inc.	
Philco Corp., Accessory Div.	8, 9
Agency: Maxwell Associates, Inc.	
Precision Tuner Service	62
Quam Nichols Co.	35
Agency: Stral Advertising Co.	
Radio Corporation of America Cover IV	
Agency: Al Paul Lefton Co.	
Rider Publisher, Inc., John F.	63
Agency: Gilbert & Felix, Inc.	
Sarkes Tarzian, Inc.—Tuner Div.	18
Agency: H. L. Ross Advertising	
Scott, Inc., H. H.	59
Agency: Arnold & Co., Inc.	
Sonotone Corp.	54
Agency: Deherty, Clifford, Steers & Shenfield, Inc.	
Sprague Products Co.	26
Agency: Harry P. Bridge Co.	
Sylvania Div., General Telephone & Electronics	Cover II
Agency: Kudner Agency, Inc.	
Tap-A-Line Manufacturing Co.	60
Agency: August Burghard, Inc.	
Technibilt Corp.	50
Agency: Glenn Advertising, Inc.	
Triad Transformer Corp.	48
Agency: Compton Advertising, Inc.	
Tru-Vac	59
Agency: Greenwald Advertising	
Tung-Sol Electric Inc.	13
Agency: E. M. Freystadt Associates, Inc.	
TV Parts House	63
University Loudspeakers, Inc.	55
Agency: John Jason, Inc.	
Walsco Electronics Mfg. Co.	61
Agency: Paul J. Steffen Co.	
Weller Electric Co.	10
Agency: Arndt, Preston, Chapin, Lamb & Keen, Inc.	

While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.

Mr. Service Technician:
Want to service transistor radios rapidly
—accurately? You can with

REPAIRING TRANSISTOR RADIOS

by S. Libes (Director Technical
Publications, Bogen-Presto)

The man who wrote this book knows his subject well and provides practical procedures that you can apply to faster troubleshooting and to finding those elusive 'dog troubles'.

Basic theory is presented in a way that you will understand easily, quickly. Operation and service of the latest transistorized circuit designs are covered. All new ideas about transistors as used in current transistor radios are explained. Also included are the latest design practices in transistor portable AM, multi-band, imported, all-transistor, auto-hybrid and FM radio receivers. High power transistorized public address power amplifiers and current high fidelity applications are covered.

Servicing is explained on a step-by-step basis including trouble check points and charts, instruction of handy-to-use test equipment (e.g. signal source, power supply). And, there's another feature—*transistor and diode substitution charts*. Also included is information on how to select test equipment and tools for repairing transistor radios. #270, \$3.50

TV SERVICING

- MASTER RECEIVING — PICTURE TUBE SUBSTITUTION GUIDEBOOK, H. A. Middleton, \$7.45
- RECEIVING TUBE SUBSTITUTION GUIDEBOOK 4th suppl., H. A. Middleton, \$1.35
- TUBE CADDY-TUBE SUBSTITUTION GUIDEBOOK, H. A. Middleton, 90c
- HOW TO TROUBLESHOOT TV SYNC CIRCUITS, I. Remer, \$2.90
- REPAIRING TELEVISION RECEIVERS, C. Glickstein, \$4.40

AUDIO & HIGH-FIDELITY SERVICING

- HOW TO INSTALL & SERVICE INTERCOMMUNICATION SYSTEMS, J. Darr, \$3.60
- HOW TO SERVICE TAPE RECORDERS, C. A. Tut-hill, \$2.90
- REPAIRING HI-FI SYSTEMS, David Fidelman, \$3.90

TEST EQUIPMENT

- HOW TO USE METERS (2nd ed.), J. F. Rider & S. Prensky, \$3.50
- HOW TO USE TEST PROBES, A. Ghirardi & R. Middleton, \$2.90
- OBTAINING INTERPRETING TEST SCOPE TRACES, J. F. Rider, \$3.00
- HOW TO USE SIGNAL & SWEEP GENERATORS, J. Richard Johnson, \$2.40
- HOW TO USE GRID-DIP OSCILLATORS, R. P. Turner P. E., K&AI, \$2.50

RADIO SERVICING

- RADIO RECEIVER LABORATORY MANUAL, A. W. Levey, M. S., \$2.00
- RADIO TROUBLESHOOTING GUIDEBOOK, VOL. 1, Rider & Johnson, \$2.40
- HOW TO INSTALL & SERVICE AUTO RADIOS (2nd ed.), J. Darr, \$3.25
- REPAIRING PORTABLE & CLOCK RADIOS, B. Crissee & D. Gnessin, \$2.75

PROFITABLE SERVICING AREAS

- HOME AIR CONDITIONING, Installation & Repair, J. Derman, M.S., F. Makstein, H. Seaman, \$3.50
- BASICS OF FRACTIONAL HORSEPOWER MOTORS & REPAIR, Gerald Schweitzer, soft cover \$3.90; cloth \$4.90
- INDUSTRIAL CONTROL CIRCUITS, Sidney Platt, \$3.90

Prices subject to revision.
At distributors or order direct!
Write for new catalog. ET-2

JOHN F. RIDER, PUBLISHER, INC.
116 West 14th Street, New York 11, N.Y.
Canada: Chas. W. Pointon, Ltd.,
66 Racine Rd., Rexdale, Ont.

TV PARTS HOUSE

SUPPLIER TO TV
SERVICEMEN ONLY

PO BOX 1971
BILLINGS, MONT.

IF YOU NEED IT—
WE CAN DELIVER!

LET'S GET ACQUAINTED!

HERE'S A SPECIAL "DOOR BUSTER" BUY IN THAT
HARD TO FIND 100 MFD—10 VOLT
TRANSISTOR FILTER • 9 for \$5.00
(NO C.O.D.—WE PAY POSTAGE ANYWHERE)



For more data, circle 2-63-1 on coupon, p. 46

For more data, circle 2-63-2 on coupon, p. 46



LEARN

SUBJECTS OFFERED AT NO COST TO YOU:

- ① TRANSISTOR FUNDAMENTALS—complete coverage of transistor theory without the use of mathematics.
- ② GUIDE-MATIC POWER HEADLIGHT CONTROL (Autronic Eye)—lecture and lab.
- ③ TWILIGHT SENTINEL ELECTRIC HEADLIGHT SWITCH—lecture and lab.
- ④ TROUBLE-SHOOTING PROCEDURES for dead or weak low voltage auto radio tuners and trigger circuits.
- ⑤ LECTURE AND LAB. PRACTICE ON "SIGNAL SEEKER" AND "WONDER BAR" auto radio tuners and trigger circuits.
- ⑥ TRANSISTOR CIRCUIT TROUBLE-SHOOTING—lecture and lab. work analyzing defects in transistor circuits.
- ⑦ HYBRID-TYPE AUTOMOBILE RADIOS—low voltage tube and output transistor circuits. Lecture and lab.
- ⑧ DELCO-MATIC ALL-TRANSISTOR GARAGE DOOR OPERATORS—lecture and lab.
- ⑨ AUTO PORTABLE RADIOS—lectures and lab. practice on all-transistor portable radios. Get prepared for the all-transistor auto radio that will appear in the next few years.

THE LATEST ON TRANSISTORS AND AUTOMOTIVE ELECTRONICS 9 SUBJECTS AVAILABLE TO YOU AT THE FREE DELCO RADIO - GUIDE LAMP ADVANCED TRAINING SCHOOL. One week of instruction. No lab. fees. No tuition charge. Textbooks supplied.

In 1960 over 900 electronics technicians completed our one-week course. You, too, can receive this same valuable training in 1961. Bring yourself up to date on transistors and automotive electronics with personalized instruction at the General Motors Training Center near you. (See schedule below.)

Classes will be conducted by graduate engineers with special training in your field. Diplomas, awarded only to those who successfully complete the courses, will mean a great deal to you—and to your customers.

Register now through your local Delco Electronics Parts Distributor or write directly to Delco Radio Division, General Motors Corporation, Kokomo, Indiana, Attention: Service Manager.

GUIDE LAMP DIVISION

GENERAL MOTORS CORP.
ANDERSON, INDIANA



DELCO ELECTRONICS TRAINING SCHOOL SCHEDULE						
DATE	REGION 1	REGION 2	REGION 3	REGION 4	REGION 5	REGION 6
1-16	Philadelphia		Detroit			
1-23		Charlotte	Detroit		Dallas	
2-6	Washington			St. Louis		
2-13	Washington	Atlanta			Houston	
2-20			Cincinnati		Houston	Los Angeles
2-27						Los Angeles
3-6	Tarrytown	Memphis		Omaha		
3-13	Tarrytown					
3-20		Jacksonville	Cleveland			San Francisco
4-10	Boston		Cincinnati	Kansas City	El Paso	Portland
4-17	Boston	Atlanta		Kansas City	El Paso	
5-1		New Orleans	Pittsburgh	Minneapolis		Los Angeles
5-8	Union		Pittsburgh		Oklahoma City	
5-15				Milwaukee		
5-22		Memphis	Buffalo			San Francisco
6-5	Philadelphia			Chicago	Denver	
6-12		Charlotte		Chicago		Portland
6-19			Cleveland			
6-26	Union	Atlanta		Minneapolis	Dallas	Salt Lake City


For more data, circle 2-64-1 on coupon, p. 46

ELECTRONIC TECHNICIAN 614

CIRCUIT DIGEST

MOTOROLA
TV Chassis
TS-STS & WTS-435

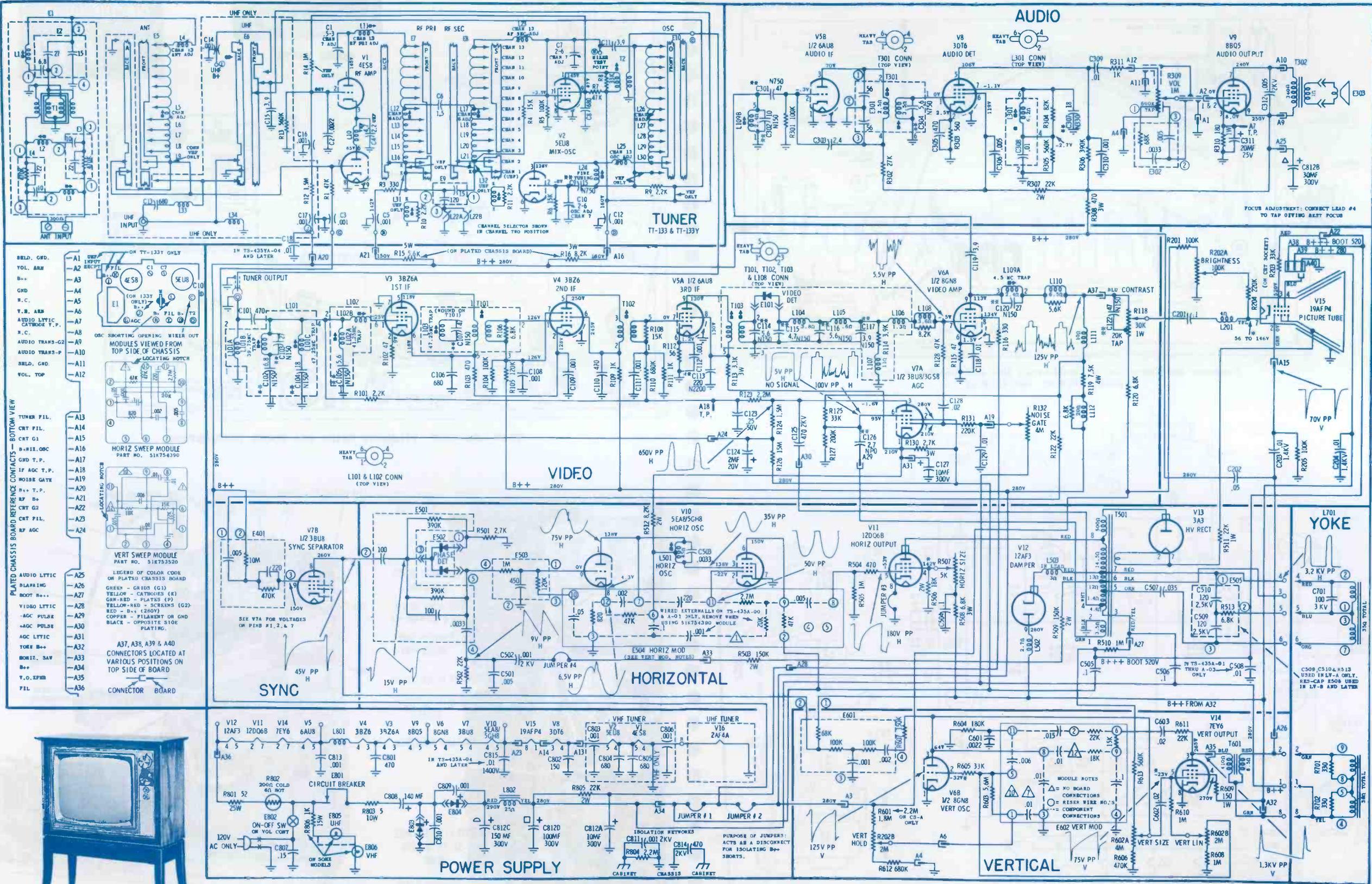Special Full-Width SPRING BINDER Holds 24 Groups of ELECTRONIC TECHNICIAN'S CIRCUIT DIGESTS Available @ \$2.95



THIS SCHEMATIC COVERS PLATED CHASSIS BOARD TS-435A-00 THRU TS-435A-04 LOW VOLTAGE CHASSIS LV-A, LV-A-1 & LV-B, HI VOLTAGE CHASSIS HV-A, CONTROL STRIP CS-A & CS-B, TUNERS TT-133 & TT-133Y. IF THE RECEIVER YOU ARE WORKING ON SHOULD HAVE A PLATED CHASSIS BOARD, OR RELATED SECTION, WHICH IS STAMPED WITH A CODE LETTER OR NUMBER LATER THAN THAT SHOWN ON THIS SCHEMATIC, THE DIAGRAM WILL STILL BE APPLICABLE SINCE THE CHANGES WILL BE SLIGHT.

More Data on Reverse Side




MODEL A19T2


MOTOROLA
TV Chassis
TS-S7S & WTS-43S

Electronic Technician
CIRCUIT DIGEST


614

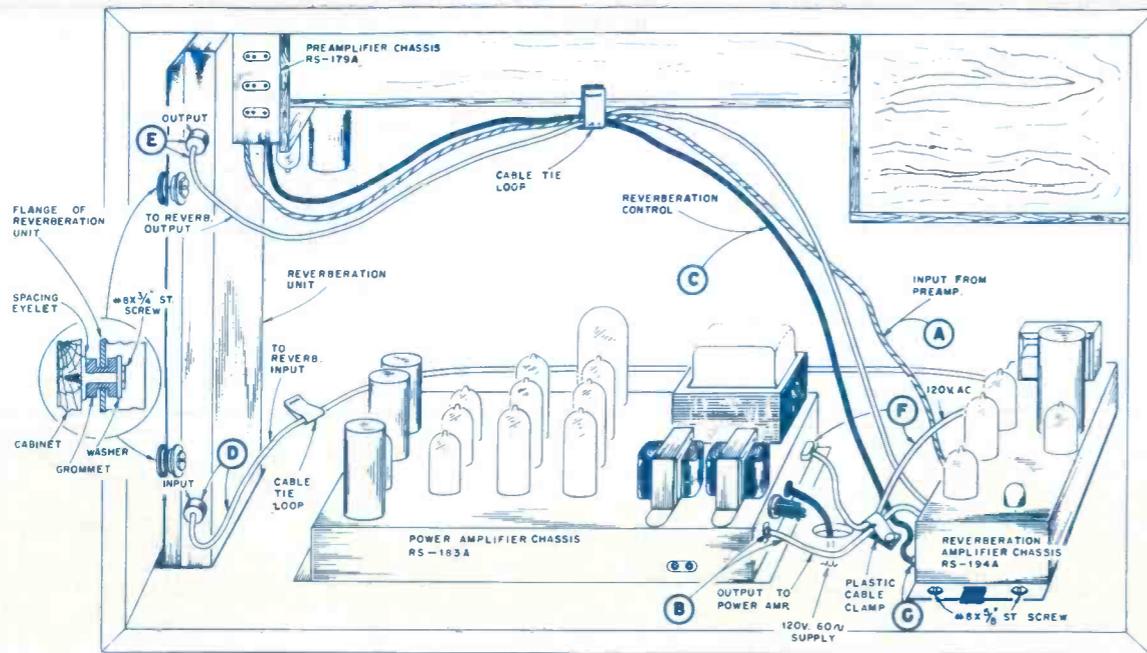

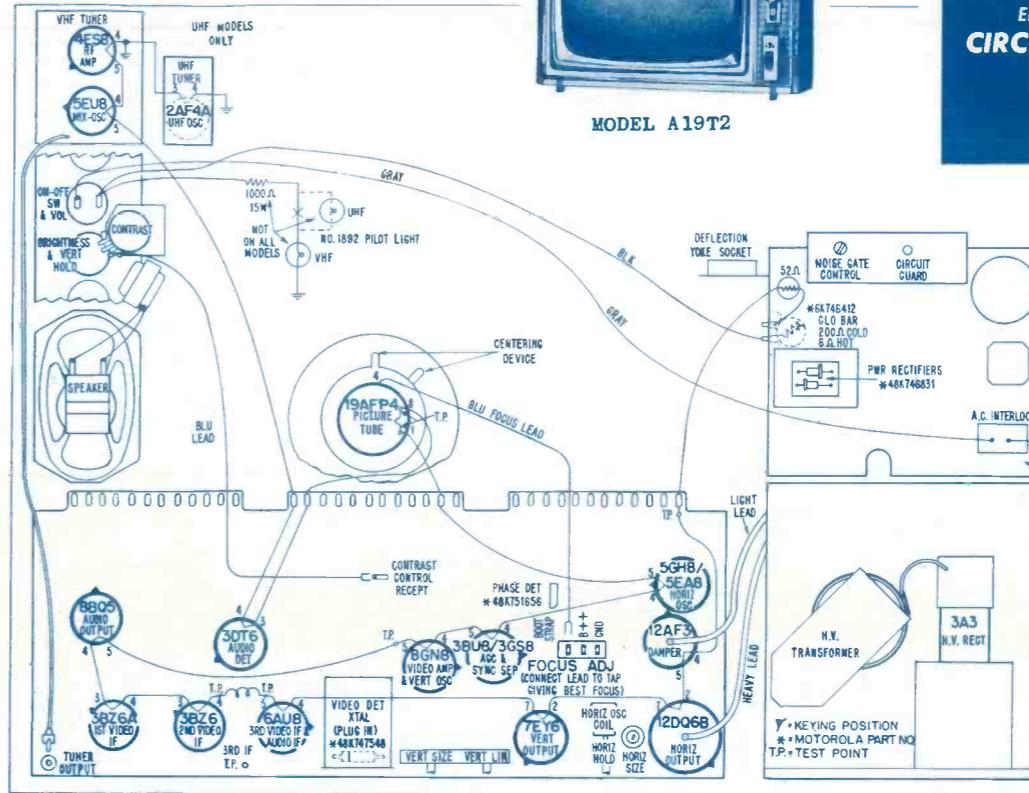
Placement and Connection of Reverberation Unit and Amplifier in Models RVCR-45, RVCR-46, and RVCR-84



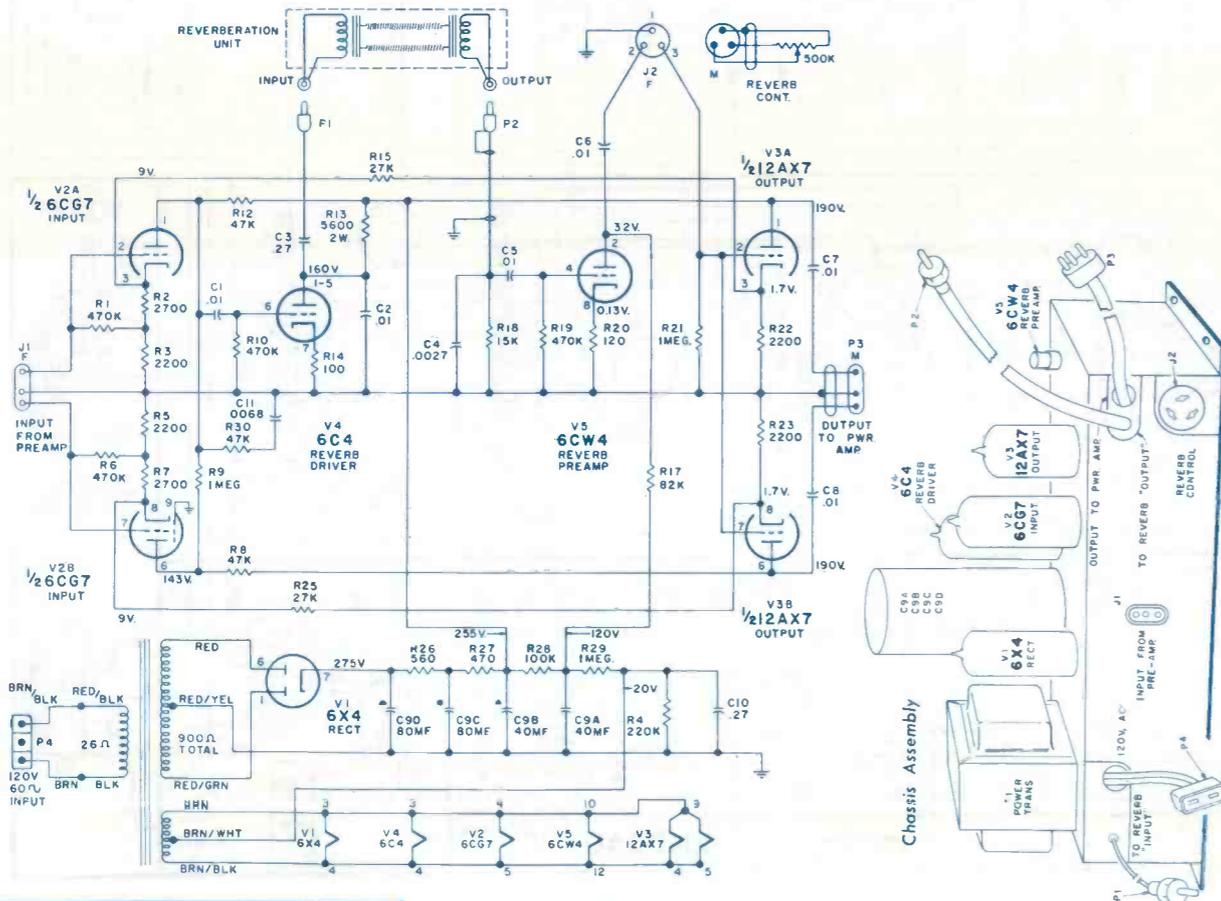TUBE LOCATION, FILAMENT GUIDE AND FOCUS INFORMATION




Reverberation Amplifier Chassis RS-194A

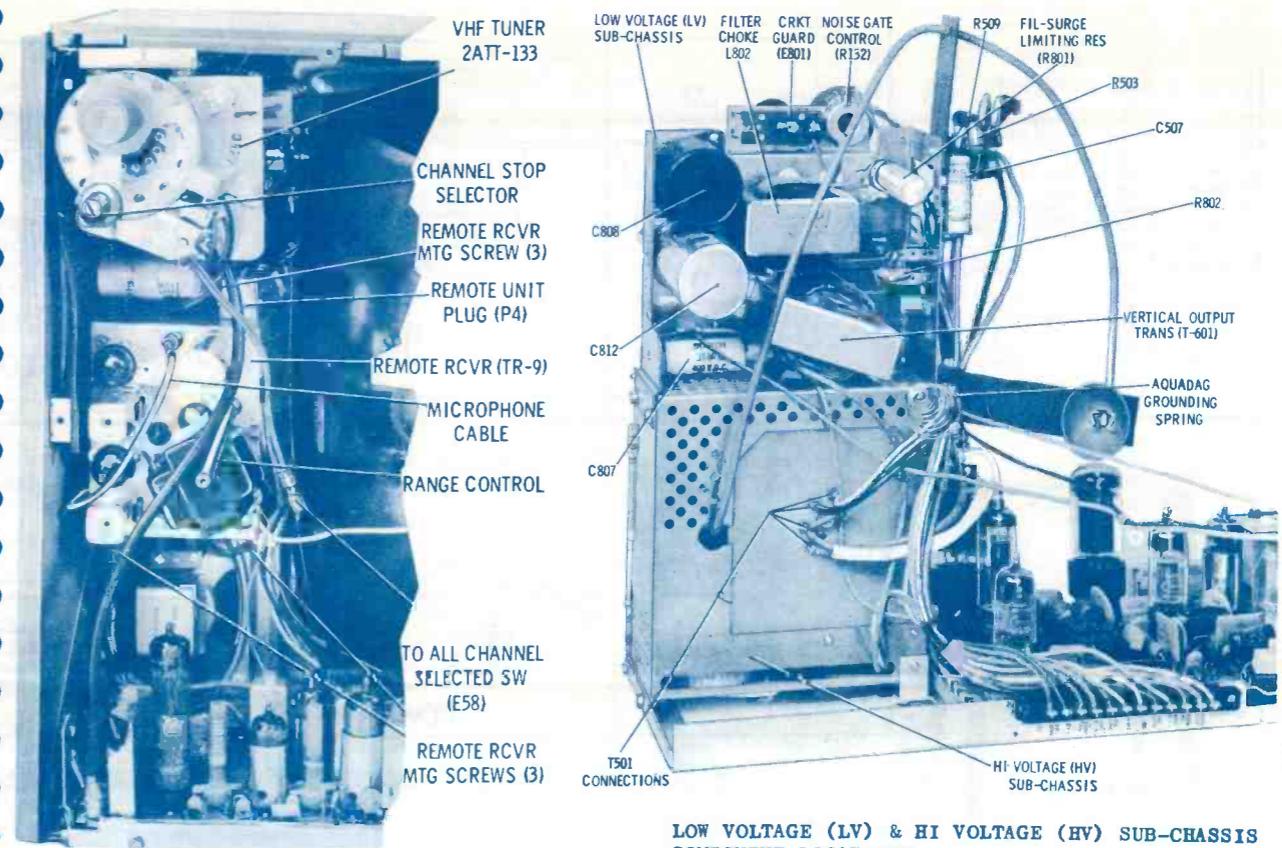


REAR VIEW OF AUTOMATIC MODELS

LOW VOLTAGE (LV) & HI VOLTAGE (HV) SUB-CHASSIS COMPONENT LOCATIONS

February • 1961

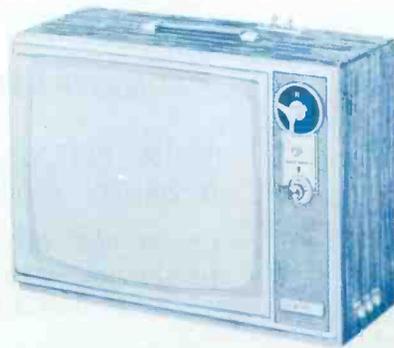

More Data on Reverse Side

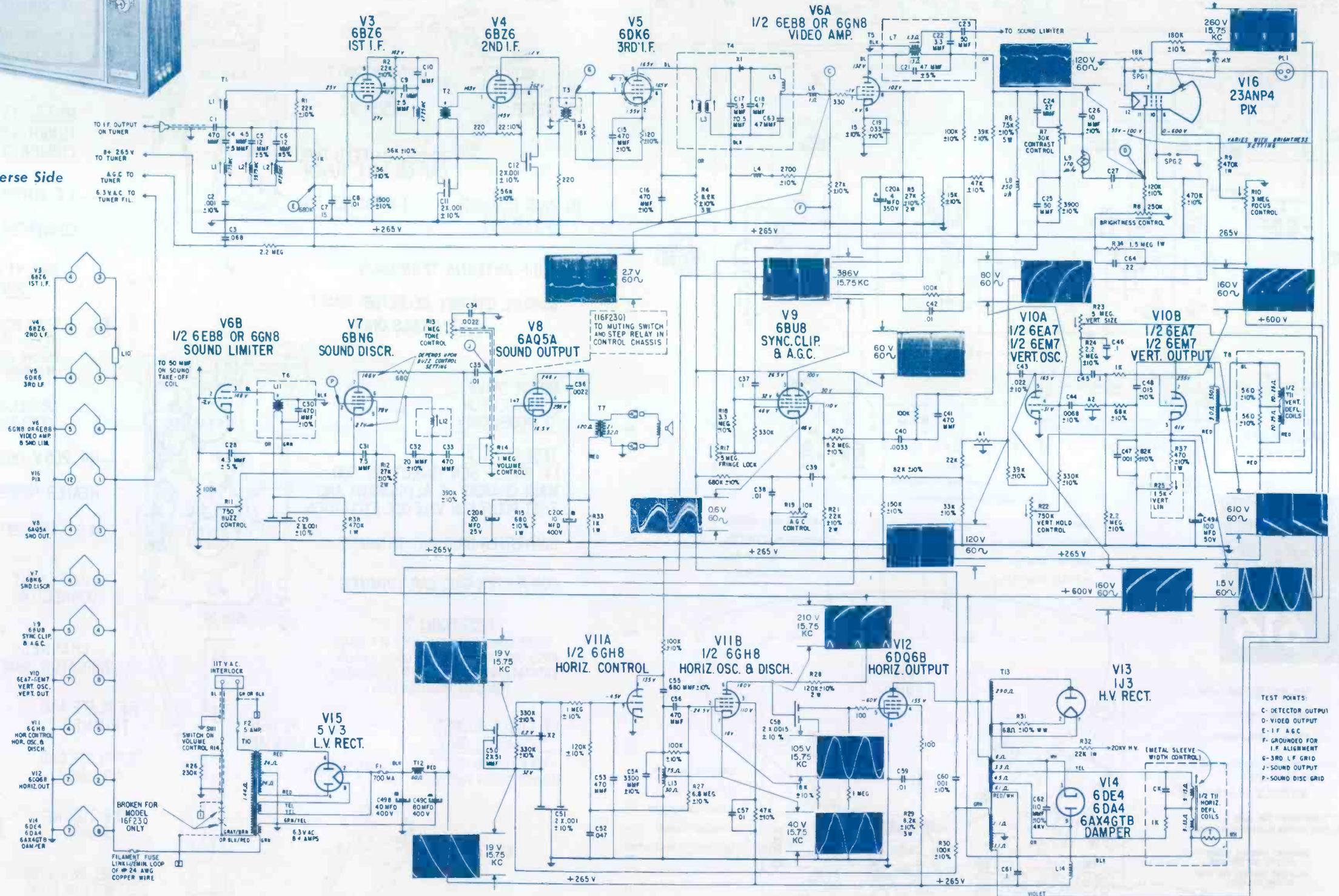

TEST PORTS:
 C- DETECTOR OUTPUT
 D- VIDEO OUTPUT
 E- I-F A.G.C.
 F- GROUND FOR I.F. ALIGNMENT
 G- 3RD I.F. GRID
 J- SOUND OUTPUT
 P- SOUND DISC GRID

CIRCUIT FUNCTION

SPG 1 AND SPG 2 SPARK GAPS


SPG 1 slips over pins 1 and 2 of the picture tube. The gap prevents heater burnout, should an arc occur in the gun. If the picture tube is replaced, install the gap as on the original tube. SPG 2 similarly protects integrator A1.

HORIZONTAL BLANKING CIRCUIT

A negative pulse from the horizontal sweep transformer (violet lead) is applied to grid 1 (pin 2) of the picture tube which cuts off the beam during the horizontal retrace period. The neon bulb acts as a switch which allows the pulse to pass through, but blocks off any transients that may reach the grid during the trace period.



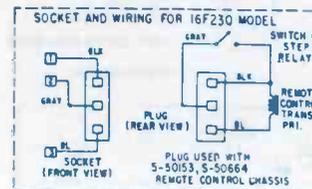
- #### EQUIVALENT CIRCUIT
- ##### A-1 and A-2 INTEGRATORS
- 87-4 R is 47K
 - 87-5 R is 33K
 - 87-7 R is 68K
 - 87-8 R is 82K



ALIGNMENT POINTS
 CIRCLED LETTERS INDICATE ALIGNMENT AND TEST POINTS.

U.H.F. CONTINUOUS TUNER 175-8

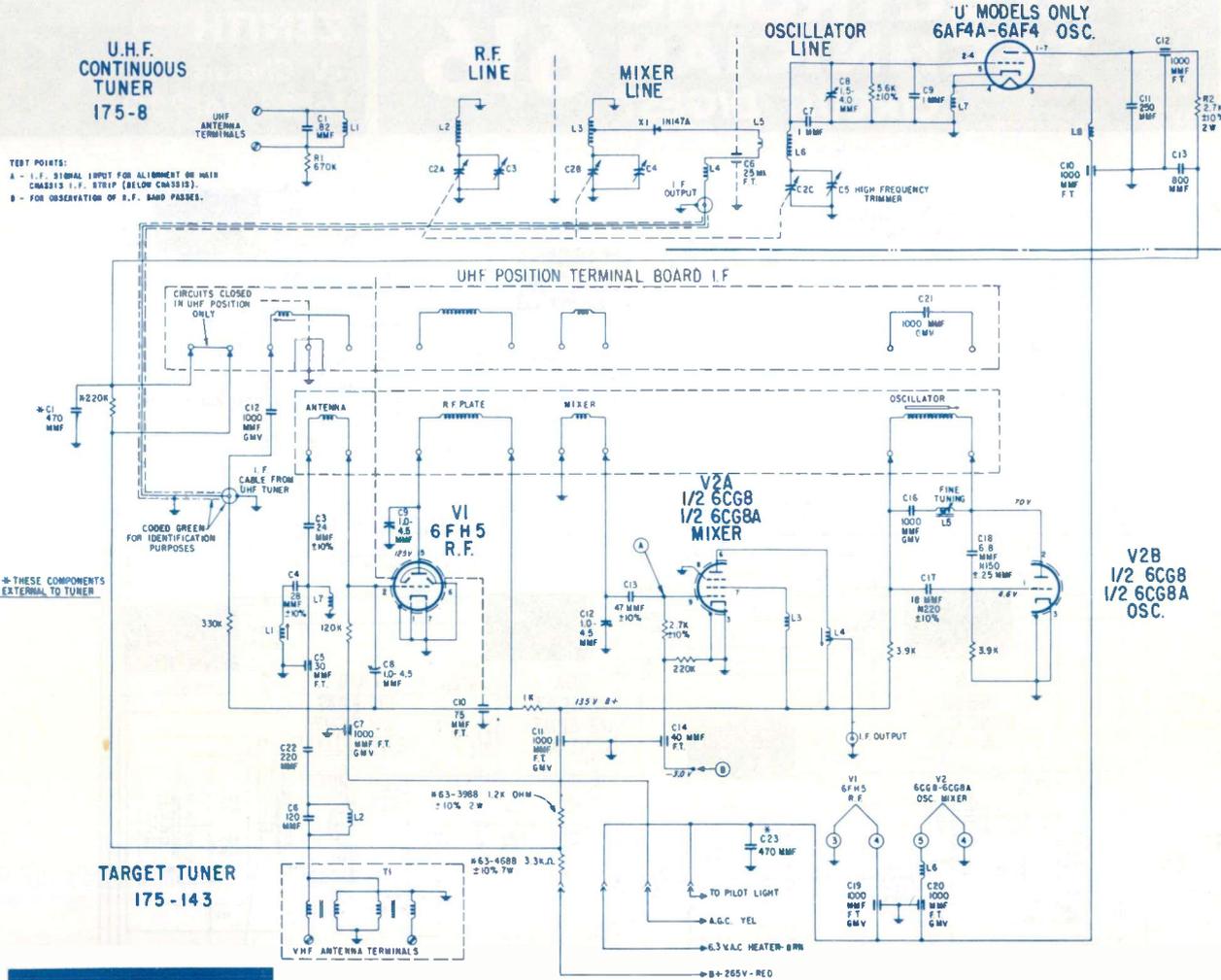
TEST POINTS:
A - I.F. SIGNAL INPUT FOR ALIGNMENT ON MAIN CHASSIS I.F. STRIP (BELOW CHASSIS).
B - FOR OBSERVATION OF I.F. BAND PASSES.




TARGET TUNER 175-143

ZENITH
TV Chassis
16F23, 16F23Q
Electronic Technician
CIRCUIT DIGEST
616

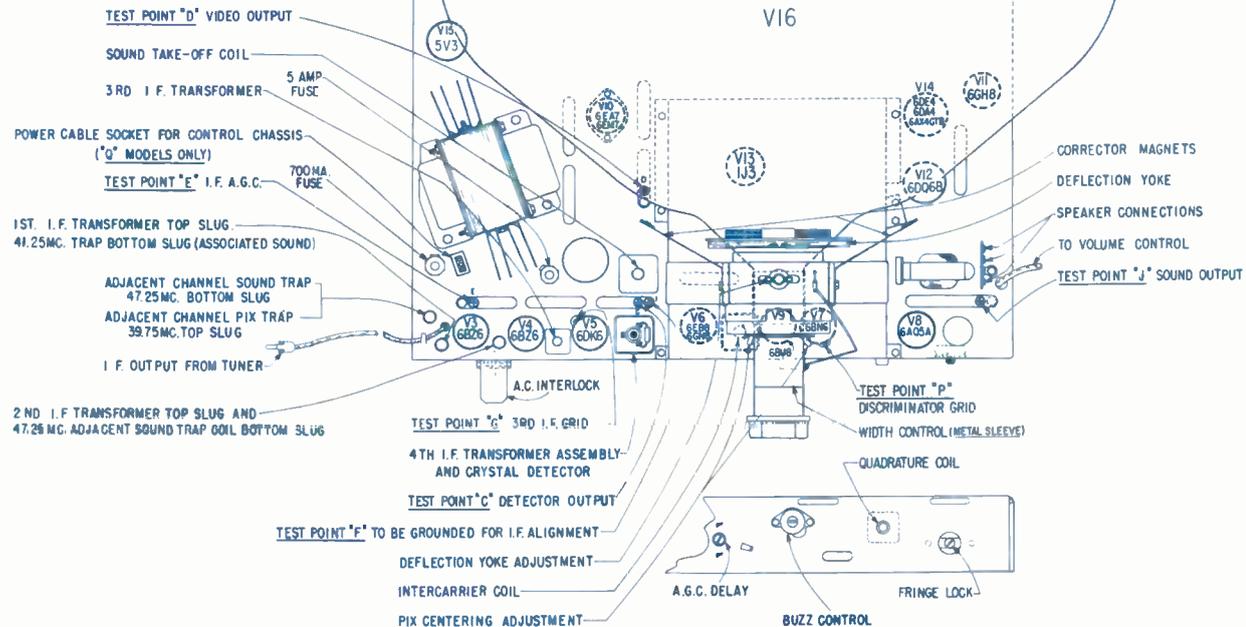- VERTICAL SIZE
- BRIGHTNESS CONTROL
- CONTRAST CONTROL
- VERTICAL LINEARITY
- VERTICAL HOLD CONTROL
- HORIZONTAL HOLD CONTROL
- TO NEUTRAL LIGHT
- A.C. YEL.
- 6.3 V.A.C. HEATER-ØRN
- B+ 265V - RED
- VERTICAL HOLD CONTROL
- HORIZONTAL HOLD CONTROL
- TONE CONTROL
- FOCUS



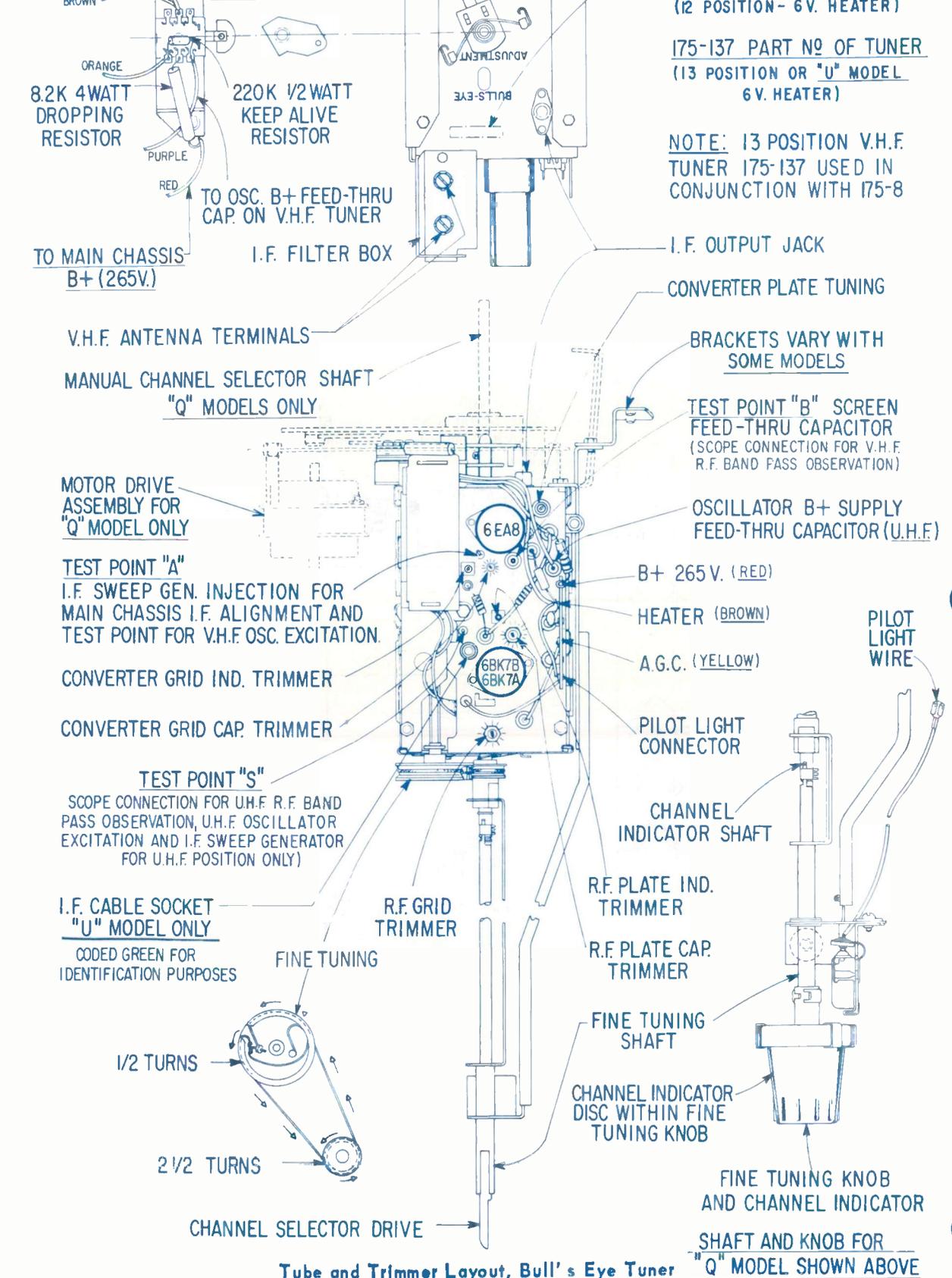FRONT VIEW OF U.H.F. CHANGE-OVER SWITCH ON "U" MODELS ONLY-SWITCH ACTIVATED ONLY IN THE U.H.F. POSITION




Tube and Trimmer Layout, Bull's Eye Tuner "Q" MODEL SHOWN ABOVE

PART NUMBER APPEARS HERE
175-138 PART NO OF TUNER (12 POSITION - 6V. HEATER)
175-137 PART NO OF TUNER (13 POSITION OR "U" MODEL 6V. HEATER)

NOTE: 13 POSITION V.H.F. TUNER 175-137 USED IN CONJUNCTION WITH 175-8





- I.F. OUTPUT JACK
- CONVERTER PLATE TUNING
- BRACKETS VARY WITH SOME MODELS
- TEST POINT "B" SCREEN FEED-THRU CAPACITOR (SCOPE CONNECTION FOR V.H.F. R.F. BAND PASS OBSERVATION)
- OSCILLATOR B+ SUPPLY FEED-THRU CAPACITOR (U.H.F.)
- B+ 265V. (RED)
- HEATER (BROWN)
- A.G.C. (YELLOW)
- PILOT LIGHT CONNECTOR
- CHANNEL INDICATOR SHAFT
- R.F. PLATE IND. TRIMMER
- R.F. PLATE CAP. TRIMMER
- FINE TUNING SHAFT
- CHANNEL INDICATOR DISC WITHIN FINE TUNING KNOB
- FINE TUNING KNOB AND CHANNEL INDICATOR SHAFT AND KNOB FOR "Q" MODEL SHOWN ABOVE
- I.F. FILTER BOX
- V.H.F. ANTENNA TERMINALS
- MANUAL CHANNEL SELECTOR SHAFT "Q" MODELS ONLY
- MOTOR DRIVE ASSEMBLY FOR "Q" MODEL ONLY
- TEST POINT "A" I.F. SWEEP GEN. INJECTION FOR MAIN CHASSIS I.F. ALIGNMENT AND TEST POINT FOR V.H.F. OSC. EXCITATION.
- CONVERTER GRID IND. TRIMMER
- CONVERTER GRID CAP. TRIMMER
- TEST POINT "S" SCOPE CONNECTION FOR U.H.F. R.F. BAND PASS OBSERVATION, U.H.F. OSCILLATOR EXCITATION AND I.F. SWEEP GENERATOR FOR U.H.F. POSITION ONLY)
- I.F. CABLE SOCKET "U" MODEL ONLY CODED GREEN FOR IDENTIFICATION PURPOSES
- R.F. GRID TRIMMER
- CHANNEL SELECTOR DRIVE
- TO MAIN CHASSIS B+ (265V.)
- 8.2K 4WATT DROPPING RESISTOR
- 220K 1/2 WATT KEEP ALIVE RESISTOR
- TO OSC. B+ FEED-THRU CAP. ON V.H.F. TUNER

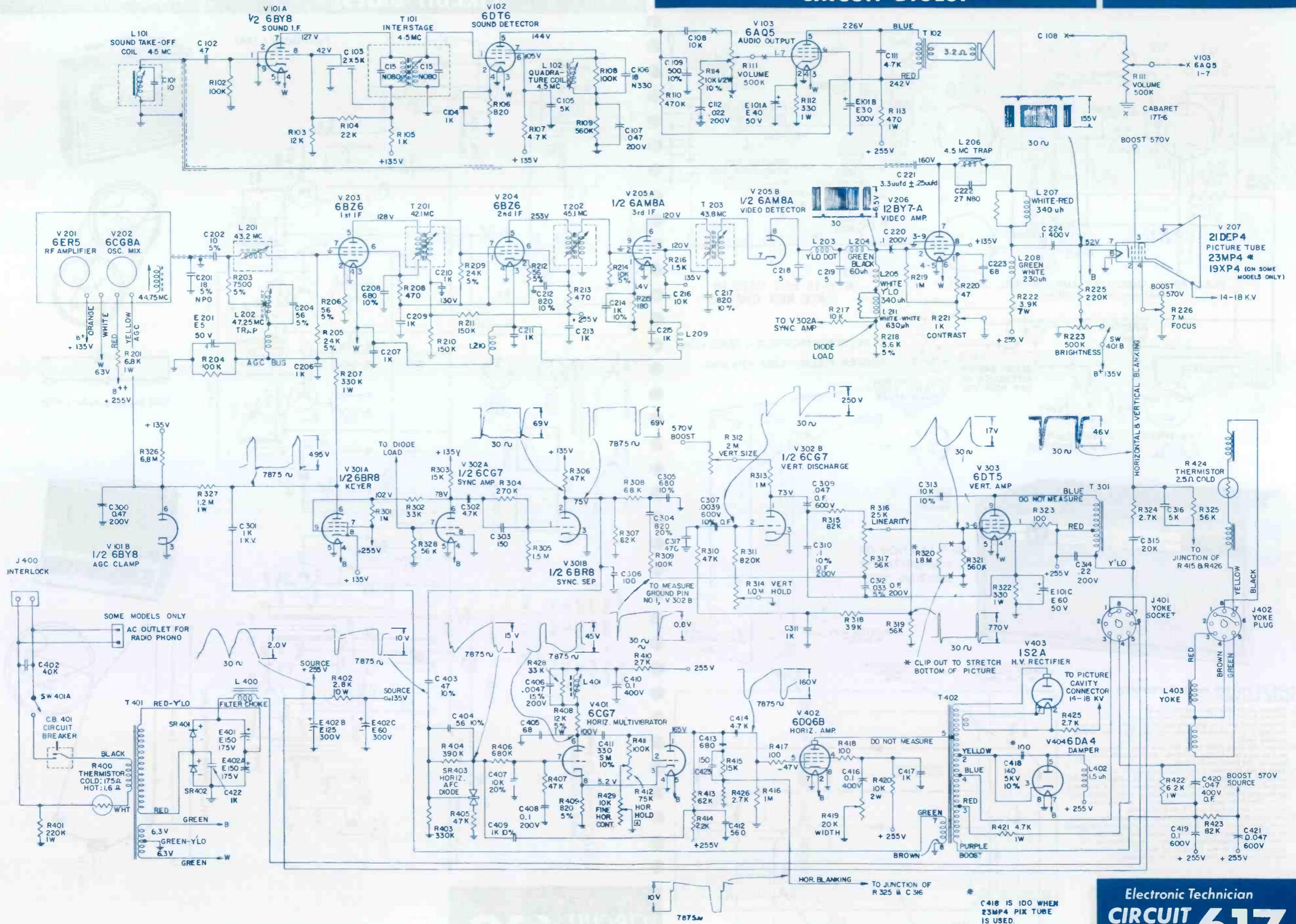

Electronic Technician
CIRCUIT DIGEST 617






* C418 IS 100 WHEN 23MP4 PIX TUBE IS USED.

February • 1961

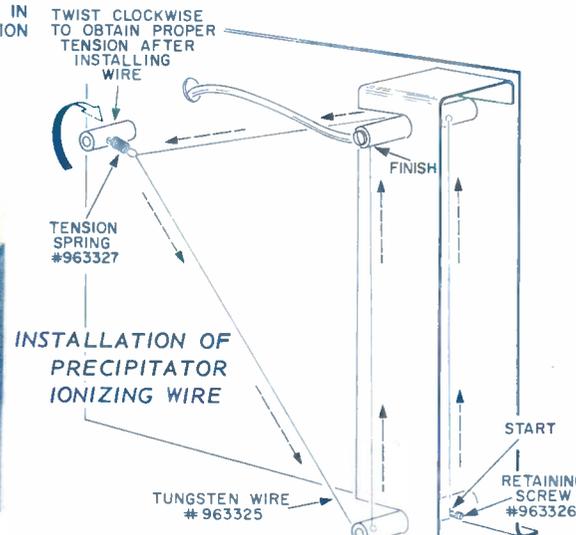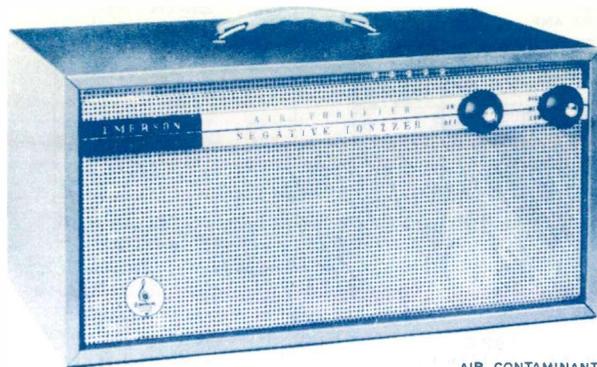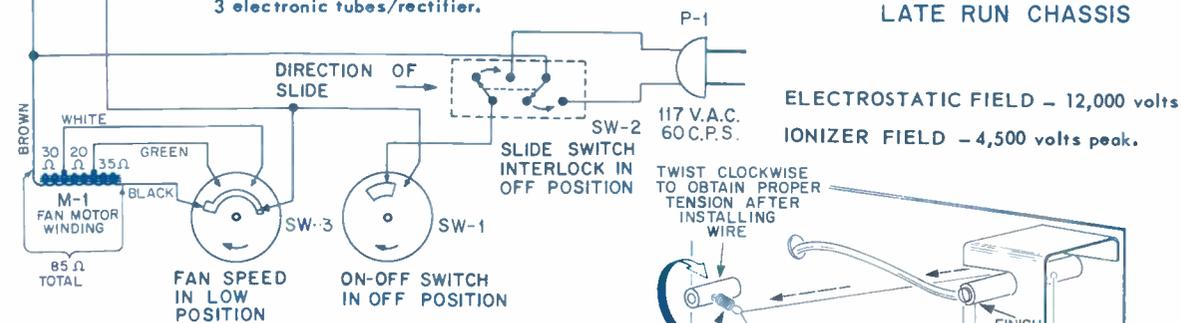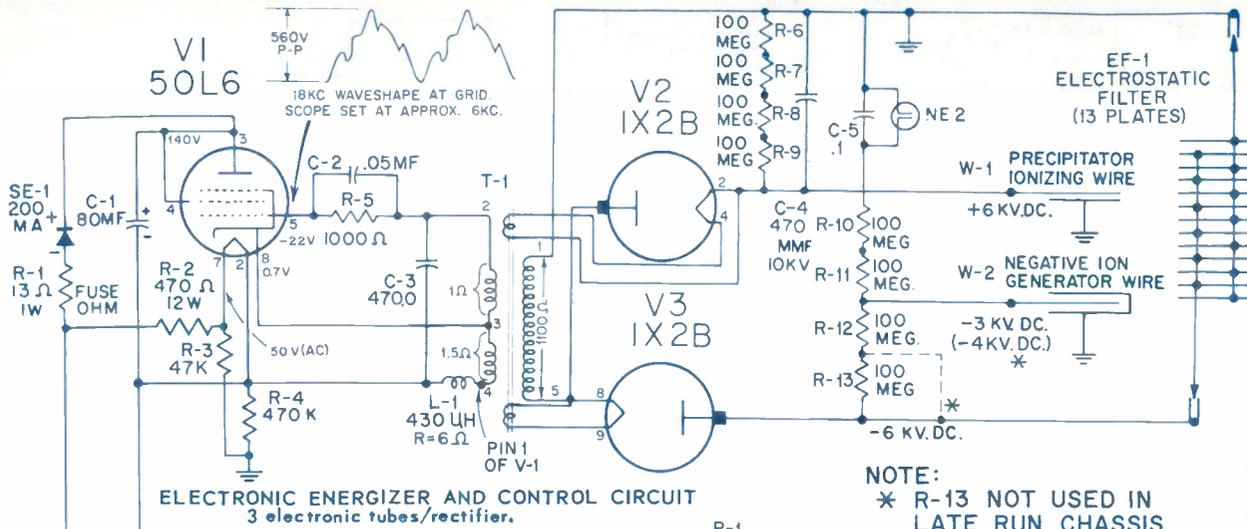

CARE OF FILTERS AND ELECTROSTATIC PLATE ASSEMBLY

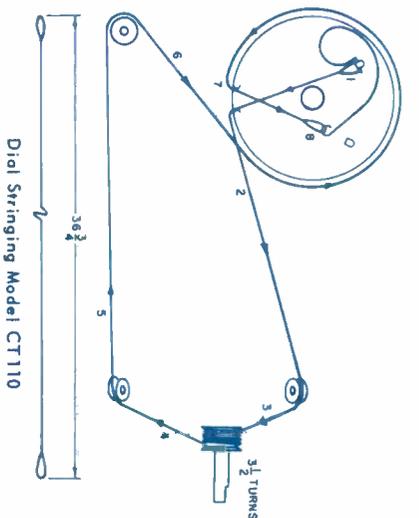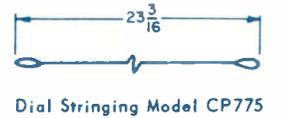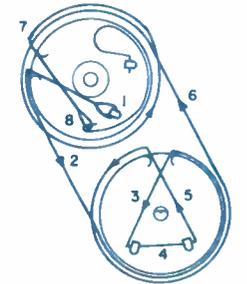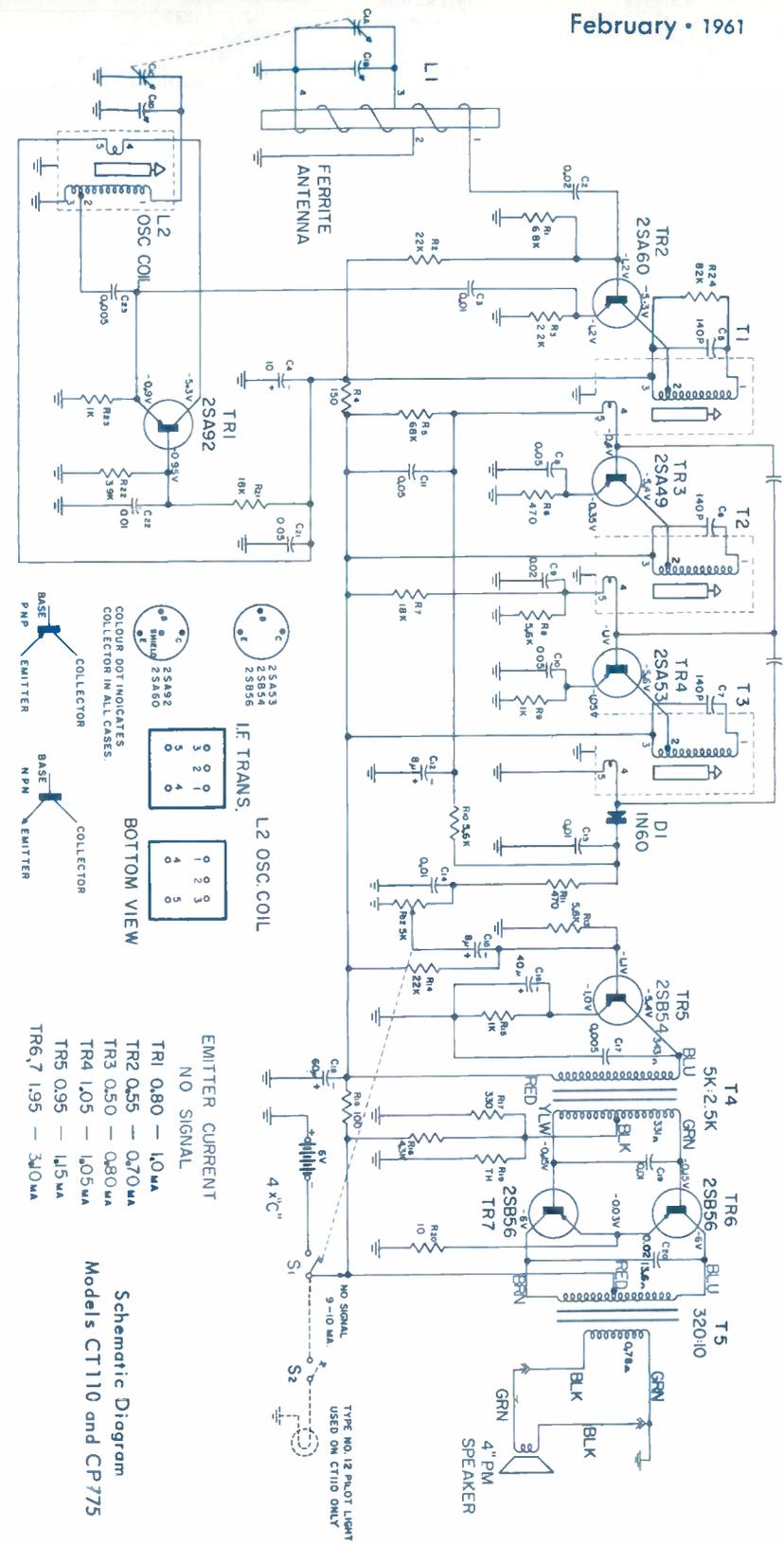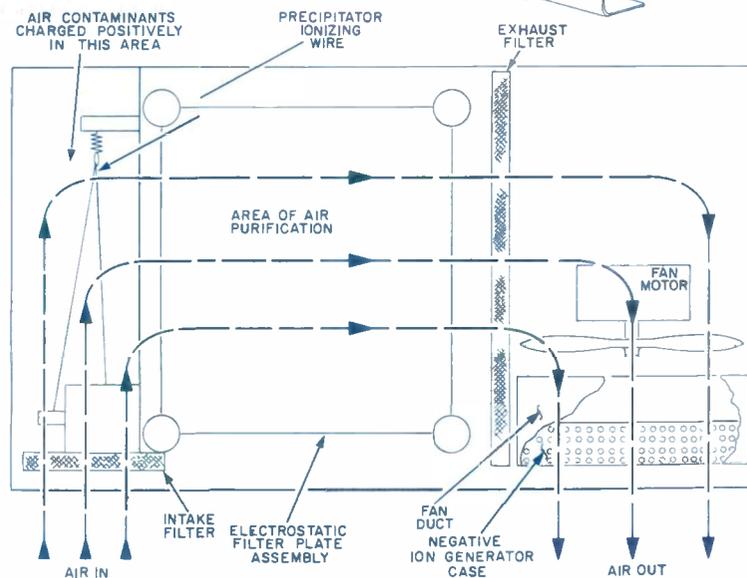
1. Remove power cord from electrical outlet.
2. Remove knobs by pulling gently forward.
3. Remove front grille by grasping bar across grille and pushing downward. This releases the top edge of grille so that it tilts outward freely.
4. Inspect the black filter on the left side first. A vacuum cleaner may be used for cleaning this filter. After a fourth cleaning, however, the filter should be replaced.
5. Each of the 13 plates in the larger electrostatic unit at the center of the ionator should be inspected for surface accumulation of dirt. When this accumulation becomes visible, it should be removed either with a vacuum cleaner or a thin wire brush or both. The plates may be removed easily by following the instructions on the back side of the front grille.
6. The large black fibre glass filter, located between the electrostatic unit, described in 4 above, and the circulation fan should be inspected from time to time. In normal use, however, this filter will not require more than an occasional cleaning. Its only function is to trap flakes which may fall from the electrostatic filter plates, due to excessive accumulation.




February • 1961




2nd Pix I-F Response

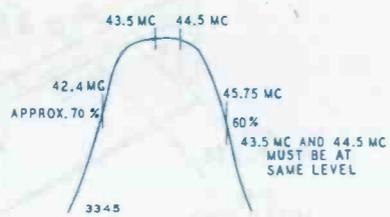

Pix I-F Response From 1st Pix I-F Grid

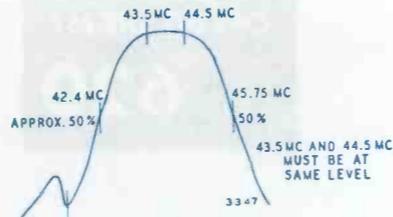


Overall Pix I-F Response

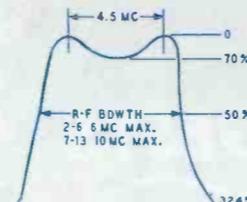


R-F Response


SOUND I-F AND AUDIO

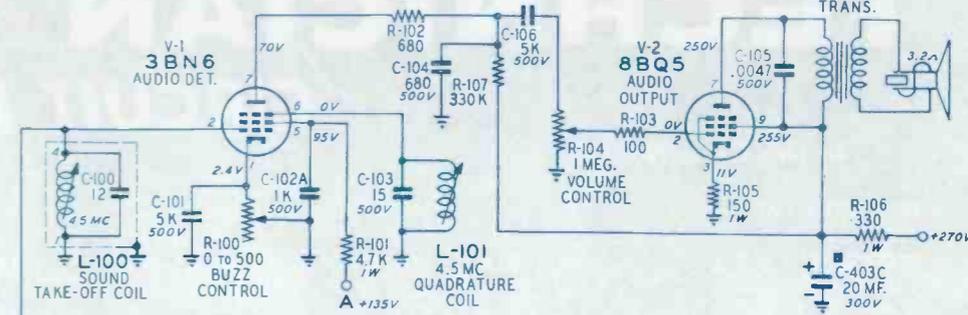


VIDEO

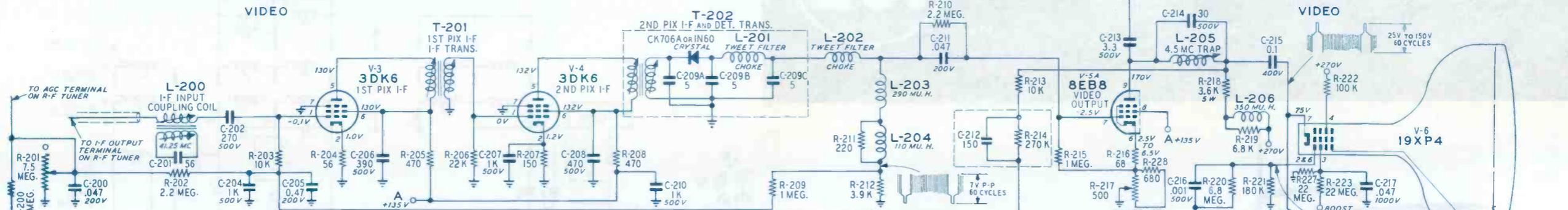

VERT. SWEEP AND SYNC.

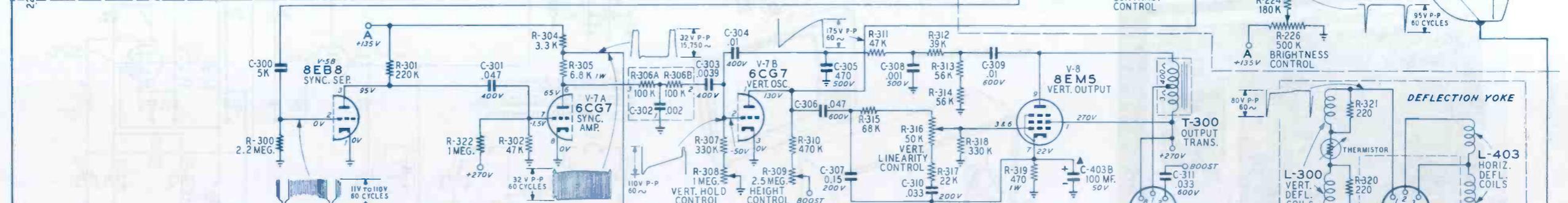

HORIZ. SWEEP AND POWER SUPPLY

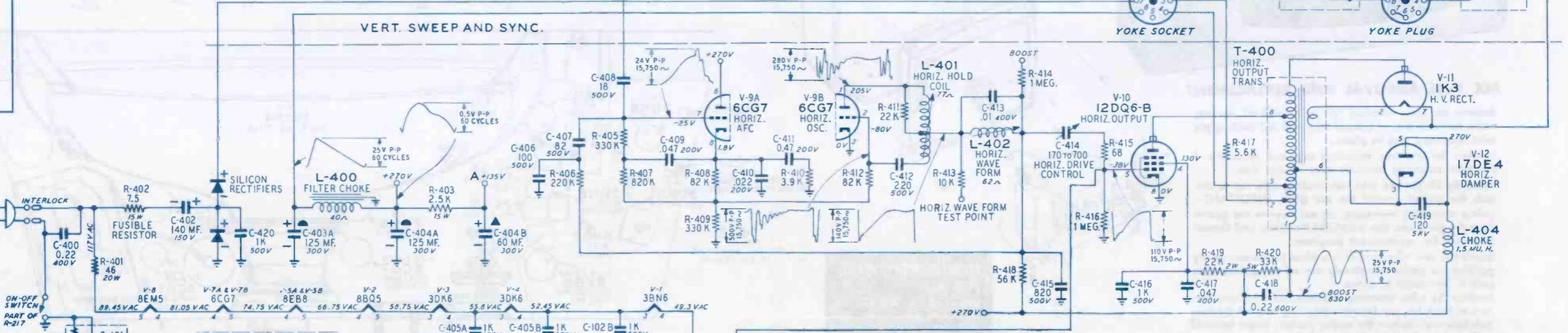

NOTE—In UHF receivers the filament voltages in the tuner and above the tuner in the heater string will be slightly greater because of the filament voltages of the tuner tubes.

More Data on Reverse Side

ELECTRONIC TECHNICIAN

CIRCUIT DIGESTS

In This Issue (No. 102)

ELECTROHOME TV Model "Selkirk"	617	MONTGOMERY WARD TV Models WG-4225A, WG4325A	620
EMERSON Air Purifier Ionizer Model EP-40	618	MOTOROLA TV Chassis TS-ST5 & WTS-435	614
GENERAL ELECTRIC Transistor Radio Models CT110, CP775	619	RCA Reverberation Amplifier Chassis RS-194A	615
		ZENITH TV Chassis 16F23, 16F23Q	616


GROUP 102

MONTGOMERY WARD
TV Models
WG-4225A, WG4325A


Electronic Technician
CIRCUIT DIGEST

620


More Data on Reverse Side

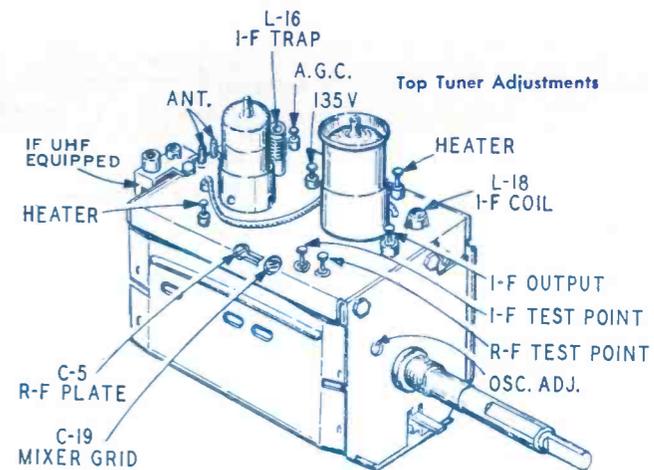

VHF TUNER SCHEMATIC

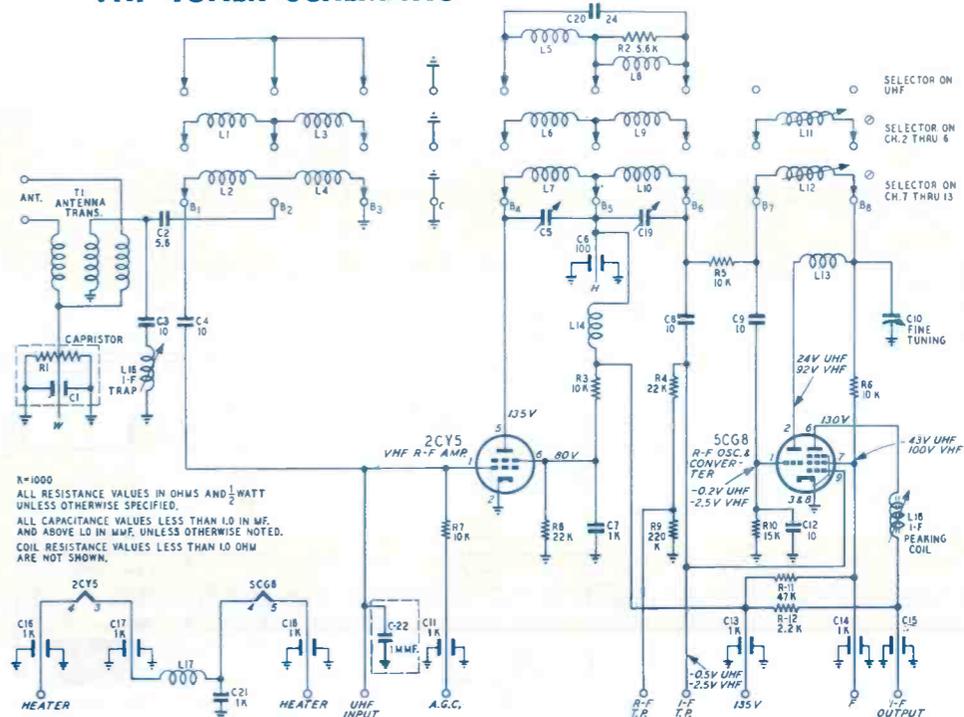

Picture Tube Removal

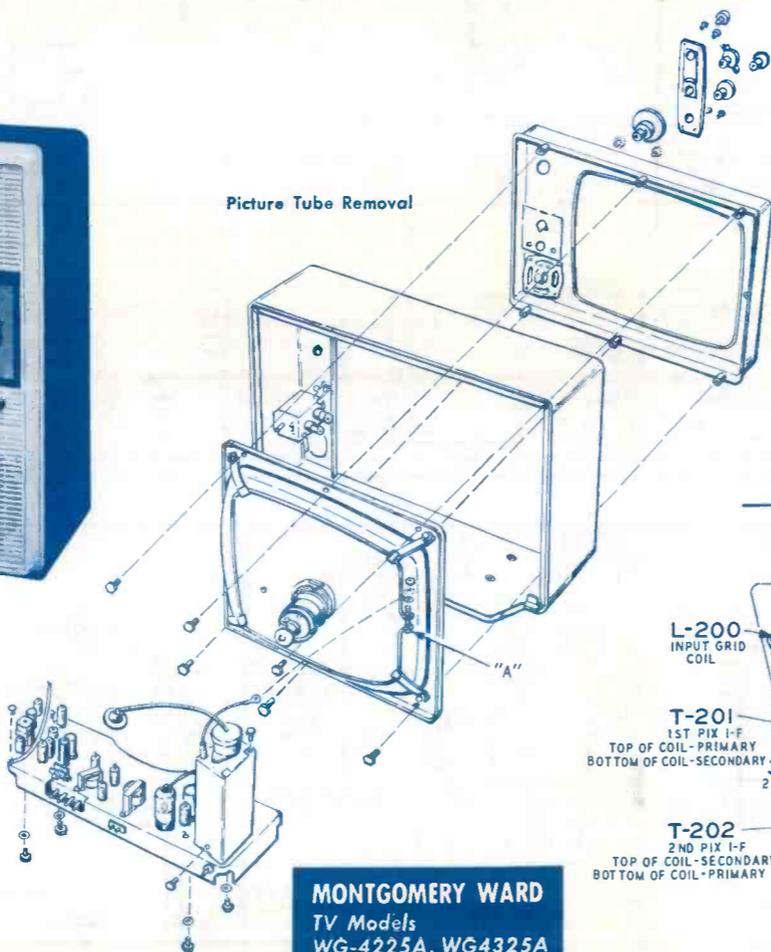

PIX TUBE REMOVAL AND REPLACEMENT

Remove the screw (marked "A" in illustration), washer, screw terminal end of ground wire and nut holding pix tube mounting ring in place.

Remove the pix tube mounting ring and move the 4 pix tube mounting brackets over to one side.

Carefully lift the pix tube out, making sure not to disturb the gasket around the pix glass. **IMPORTANT**—Unless absolutely necessary, do not remove the gasket from the pix glass. Use a 26A704 Pix Glass and Gasket Assembly for replacement purposes.

Install the new tube, and with a blunt instrument gently position the gasket completely around the picture tube until it fits snugly in place.


Position the tube mounting brackets over the four corners of the tube, slip the mounting ring around the four brackets and replace the screw, washer, screw terminal end of ground wire and nut removed.

WARNING—DO NOT TIGHTEN THE PIX TUBE MOUNTING RING SCREW IN UNTIL YOU ARE SURE THAT THE 4 PLASTIC INSULATORS ARE IN PLACE (between the bracket and the frame). If this precaution is not observed, severe shock may result.

MONTGOMERY WARD
TV Models
WG-4225A, WG4325A

Electronic Technician
CIRCUIT DIGEST

620

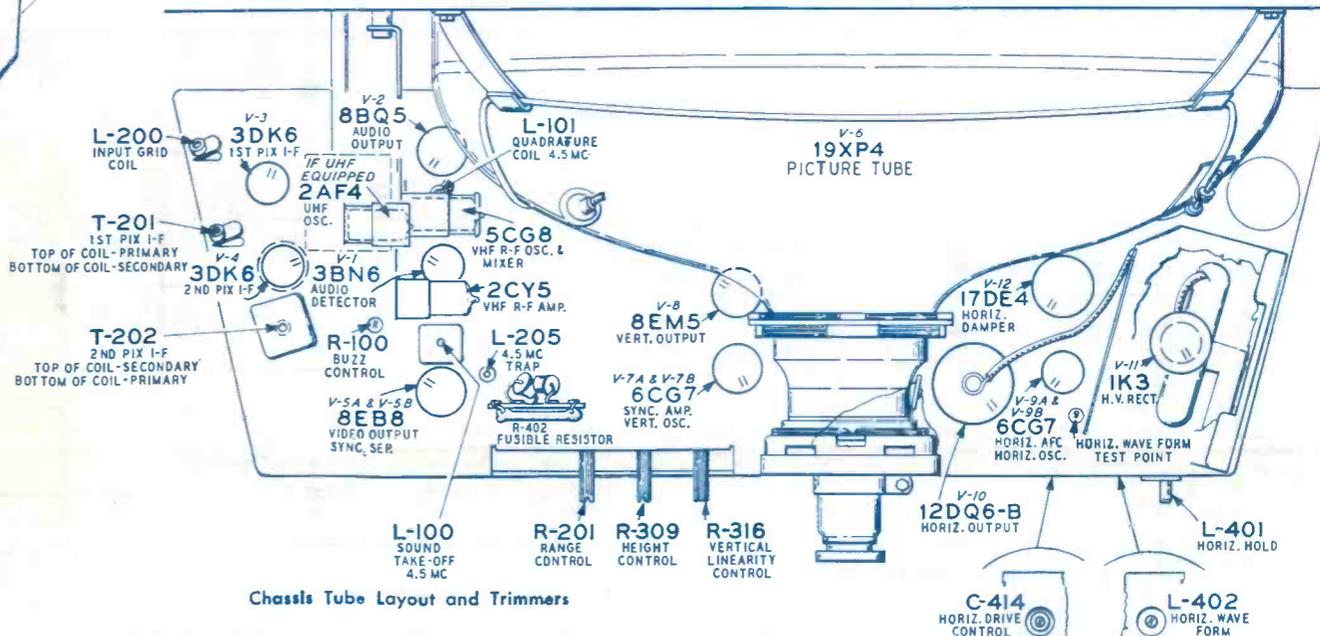

Chassis Tube Layout and Trimmers

THIS SHOP IS MAKING MONEY



with **CLAROSTAT** RTV controls

Radio and television repair shops in all parts of the country are increasing their profits with Clarostat RTV controls—the controls that are *right* for the job, *right* from the carton.

RTV controls are manufactured as matched replacements under rigid quality control standards at the factory. Clarostat offers the direct replacement for practically every radio and TV set control ever produced. RTV controls can save you many hours per man per week, raising your output and multiplying your profits.

Always ask for **CLAROSTAT!**



GET THE COMPLETE DETAILS ON RTV CONTROLS FROM YOUR DISTRIBUTOR


CLAROSTAT MFG. CO., INC.

DOVER, NEW HAMPSHIRE

In Canada: CANADIAN MARCONI CO., LTD., Toronto 17, Ont.



How do your customers rate you?

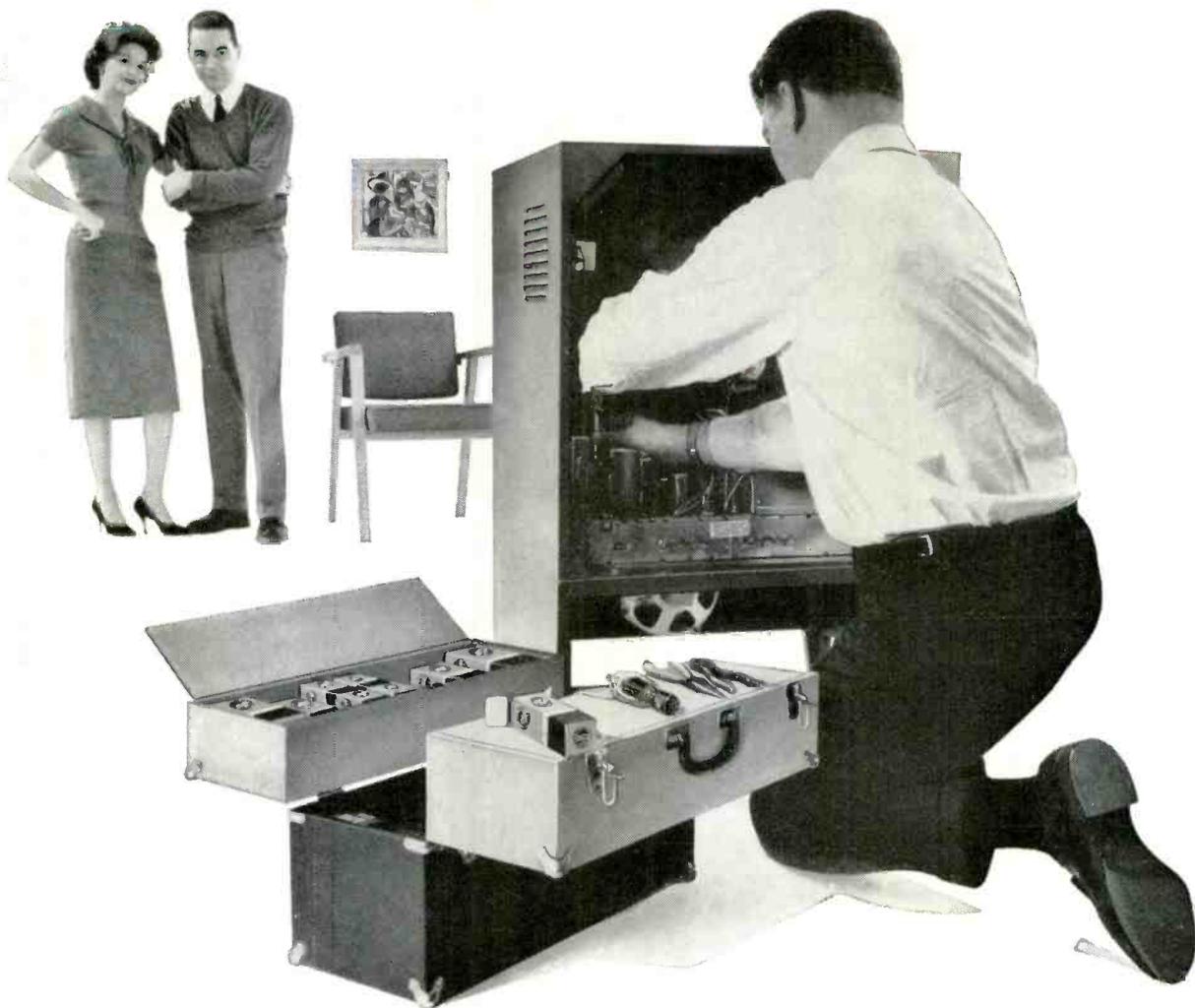

Your reputation is based largely on what happens *after* you leave the scene of each service call. For this reason the name on the tubes you install makes a world of difference. RCA tubes are designed and manufactured to assure customer confidence in you as well as in RCA.

RCA tube quality is your best insurance against call-backs due to premature tube failure.

RCA tube performance puts your workmanship in the best light and protects it through rigid quality control.

RCA's trademark symbolizes a name and reputation customers have respected for decades.

Your customers know that those red-white-and-black RCA tube cartons in your tube caddy represent the most trusted name in electronics. Remember, customer confidence is the cornerstone of your business.

To protect your service reputation before, during and after every service call, make sure your next tube order specifies . . . RCA TUBES.

RCA ELECTRON TUBE DIVISION, HARRISON, N. J.



SIGN OF A SERVICE JOB WELL DONE



The Most Trusted Name in Electronics
RADIO CORPORATION OF AMERICA