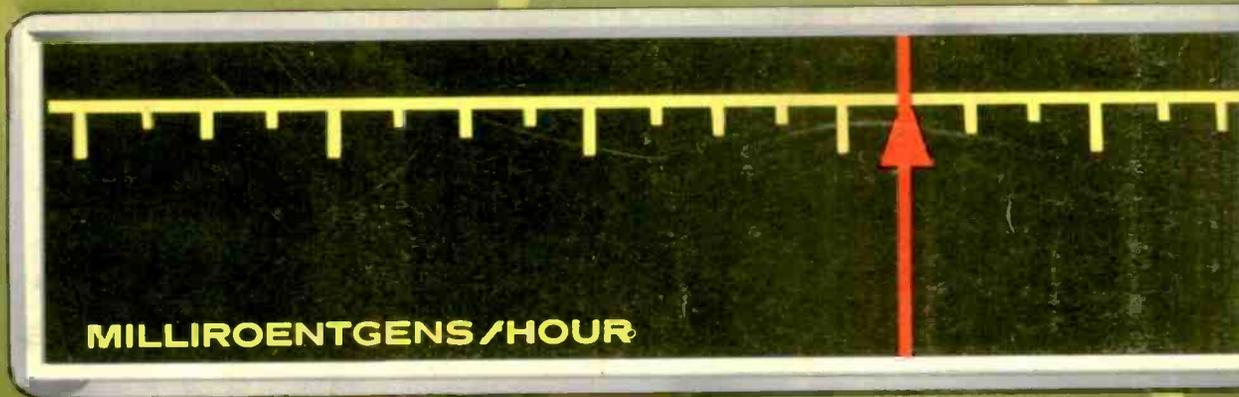


ELECTRONIC TECHNICIAN

including 16 pages of latest
CIRCUIT DIGESTS



ELECTRONIC DEVICES DETECT RADIATION

ALSO IN THIS ISSUE:

Whipping TV Transformer Problems

How to Install FM Auto Converters

MARSHALL F. TACKETT
EUBANK
KENTUCKY
101-X064-X-XXXX1-13

60¢ MARCH 1962




**3,516,032
facts of life!**

• At Seneca Falls, New York, Ottawa, Ohio, and Fullerton, California—where Sylvania manufactures picture tubes—engineers give Silver Screen 85's hours upon hours of severe performance and life tests. Tubes taken at random from production lines are actually operated in commercial TV sets typical of those your customers own. Additional tubes are placed in specially designed life test racks, where operating conditions are even more severe than in normal receivers. In this way, Sylvania gets all the facts of tube-life. These facts provide the feedback data that are essential to a continuing program of producing top-level quality picture tubes.

• What is the significance of 3,516,032? This is the number of hours of severe life testing to which Silver Screen 85's were subjected in the year 1961! Covering some 120 tube types, these over 3½ million life test hours assure Sylvania and you that Silver Screen 85 picture tubes remain second to none in life and sustained top performance. It is your most reliable assurance of no costly callbacks due to premature picture tube failure, or complaints of unsatisfactory picture performance. Remember Sylvania's 3,516,032 hours of quality monitoring—they can mean more profits for you.

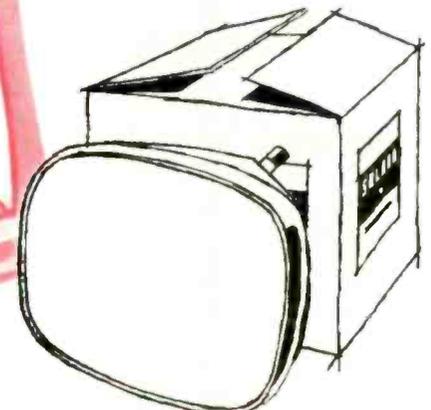Electronic Tubes Division, Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.



Sylvania Silver Screen 85 — available wherever there is TV.

SYLVANIA
SUBSIDIARY OF
GENERAL TELEPHONE & ELECTRONICS



Wake Up



A new day is dawning in electronics. Transistors are here to stay... they are now being used everywhere; in radio, television, Hi-Fi, intercoms, and in nearly all new electronic equipment...

Why put off transistor circuit servicing any longer... there's gold in them thar hills. But you must be equipped to do the job fast and efficiently. Here are the tools that you will need.



NEW SENCORE TRANSI-MASTER

This Tester will analyze the entire circuit in minutes and test transistors in-circuit or out of circuit. Here is how you can pinpoint troubles step by step.

First, check the batteries with the 0 to 12 voltmeter. If the batteries are O.K., check the current drain with the 0 to 50 milliamp meter. A special probe is provided so that you do not need to break the circuit. Excessive current indicates a short; low current indicates an open stage or cracked board. All PF schematics indicate average current.

If trouble is not located by now, isolate the trouble to a specific stage by touching the output of the harmonic generator to the base of each transistor and note spot where sound from speaker (or scope where no speaker is used) stops or becomes weak. The generator becomes a sine wave generator for audio stages to help find distortion.

If trouble points to a transistor, check it in a jiffy with the exclusive in-circuit power oscillator check provided by the TR110. A special probe is also provided for this.

If the transistor checks bad in-circuit, remove it and give it an out of circuit check with the oscillator check or the more accurate DC check.

The DC check is provided for comparison reasons, experimental or engineering work and to match transistors in audio output stages. Beta (current gain) is read direct or on a good-bad scale for service work.

DEALER NET. ONLY **\$4950**



Tests all transistors in-circuit or out-of-circuit

Model TR110

It's a COMPLETE TRANSISTOR TESTER

- SIGNAL TRACER • VOLTMETER
- BATTERY TESTER • MILLIAMMETER



NEW SENCORE TRANSISTOR AND DIODE CHECKER

Here is a low cost tester that has become America's favorite. The TR115 provides the same DC out of circuit checks as the TR110; leakage and current gain. Beta (circuit gain) can also be read direct or as good or bad. Opens or shorts in the transistor are spotted in a minute. The TR115 checks them all from power transistors to the small hearing aid type. Japanese equivalents are listed also. This famous tester is used by such companies as Sears Roebuck, Bell Telephone and Commonwealth Edison. New circuits enable you to make service checks without set-up charts even though charts are provided for critical checks.



Model TR115
Dealer Net
\$1995



SENCORE BATTERY ELIMINATOR AND TROUBLE SHOOTER

For replacing batteries during repair.

Many servicemen say that they wouldn't service transistor circuits without this power supply. The tried and proven PS103 is a sure fire answer. It can be used to charge the nickel cadmium batteries as well. Dial the desired output from 0 to 24 volts DC and read on meter. Low ripple insures no hum or feedback. Total current drawn can also be read on the PS103 by merely flicking the function switch to milliamps. The PS103 is the only supply that will operate radios with tapped battery supplies such as Philco, Sylvania and Motorola. No other supply has a third lead.



Model PS103
Dealer Net
\$1995

Now in stock at
your Authorized
Sencore Distributor



SENCORE

ADDISON, ILLINOIS

... for more details, circle 48 on page 50

Spring Comes Early...

in the wonderful

PHILCO
World of
FREE GIFTS

**Redwood and Aluminum
Foam Cushion
CHAISE**

1" tubular aluminum, weatherproof redwood back, seat and arms. 6" rubber tires, plastic covered 2" thick soft poly-foam cushion. 3 position. Folds compactly for storage. Ideal for indoors or outdoors, porch, patio or sunroom.



AD 3993



AD 3989

Folding Arm Chair

Redwood and aluminum, 1" tubular frame. Folds flat to 6" for storage. Weatherproof.

FREE with \$130 worth of purchases



AD 3967

Fitted Travel Case

For the ladies. Scuff resistant vinyl covering, fitted with Jewelite Nylon brush, comb and mirror set.

FREE with \$125 worth of purchases



AD 3965

Nylon Bag, Gloves

Clutch style purse with gold finished chain. Nylon palm stretch gloves to match. Black only.

FREE with \$60 worth of purchases




AD 3982

Ronson CFL Shaver

1962 Mark II Electric Shaver. \$23.50 value. Multi-blade miracle cutter gives quickest shaves.

FREE with \$250 worth of purchases

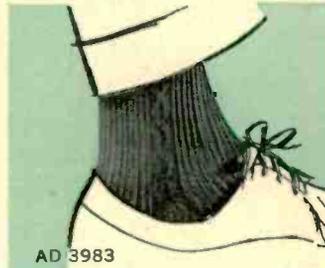

AD 3983

Men's Ban-Lon Sox

First quality, 100% Ban-Lon yarn, reinforced top and heel. Stretch type, fits sizes 10 to 13.

FREE with \$12 worth of purchases



AD 3986

3/8" Electric Drill

3/8" electric drill with new "Speedsight" for easier drilling at any angle. "Speedway" brand.

FREE with \$225 worth of purchases

FREE WITH \$415 WORTH OF PURCHASES...

\$25 LESS WITH BONUS CHECK

... for more details, circle 38 on page 50

MANY OTHER OFFERS NOT SHOWN

SEE YOUR PHILCO DISTRIBUTOR TODAY... SELECT YOUR FREE GIFTS NOW... PROGRAM ENDS APRIL 30

ELECTRONIC TECHNICIAN

Including
SERVICE
Magazine

WORLD'S LARGEST ELECTRONIC TRADE MAGAZINE

HOWARD A. REED Publisher
ALBERT J. FORMAN Editor
ARTHUR P. SALSBERG Managing Editor
JACK HOBBS Technical Editor
VIC BELL Associate Editor
B. V. SPINETTA Assistant Editor
HERB HOENE Circulation Manager
EARL HINTZ Production Manager



AN OJIBWAY
PUBLICATION

OJIBWAY PRESS, Inc.

1 East First Street
Duluth 2, Minn.
Telephone: RA 7-8511

Sales Offices:

NEW YORK: Ron Kipp, National Sales Manager, 480 Lexington Ave., New York 17, N. Y. TN 7-0011

CHICAGO: William Klusack, 221 N. LaSalle St., Chicago 1, Ill. CE 6-1600

CLEVELAND: Bernie Edstrom, 15605 Madison Ave., Cleveland 7, Ohio LA 1-7900

LOS ANGELES: Boyd B. Garrigan, 1145 W. Sixth St., Los Angeles 17, Calif. HU 2-2838



ELECTRONIC TECHNICIAN and Circuit Digests, published monthly at 1 East First Street, Duluth 2, Minnesota, by Ojibway Press, Inc., Marshall Reinig, president; Robert Edgell, executive vice president; Lawrence Rosenthal, vice president; H. B. Fryberger, Jr., secretary; E. A. Kuefner, treasurer. Single copies, 60c. Subscription rates: United States and Canada \$5 for one year; \$8 for two years; \$10 for three years. Pan American and Foreign countries, \$9 for one year; \$14 for two years; \$18 for three years. Application for second class re-entry pending at Waseca, Minn. Copyright 1962 by Ojibway Press, Inc., Duluth, Minn. Reproduction and reprinting prohibited except by written authorization of publisher. POSTMASTER: SEND NOTIFICATION (Form 3579) TO ELECTRONIC TECHNICIAN, 1 EAST FIRST STREET, DULUTH 2, MINNESOTA.

March • 1962

Vol. 75 • No. 3

FRONT COVER Radiation cannot be observed by human senses. Consequently, devices are employed to detect it, such as specially treated material that changes color to indicate "danger" or instruments that buzz or can be read on a meter. The latter two are of interest to us since they are electronic devices and measure amount of radiation as well as "danger." Circuitry and operation of these instruments are discussed starting on page 26.

FEATURES and ARTICLES

"Tuning in the Picture"	14
TV Manufacturers Technical Digest	18
Electronic Devices Detect Radiation	26
<i>by Allan Cantor</i>	
Whipping TV Transformer Problems	30
<i>by Jack Hobbs</i>	
"Tough Dog" Corner	33
<i>by Frank Salerno and Thomas Gregg</i>	
Troubleshooting Hi Fi Tone Controls	34
<i>by Mannie Horowitz</i>	
New Test Instruments for Bench and Caddy	38
TV Industry Advertising Guide	40


DEPARTMENTS

Editor's Memo	8	Free Literature	50
Letters to the Editor	10	New Products	52
Calendar of Coming Events	15	News of the Industry	60
ET Viewpoint	25	Catalogs and Bulletins	62
Technical Library	42	Audio News Letter	63
Shop Hints	46	Association News	64
New Books	74		


CIRCUIT DIGESTS PRECEDING BACK COVER

IN THIS ISSUE

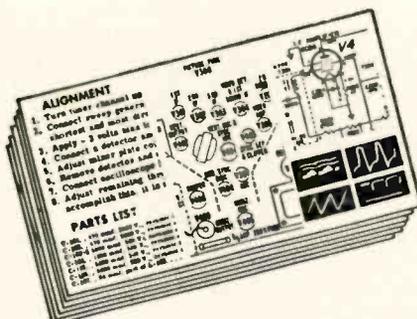- (16 pages latest schematics and data)
- ELECTROHOME: TV Chassis CHT-213-611
- EMERSON: TV Chassis 120507A,-8B, 120515C,-16D, 120541C,-42D
- FISHER: FM Stereo Tuner Model 800
- MONTGOMERY-WARD: TV Models WG-4234A, WG-4334A
- TRAVLER: TV Chassis 1156-89
- ZENITH: TV Chassis 16J28Q5



PVC

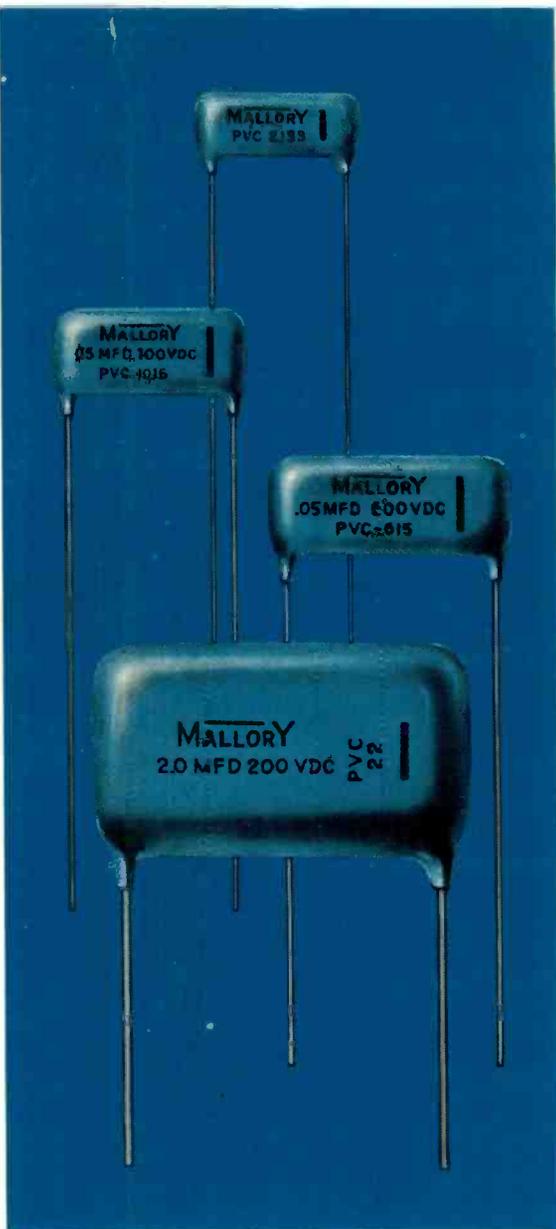

PV



TC TUBULAR ELECTROLYTICS

Economical filter capacitors. Also special TCX type for -55°C . Twin-pack keeps leads free from kinks.



FP ELECTROLYTICS

Original 85°C capacitor, now better than ever. Etched cathode gives hum-free performance. Chassis or printed circuit mounting.



STA-LOC® CONTROLS

End searching and waiting. Your distributor can custom-build, in just 30 seconds, any of over 38,000,000 single or dual controls.



GOLD LABEL® VIBRATORS

Quietest ever made . . . for the best in auto radio servicing. Buttonless contact design gives longest trouble-free service.

C

STOP CALL-BACKS WITH MALLORY PVC MYLAR* CAPACITORS

Best thing about Mallory PVC coupling and by-pass capacitors is that you can install 'em and forget 'em. They won't drift, won't pop out. Not even when you put them in a hot spot, load 'em up to full voltage (or even higher). Not even when the weather stays hot and wet for months. Here's why.

All Mylar dielectric. Not a combination of paper and Mylar that invites moisture absorption and causes voltage failure and capacitance drift. There's nothing but Mylar between capacitor foils. And you *know* that's the most moisture-impervious dielectric used today.

Performance-plus. Use PVC's at any ambient from -40 to $+105^{\circ}\text{C}$. . . no need for derating. Push them up to full rated voltage. They've been tested at *twice* the voltage marked on 'em. They won't drift . . . no danger of a call-back to fix a sweep circuit that won't hold sync.

Foolproof leads. Flexible PVC case lets you bend leadwires at sharp angles without breaking the moisture seal.

Small and handy. Rating for rating, Mallory PVC Mylar capacitors are almost one-third smaller than other capacitors. And they're furnished in a handy, zip-close reusable package.

There's a wide range of ratings, priced lower than you'd think possible for so much quality. Get Mallory PVC Mylar capacitors—and all other Mallory quality components—from your Mallory distributor.

*Registered Trademark of E. I. du Pont de Nemours & Co., Inc.

*Distributor Division
Indianapolis 6, Indiana
P. R. Mallory & Co. Inc.*

P. R. MALLORY & CO. Inc.
MALLORY



MALLORY RMC DISCAPS®

Ceramic capacitor replacements . . . tops for customer satisfaction. Long the quality standard in original equipment.



MALLORY MERCURY BATTERIES

Tops for transistor radios. Steady power, up to 3 times longer service . . . they live for years when idle. Guaranteed leakproof.



GEMS

Rugged, moistureproof tubular capacitors. Handy five-pack keeps stock clean, leads kink-free.

- - - for more details, circle 35 on page 50

MAKING ROOM AT THE TOP



AC VTVM & AMPLIFIER #250


NEW EICO ENGINEERING ACHIEVEMENT Kit \$49.95 Wired \$79.95

Phenomenally good AC VTVM, bound to make room for itself at the top of the professional market. 12 ranges from 1 mv to 300 V full-scale, 10c-600kc ± 0 db response, 10 megohms input impedance, $\pm 3\%$ of full scale accuracy. At the flick of a switch, the internal wide-band amplifier is available for external use. Provides 8c-800kc ± 0 db response, 5 VRMS output, 5 kilohm output impedance, gain control, noise -40 db. Regulated power supply, frame grid tubes.

AC VTVM #255 Kit \$44.95 Wired \$72.95

All the precision VTVM facilities of the #250, less the external use of the wide-band amplifier.

EDITOR'S MEMO

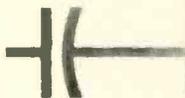

It's not unusual for customers to complain that TV sets are unreliable. Reliability, of course, is a relative thing.

Because electrical and electronic devices utilize such intricate parts which demand very critical performance, their reliability cannot be measured in terms of relatively simple devices.

To indicate that these problems are not limited to the radio-TV field, consider the fairly complex construction of an automobile. Besides the engine, automatic transmission, steering and differential, there are many other mechanical linkages. Yet it is the electrical system which is the biggest headache.

The American Automobile Association, for example, reports that of the 65,000,000 car service distress calls received during a year, some 38%, or 25,000,000 of these calls, are attributed to failures in the electrical system. And remember, the automobile electrical system is not nearly as complex as a TV receiver.

Further evidence of reliability problems being inherent in electrical and electronic equipment are the all too frequent failures in some of our guided missiles. Here, despite the most advanced engineering, despite the fact that no cost is spared, failures still occur. It's in the nature of the beast.

When one considers that TV sets have improved substantially over the past 15 years, it is to the industry's credit that this accomplishment has been accompanied by a decrease in price. Nowhere else can the consumer buy such a wealth of entertainment in such an intricate unit for, perhaps, \$200.


I think it is a feather in the cap of the TV service industry that in spite of built-in limitations, technical problems and financial difficulties, at any one time the public has over 98% of its TV sets in suitable condition for operation.

So we ought to be grateful for little things at least.


Think of the woman who bought a parrot, and after having him in the house for a day, returned him to the store complaining that the bird was undesirable. It spouted a steady stream of profane language.

The petshop owner told the woman that she should not be unhappy with the parrot because of this one small shortcoming. After all, the bird did not smoke, drink, gamble or run after wild women!

Al Forman

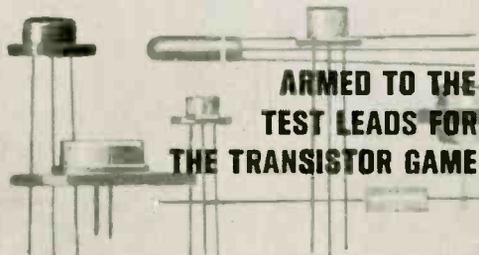

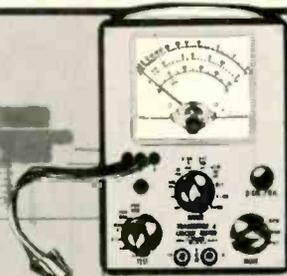
ARMED TO THE TEST LEADS FOR THE TRANSISTOR GAME



TRANSISTOR AND CIRCUIT TESTER #680

Kit \$25.95 Wired \$39.95

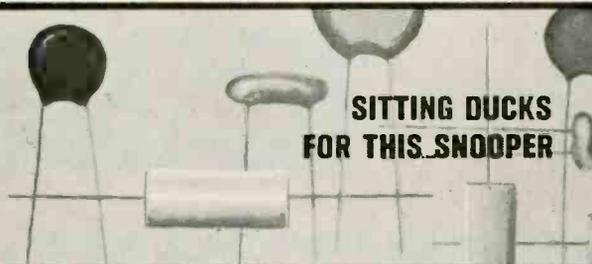Measure ICEO, ICBO & dc β directly, ac β indirectly, without charts or special settings—plus all dc volts, currents, and resistances needed to service transistor equipment. 50 μ A, 3 1/2" face meter movement provides sensitivity and scale length necessary for accurate measurements. Built-in 20,000 ohms/volt VOM facilities let you work on transistor equipment with minimum equipment tie-up.



SITTING DUCKS FOR THIS SNOOPER



IN-CIRCUIT CAPACITOR TESTER #955

Kit \$19.95 Wired \$39.95

- Leave those capacitors where they are! Without unsoldering:
 - check for shorts (even in the presence of as little as 1 ohm shunt resistance)
 - check for opens (determine the presence of as little as 5mmf in the circuit), and to confirm open indication . . .
 - measure capacitance with $\pm 10\%$ accuracy between 0.1 mf and 50 mf
 - measure RC product, convertible into dissipation or power factor.

Also New From EICO:



Battery Eliminator and Charger #1064 Kit \$43.95 Wired \$52.95



AC Bench Supplies: Model 1073—Kit \$35.95 Wired \$47.95 Model 1078—Kit \$42.95 Wired \$54.95



AC Volt-Watt Meter #260 Kit \$49.95 Wired \$79.95



For complete catalog of over 80 EICO kits and wired units—hi-fi, test equipment, citizens radio, ham gear—plus name of nearest distributor, write to dept. ET-3

ELECTRONIC INSTRUMENT CO., INC., 3300 N. BLVD., L. I. C. 1, N. Y.

Add 5% in the West

Export Dept: Roburn Agencies, Inc. 431 Greenwich St., N. Y. 13, N. Y.

SEE US AT IRE BOOTH NO. 3701

— for more details, circle 21 on page 50



CAN YOU SOLVE THIS MYSTERY?

(Using the clues below, identify the Company that offers you the industry's best service)

Service technicians—and set manufacturers, as well—use this company's capacitors oftener than any other brand.

Providing the right sizes, styles, ratings, mountings, this company offers the industry's most complete capacitor line.

Replacements for new capacitors in latest model sets are promptly made available to the service technician.

A continuous research program, employing a staff of over 500 scientists, engineers and technicians, assures our ability to keep up with new capacitor needs.

Guaranteed for performance and dependability, every type of capacitor we make is double-checked by our rigid quality control program.

Unequaled service aids include replacement guides, wall charts, service manuals, capacitor calculators, and other technical helps which simplify your job of correct capacitor selection and replacement.

Effective posters and advertising mats are available to you as part of our customer relations program for dealers.

WHO ARE WE? If you still don't know the answer, read the initial letter of each of the sentences above. This is the name that stands for the most complete and best quality line of capacitors, unsurpassed service help, continued technical assistance—and less call-backs for our friends, the service technicians.

I'd walk a mile...



for Centralab L & T Pad Attenuators



I'm not an ordinary camel—I'm a thinking man's camel—and I think highly of Centralab L & T Pad Attenuators.

These units work good—like an L & T Pad should—because of their small size, high wattage, and anti-backlash construction. Measuring less than $1\frac{1}{16}$ " deep from the mounting surface, and with $1\frac{3}{32}$ " diameter, they fit into any standard junction or switch box with room to spare.

In L & T Pads, though, it's what's in back that counts—and these Centralab units have exclusive "thermo-pass" insulation, which combines fast heat transfer with a high dielectric constant to achieve a conservative rating of 20 watts audio, 5 watts D.C., in a unit the size of conventional 2 watt controls.

Because of Centralab's anti-backlash construction, the "play" frequently found in dual controls is eliminated. The wiper contacts move in unison, so there's no alteration in frequency response due to variations in wiper position on the resistance tracks.

So hump down to your Centralab distributor and stock up on these L & T Pad attenuators. They satisfy!

B-6205S

THE ELECTRONICS DIVISION OF GLOBE-UNION INC.
902C EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN
In Canada: Centralab Canada Ltd., P.O. Box 400, Ajax, Ontario

ELECTRONIC SWITCHES • VARIABLE RESISTORS • CERAMIC CAPACITORS
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS

- - - for more details, circle 17 on page 50

LETTERS TO THE EDITOR

Radiation Instruments

Editor, ELECTRONIC TECHNICIAN:

Radiation measurement instruments are beginning to get into the customer's hands. Please publish an article on understanding and servicing these units. A technician should study radioactive monitoring as a service to himself and the country.

WILLIAM H. ANTHONY

Washington, D. C.

• *Electronic technicians can certainly play a vital role in civilian defense. The cover story article in this issue on radiation detection devices should be an aid in the national effort, and open new earning opportunities for interested service dealers.—Ed.*

Foreign Tube Replacements

Editor, ELECTRONIC TECHNICIAN:

I have a "Philips," of Holland radio in for repair. The Model No. is B3X66U with a tube complement of UCH81, UF89, UY42, UL84, UBC81. I checked these on my tube checker and the last two are bad. I cannot find any American tube listed as a substitute, and cannot find out where to order the exact replacements.

I would appreciate any help you can give me on this.

ARTHUR D. ERICKSON

St. Paul, Minnesota

• *The tube type equivalents are:*

Foreign	U. S.
UCH 81	19D8
UF 89	12DA6
UY 42	55N3
UL 84	45B5
UBC 81

All are US equivalents except the last which does not have one. The foreign tubes or equivalents can be purchased from: Amperex Electronic Corp., 230 Duffy Avenue, Hicksville, New York and International Electronics-Mullard Corp., 81 Spring St., New York 12, New York.—Ed.

Sensitive Sensitivity

Editor, ELECTRONIC TECHNICIAN:

In November's article, "Replacing Components in Transistor Radios," second paragraph on page 46, Anthony Stern used sensitivity instead of selectivity. This made his paragraph incorrect. You see, the lower the sensitivity figure, the better the receiver and the greater its ability to bring in distant or weak stations. Mr. Stern used the word sensitivity in the opposite fashion. The word to make his paragraph correct is selectivity, not sensitivity. Se-

New TRANSISTOR RADIO ANALYST

makes it Easy and Profitable to Service all Transistor Radios



B&K Model 960

TRANSISTOR RADIO ANALYST


*with Exclusive DYNA-TRACE
Single-Point Probe—and Built-in
Metered Power Supply and VTVM*

**Complete Transistor Radio
Service Shop in One Instrument**

*Signal-Generator, Power Supply,
Milliammeter, VTVM, Battery Tester,
Ohmmeter, and Both In-Circuit and
Out-of-Circuit Transistor Tester—
All in One*

Check all circuits - Pinpoint any trouble ... in minutes

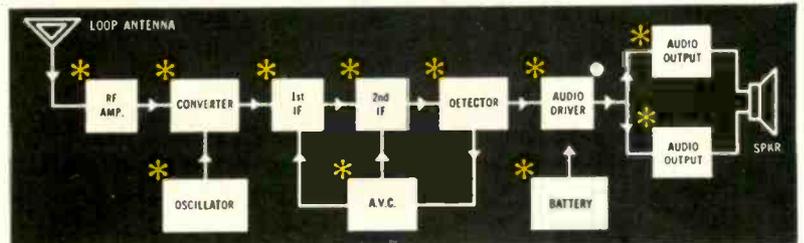Now you can profit from transistor radio servicing! This amazing new B&K "960" ANALYST gives you *everything* in one complete easy-to-use instrument. Makes transistor radio servicing *quick and easy*. Nothing else is needed except the transistor radios themselves waiting to be serviced. Brings you new customers for service, parts, and batteries. Makes this new business *yours*.



**EASILY TROUBLE-SHOOT ANY STAGE
BY UNIQUE POINT-TO-POINT SIGNAL INJECTION**

The ANALYST gives you a complete signal-generating source for point-to-point signal injection. Easily enables you to trouble-shoot any transistor radio—check all circuits stage-by-stage—isolate and pinpoint the exact trouble in minutes.

Supplies modulated signals, with adjustable control, to check r.f., i.f., converter, and detector. Supplies audio signal to check audio driver and audio output. Provides unmodulated signal to test local oscillator. Provides separate audio low-impedance output for signal injection into loudspeaker voice coils to check speaker performance.

BUILT-IN METERED POWER SUPPLY FOR EASY SERVICING

Makes it easy to operate radio under test, while you inject your own signals. Provides from 1 to 12 volts in 1½ volt steps. Supplies all bias taps that may be required.

**SIMPLIFIES IN-CIRCUIT TRANSISTOR TEST
WITH NEW DYNA-TRACE SINGLE-POINT PROBE**

Unique single-point probe needs only the one contact to transistor under test. No longer are three wires required to connect to emitter, base, and collector. Gives fast, positive meter indication. Saves time. Makes trouble-shooting simple and easy.

BUILT-IN VTVM

Includes high-input-impedance vacuum-tube voltmeter, which is so necessary for transistor radio servicing.

TESTS ALL TRANSISTORS OUT-OF-CIRCUIT

Meter has "Good-Bad" scale for *both* leakage and beta. Also has direct-reading Beta scale, calibrated 0-150. Assures quick, accurate test. Also automatically determines whether transistor is NPN or PNP. Meter is protected against accidental overload and burn-out.

Model 960. Net, **\$99⁹⁵**

Solve Every Service Problem and Profit with a Modern B&K Service Shop. See Your B&K Distributor or Write for Catalog AP18T



B & K MANUFACTURING CO.
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

--- for more details, circle 12 on page 50



Tarzian 400 and 600 volt F and H series units are available in handy Ten-Paks, in Doubler Replacement Kits, and in bulk; M150 and M500 units are available in Conversion Kits and in bulk. Nine standard tube replacement rectifiers replace over 95% of all popular

vacuum tube rectifiers; S5347 replaces 6BW4 or 12BW4 in Citizen's Band radios; your 50 to 500 ma requirements are covered by four "condensed stack" selenium rectifiers, which Sarkes Tarzian has made more efficient—and smaller—than before.

Sarkes Tarzian

...the preferred silicon rectifiers that mean fewer call-backs

■ Tarzian silicon rectifier dependability virtually eliminates call-backs that waste your time and profits. Units are available immediately from distributors throughout the country...in the shapes, sizes, and specifications you need to do your work quickly and easily.

Tarzian's industry-wide reputation for high quality at a pace-setting low price is a basic reason why more technicians like yourself prefer Sarkes Tarzian rectifiers than the next two most popular makes combined.

That statement is firmly based on the results of a 1961 mailing by Brand Name Survey, an independent research organization, to 23,000 service technicians in all major market areas of the United States, covering 36 states. You're in good company—and lots of it—when you make Tarzian rectifiers your first choice for replacement applications.

Free Tarzian "Distributor Line" catalog is available now as your guide to replacement rectifier quality. Ask your nearest Tarzian distributor for your copy.



SARKES TARZIAN, INC.

World's Leading Manufacturers of TV and FM Tuners • Closed Circuit TV Systems • Broadcast Equipment • Air Trimmers • FM Radios • Magnetic Recording Tape • Semiconductor Devices

SEMICONDUCTOR DIVISION • BLOOMINGTON, INDIANA

In Canada: 700 Weston Rd., Toronto 9 • Export: Ad Auriema, Inc., New York

... for more details, circle 45 on page 50

LETTERS TO THE EDITOR

lectivity is the ability of the receiver to bring in weak stations without interference.

DAVID CRUMPTON

Brooklyn, New York

• The author was referring to sensitivity, rather than sensitivity rating or figure. With a loss of sensitivity, the sensitivity rating increases (that is, more microvolts are required at the antenna). Incidentally, as the sensitivity loss becomes greater, the band pass peak is lower, thereby broadening the response curve and affecting the selectivity. Just keep in mind that the more sensitive a receiver is, the lower its sensitivity rating.—Ed.

Manufacturer Address

Editor, ELECTRONIC TECHNICIAN:

Can you give me the name of the manufacturer of the Seco VT Grid Circuit Tester?

• The address is Seco Electronics, Inc., 5015 Penn Avenue South, Minneapolis 19, Minn. All manufacturer addresses are listed in the annual May Directory issue.—Ed.

Evaluating UHF

Editor, ELECTRONIC TECHNICIAN:

I cannot help commenting on your editorial in the December issue of ET concerning the FCC and UHF television. For several years in New Orleans we were in the position of having two nearby UHF stations, Channel 61, which later changed to Channel 20, then finally to Channel 13. This gave us, and other TV servicemen quite an opportunity of evaluating UHF versus VHF in both communities.

Personally, in the immediate service area (20 odd miles) I consistently found UHF vastly superior to VHF TV if two important considerations were taken into account. First, the TV receiver which was mainly a matter of which manufacturer and secondly, the antenna.

It would seem to me that if the FCC makes the drastic decision to return UHF to the American public, this is a step in the right direction, provided that the industry maintain proper engineering. The failure of UHF lay primarily in the lack of public acceptance, which was due to faulty engineering of the products. Of course, the service technician got the blunt of the blame.

Being a radio engineer and physicist myself, I was able to evaluate the products. Some manufacturers would show a good picture and good sound with as little as 50 microvolts of signal from an indoor antenna. Other sets would re-

Continued on page 16

TESTS
All TV and Radio
Tubes—Old and New

TESTS
the Nuvistors

TESTS
the New 12-Pin
Compactrons

TESTS
the New 10-Pin Tubes

TESTS
for True Dynamic
Mutual Conductance (Gm)

TESTS
European Hi-Fi Tubes,
Voltage Regulators, and
Most Industrial Types

**OBSOLESCENCE
PROOF**
Designed for Maximum
Use Today and
Tomorrow



**NEWEST
FINEST
MONEY-MAKER**
*for Professional
Servicemen*

Multiple-Socket Speed

with Gm Accuracy PLUS OBSOLESCENCE PROTECTION

Model 700 DYNA-QUIK

*Fastest, Most Complete
Most Up-to-Date*

DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

*See your B&K Distributor,
or Write for Catalog AP18-T*

TESTS BOTH OLD AND NEW TUBE TYPES—SELLS MORE TUBES PER CALL
Again you benefit from proved B&K techniques! This up-to-date, obsolescence-proof, professional instrument is designed for maximum use today and tomorrow. Provides multiple-socket section to quick-check most of the TV and radio tube types the true dynamic mutual conductance way—plus simplified switch section to check new tube types in Dyna-Quik emission circuit. Also includes provision for future new sockets.

Makes test under set-operating conditions. Checks each section of multi-section tubes separately. Checks for all shorts, grid emission, leakage and gas. Makes quick "life" test. Exclusive adjustable grid emission test provides sensitivity to over 100 megohms.

Makes complete tube test in seconds. Checks average set in a few minutes. Discovers weak tubes that need replacement. Satisfies more customers. Saves call-backs. Insures your reputation.

Patented automatic compensation for line voltage variation. Large 4½" plastic meter with easy-to-read "Replace-Good" scale. Lists most commonly used tube types with settings directly on socket panel for fastest operation. Complete listing in reference chart in cover. Phosphor-bronze contacts for long life. 7, 9, and 10-pin straighteners on panel. Operates on 117 volts 50-60 cycle a.c. Handsome leatherette-covered carrying case.
Size: 16½" x 15¼" x 5½" deep. Net wt: 15½ lbs. Net, \$169⁹⁵

NEW TUBE INFORMATION SERVICE
Available every 3 months, on subscription,
for all B&K Dyna-Quik Tube Testers



B & K MANUFACTURING CO.
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

--- for more details, circle 13 on page 50

TUNING IN

CUSTOMERS NO LONGER PAY for removal and re-installation of Motorola car radios during the one year warranty, said C. J. "Red" Gentry, Car Radio Sales Manager in introducing their new line. In the past customers have had to pay if the set needed to be removed for repair during the warranty period. This expense will now be borne by the factory, according to Gentry, thus freeing dealers and distributors from this expense.

COLOR TV studies are continuing at Westinghouse, but the company has no firm plans for marketing a color receiver during 1962, according to O. H. Yoxsimer, TV-radio division general manager. He said they believe color TV is an increasing factor in TV receiver sales, probably accounting for three percent of total 1961 TV receiver sales.

TV RECEIVER factory sales for 1962 are expected to rise by more than 300,000 units over the total sold

COLOR CRT PRODUCTION



Solder application machine helps accelerate production of color CRT's at RCA's \$10 million Lancaster, Pa. plant, where \$1.5 million expansion program is underway to meet anticipated 250% increase in 1962 demand. The machine spreads a thin ribbon of special glass-sealing solder to the edge of a 21-inch type CRT envelope while it is rotating.



"Yes, we can give you terms. How about 27 dollars down and 25 cents a month for the next two months?"


in 1961, and sales of radio sets and phonographs may remain at about the same levels as last year, according to estimates released by EIA. Estimates for 1962: TV Receivers, 6,201,000; Radio, 11,463,000; Phonographs, 3,915,000. Although firm statistics for 1961 factory sales are not yet available, EIA estimates totals as: TV Receivers, 5,900,000; Radio, 11,500,000; Phonographs, 3,900,000.

ONE-GUN COLOR CRT by Paramount Pictures Corp. under consideration by domestic and foreign TV set manufacturers. Sony Corp. of Japan has just been licensed and will be the first to make and use the tube for entertainment purposes.

THREE OUNCE RADIO, reportedly world's smallest seven-transistor receiver, is made by Standard Radio Corp. of Tokyo. The "Micronic Ruby" measures 1-9/10 inches by 1-7/10 inches by 8/10 inches, about the size of a flameproof pocket cigarette lighter. Retail at about \$22 in Japan and will be introduced in the United States this spring.

AUDIOPHILES BECOME HAMS. "It's no secret that amateur radio operators were among the earliest


THE PICTURE

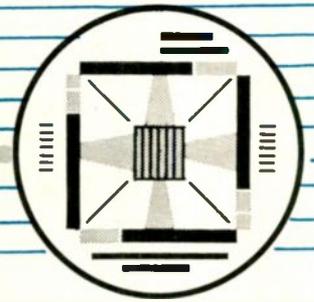

hi-fi fans," says Bill Colbert, president of Audio Exchange Stores, Inc., a New York hi-fi sale chain. "Today, the average Ham is bound to be interested in hi-fi and every hi-fi enthusiast is a potential Ham. It's come the full circle." The firm has, therefore, developed a unique "4-Way Trade-In" system for trading equipment: hi-fi for Ham; Ham for hi-fi; Ham for Ham; and hi-fi for hi-fi.

"COMPACTRON" TRADEMARK ABANDONED by the General Electric Co. The trademark, as applied to multi-function electronic devices, is now in the public domain. L. Berkley Davis, vice president and general manager of G-E's electronic components division, said the general acceptance and use of the term by the public has caused its loss of distinctiveness as an indication of origin of goods. He said he anticipates

FOGHORN FOR BLIND

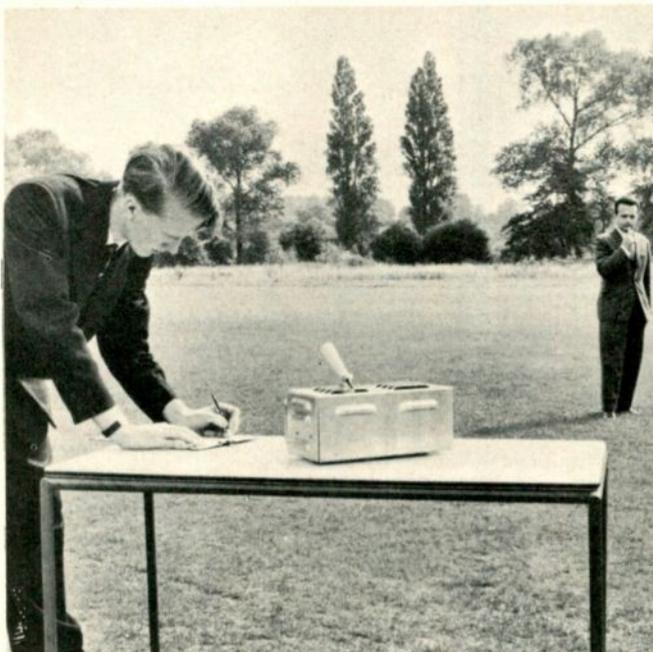

A "foghorn for the blind," has been developed by Standard Telephones and Cables Ltd., ITT British affiliate. Sound from a special, transistorized, high-frequency dog whistle, blown by the blind person, is selectively picked up by a microphone on the device and causes a self-contained bell to sound. The direction and intensity of the bell's sound enables the blind person to estimate his position in relation to the known location of the device. The range of the device is about 60 yards.

CALENDAR OF COMING EVENTS


- Mar. 20-25: 1962 Los Angeles High Fidelity Music Show, Institute of High Fidelity Manufacturers, Inc. (IHFM) Ambassador Hotel, Los Angeles, Calif.
- Mar. 21-23: 9th Annual Spring Convention and Technical Sessions, Audio Engineering Society, Ambassador Hotel, Los Angeles, Calif.
- Mar. 26-29: IRE International Convention, Coliseum and Waldorf-Astoria Hotel, New York, N. Y.
- Mar. 28-31: 11th biennial Electrical Industry Show and Conference. Electrical Maintenance Engineers Association of Calif. Shrine Exposition Hall, Los Angeles, Calif.
- Apr. 1-4: Annual Convention, National Association of Broadcasters, Conrad Hilton Hotel, Chicago, Ill.
- Apr. 11-13: S. W. IRE Conference and Electronics Show, (SWIRECO) Rice Hotel, Houston, Texas
- Apr. 29-30: 91st Convention, the Society of Motion Picture and Television Engineers, Ambassador Hotel, Los Angeles, Calif.
- May 21-24: 1962 Electronic Parts Distributors Show, Conrad Hilton Hotel, Chicago, Ill.

that other manufacturing companies, making compactrons, will continue to join G-E in using this term as a common generic term to designate these multi-function devices.

HARASSING NOISE in his home, complained Schenectady suburbanite Eugene Binkowski, in a letter to President Kennedy. Investigating technicians, from the Griffiss Air Force Base, told Mrs. Binkowski that her family's hearing is so acute it picks up high-pitched sounds others do not hear. A hearing test given a six-year old son shows that he hears sounds in the 20,000-21,000 cps range, twice the normal hearing range for high-pitched sounds. Mrs. Binkowski said one of the technicians told her the house is in the midst of a hot-bed of electro-magnetic radiation. Transmission towers of three radio stations are within sight of the house.

EMOTIONAL OUTLET FOR SMALL FRY . . . Shooting darts at moving characters on the TV screen! Patented recently, a dart game for children consists of a transparent target, which fastens over the face of a TV set, and darts with rubber suction cups. Its purpose is to provide a means for children to discharge psychic energy stimulated to highly emotional levels by TV programs.

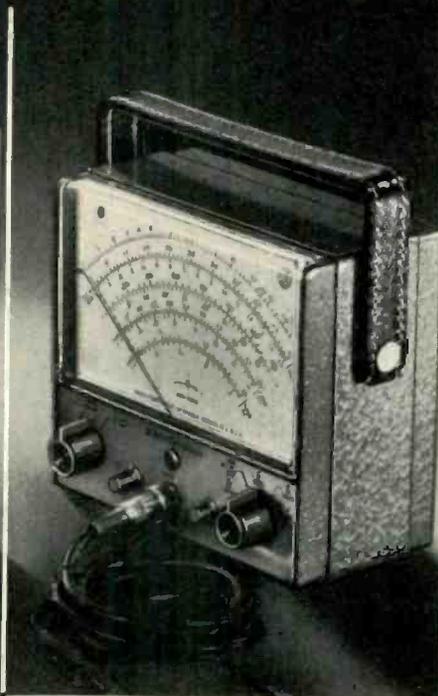Now with New Features For Added Versatility



RCA WO-91A 5-INCH OSCILLOSCOPE

New 2-Stage Sync Separator Simplifies Checking TV Horizontal and Vertical Sweep Synchronization

This popular RCA 5-inch scope now at your distributor's includes a new feature to simplify TV servicing: a built-in two-stage sync separator. This circuit, connected in the preset TV "H" and "V" positions, provides exceptionally solid lock-in action on composite TV signals.

Other "PLUS" Features:

- 5-inch screen with high resolution
- Dual bandwidth (4.5 Mc with 0.053 volt rms/in. sensitivity; 1.5 Mc with 0.018 volt rms/in. sensitivity)
- Internal calibrating voltage and calibrated graph screen
- Includes special direct/low capacitance shielded probe and cable

\$249⁵⁰*

factory-wired and calibrated

**SEE THEM BOTH AT YOUR AUTHORIZED
RCA TEST EQUIPMENT DISTRIBUTOR.**

*User Price (Optional)

RCA WV-98C SENIOR VOLTOHMYST®

New 0.5 Volt Full-Scale DC Range for Testing Transistor Circuits

Now you can check the low voltages used in transistor circuits even more accurately with the latest model of the famous RCA Senior VoltOhmyst.

The new "C" version of this time-tested instrument includes a high-sensitivity range that provides full-scale deflection at only one-half volt DC!

Other "PLUS" Features:

- Easy-to-read 6½" meter face
- 200- μ a meter movement with less than 1% tracking error
- Precision multiplier resistors accurate to 1%
- Meter electronically protected against burnout
- Separate color-coded peak-to-peak and rms voltage scales
- Die-cast aluminum case with leather carrying handle

MEASURES:

DC volts, 0.02 to 1500 volts
AC volts, 0.1 to 1500 volts rms or 0.2 to 4200 volts peak-to-peak
Resistance, 0.2 ohm to 1000 megohms

\$79⁵⁰*

factory-wired and calibrated

RCA ELECTRON TUBE DIVISION, HARRISON, N.J.



The Most Trusted Name in Electronics

LETTERS

TO THE EDITOR

Continued from page 12

quire 300 to 1000 microvolts from a good outside antenna and still get a bad picture, with inadequate sound.

One of the primary failures of sets were the older 21-26 mc i-f, where adaption to UHF reception was done by strips. These strips contained an oscillator section often obtaining the IF by beating the incoming UHF signal against the third, fourth, or even fifth harmonic of the oscillator. These almost never gave a proper picture without the best of antennas. These sets were more often better treated with a converter on an unused VHF channel.

I have measured some "directional" UHF antennas, to find that the ratio between signal strength with the antenna in the advantageous position, versus the signal strength with the antenna rotated to the least advantageous position was something like 300 microvolts to 298 microvolts, hardly a directional beam at all. One of the problems concerning UHF antennas was the flagrant use of aluminum, which is one of the worst materials manufactured for antennas in the world. The velocity of radio waves (in the UHF region) in aluminum is very poor compared with copper.

I join you with your wish that the FCC has good luck with this venture, but I differ with you since I believe the real reason for failure of this medium lies with industry.

CHARLES R. MADUELL, JR.

Delta Electronics
New Orleans, La.

Rewiring Multiplex Adaptors

Editor, ELECTRONIC TECHNICIAN

We are writing a few lines commending you for the splendid job being done by you and your staff in explaining the new multiplex system for keeping us posted on all new developments in the TV field. We have had several calls from owners on multiplex adaptors which were bought before FCC adopted the Zenith-GE method—as you know these adaptors were made for the Crosby system. We would like to know, is there a way to convert these without too much expense, and is it legal?

FRANK CERRONE

State-Television-Service
Valley Stream, N. Y.

• It's perfectly legal to redesign receiving equipment. However, it would be a tricky, time consuming job to rewire your adapter. It may be less trouble in the long run to interest the customer in a new unit. — Ed.

**MORE SERVICEMEN
USE CLAROSTAT
WIRE-WOUND CONTROLS
THAN ALL OTHERS
COMBINED BECAUSE...**



It's a fact . . . More Clarostat wire-wound controls are used by servicemen than all others combined! For over forty years the built-in quality of Clarostat wire-wound controls has proved itself to the satisfaction of servicemen and their customers alike.

Join the crowd. When you need a wire-wound control replacement, insist on Clarostat in the green box—your assurance that you're getting the control that works best.

**QUALITY
COMES
FIRST
WITH**

- ★ Series A43 and A43S 2-watt controls. With or without switch. Pick-A-Shaft convenience.
- ★ Series A58 and A58S 3-watt controls. With or without switch. Pick-A-Shaft convenience.
- ★ Series A10 and A10S 4-watt controls. With or without switch. Pick-A-Shaft convenience.
- ★ Series 39 2-watt "Humdinger" for screwdriver adjustment.

DISTRIBUTOR SALES DIVISION



CLAROSTAT

CLAROSTAT MFG. CO., INC. DOVER, NEW HAMPSHIRE


--- for more details, circle 19 on page 50

TV MANUFACTURERS TECHNICAL DIGEST

GENERAL ELECTRIC

TV Chassis MW—Correcting UHF Tuning Problem

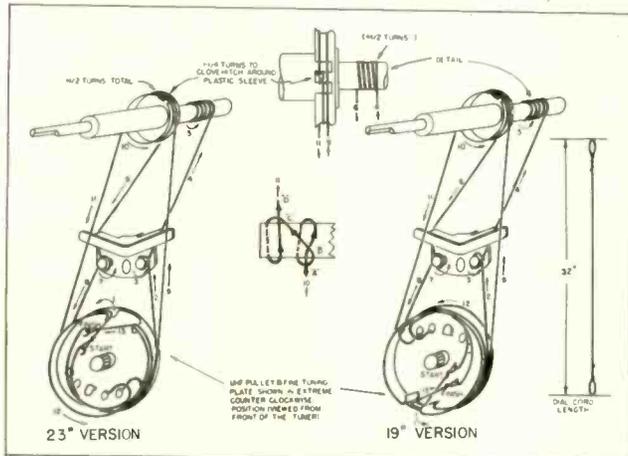If fine tuning of the UHF on "MW" receivers becomes difficult, the problem may be caused by the dial cord slipping on the fine tuning plate. The direct



UHF tuning problems in General Electric "MW" TV chassis caused by dial cord slipping on fine tuning plate, can be cured by revisions.

drive operation will perform normally, but the fine vernier tuning is affected.

This condition can be cured by restringing the assembly to provide more tension on the fine tuning plate. This revision also requires the addition of a tension spring to the UHF pulley, identical to the one already used, and employment of a slightly longer dial cord.

Note the position of the two springs on the UHF pulley, one for start and the other for finish, placing tension at each end of the dial string. Note that the springs are placed in separate holes in the pulley. Correct looping of the dial string around the ears on the fine tuning plate is important. This provides the necessary drag-increase on the fine tuning plate. Both the 19 in. models and the 23 in. set require the same length of dial cording. However, placement of the opening in the pulley in the start position differs.

MAGNAVOX

TV Chassis 38 Series—Production Changes

The following changes have been made in production to improve Magnalux circuit operation:

1. The 180K resistor (R529) in series with the brightness control has been changed to 150K, 5% tolerance.

2. The 47K resistor (R528) connected across the series combination of the LDR and the 3.3K resistor has been changed to 33K, 2W.

3. The 150K, 10% resistor (R530) in the CRT cathode has been changed to 150K, 5% tolerance.


4. Note that the schematic diagrams on pages 5 and 6 of Manual 7248 are incorrectly identified in the heading. Should read "38" instead of "36."

5. R526 is incorrectly shown on the schematic as 3.3, instead of 3.3K.

MOTOROLA

TV Chassis TS 581 Series—Removing Coil Shields

The shielded coils in this series are locked in position inside the shield. To gain access to the coil and components located within the shield, the shield must be separated from the coil form as illustrated. If coil form and shield do not separate easily, more pressure must be exerted at the sides of the shield in order to release the tabs of the coil form. Reshape shield before replacing coil. Be sure coil form locks into position

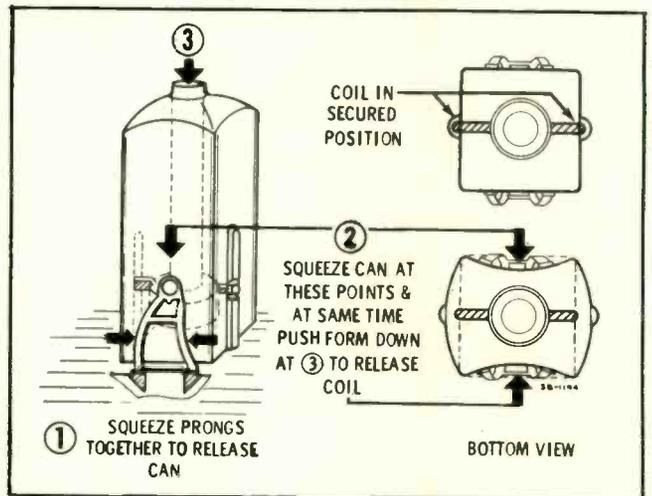

Coil shields in Motorola TS 581 series chassis can be removed for coil component replacement by following the steps outlined here.

inside the shield and that the shield prongs lock into the chassis. Coils which are dipped in wax must be replaced as an assembly to maintain proper moisture protection in high humidity areas.

PACKARD BELL

TV Combination Chassis Model 23DK2 — Separate Radio Operation & Production Changes

The radio section of this combination can be op-

This Service-Dealer is making a **\$940** profit
 in 7 minutes installing a **JFD EXACT REPLACEMENT TV ANTENNA** for a
PORTABLE TV

The Place: Any radio-TV service shop

The Time: Any working hour

The Product: Two JFD Exact Replacement No. TA386 Antennas—one of 74 different O.E.M. portable TV set antennas now in stock at your JFD distributor.

The Facts: portable TV with two broken TA386 antennas that need replacement:

Actual Selling Price (2 @ \$4.25 ea.)	\$8.50
Dealer Cost (40% off) (2 @ \$2.55 ea.)	5.10
Profit on Sale	3.40
Charge for Installation	6.00
Total Profit		\$9.40



Result: The service-dealer makes and keeps a handsome profit—the customer gets the antenna that is the precise electrical and mechanical mate for his portable TV.

No wonder more service-dealers are earning more money by selling and installing JFD Exact Replacements!

Remember, next to receiving tubes, portable and tote-able set antennas require the most frequent replacement. Makes sense, doesn't it, to call your distributor for your JFD Exact Replacement Profit Plan.

FREE SALES AIDS!

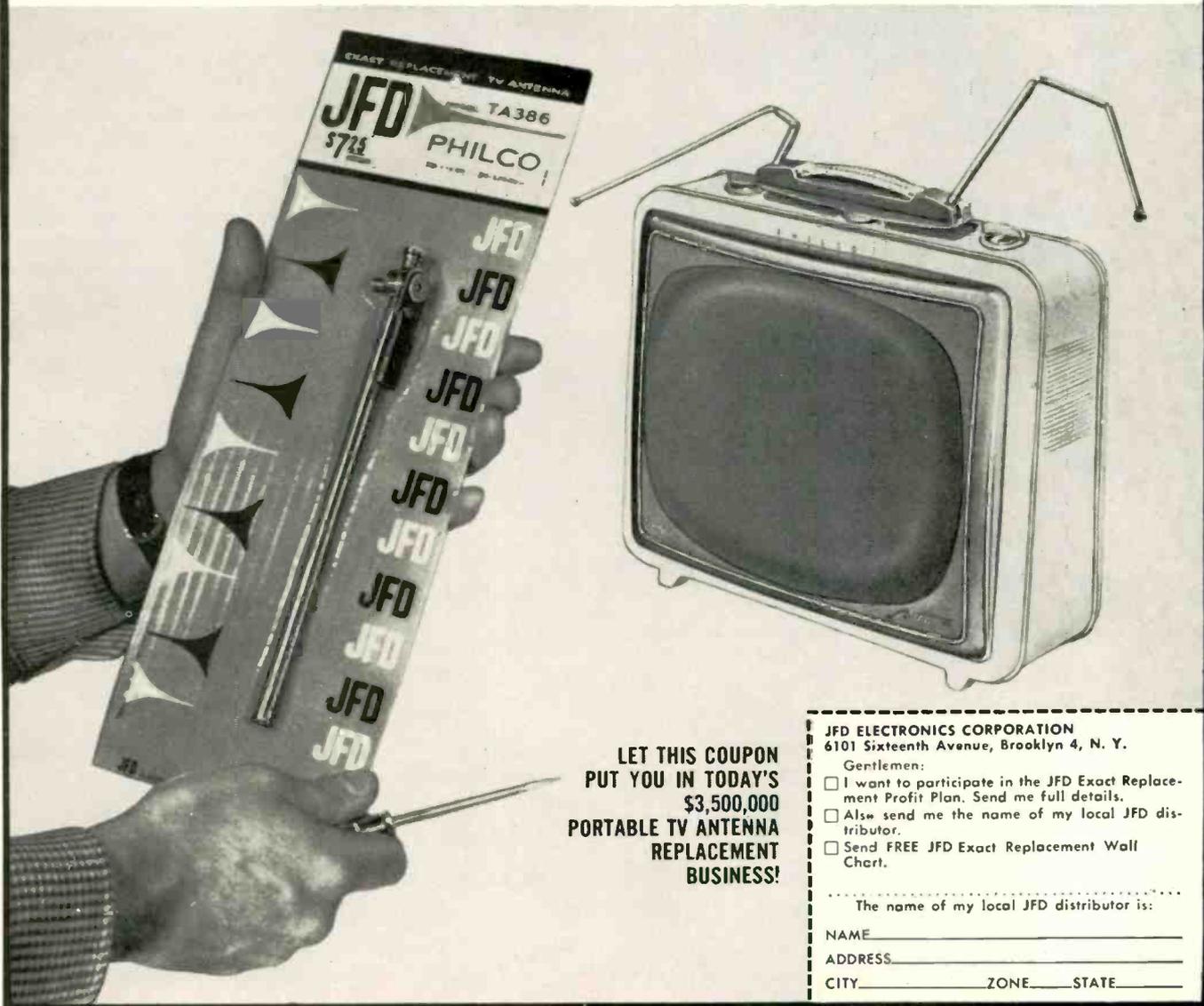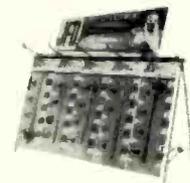Merchandisers, displays, kits, reference guides, streamers, direct mail, listings in Sams Photofact folders help you sell, sell, sell!



**LET THIS COUPON
 PUT YOU IN TODAY'S
 \$3,500,000
 PORTABLE TV ANTENNA
 REPLACEMENT
 BUSINESS!**

JFD ELECTRONICS CORPORATION
 6101 Sixteenth Avenue, Brooklyn 4, N. Y.

- Gentlemen:
- I want to participate in the JFD Exact Replacement Profit Plan. Send me full details.
 - Also send me the name of my local JFD distributor.
 - Send FREE JFD Exact Replacement Wall Chart.

.....
 The name of my local JFD distributor is: _____
 NAME _____
 ADDRESS _____
 CITY _____ ZONE _____ STATE _____

... for more details, circle 31 on page 50

...nothing cheap
but the price!

Compare performance, filtering, quality, output



New DC Power Supplies

Guaranteed 1 Year

They'll sell you on sight. Never before has so much value and performance been packed into a completely assembled power supply.

Auto radio... Use EC-2 for all servicing needs. Use EC-1 for "warm-up" and "check-out" or as low cost power source for FM and AM demonstrations.

Transistor portable servicing... Ideal as a hum-free DC voltage source.

Research and development work... Reliable performance for wide application in industry and laboratory.

	EC-2	EC-1
DC VOLTAGE OUTPUT	0-16 VDC continuously adjustable	12 VDC (adjustable)
AMPERAGE OUTPUT	0-5 ADC	0-5 ADC
RIPPLE	0.5% at 5A	0.5% at 5A
REGULATION	1.8 V/A	1.4 V/A
METER	0-20 V/O - 10A
DC IMPEDANCE	1.8 ohms	1.4 ohms
PANEL FEATURES	On-off switch, pilot light, meter function switch, variable voltage control, insulated binding posts, fuse, 6' cord.	4-position voltage adjustment switch, pilot light, wing nut output terminals. 6' cord.



Save bench space. Only 10 3/4" x 4 3/4" x 6 1/2". Use vertically or horizontally.

Write for Complete Line Catalog PS-561

Available Now at
Your Electronic
Distributor.



ELECTRO PRODUCTS LABORATORIES

4501-V Ravenswood, Chicago 40, Ill.
LONgbeach 1-1707

Canada: Atlas Radio Ltd., Toronto

Since 1936... Pioneers in Low Voltage DC Power Supplies

... for more details, circle 22 on page 50

TV MANUFACTURERS TECHNICAL DIGEST

erated without the TV section by inserting the a-c cord from the DPA-30 amplifier into an a-c outlet. Operation may be desired while the TV chassis is out for repair. This connection will bypass the a-c switch on the tuner panel, and the radio section power will be on as soon as the cord is plugged in. The plug is removed from the wall outlet to turn the set off.

The TV can be operated without the tuner chassis. Pins 2 and 3 (ccw, top view) of the 7-pin socket must be shorted together. This can be done with a 7-pin adapter plug. The socket is located at the top right corner of the chassis. Be sure the remote control cable is plugged in (two plugs) before connecting the a-c cord to the wall a-c outlet.

In some sets the two resistors, R-430 and R-431, across the loudness and balance controls, are 180K ohms instead of 150K. Change to 150K if excessive rumble is encountered.

If additional sensitivity is needed for AM reception the detector diode 1N295A should be replaced with a 1N541 diode (PB-72089). This change will be made in tuners stamped 3325 or higher. Capacitors C-204 and C-205 in tuner 8TU4 were changed from 68 pf to 150 pf (23942) to decrease tendency to oscillate. Changes will be made in chassis stamped 3353 or higher.

Two resistors, R-401.1 and R-401.2, were added in the Gorler f-m tuner as a production modification to prevent drift. R-401.1 is 500K ohms, 3/4 watt, with a negative temperature coefficient, part number 73785 (special), while R-401.2 is a standard 4700 ohms, 1/2 watt resistor.

PHILCO

TV Chassis 12N50 Series—Production changes

1. Run 2. Transformer T5 was changed from part No. 32-4745-2 to part No. 32-4745-4, to improve sound sensitivity.

2. Run 3. Capacitor C38 was changed from .02 μ f to .01 μ f, part No. 30-1262-53, to reduce drive lines.

3. Run 4. Resistor R57A was changed from 4.7 megohm to 5.6 megohm, part No. 66-5568340, to improve interference rejection. Resistor R-19 was changed from 470 ohms to 560 ohms, part No. 66-1564350, to center vertical linearity control.


4. Run 5. A four inch piece of vinyl tape was added to the 1G3 high voltage rectifier tube cap to prevent corona.

WESTINGHOUSE

TV Models With "Mobile-Sound"—Circuit Operation

A system employing an amplitude modulated r-f transistor oscillator rebroadcasts TV sound so that it can be received on any a-m radio, while the TV speaker remains silent. Sound level can be adjusted by the radio's volume control. The oscillator is attached

Another outstanding development by the makers of BUSS Fuses

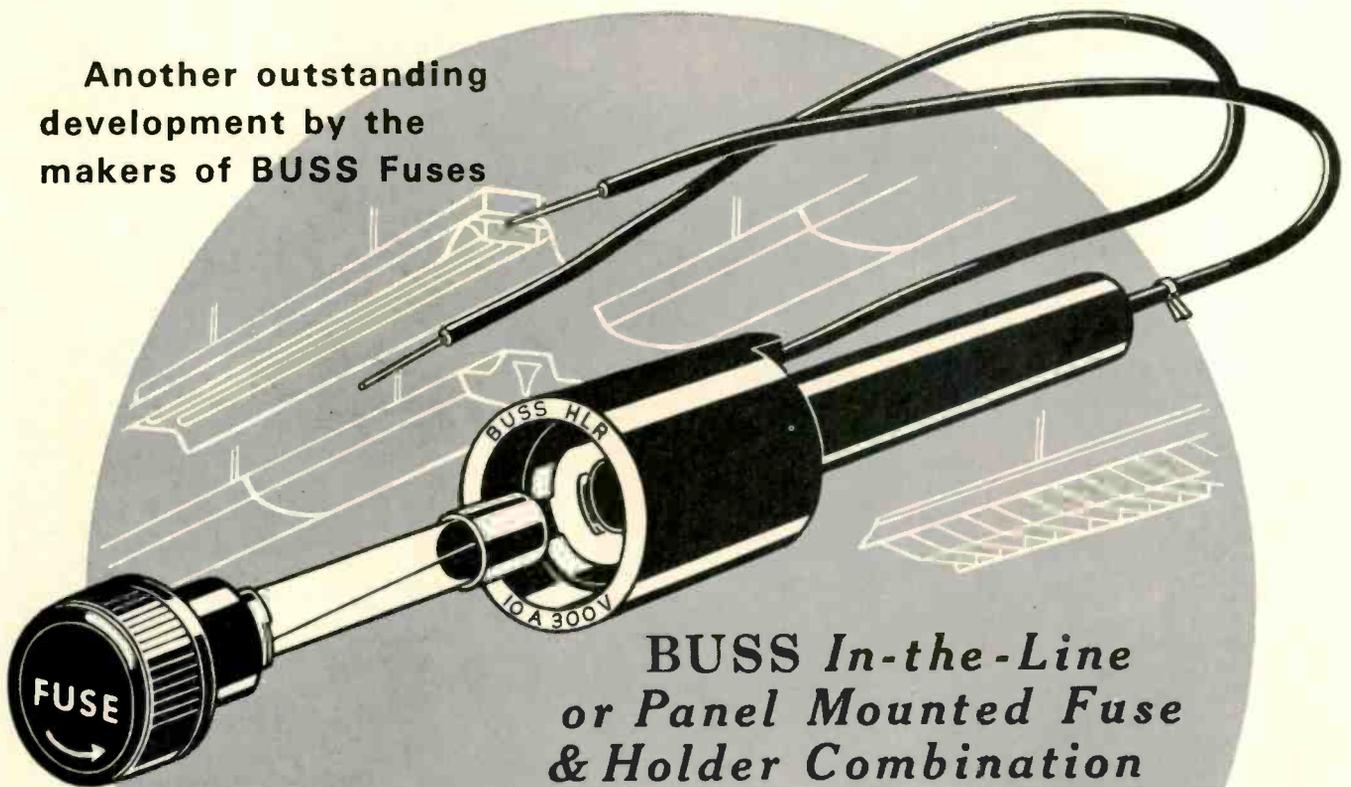

BUSS In-the-Line or Panel Mounted Fuse & Holder Combination

HLR Holder for GLR and GMF Fuse

For the Protection of Fluorescent Fixtures or Other Equipment . . . 300 Volts or less

These BUSS Fuse & Holder combinations make it especially simple to protect fluorescent fixtures. They are also being used in a wide variety of other applications to protect any device or equipment on circuits of 300 volts or less.

BUSS GLR *fast-acting* type fuses or BUSS GMF *slow-blowing* type fuses are used in combination with BUSS HLR fuseholders. Fuseholder can be installed in-the-line or panel mounted.

Fuse and knob of fuseholder are in one piece. When a fuse blows, the entire fuse knob assembly is replaced. Cap of holder is insulated to protect user against possibility of shock.

Why safety demands that fluorescent fixtures be protected.

Trouble in fluorescent fixtures generally starts when the insulation in the ballast breaks down. This causes a short which develops heat, and can result in:

Molten compound dripping on people, equipment and merchandise . . . Gases forming and exploding, injuring personnel or damaging stock and equipment . . . Fires starting in ceiling or walls near fixture . . . Short continuing until branch circuit fuse blows and cuts off all lights on circuit.

All these dangers can be minimized by proper BUSS GLR or GMF fuse protection.

To get the full story, write for BUSS bulletin SFH-6.

BUSS—The complete line of fuses & mountings of unquestioned high quality



BUSSMANN MFG. DIVISION
McGraw-Edison Co.
ST. LOUIS 7, MO.

--- for more details, circle 15 on page 50

ADD A NEW SIGN TO YOUR DOOR



Let RCA Train You at Home in COMMUNICATIONS

A completely new RCA Institutes course with brand new opportunities for electronic technicians . . . COMMUNICATIONS ELECTRONICS.

1962 starts a new era in mobile communications when you get your FCC License. Under the skilled direction of RCA Institutes experts, you can obtain at home the technical qualifications for employment in the Communications Industry. In addition to preparing you for an FCC license, you are supplied with the training needed to service and maintain 2-way radio communications for truck and taxi fleets, police, fire, bus, railroad and other public service vehicles. You also get the technical foundation for advancement in space and aviation communication electronics. This is *not* a cram course . . . *not* a rehash of old radio lessons. Learn from RCA what it takes to get ahead in the ever-expanding field of communications.

With RCA Institutes home training in Communications Electronics, you set the pace that suits your ability, finances and time. RCA's liberal Voluntary Tuition Plan is the most economical home study method, because you pay for lessons only if you order them . . . one study group at a time! If you drop out at any time, for any reason, you do not owe RCA one penny! No other obligations! Licensed by New York State Education Department. Approved for Veterans.

Prepares You for an FCC License

RCA INSTITUTES, INC.

A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.

Other home study courses available:

Electronics Fundamentals
Black & White and Color TV
Automation Electronics
Computer Programming
Transistors



The Most Trusted Name
in Electronics

RCA INSTITUTES, INC. Home Study School, Dept. ET-32
350 West Fourth Street, N. Y. 14, N. Y.

Without obligation, rush me the FREE 64-page illustrated booklet "Your Career in Electronics" describing your electronic home study training program. No salesman will call.

Name.....Age.....

Address.....


City.....Zone.....State.....

CANADIANS—Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to: RCA Victor Company, Ltd., 5581 Royalmount Ave., Montreal 9, Quebec.

TV MANUFACTURERS TECHNICAL DIGEST

to the inside cabinet base. A plastic shaft, projecting through the TV's rear cover, is attached to a tuning capacitor (C-6) which is adjusted by the customer so that the TV sound is received at a remote point on one or more a-m radio sets. The TV sound is tuned in at a spot on the radio dial where no station is transmitting.

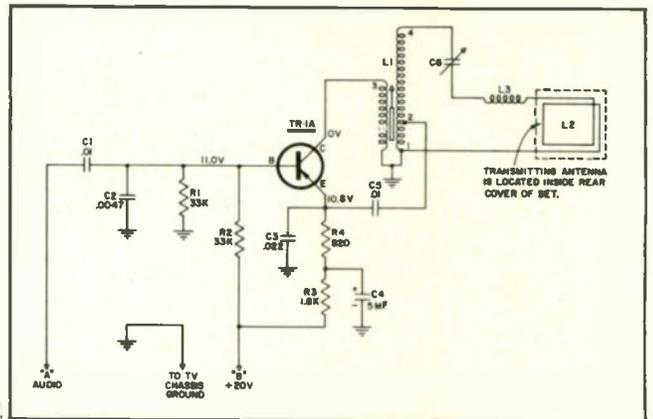The oscillator circuit consists of TR-1A; the primary of L1, C6, L3 and transmitting antenna L2; feedback capacitor C5; and C2—for r-f ground. It operates as follows: TR-1A is cut off during most of each cycle by the reverse bias that exists between its base and emitter. However, when the positive feedback, coupled to the emitter through C5, becomes suf-



Circuit of Westinghouse transistorized "Mobile-Sound" transmitter is amplitude modulated by a TV set's audio signal. Unit "transmits" the TV set's sound to any nearby a-m broadcast receiver.

ficiently positive, the instantaneous emitter voltage will rise above the base voltage. TR-1A is now forward biased for an instant. The transistor operates Class C—beyond cut off—but is driven into conduction during each cycle.

A +20 volt source, tapped from the TV set's audio output tube cathode is supplied to TR-1A through a stepping relay. This voltage is divided by R2 and R1 to provide the proper base voltage, and by R3, R4 and TR-1A to provide emitter voltage. The collector is at zero volts since there is no appreciable d-c drop across the primary of L1.

The audio signal is supplied to TR-1A through points on the stepping relay. It is then coupled through C1 and placed across the transistor's base and emitter. This audio signal varies the base to emitter bias, causing collector current to vary at an audio rate.


The collector current flowing in the primary of L1 causes a similar current to flow through its secondary and also L2, the transmitting antenna. Thus a modulated r-f carrier is transmitted.

L3 is used to suppress harmonics which could cause tweet interference; C4 drops the bass level slightly to compensate for a small loss of treble through C2; C3 equalizes the amount of oscillator output over the tuning range of C6.

The "transmitter" has been built to comply with FCC regulations and should not be modified.

Tarzian offers

FAST, DEPENDABLE TUNER REPAIR SERVICE

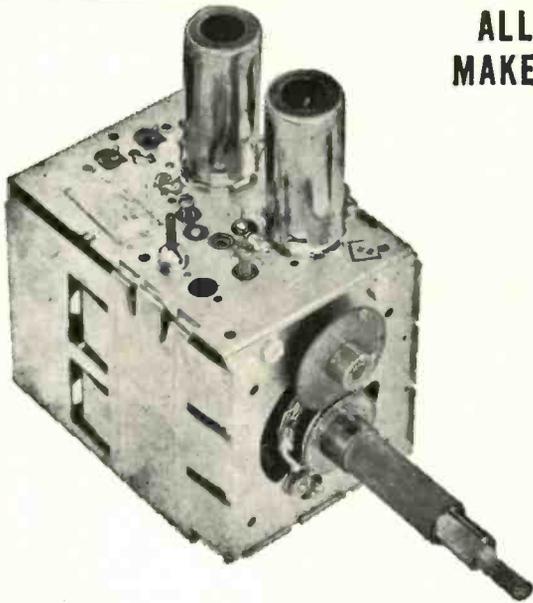

ALL
MAKES

It just makes sense that a manufacturer of tuners should be better-qualified, better-equipped to offer the most dependable tuner repair and overhaul service.

Sarkes Tarzian, Inc., pioneer in the tuner business, maintains a complete, well-equipped Factory Service Dept.—assisted by Engineering personnel—and staffed by specialized technicians who handle **ONLY** tuner repairs . . . on **ALL** makes and models.

Tarzian-made tuners received one day will be fixed and shipped out the next. Cost is only \$8.50 and \$15 for UV combinations. That includes **ALL** parts (except tubes which are furnished at our cost) and labor, and a 6-month guarantee against defective workmanship and parts failure due to normal usage. Replacements available at low cost on tuners beyond practical repair.

Tarzian-made tuners are identified by this stamping. When inquiring about service on other tuners, always give tube complement . . . shaft length . . . filament . . . voltage . . . series or shunt heater . . . IF frequency . . . chassis identification. All tuners repaired on approved, open accounts. Check with your local distributor for Sarkes Tarzian replacement tuners, replacement parts, or repair service.

SERVICE MANAGER • TUNER DIVISION • DEPT. 3A



SARKES TARZIAN INC

east hillside drive • bloomington, indiana
edison 2-7251

MANUFACTURERS OF TUNERS . . . SEMICONDUCTORS . . . AIR TRIMMERS . . . FM RADIOS . . . AM-FM RADIOS . . . AUDIO TAPE . . . BROADCAST EQUIPMENT and SHISH-KABOB GRILLES

ONLY

\$8.50

INCLUDING


ALL PARTS and LABOR

24-HOUR SERVICE 6-MONTH WARRANTY

Tuners Repaired on Approved, Open Accounts

See your distributor, or
use this address for fast,
factory repair service

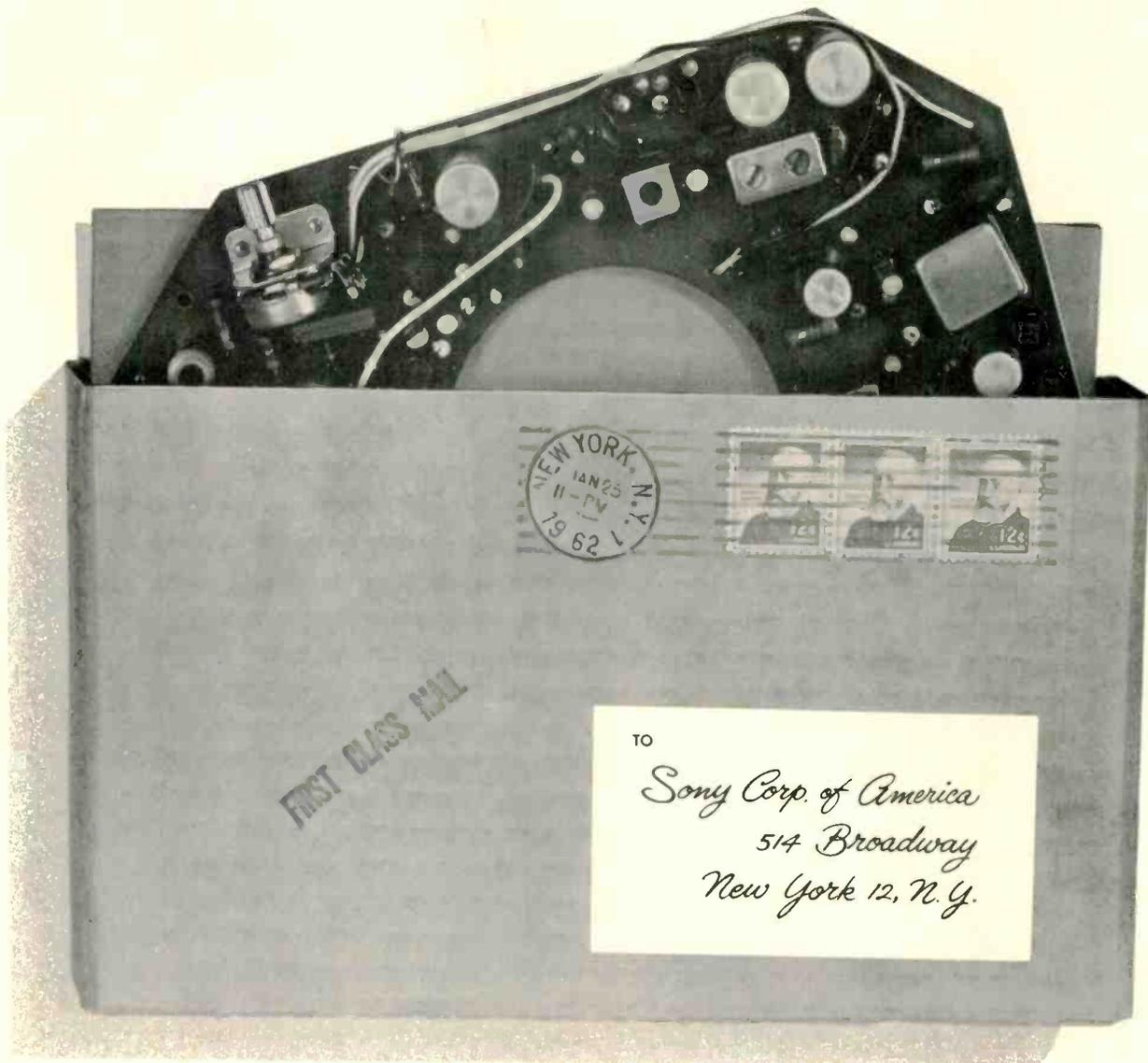
--- for more details, circle 44 on page 50



easiest way to service a TV!

SONY® *Research makes the Difference*

Put it in the mail, and we'll take it from there. Not the whole SONY 8-301W TV, of course. That wouldn't be very economical, despite its truly portable weight of only 13¼ lbs. No, just the printed circuit board, one of the three on which all 23 transistors and nearly every other component is mounted to make service an absolute cinch. No need to worry about stocking parts with SONY TV. Just isolate the faulty component, snap out the board and ship it off to us. In amazingly little time you'll have it back, good as new, and at surprisingly reasonable cost. Just another reason the SONY 8-301W TV, \$249.95 list, is a pleasure to sell—and service. *Battery Pack Optional.*

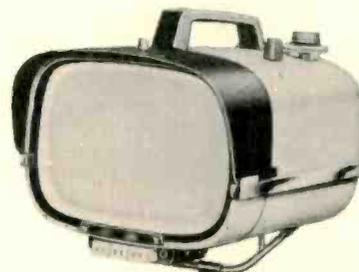

SONY CORP. OF AMERICA

514 Broadway, New York 12, N. Y.

Regional Offices:

Central: 4959 W. Belmont Ave., Chicago 41, Ill.

Western: 627 South Towne Ave., Los Angeles 21, Calif.

SONY CORPORATION OF AMERICA 514 Broadway, New York 12, N. Y.
Gentlemen: I am interested in the SONY portable television. Please rush full details.

STORE NAME
NAME TITLE.....
ADDRESS
CITYZONE.....STATE.....

--- for more details, circle 50 on page 50

MARCH 1962

A Bold Approach to Industry Problems

The electronic service industry suffers from many an ache and pain. Some are the fault of service dealers, while others are caused by manufacturers and distributors who take advantage of the dealer's inability or unwillingness to act forcibly.

Two elements operate in the area where the service technician has no one to blame but himself. First, it has always been deplorable that the great majority of technicians do not recognize the importance of being active in their local service associations. This deprives the technician of a unified voice capable of correcting industry ills. It's a cumulative effect at that, since the weaker association offers still less appeal to the unaffiliated technicians who are sitting on the fence.

The second point which operates against service dealers is their frequent reluctance to operate under sound business practices. If you made a financial analysis, you would see that there's an insufficient profit return on house calls that charge \$3.00. Furthermore, all businesses borrow money to expand and merchandise additional profitable products. Too many service dealers are hesitant to do so. Look at other businesses in your community. Locksmiths sell affiliated hardware products; watchmakers sell such gift items as radios and pens. The service dealer should at least be the community supply source for consumers who want to buy antennas, transistor portables, hi-fi components, and various hobby devices over the counter.

There is also the need to meet competition on its own ground. When self-service tube testers became popular a few years ago, some service dealers bemoaned the fact—and lost the business. More enterprising dealers set up their own tube tester routes, and so recouped the tube sales lost.

Now let's look at some of the people who take advantage of the service dealer's all too frequent inferior position. High up on the list must be the so-called distributor who buys from a manufacturer and sells retail to the public, by-passing the dealer who is often his major customer. In those communities where

the dealers stood up on their hind legs and told the distributors that they must be either retail or wholesale constructive results have been obtained. However, in other communities, technicians take the "why fight City Hall" attitude, and the unhappy status quo remains. If a distributor is willing to serve your interests, travel the extra distance or pay the extra few pennies to patronize him. In the long run, it will cost a lot more in terms of business loss when you support the distributor who doesn't think, much less care, about your welfare.

Manufacturers are far from blameless. Just as the technician catches the consumer's ire for improperly made products, and the distributor may receive the wrath of a technician, many a manufacturer is also deserving of a figurative horsewhipping. Not only do they cater to distributors who care not a fig for the service dealer, but they even turn around and push their products as hard as possible in channels entirely outside the electronic industry. When electronic products are sold through drugstores, supermarkets and department stores, particularly TV system parts and components, only the uncaring manufacturer benefits. The distributor and dealer both lose their normal business. Even the consumer often ends up spending more than he should for an improperly selected product.

We hope that readers who recognize these distasteful situations in their own community will write directly to the manufacturer. The addresses of all manufacturers are listed in our annual Directory published each May.

Lest these statements be misinterpreted, we wish to make clear our recognition of those distributors and manufacturers who do work for the welfare of the service dealer. Also, a number of enterprising service dealers can be held up as prime examples of what the industry should be doing. We have, however, emphasized the undesirable aspects because these are the ones that need attention and correction if the electronic service industry is to thrive.

Reminder for the Big Show

The 1962 Institute of Radio Engineers International Convention will be held in New York City's Coliseum, March 26-29.

Though the great emphasis is on military and industrial products, we are sure that our readers will find many informative and interesting displays.

Those technicians who are looking forward to a possible career in industrial electronics will obtain a bit of insight at this show. In this regard, you may be

interested to hear what the general maintenance foreman of a large guided missile company had to say about background requirements for electronic maintenance personnel: "Radio or TV repair experience is far more vital than any other electrical repair experience."

Furthermore, to increase one's professional knowledge and status, technicians should also consider applying for IRE membership.

Fig. 1 — Victoreen's Model 489 Thyac II transistorized meter detects alpha, beta and gamma radiation.



How Geiger and scintillation detector circuits operate

by Allan Lytel

Electronic Devices Detect Radiation

■ Radiation detectors are used for monitoring radiation leakage from X-ray machines, observing radioactive materials used in industry, and for radioactive ore prospecting. These detectors take many different forms. A typical portable unit with searching probe attached is shown in Fig. 1. The probe contains the detector and all of the circuitry is in the case. Some units have the detector built into the case itself.

Electrically, these are not complex units as may be seen from the schematic shown in Fig. 2. Radiation energy causes conduction in the ion chamber and a current flow I . This appears across R as an IR drop which is amplified by the two tubes. Output is read on M in the plate circuit of tube No. 2. Note the feedback and balance of $E-2$ is equal to $V-2$ so there is no meter reading for zero radiation.

Some radiation detector units are equipped with a flashing neon lamp

as well as earphones, or speaker (See Figs. 3 and 4) which provide both visible and audible signals indicating the presence of radiation. The heart of these devices is the radiation detector, usually a Geiger Mueller tube, for picking up the different forms of radiation. Some units employ photomultipliers in scintillation detectors.

Geiger Mueller Tube

The Geiger Mueller (G-M) tube is generally employed in low-cost Geiger counters for radiation detection. The Geiger tube consists of a thin wire of tungsten passing through an inner cylinder of thin metal or coated glass. This assembly is placed inside an outer cylinder which is filled with a gas. In effect, the tube is somewhat similar to a gas-filled voltage regulator tube.

A voltage is applied to the G-M tube, with the center wire positive,

and the inner cylinder negative. As a particle of radiation enters the tube through a window in the cylinder, the particle collides with a gas atom inside the tube and the atom loses an electron. The atom then becomes a positive ion. The freed electron is attracted to the positive wire but, in its travel, it collides with another gas atom and produces another free electron, etc. Thus, for each single particle of radiation many free electrons are produced. These are all attracted to the positive wire which acts similarly to a plate in an amplifier tube. The total number of free electrons arriving at the wire becomes the output current. The positive ions are attracted to the cylinder which has a negative potential. Here they are neutralized by picking up electrons to make them neutral gas atoms again.

Thus, when a single particle of radiation reaches the G-M tube, a

rapid multiplication of free electrons occurs, and in a very short time all of the free electrons arrive at the wire and all the gas ions arrive at the cylinder. The tube has provided an output and is now ready for the next particle.

Based upon the detection action of the G-M tube many simple, portable Geiger counters can be built. The design depends upon the nature of the particular tube and the final desired cost. Models are available from the most simple to quite complex units with complete amplifiers and several types of detectors.

Forms of Radiation

Radioactive elements, such as radium and uranium, throw off particles and rays in the process of natural disintegration. These particles and very high frequency waves are used as a means of detecting the presence of radioactive materials. This radiation has essentially three types of energy: alpha and beta particles, and gamma rays.

Alpha particles have high energies but they travel only a few inches—being stopped by a few centimeters of air. They can also be stopped by thin aluminum foil or a sheet of paper. These particles are equivalent to helium nuclei, or helium atoms which have been stripped of their orbital electrons. They are made up of two neutrons and two protons and carry a positive charge.

Beta particles are high-energy electrons with greater force than alpha particles and they travel far greater distances before they are stopped by collision with other materials. At average speed, a one-eighth inch thickness of aluminum is required to stop them. Of course, they carry a negative charge.

Gamma rays are extremely short wave-length electromagnetic radiations, or photons. They are a type of X-ray radiation which are very powerful and move easily through most materials. Depending upon their speed, they can pass through several inches of lead.

Other Detector Types

Radiation from radioactive materials can be converted into visible

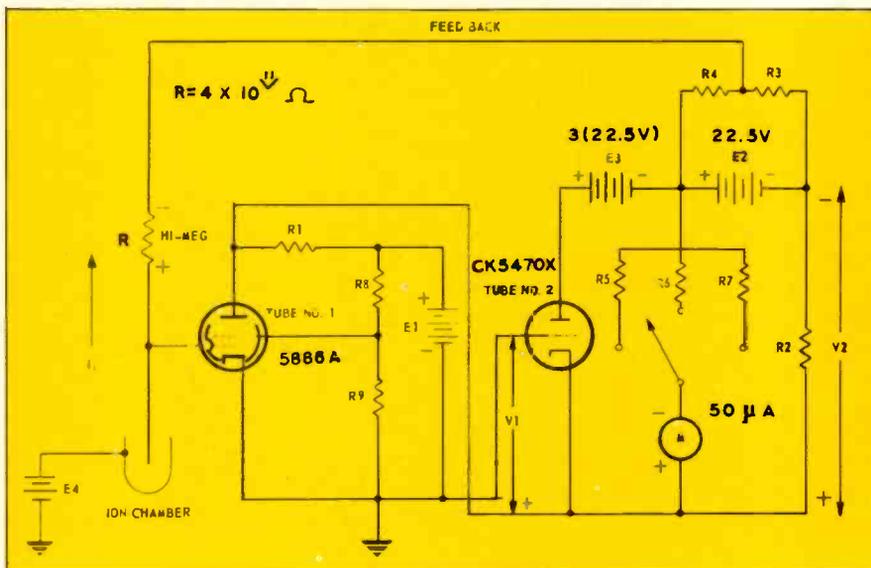


Fig. 2—Basic schematic of a portable radiation detector using a microammeter.

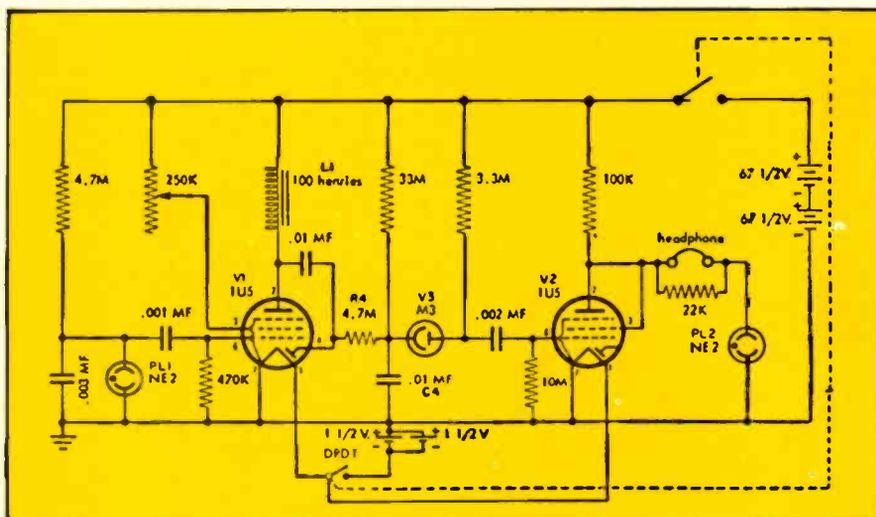


Fig. 3—Schematic of EICO's Model 803 portable radiation detector employs headphones and neon lamp for aural and visual radiation indications.

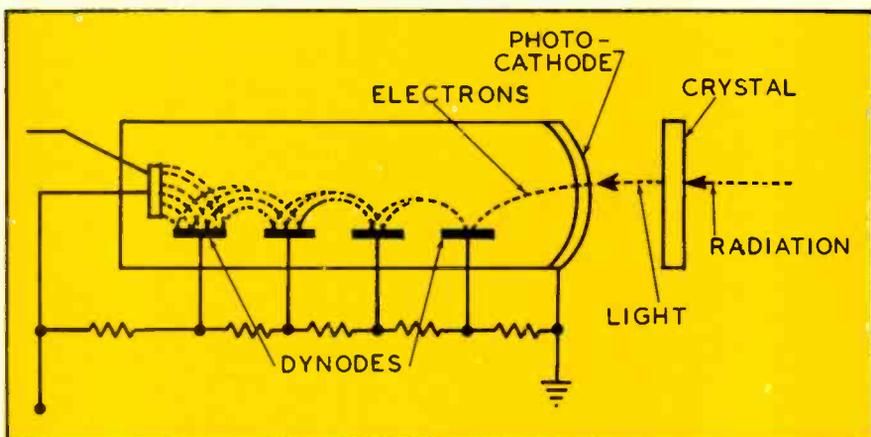


Fig. 5—Phosphor crystal converts radiation to light. Light sensitive photo-cathode converts light into electrons which are progressively increased by the photo-multiplier tube anodes.

a transformer such as that used for filament voltage. When the switch is closed the transistor oscillates, in the audio range, because of the inductive feedback. R-1 limits the base current and also determines the amount of power output. Transformer T provides about a 20 to 1 stepup of voltage. Usually about 1000 volts can be obtained with this circuit which, because of the R-C filter and rectifier drop, provides an output in the 900 volt range at 1 mill or less. This is all that is required for most G-M tubes.

The rectifier diode and filter capacitors must have at least a 1000 volt rating, or more for a safety factor but several components can be used in series to cut down the peak voltage rating required. For example, two capacitors, each .05 μf at 500 volts will provide .025 μf at 1000 volts when used in series. Voltage multipliers are also used to provide the required high

voltage. In addition, automatic control circuits are employed to make the output voltage substantially independent of normal load variations on the secondary as well as the normal range of battery voltage.

A typical radiation detector schematic is shown in Fig. 7. The various radiation detector probes are powered by the same high voltage supply with a regulated output voltage of either 900 volts or 1200 volts. The 900 volt output is required for the Geiger tube detectors and is labeled GM on the internal selector switch, S-2. The 1200 volt output is selected for the scintillation probes and is labeled SCINT. This high voltage supply is a blocking oscillator driven "fly-back" type circuit where the blocking oscillator portion of the circuit is Q-2, R-7B, transformer T-2 windings 3-4 and 5-6, and batteries BT=1 and BT=2.

When the instrument is turned

on, Q-2 conducts and an increasing current flows through winding 3-4. This current also flows through the collector of Q-2 and induces a voltage in winding 5-6 which maintains conduction of Q-2. The collector current increases until Q-2 has sufficient current gain to remain saturated, when the circuit rapidly turns off because of the regenerative action of the transformer. During the turn-off action, large fly-back voltages appear across all transformer windings. A voltage peak of about 1100 or 1400 volts (depending on whether the 900 or 1200 volt output is selected) appears across winding 1-2 because of the large number of turns in this winding. This voltage "fly-back" is rectified by diode CR-5 in a conventional half-wave rectifier. R-12 and C-4 form a filter to smooth the pulsations of voltage across C-5. A corona discharge type regulator V-3, regulates the output voltage at 1200 volts throughout the battery life, when the switch S-2 is in its SCINT or open position. When S-2 is switched to the GM or closed position, another corona regulator V-2, regulates the output at 900 volts. When V-2 is connected across V-3 by the switch S-2, the 1200 volt regulator V-3 does not conduct at all, V-2 taking all of the power supply current and preventing V-3 from firing.

The high voltage, through connector J-2 is fed to the radiation detector across the load resistor R-11. A current pulse from the detector caused by an ionizing event then appears as a negative voltage pulse at the input connector J-2. With some exceptions, the pulse shaping circuit is a blocking oscillator similar to the power supply.

This circuit is held "cut-off" by the bias formed by resistors R-9 and R-10 and the power supply battery. The blocking oscillator consists of components Q-1, T-1, L-1. CR-1 and C-1. The coupling capacitor C-1 couples the negative pulses from the radiation detector to the base circuit of Q-1. Inductance L-1 forms a high impedance for these pulses while providing a lower impedance path for direct

Continued on page 65

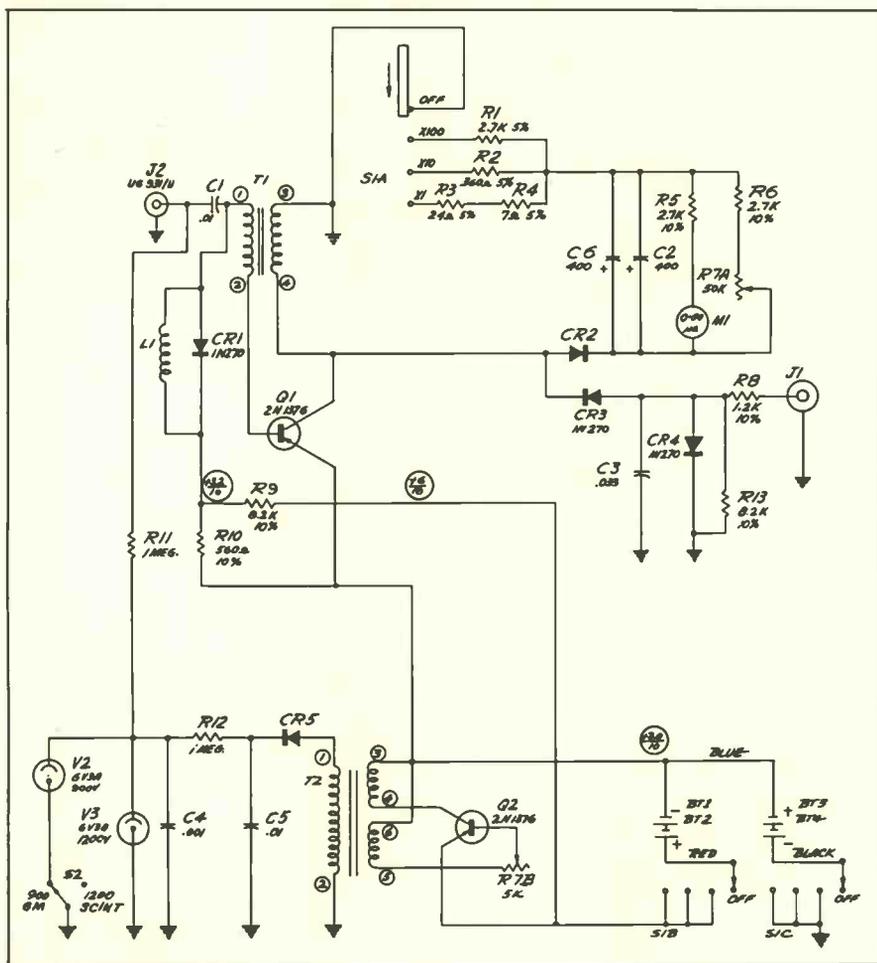


Fig. 7—Schematic diagram of the Model 489 Victoreen radiation counter which is designed to use either a Geiger-Mueller or a scintillation probe.

Whipping TV Transformer Problems

by Jack Hobbs

Technical Editor

Fault symptoms point way to isolation of defective components

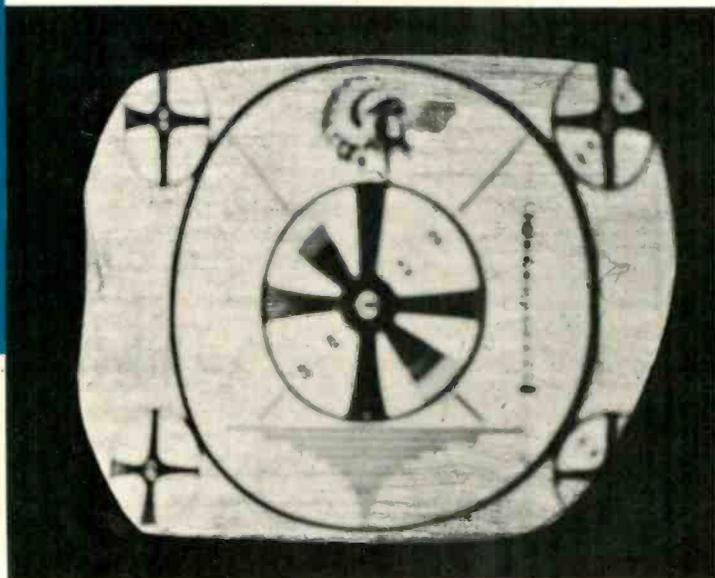


Fig. 1—Picture on TV screen after one leg of rectifier winding opened on transformer. Shrinkage and neck shadow were accompanied by a substantially darker picture.

■ Technicians are frequently confronted with troubles in one or more of five basic TV-receiver transformer types. These include the a-c power transformer; video i-f; vertical blocking oscillator and sweep output; horizontal sweep output, and audio detector and output transformers.

Technicians should have a good knowledge of symptoms which indicate defects in each transformer type and be skilled in quickly isolating trouble in each area.

Low Voltage Transformers

Low voltage power transformers supply the total "fuel" needed in all TV sets except the series-string or series-parallel string types. These transformers are generally used in full wave tube, selenium or silicon rectifier circuits, and usually have a 117-120 v, 60 cycle primary winding, a step-up secondary winding supplying from 250 to about

380 a-c volts, and one or more step-down secondary windings which supply tube heater voltages.

When the power transformer fails, completely or in part, a number of different symptoms are immediately observable in the TV set. For example, the set may be completely dead—no picture, no sound, and no raster. Tube heaters may or may not be lighted. Then again, there may be sound and no raster. In this case, the damper tube's heater winding on the power transformer may be defective. There are other possible symptoms. One side of the high voltage secondary of the transformer may open, the power supply becoming a half-wave rectifier, with results as shown in Fig. 1.

In most cases, when a regular transformer powered TV set is turned on and its tubes do not light, the trouble is usually in the set's power cord, on/off switch,

fuse, interlock connection, or the transformer's primary winding is open. Under certain rare circumstances the tubes may not light because of a poor lead connection from the transformer's heater winding. Also, when a 12.6 volt split-heater transformer is used, one open outside lead can cause part of the tubes being supplied by this transformer winding to remain lighted while the other group is out.

If the set's a-c fuse, or the house fuse blows, or the lights dim suddenly when the set is switched on, the trouble can be caused by a shorting power transformer but this generally results from a defective rectifier, a shorting filter or a heavy external load on the power supply caused by a short somewhere on the B+ line.

When the a-c input of a transformer powered set does not have a fuse, the power transformer may overheat and become damaged

when a rectifier or filter capacitor shorts, or when some other heavy load is placed on the power supply. When this occurs the transformer frequently smokes. Experienced technicians recognize this symptom by the peculiar odor given off by the overheating transformer. This odor will usually linger in the set for hours, even after the set has been turned off. A transformer which has overheated and smokes should be replaced—even though some badly overheated transformers have been known to serve for years without breaking down under normal load.

Although it is easy to determine if a power transformer winding is open by using the ohms function on a VOM, it is not always easy to isolate a shorted transformer winding by the same method.

Perhaps the easiest and most definite way is with a properly fused load-check meter (a-c watt-meter). However, if this instrument is not on hand, a 150 to 200 watt light bulb equipped with test-type insulated socket, plug and flexible leads with insulated clips, can serve as well.

As shown in Fig. 2, the lamp

is connected in series with the a-c line to the TV set. The lamp not only acts as a current limiting resistor but can be employed to indicate if a short exists in a power transformer section, a rectifier, filter capacitor, or because of a short at some other point on the B+ line.

If the TV is equipped with an a-c line fuse which blows each time the set is turned on, and the transformer is suspected, remove the transformer's secondary winding connections, including all heaters, replace the fuse, connect the lamp as shown, and switch on the set. If the lamp glows brightly the transformer is definitely defective and should be replaced. If the lamp lights dimly or not at all, the trouble is probably beyond the transformer.

However, in the latter case, the secondary windings of the transformer should be reconnected one by one, including the heaters, but with the rectifier removed from the set at this point. In this manner it can be determined if an individual circuit-section of the secondary is defective or a short exists in heater circuits.

If the lamp still does not glow

brightly, replace the rectifier. If the lamp now glows brightly, the rectifier is either defective, or a filter capacitor is shorted or a short exists somewhere in another area of the set on the B+ line. Actually, the rectifier should be checked in the beginning whether suspected or not. The set should be switched off, of course, before each test step.

Some transformers may develop hum or buzz. This is usually known as lamination hum and can be reduced or eliminated by tightening the transformer's four housing bolts.

Whenever a TV requires a replacement power transformer it is highly desirable to obtain an exact physical fit, even if the transformer is a universal replacement type with slightly different electrical specifications or with additional heater windings. A transformer that mounts to the chassis precisely as the original did, will save the technician considerable time in most cases.

Despite all this, it may be necessary on some occasions to drill new holes, enlarge or reshape a mounting hole in the chassis, or fill up a portion of the original hole.

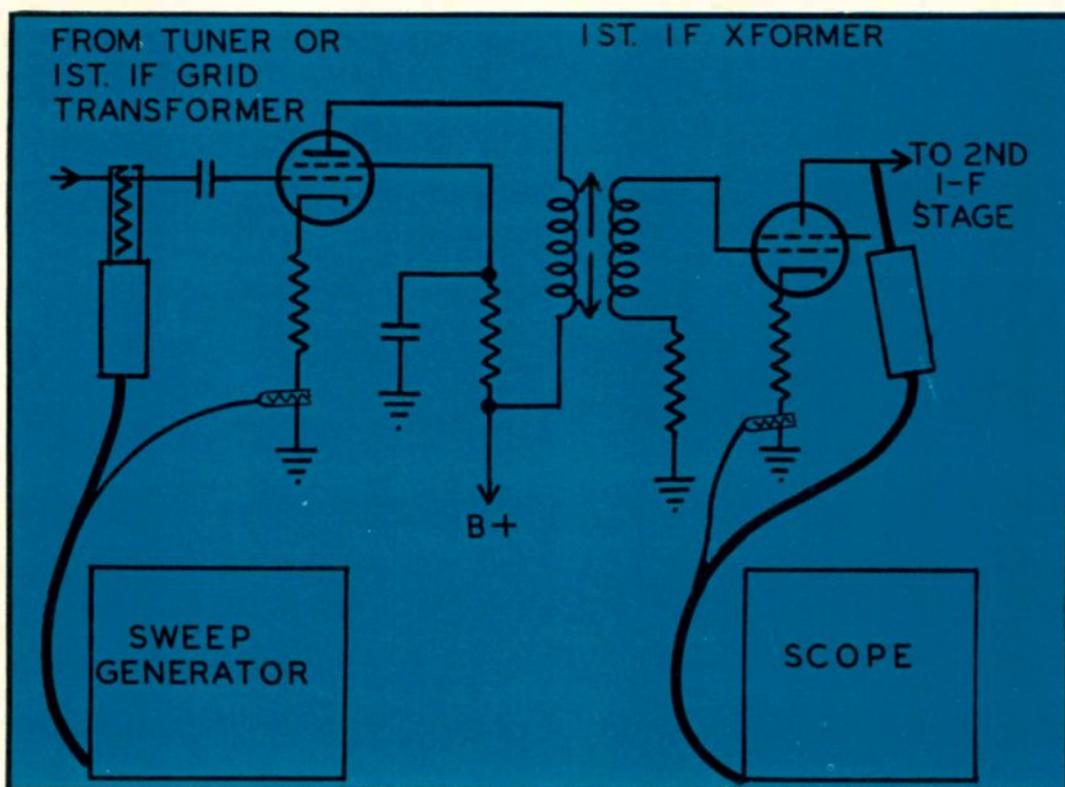


Fig. 3—A sweep generator and scope can be used to locate defective i-f transformers.

Video I-F Transformers

There are a number of i-f coupling methods, including the standard slug tuned primary-secondary transformer. Whatever the configuration, they are all used to obtain a TV receiver pass-band sufficiently wide to pass all composite video frequencies, without distortion, while they are being progressively amplified in the i-f amplifier strip.

The i-f transformers in modern sets are stagger tuned. This means, as we know, each transformer is tuned to a different frequency somewhere in the 4 mc band extending from the 41.25 mc sound channel to the 45.75 picture channel (21.25 to 25.75 mc in some older sets). Loading resistors are frequently used across a slug tuned transformer's winding to aid in broad-banding frequency response.

A defective i-f transformer can cause a complete loss of picture and sound, loss of picture and weak sound, a weak washed out picture (not accompanied by snow); picture smearing, flashing, white areas

trailing black areas, lack of definition, poor sync, and other symptoms.

The windings in some i-f transformers occasionally short, burn out or open for other reasons. Many, however, become intermittent because of cold or rosin joints at a point where the fine winding wires join the transformer's lugs.

There are a number of ways to isolate a defective i-f stage. One method is signal tracing. An oscilloscope, with a demodulator probe attached, is employed as shown in the set-up in Fig. 3. With a TV station tuned in, the probe is placed at the tuner output, and the scope's gain is turned to maximum—with its frequency set at 30 cycles. If a composite video signal is observed on the scope's screen, the probe is next moved to the first i-f tube plate. The amplitude of the composite video signal should increase considerably if the tube is amplifying normally. This process is followed alternately from grid to plate of each stage until that stage is located where the signal drops

off or disappears entirely.

Another approach substitutes an r-f sweep signal injected into an i-f grid to replace the regular TV signal (Fig. 3). In this case, the scope and demodulator probe is used to observe the pass-bands of individual i-f stages, or the combined pass-bands of subsequent added stages. A loss of signal, an increase or decrease of the response curve's amplitude, or an incorrect curve shape, is significant in finally isolating the defective stage. Some technicians begin first by employing a low capacitance probe on the scope, beginning signal tracing at the video amplifier stage, moving step by step in the opposite direction toward the first video i-f input point. Of course, a demodulator probe must be substituted for the direct probe at the video detector input.

After a fault is isolated to a given stage it can usually be pinpointed by checking the transformer's windings with an ohmmeter, with the set turned off. It is not necessary to disconnect most transformers to check for open windings, except where resistors are shunted across windings, or in some first i-f grid transformers, where the primary and secondary may be connected together. It may also be necessary to disconnect some transformers used at the last i-f output, depending upon the video detector circuit's design.

Intermittent connections can generally be located by carefully probing solder connections on transformer lugs with a small plastic rod while observing the picture on the CRT. If the bad connection is touched, the picture will usually go out momentarily or the CRT screen will be covered with flashes and streaks. A low wattage soldering iron and a drop of solder will usually take care of these problems.

When poor solder joints or open connections are encountered on the inside points of winding connection terminals, some transformer housings can be opened, their windings carefully removed, and repairs made with a soldering iron.

When a transformer replacement becomes necessary, it is again de-

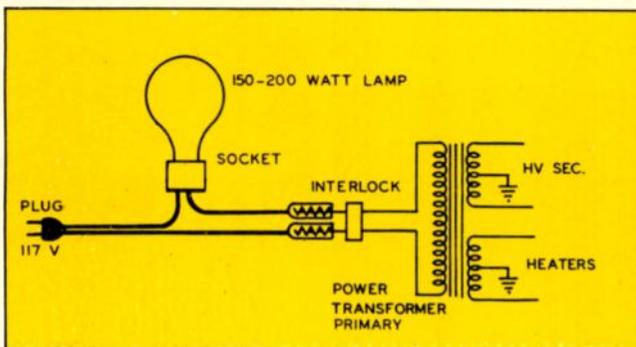


Fig. 2—If a load-check meter is not available, an ordinary lamp can be used to isolate a defective power transformer.

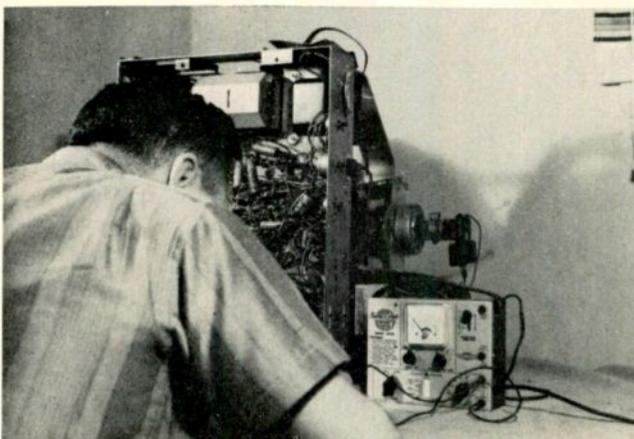


Fig. 4—Sweep-circuit tester is used to check a vertical output transformer by signal substitution.



Difficult Service Jobs Described by Readers

HV Cage Missing—Sync Unstable

A Teleking TV set, model 174, was taken to the shop with no raster. A shorted capacitor in the horizontal afc discriminator circuit was replaced restoring the raster with picture. After replacing two weak tubes and giving the set a general cleaning, it looked fine — except for one thing. When switched on from a cold start the horizontal frequency was way off.

Both the horizontal hold control and the ringing coil had to be adjusted to sync the picture, and the picture could easily be thrown far out of sync again by rapidly turning the horizontal hold control. This was a marginal condition I felt had to be corrected.

Tubes were substituted first, of course, but without correcting the trouble. I then checked all components in the afc discriminator and horizontal oscillator circuits. Everything checked normal. I even tried experimenting by substituting component values in the afc circuit but without favorable results. The only remaining component left unchecked by direct substitution was the ringing coil. Not having a replacement I ordered one.

The new ringing coil was clipped into the circuit with two long test leads and the receiver was put on test. The results were satisfying. Now the horizontal frequency was rock stable and behaved the way it should. To be 100% sure I switched back and forth from the new coil to the old coil a dozen times or so until there was no doubt that the old coil was defective.

I removed the old ringing coil from its mounting hole on the chassis rear apron and installed the new one in its place. I turned the set on and the picture came on out of sync!

Now I was really puzzled. Several hours of time were lost and I was right where I had started. I tried an experiment. I took the coil out of its mounting hole and hooked it up again with the test leads, laying the coil down on the workbench. I turned the set on and this time it came on as it should. I picked up the coil and moved it closer to its mounting position. As I approached the rear apron the frequency became unstable; as I backed off, it settled down.

Since the high voltage cage on this chassis was missing I surmised that the coil was picking up pulses from the flyback transformer.

Having no spare high voltage cover, I relocated the coil farther away from the flyback. By mounting it closer to the front apron of the chassis the receiver worked fine. —*Frank A. Salerno, Long Island City, N. Y.*


Symptoms were “static” in the sound, and varying volume. After changing audio tubes in the house without clearing up the trouble, I explained to the customer that the symptoms indicated a transformer in the sound section was breaking down.

With the set on the bench, I changed the ratio detector transformer but the trouble persisted. I pulled the video amplifier tube and tapped and probed all of the sound circuits, but no unusual scratches or noise could be created in the speaker by these methods. I then opened the circuit to the grid of the 6AU6, 1st sound i-f amplifier, and fed in a 4.5 mc signal. Sure enough, at a high input the audio level fluctuated and produced static.

I now came to the conclusion that a resistor in the sound section was arcing internally. A check of R-202, 205 and 206 proved negative. The only component left was C-209, a 5 μ f 50 v capacitor. As soon as it was clipped from the circuit the static cleared up. A new capacitor was installed and the set worked well without further difficulty — *Thomas E. Gregg, Yonkers, N. Y.*

Static And Varying Sound

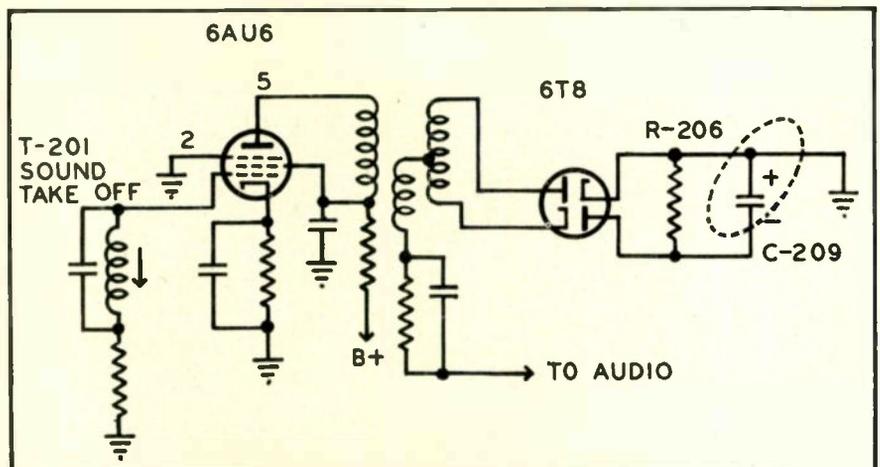I was recently confronted with an unusual intermittent in the audio section of an RCA KCS 108C TV.



Intermittent static and varying sound was caused by defective capacitor C-209.

TROUBLESHOOTING

Hi-Fi Tone Controls

Isolate defective tone networks
with specialized test set-up

by *Mannie Horowitz*
Electronic Instrument Co.

■ Tone controls are used in hi-fi units for a number of reasons. They compensate to a great extent for the normally unequal response of human ears to audible tones; the difficulties of recording at "flat" levels; reproduction deficiencies in speakers, room acoustics, and other reasons.

Technically, a complete tone control system performs five functions: The first two functions are boost and cut of low bass frequencies with respect to the rest of the audio band. This action is usually measured as boost and cut at 50 cycles with respect to 1000 cycles.

The second two functions are boost and cut of the high treble frequencies with respect to the middle and low frequencies. Measurements at 10,000 cycles with respect to 1000 cycles is the most frequently used test. The final and most important function is lack of frequency discrimination. Some position must be found in the rotation of both controls which neither attenuates nor accentuates any portion of the frequency spectrum. If this function is properly accomplished, the output from the amplifier should be perfectly flat within $\frac{1}{2}$ to 1 db from 20 to 20,000 cycles. This, as well as the four aforementioned modes, are illustrated in Fig. 1 for one type of tone control network.

Test Setup

The setup used for testing the response of any type of tone control

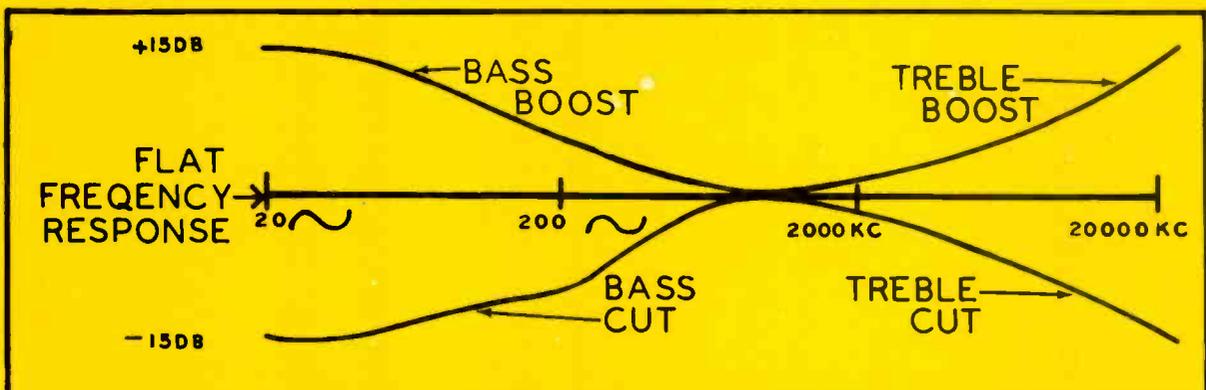


Fig. 1—Graphic illustration shows the five functions of a typical tone control.

is shown in Fig. 2. A monitored signal from an audio signal generator is fed to the amplifier's input. The voltage output from the amplifier is applied across a second meter, while the waveshape is observed on the scope.

For a reliable test, the amplifier output must be sinusoidal at all times. This requires that the amplifier and signal generator level controls be properly set to prevent amplifier overload. No overload should exist when bass and treble controls are at their maximum boost setting while being checked at low and high frequencies respectively.

Feed a 1000 cycle signal from the generator into an unequalized input. Set the amplifier tone, loudness, scratch and rumble controls to get the maximum flat response (no bass or treble attenuation or boost). Turn the level control on the amplifier to maximum. Set the generator output control to the point of maximum undistorted output as observed on the scope. Read the output meter db scale at this voltage. Now, turn down the signal generator output control until the output meter reads 18 to 22 db below the maximum undistorted reading. Choose a convenient point, for this will be your output reference level. Note this reading as well as the reading in volts on the input meter.

To test the bass control, switch the signal generator to 50 cycles and adjust its output control so that the input meter reads the same voltage as it did at 1000 cycles. Turn

the bass control to maximum and then to minimum, observing the readings in db above and below the reference level you previously noted on the output meter. The peak excursions of the output meter around the reference level is the maximum bass boost and cut the tone control can provide. Repeating this procedure at 10,000 cycles with the treble control will indicate the boost and cut capabilities of that function.

Troubleshooting any type of tone control circuit is similar to troubleshooting any other type of electronic network. You must first be certain that any vacuum tube or transistor involved is operating properly. The voltages at the various electrodes should be checked against the manufacturer's published data.

"Losser" Type Controls

This control, still frequently used in high fidelity equipment, is a hold-over from public address amplifiers. A drawing of this circuit is shown in Fig. 3.

The circuit is essentially that of a voltage divider. The input is fed across the complete divider consisting of the series combination R-3 R_c and R_d R-4. A portion of the input voltage is developed at the output across the series combination R_d R-4. Because only resistors are used here, there is no attenuation or accentuation of any specific frequency range. Capacitors added to this resistive divider network modify the response, providing the bass and treble control

action. The size of these capacitors and the associated resistors in the specific network determine the portion of the audio frequency range to be affected and by just how much.

The treble control network is lifted out of Fig. 3A and is illustrated in Fig. 4A. Resistances R_c and R_d are not shown in 4A because they are shorted out at high frequencies by C-3 and C-4 respectively. They contribute nothing significant to the treble control action.

Perhaps this should be explained briefly. Consider the treble set at the maximum attenuation position. R_b is equal to zero while C-2 shunts R-4 as well as the output. At very high frequencies, C-2 shorts R-4, permitting none of the high frequencies (above the audio range) to appear at the output. At moderately high frequencies, C-2 shunts R-4, resulting in an impedance greater than zero but less than R-4, so that only a small portion of treble signal will be at the output. At middle and low frequencies, C-2 is an open circuit. R-4 is no longer shunted and the maximum signal permitted by the resistive divider network appears across the output terminals.

This will result in the curves shown in Fig. 4B, for the condition when R_b=0. If R_b is not equal to zero, the shunting effect of C-2 will decrease as a function of the size of R_b. Depending upon the setting of the treble control, an attenuation curve intermediate between R_b=0 and the flat response will result,

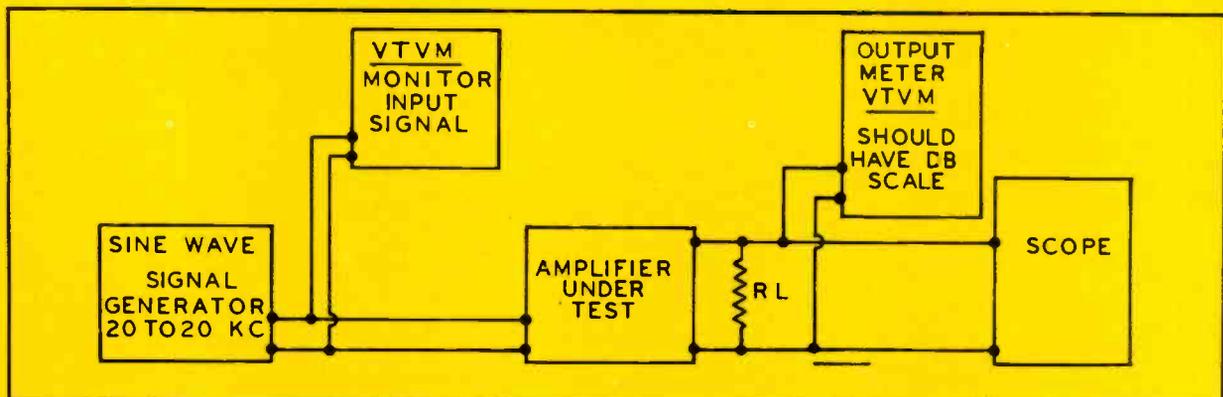


Fig. 2—Test set-up required for checking tone controls. RL is not used when the output is from a preamplifier.

In the maximum boost position, $R_a=0$ and C-1 shunts R-3. Because C-1 attenuates the lows more than the highs, the parallel impedance of C-1 R-3 will be less at high frequencies than at the middle and low portion of the band. Thus, a high frequency signal will develop across R-4, the output, larger than the middle and low frequency signals, resulting in the curve shown in Fig. 4B. As R_a is increased, the effect of C-1 is decreased, providing intermediate degrees of boost.

Trouble Symptoms

Considering treble control operation, troubleshooting this circuit is quite obvious. Little or no treble cut is caused by a defective C-2 while little or no treble boost is caused by a defective C-1. Of course, R-3 and R-4, the control, can be at fault, but are unlikely suspects. These components can easily be checked with an ohmmeter.

Bass boost and cut are merely a

matter of controlled mid and high frequency cut and boost respectively. When properly accomplished, mid and high frequency cut is the equivalent of bass boost. Mid and low frequency boost can be considered the equivalent of bass cut.

Observing the bass control network in Fig. 5A, first consider the maximum boost position when R_c and C-3 are shorted and R_b is at its highest value. The large R_d is shunted by C-4. C-4 bypasses the large R_d at middle and high frequencies, so that these frequencies are attenuated. The attenuation is controlled by the value of R-4, resulting in flat response at the high end. C-4 shunts R_d more at the high frequencies than the low frequencies, resulting in less attenuation for the extremely low bass frequencies than for the higher bass frequencies. The resulting curve is shown in Fig. 5B. As R_c increases and R_d decreases, the effect of C-4 is lessened, resulting in less bass boost.

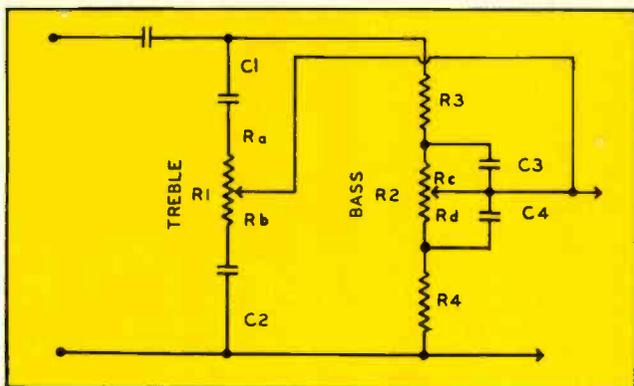


Fig. 3 — Functional diagram of "Losser" type tone control network.

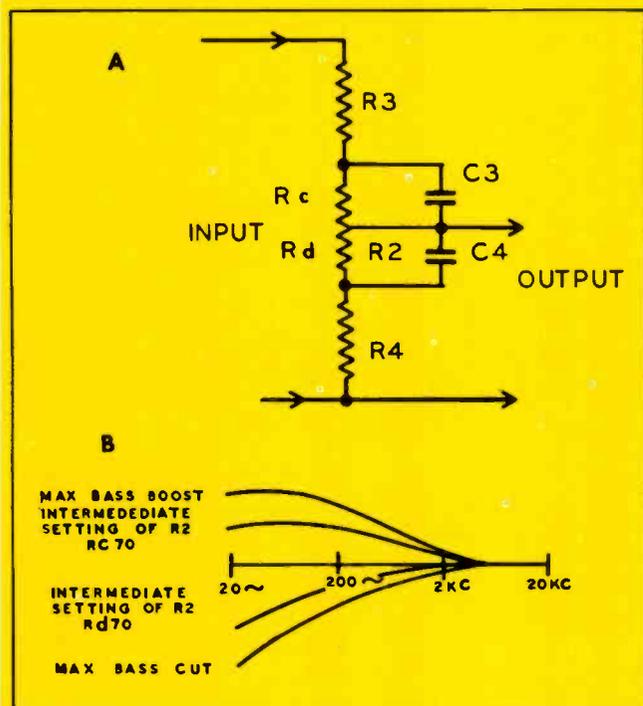


Fig. 4 (A)—Treble control network. (B)—Curves resulting from treble control action. Note that curve for intermediate setting affects center frequencies.

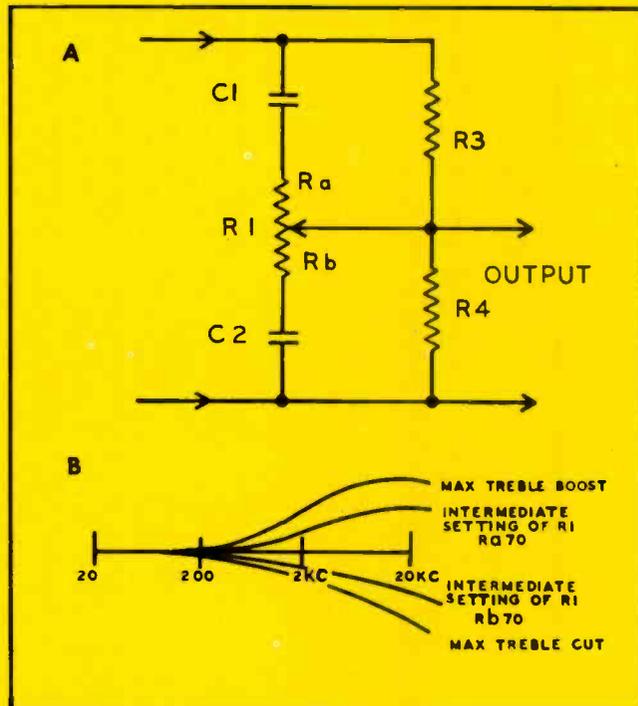


Fig. 5 (A)—Bass control network. (B)—Curves resulting from bass control action and curve for intermediate control setting affects center frequencies.

Bass attenuation is obtained through action of C-3 and R_c. When R_d=0, the maximum cut position, C-3 shunts R_c, permitting the highs to pass freely to the output through C-3, while attenuating the lows. R-3 limits the treble and mid-frequency boost, to keep the upper end of the spectrum flat. The boost at the high end and middle frequencies with respect to the lows, is the equivalent of bass cut. Decreasing R_c provides the intermediate modes of bass attenuation because of the diminishing effect of C-3.

Once again, the lack of proper action is generally caused by defective capacitors. While a defective C-3 will not permit the bass cut to behave properly, a defective C-4 will affect the bass boost. If the middle and high end does not have flat response, R-3 and R-4, as well as C-1 and C-2, are probably at fault. If the low end is not flat when the control is set at the center of rotation, one of these capacitors will frequently be found defective.

Some controls may perform only

a portion of the functions outlined above. The principle of operation as well as probable component failures remain unchanged.

Baxendall Feedback Type Networks

Feedback type circuits employ networks similar to those used in the Losser tone control described above. The important factor to remember is that if you feed back a signal through a capacitor, you are feeding back more of the high than the low frequencies. The resultant signal will be an emphasis of the low end with respect to the highs. The size of the capacitor and the rest of the resistance network will determine if this network will provide treble cut or bass boost.

The most frequently employed feedback network, designed by Baxendall, is shown in Fig. 6. The feedback is from the plate, through capacitor C-4 and the resistors R-2, R-4/R-3, and back to the grid. Other feedback paths are possible, such as through C-4, R-2, C-2, C-1,

R-1, half of R-5, C-3, and to the grid.

Complete analysis of this circuit involves a discussion of operational amplifiers, virtual ground, etc. Although very interesting, these details are involved and will not help in the troubleshooting of this network. Table I was designed to help you troubleshoot this circuit from observed symptoms.

Table I specifies the characteristics if there is an extreme defective condition, such as an open or shorted component. If resistances changed to larger values or capacitors decreased in value, the performance of the circuit would approach open circuit conditions. A tendency towards shorted component symptoms would be evident if resistance values have decreased and capacitance changed in the upward direction.

The curves produced by this circuit are shown in Fig. 7. Note that the curves on intermediate positions affect only the extremes of the band

Continued on page 48

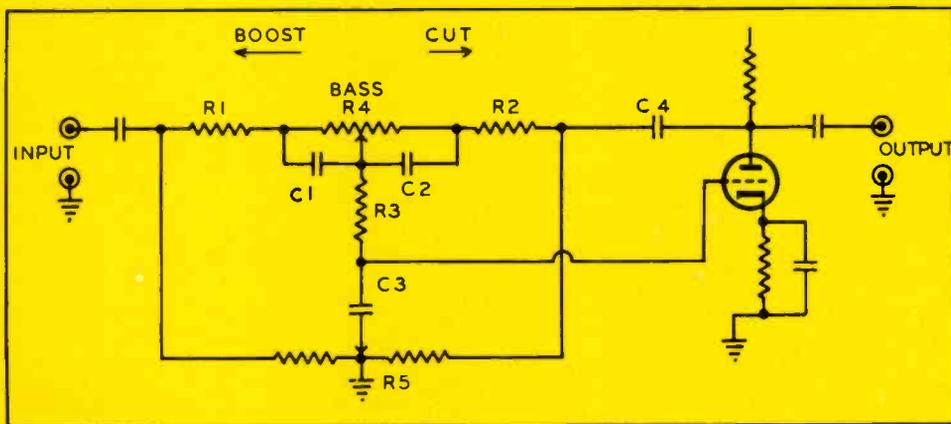


Fig. 6—Basic circuit of Baxendall feedback type tone control network.

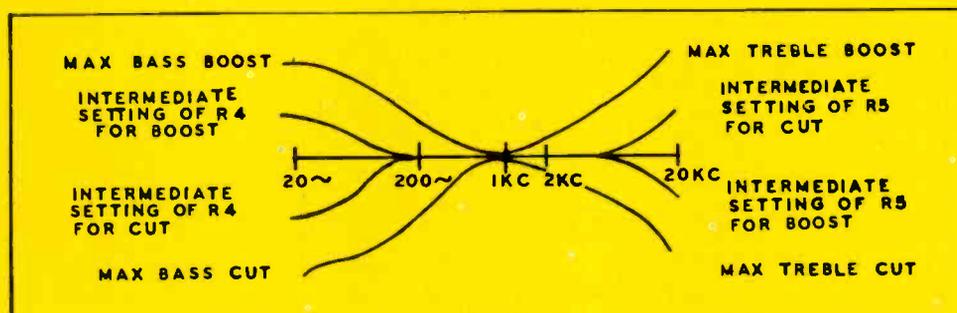


Fig. 7—Curves resulting from settings of Baxendall tone control network. Only tones at ends of band are affected.

New Test Instruments

For Bench And Caddy

ET editors examine five test units this month: a battery eliminator-charger for auto radio service work; resistor-capacitor decade box for component substitutions; Citizens Band transmitter tester for checking CB units; a combination transmitter dummy load and attenuator; and TV sweep circuit analyzer for testing horizontal and vertical circuits.

GC Electronics, Resistor-Capacitor Selector, Model 36-524 at \$24.95—A resistor-capacitor substitution unit is an asset to any electronic service shop. It enables techs to substitute a questionable part quickly. The unit examined here offers individual selection of 23 1-watt resistors (33 ohms to 10 megohms) and 22 capacitors (0.0001 μ f to 300 μ f, rated at 600 volts and higher values at 450 volts).

There's nothing complicated about operation of substitution boxes, of course. For this unit, the user simply sets a slide switch to "Resistance" or "Capacity" and sets the selector switch to the desired value. Integrated test leads with alligator clips are then connected into the circuit. A push button is depressed for capacitor operation. Release of the button automatically discharges the capacitor for the user's protection. Test leads are marked for polarity, which is necessary when substituting electrolytics.

Besides its obvious use as a quick substitution device, the unit can also be a great help when trying to determine the value of an unmarked or charred component.

Precision Apparatus, Battery Eliminator and Charger, Model P-28 at \$64.95—This is a relatively inexpensive low-ripple auto radio power supply that meets all the needs of an auto service specialist—and then some.

It's designed to meet requirements of transistorized auto radios and vacuum tube types with 6 and 12 volt ratings. The battery eliminator can also operate as a battery charger for wet cell auto batteries.

The unit has two meters: d-c volts and d-c amps, both with a range from 0-to-20. Output voltage is continuously variable from 0-8 volts d-c and 0-16 volts d-c. It also has output terminals for vibrator-type radios and special output terminals for transistor or hybrid tube-transistor radios.

A variable voltage control and indicating meters are invaluable features. The output voltage may be lowered to determine if a vibrator commences operation at, say, 5¼ volts, and if it doesn't operate at this voltage, slowly raise output until it does operate. A vibrator that doesn't operate at approximately 5¼ is a questionable component.

Another service aid offered by variable voltage is locating inter-

mittent troubles by raising voltage beyond the normal 6 volts to around 7½ or so. The higher voltage often results in a breakdown state of the intermittent part. The d-c amperes meter should be observed while raising voltage because an excessive reading could indicate a short in the receiver.

Sencore, Sweep Circuit Analyzer, Model SS-117 at \$89.50—Here's an instrument that enables TV service technicians to pinpoint television receiver sweep troubles with great speed. It's a signal injection unit, plus a yoke substitute, flyback checker, and voltage reading instrument, among others. Essentially, it's the same type as the Company's predecessor, Model SS-105 (see ET April 1961). However, it has many new, improved features which make it even more useful than the older model.


In addition to providing horizontal and vertical pulses which permit dynamic tests of TV sets, this new instrument has a separate vertical yoke output signal which drives a CRT to full vertical deflection. Also, greater output is available for horizontal and verti-



ET editor inspecting Seco's transmitter tester with a Citizens Band unit.



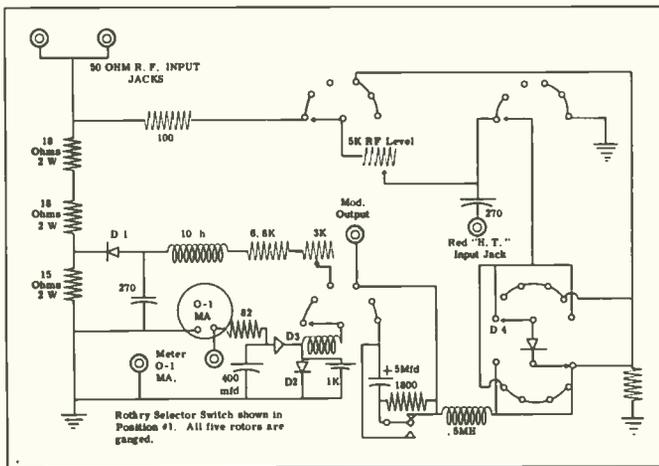Test instruments shown, left-to-right, are: Seco Model 510 Attenu-load, Precision Model P-28 Battery Eliminator and Charger, GC Model 36-524 Component Selector, Seco Model 510 CB Transmitter Tester, and Sencore Model SS-117 Sweep Circuit Analyzer.



Schematic of Seco's Model 510 Citizens Band transmitter tester.

cal pulses than the older model, resulting in fuller rasters.

The instrument permits users to monitor cathode current of the horizontal output tube through use of an adaptor socket (also used to check screen voltage without test leads). It measures 2nd anode voltage to 30 kv, too, as well as lower d-c and a-c p-to-p voltages. A 300 μ a meter is utilized for minimum circuit loading. Sync pulses, negative or positive, can be employed to troubleshoot sync circuits.

In truth, this unit has all needed provisions to allow a user to troubleshoot any part of a TV's sweep circuit without resorting to guesswork. Capping this neat test package, it has a roll chart which indicates operating data of horizontal output tubes, an all-steel carrying case with a full mirror in its cover, and two 115 volt a-c outlets in the unit's cable department. Properly employed, this unit can no doubt save the average technician considerable time.

Seco, Transmitter Tester, Model 510 at \$46.95, and Attenu-load Model 511-A at \$21.50—Here are two pieces of equipment which technicians can use to great advantage when installing, testing, and servicing CB transmitters.

Model 510 combines functions of a number of transmitter test instruments. The tester measures percentage of both positive and negative modulation, r-f ma, and power output in watts. It also doubles as a field strength meter or remote indicator; the latter requiring the use of a special r-f attenuator cable. The manufacturer also suggests that the tester may be used as an a-c voltmeter or an audio output meter.

The "Attenu-load" can be used as a dummy load bank or as a transmitter power attenuator.

The 510 test unit was designed for use with low power transmitters such as CB equipment, but when used with the model 511-A

Attenu-load, the instrument's capacity can be extended to 50 watts. The Attenu-load may also be used as a dummy load for r-f power to 50 watts.

Although Citizens Band transmitters are limited to 5 watts input by FCC regulation, if in doubt about the maximum power output of another transmitter to be tested (up to 50 watts), the transmitter is not connected directly to the tester. Instead, a 50 ohm coaxial cable supplied with the tester, is connected to the transmitter's antenna terminals and then to the Attenu-load input. A switch on the back of the Attenu-load is thrown to the "INT" position before transmitter power is applied. The transmitter tester can then be safely connected to the Attenu-load output. Power attenuation is 10 db, which represents a 10:1 power step down ratio.

This equipment should prove helpful to any shop engaged in CB installation and repair.

Recommended practices for the home entertainment electronics industry. Requirements for avoiding deceptive pricing and bait advertising

TV Industry Advertising Guide



■ An advertising code for the home entertainment electronics industry has been published by the Electronic Industries Association. Included with this industry-recommended plan are reprints of the FTC guides against deceptive pricing, bait advertising and deceptive advertising of guarantees. The EIA code text was submitted to the FTC for review, and received approval as an aid to better understanding of FTC law.

It is the EIA's view that their legal position does not allow them to enforce these recommended practices. Therefore, in the interest of keeping our readers informed, and in particular those readers who are also retailers, we are abstracting the highlights of the FTC guides, and publishing the EIA code in its entirety.

By having this information readily at hand, readers can be guided in the presentation of their own advertising, and also have a tool for monitoring the advertising of others in the industry.

EIA Recommended Advertising Practices Comparative Sales Price Advertising

A. When an advertisement, by words, figures or in any other manner states or implies a reduction

from the advertiser's usual price of the model advertised, the advertiser himself should have made actual sales at the higher price in his recent, regular course of business.

B. A statement representing or implying a reduction or savings from an established retail price should be used in advertising only if for the specific model advertised, such price has been either (a) the advertiser's usual price of the same model in his recent, regular course of business; or (b) the price charged for the same model by other sellers in the trade area in their recent, regular course of business; and (c) the advertisement clearly shows from which of these two prices the saving or reduction is claimed or implied.

C. The terms "sale," "special sale," "clearance sale," "E.O.M. (end of month) sale," "advance sale," or any other terms which imply a price reduction should not be used unless in his recent, regular course of business, the advertiser's price of the model advertised has in fact been higher. (If the advertiser has not himself offered to sell the model to which the price reduction applies, the advertiser should use such terms only if the usual and customary retail price of other sellers is higher in the trade

area where the claim is made and the advertisement clearly shows that the claim is based on such comparison, i.e., the prices of other sellers. The claim should not be made if it is based on infrequent or isolated sales by other sellers.)

D. No article should be 'pre-ticketed' with any price figure, either alone or with descriptive terminology, which exceeds the price at which the article is usually and customarily sold in the trade area or areas where the 'pre-ticketed' article is offered for sale. This rule applies to those who disseminate 'pre-ticketed' price figures for use in connection with the offering for sale of articles at retail by others, even though they themselves may not be engaged in retail sales. The term 'pre-ticketed' includes the use of price figures affixed to the article by tag, label, or otherwise, or in material such as display placards, which are used, or designed to be used, with the article at point of sale to the consuming public.

Other Price Advertising Practices

A. Whenever a price is advertised:

1. The model to which the price applies should be identified by model number, and also,
2. Any other model illustrated

in the same advertisement should be identified by model number.

B. The terms "as low as," "from," etc., should not be used in connection with a price unless a particular model is in fact available at such price in reasonable quantities and the model is identified in the advertisement by model number.

C. When prices of display models are being advertised, such models should be specifically identified in the advertisement as display models. Display models include floor samples, demonstrators, and the like.

D. When the price quoted in an advertisement is "with trade," and the trade allowance is dependent upon the model or condition of the item to be traded in, this fact should be stated.

E. Outboarding. When the advertised price does not include delivery, normal installation, service, or warranty, the advertisement should clearly and conspicuously state that there will be an additional charge for an such excluded item.

F. When reference to periodical payments is made in an advertisement:

1. If a down payment or trade-in may be required, the advertisement should so state.
2. If a terminal or balloon payment may be required, the advertisement should so state.
3. If the periodical payment applies only to certain models, the advertisement should so state.

G. When the word "free" is used in advertising the offer should be bona fide factual. If the offer is conditioned in any way, the conditions imposed should be clearly and conspicuously disclosed at the outset of the advertisement (and not merely by a footnote) so as to leave no reasonable probability that the terms of the advertisement might be misunderstood. The word "free" should not be used where the advertiser has, in connection with the offer, increased the price of the merchandise required to be purchased or reduced its quality.

H. If a premium is offered in connection with the purchase of an instrument, the statements about the premium should also conform

to these advertising practices.

I. No statement should be made in advertising which implies that the advertiser's prices or terms have any special factory sponsorship or endorsement, unless the statement is true.

Bait Advertising

A. No advertisement containing an offer to sell a product should be published unless the model advertised is then being displayed by the advertiser, is available for prompt delivery at the price and upon the terms set forth in the advertisement, and will be willingly sold by the advertiser.

B. If display models are advertised as being available at specified prices or at savings, the quantity of such models available should be specified in the advertisement, or the advertisement should state that the quantity available is limited in supply.

C. If an advertised model will be sold at all outlets listed in the advertisement, a sufficient quantity of the advertised product should be available to meet reasonably anticipated demands, unless the advertisement clearly and adequately disclosed that the supply is limited and/or the advertised product is available only at designated outlets.

D. When an advertiser anticipates that the demand for an advertised model, such as a close-out item, will exceed his ready supply (from stock, from supplier or from another regular source), the advertisement should state that the quantity available is limited.

E. The advertiser should not disparage by acts or words the advertised product or the guarantee, credit terms, availability of service, repair or parts, or in any other respect.

F. The advertiser should not show or demonstrate an advertised product which is defective, unusable or impracticable for the purpose represented or implied in the advertisement.

Product Claims

A. When an advertisement contains a claim as to the quality, performance, or features of a particular

product, the person originating the claim should be prepared to support it by suitable demonstration or credible statistical data. No illustration should be used in any advertisement which creates a false impression of the quality, performance or features of a product.

E. Comparisons between products of different manufacturers, whenever made, whether on radio or television, on the sales floor or elsewhere, should be bona fide factual and not made in such a way as to mislead the listener or viewer. There should be no unfair comparisons between the advertised product and the other product with regard to performance, features or other characteristics. There should be no comparisons under any condition unless the advertised product and the other product are of similar and comparable merchandise generally available for purchase at a comparative price in the same trade area or areas as the advertised product or, if not so available, that fact is clearly disclosed.

C. When an advertisement specifies a warranty period, but the warranty period applies only to certain parts, and not to all parts, then that fact should be stated.

D. The terms "Satisfaction or Your Money Back," "10-Day Free Trial," or similar terms, should refer to the return of the full purchase price, unless otherwise specified.

E. No advertisement containing a warranty should be published, unless the advertiser will promptly fulfill his obligations and stand behind his representations.

Federal Trade Commission — Abstract Of Guides Against Deceptive Pricing

In determining whether or not pricing practices are violative of the laws administered by the Commission, the facts in each matter are considered in view of the requirements of the Federal Trade Commission Act, as amended, and principles enunciated by the Courts in the adjudication of cases. The foremost of these principles are:

1. Advertisements must be considered in their entirety and as they would be read by those to whom they appeal.

Continued on page 72

Improve Your Skills By

Building a TECHNICAL

TWO-WAY RADIO

By Allan Lytel. For the communications technician, and those interested in entering the field, this book covers mobile and fixed base stations. Theory is presented with a minimum of math. Antennas, selective calling, power supplies and test instrument chapters are included. Photos, drawings and charts are generously used. Hard cover, 304 pages. Price \$9.50.

INDUSTRIAL CONTROL CIRCUITS

By Sidney Platt. Excellent starting point for TV technician interested in learning about industrial electronics. Non-mathematical text explains circuitry and operation of power controls, relays, timers, photoelectric devices and instrumentation found in factories. Practical applications shown. Soft cover, 200 pages. Price \$3.90.

101 WAYS TO USE YOUR SIGNAL GENERATOR

By Robert G. Middleton. A fine collection of brief explanations on how to use the generator for various tests. Twenty-five equipment checks are presented, seven antenna tests, 27 AM-FM receiver tests, 28 TV tests, 10 component tests and four miscellaneous. Each description briefly lists the required equipment connections etc. Soft cover, 123 pages. Price \$2.00.

MAGNETIC AMPLIFIERS

Principles & Applications

By Paul Mali. Written at an intermediate technical level in the tried and proven picture/text style of presentation, this excellent book covers: magnetism; electro magnetism; saturable reactors; core, compensating and polarized magnetic amplifiers. Well illustrated with photographs and drawings. Soft cover. 261 pages. Price \$2.45.

RADIO SERVICING THEORY & PRACTICE

By Abraham Marcus. This, the third edition, is the latest revision of a volume which has been, for more than a decade, one of the outstanding practical texts on radio receivers. All essential information necessary for a thorough understanding of radio theory and servicing is included. Well illustrated. Hard cover. 650 pages. Price \$8.40.

BASICS OF DIGITAL COMPUTERS 3 (vols.)

By John S. Murphy. Using the easy-to-learn picture book technique, these three volumes explain the theory and functions of digital computers. Very little mathematics. Covers counting systems, computer language, programming, memories, logic diagrams, flip-flops, clamping, input-output and data processing. Soft cover, 416 pages. Price \$8.40/set.

IMPEDANCE MATCHING

By Alexander Schure. Divided into five major sections, this informative book covers power transfer, impedance matching devices, matching at audio and r-f, and matching in transistor circuits. Complete with tables, schematics and computation examples. Soft cover, 128 pages. Price \$2.90.

APPLICATIONS OF ELECTRONICS

By Bernard Grob and Milton S. Kiver. Assumes a knowledge of elementary electronics. Subjects discussed include: vacuum tubes and transistor theory; audio amplifiers; oscillators; receiver, transmitter and pulse circuits; and industrial and military electronics. Math is kept to a minimum. Well illustrated. Hard cover. 628 pages. Price \$10.00.

HOW TO INSTALL & SERVICE AUTO RADIOS

By Jack Darr. This second edition contains much practical information of real use to technicians. In addition to service data on antennas, intermittents, noise suppression, speakers and troubleshooting, transistorized and hybrid radios are covered. 6-12 volt conversions are explained. Soft cover. 160 pages. Price \$3.25.

TUBE CADDY TUBE SUBSTITUTION GUIDE BOOK

By H. A. Middleton. A pocket size guide for caddy use, includes a list of foreign tube substitutions. It covers direct substitutions only and is divided into 4 sections. Sec. 1: lists substitutions with a "good" or "excellent" coding. Sec. 2: some ruggedized substitutions. Secs. 3 & 4: European-American substitutions. Soft cover. 56 pages. Price \$0.90.

MANAGEMENT GUIDE FOR PREVENTIVE MAINTENANCE

By Bernard T. Lewis and William W. Pearson. This text, included in the publisher's Industrial Management Series, outlines considerations needed for organizing a preventive maintenance program, systems and procedures for controlling maintenance—including inspection and work orders, inspection record systems, time studies, etc. Soft cover. 64 pages. Price \$1.25.

INFRARED RADIATION

By Henry L. Hackforth. From the basic laws, through transmission and detection, to design and practical application in various industries, this book details theory and practice of infrared. Instruments and communications are also covered. Hard cover. 304 pages. Price \$10.

VIDEO TAPE RECORDING

By Julian Bernstein. This interesting and authoritative reference thoroughly treats the system used to rebroadcast live TV programs. Written at a level understandable to all interested in video recording, with mathematical formulas absent. The text outlines methods used and circuitry employed. Many photos and drawings. Hard cover. 272 pages. Price \$8.95.

OBTAINING & INTERPRETING TEST SCOPE TRACES

By John F. Rider. This handbook shows how to get the most out of your oscilloscope. Over 800 traces are shown, including sine, square, rectangular, trapezoid, sawtooth differentiated and integrated types. Explains scope connections, manipulating controls and test setups. Soft cover. 190 pages. Price \$3.00.

BASIC ULTRASONIC

By Cyrus Glickstein. This excellent book, replete with many illustrations, covers the subject of ultrasonics from the fundamentals of sound through the various types of equipment in use, to a wide variation of applications. Topics include ultrasonic generators, transducers, pulsed output and transistorized equipment. 144 pages. Soft cover. Price \$3.50.

ELECTRONIC TECHNICIAN editors have carefully selected these books by the world's leading technical publishers. Order direct from our Book Department. Fill in coupon or separate sheet. Money-back guarantee.

LIBRARY

RADIO OPERATOR'S LICENSE Q & A MANUAL

By Milton Kaufman. This sixth edition gives you the information you need to pass FCC license examinations. In question and answer form similar to actual FCC tests, all eight elements are covered, including law, radiotelephone, radiotelegraph, aircraft and ship radar. Abbreviations, code, etc. included. Hard cover. 736 pages. Price \$7.10.

HOW TO RUN A SMALL BUSINESS

By J. K. Lasser. Here is a basic business guidebook for service dealers and other operators of retail and small manufacturing firms. Covers record keeping, avoiding frauds, tax management, credit sales, insurance programs, how to buy an established business, financing and other important topics. Hard cover. 400 pages. Price \$6.00.

SERVICING UNIQUE ELECTRONIC APPARATUS

By Jack Darr. This book explains basic operating theory and practical servicing techniques for troubleshooting and repair of a variety of unique electronic devices used primarily for industrial applications. Covers ultrasonic cleaners, diathermy, automatic flow control, photo-flash and others. Schematics, drawings and photographs included. Soft cover. 126 pages. Price \$2.50

100 ELECTRONIC CIRCUITS

By Milton Aronson & Charles Kezer. Here is a useful basic circuit reference book covering a wide variety under eight major sections, including power supplies, amplifiers, oscillators, pulse circuits, test instruments, alarms, phototubes and miscellaneous. In addition to the schematic, a page or two of text accompanies each circuit, explaining the operation and characteristics. Soft cover. 180 pages. Price \$2.00.

REPAIRING TRANSISTOR RADIOS

By Sol Libes. How transistor theory operates in radio circuits and servicing procedures is thoroughly discussed. Each radio stage is covered with a service chart that indicates "Trouble," "Possible Cause," and "What to Look For." Excellent coverage is given to AM, FM and auto radios. Interchangeability chart is included. Well illustrated. Soft cover. 168 pages. Price \$3.50.

BASICS OF FRACTIONAL HORSEPOWER MOTORS AND REPAIR

By Gerald Schweitzer. In this book the author examines: the operation of various motor types, including split-phase, capacitor, repulsion, shaded pole, universal and three-phase motors; enclosures, windings, control devices and protective devices. Two sections are devoted to motor testing, care and maintenance. 176 pages. Soft cover. Price \$3.90.

Books Described Previously

BASIC TELEVISION (5 vols.)	\$11.25
BASIC ELECTRONICS (6 vols.)	\$13.85
CLOSED CIRCUIT & INDUSTRIAL TV	\$ 4.95
PINPOINT COLOR TV TROUBLES IN 15 MINUTES	\$ 5.95
INDUSTRIAL ELECTRONICS HANDBOOK ..	\$22.50
AUDIO MEASUREMENTS	\$ 2.90
ELECTRONICS IN INDUSTRY	\$ 8.50
HOW TO SERVICE TAPE RECORDERS ..	\$ 2.90
FUNDAMENTALS OF RADIO TELEMETRY ..	\$ 2.95
HOME AIR CONDITIONING INSTALLATION & REPAIR	\$ 3.50
SERVOMECHANISM FUNDAMENTALS	\$ 5.50
ELECTRONIC COMMUNICATIONS	\$13.00
BASIC AUDIO	\$ 9.95
MODERN TRANSISTOR CIRCUITS	\$ 8.50
PHOTOTUBES	\$ 1.80
MARINE ELECTRONICS HANDBOOK	\$ 3.95
GUIDE TO MOBILE RADIO	\$ 2.85
MASTER RECEIVING PICTURE TUBE SUBSTITUTION GUIDE	\$ 7.45
SMALL APPLIANCE SERVICING	\$ 4.50
A-C MOTOR CONTROL FUNDAMENTALS ..	\$ 5.95
PIN POINT TRANSISTOR TROUBLES IN 12 MINUTES	\$ 5.95
HOW TO USE METERS	\$ 3.50
BASIC CARRIER TELEPHONY	\$ 4.25
101 WAYS TO USE YOUR AUDIO TEST EQUIPMENT	\$ 2.00
BASICS OF INDUCTION HEATING	\$ 7.80
2-WAY MOBILE RADIO HANDBOOK	\$ 3.95
SERVICING TRANSISTOR RADIOS	\$ 2.90
GETTING THE MOST OUT OF VACUUM TUBES	\$ 3.50
HOW TO TROUBLESHOOT TV SYNC CIRCUITS	\$ 2.90

To order above books, write in title and price on coupon

CUT HERE

ELECTRONIC TECHNICIAN Book Dept.

480 Lexington Avenue
New York 17, N. Y.

I plan to build my technical library. Please send me the books I have indicated below. You will pay postage. I understand that if I am not satisfied with any book for any reason, I may return it to you prepaid in good, clean condition within 7 days of receipt and receive a complete refund. Shipments outside U. S. & Possessions, add 20¢/book for soft cover, 40¢/book for hard cover. Enclosed is my check or money order, in full payment, made out to ELECTRONIC TECHNICIAN.

- ... Two-Way Radio @ \$ 9.50
- ... Industrial Control Circuits @ \$ 3.90
- ... 101 Ways to use Your Signal Generator @ \$ 2.00
- ... Magnetic Amplifiers @ \$ 2.45
- ... Radio Servicing Theory & Practice @ \$ 8.40
- ... Basics of Digital Computers @ \$ 8.40
- ... Impedance Matching @ \$ 2.90
- ... Applications of Electronics @ \$10.00
- ... How to Install & Service Auto Radios @ \$ 3.25
- ... Tube Caddy Tube Substitution Guide Book @ \$ 0.90
- ... Management Guide for Preventive Maintenance @ \$ 1.25

- ... Infrared Radiation @ \$10.00
- ... Video Tape Recording @ \$ 8.95
- ... Obtaining and Interpreting Test Scope Traces @ \$ 3.00
- ... Basic Ultrasonics @ \$ 3.50
- ... Radio Operator's License Q & A Manual @ \$ 7.10
- ... How to Run a Small Business @ \$ 6.00
- ... Servicing Unique Electronic Apparatus @ \$ 2.50
- ... 100 Electronic Circuits @ \$ 2.00
- ... Repairing Transistor Radios @ \$ 3.50
- ... Basics of Fractional Horsepower Motors & Repair @ \$ 3.90
- BOOKS IN PREVIOUS ISSUES: @ \$


Enclosed is total payment of \$ _____
(If you have New York City address, add 3% sales tax)

Name _____

Address _____

City _____ Zone _____ State _____

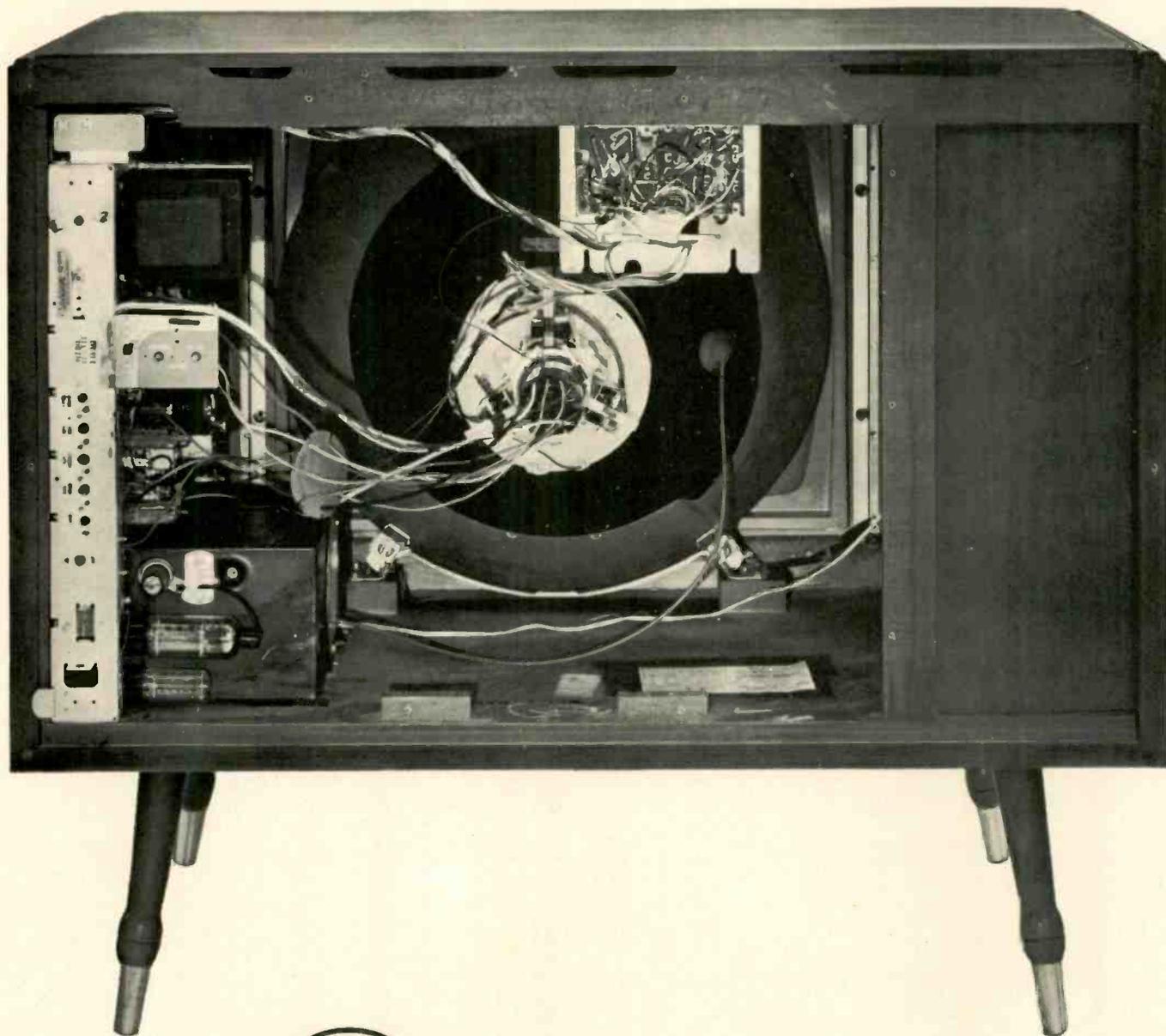Here's why color sets made by
you can service so easily and



The Most Trusted Name In Television

TMK (S) ®

RCA VICTOR are the ones with such confidence!

1 RCA VICTOR'S color TV chassis has been performance-proved for over seven years

RCA Victor's new Super Power Chassis incorporates more than seven years of refinements based on field and service experience! Features include: easy access and chassis "*remove-ability*"; easy-to-find, accessible test points; new Push-Button Circuit Breaker that eliminates "annoyance" calls.

2 RCA VICTOR'S "Roadmapped" Security Sealed Circuit Boards make servicing easier

RCA Victor Security Sealed Circuit Boards are *dependable*. This is the modern way to build television receivers! They are "roadmapped" and numbered with *you* and your job in mind.

3 RCA VICTOR'S replacement parts are performance-proved

Proved-in-use replacement parts—another by-product of seven years of *intensive* research, study and experience.

4 RCA VICTOR'S proved-in-practice service notes and literature

Those who know Color TV best learned it through RCA with help from RCA Color TV information bulletins, service data, schematic diagrams—all designed by RCA for the proper development of Color TV as an industry—a going, profitable business for you!


Join the Color "Corps" now. Get to know more about it, advertise, sell and talk Color TV—build a more profitable business! Ask your RCA Victor Distributor to help you!

SHOP HINTS

TIPS FOR HOME AND BENCH SERVICE

Novel Tool Holders

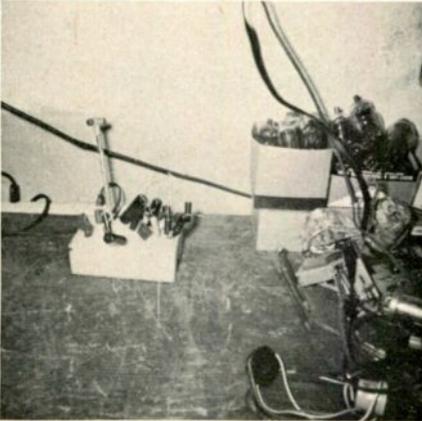A few pieces of Styro-foam, available in some five-and-ten-cent stores, make excellent holders for



Novel tool holders made from Styro-foam material keep small tools handy.

many small tools and other items found around the work bench. This material can aid in keeping an otherwise cluttered-up bench clean and small tools can be easily found at a glance. Items are merely "stabbed" lightly into the material and when needed can be easily removed. — *William R. Lacy, Syracuse, N. Y.*

Radio Hum Intermittent

The other day a small table radio was brought into the repair shop with symptoms of severe 60 cycle hum. Upon examination of this set, the service technician found that the hum temporarily went away if the power switch was first "flicked" off, and then on.

Sets exhibiting symptoms such as these frequently employ a multiple section filter capacitor. The trouble arises when the common lead which interconnects the foils develops a highly resistive contact with one of the sections. This permits hum to be internally coupled from the defective section to those which are functioning normally and the filtering action is reduced. Flicking the set off and then on permits heavy capacitive charging currents to flow through the resistive contact and temporarily weld the bad connec-

tion. Unfortunately, the weld is not satisfactory and the connection becomes resistive once again after a short period of operation.

The cure is, of course, replacement of the entire filter capacitor. — *Philco Service-Businessman, Phila., Pa.*

Polish Scuffed Plastic TV Screens

When a portable or other TV arrives in the shop with a scuffed plastic face, the simple procedure outlined here will almost completely eliminate the scuffs, and reduce even deep cuts so they are less noticeable. Minor scuffing is completely eliminated.

Obtain some plaster-of-Paris powder and mix with "Lubriplate" until you have a smooth paste. Place some on the plastic which is to be treated and rub with a circular motion, using a piece of clean cotton or linen cloth. Concentrate first on the badly scuffed area with small circular motions and gradually increase the size of the circular sweep. Watch the surface clear up almost like magic. This will come in mighty handy if a receiver gets scuffed in transit from the customer's home to the shop. — *M. G. Goldberg, St. Paul, Minn.*

Loctal Tube Conversions

Scarcity and cost of some "loctal" type receiving tubes make conversions desirable from the customers point of view, and the technician can profit also.

We have found that a 7 pin


printed circuit socket has the same radius as loctal pins. Conversion requires only removal of the loctal socket's prongs, not the socket itself. There are 8 holes, but only 7 pins—the printed circuit socket can be rotated to obtain best advantage of the terminal connections, and the original leads are then connected to the new socket tabs.

With a 14B6 at \$5.60, and a 12AV6 replacement at \$1.65, the spread makes the deal profitable both ways. — *Willard W. Waite, Wellington, Ohio.*

VTVM Probe-Lead Modification

I have eliminated the inconvenience of 3 test leads on my EICO model 221 VTVM in the following manner:

The ohms/a-c input and the com-

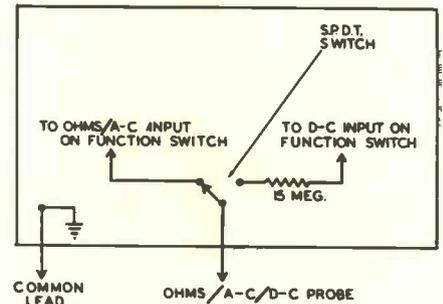

VTVM probe-lead modification employs a s.p.d.t. switch to simplify meter use.

mon or ground leads are first removed. The common jack is removed from the chassis and a single-pole-double-throw toggle switch is installed in the same mounting hole after the hole is enlarged.


The common lead is permanently installed in the a-c/ohms jack and grounded. The 15 megohm resistor in the d-c probe is removed and one side of it is connected to one toggle-switch contact and the other end is connected to the d-c input on the meter's function switch. The other toggle-switch contact is connected directly to the ohms/a-c input tap on the function switch.

These changes do not endanger

SHOP HINTS WANTED!

\$3 to \$10 for acceptable items. Use drawings to illustrate whenever necessary. A rough sketch will do. Photos are desirable. Unacceptable items will be returned if accompanied by a stamped envelope. Send your entries to Shop Hints Editor, ELECTRONIC TECHNICIAN, 480 Lexington Ave., New York 17, N. Y.

**EASY
WITH
"ET"**

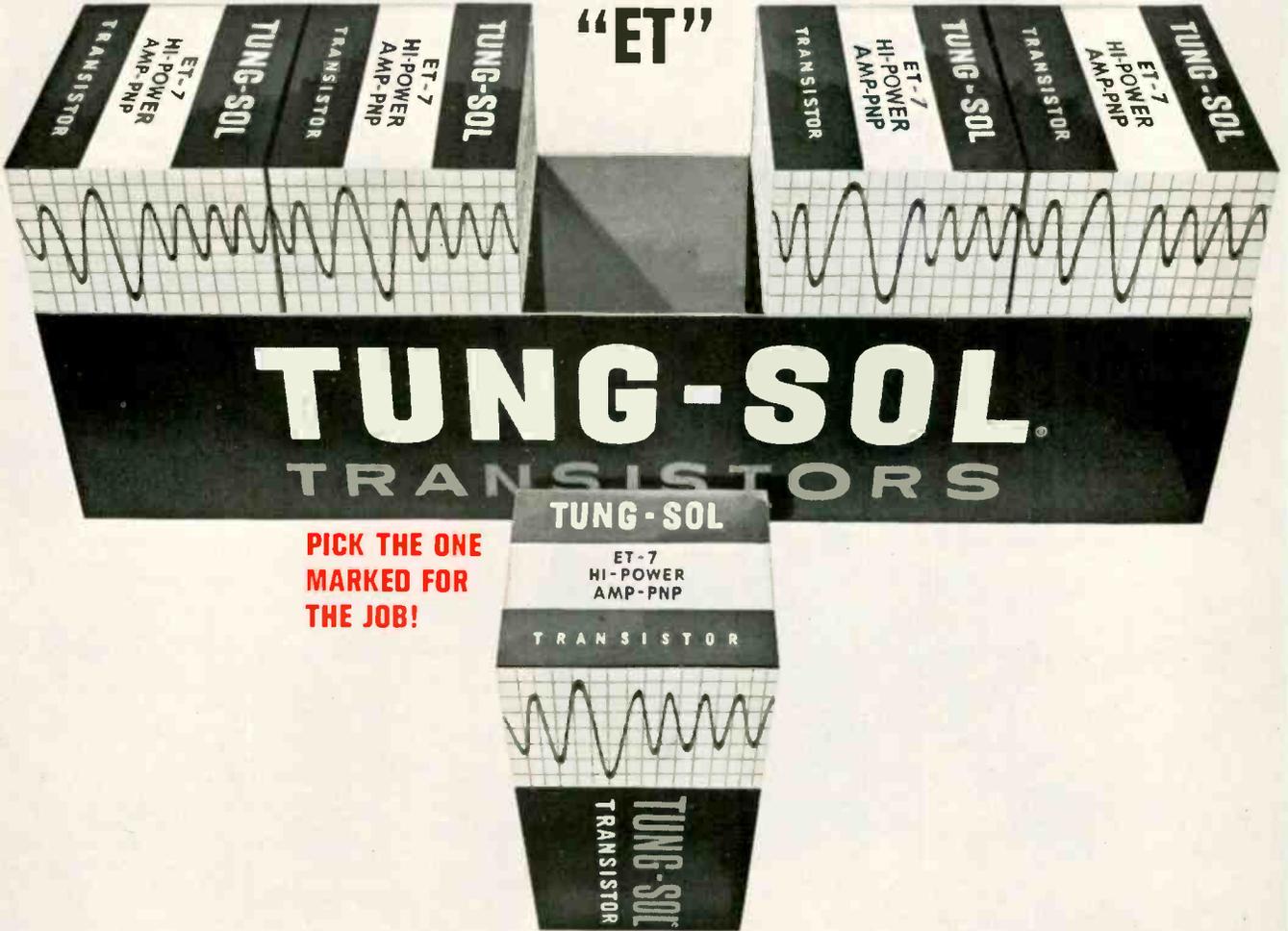

**PICK THE ONE
MARKED FOR
THE JOB!**

Tung-Sol "ET" transistor packages are marked to eliminate guesswork in selecting the correct replacement for every job. Type numbers, class of service and junction polarity is stamped on each end flap. This is a time saving feature as well as a safeguard against service slip-ups. Tells you at a quick glance where your inventory stands.

The compact "ET" line was engineered by Tung-Sol specifically to eliminate confusion in entertainment service resulting from almost endless similarity and duplication of types. Eleven PNP and NPN units replace hundreds of older transistors. "ET"

transistors measure up fully to Tung-Sol's one high standard of excellence and reliability. The most advanced quality evaluation techniques assure product uniformity, lot after lot.

When you order transistors, specify "ET." High turnover with low inventory and customer satisfaction will show that it's the profitable way to buy transistors. Tung-Sol Electric Inc., Newark 4, New Jersey.

 **TUNG-SOL®**

A TYPE FOR EVERY JOB

PNP TYPES

Low power

- ET1 Mixer/oscillator/ converter
- ET2 IF amplifier
- ET3 AF amplifier 6v.
- ET4 AF amplifier 12v.
- ET5 AF amplifier 9v.

Medium power

- ET6 AF power amplifier

High power

- ET7 AF high power amplifier

NPN TYPES

Low power

- ET8 Mixer/oscillator/ converter
- ET9 IF amplifier
- ET10 AF amplifier 9v.
- ET11 AF amplifier 12v.



Ask your Distributor for the Tung-Sol Transistor Interchangeability Guide

- - - for more details, circle 58 on page 50

**"I've got
satisfied
customers
and
profits..."**



**by improving communications equipment reliability with
IERC Heat-dissipating Electron Tube Shields!**

Extra profits in contract servicing are yours with TR type heat-dissipating tube shields—at installation, of course, and from the 2 to 12 time increase in tube life and reliability they provide. Electron tube failures, caused by heat, account for almost 70% of equipment failures. Service profits go out the window when valuable work, other service calls or "off hours" time must be given to meet service contract requirements just to change a tube! You can eliminate this problem by increasing the tube life and reliability of your customer's communications equipment with TR's—time-proved in vital military, aerospace and precision electronic equipment applications. A complete installation of TR's in almost any equipment takes only a few minutes—reliability and profits are immediate!

patented



SERVICE TECHNICIANS—
Write today for complete data on
IERC TR shields.

IERC
heat-dissipating

DIVISION
electron tube shields.

International Electronic Research Corporation
135 West Magnolia Boulevard, Burbank, California

heat-dissipating tube shields for miniature, subminiature, octal and power electron tubes

... for more details, circle 29 on page 50

SHOP HINTS

the meter or circuits in any way, nor does it upset the normal operating function of the unit. It is now very easy to flip a switch, pick up two probes, and use the meter with ease for any measurement. — *Harold Wolff, Jr., Gonzales, Texas.*

Altered Wrench For Hex-Head Screws

Transformers and other components are frequently mounted in radio and TV sets with thin hex-



Altered hex-head wrench facilitates 1/4" screw removal in hard-to-get-to places.

headed self-tapping metal screws. These are sometimes difficult to grasp with a regular hex wrench. I have found that a taper-ground tip of a 1/4" wrench is a great tool for removing these screws when they are located in close quarters and hard-to-get-to places. — *Bud Mierkey, Largo, Fla.*

... Trouble Shooting

Continued from page 37

rather than the center as well as the extremes shown for the Losser type network in Figs. 4B and 5B.

It is not unusual for a customer to complain of insufficient boost or cut. Your bench tests at 50 and 10,000 cycles will probably show the controls to be operating satisfactorily. Visual examination is very likely to prove the circuit to be of the Baxendall variety.

The answer to this is in the two curves. Because the Losser type affects the mid frequencies more, the effect is more obvious.

Actually, the Baxendall network is probably preferable. The feedback reduces distortion. The system permits control over that portion of the curve where most boost or cut is necessary. The apparent insufficient boost or cut does not condemn the network, but some other weak link in the hi-fi chain. Find this weak link and you will probably have a new component sale on your hands. ■

TRIPLETT

EXTRA QUALITY IS HIDDEN*


MODEL 630 V-O-M PRICE 1 \$49.50

Standard Of The Industry



USES UNLIMITED:

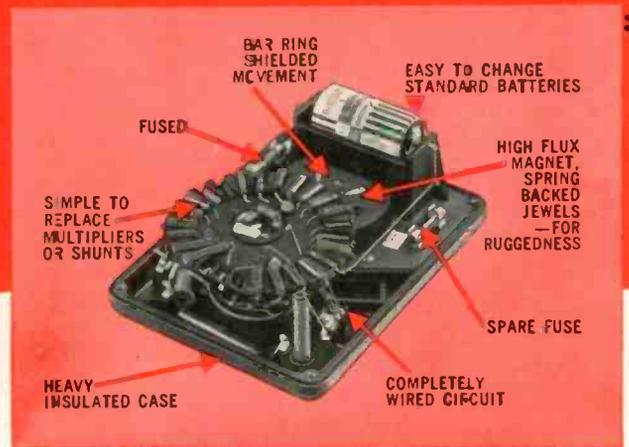- Field Engineers
- Application Engineers
- Electrical, Radio, TV, and Appliance Servicemen
- Electrical Contractors
- Factory Maintenance Men
- Industrial Electronic Maintenance Technicians
- Home Owners, Hobbyists



FACTS MAKE FEATURES:

- 1** Popular streamlined tester with long meter scales arranged for easy reading. Fuse protected.
- 2** Single control knob selects any of 32 ranges—less chance of incorrect settings and burnouts.
- 3** Four resistance ranges—from .1 ohm reads direct; 4½ ohm center scale; high 100 megohms.

Attention to detail makes the Triplet Model 630 V-O-M a lifetime investment. It has an outstanding ohm scale; four ranges—low readings .1 ohm, high 100 megs. Fuse affords extra protection to the resistors in the ohmmeter circuit, especially the XI setting, should too high a voltage be applied. Accuracy 3% DC to 1200V. Heavy molded case for high impact, fully insulated.

**630A same as 630 plus 1½% accuracy and mirror scale only \$59.50*

TRIPLETT ELECTRICAL INSTRUMENT COMPANY, BLUFFTON, OHIO

RANGES

DC VOLTS	0-3-12-60-300-1,200-6,000 at 20,000 ohms per volt.
AC VOLTS	0-3-12-60-300-1,200-6000 at 5,000 ohms per volt.
OHMS	0-1,000-10,000.
MEGOHMS	0-1-100.
DC MICRO-AMPERES	0-60 at 250 millivolts.
DC MILLI-AMPERES	0-1.2-12-120 at 250 millivolts.
DC AMPERES	0-12.

DB: -20 to +77 (600 ohm line at 1 MW).

OUTPUT VOLTS: 0-3-12-60-300-1,200; jack with condenser in series with AC ranges.

... for more details, circle 56 on last page



THE WORLD'S MOST COMPLETE LINE OF V-O-M'S. AVAILABLE FROM YOUR TRIPLETT DISTRIBUTOR'S STOCK

FREE LITERATURE

To receive the literature below without charge, simply circle the number on the coupon

- 1** **Antennas:** Literature on citizens band antennas include three new models. Covered also are antenna accessories and the DB-27 display. Antenna Specialists Co.
... for more details, circle 301
- 2** **CB Transceivers:** Literature covers a 5-watt, fully transistorized citizens band transceiver. Cadre Industries Corp.
... for more details, circle 302
- 3** **Capacitors:** A "Periodic Table" covers 18 major types of capacitors. Electrical and operating characteristics, and formulas employed in circuit design included. Chart measures 3'x2'. Cornell-Dubilier Electronics.
... for more details, circle 303
- 4** **Package Shipping:** Literature covers comparative costs by bus, rail express, air freight. Gives facts on products carried, weights, sizes, service, speed and frequency. Greyhound Corp.
... for more details, circle 304
- 5** **Loudspeakers:** Specification sheet CSP-102 gives complete technical details on new model K-950, 8" 2-way coaxial distributed sound loudspeaker. Jensen Mfg. Co.
... for more details, circle 305
- 6** **Home Study Courses:** Booklet covers a number of home study courses including: Television Servicing; Communication Electronics; Automation Electronics; Computer Programming; Transistors; and Color Television. RCA Institutes, Inc.
... for more details, circle 306
- 7** **Suppressors:** Catalog 61-KV-10 covers "Klipvolt" selenium transient voltage suppressors for reduction of transient voltages generated by motors, relays and switches. Available in polarized designs for d-c applications; non-polarized for a-c. Sarkes-Tarzian, Inc.
... for more details, circle 307
- 8** **Rectifiers:** Illustrated bulletin S-105 covers diffused silicon controlled rectifiers. Includes ratings, characteristics, performance data, applications and specifications. Semicon, Inc.
... for more details, circle 308
- 9** **Transistors:** A new chart lists approximately 2,000 transistor types most commonly used in TV, radio, hi-fi, auto and home equipment, with manufacturer's number and replacement. Includes base diagrams of five types showing locations of the leads. One section is devoted to the firm's American-made replacements for Japanese and other foreign made transistors. Chart measures 17"x22". Semitronics Corp.
... for more details, circle 309
- 10** **Parts:** Kit, model 31T 3890, covered in literature, contains mechanical and electrical parts to be used in conjunction with Sec. II of Standard Cross Reference Guide; and make up 90% of replacement parts most commonly used in field service. Standard Kollsman Industries, Inc.
... for more details, circle 310
- 11** **Antennas:** Literature covers: T-Bird (non-powered) antennas, six models; and T-Bird (powered) antennas, three models. Features include 7/16" tubing and "Delta" ("T" match) feed system. Technical Appliance Corp.
... for more details, circle 311

CUT HERE

3-62

Cut out and mail to ELECTRONIC TECHNICIAN, 1 East First Street, Duluth 2, Minn.

Use this coupon, or your letterhead, before April 20, 1962

Please send me literature of companies whose code numbers I have circled below (includes editorial and advertised items):

ADVERTISED PRODUCTS

10	23	36	50
11	24	37	51
12	25	38	52
13	26	39	53
14	27	40	54
15	28	41	55
16	29	42	56
17	30	43	57
18	31	44	58
19	32	45	59
20	33	46	60
21	34	47	61
22	35	48	62
		49	63

NEW PRODUCTS

400	404	408	412
401	405	409	413
402	406	410	414
403	407	411	415
FREE LITERATURE, CATALOGS, BULLETINS			
301	305	309	314
302	306	310	315
303	307	311	316
304	308	312	317
		313	318

Name.....Position.....

Firm.....Address.....

City.....Zone.....State.....

Note: If you have given your residence address, please enter your company name and address on this line:



TVL TWIST-LOK® CAPACITORS

These 'lytics take on the toughest TV and radio duty, give maximum trouble-free service, *without HUMMM!* They are dependable at extremely high and low temperatures. Cathodes are etched to meet the needs of high ripple currents, high surge voltages.




TVA ATOM® CAPACITORS

Atom tubulars are service favorites because they fit anywhere, work anywhere. They're the *only* small size 85 C (185 F) capacitors in ratings up to 450 WVDC. They have low leakage current, long shelf life, and withstand high ripple currents, high surge voltages.



TE LITTL-LYTIC® CAPACITORS

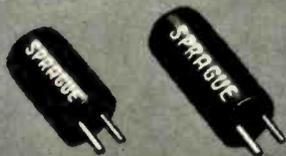The very best ultra-miniature replacements for transistor circuits, offering unusual reliability through all-welded construction. No pressure joints to cause "open" or intermittent circuits. Long shelf life—extremely important in sets used only part of the year.



VL VERTI-LYTIC* CAPACITORS

These single-ended molded tubulars are the ideal replacement for units of this type found on printed wiring boards. Keyed terminals assure fast manual mounting and correct polarity. Resin end fill protects against drying of electrolyte or entrance of external moisture.



PCL PRINT-LOK® CAPACITORS

The printed circuit version of the Twist-Lok. Universal base replaces any of the printed circuit 'lytics in use today. No makeshift mounting adapters to damage capacitor or add extra height . . . no possibility of high resistance contacts.

EVERY 'LYTIC YOU NEED . . .

- every value
- every rating
- every style

Shown here are the more popular of Sprague's big family of Electrolytic Capacitors, the broadest in the industry. Other types include Metal-encased Screwbase; Plastic-encased High-MF; Metal-encased Octal-base; Ultra-low leakage Photoflash. All are listed and described in Sprague's NEW Catalog C-614. Get your copy from any Sprague distributor, or write Sprague Products Company, 65 Marshall Street, North Adams, Massachusetts.

*TRADEMARK

SPRAGUE®

THE MARK OF RELIABILITY

WORLD'S LARGEST CAPACITOR MANUFACTURER

--- for more details, circle 52 on page 50

NEW PRODUCTS


G-E TV RECEIVERS

Three new TV receivers are: "The Century," 19" luggage style portable; has power transformer chassis, chrome carrying handle and 6"x2" front mounted speaker; three luggage finishes; \$169 to \$179. The "Fashion Designer," 21" table model; has power transformer chassis, front controls and front speaker; two cabinet finishes; \$199 to \$209. The "Golden Celebrity," 19" portable; has power transformer chassis, fold-away luggage carrying handle and power cord wind-up bracket at rear of set; three cabinet finishes; brass-finish roll-about stand and magazine rack offered free with "Golden Celebrity" but price of set not announced. Radio & Television Division General Electric Co., Electronics Park, Syracuse, N. Y.

... for more details, circle 400 on page 50

Fisher ADAPTOR

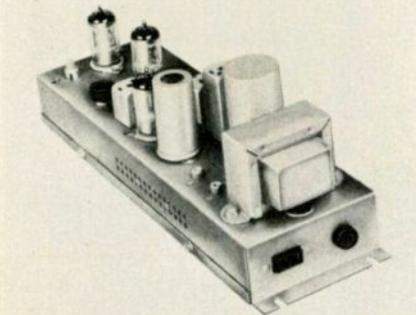Multiplex adaptor, model MPX-200, companion to Fisher Universal MPX-100, is designed especially for those who desire a unit for concealed installation. It is self-powered, compact and easily con-




ected. Can be placed up to three feet from the tuner or receiver. Features include: special control for matching exactly to the tuner or receiver with which it is used, requires setting only at time of installation; two controls to assure identical output levels from both channels; and selector switch to record stereo programs monophonically. Internal circuitry contains a 15 kc steep roll-off, low-pass filter for suppression of the 38 kc sub-carrier and side-bands. \$79.50. Fisher Radio Corp., 21-21 44th Drive, Long Island City 1, N. Y.

... for more details, circle 401 on page 50

Conar GENERATORS

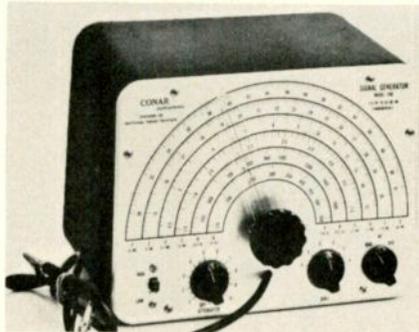Model 280 signal generator uses Hartly-type oscillator circuitry for stability plus pre-set, tuned r-f coils on low bands and ceramic trimmers on high bands. Average accuracy, without further alignment, 2%. Frequency coverage, 170 kc to 60 mc on six bands; 60 mc to over 120 mc on harmonics. Planetary drive



tuning capacitor with 6:1 ratio eliminates backlash. Has solid state power supply. Kit, \$21.50. Wired, \$29.50. Conar Instruments Div., National Radio Institute, 3939 Wisconsin Ave., Washington 16, D. C.

... for more details, circle 402 on page 50

Mercury TUBE TESTERS

Deluxe model 1200 dynamic mutual conductance tube tester features push-button settings to permit testing of any tube, under actual dynamic conditions, in a few seconds. It tests new type tubes including nuvistors, novars, compactrons and new 10-pin tubes; foreign and hi-fi tubes, voltage regulators, battery type tubes, auto hybrid tubes, thyratrons and most industrial tube types; black and white picture tubes, transistors, and batteries. Range of operation includes tests for true dynamic mutual conductance (Gm), tests for shorts and leakage between any tube elements, and for gas and grid emission. Has automatic line voltage regulation, 4½" meter; built-in 7-pin and 9-pin straighteners on



panel; and phosphor bronze tube sockets. Housed in leatherette case with compartment for cables. 18¼" x 10¾" x 4¾". \$119.95. Mercury Electronics Corp., 111 Roosevelt Ave., Mineola, N. Y.

... for more details, circle 403 on page 50

Sylvania RADIOS & TV RECEIVERS


Supplementing 1962 lines, and introduced as "drop in" models at the International Home Furnishings Market are: Table radio models, AT15 and AT16, provides 6-tube performance with one rectifier, 4" front-mounted speaker, di-

rect drive tuning, built-in ferrite rod antenna and engraved circuit chassis. 6"H, 13½"W, 5¾"D. \$19.95 and \$22.95. Also models 19P11B and 19P11E, newly styled versions of 19P11, 19" portable TV receiver. The 19P11 luggage-style cabinet has a wrap-around metal midsection and molded plastic front and back, is equipped with the firm's Bonded Shield picture tube and Super S-110 engraved circuit chassis, 3x5-inch speaker is mounted on top of set and angled toward the viewer, has top controls and chrome monopole antenna. New version 19P11B has weight-balanced plastic carrying handle. Deluxe model 19P11E has metal carrying handle. Sets are 12¾" deep. Weight, 40 lbs. A metal stand with 3-inch casters has been designed for each of the new portable models. Model 19P11B with stand \$159.95. 19P11E with stand, \$169.95. Radio & Television Div., Sylvania Electric Products, Inc., Batavia, N. Y.

... for more details, circle 404 on page 50


University SPEAKERS

Shown are two Uniline columns now available in PA loudspeakers. Model UCS-6, 60" column (6 extended-range 8" speakers); frequency range, 35-17,000 cps; 150 watts IPM; impedance, 16 ohms. \$179.95. Also model CS-4, 40" column (4 extended-range 8" speakers); frequency range, 45-17,000 cps; 80 watts IPM; impedance, 8 ohms. \$129.95. Soon to follow will be a lower powered speech model and a weatherproof music and

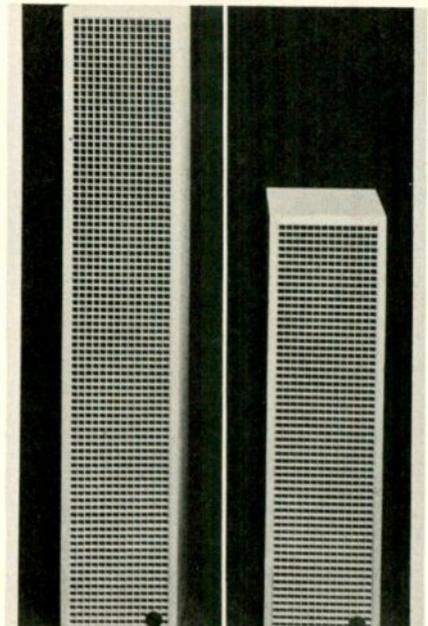

speech model. University Loudspeakers, Inc., 80 S. Kensico Ave., White Plains, N. Y.

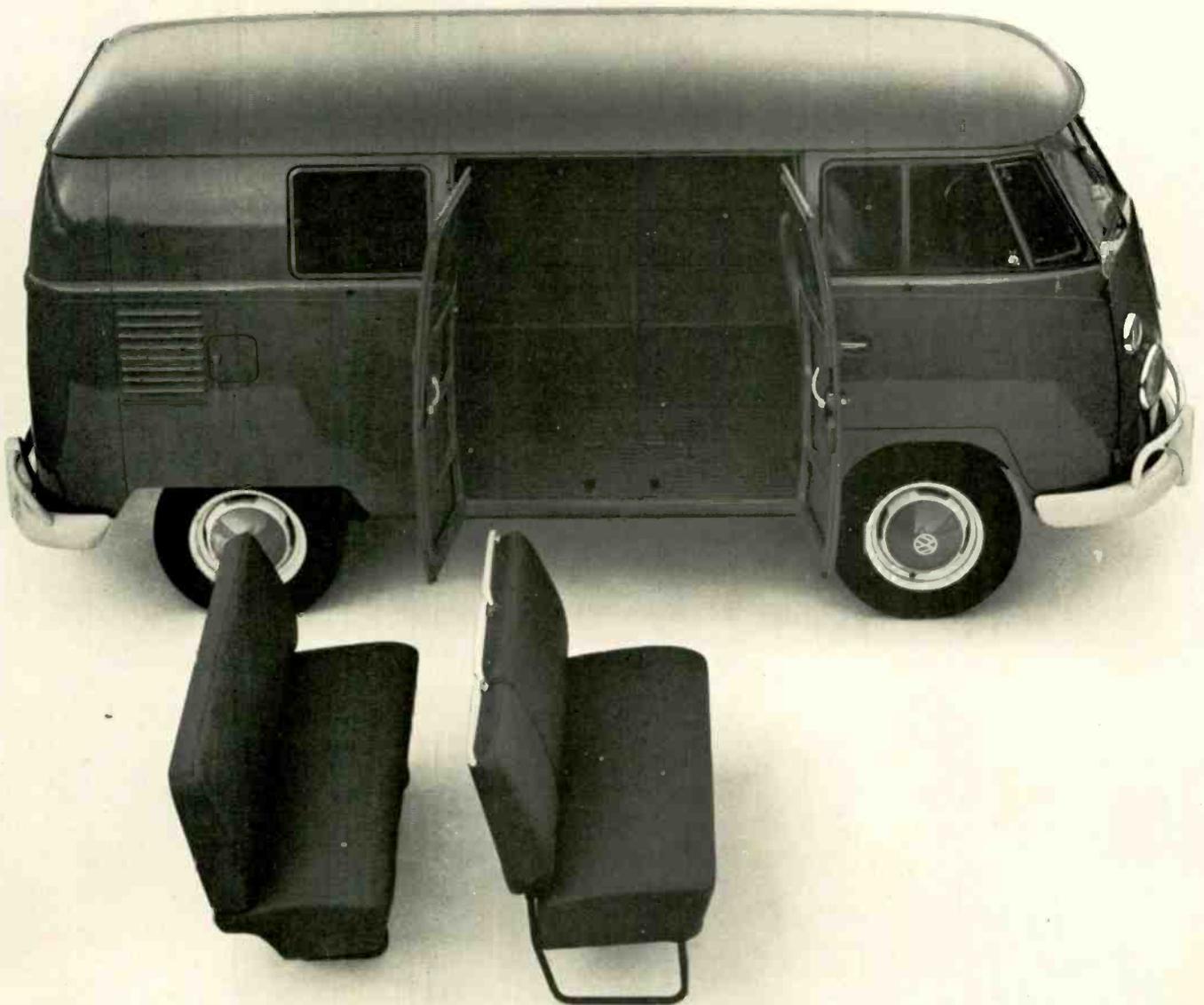... for more details, circle 405 on page 50



©1962 VOLKSWAGEN OF AMERICA, INC. *SUGGESTED RETAIL PRICE, EAST COAST, P.D.E.; \$2,115 WEST COAST.

The truck that thinks it's a station wagon.

We made it with seats and windows.
But a truck is what it is.

Take out the seats and you can put in
1,786 pounds of anything.

In just about any size or shape. The
doorway's almost 4 feet wide.

For business deliveries, this Volkswagen
costs so little to run that you can make a
profit even on dinky orders.

2½¢ a mile seems to be average for
most owners. For gas, tires, everything.

(Almost all our trucks get over 20
miles a gallon. Some even get 30.)

For weekends, you can take 8 relatives
anywhere you might want to take 8 rela-
tives.

(If you're just taking them away, there's
room for their luggage on the rear shelf.

All their luggage.)

We call this the Volkswagen Kombi.
All the usual VW virtues go with it.
Rear-engine traction in snow and sand.
The air-cooled engine that can't freeze
up or boil over. And the price,
another interesting VW virtue.

\$2,095.*

New.



--- for more details, circle 61 on page 50

General Electric reporter,
Roland Kempton, makes the rounds with
the independent service dealers . . .

Don Ellis saved
30 minutes
and \$3.75
because
one G-E
SERVICE-DESIGNED
capacitor takes
the place of 4
ordinary types

In minutes and money, Don Ellis and George Bentley, owners of QUALITY TV, Kansas City, Mo., measure some of the advantages of stocking G-E Service-Designed capacitors. Don (shown here) put it this way, "We didn't stock can-type capacitors before because we never knew what types we'd need. Now, with just 25 or 30 capacitors in stock we meet most of our requirements, and we don't have to make special trips to pick up exact replacements. I figure this saves 30 minutes and \$3.75 per trip."


And according to George, "There have been many occasions, especially on Saturdays, when we've been able to get the set out because we've had G-E capacitors in stock. Our customers really appreciate it, and we haven't had a single call back."


Yes, it pays to stock General Electric Service-Designed capacitors. Get full details from your G-E capacitor distributor. General Electric Company, Electronic Components Division, Room 1719, Owensboro, Kentucky.

Progress Is Our Most Important Product

GENERAL  ELECTRIC

 **ELECTRONICS**

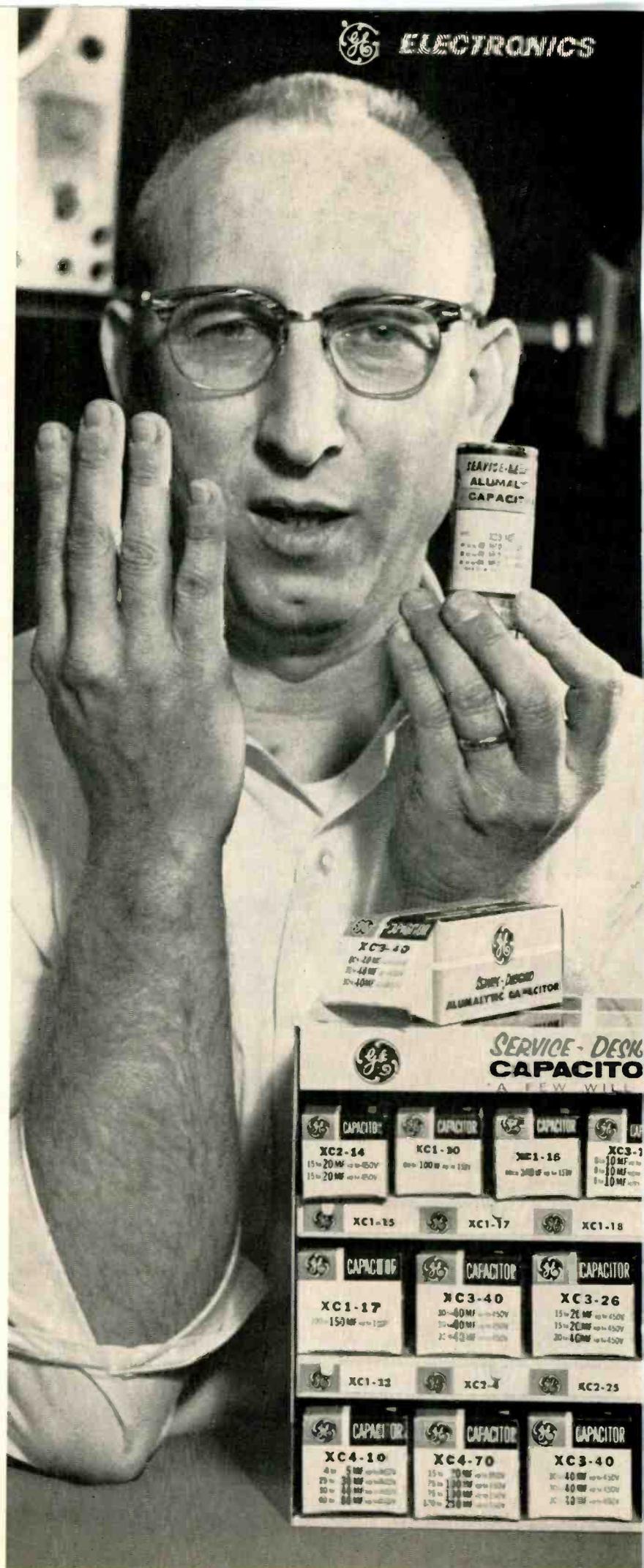

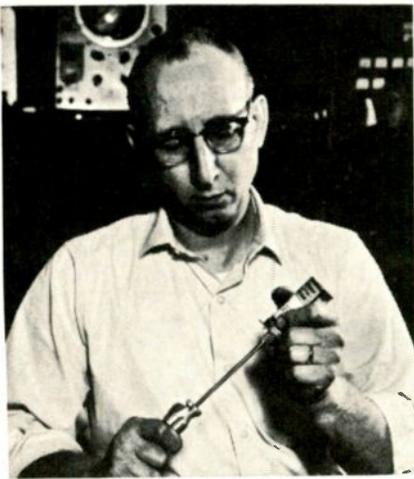


Another New Service Aid
From General Electric

SERVICE-DESIGNED

Capacitor Tab Adjuster saves time—easier to use than pliers

"How soon can I get a couple
of them?"

That was Don Ellis' first comment after he tried out this new tab adjuster. This handy Service Aid from General Electric is easier to use than needle-nose pliers—saves time on service calls and at the bench. The slotted end fits over capacitor tabs; won't slip off. A quick twist locks or unlocks the tabs. 8 inches long; plastic handle. Here's one of the most useful Service-Designed tools for the bench and in your service case. Order now from your G-E capacitor distributor or mail coupon to Chicago warehouse address shown.

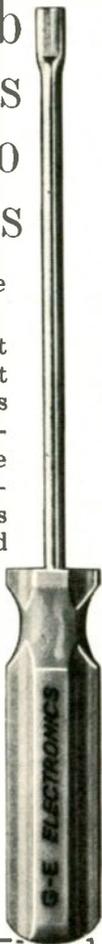

Progress Is Our Most Important Product

GENERAL ELECTRIC

General Electric Company, Dept. B
3800 N. Milwaukee Ave., Chicago 41, Ill.
Please ship prepaid:

..... ETR-2968 Capacitor Tab
Adjuster, \$1 each.

My check or money order is enclosed
for the required amount plus any sales
or use tax applicable in my area.

Name.....

Address.....

City.....Zone.....State.....

--- for more details, circle 26 on page 50

NEW PRODUCTS

Zenith RADIOS

Royal models 90, 125, and 650 small size transistor radios use new advanced design "Powersonic" transistors for greater sensitivity and range. Both royal 90 and 125 provide 80 milliwatts power output and have automatic volume control. Each plays 180 hours on two mercury batteries, or up to 75 hours with two penlite cells. Royal 125, deluxe in design, and equipped with vernier tuning dial. \$26.95 and \$29.95 respectively, less batteries. Royal 650 personal-size portable has 3½" cone speaker, provides 200 milliwatts of power output, has inverse feedback circuit, operates on 4 mercury cells or 4 penlite batteries. \$34.95, less batteries. Empress model FM-AM clock-radio with afc has sleep switch, radio buzzer alarm, appliance outlet, AM-AFC-FM and FM selector switch. \$69.95. Dreamland model AM clock-radio has a radio and buzzer alarm. \$29.95. Trumpeteer model table radio has advanced AM chassis and direct tuning control. \$19.95. Executive model has AM chassis in a cabinet only 3½" deep, 6"x4" speaker and automatic volume control. \$29.95. Conelrad or Civil Defense station frequencies, clearly indicated on dial scale of each radio. All models available in a variety of cabinet colors. Zenith Sales Corp., 6001 W. Dickens Ave., Chicago 39, Ill.

... for more details, circle 406 on page 50

Sprague CAPACITORS

EK-5 Verti-Lytic capacitor assortment consists of 30 miniature single-ended electrolytic capacitors (two each of the



15 most-frequently-used ratings) in an attractive blue case which has individually identified compartments. Space-saving Verti-Lytics, with their molded phenolic cases and moisture-resistant resin and seals, have low leakage current and long shelf life. Ideal for vertical mounting on printed wiring boards in crowded transistorized radios. Handy plastic case, free. Capacitors, \$31.92. Sprague Electric Co., North Adams, Mass.

... for more details, circle 407 on page 50

Switchcraft CORDS

Molded replacement headphone cords for Brush and RCA headphones feature a standard parallel cable with gray colored plastic jacket over two tinsel conductors #27 ga. Standard 2-conductor phone plug with cable clamp is molded securely to one end of cable. Molded "Y" junction strengthens the "Y" ter-




mination. They are recommended for replacement on most mono headset cables and are exact replacements for cable on Brush BA-200, BA-205 and BA-206 headsets; also RCA MI-38107B headset. No. 05KF88 has 2 feet of cable from phone plug to "Y" junction, \$3.00. No. 05KJ88 has 4 feet of cable from phone plug to "Y" junction, 1 foot of cable from "Y" junction to eyelet plugs, \$3.20. Switchcraft, Inc., 5555 N. Elston Ave., Chicago 30, Ill.

... for more details, circle 408 on page 50

Winegard ANTENNAS

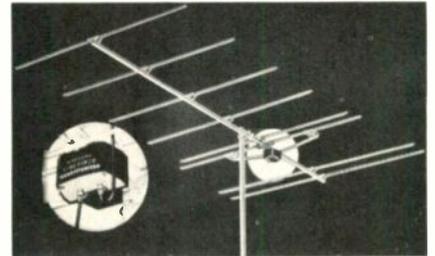Introduced are two new amplified FM antennas reported to pick up 85% of all FM stations in a 200 mile radius from



any location over normal terrain. Model PF-8 Stereo-Tron Yagi, gold anodized, minimum gain, 26 db over a folded dipole, flat frequency response, -¼ db from 88 to 108 mc. Features built-in TV-FM coupler and has 8 elements with "Tapered T" driven element directly coupled with the transistor amplifier. Available two ways: model PF-8 for 300 ohm twin lead; PF-8C for 75 ohm coax. Electronic turnstile, also gold anodized, non-directional, 16 db gain in all directions over a folded dipole. Has offset mount and transistor amplifier with built-in TV-FM coupler. The Electronic Turnstile model PF-4 has 300 ohm output only. Both models can be used with one power supply and down lead when used with a Winegard Powertron TV antenna. Winegard Co., Burlington, Iowa.

... for more details, circle 409 on page 50

Knight TUNERS

Model KN-250M ultra-compact stereo FM tuner features advanced transistor-novistor design for both FM stereo and



regular broadcast reception. Intended for addition to existing stereo hi-fi systems, it is not much larger than the average book. Dimensions, 2-5/8 x 9-3/4 x 8

NEW PRODUCTS

inches. Housed in dark brown metal cabinet, designed for perfect match with KN-400B amplifier. Has built-in multiplex circuit. Single strength meter shows quickly when tuning in on center channel for peak strength. Usable IHFM sensitivity, 2 μ volts for 30 db of quieting. \$139.95. Also, not shown: similar unit without stereo FM, \$99.95; and KN-250MC with built-in clock timer, \$154.50. Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

... for more details, circle 410 on page 50

Sencore SUBSTITUTORS

Model RC121 component substitutor, a new compact unit, is designed for on-the-spot substitution of carbon and power



resistors, capacitors, electrolytics and rectifiers. Each section offers a complete range, can be used independently, and

is identical to the equivalent single unit (H36, ES102, PR111 and RS106) except for the electrolytic which is vastly improved. It allows substitution for all dual electrolytics as well as singles. Over 25 combinations of capacitor values can be substituted by using the electrolytics as singles, duals or paralleling them to double capacity. Surge protector prevents arc, spark or heating of capacitors being bridged and automatically discharges both electrolytics when released. \$39.95. Sencore, Inc., 426 S. Westgate Drive, Addison, Ill.

... for more details, circle 411 on page 50


Ward CB ANTENNAS

Designed around their "8"-ball concept, a new L-Coil Citizens Band antenna is said to work equally well on citizens band frequencies and on AM broadcast reception. Dual L-Coil antenna comes in kit form which can be easily installed in present mounting position on most cars and trucks. Ward Products Corp., Edson St., Amsterdam, N. Y.

... for more details, circle 412 on page 50

Hitachi TAPE RECORDERS

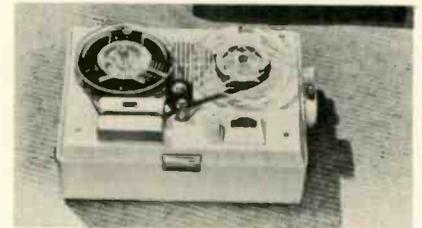Model TRQ-370 seven transistor portable tape recorder has two speeds, 3-3/4 inch/sec, and 1 1/2 inch/sec. with a max-



imum recording time of 68 minutes. Has "fast forward" speed-up device, single dial "one-control system" and level meter. Operates on four flashlight cell batteries. Printed circuit eliminates wiring breakdowns. Output, 500 mW. Takes 3" recording tape. 2 1/2" PM speaker. Complete with accessories, including dynamic microphone, monitor earphone, reel, tape, extension cord, leather carrying case. \$199.95. Sampson Co., 2244 S. Western Ave., Chicago 8, Ill.

... for more details, circle 413 on page 50

Seco TUBE TESTERS

Model 350 tube tester has sockets for the newest tubes. The panel includes 86 sockets wired through a selector switch and load system to extend tube type coverage by at least four times, with over 2200 types listed. It incorporates a VTVM type meter circuit, and the power circuit is short-circuit proof. No fuse required. Includes an automatic constant voltage regulated transformer for 100-130 volts, 50-60 cps and has an accessory panel including electronic battery analyzer, fuse and lamp continuity check and vibrator tester. \$179.50. Also, not shown, model 360, 105-125 volts, 50-60 cps. Has manual line adjustment. Does not have accessory panel. \$149.50. Seco Electronics, Inc., 5015 Penn Ave. South, Minneapolis 19, Minn.

... for more details, circle 414 on page 50

THAT SOLVES ALL YOUR TV TUNER PROBLEMS

Ask yourself

... do you have the time to fool around drilling, sawing, filing ... trying to make a "Universal" replacement tuner fit in place of the original?

... do you have all the expensive instruments and equipment to complete the alignment so essential after each tuner repair or replacement?

... can you spare the time repairing and adjusting your own TV tuners and can you charge enough to justify the time spent?

A Castle Overhaul eliminates every one of these problems. Castle replaces all defective parts, (tubes and major parts are extra at net prices) and then aligns your tuner to the exact, original specifications.

Simply send us your defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint.

Send for FREE Mailing Kit and complete details.

ONE PRICE

9⁹⁵

ALL MAKES

VHF TUNERS
UHF TUNERS
UV COMBINATIONS*

*UV combination tuner must be of one piece construction. Separate UHF and VHF tuners with cord or gear drives must be dismantled and the defective unit sent in.

90 Day Warranty

CASTLE
TV TUNER SERVICE, INC.


Pioneers in



TV Tuner Overhauling

5710 N. Western Ave., Chicago 45, Illinois • 653 Palisade Ave., Cliffside Park, New Jersey
In Canada: 136 Main St., Toronto 13, Ontario

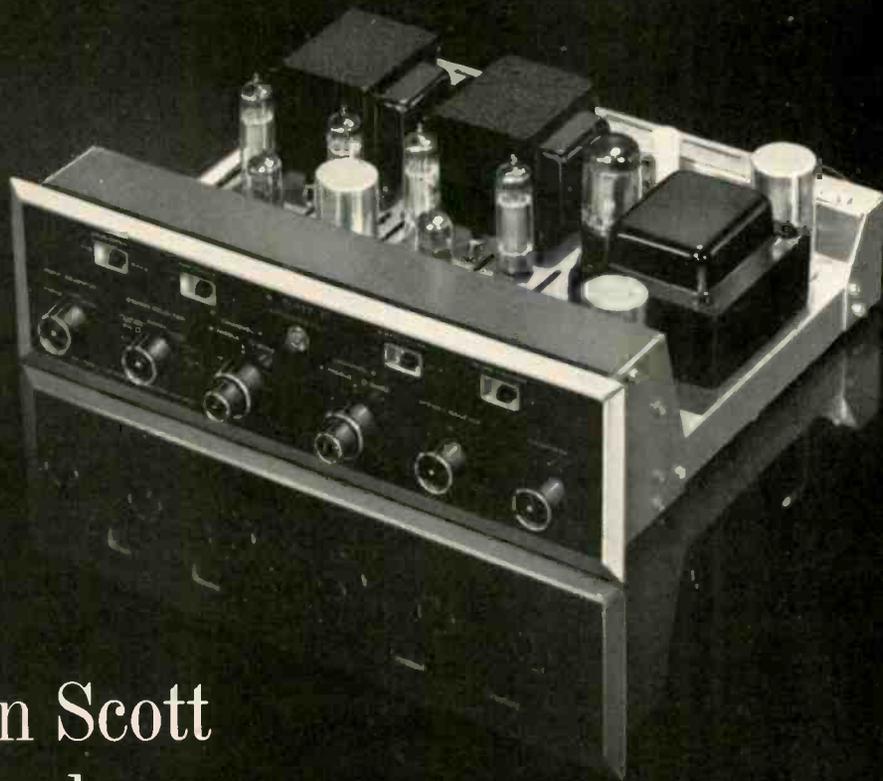... for more details, circle 16 on page 50



Hermon Scott could make this new kit for \$30 less, If...

Hermon Scott faced a basic choice . . . bring out his new LK-48 amplifier kit at \$124.95 or make it to sell for \$30 less like many other amplifier kits. All his engineering department had to do was make a few compromises.

The LK-48 is rated at 48 watts. By using a smaller power supply, ordinary output transformers, and pushing the output tubes to their limits, the amplifier might still produce 48 watts at 1000 cycles where many amplifier kits are rated. But measured at 20 cycles, where Scott engineers feel power is really important, output would be down considerably. No compromise was made. The LK-48 *actually* produces 28 watts per channel at 20 cycles, and delivers full power throughout the audio range.

Many kits use a one color instruction book. Hermon Scott decided to continue to use full color to insure factory-built performance, even at the hands of a novice.

Important Scott engineering extras like the all-aluminum chassis, DC operated preamp heaters and unique hum-null balancing could have been eliminated. Hum would have been audibly higher and distortion at levels normal to many kits, but Hermon Scott felt that the kit builder was entitled to the same performance he has come to expect from Scott factory-wired units.

Yes . . . Hermon Scott could have made the LK-48 to sell for \$30 less . . . but it would have meant compromising life-long standards. This is something he would never do. You can choose any Scott kit with complete confidence — the LK-48, the LK-72 80 watt complete stereo amplifier, the LK-150 130 watt stereo power amplifier, the LC-21 professional preamplifier, the LT-110 multiplex tuner, LT-10 FM tuner or the LM-35 multiplex adaptor. These superb kits have all the features and performance you've come to expect from the world's leader in audio engineering.



H. H. SCOTT INC., 111 Powdermill Rd., Maynard, Mass. Dept. 140-03

Please rush me your new full-color brochure telling about Scott's full line of superb stereo kits.

Name

Address

City State

Export: Morhan Exporting Corp., 458 Broadway, N.Y.C.
Canada: Atlas Radio Corp., 50 Wingold Ave., Toronto.
Prices slightly higher West of Rockies.

ANOTHER SERVICE-PROVED

PRECISION
INSTRUMENT
MODEL 650
GRID CIRCUIT
ANALYZER
TUBE TESTER
AND
MEGOHMMETER



Tests most tubes including 10-pin miniatures, 12-pin Compactrons, 5- and 7-pin Nuvistors, Novars, octals, picture tubes (with optional adapter AD-65) and a wide variety of foreign and industrial types. Indicates gas currents as low as 1 ua. Checks for intermittent shorts, gas content, grid emission, leakages (sensitivity over 100 megohms). Special megohmmeter circuitry for measurement of condenser leakage, continuity and leakage of printed circuitry. Complete in leatherette-covered case. See your PRECISION distributor or write today for a complete catalog. Net only \$69.95. AD-65 Adapter: Net only \$5.95. This and all other PRECISION PRODUCTS are guaranteed for one full year


PRECISION APPARATUS CO., INC.

SUBSIDIARY OF PACOTRONICS, INC. 70-3184th ST., GLENDALE, NEW YORK

for more details, circle 39 on page 50

NEW PRODUCTS

Don Bosco SIGNAL TRACERS

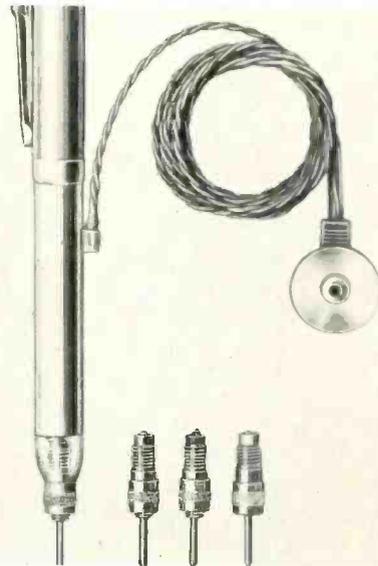

The "Siethotracer," a pen-size signal tracer quickly locates hum, oscillations, ground loop, printed circuit breaks, and other common defects. Detects and demodulates any low level μ watt audio or modulated radio frequency signal, and then amplifies it 1,000 times in a button earphone. The signal may also be observed on a scope, using an optical plug-in scope adaptor. It can be used as a pre-amplifier and is ideal for testing and troubleshooting radios, amplifiers, phonographs, magnetic tape recorders, phono pickup cartridges, dictating machines, and hearing aids. Also ideal for running continuity tests on capacitors, transistors, and other components. Complete with earphone, cord, three interchangeable attenuator probes and r-f detector-modular crystal diode probe, ground clip and battery. \$29.95. Don Bosco Electronics, Inc., Littell Rd., Hanover, N. J.

ers, phono pickup cartridges, dictating machines, and hearing aids. Also ideal for running continuity tests on capacitors, transistors, and other components. Complete with earphone, cord, three interchangeable attenuator probes and r-f detector-modular crystal diode probe, ground clip and battery. \$29.95. Don Bosco Electronics, Inc., Littell Rd., Hanover, N. J.

for more details, circle 415 on page 50

TRU-VAC

REPEAT OFFER!
BUY 1 TUBE AT THE REGULAR PRICE AND GET EVERY SECOND TUBE FOR JUST 1c

1c sale

EACH TUBE COSTS YOU ONLY 17 1/2c EACH, AND IN QUANTITIES OF 100 TUBES ONLY 16 1/2c EACH!

1c SALE ONLY ON TUBES LISTED BELOW!

*For every tube you buy at 35c each, YOU GET A SECOND TUBE FOR JUST ONE PENNY!

*Buy 100 tubes for 33c each and GET AN EXTRA 100 TUBES FOR JUST \$1! Take your pick . . . tube types may be mixed!

6AU6 6CG7 6W4GT
6AC7 6SN7GT 12SQ7

LOOK! 1,000 USED TV'S
Costly, famous make console models with little or no tube replacement! Require only minor adjustment. Perfect for resale, or as your own second set! 16", 17" and 19" screens none smaller! Sets shipped FOB, Harrison, N.J.

\$16.95 As Is

1-yr. guaranteed Radio & TV Tubes

Factory Used or Factory Second Tubes! TRU-VAC will replace FREE any tube that becomes defective in use within 1 year from date of purchase!

ALL TUBES INDIVIDUALLY BOXED!
CODE DATED & BRANDED "TRU-VAC"

Partial Listing Only . . . Thousands More Tubes in Stock!

SPECIAL!	6CB6 . . . 30¢	6CQ8 . . . 30¢
0Y4 3BN6 5V4G 6AU5GT 6B06GT 6CS7 6SA7 7A4/XXL 7Q7	0Z4 3RZ6 5V6GT 6AV7 6B07 6CU5 6SC7 7A5	12BA7 12SN7GT 36
1A7GT 3CB6 5X8 6AU8 6BR8 6CU6 6S07GT 7A6	1B3GT 3Q4 5Y3 6AV3GT 6BS8 6DE6 6SF7 7A7	12BD6 38
1H5GT 3S4 6A6 6AV6 6SV5G 6DE6 6SF7 7A8	1L4 3V4 6AB4 6AW8 6BZ6 6DG6GT 6SG7 7B4	12BE6 12V6GT 39/44
1L6 4BQ7A 6A4 6AX4GT 6BZ7 6DF6 6EM7 7B5	1N5GT 4BS8 6AF4 6AX5GT 6C4 6E5 6J7 7B6	12BF6 12W6GT 41
1R5 4BZ7 6AG5 6BB 6CA8 6F5 6K7 7B7	1S5 4C66 6AH4GT 6BA6 6C8 6F6 6SL7 7B8	12BH7 12X4 42
1T4 5AM8 6AH6 6BC5 6CD6G 6F6 6G6 7C4	1U4 5AN8 6AK5 6BC8 6CF6 6G6 6H6 7C5	12BL6 14A7/12B7 43
1U5 5AT8 6AL5 6BD6 6C8 6J5 6T4 7C6	1V2 5AV8 6AM8 6BE6 6CG8 6J7 6U5 7E5	12B8 48B 50A5
1X2 5A24 6AN8 6BF3 6CH8 6K9GT 6U8 7E6	2A4 5B7B 6AQ5 6BG6G 6CL6 6K7 6V6GT 7E7	12B7 14Q7 50B5
2B4 5C68 6AQ6 6BH6 6CM6 6N7 6W6GT 7F7	2CY5 5J6 6AQT 6BJ6 6CM7 6Q7 6X4 7F8	12CA5 17D4 50L6
3A5 5R4 6AR5 6BK5 6CN7 6S4 6X5GT 7G7	3AL5 5T8 6AS5 6BK7 6C8 6S7 6X8 7G7	12CN5 19AU4BT 56
3AU6 5U4 6AT6 6BL7GT 6CR6 6G8 6Y6 7H7	3BC5 5U8 6AU4GT 6BN6 6CS6 6S8GT 6V6GT 7A7	12D4 19B6G 80
		12E5 1918 84
		12F8 1978 80/6Z4
		12K5 24A 117Z3
		12K7 2526GT
		12L6 27
		12M7 35A5
		12R5 35B5
		12S7 35C5
		12S17 35W4
		12S7 35Z5

These tubes are made only from new parts and materials, except for the envelope which is re-used. Below listed prices do not include duty. Add Additional \$5.00 Deposit on tube sizes to 20"; on 21" and 24" tubes —\$7.50. Deposit refunded immediately when duty is returned prepaid. Aluminized tubes—\$4.00 extra. Picture tubes shipped only to continental USA and Canada—All tubes F.O.B., Harrison, N.J.

1-YEAR GUARANTEED TV PICTURE TUBES

Money cheerfully refunded Within Five (5) Days, If Not Completely Satisfied!

TRU-VAC (R) PAYS YOUR POSTAGE—On orders of \$5 or more in USA and Territories. Send approximate postage on Canadian and foreign orders. Any order less than \$5 requires 25c handling charge. Send 25% on C. O. D.'s. All orders subject to prior sale. Complying with Federal regulations, the following statement appears in all Tru-Vac advertising: Tubes in this ad may be FACTORY SECONDS or USED tubes and are clearly marked.

35¢ ea.

\$33 Per 100 TUBES

Any tube not listed also available at 35¢ each!

Sensational Offer!
"Self Service"
TUBE CHECKERS
\$37.95


FOB Dur Warehouse

Let your customers test their own tubes! These reliable, reconditioned 22-tester tube checkers will return your investment with little or no effort on your part! Handmade, gold-tipped console models COMPLETE WITH KEY FOR BOTTOM DOOR AND NEON-LIGHTED HEAD!

TRU-VAC Dept. ET2

Harrison Avenue • Box 107 • Harrison, N. J. Humboldt 4-9770

for more details, circle 57 on page 50

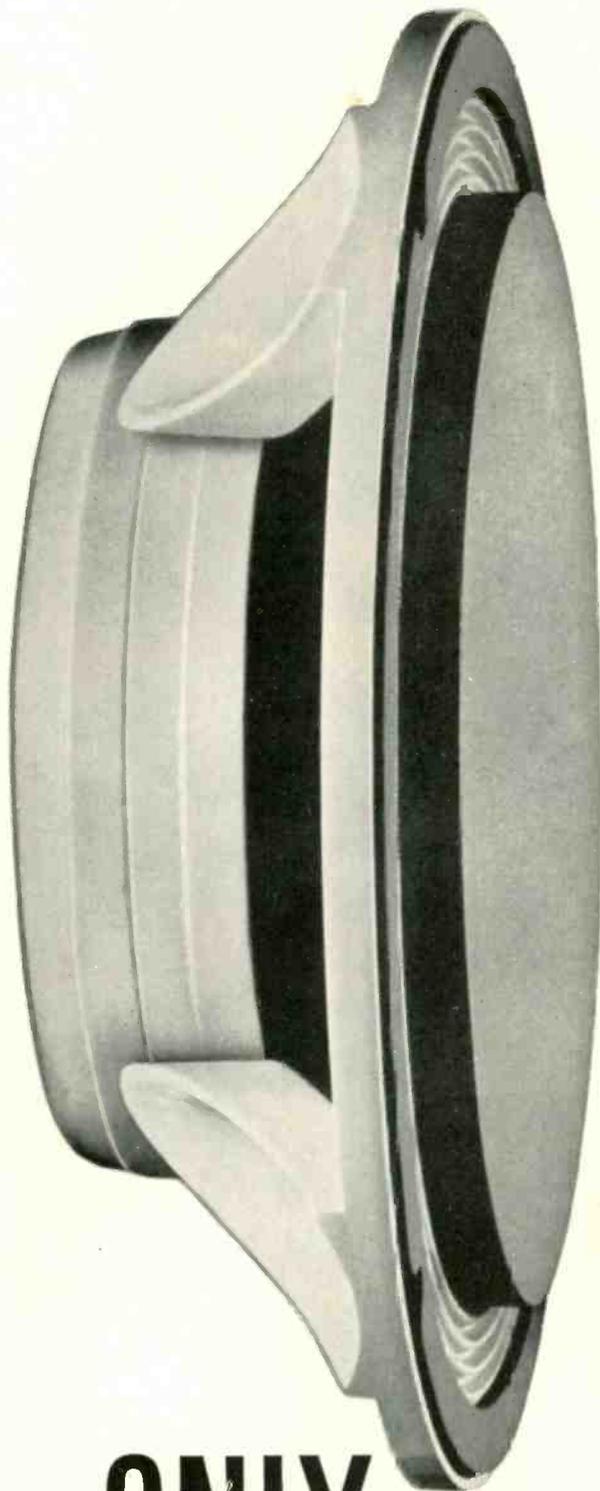


Only Jensen, in the new 3-P systems, has a woofer like this. It has a rigid, circular, POLYTEC* plane piston . . . an ideal acoustic radiator. It is so shallow it can go in a cabinet a mere 3⁵/₈" thin, yet has full-scale, long-travel, big-woofer performance.

One thing you won't find in 3-P systems is "bass-boom". The low end is so clean, so highly damped that exaggeration of sounds is impossible . . . every note, down to the extreme bottom, is reproduced with rare accuracy.



3-P Systems are for discriminating listeners. Six styles to choose from, priced at \$119.50 to \$159.50.

Write for Catalog 165-G.

*T.M.

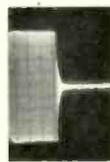

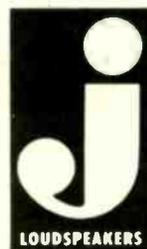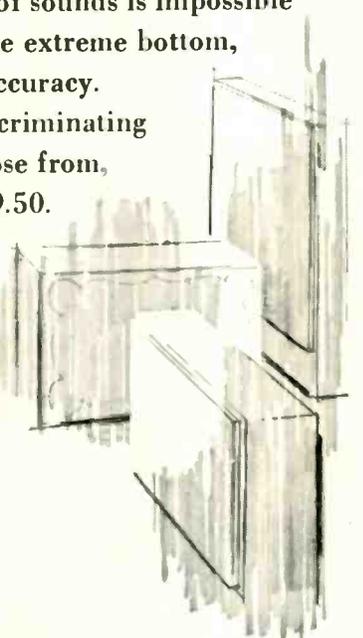Improved transient response means new, clear, clean sound without hangover.




jensen MANUFACTURING COMPANY
Division of THE MUTER COMPANY

ONLY ONE WOOFER LIKE THIS

Jensen Manufacturing Co., 6601 S. Laramie Ave., Chicago 38, Ill. / Canada: Radio Speakers of Canada, Ltd., Toronto / Mexico: Universal De Mexico, S.A., Mexico D.F.
... for more details, circle 32 on page 50

YOU WON'T FIND THIS FILTER

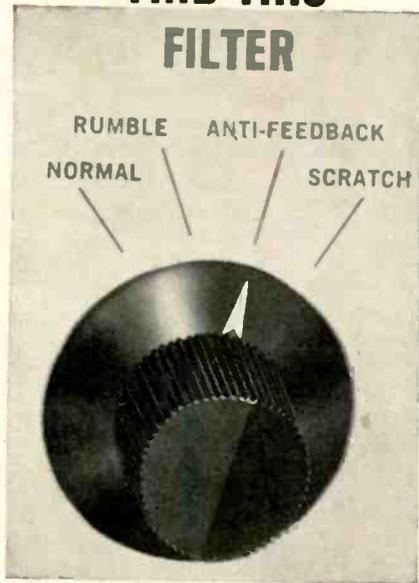

CONTROL ON ANY OTHER P.A. AMPLIFIER IN THIS PRICE CLASS



What's different? The anti-feedback position—which equalizes frequencies most sensitive to generation of feedback "howl" without reducing articulation. This increases sound output under difficult acoustical conditions by at least 100%. And there's plenty more that makes the new Harman-Kardon COMMANDER Series of public address amplifiers different. Features usually reserved for much costlier equipment are included: 25 & 70 volt and recorder outputs, fader/mixer and master volume controls, magnetic cartridge input, locking covers, etc. Find out why sound men now use the COMMANDER Series for all their needs. Write for detailed catalog. Commercial Sound Division, Harman-Kardon, Plainview, L.I., N.Y.

Send free detailed catalogs: Desk 3G

Name _____

Address _____

City _____ State _____

harman kardon

- - - for more details, circle 27 on page 50

NEWS OF THE INDUSTRY

Alpha Wire—MARTIN L. ROTH resigns as sales manager.

Harry P. Bridge Co.—HARRY P. BRIDGE, JR., chairman of the board, died suddenly.

Progress Webster Electronics—elections: MAURICE M. ROSEN as president, succeeding STUART CAINE, resigning; PAUL GOLDSTEIN, as a director and vice president of Frank Industries Div.; RALPH MEHR as vice president of Chester, Pa. division.



Rosen



Connor

Sylvania—Home and Commercial Electronics Div., formed to replace Home Electronics Corp., Batavia, N. Y. with GEORGE C. CONNOR, senior vice president, as general manager and chairman of the Board and PETER J. GRANT as president. WILLIAM J. PETERSON has assumed the additional responsibility of sales service, Receiving Tubes, New York, N. Y. Also negotiations have been completed for the sale of the firm's interest in the Golden Shield Corp., Great Neck, N. Y.

Electric Soldering Iron—WILLIAM W. PURTELL, JR. joins staff as vice president.

Amperex—Semiconductors & Tubes appointments: LARRY MAY as product specialist and MARTIN WOLPERT as commercial engineer.

Westinghouse, Electronic Tube Div.—B. W. SAUTER, general manager, predicts 10% sales growth increase for 1962.

Volkswagen—appointed H. J. RITSCHER as vice president of Administrative Div.

Sprague Products—second edition of 36-page manual entitled, Electrolytic Capacitor Replacement, may be ordered for 10c mailing cost.

Pilot Radio—LUTHER MARTIN SANDWICK, vice president, will become staff director of Consumer Products Div. of Electronic Industries Association on January 15th.

J F D Electronics—donation given to New York City Cancer Committee by ALBERT FINKEL, president, on behalf of employees and customers.

Multicore Sales Corp. Port Washington, N.Y.

For information, write Department MC 522

- - - for more details, circle 36 on page 50

Duotone needles, of course... tipped with genuine diamonds, sapphires or osmium. Most people forget to change their styli or don't know how to change them. Why not suggest a Duotone diamond needle replacement for every phonograph that comes into your shop? It's the stylus with the whole diamond tip that's handset and hand polished. Your customers will appreciate the service and you'll appreciate the increase in business.

Write for Free 1962 Duotone Needle Wall Chart and see DUOTONE Distributor.

DUOTONE

COMPANY INC. KEYPORT, N. J.

- - - for more details, circle 20 on page 50

ELECTRONIC TECHNICIAN

Jersey Specialty—promotes AL GOLDSTEIN from national sales manager to vice president in charge of sales.

Lescarboursa Advertising—AUSTIN LESCARBOURA, pioneer electronic writer and advertising leader, died recently.

Motorola—announces plans for huge consumer products advertising program on both national and local level, designed to create new highs in sales action.

Muntz TV—elects SAMUEL W. COE to board of directors.

Brand Name Surveys—Conducting ninth year of manufacturer's questionnaire survey for 25,000 servicemen's preferences in replacement components.

Jerrold — DAN O'CONNELL named sales manager of Taco's Consumer Products Div.

Executone—termination of long standing patent litigation on intercommunication circuitry jointly announced with DuKane, new licensing plan has been formulated for exchange of certain patent rights.

General Electric—stocks of replacement semiconductors for Electronic Component Div. for distributor market now will be maintained in warehouses in Los Angeles, Seattle, Chicago, Clifton, N. J. and Owensboro, Ky., along with franchising wholesale parts jobbers to facilitate distribution.

Philco—included in recent elections for wholly owned Ford Motors subsidiary, Philco Corp., are: board chair-


man—IRVING A. DUFFY and CHARLES E. BECK as president and chief executive officer. Vice presidents are: HENRY F. ARGENTO for government product planning & marketing; HENRY E. BOWES—Consumer Products Div.; ROBERT F. HERR—TechRep. Div.; HENRY R. NOLTE as secretary and general attorney; DAVID B. SMITH—engineering & research. MARC J. PARSONS is director of public relations, replacing LARRY F. HARDY, retiring. Consumer Products Div. appointments include: KENNETH COOPER—general sales manager; J. A. WINFIELD—special markets manager and G. B. KENNEDY as marketing manager. A '62 national advertising program will be launched for consumer electronic and appliance products.

Now! A new, all-in-one, Multiplex Generator with built-in FM signal generator—

Laugh . . .
a little!



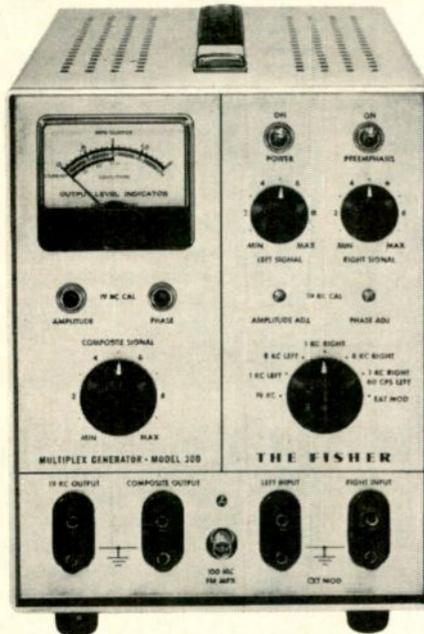"Hi! Did you find the buzz that sounded like a swarm of bees?"



and it's by Fisher!

Only Fisher Could Have Designed the New Model 300 Portable Multiplex Generator —because only Fisher has the engineering depth in FM Stereo tuners and receivers to create the ideal test equipment for servicing them. The future of high-fidelity radio unquestionably belongs to FM Stereo Multiplex and the Model 300 is the instrument for the service technician in search of new business. It is compact, fully portable and completely self-contained. It has its own built-in FM signal generator. In addition to a composite MPX signal, it also generates low-distortion, stable audio signals. Thus it requires no companion instrument for full alignment of Multiplex equipment. Best of all, **FISHER** it costs only \$495.00.

Save \$100! Act now!

If—and only if—you mail this coupon immediately, you will receive a \$100.00 credit certificate toward the purchase of a Fisher Model 300. This is strictly a pre-production offer—pay only \$395—so act now!

Fisher Radio Corporation
21-24 44th Drive, Long Island City 1, N. Y.

Please send Multiplex Generator Credit Certificate.

Name

Address

City.....Zone.....State.....

... for more details, circle 25 on page 50



"The clouded effect calls for rare and special treatment — a soft cloth, warm water and soap . . ."

ATR

PRODUCTS FOR MODERN LIVING



ATR PLUG-IN TYPE PORTABLE INVERTERS*

A.C. Household Electricity Anywhere . . . in your own car, boat or plane Operates Standard A.C. ● Record Players ● Dictating Machines ● Small Radios ● Electric Shavers ● Heating Pads, etc.

MODELS
6-RMF (6 volts) 60 to 80 watts. Shipping weight 12 lbs. DEALER NET PRICE. . . . \$33.00
12T-RME (12 volts) 90 to 125 watts. Shipping weight 12 lbs. DEALER NET PRICE. . . . \$33.00
*Additional Models Available



ATR "A" Battery ELIMINATOR

For Demonstrating and Testing Auto Radios—TRANSISTOR or VIBRATOR OPERATED!
Designed for testing D.C. Electrical Apparatus on Regular A.C. Lines—Equipped with Full-Wave Dry Disc-Type Rectifier, assuring noiseless, interference-free operation and extreme long life and reliability.

MAY ALSO BE USED AS A BATTERY CHARGER
MODEL 610C-ELIF . . . 6 volts at 10 amps. or 12 volts at 6 amps. Shipping weight 22 lbs.
DEALER NET PRICE. . . . \$49.95
MODEL 620C-ELIT . . . 6 volts at 20 amps. or 12 volts at 10 amps. Shipping weight 33 lbs.
DEALER NET PRICE. . . . \$66.95

AUTO-RADIO VIBRATORS



By every test ATR Auto-Radio Vibrators are best! . . . and feature Ceramic Stack Spacers, Instant Starting, Large Oversized Tungsten Contacts, Perforated Reed, plus Highest Precision Construction and Workmanship and Quiet Operation!

There is an ATR VIBRATOR for every make of car!
Ask your distributor for ATR's Low Priced type 1400, 6 volt 4-prong Vibrator; and 1843, 12 volt 3-prong; or 1840, 12 volt 4-prong Vibrator. THE WORLD'S FINEST!

There is a trim plate kit for YOUR CAR!

ATR CUSTOMIZED KARADIO

Vibrator-Operated with Tone Control

ATR KARADIO . . . is ideal for small import cars, or compact American cars! Unit is completely self-contained—extremely compact! Powerful 8-tube performance provides remarkable freedom from engine, static, and road noises. The ATR Customized Karadio comes complete with speaker and ready to install. Can be mounted in-dash or under-dash—wherever space permits! No polarity problem. Neutral Gray-Tan, baked enamel finish. Overall size, 7" deep, 4" high, and 6 1/2" wide. Shipping weight, radio set, 7 lbs. Model K-1276—12 for 12V Dealer Net Price. . . \$33.57
Model K-1279—6 for 6V Dealer Net Price. . . \$33.57

Airplane Style Overhead Mounting under Cab Roof NO PRINTED CIRCUITRY

ATR TRUCK KARADIO

Excellent Tone, Volume, and Sensitivity!

Compact, yet powerful! Fits all trucks, station wagons, most cars and boats. Just drill a 3/8 inch hole in roof and suspend the one-piece unit (aerial, chassis and speaker) in minutes. Watertight mounting assembly holds antenna upright. Yoke-type bracket lets you tilt radio to any angle.

Extra-sensitive radio has 6 tubes (2 double-purpose), over-size Aincio 5 PM speaker for full, rich tone. Big, easy-to-read illuminated dial. Fingertip tuning control. Volume and tone controls. 33-in. stainless steel antenna. Neutral gray-tan enameled metal cabinet, 7 x 6 1/2 x 4 in. high over-all. Shipping weight 10 1/2 lbs.
Model TR-1279—12A for 12V Dealer Net Price \$41.96
Model TR-1279—6A for 6V Dealer Net Price \$41.96

SEE YOUR ELECTRONIC PARTS DISTRIBUTOR WRITE FACTORY FOR FREE LITERATURE . . .

ATR ELECTRONICS, INC.
Formerly American Television & Radio Co.

Quality Products Since 1931
ST. PAUL 1, MINNESOTA—U.S.A.

for more details, circle 11 on page 50

CATALOGS AND BULLETINS

TOOLS: Covered in illustrated bulletin 1621 is a specially designed terminal wrench for removing spanner nuts on external antenna and ear phone jacks of imported transistor radios. Xcelite, Inc., Orchard Park, N. Y.

for more details, circle 312 on page 50

STEREO CARTRIDGES: Literature covers compact snap-in stereo cartridges, catalog designation "S" and "T" designed as replacements for all crystal stereo cartridges. The new snap-in cartridge complete with two needles makes it easier to change the entire cartridge rather than the needle alone. Jensen Industries, Forest Park, Ill.

for more details, circle 313 on page 50

TUBES: Interchangeability guide (ETR-2773) lists standard prototypes which can be replaced with "Five Star" high reliability tubes. Features, specifications and typical applications included. Receiving Tube Dept., General Electric Co., Owensboro, Ky.

for more details, circle 314 on page 50

CB TRANSMITTERS: Six-page, 2-color, brochure contains description and complete specifications for model 23/S-NINE citizens band transmitter. Browning Labs., 100 Union Ave., Laconia, N. H.

for more details, circle 315 on page 50

AMMETERS: Eight-page, illustrated, bulletin covers complete line of improved Tong Test AC-DC snap-around ammeters. Tong Test is reported as the only ammeter of its type that measures both a-c and d-c. Columbia Electric Mfg. Co., 4511 Hamilton Ave., Cleveland 14, Ohio.

for more details, circle 316 on page 50


STEREO-HI-FI: Literature covers an AM hi-fi stereo console which can be promoted under \$80. Has six tubes, four speakers and automatic changer. Also, at same price, an AM/FM, FM stereo table radio with 13 tubes and four speakers. Both units made by the Victor Co. of Japan. Delmonico International Div., Thompson-Starrett Co., 120-20 Roosevelt Ave., Corona, N. Y.

for more details, circle 317 on page 50

T A P E RECORDERS: Swedish-made Luxor Magnefon MP-410-A stereo tape recorder is covered in literature. May be used to record and play back in two track stereo or four track mono from phonograph, microphone, radio, etc. AmeLux Electronics Corp., 60 E. 42nd St., New York 17, N. Y.

for more details, circle 318 on page 50

VERY BIG ON RESPONSE

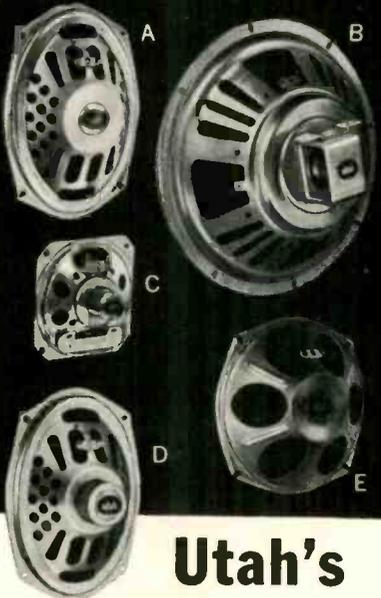

Utah's famous micro-gap replacement SPEAKERS

Better response — better sound reproduction than original equipment! Better customer response, too, when you install Utah Micro-Gap replacement speakers. Single-packed in custom-fitted cartons. Illustrated above:

- A** SP69NF 6x9" Oval Inverted Auto Speaker
- B** SP12J 12" Round Speaker
- C** SP4A 4" Square Outdoor Speaker
- D** SP69G 6x9" Oval Auto Speaker
- E** SP8NF 7 1/2" Inverted Pin Cushion Speaker.

Write for illustrated literature



HUNTINGTON, INDIANA
for more details, circle 59 on page 50

ELECTRONIC TECHNICIAN

AUDIO NEWS LETTER

PENTRON reports resignation of Irving Rossman, president.

ROBINS offers felt replacement pressure pads for tape recorders. A package of 40 pads (cat. #PP-1) lists at \$1.00.

JERROLD acquires Pilot Radio Corp. on all-cash transaction. Pilot will continue to operate as an autonomous company.

JENSEN INDUSTRIES supplies "reminder cards" to its dealers to help them nudge their customers into replacing worn-out needles.

ALLIED is marketing a new, compact stereo FM adapter kit, model KS-10. Says it can be used with any FM or AM-FM tuner equipped with a multiplex output. \$19.95.

LOS ANGELES MUSIC SHOW drawing for rooms resulted in largest assignment in the history of this industry's shows. Fifty-four rooms were drawn, with eighteen remaining available at last count.

BOGEN-PRESTO appoints Heaton-Marco Associates, San Francisco, as factory sales rep for all Bogen products in northern Calif. and northern Nev. Also acquires "Page-master" from Stromberg-Carlson.

SWITCHCRAFT's new molded cable assembly, Part #10FK25, interconnects a stereo mixer to stereo or mono recorders without soldering, wiring or using tools. Designed for stereo recorders with 3-conductor dual inputs. \$4.00.

BELL SOUND reports resignation of Andrew Lorant, advertising, sales promotion and public relations manager, effective Jan. 15. Distribution pattern being realigned. Program underway in effort to put the company back on a one-step basis in most markets and combined one-step and two-step distribution basis in key areas for audio components.

NEXT BEST THING TO THE
WINEGARD ELECTRONIC
POWERTRON TV ANTENNA

NEW TRANSISTOR TV-FM WINEGARD TENNA- BOOST

MOUNTS ON ANY ANTENNA

MOUNTS ON
ANTENNA

ON MAST

ON WALL

Model
MA-300

\$34⁹⁵
only LIST

INSTALL IT... FORGET IT!

ALL ELECTRIC, ALL-AC POWER SUPPLY costs less than 27c a year to operate. Many exclusive features.

No costly, nuisance batteries!



Built-in two set coupler.



AC outlet on power supply.

19 DB GAIN! CUTS SNOW...BOOSTS SIGNAL!

Now you can make any TV or FM antenna work better by magnifying signals with the new Winegard transistor Tenna-Boost.

Tenna-Boost has up to 19 DB gain, no peaks and valleys. Ultra low noise. Linear frequency response. VSWR input better than 1.5:1 across all frequencies. Output VSWR 1.8:1 or better. This fine frequency response plus the very low VSWR make Tenna-Boost excellent for color.

Winegard's *exclusive* input band-pass filter eliminates interference from citizen's band, Hams, garage door openers, etc. Only TV and FM signals are amplified.

All metal parts are anodized, irridized or stainless steel. Completely weather-proof, trouble-free. Install it... forget it.

There's a big difference in antenna amplifiers! Ask your distributor or write for technical bulletin.

FOR THE ULTIMATE IN
TV RECEPTION

Winegard Transistorized Electronic Powertron TV Antennas. 3 Models to Choose From.



Winegard

ANTENNA SYSTEMS

3019-3B Kirkwood • Burlington, Iowa

for more details, circle 62 on page 50

R FOR "DOCTORS OF
SERVICING"



THE PROFESSIONAL
SERVICE MAN'S
CLEANER

cleans contacts CLEANER!

Want total cleaning power that helps you do a better servicing operation 3 ways? Spray electrical contacts and switches with triple action Contact Shield. Cleans, lubricates, and safeguards, like no other cleaner can! Gives lasting protection in seconds . . . thanks to Silicone base. Independent laboratory tests prove it! Technicians approve it! Write for handy guide-book to more efficient servicing . . . Channel Master Corp., Ellenville, N.Y.

© 1962 CMC

--- for more details, circle 18 on page 50

SOUND WAYS TO EXTRA PROFITS

Get into the all-year-round commercial sound trade and do away with seasonal repair work slumps! This steady-profit business—sales, installation and service—is available right in your own neighborhood! Factories, restaurants, schools, offices, bowling alleys . . . outdoors, athletic fields, swimming pools, etc. . . all are prospects for you.

Atlas Sound products, built to quality standards and backed by over 25 years of "know-how", are insurance for your reputation. Your Atlas Distributor can supply you with a complete line of performance-proven job-rated equipment: speakers, mike stands and related accessories for a professional sound installation.



Write for latest catalog and names of Atlas Distributors.

ATLAS SOUND DIVISION
American Trading and Production Corporation
1419-51 39th Street, Brooklyn 18, New York
In Canada: Atlas Radio Corporation, Toronto

--- for more details, circle 10 on page 50

ASSOCIATION NEWS

California

Slogan Wanted

CSEA, Sacramento, has asked members to suggest a slogan that is unique and will identify the service industry. It should be equivalent, for the service industry, to the florists' "Say it with Flowers," or the plasterers' "Knock on the Wall."

TSDA, San Francisco, is conducting a survey of its members to determine losses from theft and shoplifting at the TV dealer level. Study results will come before law enforcement agencies.

New York

TV Tube Labelling Law

ESFET, Kenmore, president Douglas Cook, of the Empire State Federation of Electronic Technicians Associations, says very few of the state residents are even aware of the TV tube labelling law which went into effect over a year ago. "This fact has been brought out clearly," said Mr. Cook, "by a recent survey of N. Y. TV technicians who said that few or none of their customers knew the law existed." The 1960 law requires all TV replacement tubes to be labelled as to their true condition—"new" or "used—on both the tube and the carton the tube comes in. It further requires the technician replacing the tube to give a written statement to the customer about whether the tube is new or used.

Ohio

ARTSD, Columbus, elects: Pres., Jack Voiget; V.P., Frank Shannon; Recording Sec'y, Walter Driscoll; Corresponding Sec'y, Rex Rice; Treas., Paul Boyer. Board of Directors: Lou Benhard, George Dykes, Bill Hetrick, Bob Kapp, elected to serve as the Jobber Representative. NATESA Director, John Graham. TESA Ohio Director, Herman Francis.

Pennsylvania

TSA of D. V., Philadelphia. Allen Roberts reports a recent meeting held at Motorola's request with TSA president, Herman Shore, on handling carry in service on Motorola portable and table model TV sets, now carrying one year parts warranty. After lengthy discussion on rates, Pres. Shore requested a meeting with executive sales and management but service would not agree to the meeting. Rates originally discussed were fairly realistic and competitive. The discussions continued and after numerous phone conversations, which were all that could be arranged at the time, the rate structure was suddenly decreased to a ridiculously low figure. Pres. Shore would not negotiate at these figures and again insisted on meeting with the top management. This meeting could never be arranged . . . and at this point negotiations were ended.

. . . Electronic Devices

Continued from page 29

current. CR-1 prevents oscillation from occurring across L-1. When Q-1 is "turned-on" by a detector pulse, it saturates and nearly all of the battery voltage of BT-3 and BT-4 appears across winding 3-4 of T-1. The current in this winding increases and a voltage is induced in winding 1-2. This induced voltage is in a direction such that conduction of Q-2 is maintained. Winding 3-4 current increases linearly until the transformer core saturates. At this time the circuit rapidly "turns-off" and an inductive "fly-back" appears across both windings.

A rectangular voltage pulse of about 110 microseconds duration appears across winding 3-4 of T-1 for each detector pulse. This shaped pulse charges the integrating capacitors C-2 and C-6 by rectifier CR-2 with an amount of charge determined by the range resistor R-1, R-2, or R-3 and R-4. The charge placed on these capacitors is discharged through the meter M-1 and its series resistor R-5. The meter current then is dependent on the charge per pulse and the pulse repetition rate. Resistors R-6 and R-7A are used to adjust calibration. Three ranges are provided: The first or X-100 requires 80,000 pulses per minute for full scale indicators; the second or X-10, 8,000 pulses per minute; and the third or X-1, 800 pulses per minute. The response time constant of the instrument is fixed essentially by the values of C-2, C-6, R-5 and the meter resistance. It is nominally 8 seconds for 63% response or 24 seconds (3 time constants) for 95% response. Response time can be reduced by removing one of the capacitors C-2 or C-6, or can be increased by adding additional capacity.

The voltage pulse for the headphones is taken from fly-back winding 3-4 by diode CR-3. C-3 is an integrating capacitor to "stretch" the "fly-back" pulse. R-8 is an isolating resistor and CR-4 damps

IF YOU CHANGE YOUR ADDRESS

Notify us at 1 East First Street, Duluth 2, Minn. Please include the address label from a recent issue and allow 30 days for the change.

4 STEPS TO BIG MONEY IN MASTER TV INSTALLATION WITH BLONDER-TONGUE

Thousands of service technicians are now reaping a financial harvest in Master TV system installations. Motels, schools, apartment houses, trailer camps and hospitals are just a few of the growing markets for Master TV systems. If you're a TV service technician with just a little extra initiative, it's easy to get started in Master TV. Here's how:

1. Start with the Blonder-Tongue 'Planning and Installation' Manual. It will give you a practical working knowledge of Master TV systems. Further, the 'packaged systems' shown will enable you to handle most Master TV jobs. Write for free manual.

2. Next, use Blonder-Tongue's free system layout service. It puts you in a position to specify the right products for a system and make a competitive bid.

3. For real big systems, on-the-spot engineering is available at a nominal cost.

4. Finally, draw upon the world's only matched and integrated line of master TV, educational TV, closed circuit TV and community TV equipment.


There's a Blonder-Tongue product for every possible application. Each is designed to do a specific job — yet each is matched to bring out the best in the others. And, Blonder-Tongue quality, a result of its vast experience, protects you against expensive call-backs. *Blonder-Tongue does not compete with its customers.*

Don't hesitate. Get started today. For full details on how to become a Blonder-Tongue installer, write:

engineered and manufactured by


BLONDER-TONGUE
9 Alling St., Newark, N. J.

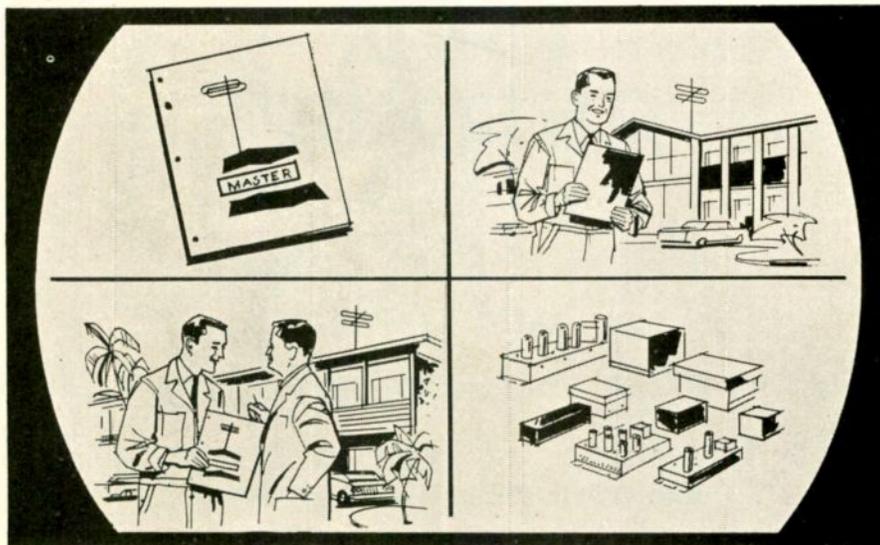Canadian Div.: Benco Television Assoc., Toronto
Export: Rocke Int'l. Corp., N. Y. 16, N. Y.—CABLES: ARLAB



. . . for more details, circle 14 on page 50

For your custom stereo installations

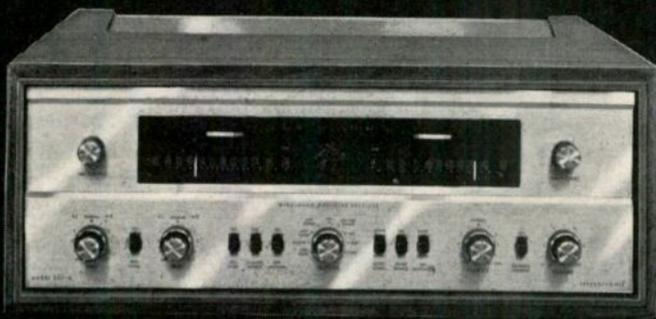

THE FISHER 800-B

Three of the world's finest components on one chassis

1 AM-FM-Stereo Multiplex Tuner: separate tuning indicators for FM and AM; exclusive Fisher STEREO BEAM automatically shows whether an FM station is broadcasting in stereo.

2 High-Power Stereo Amplifier: 65 watts music power; special center-channel output connection for third speaker.

3 Master Audio Control-Preamplifier: complete, easy-to-use control system assures total flexibility; provisions for every type of input. Price \$429.50*

*Walnut or Mahogany cabinet \$24.95; prices slightly higher in the Far West

USE THIS COUPON FOR DETAILED INFORMATION

Fisher Radio Corporation
21-54 44th Drive, Long Island City 1, N. Y.

Please rush the following FREE literature:

- Complete specifications on the Fisher 800-B Receiver.
- The 1962 Fisher Handbook, a 40-page illustrated reference guide and component catalogue for custom stereo installations.

Name _____

Address _____

City _____ Zone _____ State _____

PF-201

- - - for more details, circle 24 on page 50

IRE SHOW



presenting

"THE GOLDEN AGE OF ELECTRONICS"

March 26-29, 1962

The New York Coliseum

... part of the

International Convention of the IRE

The Institute of Radio Engineers
1 East 79th Street • New York 21

Members \$1.00. Non-members \$3.00. Age limit: over 18

- - - for more details, circle 30 on page 50

"ringing" of the headphones. A pulse between 5 and 10 volts in size with an approximate duration of 60 μ s at mid-value is available across a 3000 ohm resistive load connected to J-1. This pulse provides a headphone click.

Calibration and Servicing

The aforementioned unit can be calibrated in counts per minute by applying a pulse generator output to the unit's input and adjusting the CAL adjusting potentiometer. A pulse generator producing negative pulses at least 0.5 volts in amplitude, approximately 5 μ s in duration, and a repetition rate of approximately 6000 pulses per minute is required. Calibration is accomplished in the following manner:

1. Remove the case bottom from the instrument.
2. Connect the pulse generator output, in series with a 500 pf 1200 volt capacitor, to the input connector on the case top.
3. Turn the switch to the X-10 range and adjust the CAL potentiometer until the meter scale is identical with the pulse repetition rate of the pulse generator.

The instrument will then be calibrated in all its ranges. The instrument will be about 15% too sensitive on uniformly spaced pulses near full scale on the X-100 range. This added sensitivity on the X-100 range is deliberately built-in to compensate for the dead-time of the Geiger tube and instrument electronics on randomly spaced pulses of high repetition rate. Dead-time correction is not required on the X-10 or X-1 range.

Servicing: When the power supply is operating, a buzz of about 100 cps in frequency can be heard due to the oscillations of the power transformer laminations. If this buzz is not audible, the oscillator section is probably not operating and the setting of R-7B should be checked. This screwdriver adjustment is set properly by the following procedure:

1. Insert a 0-100 ma meter in series with the power supply batteries, BT-1 and BT-2.
2. Turn the "HV" adjustment fully counter-clockwise.
3. Turn the instrument "ON".
4. Advance the screwdriver adjustment clockwise until the meter

reads 33 ma with new batteries.

The high voltage output of the power supply should be tested with an electrostatic voltmeter. The voltage should read 900 volts with the high voltage selector switch in the "GM" position and 1200 volts in the "SCINT" position. This voltage may also be measured with a 20,000 ohms-per-volt voltmeter on the 5000 volt range with new batteries in the instrument.

The nominal resistance values for the transformer (T2) windings are:
Winding 1-2, 4,500 ohms.
Winding 3, 4, 11 ohms.
Winding 5-6, 5 ohms.

To check operation, after indicated continuity tests have been made, the integrating circuit may be tested further with an oscilloscope. The proper pulse wave shape on the collector of Q-1 is a positive 3 volt square wave of a nominal 110 μ sec in duration followed by a "fly-back" of about -20 volts in amplitude. If the wave shape at the anode of CR-1 shows "ringing," CR-1 is probably defective. Diodes CR-1 through CR-4 may be tested with an ohmmeter on the R x 10,000 range. One end of the diode under test should be disconnected from the circuit for this test. The indication of a good diode is a very low resistance with the ohmmeter leads connected one way. With the leads reversed, the resistance reading should be 100,000 or greater for CR-1, CR-3, and CR-4. CR-2 should be 1 megohm or greater. Diode CR-5 in the high voltage power supply will not respond to this test. ■

... Transformer Problems

Continued from page 32

sirable to obtain an exact fitting component. If a universal replacement type is used, new mounting holes may sometimes be required.

A number of precautions are necessary when replacing i-f transformers. Because of the relatively high frequency, all wire leads to the transformer should be dressed as originally prevailed, and these connections should be the exact same length.

If a load resistor is used across a transformer winding, it should be checked to determine if the resistance value is correct. When removing or changing a resistor, its position and soldered lead lengths



ONLY
\$69⁵⁰
net

GUARANTEE

Each Seco Model 88 is unconditionally guaranteed to be up-to-date for the testing of receiving type tubes. Adaptor kits or set-up data will be furnished without cost to keep your tester current for one year from date of purchase.

A SECO PLUS!

© SEI 1962

New Seco Model 88 Tube Tester is guaranteed against obsolescence. Gives you patented Seco GRID CIRCUIT, also CATHODE EMISSION tests—tests over 2,200 tube types including Nuvistors, Novars, Compactrons, new 10-pin types and battery types. You also get:

- A check for troublesome grid emission and all common leakage and short faults in one operation. READ ON METER.
- A cathode emission test in special low impedance circuit.
- A burnout-proof meter employing a VTVM amplifying circuit.
- Few controls—simple operation—compact, lightweight size.
- Convenient fast-find setup information in cover.
- A check for filament continuity and open elements.

For full information write or send coupon below to Seco, originator of the famous Grid Circuit Test.



SECO ELECTRONICS, INC.
5021 Penn Ave. So., Minneapolis 19, Minn.

Please send free Model 88 information "How to Test Tubes"

NAME _____

ADDRESS _____

CITY _____ STATE _____

... for more details, circle 47 on page 50


COLOR CODED NUTDRIVER SETS

no fumbling...
you reach for
the right one
every time!



No. 17
HANDY
BENCH STAND

- 7 Most-used sizes — $\frac{3}{16}$ " thru $\frac{3}{8}$ "
- High carbon steel, polished and plated
- Precision fit case-hardened sockets
- Shockproof plastic handles (UL)
- Large, readable size indexes

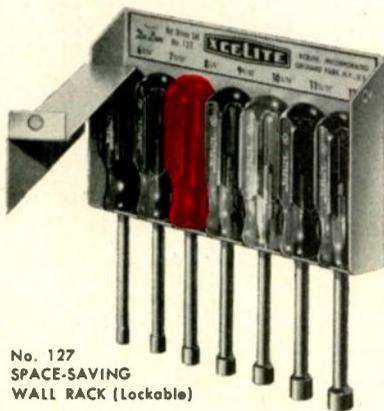

No. 127
SPACE-SAVING
WALL RACK (Lockable)

OTHER SETS, TOO: hollow-shaft or mixed
PLUS A FULL RANGE OF SEPARATE NUTDRIVERS:
3/32" thru 3/4" — Regular, Stubby, Extra-long,
Midget (Pocket clip)
available through leading electronic distributors

XCELITE, INC. — ORCHARD PARK, N. Y.
Canada: Charles W. Pointon, Ltd., Toronto, Ont.

XCELITE

HAND TOOLS

Quality screwdrivers, nutdrivers, pliers,
wrenches, service kits, and special purpose tools.

... for more details, circle 63 on page 50

should be similar to the original configuration.

It is sometimes necessary to re-align the entire i-f section after changing a transformer if any difficulties, such as smearing, trailing whites, lack of definition or poor vertical or horizontal sync prevail.

Vertical Sweep Transformers

Two different vertical transformers may be employed in some of the modern TV sets made today. A transformer is used in all vertical blocking or feed-back oscillators, and another is used in the vertical amplifier's output. The blocking oscillator transformer couples the oscillator tube's plate and grid circuits, and the vertical output transformer couples sawtooth power from the vertical output tube to the vertical windings in the deflection yoke.

Vertical output transformers usually fail more often than blocking oscillator transformers, perhaps because of the higher currents passing through them. Defects in either may be indicated in a number of ways — usually by a complete collapse of vertical sweep, a few inches of vertical sweep, or insufficient sweep, top or bottom.


Although technicians use a wide variety of troubleshooting approaches when a defective vertical transformer is suspected, the general approach calls for signal substitution. This is true whether a modern signal-substitution instrument is used, a signal is obtained from another operating TV set, or an inexpensive make-shift method is employed to obtain a substitute signal from the ailing TV set's heater windings.

As shown in Fig. 4, a sweep troubleshooter is used to quickly determine if a vertical output transformer is at fault. A vertical sawtooth signal generated by the instrument is fed to the vertical output tube's plate. If the raster spreads substantially in a vertical direction, the amount of spread depending upon the signal input amplitude, it can generally be assumed that the vertical output transformer is good. If no perceptible increase in vertical sweep, the output transformer or the deflection yoke can be at fault.

If an increase in sweep is obtained with a signal at the vertical output tube's plate, then the d-c

TV TIPS FROM TRIAD

NO. 16 IN A SERIES

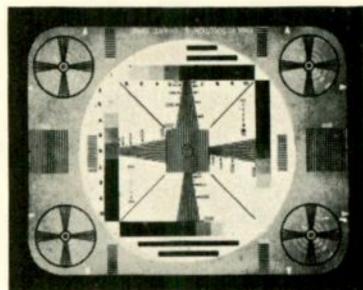

"Where's Joe?" asked parts salesman Al.

"Reading up on electrolytics, I suppose," smiled Bill, the Senior PTM.

"How's that?"

"Well, Joe got this 19-inch portable job that was keystoneing. Right away, he says to himself it's got to be the yoke. But it wasn't, and he fooled with that thing for the longest time. He'd still be at it if I hadn't pointed out that a lot of new 19- and 23-inchers use the B+ boost voltage for the vertical output stage rather than the B+ source!"

"Has to do with giving you enough vertical scan on the big CRT's, doesn't it?" said Al.

"Right. In a lashup like that, they've got a filtering capacitor, usually an electrolytic, to take care of the horizontal spike coming from the B+ boost voltage source. When this capacitor opens the filtering action drops. This causes the spike to show up at the plate of the vertical output stage and in the vertical yoke coils. The rest is simple. You lose some in the vertical and horizontal sweeps and it's just like a keystone from a flubbed out yoke!"

"Hmm," said Al slyly, "I guess Joe will make a better Keystone cop from now on!"

MORAL: Don't knock the Triad Y-66-1 until you've checked out the filtering capacitor. In the meantime, get on Triad's permanent mailing list and receive the new catalog TV-62 as well as other helpful literature. Write *Triad Distributor Division*, 305 No. Briant St., Huntington, Indiana.

A DIVISION OF LITTON INDUSTRIES

... for more details, circle 55 on page 50

ELECTRONIC TECHNICIAN

voltage at the blocking oscillator's plate should be checked with the volt meter. If this conforms closely with the manufacturer's specification, then check the voltage at the oscillator's grid. The voltage here should be as specified, and may vary from —15 to —30, depending upon the particular oscillator design and the hold control setting. If this voltage appears positive or has a lower-than-normal negative voltage, the blocking oscillator transformer may be leaking. If there is no voltage indicated and the grid reads zero, the transformer winding can be open. Of course, a possible fault in C-1, R-1 or R-2 should be considered.

Blocking oscillator transformer replacements are not too critical, except that one with the exact turns ratio should be obtained. If the physical size or shape is different, it may be necessary to drill one additional mounting hole in the chassis. Vertical output transformers are sometimes critical. An exact replacement should be provided. Most replacement parts manufacturers list exact replacements for most sets in their catalogs, giving essential electrical and physical data. Lead dressing around these transformers should also not be disturbed. Both transformers can also develop lamination hum or buzz.

HV Transformers

Known as the flyback, horizontal output, or high voltage transformer, this TV component supplies high voltage to the horizontal output tube's plate and to the plate of the high voltage rectifier tube. A stepped-down heater voltage for the high voltage rectifier tube is also obtained from the flyback. In addition, the transformer generates, through combined action of the yoke and the damper tube, a B+ "boost" voltage. It also frequently supplies a medium high voltage p-to-p pulse for keyed agc circuits, or to afc circuits for controlling the horizontal oscillator.

Fault symptoms caused by the flyback can be complete loss of raster, insufficient brightness, a "blooming" raster (raster expands when brightness control is advanced), streaks in the raster (internal arcing in transformer), loss of boost voltage, agc or afc pulses.

Here again, the best approach to suspected flyback problems is



STOCK—Hang it on the wall, stand it on a shelf, slip it into your caddy. Cartridge model number is always visible for quick identification.

SAVE—Save money on purchase of any 6 SONOTONE cartridges—save time by always having the right replacements.

SERVICE—You always have the right replacement to service virtually every record player on the market.

SELL—In your shop, an eye-compelling display (unique bonnet fits over 6-Pak to remind your walk-in customers to modernize their record players). In your caddy—a variety of cartridges for nearly every replacement.

Every time you buy 6 SONOTONE cartridges from your distributor, they come in the new attractive 6-Pak cartridge sleeve. You can select any 6 SONOTONE cartridges, or one of three pre-selected 6-Paks which include the most needed cartridges for the most often faced replacement situations.

- **STEREO 6-PAK**—covers nearly every stereo replacement or conversion. Six stereo cartridges from the audiophile's favorite, the 9T, to the budget-priced stereo crystal cartridge, the 12T. Consists of models: 9T, 8T-A, 16T, 18T, 10T and 12T.

- **STEREO/MONO 6-PAK**—covers most stereo or mono replacement needs. Consists of 3 stereo ceramics models 8T-A, 9T, 16T; and 3 mono ceramics: 1P, 2T, 3T.

- **MONOPHONIC 6-PAK**—covers virtually all most called for monophonic replacements. "LB" denotes "less bracket" for slim tonearms. Consists of models; 1P, two 2T's, 2T-LB, 3T-LB.

The 6-Pak is just another way that SONOTONE simplifies your inventory and makes it easier to sell cartridges. Order a SONOTONE 6-Pak today at your parts distributor.

FREE: The new SONOTONE cartridge cross-reference chart catalog is available at your distributor, or write: Dept. ET-3

SONOTONE® CORPORATION ELMSFORD, NEW YORK
ELECTRONIC APPLICATIONS DIVISION In Canada: Atlas Radio Corp., Ltd. Toronto
Cartridges • Speakers • Tape Heads • Mikes • Electronic Tubes • Batteries • Hearing Aids

— for more details, circle 49 on page 50



CITIZEN BAND CLASS "D" CRYSTALS

All 22 Frequencies in Stock
3rd overtone .005% tolerance—to meet all FCC requirements. Hermetically sealed HCG/U holders. 1/2" pin spacing — .005 pins. (.093 pins available, add 15c per crystal.) **\$2.95 EACH**

The following Class "D" Citizen Band frequencies in stock (frequencies listed in megacycles): 26.965, 26.975, 26.985, 27.005, 27.015, 27.025, 27.035, 27.055, 27.065, 27.075, 27.085, 27.105, 27.115, 27.125, 27.135, 27.155, 27.165, 27.175, 27.185, 27.205, 27.215, 27.225.

Matched crystal sets for all CB units . . . \$5.90 per set. Specify make and model numbers.

RADIO CONTROL CRYSTALS IN HCG/U HOLDERS

Specify frequency, 1/2" pin spacing . . . pin diameter .05 (.093 pin diameter, add 15c) **\$2.95 ea.**

FUNDAMENTAL FREQ. SEALED CRYSTALS

in HCG/U holders
From 1400 KC to 2000 KC .005% Tolerance **\$4.95 ea.**
From 2000 KC to 10,000 KC any frequency .005% Tolerance **\$3.50 ea.**
SEALED OVERTONE CRYSTALS
Supplied in metal HCG/U holders
Pin spacing .486, diameter .050
15 to 30 MC .005 Tolerance **\$3.85 ea.**
30 to 45 MC .005 Tolerance **\$4.10 ea.**
45 to 60 MC .005 Tolerance **\$4.50 ea.**

QUARTZ CRYSTALS FOR EVERY SERVICE

All crystals made from Grade "A" imported quartz—ground and etched to exact frequencies. Unconditionally guaranteed! Supplied in:
FT-243 holders MC-7 holders
Pin Spacing Pin Spacing
1/2" Pin Diam. 3/4" Pin diameter .093
Cria/ar Holders FT-171 holders
Pin Spacing 1/2" Pin Spacing
Pin Diameter 3/4" Banana pins .125

MADE TO ORDER CRYSTALS

1001 KC to 2600 KC: **\$4.50 ea.**
.005% tolerance
2601 KC to 9000 KC: **\$2.50 ea.**
.005% tolerance
9001 KC to 11,000 KC: **\$3.00 ea.**
.005% tolerance
Specify holder wanted

Amateur, Novice, Technician Band Crystals
01% Tolerance . . . \$1.50 ea.—80 meters (3701-3749 KC), 40 meters (7152-7198 KC), 15 meters (7034-7082 KC), 6 meters (8335-8650 KC) within 1 KC

FT-241 Lattice Crystals in all frequencies from 370 KC to 540 KC (all except 455 KC and 500 KC) 50c ea.

Pin spacing 1/2" Pin diameter .093
Matched pairs ± 15 cycles \$2.50 per pair
200 KC Crystals, \$2.00 ea.; 455 KC Crystals, \$1.25 ea.; 500 KC Crystals, \$1.25 ea.; 100 KC Frequency Standard Crystals in HCG/U holders \$4.50 ea.; Socket for FT-243 crystal 15c ea.; Dual socket for FT-243 crystals, 15c ea.; Sockets for MC-7 and FT-171 crystals, 25c ea.; Ceramic socket for HCG/U crystals 20c ea.
Write for new free catalog #961 complete with oscillator circuits

ASK YOUR PARTS DEALER FOR TEXAS CRYSTALS

See big red display . . . if he doesn't stock them, send us his name and order from our Florida plant.

Now! Engineering samples and small quantities for prototypes now made either at Chicago or at Ft. Myers Plant. 24 Hour Service.
IN CHICAGO, PHONE GLADSTONE 3-3555

RUSH YOUR ORDER TO OUR NEW PLANT
Use coupon below for 1st Class shipment.

TEXAS CRYSTALS

Dept. T-12, 1000 CRYSTAL DRIVE, FORT MYERS, FLORIDA
For extra fast service, Phone WE 6-2100

ATTACH THIS COUPON TO YOUR ORDER FOR SHIPMENT VIA 1ST CLASS MAIL AT NO EXTRA COST

TERMS: All items subject to prior sale and change of price without notice. All crystal orders must be accompanied by check, cash or M.O. with **PAYMENT IN FULL.**
Dept. T-12

signal substitution or injection (See ELECTRONIC TECHNICIAN May 1961). Commercially available equipment for making these tests are ideal. Inexpensive, simple-to-operate flyback checkers are also available. And some technicians substitute voltages from a good operating TV to the dead set in order to isolate faults.

Flyback transformers are highly critical, electrically and physically, and exact replacements should be obtained. All HV leads, including rectifier filament leads, should be dressed as originally established.

Audio Transformers

In addition to the 4.5 mc sound take off, limiter grid input, and sound i-f coils and transformers, which seldom give trouble, the conventional f-m detector and audio output transformers are employed. These are usually the most troublesome. Trouble symptoms may be complete loss of sound, insufficient volume, or distorted sound.

The conventional detector transformer contains two "gimmicks" sealed inside the transformer's housing (small value capacitors) which, in addition to cold and rosin solder joints at winding lead connections, create considerable problems in TV sound sections. Faults should be approached in a somewhat similar manner as those in Video i-f transformers.

An exact replacement with similar electrical and physical characteristics is highly desirable, although in a pinch a larger or smaller transformer can be made to work if electrical characteristics are similar. The transformer should be aligned after replacement, employing a sweep generator, marker generator and scope. Manufacturers specifications for this alignment should be followed closely.

Audio output transformers are designed to match the impedance of the output tube's plate to the speaker, and couple the audio signal voltage to the speaker. They are not exceptionally critical but an exact replacement is desirable to avoid possible complications. Trouble in the transformer can generally be easily isolated by feeding an audio signal to the output tube's plate. If electrical characteristics of the replacement are proper, physical size becomes a problem only in mounting.

How to get more work out of your OSCILLOSCOPE



A complete guide to the handiest instrument of all

MODERN OSCILLOSCOPES AND THEIR USES by J. H. Ruiters gets right down to earth in bringing you the complete "know how" of getting the most out of these amazingly versatile instruments. Particular attention is paid to alignment procedures. Every testing detail is explained from connecting the scope and setting its controls to adjusting components in the chassis under test. Illustrated instructions teach you pattern analysis. Includes data on quantitative measurements (as used in color TV work) and use of scopes in industrial electronics, teaching and atomic work. 346 pages, over 350 illustrations. Price \$8.75.

Get your COMMERCIAL OPERATOR'S LICENSE!

A fast, low-cost guide to FCC exams

Train for radio's best paid, most interesting jobs as a commercial operator aboard ship, in aviation, broadcasting, telecasting and other places where an FCC operator's license is a "must." **LICENSE MANUAL FOR RADIO OPERATORS** is a quick, low cost guide to help you "breeze" through FCC exams. Clearly written and makes things easy to remember. Reviews almost 2200 typical exam questions so you'll know what to expect. Only \$6.75.

Cash in on ELECTRICAL APPLIANCE REPAIRS!

A good-paying side line or full time business for trained men

Nothing is more logical than for electronic service technicians to boost their profits through electrical appliance repairs—and here is a 370-page, low cost book that shows you how to handle every step of the work! Includes "fast find" troubleshooting charts—even trains you in modern appliance refinishing methods. Gives step-by-step service details on practically every home appliance including washers; ironers; toasters; ranges; cleaners; mixers; hotplates; razors; clocks; motors; water heaters and many more. **Electrical Appliance Service Manual**—Price only \$6.75.

10 DAY FREE TRIAL

Dept. ET-32, Technical Division #623900
Holt, Rinehart and Winston, Inc.
383 Madison Ave., New York 17, N. Y.

Send books checked for **FREE EXAMINATION**. In 10 days I will either remit prices indicated plus postage or return books and owe nothing. (Save! Send cash with order and we pay postage. Same 10-day return privilege with money promptly refunded.)

- MODERN OSCILLOSCOPES AND THEIR USES (#708818) **\$8.75**
- LICENSE MANUAL FOR RADIO OPERATORS (#708537) **6.75**
- ELEC. APPLIANCE SERVICE MANUAL (#708172) **6.75**

Name _____

Address _____

City, Zone, State _____

OUTSIDE U. S. A.—Cash with order only. Add 50c to price of each book. 10-day return privilege with money refunded.


Above offers expire Dec. 15, 1962

2 YEAR FIELD TEST PROVES

U.S. PAT. NO.
2875440

\$14⁹⁵
List Price

Focus
F-38K

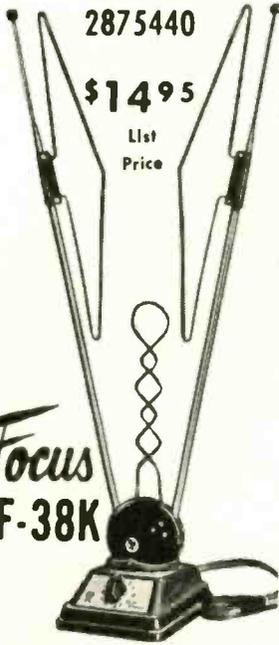

Dept. ET

- THE "FOCUS" F-38K OUTPERFORMS ALL OTHER INDOOR ANTENNAS!
- THE ONLY INDOOR ANTENNA COMPARABLE TO AN OUTDOOR ANTENNA!
- BEST RECEPTION ON VHF, UHF, COLOR, AND FM . . . EVEN IN SEMI-FRINGE AREAS!

FEATURES

1. 102" of Dipole when fully extended.
2. Patented Diamond Phasing Loops producing the Power of 3 separate switch type indoor antennas.
3. 12 Position Switch for maximum signal.

ELIMINATES GHOSTS AND CO-CHANNEL INTERFERENCE!

SOLD ON A MONEY BACK GUARANTEE BASIS!

RMS

ELECTRONICS, INC.
BRONX 62, N. Y.

--- for more details, circle 41 on page 50

Over 15 Years
Selling Electron Tubes
Direct to You . . .
At Low, Low Prices!



BUY DIRECT FROM RAD-TEL
Save on Rad-Tel's Quality **BRAND NEW TUBES**

NOW! { Over 500 Types
Up to **75% OFF**

1-Year Guarantee • 1-Day Service

- Send For New Tube & Parts Catalog
- Send For Free Trouble Shooting Guide

SAMPLE OF RAD-TEL'S AVAILABILITY

Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price
—	1B3	.79	—	6AL5	.47	—	6BZ6	.55	—	12AU7	.60
—	1X2B	.82	—	6AU6	.52	—	6CB6	.55	—	12BH7	.77
—	3CB6	.54	—	6AX4	.66	—	6CG7	.61	—	35W4	.42
—	4BQ7	1.01	—	6BQ6	1.05	—	6SN7GT	.65	—	35Z5	.60
—	5U4	.60	—	6BQ7	1.00	—	6U8	.83	—	50C5	.53



RAD-TEL TUBE CO.

Dept. ET 55 CHAMBERS ST., NEWARK 5, NEW JERSEY

TERMS: 25% deposit must accompany all orders, balance COD. Orders under \$5: add \$1 handling charge plus postage. Orders over \$5: plus postage. Approx. 8 tubes per 1 lb. Subject to prior sale. No COD's outside continental USA.

--- for more details, circle 42 on page 50

34¢

EACH
ELECTRONIC MARKET
1 YEAR GUARANTEED
RADIO-TV TUBES

\$32
per 100

25¢

QUANTITY DISCOUNT
per tube

When purchasing lots of 50 or more same type tube Applies to tubes below only

All tubes not necessarily new, but may be electronically perfect factory 2nds or used. Each clearly marked. ELECTRONIC MARKET will replace FREE any tube that becomes defective in use within 1 year from date of purchase. All tubes individually boxed and marked. Partial Listing Only—Thousands More Tubes in Stock!

024	5AV8	6AX5GT	6CH8	6SK7	12BH7
1A7GT	5AZ4	6B15T	6CL8	6SL7	12B6E
1B3GT	5CB8	6BA6	6CM6	6SQ7	12BT
1W5GT	5RA	6BC5	6CM7	6S7	12CA5
155	5T8	6BC8	6CW7	6T4	12D4
174	5U4	6B08	6C08	6T8	12F6
192	5UB	6B08	6CR6	6U5	12K5
195	5UB	6B08	6CR6	6U5	12K7
192	5V4G	6B75	6C57	6V8GT	12L6
1X2	5V6GT	6B86G	6C06	6V8GT	12L6
2AF4	5Y3	6B86	6C06	6V8GT	12L6
2B4	5Y3	6B86	6C06	6V8GT	12L6
2C15	6AB4	6B85	6C08	6B8	12S47
3AL5	6AH4GT	6B87	6D6GT	6Y4G	12X7
3B6	6AL5	6B86	6B8	12AB5	12X7GT
3B6	6AH8	6B86GT	6H6	12A05	12Y07
3B75	6AG5	6B87	6I5	12A06	12Y07
354	6A07	6B88	6I7	12A06	12Y07
3V4	6A07	6B88	6I7	12A06	12Y07
4BQ7A	6A55	6B75G	6Q7	12AV7	19AU4GT
4B58	6AT6	6B78	6SA7	12A27	19B06
4B7	6AU4GT	6B7	6SD7GT	12B4	25Z6GT
4CB6	6AU5GT	6C4	6S7GT	12B4	25Z6GT
5A9A	6AU8	6C4B	6S7	12B4	25Z6GT
5AN8	6AT5GT	6C8B	6S7	12B4	25Z6GT
5AT8	6AV8	6C06G	6S7	12B4	25Z6GT
	6AX4GT	6C78	6S7	12B4	25Z6GT

ORDER SHIPPED SAME DAY RECEIVED

SHIPPING INSTRUCTIONS: ELECTRONIC MARKET PAYS YOUR POSTAGE on orders of \$10 or more in U.S.A. and Territories. Send approx. postage on Canadian and foreign orders. Any order less than \$10 requires 25¢ handling charge. Send 25% on C.O.D.'s. ANY RECEIVER TUBE NOT LISTED ALSO AVAILABLE AT 34¢ EACH!

74¢
EACH
\$49
per 100


SILICON RECTIFIERS
ALL PURPOSE
Epoxy construction
500 MA - 'TOP HAT'

COMPLETE LINE OF INDUSTRIAL TUBES
ONE OF THE LARGEST INVENTORIES IN THE COUNTRY
ELECTRONIC MARKET
3750 E. 10th CT., HIALEAH, FLORIDA
Phone: DXford 1-5331

--- for more details, circle 23 on page 50

NEW KRYLON CLEANER LUBRICANT SPRAY

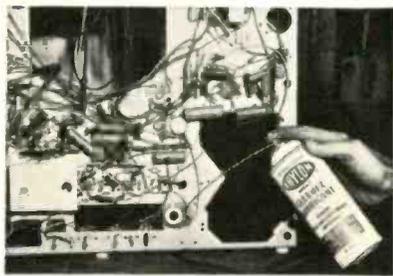To service volume controls, tuners, switches



Cleans away dirt and gummy deposits. Provides a nondrying lubricating film on contact surfaces. Gives long-lasting protection against corrosion. Comes with 5-in. flexible plastic hose for controlled spraying in hard-to-reach places.

KRYLON CRYSTAL-CLEAR ACRYLIC SPRAY



Protects electronic parts. Use on TV, radio, hi-fi, transmitting or test equipment. Protects against humidity, dust, corrosion and leakage currents. Long lasting. High dielectric strength.

KRYLON SPRAY PAINTS




Choice of 24 standard colors and 7 glowing fluorescent spray paints. Use for touchup, color coding, safety, or repainting cabinets and enclosures. DRY IN MINUTES.

If you prize it . . . KRYLON-ize it!
Contact your Radio-TV jobber or write for Krylon's new industrial products catalog
KRYLON, INC., NORRISTOWN, PA.



--- for more details, circle 34 on page 50

Outperforms them all! Outsells them all!

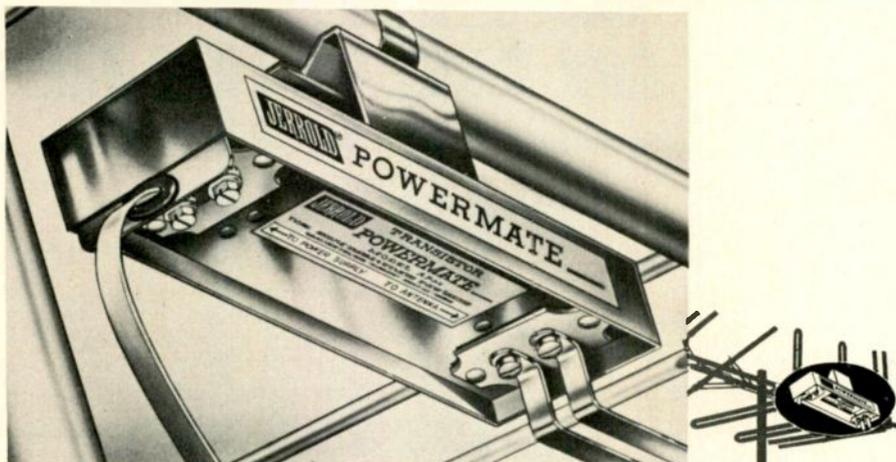

JERROLD®

TRANSISTOR

POWERMATE

PREAMPLIFIER

BY FAR THE BEST antenna preamplifier in the business—that's POWERMATE! On black-and-white, and where it *really counts*—on color TV—POWERMATE's superiority shows up across the country.

The better VSWR (impedance match), flat response, ultra-high gain, special broad-band neutralizing transformer, and better power-supply filtering—all add up to an outstanding product. No polarity problems . . . no call-backs . . . transistor protected from lightning-coupled surges . . . remote a-c power supply feeds 2 sets.

Step up to POWERMATE, and step up to a tremendous new profit opportunity. See your Jerrold distributor now.

Model APM-101 \$39.95 *list, complete*

JERROLD ELECTRONICS CORPORATION

Distributor Sales Division, Dept. IDS-216, Philadelphia 32, Pa.
Jerrold Electronics (Canada) Ltd., Toronto • Export: CBS International, New York 22, N. Y.

... for more details, circle 33 on page 50

... Advertising Guide

Continued from page 41

2. Advertisements as a whole may be completely misleading although every sentence separately considered is literally true. This may be because things are omitted that should be said, or because advertisements are composed or purposely printed in such way as to mislead.
3. Advertisements are not intended to be carefully dissected with a dictionary at hand, but rather to produce an impression upon prospective purchasers.
4. Whether or not the advertiser knows the representations to be false, the deception of purchasers and the diversion of trade from competitors is the same.
5. A deliberate effort to deceive is not necessary to make out a case of using unfair methods of competition or unfair or deceptive acts or practices within the prohibition of the statute.
6. Laws are made to protect the trusting as well as the suspicious.
7. Pricing representations, however made, which are ambiguous will be read favorably to the accomplishment of the purpose of the Federal Trade Commission Act, as amended, which is to prevent the making of claims which have the tendency and capacity to mislead.

Limitations

No statement which represents or implies a reduction or saving from an established retail price or from the advertiser's usual and customary retail price should be used if, (a) an artificial mark-up has been used to provide the basis for the claims, or (b) the claim is based on infrequent or isolated sales, or (c) the claim is based on a past price, unless this fact is clearly and adequately disclosed.

"Two For One Sales"

No statement should be made in connection with the offering for sale of a product to the consuming public of a "factory" or "wholesale"

price, or other such expression, which represents or implies that the consuming public can purchase the article at the same price that retailers regularly do, and provides a saving from the usual and customary retail price for the article in the trade area, or areas, where the claim is made unless such statement is true.

"Pre-Ticketing"

No article should be "pre-ticketed" with any price figure, either alone or with descriptive terminology, which exceeds the price at which the article is usually and customarily sold in the trade area, or areas, where the "pre-ticketed" article is offered for sale.

Bait Advertising Defined

Bait advertising is an alluring but insincere offer to sell a product or service which the advertiser in truth does not intend or want to sell. Its purpose is to switch consumers from buying the advertised merchandise, in order to sell something else, usually at a higher price or on a basis more advantageous to the advertiser. The primary aim of a bait advertisement is to obtain leads as to persons interested in buying merchandise of the type so advertised.

Guarantees In General

In general, any guarantee in advertising shall clearly and conspicuously disclose—

- (a) The nature and extent of the guarantee.

This includes disclosure of—

- (1) What product or part of the product is guaranteed,
- (2) What characteristics or properties of the designated product or part thereof are covered by, or excluded from, the guarantee,
- (3) What is the duration of the guarantee,
- (4) What, if anything, any one claiming under the guarantee must do before the guarantor will fulfill his obligation under the guarantee, such as return of the product and payment of service or labor charges;

and

- (b) The manner in which the

guarantor will perform. This consists primarily of a statement of exactly what the guarantor undertakes to do under the guarantee. Examples of this would be repair, replacement, refund. If the guarantor or the person receiving the guarantee has an option as to what may satisfy the guarantee this should be set out;

and

- (c) The identity of the guarantor. The identity of the guarantor should be clearly revealed in

all advertising, as well as in any documents evidencing the guarantee. Confusion of purchasers often occurs when it is not clear whether the manufacturer or the retailer is the guarantor.

"Satisfaction Or Your Money Back" Representations

"Satisfaction or Your Money Back," "10-Day Free Trial," or similar representations will be construed as a guarantee that the full purchase price will be refunded at the option of the purchaser. ■

TRAIN WITH THE LEADER



**FOR YOUR
FCC LICENSE**

Prepare for your First Class FCC License through NRI's special and up-to-date FCC home-study course. Qualify for better paying jobs and growing opportunities open to you with your FCC "Ticket." Train with NRI—oldest and largest school of its kind. **MAIL NOW** ➔

National Radio Institute
Washington 16, D. C.

Send me information on NRI's special FCC License training. (No representative will call.)
PLEASE PRINT

Name.....Age.....
Address.....
City.....State.....
Accredited Member National Home Study Council

- - - for more details, circle 37 on page 50

Binders . . .

for your **CIRCUIT DIGESTS**

10 3/4" x 14 1/4"

are now available to **ELECTRONIC
TECHNICIAN** subscribers!

These sturdy spring-type (no holes to punch) binders are bound in dark red, hard bookcover material . . . they hold 24 monthly issues of **CIRCUIT DIGESTS** plus other reference literature . . . and are embossed in gold on the front and the back binding. Another **ELECTRONIC TECHNICIAN** service — to help you preserve and get more convenient use out of your valuable **CIRCUIT DIGESTS**!

\$2.95 each—Postpaid
(for Canada and Foreign—add 50¢ postage)

ELECTRONIC TECHNICIAN
1 East First St., Duluth 2, Minn.

Please ship....."CIRCUIT DIGEST BINDERS." I enclose
\$.....
(please print)

Name.....
Street & No.....
City.....Zone.....State.....

NOW-FIRST TIME EVER!
The exact or equivalent
replacement for nearly every
record player made since 1930


MASTER CARTRIDGE SUBSTITUTION GUIDEBOOK

by Jack Strong

For everyone who services or sells record players this
guidebook will pay for itself over and over again by:

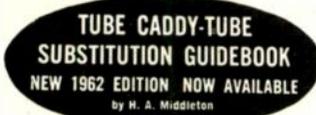1. saving time in locating the right replacement quickly.
2. saving money by cutting down on the number of cartridges you need to stock.

This cross reference guide book will help you locate the exact replacement or equivalent cartridge (mono or stereo) for virtually every record player made since 1930. Even the old record players can be serviced through the use of universal replacement types. The book consists of two parts. In Part I, substantially all cartridges made since 1930 are listed, first by numerical order, and then in alphabetical order. This listing also shows one or more equivalent cartridge types and its manufacturer. Part II, lists (60) record player manufacturers, and the model numbers of their players, and the part number of the original cartridge used. #288, \$2.00.



(Direct Receiving Tube Substitutions Only... plus added new feature—1300 direct CRT substitutions)

This direct substitution guide, designed to be carried in the tube caddy, contains only direct receiving tube substitutions which can be made without modification of the wiring.

This guidebook will—

- save you time
- eliminate carrying needless tube types
- enable you to select the best substitution
- minimize sales losses because you don't have the right tube


It will pay for itself on the first service call!
It contains substitutions for: • Receiving tubes • Ruggedized tubes • European-to-American tubes • American-to-European tubes • Cathode-Ray Picture tubes.
Cat. #299... still only 90c

CAUTION—You can't afford to be without this book!
HOW TO AVOID LAWSUITS IN TV-RADIO-APPLIANCE SALES & SERVICE by Leo Parker. "... A valuable manual for the technician..."—ELECTRONICS WORLD.
• When can a serviceman collect for repairs?
• When is a service guarantee enforceable?
• When can a serviceman demand cash payment?
• When does a lien protect a serviceman?
• How can a knowledge of contract law earn profits?
• How valid are written contracts?
• What are the insurance laws?
• These are just a few of the vital questions that are answered in this book written by an experienced lawyer. It covers many situations that you may face if you sell equipment, enter a home to service it or receive equipment for servicing in your shop. #283, \$1.00.

You can depend upon any of the direct substitutions in **INTERNATIONAL TRANSISTOR SUBSTITUTION GUIDEBOOK** by Keats A. Pullen, Jr. Eng. D. (Scientific Staff, Ballistics Research Labs., Aberdeen Proving Grounds) direct substitutions only "possible substitutions deemed doubtful", that is they work only in some cases, were omitted... thus, substitution guide is a 'safe' guide."—INDUSTRIAL ELECTRONIC ENGINEERING AND MAINTENANCE. It's complete and comprehensive—lists 4500 direct substitutions comprised of American, Japanese, British, French, German, Dutch and Italian transistor types. Includes both triodes and tetrodes. Not only are the direct electrical substitution shown, but case styles, dimensions and basing diagrams for the original and substitute also are given. #276—\$1.50.

At your Electronic Parts Distributor,
or order direct from publisher.

Dept. ET-3

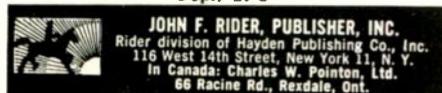

... for more details, circle 43 on page 50

74

NEW BOOKS

SERVICING TRANSISTOR TV RECEIVERS. By Milton Kiver and Charles Gray. Published by Howard W. Sams & Co., Inc. 269 pages, soft cover. \$4.50. This is an inviting book that offers readers a detailed view of transistor television sets. Commencing with two chapters covering basic transistor theory and circuits, the authors then dig into how they're used in TV receivers. Each section of a receiver is examined in turn. How they work and why—including circuit values—is covered in seven meaty chapters. A final chapter discusses servicing techniques, including key test points. The book is well illustrated and lucidly written. Some math is included for those interested, but it may be skipped by readers without losing the flavor of the book. Highly recommended.

WORKING WITH TRANSISTORS. By A. C. W. Saunders. Published by Electronic Technical Publishing Co., Box 306-Astor Station, Boston 23, Mass. 126 pages, soft cover. \$4.95

Elements of transistors and how they are used in various circuits is presented in this book. It's divided into lessons rather than chapters; perhaps due to its logical building blocks starting with basic theory and concluding with special circuits such as protective circuits and gas fume detectors. The book is easy to read; drawings and schematics are very large and math is limited to simple arithmetic when employed. Good, detailed descriptions of transistor circuit operations will probably untangle some confusing concepts held by technicians not too familiar with transistors. Excellent home study book.

THE HORIZONTAL OUTPUT SYSTEM. Published by M. A. Schwarz, Petersburg, Va. 34 pages, soft cover. \$2.95

This is a manual that purports to describe a new technique of testing horizontal output systems using a VTVM instrument only. We do not believe it accomplishes its goal. The text's essence is the author's interpretation of how a horizontal output system and its components operate. It includes some ambiguous and incorrect statements. Additionally, it has not been edited properly, in our opinion, for clarity and continuity. We wish we could recom-

IF YOU CHANGE YOUR ADDRESS

Notify us at 1 East First Street, Duluth 2, Minn. Please include the address label from a recent issue and allow 30 days for the change.

mend this book, but unfortunately we can't.

FM STEREO MULTIPLEXING. By Norman H. Crowhurst. Published by John F. Rider Publisher, Inc. 282 pages, soft cover. \$1.25.

Here's a most timely book. It covers the FM stereo system of broadcasting and reception in a welcome manner. FCC standards are explained and receiver circuitry is thoroughly covered from theory to practical circuit operation. A third of the book is devoted to installation and conversion problems, alignment and performance checks, and troubleshooting procedures. Many schematics of stereo tuner sections and complete stereo FM adapters are included. This is an excellent technicians' primer for stereo FM.

HINTS and KINKS FOR TV, RADIO, AUDIO. Edited by Martin Clifford. Published by Gernsback Library, Inc. 128 pages, soft cover. \$2.35.

Hundreds of gimmicks and gadgets for TV, radio, and audio equipment, shops, and instruments are presented here. They have been selected from items previously published in periodical form. Many will interest technicians; some will probably be used to substitute for unavailable gadgets that could simplify a particular task.



those who
Serve Best
Use

QUIETROLE



6 oz. SPRAY PACK CAN
(with FREE Extender Tube)

2, 4, 8 oz. Bottles
(with dropper)

Product of
QUIETROLE
COMPANY

Spartanburg, South Carolina

in Canada: CROSS CANADA ELECTRONICS
12 Laurel Street, Waterloo, Ontario

There's never any doubt with QUIETROLE... it always says "Sh, Sh" to noisy controls and switches on TV, radio and electronics instruments. Now, Quietrole is even easier to use... has FREE EXTENDER TUBE that hits those hard to reach places right on the button. It's Quality Quietrole that makes those once pesty repairs easier than ever. See how Quietrole can ease the jangled nerves of even your hardest to please customers. Quietrole, helps the serviceman serve better than ever.



... for more details, circle 40 on page 50

ELECTRONIC TECHNICIAN

TOP

Higher Gain

Lower Noise

OF THE HEAP

85% of all TV servicemen prefer Standard turret type replacement TV tuners.

1 year guarantee backed by the world's largest TV tuner manufacturer.

Trade-in allowance for the defective tuner being replaced.

In TV It's Standard

See your local authorized Standard Coil Distributor

standard kollman

INDUSTRIES INC.

FORMERLY STANDARD COIL PRODUCTS CO., INC., MELROSE PARK, ILLINOIS

Important News for Independent TV-Radio-HiFi Service Dealers...



RCA Announces A Major New Program

THIS PROGRAM WILL...

- Identify You as a Trusted Service Dealer
- Highlight Your Technical Competence
- Enhance Your Community Prestige
- Symbolize Your Professional Integrity
- Build Your Public Recognition and Acceptance
- Help Increase Your Business Volume and Profits

See your Authorized RCA Tube Distributor for full details on how you can participate in the *RCA Key to Trusted Service Program*, which is heavily advertised to consumers through TV Guide and NBC-TV.

RCA ELECTRON TUBE DIVISION,
HARRISON, N. J.



The Most Trusted Name in Electronics