

DECEMBER 1976 • 75 CENTS



A H. ROBERT BRACE JOVANOVIĆ PUBLICATION

ELECTRONIC TECHNICIAN/DEALER


WORLD'S LARGEST TV-RADIO SERVICE & SALES CIRCULATION

Isolating AGC Troubles In Solid-State Color

Noise in TV Antenna Systems

Medical Electronics: Servicing Defibrillators

Troubleshooting Power Supplies

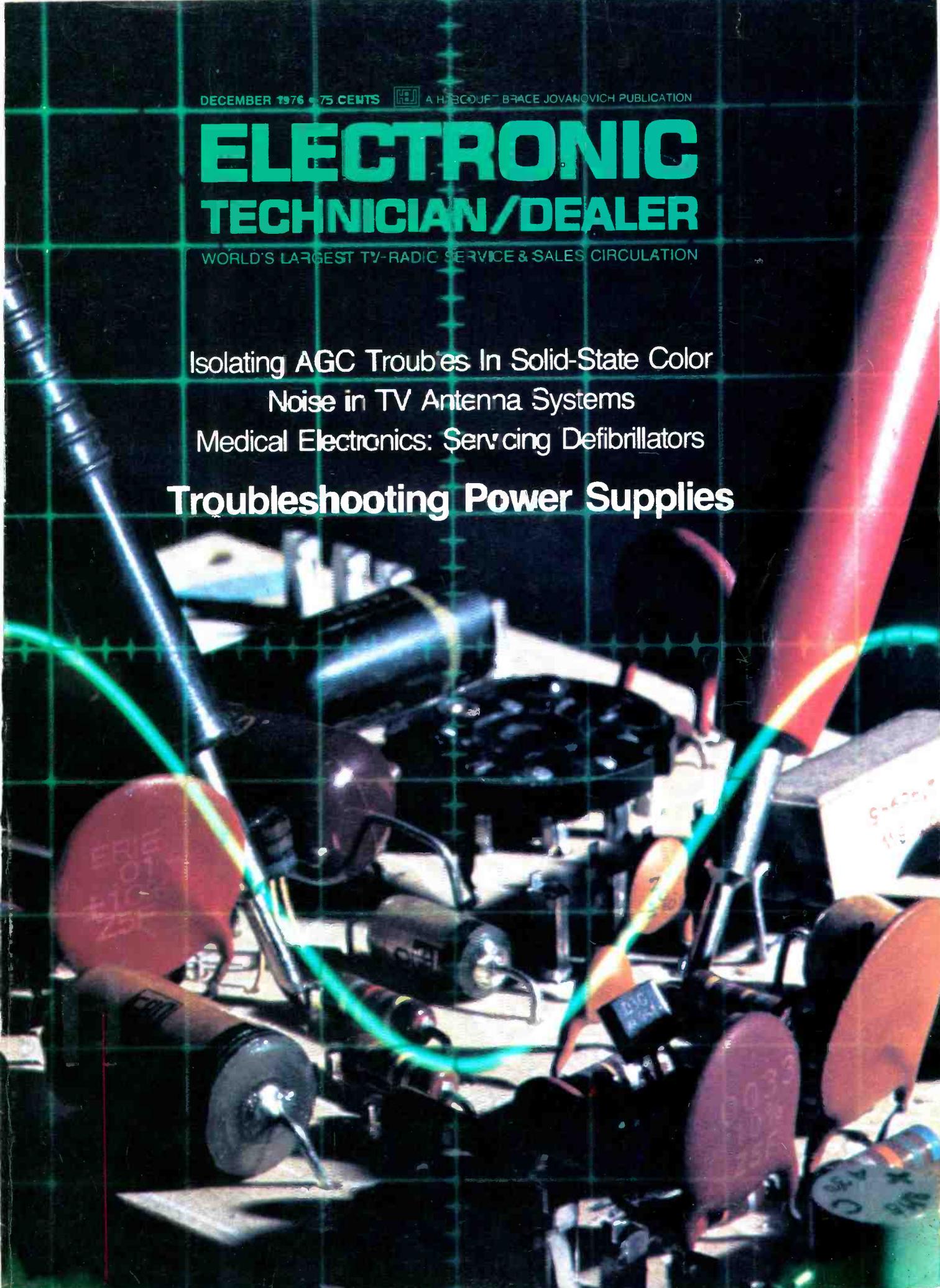

WANTED






TUNERS NEEDING REPAIR

\$\$\$ REWARD \$\$\$


Fast!! Expert Rebuilding Service

REWARD: Increase your profits, save time and gain customer satisfaction with the PTS Tuner Rebuilding Service.

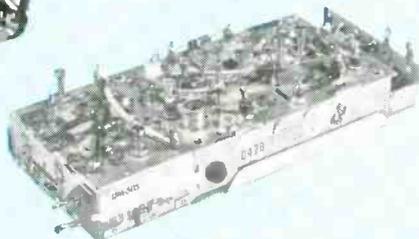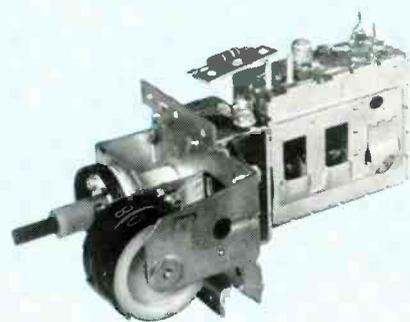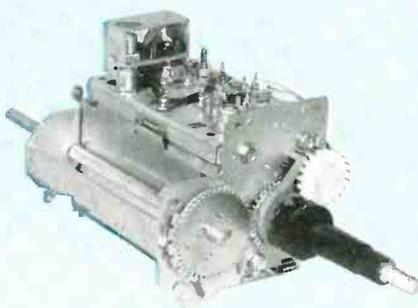- **Eight Hour Service** on any make any model Tuner including foreign makes. Color, Black and White, Tube, Transistor or Varactor.
- **Original Parts**
- **One Year Warranty**
- **Quality**—Professional technicians with major TV manufacturers recommendation do the work.



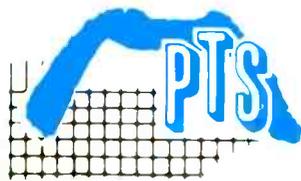- **Protective Packaging**—Protects during shipping and storage.
- **Convenience**—Over 40 PTS company-owned servicenters located throughout the U.S. and Canada. See opposite page for nearest servicenter.



PTS ELECTRONICS, INC.

PRECISION TUNER SERVICE

General Headquarters: P.O. Box 272, Bloomington, IN 47401

...for more details circle 102 on Reader Service Card

EDITOR'S MEMO

On June 7 of this year, the Federal Communications Commission issued a Notice Of Inquiry into its Radio Operator Licensing program.

The purpose of this Notice Of Inquiry was "to solicit comments or recommendations from interested parties concerning changes or revisions which the public believes should be considered by the Commission in its review of the relevancy of its radio operator rules to the current state of the communications industry."

Specific questions asked by the Commission in its Notice Of Inquiry are:

- Should the Commission drop its requirement that the adjustment, repair and maintenance of radio transmitting equipment be performed only by a person holding either a First or Second Class Radiotelephone License? (The Commission refers to such licensed service technicians as 'Service Operators')

- If the 'Service Operator' license requirements are retained, to what degree should the 'Service Operator' be held responsible for the technical performance of transmitting equipment which he installs and/or services? (The Commission's present position is that the 'ultimate responsibility' for the proper technical performance of the equipment rests with the equipment owner, or licensee).

- Do current First and Second Class Radiotelephone License examinations accurately reflect the knowledge required to install and service today's communications equipment?

- Would it be more realistic for the Commission to issue a 'basic operator/technician' class of license with optional specialized endorsements for specific classes of equipment such as AM Broadcasting, TV Broadcasting, Land Mobile, etc.?

- If retained, should the 'service operator' type of licenses be issued for the lifetime of the holder, or, as is current policy, should they be issued for a five-year period with no re-examination required for renewal, or should a five-year re-examination be implemented to determine whether or not the technician's ability has kept pace with technology?

The deadline originally set by the FCC for comments and recommendations regarding these questions was September 1, but, at the request of the National Association of Broadcasters and the Land Mobile Communications Section of the Electronic Industries Association, the deadline subsequently was extended to November 1.



For some as yet unexplainable reason, few members of the consumer electronic service industry were notified of this official FCC inquiry. In fact, the editorial staff of ET/D did not learn of the Notice Of Inquiry until November 9, when Merrill See, the owner/operator of an electronics service firm in Kalamazoo, Michigan,

called us to solicit our comments.

Although the deadline for 'official' comments has passed, I nevertheless will take this opportunity to make the following personal observations regarding the areas covered by the Commission's inquiry:

ASSIGNMENT OF LEGAL RESPONSIBILITY—If the transmitter performance criteria established by the FCC is really necessary to insure both optimum utilization of the RF frequency spectrum and quality communications with minimum man-made interference, then *somebody* has to be held *legally responsible* for insuring that the performance of the transmitting equipment continues to meet established criteria after it is purchased and put into use.

Responsibility Of The Owner—Unless the owner of the equipment (licensee) is assigned some degree of legal responsibility for the technical performance of his or her transmitting equipment, there will exist no real motivation for him or her to have it serviced except when it fails to provide the minimum quality of communications which he or she expects—and we all know that most types of transmitting equipment can 'fail' in a manner which causes interference with other users of the frequency spectrum, yet still provides the owner (or operator) the minimum quality of communications he or she expects.

However, because most owners (and operators) of transmitting equipment have neither the knowledge nor technical skill needed to accurately determine whether or not their equipment is performing in accordance with FCC criteria, they realistically should not be held legally responsible for making such a judgment. Instead, their legal responsibility in the event of 'obvious' equipment failure or upon notification of equipment performance in violation of FCC criteria should be limited to the requirement that they immediately turn off the equipment and turn it over to a technician qualified to repair it.

Responsibility Of The Technician—Unless the servicing technician also is assigned some degree of legal

continued on page 46

YOU'VE GOT US WHERE YOU WANT US!

THE WORLD'S LARGEST TUNER SERVICE IS CLOSE TO YOU!

MIDWEST

Home Office
BLOOMINGTON, IN 47401
5233 S. Hwy. 37, P.O. 272
812-824-9331
CLEVELAND, OH 44134
5682 State Road
216-845-4480
KANSAS CITY, KS 66106
3116 Merriam Lane, P.O. 6149
913-831-1222
MINNEAPOLIS, MN 55408
815 W. Lake St., P.O. 8458
612-824-2333
ST. LOUIS, MO 63130
8456 Page Blvd., P.O. 24256
314-428-1299
DETROIT, MI 48235
13707 W. 8-Mile Rd.
313-862-1783
GRAND RAPIDS, MI 49501
1134 Walker Northwest
P.O. 1435
616-454-2754
CINCINNATI, OH 45216
8172 Vine St., P.O. 15491
513-821-2298
MILWAUKEE, WI 53218
3509 W. National
414-464-0789
COLUMBUS, OH 43227
4005A E. Livingston
614-237-3820
INDIANAPOLIS, IN 46202
28 E. 14th St.
317-631-1511
DAVENPORT, IA 52805
2024 E. River Dr., P.O. 187
319-323-3975
OMAHA, NE 68132
5008 Dodge Street
402-558-1800
CHICAGO
Berkeley, IL 60163
1752 S. Taft Street
312-449-7640

SOUTH

JACKSONVILLE, FL 32210
1918 Blanding Blvd., P.O. 7923
904-389-9952
WASHINGTON, DC
Silver Spring, MD 20910
8880 Brookville Rd.
301-565-0025
CHARLOTTE, NC 28225
724 Seigle Ave., P.O. 5512
704-332-8007
BIRMINGHAM, AL 35222
524-32nd St. So., P.O. 31004
205-323-2657
MEMPHIS, TN 38118
3614 Lamar Ave., P.O. 18053
901-365-1918
NORFOLK, VA 23504
3118 E. Princess Anne Rd.
804-625-2030
NEW ORLEANS
Metairie, LA 70004
3920A Airline Hwy., P.O. 303
504-837-7569
TAMPA, FL 33690
2703 S. Macdill, P.O. 14301
813-839-5521
NASHVILLE, TN 37214
2426 A Lebanon Rd.
615-885-0688

NORTHEAST

SPRINGFIELD, MA 01103
191 Chestnut, P.O. 3189
413-734-2737
PHILADELPHIA
Upper Darby, PA 19082
1742-44 State Road
215-352-6609
PITTSBURGH, PA 15202
257 Riverview Ave., P.O. 4130
412-761-7648
E. PATERSON, NJ 07407
158 Market St., P.O. 357
201-791-6380
BUFFALO, NY 14212
993 Sycamore St., P.O. 1241
716-891-4935
BOSTON
Somerville, MA 02144
52 Holland St., Davis Sq.
617-666-4770
SYRACUSE, NY 13204
418 Solar St., P.O. 207, Salina St.
315-475-2330

PACIFIC

SACRAMENTO, CA 95841
4611 Auburn Blvd., P.O. 41354
916-482-6220
SAN DIEGO, CA 92105
5111 University Ave., P.O. 5794
714-280-7070
LOS ANGELES, CA 90023
4184 Pacific Way
213-266-3728
PORTLAND, OR 97213
5220 N. E. Sandy Blvd.
P.O. 13096
503-282-9636
SEATTLE, WA 98109
432 Yale Ave. N., P.O. 9225
206-623-2320

MOUNTAIN

DENVER
Arvada, CO 80001
4958 Allison St., P.O. 672
303-423-7080
SALT LAKE CITY, UT 84106
1233 Wilmington Ave.
P.O. 6218
801-484-1451
PHOENIX, AZ 85061
2412 W. Indian School Rd.,
P.O. 27248
602-266-0582

SOUTHWEST

LONGVIEW, TX 75601
Mapac Rd., P.O. 7332
214-753-4334
OKLAHOMA CITY, OK 73106
3007 N. May, P.O. 60566
405-947-2013
HOUSTON, TX 77207
4326 Telephone Rd., P.O. 26616
713-644-6793

CANADA

MONTREAL, P.Q.
8400 St. Lawrence Blvd.
Room 205
514-381-4233



PTS ELECTRONICS, INC.
PRECISION TUNER SERVICE

...for more details circle 102 on Reader Service Card

J.W. PHIPPS
Editor
1 East First Street
Duluth, Minn. 55802
(218) 727-8511

ALFRED A. MENEGUS
Publisher
757 Third Avenue
New York, N.Y. 10017
(212) 754-4382

TOM GRENEY
Publishing Director

DONALD W. MASON
Managing Editor

JOHN PASZAK
Graphic Design

DEBI HARMER
Production Manager

BERNICE GEISERT
Production Supervisor

LILLIE PEARSON
Circulation Fulfillment

GENE BAILEY
Manager, Reader Services

ROZ MARKHOUSE
Classified Ad Manager

DISTRICT MANAGERS

DAVE HAGELIN
43 East Ohio Street
Chicago, Ill. 60611
(312) 467-0670

CHUCK CUMMINGS
Ad Space South/West
613 North O'Connor
Irving, Texas 75061
(214) 253-8678

ROBERT UPTON
Tokyo, Japan
C.P.O., Box 1717

ELECTRONIC TECHNICIAN/DEALER

DECEMBER 1976 • VOLUME 98 NUMBER 12

THE COVER: The scope and circuit highlight the subject of two scope-related articles in this month's issue—TV Power Supply Troubleshooting, on page 14, and Scope That Power Supply, on page 31.

10 Discrete AGC In Solid-State Color TV

A description of various discrete AGC designs, how they function, and generalized troubleshooting methods. By Paul Shih

14 TV Power Supply Troubleshooting

A Tech Book Digest of Chapter 11 from Robert L. Goodman's TAB book, "Troubleshooting With The Dual-Trace Scope." Plus a review of the complete book.

24 Noise and Noise Figure

What "noise figure" is—where it comes from—how it is determined—and what it means to TV picture quality. By James E. Kluge

28 Intro to Defibrillator Servicing

A look at a fairly simple piece of medical electronic equipment—and how it can be serviced for additional shop income. By Joseph J. Carr

31 Scope That Power Supply

The technique of trouble-shooting power supplies with a scope—and how it can solve many "tough dog" problems. By Joseph J. Carr

DEPARTMENTS

- | | |
|---------------------------|----------------------|
| 1 EDITOR'S MEMO | 48 CLASSIFIED ADS |
| 4 NEWS OF THE INDUSTRY | 50 ADVERTISING INDEX |
| 8 TECHNICAL LITERATURE | 51 READERS SERVICE |
| 38 TEST INSTRUMENT REPORT | 53 TEKFAQ |
| 41 NEW PRODUCTS | |

 A HARCOURT BRACE JOVANOVICH PUBLICATION



HARCOURT BRACE JOVANOVICH PUBLICATIONS. Robert L. Edgell, President, Lars Fladmark, Senior Vice President, Richard Moeller, Vice President/Treasurer, Thomas Greney, Vice President, Ezra Pincus, Vice President, James Gherna, Vice President, Lois Sanders, Vice President, George Glenn, Editorial Director.

ELECTRONIC TECHNICIAN/DEALER is published monthly by Harcourt Brace Jovanovich Publications. Corporate offices: 757 Third Avenue, New York, New York 10017. Advertising offices: 43 East Ohio Street, Chicago, Illinois 60611 and 757 Third Avenue, New York, New York 10017. Editorial, Accounting, Advertising Production and Circulation offices: 1 East First Street, Duluth, Minnesota 55802. Subscription rate: one year, \$7; two years, \$12; three years, \$16 in the United States and Canada. Other countries: one year, \$15; two years, \$24; three years, \$30. Single copies: 75¢ in the U.S. and Canada; all other countries: \$2. Second Class postage paid at Duluth, Minnesota 55806 and at additional mailing offices. Copyright © 1976 by Harcourt Brace Jovanovich, Inc. All rights reserved. No part of this publication may be reproduced or transmitted in any form or by any means, electronic or mechanical, including photocopy, recording, or any information storage and retrieval system, without permission in writing from the publisher.

POSTMASTER: Send Form 3579 to ELECTRONIC TECHNICIAN/DEALER, P.O. Box 6016, Duluth, Minnesota 55806.

Sylvania introduces the first 5-year warranty* on picture tubes.

How can we give you a limited warranty this good?

Because we have complete confidence that our Color Bright 85[®] picture tubes will outlast this 5-year warranty and keep on giving your customers beautiful pictures.

We produce these tubes on the same equipment as our All-New line which is sold as original equipment to TV set manufacturers.

It's terrific to be able to offer your customers a high-quality tube with a warranty like this at no risk to you. There's good profit in it, too. So get in touch with your local distributor today, and get cracking on your first five years.

*Limited Warranty, naturally.
It doesn't cover labor for replacing a tube.

GTE SYLVANIA


GTE Sylvania, Electronic Components Group, 100 First Ave., Waltham, MA 02154

YOU CAN BE SURE

MORE TIMES IN MORE CIRCUITS WITH SENCORE DIGITAL MULTIMETERS

SENCORE

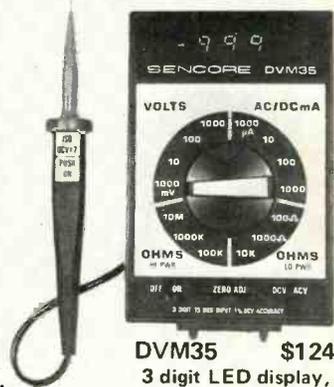A NEW BREED OF DVM's
BACKED BY 25 YEARS OF
ALL AMERICAN CRAFTS-
MANSHIP, WITH SIX EX-
CLUSIVE FEATURES, SO
YOU CAN BE MORE SURE,
MORE OFTEN
AND ALL WITH HI & LO
POWER OHMS FOR MEAS-
URING ACCURATELY IN
SOLID STATE CIRCUITS.



DVM35 \$124
3 digit LED display,
1% DCV accuracy,
battery or AC operated



1 ONE THIRD LESS CIRCUIT LOADING to make you sure that you are affecting the circuit being tested as little as possible for more accurate measurements. Sencore digitals are 15 megohm, others are 10 megohm.



2 2000 DCV range to make you sure that you can measure TV boost volts, scope voltages, medical equipment, etc. Other digitals stop at 1000 volts. High voltage probe extends measuring capabilities to 50 KV.



3 PROTECTED INSIDE AND OUT so you can be sure that your meter is working and not in the repair shop. Drop it from 10 feet, apply 1000 volts overload and even apply volts on ohms accidentally and Sencore digitals keep right on working.

NEWS OF THE INDUSTRY

Texas Survey Provides An Electronic Service Dealer Profile

A survey of Texas area electronic service dealers conducted by the Texas Electronic Association (TEA) earlier this year, and reported in *TEA Times*, revealed that:

- *Home service calls in Texas cities over 100,000 were priced from \$10.95 to \$30, with an average of \$18. In cities less than 100,000 the rates ranged from \$7.50 to \$28.50, with an average of \$14.
- *50% of the dealers were mainly in service with some sales—27% were strong in both sales and service—and 23% were service only.
- *The average service-only dealer in the survey reported a net profit of 10%. The average sales and service dealer reported a net profit of 6%—and 75% of all surveyed said they made more money in 1975 than in 1974.
- *The largest operator in the survey employed 11 outside technicians, but the average shop had only one outside technician.
- *A 40-hour work week for service personnel was reported by 61% of the dealers with answers varying from 35 hours to 60 hours.
- *The average service calls per day in large cities was 8—and in small communities, 7.
- *Outside accountants were employed by 77% for the firm's bookkeeping.
- *42% had been in business 5 years or less—10% had been in business from 5 to 10 years—17% from 10 to 20 years—and 28% for more than 20 years.

GTE Sylvania Will Realign TV Manufacturing Operations To Meet Foreign Competition

An effort to "meet unfair price competition from foreign sources" is the reason given by GTE Sylvania for their consolidation of all color TV final assembly operations in one U.S. facility. GTE Sylvania is a subsidiary of General Telephone & Electronics Corporation.

Frank R. Lann, senior vice president of the company's Entertainment Products group, said that all final assembly of Sylvania and Philco color television sets in the U.S. will be consolidated in the group's Smithfield, N.C. manufacturing facility beginning Jan. 1, 1977.

"The increasing penetration of the U.S. color television market by certain Japanese manufacturers, using unfair competitive practices, is forcing American set manufactur-



DVM36 \$148
 3½ digit LED display,
 .5% DCV accuracy,
 battery or AC operated



DVM32 \$198
 3½ digit LED display,
 .5% DCV accuracy,
 battery or AC operated
 with automatic battery saver



DVM38 \$348
 3½ digit LED display,
 .1% DCV accuracy,
 AC operated, auto-ranging,
 auto-zero, king size pushbuttons



14 BATTERY SAVING FEATURES WHEN INSTRUMENT IS NOT IN USE so you can be sure that your meter will be ready the next time you need it. Push the button on the probe on the DVM35 and DVM36 and only then do you start drawing current from your battery. An automatic patented circuit does the same job for you automatically when you apply voltage to the DVM32. The DVM38 is AC operated.



15 10 DAY FREE TRIAL to be sure that Sencore digitals are all that we say they are. Simply march into your Sencore distributor and ask for a free trial or pay cash with a promise of a 10 day money back guarantee, if not 100% satisfied. Or, write Sencore, and we will see that our distributor contacts you.



16 100% MADE RIGHT LIFETIME GUARANTEE so you can be sure your meter was made right. If at any time you discover that a Sencore DVM was not made right, Sencore will make it right, parts and labor free of charge, for the lifetime of the product.

Plus other "make sure" features such as - direct reading with no parallax error - no effect from magnetic fields such as motors & RF fields - lab accuracy with high resolution - auto-polarity auto-zeroing and auto-ranging on the DVM38 . . . and you can see why you can be sure more times, in more circuits, than with any other multimeter on the market today - and for less money than old fashioned analog meters.

SENCORE 3200 SENCORE DRIVE
 SIOUX FALLS, S.D. 57107

...for more details circle 123 on Reader Service Card

ers to adopt extreme measures to remain competitive," Lann said. "We intend to meet this competition. However, to do so we are forced to make internal adjustments in our production strategy."

"We deeply regret that this decision to consolidate will require the layoff of 488 hourly and salaried employees of the current 1,200 Batavia employees," Lann said.

Headquarters for the Entertainment Products Group, however, will remain in Batavia.

FCC Says Most CB Interference Of TV Is Caused By TV Set Design

The FCC decision in October that generally upheld CB rules on radiation standards and denied the television industry's petitions for stricter CB radiation standards contained a condemnation of the interference susceptibility of TV receivers. As reported in *TV Digest*, a memo from the Safety & Special Bureau of the FCC said, "Although it is quite true that harmonic radiation from some Class D transmitters causes TV interference some of the time to some TV receivers, it is equally true that the majority of complaints received by the FCC result directly from poor TV receiver design, lack of adequate filtering in TV receivers presently on the market, and inability of TV receivers adequately to reject unwanted or adjacent-channel signals."

A spokesman for the FCC, according to the report, expressed hope that TV manufacturers would voluntarily improve designs, in that the FCC currently has no jurisdiction over the aspect of TV receiver design.

Whirlpool To Sell TV Business of Warwick to Sanyo

Pending stockholder and government approval, the Whirlpool Corporation has agreed to sell the controlling interest in the TV business of their subsidiary, Warwick Electronics, to Sanyo Electric. According to *Consumer Electronics Daily*, "Sanyo will acquire all of Whirlpool's stock interest in the new subsidiary for \$10.3 million, or \$4.16 a share, and Sanyo will offer to buy the stock interest of other shareholders with the exception of 25 per cent interest held by Sears, Roebuck.

Channel Master Announces A "Retrofit Or Swap" Option To Cb'ers

Another CB manufacturer, Channel Master, has announced a program to convert their

23-channel models to 40-channel operation. The Channel Master approach will allow purchasers of 23-channel sets the conversion privilege over the next 2½ years, or until June 30, 1979. The buyer has the option of either returning his 23-channel unit for conversion to 40 channels, or he can return the receiver in exchange for a comparable 40-channel model. Depending on the model, conversion prices will be \$39.95 and \$44.95, and exchange prices will be \$69.95 and \$74.95.

RCA Continues to Convert Factory Distributorships To Private Ownership

RCA has converted their factory-branch distributorship for TV receivers and other products in Atlanta to private ownership. The Atlanta operation is the fifth branch of the RCA Distributing Corporation to be turned over to independent ownership in the past two years. The new distributor, the Southco Sales Corporation, will be headed by William T. Blamire, president, who had been with RCA since 1967.

Only three RCA-owned distributorships are left in the country now. They are in Detroit, Los Angeles and San Francisco.

The Winter CES For 1977 In Chicago Is Sold Out

The fifth annual Winter Consumer Electronics Show, January 13-16, at the Conrad Hilton Hotel in Chicago promises to be the largest Winter Show ever held. "We're sold out," Bill Glasgow, show manager, said, "with over 325 exhibitors in the show this year compared to 275 last year—and we have a waiting list of over 30 exhibitor applicants.

Part of the Show's expansion is attributed to the increase in CB radios and accessories exhibitors which total more than 100. Also, more than 15 exhibitors of video home games have signed up.

Newcom '77 To Place More Emphasis On Industrial Electronics

The 1977 Newcom Show, to be held in Las Vegas, May 1 to 5, will focus more attention on the industrial electronics segment of the industry, with panel discussions planned for OEM and MRO distributors. In a report in *Electronic Buyers' News*, Newcom Show executive vice president David Fisher said that "industrial electronics distributors at last year's Newcom—which comprised about one-third of the exhibitors—were overwhelmed by the frenzy created by citizens' band radio exhibits."

New Trade Show Just For Audio Dealers To Make Debut In 1977

Billed as the "first trade event ever devoted wholly and entirely to the audio industry," Audex will make its debut April 25-28 in Las Vegas. A spokesman for the sponsoring organization, the International Audio Exposition, said that with an annual volume of over 6.3 billion dollars, "the audio industry needs its own trade show where the display and demonstration of its products are primary and not subordinated to the exhibit of extraneous and incompatible items."

To learn more, write: Audex, 311 Madison Ave., New York, N.Y. 10017.

ISCET Yearbook To Include Directory of CET's

The International Society of Certified Electronic Technicians (ISET) will add a CET Directory system to the 1977-78 Electronic Service Industry Yearbook, soon to be published. A recent survey by ISCET indicated that a majority of CETs consider a national directory of CETs would be of value. All CETs who want to be included in the directory are asked to send their name, address, telephone number, and CET number, along with \$5.00 to: ISCET, 1715 Expo. Ln., Indianapolis, IN 46224. Deadline is Jan. 1, 1977.

PTS Opens Two New Servicenters For A Total of 42

New servicenters in Chicago and Omaha bring the total of tuner servicenters owned and operated by PTS in the United States and Canada to 42. The Chicago servicenter, now located in the suburb of Berkeley, was formerly Central Tuner Service, which PTS recently purchased. The new PTS servicenter in Omaha is located at 5008 Dodge St., and serves Nebraska and parts of Iowa.

National headquarters for PTS are in Bloomington, Indiana.

Co-op Advertising For CB To Increase

According to a report in *Consumer Electronics Daily*, retailers, distributors and manufacturers of CB radio are now relying more on co-op advertising to get the brand names before the public, now that the CB boom has leveled off a bit. "Many distributors and retailers are only now taking advantage of the co-op money available. When times were good," the report indicated, "there was little need to advertise and the paperwork just wasn't worth the trouble. Most CB suppliers have co-op programs—some very elaborate, but each with its own little wrinkle." ■



HEP NOTE



APPLY YOUR SKILLS TO THESE PROJECTS!

THEY'RE JUST WAITING FOR YOU TO TRY IN THE NEW MOTOROLA HEP NOTES


Keeping up with the leading edge of semiconductor technology is sometimes difficult because of the rapid changes that are taking place. HEP has found that one of the better ways to maintain the knowledge necessary is to "do-it-yourself" — keep up with the latest through a "hands-on" program.

HEP NOTES are designed so that you can use some of the newer technologies in a practical manner by building projects that are not only educational, but can be useful in your business. Try one — we think you'll want to try them all! They're available through local HEP distributors.

- HEP NOTE 100 — An 80 Watt, 50 Ohm VHF Amplifier Project
- HEP NOTE 101 — A CMOS Tone Encoder Project
- HEP NOTE 102 — TWO CMOS PROJECTS
 - 1) CMOS Touch Switch Project
 - 2) CMOS Programmable Time Delay Circuit Project
- HEP NOTE 103 — A CMOS Digital Clock Project with Optional 12 or 24 Hour Display
- HEP NOTE 104 — A 99 Minute CMOS Timer Project
- HEP NOTE 105 — A Cordless, CMOS, Liquid Crystal Display Clock Project

SEE YOUR DISTRIBUTOR

... TODAY!

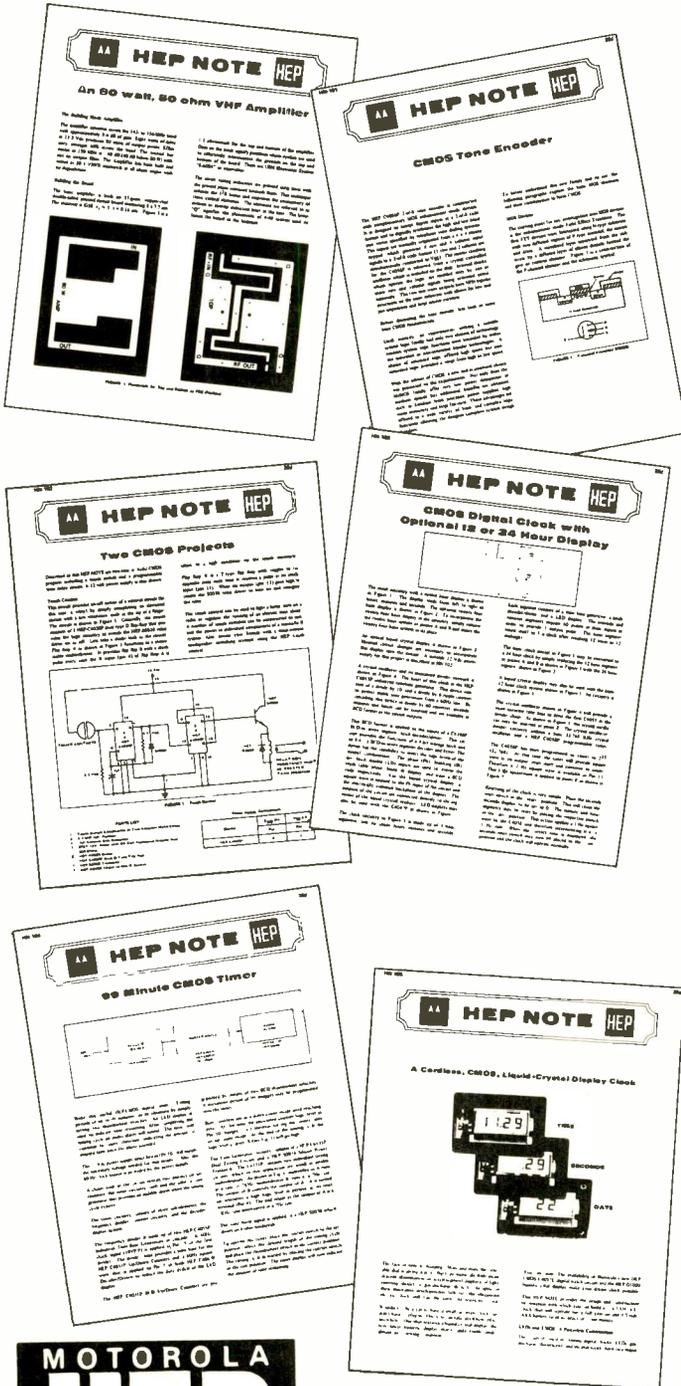

MOTOROLA Semiconductor Products Inc.
HEP/MRO Operations — P. O. Box 20902 — Phoenix, AZ. 85036

TECHNICAL LITERATURE

Sound Systems And Components are presented with photos and descriptions in a new 12-page, 3-color catalog from Argos Sound. Included is a selection of sound columns, a portable sound system, baffle/speakers, wall baffles and CB base and mobile speakers. Specification include weights and measures in standard and metric systems. Free from *Argos Sound*, 600 South Sycamore, Genoa, Ill 60135.

RF Semiconductors for linear applications are described in a new 12-page booklet form TRW. The booklet contains complete data for hybrids and discretes for RF linear applications from microwatts to kilowatts of output from 1 MHz to 4 GHz. It includes specifications, application block diagrams and reliability notes. Available free from *TRW RF Semiconductors*, 14520 Aviation Blvd., Lawndale, Calif. 90260.

Test Instruments for industry, education and service are fully described and pictured in the 1976/77 catalog from Leader. Included complete with specifications, illustrations and prices is the firm's complete line of oscilloscopes/vectorscopes, multimeters, color bar and pattern generators, DVM's, millivolt meters, signal generators, wattmeters, sweep/marker generators and accessories. Available for \$1.00 from *Leaders Instruments Corp.*, 151 Dupont St., Plainville, N.Y. 11803.

Do-it-yourself Electronic Kits, Tools and Supplies are illustrated and described in the latest catalog, No. 21-1976, from Conar. The new catalog lists hundreds of items for young people, electronic servicers and hobbyists, including test instruments, sound systems, clocks, electronic kits, automobile troubleshooting equipment, and hobbyist books. Prices and mail-order instructions are included. Available free from *Conar Division*, National Radio Institute, 3939 Wisconsin Avenue, Washington, D.C. 20016.

CB Antennas, in full color, are described in the latest catalog from Avanti. Included are antennas that utilized the Avanti principle of co-induction, including the omnidirectional Astroplane and the direction Astrobeam, PDL-II, and Moonraker. Facts about CB mobile and base

antennas, the principle of co-induction, and full specifications are included. Free from *Avanti Research & Development*, 340 Steward Avenue, Addison, Ill. 60101.

Electronic Test Instruments are displayed and described in full color in the latest catalog from Sencore. Included are descriptions of the Sencore 'family' of Cricket transistor tester/analyzers, the Big Henry Multimeters, the Mighty Mite tube tester, the Big Mack and Super Mack CRT testers and restorers, and the Little Huey digital color bar generator, plus the full line of other test equipment, including the CB Analyzer. Prices are included. Available free from *Sencore Instruments*, 3200 Sencore Drive, Sioux Falls, S.D. 57107.

A New Audio Connector Series with 7-circuit capability for multi-circuit interconnecting is described in a new product bulletin from Switchcraft, Inc. The 7-pin "Q-G" connector series is presented in response to requests for multi-circuit interconnecting applications such as instrumentation systems, computer peripheral equipment, audio-visual systems, audio consoles, and amplification systems. Included in the series are 13 straight and right angle cord plugs and receptacles and inserts for chassis and special purpose mounting. Available free from Sales Dept., *Switchcraft, Inc.*, 5555 No. Elston Ave., Chicago, Ill. 60630.

Air Suspension Speakers for home and auto hi-fi are described and illustrated in a new min-brochure from the Quam-Nichols Company. The leaflet highlights nine different Quam home and auto high fidelity speakers, indicating the size, frequency response, power handling capacity, voice coil impedance and voice coil diameter, magnet weight, depth and shipping weight, as well as the list price. Notes indicate which speakers have been given a "big bass sound" designation and which incorporate a "whizzer" cone or an integral tweeter. For free copies of the Form 76-4 leaflet, write to: *Quam-Nichols Co.*, 234 E. Marquette Road, Chicago, Ill. 60637.

The 1976 Heathkit Christmas Catalog, describing nearly 500 electronic kits for every do-it-yourself interest, is now available. Product categories include: amateur radio, hi-fi components, color TV, test instruments, digital clocks and weather instruments, radio control equipment, marine, aircraft and auto accessories. New prod-

ucts described are: synthesized 2-meter transceiver, a totally programmable color TV system, an audio control center, scanners, and a freezer alarm. Available free from *The Heath Company*, Benton Harbor, Mich. 49022.

Pricing Methods For Small Business Operators are described in a new booklet from the U.S. Small Business Administration. Titled "A Pricing Checklist for Small Retailers," the 8-page booklet provides a checklist for the owner-manager of a small retail business with 52 questions that probe those considerations—from markup to pricing strategy to adjustments—that lead to correct pricing decisions. Available free from field offices and headquarters of the *U.S. Small Business Administration*, Washington, D.C. 20416.

Business Letters—They're Easier Than You Think—is the topic of a new booklet produced for electronic service shops by Dick Pavlek of Tech Spray. While it has nothing to do with the firm's products, it does provide a lot of good hints on effective business letter writing, including collection letters, parts order communication and promotional letters. The suggestions in the booklet take the ineffective stuffiness out of traditional business letters. Free from *Tech Spray*, P.O. Box 949, Amarillo, Texas 79105.

Professional Electronic Tools and Safety Equipment are catalogued and described in the latest 80-page catalog from Klein Tools. The book is organized for easy reference and fully indexed and contains product descriptions, reference tables, information on OSHA and ANSI regulations and tips on proper use of hand tools. Products listed include: pliers, wrenches, screwdrivers, saws, hammers, measuring tapes, knives, and bull pins. Available free. Ask for Catalog 120 from *Klein Tools, Inc.* 7200 McCormick Rd., Chicago, IL 60645.

Microphones, Antennas, Test Equipment and Accessories for CB are listed and pictured in the latest booklet from Mura Corp. Included in the booklet are variable gain power microphones, three-level gain power microphones and base-station power microphones. A selection of mobile and base station CB antennas and test equipment such as meters, impedance matchers, and multitestors is also included. Free from *Mura Corporation*, 177 Cantiague Rock Road, Westbury, N.Y. 11590. ■

Now... push-button remote TV control... for all channels... for all TV sets.



Jerrold's new all-channel Universal TV Remote Control, Model TRC-82, provides instant push-button selection of *all* TV channels, UHF as well as VHF. Your customers will love the ease with which UHF channels pop in. Tuning is electronic with direct access to the desired channel. There are no motors and no movement, eliminating wear and tear on the TV tuner.

See us at
C.E.S., Exhibit
E-206

The TRC-82 can be attached to the back of *any* Color or Black and White TV set in minutes. It turns the set on and off and fine tunes, in addition to changing channels. The TRC-82 also amplifies incoming signals and eliminates direct pick-up ghosts for better picture quality.

Once you demonstrate this new electronic, all-channel TV Remote

Control, your customers won't want to be without it!

It's packaged in a sturdy, colorful, self-selling carton.



JERROLD ELECTRONICS

GENERAL INSTRUMENT CORPORATION



JERROLD ELECTRONICS CORPORATION • 200 Witmer Road • Horsham, Pennsylvania 19044 • (215) 674-4800

...for more details circle 116 on Reader Service Card

DECEMBER 1976, ELECTRONIC TECHNICIAN/DEALER / 9

Discrete AGC In Solid-State Color TV

By Paul Shih

How various discrete designs function, and generalized procedures for servicing them

■ The principal function of the automatic gain control (AGC) system in a TV receiver is to maintain the "average" output of the video detector at a constant level regardless of fluctuations in the strength of the received signal. Without an effective AGC system, the picture contrast and level of sound produced by the TV receiver would fluctuate in direct proportion to the strength of the received signal. Also, the sync stability would be reduced.

As illustrated in Fig. 1, the AGC systems in modern all-solid-state color TV receivers are closed-loop types in which the level of the horizontal sync pulses in the composite video output of the video amplifier is "sampled" and used to develop a DC control voltage which, in turn, is used to vary the gain of the RF and video IF sections in *inverse proportion* to the strength of the received signal.

REVERSE VS FORWARD AGC

The gain of a tube-equipped video IF stage is controlled by varying the amount of negative (reverse bias) voltage applied to the control grid. Increasing the negative voltage reduces gain.

However, because application of reverse bias to the base-emitter junction of a bipolar transistor-equipped stage completely cuts off the stage, AGC voltage in the form of reverse bias is not used in receivers with bipolar transistor-equipped RF and video IF stages.

Instead, as illustrated in Fig. 2, the gain of RF and video IF amplifiers equipped with bipolar transistors is controlled by shifting the

forward bias of the base-emitter junction either above or below the value which provides maximum gain. In the method called 'reverse' AGC, the gain of the stage is decreased by *decreasing* the forward bias. In the method called 'forward' AGC, the gain of the stage is decreased by *increasing* the forward bias above the value which provides maximum gain.

Despite the fact that the increase in base-emitter junction capacitance caused by forward AGC can attenuate the high-frequency components of a signal, thereby reducing the bandwidth of the stage, forward AGC is nevertheless the most prevalent type employed in today's all-solid-state color TV receivers, principally because, as evident in Fig. 2, it produces a more linear and more gradual reduction in gain than does reverse AGC.

To minimize the bandwidth-reducing characteristic of forward AGC, some color TV designers use both forward and reverse AGC—forward for the first gain-controlled video IF stage, and reverse for the second stage.

NEGATIVE VS POSITIVE AGC VOLTAGE

The polarity of the DC control voltage developed by the AGC system in an all-solid-state TV receiver depends upon the "polarity" and type of RF and video IF transistors to which it is applied.

If the gain-controlled stage is equipped with an NPN bipolar transistor, the polarity of AGC voltage applied to the base will be *positive*. Conversely, if it is equipped with a PNP bipolar tran-

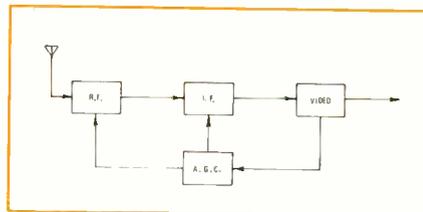


Fig. 1—Illustration of the 'closed loop' configuration of AGC system employed in most color TV receivers.

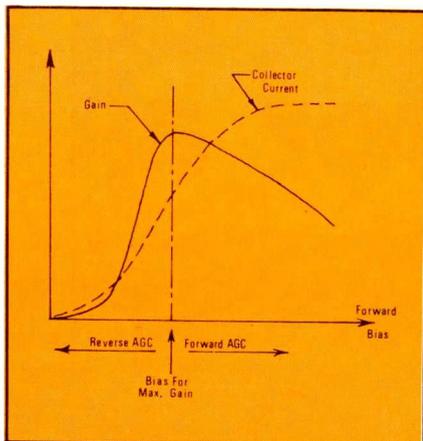


Fig. 2—Graph which illustrates that the gain of a transistor can be reduced by either increasing ('forward' AGC) or decreasing ('reverse' AGC) the base-emitter forward bias.

sistor, the AGC voltage applied to the base will be *negative*.

If, as is becoming more common, the gain-controlled stage is an N-channel dual-gate MOSFET, the AGC voltage applied to the "second" gate of the MOSFET will be *negative* if the device is a *depletion* type and will be *positive* if the device is an *enhancement* type. (The polarities of AGC voltages applied to P-channel dual-gate MOSFETS are opposite those applied to N-channel devices of like types.)

KEYED AGC

The 'keyed' type of AGC system probably is used in more existing TV receivers than any other basic type. Fig. 3 is a simplified schematic diagram of a typical keyed AGC system equipped with and used to control the gain of bipolar transistors.

AGC keyer transistor Q3 in Fig. 3 conducts only when it is "keyed on" by the *simultaneous* presence of a negative-going flyback-originated pulse on its collector and a negative-going horizontal sync pulse in the composite video applied to its base. Fig. 4 is a photo of these two pulses as displayed on the screen of a dual-trace scope.

A negative voltage developed

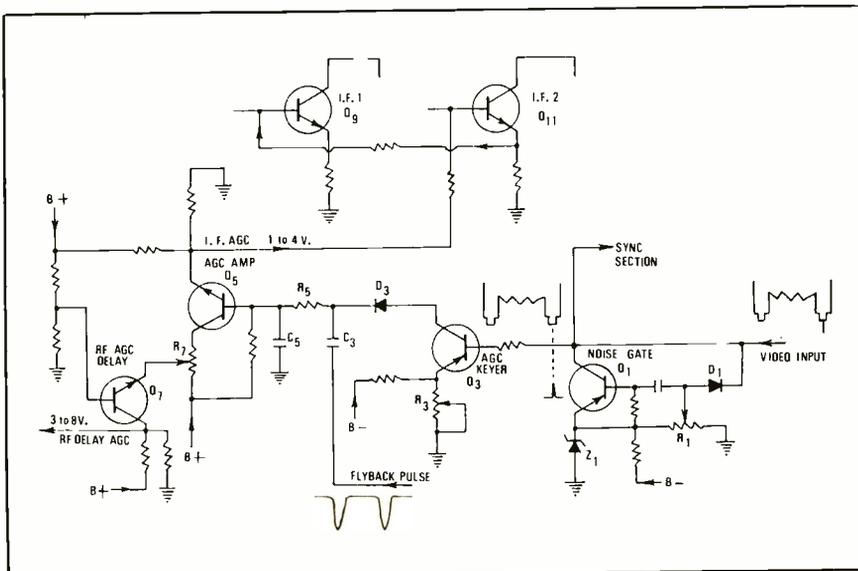


Fig. 3—A typical all-solid-state keyed AGC system.

across a voltage divider in the emitter circuit of Q3 reverse biases the base-emitter junction, holding Q3 in a cut-off condition until the amplitude of the negative-going horizontal sync pulse on the base exceeds the negative voltage on the emitter by .6 volt. Because the level of the negative voltage on the emitter is dependent on the setting of AGC control R3, this control therefore determines at what amplitude of the horizontal sync pulse Q3 will begin to conduct. And, because the amplitude of the horizontal sync pulse on the base of Q3 is directly proportional to the strength of the received signal, the conduction of Q3 and the AGC voltage developed by its conduction will be directly proportional to the strength of the received signal.

Conduction of Q3 charges up coupling capacitor C3, and the DC voltage thus developed across the capacitor is directly proportional to the amplitude of the horizontal sync tip on the base of Q3, which, in turn, is directly proportional to the strength of the RF carrier.

Video information, as well as noise pulses between the horizontal sync pulses, can not affect the AGC voltage, because the keyer, in the absence of the flyback keying pulse on the collector, does not conduct during the horizontal scanning period. In addition, any strong noise pulse that may be present during the horizontal sync period will be effectively cancelled out by noise gate Q1, which is ahead of AGC keyer Q3.

Pulse diode D3 performs two

functions: It rectifies the flyback pulse, and also prevents the charge in C3 from leaking through the base-collector junction of Q3.

The voltage appearing across C5 is the initial AGC voltage.

The time constant of filter R5/C5 can be made very short because the lowest ripple frequency component needed to be filtered out is the horizontal pulse rate of 15,750 Hz, not the 60-Hz field rate as in simple non-keyed AGC circuits. With a short time constant, the keyed AGC system is capable of responding to fast signal variations (such as reflected signals from a passing airplane), thus providing more stable operation.

Video IF AGC

AGC amplifier stage Q5 steps up the AGC current capacity. The amplified AGC voltage for application to the video IF section is taken from the emitter of Q5 because it provides better low-impedance matching into the base circuit of the 2nd video IF stage. The positive AGC voltage may vary from 1 volt for a weak signal, to 4 volts for a strong one.

The IF AGC voltage can be applied to the bases of the 1st and the 2nd IF amplifiers either in parallel or in series. The series connection shown in Fig. 3 minimizes the loading effect between the two stages.

Delayed AGC To RF Amplifier

Application of AGC control voltage to the RF amplifier in the tuner is delayed until the input signal becomes relatively strong.

The reason for this is that the RF amplifier, being the first stage and having the lowest level of input signal, must be allowed to operate at its maximum gain, for a favorable signal-to-noise ratio. The level of the signal at the output of the RF amplifier must be high enough to override the noise generated in the mixer stage. No AGC voltage is applied to the tuner as long as there is no danger of overloading the mixer stage, and the IF AGC is still able to adequately control the gain of the IF stages.

However, an exceptionally strong signal can cause overloading in the mixer (in the form of crossmodulation) or in the IF stages (in the form of signal clipping or distortion). Before this happens, AGC voltage must be applied to the RF amplifier, to reduce its gain. Once this takes place, the RF AGC voltage normally increases more rapidly than does the IF AGC, to prevent the onset of overloading.

There are several ways to delay the application of AGC voltage to the RF amplifier.

The simplest way is to insert an opposite-polarity DC voltage on the RF AGC line through a high-value "bucking" resistor. Before it can impose control action on the RF stage, the AGC bias must exceed the level of the inserted opposite-polarity voltage.

Other designs of delay circuits employ conventional or zener diode clamping networks connected to the AGC bus line to produce the delaying action.

In the keyed AGC system in Fig. 3, a separate amplifier stage, Q7, is used to delay the application of AGC voltage to the RF amplifier. Q7 does not conduct until a strong signal is received and the collector voltage drops on Q5 due to a high collector current. Once Q7 begins to conduct, its collector voltage, or the RF delayed AGC voltage, increases from 3 to 8 volts. This 'forward' AGC is applied to the NPN transistor in the RF stage, decreasing its gain. RF AGC delay control R7 is provided for setting the conduction point of Q7 to assure snow-free reception from weak stations and no overloading from strong ones.

NON-KEYED AGC PEAK DETECTION

A somewhat unconventional

AGC circuit is used by Sony in a number of their color chassis. A simplified schematic of such a circuit is shown in Fig. 5.

The composite video signal from the first video amplifier is fed to a pair of AGC amplifiers, Q209 and Q210. The output from Q210 is then peak detected by a diode, D202, and the current through the diode charges up capacitor C237. The average DC voltage developed across C237 is directly proportional to the amplitude of the incoming sync tips.

If a positive noise pulse with a greater amplitude than that of the sync tip arrives at the input of Q209, it will pass through diode D204 and turn on Q208. With Q208 saturated during the noise pulse period, the base of Q209 is effectively grounded, resulting in the removal of the video signal to the AGC and sync systems. The cutoff of the input signal is so short that no change in the sound or the picture can be perceived. This noise immunity system prevents the noise pulses from interfering with the operation of the AGC and sync systems.

The AGC voltage across C237 is amplified by Q304. The output at the collector is filtered by C337 and applied to the 2nd IF amplifier, Q601. The level of this control voltage can be adjusted by IF AGC control R304.

The IF AGC voltage is routed from the emitter of Q601 to the base of Q603, the 1st IF video amplifier. During reception of a strong signal, the resultant increased conduction of Q603 causes its collector voltage to decrease (become less positive). The less-positive voltage, in turn, switches on the RF AGC gate, Q955. The output from Q955 is amplified by the VHF AGC amplifier, Q953, and then is coupled to the "AGC control" gate of a MOSFET RF amplifier in the VHF tuner. The voltage from Q953 is inverted, and its amount of variation is reduced by UHF AGC amplifier Q954. An NPN RF amplifier in the UHF tuner is controlled by this inverted AGC voltage from Q954.

Controls R953 and R954 are provided to vary each of the RF delay AGC voltages. They are normally adjusted for maximum contrast and minimum snow in the picture during reception of weak VHF and UHF stations, re-

spectively.

TROUBLESHOOTING DISCRETE AGC SYSTEMS

The AGC voltage in a closed-loop AGC system directly controls the operation of the IF and RF stages and also can affect the functioning of the video, noise gate, and sync circuits. In turn, the operation of all these circuits in the loop can affect the function of the AGC system. Troubles anywhere in the loop can cause reactions along the entire loop.

Trouble Symptoms And Typical Causes

Some of the more common trouble symptoms caused by faults in the AGC system are: no sound and no picture, weak or washed-out picture, overloaded or dark picture with or without sound buzz, picture bending or 'flagwaving', poor vertical locking, busy background or snow on strong channels, co-channel interference and cross modulation, video flutter, line flashing, and picture shading.

Overload and bending of the picture is associated mostly with *insufficient* AGC action, while "washed-out" or "snow" symptoms are the result of *excessive* AGC control. Spurious AC signals riding on the DC AGC voltage can cause picture shading, unstable sync, horizontal line flashing and other 'odd' symptoms.

Preliminary Troubleshooting Procedures

The trouble symptoms described previously are by no means unique to AGC defects. Similar symptoms could be caused by troubles in any stage within the AGC loop system. It is, therefore, important that: 1) the symptom itself be carefully diagnosed, and 2) a logical, systematic procedure be used to isolate the trouble to a particular section during the early stage of troubleshooting.

As a preliminary assessment of the functioning of the AGC system, closely watch the picture while rotating the video IF AGC control. The quality of the picture should vary from "washed-out" at one end of control rotation, to over-contrast, bending or black out at the other end of rotation. The RF delay AGC control can be checked by turning it CCW on a weak signal while noticing the increase of snow in the picture. The

RF AGC control can also be checked on a strong signal by turning it CW while watching for the effects of overloading and cross-modulation in the form of picture streaks following the sound information.

If rotation of the AGC control(s) affects the picture quality in a normal manner and reduces or eliminates the trouble symptom, attempt to adjust the control(s) in the manner and sequence specified in the service literature.

Some receivers do not have any AGC control, while a few have as many as three AGC-related controls. Most receivers have one IF AGC control and one RF AGC Delay control. Whenever possible, the adjustment procedure outlined by the manufacturer should be followed.

The generalized procedure for most sets is as follows: 1) tune in a strong station and turn the contrast control fully CW; 2) advance the AGC level control CW to a point where the picture just begins to bend or distort and then rotate the control CCW slightly; 3) switch the channel selector to a weak station and rotate the RF delay control CW until snow just disappears from the picture; and, finally, switch the receiver back to a strong station again and check for overloading. If overloading or distortion does occur, rotate the RF control CCW slightly and then repeat the IF and RF AGC control adjustments. When consistent, maximum contrast is obtained on all active channels, the contrast control then can be rotated away from its full CW position, if necessary, for normal viewing.

The interaction between the AGC controls and the noise gate control, if one is provided, should

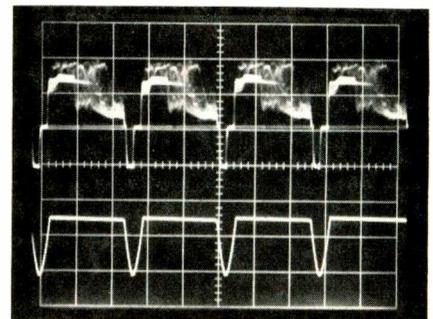


Fig. 4—Photo of the two 'keying' pulses required for conduction of AGC keyer transistor Q3 in Fig. 3. Top) Negative-going horizontal sync pulses in composite video signal applied to base of Q3. Bottom) Flyback-originated negative-going horizontal pulses applied to the collector of Q3.

not be overlooked. Rotating the noise gate control should produce voltage variations in the AGC system. Improper adjustment of the noise gate control can render the AGC and sync sections inoperative. Proper setting of the noise gate control can be accomplished by first turning it fully CCW and then performing the AGC control adjustments outlined previously. Then, slowly advance the noise gate control CW to the point where the video just begins to break up, then rotate it CCW slightly.

Localizing And Isolating The Trouble

If adjustment of the AGC-related controls does not completely eliminate the trouble symptom(s), scope the composite video waveform at a test point in the video section, such as the output of the video detector or the first video amplifier. The amplitude and shape of the waveform should agree with what is specified by the manufacturer. Also, a DC voltmeter connected between the AGC test point and ground should indicate voltage variations when the receiver is tuned from an unused (or weak) channel to a strong one. (A weak station may be simulated on a strong channel by disconnecting and loosely coupling the antenna leads to the receiver.)

If rotation of the AGC controls produces erratic or abrupt increases or decreases of the AGC voltage and/or the amplitude of the video waveform, a defective AGC control should be suspected.

If the video waveform and AGC voltage are both abnormal and adjustment of the AGC controls does not eliminate the abnormality, there undoubtedly is a defect somewhere in the AGC loop. To isolate the trouble, the AGC

source in the loop must be overridden temporarily by an external bias voltage, such as that provided by a bias box.

The reason for using the external bias source is to 'break' the AGC loop. By doing so, the trouble can be narrowed down to one half of the loop—either the *controlling* stages, or the *controlled* stages.

The polarity and the amplitude of the bias to be used generally can be determined quickly by studying the schematic. A general rule of thumb is that a *positive* bias voltage is required for video IFs equipped with NPN transistors or N-channel *enhancement* type MOSFETs, whereas a *negative* voltage is required for video IFs equipped with PNP transistors or N-channel *depletion* type MOSFETs.

To avoid damaging the transistor or FET, the amplitude of the external bias should be initially set at minimum and then gradually increased to the correct value.

If overloading of the external bias source is evident, disconnect the external bias and look for a short somewhere along the AGC bus line or in the input circuit of the controlled stage.

To avoid excessive loading of the AGC, RF and video stages in certain receivers, it is necessary to open the AGC bus line before inserting the external bias in the IF or RF input circuit.

If the insertion of the external bias fails to eliminate the trouble symptom, a defect in the IF or RF section is evident. The best way to deal with a defect in these sections is to measure the DC voltages on the elements of each transistor, along with signal tracing in the associated stage. Incorrect DC voltages or missing or distorted

waveforms are key clues.

The most common defective AGC-related components are shorted or leaky transistors, defective by-pass or decoupling capacitors, and an open component in the signal path, such as a coupling capacitor or a peaking coil.

Trouble in the AGC circuit is indicated if application of the external bias clears up the trouble symptom. Observe the video sync or flyback pulses on the AGC keyer or on the peak AGC detector, in addition to standard DC voltage measurements. If a pulse is missing, signal trace back to its origin. If a distorted pulse or incorrect DC voltage is encountered, focus your attention on the associated transistor and its directly related components.

There should be no pulses or AC ripple on the AGC bus line. If horizontal pulse components are observed on the bus line, look for an open AGC filter capacitor or a defective pulse diode. A defective AGC DC power supply filter capacitor can cause either 60- or 120-Hz ripple voltages to appear in the AGC source. Other common defects beside the filter capacitor are a shorted pulse diode, a leaky or open transistor, a defective "bucking" resistor or clamping diode, and a flyback AGC pulse winding connected in reverse during transformer replacement.

'AGC' Troubles Caused By CATV

Defective components in the chassis are the most common causes of what are or appear to be AGC troubles. However, there are certain types of 'AGC' trouble symptoms that are not caused by defects in the chassis, but, instead, are caused by the antenna distribution system. This is particularly true in CATV systems in which excessively strong signals are present. These can overload receivers which have 'marginal' AGC systems. A simple remedy to this problem is to add a resistive-pad or attenuator in the cable, to reduce the signal to a level which the AGC system in the receiver can handle.

NEXT: IC-Equipped AGC Systems—An analysis of the theory of operation of integrated-circuit AGC systems and procedures for troubleshooting them will be presented in a near-future issue of ET/D. ■

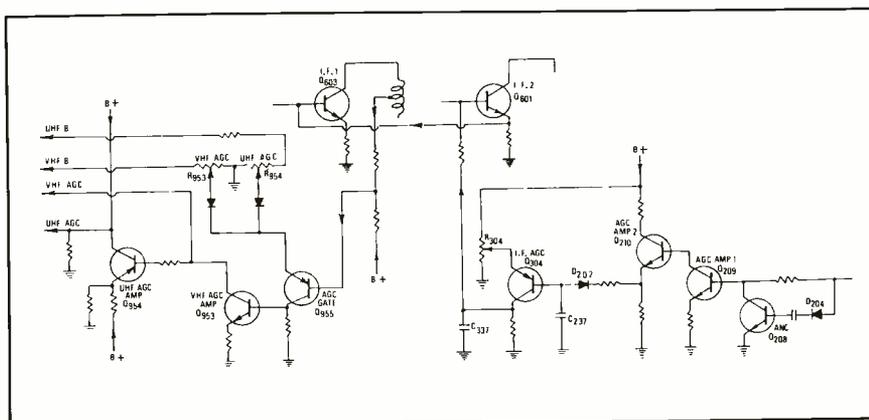


Fig. 5—Simplified schematic diagram of peak detection AGC system used in some Sony color TV receivers.

TECH BOOK DIGEST

Condensed from a single chapter of a recently introduced TAB book, by permission of TAB BOOKS, Blue Ridge Summit, Pa. 17214

TV Power Supply Troubleshooting

CONSTANT-VOLTAGE TRANSFORMER

■ Many of the newer color sets are incorporating the *constant-voltage power transformer* regulation system. This transformer self-regulates all of its secondary voltages. Within the constant-voltage transformer (CVT) the primary and secondary windings are loosely coupled. This is accomplished by placing the windings on separate legs of the core. The regulating circuit consists of an extra winding connected to the high-voltage secondary and a capacitor shunting the total secondary winding.

This CVT system eliminates the need for any additional transistors, zener diodes, or semiconductors to regulate the DC voltages of the power supply. The CVT will also suppress transient pulses from the incoming AC power line. For example, should a 30V transient appear in the primary for approximately 2 seconds, it will appear on the output secondary at less than 15V in amplitude for a duration of only about 100 msec. This helps reduce semiconductor failure in the receiver chassis due to spikes. Since there are no zener diodes or regulator transistors in the power supply, the possibility of a voltage increase due to a zener diode or transistor failure is eliminated. The CVT helps smooth out any voltage surges.

CVT Operation

In a conventional power transformer, the primary is tightly coupled to the secondary. Probably the most frequently used method is for the secondary coil to be

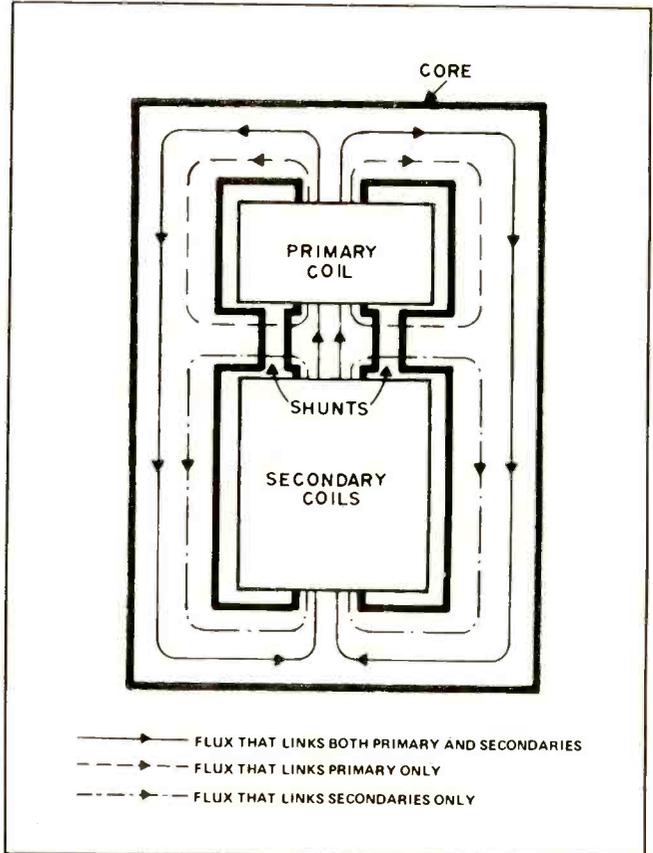


Fig. 1—Constant-voltage transformer construction.

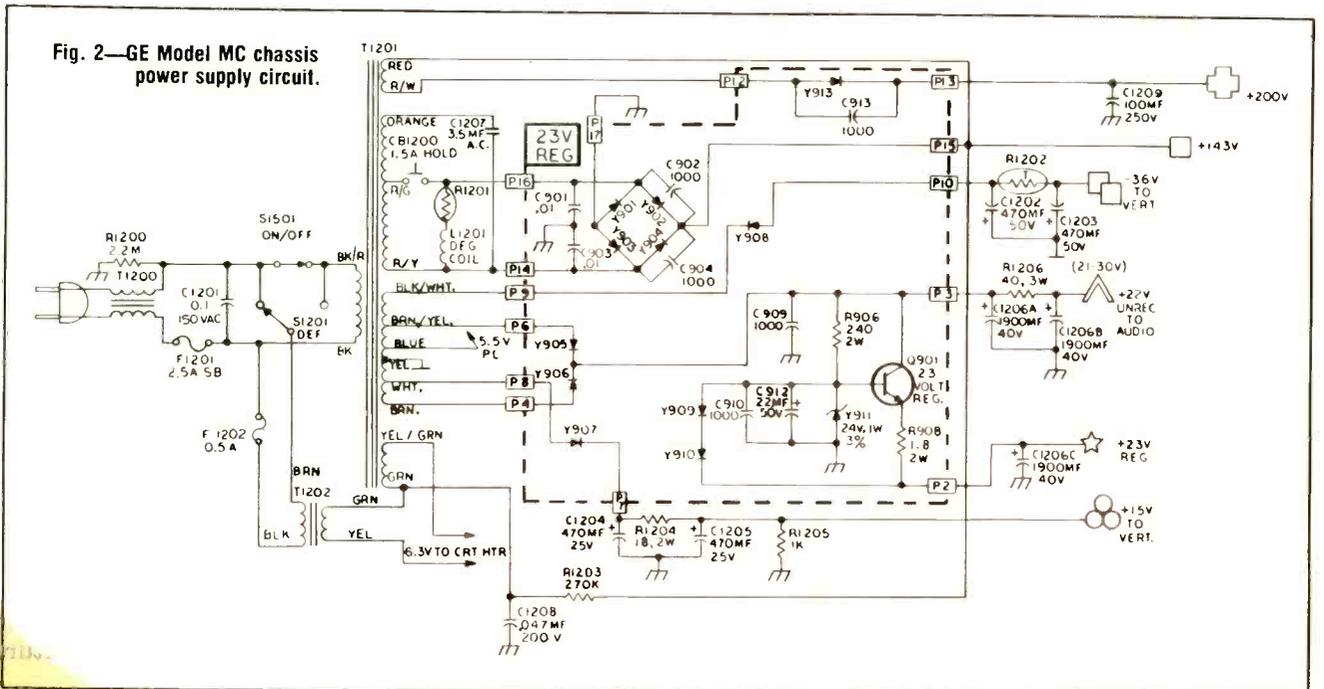


Fig. 2—GE Model MC chassis power supply circuit.

FORD. YOUR FIRST CHOICE IN PARCEL VANS.

14-ft. body
is largest of any parcel delivery van. 8 ft. wide, 6'2" headroom. Ford also offers 12-ft. body.

40% more cube
than Ford's largest previous-design body to take on bigger jobs.

2,200 lbs. more
weight rating than older Fords. GVW's now go to 10,500 lbs.

Separate frame
provides strong support for the longer body. No other parcel van is built this way.

Power choice
includes 300 Six standard, 351 and 460 V-8's optional.

Wide doors
and forward axle location make it easy to step into the roomy cab interior.

Dual rear tires
can take heavy weight, keep load floor low.

Ford Parcel Delivery Vans not only take on big jobs, they make the driver's job easy.

The engine's forward out of the way. There's more room to get in, more room to drive in. You can step right across the cab or into the load area. Power front discs are standard, Cruise-O-Matic Drive available. See what's new in vans; see your local Ford Dealer.



...for more details circle 115 on Reader Service Card

93 out of 100 of all Ford trucks registered over the last 12 years are still on the job.

FORD ECONOLINE VANS

FORD DIVISION



wound over the primary coil on the same leg of the magnetic core. If the AC line voltage changes, then the secondary voltage will change in a linear manner. There is no voltage regulation with a conventional power transformer.

In order for a power transformer to regulate, it must operate in a nonlinear manner. The secondary voltage must not change even though a change does occur in the primary voltage. These conditions are met with the constant voltage transformer illustrated in Fig. 1. The obvious difference in construction between the conventional transformer and the CVT are the *shunts* between the primary and secondary coil windings.

There are three different magnetic flux paths in the CVT. As in the conventional transformer, there is a flux that links both primary and secondary windings, and this sets up the output voltage from the secondary. But in the CVT, the shunts permit the establishment of two other flux paths. As shown in Fig. 1, one set of flux lines remains around the primary coil only, and another set remains around the secondary coil only. It can be said that these two latter sets of flux lines are isolated from each other; therefore, a certain amount of isolation exists between the primary and secondary coils (because of the shunts).

When a capacitor is connected across the secondary output, a capacitive current flows throughout the entire secondary winding. The current flow sets up a flux that is in phase with the flux in the primary winding; this effectively adds to the flux in the core of the secondary. The two fluxes combine to drive the secondary windings into saturation. Since the primary core is not saturated, we have a nonlinear device. Changes in the primary voltage (above certain lower limits) will not affect the secondary, because the secondary coil is already saturated. By keeping the primary unsaturated, we will not draw excessive line currents. With a normal load, the saturated secondary will maintain a constant output voltage over wide ranging primary voltages.

The output wave shape at the secondary winding of the CVT used in some TV receivers is a modified square wave. With 70V AC on the primary, the transformer core under the secondary winding is nearly saturated and the 140V DC supply will be at 80% of its rated value. At 105V AC on the primary, the secondary core is saturated and remains saturated for any further increase in primary voltage.

The operating temperature of the CVT will be higher than a conventional power transformer due to continuous operation in a saturated condition. Thus, the excessive heat does not indicate a defective transformer.

AC Voltage Checks and Square Waves

If AC measurements are made on the regulated secondary windings, you should use a meter that reads true RMS, or use an oscilloscope for peak-to-peak readings. The reason to be particular about the meter is that a *square* wave is present on the CVT secondary winding. You may recall that most (From Chapter 11, *Troubleshooting With The Dual-Trace Scope*, by Robert L. Goodman, TAB BOOKS, Copyright 1976. A review of the complete book follows this article.)

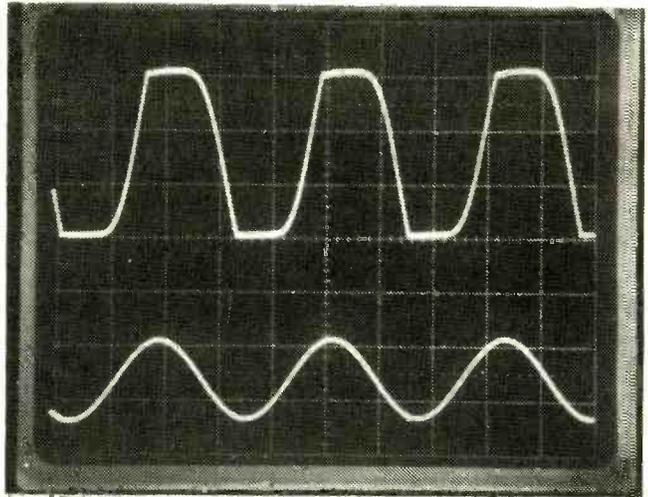


Fig. 3—Scope traces for normal line voltage.

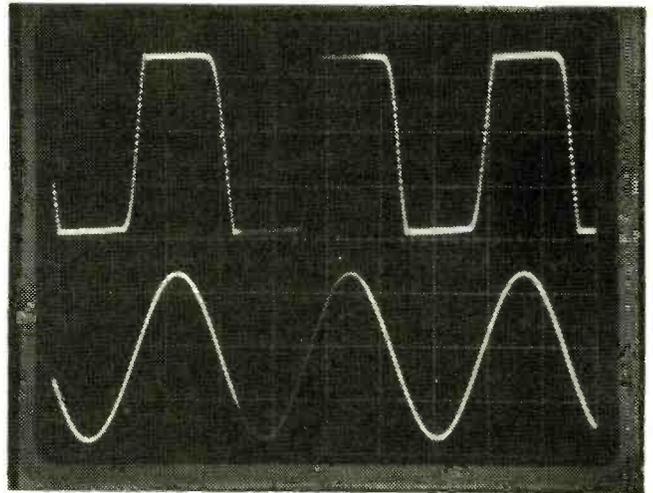


Fig. 4—The AC line voltage set at 60V.



Fig. 5—Good picture even at a line voltage of 60V.

general-purpose instruments are peak-reading meters with a calibrated RMS scale, and do not provide true RMS readings. With the improper meter, the voltage reading at this point will vary with the *peak-reading* type of meter used, and the voltages read will not give a true indication of the circuit conditions.

The oscilloscope can be used with this regulation system. As shown in the power supply schematic in Fig. 2, connect one probe of the dual-trace scope to the AC line voltage input and the other probe to the secondary of power transformer T1201. The bottom waveform in Fig. 3 is the normal 120 V AC line



Fig. 6—Viewable picture even at a line voltage of 50V.

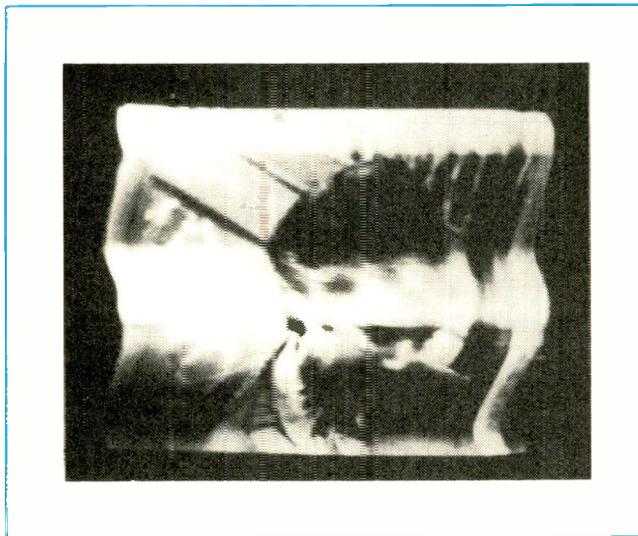


Fig. 7—Ragged picture at a line voltage of less than 50V.



Fig. 8—Small picture caused by open C1207.

voltage sine wave fed to the transformer primary. At the same time, the top trace in Fig. 3 shows the square wave output of the secondary to be 150V p-p. The input AC voltage was lowered to 60 volts AC with an autotransformer. This action is shown in the bottom trace of Fig. 4, but the secondary square-wave voltage shown in the top trace is still approximately 150V p-p. With the AC line voltage down to 60V, a normal, bright picture is still seen, as shown in Fig. 5. Even with the line voltage down to 50V, the picture is pulled in slightly but still viewable (Fig. 6). Below 50V the system cannot properly filter or regulate and

the picture looks quite ragged (as viewed in Fig. 7).

CVT Troubleshooting

Several circuit faults could cause the circuit breaker to trip. A heavy overload of the +143V supply by circuits within the chassis will trip the breaker. A shorted 3.5 mfd timing capacitor (C1207, Fig. 2) will blow the line fuse. The same is true if similar conditions would occur in the +22V or +23V lines. Shorted diodes Y901 through Y904 will cause a heavy overload and blow fuse F1201.

Since there is a chance that 3.5 mfd timing capacitor C1207 may fail, it should not be overlooked during circuit diagnosis. If all B+ voltages and the CRT filament voltages are about 20% low, chances are the resonant circuit, which is formed with a 3.5 mfd capacitor across the total secondary winding, is open. If this capacitor is faulty (open), the picture will be pulled in from the sides, top, and bottom (Fig. 8).

A voltage measurement between the orange and red/yellow leads from the transformer is a good check. This voltage should be approximately 300V RMS under normal conditions. In the event this capacitor fails, it is important to replace it with the correct GE part. Any variation will affect power supply and receiver performance. A higher value will increase the B+ voltage, and this may result in excessive X-radiation.

The circuit schematic in Fig. 9 shows another portion of the power supply system used in GE chassis. Filter choke L1702 and filter capacitors C1702A and B are used on the +143V line in conjunction with the saturable reactor high-voltage regulation transformer. A B+ voltage regulating circuit is not required in this chassis because of the CVT. A similar saturable-core regulation system (Fig. 10) is used in some Zenith color chassis.

If the filter choke (L210, Fig. 10) becomes faulty, it may be difficult to locate, as the only noticeable difference from a perfect picture is a slight vertical bending of the picture. If the picture moves to the right as shown in the photo in Fig. 11, the cause is a shorted filter choke. There is a slight bending on the left edge of the picture raster. Using a dual-trace scope with the probes at the input and output of the filter choke, the ripple trace voltages will look identical on the scope if the choke is shorted. If the choke is good, the input waveform will have some ripple but the output will show a smooth scope trace.

If zener CR211 opens, the picture will pull or weave and produce the same symptoms as an open filter capacitor in a tube-type chassis. Some regulator zeners have been known to oscillate, and this may produce a faint white horizontal bar across the screen that will roll through the picture. A scope can be used to locate this oscillation. If the zener opens, the +24V supply line will measure slightly more than +24V. A faulty Q212, the +24V regulator transistor, will cause a hum in the sound and some hum bars across the screen.

Another version of the saturable-core reactance power transformer is used in the Quasar TS-942 color chassis. Output voltage of this supply is regulated to maintain about 100V throughout the range of AC line voltages normally encountered.

As shown in Fig. 12, the transformer secondary and

capacitor C802 form a resonant circuit. Under normal conditions, the secondary circuit has a high circulating current, resulting in partial saturation of the specially designed core of the transformer. This makes output voltage relatively independent of line voltage variations.

Increased load current reduces the Q of the resonant circuit resulting in decreased saturation of the core and increased transfer of energy from the primary to the secondary. The reverse action occurs for a decreased load. Thus, the supply regulates output voltage for both line and load variations. A circuit breaker in the AC line and fuses in the supply lines protect against excessive currents.

HORIZONTAL SCAN RECTIFICATION

Many modern TV chassis now combine a half- or full-wave rectifier system with a scan rectifier that is needed for the lower regulated DC voltages.

Scan rectification is an efficient method of converting horizontal sweep energy into a DC voltage. A typical circuit, the GE JA color chassis power supply, is shown in Fig. 13. To accomplish the conversion, a winding on the horizontal output transformer inductively transfers horizontal sweep voltage to the scan rectifier, Y402. The sweep voltage is then rectified by Y402 during the relatively long scanning period.

Diode Y402 is reverse biased and does not conduct during the short duration of the retrace pulse (as illustrated in Fig. 14). The output of Y402 is then filtered by capacitor C418 and regulated by Q400 and its associated components to produce the +22V source.

Regulator Q400 is series operated without feedback. A stable 22.5V reference is developed on the base of Q400 by zener Y404, through the path provided by Y403 and R416. The circuit composed of Y404, R418, and C420 also doubles as a separate +22V supply to the sweep circuits in the receiver. Transistor Q400 regulates by operating as a variable resistance. With an increase in circuit current, emitter voltage begins to decrease due to the increased voltage drop across Q400. This condition increases the forward bias on the base-emitter junction of Q400, causing it to conduct more heavily. Greater conduction by Q400 is comparable to a decrease in its resistance, thus restoring the supply voltage to normal. For decreases in circuit current, the reverse effect occurs. R414 and Y405 are for a measure of protection against momentary short-circuit conditions in the 22V line by limiting the amount of current through Q400 in overload conditions. The most common fault in this circuit is a shorted Y402 diode, and that will probably open resistor R412. Leakage in Q400 and faulty Y404 zeners have also caused some problems. Use the oscilloscope to check for the correct pulse (see Fig. 14) that will be found in R412.

There are several different circuit designs that use the stored energy available in the horizontal output transformer to supply low-voltage power to several circuit systems. As shown in the simplified circuit in Fig. 15, energy from the sweep transformer is available during the scan interval and is rectified by diode CR208 to provide a 20V source. This source is resistively divided to provide an additional 12V supply.

Power input from the AC line through a half-wave rectifier provides the higher 115V DC requirements.

ELECTRONIC REGULATION

Because ICs and other solid-state devices are sensitive to excessive voltages, a regulation system is needed in the power supplies. The regulators use a zener diode or a zener-controlled transistor to smooth out the DC voltages and keep the output constant under changing load conditions. These regulators react to changes so rapidly that they are sometimes called electronic filter circuits. Extensive filtering

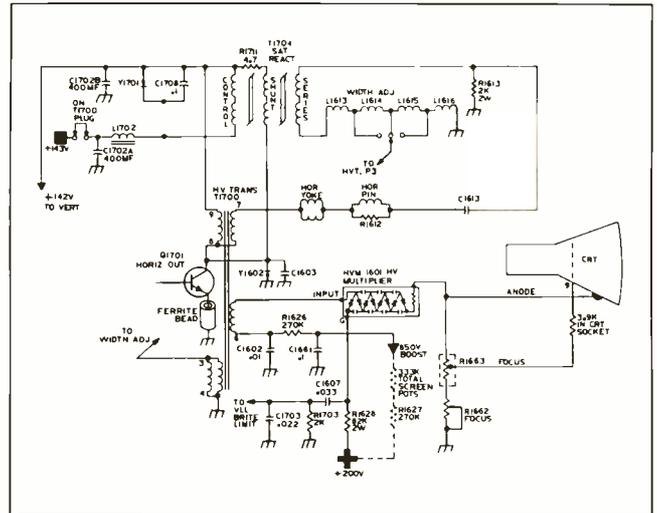


Fig. 9—GE MC chassis filter and high-voltage circuits.

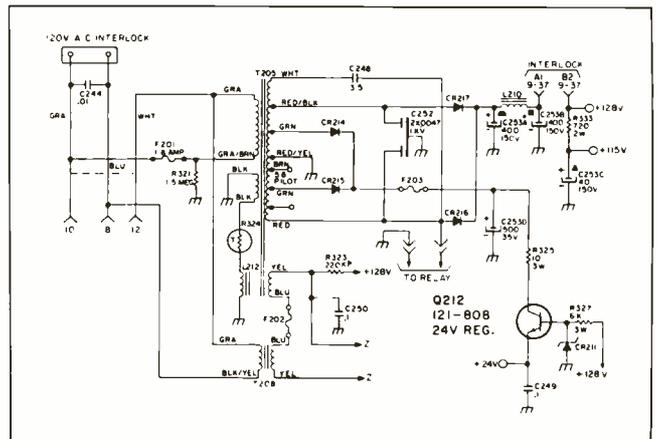


Fig. 10—Zenith 25DC56 power system.



Fig. 11—Slight picture bend due to shorted choke.

with heavy chokes and large capacitors are a thing of the past. Some regulated circuits may have a small 200 mfd filter capacitor; but without the solid-state electronic filter, a huge 10,000 μ F capacitor would be required to do a comparable job.

Shunt Regulator

A simple zener regulator circuit is shown in Fig. 16. It is called a shunt regulation system because the regulating device is in parallel with the load. Basic considerations for the shunt regulator circuit require that when no load is applied, the zener must pass the

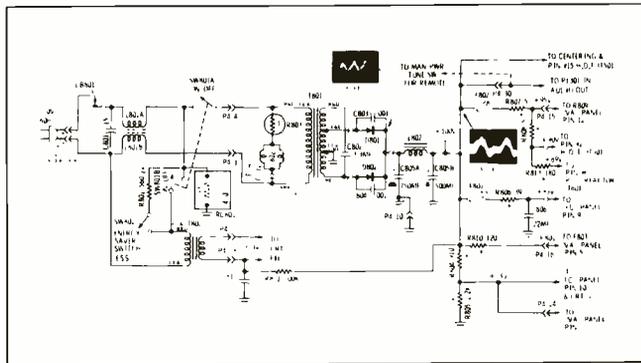


Fig. 12—Motorola TS-942 regulated power supply.

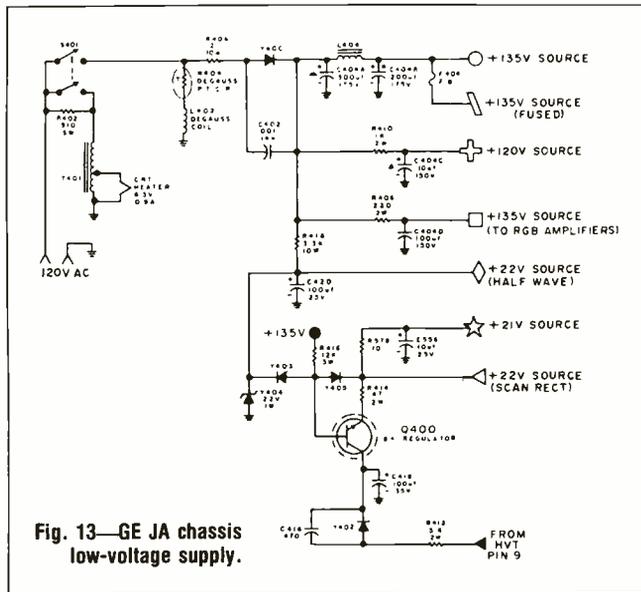


Fig. 13—GE JA chassis low-voltage supply.

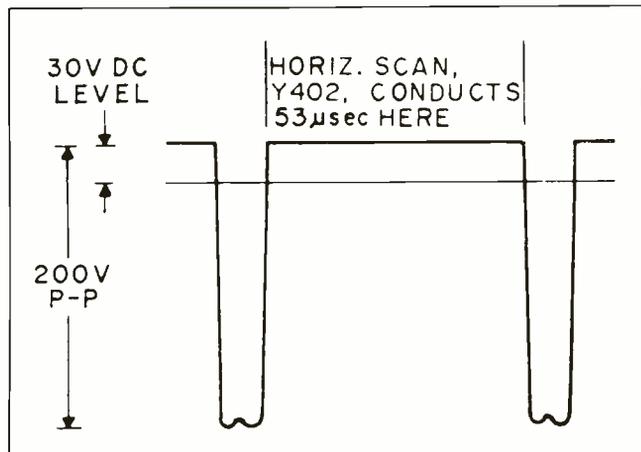


Fig. 14—Horizontal retrace pulses used in scan rectification.

amount of current the load would require, and also an additional amount of current that would keep the zener regulating when the load is applied.

This total amount of current is determined by the value of R_s . If the value of R_s increases, the available current to the load and zener would be less. The R_s resistance value must be small enough to maintain zener regulation during maximum current drain of the load. Shunt regulation is not very efficient because there is always current flowing through the zener that is of no value to circuit operation.

Series Regulator

A more efficient regulator system is the series-type zener regulator. A series regulator system (Fig. 17) requires a control device, such as power transistor Q212, to be in series with the load. The majority of the current flows through Q212. A change in current flow through the transistor will tend to cause a voltage change at the collector. Since the base is biased at a constant voltage by CR213, the change in potential from the base to the collector will affect the current flow through the transistor. This, in turn, automatically restores the emitter output voltage to +24V. Because the transistor is used as an emitter follower, the emitter will remain very close to the zener rating, provided the load does not draw excessive current. In this circuit the zener draws very little current. If a short occurs in the load circuit and heavy current is drawn, the transistor would be damaged if it were not for limiting resistor R322.





Darlington Regulator

One way of increasing current gain and maintaining voltage regulation is to use a Darlington circuit such as that shown in Fig. 18.

The advantage of a Darlington regulator is that a large amount of current can be handled with good voltage regulation. In the typical 125V regulator, more than 500 mA is the normal current flow. This means the current in the base circuit of the regulator driver will be near 0.5mA. To achieve a reasonable percentage of voltage regulation, the current through the zener should be at least twenty times greater, or 10 mA. Therefore, the wattage rating of the zener would have to be at least 3W. Because of several factors, in particular the temperature characteristics, a zener with a 0.5W rating is much more desirable than a 3W zener. A 0.6W zener has more temperature stability and a greater degree of built-in temperature compensation. In this configuration, the driver transistor operates in the same manner as the series regulator transistor. However, its emitter provides base bias for the regulator transistor, and this controls the current flow through the regulator transistor.

RECTIFIER SYSTEMS

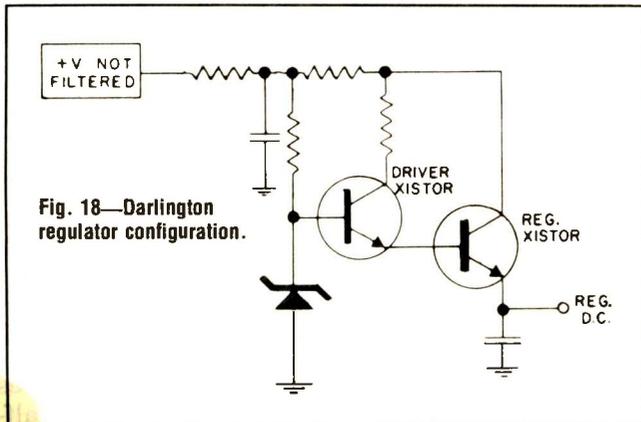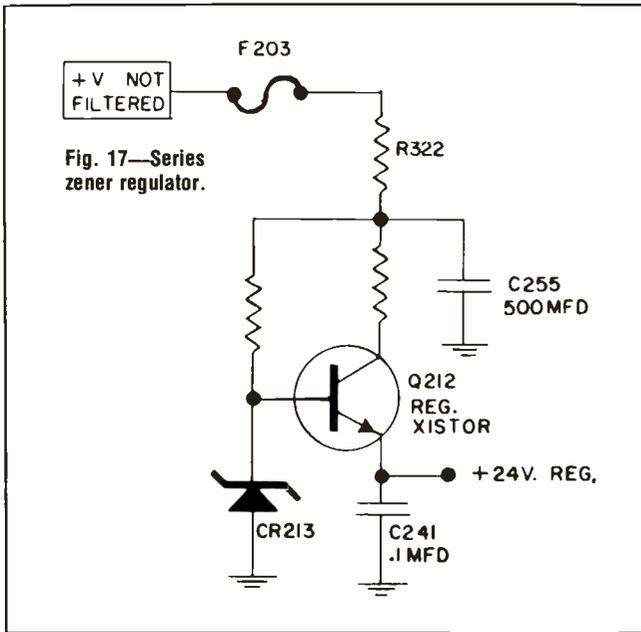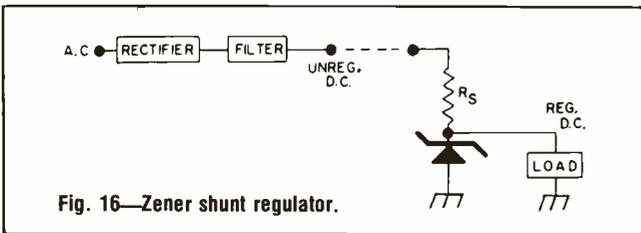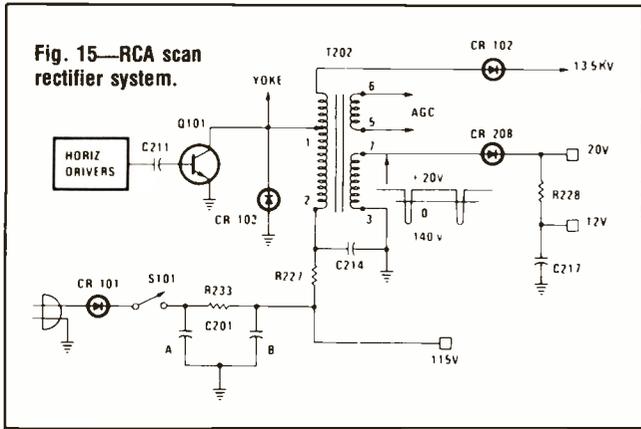The output frequency of a half-wave power supply is 60Hz. A smoother DC voltage can be obtained from a full-wave supply because its output frequency is 120Hz, so a smaller filter capacitor system is required. In Fig. 19, diode D1 conducts when the top of the secondary winding of T1 is positive. This provides a charge to filter capacitor C1. During the next half-



cycle, diode D1 is reverse biased and is cut off. At this same time, the bottom half of the secondary is positive, diode D2 conducts, and capacitor C1 is further charged. One diode will always conduct, regardless of the phase of the incoming AC.

The full-wave power supply has an output ripple frequency of 120 Hz because the output from the diodes occurs on each half-cycle of the incoming AC. The big advantage of a full-wave rectifier system is that the 120 Hz ripple is much easier to filter than the 60 Hz ripple.

If either diode shorts, a short will exist across the power transformer secondary and the fuse will blow. If the input filter capacitor C1 opens, the output DC voltage will be considerably lower, and a high ripple will be seen by a scope check of the B+ line.

Bridge

The full-wave bridge rectifier system is now found in most color TV receivers. The bridge circuit (Fig. 20) requires four diodes but does not need a center-tapped power transformer secondary. In this circuit, the chassis ground is the *negative* terminal, and it receives a *charge* on each half-cycle of the incoming AC. As the top lead of the transformer secondary goes positive, the bottom lead will be going negative. Thus, diodes D2 and D3 will conduct—D2 providing a negative charge to ground, and D3 providing a positive charge to the output circuit. During the next half-cycle, when the top lead of the secondary is negative and the bottom lead is positive, diode D1 conducts negative to ground, and diode D4 feeds a positive voltage into the output circuit. For each half-cycle of the AC input, the output line is positive.

Voltage Doubler

A full-wave voltage doubler circuit is shown in Fig. 21. The C2 capacitor has a different function than a filter capacitor. Operating with D1, C2 charges to the peak value of the applied AC voltage. The second rectifier, D2, charges C1, also to the peak value of the applied AC voltage. Since these two capacitors are connected in series, the voltage across both of them, from point W1 to ground, is equal to the sum of the individual voltages. The DC obtained is nearly two times the RMS value of the supplied AC voltage from the secondary of the transformer.

Some of the normal scope waveforms are shown with the circuit schematic. Because this is a full-wave circuit, the output will have a ripple frequency of 120 Hz. W2 should have an amplitude of less than 2V peak-to-peak, while W1 should be double that of W2.

POWER SUPPLY FILTER SYSTEM

A smooth DC voltage is required for nearly all electronic devices, especially those that use solid-state components. To develop this smooth DC voltage after the AC has been rectified, a filter choke (or a resistor) and filter capacitors are required. A power supply filter circuit is shown in Fig. 22. This is a *capacitive*-input pi circuit using two capacitors and a filter choke. The first capacitor filters the pulsating

THE CB SERVICE MONITOR BY MEASUREMENTS



MODEL CB 27E
\$495.00*

Low-cost, rugged, portable instrument for accurately checking, trouble shooting and aligning Citizens Band Transceivers operating in any of 40 Channels presently assigned.

- Phase-locked loop circuitry referenced to "AT" cut crystal.
- Monitor and transmitter are both protected against overloading if transmitter is accidentally keyed.
- Provision for adding future channels.
- Built-in transmitter power meter.
- Built-in speaker monitors transmitter frequencies down to zero-beat and provides on-the-air voice evaluation.

Write or call for additional information.

*F.O.B. Manchester, N.H.



McGRAW-EDISON COMPANY
Edison Electronics Division

Grenier Field Municipal Airport, Manchester, N.H. 03103
(603) 669-0940 • TWX 710-220-1747

...for more details circle 112 on Reader Service Card

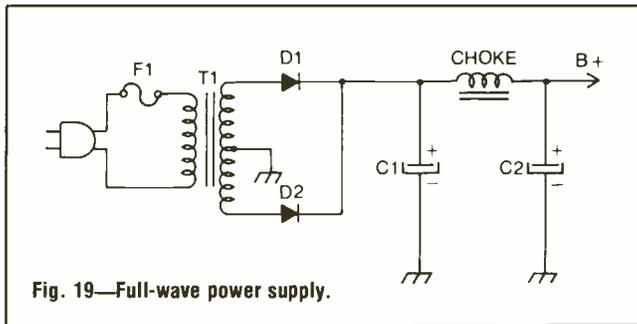


Fig. 19—Full-wave power supply.

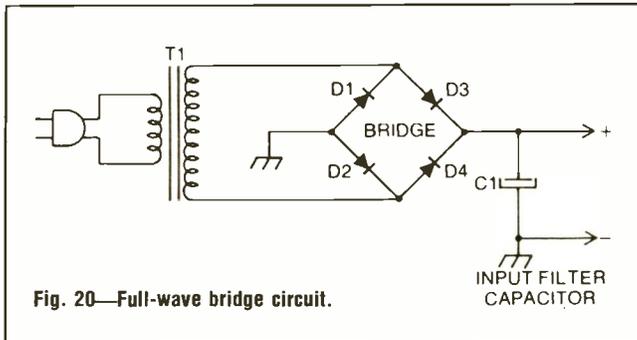


Fig. 20—Full-wave bridge circuit.

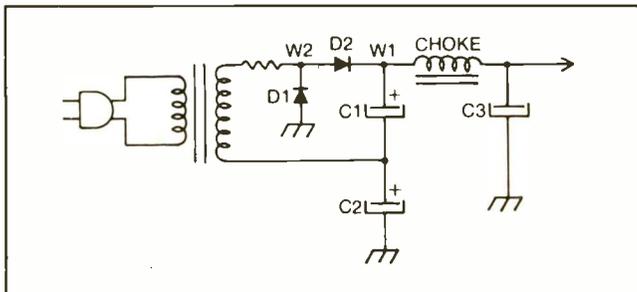


Fig. 21—Full-wave doubler circuit.

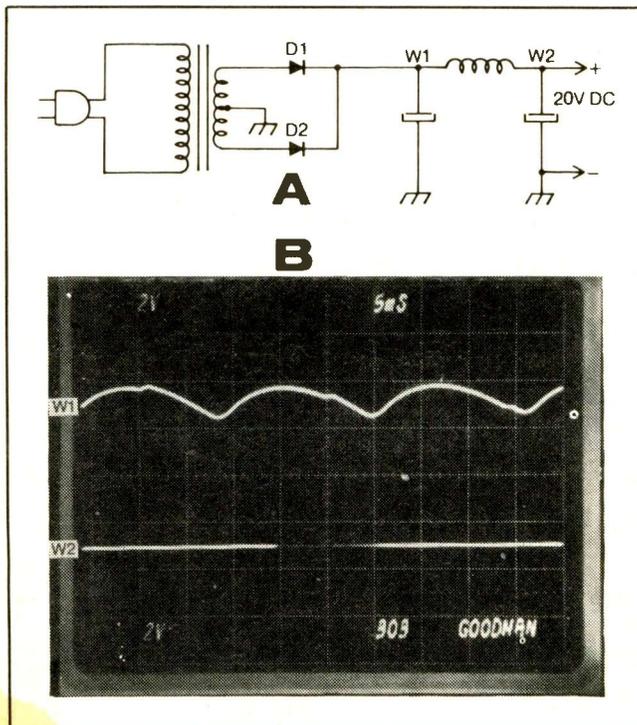


Fig. 22—Low voltage power supply with scope traces.

DC as it comes from the diodes. The choke opposes any change in current, resulting in a relatively smooth DC flow. The output capacitor further tends to keep the voltage constant. A resistor is occasionally used in place of the choke, but it has no filtering characteristics. The choke and filter capacitor values are chosen for a balanced system and efficient operation.

The dual-trace scope can be used to quickly check out the choke and filter capacitor circuits. The two probes from the dual-trace scope are connected to each side of the choke (input and output) at points W1 and W2, as shown in Fig. 22A. Under no-load conditions in a properly operating system, the display will be as shown in Fig. 22B. In Fig. 23 the choke has a 3 mfd capacitor across it. With the scope probes connected as shown, and a load applied to the power supply, the scope display in a good system will be as shown in Fig. 24. If either the choke or the capacitor across the choke is shorted, the waveforms on the dual-trace scope will be identical, as shown in Fig. 25.

A three-section filter system is shown in Fig. 26 along with the scope waveforms that should be found. The choke and capacitors are considered the primary filter circuits. Capacitor C1 refines the pulsating DC to a ripple of not more than 10%. Capacitor C2 and the choke reduce this ripple to about 4%. Capacitor C3 produces a relatively smooth DC voltage. Capacitor C3 also bypasses to ground any stray signals that may be picked up along the supply line. If C3 should open, the scope would display some ripple on the waveform.

TECH BOOK REVIEW

TITLE: *Troubleshooting With The Dual-Trace Scope* (TAB BOOK No. 772)

AUTHOR: Robert L. Goodman

PUBLISHED: 1976

SIZE: 224 pages, 252 illustrations

PRICE: \$5.95 softbound, \$8.95 hardbound

Veteran servicer Goodman's new book tells all about the dual-trace scope and its features, how to use the triggered and automatic-sweep modes, dual-alternate and dual-chopped sweep modes, and all the

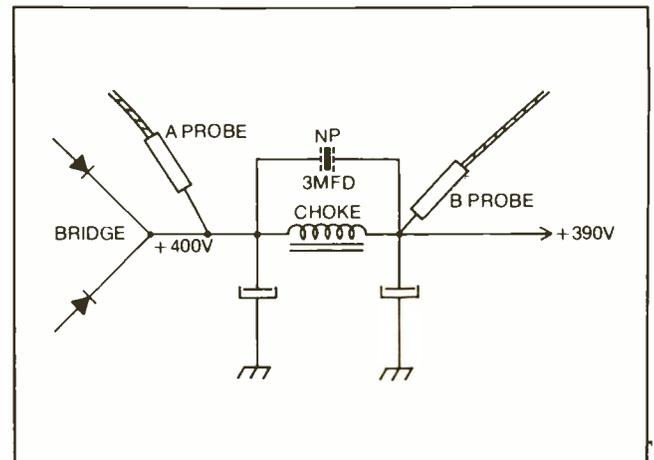


Fig. 23—Dual-trace connections for checking the filter system.

other features of these instruments. Each Chapter is packed with color TV troubleshooting tips, and how the dual-trace scope can be used to locate a whole host of problems, from one end of the receiver to the other. The first Chapter describes several of the various models of dual-trace scopes available; it lists features, and defines the specialized operation of these scopes and their application to color TV and hi-fi stereo system troubleshooting.

The author provides tips on locating the specific problem, tells how to use a dual-trace scope to trouble-track and fault-isolate in a quarter of the time required for single-sweepers. The reader will learn the most important specs to look for before buying a dual-trace scope, such as horizontal sweep speed, vertical amplifier frequency response, rise time, sensitivity, and all the other factors important in TV service work. Uses for the dual-trace scope are described in detail, such as stereo channel comparison testing, stage-gain measurements, comparison of pulse widths, checking countdown and frequency-divider circuits, time measurements in delay lines, timing checks, and many more applications.

A good part of this book deals with troubleshooting various sections of modern color TV receivers. The author takes the reader step by step through a variety of specific color TV modules to show how each troubleshooting sequence is performed. His systemized procedure can be applied to any make, any model, to cut troubleshooting time by 75%! Over 125 photos of actual scope traces illustrate both abnormal and normal waveforms. Circuits and circuit modules are carefully analyzed and explained. A multitude of typical problems are discussed, along with the procedures for isolating those problems to specific components. This is an invaluable guide for anyone who now owns, or is considering purchasing, a dual-trace scope.

CONTENTS: Introduction to the Dual-Trace Oscilloscope—Triggered-Sweep Scope Features—Waveform Observations—Convergence and Pin-cushion Circuit Troubleshooting—Horizontal AFC Circuit Analysis—Solid-State Push-Pull Vertical-Sweep System—Conventional Solid-State Sweep

Systems—Solid-State Horizontal-Sweep System Module Service Techniques—IF and Video Amplifier Systems—Troubleshooting the Chroma Circuits—Analyzing and Checking the Power Supply System—Vertical Internal Reference and Test Signals. ■

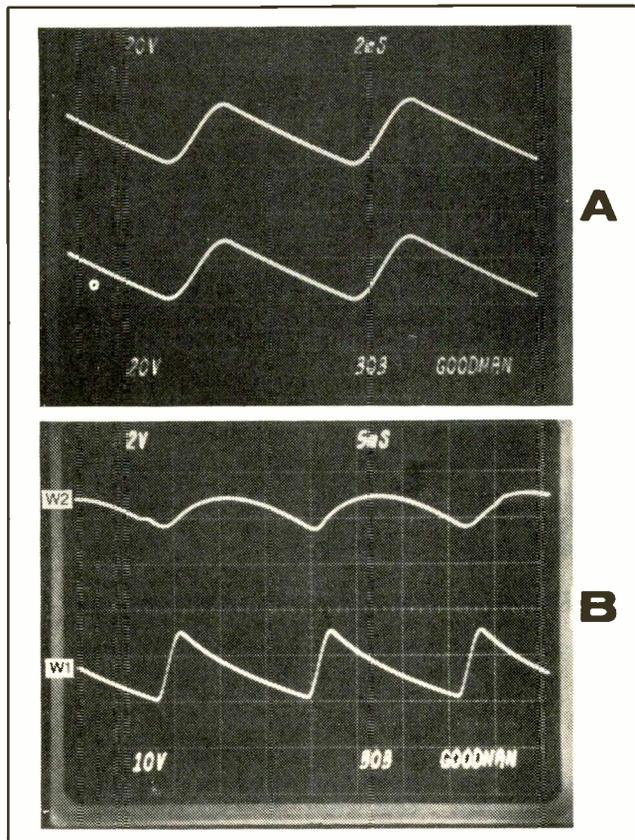


Fig. 25—Waveforms indicate a shorted choke.

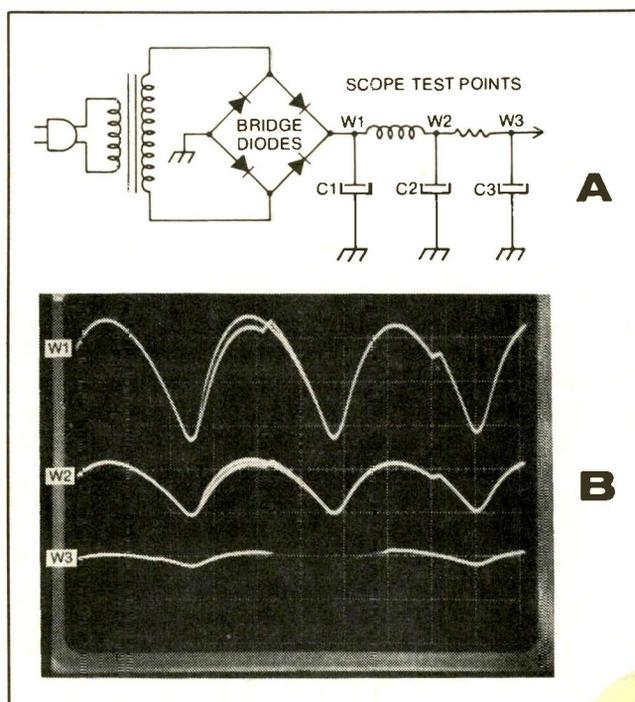


Fig. 26—Three-section filter system.

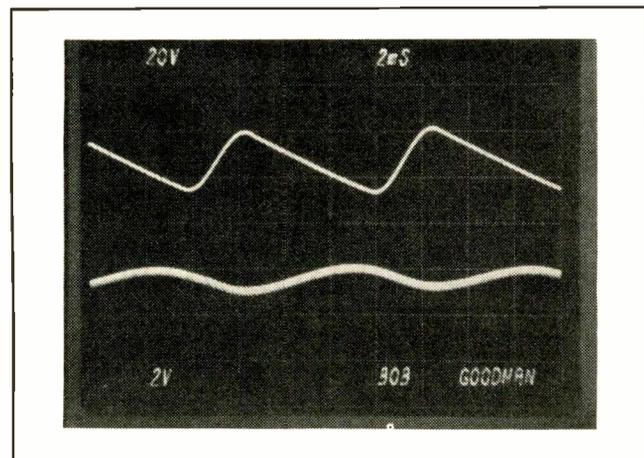


Fig. 24—Normal scope waveforms.

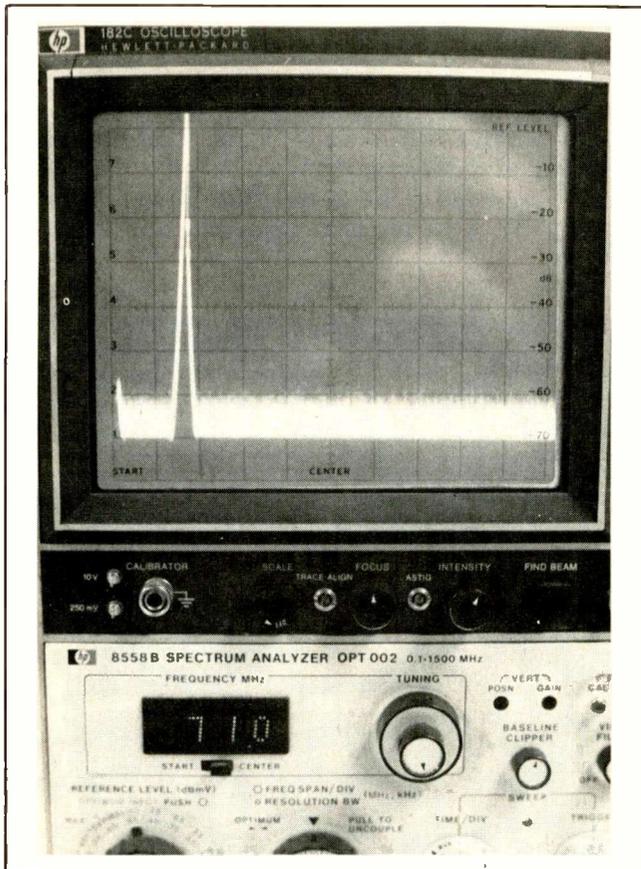


Fig. 1—The trace appearing on a spectrum analyzer shows white noise along the frequency base line. Broad-band noise appears like grass, as if one were looking at a cross-section of thick turf. On a TV picture tube, it appears as snow. From a loudspeaker, it is a frying noise.

Noise and Noise Figure

By James E. Kluge*

How the “noise figure” of an antenna system is determined and what it means to the TV picture quality

■ Noise Figure is the term of measurement that indicates how much noise is contributed by the transistors and/or tubes in the circuitry of an antenna pre-amplifier or other MATV amplifier. The Noise Figure rating is developed by comparing the device to be measured with a perfect—but non-existent—amplifier that would be able to amplify the input signal without adding any noise of its own.

Antenna Provides Input Signal

Let's start with the input signal, which is generally the voltage developed by the antenna as it intercepts the electromagnetic-wave energy in the air. Looking back 'into' a VHF antenna from its output terminals

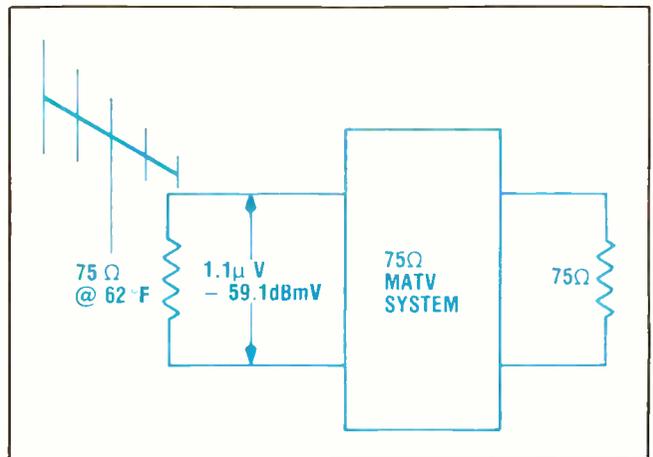


Fig. 2—Diagram of 75-ohm matched impedance MATV system showing that theoretical-minimum thermal-noise voltage is $1.1 \mu\text{V}/\text{ch}$ (-59.1 dBmV) at room temperature.

we see a 75-ohm device. The pre-amplifier input to which the antenna is to be connected also 'looks' like 75 ohms. When we connect the 75-ohm antenna to the 75-ohm input of the preamp, we say they are properly matched for maximum signal-energy transfer from antenna to preamp.

Now suppose that instead of connecting the antenna to the preamp input we simply connect a 75-ohm resistor to the preamp. The preamp doesn't know (and doesn't care) whether its input is terminated by a 75-ohm antenna or a 75-ohm resistor. Since the preamp has no eyes to see with, it doesn't know what's connected to its input, except that the device "feels" like a 75-ohm resistance, which "pleases" the preamp.

Resistors Are Noise Generators

Now, because the resistor is not an antenna, it cannot generate a TV signal voltage at the preamp input.

However, if we look at the voltage at the preamplifier output terminals with an oscilloscope or spectrum analyzer we will see what engineers and technicians commonly call "grass".

This "grass", which is seen at the bottom of the scope in Fig. 1, is comprised of millions of tiny sine waves of infinite frequencies all added together to create a uniform low-level signal across the entire frequency range. The technical name for this "grass" is *white noise*.

It is termed "white" because like white light, which consists of energy at all the frequencies of the visible spectrum, it is comprised of energy at all the frequencies of the RF spectrum.

Electron Motion Generates Noise Voltage

You might ask at this point "Where do all these voltages come from?" It is a phenomenon of nature that in any finite resistance (which includes most known materials) the rate of electron motion in the resistance is a function of the temperature of the material. For this reason, it is termed *thermal noise*. The higher the temperature, the faster the electrons move, and the higher is the white-noise energy and voltage across the resistance. By restricting the frequency bandwidth with such things as filters and measuring instruments we reduce the noise voltages

*The author is a technical editor for the Winegard Company

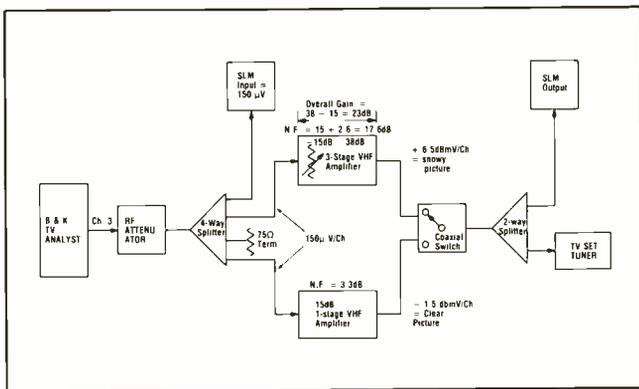


Fig. 3—An illustrated block diagram demonstration of noise-figure vs gain to show how high-gain amplifier with a poor noise figure causes picture-quality deterioration. The moral is: 1) don't try to distribute TV signals less than 1000 μ V (0 dBmV) and, 2) use an amplifier having maximum gain more equal to what is required rather than padding down the input of high-gain amplifiers, thus increasing their noise figure.

and thus eliminate the characteristic of white noise.

Mathematical Relationship For Thermal Noise

It may be of interest to know that there is a mathematical formula for the determination of thermal noise. The formula, or equation reveals that any increase in resistance, temperature or bandwidth causes a corresponding increase in the thermal-noise voltage across the resistance. The mathematical expression for this open-circuit voltage is: $E^2 = 4kRT(BW)$. Across a matched load impedance it is: $E^2 = kRT(BW)$. The values are as follows:

E^2 = mean value of the squares of all the individual noise voltages.

K = Boltzmann's constant, named after the physicist who developed this physical constant = 1.38×10^{-23} Joules/K.

R = resistance (in our case, 75-ohms).

T = temperature of the resistance material in Kelvins (generally considered $290K = 62^\circ F$ as standard).

BW = frequency bandwidth = 4.2 MHz for TV channels.

Shot-Effect Noise From Transistors

It is also important to mention at this point that up until now, we have been talking only about thermal noise which characterized itself as uniform snow throughout the TV picture or a constant hissing or frying noise from the speaker.

A second source of noise is the transistor. Bias current in transistor and diode junctions generate "shot-effect" noise as well as thermal noise in the base resistance.

Electromagnetic Noise


Other types of noise not generated in the amplifier are: 1) man-made electrical noise from brush-type motors, diathermy machines and auto ignition; 2) atmospheric noise from lightning, corona, and other electrical discharges in the atmosphere characterized by random momentary streaks in the picture or crackling in the speaker; 3) galactic noise (sun spots and solar-flare activity). All these "other" types of noise exist as electromagnetic energy which is generated outside of and picked up by the antenna along with the TV signal.

It's Bound to be a Profitable Deal for You...



MODEL 10043

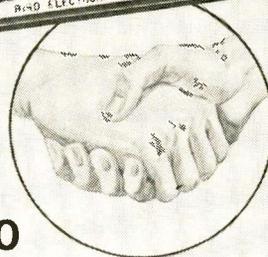...When these Two Great Pros reach an Agreement.



A Citizens Band (27 MHz) Antenna THRULINE® Wattmeter & SWR Bridge Manufactured Exclusively by Bird Electronic Corporation for Antenna, Incorporated.

"The Name of Quality"

Proven the best American made test meter for tuning all types of antennas, the THRULINE® Wattmeter is an extremely accurate instrument for continuous monitoring of RF power output and antenna SWR.

Model 10043 Wattmeter measures forward RF power up to 10 watts, reflected power to 2.5 watts as well as giving direct reading SWR of the antenna system — does not require a perfect (50 ohm) line impedance to provide accurate readings in either power or SWR modes — designed to be left permanently in the line for continuous monitoring or to be used as a highly accurate portable test instrument by dealers, servicemen, technicians or installers during initial installation and tune-up of CB systems.

Take it from the Pros — Model 10043 THRULINE® Wattmeter positively belongs in your stock of profitable CB accessories and is available only from Antenna, Incorporated. Suggested Resale Price is \$88.00.

Antenna Incorporated

Antenna, Incorporated
23850 Commerce Park Road, Cleveland, Ohio 44122
(216) 484-7075
In Canada: E.S. Gould Marketing Co., Ltd.
109 Montee De Lesse Montreal, Quebec H4T 1S9 Canada
Antenna, Incorporated, International Division
P.O. Box 1002 Rockville Centre, New York 11571

® Trade mark of Bird Electronic Corp.

...for more details circle 106 on Reader Service Card

Noise figure is concerned only with thermal and "shot-effect" noise generated in the amplifier's semiconductor devices and associated resistances. *The major contribution is from shot-noise.*

Minimum Antenna Noise

Noise voltage caused by thermal agitation of electronics in a 75-ohm antenna or terminating resistor is about $1.1 \mu\text{V}/\text{Ch}$, or -59.1 dBmV at room temperature, as illustrated in Fig. 2. At -25°F it drops to -60 dBmV ($1.0 \mu\text{V}$) and rises to -58.6 dBmV ($1.175 \mu\text{V}$) at $+140^\circ\text{F}$. So, for all practical purposes, we can consider the minimum noise voltage in round numbers as $1 \mu\text{V}/\text{Ch}$, or -60 dBmV across 75 ohms. This means that there will always be a theoretical, bare-minimum noise level of $1 \mu\text{V}/\text{Ch}$ of thermal noise measured anywhere in a 75-ohm system from the antenna to the TV set.

For this reason, the signal voltage generated by the antenna must be sufficiently higher than the noise (and maintained so throughout the system) to provide a snow-free picture at the TV set. A $100 \mu\text{V}$ (-20 dBmV) signal then provides only a 40-dB signal-to-noise ratio (S/N). This is a marginal signal level which does not provide for amplifier noise, fading and system losses. For this reason, we strive for a minimum $1,000 \mu\text{V}$ (0 dBmV or $\text{S/N} = 60 \text{ dB}$) signal level at the antenna and throughout the system until it reaches the TV-set tuner.

Noise Figure Degrades S/N

The noise figure of a good low-noise preamp is typi-



Fig. 4—Photo shows good picture quality resulting from a $150 \mu\text{V}$ (-16.5 dBmV) signal amplified through a single-stage 15-dB amplifier with a rated N.F. of 3.3 dB, which provides the tuner with an $840 \mu\text{V}$ (-1.5 dBmV) signal.

cally 4 to 5 dB at VHF and 7 to 8 dB at UHF. A $1,000 \mu\text{V}$ signal at the antenna has a S/N of 60 dB. A $100 \mu\text{V}$ signal at the antenna has a S/N of 40 dB. Running these signals through an antenna preamp having a 10 dB noise figure will reduce the S/N to 50 dB for the $1000 \mu\text{V}$ signal and 30 dB for the $100 \mu\text{V}$ signal. A S/N of 45 dB is considered an excellent picture with no snow, while a S/N of 30 dB is a marginal-quality picture with objectionable show.

Now, you can begin to see why noise figure in an antenna preamp is so important in a weak-signal area. The noise figure of a preamp will degrade the S/N by adding shot noise to the signal while it is

UNIVERSAL TV ANTENNA REPLACEMENT RODS
REPLACES MAJORITY OF ALL BUILT-IN ANTENNA RODS

PROG. NO. 49-458
(27" W x 19 1/4" H x 6 1/2" D)

COUNTER-TOP DISPLAY CONTAINS:

- 14 ANTENNA REPLACEMENT RODS-- 10 DIFFERENT MODELS
- 2 ROD ADAPTORS
- 5 REPLACEMENT GUIDES
- 1 PRECISION CUTTING TOOL

we've got you covered!

Handle 90% or more of all TV antenna rod replacements with a minimum of stock! Antenna Replacement Rod Program No. 49-458 features 10 different rods with exclusive adaptor to fit 7mm and 8mm diameter rods, and precision cutting tool. Also included is a pocket-sized TV Antenna Rod Replacement Guide and Cross Reference.

PRECISION CUTTING TOOL
Cuts broken antenna fast and easily.

TV ANTENNA ROD REPLACEMENT GUIDE & CROSS REFERENCE
Quick cross reference and replacement method guide for all popular TV antenna rods. 3-5/8" x 8" - fits in your pocket!

GC ELECTRONICS
DIVISION OF HYDROMETALS, INC.
ROCKFORD, ILLINOIS 61101 U.S.A.

CONTACT YOUR GC DISTRIBUTOR TODAY!

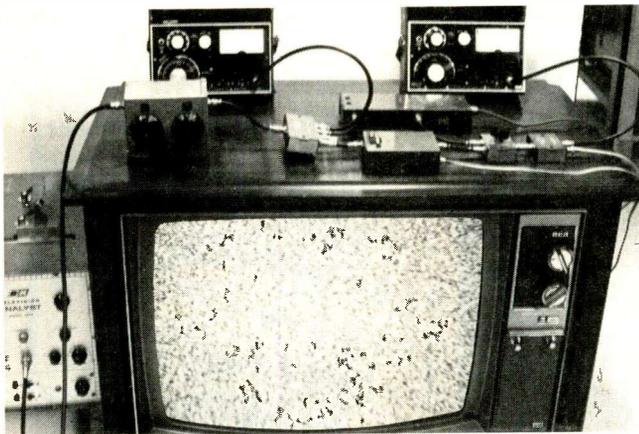


Fig. 5—Photo of a snowy picture resulting from using an amplifier with excessive gain (38 dB) and N.F. rating of 2.6 dB. Input gain control was turned down 15 dB, amplifying the 150 μ V input signal 23 dB (or 14 times) to provide the tuner with a 2100 μ V (+6.5 dBmV) signal.

undergoing amplification in the transistors. However, if the S/N at the input is excellent (i.e., 45 dB or higher), a good quiet preamp will have little effect on picture quality.

It should also be understood that the antenna preamp will establish the maximum S/N for the entire system. That is, *the S/N coming out of the preamp can not be improved*—that's it! The most important thing you can do is to *preserve* it.

Any passive (non-amplifying) device causing attenuation or loss in the system is considered to have a noise figure in dB equal to that loss in dB. For example, a 6-dB pad can be considered to have a noise-figure of 6 dB. This is so because it attenuates the signal 6 dB, thereby reducing the S/N by 6 dB. For example, a 6 dB pad ahead of a preamp with a 6 dB noise figure yields an overall noise figure of 12dB. This is why it is so important to amplify a weak antenna signal *before* it experiences any attenuation caused by pads, cable, connectors or a mismatch of impedances.

If you have a weak signal, it is best to amplify it up to 0 dBmV with an amplifier having as low a noise figure as possible. In order to preserve the low noise figure of the amplifier there should be a very minimum of loss between the signal source and the input amplifier. If the amplifier has too much gain, pad down the amplified signal *after* the amplifier—not ahead of it. Better yet, choose a smaller amplifier having the right amount of gain. Some distribution amplifiers have a variable gain control that can be used to increase their input-signal handling capability at the input. Attenuating the input signal this way is acceptable in the case of strong or high-level signals, but not for weak ones.

Antennas Considered Noiseless

All antennas are considered to be noiseless and lossless, or, in other words, their noise figure (NF) is 0 dB. They do not attenuate or amplify voltages. The more signal you can get from the antenna, the better your TV picture will be. In contrast to a preamp, a larger antenna will increase the signal without increasing the noise.

Measuring Noise Figure

Noise generated in the transistors and/or tubes of

an amplifier appears throughout the various stages and will appear as a single combined noise voltage in the output load. It is accepted practice to refer this noise voltage (or power) back to the input by dividing it by the overall gain of the amplifier. Normally, we refer to noise in terms of power, but in a 75-ohm MATV system we can treat it and measure it as a *voltage* across a 75-ohm matched-load resistance.

Noise figure is measured by terminating the amplifier *input* with 75 ohms and measuring the noise power across a 75-ohm output load. Then a 3-dB matched attenuator is inserted ahead of the load and a 75-ohm calibrated noise generator is connected to the input in place of the terminating resistor. The noise-generator output signal then is increased until the original noise-power reading is obtained in the output load. The noise-generator output then is equal to the noise figure of the amplifier.

This measurement must be made in a shielded enclosure (screen room) so that the noise power reading is the noise generated in the amplifier, and from the calibrated noise generator only—not from direct pickup of extraneous signals and/or noise.

Tuner N.F. Notoriously Poor

TV-set tuners should also be an important consideration regarding picture quality. They are notorious for having poor noise figures (e.g. 15 dB). Therefore, it is important that they be fed at least 100 μ V/ch, so that the signal-to-noise ratio at the TV set antenna terminals will be 55 dB or better, for a snow-free picture.

Almost every TV set has a lossy balun between the 300-ohm antenna terminals and the 75-ohm input of the tuner. To make things worse, a 75-ohm coax downlead requires an external balun before connecting to the receiver's 300-ohm antenna input terminals.

For this reason, it is desirable to provide a 75-ohm connector at the rear of the set, and then use a short length of coax to connect it directly to the tuner input. This method not only eliminates the loss in two back-to-back baluns which results in degradation of tuner noise figure but also frequently eliminates leading ghosts caused by direct signal pickup in the short, unshielded 300-ohm line between the antenna connections of the set and the TV tuner.

Summary

Let's summarize the important points made in this article:

- * Noise figure indicates the relative amount of noise added by the amplifying devices (i.e., tube or transistors) in an amplifier.
- * Noise-figure contribution is mainly shot noise from tubes and transistors.
- * The S/N ratio of the signal applied to the receiver's antenna input terminals cannot be improved by the receiver circuitry.
- * Use a preamp to compensate for losses in the downlead, splitters, couplers, etc. between the antenna and next amplifier in the system, which in many cases will be the tuner in the TV set.
- * Because of poor noise figure of most tuners it is important that you have at least 1000 μ V of signal at the TV set to achieve a clean picture. ■

Intro to Defibrillator Servicing

By Joseph J. Carr, C.E.T.

A look at another source of business and profit for electronic technicians

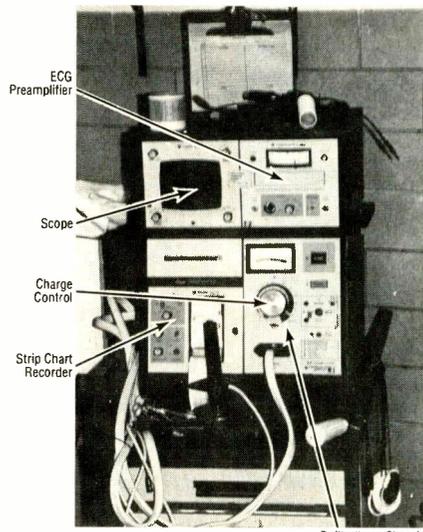


Fig. 1—A typical defibrillator resuscitation cart.

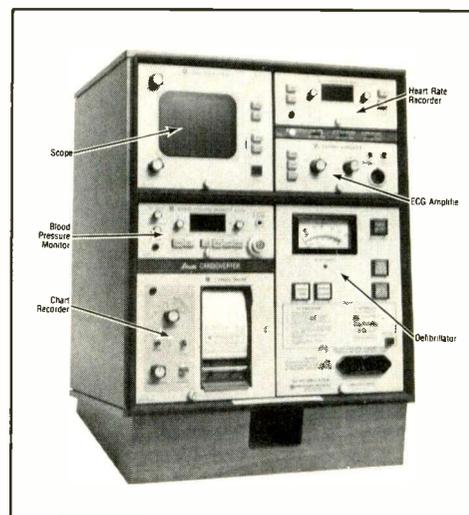


Fig. 2—A bedside defibrillator and monitoring package. (courtesy of American Optical)

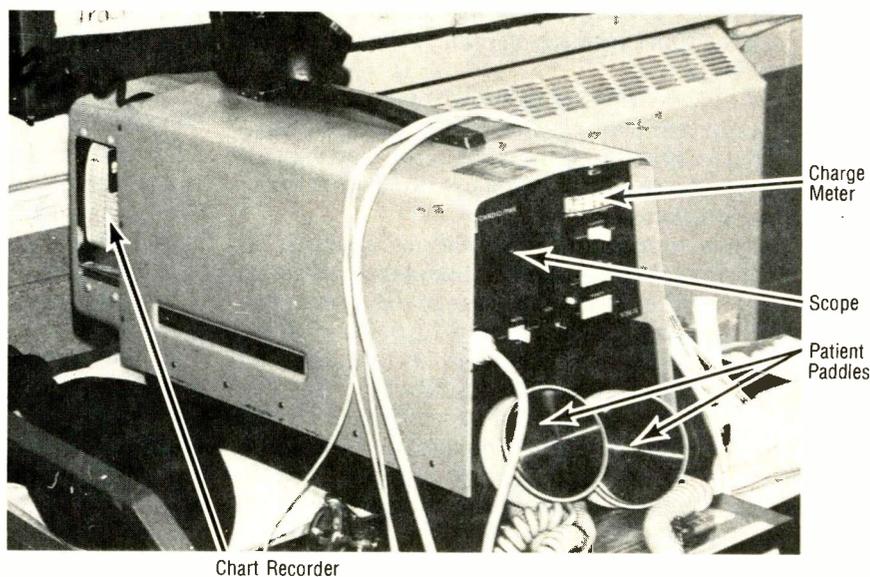


Fig. 3—A battery-operated portable defibrillator.

■ Defibrillators are a relatively simple medical instrument and are amenable to servicing by local, independent technicians and service firms. The simplicity of most such instruments and the speed with which they must be serviced makes it more attractive for a hospital to have a local independent electronics servicer handle these instruments, rather than the somewhat slower factory or authorized factory service contractor.

Defibrillators are used to shock a heart attack victim's heart so that normal rhythm can be restored. The electrical charge is stored in a capacitor, which is connected across the patient paddle electrodes and is delivered to the patient when the operator presses a discharge switch located either on the front panel or the paddle

assembly itself.

The name 'defibrillator' is derived from the particular fatal cardiac arrhythmia the instrument is designed to correct—ventricular fibrillation, a condition in which the patient's heart is quivering rather than beating, and where contractions are too shallow to produce effective blood pumping action.

Typical Defibrillators

Figures 1, 2, and 3 show several typical defibrillators as might be found in a typical hospital. Fig. 1 shows a resuscitation cart. Storage cabinet drawers in the lower section are used for keeping drugs and supplies needed during the emergency. The actual defibrillator chassis is the unit in the lower right hand corner of the upper section. Next to the defibril-

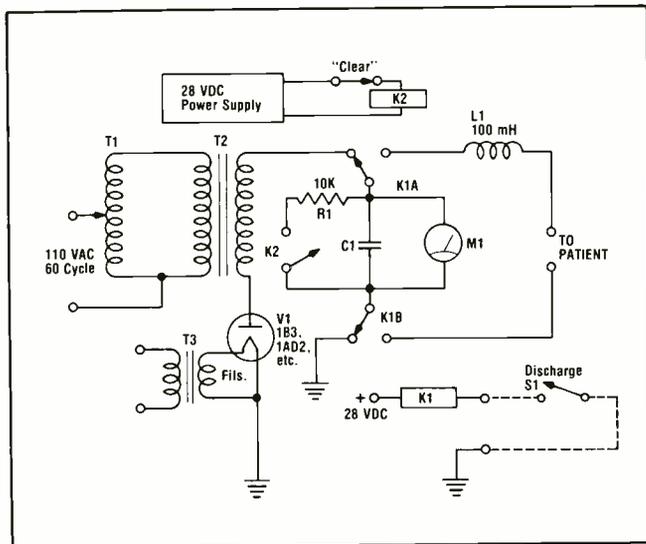


Fig. 4—A simplified schematic of a typical defibrillator.

lator chassis is a strip chart recorder which is used to draw a permanent record of the patient's ECG waveform on a piece of thermally sensitive graph paper. In the upper right hand corner we see an ECG preamplifier chassis. A patient cable attached to electrodes on the victim's chest or limbs acquires the tiny ECG voltages which are processed by this amplifier.

The oscilloscope is a special medical type which is very much like any other scope except that the CRT uses a special long persistence phosphor such as the P7. The input to this oscilloscope is connected in parallel with the input to the strip chart recorder.

The size of the charge to be stored in the capacitor is determined by the charge control knob on the front panel and is read from the calibrated panel meter. Fig. 2 shows a similar instrument but of more recent vintage. The charge control knob in this later instrument has been replaced by pushbutton switches.

The model in Fig. 3 is a battery operated portable. This model uses the defibrillator paddles to also acquire the patient's ECG signal which saves time over the method of using a separate patient ECG cable.

Portables have become much publicized in recent years by TV shows such as "Emergency" and the proliferation of rescue squad paramedic teams. The portables are also popular in smaller hospitals where one instrument must be used to serve several areas of the building and must be hand carried

to the location of the emergency.

Defibrillator Circuitry

A simplified defibrillator circuit is shown in Fig. 4. The main charge is stored in capacitor C1, which is usually a 16 μ f, high voltage, oil-filled capacitor. Relay K1 is a high voltage, vacuum type of relay such as the Torr model TMR10. When the defibrillator is turned on, relay K1 connects the capacitor across the high voltage DC power supply for charging. Then, when the "discharge" button is pressed, the energized relay coil connects the capacitor across the output circuit consisting of a 100mH choke coil, L1, and the patient's body resistance which has about 50 ohms nominal value.

Relay K2, as a safety feature, clears the capacitor charge when the machine is turned off, or when the operator presses a special "clear charge" switch (S2). The relay connects a 10k/50 watt bleeder resistor, R1, across the capacitor for a safe discharge. Some technicians who work on defibrillators carry with them a bleeder resistor with well-insulated alligator clip leads in case they find an open bleeder resistor on the instrument itself.

The high voltage DC power supply circuit consists of variac T1, high voltage transformer T2 and a rectifier, V1. The rectifier in many older instruments will be a TV-type, such as the 1B3 or 1AD2, while in more modern instruments it will be a solid-state diode stack not unlike some of those seen in TV chassis. The variac in this case is mounted to the front panel

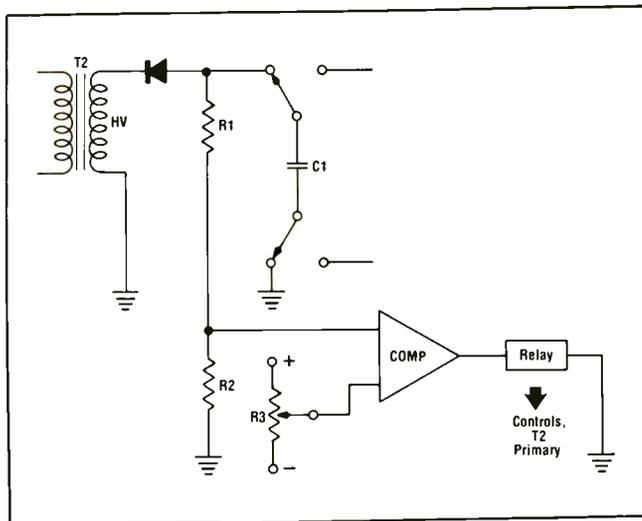


Fig. 5—A simplified schematic of the automatic charge control circuit in a defibrillator.

and is the "charge" knob from Fig. 1.

The meter in the circuit, M1, is actually a kilovoltmeter, but the face is calibrated in watt-seconds or joules ($1j = 1w-s$).

A partial schematic of another type of defibrillator control circuit is shown in Fig. 5. In this case, a comparator circuit, which might be an IC such as the LM311 or discrete components, is used to compare a sample of the capacitor voltage obtained from voltage divider R1/R2 to a reference voltage from potentiometer R3. When the two voltages are equal the comparator output goes high and turns off the AC primary voltage applied to transformer T2. Potentiometer R3 is mounted to the front panel and replaces the variac as the charge control.

The inner works of the AO defibrillator in Fig. 1 are shown in Fig. 6, to give you an idea of the size of the main capacitor. *Make no mistake about it—that capacitor stores a potentially LETHAL charge!* Always work on these instruments using good high voltage technique just as if you were working on a high power radio transmitter, or other similar device.

Testing Defibrillators

Several techniques can be used to check defibrillator performance. The simplest method is to use a kilovoltmeter to measure the voltage across the capacitor at full charge. This voltage level is computed from: $E = \frac{2S}{C}$. S is the stored charge in watt-seconds (joules) and C is the capacitance in farads. For a 16 μ f capacitor

MEET OUR FAMILY of GRABBERS



MODEL 4233 MICRO GRABBER
Tests high density packaging



MODEL 3925 MINI GRABBER
Tests conventional packaging



MODEL 4011 THREADED GRABBER
Accepts 6-32 threaded leads



MODELS 3780 - 3789 GRABBER LEADS
10 choices of connectors other end

Our Grabber family is five years old now, and we're adding new members to keep pace with the complexities of state-of-the-art electronic packaging. Grabber is our name for a series of test clips designed to simplify testing of electronic packages from conventional components to maximum density DIP's. They're rugged, dependable, versatile, and very easy to use. Write for our catalog and get the complete story on the whole family of Grabbers. Find out why they are your best solution to your electronic testing problems.

**AVAILABLE THROUGH YOUR
FAVORITE ELECTRONIC
PARTS DISTRIBUTOR**

MODEL 4225 MAXI GRABBER
Tests high rise packaging

All Grabbers shown actual size

ITT POMONA ELECTRONICS

1500 East Ninth St., Pomona, Calif. 91766
Telephone (714) 623-3463, TWX: 910-581-3822

...for more details circle 121 on Reader Service Card



charged to 400 watt-seconds the value of E will be 7.07 Kv.

There are two serious limitations to this first test method, however. One is the uncertainty of errors in the typical low-cost kilovoltmeter and the other is the fact that *static* testing of high voltage devices is not nearly as good as *dynamic* testing. Many components test out all right under static conditions but fail badly in actual operation.

A better way to test these instruments is to use a dynamic defibrillator tester. One of the testers available uses a 50 ohm dummy load to absorb the power, and it contains an integrating voltmeter to compute the deliv-

continued on page 47



PC Board Capacitor
Fig. 6—The inner works of the defibrillator shown in Fig. 1, to illustrate the relative size of the capacitor.

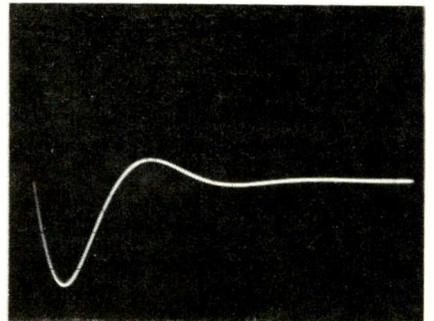


Fig. 7—A typical waveform taken across a 50 ohm dummy load in a properly operating defibrillator.

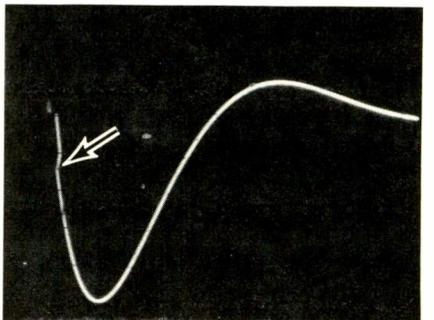


Fig. 8—This is an expanded scope display of the left portion of the waveform in Fig. 7. Arrow points to the "glitch" caused by a defective HV relay.

Scope That Power Supply

By Joseph J. Carr, C.E.T.

How to use the oscilloscope for fast, accurate diagnosis of power supply troubles.

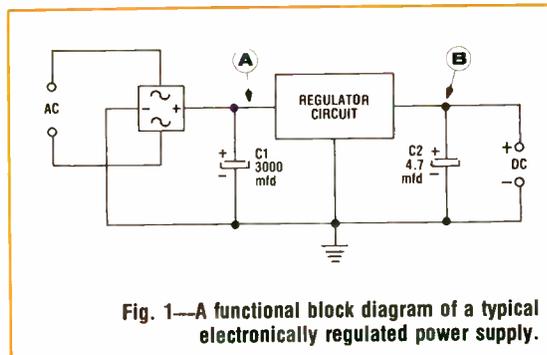


Fig. 1—A functional block diagram of a typical electronically regulated power supply.

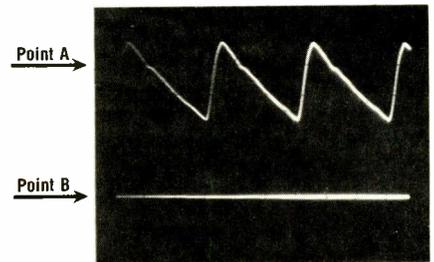


Fig. 2—Waveforms produced by the power supply circuit shown in Fig. 1. (A) shows the ripple present at point A in Fig. 1. (B) shows the waveform at point B in Fig. 1, after regulation.

■ Let me pose a question to you. How often do you examine the output of a power supply circuit with an oscilloscope? If you're like many servicers (myself included), the answer is probably "not often enough." Most of us tend to take the power supply for granted. If it's producing DC, we look elsewhere for the trouble. The truth of the matter is, examining the DC voltage with a scope—and *knowing what to look for*—can lead to the solution of many "tough dog" problems.

A lot of modern electronic equipment is operated from internal regulated power supplies. One feature of such power supplies is that almost all of the AC ripple normally encountered in rectifier circuits is suppressed by the regulator. Fig. 1 shows a functional block diagram of an electronically regulated supply. The waveforms to be found at points A and B are shown in Fig. 2. (The vertical amplifiers in the dual-trace oscilloscope have been adjusted to have the same sensitivity so that the relative amplitudes of two voltages can be compared.)

The top waveform in Fig. 2 shows the ripple present at point A in Fig. 1. This point is at the output of the rectifier bridge and be-

fore the regulator circuit. The lower waveform shows the ripple present at point B, after regulation. Note that, on the same voltage scale, this waveform appears very nearly pure DC. To be sure, if we amplified the lower trace quite a bit we would be able to see plenty of ripple. It is, though, so low as to be almost ineffectual in most circuits.

If the regulator circuit were to become inoperative because of a shorted series pass transistor, we would find the high ripple component on *both* the A and the B waveform. Also, the DC voltage at point B would be excessive. To the TV servicer this would cause, at the least, a heavy 120 Hz hum bar in the picture, plus whatever other symptoms that might accompany high ripple and excessive DC supply voltages. To the industrial, medical, test equipment, digital or communications servicer these problems might produce any number of unusual symptoms.

We should also be interested in what happens in the DC power supply at the instant of turn-on. This is a dynamic time in many electronic circuits, and may be the root cause of many difficult-to-find problems. Fig. 3 shows the normal rising waveform of a positive

An Extraordinary Offer

to introduce you to the benefits of Membership in
ELECTRONICS BOOK CLUB
for a limited time only you can obtain

**THIS
GIANT
434-Page**

Color TV Trouble Factbook for only

49¢
WITH
TRIAL
MEMBER-
SHIP

May we send you this helpful new book as described on the facing page as part of an unusual offer of a Trial Membership in Electronics Book Club?

This is a quality hardbound volume, especially designed to help you increase your know-how, earning power, and enjoyment of electronics.

This handsome, hardbound book is indicative of the many other fine offerings made to Members . . . important books to read and keep . . . volumes with *your* specialized interests in mind.

Whatever your interest in electronics—radio and TV servicing, audio and hi-fi, industrial electronics, communications, engineering—you will find Electronics Book Club will help you.

With the Club providing you with top quality books, you may broaden your knowledge and skills to build your income and increase your understanding of electronics, too.

How You Profit from Club Membership

This special offer is just a sample of the help and generous savings the Club offers you. For here is a Club devoted exclusively to seeking out only those titles of direct interest to you. Membership in the Club offers you several advantages.

1. **Charter Bonus:** Take "COLOR TV TROUBLE FACTBOOK" . . . publisher's list price \$9.95 . . . for only 49¢ with your Trial Membership.

2. **Guaranteed Savings:** The Club guarantees to save you 15% to 75% on all books offered. All books are offered at low Member prices (plus a small shipping charge).

3. **Continuing Bonus:** If you continue after this trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates, plus payment of the nominal sum of \$1.99, will entitle you to a valuable Book Dividend which you may choose from a special list provided members.

4. **Wide Selection:** Members are annually offered over 50 authoritative, new books on all phases of electronics.

5. **Bonus Books:** If you continue in the Club after fulfilling your Trial Membership, you will receive a Bonus Dividend Certificate with each additional Club Selection you purchase. For the small charge of only \$1.99, plus three (3) Certificates, you may select a book of your choice from a special list of quality books periodically sent to Members.

6. **Prevents You from Missing New Books:** The Club's FREE *News* gives you advance notice of important new books . . . books vital to your continued advancement.

This extraordinary offer is intended to prove to you, through your own experience, that these very real advantages can be yours . . . that it is possible to keep up with the literature published in your areas of interest . . . and to save substantially while so doing.

How the Club Works

Forthcoming selections are described in the FREE *Club News*, published thirteen times a year. Thus, you are among the first to know about, and to own if you desire, significant new books. You choose only the main or alternate selection you want (or advise if you wish no book at all) by means of a handy form and return envelope enclosed with the *News*. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway . . . without the substantial savings offered through Club Membership.

Limited Time Offer!

Here, then, is an interesting opportunity to enroll on a trial basis . . . to prove to yourself, in a short time, the advantages of belonging to Electronics Book Club. We urge you, if this unique offer is appealing, to act promptly, for we've reserved only a limited number of books for new Members.

To start your Membership on these attractive terms, simply fill out and

mail the postage-paid airmail card today. You will receive "COLOR TV TROUBLE FACTBOOK" for 10-day inspection.

SEND NO MONEY! If you are not delighted, return it within 10 days and your Trial Membership will be cancelled without cost or obligation. Electronics Book Club, Blue Ridge Summit, Pa. 17214.

Typical Savings Offered Club Members on Recent Selections


Master Tube Substitution Handbook	List Price \$8.95; Club Price \$3.95
Transistor Ignition Systems	List Price \$8.95; Club Price \$5.95
Master Transistor Substitution Handbook	List Price \$11.95; Club Price \$5.95
Practical Solid-State DC Power Supplies	List Price \$9.95; Club Price \$6.95
106 Easy Elec. Proj./Beyond the Transistor	List Price \$8.95; Club Price \$5.95
Understanding/Using Mod. Signal Gen.	List Price \$9.95; Club Price \$4.95
Understanding/Using Mod. Elec. Svcg. Test Equip.	List Price \$8.95; Club Price \$4.95
Photo/Symptom Guide/Solid-State Color TV Tbls.	List Price \$8.95; Club Price \$4.95
CET License Handbook	List Price \$12.95; Club Price \$7.95
Master Hdbk. Digital Logic Applications	List Price \$11.95; Club Price \$7.95
CBer's Handybook of Simple Hobby Pjts.	List Price \$6.95; Club Price \$3.95
CB Radio Schematic/Service Manual #4	List Price \$8.95; Club Price \$4.95
Modern Electronics Math	List Price \$12.95; Club Price \$8.95
Modern Guide to Digital Logic	List Price \$9.95; Club Price \$5.95
Impedance	List Price \$8.95; Club Price \$5.95
Build Your Own Working Robot	List Price \$8.95; Club Price \$5.95
TV Schematics: Read Between the Lines	List Price \$8.95; Club Price \$4.95
Tblshg. with the Dual-Trace Scope	List Price \$8.95; Club Price \$4.95
Switching Regulators & Power Supplies	List Price \$9.95; Club Price \$5.95
OP AMP Circuit Design & Applications	List Price \$9.95; Club Price \$5.95
Build-It Book/Min. Test/Msrmt. Instr.	List Price \$7.95; Club Price \$4.95
Electronic Conversions, Symbols/Formulas	List Price \$8.95; Club Price \$4.95
Microprocessor/Microprogramming Hdbk.	List Price \$9.95; Club Price \$5.95
Digital/Logic Electronics Handbook	List Price \$9.95; Club Price \$6.95
Master Hdbk. 1001 Pract. Elec. Circuits.	List Price \$12.95; Club Price \$7.95

SEND NO MONEY! Simply fill in and mail postage-paid Airmail card today!

COLOR TV TROUBLE FACTBOOK—

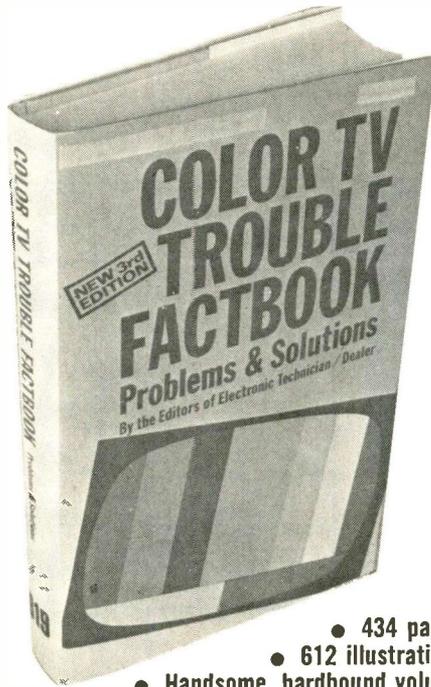Problems & Solutions

The most comprehensive single "all-makes" guide to color TV troubles and solutions ever published . . . NEW, completely revised and enlarged by over 30%, 3rd Edition!



- 434 pages
- 612 illustrations
- Handsome, hardbound volume

Partial List of Contents

Admiral—Chassis G11/G13/H12/K15, G13 and H12, K10, 4H12, 11A9N/53776AN, H10-H12, 4K10, G11/G13/H10/H12/K15, G11/G13, 14H12, K20, K16, K16/K17/K18/K20, 12K20, G11, M20, K18, K19/K18/K19, M10, 1M30B, 3M20/3K19/T41K10, M24/M25/M30, T15K10/16K10, 3K19, 5L5851/5L5853/5L5855. **Canadian General Electric**—Chassis M663, M678, M678/M679. **Dumont**—Chassis 120957/958. **Emerson**—Chassis K20, K17/K18, M20. **General Electric**—Chassis CB, C1, G1, H, H1, H3, KC & CB, KC-KD, KE, P, N1, N2, C1/L1, U1, JA, C1/L1 & C2/L2, MA, C2/CD, L2/LB, HE, C, XA, MC, MB-75, 19QB. **Magnavox**—Chassis T904 & 45, T911/T918/T920/T931, T919, T924, T931/T933/T38, T940, T924/T939, T936, T935, T936/T939/T940, T939 & T940, T931/T933/T940, T947, T924/939/950, T951, T950 with 704059, T931/T933, T936/T950/T951/T952, T958/T962, early T950/T951, T958 with 704065 remote, T938, T918, T946, T962-10, T974/T936/T956/T957, T979, T939, T936/956/957, T958 and T974, T979, T979/989, T989, T960, T985/T986, T966, T998, T981/T982/T987, T995, TS934. **MGA**—Chassis T50, CH160, CH-190, CH191. **Motorola**—Chassis TS908, TS914/918, TS915, TS918, T921, TS924, TS929/931/938, early 16 and 18TS929, TS934. **Olympic**—Chassis CTC19/20/21, CTC19/21, CTC19/21/31, CT910, CT911, CTC20/30, CTC30. **Philco**—Chassis 16M91, QT85. **Philco-Ford**—Chassis 14M91/15M-91/15M91, 17MT80A/18QT86, 18QT85/18MT70, 16QT85 & 16NT82, 20KT40/20KT41, 20QT88/20QT, 3CS90/91/3CY90/91, 3CS90/3CS91/3CY90—3CY91, 3CS90/3CY90, 22QT80/21KT40/21KT41, 4CS73/4CY91. **RCA**—Chassis 1966 Color, CTC17/17X, CTC20, CTC21, CTC30, CTC36, CTC-38, CTC40, CTC52/43/44/47, CTC40/44/47, CTC38/39, KRK170, CTC44/47, CTC46, CTC55, CTC51, CTC50, CTC22/41/42, CTC-44/46/47/49/54, CTC54, CTC52, CTC59, CTC63, CTC46/54/59, CTC48, XL-100. **Setchell-Carlson**. **Sylvania**—Chassis D-01 and D02, D02/D10, D06, D06/D07/D08/D10, D12, D14, D12-09-09/D12-15-07, D12-21-50/D12-11-06, D12-20-50, D14, D15, and D16, E02-1, 2, E04, E08. **Truetone**—Chassis 2DC4815. **Westinghouse**—Chassis V2655, V8001, V2655/V2656. **Zenith**—Chassis 20X138, 14A9C51, 12A13C52, 25DC57, 19DC12/22/28, 17/19-EC45, 25FC45.


Here it is—the hottest all-makes problem-and-cure guide ever—the fully updated master guide to troubles and circuit problems in American-made color TV receivers—the guidebook that can save you hours (and even days!) of troubleshooting time! This valuable book packs more facts per page than any other, and it describes in words, diagrams, and schematics the kinds of troubles you don't ordinarily see in books—like original-set wiring errors, corrections to manufacturers' printed schematics, maker-originated modifications to improve set performance, and scores of service tips for individual models of specific makes. It's a fully indexed all-in-one reference guide to color-set troubles and recommended solutions, manufacturers' service notes, and production change data—all alpha-numerically arranged by manufacturer and model. This low-cost handbook contains service tips, troubleshooting data, and a wealth of special problem-solving aids for all popular U.S. and Canadian color TV makes and models, from A (Admiral) to Z (Zenith).

But that's not all! Included also are details concerning repetitive troubles, field-factory changes, new and unusual circuits and descriptions of how they work, special adjustment procedures and hosts of other invaluable service information. Of particular importance are the manufacturer's production changes—this book includes a detailed accounting of such changes where they might logically affect set

performance and where the serviceman might replace a "factory" component with an unsuitable substitute.

This book is a "must" for every practicing professional TV service specialist . . . the data it contains will easily save you hours of time repairing "tough-dog" color TVs. Partial schematics, location diagrams, chassis layouts, and sketches are included as necessary to make every entry easy to understand and simple to implement in the field. To our knowledge, no other single volume contains so much easy-to-find information about so many individual models and brands of color receivers. A complete cross-reference index is provided to enable you to quickly find the specific material you need. In all, over 1000 specific items are included.

If you service color TVs, this organized file of data will pay for itself time and again. It provides instant solutions to many color TV circuit troubles, enabling you to diagnose and repair hundreds of otherwise difficult-to-solve problems. The material was carefully selected from the pages of Electronic Technician/Dealer magazine on the basis of its lasting usefulness to active members of the TV servicing fraternity. Thumb-indexed for instantaneous reference. 434 pps., hundreds of schematics and diagrams. Hardbound. Publisher's list price \$9.95.

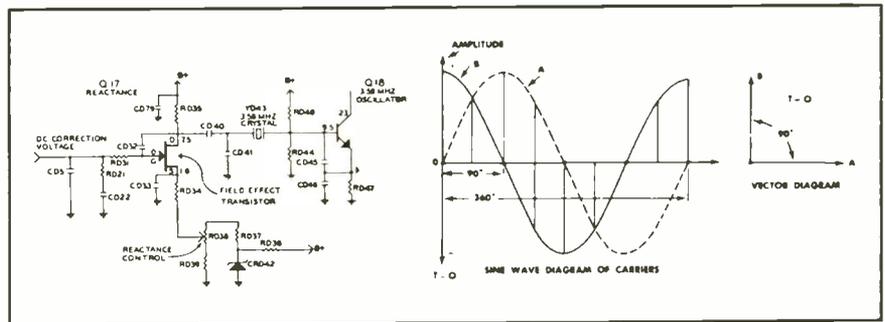

Literally hundreds of complete and partial schematics and illustrations make each of the thousands of entries in "Color TV Trouble Factbook" easy to understand.

...for more details circle 125 on Reader Service Card

AN EXTRAORDINARY OFFER...

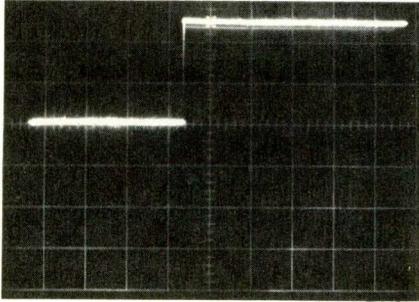


Fig. 3—A normal rising waveform of a positive power supply that is mostly resistive.

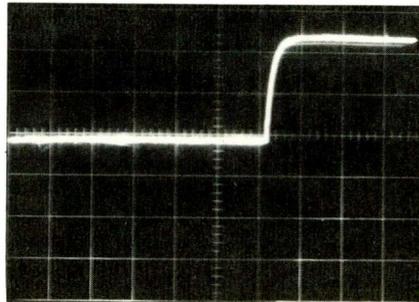


Fig. 4—A slightly damped waveform produced at turn-on in a high capacitance power supply.

power supply that is mostly resistive. Fig. 4, on the other hand, shows the slightly damped waveform to expect when turning on a high capacitance power supply. This particular waveform was taken from a power supply with a 2000 Mfd capacitor.

Ordinarily, this information is of little interest, but every now and then we see a piece of equipment which seems to become latched up on turn-on. Such circuits generally use dual polarity power supplies and may use op-amps, or other linear IC devices, or they may use regular transistors and diodes. The problem is caused by having one of the two opposite polarity supplies lag a little behind its companion when turning on. An open capacitor will substantially reduce the turn-on time constant and that is the root of these problems. This can be diagnosed by using a dual trace scope with one input on each of the two supplies. Examine the rise times to see that they are approximately equal.

Similarly, we should also consider what happens at turn-off. This is especially true in dual supply IC circuits—in fact, it is often critical.

Most IC devices have PN junctions between the active transistors and other components of the device and the substrate of the IC. In normal operations, these PN junctions (in effect, diodes) are reverse biased, so they are inert in the circuit.

In some IC circuits, particularly those with dual-polarity DC power supplies, certain conditions can

cause this PN junction (or "diode") to become inadvertently forward biased. Under this condition, if sufficient current flows, the IC would be destroyed.

A common type of IC linear circuit configuration is shown in Fig. 5. U1 is an IC amplifier or signal processor device. For purposes of this discussion we will not specify which type it is, because the problem is almost generic to dual-polarity linear ICs.

In this particular circuit, there are three sources of rather substantial current flow: Vcc(+), Vee(-), and the current stored in capacitor C1. If the Vcc and Vee voltages decay unequally, then there might exist a brief moment in which the voltage between one power supply terminal and the top of C1 is opposite its normal relationship. In most cases, especially op-amp circuits, the actual failure mode is the reversal of the relationship of the Vee-C1 voltage. This may forward bias the substrate "diode" and allow a current to flow that is great enough to cause permanent damage. In this type of failure, the probability of damage is directly proportional to the length of the decay time lag and the value of C1. Large capacitors for C1 store more current and discharge more slowly.

If an oscilloscope examination reveals a substantially unequal decay time for Vcc and Vee, then suspect this as the possible cause of recurrent IC failure.

The cure for this problem might be to find the reason why the power supplies decay unequally. In normal operation we can rea-

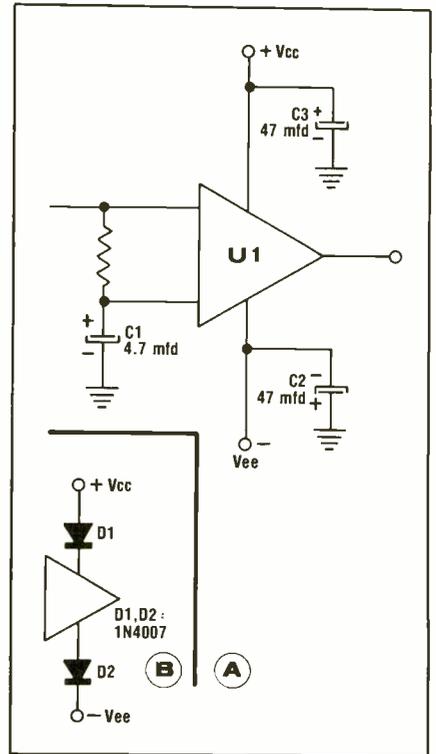


Fig. 5—This is a common type of IC linear circuit configuration, serving as an IC amplifier or signal processor device.

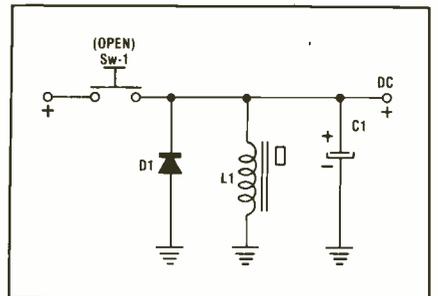


Fig. 6—Diagram of an inductive power supply circuit that could be a solenoid, relay coil, flyback coil, or deflection yoke.

sonably expect both supplies to decay evenly. A defect in an electronic regulator, or an open filter capacitor, may tend to upset this delicate balance.

Another cure, although this may also be classified as a modification, is to series connect a rectifier diode in each of the two power supply lines. These diodes are connected with their polarity arranged so that only current of the right polarity can pass (see Fig. 3B).

Now let's consider the type of power supply circuit shown in Fig.

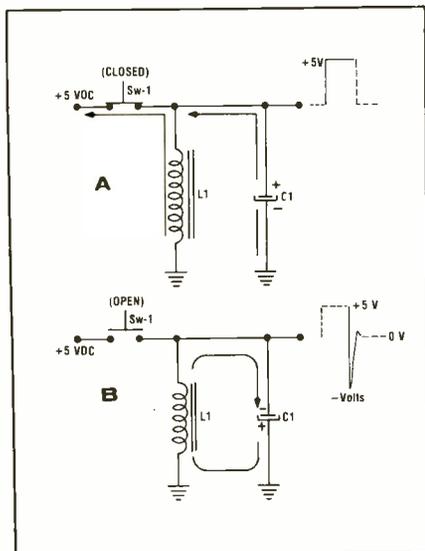


Fig. 7—Diagrams of an inductive power supply circuit without a suppressing diode, in the 'on' position (7A) and the 'off' position (7B).

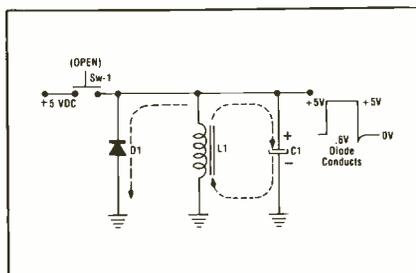


Fig. 8—The inductive power supply shown in Fig. 7 with the suppressing diode added to the circuit in the 'off' position.

6—an inductive circuit that includes a switch (S1), a diode (D1), a capacitor (C1), and a coil (L1). The coil could be a solenoid or a relay coil—or in a more abstract sense—a flyback coil or deflection yoke. What the circuit amounts to is a high inductance hit by a repetitive DC step voltage that is produced by depressing and releasing the pushbutton switch, or in other words, turning on and turning off the circuit.

A diode (D1) is usually placed in this kind of inductive power supply circuit to eliminate, or suppress, the so-called inductive kick, or "spike" which occurs each time the circuit is turned off. If the diode were to open, and the spike was not suppressed, you could easily end up with blown transistors, diodes, or IC devices. In digital circuits, the spike could also create a

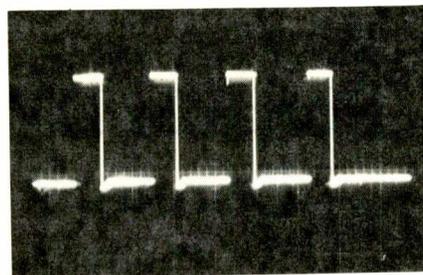
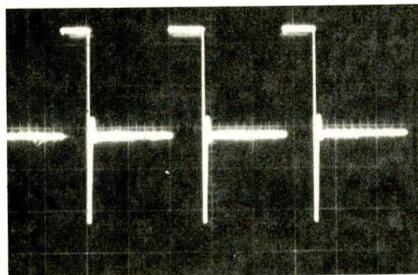


Fig. 9—Waveforms of an inductive power supply produced during several on/off cycles. Fig. 9A shows the negative spike produced when the suppressing diode is open or missing. Fig. 9B was produced by a power supply circuit with a properly operating suppressor diode.

"glitch" that would reset flip-flop or register circuits—or gate them on or off at inappropriate times.

To better understand where the "negative spike" comes from and how a diode serves to eliminate or suppress the spike, let's take a look at Figs. 7A and 7B which show the on and off operations of a power supply circuit without the suppressing diode.

In Fig. 7A, the switch (SW1) is depressed and the circuit is turned on. The applied voltage of +5 VDC charges the capacitor C1 and creates a magnetic field around the coil (L1). The output voltage of the power supply circuit at this point is +5VDC. A drawing of the waveform produced at the moment of turn-on is shown at the right of the diagram.

In Fig. 7B., the switch is released and the circuit is turned off. The capacitor (C1) discharges and the field around the coil collapses. The combined current of the capacitor discharge and the counter electromotive force (CEMF) of the collapsing field of the coil (CEMF is series-aiding to the discharge current of the capacitor) produces a negative spike (or inductive kick). The negative spike that is produced is shown in the waveform drawing to the right of the diagram in Fig. 7B.

In Fig. 8, a diode (D1) has been added to the circuit. Now, when the switch is released and the circuit is turned off, the capacitor (C1) discharges and the field of the coil collapses as before, but now, when the voltage produced reaches -6VDC , the diode starts to conduct and returns the voltage

to ground, eliminating, or suppressing, the negative spike. The waveform produced by this circuit is represented by the drawing to the right of the circuit diagram in Fig. 8.

Actual photographs of the waveforms produced by connecting an oscilloscope input across the power supply circuit at capacitor C1 during several on/off cycles are shown in Figs. 9A and 9B. Please note that the leading edge of the waveforms is missing in the photographs because of a slow rise time in the particular scope used.

Fig. 9A is the waveform, complete with negative spike, produced when the diode is either open or missing. Fig. 9B is the waveform produced by a power supply circuit that includes a properly operating suppressor diode.

As we said in the beginning, using an oscilloscope to examine power supply circuits—and knowing what to look for—can solve a lot of your "tough dog" problems. In fact, it probably is safe to say that the scope is a necessary piece of equipment for truly successful power supply troubleshooting.

Of course, as is the case with other electronic circuits and devices, if the problem still can't be solved with the knowledge and equipment you have at hand—a call or a letter to the manufacturer's service department, or even the engineering department, might be necessary. It's possible that this has been a recurring problem with this particular device and the manufacturer may be able to recommend a cure. ■

TEST INSTRUMENT REPORT

Portable DMMs—Systron-Donner's Model 7003 & Dana's Model 2100A



Systron-Donner Model 7003 Digital Multimeter. For more information about this test instrument, circle number 144 on Reader Service Card.

SYSTRON-DONNER MODEL 7003

■ If you've been looking for a portable digital multimeter which is not only 'drop-proof' but also virtually crush-proof, Systron-Donner's Model 7003 could be the answer.


As shown in an accompanying photo, the clamshell-shaped, Cycloy case of the 7003 easily supports the 355 pounds of Systron-Donner design engineer Phil Kearney. (Cycloy is an ABS/Polycarbonate plastic alloy which also is used in professional football helmets and in the bumper assemblies of 1976 cars.)

The 7003 is equipped with a 3-½ digit LED display with .4-inch-high orange numerals against a black background and is capable of measuring DC voltages from .1mV to 1000 volts, AC voltages (*true RMS readout*) from .1mV to 500 volts, DC current from .1μA to 1999mA, AC current (*true RMS*

readout) from .1μA to 1999mA, and resistances from .1 ohm to 19.99 megohms. (Specific ranges, accuracies and other electrical characteristics of the 7003 are detailed in the accompanying specifications table.)

Display features of the 7003 include automatic polarity indication, with both positive and negative indicators; automatic positioning of the decimal point for each of the six range pushbuttons; automatic zeroing on all functions and ranges; and automatic over-range indication (flashing of the entire display). In addition, the word "ERROR" is illuminated to the right of the main display when the wrong combination of function and range is selected.

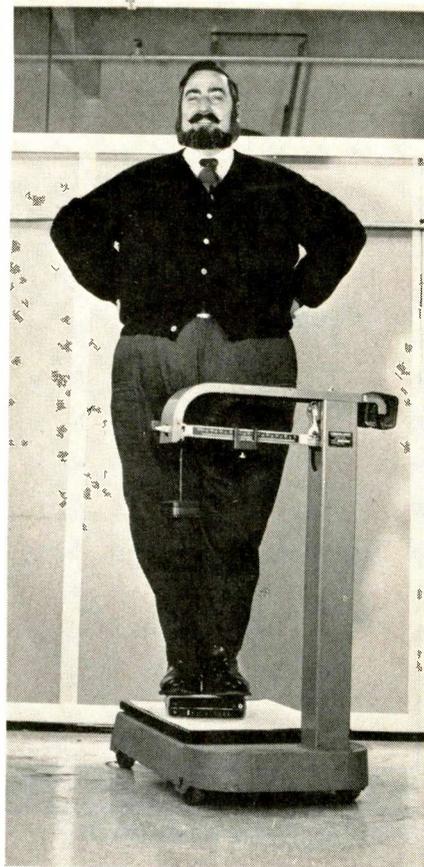Input to the 7003 is via three jacks in the upper right-hand corner of the front panel—the red jack, labeled 'V/Ω', is used in conjunction with the 'COM' jack for



Not even the 355 pounds of Systron-Donner design engineer Phil Kearney can crush the clamshell-shaped Cycloy case of the Model 7003.

voltage and resistance measurements, and the white jack, labeled 'mA' is used in conjunction with the 'COM' jack for current measurements.

The 'mA' input circuit is protected against currents exceeding 2 amps by an externally resettable circuit breaker, the reset button of which is conveniently positioned above the input jacks on the front panel.

As is evident in the accompanying close-up photo of the 7003, the four function and six range pushbuttons are grouped separately on the front panel under conspicuous 'FUNCTION' and 'RANGE' labels. In addition, a white, green, gold, blue, or orange 'panel' automatically appears behind the clear plastic of the pushbuttons whenever they are pushed in, providing a clear visual indication of which function and range has been selected.

The basic version of the 7003 is AC powered, but it also is available optionally with a built-in rechargeable nicad battery pack/charger system which provides six hours of continuous operation be-

SPECIFICATIONS SYSTRON-DONNER MODEL 7003 DIGITAL MULTIMETER

DC VOLTAGE

Fullscale Ranges: +199.9 mV (0.2), +1.999V (2), +19.99V (20), +199.9V (200), +1999V (2000)

Resolution: 100 μ V to 1V

Polarity Selection: Automatic with plus and minus indicator.

Input Impedance: 10 megohms all ranges

Accuracy (1 year):

0.2 range (25+5°C): +0.2% rdg. + 2 counts
2, 20, 200 and 2000 range (25 +5°C): +0.1% rdg. + 1 count

Maximum Input: +1000VDC or Peak AC

DC CURRENT

Fullscale Ranges: +199.9 μ A (0.2), +1.999 mA (2), +19.99 mA (20), +199.9 mA (200), +1999 mA (2000)

Resolution: 100 nA to 1mA

Polarity Selection: Automatic with plus and minus indicator

Accuracy (1 year):

0.2, 2, 20, and 200 ranges (25 +5°C): +0.5% rdg. + 2 counts
2000 range (25 +5°C): +1.0% rdg. + 3 counts

Terminal Voltage:

0.2, 2, 20, 200 ranges: 0.2V at F.S.
2000 range: 0.6V at F.S.

Maximum Input: +2000 mA. Circuit breaker protected (Operates under 3A load for 6 seconds)

AC VOLTAGE

Fullscale Ranges: 199.9 mV (0.2), 1.999V (2), 19.99V (20), 199.9V (200), 1999V (2000)

Resolution: 100 μ V to 1V

Input Impedance: 10 M Ω in parallel with 100 pF

Frequency Range: 50 Hz to 10kHz

Accuracy (1 year):

0.2 and 2000 ranges (25 +5°C): +1% rdg. + 3 counts (applies 1% F.S.)
2, 20, and 200 ranges

(25 +5°C): +0.75% rdg. + 3 counts (applies 1% F.S.)

Maximum Input: 500V (RMS)

AC CURRENT

Fullscale Ranges: 199.9 μ A (0.2), 1.999 mA (2), 19.99 mA (20), 199.9 mA (200), 1999 mA (2000)

Resolution: 100 nA to 1 mA

Frequency Range: 50 Hz to 10 kHz

Accuracy (1 year):

0.2 and 2000 ranges (25 +5°C): +1.5% rdg. + 3 counts (applies 1% F.S.)
2, 20, and 200 ranges (25 +5°C): +1% rdg. + 3 counts (applies 1% F.S.)

Terminal Voltage:

0.2, 2, 20, and 200 ranges: 0.2V at full scale
2000 range: 0.6V at full scale

Maximum Input: 2000 mA (Circuit breaker protected)

RESISTANCE

FULLSCALE RANGES

FULLSCALE RANGES	CURRENT THRU RX	RESOLUTION	F.S. VOLT DROP
199.9 Ω (0.2)	1mA	0.1 Ω	1.999
1.999K Ω (2)	1mA	1 Ω	1.999
19.99K Ω (20)	100 μ A	10 Ω	1.999
199.9K Ω (200)	10 μ A	100 Ω	1.999
1999 K Ω (2000)	1 μ A	1K Ω	1.999
19.99M Ω (20 M)	0.1 μ A	10K Ω	1.999

Accuracy (1 year) (25 +5°C):

0.2 range: +0.4% rdg. + 2 counts
2 range: +0.3% rdg. + 2 counts
20 and 200 ranges: +0.2% rdg. + 2 counts
2000 range: +0.4% rdg. + 3 counts
20 M range: +0.5% rdg. + 4 counts

Maximum Open-Circuit Voltage: 4 volts

Voltage Protection (without damage): 250 Vrms

GENERAL

Size: 2. in. high x 8.75 in. wide x 10.88 in. long

Weight: w/out battery option, 3 lbs. 3 oz; w/battery option, 4 lbs

Power Requirements: 110-115 VAC (RMS) or 200-230 VAC (RMS), choice selected by jumpers on main printed-circuit board

two types of carrying cases, 30-KV high-voltage probe, and a rack mounting kit.

DANA MODEL 2100A

'A truly portable, 3½ digit, all-solid-state digital VOM' is an apt description of Dana's Model 2100A (Danameter II).

Included among the design features which have earned the Model 2100A its 'truly portable' label are its:

- *Small size*—its 4 in. x 7¼ in. x 2¼ in. dimensions are only slightly larger than an out-stretched hand.

- *Light weight*—a mere 1 lb., including battery.

- *Rugged construction*—a virtually unbreakable Cylocac[®] case with molded shoulders which protect the readout window and single operating switch, combined with solid-state circuitry, make the Model 2100A capable of withstanding the extreme abuse which test instruments inevitably are subjected to in off-the-bench and out-of-shop servicing situations.

- *Extended-operation capability from a built-in power source*—powered by a single non-chargeable 9-volt 'transistor radio' battery, the Model 2100A is capable of performing about 3000 hours (or about one year) of in-spec measurements before battery replacement is necessary.

Complementing the preceding 'portability' features of the 2100A are: 1) a 3½ digit liquid crystal display (LCD)—which can be read easily in dimly lighted environments, as well as in bright sunshine; 2) a versatile measuring capability—DC voltages from 1mV to 1000 volts, AC voltages from 1mV to 700 volts RMS, DC current from .01 μ A to 1.999A, and resistances from 1 ohm to 19.99 megohms; and 3) single-switch operation—all functions and ranges, including on/off and battery test, are selected by one large 18-position switch on the front panel.

Other ease-of-operation features are: automatic zeroing, automatic decimal positioning, automatic polarity indication (depending on the polarity of the DC voltage or current being measured, either a negative (-) or plus (+) sign is displayed on the left side of the readout, eliminating

tween recharges. The built-in charger continuously recharges the battery pack whenever the instrument is plugged into an AC source, regardless of whether the instrument is on or off. Complete recharging is accomplished in 16 hours. The brightness of an internal ballast lamp, viewable through the rear panel vent, indicates the rate of charge and, therefore, the state of charge of the battery pack—a dim lamp indicates a slow rate of charge and, therefore, a fully charged battery pack.

Access to the battery pack, the line fuse (½-amp Slo-Blow, for 115 VAC operation) and the circuitry of the 7003 is accomplished by removing six screws on the bottom of


the instrument and lifting off the top half of the case. The optional battery pack is securely mounted to the underside of the top half of the case.

The case of the instrument has a built-in handle at the rear, and an adjustable stand is supplied with the instrument, for insertion in slots in either the front or back underside of the case. Also supplied with the 7003 is a plastic protective cover which slips over the front panel of the instrument.


The price of the basic (AC power only) version of the Model 7003 is \$295, and the AC/DC-powered version with built-in battery pack/charger is \$340. Other options available include test leads,



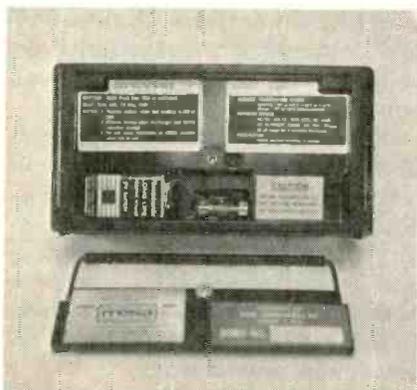Dana Model 2100A Digital VOM. For more information about this test instrument, circle number 145 on Reader Service Card.



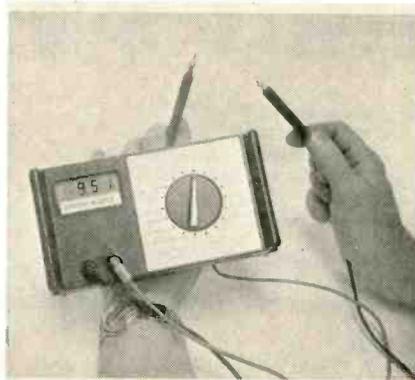Rear view of Dana Model 2100A Digital VOM with cover of battery/fuse compartment removed. Single non-chargeable 9-volt battery provides one year of operation.



In awkward servicing situations the Dana Model 2100A can be worn on the back of a hand like a wrist watch, freeing both hands for test lead placement.

the need for reversing the test leads), and *overrange indication* (if the quantity being measured exceeds the capability of the selected range, the letters 'OL' are displayed by the readout, indicating the need to select a higher range).

Overload protection of all voltage and resistance ranges and 20 μ A current range, up to the associated maximum input levels indicated in the accompanying table of specifications, is provided by the inherently high input impedances of these functions and ranges.

Overload protection for the 2mA, 200mA and 2A DC current ranges is provided by a 2½ amp fast-blow fuse, which, along with the battery, is housed in a compartment in the back of the in-

strument. (Access to the fuse or battery is accomplished by loosening the single screw which secures the cover of the battery/fuse compartment and then sliding the cover up and out.)

Another design feature which enhances the ease with which the 2100A can be used in off-the-bench applications is a built-in, two-position, bail-type stand on the back of the instrument. In addition to serving as a stand which can be tilted to two positions for ease of viewing on the bench, the bail also makes it possible to wear the 2100A on the back of one hand like a wrist watch in awkward servicing situations, thereby freeing both hands for test lead positioning.

Price of the Model 2100A, com-

SPECIFICATIONS DANA MODEL 2100A DIGITAL VOM

DC VOLTAGE

Full-Scale Ranges: +1.999V (2V), +19.99V (20V), +199.9V (200V), +999V (1000V)

Resolution: 1mV to 1V

Polarity Selection: Automatic with plus and minus indicator

Input Impedance: 20 megohms, all ranges

Accuracy (1 year 20° C -30° C):

2V range: +(.25% rdg. + 1 count)
20V, 200V, 1KV: +(.35% rdg. + 1 count)

Maximum Input: +1000 VDC or PEAK AC

AC VOLTAGE

Full-Scale Ranges: 1.999V (2V), 19.99V (20V), 199.9V (200V), 999V (1000V)

Resolution: 1mV to 1V

Input Impedance: 2 megohms in parallel with 50 pF

Accuracy (1 year, 20°C-30°C):

45Hz to 400 Hz: .5% rdg + 2 counts
400Hz to 4KHz: 1.5% rdg. + 2 counts
*2KHz on 2V range

Maximum Input: 1000V PEAK AC or 250VDC

DC CURRENT

Full-Scale Ranges: +19.99 μ A (20 μ A), +1.999mA (2mA), +1.99.9 μ A (200mA), +1.999A (2A)

Resolution: .01 μ A to 1 mA

Polarity Selection: Automatic with plus and minus indicator

Accuracy (1 year, 20°C-30° C): +(.5% rdg. + 2 counts) for all ranges except 2A

Maximum Input:

Voltage: 250VDC or AC RMS (5 sec. max. on 20 μ A range)

Current: 2 amps (fuse protected)

RESISTANCE

FULL-SCALE RANGES	CURRENT THRU RX	RESOLUTION
1.999K Ω (2K Ω)	100 μ A	1 Ω
19.99K Ω (20K Ω)	100 μ A	10 Ω
199.9K Ω (200K Ω)	10 μ A	100 Ω
19.99meg Ω (20meg Ω)	1 μ A	10K Ω

Accuracy (1 year, 20°C-30° C):

2K, 20K, 200K ranges: .5% rdg. + 2 counts
20meg Ω range: .75% + 1 count

Maximum Open-Circuit Voltage: 4V

Maximum Input Voltage: 250VDC or AC RMS

GENERAL

Size: 4 in. high x 7¼ in. wide x 2¼ in. deep

Weight: 1 lb. (including battery)

Power Requirements: One 9V dry cell (NEDA No. 1604)

plete with test leads, is \$199.50.


Accessories available on an optional basis include shunts for AC current measurement, a 50-KV high-voltage probe, a 200-MHz RF probe, and a carrying case. ■

NEW PRODUCTS

Descriptions and specifications of the products included in this department are provided by the manufacturers. For additional information, circle the corresponding numbers on the Reader Service Card in this issue.

MINIATURE DIGITAL MULTIMETER 127

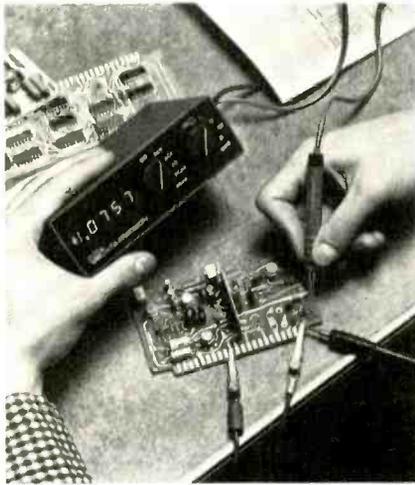
A miniature portable digital multimeter which is said to be the first miniature to provide high accuracy and sensitivity with true RMS measurement of AC volts and current has been introduced by *Data Precision Corporation*. Measuring 1¾ inches high, 5½ inches wide and 3½ inches deep, the Model 248 is a full-function,




high-resolution unit offering 4½ digit resolution on all parameters. It is convertible for bench use with an optional bench stand, and features 10 microvolt sensitivity DC and AC and basic one-year accuracy of ±0.05% of input. Most logic components in the Model 248 are contained in a single LSI chip. It has only two controls, function and range. Priced at \$345.

MAGNETIC VEHICLE DETECTOR 128

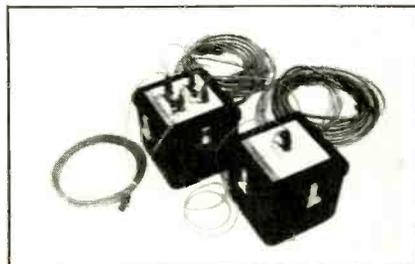A loop vehicle detector, designed for direct burial in the earth, parking lot, or other surface, has been introduced by *Mountain West Alarm Supply*. Called the T10 detector, the new device is said to be ideal for unattended use in surveillance of remote access areas or perimeters, and for use in urban environments for surveillance



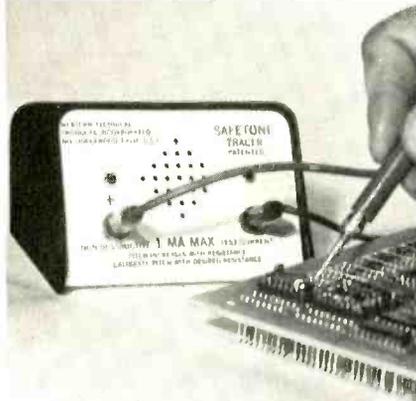or to alert attendants while on duty. The detector provides coverage of from a few feet to more than 400 feet with a single unit. Signal recognition circuitry coupled with adjustable sensitivity provides for detection of targets ranging from small magnets and bicycles to motorcycles, snowmobiles, and automobiles, while rejecting false alarms. Sells for \$680.00.



AUDIBLE CIRCUIT TESTER 129

A new current-limited audible circuit tester for rapid tracing of electronic circuits is being introduced by *Western Technical Products*. Called the Safetone Tracer it has been designed for rapid tracing or troubleshooting of circuits, IC's, semiconductors, logic components, harnesses, pots and relays. Unlike ohmmeters, test lights, buzzers, and high current testers, the new tracer will not degrade or damage components, according to the manufacturer. While listening to the tone pitch, which increases with resistance, the user is able to sweep rapidly across circuits with freedom of eye and body. Replaceable test leads can be extended to allow for 2-man testing. The tracer uses two standard size D batteries. Retail price is \$29.50.

SEALED LEAD-ACID CELLS & BATTERIES 130

A new line of rechargeable sealed lead-acid (SLA) cells and batteries has just been released by *General Electric*. They feature the same type of wound-plate construction used in GE's nickel-cadmium batteries. The first units marketed will be the "D" size; high capacity "X" cells will be available shortly. These new cells are sealed so they can be used in any position, but a resealable safety vent is provided to prevent cell bursting under extreme abusive use. The "D" cells provide 2.5 ampere-hours capacity at the 250 milliamper discharge rate. They are capable of delivering continuous current up to 40 amps or

Autoranging Frequency Counting to 60 MHz with 1 Hz Resolution



B&K-PRECISION MODEL 1801 \$240

- For laboratory, production line or maintenance applications
- Automatic ranging, 20 Hz to 40 MHz is guaranteed...readout to 60 MHz is typical
- TTL circuitry updates the six-digit display five times per second
- Resolution to 1 Hz obtained by suppressing digits above 1 MHz when switching to 1 SEC mode



MHz display of
3.579548 MHz input (AUTO mode)



KHz display of overflow of
3.579548 MHz input (1SEC mode)

- Available for immediate delivery, from local B&K-PRECISION distributors
- 10-day free trial offer

B&K PRECISION
PRODUCTS OF DYNASCAN

6460 West Cortland Avenue
Chicago, Illinois 60635 • 312/889-9087
In Canada: Atlas Electronics, Toronto

...for more details circle 108 on Reader Service Card




momentary currents (one second) of 75 amps. Standard batteries made from "D" cells are also available in 6 and 12 volt designs. Dimensionally, the batteries will be interchangeable with batteries of other manufacturers. The "D" cells are priced from \$2.49 to \$4.80, depending on size of order.

ALUMINUM FOIL-SHIELDED CB CABLES 131

A new line of CB cables with an aluminum foil-shield is being introduced by *Columbia Electronic Cables*. The bonded feature of the new foil-

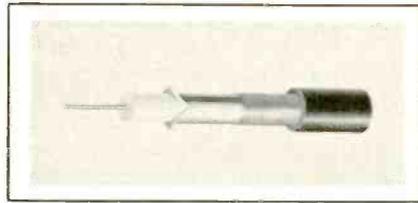shielded cable, called Stat-Stop, is said to prevent shield pushback during connector application. Shield pushback and the resultant gap in the shield and connector are common



causes of poor reception. The new cable consists of a 20 AWG bare copper conductor insulated with cellular polyethylene. The shield is wrapped and adhesive bonded over the insulation. A 95% tinned copper braid shield supplies additional shielding and the entire assembly is protected by a black vinyl jacket with a nominal overall diameter of 195 inches.

DIGITAL MULTIMETER 132

A new battery/ac portable 4½ digit, five-function digital multimeter that features a 'touch-hold' probe as an accessory is being introduced by *Hewlett-Packard*. The 'touch-hold' probe allows the user to freeze the reading on the display when probing closely-packed circuit boards. Called

the Model 3465B, the meter has a DC measurement range from 1 microvolt to 1 kilovolt with a mid-range accuracy of $\pm (0.02 \text{ of rdg. } \pm 0.01\% \text{ of range})$ for one year. AC measurement range is 10 microvolt to 500 volts with a mid-range accuracy of $\pm (0.15\% \text{ of rdg. } \pm 0.05\% \text{ of range})$ over a 40 Hz to 20 kHz bandwidth. AC and DC current



measurement range is from 10 nanoamps to two amps. The DMM, with rechargeable nickel-cadmium batteries, sells for \$500. The touch-hold probe sells for \$40.

MAGNETIC CB MOUNT 133

A new two-way radio mount that uses magnetic power to hold the transceiver in place has been introduced by *Cornell-Dubilier Electronics (CDE)*. The new mount also provides a quick

\$1,550 Puts Lampkin 109 Quality on Every Job, CB to 500 MHz.

- Measure / Generate better than 0.001%
- Optional eight 12 MHz bands to 512 MHz
- Eight-digit display to 512 MHz
- Calibrated output 50 mv to 0.1 mv
- Measure / Generate 0-100% AM, metered
- Internal Mod 5G Hz to 6000 Hz
- Optional full FM function, 1 MHz sweep, frequency error meter.
- \$1,550. Options extra.




Manufacturers of Precision Communications Test Equipment Since 1932
LAMPKIN LABORATORIES INC. P.O. Box 9048 • Bradenton, Fla. 33506 • Ph. 813 746-4175

©1976 Lampkin Laboratories Inc.

...for more details circle 117 on Reader Service Card

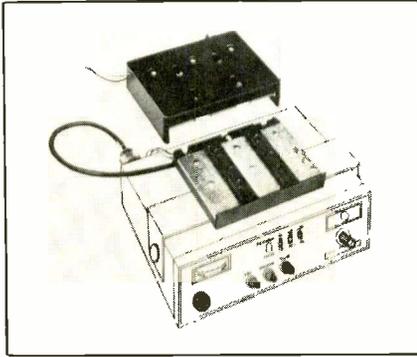
connect/disconnect system for antenna and power. Called the Easy Mount, the new device uses three powerful permanent magnets to make positive contact, assuring maximum signal transfer with perfect VSWR match. Installation is simple and gives a flush mount appearance. User has choice of dash or transmission hump



installation. Contacts are cadmium plated, main frame is molded of ABS filled high impact plastic. Magnet structure is U-channeled permanent ceramic. The mount weighs 1.25 lbs, and comes with a full year warranty.

"UNDER COVER" CB ANTENNAS 134

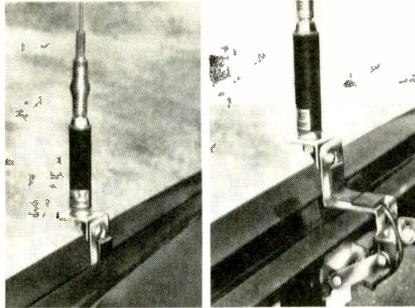A new line of full-sized, 40 channel, coil-loaded whip antennas that can be



flipped down and hidden in the automobile trunk when not in use is being introduced by *Channel Master*. Base-loaded and center-loaded models are available, mounted on a heavy gauge, two-way 'under-cover' bracket, which allows the user to mount the antenna in a perfectly vertical position, regardless of the slope of the car's rear deck, and also allows the antenna to fold down into the trunk, completely out of sight. Within in the trunk, the bracket keeps the antenna suspended horizontally, out of the way of luggage. The chrome-plated bracket serves as a self-grounding base.

TUNER CLEANER/DEGREASER 135

A new tuner cleaner/degreaser called Big Bath has been introduced by *GC Electronics*. The new cleaner comes in a 24 oz. aerosol can that re-

FREE EICO CATALOG

358 Ways To Save On Instruments, Citizens Band, Burglar Alarms, Automotive & Hobby Electronics!

The more you know about electronics, the more you'll appreciate EICO. We have a wide range of products for you to choose from, each designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

"Build-it-Yourself" and save up to 50% with our famous electronic kits.

For latest EICO Catalog and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.


**EICO—283 Malta Street,
Brooklyn, N.Y. 11207**

*Leadership in creative electronics
since 1945.*



...for more details circle 113 on Reader Service Card

CUTTERS WITH THE DURABLE CUTTING EDGE.

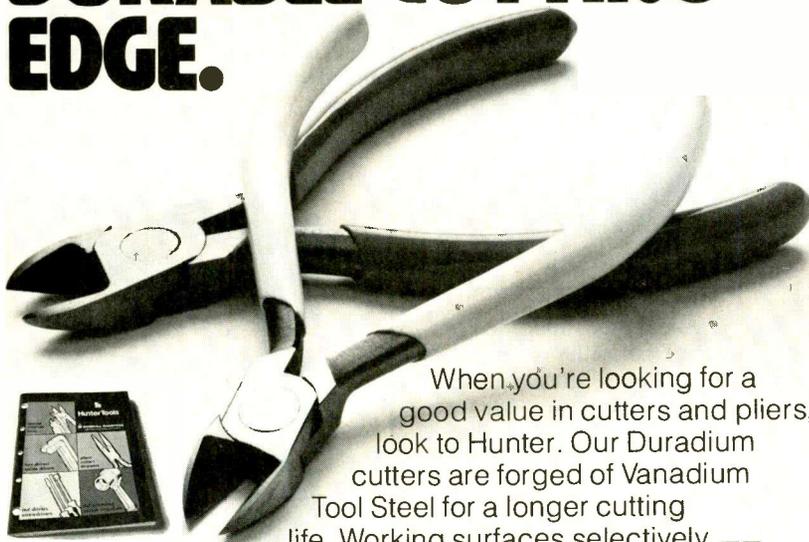


FREE CATALOG

When you're looking for a good value in cutters and pliers, look to Hunter. Our Duradium cutters are forged of Vanadium Tool Steel for a longer cutting life. Working surfaces selectively hardened for 1000's of wear-free cuts.

Free Catalog of our cutters and other hand tools, write to Hunter Tools, 9674 Telstar Ave., El Monte, Ca. 91731.

Hunter Tools
From the Group Called Marshall

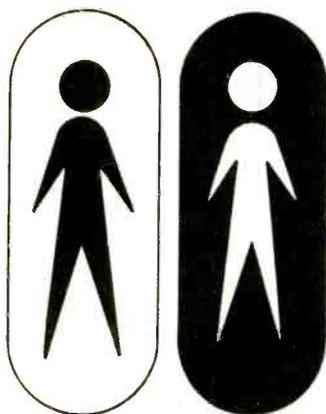...for more details circle 126 on Reader Service Card



LIFE OR DEATH SITUATION

Not all 2-way radios warn about Smokles taking pictures.

Professional FM two-way radios—the most important ones—are for bringing help fast in life or death emergencies. And if you've had some serious electronics experience you just might fit into this important, expanding field.

MTI is the only home study school that deals exclusively with service and repair of professional two-way radios.

Think you're good enough to become part of it all? Drop us a line to find out.

Please send me more information.

Name

Address

Code

- I am a former MTI student.
 I am presently in the military.
 I am a veteran. Z9



Formerly

MOTOROLA TRAINING INSTITUTE

College Hill Road
 Summerville, PA 17093
 (717) 732-3636


...for more details circle 118 on Reader Service Card



leases a high pressure stream which is said to penetrate through dirt, dust and grime to protect tuners from corrosion. According to the manufacturer, Big Bath will not harm plastics, will not detune and will not cause residue build-up. Introduction of this new item includes a premium offer of a 6-piece color TV alignment kit for every 5 Big Bath labels sent in to manufacturer.

FM DEVIATION METER 136

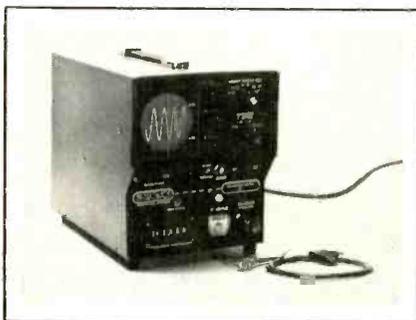A new FM deviation meter that can double as a signal generator is now available from *Bi-Tronics*. The unit has been designed for use in repair and maintenance of VHF FM marine and VHF/UHF land mobile transceivers. Instantaneous peak deviation is measured on a graticule scale in the front




of a 3 inch cathode ray tube. This permits the wave form to be observed so that identification of distortion and hum can be visibly noted. Accurate modulation measurement is obtained. Each unit, which also functions as a monitor receiver with .0005% accuracy, includes an external uncalibrated attenuator which permits unit to be used as a signal generator. The meter is warranted, part and labor, for 90 days. Sells for less than \$1100.

CB INTERFERENCE SUPPRESSOR 137

A T-30F matching transformer with high pass filter for the suppression of

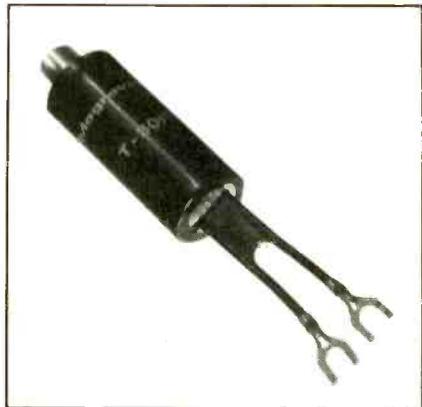
interference from CB transceivers has been introduced by the *Magnavox CATV division*. Designed to block sub-low interference, the T-30F prevents signals in the 5-30 MHz range from disturbing 50 to 300 MHz TV reception. Transformer specifications in-



clude: high phase balance, low insertion loss, effective filtration and voltage blocking capacitors. The unit has a die cast metal casing and plastic cover, plus heavy-duty twin leads with soldered and crimped lugs.

AUTO-RANGING VOLT OHMMETER 138

A new 3½ digit auto-ranging volt ohmmeter with temperature measuring capability has been introduced by *Philips Test & Measuring Instruments*. The instrument incorporates an 11 mm LED display with polarity indication. Overloading is indicated by a flashing display and lead changing is eliminated since the same input sockets are used for voltage and resistance measurements. Functions are selected with a rotary switch. Automatic decimal point positioning provides maximum resolution for each measurement. Auto-ranging can be stopped at the last range in use by

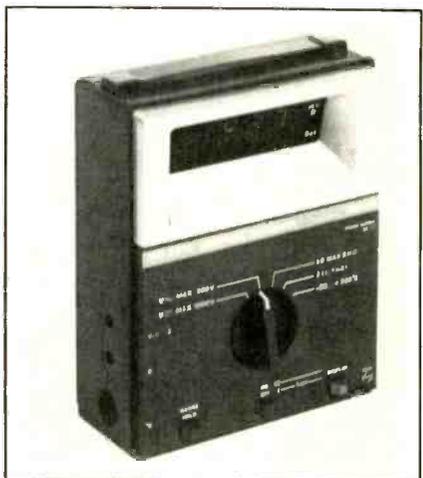

means of a range hold button. This PM2514 meter also has a low battery indication separate from the numeric display, and has an optional external

power supply for use off the line. Priced at \$255.

QUICK-CHANGE STORE SIGNS 139

A new line of low cost, changeable message signs for retail businesses is being introduced by *Berloc Signs*. Constructed of rugged aluminum and guaranteed for 20 years, the new signs are available in assorted styles. The



baked enamel finish can include store name and emblem in choice of colors, and each sign comes with 150 unbreakable aluminum letters and numbers. Sizes range from 8 ft by 44 in. to 14 ft. by 7 ft. Signs are shipped fully assembled and ready for immediate use. Price is from \$307.

REFLEX HORN SPEAKER 140

A 5½ inch reflex horn speaker for CB radios, for paging and patio use is now available from *RMS Electronics*. Constructed of heavy duty aluminum, the speaker is anodized for indoor and



outdoor use. It is rated at 8 ohms, 8 watts, and is for use on cars, trucks, vans, boats and at home. Comes complete with mounting bracket and long hook-up cable. Priced at \$12.95.

AUTO AND CB SECURITY SYSTEM 141

A new anti-theft alarm system for cars that is easy and quick to install has been developed by *Harcor International*. The new "quick connect" system, Model 3001, is triggered by the



current flow that occurs when any light in the auto is turned on—such as when a car door or trunk lid is opened. Upon triggering, an integrated circuit in the unit beeps the car horn for 2½ minutes, then shuts itself off and automatically rearms itself. Solderless connectors and a simple 3-wire hook-up allow installation in less than 30 minutes. By connecting a fourth wire, the unit will disable the car's ignition when the alarm switch is activated. A delay circuit allows the car owner from 7 to 10 seconds to disarm the device in case of accidental triggering. Sells at retail for \$17.95.

TV INTERFERENCE FILTERS FOR CB 142


Three new interference filters that prevent CB transmissions from bothering TV reception have been introduced by *Avanti Research and Development*. The new filters are designed for interference problems at the transceiver, the TV set or the AC power line. The model AV-800 Low Pass Filter is for use when the transceiver is radiating harmonics of the same frequency assigned to one or more of the local TV channels. The model AV-811 filter is installed on the TV lead-in if the problem is at the TV



QUICK CHARGE IRON-QUICK CHANGE TIPS

ISO-TIP® Quick Charge Cordless Soldering Iron recharges in 3-4½ hours. Uses any of **Wahl's 16 snap-in tips.**

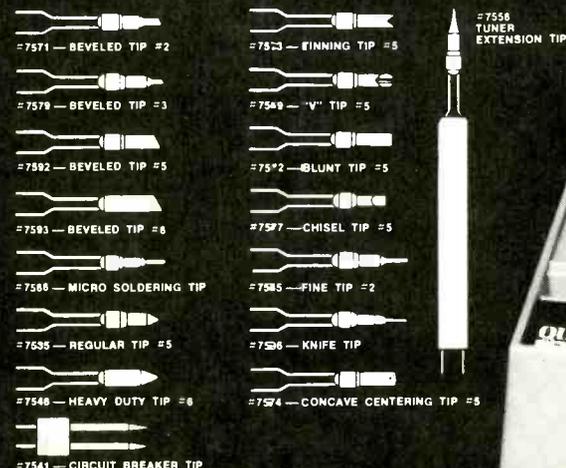Low voltage, battery powered, ground free isolated tip design.




WAHL CLIPPER CORPORATION
 ORIGINATORS OF PRACTICAL CORDLESS SOLDERING.
 Sterling, Illinois 61081 (815) 625-6525
 "Manufacturing Excellence Since 1919"

...for more details circle 124 on Reader Service Card

receiver due to so-called "front end" overloading—and model AV-820 AC line filter is for interference caused by transmission of the CB signal through the AC power lines.

SOLDERING STATION 143

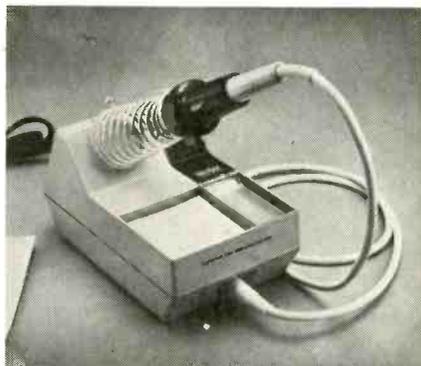A new controlled output soldering station has been introduced by *Weller*. The new model, WTCPN, is a transformer-powered unit complete with a low voltage, temperature controlled soldering pencil with heat shield. The unit features a "closed loop" method of controlling maximum tip temperature, protecting heat-



sensitive components while the ground tip protects voltage and

current-sensitive parts. It utilizes an assortment of 17 types of replacement tips, each available in 600°, 700° and 800° F, heavily iron plated with an anti-oxidation coating.

UPCOMING IN THE JANUARY ISSUE OF ET/D:

- TV Warranty Servicing: Profit Source Or Necessary Evil?
- Professional Audio Tests & Measurements
- Noise Sources In Auto Electronics
- Annual Subject Reference Index

EDITOR'S MEMO

continued from page 1

responsibility for the technical performance of the transmitting equipment he installs and/or services, his only real motivation for insuring that it adheres to FCC performance criteria is the possibility of loss of the business of a customer who has been cited (and perhaps fined) by the FCC for equipment performance violations.

However, failure of a transmitting system to meet FCC performance criteria can be, and often is, caused by 'normal' degradation resulting from 'normal' use or from abuse or illegal modification or

CORNELL ELECTRONICS COMPANY

4213 N. UNIVERSITY AVE. SAN DIEGO CALIF. 92105

Same Low Price
East or West Coast!

★ Bargain Tools
★ Transistor Tester
★ Technician's Library

SPECIAL OFFER

ON ALL ORDERS OVER \$10.00

25¢

PER TUBE (NO LIMIT) FROM THIS LIST

6AG5 6CB6
6AU6 6J6
6AX4 6SN7

SEND FOR FREE NEW 48 PAGE COLOR CATALOG

★ Dumont Picture Tubes
★ Diodes—Transistors—Kits
★ Tube Cartons

THE ORIGINAL HOME OF

36¢ PER TUBE

UNLESS OTHERWISE PRICED

100 TUBES OR MORE

33¢ PER TUBE

ONE YEAR GUARANTEE

INDIVIDUALLY BOXED

5 DAY MONEY BACK OFFER

LAB TESTED USED

Your Order FREE if Not Shipped in 24 Hours

...for more details circle 110 on Reader Service Card

NOW... 97% ACTIVE INGREDIENTS

Plus

WARMER SPRAY FOR MORE CLEANING POWER

TUN-O-WASH has long been the industry standard in tuner degreasers. Now, it's better and more economical than ever.

No, we haven't tampered with the famous TUN-O-WASH formula. That's too good to change. What we have changed is the propellant. We now use carbon dioxide (CO₂) as a propellant. This permits us to fill the can with 97% active ingredients, compared with only 65% active ingredients before this development. The can is the same size, but you get more cleaning power for your money.

There are other advantages to using CO₂ as a propellant. FIRST, the spray comes on 10° warmer. Everyone knows that heat increases solvent action. SECOND, the particles of solvent come out in larger drops, making for a wetter spray. And, finally, CO₂ enables us to maintain a uniform 70 pound pressure until the can is completely empty.

This is another first from the electronics industry's leading chemical manufacturer.

CHEMTRONICS INCORPORATED

45 HOFFMAN AVE. HAUPPAUGE, N.Y. 11787 • (516) 582-3322

GO DIGITAL,
GO DANAMETER®

(The New VOM For Today's Needs.)

- 0.25% Accuracy
- Full Overload Protection
- Really Drop-Proof
- Full One Year Battery Life

Dana Laboratories, Inc.

2401 Campus Dr, Irvine, Ca 92715, (714) 833-1234

...for more details circle 111 on Reader Service Card

misadjustment by the operator. Therefore, the technician's legal responsibility should be limited to insuring that the equipment meets FCC performance criteria at the time he completes the installation and/or servicing of it and 'returns' it to the owner.

In my opinion, this 'shared but divided' method of assigning equipment performance responsibility to both the owner and the servicing technician is the most realistic approach to effective enforcement of transmitter performance criteria. **SERVICE TECHNICIAN LICENSING**—So long as transmitting equipment must meet specific performance criteria established and enforced by the FCC, with legal responsibility for meeting such criteria assigned to the owner and/or service technician, and so long as there exists the possibility that such performance criteria can be adversely affected by installation and/or servicing, in my opinion, there will continue to exist the need for some method of evaluating and 'certifying' the competency of technicians who wish to undertake the installation and servicing of transmitting equipment.

However, I believe that the 'all-encompassing' type of Radiotelephone licenses and related exams presently administered by the FCC are unrealistic, principally because, on the one hand, they require some areas of knowledge which are not relevant to the servicing of particular types or classes of equipment and yet, on the other hand, they fail to adequately evaluate some areas which are relevant.

The 'basic operator/technician' license with class-of-equipment options, as proposed by the Commission in its Notice of Inquiry, in my opinion, would be much more realistic for everyone concerned—equipment owners, service technicians and the FCC. ■
J. W. Phipps

DEFIBRILLATOR

continued from page 30

ered energy, which should not be less than 70% of the stored energy found by static testing of the capacitor voltage.

There are a number of suitable defibrillator testers on the market today, but I do not recommend the use of the simple flashing lamp type of tester, as I feel they give false indications.

The best way to test a defibrillator is to use a tester with an oscilloscope waveform jack and an oscilloscope equipped with a camera. If you don't have a scope with a camera, it is possible to accomplish much the same thing with a relatively low-cost hand-held Polaroid CR9A. Typical

waveform photographs taken with a hand-held Polaroid are shown in Figs. 7 and 8. The waveform in Fig. 7 is normal, and that in Fig. 8 shows a defibrillator with an impending HV relay failure. The condition is serious enough to warrant replacement of the relay, but allows time for parts ordering before becoming critical. This machine passed the test using only a defibrillator tester but failed when the expanding scale waveform was viewed on an oscilloscope.

IN SUMMARY

To give you some idea of what service work you're liable to run into when servicing defibrillators, here is an excerpt from the author's repair log on defibrillators for one major East coast hospital. It shows 29 defibrillator failures in an 18 month period.

They break down as follows:

- 13 open 'patient cables'
- 2 bad HV vacuum relays
- 6 bad LV control relays
- 8 miscellaneous problems

Obviously, from the above log, a defibrillator serviceman should carry with him an ohmmeter to

check patient cable continuity, a HV relay, a collection of common small relays, and that bleeder resistor mentioned earlier.

Servicing defibrillators can be a relatively easy job—and there is a real need for this service. Most hospital people become a little nervous if their defibrillator equipment is out of service. They will probably be happy to know that a responsive and responsible local servicer is available to handle repairs.

Be aware, however, that few markets are as critical as the medical market. You can ruin all opportunities if you find yourself offering excuses in place of good service. Try offering the old "awaiting parts" story to a coronary care unit head nurse and you will find out fast how critical the business really is. ■

FREE ALARM CATALOG

Huge selection of burglar & fire systems, supplies. Motion detectors, infrared beams, controls, door switches, bells, sirens. 900 items, 64 pp. packed with technical details, notes.

Phone (602) 263-8831



mountain west alarm


4215 n. 16th st., phoenix, az. 85016

...for more details circle 120 on Reader Service Card

Money Generator

PAT. PEND.

\$299.95

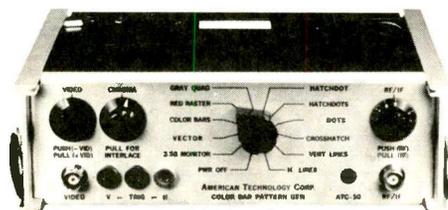

ATC-10 GENERAL TELEVISION SERVICER

- Extra wide range RF/IF attenuator for testing receiver sensitivity.
- GRAY QUAD pattern for gray scale tracking checks/adjustments.
- COLOR BARS pattern with 6th bar marked to make your job easier.
- 3.58 MONITOR pattern for oscillator frequency checks with no need to short the AFPC test point.
- RED RASTER pattern for checking and adjusting purity at the flip of a switch.
- All dot patterns have fine pinpoint dots.
- High level, 75 ohm video output.
- 2 year factory warranty.
- 30 day money back guarantee.




American Technology Corporation

225 Main Street, Dept. 11B, Canon City, Colorado 81212

Credit card & COD phone orders accepted. Same day shipment. (303) 275-8991, ext. 2

Versatile

Carl Babcoke (Electronic Servicing) says, "If I could choose only one of the many kinds of dot or crosshatch patterns, I would want this one." Think how much easier the composite HATCHDOTS pattern below would make your job. It can also perform size, linearity, pincushion and centering checks. It's only one of several unique patterns produced by the ATC-10 that can save you time, trouble and most important—money. We'd love to show you how. Write us.

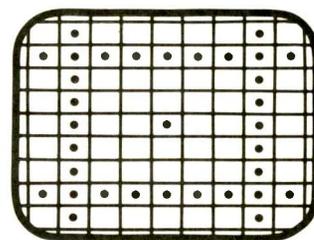

...for more details circle 105 on Reader Service Card

CLASSIFIED

RATES: 40¢ per word; 50¢ per word Bold Face Type. Add \$3.00 if you wish Box Number. Minimum \$10.00 charge. Classified Display Rate billed \$43.00 per inch, 1 inch minimum. Remittance must accompany order. Mail ad copy to: Roz Markhouse, ET/D, 757 3rd Ave., N.Y., N.Y. 10017

Business Opportunities

HOW & WHERE TO BUY USED TV for rebuilding in quantity. Complete information and method, \$10. ppd. EPS, Box 8736, Denver, CO 80201. TF

T-V, Radio & C-B business established 21 years. 40' x 48' building, lot, and equipment-\$25,000 + inventory, about \$12,000. Sylvania franchise. Experienced technician and wife could net \$20,000 year. Also home and 5 acres next door available next summer. Will help a month or two to get you started. Gene's T-V, Elma, Wash. Call 206/482-2904. 12/76

TV Sales/service. Southeast Nassau County L.I. Good Profitable operation for 1-2 man shop. 1000 square feet, \$250.00/month rent. Will sell with/without inventory or equipment. We're moving west. Paul Reindorf, 6 Milford Place, Farmingdale, L.I. 11735. 1/77

ELECTRONICS/AVIONICS EMPLOYMENT OPPORTUNITIES. Report on jobs now open. Details FREE. Aviation Employment Information Service, Box 240 Y, Northport, New York 11768. 6/77

Ten Year Old T.V.-C.B. Service and C.B. Sales Company in California Coastside Town, 15 Miles South of San Francisco, With 40,000 Population. Better Than \$100,000 Yearly Gross-With Right Management Could Double. Retirement In View-Price \$55,000 Cash- No Trucks. Ed. Zinn Jr., 848 Dell Road., Pacifica, CA 94044. 1/77

SURPRISE! SURPRISE! Digital Piano Tuning Device tunes ALL musical instruments Accurately! Perfectly! Inexpensively! Tuner Construction—Piano Tuning Instruction PLAN SET Complete \$12.98 Airmailed Postpaid! Moonlighting quickly repays \$40 electronics investment!! **GREEN BANK SCIENTIFIC**, Box 100W, Green Bank, WV 24944. TF

TV Sales and Service in same location 15 years. Nets over \$25,000. Retiring. Including truck, equipment, & inventory 25,000. A. Bolin, 6361 Balsam Lake, San Diego, CA 92119. TF

TV Shop Owners. Letter & produce your own signs, enlarge emblems. Indoor-outdoor. Tips, tricks & techniques pros use. \$5.95 ppd. EPS, Box 8736, Denver, CO 80201. 12/76

TIRED OF CUSTOMER ABUSE? EXPAND INTO LUCRATIVE PATENTED MATV. PRELIMINARIES \$3.00. BOX 809, BOYNTON BEACH, FLA. 33435. 4/77

Construction Plans

SURPRISE! Free Catalog! WE SELL THE MOST UNUSUAL CONSTRUCTION PLANS USING NUMERICAL READOUTS!! Digital Plans: Capacitance Meter, VOM, Frequency Counter, Oral Thermometer, Automobile Tachometer, Speedometer, Sobriety Tester. ALSO: Ten Band Graphic Equalizer, LED Volume Indicator, Human Pluse Tachometer, TV Video Ping-Pong Game. **PLAN SETS** are \$3.49 each or **ALL** eleven for only \$15.98 Airmailed Postpaid! **GREEN BANK SCIENTIFIC**, Box 100X, Green Bank, WV a. 24944. TF

NEGATIVE ION GENERATOR BUILT AT HOME. Dual stage design. Detailed construction plans and schematics. \$7.50. Golden Enterprises, Box 1282ET, Glendale, Arizona 85311. 12/76

TRANSISTOR TESTER. Convert Transistor Radio Into In-circuit Transistor Tester. Tone Indicates Good Transistor. Plans \$2.00. SZA Electronics Systems Inc., 39 Bayberry Lane, Levittown, NY 11756. 12/76

send a message...
...write here.

1. Number of insertions: (circle) 1 2 3 6 12
2. Start with (month) _____ issue (Copy must be in by 1st of month preceding)
3. Amount enclosed: \$ _____

PAYMENT MUST ACCOMPANY ORDER WE'LL BILL RATED FIRMS NO AGENCY COMMISSION

NAME _____ COMPANY _____

STREET _____

CITY _____ STATE _____ ZIP _____

MAIL COPY FOR AD(S) TO: ROZ MARKHOUSE, Electronic Technician/Dealer, 757 Third Ave., New York, N Y 10017

RATES: 40¢ per word; 50¢ per word Bold Face Type. Add \$3.00 if you wish Box Number. Minimum \$10.00 charge. Classified Display Rate billed \$43.00 per inch, 1 inch minimum.

ELECTRONIC TECHNICIAN/DEALER CLASSIFIED

Magnavox Color Troubleshooting Guide. \$7.50 ppd. Loaded with actual field breakdowns. Covers T904-T981. Electronic Publishing Service, Box 8736, Denver, CO 80201. 1/77

TEST EQUIPMENT: Capacitor Tester, Square Wave Generator, Transistor Tester, Variable Power Supply. Build each for under \$5.00. Send \$2.00. Electro-Research, P.O. Box 712A, Springfield, Tenn. 37172. 1/77

Wanted

WANTED: PICTURE TUBE REBUILDING EQUIPMENT in good working condition. Call or write, Atoll TV, 6425 W. Irving Park, Chicago, IL 60634. (312) 545-6667, between 1PM-8PM. 1/77

For Sale

JAPANESE TRANSISTORS - All Transistors Original Factory Made. Free Catalog. West Pacific Electronics, P.O. Box 3879, Torrance, Ca., 90510. 12/76

Color-Bar Generator, 16 Patterns, Pocket Size. CMOS-LSI Chip, One Transistor. Complete Plans \$5.00. P.C. Boards, Kits Or Wired Units Also Available. Science Workshop, Box 393-ET, Bethpage, New York 11714. 12/76

LINEAR AMPLIFIER for C.B., 2-meter, walkie-talkie. Tiny Solid-State Portable Unit produces 100 Watt PEP from Milliwatts and can be inserted inside existing unit. Build for about \$20. Send \$5.00 for plans to: J. Martin Peter, P.O. Box 07071, Milwaukee, WI 53207. 1/77

REPLACEMENT COLOR YOKES-DEALERS ONLY. Zenith 95-2501-2532-2638-2667-S89633 etc. \$14.95. Magnavox 361380-1 \$18.95 etc. Sylvania, G.E. etc. \$14.95 to \$19.95. Request for price list on your letterhead. David Sims Enterprises, Inc., 665 Jerricho Turnpike, Huntington Station, N.Y. 11746. TF

- (5) ZENITH IC, S 221-42, 221-69 \$4.95
- (10) POPULAR SLIDE CONTROLS \$3.80
- (40) ASSORTED TV, STEREO CONTROLS \$2.45
- (1LB.) SMALL PARTS GRAB BAG (A BEAUTY) \$1.95
- (25) MINIATURE CONTROLS, ASSORTED \$3.95
- (20) WIRE WOUND SQUARE RESISTORS \$2.40
- (40) MYLAR, BY PASS COUPLING CAPAC. \$3.95
- (50) LOW VOLT ELECTROLYTICS \$6.75
- (150) DISCAPS, ASST. P.C. LEADS \$2.95
- (1) ELECTROVOICE 6012D CARTRIDGE MAGNETIC, (LESS STYLUS \$48.00 LIST) \$5.75
- (50) ASSORTED TV RADIO KNOBS \$2.60
- (1) 4x8 SPEAKER 8 OHMS \$1.90
- (1) 340177-7 MGX. SOLID STATE TUNER \$6.95
- (20) TRANSISTOR SOCKETS (TO-5) (TO-92) \$1.95
- (100 FEET) 40 KV ANODE WIRE \$4.95
- (1) 361521-1 MAGNAVOX FLYBACK \$6.95
- (3) COLOR CONVERGENCE YOKES \$4.00
- (3) 110 DEGREE C.R.T. SOCKET & LEADS \$1.95
- (8) 6x9 8 OHM SPEAKER (8 TO BOX) \$15.00
- (1) 361350 MAGNAVOX COLOR DEF. YOKE \$11.95
- (500 FT.) ASSORTED HOOKUP WIRE \$3.95
- (100) RCA PHONO JACKS \$5.20
- (3) BLUE LATERAL MAGNETS (UNIVERSAL) \$2.95
- (3) 2000 MFD. @ 50 VOLTS FP INS. CAN \$3.95

BONUS PLAN—Order 1 line of each item listed above (113.15) for only—\$89.95

ALL ITEMS FULLY GUARANTEED
 ORDERS UNDER \$25.00 ADD \$2.50 SHIPPING
 SATISFACTION GUARANTEED OR 100% REFUND
 WRITE FOR FREE LISTINGS OF ALL ITEMS
PARTS BROKERS, INC.
 P.O. Box 60277 Nashville, Tennessee 37206



TELEVISION PICTURE TUBES

STOP...

Don't junk that television set. ASE manufactures the world's most complete line of television picture tubes. No other company offers:

- Over 2200 types of television picture tubes.
- Most types immediate delivery.
- Transportation paid in some areas.
- Tubes for Old or New Models.
- Complete line of both black & white and color.
- Full 2-year factory warranty.
- Lowest prices anywhere.
- Finest quality.

Write today for more information.

Allied Sales & Engineering, Inc.
 Dept. 41, Pimento, Ind. 47866
 Telephone 812-495-6555

We Accept BankAmericard and Master Charge.

Look no further for CB transistors. Delivery from stock. Write or telephone for lowest prices possible. American Microsemi-conductor Inc., 145 Main St., Madison, N.J. 07940, (201) 377-9566. 12/76

For Sale: B & K 1077B Television Analyst \$250. RCA Cold Test Jig \$150. ELECTRONIC TECHNICIAN/DEALER w/ schematics Sept. '65 - present \$30. John Shoemaker, 8700 Dulwick Court, No. 22, Laurel, MD 20811. 12/76

REPAIR TV TUNERS-High earnings, Complete Course Details, 12 Repair Tricks, Many Plans, Two Lessons, all for \$2. Refundable. Frank Bocek, Box 3236, Ent., Redding, CA 96001. TF

PICTURE TUBE MACHINE

We buy and sell NEW AND USED CRT rebuilding machinery. COMPLETE TRAINING. Buy with CONFIDENCE from the ORIGINAL MFRG. For complete details, send name, address and zip code to.

LAKESIDE INDUSTRIES

3520 W. Fullerton Ave., Chicago, IL 60647
 Phone 312-342-3399

OLD SAMs, #300 through 700. Will take \$500.00 for lot or will trade for NEW B & K Mod. 1077 analyst. Contact: **PYRAMID SERVICE CO., P.O. BOX 517, LORD-BURG, N. M. 88045; PH 505-542-8186.** 12/76

TV REPAIR HINTS. Send make and model with symptoms. (State if TV Tech.) \$2.00 plus stamp. Charles TV, 2033 McGraw Ave., New York, NY 10462. 12/76

TV & RADIO TUBES .36¢ EA!! Send for free color parts catalog. Your order free if not shipped in 24 hours. Cornell Electronics 4215-17 University San Diego California 92105. TF

Alarm Systems

BURGLAR ALARM DIALING UNIT automatically calls police. Easy to program and easy to install. Immediate delivery \$29.95. Free literature. S&S Systems, 5619-E St. John, Kansas City, Mo. 64123 (816) 483-4612. 12/76

ALARM EQUIPMENT FOR SALE: High Quality Professional Equipment at Low Prices. Industrial, Commercial, Residential and Auto. Write for Free Literature. B. Johnson Alarm Co., 180 Prospect St., East Orange, NJ 07017. 4/77

Can anyone do what you do any better?

You're pretty darn good at your job. But today, we all have to consider how we can do our work a little better. That's how each of us can help keep our jobs here in America.

For now and for the future.

America. It only works as well as we do.



The National Commission on Productivity, Washington, D.C.

SEND FOR

FREE CATALOG WITH ALMOST 3000 ITEMS

INCLUDING
B&K, EICO, RCA,
FLUKE, SENCORE,
SIMPSON, HICKOK
and LEADER

plus a complete line
of tubes, tools and
electronic supplies
at prices you won't
believe.


FORDHAM

RADIO SUPPLY CO., INC.

855R Conklin St., Farmingdale, N.Y. 11735
Tel. (516) 752-0050

...for more details circle 114 on Reader Service Card

NEW! CB WINDOW ANTENNA MOUNT

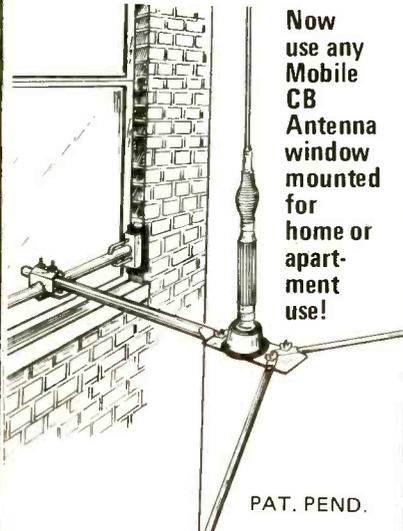

Now
use any
Mobile
CB
Antenna
window
mounted
for
home or
apart-
ment
use!

Simple assembly and installation. Adjustable extension fits windows up to 42". Additional extensions available for larger windows. For vertical or horizontal mount. Has ground plane elements similar to larger CB base station antennas. Self grounding. Sturdy, heavy duty all aluminum weather-proof elements and steel mounting bracket and hardware. **MODEL #CBWM-50**
RMS ELECTRONICS, INC.
50 Antin Place, Bronx, N.Y., 10462
Tel. (212) 892-6700

...for more details circle 122 on Reader Service Card

READER SERVICE INDEX

ADVERTISER'S INDEX

- 105 American Technology Corp. 47
- 106 Antenna, Inc. 25
- 107 Avanti Research & Devel., Inc. 50
- 108 B & K Div., Dynascan 41
- 109 Chemtronics, Inc. 46
- 110 Cornell Electronics 46
- 111 Dana Laboratories, Inc. 46
- 112 Edison Electronics Div. 21
- 113 Eico Electronic Instruments Co. 43
- 125 Electronic Book Club 32-35
- 114 Fordham Radio Supply Co., Inc. 50
- 115 Ford Motor Co. 15
- GC Electronics Co. 26
- GTE Sylvania, Consumer Renewal Cover 3, 3
- 126 Hunter Tools 43
- 116 Jerrold Electronics Corp. 9
- 117 Lampkin Laboratories Inc. 42
- 118 MTI 44
- Motorola Semiconductor Prdts., Inc. 7
- 120 Mountain West Alarm Supply Co. 47
- 102 PTS Electronics, Inc. Cover 2, 1
- 121 Pomona Electronics 30
- 122 RMS Electronics, Inc. 50
- 123 Sencore, Inc. 4, 5
- 103 Triplet Corp. (for information) Cover 4
- 104 Triplet Corp. (for demonstration) Cover 4
- 124 Wahl Clipper Corp. 45

This index is furnished for the readers' convenience. However, the publisher can not guarantee its accuracy due to circumstances beyond our control.

avanti SOLVES TV INTERFERENCE

Interference between television and CB radio is an annoying and not uncommon problem. Avanti solves these problems with 3 line filters...



AV 800 TV interference filter (low pass) installs in CB antenna line and is especially useful for interference on CH2 and 5 of poorly filtered TV receivers.
impedance = OHMS
line loss = negligible
VWSR = 1.1:1
attenuation on CH2 (54 MHz) = 80db.
1000 watt capacity
3db cutoff frequency = 43 MHz



AV 811 TV interference filter (hi-pass) installs in TV antenna line and supplements inadequate TV filtering to prevent interference between TV or FM and CB or other high frequency radio services.
impedance = 300 OHMS
line loss = negligible
VSWR = 1.1:1
cutoff frequency = 54 MHz



AV 820 A.C. line filter prevents transmission of CB signal through AC power lines. Suitable to contain signal at C.B. transceiver or to prevent outside signal from entering TV through AC line. 1200 watt capacity.

Avanti makes a complete line of high performance mobile and base CB antennas from \$11.95 to \$373.95

Free 24 page color catalog.

avanti

RESEARCH AND DEVELOPMENT, INC.
340 Stewart Avenue, Addison, IL 60101

Creators of the famous



...for more details circle 107 on Reader Service Card

COMPLETE MANUFACTURER'S CIRCUIT DIAGRAMS
AND TECHNICAL INFORMATION FOR 5 NEW SETS



SCHEMATIC NO.	SCHEMATIC NO.
GENERAL ELECTRIC VIR Module (Employed in some color TV models equipped with YM and YC-2 TV chassis).....1670	RCA B/W TV Chassis KCS201T/U.....1674
QUASAR Color TV Chassis TS-958.....1671	ZENITH Color TV Chassis 23HC45.....1673
QUASAR Color TV Chassis TS-959.....1672	

ADJUSTMENTS

(Set Must Be Receiving a VIR Signal)

COLOR PREFERENCE — With the VIR SWITCH ON, adjust the COLOR PREFERENCE CONTROL for desired color amplitude.


TINT PREFERENCE — With the VIR SWITCH ON, adjust the TINT PREFERENCE CONTROL for desired color fleshtones.

COLOR SET UP (R82) — (NORMALLY FACTORY PRE-SET.) With the VIR SWITCH ON and COLOR PREFERENCE set to midrange adjust for desired color amplitude.


NOTE: If set too high chroma level will not track properly with Custom Picture Control.

TINT SET UP (R45) — (NORMALLY FACTORY PRE-SET.) With the VIR SWITCH ON and TINT PREFERENCE set to midrange adjust for desired color fleshtones.

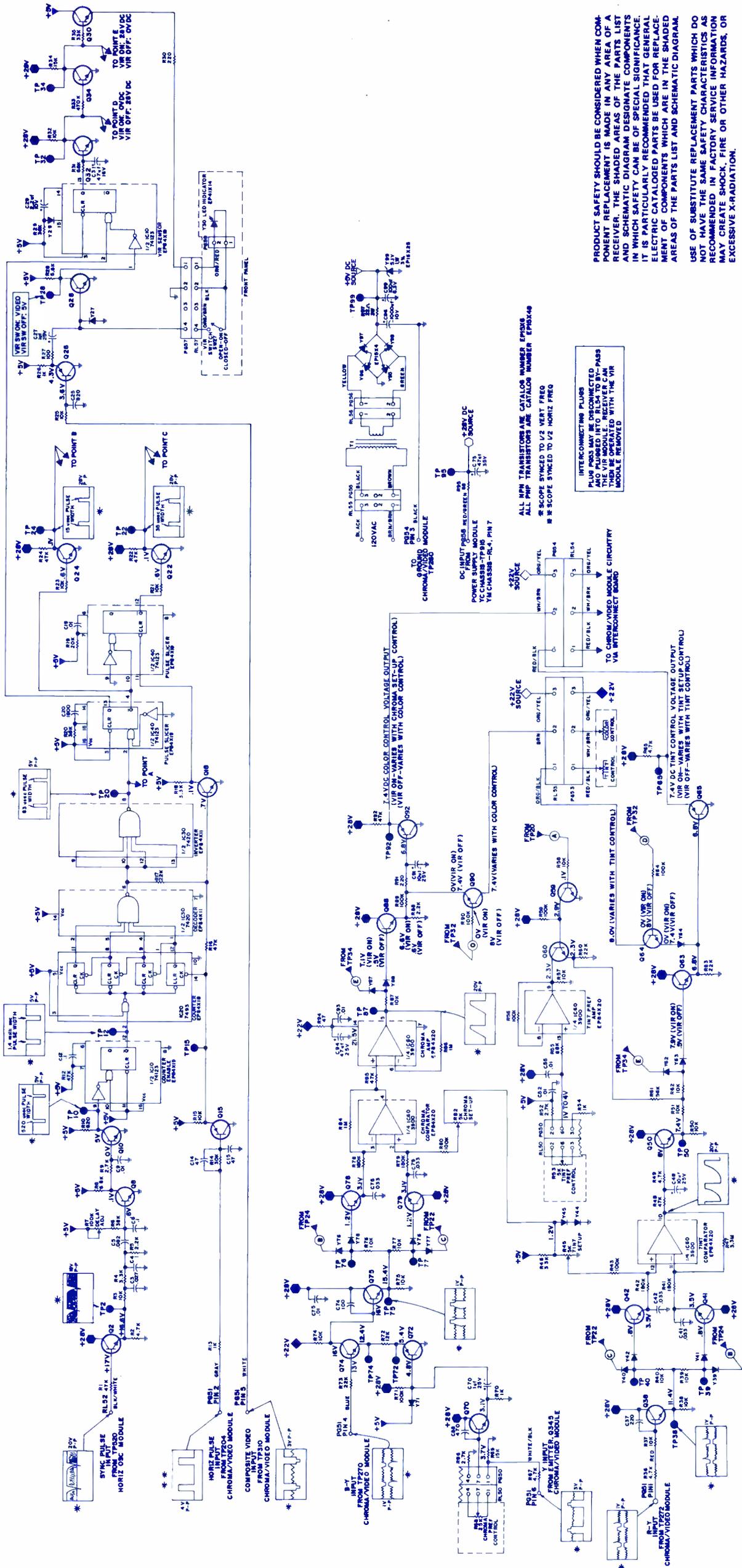
DELAY (R7) — (NORMALLY FACTORY PRE-SET.) With the VIR SWITCH ON, set the DELAY ADJUSTMENT to midrange position, "rock" the control around the center position until proper automatic operation is achieved.



PRODUCT SAFETY SHOULD BE CONSIDERED WHEN COMPONENT REPLACEMENT IS MADE IN ANY AREA OF A RECEIVER. THE SHADED AREAS OF THE PARTS LIST AND SCHEMATIC DIAGRAM DESIGNATE COMPONENTS IN WHICH SAFETY CAN BE OF SPECIAL SIGNIFICANCE. IT IS PARTICULARLY RECOMMENDED THAT GENERAL ELECTRIC CATALOGED PARTS BE USED FOR REPLACEMENT OF COMPONENTS WHICH ARE IN THE SHADED AREAS OF THE PARTS LIST AND SCHEMATIC DIAGRAM. USE OF SUBSTITUTE REPLACEMENT PARTS WHICH DO NOT HAVE THE SAME SAFETY CHARACTERISTICS AS RECOMMENDED IN FACTORY SERVICE INFORMATION MAY CREATE SHOCK, FIRE OR OTHER HAZARDS, OR EXCESSIVE X-RADIATION.

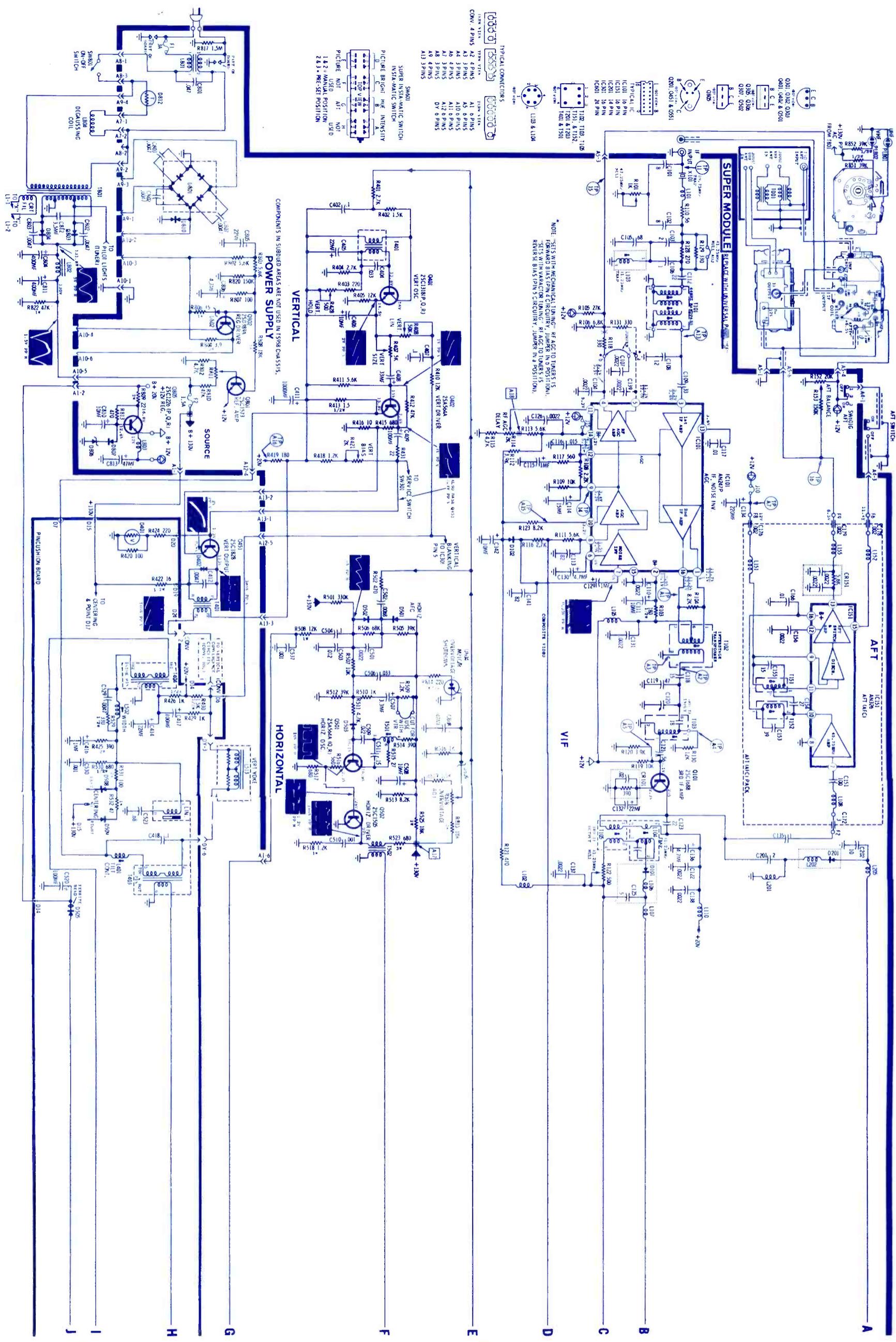

QUASAR
Color TV Chassis
TS-958

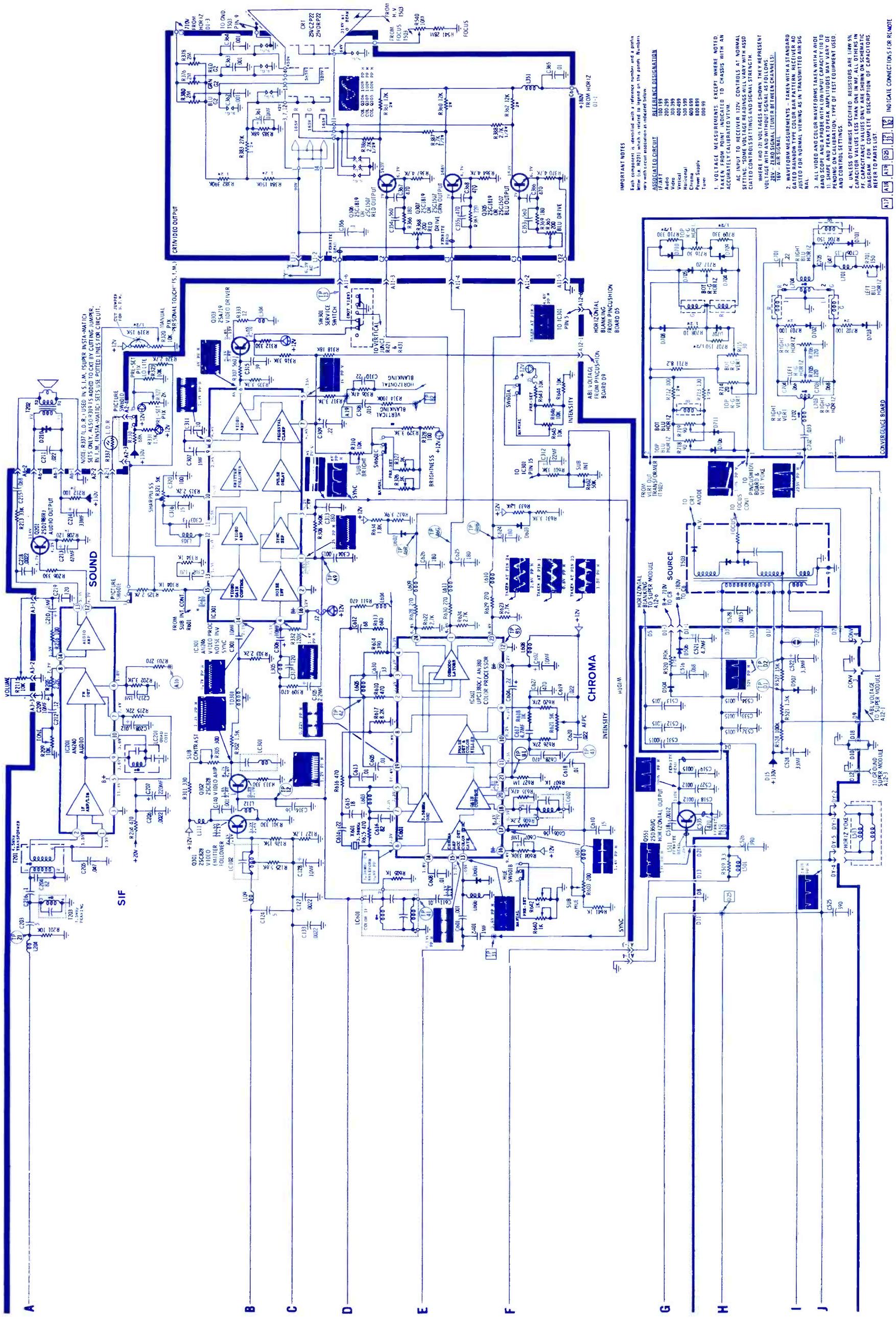

IMPORTANT NOTES
Each component is identified with a reference number and a prefix letter. The reference number is the primary identifier, and the prefix letter indicates the location of the component within the chassis.

ASSOCIATED CIRCUIT
100-199 Video
200-299 Audio
300-399 Sync
400-499 Chroma
500-599 Horizontal
600-699 Vertical
700-799 Power Supply
800-899 Tuner

REFERENCE DESIGNATION
RESISTOR
CAPACITOR
TRANSISTOR
DIODE
TUBE
RELAY
SWITCH
CONNECTOR
CIRCUIT BOARD
CIRCUIT BOARD ASSEMBLY
CIRCUIT BOARD SUB-ASSEMBLY
CIRCUIT BOARD MODULE
CIRCUIT BOARD SUB-MODULE
CIRCUIT BOARD COMPONENT

1. VOLTAGE MEASUREMENTS - EXCEPT WHERE NOTED, TAKEN FROM POINT INDICATED TO CHASSIS WITH AN AC INPUT TO RECEIVER 120V. CONTROLS AT NORMAL SET POINTS. ALL VOLTAGES ARE SHOWN IN RMS UNLESS OTHERWISE SPECIFIED. SIGNAL STRENGTH, GATED CONTROL SETTINGS AND SIGNAL SETTINGS ARE SHOWN IN VOLTAGES WITH AND WITHOUT SIGNAL AS FOLLOWS:
120V - ZERO SIGNAL (TUNER BETWEEN CHANNELS)
15V - AIR SIGNAL


2. WAVEFORM MEASUREMENTS - TAKEN WITH A STANDARD GATED PULSE GENERATOR. COLOR AND BRIGHTNESS MEASUREMENTS FOR NORMAL VIEWING AS IN TRANSMITTER AIR SIG.

3. ALL VIDEO AND COLOR WAVEFORMS TAKEN WITH A WIDE BAND SCOPE AND A PROBE WITH LOW INPUT CAPACITY (10 TO 20 PF). SHARP AND PEAK TO PEAK AMPLITUDES MAY VARY DEPENDENT ON THE TYPE OF TEST EQUIPMENT USED.

4. ALL CAPACITANCE SPECIFIED - RESISTORS ARE 1/4W 5% UNLESS OTHERWISE SPECIFIED. CAPACITORS ARE 50V UNLESS OTHERWISE SPECIFIED. CAPACITANCE VALUES ONLY ARE SHOWN ON SCHEMATIC DIAGRAM FOR COMPLETE DESCRIPTION OF CAPACITORS REFER TO PARTS LIST.

17 **18** **19** **20** **21** **22** **23** **24** **25** **26** **27** **28** **29** **30** **31** **32** **33** **34** **35** **36** **37** **38** **39** **40** **41** **42** **43** **44** **45** **46** **47** **48** **49** **50** **51** **52** **53** **54** **55** **56** **57** **58** **59** **60** **61** **62** **63** **64** **65** **66** **67** **68** **69** **70** **71** **72** **73** **74** **75** **76** **77** **78** **79** **80** **81** **82** **83** **84** **85** **86** **87** **88** **89** **90** **91** **92** **93** **94** **95** **96** **97** **98** **99** **100**

QUASAR
Color TV Chassis
TS-959

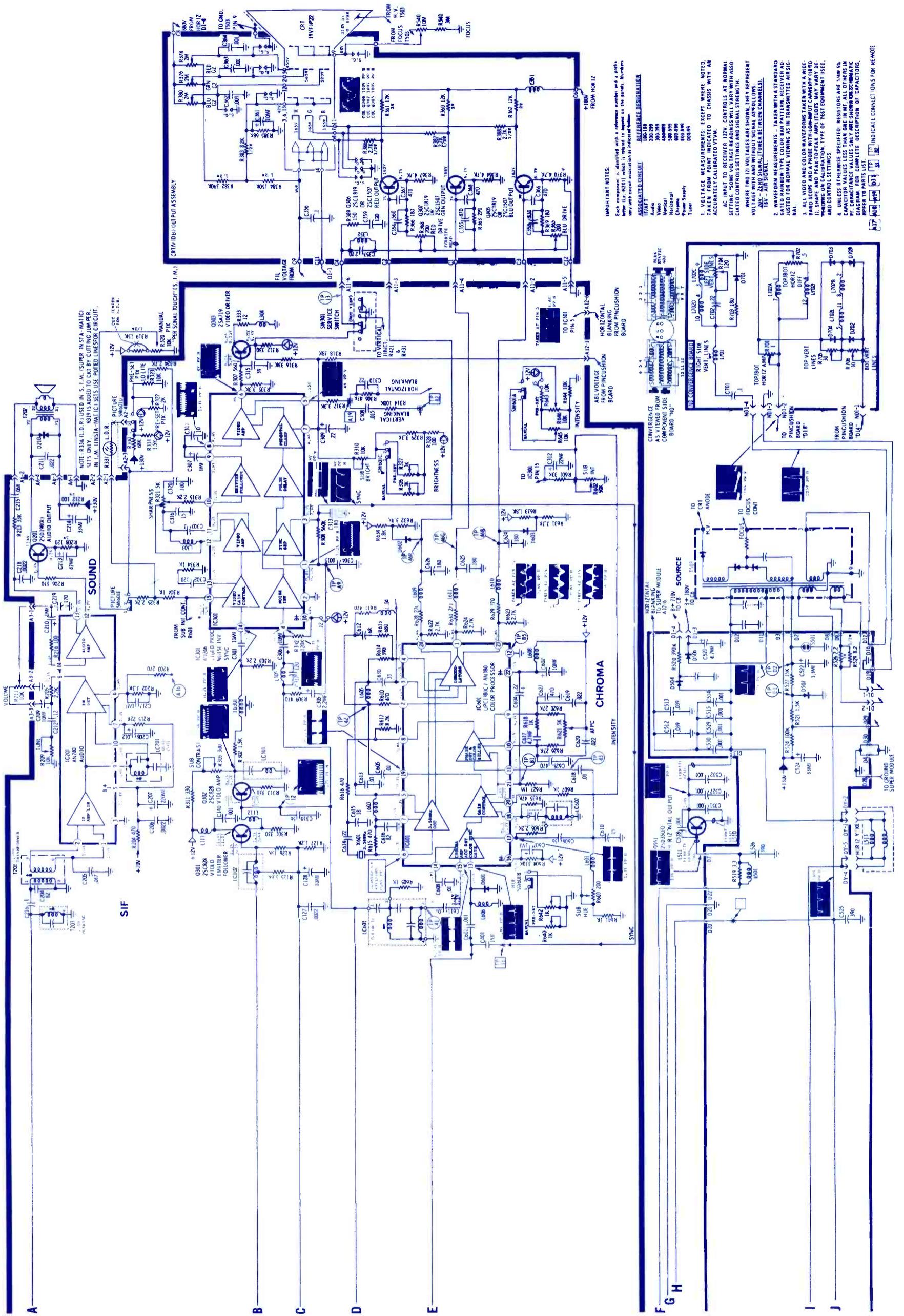


IMPORTANT NOTES:
Each component is identified with a reference number and a prefix letter (e.g., R201) which is related to the panel, numbers vary with certain variations of indicated equipment.

ASSOCIATED SUBCIRCUITS






100-100	Power Supply
100-101	Tuner
100-102	Video
100-103	Audio
100-104	Picture Control
100-105	Color Control
100-106	Color Processor
100-107	Color Burst
100-108	Color Processor
100-109	Color Processor
100-110	Color Processor

1. VOLTAGE MEASUREMENTS: EXCEPT WHERE NOTED, TAKEN FROM POINT INDICATED TO CHASSIS WITH AN ACCURATELY CALIBRATED VTVM.
2. WAVEFORM MEASUREMENTS: TAKEN WITH A STANDARD GATED RAINBOW-TYPE COLOR BAR PATTERN. RECEIVER ADJUSTED FOR NORMAL VIEWING AS IN TRANSMITTED AIR SIG. WALL.
3. ALL VIDEO AND COLOR WAVEFORMS TAKEN WITH A WIDE BAND SCOPE AND A PROBE. WAVEFORMS MAY VARY TO SOME EXTENT WITH DIFFERENT TYPES OF TEST EQUIPMENT USED.
4. UNLESS OTHERWISE SPECIFIED, RESISTORS ARE 1/4W 5% CAPACITANCE VALUES LESS THAN ONE IN MF. ALL OTHERS IN CAPACITANCE VALUES ONLY. SHOWN IN MICROFARADS. REFER TO PARTS LIST FOR COMPLETE DESCRIPTION OF CAPACITORS.

INDICATE CONNECTIONS FOR REMOTE

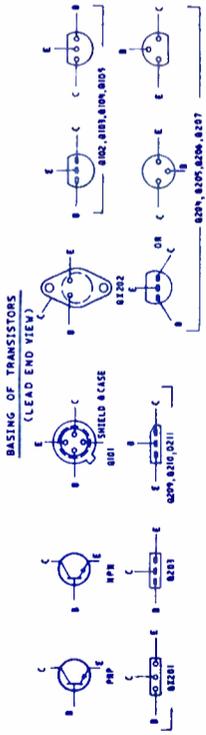

MODULES USED	ALTERNATES	DESCRIPTION
9-86-02		CHROMA
9-87C	9-87, -87A	AGC
9-88-03		LOW LEVEL LUM
9-89F	9-89E, -89-01C	VIDEO OUTPUT
9-90-01B		HORIZ
9-147A	9-147, -928, -92C	VERT
9-103-01		AUDIO
9-123-01		POWER SUPPLY
9-126-01		ZOOM
150-190D		VIDEO I.F.

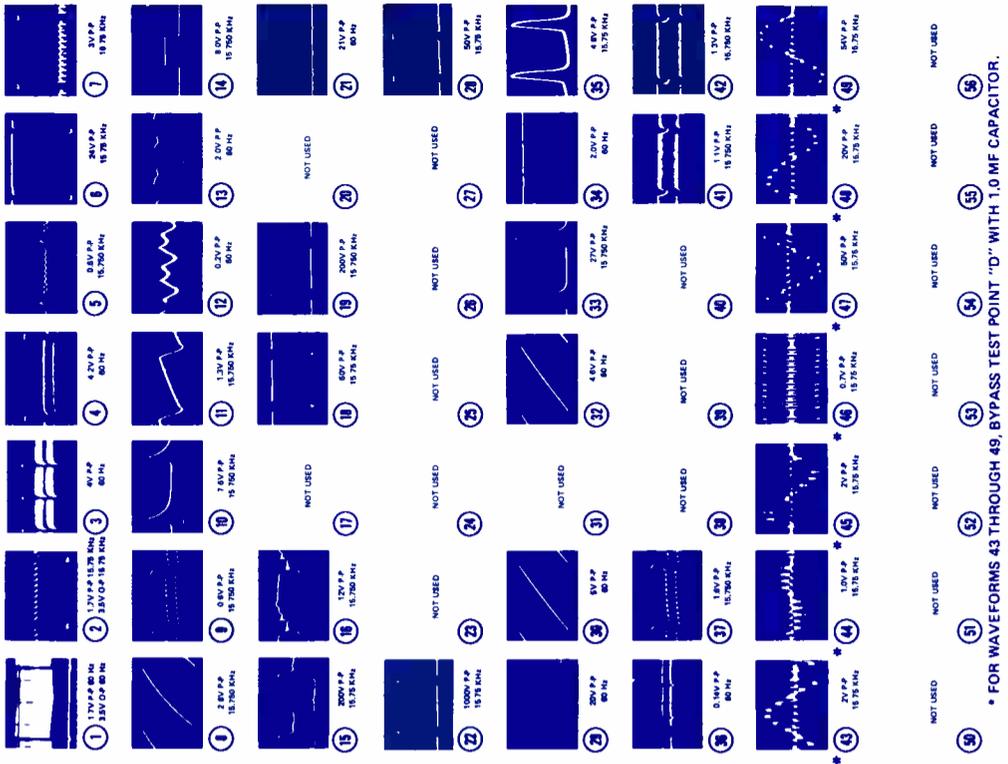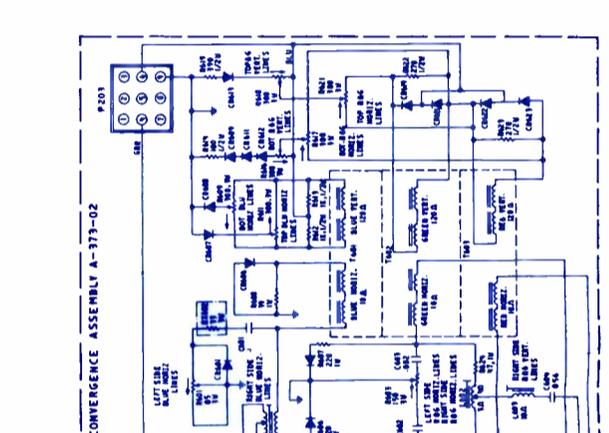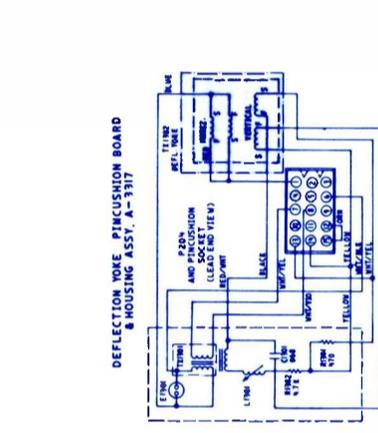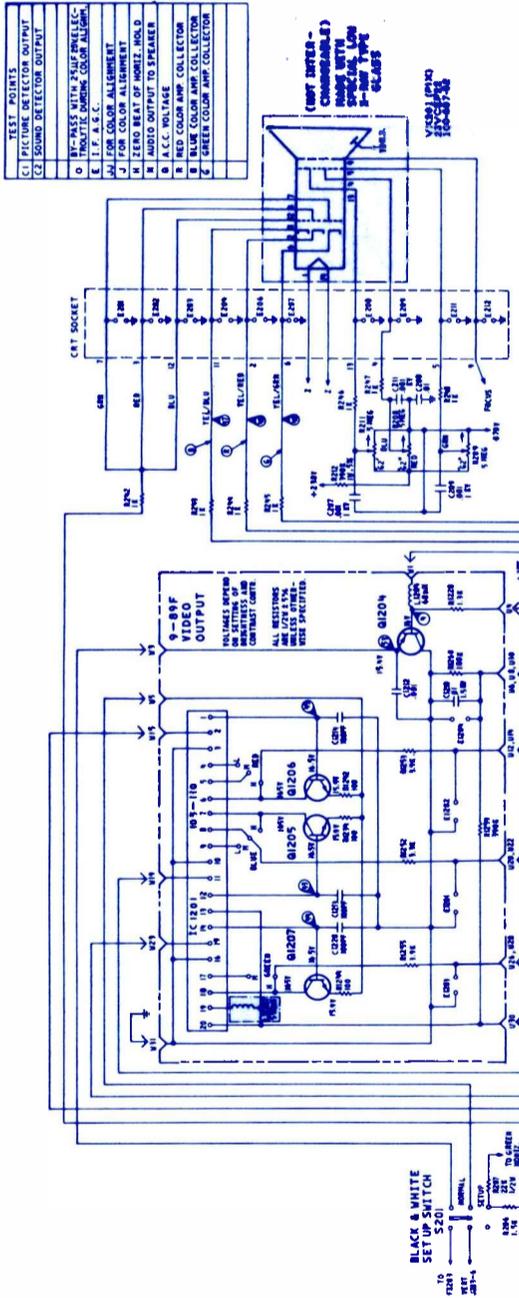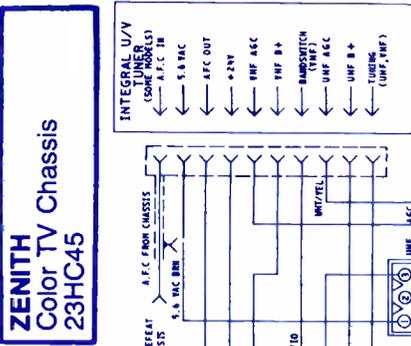

* FOR WAVEFORMS 43 THROUGH 49, BYPASS TEST POINT "D" WITH 1.0 MF CAPACITOR.



What d'ya mean, you can't fix CBs?

Introducing the Sylvania ECG™ CB10-4 service kit.
26 semiconductors that can turn CB problems into profits.

Until now, the toughest problem in handling CB repair jobs was getting the right replacement part.

Now, we've put the solution to 1,047 of these parts problems in one kit that will fit right on your bench.

The CB10-4 kit has 23 transistors and 3 integrated circuits that are the most frequently needed replacements in transceivers and other CB equipment. And the interchangeability

guide that comes with the kit tells you the right ones to use as replacements. With the CB10-4 most of your parts needs are right at your fingertips. And you can get the others in the same place you bought the kit—at your Sylvania distributor.



We're helping you make it.

GTE SYLVANIA

The easy-to-read 630 makes learning easy.

The Model 630 V-O-M is priced at a thrifty \$78.

The rugged, general purpose Triplet Model 630 is the kind of dependable V-O-M that both teachers and students appreciate. And for the same reasons the electronic and electrical maintenance professionals do. Uncompromising accuracy. Sturdy lightweight (only 3 lbs. with batteries). Simplified single switch operation holds errors to a minimum, and diode overload protection for the meter suspension movement reduces the chance of tester damage when mistakes do occur.

With long, clean scales covering 27 ranges in only four arcs, the Triplet Model 630 is remarkably easy-to-read.

It's packed with major features:

1. Diode overload-protected suspension movement V-O-M; single range switch minimizes error.
2. 4 Ohmmeter range with 4.4 ohms center scale.
3. Simplified scale—only 4 arcs for all 27 ranges.

Sensitivity is 20,000 Ohms per Volt DC, 5000 Ohms per Volt AC.

Accuracy is an excellent 2% on DC, and 3% on AC. Measures resistance to 100 megohms, with 6,000 Volt AC and DC capability.

Handles DC microamperes 0-60, and DC milliamperes 0-120, both at 250 mV, and can read DC amperes 0-12.

Rugged black molded plastic case with removable black leather carrying strap. All this for just \$78.

Get the same convenience and operating advantages plus 1½% DC accuracy and mirrored scale with the Triplet Model 630-A, priced at only \$90.

See them for yourself. Just ask a Triplet distributor or sales represen-

tative to give you a free demonstration of the tester that fits your needs. You'll be glad you did. So, do it today. Triplet Corporation, Bluffton, Ohio 45817.

TRIPLET
ALL YOU'LL EVER NEED IN V-O-M's.



Triplet. The easy readers.

...for more details circle 103 on Reader Service Card
...for FREE demonstration circle 104 on Reader Service Card