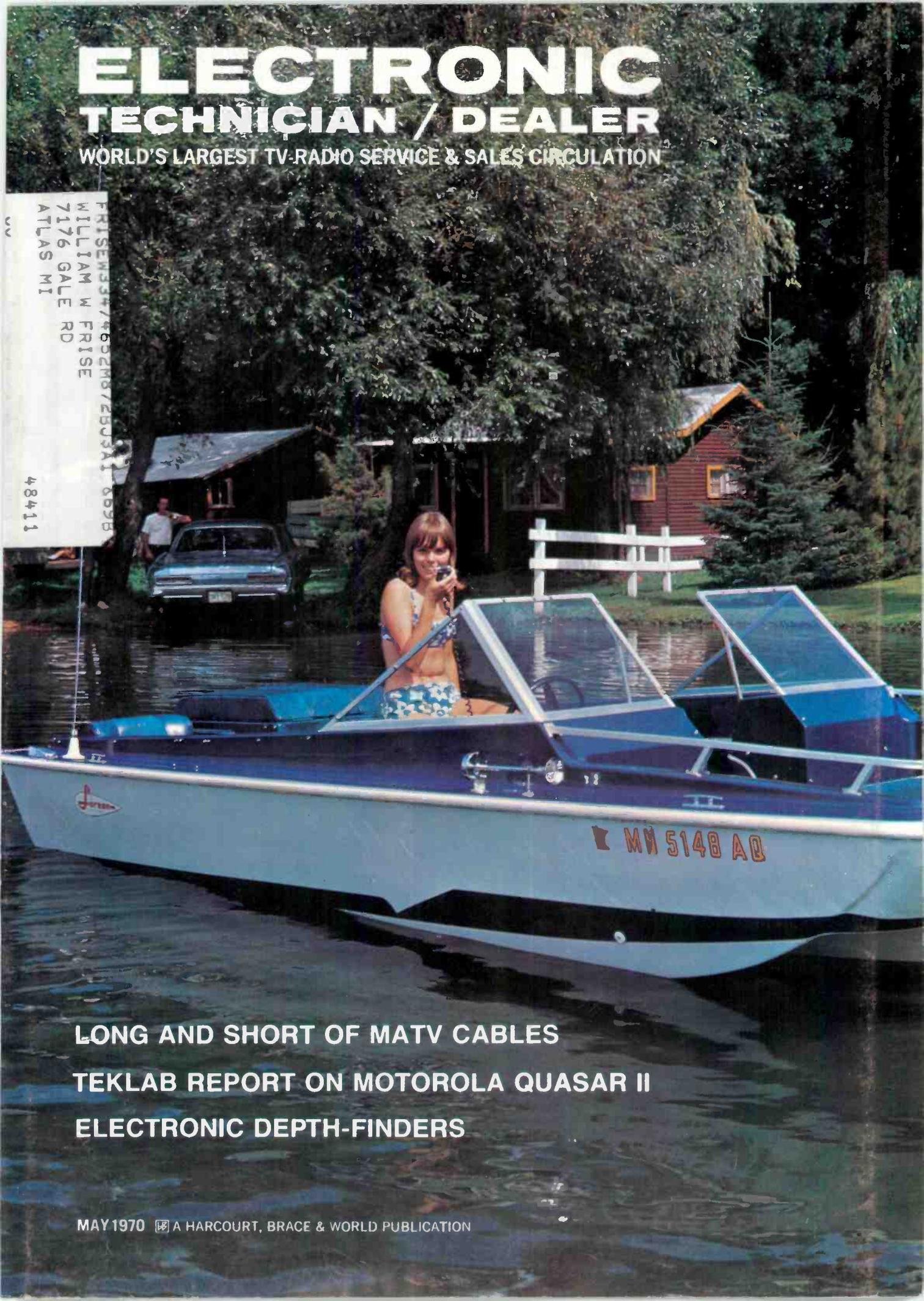


ELECTRONIC TECHNICIAN / DEALER

WORLD'S LARGEST TV-RADIO SERVICE & SALES CIRCULATION

FRISEM33474692M87EB03A1 699B
WILLIAM W FRISE
7176 GALE RD
ATLAS MI
48411



LONG AND SHORT OF MATV CABLES

TEKLAB REPORT ON MOTOROLA QUASAR II

ELECTRONIC DEPTH-FINDERS

The big difference in TV Alignment instruments: Ours Works.

The B & K Model 415 Sweep/Marker Generator not only works, but it makes alignment jobs faster and more accurate.

Why? Because it eliminates the need for a separate marker generator, sweep generator, marker adder, and bias supply. You get it all in one compact instrument.


And it's so easy to use. The IF and chroma bandpasses are simulated on the front panel for constant reference. Lights tell you which of the crystal-controlled markers are in use and where they should be located. And the exclusive marker tilt feature lets you place the markers either horizontally or vertically, so you can always identify their exact positions.

Put the B & K Model 415 Sweep/Marker Generator to work for you.

Ask your distributor for complete details.



Product of
DYNASCAN CORPORATION
1801 W. Belle Plaine
Chicago, Illinois 60613

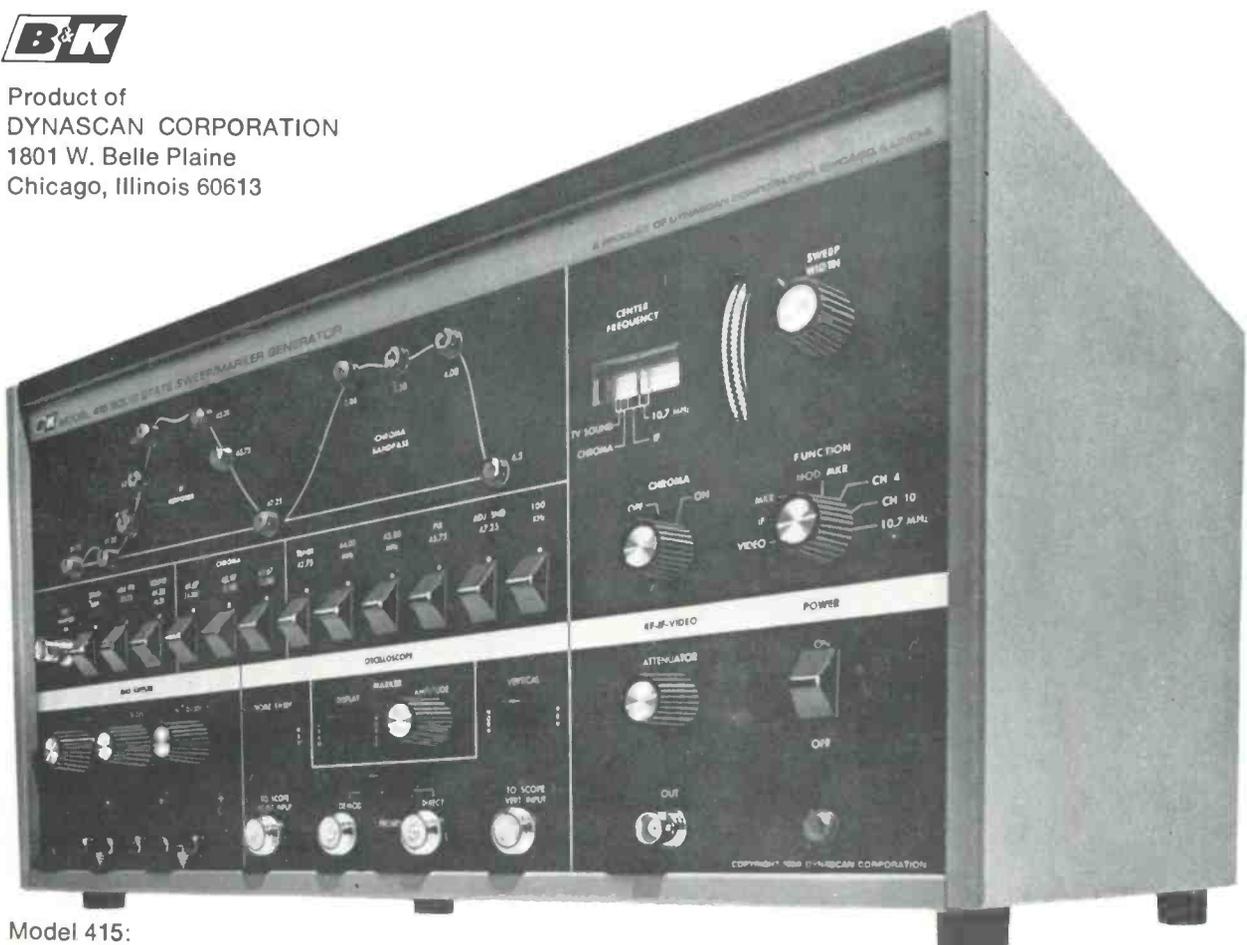

Model 415:
\$399.95


TEKFAX

COMPLETE MANUFACTURERS' CIRCUIT DIAGRAMS
AND TECHNICAL INFORMATION FOR 6 NEW SETS


GROUP
213

SCHEMATIC NO.	SCHEMATIC NO.
ADMIRAL.....1294 TV Chassis T3K3-1A, T3K3-1B	MOTOROLA.....1296 Color TV Chassis TS-934
AIRLINE.....1295 Color TV Models GC1-12420A,B	MOTOROLA.....1298 TV Chassis TS-599
MAGNAVOX.....1297 TV Chassis T948	PHILCO-FORD.....1299 TV Chassis 20P22

SYMBOL	DESCRIPTION	ADMIRAL PART NO.
R151	—15K 2w	60820-153
R208	—1M, vol control w/sw	75C1-176
R311	—30K contrast control	75C112-13
R313	—100K, bright control	75C113-13
R411	—5M height triple control	75C129-3
R417	—1.2M, vert hold triple control	75C129-3
R421	—500K, vert lin triple control	75C129-3
R501	—5.5Ω, fusible resistor	61C48-1
R502	—330Ω 5w	61C20-66
R503	—80Ω 5w	61C20-101
C203	—47pf 500v NPO cer disc	65D10-198
C204	—82pf 5% 500v NPO cer disc	65D10-98
C301	—10pf 10% 500v NPO cer disc	65D10-87
C307,308	—6.8pf 10% 500v NPO cer disc	65D10-102
C428	—82pf 10% 4kv N1500 cer disc	65D10-425
C503A	—250μf 165v elect	67C30-11
C503B	—150μf 150v elect	67C30-11
C503C	—200μf 150v elect	67C30-11
L201A,B	—sound IF & phase shift coil	72C301-4
L202	—ratio det.	72C132-82
L303	—5.6 UL RF choke	73C53-243
L304	—RF choke	73C31-3
L307	—video peaking	73D55-26
L401	—horiz lock coil	94D17-19
L402	—RF choke	73C31-11
T201	—audio output xfmr	79C124-3
T301	—1st IF xfmr	72C308-2
T303	—sound take off coil	72C185-7
T401	—vert output xfmr	79C139-2
T402	—def yoke ass'y	700C1089-6
T403	—horiz output	79D138-4
UHF tuner		94D361-2
VHF tuner		94D363-2

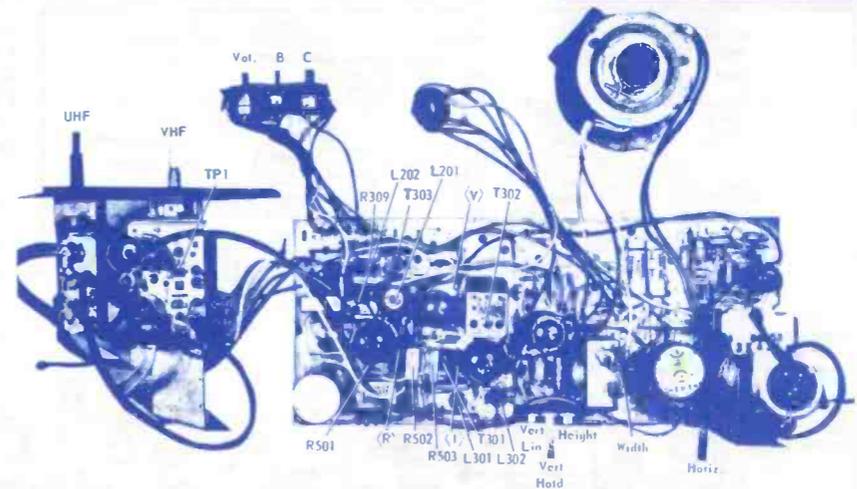


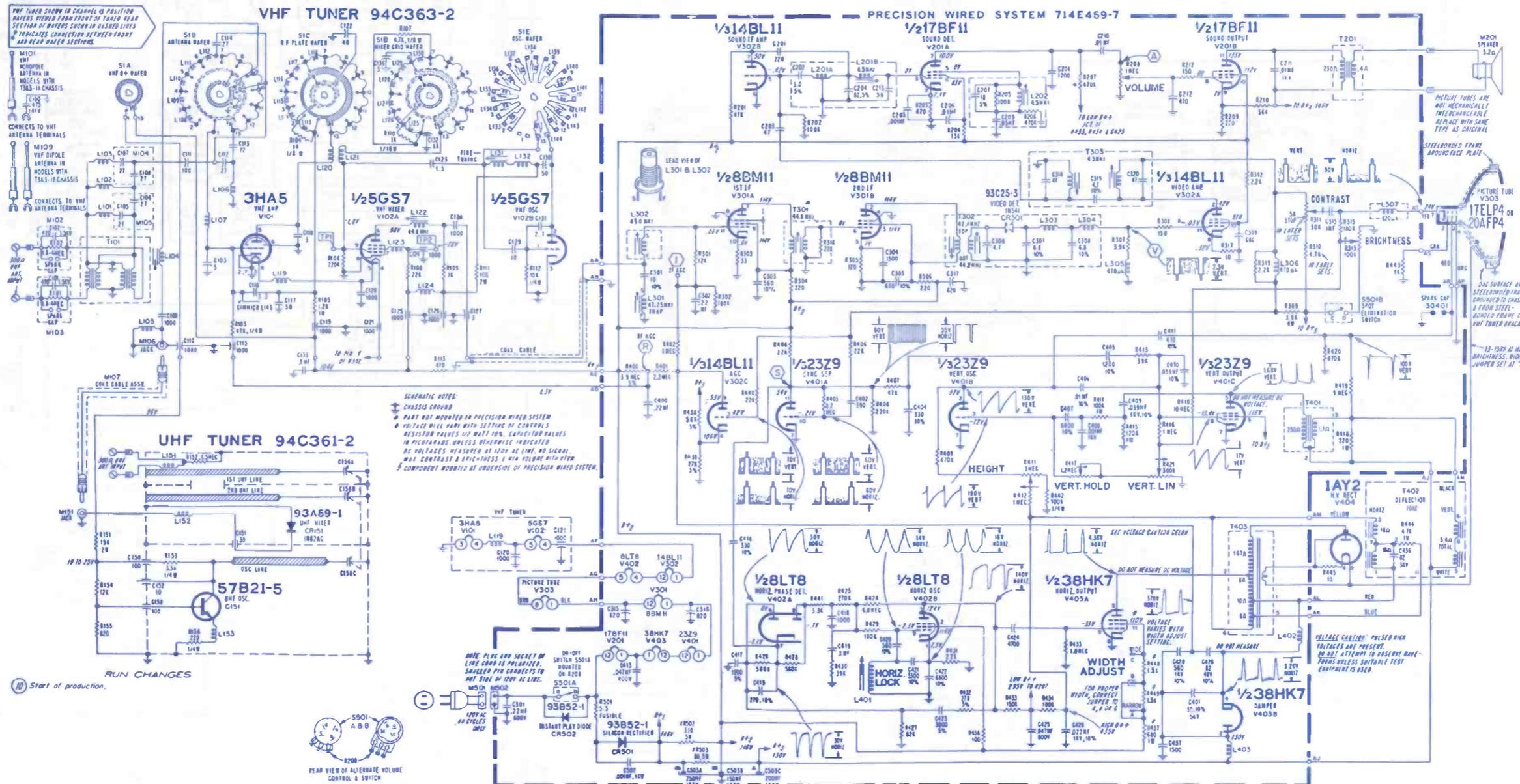
TOP VIEW OF CHASSIS SHOWING ALIGNMENT & SERVICE ADJUSTMENT LOCATIONS




1. ALL RESISTORS ARE 1/2 WATT, 10%, UNLESS OTHERWISE NOTED.
2. ALL CAPACITORS ARE IN MFD, UNLESS OTHERWISE NOTED.
3. CAUTION: USE ISOLATION TRANS WHEN WORKING ON CHASSIS.
4. DC VOLTAGES MEASURED WITH "VTVM" PLACED BETWEEN POINTS INDICATED & CHASSIS GND, WITH NORMAL SIGNAL INPUT
(*) INDICATES VOLTAGE READINGS TAKEN WITH BRIGHTNESS CONT. AT MAXIMUM ROTATION (FULLY CW).
(*) INDICATES VOLTAGE READINGS TAKEN WITH BRIGHTNESS CONT. AT MINIMUM ROTATION (FULLY CCW).
f INDICATES VOLTAGE READINGS TAKEN WITH COLOR SIGNAL.
5. WAVEFORMS ARE TAKEN WITH NORMAL SIGNAL INPUT.
6. LINE VOLTAGE INPUT SET AT 120 VAC.

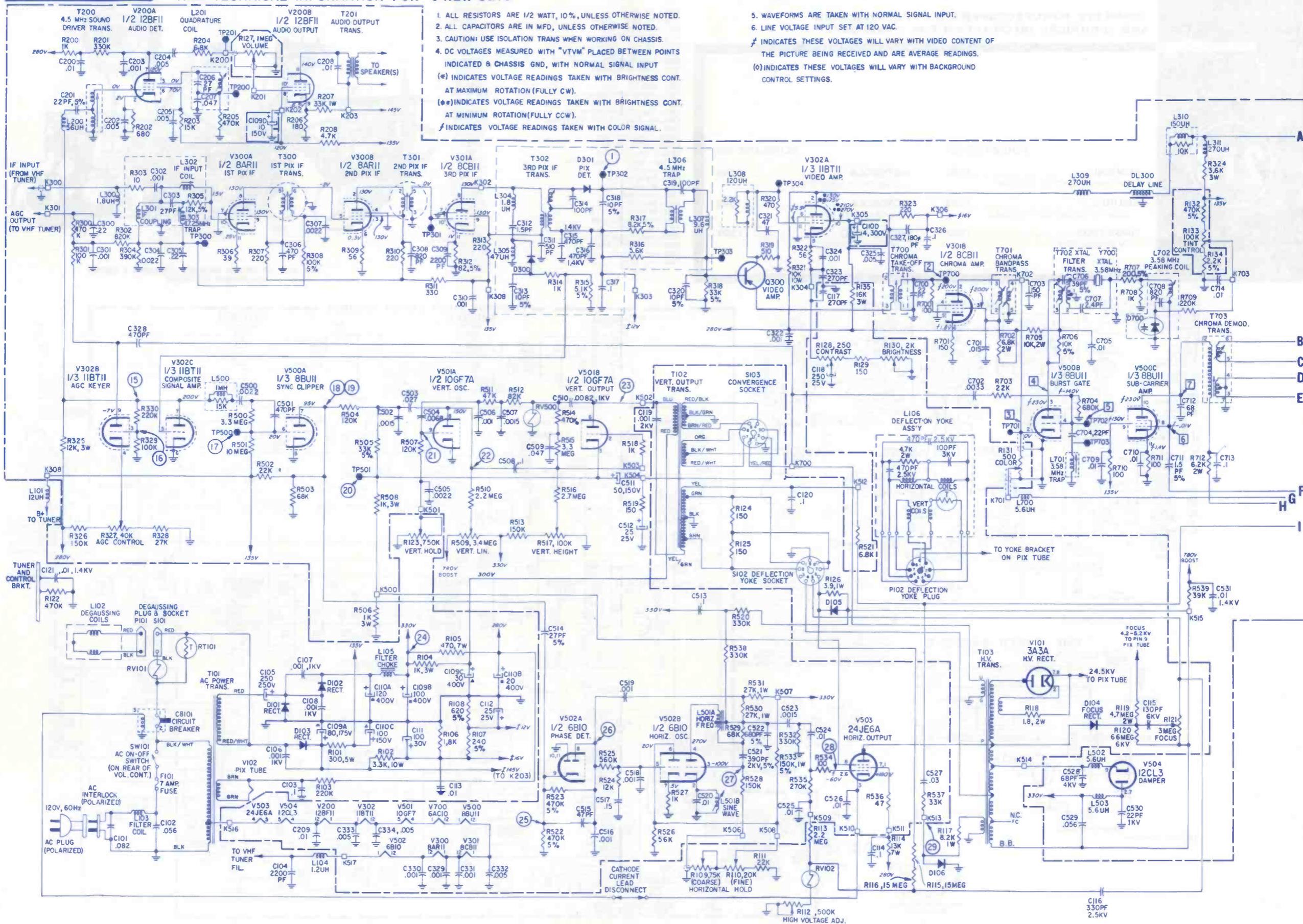7. (*) INDICATES THESE VOLTAGES WILL VARY WITH VIDEO CONTENT OF THE PICTURE BEING RECEIVED AND ARE AVERAGE READINGS.
8. (f) INDICATES THESE VOLTAGES WILL VARY WITH BACKGROUND CONTROL SETTINGS.



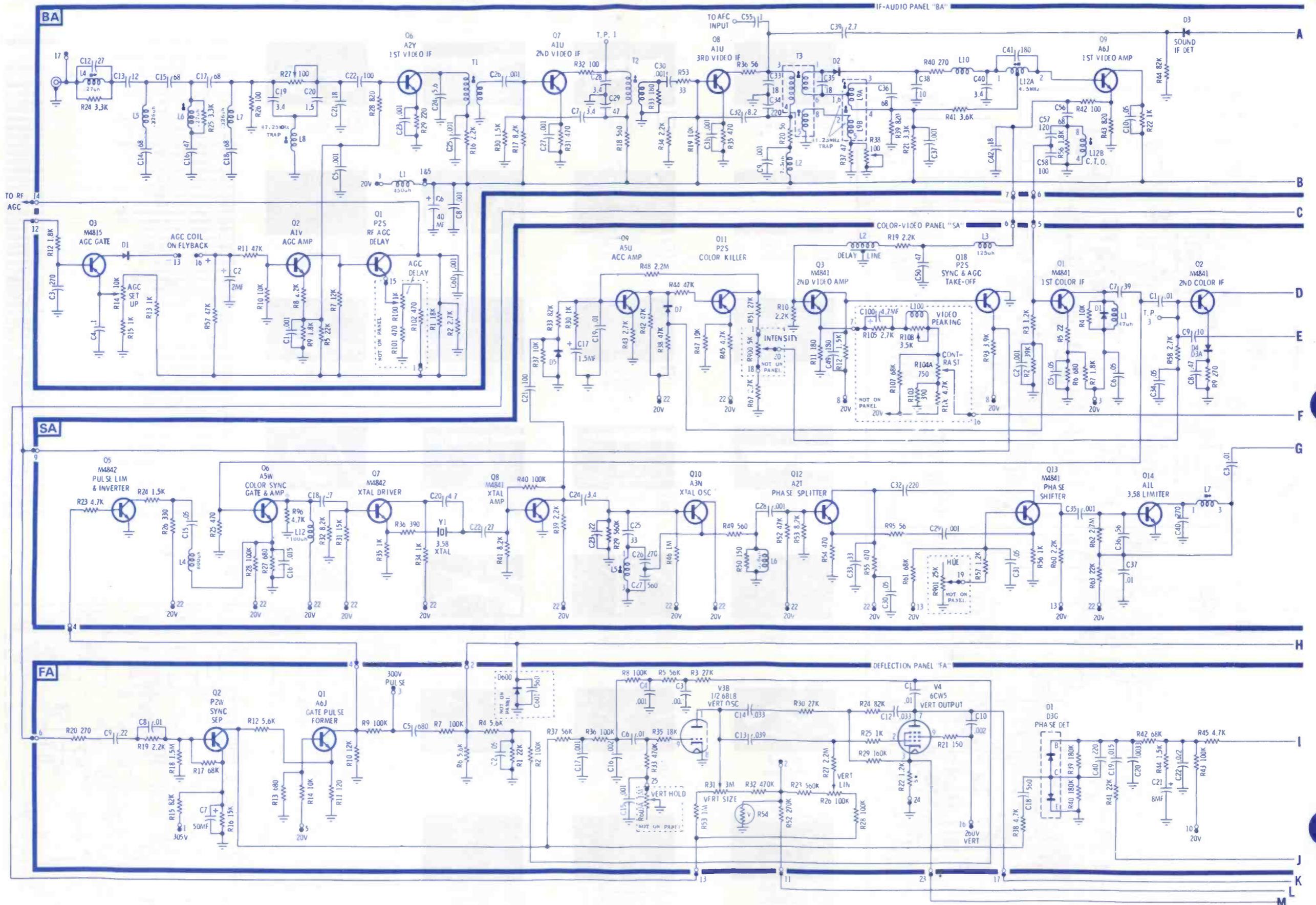

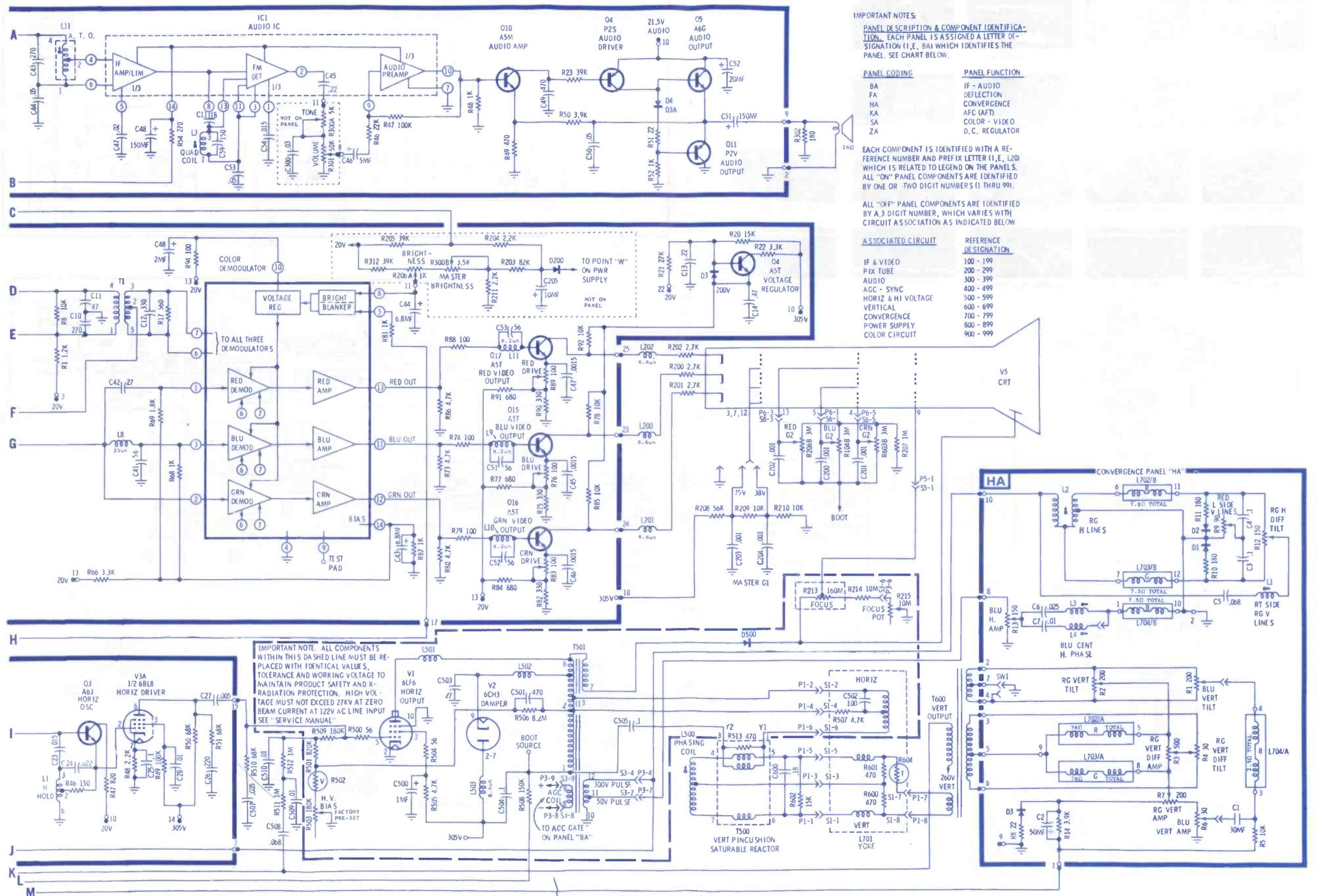




IMPORTANT NOTES:
PANEL DESCRIPTION & COMPONENT IDENTIFICATION. EACH PANEL IS ASSIGNED A LETTER DESIGNATION (I, E, BA) WHICH IDENTIFIES THE PANEL. SEE CHART BELOW.

PANEL CODING	PANEL FUNCTION
BA	IF - AUDIO
FA	DEFLECTION
HA	CONVERGENCE
KA	AFC (AFT)
SA	COLOR - VIDEO
ZA	D.C. REGULATOR

EACH COMPONENT IS IDENTIFIED WITH A REFERENCE NUMBER AND PREFIX LETTER (I, E, L20) WHICH IS RELATED TO LEGEND ON THE PANELS. ALL "ON" PANEL COMPONENTS ARE IDENTIFIED BY ONE OR TWO DIGIT NUMBERS (1 THRU 99). ALL "OFF" PANEL COMPONENTS ARE IDENTIFIED BY A 3 DIGIT NUMBER, WHICH VARIES WITH CIRCUIT ASSOCIATION AS INDICATED BELOW.

ASSOCIATED CIRCUIT	REFERENCE DESIGNATION
IF & VIDEO	100 - 199
PIX TUBE	200 - 299
AUDIO	300 - 399
AGC - SYNC	400 - 499
HORIZ & HI VOLTAGE	500 - 599
VERTICAL	600 - 699
CONVERGENCE	700 - 799
POWER SUPPLY	800 - 899
COLOR CIRCUIT	900 - 999

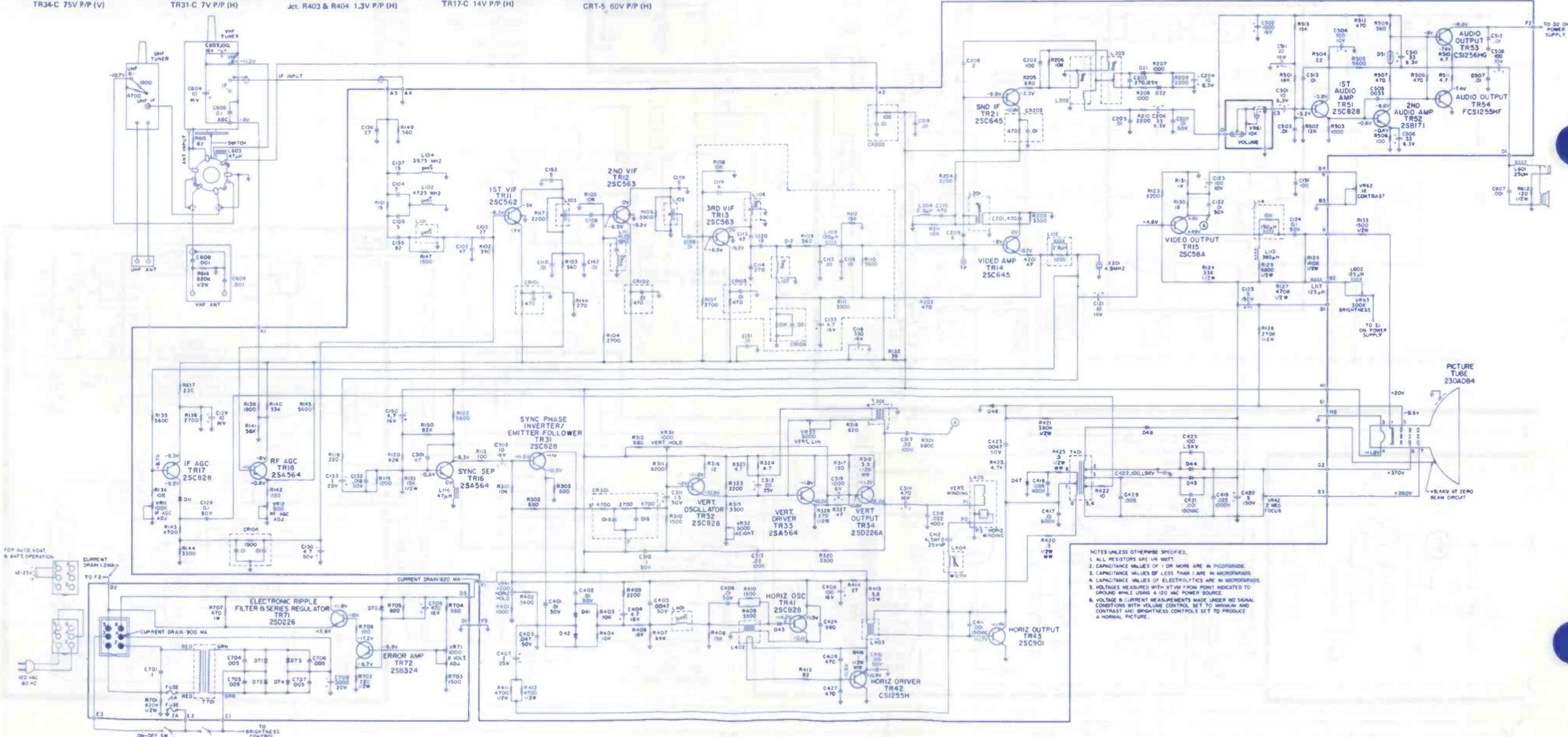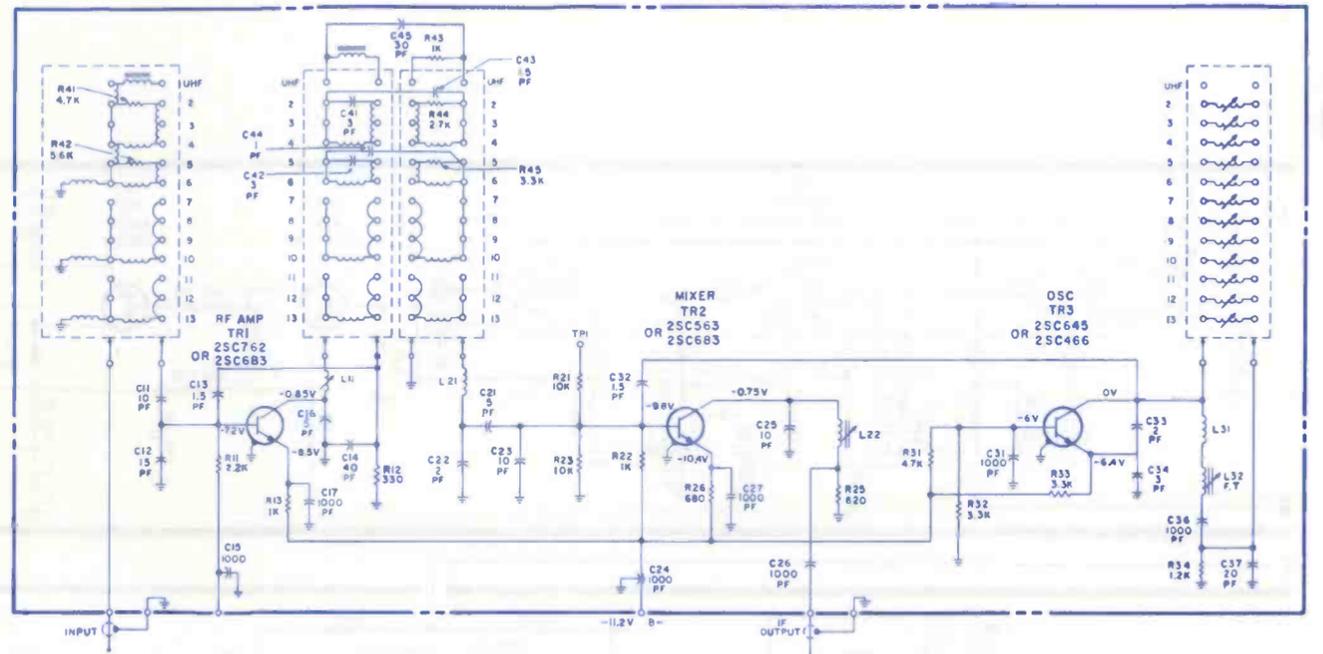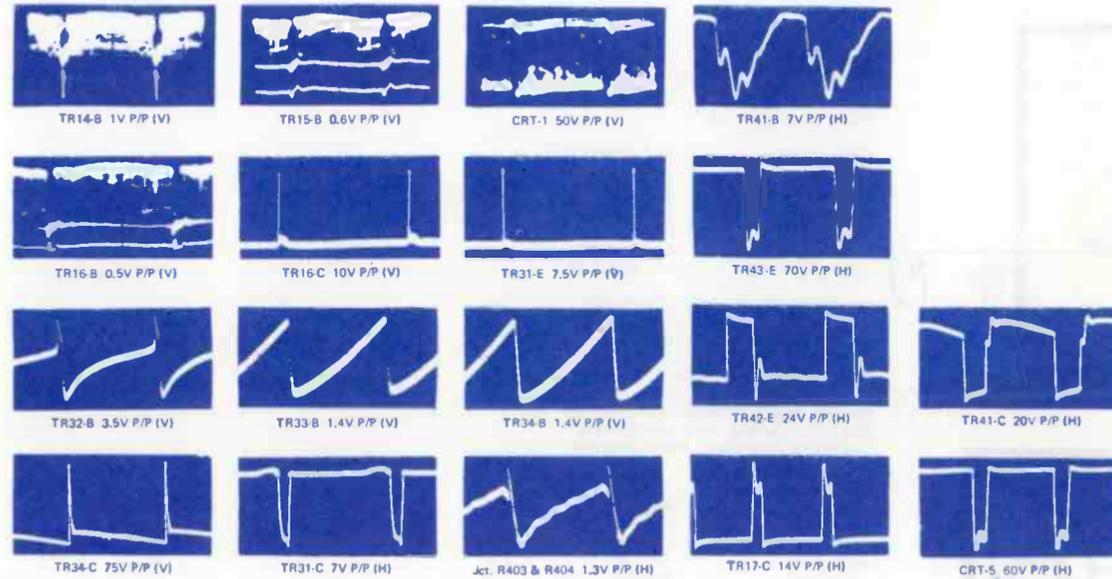IMPORTANT NOTE: ALL COMPONENTS WITHIN THIS DASHED LINE MUST BE REPLACED WITH IDENTICAL VALUES. TOLERANCE AND WORKING VOLTAGE TO MAINTAIN PRODUCT SAFETY AND X-RADIATION PROTECTION. HIGH VOLTAGE MUST NOT EXCEED 27KV AT ZERO BEAM CURRENT AT 122V AC LINE INPUT SEE "SERVICE MANUAL"




NOTES UNLESS OTHERWISE SPECIFIED:
 1. ALL RESISTORS ARE IN OHMS
 2. CAPACITANCE VALUES OF 1 OR MORE ARE IN MICROFARADS
 3. CAPACITANCE VALUES OF LESS THAN 1 ARE IN MICROFARADS
 4. CAPACITANCE VALUES OF ELECTROLYTICS ARE IN MICROFARADS
 5. VOLTAGES MEASURED WITH VTVM FROM POINT INDICATED TO GROUND WHILE USING A 120 VAC POWER SOURCE
 6. VOLTAGE & CURRENT MEASUREMENTS MADE UNDER NO SIGNAL CONDITIONS WITH VOLUME CONTROL SET TO MINIMUM AND CONTRAST AND BRIGHTNESS CONTROLS SET TO PRODUCE A NORMAL PICTURE.

SYMBOL	DESCRIPTION	MOTOROLA PART NO.
E300	integrated circuit: 11H rec silicon	
L104	choke, RF	24D65947A94
R113	video bias: 10K	18D66401A19
R128	optimizer: 1K/vert size: 30K/vert lin: 10K	18D67678A09
R306	varistor	6C66263A16
R616	varistor	6C66263A16
T300	4.5MHz trap & ATO	24D68822A07
T301	ratio detector	24D68517A16
T302	audio output	25D67552A25

T600	vert output	25D69990A01
C803	400µf/100v, 600µf/100v, 120µf/100v, 80µf/100v lytic	23C69772A02
L500	horiz osc: incl core	24D68130A03
L501	choke, horiz speed up	24D69044A04
L502	choke, horiz suppressor	24D69707A18
L504	horiz size	24D69163A04
L505	choke, horiz suppressor	24D65947A74
L800	choke, line: incl C806 & 807	24V68638A15
R403	RF AGC: 18K	18D66401A20
T500	horiz driver	25D67440A03

T501	HV xformer: complete	24D69826B02
L700	yoke, deflection: 114"	24D68523A05
L801	choke, filter	25D67554A15
R124	contrast: rotary: 1K C21, D21T5-599	18D67502A14
R201	bright: slide: 100K C19T5-599	18D68443A14
R602	vert: slide: 3K C19T5-599	18D67637A63
	vert: rotary: 3K C21, D21T5-599	18D68443A13
	vert: rotary: 3K C21, D21T5-599	18D67637A64
T800	power	25D68499D04
	VHF tuner, CPTT, OPTT-413	
	UHF tuner, KTT-626	


- NOTES
- VOLTAGE MEASUREMENTS
- TAKEN FROM POINT INDICATED TO CHASSIS WITH A VTVM - 20"
 - LINE VOLTAGE MAINTAINED AT 120V AC
 - TAKEN WITH CONTRAST CONTROL AT MINIMUM AND ALL OTHER CONTROLS IN NORMAL OPERATING POSITION.
 - WHERE TWO VOLTAGES ARE SHOWN, VOLTAGE ABOVE BOX WITH NO SIGNAL INPUT, TUNER ON CHANNEL WITH LEAST NOISE AND ANTENNA TERMINALS SHORTED.
 - VOLTAGE IN BOX WITH TUNER ON STRONG STATION AND OUTSIDE ANTENNA.
- WAVEFORM MEASUREMENTS
- TAKEN FROM POINT INDICATED TO CHASSIS WITH A 4"IDE - BAND OSC ILLOSCOPE.
 - OSC ILLOSCOPE SYNCED TO LINE SWEEP RATE INDICATED.
 - TAKEN WITH STRONG SIGNAL, CONTRAST CONTROL AT MAXIMUM, ALL OTHER CONTROLS IN NORMAL OPERATING POSITION.
- ** INDICATES VOLTAGE VARIES WITH CONTROL SETTINGS, UNLESS OTHERWISE SPECIFIED. CAPACITOR VALUES LESS THAN ONE IN RF, ALL OTHERS: 1K PP. CAPACITANCE VALUES ONLY ARE SHOWN ON SCHEMATIC DIAGRAM. REFER TO PARTS LIST. RESISTORS ARE 10³ 1 2K. COIL RESISTANCES LESS THAN 1 OHM NOT SHOWN.

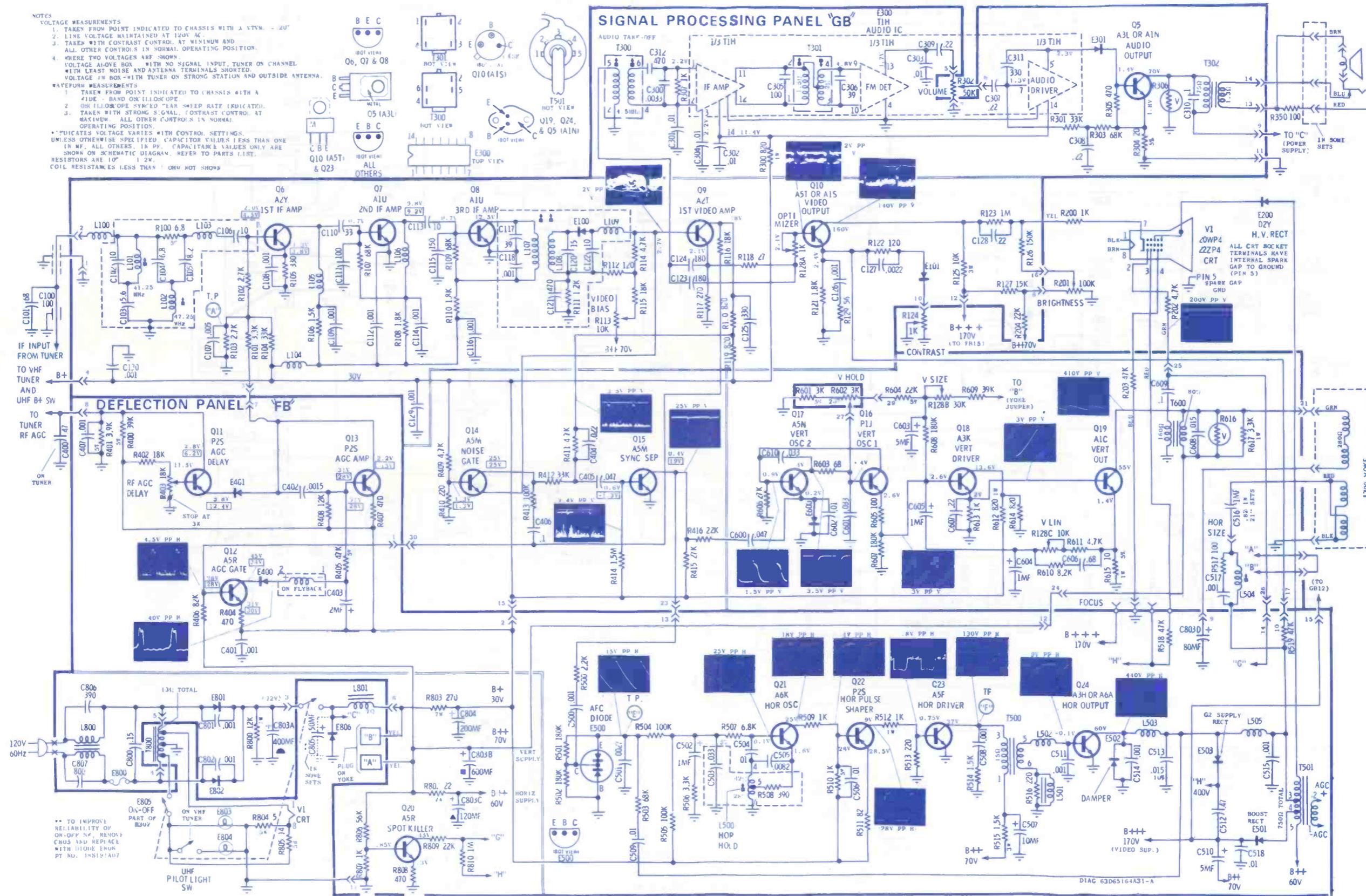

SYMBOL	DESCRIPTION	PHILCO-FORD PART NO.
C48A-D	160/240/240/5 @ 175v B+ filters	30-2601-33
L7	quad. snd det.	32-4876-1
L8	MHz trap & snd take-off	32-4688-13
L12	horiz stabilizer	32-4754-3
L13	47.25MHz trap	32-4652-78
L14	41.25MHz trap	32-4652-80
L17	40MHz det choke	32-4837-1

M3	vert integrator	30-6030-12
N5	phase comp	30-6035-2
N6	CRT Isolation	30-6058-2
R15A	6.8K 3w video plate	33-1363-46
R40	varistor vert yoke	33-1373-6
R63	3W fusible resistor	33-1381-5
T1	audio output	32-10013-2
T2	filter choke	32-10118-4
T3	horiz output	32-10008-7

T4	vert output	32-10012-6
VR1A-C	500K V size 2M lin. 60K H. hold	33-5595-8
VR4A-B	100K bright 15K contrast	33-5618-17
VR5	3K width	33-5620-1
VR6	150K vert hold	33-5619-9
VR7	1M vol-on-off, w/cb	33-5634-5
	VIF detassy w/comp (module "B")	38-10302
	Tuner, UHF TT152	76-13827-1
	Tuner, VHF TT164A	76-13579-7

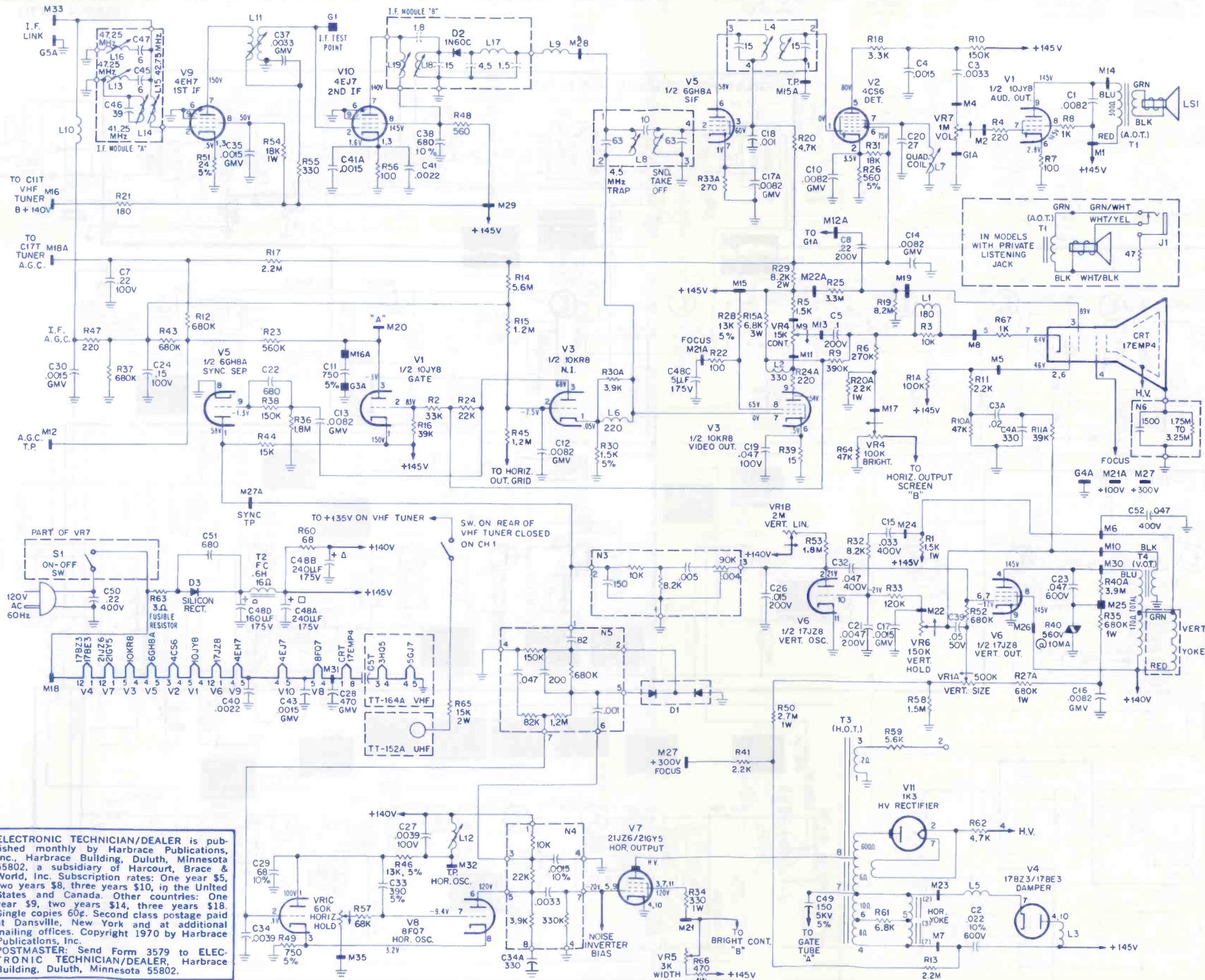

ELECTRONIC TECHNICIAN/DEALER is published monthly by Harbrace Publications, Inc., Harbrace Building, Duluth, Minnesota 55802, a subsidiary of Harcourt, Brace & World, Inc. Subscription rates: One year \$5, two years \$8, three years \$10, in the United States and Canada. Other countries: One year \$9, two years \$14, three years \$18. Single copies 60¢. Second class postage paid at Dansville, New York and at additional mailing offices. Copyright 1970 by Harbrace Publications, Inc. POSTMASTER: Send Form 3579 to ELECTRONIC TECHNICIAN/DEALER, Harbrace Building, Duluth, Minnesota 55802.



\$975

TUNER SERVICE CORPORATION

PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS AT ONE PRICE.

TUNER REPAIR

VHF Or UHF Any Type \$9.75.
UHF/VHF Combo \$15.00.

In this price all parts are included. Tubes, transistors, diodes, and nuvistors are charged at cost.

Fast efficient service at our four conveniently located service centers.

1 year guarantee backed up by the largest tuner manufacturer in the U.S.—SARKES TARZIAN, INC.

All tuners are cleaned inside and out, repaired, realigned and air tested.

TUNER REPLACEMENT

Replacement Tuner \$9.75.

This price buys you a complete new tuner built specifically by SARKES TARZIAN INC. for this purpose.

The price is the **same** for every type of universal replacement tuner.

Specify heater type

Parallel 6.3V
Series 450 mA
Series 600 mA

All shafts have the same length of 12".

Characteristics are:

Memory Fine Tuning
UHF Plug In
Universal Mounting
Hi-Gain Lo-Noise

If you prefer we'll customize this tuner for you. The price will be \$18.25. Send in original tuner for comparison purposes to our office in INDIANAPOLIS, INDIANA.



TUNER SERVICE CORPORATION

FACTORY-SUPERVISED TUNER SERVICE

MIDWEST 817 N. PENNSYLVANIA ST., Indianapolis, Indiana TEL: 317-632-3493
(Home Office)
EAST 547-49 TONNELE AVE., Jersey City, New Jersey TEL: 201-792-3730
SOUTH-EAST 938 GORDON ST., S. W., Atlanta, Georgia TEL: 404-758-2232
WEST SARKES TARZIAN, Inc. **TUNER SERVICE DIVISION**
10654 MAGNOLIA BLVD., North Hollywood, California TEL: 213-769-2720

Crime does pay.

If you're an alert distributor.

Because we are introducing a new product with a suggested retail list of \$89.95 that will sound a warning when it detects an intruder, vandal or trespasser. It's the Mallory Crime Alert® ultrasonic intruder alarm.

This new Mallory product is easy to stock—no time consuming installation—no big warehouse space needed. It's bound to be a sure-fire seller because it's so beautifully simple and effective. It gives 24-hour surveillance for homes, offices, stores and plants at small cost and needs no maintenance.

In use, there are no wires, no light beams, no door and window devices . . . just the compact Crime Alert unit itself. Set up in a room or hall, it sends out continuous ultrasonic waves that can't be seen, heard, or avoided. Yet the smallest movement is detected in a split second, activating the built-in alarm and any spotlights, sirens, recorders or other devices plugged into it.

The same type of system is used in the Pentagon to guard the security of top secret areas. It's an item everybody needs today. So put in an order now.

MALLORY

MALLORY DISTRIBUTOR PRODUCTS COMPANY

a division of P. R. MALLORY & CO. INC.
Box 1559, Indianapolis, Indiana 46206; Telephone: 317-636-5353

Batteries • Capacitors • Cassette Tapes • Controls Crime Alert® Resistors • Semiconductors • Sonalert® • Switches • Timers • Vibrators

ACTUAL SIZE



... for more details circle 129 on Reader Service Card

HUGH "SCOTTY" WALLACE

Publisher

Chicago:

(312) 467-0670

PAUL DORWEILER

Editor

PHILLIP DAHLEN

Managing Editor

JOSEPH ZAUHAR

Technical Editor

KATHIE PONTINEN

Production Editor

BOB ANDRESEN

Graphic Design

LILLIE PEARSON

Circulation Fulfillment

JOHN KESSLER

Manager, Reader Services

BERNICE GEISERT

Advertising Production

OFFICES

757 Third Avenue

New York, N.Y. 10017

Phone: (212) 572-5000

Telex: 01-26286

43 East Ohio St.

Chicago, Ill. 60611

Phone: (312) 467-0670

Telex: 02-53549

1901 West 8th St.

Los Angeles, Calif. 90057

Phone: (213) 483-8530

Harbrace Building

Duluth, Minn. 55802

Phone: (218) 727-8511

Telex: 02-94417

MANAGERS

HUGH "SCOTTY" WALLACE

Chicago: (312) 467-0670

DEAN GREENER

Chicago: (312) 467-0670

ALFRED A. MENEGUS

New York: (212) 572-4829

DONALD D. HOUSTON

Los Angeles: (213) 483-8530

ROBERT UPTON

Tokyo, Japan

I.P.O., Box 5056

CHARLES S. HARRISON,

CY JOBSON

San Francisco:

(415) 392-6794

HARBACE PUBLICATIONS, INC.

JOHN B. GELLATLY

President

RICHARD MOELLER

Treasurer

LARS FLADMARK

Senior Vice-President

HARRY RAMALEY

Vice-President

JAMES GHERNA

Art Director

EDWARD CROWELL

Director of Marketing Services

ELECTRONIC TECHNICIAN / DEALER

WORLD'S LARGEST TV-RADIO SERVICE & SALES CIRCULATION

MAY 1970 • VOL. 91 NO. 5

45 INTRODUCING MOTOROLA'S QUASAR II COLOR TV

That is the theme of this month's TEKLAB report which will present a description of the circuits in this unit in two parts; part two follows next month. The circuits covered this month will include the power supply, ACC amplifier, color killer and others.

49 HIGH POWER TUNER/AMPLIFIERS

This article by Homer L. Davidson provides some practical service procedures with simple techniques a technician can use as he learns more about solid-state amplifiers.

53 THE LONG AND SHORT OF MATV CABLES

Robert Sharp and Paul Miller, two men who know the whys and wheres of cable, collaborated on this informative article which explains how a multiple antenna system can pick up a normal TV signal only to have it reach a customer's set distorted because of a poorly designed or installed cable system.

59 ELECTRONIC DEPTH FINDERS

This timely feature on marine electronic equipment and more specifically, on electronic depth finders, explains the operation and maintenance of these increasingly popular instruments. The article also includes a complete circuit description of the Heath Model MI-29 with diagrams and schematics.

63 TESTLAB REPORT

Our lab technicians give a first-hand account of the EICO Model 240 solid-state FET-VOM which was assembled from a kit and checked out on the bench. The report also lists the manufacturer's complete specifications.

22 EDITOR'S MEMO

72 DEALER SHOWCASE

26 NEW AND NOTEWORTHY

80 NEWS OF THE INDUSTRY

30 LETTERS TO THE EDITOR

84 NEW PRODUCTS

36 TECHNICAL DIGEST

90 CATALOGS AND BULLETINS

40 COLORFAX

92 ADVERTISER'S INDEX

COVER

Our cover this month was taken on one of Northern Minnesota's beautiful lakes and attempts to illustrate the increasing popularity and use of marine electronic equipment as part of the boating enthusiast's basic requirements for safer boating.

TEKFAQ • 16 PAGES OF THE LATEST SCHEMATICS • Group 213

ADMIRAL: TV Chassis T3K3-1A, T3K3-1B

AIRLINE: Color TV Models GC1-12420A, B

MAGNAVOX: TV Chassis T948

MOTOROLA: Color TV Chassis TS-934

MOTOROLA: TV Chassis TS-599


PHILCO-FORD: TV Chassis 20P22



A HARCOURT, BRACE & WORLD PUBLICATION
Harbrace Publications, Inc.



ELECTRONIC TECHNICIAN/DEALER is published monthly by Electronics Technician, Inc., a subsidiary of Harbrace Publications, Inc. Corporate Offices: 757 Third Avenue, New York, New York 10017. Advertising Offices: 43 East Ohio Street, Chicago, Illinois 60611 and 757 Third Avenue, New York, New York 10017. Editorial, Accounting and Circulation Offices: Harbrace Building, Duluth, Minnesota 55802. Subscription rates: One year \$5, two years \$8, three years \$10, in the United States and Canada. Other countries: one year \$9, two years \$14, three years \$18. Single copies: 75¢ in the U.S. and Canada; all other countries \$2. Second class postage paid at Dansville, New York 14437 and at additional mailing offices. Copyright 1970 by Electronics Technician, Inc. POSTMASTER: Send form 3579 to ELECTRONIC TECHNICIAN/DEALER, Harbrace Building, Duluth, Minnesota 55802.

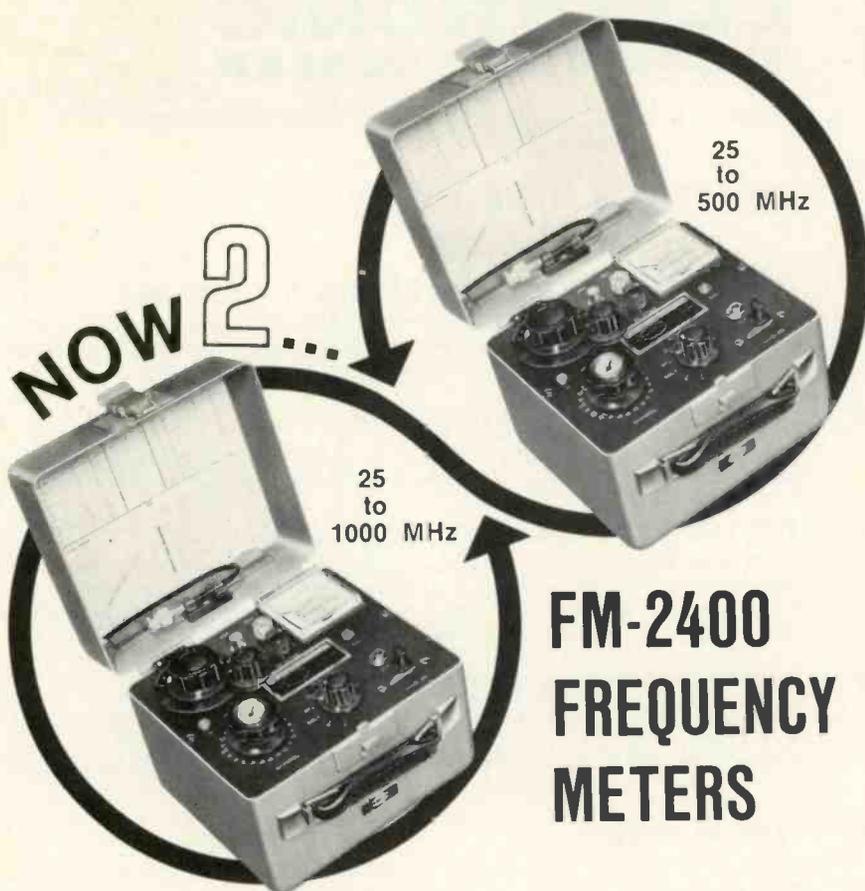

FM-2400 FREQUENCY METERS

FM-2400CH (New)

- Tests Predetermined Frequencies 25 to 1000 MHz
- New Extended Range Covers 950 MHz Band
- Pin Diode Attenuator

FM-2400C

- Tests Predetermined Frequencies 25 to 500 MHz

The new FM-2400CH and the FM-2400C provide an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies. The FM-2400CH with its extended range covers 25 to 1000 MHz. The Model FM-2400C covers 25 to 500 MHz. The frequencies can be those of the radio frequency channels of operation and/or of the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability: $\pm .0005\%$ from $+50^{\circ}$ to $+104^{\circ}\text{F}$

Frequency Stability: with built-in thermometer and temperature corrected charts. $\pm .00025\%$ from $+25^{\circ}$ to $+125^{\circ}$ ($.000125\%$ special 450 MHz crystals available)

Both the FM-2400CH and the FM-2400C are self contained in small portable cases. Complete solid state circuitry. Rechargeable batteries.

FM-2400CH (meter only) .. \$595.00
 RF crystals (with temperature correction) 24.00 ea.
 RF crystals (less temperature correction)..... 18.00 ea.
 IF crystals..... catalog price

FM-2400C (meter only) ... \$445.00
 RF crystals (with temperature correction) 24.00 ea.
 RF crystals (less temperature correction)..... 18.00 ea.
 IF crystals..... catalog price

Write for catalog



CRYSTAL MFG. CO., INC.

10 NO. LEE • OKLA. CITY, OKLA. 73102

... for more details circle 121 on Reader Service Card

Educational TV

I just returned from the IEEE convention in New York and have to admit that with the airline controllers' sick-in it was something of a long trip. I never spent so much time on one airplane going nowhere in my life.


But if something good were to come of it all, I would say that the IEEE and several of the press conferences were worth it. One of the most interesting meetings I attended was sponsored by CBS for their color EVR (Electronic Video Recording) division. The meeting had as guest speakers Mr. Frank Stanton, CBS president, Mr. E. H. Wavering, President of Motorola, and Mr. Daryl F. Zanuck, Chairman of the Board of 20th Century-Fox Films. The meeting took place in the Grand Ballroom of the Hotel Pierre in N.Y. City in which were set up several Motorola production line monitors, color of course, and several video tape players.

CBS president Frank Stanton and Motorola president Elmer H. Wavering were joined by Daryl F. Zanuck in announcing plans to make 20th Century-Fox theatrical films available for conversion to the new EVR system of showing on home receivers. The color EVR system was developed by CBS, and Motorola obtained the exclusive license to manufacture the players in North America. The players are capable of either black and white or color with only a simple hookup to the regular antenna outlet on rear of the TV set.

Since the premier showing of the EVR system, plans now call for a demonstration tour which will include exhibits at 17 major cities across the nation. Just think, soon you may be selling CCTV and video tape recorders to your color TV customers so they can show their own home color movies from a popular selection of the best of 20th Century films.



Paul A. Rowland

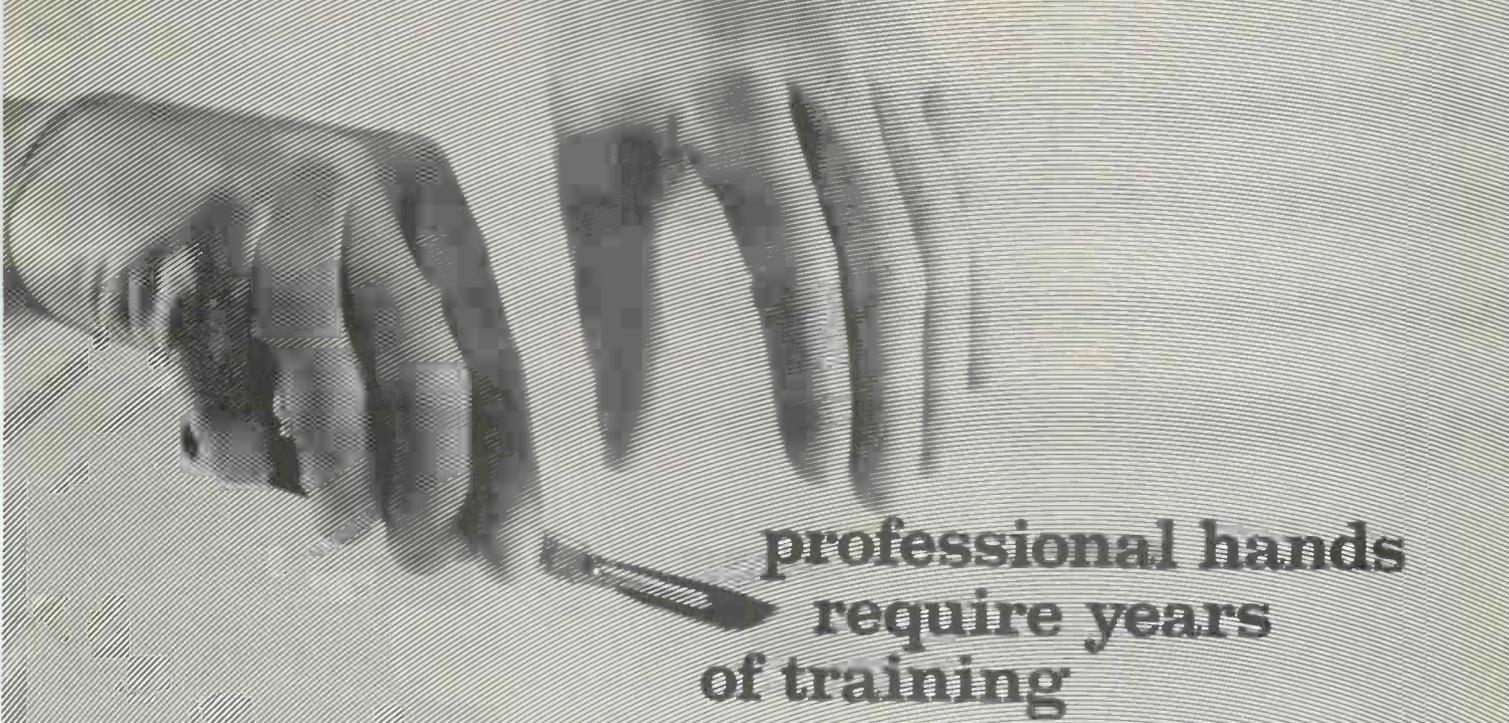

**professional hands
require years
of training**

**professional TV
service dealers insist on
GE receiving tubes**
(made by professionals for professionals)

GENERAL  ELECTRIC

**TUBE DEPARTMENT
OWENSBORO, KENTUCKY 42301**

... for more details circle 177 on Reader Service Card



NEW AND NOTEWORTHY

For additional information on products described in this section, circle the numbers on Reader Service Card. Requests will be handled promptly.



COLOR CRT ONE GUN BOOSTER

Boosts only weak gun for proper color balance **700**

Introduced is a solid-state one gun booster for color TV picture tubes. The booster extends color gun life by restoring the brilliance of either the red, blue or green gun.

This unit is not the same as a regular brightener that boosts all three colors equally, but will boost the one weak color as needed for a balanced color picture.

Installation is easy with self-stripping connectors that are included in the package. Workman.

SOLDERING IRON/POWER UNIT


Tips changed without tools

701

Announced is the Model W-TCP Temperature Controlled, Low Voltage Pencil Iron and Power Unit. The unit represents the most advanced equipment available for production line manual soldering and technical use.

The pencil, weighing 1 $\frac{2}{3}$ oz (2 $\frac{1}{2}$ oz including cord) reportedly packs the heating capacity of irons weighing a pound or more. It automatically adjusts to handle jobs in the 15 to 75w conventional iron range and an extended range up to 100w, where production rate is not excessive.

The unit uses interchangeable, premium plated tips, each with its own magnetic temperature sensor for selected tip idle temperature. A wide variety of screwdriver, conical and pyramid tips are available. The power unit furnishes the soldering pencil with a source of 24v current and is equipped with a handy stand for the pencil. A heavy duty transformer, rated at 60w, 120v, 50/60Hz is housed within the phenolic case, which is also provided with a sponge for tip cleaning. Weller.

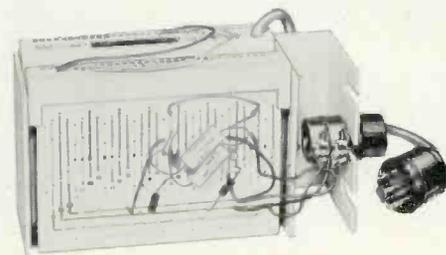

PATCH-BOARD 702

More economical than conventional breadboarding

Introduced is the EU-53A "Stack-n-Patch" . . . a technique for circuit design and teaching that is faster, easier and more economical than conventional breadboarding.

The board consists of a small desk-top chassis, a Power Patch Card and a Component Patch Card. Patching up a design is fast and simple . . . pick your choice of power supply and connect it to the Power Patch Card . . . stack the Component and Power Patch Cards in the Chassis . . . and patch components or hook-up wire into the Component Card. The Patch-Board eliminates soldering . . . the special connectors on the cards make a tight, electrically stable connection just by inserting the wire into the connector. The 177 connectors on the board are arranged according to common circuit board practice and closely simulate the circuit density and "stray" interaction of today's printed circuits.

For IC work and other types of design that can't be conveniently built on the component card, a wide variety of factory assembled cards to stack in the chassis is offered. The Model EU-53A is \$37.50. Heath.

**FOR MORE
NEW PRODUCTS SEE
PAGES 72 & 84**

Now the Chromacolor revolution comes to replacement tubes too!

Now you can install Zenith's patented Chromacolor picture tube that outcolors, outbrightens, outcontrasts and outdetails every other 23" diag. color picture tube.


With a full 2-year warranty!

After years of pioneering research and development, Zenith has perfected a color TV picture tube different than any other on the market. So revolutionary that it outcolors, outbrightens, outcontrasts and outdetails every other 23" diag. color tube. And it's a Zenith exclusive—covered by U.S. Patent No. 3,146,368.

Before Chromacolor, every giant-screen color picture was made up of tiny dots on a gray background.

But Zenith made the dots smaller, surrounded them with jet black and, for the first time, *fully* illuminated every dot. Result: the brightest, sharpest picture tube in giant-screen color TV.

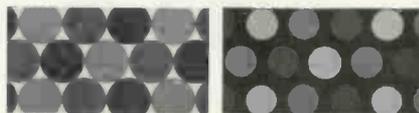The Zenith Chromacolor tube will readily replace the 23" diag. tube in almost any TV, whatever brand. And, unlike most replacement tubes, it's warranted for two full years.



Magnified drawing of ordinary color TV screen before Chromacolor

Magnified drawing of Zenith Chromacolor TV screen

Order the Zenith Chromacolor picture tube from your Zenith distributor for your next installation. And put your customer in a better light.

At Zenith, the quality goes in before the name goes on.®

TWO-YEAR WARRANTY


Zenith Radio Corporation warrants the replacement CHROMACOLOR picture tube to be free from defects in material arising from normal usage for two years from date of original consumer purchase. Warranty covers replacement or repair of picture tube, through any authorized Zenith dealer; transportation, labor and service charges are the obligation of the owner.



Simulated TV picture

ZENITH
CHROMACOLOR™

ONLY ZENITH HAS IT

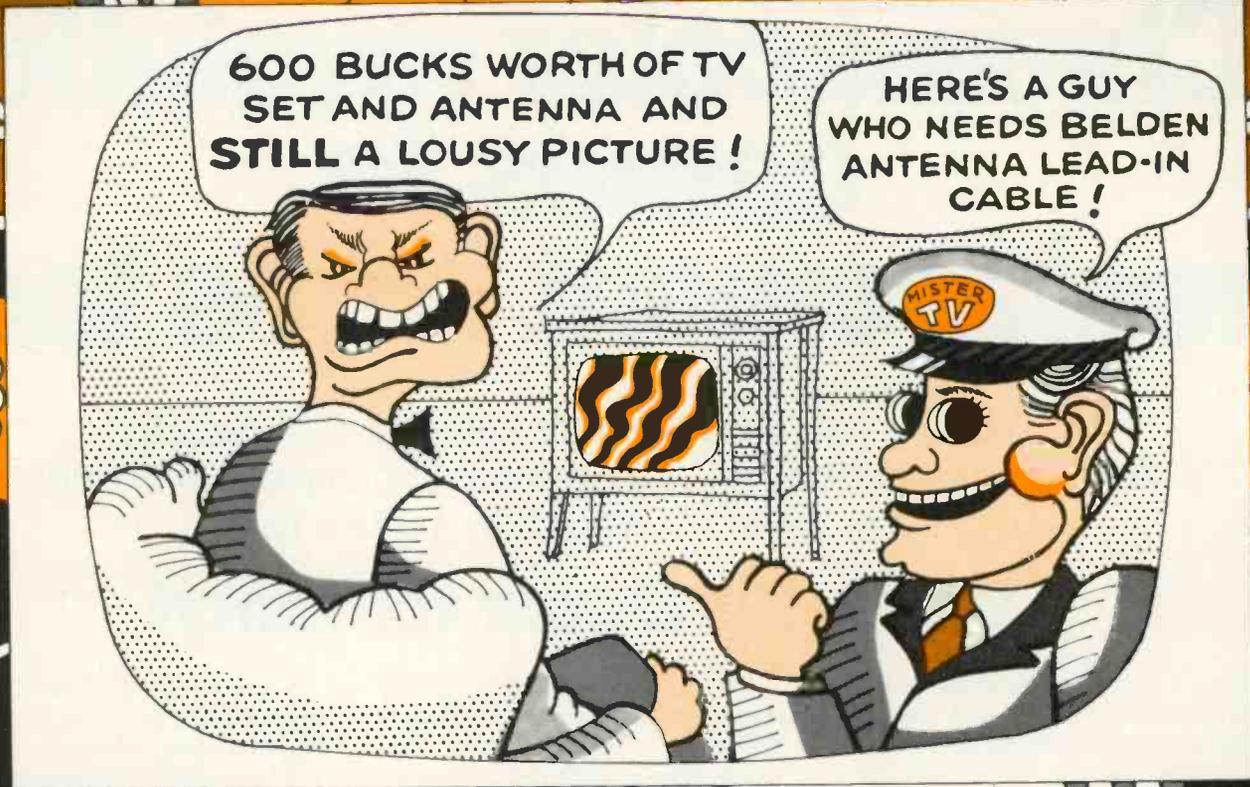

Color or UHF set perfect? Antenna perfect? Then obviously there's a missing link. Check that antenna lead-in cable. Old, worn-out, weather-beaten cable, or the ordinary flat ribbon kind designed for black and white VHF, causes more fuzzy, distorted pictures than you can count. It's your opportunity to upgrade these customers to a cable matched to their particular signal reception situations. One of Belden's Big Four—the link to perfect reception.

FOR CONGESTED AREAS...

8290 SHIELDED PERMOHM®



In congested, in-city areas, stray electrical interference and noise are at their worst. For perfect, all-82 channel reception—color or B/W—replace old cable with Belden's 8290 Shielded PermoHM. Its aluminum Beldfoil® shielding prevents pickup of ghost signals and electrical noise by the lead-in. Weather-proof and water-proof. You can tape it right to the mast. Or install it underground, in conduits—even in rain gutters.



AWG & (Stranding)	Color	Nom. O. D. (Inch)	Nom. Velocity of Propagation	Nom. Capacitance (mmf/ft.)	Nom. Attenuation per 100'	Standard Package Lengths in ft.
22 (7 x 30)	Brown	.305	69.8%	7.8	57	1.7
		x			85	2.1
		.515			177	3.2
					213	3.5
					473	5.4
					671	6.6
		887	7.7			

Copperweld, 2 conductors, orange polyethylene insulation and web between conductors, cellular polyethylene oval insulation, Beldfoil shield, stranded tinned drain wire, polyethylene jacket.

50', 75', 100' coils have terminals attached.
Available in counter dispenser.
250', 500' spool.

BELDEN 8285 - PERMOHM

FOR FRINGE AREAS...

8285 PERMOHM®

Antenna cable in uncongested or fringe areas picks up little electrical interference. But does get a lot of weathering, which degrades an already weak signal. These customers need encapsulated cable. Belden 8285 Permohm. Its special polyethylene jacket protects the energy field, regardless of weather conditions. It delivers the strongest signal of any unshielded twin lead under adverse conditions. Requires no matching transformers and connectors. For all 82 channels, color or B/W.



AWG & (Stranding)	Color	Nom. O. D. (inch)	Nom. Velocity of Propagation	Nom. Capacitance (mmf/ft.)	Nom. Attenuation per 100'		Standard Package Lengths in ft.
					mc	db	
22 (7 x 30)	Brown	.255 x .468	73.3%	5.3	100	1.4	50', 75', 100' coils have terminals attached. Available in counter dispenser. 250', 500' coils and 1000' spool.
					300	2.8	
					500	3.8	
					700	4.8	
					900	5.6	

Copperweld, 2 conductors parallel, orange polyethylene insulation and web between conductors, cellular polyethylene oval jacket.

FOR LOCAL BLACK AND WHITE...

8275 CELLULINE®

BELDEN 8275 CELLULINE 300 OHM UHF TRANSMISSION LINE PAT. NOS. 278229



Cracked, corroded, weathered cable, full of dirt and moisture, loses signal strength; prevents any TV set from delivering a quality picture. Upgrade B/W VHF and local UHF customers to Belden 8275 Celluline. Performance is improved because all possible moisture between conductors has been eliminated. Abrasion-resistant and weather-resistant for a long, long service life. And, it requires no end sealing.

AWG & (Stranding)	Color	Nom. O. D. (inch)	Nom. Velocity of Propagation	Nom. Capacitance (mmf/ft.)	Nom. Attenuation per 100'		Standard Package Lengths in ft.
					mc	db	
20 (7 x 28)	Brown	.300 x .400	80%	4.6	100	1.05	50', 75', 100' coils in counter dispenser. 250', 500', 1000' spools.
					200	1.64	
					300	2.12	
					400	2.5	
					500	2.98	
					700	3.62	
					900	4.3	

Bare copperweld; 2 conductors parallel, polyethylene jacket with inert gas filled unicellular polyethylene core.

FOR MATV AND CATV...

8228 DUOFOIL® COAX

Got an apartment or townhouse complex in your area? Motels or hotels? Or is CATV coming? Use Belden's new 75 ohm coaxial cable—8228 Duofoil. Shielding is 100%—sweep tested 100%. Spiral wrapped drain wires provide long flex life. Small diameter saves space in conduit installations. Use Duofoil for all coaxial color and B/W VHF, UHF and CATV applications.



AWG & (Stranding)	Color	Nom. O. D. (inch)	Nom. Velocity of Propagation	Nom. Capacitance (mmf/ft.)	Nom. Attenuation per 100'		Standard Package Lengths in ft.
					mc	db	
18 Solid, Bare	Black	.242	78%	17.3	50	1.5	100', 500', 1000' spools.
					100	2.1	
					200	3.1	
					300	3.8	
					400	4.5	
					500	5.0	
					600	5.5	
					700	6.0	
					800	6.5	
					900	6.9	

Don't forget to ask them what else needs fixing.

See your local Belden distributor for full details or to order. For a free copy of the recent reprint article, "Electronic Cable," write: Belden Corporation, P.O. Box 5070-A, Chicago, Illinois 60680.


BELDEN 

8-6-84

**This is 30,000
solid state replacement parts.**



So is this.

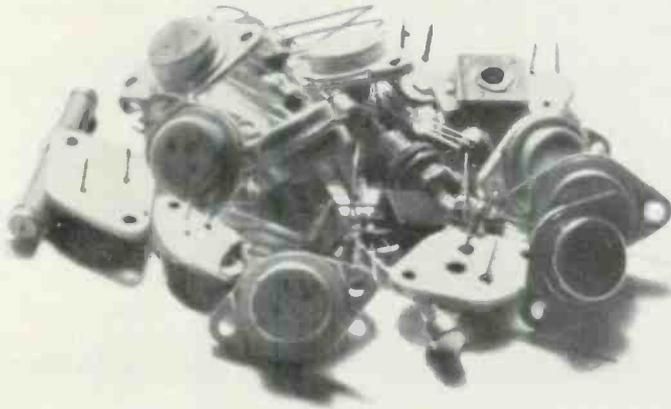

It used to be if you wanted to satisfy everyone, you had to stock over 30,000 different solid state replacement parts.

Well, everyone realized that was ridiculous. So some enterprising people came up with a bunch of universal replacements.

Then you only had to stock about eleven or twelve hundred.

That was a lot better, but we still thought it was a little ridiculous.

So two years ago (when we went into this business), we figured out how to replace all 30,000 with only 60.

Now all you have to do is stock 60 of our diodes, transistors, integrated circuits, etc., and you can replace any of the 30,000 parts now in use. Including

all JEDEC types, manufacturers' part numbers, and foreign designs.

That means you invest less money.

You don't tie up valuable space.

You do away with complicated inventory control.


And you operate more efficiently.

To make life even easier, we've got a new book that gives you all the cross references you need to figure out which part replaces which.


It's available from your Sylvania distributor.

If the whole thing sounds rather incredible, you're right. But why not give your distributor a call and let him narrow the incredibility gap.

SYLVANIA
GENERAL TELEPHONE & ELECTRONICS

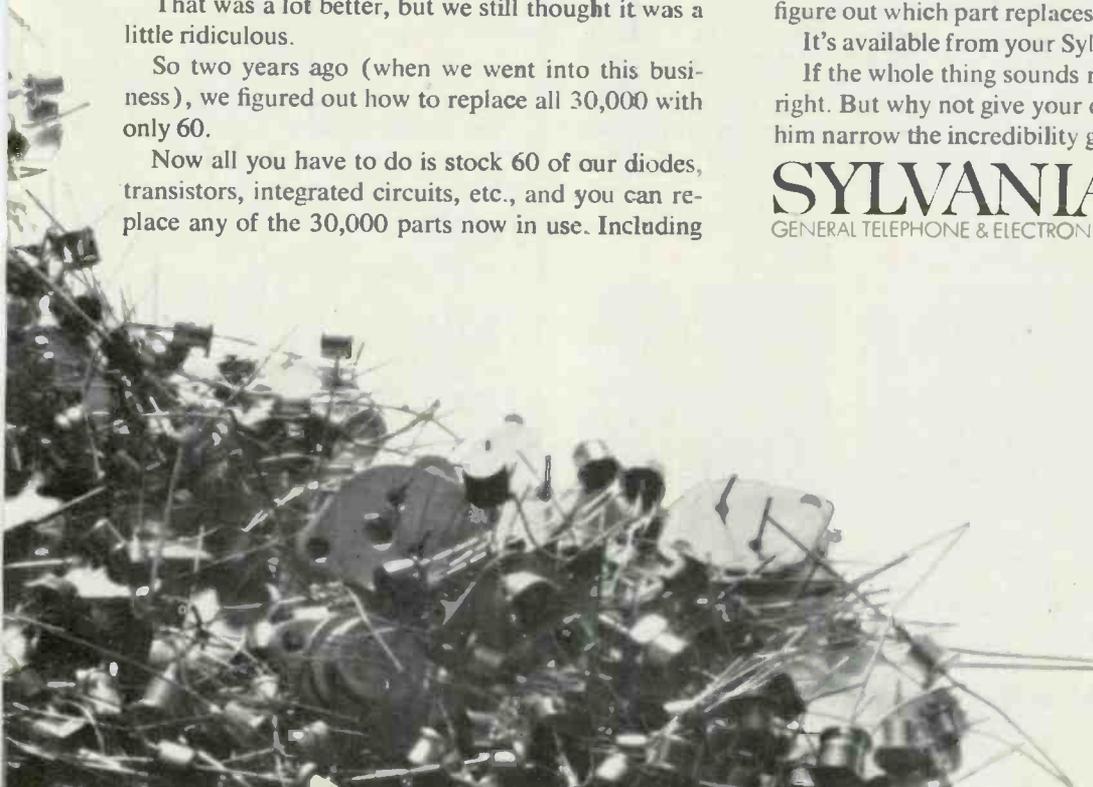

the new Gold Rush

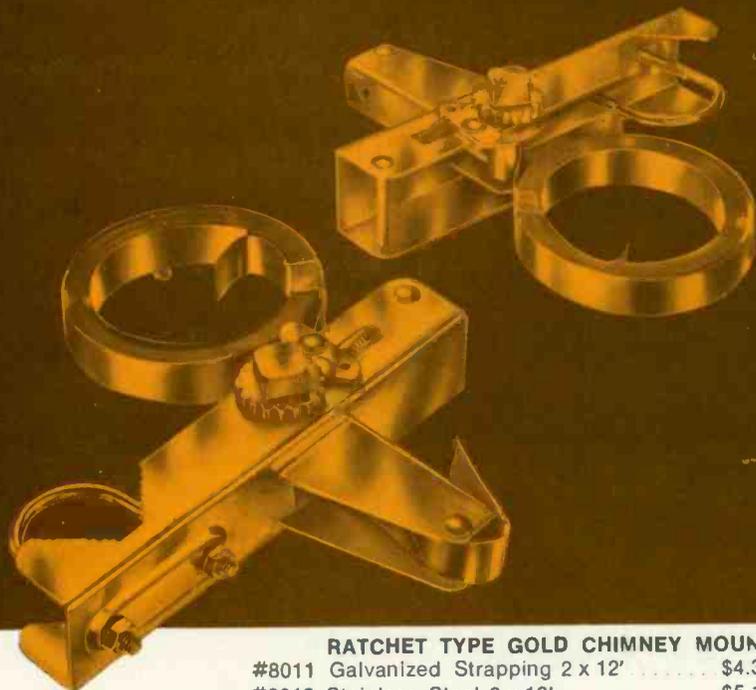

RATCHET TYPE GOLD CHIMNEY MOUNT

- #8011 Galvanized Strapping 2 x 12' \$4.33
- #8013 Stainless Steel 2 x 12' \$5.18

There's Profit In Gold


1. GOLD RATCHET MOUNT — New gold finish — first available on the market. New heavy gauge — non-strip ratchet features. Here is the quality constructed two-bracket chimney mount designed to give maximum service in high wind, seasonal storms, adverse weather conditions. **2. GOLD TRIPOD TOWERS** — Boxed — contains 6 lag screws supplied with self-adhesive weather patch, 1 1/4" tubing. **3. GOLD CHIMNEY MOUNTS** — Both Snap-in chimney mounts and GC-Telco "Y" Mounts are heavier gauge metal with new design. GC chimney mounts are strengthened at the stress point. Buy with confidence from the world's largest basic manufacturer of television hardware... you'll make your job easier, faster, and more profitable... more satisfying to your customer.

GOLD TRI-POD TOWER ANTENNA BASES




- #9146 3' \$5.86
- #9145 5' \$9.28

HEAVY DUTY GOLD SNAP-IN CHIMNEY MOUNTS

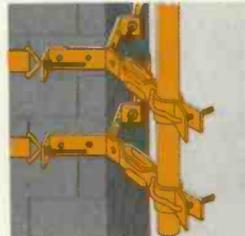

- #8646 Galvanized Strapping 2 x 12' \$3.09
- #8946 Stainless Steel 2 x 12' \$4.46

GC-TELCO GOLD CHIMNEY "Y" MOUNTS

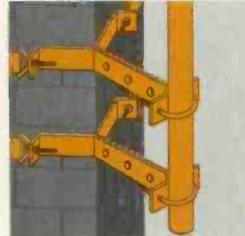

- #8616 Galvanized Strapping 2 x 12' \$3.85
- #9031 Stainless Steel 2 x 12' \$5.03



GC ELECTRONICS

MAIN PLANT: ROCKFORD, ILL. U.S.A.
A DIVISION OF HYDROMETALS, INC.



ET/D

LETTERS
TO THE EDITOR

Reader's Aid

We need a schematic and instruction manual for a Sonora electronic organ, Model 200 400. This company, Sonora Electronic, Inc., has been out of business for many years. Any help will be much appreciated.

NORMAN L. FITKIN

Norman L. Fitkin Television Sales
and Service
207 Circle
Sebring, Fla.

We have a Citizens Band transceiver made by Polytronics, which was located at 900 Burlington Ave., Silver Springs, Md. 20910.

I wrote to them and the mail has been returned, so I presume they are no longer in business. We cannot locate a dealer or distributor that could furnish me with the schematics and instructions for the above mentioned transceiver. It is a Poly-Comm 30 Serial No. 126A21, issue No. 1. If there is any way you can help me, I would gladly pay all costs involved.

Your magazine has been very beneficial and we definitely look forward to its arrival each month.

LOU WEISS

Better Radio & Television Service
957 Morris Park Ave.
Bronx, N.Y.

I am a subscriber of your magazine in need of some information that I am unable to find anywhere. Could you please tell me where I can obtain parts for Webcor models?

I know that they went out of business, and I am having difficulty trying to find parts for them.


JAMES R. CAHILL

Jim Cahill
Radio, Television & Electronic
Servicing
Wilmot Flat, N.H. 03287

As a subscriber of ELECTRONIC TECHNICIAN/DEALER, for I believe 20 years, I have yet to see very much covering the subject of marine radio equipment in the 2 to 4 MHz band, or much if anything on mobile radio equipment in the 150 to 174 MHz band. I presume it is mostly because there is a much greater demand for the entertainment type of electronic gear. However, there must be many other technicians interested in com-

Do you judge capacitors
on the same basis
Bill Dickerson does?

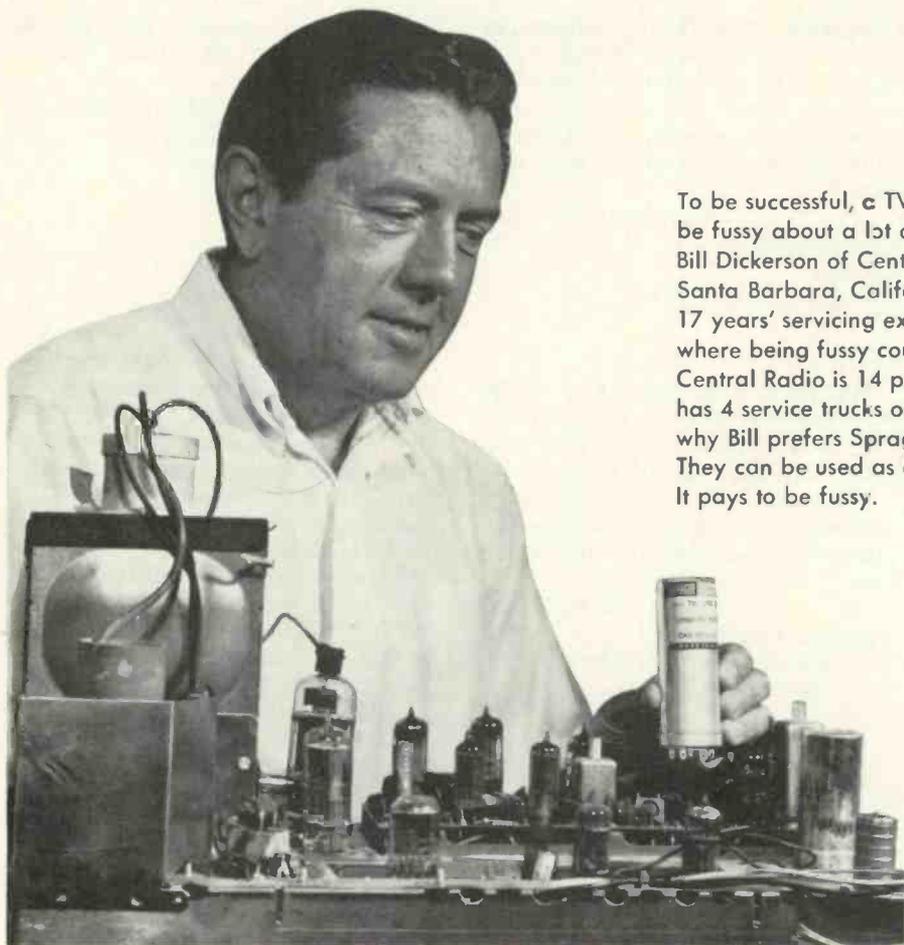Then you'll use
Sprague Twist-Lok[®] Capacitors when
you need twist-prong electrolytics.



To be successful, a TV service dealer has to be fussy about a lot of things. No one knows it better than Bill Dickerson of Central Radio and Television, Santa Barbara, California. He's building on his 17 years' servicing experience every day in a spot where being fussy counts a lot. Central Radio is 14 people strong and has 4 service trucks on the go. It's easy to see why Bill prefers Sprague Twist-Lok Capacitors. They can be used as exact replacements to avoid call-backs. It pays to be fussy.

Ask your Sprague distributor for a copy of Sprague's Electrolytic Capacitor Replacement Manual K-109 or write to:
Sprague Products Company, 65 Marshall St., North Adams, Mass. 01247

P.S. You can increase your business 7½% by participating in EIA's "What else needs fixing?" program. Ask your distributor or write to us for details.



FAST

COMPLETE SERVICE ON ALL MAKES OF TV TUNERS

Maximum Time In Shop 24 Hrs.


(WE SHIP C.O.D.)
YOU PAY SHIPPING

(90 Day Warranty)

\$9.95

Black &
White
or Color

VHF or
UHF

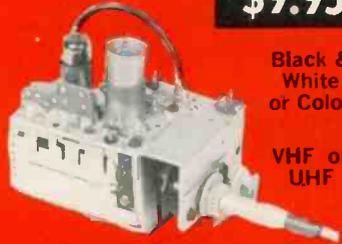

UV Combo's, \$16.50

Price includes all labor and parts except Tubes, Diodes & Transistors. If Combo tuner needs only one unit repaired, disassemble and ship only defective unit. Otherwise there will be a charge for a combo tuner. When sending tuners for repair, remove mounting brackets, knobs, indicator dials, remote fine tuning arrangements and remote control drive units.

All tuners must have remote control units and/or mounting brackets removed before tuner can be cleaned and repaired. Please remove these accessories before shipping, as we will not be responsible for loss or damage.



All tuners are serviced by **FACTORY TRAINED TECHNICIANS** with years of experience in this specialized field. All tuners are **ALIGNED TO MANUFACTURER'S SPECIFICATION** on crystal controlled equipment and air checked on monitor before shipping to assure that tuner is operating properly.

GEM CITY TUNER REPAIR SERVICE

Box 6D Dabel Station
2631 Mardon Drive
Dayton, Ohio 45420

ET/D

LETTERS TO THE EDITOR

munications equipment topics also.

My real reason for writing you is that I am looking for a recommended list of test equipment most needed to adequately equip my shop for the installation and servicing of communications equipment, such as the above mentioned. Would you be so kind as to tell me what you and your staff might recommend, and furnish me with a listing of manufacturers that I might contact for their catalogs and price information. Of course, if you can help me in any other way I would certainly appreciate it.

Radio and TV servicing has been my trade for the last 20 years, but I feel that I must slow down a little so I am giving up all the TV and radio business, only keeping my marine radio work. In so doing I am invited to service all the local mobile radio equipment on the Island of Nantucket and to do so will naturally require me to invest in, I presume, considerably more test gear than what I have had heretofore.

FREDERICK W. COOK

Cook's Electronics
Box 831
Nantucket, Mass. 02554

We have a dc voltmeter, Model 20A, manufactured by F. L. Mosley Co. of Pasadena, Calif. This voltmeter was made for the Navy.

We would like to know if any of your readers has any information, diagrams or an address for the Mosley Co.

CHARLES F. MEYER

Electronics Instructor
Twin Falls Senior High School
Twin Falls, Idaho 83301

Please send me the address of Russell Industries. They manufacture shielding. If you do not have this address, then can you tell me where I can get it?

PAUL CAPITOL

Capitol Radio Service
637 West 21 St.
Erie, Pa. 16502

I am in need of information on a Grundig record player and hope you or a reader can help me. A letter to Grundig in New York resulted in the information that they did not import that model. It is a Grundig Model Mandello-b No. 5263 HE.

What I need is a cross reference to one of the tubes, an EAF-801 and a cross reference on the cartridge or needle. The cartridge number is AG 3306 AHDT or AG 3310 AHDT.

Any help would be appreciated.

DONALD C. TREECE

Don's Electronic Service
Route No. 3
Kahoka, Mo. 63445

Selling Business

I have an excellent going business here in South Georgia. The people are friendly and the climate is very good, but the time has come for me to step down, due to age.

It would be an excellent opportunity for one or two younger men to take over a fully equipped and going business of 21 years. If you can pass this along to your readers, I will furnish all particulars.

I have enjoyed your publication for years, in fact we are paid up for the next three. I hope to at least be able to keep up with the trade for some time to come.

WILLIAM H. REYNOLDS, SR.

Emerson Park TV & Electrical
Appliance Service Co.
RFD No. 3, Box 217
Waycross, Georgia

Comments on Articles

I would like to say how much I enjoy reading your magazine. It is probably one of the finest technical publications available.

I am employed as a communications technician with the Ontario Hydro Power Commission. While I do not become involved in TV servicing, we are involved in FM, AM, SSB, microwave and multiplex systems (not to be confused with transmitted radio multiplex).


One feature which I think your readers might find enjoyable would be a series of articles on the early history of electronics. I think it would make a fine series.

I am interested in obtaining a complete set of your "Semiconductors From A to Z" series. Would this be available in book or pamphlet form? Unfortunately, I started to get your magazine about halfway through the series.

EDDIE LEHMAN

The "Semiconductors From A to Z" series was printed in book form by Tab Books and the book is now in its second printing. The book has been listed in many of their advertisements in ELECTRONIC TECHNICIAN/DEALER, as well as being listed in Lafayette Electronic Corp.'s 1970 catalog. Ed.

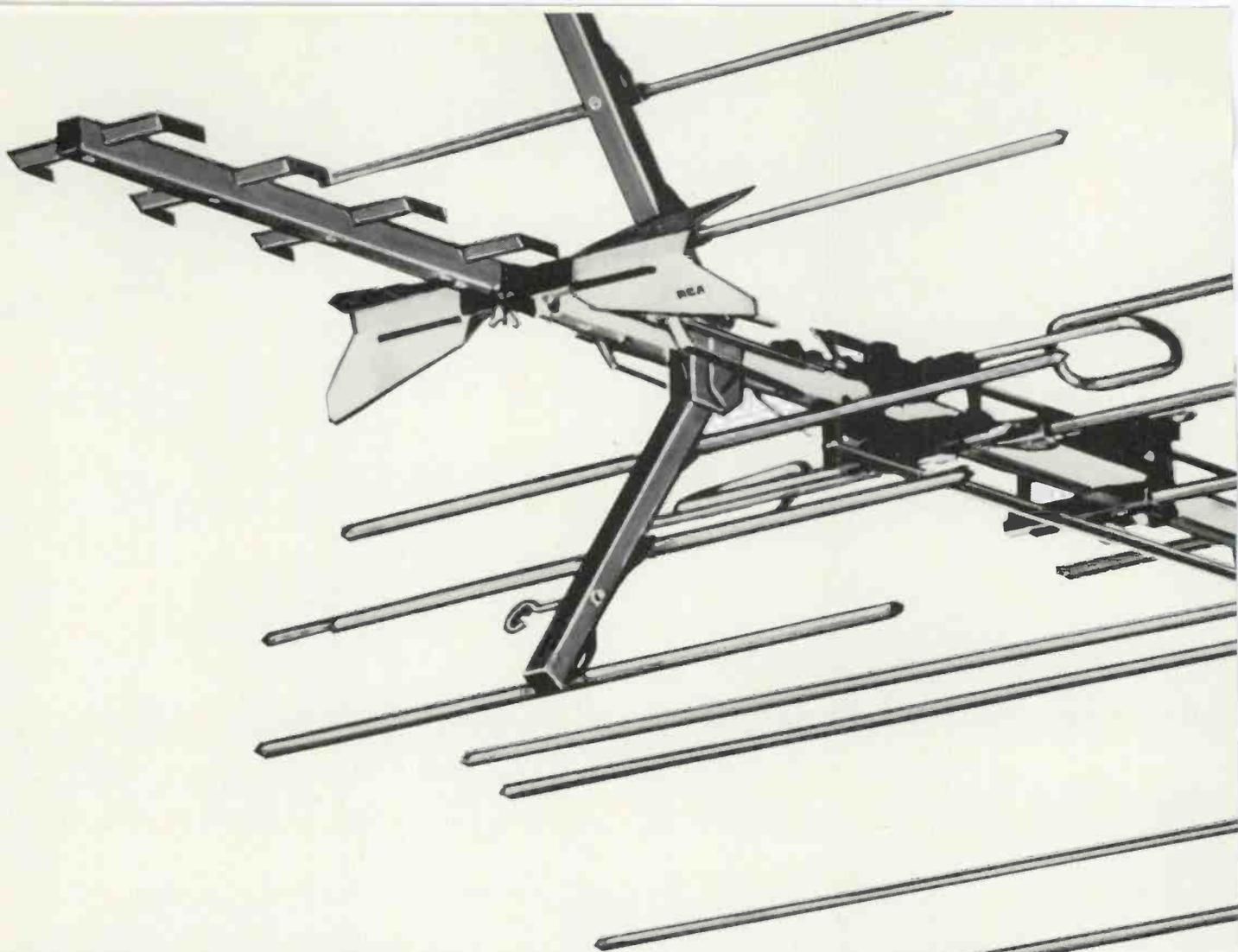**When
RCA engineers
put their minds
to antennas,
outstanding things
happen:**




RCA Permacolor

Permacolor is not just an improved antenna, it's a completely new antenna. New in looks. New in design. Very easy to set up and install.

And Permacolor is manufactured exclusively by RCA. Here are a few of its many unique features:

Permanent Connections.

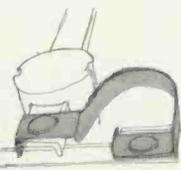
Any antenna is as permanent as its electrical connections. Particularly between the elements and the feed line. If a connection fails, ghosts, streaks, "noise," even total reception failure may occur.



On a Permacolor an aluminum strap solidly connects every active element to the feed line. Connection failure is virtually eliminated.

Tuned Circuits.

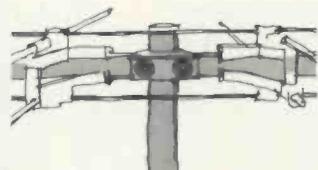Permacolor elements are integral parts of tuned circuits and many perform more than one function. Circuits stay "perma-tuned" because elements are permanently connected. Feed lines are unbroken aluminum strips perfectly balanced for optimum impedance match and minimum ghost pick-up.




Revolutionary Insulators.

Permacolor insulators are polypropylene, a tough, flexible, water-proof plastic with superior electrical properties. Their unique design includes many ribs and barriers to make leakage paths longer.

On a Permacolor, elements do not pivot. Instead, the elements are assembled right into the insulators. Each insulator, gripping 5½ inches of element, pivots as a unit. When the Permacolor unfolds, insulators snap in place and permanently lock to form a rigid truss. There's no point of high



stress along the entire assembly.

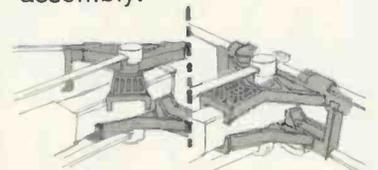

Superior Combinations.

UHF and VHF get bigger boosts on Permacolor combinations. On the corner reflector, the angle is increased to 110° for optimum efficiency. And for the first time, a bow tie is included. This best type of UHF dipole is integrated into a single download, made possible by a newly designed three-tuned-circuit coupling/isolating network.

RCA

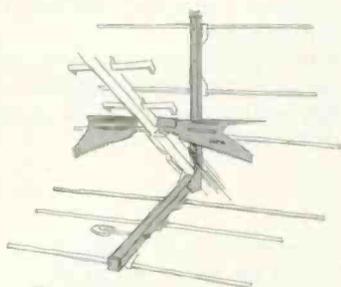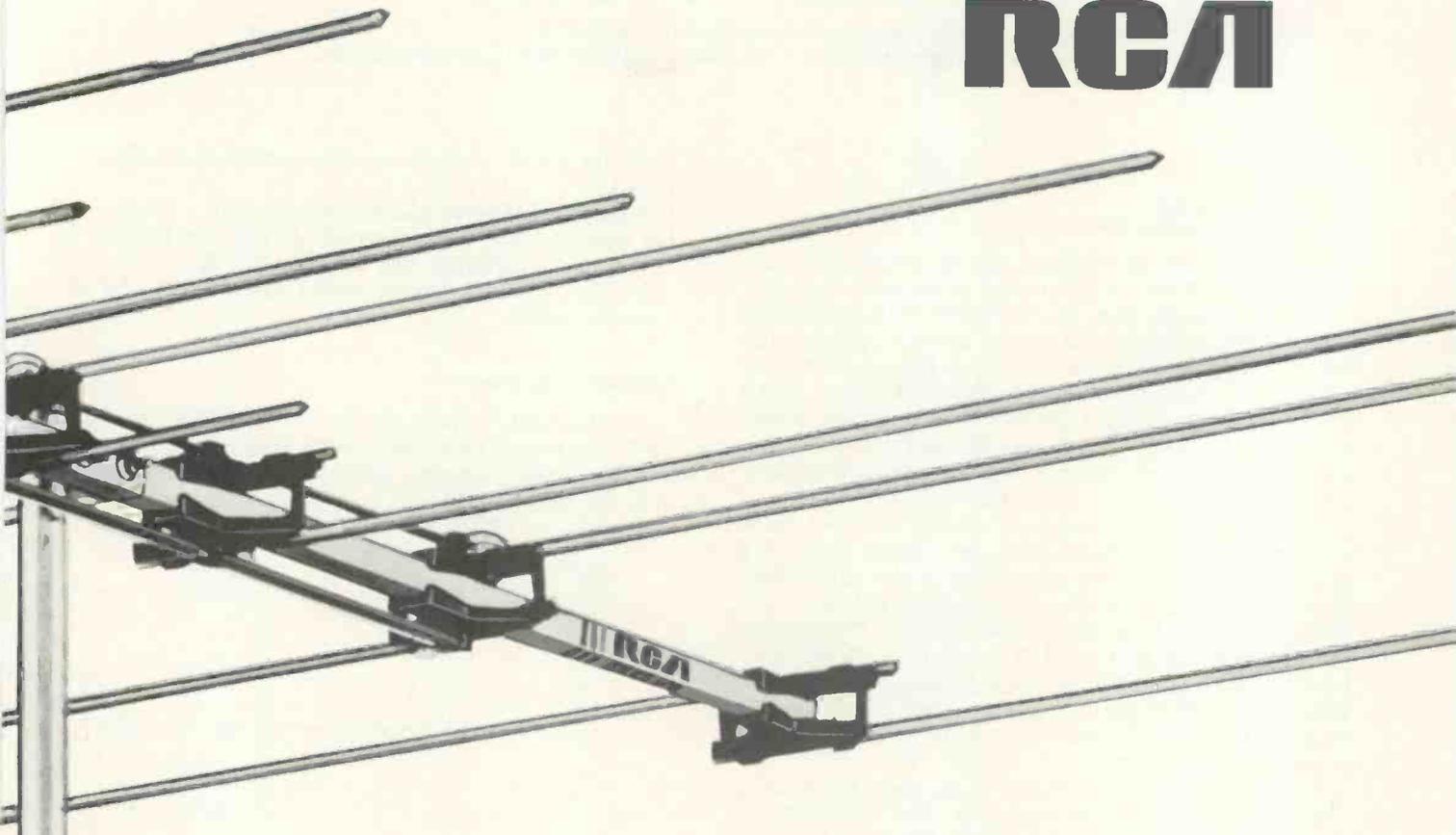

Permacolor combinations are uncompromising all-channel antennas.

Square Boom.

A square boom supports the Permacolor. And it isn't a feed line—it's at ground potential. Detuning effects that often occur when a grounded mast is coupled to a signal carrying boom are eliminated.

The mast clamp is heavy plated steel and locks

around the boom without rivets. A double set of serrated teeth take a vise-like bite on the mast to prevent slipping or twisting.

Goes Up Easier.

A Permacolor goes up in one piece. On the roof. Not on the ground. There's no bag of parts. There's nothing to take apart. An installer's job has never been easier or faster.


And installation is just as easy on larger models. A double boom gives added strength, yet takes up only 10 inches on the mast. This allows Permacolor to be placed closer to a

rotator, thus minimizing stress on the rotator as well as the mast.

Tough Finish.

Permacolor has a tough blue and gold vinyl finish on all aluminum parts—even the hidden areas. It's similar to the long-lasting coating on aluminum siding for homes.

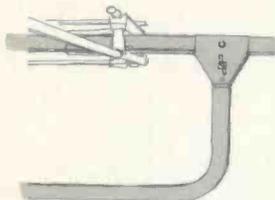There's not another antenna like the new, trim, clean RCA Permacolor.



See the complete line of Permacolor antennas today. Your RCA Parts and Accessories Distributor has them now.

Parts and Accessories Deptford, N.J.



**professional
hands require
years of training**

**professional TV
service dealers insist on
GE ULTRACOLOR picture tubes
(made by professionals for professionals)**

GENERAL  ELECTRIC

**TUBE DEPARTMENT
OWENSBORO, KENTUCKY 42301**



To service Color TV you need:

1. vectorscope
 2. color bar generator
- and you can't use one without the other!**



One Year Warranty

portable



for home or shop

only the V7 gives you both

- The only complete one unit color vectorscope/color-bar generator available anywhere!
- Completely portable for servicing color TV in the home . . . no need to bring set to the shop!
- The only one with detailed instructions on color circuit alignment and color adjustment. And, additional instructions are available as new sets are introduced!
- Recommended by leading TV manufacturers!
- Proven performance . . . over 4 years of use in field and shop by thousands of technicians . . . no other vectorscope manufacturer can make this claim!

V7

- Checks and aligns demodulators to any angle.
- Checks and aligns bandpass-amplifier circuit.
- Pinpoints troubles to a specific color circuit.

Exclusive Features: Self-Calibrating—adjust timing circuit without external test equipment, Dial-A-Line—adjust horizontal line to any width from 1 to 4. Plus: All Crosshatch, Dots, and Color Patterns; Voltage Regulated; Fully Enclosed Cable Compartment. Free copy of Wayne Lemon's Book, "Color TV Servicing Simplified with Vectorscope!" Net **19950**

Remember . . . V7—the complete one

See your distributor or write Dept. ET-5
LECTROTECH, INC.

4529 North Kedzie Ave., Chicago, Ill. 60625

... for more details circle 128 on Reader Service Card

ET/D TECHNICAL DIGEST


Q1 collector impedance is a very low value (essentially a short) as represented by the switch. R4, R5 and Q1 now act as a voltage divider and apply the correct grid bias to the CRT.

When the receiver is turned off, the voltage applied to the Q1 transistor base circuit decays faster than the boost voltage. As a result, Q1 is no longer forward biased and is essentially an open circuit. The "switch" is now open and there is no longer a voltage divider.

The boost voltage is applied through R5, to the control grid of the CRT. Control grid, G1 is now highly positive, at the same time the cathode voltage is near ground potential. As a result, the CRT conducts heavily and discharges any remaining charge at the anode and the spot is "killed."

Video Expander Diode

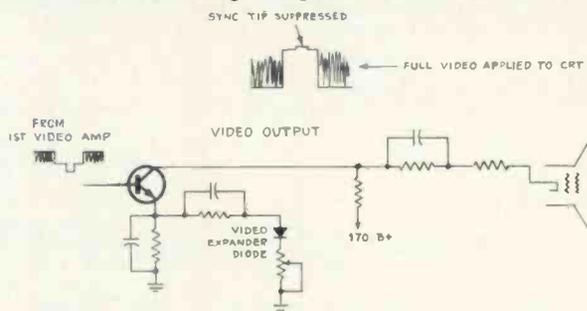The video expander diode allows greater contrast on the picture tube. This is achieved by eliminating the sync pulses of the incoming composite video signal from the




linear conduction range of the transistor.

The diode is in series with the contrast control and an RC circuit in the emitter return. The diode acts to bias the transistor just at the point of conduction for the pedestal level of the incoming signal, with the negative-going sync pulses below conduction. Sync pulses are 20 percent of the composite signal, which means that without this diode only 80 percent of the input swing can be for "black and white" information.

RCA VICTOR

Stereo VLT/VMT Series—Center Lid Opening

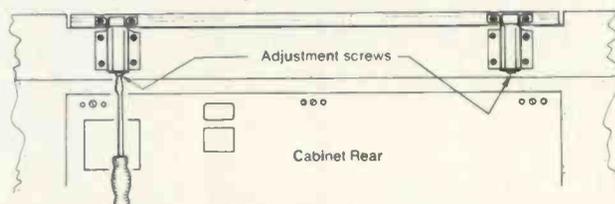Instruments using the center lift lids may be received with the lids jammed in the closed position. In most cases, this is caused by either a small amount of "Spray Lacquer" binding the hinges or the foam block placed between the lid and latch (for shipment) has been inserted wrong. In either case, follow the procedure outlined below.



- (1) Turn the adjustment screws (hinges) clockwise as far as possible (maximum tension).
- (2) Press down firmly on the lid to release the latch.
- (3) Open and close the lid several times to free the hinges. Then remove the foam block and clean any bits of foam out of the latch.
- (4) Readjust spring tension so that lid lifts 6 to 8 in. when unlatched.


POWERFUL

One \$100 Winegard Color-Wedge equals the performance of twelve ten-element yagis!

Sound impossible?

Then try one for yourself and see what a powerful performer the Winegard Color-Wedge is. Also available in the popular 82-channel version with comparable performance on VHF-UHF-FM (CW-1000, \$100.00 list).


Model CW-2000
VHF-FM
\$100.00 list

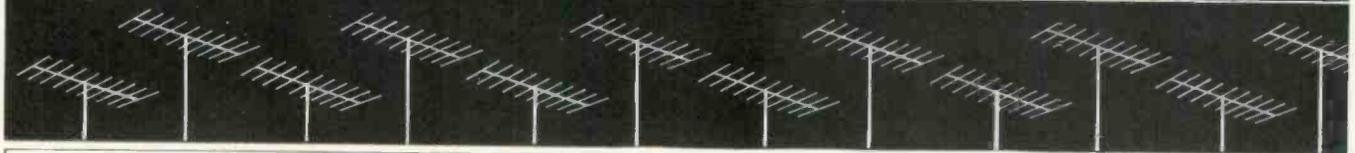

example A: CHECK DB GAIN

Channel	CW-2000	10-Elem. Yagi
2	7.2	7.8
4	7.2	7.6
6	7.4	8.0
7	12.2	10.8
10	11.4	11.0
13	12.0	11.5

example B: CHECK DIRECTIVITY

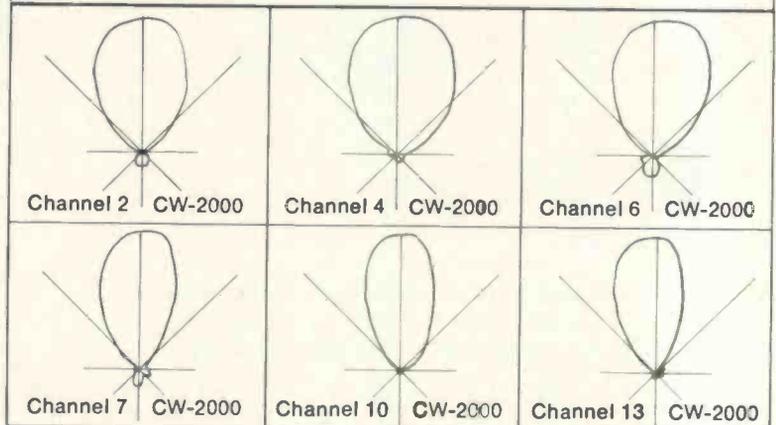


example C: CHECK FRONT-TO-BACK RATIO

CW-2000	CH. 2	CH. 4	CH. 6	CH. 7	CH. 10	CH. 13
DB	22	26	17	20	35	30

 **Winegard** © Copyright, 1969
® ANTENNA SYSTEMS

WINEGARD COMPANY • 3019-13 KIRKWOOD STREET
BURLINGTON, IOWA 52601

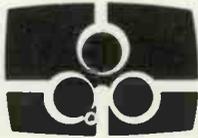SEE YOUR WINEGARD DISTRIBUTOR AND WRITE FOR FACT-FINDER #284




COLORFAX

The material used in this section is selected from information supplied through the cooperation of the respective manufacturers or their agencies.

MAGNAVOX

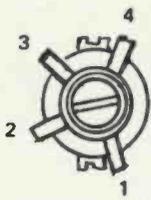Focus Transformer Part No. 360957-6—Terminal Identification



There is apparently some confusion in the field concerning the identification of terminals on this transformer when it is used as a replacement for the 360957-5. There is a blue dot located between terminals 3 and 4, however, this dot is not always clearly visible. The best way to identify these terminals is to view the transformer from the rear as illustrated and count the terminals clockwise from one to four.


Color TV Chassis T935—Horizontal Retrace Blanking

Early production models of the 1T5007, which uses the T935 chassis, could exhibit a horizontal retrace blanking line on the left video of the screen. This line shifts in the opposite direction of the video information when the horizontal hold control is adjusted.

The problem can be corrected by adding a series network consisting of a 15K, 1/2w resistor and a 1000pf, 500v capacitor between J13 (G1 of the CRT) and the junction of R406/C403. This circuit has been incorporated in later production.

Color TV Chassis T940—Increasing Range of ACC

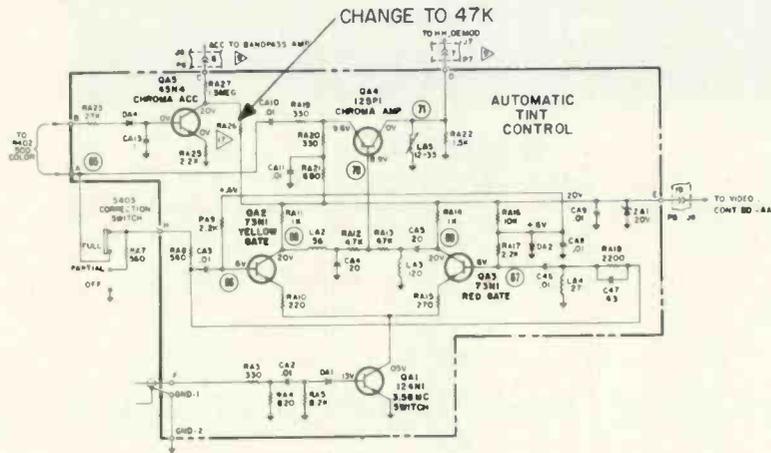
A recent production change has been made in the T940 chassis changing RA26 on the ATC board from 10K to 47K



in value. This change provides an increase in the range of the Automatic Chroma Control circuit to compensate for wider variations in chroma level in the transmitted signal.

Color TV Chassis T924/T939—Purity Shift

Some of these chassis have evidenced a tendency to shift purity when the instrument is turned on within a five minute period after having been turned off. The purity shift is not evident, however, if the set has been turned off for a period of time longer than five minutes. This problem can be eliminated by adding a 68K resistor across C302, in the power supply. This change has been made in later production of the T939 chassis.

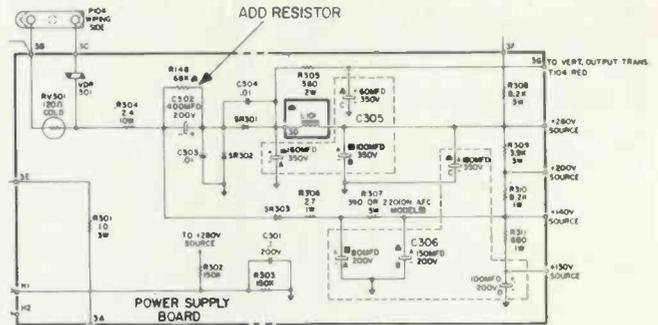


Remote Control Model 1C6313—Remote Sensitivity Control

If you should encounter a Model 1C6313, using the T939-06 chassis, on which the remote sensitivity control seems to have no effect, check the wiring of the control. If there is no connection to the center tap of the remote sensitivity control, connect a jumper wire between the center tap and the end terminal having the red wire connected to it.

RCA VICTOR

Color Remote Control TV "G" Series—Pilot Lamp Lead Dress

The remote color television receivers referenced to this bulletin use a twin-lead for power to the pilot lamp. In some instances (specifically after normal service operations and during reinstallation of the tuner mounting assembly), the "high" side of the lamp power lead could be accidentally "pinched" between the TMA bracket and chassis "shorting" the lamp to chassis. The following corrective steps are to be performed when the referenced receivers are serviced: (1) Make a visual check of the pilot lamp supply lines (twin lead) to find out if lead has been "pinched" or "shorted" by TMA bracket. (2) If lead has been pinched or shorted, remove TMA and place a "spaghetti" sleeve over the pilot lamp leads. (3) Check physical location of

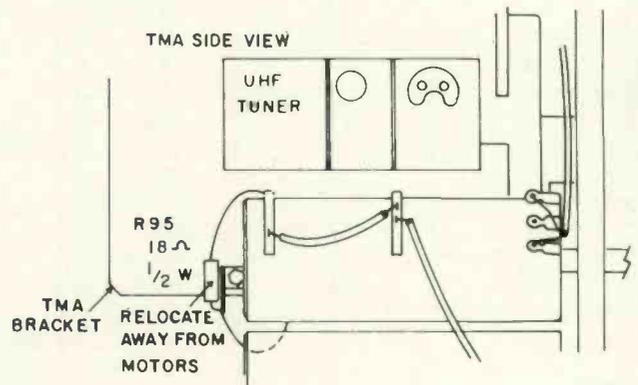

pilot lamp series resistor R95 (18Ω 1/2w). This resistor, shown in illustration, may be located in close proximity to the color remote motor. Take corrective action necessary (relocate terminal board leads, and/or "body" of resistor)

continued on page 70

Stack These Up Against The Others

your best buys in meters
come from Heath

For over 20 years, Heath has been the first choice in meters for tens of thousands of service technicians, schools and home labs. There's a reason for this continued popularity — Heath meters are designed to have that balance of versatility, needed features and low cost that make them your best buy. For the price of just a couple of meters from others, you can buy every meter Heath makes. We believe that you should still be able to get a stack of meters without spending a pile of money. When you need a meter, look to Heath. For performance, versatility and top dollar value, the others just don't stack up.

1 \$21.95* Buys A Portable Solid-State Volt-Ohm-Meter. Four ranges on AC & DC volts measure 1-1000 volts full scale. Four resistance ranges measure 0.1 ohm to 1000 megohms. Features convenient battery operation ... zero & ohms adj. controls ... DC polarity reversing switch ... spare jack for HV & RF probes ... rugged polypropylene carrying case. IM-17, 4 lbs.

2 \$31.95* Buys A Portable Volt-Ohm Milliammeter. Measures AC & DC volts 1.5-5000 full scale. DC current from 150 uA to 15A. Resistance midscale from 15-150,000 ohms. Large 4 1/2" 50 uA movement meter for extra accuracy. MM-1, 5 lbs.


3 \$29.95* Buys An Accurate VTVM. 7 AC & DC ranges measure RMS volts from 1.5-15000 full scale ... AC P-P from 4.0-4000 ... 7 resistance ranges from 0.1 ohms to 1000 megohms. 25 Hz — 1 MHz response. Single probe makes all measurements. IM-18, 5 lbs. Assembled IMW-18, 5 lbs. ... \$49.95*

4 \$41.95* Buys A Laboratory AC VTVM. Especially useful for low-level AC & audio work. Ten RMS ranges from 0.01-300 V full scale ... measures dB from -52 to +58. ±1 dB response from 10 Hz-500 kHz. 10 meg. input impedance. IM-38, 4 lbs. Assembled IMW-38, 5 lbs. ... \$49.95*

5 \$39.95* Buys A Big Service Bench VTVM. Has the same high performance as the IM-18 above, plus added features to make it more useful for service work ... separate 1.5 & 5 VAC scales ... calibration controls that are adjustable from the front panel ... versatile gimbal mounting ... large 7" meter. IM-28, 7 lbs. Assembled IMW-28, 7 lbs. ... \$59.95*

6 \$46.95* Buys A Big Solid-State Volt-Ohm Meter. Battery-powered portability plus built-in AC supply. 8 AC & DC ranges 0.5-1500 full scale ... 7 resistance ranges (10 ohm center scale) x1-x1 meg. High input impedance & 6" meter for greater accuracy. IM-16, 10 lbs. Assembled IMW-16, 11 lbs. ... \$69.95*

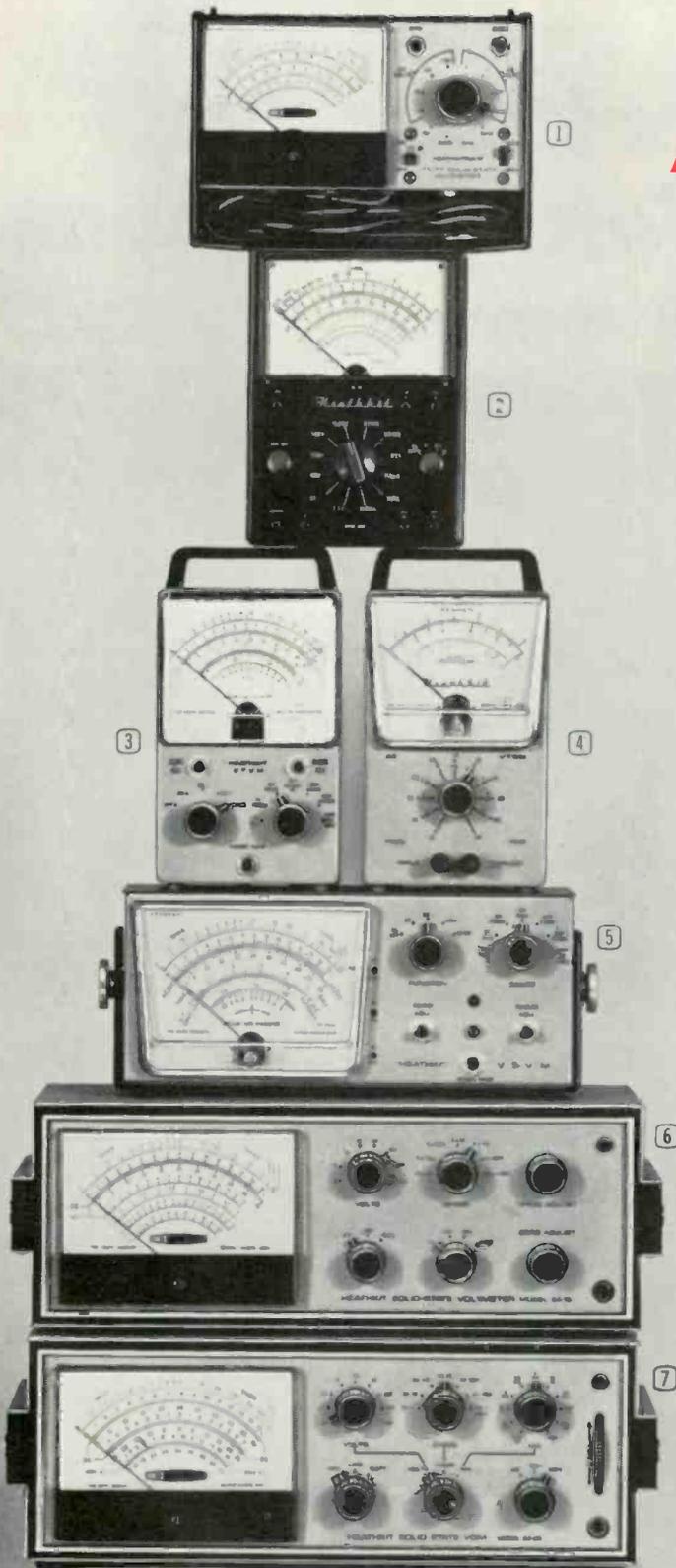7 \$85.00* Buys A Deluxe Solid-State Volt-Ohm Milliammeter. 9 AC & DC ranges from 150 mV-1500 V full scale ... 7 resistance ranges measure from 1 ohm to 1000 megohms ... 11 current ranges from 15 uA-1.5 A full scale. 100 kHz response ... high input impedance ... large 6" meter with zero center. IM-25, 10 lbs. Assembled IMW-25, 10 lbs. ... \$120.00*



a Schlumberger company

HEATH COMPANY, Dept. 24-5
Benton Harbor, Michigan 49022

Enclosed is \$ _____, plus shipping.

Please send model (s) _____

Please send FREE Heathkit Catalog. Please send Credit Application.

Name _____

Address _____

City _____ State _____ Zip _____

*Mail order prices; F.O.B. factory. Prices & specifications subject to change without notice. TE-221R





NEW

FREE 1970 CATALOG

Now with more kits, more color
Fully describes these along with
over 300 kits for stereo/hi-fi
color TV, electronic organs, guitar
amplifiers, amateur radio
marine, educational, CB, home
& hobby. Mail coupon or write
Heath Company, Benton Harbor
Michigan 49022.

You'll see better ideas clear through Ford's Econoline

Small wonder it outsells all other vans

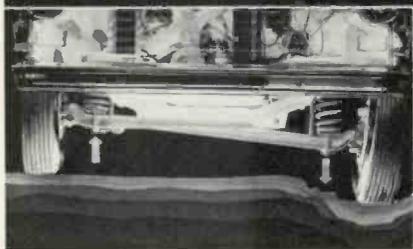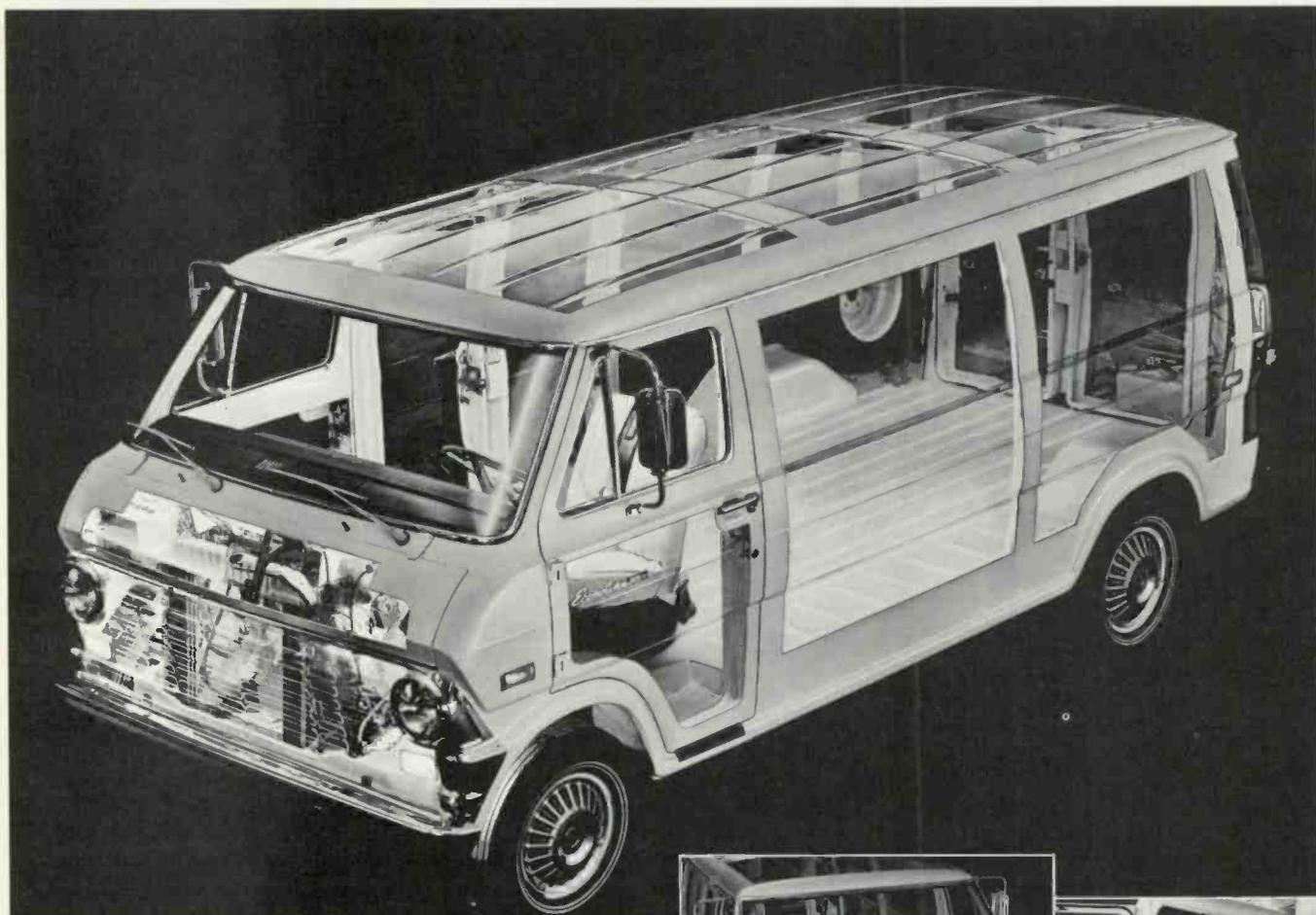

Twin-I-Beam ride. The independent front suspension made famous by Ford pickups: Twin-I-Beam. Two I-beam axles for strength... big coil springs for easy ride. Twin-I-Beam gives you greater stability, less wind wander, and a better ride. Only Ford has it.

"Walk-thru" to rear. Because the engine is forward out of the way, the driver can step from his seat into the load area and exit through side or rear doors. The loadspace is not only bigger than in older vans, it's easier to reach. See all the better ideas in the best selling van at your Ford dealer's.

Outside service center. Just raise the hood, and all these service points are at hand: oil, water, battery, windshield-washer water, wiper motor, brake master cylinder, voltage regulator. Ford's better idea vans make everything you do easier to do.

Greater payload than ever before. Now Ford vans can take on loads that vans never before were designed to take. Choose from three Econoline series and two body lengths. Power choices include two economical Sixes and a top-performance 302-cu. in. V-8.

FORD ECONOLINE VANS



... for more details circle 114 on Reader Service Card

We've finally succeeded in dividing the country.

Nothing military. Simply a 5-way split, so that we can offer you a Panasonic Replacement Part Depot close enough to call home.

Our intention is not to sell you parts to put in other manufacturer's products. (Although you may wind up doing just that!) All we want to do is to provide you with genuine Panasonic parts when they are needed.

Last year alone, several million people bought our TV's, radios, phonographs, tape recorders, etc. And while we don't manufacture our products with planned obsolescence in mind,

certain parts will wear out. No amount of quality control can put an end to that. So when a customer with a Panasonic product comes in and you determine that it requires a part which is not in your inventory, don't turn him away. Order a genuine Panasonic part.

A part which is more than just a replacement. Because each and every Panasonic component is made by Panasonic, engineered by our scientists and technicians to provide maximum efficiency and reliability. Quality Control is not just another factor in our manufacturing process; it is our manufacturing process.

Take tubes and transistors, for instance. For TV. For radio. You name it. *Nobody in the world makes a better tube or transistor than Panasonic.* That's a fact. And we know that nobody can fool *you* about component quality.


One last thing. When you replace Panasonic with Panasonic, you won't have to concern yourself with call backs. We make it right the first time.

So the next time you don't find what you're looking for on the shelf, order it from the Panasonic Parts Depot serving you. Panasonic parts for Panasonic products. It makes sense.

LOS ANGELES
2121 Yates Avenue
City of Commerce, Calif. 90022
(213) 723-6271
TWX 910-580-1960

CHICAGO
371 N. 3rd Avenue
Des Plaines, Illinois 60016
(312) 299-8886
TWX 910-233-2641

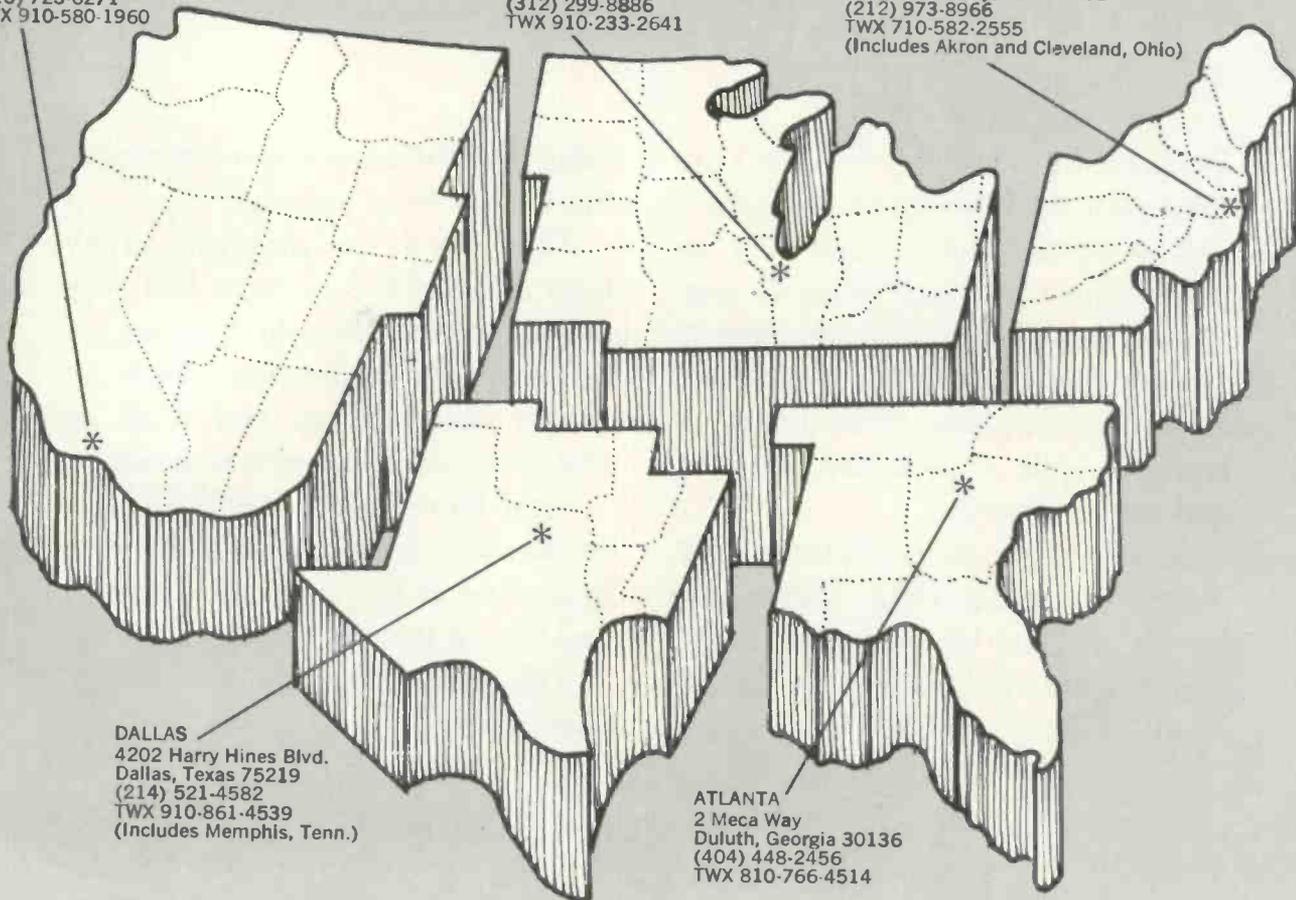NEW YORK
10-16 44th Drive
Long Island City, N.Y. 11101
(212) 973-8966
TWX 710-582-2555
(Includes Akron and Cleveland, Ohio)



DALLAS
4202 Harry Hines Blvd.
Dallas, Texas 75219
(214) 521-4582
TWX 910-861-4539
(Includes Memphis, Tenn.)

ATLANTA
2 Meca Way
Duluth, Georgia 30136
(404) 448-2456
TWX 810-766-4514

PANASONIC®

just slightly ahead of our time.

... for more details circle 131 on Reader Service Card

Matsushita Electric Corporation of America
National Headquarters, Service and Parts Division
10-16 44th Drive, Long Island City, N.Y. 11101

Are you going to sit on the sidelines all your life?

Don't get the idea it's safer sitting on the bench than joining in the battle.

The battle your community is fighting right now isn't going to stay in the playing field. The battle against crime, against drugs, against despair, against deprivation. That battle is going to spill all over the sidelines and into the stands.

It already has, in many places. And it can do it again. Here. Unless you get up off your big fat complacency and into the fight. Unless you give a hand to those who are working to

solve the problems—the volunteers of the United Way agencies.

They know the problems. They have a lot of the answers. But they need you. Your strength. Your enthusiasm. Your know-how. Pick an agency that interests you. Call up and make a date to see how it works.

Who knows? You could find the battle more satisfying than the sidelines. And in the long run, you may find it a lot less risky.

**This year, give more than money.
Give you.**

Space contributed as a public service by this magazine.

ET/D TEKLAB REPORT

Receiver service by panel substitution has simplified troubleshooting—but in-depth servicing requires circuit knowledge

Introducing Motorola's Quasar II Color TV

■ Expanding the “works in a drawer” concept Motorola introduced the Quasar II, employing the TS-934 color chassis. The plug-in panel arrangement used in this chassis is similar to the TS-915/919 chassis which is the top of the line chassis.

The TS-934 hybrid chassis employs six mini-circuits that plug-in and are all solid-state with the exception of four tubes.

Tubes are employed in the vertical oscillator and vertical output, horizontal driver, horizontal output and damper circuits.


We found a number of important features employed on this chassis which include: Automatic Fine Tuning (AFT), transformer powered, solid-state HV rectifier, automatic degausser, integrated circuits used in

the sound and color demodulators, regulated low voltage supply, automatic color control and double gated automatic control.


Viewing the set from the front we found the customer controls conveniently located on the front panel with the exception of the horizontal hold control which is located on the chassis but should seldom need adjusting, and the TINT control which is employed on the TS915/915 chassis is eliminated.

The chassis can be pulled forward for servicing, by removing one ¼ in. hex head screw near the ac interlock and releasing the chassis lock. This can be done without removing the back cover.

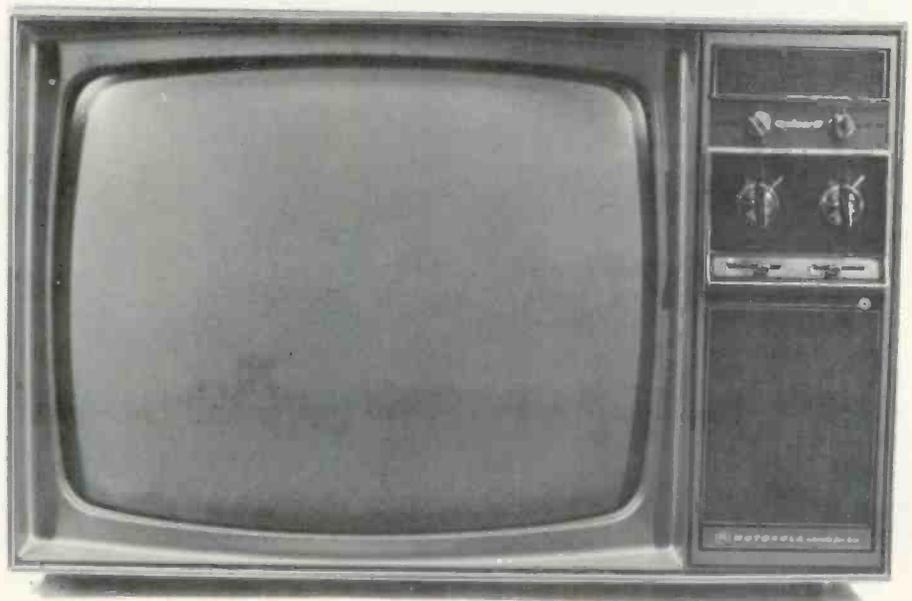After we pulled the chassis forward a number of features were re-



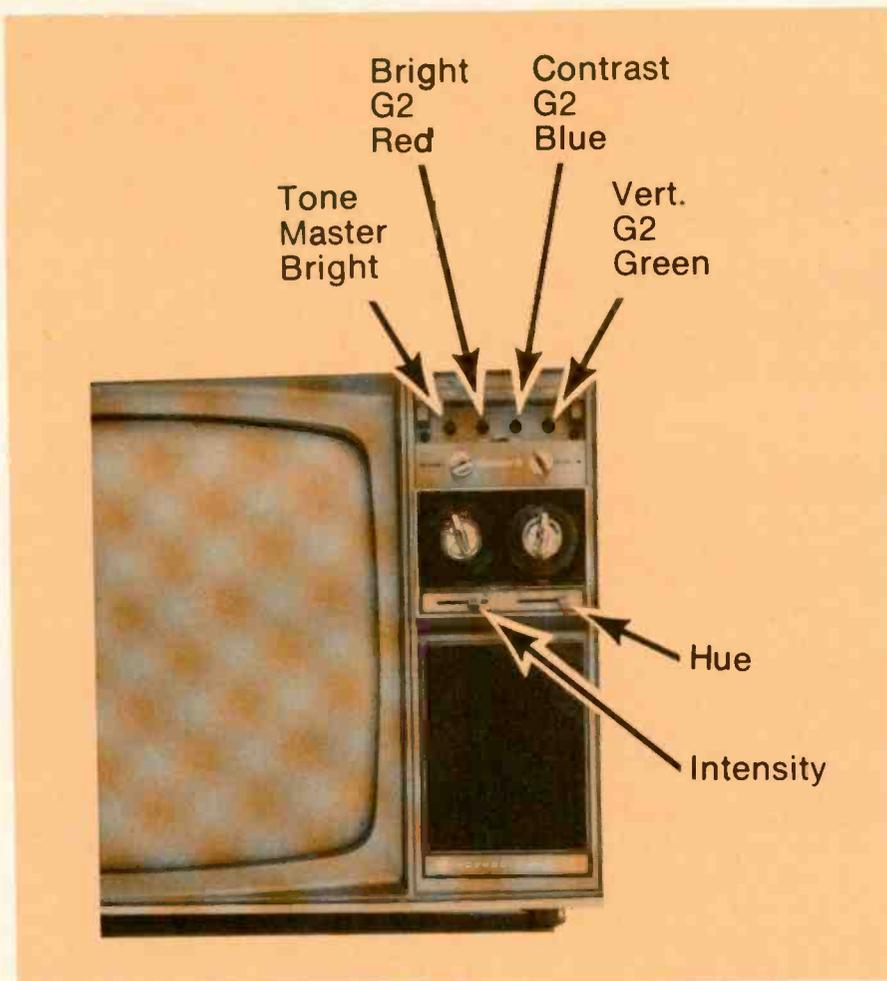Motorola's Quasar II, Model WT678FW, employing the TS934 Color Chassis.



A flip-down panel conceals the hollow shaft dual purpose controls. The two-color controls are the slide throttle type for the adjustment of the color and hue.

vealed of interest to the service technician. The convergence panel is up front, the tuner is placed in the open for easy cover removal if cleaning is needed, and by removing three screws the control panel swings open on a hinge for component and control replacement if needed. The tuner has provisions for 300 or 75 Ω input.

The panels are conveniently located and all the panels can be removed with the chassis pulled forward and the components can be changed without removing the chassis from the cabinet.

If it should become necessary to remove the chassis, all wires have Molex connectors and by releasing a chassis lock the chassis can be removed from the slide rail mounting.

Viewing the set from the rear we found the low voltage transformer and horizontal output circuits mounted on a separate chassis in the center rear portion of the cabinet.

Many of the service controls that are adjusted during the set-up procedure are factory pre-set and nor-

mally require no adjusting. The controls in the HV circuits are cemented and require no adjustments, but if component replacement is necessary make sure you use exact replacement close tolerance parts.

Troubleshooting by panel replacement in home chassis servicing can be done if you carry a complete set of replacement panels.

The suggested exchange list price of the panels range in price from \$6.50 to \$18.00 apiece.

If you should decide to repair the panel circuits, you should have an idea how the circuits function. We will review the new circuits.

This month's TEKFAK schematic No. 1296 has complete coverage of the circuits used in this chassis.

POWER SUPPLY

The power supply shown in Fig. 1 employs voltage regulation on the 20v line supplying most of the transistorized circuits. The dc regulator panel providing this voltage operates from the 27vac winding on the transformer. This output is adjust-

able and uses a Zener reference and amplifier. A current limiter prevents the current from exceeding a predetermined maximum.

THE DC PATH

DC coupling is employed from the second detector through the "IC" all the way to the CRT. Forward bias for the first video amplifier is established by R1 and R2. The second video amplifier also conducts as a result of voltage applied to the base from the emitter of the first video amplifier.

It is important that the correct dc be applied to the "IC" as this is the bias voltage for the first stages in the "IC." The resistors R3, R4, R5 and R6 determine the voltage across the contrast control, the control being a part of this voltage divider.

Because these stages are direct coupled, a defect in the video amplifiers can cause a change in brightness, as well as a detrimental effect on video. An open video amplifier transistor, for example, will cause excessive brightness, whereas a shorted stage will reduce brightness.

ACC AMPLIFIER AND COLOR KILLER

The ACC amplifier, shown in simplified schematic Fig. 2, is the first stage of a solid-state switch and in the absence of a color signal neither stage conducts. When a color signal is being received, 3.58MHz CW signal from the crystal output amplifier is present at the ACC rectifier (in the amplifier base circuit). The resulting positive voltage turns on the ACC amplifier and the collector voltage drops. Direct coupled to the preceding stage, this negative going voltage turns on the killer transistor (PNP) and the collector voltage becomes positive. To improve the action of this circuit, it is made regenerative by a resistor from the collector of the killer and is returned to ground through the color intensity control. Positive voltage developed at the collector biases on the 2nd color IF amplifier and the gain in the 2nd color IF is determined by setting of the INTENSITY control.

Bias for the first color IF is set up by voltage dividers to provide maximum gain, but is automatically reduced depending on color sync amplitude. The dc voltage on the collector of the ACC amplifier is proportional to the amplitude of the

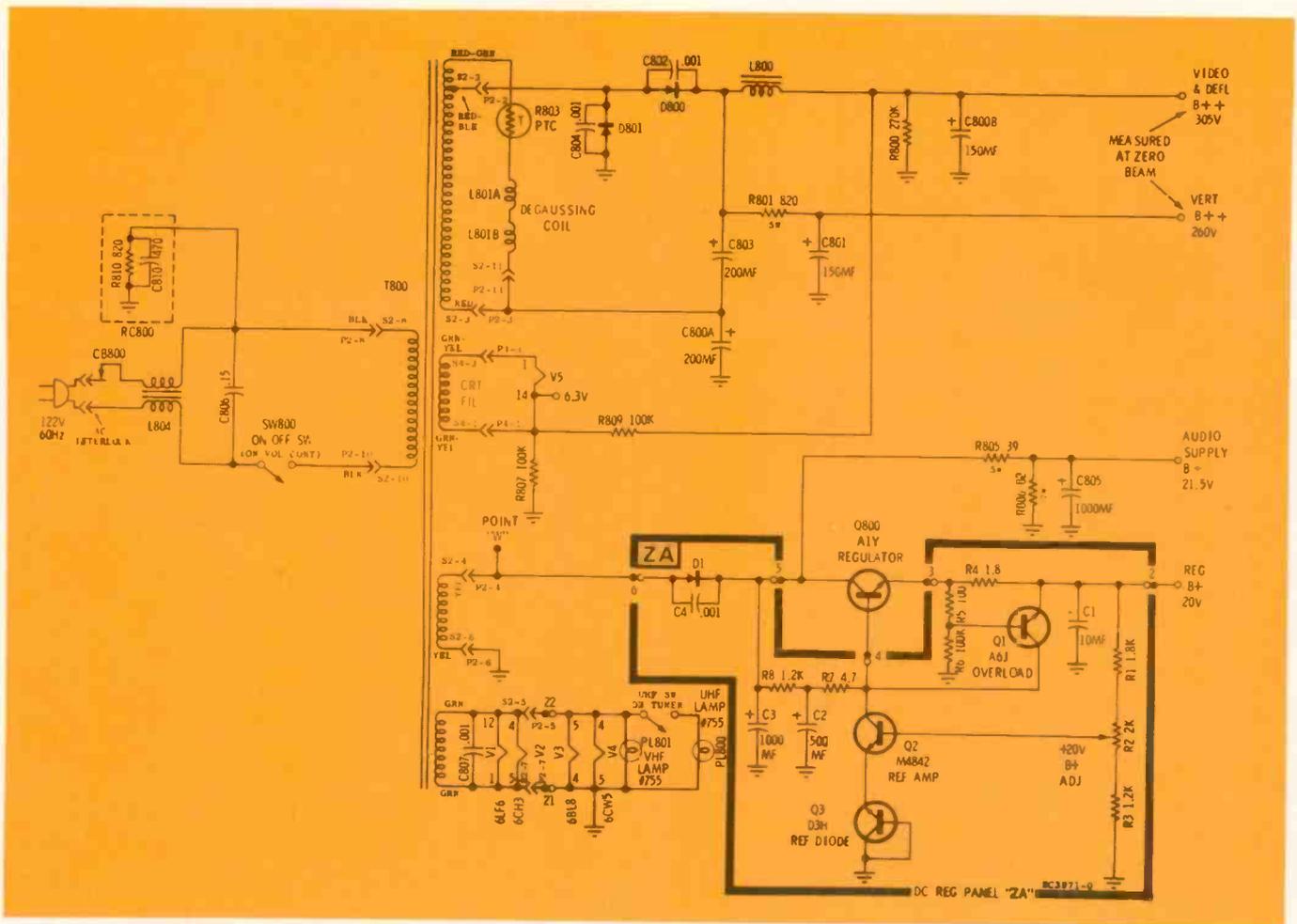


Fig. 1—A schematic of the low voltage power supply with voltage regulation on the 20v line which supplies most of the transistorized circuits.

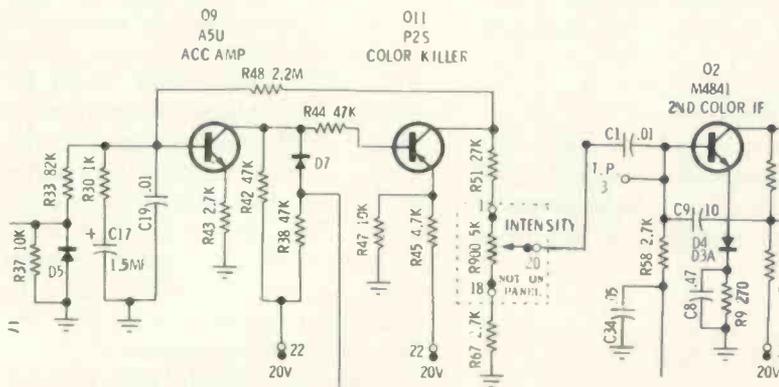


Fig. 2—The ACC Amplifier and Color Killer circuits.

3.58 CW signal applied to the ACC rectifier. As this amplitude increases, the collector voltage on ACC amplifier decreases, forward biases the ACC delay diode and reduces the gain of the first color IF.

CRYSTAL DRIVER, AMPLIFIER AND 3.58MHz OSCILLATOR

The crystal driver stage receives the 3.58MHz color sync signal from the gated color sync amplifier. This

is an emitter follower stage and drives the crystal to supply a CW signal. The 4.7pf capacitor is approximately equal to the crystal capacity to cancel noise which could otherwise be coupled through the crystal capacity.

The Q is reduced to increase bandwidth by placing a 390Ω resistor in series with the crystal.

The burst of color sync and the resulting output from the ringing

crystal, is applied to the crystal output amplifier. This stage is degenerative (and dc stabilized) by the 100K resistor from collector to base.

The oscillator is a modified Colpitts, free running at about 3.58-MHz. It is locked in frequency and phase with the transmitted color sync when a color signal is received. A very small capacity is used to couple the 3.58MHz signal to control the oscillator. Output of the oscillator is taken from the emitter through a low impedance-isolation network to the phase splitter. Some phase correction is introduced by the 5.6µh choke.

The crystal output amplifier also supplies a 3.58 CW signal to the ACC rectifier to develop a positive dc voltage to turn on the ACC amplifier. The only adjustment in these stages is the 3.58MHz oscillator coil.

Next month we will review the Red, Blue and Green Video Output stages, the IC Color Demodulator, Horizontal Oscillator Driver and Output stages and the Audio IC Circuit employed in this new chassis.

High-Powered Tuner Amplifiers

by HOMER L. DAVIDSON

Some fairly simple servicing techniques can be developed by technicians that understand how these solid-state amplifiers function

■ Some of the amplifiers found in solid-state AM-FM tuners are rated as high as 50 to 500w. These deluxe stereo models may incorporate up to 50 transistors and 25 diodes, and their frequency response usually ranges from 25Hz to 22kHz.

Most stereo combinations use from 6 to 12 speakers, including horns and additional speaker jacks. These speakers may be in a combination cabinet or in separate shelf and console floor models.

The solid-state circuits are quite common throughout all AM-FM tuners. Some models do have additional features within the tuner circuitry. This service article, however, deals primarily with the audio portion of these units.

CIRCUIT ISOLATION

Before attempting to signal trace the defective stage of the audio amplifier, try to isolate the trouble to a given section. Should the tuner section be functioning properly, then the trouble must lie in the audio portion. See if the stereo phonograph plays through both audio channels. Also, see if the FM stereo multiplex

section is functioning normally. For instance, if the stereo multiplex section is functioning and one channel is dead on phono position, suspect a defective phonograph cartridge. If the phonograph section is normal, but FM stereo music comes from only one set of speakers, suspect a defective multiplex section. Always try to isolate the trouble to a certain section of the AM-FM chassis (a block diagram of one such chassis is shown in Fig. 1).

Select the proper circuit diagram, isolate and locate the troubled section upon the diagram and chassis—most tuner-amplifier sections are stacked and these units must be separated if the audio portion is to be properly serviced. Always take a top and bottom layout view of the isolated section (Fig. 2), making sure you have the correct section before attempting to locate the defective component.

SIGNAL TRACING

A defective stage in the audio section can be located with either signal tracing methods or voltage measurements. An audio-signal generator

(possibly of pencil-type design) should be used in locating weak- or low-signal conditions. Start with the volume control and go from collector to base of each audio stage. In high-grain pre-amplifier and driver stages, simply touch the pencil probe to the metal cover of each transistor and notice the gain of each audio transistor.

If the pre-amplifier (Fig. 3) and driver (Fig. 4) stages are not performing, start at the audio output transistors and work towards the volume control. Dead channels are easy to locate, while intermittent and low-signal losses are more difficult. Use a scope in conjunction with the audio-signal generator to locate a weak stage, comparing the weak stage with the good audio channel.

Many times when an audio-signal generator or VTVM test probe is applied to the base terminal of a suspected transistor, the stage will begin to function. Normally, this transistor is intermittent and should be replaced. Do not overlook the possibility of a second defective transistor in a directly connected transistor stage. *Be very careful not to short the base and collector terminals together with the test probe.*


VOLTAGE MEASUREMENTS

After the defective stage has been located, take voltage measurements of the suspected transistor, using either a VTVM or FET VOM for correct low-voltage measurements (Fig. 5). When one transistor is defective, erroneous voltage readings will be noted on direct-driven transistors. This makes it much more difficult to locate a defective transistor with voltage readings in a direct-driven circuit. Generally, the transistor with the greatest change in voltage is the defective one. The suspected transistor should be removed from the etched board and tested.

Collector voltages in the pre-amplifier section will vary from 2.5v to 16v. Emitter and base voltage readings are from 0.12v to 2v. Remember that voltage readings taken in the pre-amplifier circuits are very low compared to those in the main amplifier section.

The audio-frequency and driver transistors have collector voltage readings from 2.5v to 35v, while some power output collector voltages may go as high as 75v. Emitter and base voltages are from 0.12

Fig. 1—Block diagram of a typical solid-state stereo amplifier.

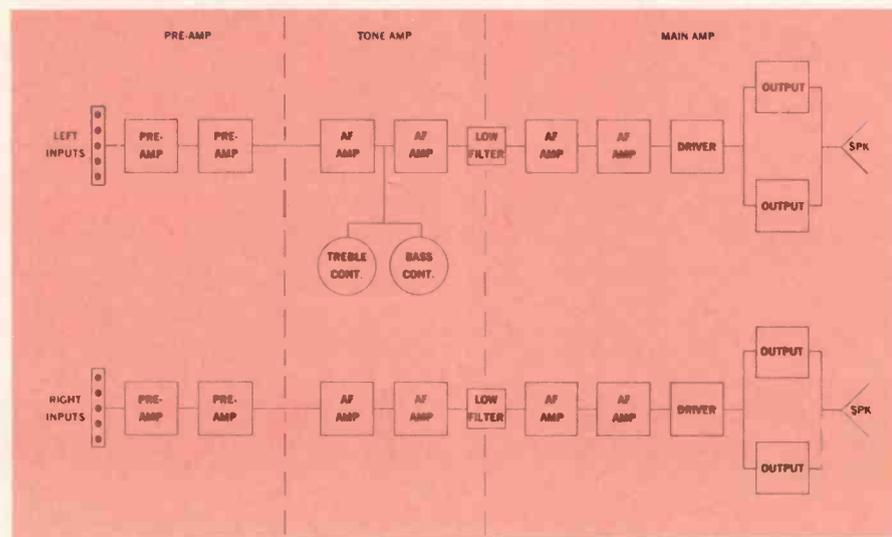

8v, while in the direct-driven circuits the collector terminal of the first transistor and the base terminal of the driven transistor have the same voltage.

Resistance measurements within these transistor circuits are not accurate. Base and emitter resistor measurements should be made with the transistor out of the circuit. Emitter resistors in the power output stages will vary from 0.18Ω to 0.47Ω . Always remove one end of a suspected diode or resistor to be

sure of a correct reading.

CHECKING TRANSISTORS

In-circuit transistor testing may be accomplished in the pre-amplifier and driver stages without high-leakage indications. Even transistors in the direct-driven stages may show an open condition. Proper leakage tests on direct-driven transistors should be made with either the collector terminal or the entire transistor removed from the circuit board.

Many in-circuit transistor tests

will show an open or shorted condition, but a small amount of leakage may not indicate the transistor producing distortion. When in doubt, replace the suspected transistor. Transistors cause about 75 percent of the trouble found in the audio section. When making transistor tests, make certain that the transistor polarity switch is in the correct position. Leakage readings are very high when the polarity is wrong.

It is best not to use an in-circuit tester on a suspected intermittent audio transistor. In many instances, when a beta tester is attached the intermittent transistor will "pop" on.

Several tests should be made before removing the suspected transistor. An intermittent transistor can be located by applying heat or squeeze spray. Always have the audio section operating when spraying the suspected transistor. Spray the transistor several times before removing it. Sometimes intermittent plastic transistors begin to act up when twisted. Double check the suspected transistor with a transistor test out of the circuit.

When one power output transistor has a shorted or leaky condition, always check the other power transistors. These transistors can be checked in the circuit with their collector terminal wire removed. Remember, power output transistor leakage readings are very low compared to other audio transistors. Properly matched audio output transistors will have close beta and leakage readings.

TRANSISTOR REPLACEMENT

Always test the replacement transistor before mounting it on the printed-circuit board. Be very careful not to damage surrounding components when soldering connections on the etched board, and use a heat sink or a pair of long-nose pliers to protect the new transistor when soldering the small terminal wires. Make sure the replacement transistor terminals are not touching other components.

Apply silicone grease to both the power transistor and its heat sink. Check to see if a thin piece of insulation had been used between the transistor and heat sink. It should be replaced if a new one was provided with the replacement transistor. Replace the small plastic insulators (if found) between the transistor and


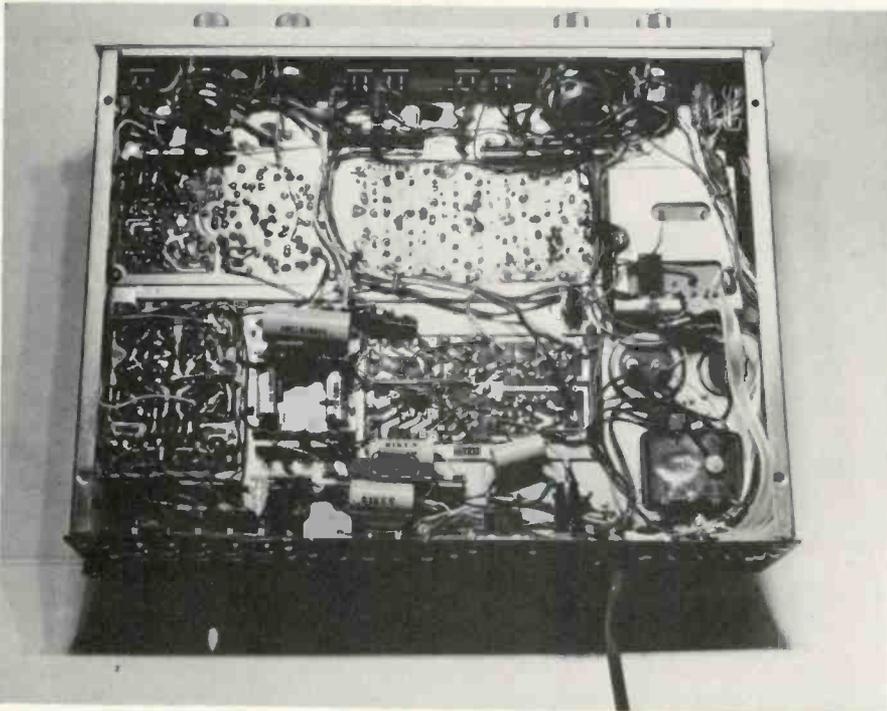


Fig. 2—Check the bottom wiring area with the top section before attempting to remove a defective component.

Fig. 3—A solid-state circuit in the left-channel pre-amplifier of a typical receiver.

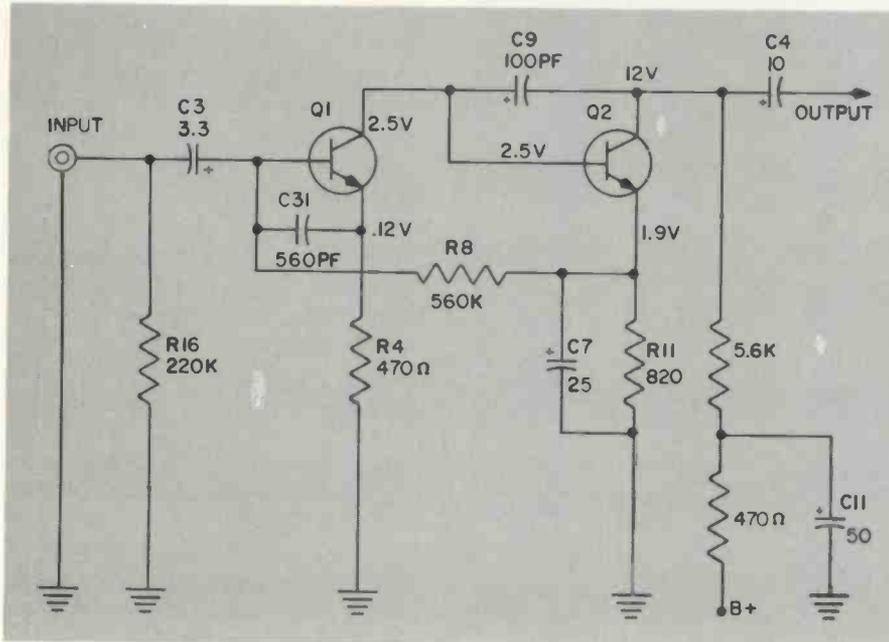

mounting screws. Before connecting the terminal wires, take an ohmmeter reading between the transistor body and metal heat sink. This may save hours of frustration. A short between the heat sink and transistor can produce distortion and arcing conditions.

Both power output transistors should be replaced when one is found to be shorted or leaky. When

exact transistor replacements are not available, a matched pair of universal power transistors should be used. All power transistors should be checked in both stereo channels when one or more leaky transistors are found.

AUDIO DISTORTION

Extreme audio distortion is generally found in the power output

stages. When very weak sound and extreme distortion occurs, it can usually be located by power transistor replacement. It is also helpful to check for visual signs of burned bias resistors around the power transistors, following the circuit from burned resistor to corresponding power transistor. Always check the condition of the base- and emitter-bias resistors when a shorted or leaky power transistor is found.

Very weak distortion can be located with an audio-signal generator and scope. After using these test instruments to locate the distorted stage, make voltage measurements and test the suspected transistor out of circuit.

When distortion is noted in the pre-amplifier or driver stages, comparison tests can be made against the good audio channel. Feed the same audio signal into both channels and take comparison waveforms of each stage, suspecting a defective transistor or bias resistor as the cause of distortion. A dried out or leaky coupling capacitor may also produce weak or distortion conditions. Distortion meters are handy test instruments for locating distortion problems, but they usually are quite expensive for the small service shop.

DEFECTIVE POWER SUPPLIES

Most tuner amplifiers have power supplies containing transistor and zener diode voltage regulation (such as the power supply shown in Fig. 6). They generally also contain a step-down transformer in either a bridge or fullwave rectifying circuit, using single or multi-section silicon rectifiers. A defective power supply should be suspected when no sound is heard in either audio channel.

Most power supplies are protected by low-amp fuses or circuit breakers. When fuses are being blown as the power switch is turned on, suspect a shorted silicon diode. Should the fuse blow after some sound has been heard, there is probably an overloaded condition in the circuits connected to the power supply.

If the power supply seems defective, check the condition of the silicon diodes. A good diode will measure 10Ω in one direction, with no resistance reading when the test leads are reversed. Always remove one lead of a suspected diode for


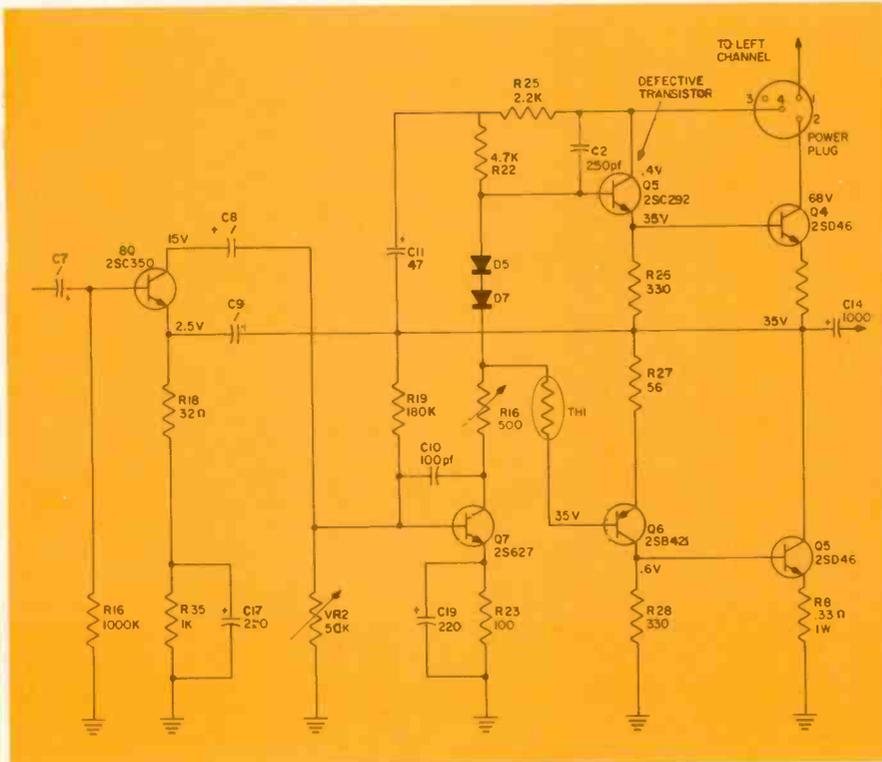


Fig. 4—A solid-state main-amplifier circuit in the right channel of a Kenwood Model TK88U receiver.

Fig. 5—Taking voltage measurements in the audio output stage of a General Electric chassis.

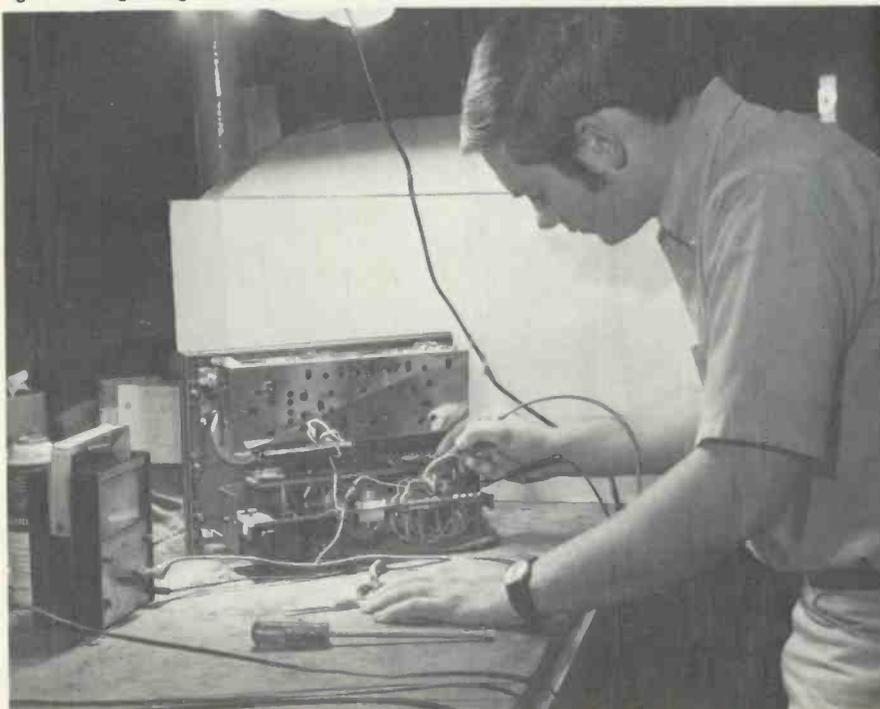

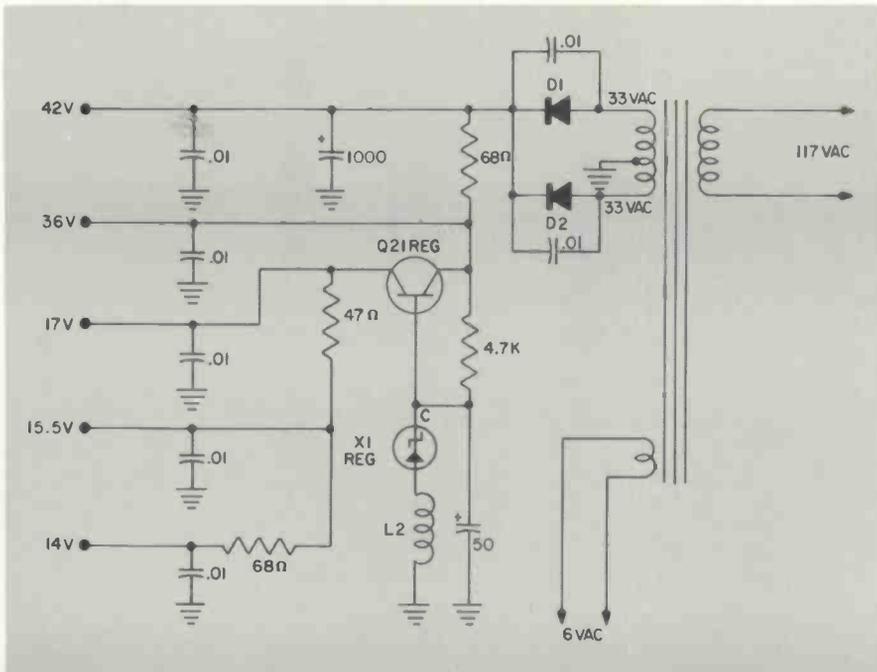


Fig. 6—Most tuner amplifiers have power supplies containing transistor and zener diode voltage regulation.

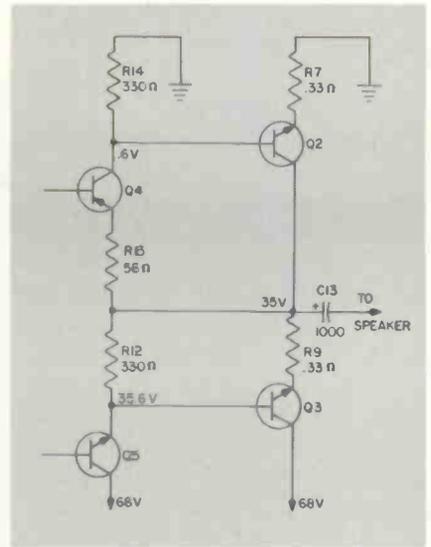


Fig. 7—A solid-state amplifier circuit in a Kenwood Model TK140 chassis.

network before turning the amplifier on—transistors in the power supply and audio circuits can be damaged when shunting a large capacitor when the power is on.

BLOWING FUSES

A Kenwood AM-FM Model TK88U would blow 2 amp fuses. The silicon diodes were checked and found good, and the overloading conditions appeared to be outside the power supply circuits. A 500ma meter was inserted in the power supply output and a heavy current was indicated. Each voltage lead was then removed from the voltage source until the lead containing the overload was found.

In this instance the overloading condition was in the push-pull output stages (Fig. 4). Power-output transistors Q3 and Q5 were removed from the circuit and measurements indicated that transistor Q3 had high leakage. Before replacing the output transistor, bias resistances were checked and a bias diode (D7) was found open. Its replacement solved the overloading condition.

DEAD RIGHT CHANNEL

The right channel in a Kenwood Model TK140 receiver was dead on both the FM and phonograph stereo positions. Signal injection indicated that the trouble was in the power output stages (Fig. 7). Transistors Q2 and Q3 were then removed from their heat sink and tested. Both power transistors had high leakage with low beta readings. These 2SD46-type transistors were replaced with RCA SK3027 universal-

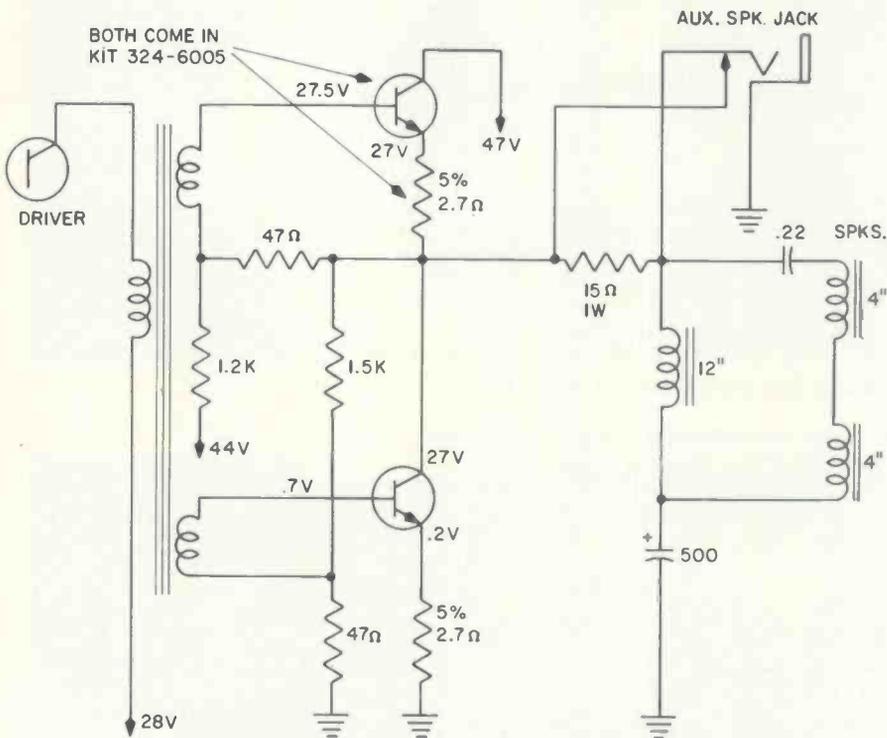


Fig. 8—The audio-output circuit in a Philco N255T chassis.

correct resistance measurement. Most silicon diodes will appear open or shorted, and one or more diodes may be damaged in a bridge-type circuit.

When overloading conditions exist outside the power supply, try to isolate the defective stage. Insert a current meter in the power supply voltage source and clip off each wire leading to tuner and amplifier circuits until the overload condition is

indicated. Most overload conditions are traced to the power output stages of the amplifier.

Excessive hum in the speaker can be caused by a defective transistor or filter capacitor. With the volume control turned down, isolate the hum in either the amplifier or tuner. Most loud hum conditions are traced to the filter decoupling capacitor networks. Shunt a large electrolytic capacitor across the suspected filter

type transistors, which corrected the problem.

IMPROPER LOADING

The owner of an AM-FM stereo Philco combination Model N255T had connected several outside speakers and damaged the solid-state amplifier. One power-output transistor was found open and two others had high leakage. The etched circuit board (Fig. 8) smelled of burned resistors.

Special output transistors were ordered from Philco as part No. 324-6005, each kit consisting of a transistor and a 2.7Ω emitter resistor. All suspected bias resistors were also replaced, and care was taken to make certain that all metal heat sinks were replaced and soldered to the correct terminals on the etched circuit board—a blob of solder could have destroyed the new transistors. Since the separate heat sinks were located very close together, they were insulated with some rubber silicone cement.

DISTORTED AMPLIFIER

A General Electric AM-FM Model RC8571 receiver was found to have excessive hum and only weak reception from one channel. The owner complained of something burning. Removing the solid-state chassis revealed a burned bias resistor (Fig. 9). The burned resistor was traced to its respective output transistor, which was removed from the chassis and found shorted.

Each audio-frequency direct-coupled transistor was tested in the circuit since these transistors may have become leaky and placed the wrong bias voltage on the base terminal of the final output transistor.

WEAK LEFT CHANNEL

Another problem was a weak left channel in an RCA RS-215A amplifier. Signal tracing with an audio signal generator and scope revealed a weak 2N2614 driver stage (Fig. 10).

The transistor was tested in the circuit and appeared normal. All voltage readings were good. Emitter and base-bias resistors were of correct value. Even the audio-frequency direct-driven transistor was normal. But, when another electrolytic capacitor was shunted across the emitter bypass capacitor, the volume returned to the left channel. ■


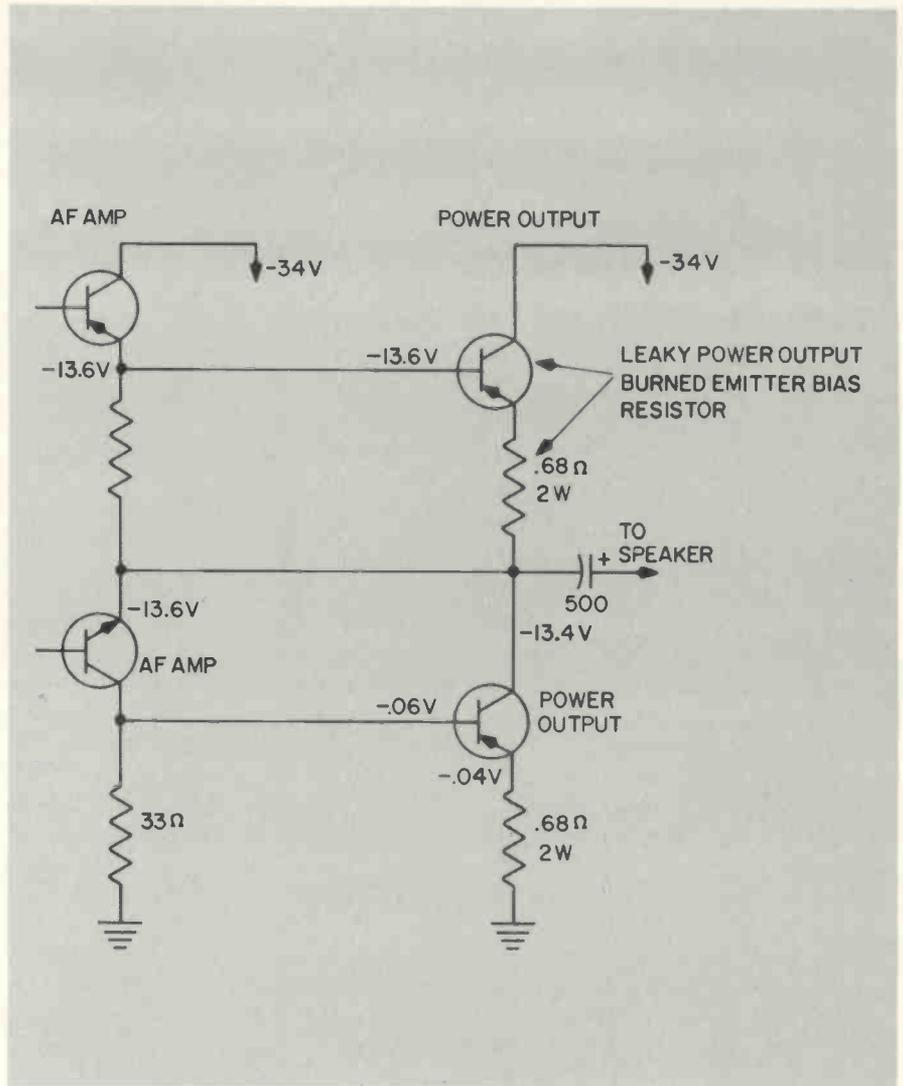


Fig. 9—The audio-output circuit in a General Electric RC8571 chassis.

Fig. 10—The final audio-amplifier stages in an RCA R-215 chassis.

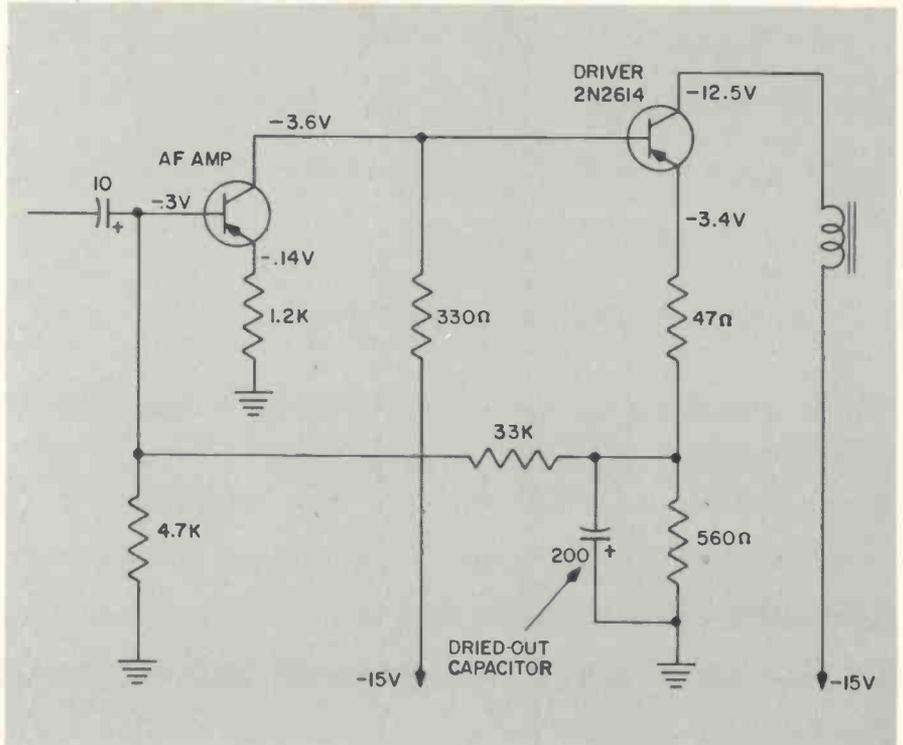

The Long and Short of MATV Cables

by ROBERT SHARP and PAUL MILLER

Antenna systems may pick up distortion-free TV signals, but these signals can become significantly distorted unless they are transferred to receivers through a well designed cable system

■ For over 20 years television has had a tremendous impact on American life. The TV set has become as popular as the refrigerator and washing machine. Over 90 percent of the households own at least one set. Yet, despite this overwhelming acceptance, the wiring from the antenna to the set is generally still the same sort of jerry-rigged afterthought as when antennas first started sprouting from house tops in the days right after World War II.

This is incongruous. Even a house built in 1970 seldom includes a signal distribution system. Almost invariably, the new occupant himself installs an antenna on the roof (where no provision for such installation has been allowed) and runs a twin lead down into a window or through a wall. An apartment dweller must often depend on a portable "rabbit ear" antenna alone. For both, TV watching is usually restricted to one room and reception is poorer than it should be. Such treatment of a TV signal distribution system in this day and age makes about as much sense as running electric wires from a power line through a window, hooking it up to a light and saying, "Well, that takes care of our electrical needs."

But things are due for a change. VHF-only black-and-white TV receivers in the past could pick a signal out of almost any kind of antenna system and make something worthwhile of it. This is not so with a UHF signal: when it travels through a dirty old twin lead on a rainy night, for instance, its strength can be so dissipated that little re-

mains to reach the set. Color sets are even more demanding. They require a strong, ghost-free, undistorted signal. It is surprising how many viewers will purchase an expensive color TV set and antenna, and then connect them together with lead-in wire in a manner that is electronically about as sound as baling wire and chewing gum.

The plain fact is that many home TV signal distribution systems are hopelessly outdated. The consumer, architect, antenna-system installer and builder must recognize that the time is long past due for a change in thinking. They must be sold on the benefits of a quality master antenna television (MATV) system technologically in tune with today's more sophisticated receivers, antennas, transmitters and broadcast equipment—and which complements the tremendous role TV plays in today's entertainment, communications and educational activities. The technology, materials and equipment *are* available.

MATV systems have been around for years. However, because they have frequently been poorly designed and installed, their quality has often left a lot to be desired. A very large market exists for well planned and properly installed MATV systems in hotels, motels, apartment buildings, hospitals, nursing homes, schools, dealer showrooms—and the home. The home is the biggest untapped MATV market.

MATV SYSTEMS

An MATV system has one antenna or antenna system serving numerous sets (or outlets). The system is designed so that the sets can be tuned to different channels at the same time without affecting one an-

The authors are electronic wire and cable product development engineers at Belden Corp.'s Technical Research Center.

other, allowing each set to receive satisfactorily strong and clear signals on all channels. This month's article will concentrate on the cables involved in such a system. Hardware and system design will not be covered this month except where they relate to cable selection.

TWIN LEAD

Most consumer TV sets offer only one type of input—300Ω twin lead. This is a carryover from the early days of television when the first simple antennas required lead-in wire of this impedance. The familiar twin lead helped perpetuate the 300Ω standard because of its low cost and ease of installation. When clean, dry and carefully installed, the simple twin lead is still the most efficient (lowest loss) lead in for VHF or UHF on the market—and that includes coax.

As TV technology progressed and we moved into the UHF channels and more complex color transmission, loss problems with the simple twin lead became apparent and spurred the development of improved twin leads.

Foam encapsulated types, such as Belden's 8285, cut losses by providing a layer of low-loss cellular plastic between the insulated conductors and the outer insulation—the surface exposed to conductive contaminants.

Later, shielded versions of the foam encapsulated types, such as Belden's 8290, were developed. Their mylar shield reduces interference from ignition systems and electrical gear. This shield also permits running the 300Ω line through or next to metal, permitting installations not possible with regular twin leads.

COAXIAL CABLE

Paralleling the evolution of the 300Ω twin lead were the 75Ω coaxial cables (Fig. 1) now widely used in CATV and MATV systems. (The 75Ω impedance was chosen because coaxial cables are most efficient for their size when produced for this value.) These cables are descendants of the cables developed during World War II for military communications and radar. In fact, MATV and CATV cables are still so closely allied to their military counterparts that they are commonly identified by their military specification RG/U designations.

It should be remembered, however, that commercial cables for TV distribution are really RG/U type cables. (It is common in the industry to refer to commercial coaxial cables as RG/U type cables, while referring to MIL spec varieties as plain RG/U cables.) Commercial cables are modifications of MIL spec cables, specifically tailored to meet

the needs of MATV. Designed primarily for low signal loss, the commercial cables are less expensive since they are not designed to meet military specifications more stringent than those required for commercial use. Furthermore, MIL spec cables are only available in solid polyethylene insulation, braided shields, non-contaminating black vinyl jackets and to meet one set of electrical characteristics.

Quality commercial 59/U type cables, on the other hand, are more satisfactory for the requirements of TV signal distribution, feature a range of electrical characteristics and are available in solid or cellular (foam) polyethylene insulations, braided or film-supported foil shields and have vinyl or polyethylene jackets—in black, white or colors.

Since the purchaser is not protected by the test documentation of a MIL spec, the quality of a 59/U type cable (or a 6/U or 11/U type cable) can be subject to variations depending upon a manufacturer's integrity. Buying from a manufacturer with a reputation for quality is the best assurance of receiving a quality product.

[Editor's Note: When checking through a recent industrial catalog, we noted three types of 59/U cable produced by one manufacturer under different manufacturer type num-

Table I—Comparison of MATV Coaxial Cables.

RG TYPE	CONDUCTOR, GAUGE AND TYPE	POLYETHYLENE INSULATION AND DIAMETER, INCHES	SHIELD TYPE	JACKET TYPE AND DIAMETER, INCHES	APPROX. WEIGHT PER 1,000 FEET, POUNDS	NOMINAL ATTENUATION, db PER 100 FEET	
						CH. 13	CH. 83
59 ^a	22, Solid Copperweld	Solid, 0.146	Braid	PVC, 0.242	35	5.0	10.9
59 ^b	22, Solid Copperweld	Foam, 0.146	Braid	PVC, 0.242	34	4.2	8.6
59 ^c	18, Solid Copper	Foam, 0.180	Duofoil	PVC, 0.242	24	3.2	6.8
11 ^d	18, Stranded Copper	Solid, 0.285	Braid	PVC, 0.405	93	3.1	7.1
11 ^e	14, Solid Copper	Foam, 0.285	Braid	PE, 0.405	81	2.3	5.2

Belden ^a8241, ^b8221, ^c8228, ^d8238, and ^e8213

bers. One (59^a in Table I), listed under MIL-C-17A, reportedly had a low-loss, flexible polyethylene inner jacket, covered with a copper-braid shield and a black plastic outer jacket. It was rated at 73Ω impedance and 21.0pf capacitance, the listed price being \$19.95 for a 500-ft spool. The other two cables were listed as special-purpose, low-loss coaxial cable suitable for community TV cable systems. They reportedly have stable electrical characteristics, even with changes in temperature and frequency. One was rated at 75Ω impedance and 17.3pf capacitance, the listed price being \$23.65 for a 500-ft spool. The other (59^b in Table I) was rated at 75Ω impedance and 16.3pf capacitance, the listed price being \$21.30 for a 500-ft spool. (The 59^c cable in Table I was not yet listed in the catalog.) Types 11/U were also listed in the catalog. One (11^d in Table I) had the same military classification number as the first (59^a). It was rated at 75Ω impedance and 20.5pf capacitance, the listed price being \$11.85 for a 100-ft spool (we assume that 500 ft

would cost about \$55.00). The other (11^e in Table I) was listed (like 59^b) as general purpose coaxial cable. It was rated at 75Ω impedance and 17.3pf capacitance, the listed price being \$62.50 for a 500-ft spool. The 300Ω shielded twin lead (described earlier in this article) was listed at \$47.90 for a 500-ft roll.]

Electrical loss characteristics of the numerous commercial coaxial cables vary widely. For instance, a new 59/U type cable (59^c in Table I) with the same outside diameter as MIL-C-17 RG-59B/U (0.242 in.), but with a foam core approximately the same size as a 6/U cable, has only about 60 percent of the MIL spec cable's losses. Additionally, its losses are only 80 percent of those of the average 59/U type and about equal to those of the larger, 0.332-in. diameter foam 6/U type.

COAXIAL CONNECTORS

There is some confusion among users over conductor sizes in coaxial cables. For example, Belden manufactures commercial and govern-

ment spec 59/U cables in four conductor sizes. Most common is the 22-gauge conductor, supplied in foam and solid insulated commercial types. This manufacturer also supplies a foam commercial type with a 20-gauge conductor and a solid MIL spec variety with a 0.023-in. diameter conductor (between 22- and 23-gauge). However, the conductor size by itself means little to the user as long as his connectors fit. (It is best to buy hardware that will accept all conductor sizes presently produced, thereby covering all eventualities.) Most important to the user are the loss characteristics of the cable, conductor size being only one determining factor.

When ordering connectors and other hardware, be certain they are compatible with the cable insofar as the female part will accept the conductor size and the connector body will accept the particular cable.

INSULATION AVAILABLE


In general, foam polyethylene insulated cable is preferable to the solid type for MATV. The cost is only slightly higher, it is lighter, more flexible, easier to install and offers the lowest signal losses. The availability of low-loss foam cable has accelerated the trend in recent years toward the generally superior "on-channel" UHF MATV distribution system.

The only advantage of a solid polyethylene insulated cable, besides its slightly lower cost, is its greater toughness. It is more crush-resistant and the conductor is less likely to be moved off center when the cable is bent sharply (which is not a recommended practice).

TWO SHIELDS

In the past most MATV cables had braided copper-wire shields, which do a reasonably good job of protecting the signal from electrical disturbances. However, some of the newer cables feature film supported foil shields, which in several ways are superior to braid shields. They provide 100 percent coverage (which no single braid shield can do), and they are thinner, which allows more space to be devoted to conductor and insulation—resulting in lower losses. They also block contaminants, which could pass through a braid shield to attack the insulation and possibly alter a cable's elec-

Fig. 1.—Comparison of shielded twin lead and coaxial cables.

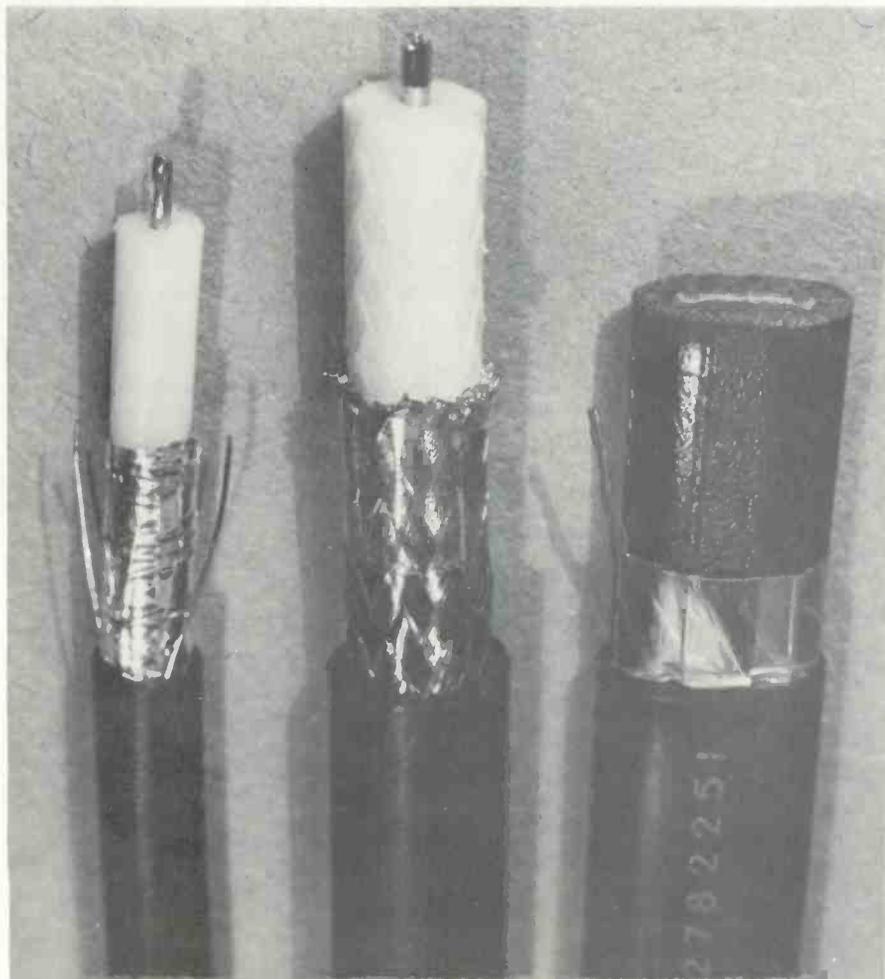

trical characteristics. Foil-film shielded cables are also easy to terminate.

TWO JACKETS

Coaxial cables for TV-signal distribution are supplied with jackets of either polyethylene or vinyl, vinyl being the most popular and acceptable for MATV. Compared to polyethylene, vinyl is softer, more flexible, easier to terminate and flame retardant. It will also accept paint better and is supplied by some manufacturers in three colors. Polyethylene (available in black only) is seen most often on CATV cables where its relative lack of stiffness at low temperatures and its outstanding resistance to sunlight, weathering and abrasion from tree branches is helpful.

Another thing to consider when purchasing a coaxial MATV cable is whether it has been sweep tested by the manufacturer. Sweep testing is a quality control operation for detecting faults that may cause excessive signal losses on certain channels.

TWIN LEAD OR COAXIAL CABLE

Theoretically, an MATV cable system could be made up of either 300Ω twin lead or 75Ω coaxial cable. In practice, the systems are almost 100 percent coaxial cable.

This is not to say that twin lead should never be used. A very simple MATV system, with four sets or outlets, could be made up with a four-set coupler and carefully routed twin lead. In a location where signal strength is adequate and where interference is minimal, this system would be inexpensive and serviceable. Such a system could be installed in a home in the suburbs.

For a slight increase in cost, such a system could be improved with the use of a shielded twin lead to eliminate interference and secondary signal pickup. The shielding also permits routing near conductive objects or installation in conduit. In areas where the signal strength is weak, an antenna-mounted amplifier, attic or basement amplifier-coupler could be added to boost signal levels and permit the use of additional couplers and more outlets.

[Editor's Note: Shielded twin lead generally has less signal loss than the coax and there are fewer problems of ghosts resulting from impedance mismatching.]

COAXIAL CABLE OFFERS VERSATILITY

Although a shielded twin lead system, like the one just described, can do an excellent job, there are practical and economic limits restricting its use in an MATV system. Shielded twin-lead is more expensive and harder to route than plain twin-lead or 59/U type coaxial cable. It doesn't take too many feet before coaxial cable and matching transformers are less expensive than a shielded twin-lead system.

For all but small, uncomplicated systems, coaxial cable is the most practical answer. It is the lowest cost form of shielded TV lead. Handling, routing and pulling in conduit are easy because of its round configuration, flexibility in all directions and lack of stiffness or bulkiness (at least in the 59/U size). Additionally, it is easier and faster to install and terminate than a shielded twin lead.

But most important, a wide variety of hardware is available for coax-amplifiers, splitters, mixers, multiplexers, taps, attenuators, filters, connectors, single-channel antennas, converters, etc. The availability of such hardware makes complex signal processing and balancing possible for the larger MATV installations carrying numerous channels. System design can be approached with confidence because electrical characteristics can be accurately determined. Furthermore, the systems can be quickly installed.

Because of these advantages, the balance of the article will deal exclusively with systems containing coaxial cable.

SELLING THE SYSTEM CONCEPT

MATV distribution systems are becoming as important to modern buildings as electric-power distribution systems; and, therefore, they should be included right from the start in the electrical planning. Equipment, riser and tap locations should be determined early and space provided. MATV dealers and contractors must get to know architects and builders and educate them in the potential of MATV systems.

GOING-ON CHANNEL

The trend in MATV is toward on-channel systems in which the

Channel No.	Freq. Range	Channel No.	Freq. Range
VHF			
2	54-60	41	632-638
3	60-66	42	638-644
4	66-72	43	644-650
5	76-82	44	650-656
6	82-88	45	656-662
		46	662-668
		47	668-674
FM-98 mc			
7	174-180	48	674-680
8	180-186	49	680-686
9	186-192	50	686-692
10	192-198	51	692-698
11	198-204	52	698-704
12	204-210	53	704-710
13	210-216	54	710-716
		55	716-722
		56	722-728
UHF			
14	470-476	57	728-734
15	476-482	58	734-740
16	482-488	59	740-746
17	488-494	60	746-752
18	494-500	61	752-758
19	500-506	62	758-764
20	506-512	63	764-770
21	512-518	64	770-776
22	518-524	65	776-782
23	524-530	66	782-788
24	530-536	67	788-794
25	536-542	68	794-800
26	542-548	69	800-806
27	548-554	70	806-812
28	554-560	71	812-818
29	560-566	72	818-824
30	566-572	73	824-830
31	572-578	74	830-836
32	578-584	75	836-842
33	584-590	76	842-848
34	590-596	77	848-854
35	596-602	78	854-860
36	602-608	79	860-866
37	608-614	80	866-872
38	614-620	81	872-878
39	620-626	82	878-884
40	626-632	83	884-890

Table II—Frequencies Assigned VHF and UHF Television Channels.

UHF channel signals are not converted to VHF but are distributed and fed to the sets at their transmitted frequencies. (Table II lists the frequencies assigned the VHF and UHF television channels.) The availability of lower-loss cables and all-channel hardware, plus the predominance of all-channel TV sets, makes the conversion from UHF to VHF unnecessary. An on-channel system is obsolescence proof since it can easily be expanded as new channels come on the air. The cost of converters is eliminated; and additionally, sound traps to prevent interference between adjacent VHF channels, when UHF channels are converted to VHF, are unnecessary.

SELECTING THE CABLE

Loss characteristics are the major consideration when determining the type of coaxial cable to be used. Every cable type has its own characteristic curve, which details losses in decibels (dB) per 100 ft in relation to frequency. (A sample set of characteristic curves is shown in Table III.)

Generally, the larger the cable the lower the losses. Foam polyethylene insulated types offer lower losses than similarly sized solid polyethylene insulated types. But loss char-

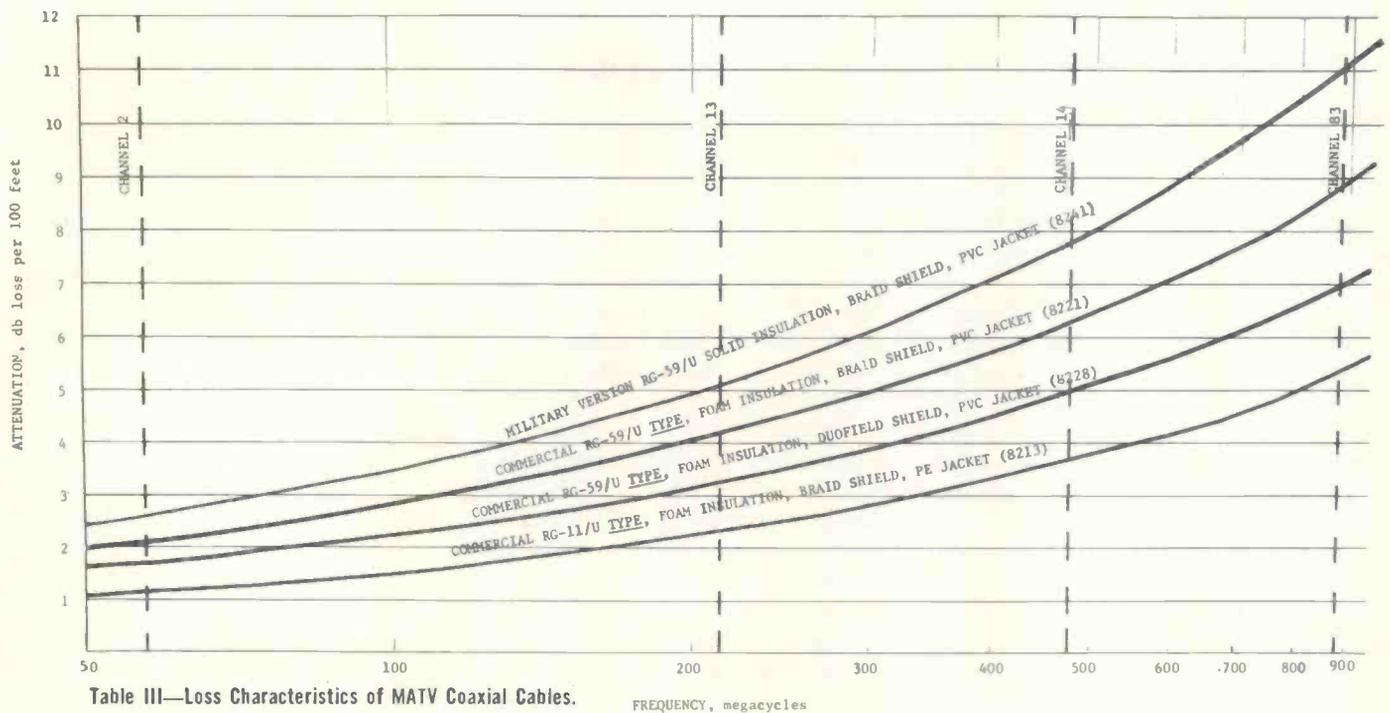


Table III—Loss Characteristics of MATV Coaxial Cables.

acteristics can vary considerably even among foam types of the same size.

Signal losses also increase as their frequency increases, roughly in direct proportion to the square root of the frequency. As an example, cable losses at 400MHz are roughly 20/30ths (or $\frac{2}{3}$) the losses at 900 MHz.

Cable losses increase directly with length. A cable section twice as long as another of the same type has twice the decibel loss. When calculating cable losses, the decibels are simply added. If the run is 400 ft and the cable has a loss characteristic of 7dB per 100 ft at the frequency in question, the total loss will be 28dB.

Always be sure to calculate losses at the frequencies for Channel 13 and Channel 83 (where losses are highest for their particular bands) even though no transmitters may be broadcasting in your area on these higher channels. In this way, provision is made for new stations.

ASSUME 59/U TYPE CABLE

When making calculations to determine what cables to specify for an MATV distribution system, it is best to assume that a 59/U type cable of the most efficient design will be used, unless it is known from previous experience that a larger size

cable will be necessary. For most jobs an ultra low loss 59/U type cable will be adequate.

Unlike 60Hz electrical wiring, the load, or number of TV sets to be hooked on the line, has no effect on the size cable needed. It does not make any difference whether the length is feeding one set at the end of a system or is the main trunk for hundreds of sets.

The use of larger, more efficient 6/U and 11/U type cables is seldom necessary except for systems with very long runs. Their cost is high—an 11/U type cable lists at about three times the price of a similarly constructed 59/U type cable. Furthermore, they are stiff, bulky, harder to run and require larger, more expensive conduits.

On many smaller MATV systems, the designer quickly realizes that cable losses can be small compared to the losses in certain hardware. Even so, it is still wise to choose as efficient a cable as possible to provide maximum capacity for future extensions. Also, the amplifier specified can be of minimum capacity, and balancing will be easier since differences in signal levels at the taps will tend to be minimized.

CALCULATE CONSERVATIVELY

When calculating losses, always figure that the TV set requires 1000

to 2000 μ v at 75 Ω to operate, and then work your way back from the farthest set to the antenna. Modern TV sets can operate with signal levels as low as 150 μ v, but this value should not be used in your calculations. This provides a safety factor for possible TV set and distribution system deterioration through age. Under certain environmental conditions, such as high temperatures, coaxial loss levels can exceed the nominal values used for calculations. By calculating with a base of 1000 to 2000 μ v at the set, any such system degradation will not be noticed.

PURCHASE WISELY

When purchasing cable, be sure to obtain a type that is primarily designed for MATV systems, or for CATV systems as an alternative. CATV cables, with polyethylene jackets, are designed for outdoor use and are inherently stiffer and harder to terminate.

Be careful not to accidentally order an MIL spec cable since you will be paying for documentation of tests that do not apply to the characteristics that are important in an MATV system.

"Precision video" cables should also be avoided since they are intended for entirely different applications. Again, the cost would be way out of line as far as MATV is

concerned, and the quality would be unnecessary.

INSTALLING THE CABLE

Coaxial cable, unlike unshielded twin lead, can be routed either in or out of conduit. Be sure to check local codes concerning conduit requirements. In any case, never install coaxial cable in the same raceway or conduit as power cable.

Always remove the cable from a spool by rotating the spool rather than by taking it over the end of the spool. When reeling over the end, one revolution of twist is put into the cable for every turn taken off the spool. This will cause the cable to kink (which can damage it) and make pulling the cable more difficult.

When pulling a braid-shielded cable into a conduit, always tie the braid, rather than the center conductor, to the pulling device. On the other hand, when pulling foil-shielded cables, the drain wires should be tied to the center conductor. Special caution should be exercised when pulling by the center conductor in order to avoid stretching it. If necessary, use a pulling lubricant to ease the job. Make sure that the label on the lubricant states that it can be used with the cable jacketing material.

If possible, before pulling a cable during the winter months, warm the cable to room temperature. The vinyl jackets common to MATV cables tend to stiffen when cold, which makes the cables more difficult to pull and can result in damage to the jacket.

Never jerk the cable or permit it to kink. Do not allow it to be scuffed, nicked or cut so that water, moisture or contaminants can get beneath the jacket and have a chance to attack the insulation and shield.

The minimum bend radius for an MATV cable varies according to whether it is being pulled into conduit or stapled to a wall. A 59/U type cable should not be pulled through a conduit containing a bend of less than 5 in. radius. If the cable is being stapled to a wall where no flexing or pulling is done, the radius can be reduced to 10 times the cable diameter.

If the cable does not have to be run through a conduit, it is easier to just staple it to a wall or run it

through clips. A staple that fits the cable with a round crown should be used, taking care without crushing it. The staple should never constrict the cable since that might cause signal reflection problems.

Do not be too precise when spacing staples. They should be placed randomly rather than at measured intervals. Standing-wave reflections may result on one of the TV channels if staples are installed at measured intervals that happen to correspond to the wavelength of the signal received.

Do not run the cable through any areas where the temperature may become greater than 180°F. Polyethylene insulation will soften at this temperature, with the conductor possibly shifting off center. This would result in an impedance change in the cable and possibly degrade the picture.

Generally, if the MATV system is to be installed in a building located within 15 miles of a transmitter, use coaxial cable right up to the TV set before converting over to 300Ω twin lead with a matching transformer. *[Editor's Note: Some of the more recent TV sets have 75Ω tuners and the coaxial cable can then be plugged directly into the set without using a matching transformer.]* Signal strength from a nearby transmitter can be so high that a short length of unshielded lead can pick up a ghost-producing signal.

TERMINATING COAXIAL LINES

Always remember that the end of a coaxial line must be terminated with its characteristic impedance—either in a specially designed termination, a tap or other device that produces the same effect. A coaxial cable cannot be just cut off and left hanging because the signal will then bounce back down the cable and create ghost reflections in all of the sets.

It is a good idea to wear safety glasses when making up connectors. Occasionally the end of a conductor must be snipped off and the little fragments of wire can be extremely dangerous. The center conductor of an MATV cable is frequently copper-covered steel rather than solid copper, and the snipped fragment usually flies off like a bullet. Even a "soft copper" conductor fragment can result in the loss of an eye. ■

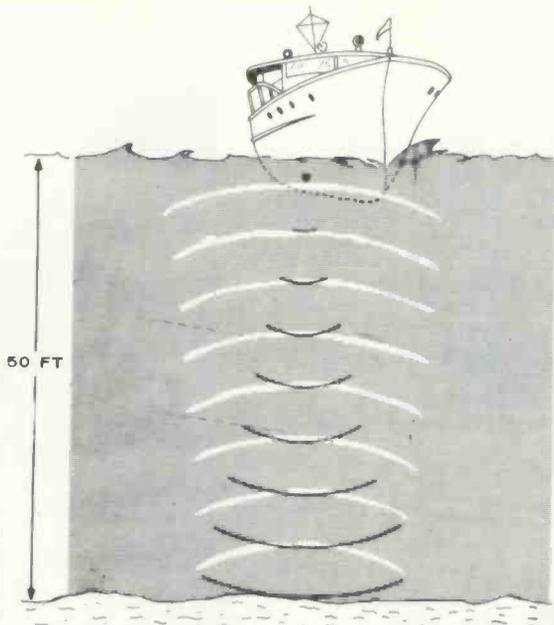


Fig. 1 shows depth-finder pulse being transmitted and "reflected" back from the bottom to provide a depth indication. (Courtesy Heath Co.)

Electronic Depth-Finders

If your service shop has room for additional business, you might consider marine electronic sales and service including the popular depth-finder or depth-sounder units which are designed to operate on almost any size boat.

■ One of the biggest booms in the country today is pleasure boating. Everyone is taking to the woods with tents, trailers, campers and boats to fish their favorite area or enjoy a weekend in the sun. And right along with today's sportsman goes his desire to communicate. Where he used to take a portable radio, he now carries a compact battery operated TV. In fact, many sportsmen today consider units such as marine two-way radio and direction finders essential

to their boating activities whether for fun or fishing.

Another boon to boating which has gained considerable popularity is the depth-sounder or fish-finder type of equipment. Actually, these are the same instrument in most cases as their operating characteristics provide for an "echo" or reflected signal any time the transmitted signal hits a sufficiently solid underwater object.

The instrument operates some-

what like a sonar set which, in general terms, could be considered as an underwater radar. It operates on the principle that sound waves in water travel at approximately 4800 ft per second. This speed will vary depending on the salt content and the temperature of the water. Sonar equipment such as used on ocean-going fishing boats are calibrated or compensated for the water temperature or thermal layers at various depths. However, most of the instruments normally found on pleasure craft are not concerned with these factors as operation is limited to relatively shallow fresh water areas.

The depth-finder or fish-finder instrument uses a "transducer" as its transmitting and receiving antenna. It is normally the most delicate part of the system and should be handled with care. The transmitter puts out a signal consisting of pulses at a frequency of 200kHz, which are transmitted into the water through a special element in the transducer. The transducer acts much like a radio speaker except that, instead of moving air, it moves water. The pulses are actually directed into a narrow beam as shown in Fig. 1. The pulses are sent out and reflected to be picked up by the transducer. The time it takes for the pulse to go out and then return is measured and calibrated on the instrument's meter in terms of feet.

We indicated that sound in water travels at approximately 4800ft per second or .000208 seconds per foot.

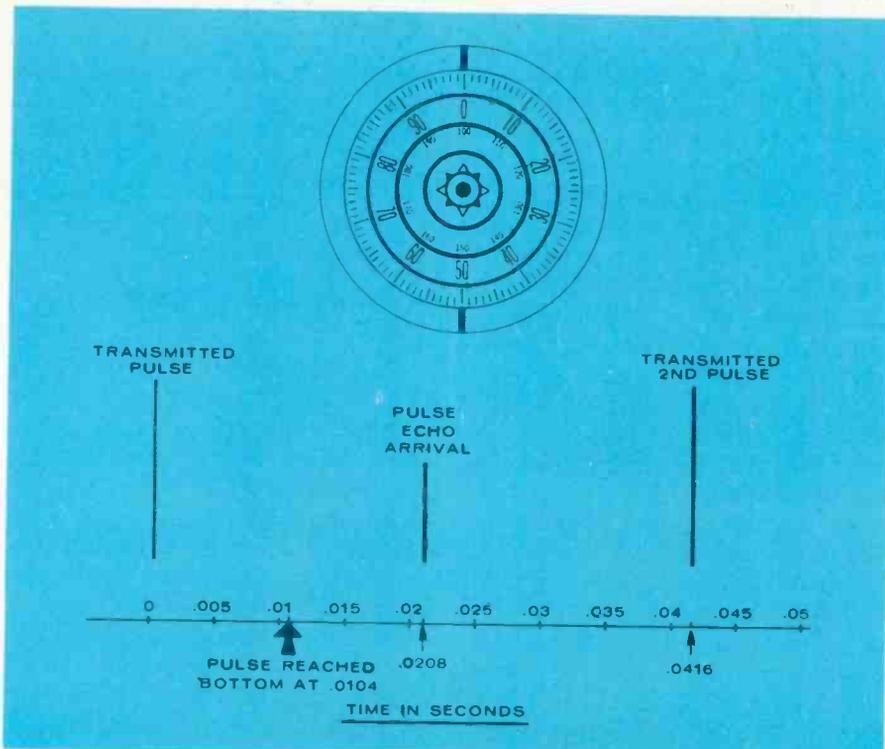


Fig. 2 illustrates the time lapse between the transmitted and received signals which determine the distance in feet from the transducer to the reflecting object. (Courtesy Heath Co.)

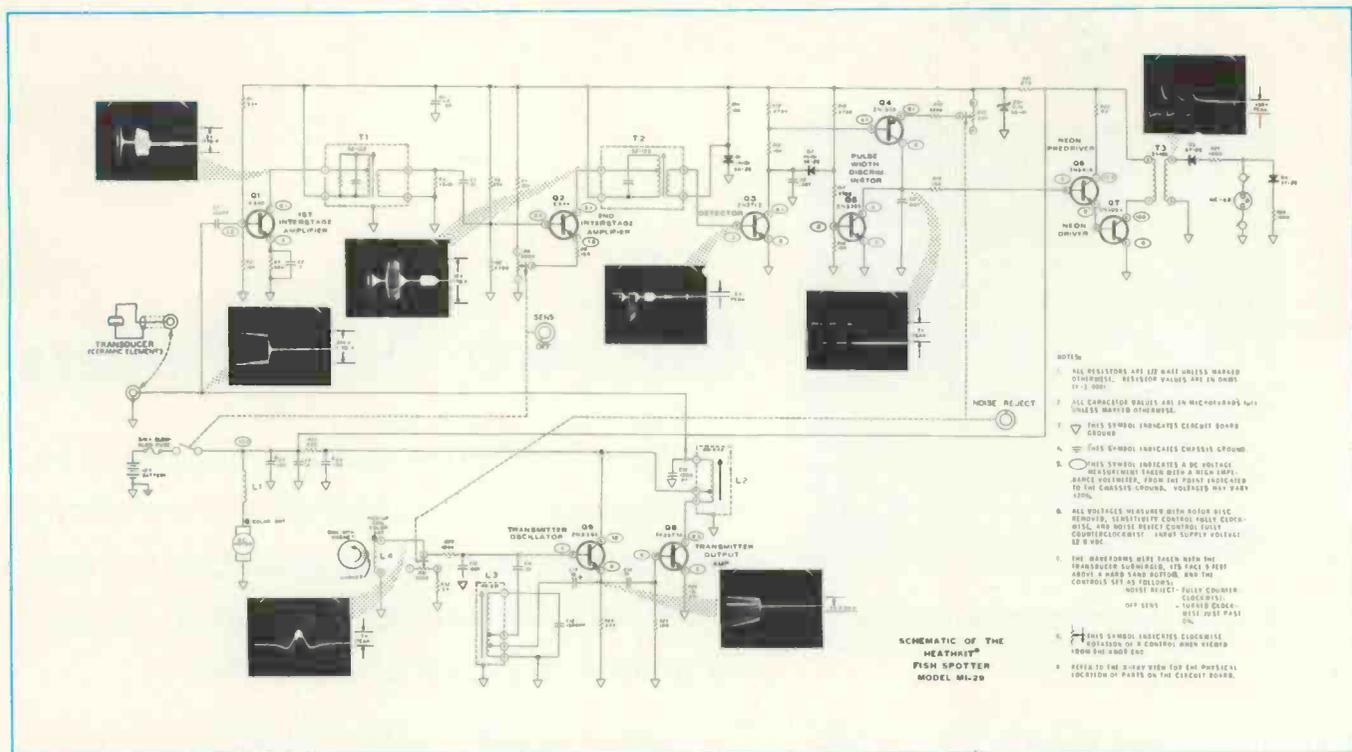


Fig. 3—Schematic Diagram of the Heath MI-29. (Courtesy Heath Co.)

Supposing then, that we are operating a depth-finder on a lake over a spot 50ft deep. The time for the pulse to go to the bottom will be 50 times .000208 or .0104 seconds (104 milliseconds). Since the signal must also reflect back to the transducer, the round trip time is 2 times .0104 or .0208 seconds. The diagram in Fig. 2 shows how this would appear if we could see the pulse go out and return.

TYPES OF "DEPTH-FINDERS"

The accompanying photos show several types of depth-finding or fish-finding instruments. The Raytheon Model DE-732 Fathometer is a solid-state depth-sounder designed to operate from 12vdc. Since it is transistorized, the current requirement is low, approximately 200ma, and this means it can be operated from a boat's 12-volt electrical system or from a 12-volt lantern battery. The unit is housed in the indicator assembly shown with the transducer and power plugs at the rear.

The Sonar Model D120 Depth Indicator is a tube operated unit for 12 or 6vdc and provides readings to 250ft. This unit uses a flashing type of indicator and can be used for locating fish, wrecks and other objects. The instrument has two scales, an outer scale for depths to 125ft and an inner scale for depths to 250 ft.

The second revolution of the indicator is provided for the 125 to 250 ft depths. The D120 operates from a heavy-duty power supply and a synchronous motor. A 115Hz vibrator determines the motor speed. The circuitry consists of a 200kHz power oscillator, a wideband amplifier and a magnetically controlled keying amplifier.

The transducer is a ceramic element housed in a machined bronze casting and encapsulated. It also has provision for either through-the-hull type mounting, or it can be mounted externally on the transom. The indicator includes plug-in jacks for the dc power source and cabling to the transducer. Since this is a tube operated instrument, the power requirements are somewhat higher than those of the solid-state units, but still nominal for most installations. It requires approximately 2¾ amps for 12-volt operation and 5.5 amps for 6vdc use. The instrument weighs 6½ lb.

Allied Radio's new Model KG-711 Ultrasonic Depth Meter is a Knight-Kit instrument, which is designed to operate on eight self-contained flashlight ("C" size) batteries or from the boat's electrical system. The unit has a gimbal mounting bracket for the meter and comes with a transducer mounting assembly. Specifications indicate operation

to 200ft on hard bottom and 100ft on soft bottom.

The Heath MI-29 Fish-Spotter is a transistorized unit which will read depths to 200ft on two scales. It is completely portable as it operates from two self-contained 6vdc lantern batteries and comes with a suction cup transducer mounting bracket. The carrying case is waterproof and also floats if accidentally dropped overboard. Storage space is provided for the transducer and cable in the case. This instrument has nine transistors and five diodes to produce a 200kHz pulse frequency. The power required of the lantern batteries is between 80-100ma for a nominal battery life of 80 hours.

CIRCUIT DESCRIPTION— TRANSMITTER

The schematic diagram of the Heath MI-29 is shown in Fig. 3 to illustrate the operation of depth-finder or fish-finder instrument. The circuit can be divided into two parts, transmitter and receiver. A brief explanation of how the circuits operate will help you do a more efficient service job.

The rotor disc assembly is rotated by the motor and has a permanent magnet mounted on it. Each time the magnet passes the pickup coil, L4, it induces a current in the coil. This current flows through L4 and



Raytheon DE-732 fathometer depth-sounder is a transistorized unit for reading. (Courtesy Raytheon Co.)

produces a pulse which is applied through R31 and R29 to the base of the oscillator transistor, Q9. The pulse causes Q9 to conduct and when it conducts, the oscillator operates at 200kHz. This signal is then coupled through C13 to a small portion of the oscillator coil, L3. This signal is stepped up and coupled back through C15 to the base of Q9, which completes the feedback loop and causes oscillation.

The oscillator operating frequency is determined by the tuned circuit of L3 and C12. The control, R31, adjusts the amplitude and duration of the oscillator trigger pulse, which subsequently determines the duration of the transmit signal. The 200kHz signal is coupled through C14 to the transmitter output, Q8, where it is amplified and coupled to the output coil, L2. Here the voltage is stepped up to approximately 200 volts (peak-to-peak) and coupled to the transducer where it is converted to a mechanical, ultrasonic signal. Since the output signal occurs only when the magnet rotates past L4, the transducer is free to receive reflected signals through the rest of the rotor-disc's arc.

CIRCUIT DESCRIPTION— RECEIVER

The receiver circuits operate continuously whenever the MI-29 is turned on. The transmitted signal is reflected from the bottom or from some other submerged object. This reflected signal is picked up by the transducer and changed back into an electrical signal. It is coupled through C1 to the base of Q1 where it is amplified and coupled to the interstage transformer, T1.

From T1, the signal is coupled through C3 to the base of Q2 for further amplification. The gain of transistor Q2 is controlled by the SENSITIVITY control, R8, which in turn, varies the amplitude of the signal to the interstage transformer, T2. The signal from T2 is coupled directly to the base of Q3. Transistor Q3 is connected in a detector circuit with R13 and C5. R11 and D1 bias Q3 so it will pass only the positive portion of the applied signal. The detected signal at the collector of Q3 is in the form of a square wave pulse. This pulse is then coupled through R13 to the base of Q4 which is normally biased off. It is biased on by the pulse at a level set

by the NOISE REJECTION control, R15.

When transistor Q4 conducts, C6, which is connected to the collector of Q4 begins to charge. When the charge on C6 reaches approximately 1.2vdc, transistors Q6 and Q7, which are normally biased off, will conduct. The output signal from Q6 and Q7 is then coupled through the output transformer, T3, where it is stepped up to sufficiently fire the neon lamp. Noise pulses, even though high in amplitude, are generally too short in duration to charge C6 and bias Q6 and Q7 into conduction. This insures that the neon lamp will not flash and indicate false readings. The charging time of C6 can be controlled by changing the resistance of the NOISE REJECT control, R15. At the end of the signal pulse, Q3 is again cut off and its collector voltage increases. This increases the bias voltage of Q5 and causes it to conduct, which then discharges C6. Diodes D3 and D4 in the secondary of T3 keep the negative voltage produced by the collapsing magnetic field of T3 (at the end of a pulse) from firing the neon lamp.

INSTALLATION

The installation of electronic depth-finder equipment varies slightly between the various manufactured types, but all require mounting a transducer and control or indicating unit. The different mounting configurations normally concern only the installation of the transducer.

The Raytheon DE-732 has three transducers available: a through-hull mounting type, transom mounted type and one to mount in sailboat fore-foot. The Sonar Model D-120M allows for two mounting configurations: either through-hull or transom. The Heath MI-29 is a portable instrument and designed to be moved if necessary from boat to boat so it is the simplest of all to install. It comes with a transducer mounting bracket attached to a suction cup unit for attachment to the transom or hull of any boat. The Heath Company also manufactures a Model MI-19 Depth-Sounder, which can be purchased for through-hull or transom operation in a fixed installation. The difference between the MI-19 and MI-29 is that the MI-29 is made to be completely portable for the fisherman and so



The Sonar Model D120 Depth Indicator is tube operated for use on 6 or 12vdc and provides readings to 250ft on two scales. (Courtesy Sonar Radio Corp.)



The Heath Model MI-29 Fish Spotter is transistorized and completely for tube using self-contained lantern batteries for operation in depths to 200ft. (Courtesy Heath Co.)

has internal batteries and a movable transducer assembly.

The diagrams in Fig. 4 and Fig. 5 show the two common types of fixed transducer mountings. The transducer cable to the indicator in all cases is a fixed length and cannot be changed regardless of how long it is. When the installation is planned, it should be made so that the cable will reach. Any extra cable can be rolled up and taped out of the way. As shown in the diagrams, the transducer should be mounted above the level of the bottom of the keel. This will afford some degree of protection for the transducer face. A through-hull installation should be made with the transducer located slightly forward of amidships. It should in all cases be mounted so

that its face is parallel to the water line. Through-hull installations should be located away from any other through-hull opening which could cause turbulence around the transducer. Be sure to pick a mounting spot which will allow room in-

side the boat for securing the transducer mounting hardware and for routing the cable. The transducer cable should be routed away from the boat's electrical system if possible as it can pick up noise.

If noise does show up, it should



The Knight Model KG-711 Ultrasonic Depth Meter kit operates on either eight self-contained "C" batteries or from the boat's electrical system for depth indications to 200ft on hard bottom. (Courtesy Allied Radio Corp.)

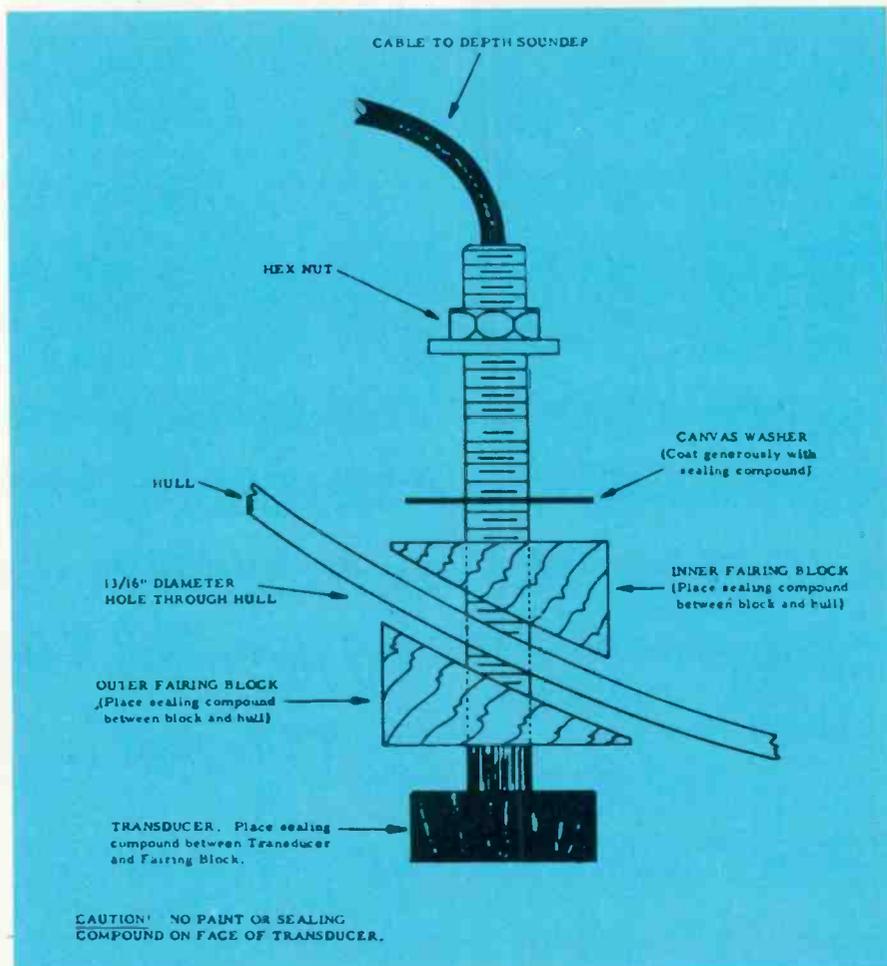


Fig. 4—Typical through-hull transducer installation shows use of fairing blocks to provide parallel mounting. (Courtesy Raytheon)

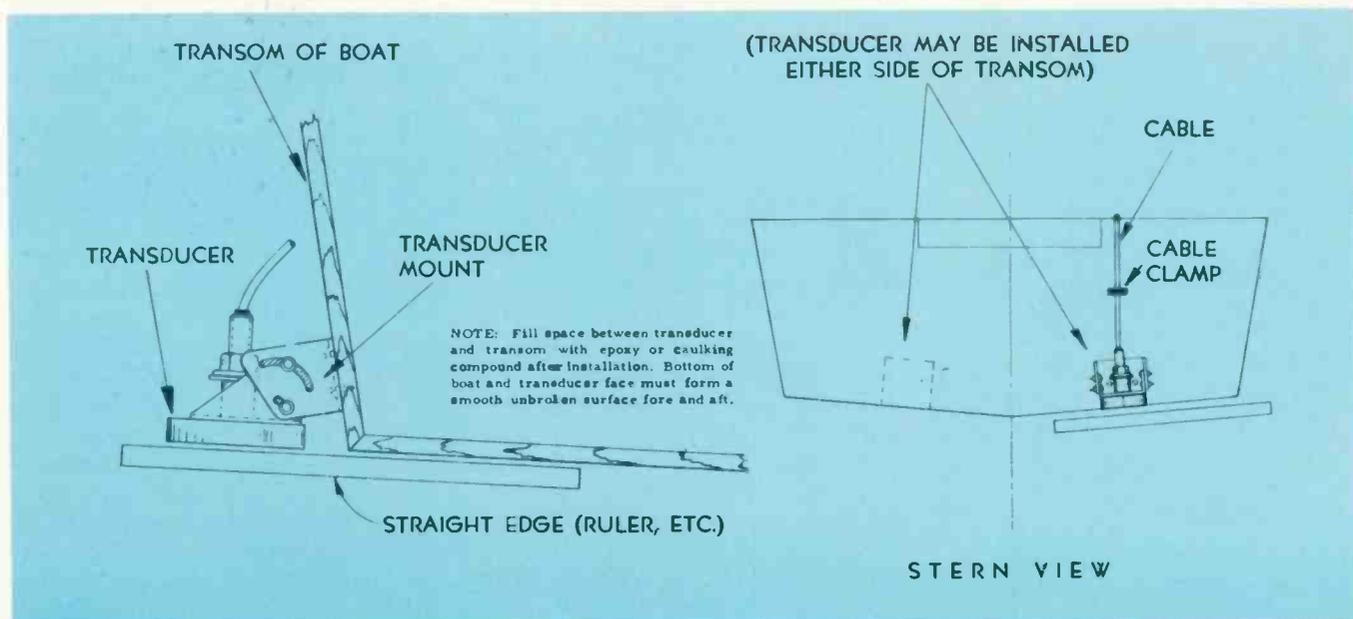


Fig. 5—Transom mounted transducer is located off keel center line and placed flush with bottom of boat sideways and lengthwise. (Courtesy Raytheon)

be handled much the same as automobile noise in a two-way radio system. Bond all electrical grounds and metal-to-metal contacts. Make good ground connections and check all ignition fittings.

If the transducer installation is to be a transom mounted system, be sure that the transducer is secured parallel to the water line. On boats with one engine, place the transducer mounting at least fifteen inches to one side of the centerline. If the boat has two engines, the transducer should be placed exactly on the centerline.

When mounting the indicator unit, it is best to place it where it is out of the glare of the sun even though some of the meter units are shielded. The indicator mounting brackets should always be set for the best viewing angle. Power connection for most of the depth-finders is simply a matter of connecting two leads to the 12 or 6vdc source. A power cable is provided with all of the instruments discussed in this article.

MAINTENANCE

The amount of maintenance required on the instruments outlined in this article is relatively small. Normally, it will be limited to an occasional indicator lamp replacement and slip-ring cleaning. Replacement of the indicator lamp in the Raytheon DE-732 is accomplished by simply removing the rotor assembly and inserting the new lamp in the fahnstock clips. The rotor is accessible by removing a couple of screws on the back of the indicator and three on the printed circuit board. The only other maintenance on this instrument is to be sure that the magnet is in line with the center of the rotor for maximum pulse amplitude.

The Sonar Model D-120M requires periodic cleaning of the commutator rings. The rotating indicator arm is accessible after removing the four corner screws in the dial hood. The rotor arm is fastened to the motor shaft with a set screw. Loosen the set screw, remove the rotor arm and carefully clean the arm commutator ring. The indicator lamp, which is neon, is held in place on the indicator arm by a spring clip. The lamp electrodes are pressed into small spring clips. The replacement

continued on page 91

TEST LAB REPORT ET/D

EICO Model 240 Solid-State FET-VOM

Here's how to have the latest
in a solid-state voltmeter and still
save a few bucks

■ It takes a fast-moving technician with a fairly hefty budget to keep his shop equipped with the many new test equipment items introduced in the past several years. Even that old 'work-horse' of test equipment, the vacuum tube voltmeter, has been updated with solid-state circuitry and is now called by the initials EVM, SSYM or FET-VOM. One way for the technician to make his equipment buying dollars stretch a little farther is through the assembly in his own shop of one of the kits now being offered by several manufacturers.

We recently assembled EICO's Model 240 Solid-State FET-VOM in the ET/D laboratory at a savings of around \$20 from the factory wired price. For a few hours of work and the use of a few shop tools, we wound up with a modern, totally transistorized FET-VOM.

The Model 240 features an ac power supply for bench work and a battery supply for field use. Its semiconductor circuitry provides flexibility for not only the servicing of vacuum-tube equipment, but a low 1 volt dc full scale for semiconductor circuit testing. Voltages as low as .02 volt dc are easily and accurately read with good indication available down as low as .01 volt. Direct readings may be made up to 1000 volts dc and with the addition of an HVP probe (not supplied with the kit) readings can be extended to 30,000 volts dc.

The seven ac ranges cover the complete gamut of voltage measurements from 1 volt rms (full scale)

to 1000 volts rms (full scale). The meter scales are calibrated in both rms and peak-to-peak to enable accurate conversions. Covering the frequency range from 25Hz to over 2MHz, you can perform most required ac measurements with the ac portion of the 240.

Seven ohmmeter ranges are available to read up to 1000 megohms. A low voltage supply is used in the ohmmeter section to avoid accidental damage to semiconductors in the equipment under test. However, this voltage is high enough for use in testing both diodes and transistors.

An FET-input semiconductor, differential amplifier, tight voltage regulation and close-tolerance resistors seem to provide stability and




EICO Model 240 solid-state FET-TVM

... for more details circle 900 on Reader Service Card

The hunt is on!

(Beware of the Grope.)

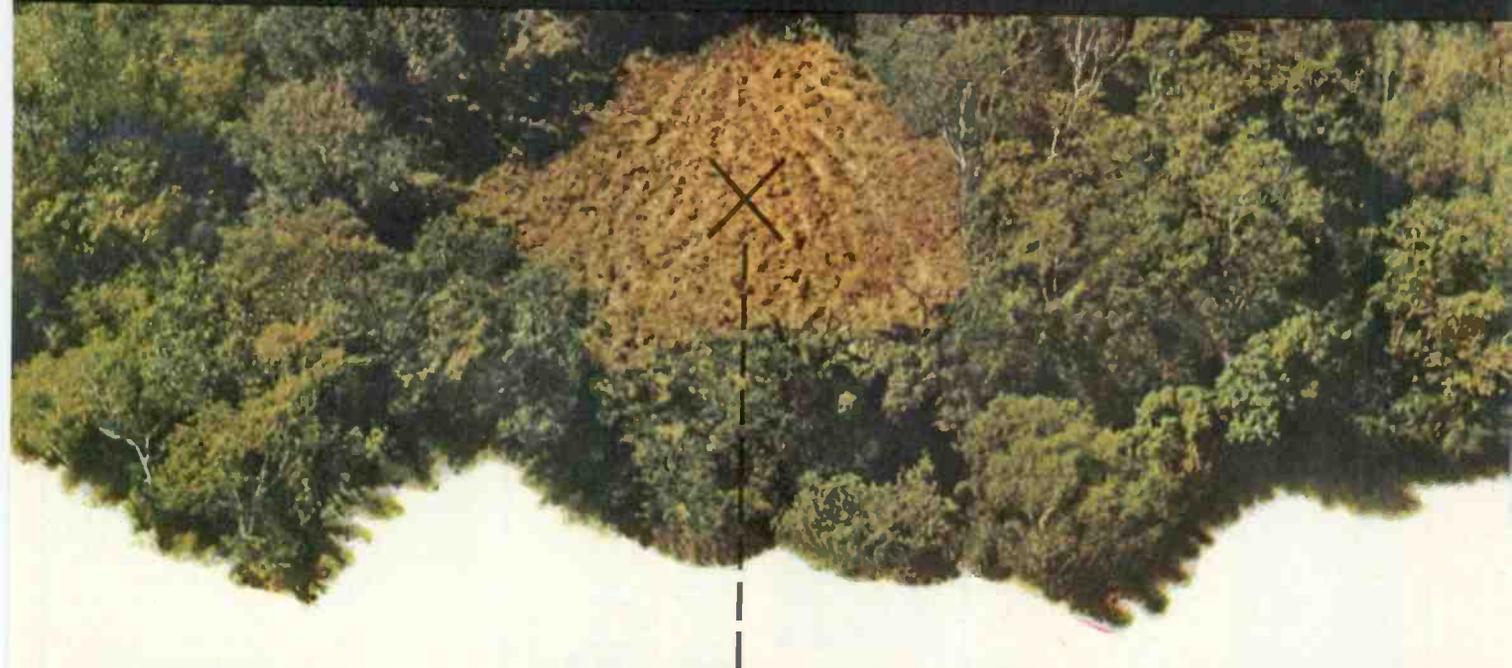

How to head the hunt away from the Grope.
Draw your prospect a map.



The Grope footprint goes in all directions, like you without the Yellow Pages.

That dratted Grope! He preys on people who don't know where to find what they're hunting for

... turning their search for you into a jungle hunt! So be prepared. Have your own special map in the Yellow Pages, so the only one that loses out is the Grope. It's easy, and it's the best selling map in town.

Here's your do-it-yourself speed lesson on the Yellow Pages Map Drawing course.

Call your local Yellow Pages representative today and place your Map with him!



The Yellow Pages

**Emergency Service
Day or Night**

BARRY'S HEATING & PLUMBING

Since **BHP** 1921

**COMMERCIAL,
INSTITUTIONAL, RESIDENTIAL,
INSTALLATION & REPAIRS**

Complete line of:

• Kitchens	• Water Pumps
• Laundries	• Heating Systems
• Sewage Systems	• Pipes and Drains

★ References	★ Estimates
★ Ample Parking	★ Delayed Payment Plans

phone **678-0743**

77 Locust Lane. (Between Main and Central, one mile from RR. Station).

Tell people what you will do for them. How you're different.

Be under the proper headings so people can find you fast. Maybe you should be under more than one heading. Think about that!

Use your logotype to gain recognition. Give facts about your qualifications.

Tell people about your special services . . . repairs, rentals.

List the products you carry.

Tell how easy it is to deal with you . . . credit, parking, hours, delivery.

Give telephone number and address, and if you're hard to locate, directions.

Electronic Circuit Design Handbook



New Third Edition—A brand-new, enlarged edition of the ever popular circuit designer's "cookbook," now containing over 600 proven circuits, for all types of functions, selected from thousands on the basis of originality and practical application. Now you can have, at your fingertips, this carefully-planned reference source of tried and

tested circuits. Selected from thousands submitted by distinguished engineers, these "thought-starters" are a collection of original circuits selected on the basis of their usefulness. This detailed compilation of practical design data is the answer to the need for an organized gathering of proved circuits... both basic and advanced designs that can easily serve as stepping stones to almost any kind of circuit you might want to build. 384 pps., 19 big sections, over 600 illus., 8½" x 11".

List Price \$17.95 ● Order No. T-101

Motorola Color TV Service Manual




This brand-new all-in-one handbook covers all models using the TS-907 through TS-924 chassis — including the all-transistor TS-915/919 chassis — all the information you need to know about setup, alignment troubleshooting, etc., slanted specifically to unique Motorola characteristics. In addition to general data, there's specific in-

formation on each chassis, detailing special features, test-point locations, individual alignment procedures, setup kinks unique to each chassis, CRT replacement instructions, troubleshooting tips and modifications, etc. Also, there's a BIG 18-page foldout section with complete schematic diagrams for ALL Motorola Color chassis. 160 pps., BIG 8½" x 11" size, plus 18-page schematic foldout section. Long-life vinyl cover.

List Price \$7.95 ● Order No. 509

Electric Motor Test & Repair

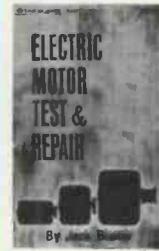


A guide to maintenance practices for all types of small horsepower motors. While many of the larger motor repair shops find it more expedient to replace low horsepower units, re-winding of small electric motors is still a wide-spread and profitable practice. This practical guide contains a wealth of information on testing and re-

winding small motors of every type, including fan, starter, polyphase, capacitor, induction, synchronous, etc. Early chapters tell you how to set up a motor test panel, make general tests and measurements, and advise you about the tools and equipment necessary (such as an armature winder, wedge driver, cutting and gauging board, coil taper, puller plate, etc.). 160 pps., 102 illus. Comb-bound with soft cover.

List Price \$6.95 ● Order No. T-97

Color TV Trouble Factbook

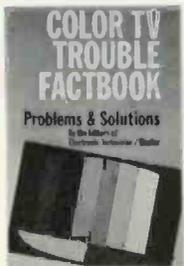

Here's a complete guide to color TV troubles and solutions, arranged by make and model, a low-cost, all-in-one reference handbook every TV service technician should own. The information it contains may easily save you hours of time repairing a "tough-dog" color TV. Included are details concerning repetitive troubles, field-factory

changes, new and unusual circuits and descriptions of how they work, special adjustment procedures and other such pertinent service information. The content is arranged by brand names, covering every major make of color TV receiver produced in the past several years. Models and chassis covered are arranged in alpha-numerical order. 176-pps. Hardbound.

List Price \$6.95 ● Order No. 519

Audio Systems Handbook



Complete reference and guide to audio system design, encompassing home entertainment, commercial sound and studio installations. Chapter 1, covering amplifiers and amplification, explains db and impedances, level limitations, insertion gain, plus a host of other basics necessary for practical system design.

The author goes to great lengths to impart an understanding of these vital ingredients as they apply to overall operation. The same may be said of the treatment in succeeding Chapters on equalizers, mixers, filters, distribution systems, program sources, commercial systems, studios, and loudspeaker systems. 192 pps., 125 illus. Hardbound.

List Price \$7.95 ● Order No. 494

104 Easy Transistor Projects You Can Build



How would you like to have a high-gain telephone pickup, a wireless mike, an electric megaphone, a CB receiver, light dimmer, fence charger, or any one of 104 such useful devices? You can build them yourself, at very little cost, and have a lot of fun in the process. What's more, you're bound to learn a

lot about transistor circuits (including FETs and SCRs). A complete schematic diagram is included for each device, along with a parts list, plus a brief description of its operation and application, and notations concerning any critical points. All of the devices have practical application in the home, on the repair bench, in the ham shack, on your car, boat, airplane, etc. 224 pps. Hardbound.

List Price \$6.95 ● Order No. 462

Handbook of Semiconductor Circuits




Contains 124 examples of standard transistor circuits, complete with operational data for amplifiers, oscillators, logic and switching circuits, power supplies, and various nonlinear circuits. The broad range of circuits included were selected on the basis of application and practicality. A design philosophy section is

included with each group of circuits, thereby providing a basis for understanding circuits other than those selected as examples. This is not a handbook of "preferred" circuits, but rather a collection of practical circuits which have wide application and exemplifying good engineering design. Each circuit description includes data concerning any unique design or operational data, along with schematic diagrams. Hundreds of illustrations and diagrams. 448 pps., 6" x 9". Hardbound.

List Price \$8.95 ● Order No. G-30

Digital Computer Theory

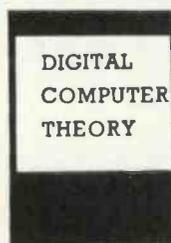

Whether you are a technician or engineer who needs comprehensive knowledge of computer operation, or simply a hobbyist with a passing interest in the subject, this outstanding text is for you. In the first section you are acquainted with basic computer technology, including computer codes and language programming. The second

section presents a detailed study of modern computer logic circuits, such as AND, OR, NAND, and NOR gates. In addition, thorough explanations of basic circuit blocks are discussed—bistable, monostable, and astable multivibrators, Schmitt trigger circuits, etc. Finally, the third section covers memory, control, arithmetic, and input-output units. 320 pps. Hardbound.

List Price \$7.95 ● Order No. 276

Semiconductors From A to Z



Here it is—everything you need to know about semiconductors — from basic diodes and transistors to FETs, MOS FETs, tunnel diodes, integrated circuits, varicaps, photoFETs, light-sensitive and light-emissive devices, incandescent and luminescent optic-electronic circuits, unijunction transistors, field-effect

diodes, SCR and zener diodes, etc. Explains how these various devices work and how they are used, with descriptions of all the common and unique circuits used in modern semiconductor technology. Attention is given to integrated circuit applications — variable-current and constant-current sources, unbalanced differential amplifiers, IC applications in FM and TV receivers, TV sound circuits, discriminator circuits, and cascade amplifier networks. 272 pps., over 300 illus., 26 Chapters.

List Price \$7.95 ● Order No. 493

AN EXTRAORDINARY OFFER...

An Extraordinary Offer

to introduce you to the benefits of Membership in **ELECTRONICS BOOK CLUB**

for a limited time only you can obtain

ANY 3 OF THESE UNIQUE BOOKS ... yours for only **99¢** each
...with Trial Club Membership
(Combined List Price \$34.85)

May we send you your choice of any three books on the facing page as part of an unusual offer of a Trial Membership in Electronics Book Club?

Here are quality hardbound volumes, each especially designed to help you increase your know-how, earning power, and enjoyment of electronics.

These handsome, hardbound books are indicative of the many other fine offerings made to Members . . . important books to read and keep . . . volumes with *your* specialized interests in mind.

Whatever your interest in electronics—radio and TV servicing, audio and hi-fi, industrial electronics, communications, engineering—you will find that Electronics Book Club will help you.

With the Club providing you with top quality books, you may broaden your knowledge and skills to build your income and increase your understanding of electronics, too.

How You Profit From Club Membership

This special offer is just a sample of the help and generous savings the Club offers you. For here is a Club devoted exclusively to seeking out only those titles of direct interest to you. Membership in the Club offers you several advantages.

1. Charter Bonus: Take any three of the books shown (combined values up to \$34.85) for only 99¢ each with your Trial Membership.

2. Guaranteed Savings: The Club guarantees to save you 15% to 75% on all books offered.

3. Continuing Bonus: If you continue after this trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates, plus payment of the nominal sum of \$1.99, will entitle you to a valuable Book Dividend which you may choose from a special list provided members.

4. Wide Selection: Members are annually offered over 50 authoritative books on all phases of electronics.

5. Prevents You From Missing New Books: The Club's FREE monthly *News* gives you advance notice of important new books . . . books vital to your continued advancement.

This extraordinary offer is intended to prove to you, through your own experience, that these very real advantages can be yours . . . that it is possible to keep up with the literature published in your areas of interest . . . and to save substantially while so doing.

How the Club Works

Forthcoming selections are described in the FREE monthly *Club News*. Thus, you are among the first to know about, and to own if you desire, significant new books. You choose only the main or alternate selection you want (or advise if you wish no book at all) by means of a handy form and return envelope enclosed with the *News*. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway . . . without the substantial savings offered through Club Membership.

Limited Time Offer!

Here, then, is an interesting opportunity to enroll on a trial basis . . . to prove to yourself, in a short time, the advantages of belonging to Electronics Book Club. We urge you, if this unique offer is appealing, to act promptly, for we've reserved only a limited number of books for new Members.

To start your Membership on these attractive terms, simply fill out and mail the postage-paid airmail card today. You will receive the three books of your choice for 10-day inspection. SEND NO MONEY! If you are not delighted, return them within 10 days

and your Trial Membership will be cancelled without cost or obligation. Electronics Book Club, Blue Ridge Summit, Pa. 17214.

Typical Savings Offered Club Members on Recent Selections

Philco Color TV Service Manual	List Price \$7.95; Club Price \$4.95
Dictionary of Electronics	List Price \$6.95; Club Price \$5.50
CATV System Engineering	List Price \$12.95; Club Price \$7.95
Solid State Circuit Design & Operation	List Price \$9.95; Club Price \$5.95
1970 Tube/Transistor Substitution Guide	List Price \$4.95; Club Price \$2.50
How to Build a Working Digital Computer	List Price \$7.95; Club Price \$3.95
Small Appliance Repair Guide	List Price \$7.95; Club Price \$4.95
Solid State Circuit Design & Operation	List Price \$9.95; Club Price \$5.95
101 TV Troubles	List Price \$7.95; Club Price \$4.95
Zenith Color TV Service Manual	List Price \$7.95; Club Price \$4.95
Servicing Electronic Organs	List Price \$7.95; Club Price \$4.95
Digital Computer Analysis	List Price \$10.95; Club Price \$7.95
How to Test Almost Everything Electronic	List Price \$5.65; Club Price \$3.95
How to Use Your VOM, VTVM & Scope	List Price \$6.95; Club Price \$4.95
Radio Operator's Q & A Manual	List Price \$8.95; Club Price \$7.50
Tape Recording For Fun & Profit	List Price \$7.95; Club Price \$4.95
Elements of Tape Recorder Circuits	List Price \$7.95; Club Price \$3.95
Industrial Electronics Made Easy	List Price \$8.95; Club Price \$5.95
Electronic Test & Measurement Handbook	List Price \$7.95; Club Price \$4.95
Installing Hi-Fi Systems	List Price \$7.95; Club Price \$4.95
Pinpoint TV Troubles in 10 Minutes	List Price \$6.95; Club Price \$4.95
Easy Way To Service Radios	List Price \$6.95; Club Price \$3.95
Practical Color TV Servicing Techniques	List Price \$8.95; Club Price \$5.95
Mathematics for Electronics	List Price \$10.95; Club Price \$7.95
Transistor Projects	List Price \$5.95; Club Price \$2.95
Electronic Musical Instruments	List Price \$10.00; Club Price \$7.95

SEND NO MONEY! Simply fill in and mail postage-paid Airmail card today!

IF YOU SELL OR SERVICE TV SETS BY

**HITACHI
COLUMBIA
SHARP
MIDLAND
DELMONICO
SANYO
HAYAKAWA**

... YOU CAN NOW BUY THE SAME HITACHI REPLACEMENT RECEIVING TUBES AND CRT'S THAT WERE SELECTED BY THESE MANUFACTURERS AS THE FINEST ORIGINAL EQUIPMENT AVAILABLE!

International Importers assures IMMEDIATE DELIVERY of America's most complete inventory of high quality, high performance HITACHI receiving tubes and picture tubes for black and white and color TV, Hi-Fi and communication equipment.

Contact us for the name of your nearest distributor



INTERNATIONAL IMPORTERS, INC.
2244 South Western Avenue • Chicago, Illinois 60608
Telephone: (312) 847-6363



ET/D

COLORFAX

continued from page 40

to position body of resistor in a location at least two to three inches away from any of the remote control motors (i.e., color, tint, volume). This action may involve a simple relocation of the terminal board further rearward on the TMA bracket. Resistor R95 is accessible without pulling the TMA or chassis.

It is recommended that all service technicians carry sleeve "spaghetti" and small, isolated-type terminal boards when making in-home service calls on referenced receivers.

SYLVANIA


Color TV—Testing the Focus Rectifier

One problem confronting the TV technician is finding a method to check color TV focus rectifiers either in the home or shop.

Normally, the technician usually checks the raster scan line sharpness while adjusting the focus to determine the rectifier's merit, then moves on to the next decision.

Obvious failure usually generates a very pungent odor, smelling of burned selenium, or show scorched spots along the cell's outer covering.

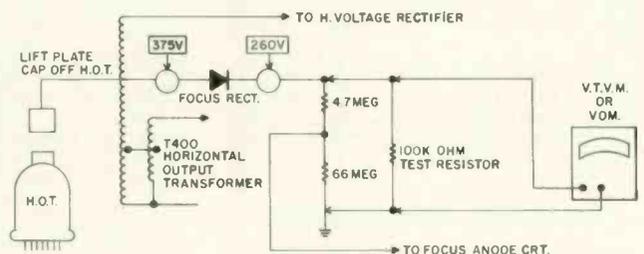Focus rectifiers, like many other type electrical components, can look normal and be right on the money in its capability to generate the correct focus anode voltage. However, there are times when a focus rectifier may seem normal, but when used as a replacement part, proves no better than the defective one, producing the original symptom.



Circuit tests for a focus rectifier are somewhat different than a power diode or signal diode due to the high voltage required to forward bias the cells into conduction. An in-circuit testing procedure other than the visual CRT inspection is needed.

There is a focus rectifier testing circuit built into every color TV chassis, whereby the rectifier's merit can be determined. It means simply, to use the circuit formed by the horizontal transformer, focus rectifier and voltage divider in the following manner. (1) Remove the horizontal output tube from socket. (2) Shunt a 100K (one to two watts) across the divider to ground (4.7M and 66M ohm resistors). (3) Place a voltmeter across the 100K resistor (use 500vdc scale as a protective measure). (4) Turn on the TV power. (5) Note the voltage drop across the 100K resistor. (6) Move the voltmeter probe to the rectifier's other end (anode). Note the voltage. (7) The focus rectifier's merit factor should be over 60 percent as figured in the following way:

$$\frac{E_{100K}}{E_{anode}} = F \text{ merit} \times 100 = F \text{ merit percent}$$


The rectifier with the highest merit factors are the best.



KAY-TOWNES

THE COMPLETE LINE OF
UHF-VHF-FM ANTENNAS AND SYSTEM COMPONENTS


"FOR A BETTER PICTURE FROM ANY SET"

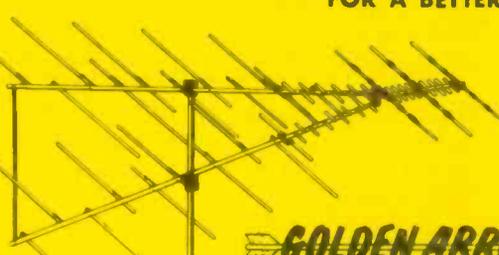

GOLDEN ARROW
Engineered for the
Ultimate in Color Reception


(GA-110 UVG)

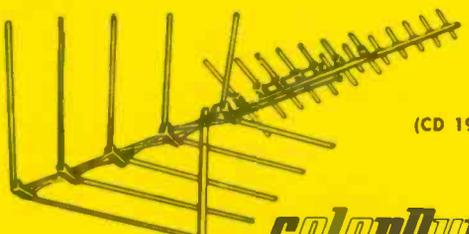12 MODELS FOR EVERY VHF and UHF-VHF-FM NEED



colorDyne
UHF-VHF-FM COMBINATION
4 MODELS
FOR EVERY RECEPTION NEED

(CD 19G)

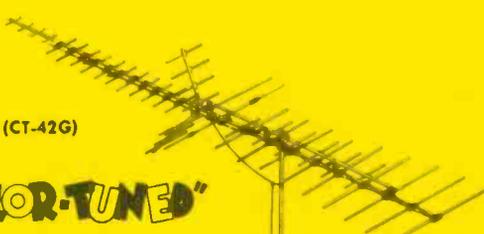

"COLOR-TUNED"
5 MODELS
Engineered for Color Perfection UHF-VHF-FM

(CT-42G)



colorphase
COMBINATION
All 82 Channels

Now 7 MODELS
For All UHF-VHF-FM Needs

(CPC-27G)


All New!

KAY-TOWNES HI-CARBON
GOLDEN MASTS

Telescoping or Straight Lengths

The ONLY DOUBLE PROTECTED Gold Telescoping Mast in the industry! High lustre Chromate Gold Finish over pre-galvanized steel tubing. Individually wrapped in heavy cardboard tube for protection in shipping. 5 and 10 ft. expanded end, telescoping mast to 50 ft.

Double Protected Inside and Out!

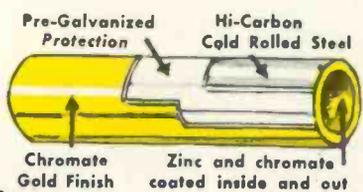

ALSO
STANDARD
PRE-GALVANIZED

New DISTRIBUTION AMPLIFIERS



Solid State-Broad Band
Lightning Protected
Circuitry

Three, rugged, high gain amplification systems allowing use of 4 sets from one antenna on all 82 channels. Especially designed for better color reception.

ColorAmp 4
(75 or 300 ohms)

ColorAmp Tandem 4
(75 ohms)

5 Transistor, high gain, 4 set distribution amplifier for extreme fringe areas.

HI-GAIN AMPLIFIERS ANTENNA MOUNTED

ColorAmp A-2

High gain, 2 set, antenna mounted amplifier. 3 transistors. For extreme fringe areas.

ULTRA LOW LOSS MATCHING TRANSFORMERS SPLITTERS - COUPLERS



A Model For Every Need

SEE US AT THE CHICAGO NEW SHOW
BOOTHS 3511-13
And In Our Hilton Hospitality Room

KAY-TOWNES antenna co.
P. O. BOX 593 · ROME, GA. 30161 (404) 235-0141

... for more details circle 125 on Reader Service Card

For additional information on products described in this section, circle the numbers on Reader Service Card. Requests will be handled promptly.

COLOR TV

703

Finished in dark pine

An Early American television console is among five color television sets and a B/W model introduced. The



CF722N is finished in dark pine and has a 23in. picture measured diagonally (29.5sqin. viewable). It includes Sylvania's Color Bright 85 high contrast picture tube and the Gibraltar chassis designed for maximum reliability. The television has the Instant Color feature which assures a picture seconds after the set has been turned on. Also included are automatic fine tuning control (AFC) and lighted channel indicators. Manufacturer's suggested list price for the CF722N is \$579.95. Sylvania.

BIAS SUPPLY

704

Three separate bias supplies

Announced is a bias supply for color TV alignment. The company's earlier model, BE113, provided only two



negative output 20v supplies. The BE156 supply meets the demands of the TV manufacturers by providing three separate 25v supplies that can be switched positively or negatively as indicated in the alignment instruc-

tions. Tube operated receivers require negative voltages while most solid-state receivers specify positive voltages. The seventh range of negative zero to 75v has been provided to meet the specifications of the manufacturers who use 67.5v to bias the chroma amplifiers during alignment. The seven-in-one bias supply is said to be universal so that it can be used with any sweep and marker generators. All three supplies are well filtered at 1/10 of one percent ripple and have little or no interactions between them. Price is \$24.95. Sencore.

705

CCTV CAMERA AND MONITOR

Automatically adjusts to line voltage variations

An all solid-state circuit television camera and 9in. monitor designed to meet the need for an economical yet reliable CCTV system is introduced. The new units are compatible with existing systems and offer the same quality as the heavy duty industrial CCTV system. The camera incorporates the latest space-age technology with all components, except the vidicon and deflection assembly, on a sin-



gle snap-out circuit board for optimum serviceability. The camera includes standard features not generally available with low-cost units such as three-in-one lens kit for wide, medium and tight angle viewing and no external or exposed controls except a simple on/off switch. Once installed and adjusted, the unit cannot be accidentally misadjusted. The camera is designed to automatically adjust to line voltage variations typically encountered in large plants and industrial buildings. The unit also has a 24vac operational capability which often eliminates the need for power line and conduit installations. The camera provides 650 lines horizontal resolution and is equipped with an RF output which permits hook-up to any


standard broadcast TV receiver. Ideal for retail stores, banks, manufacturing plants, transportation companies or any CCTV application with a standard indoor environment, the camera is priced at \$625 and the 9in. monitor \$175. Motorola.

TV CARTON/DISPLAY

706

Converted in seconds into a dealer display

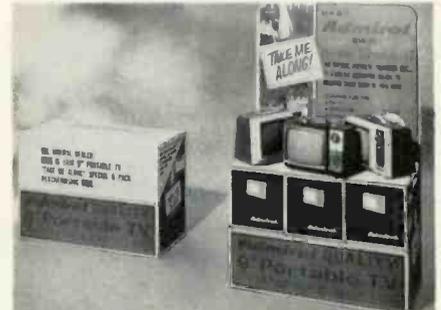A specially designed shipping carton for six portable television sets that can be converted in seconds into a dealer display case is introduced. The



three-color, self-contained display/shipping carton requires only three square feet of floor space and contains 9in. models in white (1), red (2), avocado and white (2), and walnut grain (1) cabinets. The header display card, when set in place, reads as follows: "Take me along. New 1970 Admiral Quality Playmate 9 Portable TV. The anytime, anywhere, television set. . . In sparkling decorator colors to brighten every room in your home. Designed for the patio, bedroom, family room, den, kitchen and workshop." The upper front of the carton is scored, and when removed, it displays a row of three receivers. There is also room for displaying three additional units out of their cartons. Admiral.


INSULATING SPRAY

707

Coating withstands up to 30kv

An improved high voltage insulating spray is announced. The aerosol spray is based on the original insulating formula developed and sold to TV technicians for more than ten years under the name NO-ARC. Reportedly, it has been impossible to use the

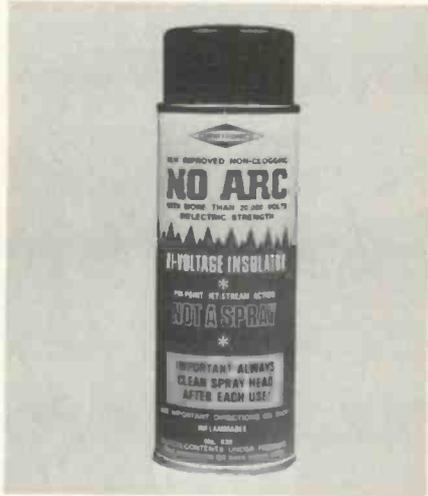original NO-ARC formula in aerosol form because when it dried, it clogged the valves. The aerosol leaves a tough, thick, smooth protective red insulating coating capable of withstanding up to 30kv. The spray is excellent for



stopping arcing and corona shorts in high voltage circuits, especially on color chassis. The aerosol is also recommended for "potting" components as well as waterproofing and insulating printed circuit boards and exposed wiring. NO-ARC is available in an 8 oz can for \$2.79 net. Chemtronics.

STEREO SYSTEM 708

With omni-directional speakers

An Astrosonic custom stereo radio-phonograph that features duo omni-directional speakers is introduced. The new dimension in omni-directional speakers is designed to project stereo



sound in every direction. The unit is equipped with the Air-Suspension speaker system. Speakers are completely isolated from their environment so that the cones literally "float" back and forth for superb response, eliminating feedback and distortion. Two deflector cones disperse sound a full 360 degrees from top and bottom of each speaker system. The modular

Now it costs less to own the best oscilloscope you need.



The New RCA WO-505A Solid-State Oscilloscope

The best you need is the new 5-inch RCA WO-505A, all solid-state oscilloscope. It makes yesterday's general-purpose 'scopes look old-fashioned.

At just \$298.50† the WO-505A offers an unmatched list of features usually found only in more expensive, laboratory type instruments. For example there's the all solid-state circuitry... an illuminated graph screen calibrated directly in volts, and a deep-lip bezel for exceptional clarity. The regulated power supply minimizes trace bounce and provides excellent stability. And the camera mounting studs offer still more evidence of the functional value built into the new WO-505A.

But you've got to see this new RCA 'scope in operation—see the sharp, clean trace it provides—to appreciate it.

Some statistics:

- High-frequency response, usable to 8 MHz.
- High Sensitivity (.05 V p-p range).
- DC vertical amplifier; DC/AC input.
- Return trace blanking... Trace polarity reversal switch... Phase control.
- High-frequency horizontal sweep; solid lock-in on 5 MHz.
- Preset TV "V" and "H" frequencies for instant lock-in.
- Built-in square-wave signal for calibrating P-P voltage measurements.
- Provision for connection to vertical deflection plates of CRT.

Some statistics! For complete details, contact your RCA Distributor.

RCA | Electronic Components | Harrison, N. J. 07029
... for more details circle 134 on Reader Service Card

RCA

*Inexpensive Quality

†Optional Distributor Resale Price

ARROW


AUTOMATIC
STAPLE GUNS

CUT WIRE & CABLE INSTALLATION COSTS

... without cutting into insulation!

SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!

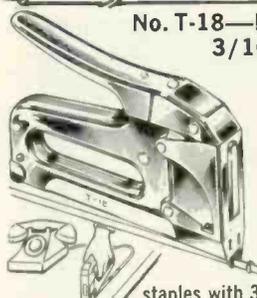No. T-18—Fits wires up to 3/16" in diameter.



BELL, TELEPHONE, THERMOSTAT, INTERCOM, BURGLAR ALARM and other low voltage wiring.

Uses T-18 staples with 3/16" round crown in 3/8" leg length only.

No. T-25—Fits wires up to 1/4" in diameter.




Same basic construction and fastens same wires as No. T-18.

Also used for **RADIANT HEAT WIRE**

Uses T-25 staples with 1/4" round crown in 9/32", 3/8", 7/16" and 9/16" leg lengths.

T-18 and T-25 staples also available in Monel and with beige, brown and ivory finish at extra cost.

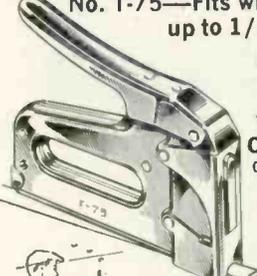No. T-75—Fits wires and cables up to 1/2" in diameter.



RADIANT HEAT CABLE, UF CABLE, WIRE CONDUIT COPPER TUBING or any non-metallic sheathed cable.

Also used as **DRIVE RINGS** in stringing wires.

Uses T-75 staples with 1/2" flat crown in 9/16", 5/8" and 7/8" leg lengths.

Arrow Automatic Staple Guns save 70% in time and effort on every type of wire or cable fastening job. Arrow staples are specially designed with divergent-pointed legs for easier driving and rosin-coated for greater holding power! All-steel construction and high-carbon hardened steel working parts are your assurance of maximum long-life service and trouble-free performance.

Ask your Electrical Supply Dealer or write for further details.

ARROW FASTENER COMPANY INC.
Saddle Brook, New Jersey 07883
*"Pioneers and Pacesetters
For Almost A Half Century"*

... for more details circle 104 on Reader Service Card

ET/D DEALER SHOWCASE

custom unit is in walnut with metal trim. The speakers measure 11in. long, 11in. deep and 15in. high. The tuner-changer unit is 25in. long, 16in. deep and 8 1/4 in. high. A Micromatic record player with diamond/sapphire stylus handles records with precision and greatly lengthens record life. Constant turntable speed is provided by a synchronous four-pole motor. Additional features: muting switch which eliminates noise during change of records; automatic shut-off which turns off the player and amplifier after the last record has played; tone-arm brush to prevent record wear; and lock-down latches that permit moving the component without damage to the player. Included are 45 rpm adapter and dust cover. The tubeless solid-state radio brings stereo FM, noise-free monaural FM plus powerful AM radio. A tuned RF state on FM provides optimum sensitivity and selectivity. The 20w (EIA) solid-state amplifier contributes essential power and flexibility to provide undistorted music reproduction with maximum total purity. Audio control functions include separate variable bass and treble plus compensated loudness and stereo balance controls. A no-drift FM Automatic Frequency Control (FM/AFC) keeps FM stations "locked-in" and an indicator light shows when stereo FM is being received. Auxiliary connections include input and output jacks for component tape recorders and players, as well as jack for stereo headphone. The Astro-Sonic Component FM/AM Radio-phonograph System (Model 1E9274) has a retail price of \$279.90. Magnavox.

VIDEOTAPE SYSTEM 709

Complete low-cost system

A videotape system package is introduced. The VR-50 record/playback system comprises a 1/2 in. video



tape recorder, crystal controlled vidicon camera and an 8in. receiver/monitor. The video tape recorder is

a 1/2 in. unit made by Sony for General Electric. It is compatible with all other Sony 1/2 in. VTR's, including battery operated portables. Completely solid-state, the recorder is a helical scan type with two video heads and one audio head. The camera is the solid-state Model VX-922, with crystal controlled 15,750Hz horizontal frequency. It features 550 line resolution, dual focus, 4000 to 1 automatic light compensation and a 25mm f1.8 lens. Completing the package is a Sony CVM 51UWP-9in. receiver/monitor. This unit can be used to pick up off-the-air broadcasts and process them for videotaping. It can also be used as a playback monitor. The package is easy to operate because it plugs together with ease and most controls are automatic. It can be used for taping broadcasts off-the-air, as well as the pickup of the vidicon camera. If a microphone is added, sound and picture are recorded simultaneously with good synchronization. The VR-50 package sells for \$595. GBC.

CASSETTE STEREO 710

Features a fast forward/fast rewind

An addition to the line of car stereo players is a cassette stereo tape player, Model CS-204. It features a fast forward/fast rewind control and uses



the same pre-recorded cassettes that are in such widespread use in home stereos and portable cassette players. The cassette car stereo is turned on automatically when you insert the cassette through the dustproof door. The cassette is ejected automatically when the end of the tape is reached, or it can be removed at any time by pushing the reject button. This also serves to turn the unit off. There are separate volume, and tone controls, plus a balance control. An indicator lamp glows when the set is on. The unit is all solid-state and operates from a 12v car battery. The lightweight, compact unit mounts easily under the dash with a mounting bracket provided. Specifications: Power Source: 12v car battery (neg. ground); Output: 10w (each channel); Frequency Response: 40-10,000Hz; Track system: 4 track, 2 channel; Tape speed: 1 7/8 ips; Semiconductors: 19 transistors, 1

GREATEST TV Schematic Bargain EVER Offered

NOW-Complete TV Schematics for less than 5¢ each

COLOR TV
Covers ALL
Color Sets
1960 - 1968

BLACK & WHITE
Coverage for
23 U.S. Brands
1965 - 1968

TV TECH/MATICS - 8 Giant Volumes

Cover 99% of Color TV-4 Years B&W!

Here are FABULOUS savings on nationally-known TV schematic and service data. Here is everything you need to fill your vital service data needs for TV model years 1965 through 1968 . . . plus COLOR TV coverage from 1960 through 1968! What it amounts to is a low, low cost of less than \$7.50 per year for your TV service data . . . with an extra 5 years of Color TV coverage thrown in for good measure!

SERVICE DATA FOR MORE THAN 20 BRANDS

TV TECH/MATICS is the ideal Service Data package for today's modern technician. It includes complete schematic diagrams and vital servicing data for every TV receiver produced by more than 20 leading American Manufacturers for 1965, 1966, 1967, and 1968. All diagrams and servicing details are completely authentic, based on information provided by the original equipment manufacturers. Each year's coverage is permanently bound into two convenient-to-use volumes which open flat to 11" x 29½", ready to provide you with instant service data at your workbench. Some of the diagrams are as large as 58" x 22".

EASY TO USE

TV TECH/MATICS is easy to use. Brand names are arranged alphabetically by model year. No more hunting through several file drawers to find the schematic you need! And at the special low price, think of the savings you will enjoy on your schematic needs . . . think of the time you'll save by having the schematics you need right at your fingertips in handy, permanently-bound form!

TV TECH/MATICS is the ideal way to cut down your schematic expenses, and to enjoy the convenience of having all your data needs right at your fingertips.

HERE'S WHAT YOU GET

You receive 8 BIG volumes in all, two for each year from 1965

8 BIG Volumes
Regular Price **\$79.60**
... NOW YOURS
for only **\$29.95**

through 1968. Included is a clearly detailed and annotated TV schematic diagram for each specific model. You also get complete replacement parts lists, alignment instructions, tube and component location diagrams, plus key waveforms and voltage readings . . . all the information you need to service over 90% of the TV receivers you'll encounter!

Compare that with the over \$100 a year you may now be paying for comparable information.

STREAMLINED AND CONVENIENT

All the information for a given model is contained on two facing sheets. The special bound-leaf format allows pages to lie flat when open. Each volume is organized alphabetically by manufacturer, then numerically by model number. In addition, a handy Chassis/Model Finder is bound into each volume. Regular list price for each year's coverage — 2 BIG volumes — is \$19.90. All 8 volumes normally sell for \$79.60. Your price is ONLY \$29.95 . . . a savings of nearly \$59.00!

MONEY-BACK GUARANTEE

You MUST be satisfied that TV TECH/MATICS is the greatest bargain in TV Schematics ever offered. Order at our risk for FREE 10-day examination. Prove to yourself they are worth many times the price. You can return them in 10 days for full refund or cancellation of invoice. No need to send money. But, the supply is limited, so fill-in and mail the NO-RISK coupon today to obtain these time-saving, money-making manuals.

-CONTENTS-

CONTENTS 1965 MODELS

Covers all 1965 models for: Admiral, Airline, Andrea, Coronado, Curtis Mathes, Dumont, Electrohome, Emerson, Firestone, General Electric, Magnavox, Motorola, Muntz, Olympic, Packard-Bell, Philco, RCA Victor, Sears-Silvertone, Satchell-Carlson, Sylvania, Truetone, Westinghouse, and Zenith . . . plus all color sets 1960-1965, at no extra cost!
PUBLISHER'S LIST PRICE . . . \$19.90

CONTENTS 1966 MODELS


Covers all 1966 color and B & W models of: Admiral, Airline, Andrea, Coronado, Curtis Mathes, Dumont, Emerson, General Electric, Hoffman, Magnavox, Motorola, Olympic, Packard-Bell, Philco, RCA Victor, Sears-Silvertone, Satchell-Carlson, Sonora, Sylvania, Truetone, Westinghouse, and Zenith.
PUBLISHER'S LIST PRICE . . . \$19.90

CONTENTS 1967 MODELS

Covers all 1967 color and B & W models of: Admiral, Airline, Andrea, Coronado, Curtis Mathes, Dumont, Emerson, General Electric, Hoffman, Magnavox, Motorola, Olympic, Packard-Bell, Philco-Ford, RCA Victor, Sears-Silvertone, Satchell-Carlson, Truetone, Westinghouse, and Zenith.
PUBLISHER'S LIST PRICE . . . \$19.90

CONTENTS 1968 MODELS

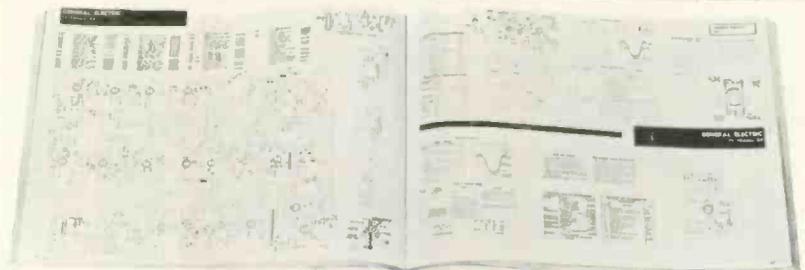Covers all 1968 color and B & W models for: Admiral, Airline, Andrea, Coronado, Curtis Mathes, Dumont, Emerson, General Electric, Hoffman, Magnavox, Motorola, Olympic, Packard-Bell, Philco-Ford, RCA Victor, Sears-Silvertone, Satchell-Carlson, Sonora, Sylvania, Truetone, Westinghouse, and Zenith.
PUBLISHER'S LIST PRICE . . . \$19.90



LARGE PAGES contain complete circuit schematics, replacement parts lists, alignment instructions, critical part locations, important waveforms and voltage readings.

NO RISK COUPON-MAIL TODAY

TAB Books, Blue Ridge Summit, Pa. 17214

- I enclose \$29.95 for which please send me your complete 8-Volume Tech/Matics Schematic offer postage prepaid.
 Please invoice me for \$29.95 plus postage. Same return privileges.

Name
Company
Address
City State Zip
(Paid orders shipped prepaid. Pa. resident add 6% Sales Tax. Outside USA 10% extra.)

ET57

ET/D DEALER SHOWCASE

diode, 4 thermistors; Dimensions: 7 $\frac{1}{2}$ in. W x 2 $\frac{3}{4}$ in. H. x 6 11/16 in. D; Weight: 6 $\frac{3}{4}$ lbs. Price \$89.95. Hitachi.

SPEAKERS

711

Dome cap provides directivity of high ranges

Announced is the release of the Imperial series of full-range custom speakers. The line consists of wide range single cone speakers, custom designed and engineered for studio and home. Each speaker is individually handcrafted to exacting specifications and tolerances. The speaker reportedly will deliver sound quality equal to the finest two and three speaker systems. Cone shaping techniques, together with Barium Ferrite magnets for high magnetic flux, deliver true sound to all input levels. The special dome cap at the apex provides directivity of the high ranges. The Imperial line consists of: FR-4A, 4in. speaker with 16oz Barium Ferrite magnet. FR-5A, 5in. speaker with 20oz Barium Ferrite magnet. FR-6A, 6in. speaker with 24oz Barium Ferrite magnet. FR-8A, 8in. speaker with

36oz Barium Ferrite magnet. All of the speakers develop a claimed basically flat audio response at all levels



of input. Dealers will be supplied with an attractive walnut counter display for point of sale merchandise. Speco.

712

CASSETTE TAPE RECORDER

Features hidden miniature microphone

Introduced is the Model 110 Cassette-Corder featuring a built-in hid-

den electret condenser microphone. The unit is light weight, compact, easy to operate and features the Sony-automatic Recording Control which automatically adjusts varying sound levels to a constant volume when recording. It also features an auxiliary high level input for recording from radio, television, telephone pick-up or other high level sources. In addition, an End-of-Tape-Alarm gives an audible warning signal when the end of the cassette has been reached during recording. The unit measures 5 $\frac{1}{2}$ x 2 $\frac{3}{8}$ x 9 $\frac{3}{8}$ in. and weighs less than five pounds. It has a piano-key-type push-button release and cassette ejector for quick and easy access to tape cas-




ettes, as well as piano-key-type push-buttons for other control functions. The unit may be operated with either a built-in snap-on battery pack containing four "C" cells or a rechargeable nickel cadmium battery pack.

flameless 1000° heat

Instant, precise heat for 1001 uses — shrink tubing, soldering-desoldering, forming, bonding, deburring, drying, setting adhesives. World's most complete line. Models from 200-1000°F. Send for new free Catalog 109.

you can hold in your hand

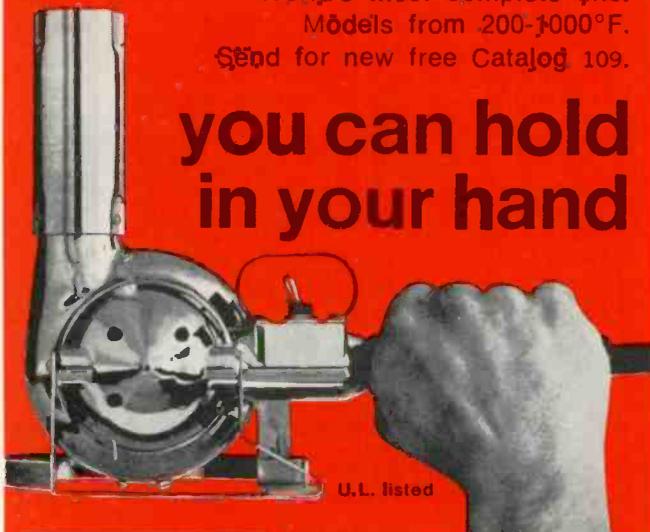


U.L. listed

MASTER HEAT GUNS

1745 FLETT AVE., RACINE, WI 53403

"IT'S GOOD BUSINESS
TO HIRE THE HANDICAPPED."

ISN'T THAT A GREAT IDEA, SNOOPY?

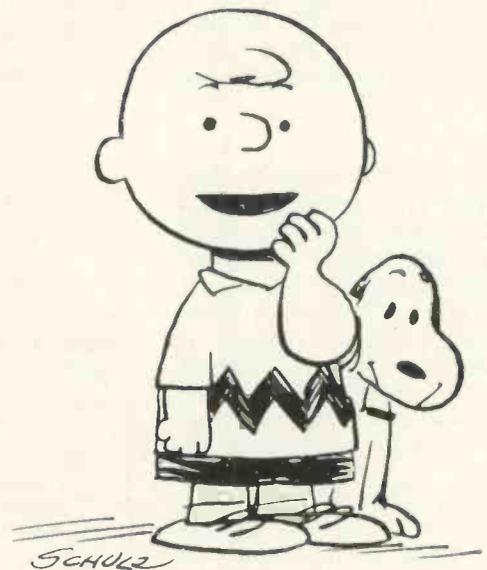

THE PRESIDENT'S COMMITTEE ON EMPLOYMENT
OF THE HANDICAPPED, WASHINGTON, D. C.

The unit includes a cardioid microphone with remote start and stop switch, earphone, leather carrying case and a 60-minute tape cassette. Price \$99.50. Sony.

DESOLDERING TOOL 713

*Self-cleans
tip when loaded*

Introduced is a low-cost desoldering tool. The Soldavac is within the price range of everyone, yet it offers similar features of the industrial desoldering tools. The high vacuum desoldering action is accomplished by release of a spring loaded plunger. The tool is re-loaded by pushing forward on the plunger tab until latched. To desolder,




simply position the tip of the loaded Soldavac tool lightly against a heated solder joint and depress the trigger lever. Molten solder is instantaneously drawn up into the barrel by the high vacuum stroke. The desoldering tool made from lightweight, durable plastic is easy to handle and it self-cleans the tip each time it is loaded. Retail price \$2.95. Edsyn.

STEREO TUNER 714

*Employs five gang
tuning capacitor*

Introduced is the Model AT-200U Stereo Tuner which incorporates a five gang tuning capacitor in its front end as well as three field effect transistors. The front end is designed with emphasis on sound quality, selectivity and sensitivity. This unit incorporates

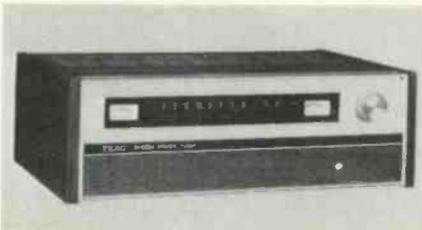hybrid IC's and mechanical filters in the IF stage. It also has an active filter for sub-carrier elimination, a high-




blend noise canceler circuit, and an adjustable FM separation circuit. TEAC.

CASSETTE CIRCULATOR 715

*Ideal accessory for
continuous play*

A cassette "circulator" a snap-on device that gives continuous playback capacity to automatic cassette changers, is announced. The CC6 circulator—a simple but ingenious device with no moving parts—makes possible 12 hours of non-stop, no-repeat playback and then starts the cycle over again. It functions with four to six cassettes, automatically flips each for second-side play, and re-stacks the cassettes for playing again. A cassette moves into the changer's playing chamber and, when finished, is pushed forward by the next cassette. The

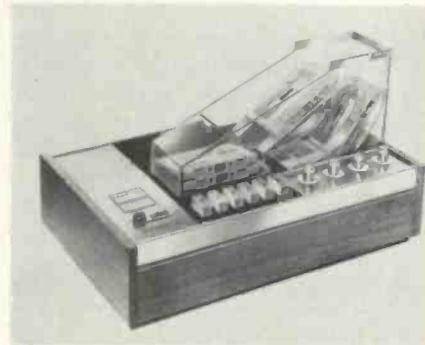fourth cassette nudges the first 'over the hill' and it slides down and back into the playing stack. Styled in tinted plastic and standing five inches high, the circulator is simply snapped on for instant use. It is compatible with Norelco cassette changer models 2401,



2401A, and 2502, as well as Bell & Howell models 332 and 337, and the Ampex Micro 90 and 95. List price is \$19.95. Norelco.

TELEVISION/FM/AM RADIO 716

*Rechargeable battery provides
3.5 hours of viewing*

Introduced is the Pandora Model TR-425BA. At the touch of a button, a 5in. TV screen pops up from a streamlined carrying case. The unit is

Don't shoot till you see the tenths of a volt.

The sure way to troubleshoot solid state TV is with a scope that measures DC.

Take Leader's five-inch LBO-53B:

It gives you a drift-free DC input, so you can see those tenths of a volt. It gives you a bandwidth to 10 MHz. And it gives you a sensitivity of 10 mv/cm or better.

Now for the shocker. You can have a Leader LBO-53B for just \$229, about half the price of any other scope with the same capabilities.

Since the proof is in the seeing, we direct you to your Leader distributor. Ask to see our color bar generators too; you haven't seen the finest until you've seen Leader's.



Seeing is believing.

Leader Instruments Corp.

37-27 27th Street, Long Island City, N. Y. 11101, (212) 729-7411

... for more details circle 127 on Reader Service Card

crafted in midnight black with silver trim. It contains a built-in FM/AM radio—making it a complete portable entertainment unit weighing 12½lbs. The colloid-type batteries fit inside the set but contains no liquid—the chemical is “suspended” in a colloid gell, with never a worry about leakage. The receiver features overnight recharging and provided 3.5 hours of viewing on a single charge. The battery has a life-span of more than 500 hours. The unit features up-front slide-rule tuning for UHF, an up-front 3½in. dynamic

speaker and personal earphone. The aluminized picture tube with the coil



heater insures long tube life. \$179.95. Panasonic.

CASSETTE TAPE

717

Frequency response from 30 to 20,000 Hz

Introduced is a tape cassette called Super Dynamic SD tape. The cassette offers high fidelity reproduction claimed from 30 to 20,000 Hz, with a virtually flat response curve from 50 to 10,000 Hz. This is made possible by a new type of gamma ferric oxide developed especially for high fidelity reproduction. The tape features greatly improved signal-to-noise ratio; it also substantially reduces head wear. All remarkable properties of tape are based on a combination of new magnetic materials, a special binder system and coating technique as well as an exclusive surfacing process. The



new ferric oxide formulation employs a needle-like particle shape as compared to the rectangular shape of standard tape oxides. This permits eight times greater density of magnetic particles, improving resolution and reducing sound distortion. The new binder system reduces cross modulation and static charge. There is no shedding of magnetic coating, so drop-outs are eliminated. The thickness of the magnetic coating is controlled to .001mm, resulting in low level fluctuations. The tape is packaged in the C-60. TDK.

718

CARTRIDGE TAPE RECORDER

Features hidden cartridge bin

The Bainbridge, Model RS-820S, 8-track stereo cartridge tape recorder with FM/AM and FM stereo radio is



introduced. It features a hidden cartridge bin and four full-range dynamic speakers with 32w of output. The unit

CHANNELLOCK

Gives You More In Hand Tools Including

**THE
HANDIEST
PLIERS
OF THEM
ALL**

Ask any good mechanic. He'll tell you his CHANNELLOCK tongue and groovers are the handiest pliers he owns. Try one . . . you'll agree. A word of caution: be SURE you're getting the original, genuine CHANNELLOCK. It's the only tongue and groove plier with machined, smooth working, undercut channels that never jump out. Look for the CHANNELLOCK trade mark on the handle. GET ALL THE FACTS. Send for our catalog . . . yours for the asking.



TOOLS BY
CHAN NEL LOCK
MEADVILLE, PA. 16335

. . . for more details circle 109 on Reader Service Card

features solid-state design, ac bias and erase. An accidental-erasure guard stops the tape automatically at the end of the last channel. In the selection of FM stations, the AFC control locks in signals to assure drift-free reception. Sliding volume, balance, bass and treble controls are offered. Retail price \$349.95.

BATTERY DISPLAY 719

Self service convenience saves space

Announced is a transparent plastic battery display which saves restocking time and counter space. At the same time it stimulates battery sales with self-service convenience. Impulse carded merchandise is held in removable side hangers. Batteries are gravity fed into position with every sale. Ideal dis-



play for high-traffic areas—reusable and an eyecatcher as a single display or side-by-side units. Stocks flashlight (both "C" and "D" sizes), penlight and transistor batteries. Burgess.

HEAD DEMAGNETIZER 720

Built into cassette cartridge

A demagnetizer which removes excessive magnetic buildup from cas-




sette-equipment heads is introduced. A flat, mylar-copper laminate lead wire permits closing the cover of the player. Other features include a pilot light and operation on standard current. The Model TD-10 lists at \$8.30. Robins.

POWER SUPPLY 721

Solid-state construction

Introduced is a power source for almost any digital, linear or total system application. For digital application the Model PZ-801-A employs a high efficiency power conversion circuit to provide output currents to 5a or 25w from 0-25 volts. Regulation is claimed better than .2 percent and ripple less than 10mv. With the flick of a switch, the unit becomes a regulated (.1 percent) low ripple (1mv) 0-25v, 1a source for linear or general purpose applications. The unit features a 10-turn voltage control, rear

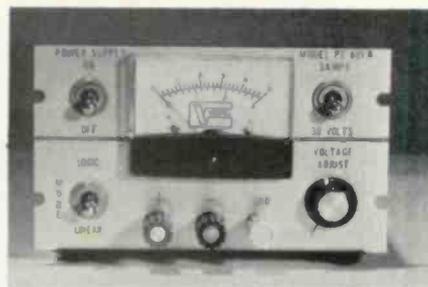panel remote sensing and programming, electronic current limiting, floating output, versatile bench or



rack mounting case, and one year warranty. Only silicon diodes, transistors and integrated devices are used. Price is \$78. Viking.

ACA

ANTENNA CORPORATION of AMERICA

HARRY E. RHEINSCHMIDT

General Manager

BROOKS TOWERS
SUITE 22-D
1020 15TH STREET

DENVER, COLORADO
80202
(AC-303) 892-1481

CLIP and SAVE!

ANNOUNCING...

a new line of patented TV antennas
from a most reliable source

The new ACA Citation line offers a complete selection of VHF, UHF, FM reception in color and black/white. Priced for today's market, with all of the top quality features you expect, including gold-anodized, high tensile aluminum elements, die cut impedance correlators, dual action director/reflector screen and tetrapole collector element.


Also, available from ACA — antenna preamplifiers, booster couplers, matching transformers. Line up today with ACA!

For complete details, write or call:

ACA ANTENNA CORPORATION of AMERICA

Brooks Towers, Suite 22-D • 1020 15th St. • Denver, Colo. 80202 • Tel. 303/892-1481

How to cool off hot-headed customers...

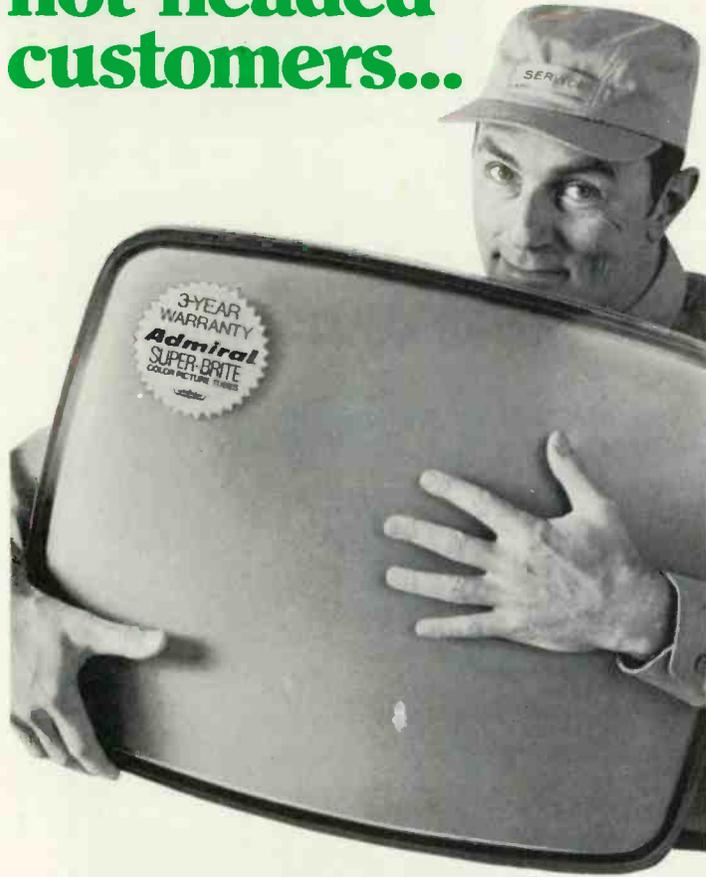

Install Admiral Super-Brite replacement color picture tubes with the 3-year warranty.

Admiral is the only replacement color picture tube with a 3-year warranty. That's a full year more protection for your customers.

Admiral Super-Brite replacement color picture tubes aren't rebuilds. They're brand new. And they're available in the U.S.A. and Canada. From Admiral, producers of more rectangular color picture tube sizes than anyone in the world.

Now, watch your customers warm up to you for steering them right.

Admiral

Mark of Quality

Admiral Corporation warrants this picture tube to be free from defects in material or workmanship for 3 years after date of sale to the customer. Admiral's obligation is limited to supplying a suitable replacement picture tube. This warranty is effective if the picture tube is registered with Admiral within 10 days after date of sale to the consumer.

... for more details circle 101 on Reader Service Card

ET/D NEWS OF THE INDUSTRY

Fairchild DuMont Announces Implosion Protected CRT

A computer readout CRT with implosion protection is announced by DuMont Electron Tubes, a division of Fairchild Camera and Instrument Corp.

According to E. W. Swenarton, division sales manager, this tube is certified to meet the Underwriters Laboratories, Inc. testing criteria for bonded frame picture tubes.

This tube, the DuMont Type KC2827P31M has been extensively tested for performance, life, and safety. The close spacing between operator and terminal in most applications dictate strict safety requirements. This tube is but one of a series of terminal oriented system display tubes that range in size from 2¾ by 3¾ in. up to 16½ by 20½ in. with resolution capability up to 40,000 distinct spots per square inch of screen.

The tube can be mounted in any position and can be driven by highly efficient transistor and/or IC circuits. Design parameters include low heater power, zero power low voltage electrostatic focus and low magnetic deflection power. The small 20mm diameter neck contributes to the overall small size and performance. DuMont can design any size and shape CRT to meet your requirement of mechanical, electrical or safety designs. Price is under \$40.00 for production quantities. Samples can be obtained in three to five weeks, ARO. Fairchild.

Color CRT Sales Up in 1969

Color television picture tube unit sales were up 1.3 percent to 6,255,000 units in 1969, according to figures released by the EIA Marketing Services Department.

Sales to the renewal market increased 19.3 percent to 765,000 units, while exports were up 54.9 percent to 175,000 units, EIA statistics show.

Unit sales of TV picture tubes were down 6.5 percent during 1969, totaling 11,232,000 units compared with 12,018,000 units in U.S. factory sales during 1968.

Monochrome TV picture tube sales amounted to 5,077,000 units valued at \$80.5 million during 1969, a decrease of 14.7 percent and 9 percent respectively from unit and dollar sales during 1968. Dollar sales decreases were registered by sales to original equipment manufacturers, the renewal and export markets.

Belden to Expand Electric Cord Plant

Belden Corp. will expand its Electric Cord Products Co. manufacturing plant at Franklin, N.C. The announcement was made by Robert W. Hawkinson, president of the Chicago-based company.

He said a 17,000sqft addition will be constructed as part of the company's present 46,000sqft plant, which has been in production since 1966. "The expansion will increase Belden's cord manufacturing capacity by 25 percent at Franklin. Scheduled for completion in the third quarter of 1970, this major project reflects our confidence in the appliance cord market, particularly in the original equipment segment," Hawkinson said.

The expansion will add 50 to 60 employees to the Franklin plant's current employment of approximately 190.

The expansion is the second major capital expenditure announced by Belden. On March 3, the company disclosed plans to construct an insulation compounding facility adjacent to its Jena, La., plant. The automated, \$3 million facility, scheduled for completion in the second quarter of 1971, will produce insulation used at the company's transportation products and electrical lead wire plant at Jena and at other company plants.

Belden's wire, cable and cord products are used in electrical, electronic, transportation and consumer markets. In addition to its plants in Franklin, N.C., and Jena, La., Belden has plants in Chicago, Richmond, Ind., and Pontotoc, Miss. A manufacturing subsidiary, General Wire and Cable Co., Ltd., has two plants in Cobourg, Ontario, near Toronto.

RCA Plans to Provide Service For All Makes of Television

RCA has announced plans for the establishment of a new subsidiary company to provide servicing of all makes of television sets and other home entertainment units.

Anthony L. Conrad, Executive Vice-President, Services, said the new company will operate independently of the RCA Service Company branches, which will continue to concentrate exclusively on the servicing of RCA products and Whirlpool appliances.

"The decision to service other brands was based on extensive internal studies and governmental agency consumer reports which indicated an expanding need for service in the entire consumer products industry," Mr. Conrad said.

The new company will be initially established in selected urban areas and gradually expanded to operate on a national scale. Present plans call for the first of the new service centers to be opened in the Philadelphia area by mid-year, with the San Francisco area listed for late September.


TV, Radio and Tape Equipment Have Record Sales Year in 1969

1969 total U.S. sales of consumer electronic products, including domestic label and foreign label imports, were released by the Electronic Industries Assn.'s Marketing Services Department. Television, radios and tape equipment sales hit all time highs. Phonograph sales were only slightly below their record year of 1968.

Total television sets sales were 13,307,889 compared with 13,211,206 sets sold in 1968, which was the industry's next best year. Color TV sales were 6,191,307 sets in 1969 vs. 6,213,347 sets in 1968, and monochrome TV 1969 sales were 7,116,083 sets vs. 6,995,736 sets in 1968.

Total U.S. radio sales passed the 50 million unit mark for the first time. Radio sales were up 9.6 percent in 1969,

Join the Admiral S&H book club.

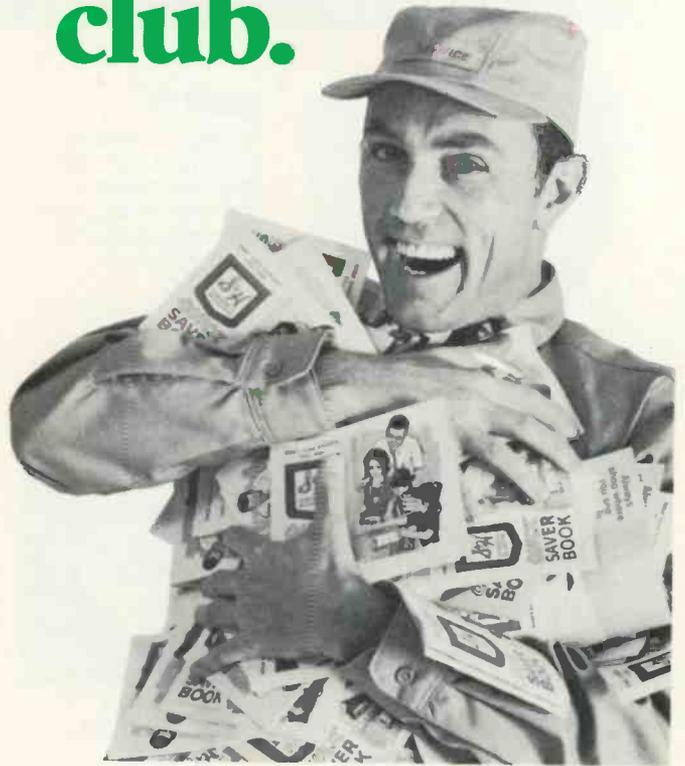

Get a free book of S&H Green Stamps with every Admiral Super-Brite color picture tube purchase.

Get a certificate worth 600 stamps (½ book) with every Magna-Brite color picture tube you buy.

Every book puts you closer to owning a set of luggage, a pool table, or any other item in the 180-page S&H Gift Catalog, including a 14-foot sailboat.

Register now with your Admiral Distributor and learn all the details about "A Brighter Year Ahead." Or use the Reader Service card.



Admiral Corporation,
3800 Cortland Street, Chicago, Illinois 60647.

Admiral

Mark of Quality

... for more details circle 102 on Reader Service Card

TOOL KITS

FIELD ENGINEER TOOL KIT JTK-17



More than 100 fine tools required for servicing in the field. Used on communications equipment, business machines, computers, all kinds of electronic systems. All tools and VOM tester are furnished in deluxe attache' case. Write for details.

JTK-17 \$212.00

Free Catalog — ELECTRONIC ASSEMBLY TOOLS


JENSEN TOOLS and ALLOYS
4117 N. 44th Street, Phoenix, Arizona 85018

... for more details circle 123 on Reader Service Card

You're making money in electronics now.

RCA Offers 4 Ways to Make More.

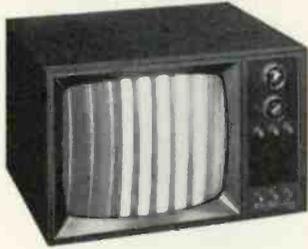Study at home... set your own pace.
RCA Institutes has an easy approach
to bring you bigger earnings.



COLOR TV:

During this course you'll perform over 50 experiments—and receive all parts and instructions to build your own color TV.


The cost of the Color TV Kit is included in the tuition in both the beginner's program and the advanced course in color TV servicing.

Course is based on the latest receiver circuitry and equipment.

SOLID STATE TECHNOLOGY

New courses include the latest findings and techniques in this field.

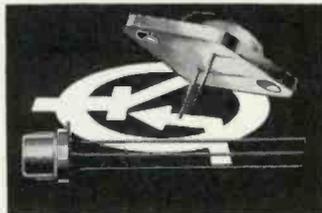Information you must have if you are to service the multitude of solid state instruments and devices used in TV, Digital, and Communications equipment.



FCC LICENSE TRAINING:

Choose the course for the FCC License you want: third, second or first phone. If you need basic training first, apply for the complete License Training Program. Get your License—or your money back.

CATV TRAINING:

You'll receive two comprehensive lessons, covering the practical phases of CATV systems in either the Television Servicing or Communications courses.

Licensed by New York State Education Department. Approved for Veterans. Accredited Member National Home Study Council.

RCA

MAIL THE COUPON NOW FOR COMPLETE INFORMATION.

RCA INSTITUTES, Inc., Dept. 225-005-0

320 West 31st Street, N.Y., N.Y. 10001

Please rush me FREE illustrated catalog. I understand that I am under no obligation.

Name _____ Age _____
(please print)

Address _____

City _____

State _____ ZIP _____

... for more details circle 132 on Reader Service Card

ET/D NEWS OF THE INDUSTRY

totaling 51,352,742 units vs 46,832,140 in 1968, and personal radio sales of 39,413,857 units also was a record year—and radios with FM exceeded AM only radio sales for the first time ever. Auto radio sales of 11,938,885 units in 1969 were slightly behind the record 12,509,841 sold in 1968.

Phonograph sales of 6,320,248 in 1969 were slightly below the 1968 total of 6,494,612.

Although EIA's total U.S. sales figures for magnetic tape equipment (a category which includes reel to reel, cartridge and cassette units) are incomplete, tape recorder and cassette sales increased 24.3 percent over 1968—6,929,527 vs. 5,573,145. Also tape cartridge player imports doubled in 1969, indicating a record year in the entire tape equipment category.

Color TV Ahead Consumer Electronics Off

Distributor sales to dealers were generally off the October 1968 pace. However, color television, auto radio and portable and table phonograph year-to-date sales were slightly ahead of 1968, the Electronic Industries Assn.'s Marketing Services Department reported.

Distributor sales of color television sets to dealers were down 22.5 percent during October as compared with sales during the same month the year before. In October, 506,358 sets were sold to dealers, compared with 653,691 the same month last year, EIA reported. Color TV sales to dealers were 4,568,602 sets for the year-to-date, 1.4 percent ahead of the 4,507,537 sets sold in the same period in 1968.

Monochrome TV sales in October, at 442,161 sets, were down 17.7 percent from the 537,250 sets sold in the same month last year. Total TV sales to dealers, on a year-to-date basis were down 3.2 percent; 8,692,808 in 1969 to 8,977,045 sets the first ten months of 1968.

Total phonograph sales decreased 16.4 percent in October over the same month a year ago and is now 1.1 percent behind a year-to-date basis.

Total radio sales to dealers declined in all categories and are now running 6.6 percent behind on a year-to-date basis.

Essex Acquires Fort Wayne Tool & Die, Inc.

The acquisition of Fort Wayne Tool & Die, Inc., by Essex International, Inc., was jointly announced by Walter Probst, Essex chairman, and Richard G. Nill, president of Fort Wayne Tool & Die.


The firm joins Essex as a wholly owned subsidiary of the company and will continue its operations on an independent basis under Nill's direction. All production and sales personnel of Fort Wayne Tool & Die will be retained and all manufacturing processes will continue at its Engle Road plant in Fort Wayne.

Founded in 1940, Fort Wayne Tool & Die is a pioneer innovator and manufacturer of the automatic stator winding equipment used by electric motor manufacturers.

The acquisition was described by Essex as part of the company's long standing program of servicing the total electrical industry in depth with raw materials, components, finished products, as well as with production oriented equipment.

Essex International, Inc., is a broadly diversified producer of electrical products and controls, metal products and plastics. The firm operates 96 plants in the U.S. and Canada through 10 manufacturing and marketing divisions.

the set choice is yours...

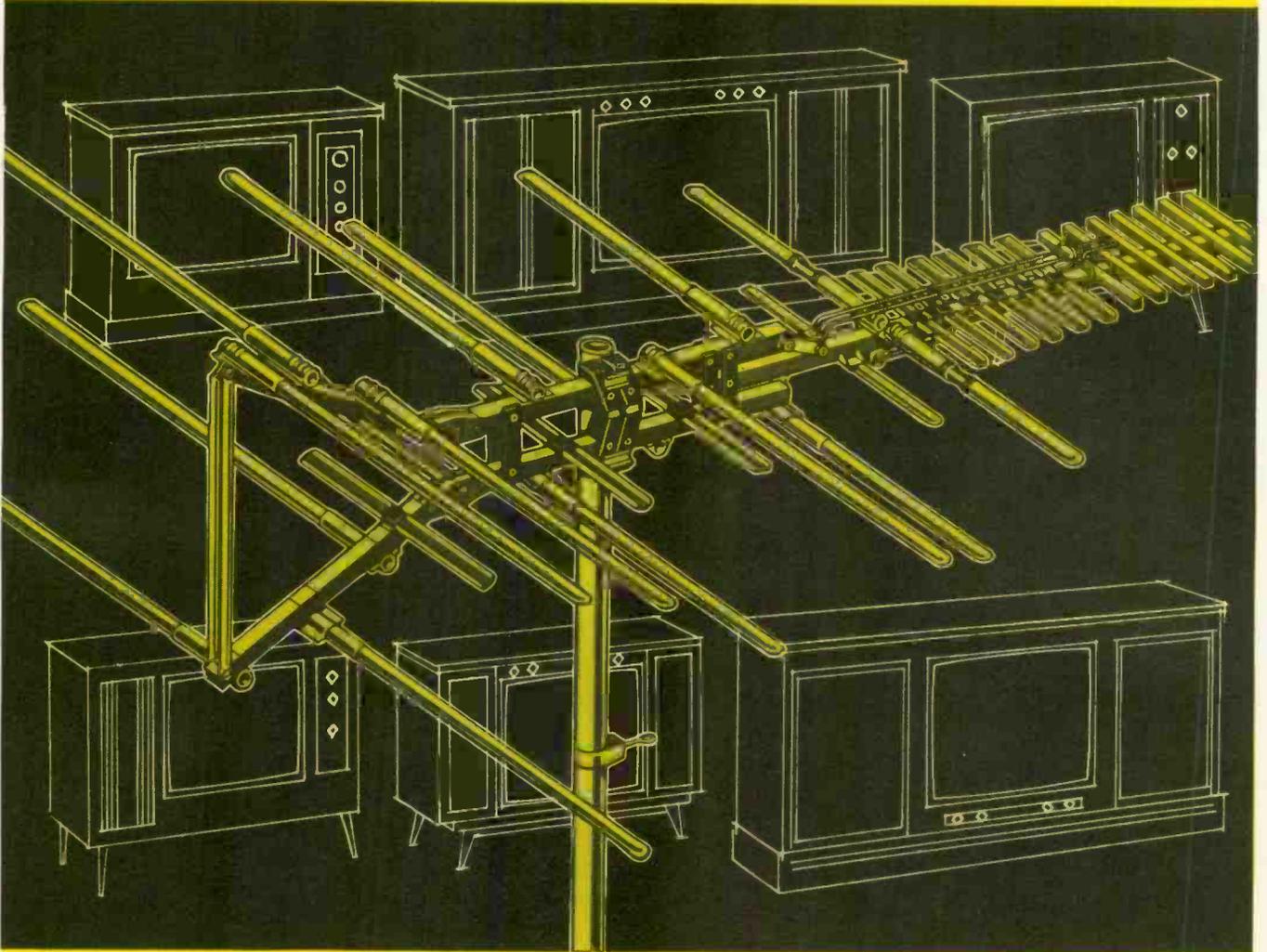

the antenna choice is...

FINCO®

NEW '70 SERIES COLOR SPECTRUM TV ANTENNAS

Send for free Catalog 20-556

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____



**THE FINNEY
COMPANY**

34 WEST INTERSTATE STREET
DEPT. 110-5
BEDFORD, OHIO 44146


For additional information on products described in this section, circle the numbers on Reader Service Card. Requests will be handled promptly.

STAPLES

722

Chemically coated to improve holding power

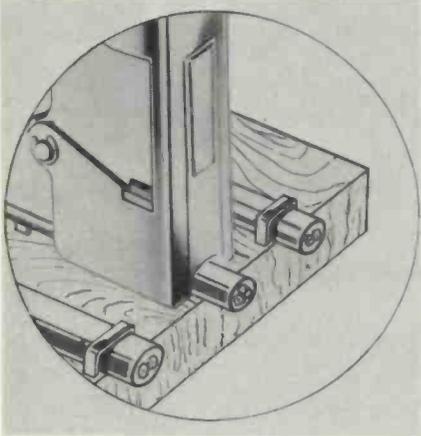Announced is the development of a special chemical coating process, designed to greatly improve the perform-



ance and holding power of their T-75 Staples.

The new staple, to be known as "Grip-Tite," is for use in the T-75 Staple Gun Tacker, a model specially designed for fastening any wire or cable up to 1/2 in. in diameter.

Reportedly the improved staple drives deeper, penetrates more flush and provides many times the gripping power of plain staples without this special chemical coating.

The staples are available in 9/16, 5/8 and 7/8 in. leg lengths, each size individually boxed. Arrow.

CB ANTENNA

723


100w of power from a 5w CB set

Announced is a CB base station called the Boss 404.

The antenna uses yagi beam design with tapered elements to focus signal into a narrow beam, only 52deg at the half power points. Operating in

both the horizontal and vertical modes, the antenna reportedly will produce a signal with an effective rated power of 100w from a 5w CB set.

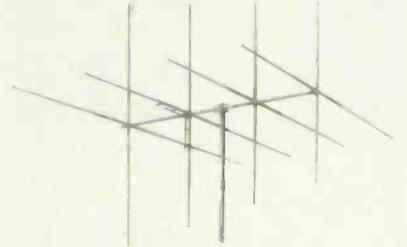The absence of gimmick wires which distort radiation patterns permit this antenna to achieve optimum spacing with a 17ft boom. The antenna can be rotated with a low-cost rotator instead of the expensive units generally required for ham antennas with similar performance. Aircraft aluminum construction with heat-



Little GIANT



SENCORE CG19 CADDY BAR COLOR GENERATOR

Small enough, light enough to carry right in your tube caddy—so you have it handy on every color TV service call.

Little giant in performance. All crystal controlled standard RCA licensed color bars, crosshatch, white dots, vertical lines, horizontal lines. Rock solid or your money back.

New circuitry. Less current drain permits full voltage regulation on all circuits, and increases battery life.

Timer range doubled over previous models.

Lowest priced unit available, \$84.50 All Domestic Made

IN STOCK AT YOUR LOCAL PARTS DISTRIBUTOR.



SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

3200 Sencore Drive, Sioux Falls, South Dakota 57100

... for more details circle 136 on Reader Service Card

treated boom and elements allows the antenna to withstand 90 mph winds.

The optimum spaced elements produce maximum front-to-back and front-to-side ratios greatly reducing interference. Precision horizontal and vertical gamma-match feeds, identical to those used on A/8 ham antennas, produce a VSWR of less than 1.5 to 1, and 1 to 1 if the user likes to fine tune.

The antenna lists for \$99.95. Antenna Specialists.

GOZINTA

724

Cleans controls without removing chassis

A tool designed for effective cleaning and lubricating controls on TV and auto radios, from the front panel is introduced.

It is manufactured from an aluminum alloy with female threads machined on one end. This adapts to the bushing of the control after the knob is removed. A plastic valve extension is contained on the other end, which will pressure-fit the usual aerosol valve of contact cleaners.

Pressure on the valve will force-clean the control. An adapter is supplied for car radios, which eliminates the necessity of removing the radio from the car.

The Gozinta, Model No. wJL and car radio adapter is packaged with a



three-ounce aerosol can of Lubrite. Dealer price is \$2.67. Workman.

SPEAKERS


725

Round design utilizes flat plastic panel

Announced is the addition of a series of flat plastic speakers. Designated as the "Roly-Poly" series, the speakers feature a round thin silhouette construction which permits exact RETMA replacement of the cone speaker equivalent. Constructed entirely of polystyrene material, they offer the advantages of wide range hi-fi reproduction, low distortion, bi-direc-

tional wide angle dispersion and high sensitivity. Light in weight, impervious to moisture and climatic conditions and with minimum depth, the speakers are ideal for all hi-fi applications, public address, industrial, automotive, build-in, and replacement service.

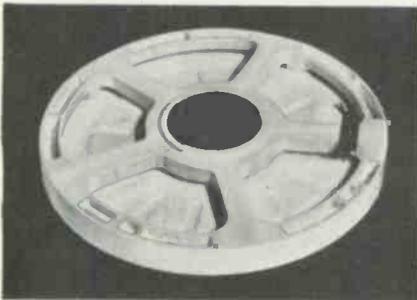A typical unit in the series is the Model RP8. Diameter of this model is 8in. and overall depth is 1in. Frequency response is 40Hz to 20,000Hz, and power handling capacity is 10w RMS, 20w peak. Sensitivity is 90dB/M for one watt electrical input. Directional characteristics are essentially



cardioidal with bi-directional dispersion. The unit uses an electromagnet movement and standard impedance is 8Ω although other impedances are available on order. The speaker can operate at full ratings over the temperature range of -20°F to +175°F. Weight is 11oz. Magitran.

VIDEO/RF SELECTOR— CONTROL CENTER

726

No external power is required

The Model CCV3, a three-position control center that has many uses in video or RF layouts is introduced.



Typical uses allows control of three TV cameras and a monitor, or three monitors and one camera; or for switching low-power RF antenna systems.

The "push-ON" and "push TO RELEASE" switches allow the user to optionally select any of the equipment described.

The unit uses standard "M" type (SO-239) connectors on input and all outputs. The easy access connectors are located on the rear of unit. No external power is required for operation. No internal resistor is used to

NEW ENDECO Desoldering Kits

MODEL 300-K KIT SHOWN



All you need to handle almost any desoldering and resoldering job!



Kit 300K includes the famous Endeco pencil desoldering iron Model 300, six different size tips (.038 to .090) for any job, tip cleaning tool, and metal stand for iron . . . all in a handy lifetime steel storage box. \$19.90 net. Model 300K-3 with a 3-wire cord \$20.90. Also a similar kit for military users. Kit 100K with large Endeco iron (Model 100A) is \$27.40, and 3-wire Kit 100AD-3 \$28.40.

SEE YOUR DISTRIBUTOR OR WRITE



ENTERPRISE DEVELOPMENT CORPORATION

5127 E. 65th St., INDIANAPOLIS, IND. 46220




DECISION MAKER

The Sencore CRT Champion. Judge and jury when it comes to color CRT analyzing. Reaches a verdict in seconds — tells you if the tube has adequate emission, and if it will track in the TV set.

Automatic color tracking according to industry standards with exclusive 3 Gun G2 Control.

One-step controlled rejuvenation with automatic RC timer. A Sencore exclusive.

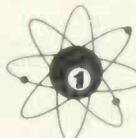Lots more, too. So try the decision maker — the Sencore CRT Champion — at your distributor today. You'll reach the right verdict. \$119.50



SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

ET/D NEW PRODUCTS

affect impedance matches. Cross talk between adjacent channels is negligible.

It has a rugged construction and decorator styled to be placed with any of the newest video and audio equipment. Size: 5 $\frac{5}{8}$ in. x 2 $\frac{1}{8}$ in. x 3 $\frac{9}{16}$ in. Priced at \$19.95. Alcoswitch.

DIGITAL MULTIMETER 727

Low voltage
sensitivity of 1 μ v


Announced is the accuracy of a digital display, coupled with unmatched low-voltage sensitivity of 1 μ v per digit, is available for the first time in a medium-priced 3 $\frac{1}{2}$ digit dc multimeter.

With its wide range of voltage, resistance, and current measuring capability, the Model 160 reportedly offers as much dc versatility as is likely to be useful in any field other than basic research.

DC voltage range of this instrument is reportedly $\pm 1\mu$ v per digit on the most sensitive range to ± 1000 volts maximum, in seven decade ranges. Also, an ac/dc probe is available.

Accuracy, over all ranges, is ± 1 digit, or ± 0.1 percent of the reading at any range.

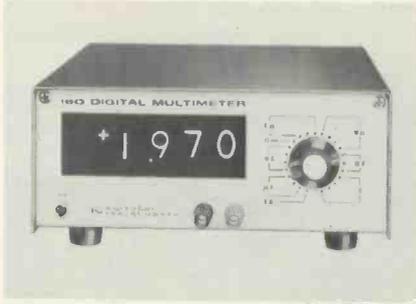Instrument circuitry is designed with a buffer amplifier at the front end instead of the input chopper found in many other meter circuits. The input impedance is 10M on all but its lowest range, where it is 1M. Use of the buffer amplifier also makes it possible for the unit to drive a recorder. The analog recorder output jack is located on the back panel of



the instrument. Recorder output is ± 1 volt, at up to 1ma.

Normal-mode rejection characteristics are excellent, providing a rejection ratio of 80dB at a voltage of line frequency or twice line frequency on the most sensitive range. This value decreases to 60dB on 1kv P-P or higher ranges. Common-mode rejection is greater than 140dB, or up to 1kv P-P.


Settling time to rated accuracy is 2sec.

Check'em ALL!

TRANSISTORS FET'S IN OR OUT OF CIRCUIT



The TF17 works every time using tried and proven signal injection techniques. New, improved tests on special RF transistors and the latest high power transistors, mean that the TF17 is the only up-to-date transistor tester on the market. A new, exclusive setup book in rear compartment guides you to every test for over 12,000 transistors and FETs. The book is not needed for general service troubleshooting. Regular transistors are checked for beta gain and I_{cbo} leakage. FETs are checked for transconductance and I_{gss} leakage. **Only \$109.50**

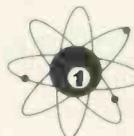

SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

... for more details circle 138 on Reader Service Card

The unit spans a resistance range from the lowest reasonable values that can be measured using two-terminal leads (0.1 Ω per digit), to almost open-circuit readings (2,000M, full scale), in eight decade ranges. Accuracy is claimed within ± 0.3 percent of readings, or ± 1 digit on the 100 Ω to 1M range, decreasing to ± 10 percent on the 100M range. The 1,000M range, intended for relative resistance measurements only, gives ± 50 percent accuracy, satisfactory for these purposes.

Operated as an ammeter, it is capable of excellent accuracy in measuring current all the way from well down in the field-effect transistor leakage current range, up to 2a—as much dc current capability as is likely to be of interest in normal bench use. Scale range is ± 0.1 na per digit to ± 2 a full scale, in eight decade ranges. Accuracy is ± 0.2 percent of reading, or ± 1 digit for all ranges. Input resistance is 100K on the 0.1 μ a range, decreasing to 0.1 Ω for the 1a range.

Temperature stability is reportedly $\pm 0.3\mu$ v per degree centigrade, $\pm 1\mu$ v per day after a 30-minute warm-up. Temperature extremes will not produce a zero shift down through the 100mv range. Even on the most sensitive range, in the typical air-conditioned lab, no more than a one digit zero shift (1 μ v) will occur in the course of an average day.

A rear panel switch permits a choice of grounded or floating input. Resistance between circuit ground and chassis ground is greater than 100M, shunted with a 0.01 μ f capacitor. Circuit ground may be floated up to ± 500 v with respect to chassis ground, for the most exacting measurements.

Function and range selection positions on the single knob control are arranged for maximum ease of operation. Voltage and resistance reading sectors, usually the most frequently used, are adjacent.

The 160 operates on 105/125v or 210/250v, 50 or 60Hz and is therefore usable nearly anywhere in the world. Power consumption is 15w. The unit measures 3 $\frac{1}{2}$ x 8 $\frac{3}{4}$ x 11in. and is priced at \$545. Keithley Instruments.

VTVM

728

Large meter
with mirror scale

Introduced is the Model 1700C, an advanced design VTVM that will meet the technician's most rigid requirements. It has a large 6-in. wide-view meter, mirror scale, with highest quality components utilized throughout. Wide frequency response on ac voltage for compatibility with color TV

servicing. FM multiplex troubleshooting and general industrial application. Double jewelled, inspected D'Arsonal



movement with individual side and tail weights.

This VTVM weighs 5lb and is 8 1/2 x 6 7/16 x 4 1/2 in. Priced at \$49.95, wired. Kit form \$39.95. Mercury.

VIDEO DISC RECORDER 729

Plugs into CCTV or monitoring system

A low-cost, instant playback, slow motion and stop action video disc recorder which can be plugged in to any CCTV or video monitoring system is introduced.

Called the 1310 Video/Disc Recorder, the unit records a 10 or 20sec segment, either direct from camera or from a videotape recorder, for immediate playback at speeds adjustable from 2 frames per second to 60 frames per second. During playback, any one of 60 frames can be stopped and held indefinitely for study or

analysis. The recorded segment can also be transferred back to the videotape recorder to provide a video program combining "live action," slow motion, and stop action.

The unit has been thoroughly field tested and features pushbutton controls designed so that if the operator pushes the wrong button, or any wrong sequence of buttons, the operation of the recorder will not be affected.

Applications for the recorder are seen in instructional systems, security and surveillance, CATV, process control, Q.A. monitoring, equipment and materials testing, tape recorder check-out, and other applications where the



addition of instant playback, slow motion and stop action increases the versatility of CCTV and video monitoring systems.

Weight of the recorder is 34lb com-

Model No. WG1

SOLID STATE ONE GUN BOOSTER FOR COLOR TV

EXTENDS COLOR GUN LIFE

RESTORES RED, BLUE OR GREEN BRILLIANCE

EASY TO INSTALL
(INSTRUCTIONS ON BACK)

WORKMAN Electronic PRODUCTS, INC.
SARASOTA, FLORIDA

BEFORE WEAK SERVICE LINE **AFTER** BOOSTED SERVICE LINE

MODEL NO. WG1

installation of **ONE GUN BOOSTER**
Boosts the one weak color needed for a **BALANCED** color picture.

MANUFACTURED BY **WORKMAN Electronic PRODUCTS, INC.**
SARASOTA, FLORIDA

... for more details circle 145 on Reader Service Card

NOW A ONE STOP SHOPPING CENTER FOR YOUR AUTO RADIO AND 8 TRACK STEREO PARTS. AT FACTORY DISCOUNTS

WE ARE AUTHORIZED PARTS DISTRIBUTORS FOR:

DELCO	PANASONIC
BENDIX	PHILIPS
MOTOROLA	BELLE WOOD
LEAR JET	WARD
TENNA	QUICKMOUNT
METRA	DEWEKO
AUTOMATIC	AC SPEEDO
ON GUARD	KING SEELEY
CRAIG	STEWART WARNER


STEREO LOCK MOUNTS

SEND YOUR ORDERS WITH PART NUMBERS TO

Laran Electronics, Inc.

3768 BOSTON ROAD
DEPT. 100 BRONX, N.Y. 10469

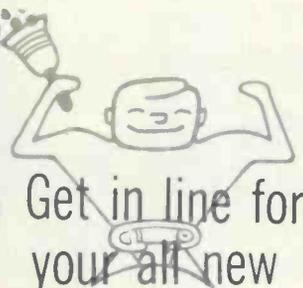OR SEND MODEL, MAKE AND DESCRIPTION OF PART WANTED.



Get in line for your all new solid state instant-on

MIGHTY MITE VI

- Now faster than ever. Instant-on action with all solid state FET circuitry—no waiting for warm-up.
- New push-button operation speeds up every test—saves you valuable time.
- New 13th socket checks still more tubes—now over 3000 including foreign.
- New hi-style case—vinyl-clad and brushed steel. A professional instrument designed for professionals.

At your distributor now, only **\$99.50**



SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

... for more details circle 126 on Reader Service Card


MAY 1970

... for more details circle 139 on Reader Service Card

**A NEW AND IMPORTANT
DEVELOPMENT FOR
TV SERVICING**

12 MODELS

SANS-A-FUSE®

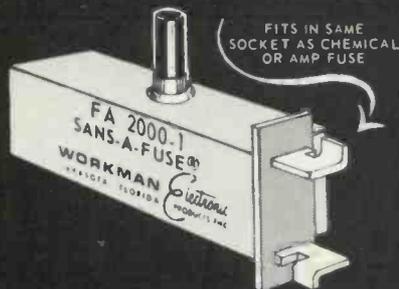

FITS IN SAME
SOCKET AS CHEMICAL
OR AMP FUSE

**COLOR CODED CIRCUIT
BREAKER REPLACEMENT
FOR CHEMICAL OR
AMP FUSE**

**SAVES TIME AND FUSES
WHEN LOCATING SHORTS
IN TELEVISION CIRCUITS**

DEVELOPED AND
MANUFACTURED BY

WORKMAN

BOX 3828 SARASOTA, FLA. 33578
TELEPHONE: Area Code 813




955-4242

... for more details circle 144 on Reader Service Card

TeleMatic

**SAVES
that
COLOR TUBE**

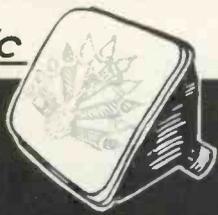

(WITH CATHODE HEATER SHORTS)

**GET THE NEW
2-IN-1**

**ISOLATION
BRIGHTENERS**

BOOST OR NO BOOST, AT THE
FLIP OF A SWITCH.

MODEL CR-300 FOR 70° TUBES
MODEL CR-350 FOR 90° TUBES

TeleMatic

Telematic Div. U. X. L. CORP.
BROOKLYN, N.Y. 11207, U.S.A.

... for more details circle 141 on Reader Service Card

ET/D NEW PRODUCTS

plete, and all components are housed in a portable case. Dimensions are 8 in. H x 13¼ in. W x 14½ in. D and power equipment is 115vac, 60Hz. Newell.

FM ATTENUATOR TRAP 730

*Attenuates FM
band by 20dB*

A MATV trap which attenuates the entire FM band by 20dB is introduced. Reportedly the first unit of its kind, the new FM attenuator trap is designed for use in broadband MATV systems. Strong FM signals are attenuated before they are fed from the antenna to the headend amplifier to eliminate cross modulation in the low VHF band (Channels two to six) and second harmonic beats in the high VHF band (Channels seven to thirteen).

Designated Model 8488, the unit is compact, rugged and easy to install and designed to pass all VHF channels without attenuation.

It provides a 20dB attenuation across the entire FM band and channel six is reportedly virtually unaffected.

The trap has less than 1.5dB attenuation at 88MHz, which is the edge of channel six. VSWR is good at 1.2 to 1.



While the trap does not pass UHF frequencies, it can be used in an '82' channel system. It is simply installed directly before the VHF input to the head end amplifier. List price \$12.50. JFD.


CB MOBILE ANTENNA 731

*VSWR of 1.5 to
1 or better*

Introduced is the Lancer 500 Series, designed for the CB'er looking for the classic features, styling and

performance previously available only with much higher priced mobile antennas.

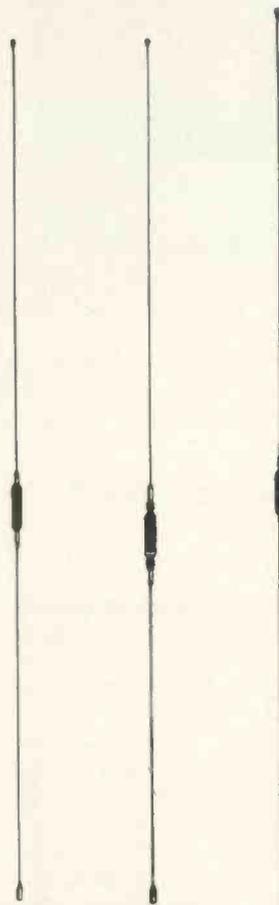Each of these antennas (Models 500A, 500B and 500C) is designed with a deluxe high "Q" coil resulting in reduced mechanical height while reportedly maintaining power capa-



MODEL
C-500 A

MODEL
C-500B

MODEL
C-500C

bility up to 500w. Each high impact, solid-state, polystyrene coil is permanently sealed against moisture. Models 500B and C feature a machined capacity coupler that works with the loading coil to extend the skin area of the radiator for increased antenna efficiency.

An exclusive guying device located just above the coil reportedly prevents antenna lay-back at top highway speeds. The antenna is factory pre-tuned to minimum VSWR of 1.5 to 1 or better with feed point impedance of 52Ω and the ¾ in. critical adjustment may be made after mounting.

For lowering, the Model 500C has a break-over (hinge) feature so that antenna may be lowered and secured from either trunk or bumper mounting position.

Each antenna is topped with a static ball which reduces corona effect and prevents loss of power.

Antennas come complete with top quality, corrosion-resistant materials, along with detailed, easy-to-follow installation instructions. Mosley.

WHEELERS AND DEALERS OF AMERICA YOUR TIME HAS COME



JERROLD DISTRIBUTORS HAVE SOMETHING BIG BREWING FOR YOU

BUY SOME JERROLD COLOR TV RECEPTION AIDS
—ANTENNAS, BOOSTERS, COUPLERS, CABLE KITS,
AND TRANSFORMERS—THINGS LIKE THAT ...




And there's something special that's likely to go with it.



Maybe some free Jerrold reception aids.



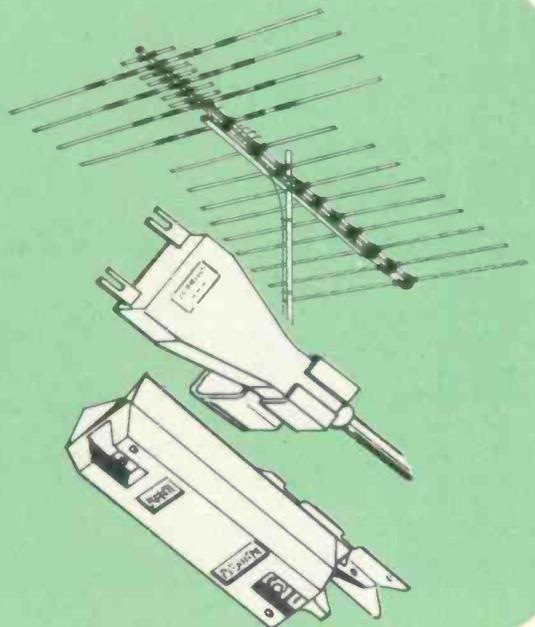And ask about those free Jerrold barbecue grilles
and the high-powered drills.



See your Jerrold Distributor soon.

He's ready to wheel and deal. And some of his deals
are too good to last forever.

If in doubt, write: Jerrold Electronics Corporation,
Distributor Sales Division, 401 Walnut Street,
Philadelphia, Pa. 19105



*Focusing on
one thing
—better
reception*

a GENERAL INSTRUMENT company TM

Silicone Products 400

A 44-page book lists the complete line of silicone industrial products. The book is divided into four sections—RTV silicone rubber, greases and compounds, fluids, and insulating varnishes. Each section contains a product and property listing, suggested application techniques and recommended procedures for handling specific materials. The silicone grease and compound section also has a table of Federal stock numbers that correspond with GE's product numbers. General Electric.

TV Coaxial Cable 401

An illustrated data sheet on coaxial cable for UHF/VHF home color television reception is published. This sheet describes the advanced design of Dura-Color RG-59/U type cable, part no. 5750. Dura-Color is 100 percent shielded, the shield consisting of a mylar film coated on both sides with aluminum foil and four stranded tinned copper drain wires for conductive continuity. This type of shield is electrically more stable and is highly resistant to moisture. The cable accepts standard F type 59/U connectors. The low loss capability and other outstanding characteristics are described in illustrated form. Also included are descriptions of two 75Ω Dura-Color kits, one for UHF and VHF reception and the other for UHF or VHF reception. Columbia.

Product Testing 402

"You've Seen It a Million Times," a leaflet explaining the significance of the Underwriters' Laboratories label, is being offered free of charge to interested parties. Large quantities are available to organizations and firms for distribution to their employees or customers. The brochure is designed to acquaint the consumer with some basic facts about Underwriters' Laboratories, Inc., and the testing activities behind the familiar UL seal. UL.

Tape and Accessories 403

An illustrated, multicolor, 40-page catalog—a complete guide to cassette, cartridge and reel-to-reel tape and audio accessories is published. The catalog is not only the biggest ever issued in its 15-year history, but it also represents the broadest line of comparable products available from any one manufacturer. In addition to cassette, cartridge and other tape-recorder

products in various sizes and price ranges, the catalog incorporates phono accessories, patch cords, adaptors and XL and XLP audio connectors. A front-page index and parallel presentation make it easy to find any of the hundreds of individual products. These range from brushes to splicers, and from all-U.S.-made cassettes and other tape formats to such amateur and professional electronic devices as demagnetizers. Robins.

Wire, Cable and Electronic Products 404

An illustrated 63-page catalog is available featuring wire, cable and electronic products. Complete and extensive delineation has been made regarding all types and construction of wire and cables used by the communications trades. Pictorially depicting wire and cable as well as electronic products, this IDS/MATV equipment catalog has a handy thumb-thru index as well as a complete alpha-numerical index. Vikoa.

Solid-State Components 405

Published is a new short form catalog containing: Junction FETs, MOS FETs, Dual FETs, Multi-Channel FET Switches, Current Limiters, Voltage Controlled Resistors, Digital Integrated Circuits, Linear Integrated Circuits, Integrated Drivers, and Driver/Switch Combinations. Siliconix.

Capacitors 406

A line of welded-construction, non-polarized capacitors are added to the expanding variety of aluminum electrolytic capacitors. The new units, type TNPW, have welded connections joining the risers, and external leads assure a low dissipation factor and freedom from intermittent or open circuits. They offer a complete range of capacitance values from 1.0 to 100μf and are available in voltages of 25, 35 or 50v. Price: under \$.10 to \$.40 each, depending on type and quantity. The new capacitors are fully described in I.E.C. Capacitor Bulletin EC81. International.

Test Instruments 407

A test equipment catalog (Bulletin 2080) which introduces five new instruments and gives complete operating specifications for equipment serving needs for industrial electronic and electrical testing including radio and TV servicing, communications, automotive, air conditioning, refrigeration and heating is available.

The Model 202 ACCU-LOG is the first VOM with maximum accuracy anywhere on a quasi-logarithmic scale. The logarithmic portion of the seven-

inch scale gives consistent percent of reading accuracy, while the linear portion permits easy zero-adjust.

Model 603 portable chart recorders are available in ac voltage, ac current, dc voltage and dc current measuring ranges. Other special features including a 110vac event channel, pressure sensitive recording paper and four built-in, switch selectable chart speeds, make this a useful instrument for monitoring power consumption or voltage fluctuations.

Two multi-testers (Models 256, 257) measuring voltage, current, capacitance and resistance, a current leakage tester (Model 229) and a solid state VOM (Model 313) round out the list of new items in Bulletin 2080. Simpson.

Electronic Electrical and Hobbyist Books 408

The 1970 catalog describing over 125 current and forthcoming books covers the following subject areas: Schematic/Servicing Manuals; Broadcasting; basic technology; CATV; electric motors; electronic engineering; reference; television, radio and electronics servicing; audio and Hi-Fi hobby and experiment; test instruments and transistors. Among the new and forthcoming titles featured is the revised edition of the "Tube/Transistor Substitution Guide." Tab Books.

Sub-Miniature Indicator Lights 409

The 56-page Selector Guide aids in the selection and procurement of more than a million and a half indicator lights, readouts and illuminated push button switches. Data is given in illustrated sections and each section is devoted to indicators by size (Sub-Miniatures, Miniatures, Large) or by product groupings. Separate sections of the guide are also devoted to illuminated push button switches and readouts. Four indexes, including one with military cross-references, assist the user in obtaining the desired information. Dialight.

Tools 410

A 24-page, fully illustrated catalog offering several new, unusual and extremely useful hard-to-find tools is available. The catalog contains precise and detailed descriptions and applications of each tool in this unique collection. The tools are rarely sold by industrial distributors or stores. Among the many new items offered are tungsten carbide saw blades, miniature rifferler files, torch lamp, miniature screws, nuts, bolts, washers, stainless steel pliers and hard chromed needle files. Also included are wood

working tools, electronic tools, jewelers' tools, diamond pencil and glass cutter, unusual solders, rust remover, hard-wire cutters, glass drills plus scores of other versatile hand tools and small power tools. Brookstone.

Miniature Lamps 411

A 21-page catalog containing valuable basic design information, technical discussions of the various parameters involved in lamping and a useable cross reference guide to lamp substitution is available. The catalog features a revised layout of technical data on each lamp, giving the all-important design voltage for each lamp first, allowing the engineer to tailor his selection to the voltage required. The technical discussion section of the catalog will serve as a valuable piece of reference information for the engineer working with lamps. Chicago Miniature Lampworks.

DEPTH FINDER ...

continued from page 63

lamp can be simply and quickly installed in the same clips after removing the defective lamp.

The Heath MI-29 maintenance provides for cleaning the slip-rings and in addition has a motor speed adjustment. The slip-rings can be occasionally cleaned using lighter fluid or other solvent. The service manual also states that if, after long periods of use the motor governor no longer maintains the correct speed, it may be necessary to clean the governor contacts. This simply involves removing the small piece of vinyl tape covering the access hole on the motor housing and applying a couple of drops of good contact cleaner or solvent.

The motor speed adjustment on the MI-29 is more critical and should not be tampered with unless you have checked all other possibilities for motor speed variation. The accuracy of the unit depends on the motor speed. If the motor speed is at fault, remove the vinyl tape covering the access hole located on the motor housing. Rotate the motor by hand and find the adjustment screw in the hole. Place the transducer in water with a known depth, then turn the unit on and note the reading. Turn the indicator off and turn the adjustment screw very slightly. Take another depth reading


and keep re-adjusting the unit until it reads the correct depth.

GENERAL HINTS

When installing or repairing these instruments, keep in mind that the transducer is a delicate part of the unit and must be handled with care. All of these units operate from battery-power and any deviation from normal operation should first lead to a check of the battery condition. Depth accuracy is determined by the speed of the motor, which is also de-

termined by the condition of the battery. Noise is one of the depth-finder's worse enemies and shows up as intermittent flashes on the indicator. Noise will be random, in other words, at no special depth. This could mean ignition shielding of some type is required. Basically, the depth-finder units are easy to install and service providing you understand their operation. It could be a comfortable and profitable introduction into marine electronics for your shop.

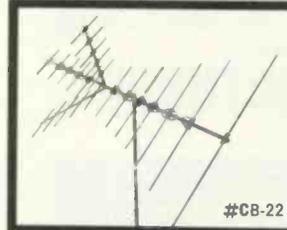
DEPENDABLE ANTENNAS AND ACCESSORIES FOR PROFITABLE INSTALLATIONS...



#CB-22

RMS COLOR-BOOSTER UHF/VHF SINGLE DOWN-LEAD ANTENNAS...

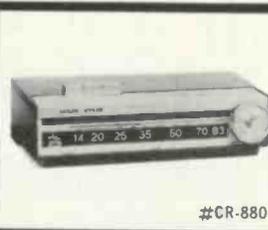
#CB-22: 22 elements, #CB-28: 28 elements, #CB-34: 34 elements. Adds mileage to UHF/VHF TV reception. Features Reynolds Aluminum Colorweld weather-proof Gold finish.


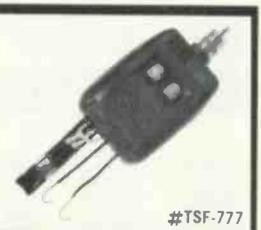
#CR-880

RMS MODEL CR-880 SOLID-STATE UHF CONVERTER...


Powerful amplifier and Local/Distant Switch provides 30 db gain! Brings in clearest Color and Black and White UHF reception even in areas where other Converters fail to!


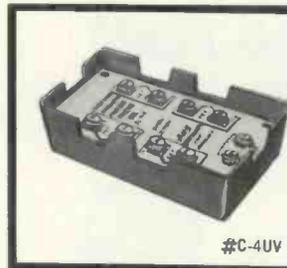
#TSF-777

RMS HAS THE MOST COMPLETE LINE OF UHF/VHF/FM SPLITTERS AND MATCHING TRANSFORMERS


For all multi-set home installations, master antennas, and closed circuit TV systems. All configurations for every requirement.


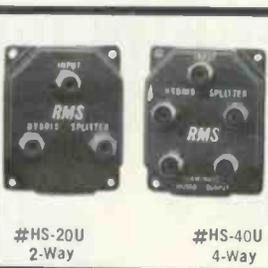
#C-4UV

RMS UHF/VHF/FM HIGH GAIN 4-SET COUPLER

Couple 4 TV and/or FM Sets to a single antenna with low signal loss—minimum interference between sets. Or couple 2 antennas, (VHF, UHF or FM), to a single down-lead.



#HS-20U
2-Way

#HS-40U
4-Way

UHF/VHF 2-WAY AND 4-WAY HYBRID SPLITTERS

For multi-set home and master antenna installations. Unbeatable specifications. Also top performing UHF/VHF Tap-Offs.



#CTB-70

DEPENDABLE ALL-PLASTIC COLOR-TUBE BRIGHTENERS

Reusable. Simple installation. Plugs in between color tube and color tube socket. #CTB-70 for 70° button base tubes. #CTB-90 for 90° button base picture tubes.

Couplers, Splitters, Matching Transformers, Hybrid Splitters, Tap-Offs, and Color-Tube Brighteners are individually blister sealed on attractive Peg-Hang Cards. Write for latest Catalog—


RMS ELECTRONICS, INC.

50 Antin Place, Bronx, N.Y. 10462 • Tel. (212) 892-6700




See Us at the NEW "Parts" Show Booths 4109-4111
... for more details circle 135 on Reader Service Card

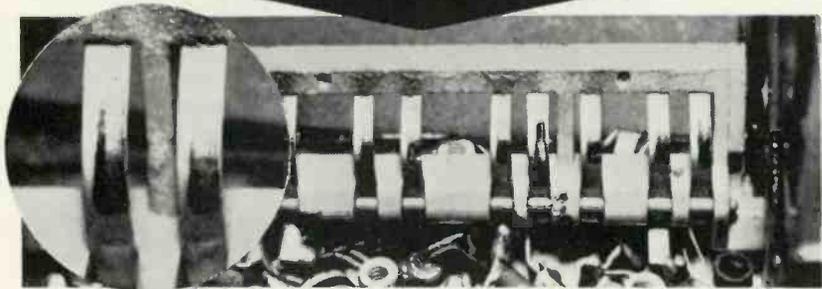HERE'S PROOF TUN-O-FOAM KEEPS TUNERS WORKING BETTER, LONGER!



**THIS TUNER
WAS USED AS IT
CAME FROM THE MANUFACTURER**

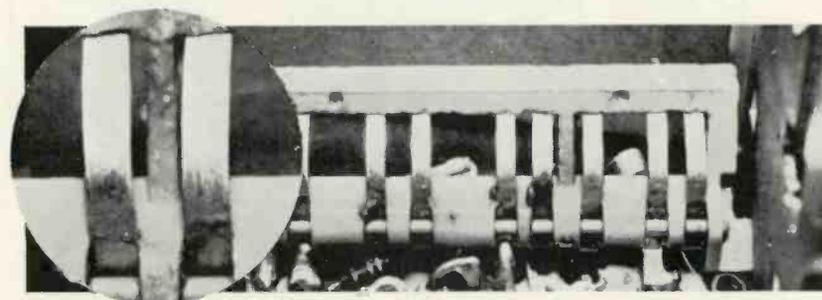After 36,000 revolutions, the silver has been worn away. The tuner does not function on any channel.



**THIS TUNER
WAS SPRAYED WITH TUN-O-FOAM**

After 36,000 revolutions there is no sign of wear. The tuner brings in all channels, sharp and clear.

THE PROFESSIONAL'S TV TUNER CLEANER

Foams into the tightest places. Won't cake up, dry out or detune. Keeps cleaning and lubricating contacts each time channel is changed. Guaranteed to be the best tuner lubricant cleaner you've ever used, or money refunded. Six-month no-callback guarantee.



1260 RALPH AVENUE,
BROOKLYN, N.Y. 11236

For export: **ROBURN AGENCIES INC., NEW YORK, N.Y. 10014**
In Canada: **MAGNASONIC CANADA LTD., MONTREAL 9, CANADA**

... for more details circle 110 on Reader Service Card

Get More Facts

NEW PRODUCTS

700	Color CRT One Gun Booster	24
701	Soldering Iron/Power Unit	24
702	Patch-Board	24
703	Color TV	72
704	Bias Supply	72
705	CCTV Camera and Monitor	72
706	TV Carton/Display	72
707	Insulating Spray	72
708	Stereo System	73
709	Videotape System	74
710	Cassette Stereo	74
711	Speakers	76
712	Cassette Tape Recorder	76
713	Desoldering Tool	77
714	Stereo Tuner	77
715	Cassette Circulator	77
716	Television/FM/AM Radio	77
717	Cassette Tape	78
718	Cartridge Tape Recorder	78
719	Battery Display	79
720	Head Demagnetizer	79
721	Power Supply	79
722	Staples	84
723	CB Antenna	84
724	GoZinta	84
725	Speakers	85
726	Video/RF Selector—Control Center	85
727	Digital Multimeter	86
728	VTVM	86
729	Video Disc Recorder	87
730	FM Attenuator Trap	88
731	CB Mobile Antenna	88

CATALOGS AND BULLETINS

400	Silicone Products	90
401	TV Coaxial Cable	90
402	Product Testing	90
403	Tape and Accessories	90
404	Wire, Cable and Electronic Products	90
405	Solid-State Components	90
406	Capacitors	90
407	Test Instruments	90
408	Electronic Electrical and Hobbyist Books	90
409	Sub-Miniature Indicator Lights	90
410	Tools	90
411	Miniature Lamps	91

TEST INSTRUMENTS

900	EICO Model 240 Solid-State FET-VOM	63
-----	------------------------------------	----

ADVERTISER'S INDEX

101	Admiral Corp.	80
102	Admiral Corp.	81
	American Telephone & Telegraph	65
103	Antenna Corp. of America	79
104	Arrow Fastener Co., Inc.	74
105	B & K Division Dynascan Corp.	2nd Cover
106	Belden Corp.	26-27
107	Book Club—Tab Books	66-69
108	Book Club	75
109	Channellock, Inc.	78
110	Chemtronics, Inc.	92
111	Cornell-Dubilier	3rd Cover
112	Enterprise Development Corp.	85
113	Finney Co., The	83
114	Ford Motor Co.	42
115	GC Electronics, Inc.	30
116	Gem City Tuner Service	32
117	General Electric Co.	23
118	General Electric Co.	37
119	Grantham School of Engineering	92
120	Heath Co.	41
121	International Crystal	22
122	International Importers	70
123	Jensen Tools & Alloys	81
124	Jerrold Corp.	89
125	Kay-Townes Antenna Co.	71
126	Laran-Electronics, Inc.	87
127	Leader Instrument Corp.	77
128	Lectrotech, Inc.	38
129	Mallory Distributor Products Co.	76
130	Master Appliance	76
131	Panasonic	43
	RCA Electronic Components	
	Entertainment Tubes	4th Cover
132	RCA Institutes	82
133	RCA Parts & Accessories	33-35
134	RCA Test Equipment	73
135	RMS Electronics, Inc.	91
136	Sencore, Inc.	84
137	Sencore, Inc.	85
138	Sencore, Inc.	86
139	Sencore, Inc.	87
140	Sprague Products Co.	31
	Sylvania Electric Products	28 & 29
141	Telematic Division UXL Corp.	88
142	Tuner Service	19
143	Winegard Co.	39
144	Workman Electronic Products, Inc.	88
145	Workman Electronic Products, Inc.	87
	Zenith Radio Corp.	25

Technicians, Earn Your Associate

DEGREE


mostly by correspondence

Accredited by the Accred. Comm. of National Home Study Council. G.I. Bill Approved. Free catalog.

Write: **Dept. T**
Grantham School of Engineering
1505 N. Western, Hollywood, Calif. 90027

... for more details circle 119 on Reader Service Card

ELECTRONIC TECHNICIAN/DEALER

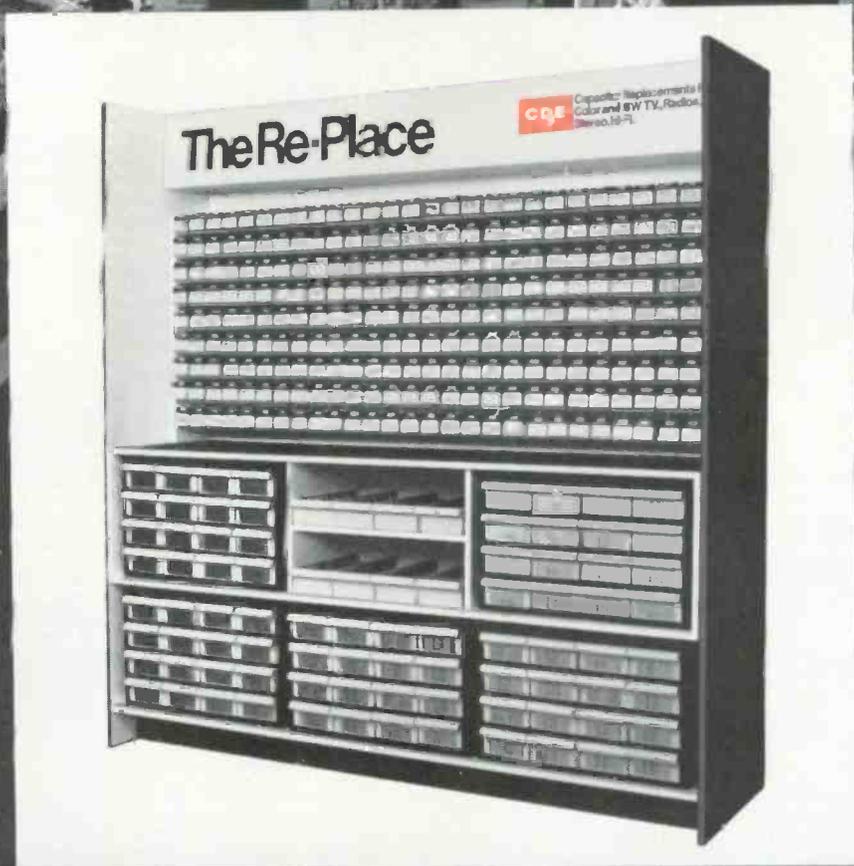

Put your parts in order.

All it takes is genius to arrive at simplicity. This new display stand is deceiving. It's more than a display stand. It's set up to operate like a store within your store for instant servicing.

Here, within this unit, is a complete stock of all the wide range twist prongs you'll need plus micas, miniature electrolytics, ceramics, wide range tubulars and dipped paper Mylar.* The selection was based on an extensive study of all capacitors used in the replacement market. Now, with the Re-Place, you're in the capacitor

replacement business. The Re-Place only takes 2' x 5' in space and you have all your parts in order.

Interested? Write for our new catalog on The Re-Place™ capacitor line. "The Replacers" — the most complete line of replacement capacitors in the smallest possible package.

CDE CORNELL-DUBILIER

We hope to see you at Booths 4202-04

*Du Pont Trademark

... for more details circle 111 on Reader Service Card

Put your money (only \$2.00)* where your profits are.



**New and bigger than ever!
The RC-27**

Solid-state design is the big thing in electronics today, but your profit margin is—and will be for years—directly related to your tube business.

That's why we keep on expanding and up-dating the RCA Receiving Tube Manual—the "bible"—to help you continue to save time (and make more money) in the servicing of tube-designed equipment.

Now 672 pages, the manual includes comprehensive technical data and curves for all active RCA receiving tubes . . . a useful circuits section . . . handy Applications Guide . . . tabulated data on color and black-and-white picture tubes, voltage-reference and VR tubes . . . plus a Replacement Guide.

Get a copy today from your RCA Distributor. It's almost as indispensable as your tube-tester and V-O-M!

RCA Electronic Components | Harrison, N. J. 07029

*Optional Price

RCA