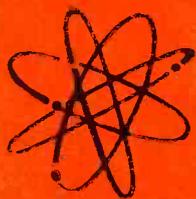


ELECTRONIC SERVICING

AUGUST

1957

50c



Horizontal Retrace
Blanking



Servicing Intermittents

Production Line
Fugitives

Outboard Motor
Electronics

Electronic Service
Firms Analysis

1957 Philco TV

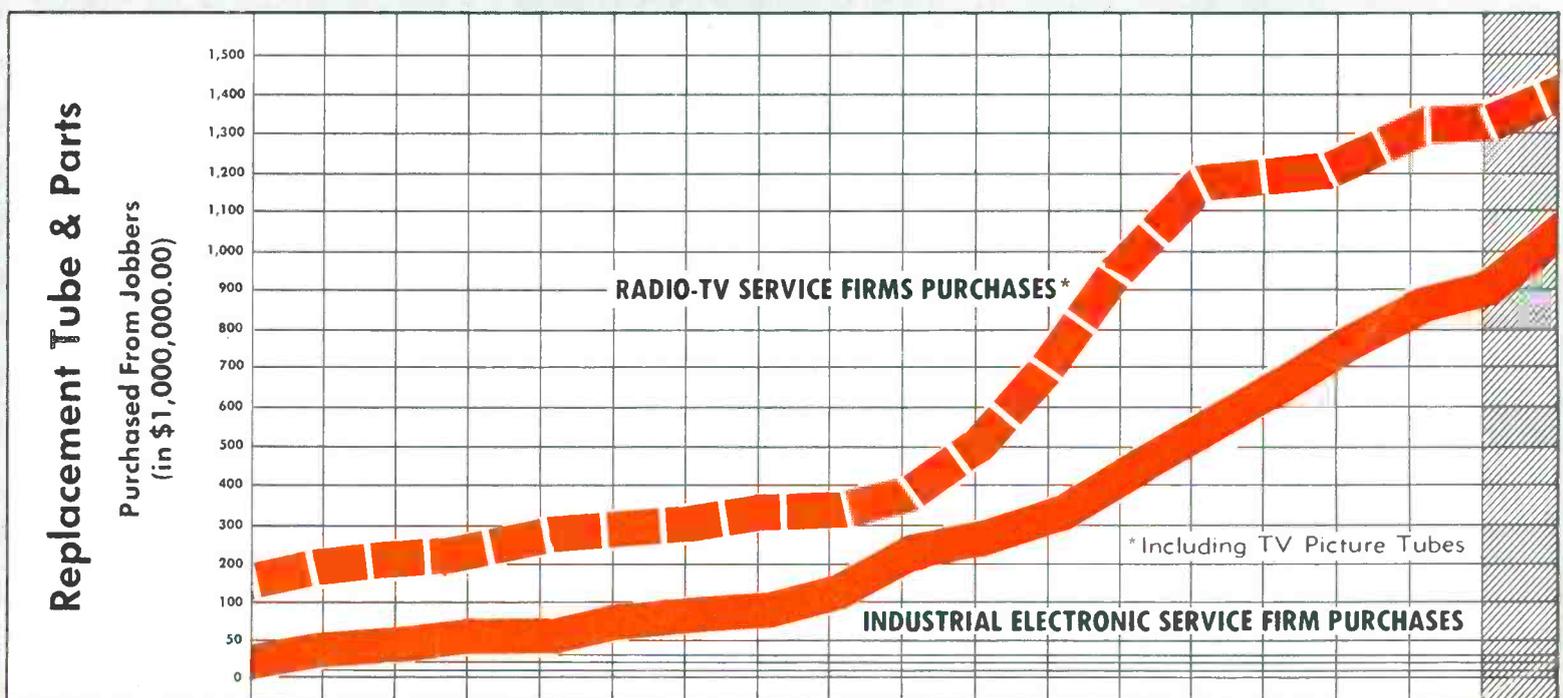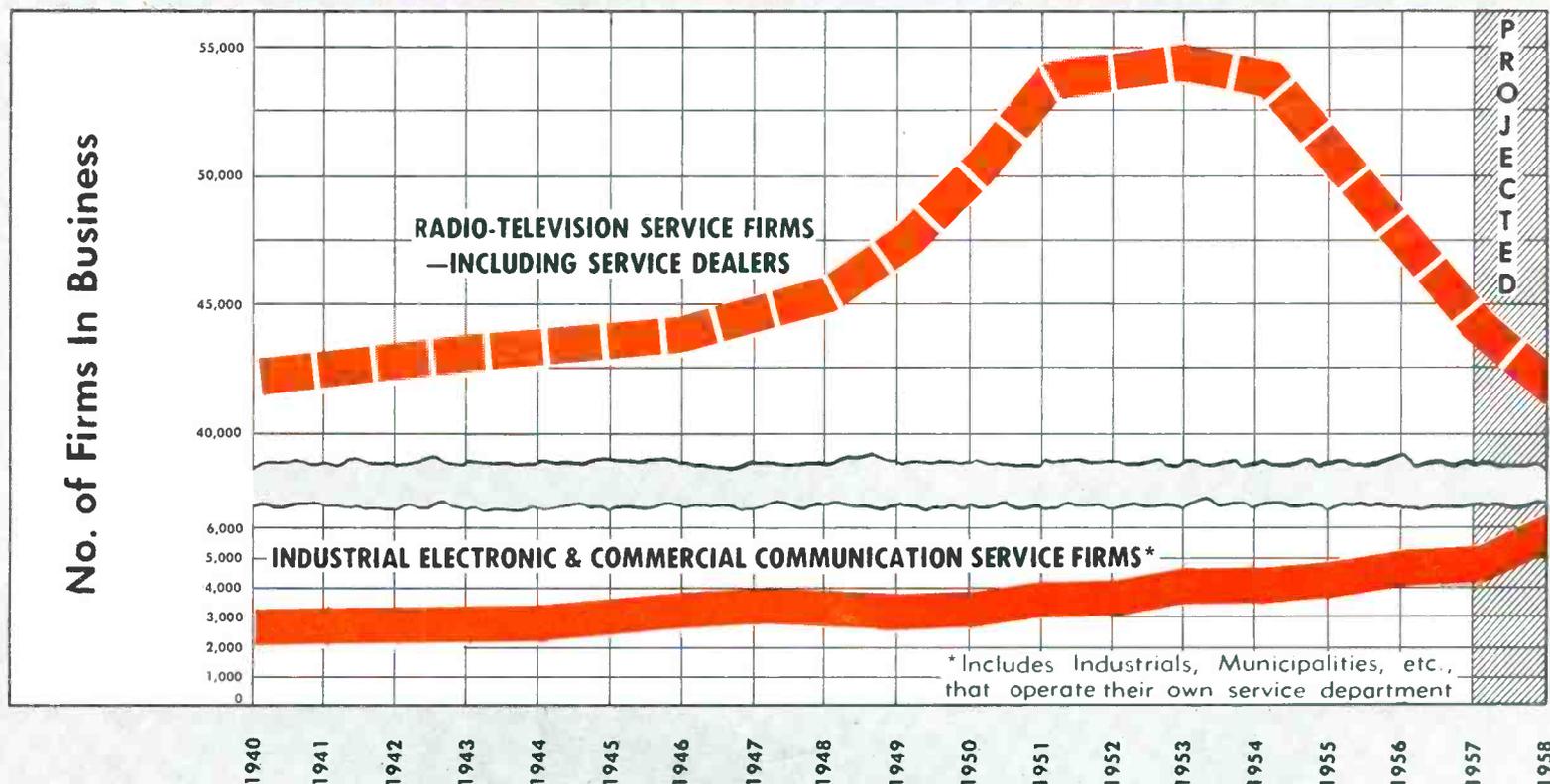


all figures from U.S. Gov't Bureau of Statistics (Feb. 1957) and the RETMA "1957 Fact Book"

give them




AR-22

what they want...

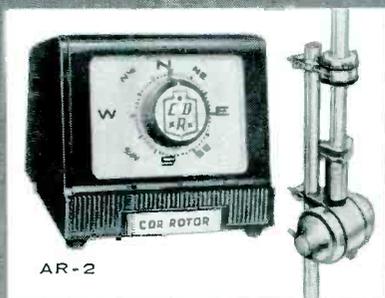


AR-2

give them—
CDR

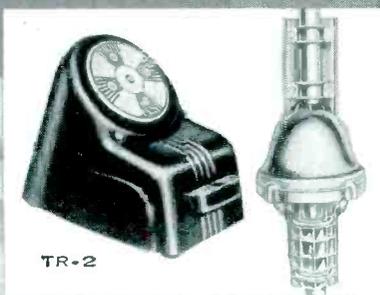

TR-2

ROTORS

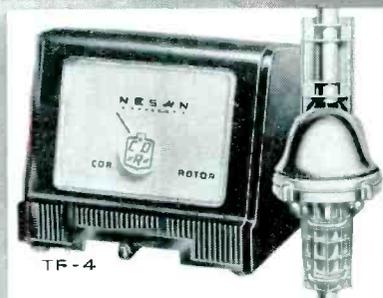

TF-4

It's easy for you to give your customers EXACTLY what they want...and at the same time EXACTLY what is BEST for them ...because CDR ROTORS are the single answer! The complete line with a model for every need...proven performance and dependability through years of experience. This combination has made CDR ROTORS the favorites everywhere...that is why your customers should have CDR ROTORS!



TR-15 and 16

Especially important for color TV reception. Critical tuning requirements call for CDR Rotors.



CORNELL-DUBILIER
SOUTH PLAIN FIELD, N. J.



THE RADIART CORP.
CLEVELAND 13, OHIO

EDITORIAL STAFF

Sanford R. Cowan	Publisher
Samuel L. Marshall	Editor
Oscar Fisch	Associate Editor
Robert T. Dargan	Technical Editor
David Fish	Editorial Assistant
Irving Tepper	Editorial Assistant
Charles W. Gardner, Jr.	Production Manager
San D'Arcy	Contributing Editor
Paul Goldberg	Contributing Editor
Elbert Robberson	Marine Communications Editor
Lawrence Fielding	Hi-Fi & PA Editor

BUSINESS STAFF

Advertising Sales

New York and East	Richard A. Cowan Jack N. Schneider 300 West 43rd Street New York 36, N. Y. JUdson 2-4460
--------------------------	--

Chicago and Midwest	Jim Summers Suite 55 C Pure Oil Building 35 E. Wacker Drive Chicago 1, Ill. ANdover 3-1154
----------------------------	---

West Coast	Ted E. Schell 2700 West 3rd Street Los Angeles 57, Calif. DUNkirk 2-4889
-------------------	---

	Charles W. Hoefer 1664 Emerson Street Palo Alto, Calif. DAvenport 4-2661
--	---

David Saltman	Business Mgr.
---------------	---------------

CIRCULATION

Harold Weisner	Circulation Manager
Carol J. Binderman	Ass't Circulation Mgr.
Rose Mercurio	Circulation Dept.

ELECTRONIC SERVICING (formerly Radio-TV Service Dealer) is published monthly by Cowan Publishing Corp., 300 West 43rd Street, New York 36, New York, JUdson 2-4460. Subscription Price: \$3.00 one year, \$5.00 two years in the United States, U. S. Possessions, Canada and Mexico. Elsewhere \$1.00 per year additional. Single copies 50c. Second Class Mail privileges authorized at New York, N. Y.

POSTMASTER: SEND FORM 3579 TO ELECTRONIC SERVICING, 300 WEST 43rd STREET, NEW YORK 36, N. Y.

ELECTRONIC SERVICING

VOL. 18, NO. 8

Member

AUGUST, 1957



FEATURE ARTICLES

- Horizontal Retrace Blanking**, by Irving Tepper 4
Symptoms and cures for defective horizontal retrace blanking.
- Production Line Fugitives**, by Allan Kinckiner 6
Tips for finding "built-in" television troubles.
- Servicing Intermittents**, by George Kravitz 8
Suggestions for finding and repairing intermittent troubles.
- Outboard Motorboat Electronics**, by Elbert Robberson 10
Electrical systems used in outboard motors.
- Electronic Service Firms Analysis**, by San D'Arcy 12
Survey of types of business, dollar volume, test equipment used, etc.
- 1957 Philco TV Receivers, Part 2**, by H. S. King 14
A continuation of the analysis of features in the new Philco line.

CIRCUIT AND SERVICE FORUM

- Complete Manufacturer's Schematics—TV** 15-22
GE "T" Line
Hoffman 329, 330
- Workbench** 28
- Video Speed Servicing Systems** 29-32
C.B.S. 1601/1602
Firestone 13 G 168

DEPARTMENTS

- S. R. Cowan Ad Libs 2 Advertisers' Index Cover III
- Trade Flashes 24

THIS MONTH'S FRONT COVER

Facts and Figures Chart of Industrial and Commercial Radio and TV firms compiled from U. S. Government Bureau of Statistics (Feb. 1957) and the RETMA "1957 Fact Book."

ACKNOWLEDGMENT

The photograph on last month's front cover illustrating a stage in transistor fabrication was supplied by the General Transistor Company of Jamaica, New York.

Entire Contents, Copyright 1957, Cowan Publishing Corp.

COWAN PUBLISHING CORP., 300 West 43rd Street, New York 36, N.Y.

ELECTRONIC SERVICING • AUGUST, 1957

AMPHENOL

TWIN LEAD HANKS

*...make your
Job Easier!*


AMPHENOL job-size hanks make your selling job, your installing job easier! Pre-assembled with lugs on one end, attractively packaged in convenient 25, 50, 75 and 100 foot lengths, AMPHENOL hanks are easy to use for new and replacement installations, easy to sell to the "do it yourself" market. No bulky spools to handle, just job size hanks for every twin lead application!

Lighten up your work load, boost your sales with AMPHENOL Twin Lead hanks!

50 FEET
GENUINE

AMPHENOL

no. 214-056
FLAT
TWIN LEAD

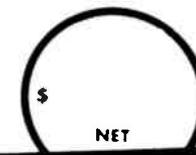

PREASSEMBLED!
WITH LUGS ON ONE END!

AMPHENOL ELECTRONICS CORPORATION
CHICAGO 50, ILLINOIS

SEE OTHER SIDE

Part No.	Description	Available in Hanks of			
		25 ft.	50 ft.	75 ft.	100 ft.
214-318	Indoor—60 mil. 7 28 pure copper cond.	✓	✓	✓	✓
214-056	Standard—60 mil. 7 28 pure copper cond.	✓	✓	✓	✓
214-559	Steelcore—72 mil. 7 28 copperweld cond.		✓	✓	✓
214-298	Rotator—4 conductor—7 28 pure copper cond.		✓	✓	✓
214-100	Century—100 mil. 7 28 pure copper cond.		✓	✓	✓
		Now Available in Coils			
214-271	Air-Core—U.S. Pat. 2543696 7 28 pure copper cond.		✓	✓	✓


Remember
for finest quality, virgin
polyethylene is used in all
AMPHENOL Twin Leads.

PRE-ASSEMBLED
with lugs on one end!



AMPHENOL ELECTRONICS CORPORATION
chicago 50, illinois

CLIP THESE NOW,
FOR REFERENCE

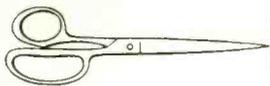

NEW 1958 HOTPOINT TV TUBE LOCATION CHARTS

Hotpoint's new 1958 TV line is now in the stores—featuring 110° Picture Tubes in every model.

Note that two 21" models (21S405 and 21S505) use the M3 chassis.

All tubes and fuses are conveniently located at the back of the chassis and can be easily replaced by removing the cabinet back. Single printed circuit board further simplifies servicing. Test points accessible from rear of chassis for quick checks.


Complete service information on this new line is now available from your Hotpoint Distributor, and you are invited to contact him and order Hotpoint TV Service Data today.

Published as a service
to servicemen by


Hotpoint

(A Division of General Electric Company)

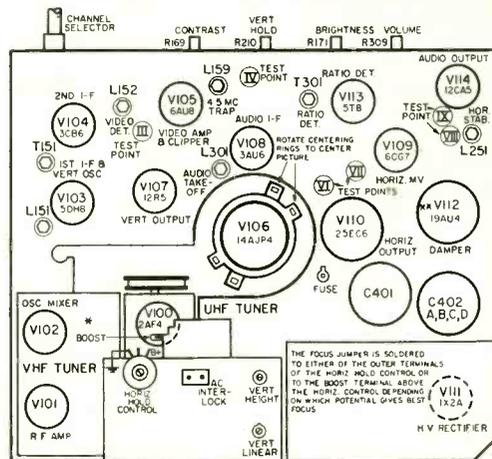
5600 West Taylor Street
Chicago 44, Illinois



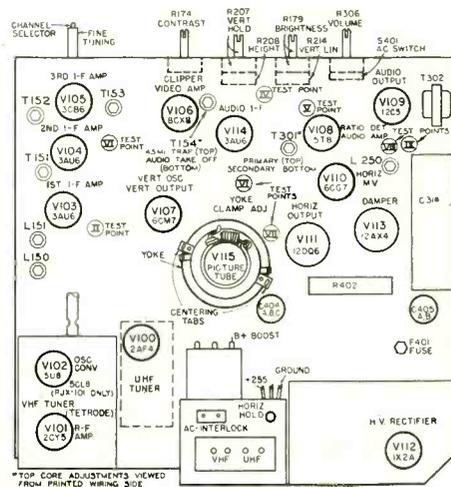CHASSIS Q2—Covers models 14S206 and 14S207 in VHF and UHF versions.



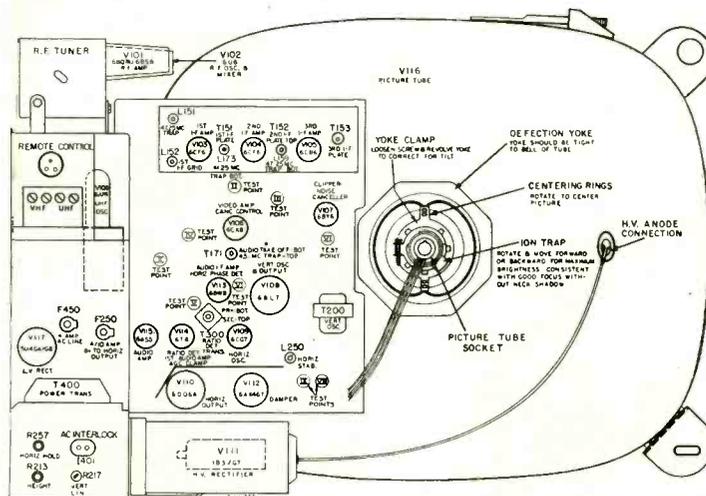CHASSIS M3—Covers models 17S305, 17S306, 21S405, and 21S505 in VHF and UHF versions.



CHASSIS U2—Covers models 21S406, 21S455, 21S456, 21S507, 21S508, 21S555, 21S556, 24S805, 24S806, 21S605 and 21S606 in VHF and UHF versions.



Ad Libs

by S. R. COWAN

Facts and Figures Worth Analyzing

ALTHOUGH it has been said, "There is no such thing as an average man" I believe there are "average businesses." If, in a town, there are two Five & Dime stores grossing a half-million dollars each annually and two other such stores each grossing one hundred thousand dollars per annum, then the "average" Five & Dime store in that town grosses \$300 thousand and obviously two of the stores are well above average while two are obviously well below average. Using this basic and fundamental information as a gauge, the operators of the two smaller establishments could logically deem it expedient to try to get a proportionately larger share of business so that their respective firms could be more close-to-average rather than remain in a below-average status. Usually an average (or normal) store earns average profits while most sub-normal or below-average stores earn less than average or normal profits. That business truism is the underlying reason why statisticians compile statistics which serve as guides for interested parties.

We've done that! We've compiled statistics about radio-TV service firms and about firms that specialize in industrial electronic servicing. Then by striking "averages" we show our readers how they may gauge their relative position in the competitive scheme of things. Our readers can then decide for themselves whether or not they wish to concentrate on some phase of business

which might elevate their earning-power. Or, they might decide that because their test equipment is over-age, as compared to the "average," that it would be worth their while to trade it in now for newer, more efficient instruments that will enable them to work faster and earn more. You must judge for yourself just how you want to utilize the information given in the article "Electronic Firms Analysis" which appears on page 12 of this issue. And, to the nearly 600 ELECTRONIC SERVICING subscribers who helped us compile this data, may we express our thanks and appreciation.

Licensing

Occasionally a subscriber writes me a letter expressing vehement objection to any type of legislation in regard to municipal, or other, licensing of radio/TV technicians. (We have editorialized often that we believe that properly planned and policed licensing will, in the long run, assuredly benefit everyone in the radio/TV service industry as well as the set-owning public.)

Of late, practically every objector to licensing, who has written me, is a part-time independent serviceman. Undoubtedly there are still some professional full-timers who have not yet been "sold" on the licensing idea. Just now we cannot call to mind a single Serviceman's Association which has gone on record that its membership opposes licensing, provided that Association is permitted to collaborate in the promulgation of the legislation itself.

In mail (June 20th) we find a letter from Joe Driscoll, Secretary of TESA, St. Paul, Minnesota and with it a clipping taken from the St. Paul Sunday Pioneer Press of June 16th. This excerpt under the byline of feature writer Carl G. Langland, is quite illuminating and effectively supports proponents of licensing. Here's the Langland article, quoted verbatim:

"The value of a city ordinance to license individuals and firms in the television service industry—or any other service which sends men into private homes—was illustrated forcefully in a recent City Council session.

"In that instance, a man made appli-

[Continued on page 23]



DOOR BAR



TRUCK DECAL



TV SCREEN POLISHING CLOTH



ILLUMINATED CLOCK



TUBE AND TOOL CARRYING CASES

OUTDOOR THERMOMETER



INDEPENDENT SERVICE DEALERS!

These useful Shop and Sales Aids were created specially for You!

ASK YOUR



TUBE DISTRIBUTOR FOR THEM

DISPLAYS



OUTDOOR HANGING METAL SIGNS

Pictured are but a few of a most complete line of tested and proven shop, sales and business aids Raytheon has produced for you. All of them are specially designed to help make your work easier and more profitable. Many are free and the rest available to you through your Raytheon Tube Distributor at far below normal cost.



TRANSPARENT WINDOW STREAMERS



ALUMINUM Snap-Out-Form POCKET CASE



Ask your Distributor for the new Raytheon Business Builders folder or write to Department G Raytheon Manufacturing Company, Receiving and Cathode Ray Tube Operations, Newton 58, Mass.



RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations

Newton, Mass. • Chicago, Ill. • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes all these { Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.



Excellence in Electronics



Fig. 1—The faint white line at the left may be due to a defect in the damping circuit. Courtesy G.E.

Horizontal Retrace Blanking

by Irving Tepper

Too long a horizontal retrace time causes a type of trouble with specific symptoms. These symptoms, their causes, and remedial measures are discussed here.



Fig. 2—Horizontal fold-over usually caused by too long a horizontal retrace time. Courtesy G.E.

FEW servicemen are aware of the problem of faulty horizontal retrace and its effect upon the picture, although most are familiar with the appearance and elimination of vertical retrace lines. Defective horizontal retrace may be recognized by the following symptoms:

- 1—The presence of a hazy vertical line superimposed on the picture, left of center as shown in Fig. 1, or foldover from left to right as shown in Fig. 2.
- 2—The hazy line moves in a direction opposite to that of the picture as the horizontal hold control is rotated.
- 3—People or objects, when leaving the scene on the left side, reappear momentarily and then disappear towards the center of the screen.
- 4—The haze may be moved off the screen by rotation of the horizontal hold control, but the point at

which the haze is off the screen leaves the horizontal in a very unstable state, where a camera shift or any other momentary interruption of sync will throw the set out of hold.

Cause of the Trouble

This defect is caused by too long a horizontal retrace period. A comparison between normal and abnormal waveforms is shown in Fig. 3. The retrace of the normal sawtooth occurs within the blanking pulse period of 10 microseconds, having an approximate duration of 7 microseconds. Since the entire retrace period is blanked out, no defect will be observed in the set's performance. The sawtooth illustrated at the bottom of Fig. 3 has a retrace that starts during the blanking pulse but is still active after the blanking pulse has ended. This means that portion AB of the retrace will be seen on the screen and this retrace portion corresponds to the video

information shown above from A' to B'. It can also be seen that the picture information between B' and C' will be presented on the screen in the same area as the information between A' and B'. This overlapping of course, is what the term foldover refers to.

Thus, the video content of area AB, instead of being swept normally from left to right, starts at left of center and sweeps from right to left as shown by the arrows in Fig. 4. Since the retrace is very rapid, the video has low intensity in area AB and has a hazy appearance.

Cause of Foldover

The cause of excessive retrace time may usually be isolated to the area of the flyback transformer. The problem first appeared when large screen conversions were in vogue. In order to increase width many servicemen wired a paper tubular condenser in parallel with the width coil. Although this invari-

ably increased the width, a simultaneous occurrence was the lengthening of the retrace time.

This may be explained as follows. When retrace occurs, a shock excited oscillation is produced in the flyback secondary circuit. It is the purpose of the damper tube to suppress this oscillation and use its energy for the initial portion of the sweep. The first half cycle of oscillation produces retrace. Since this must take place in about 7 microseconds, the full cycle of oscillation would require about 14 microseconds. This corresponds to a frequency of about 70 kc. As the resonant frequency of the output circuit is lowered, the time taken by the first half cycle of oscillation (retrace) is increased. When its duration exceeds 10 microseconds we have horizontal foldover. The additional condenser across the width coil has the effect of lowering the resonant frequency, thus not only increasing the transfer of energy to the

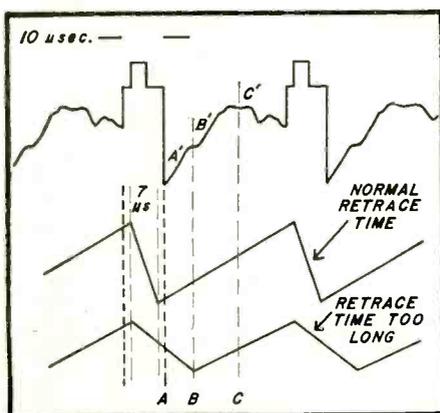


Fig. 3—Graphical illustration of the effect of too slow a horizontal retrace on picture presentation.

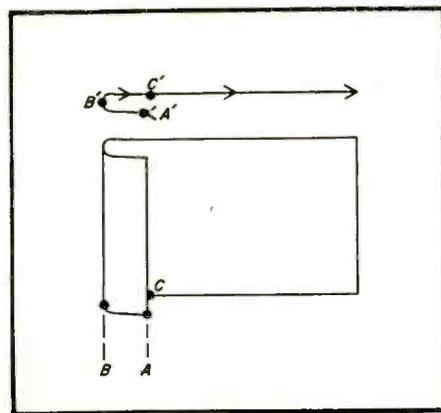


Fig. 4—Three dimensional illustration of the manner in which foldover occurs because of long retrace.

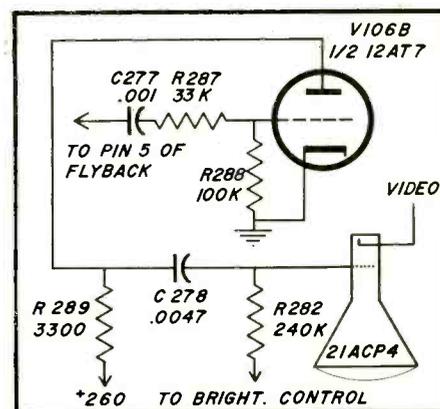


Fig. 5—The horizontal blanking circuit used in the General Electric model 21 C 350 chassis.

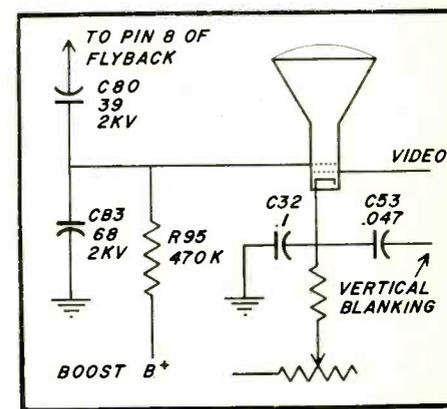


Fig. 6—A variation of horizontal blanking circuitry used by Majestic in their Model 123.

yoke but also increasing the retrace time.

Blanking the Retrace

The basic principle involved in blanking the horizontal retrace is to make the blanking period as long as the actual retrace time. The blanking pulse is generated by taking a portion of the output of the flyback transformer and properly attenuating and shaping it. It is then applied to an appropriate element of the CRT to blank the screen during retrace. The element to which the blanking pulse is applied is determined by the polarity of the blanking pulse.

Typical Circuits

Three typical blanking circuits are shown in *Figs. 5, 6, and 7*. The General Electric circuit shown in *Fig. 5* makes use of one half of a 12AT7, V106B, as a blanking tube. When horizontal retrace occurs a positive pulse, taken from the flyback, is applied to the grid of V106B. In the process of amplification the pulse is inverted 180 degrees by V106B, thus producing a negative pulse suitable for application to the control grid of the picture tube. The negative pulse will cut the picture tube off during retrace and the period of cut off is determined by the duration of this negative pulse and not by the blanking pulse contained in the composite video signal.

The circuit illustrated in *Fig. 6* makes use of a capacitive voltage divider (C80 and C83) to reduce the amplitude of the pulse taken from the flyback. During
[Continued on page 34]


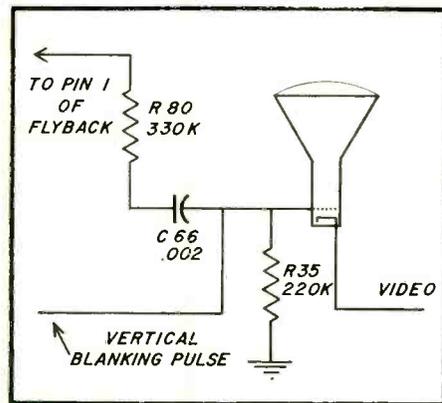


Fig. 7—The Olympic model 21CV16 uses the horizontal blanking circuit illustrated above.

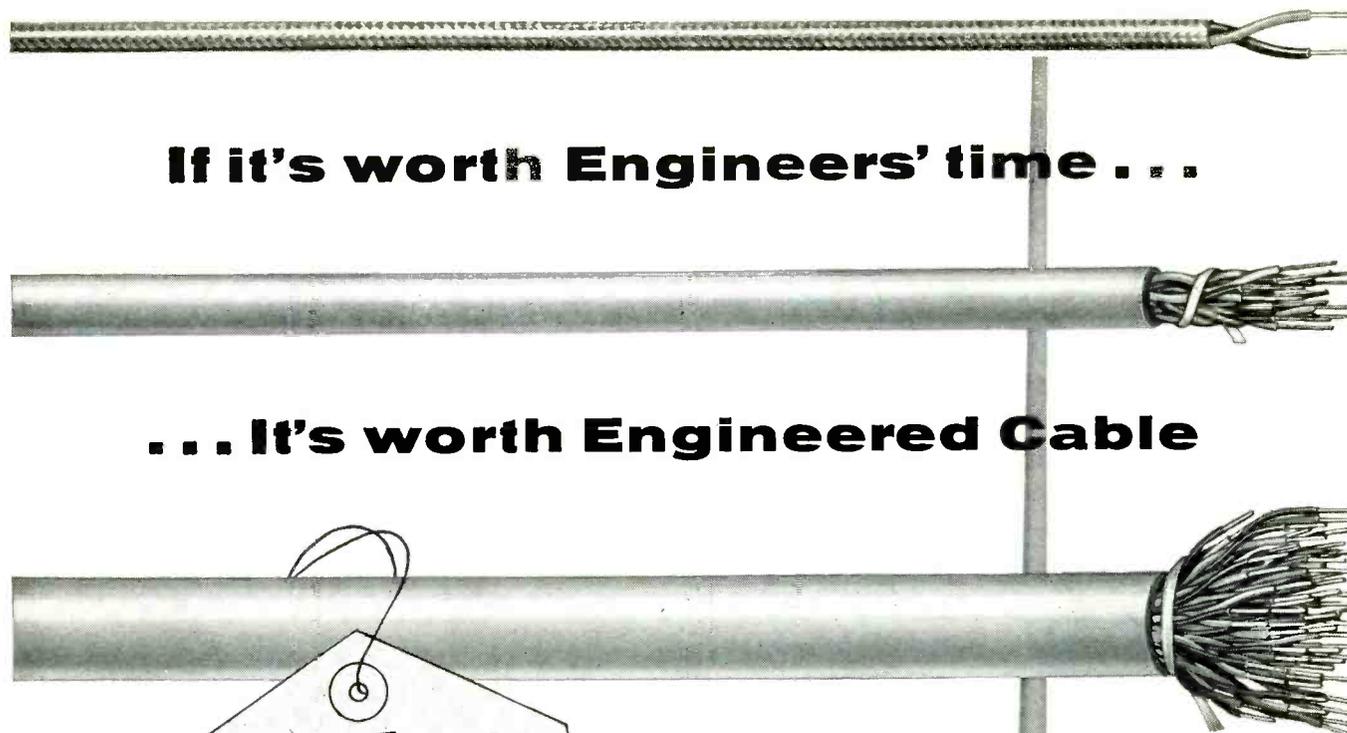

If it's worth Engineers' time . . .

. . . It's worth Engineered Cable

Belden
INTERCOMMUNICATING
AND
SOUND SYSTEM CABLES

Indoor-outdoor, phones
or speakers—there is a
Belden engineered cable
to meet your needs for
a permanent, trouble-
free installation.

"Items from the
Complete Belden Line"

The TV station, the systems for
music, paging, and intercom-
munication in the new
Prudential Insurance Company
of America's Building in Chicago
have been—wired by Belden.



Belden

WIREMAKER FOR INDUSTRY
SINCE 1902
CHICAGO

8-8

Magnet Wire • Lead and Fixture Wire • Power Supply Cords, Cord Sets and Portable Cord • Aircraft Wires
Welding Cable • Electrical Household Cords • Electronic Wires • Automotive Wire and Cable

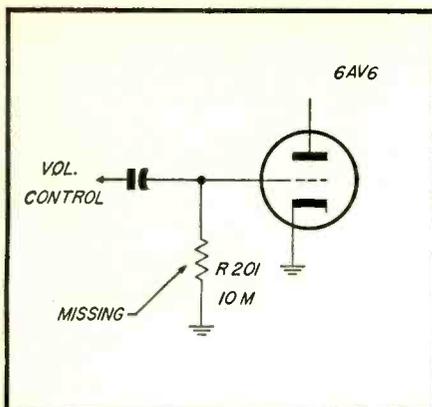


Fig. 1—Trouble caused by missing part.

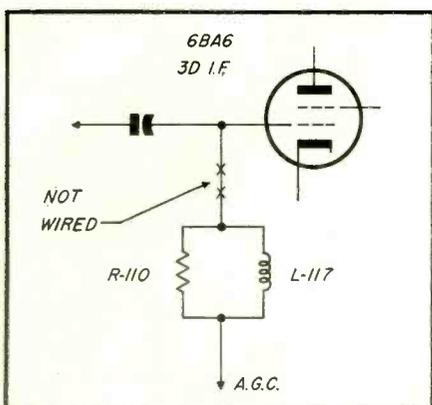


Fig. 2—The agc line was left unwired.

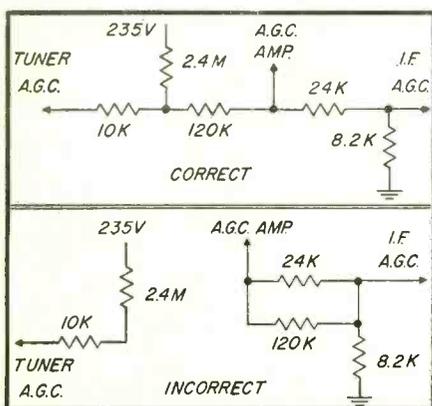


Fig. 3—Wiring error was culprit here.

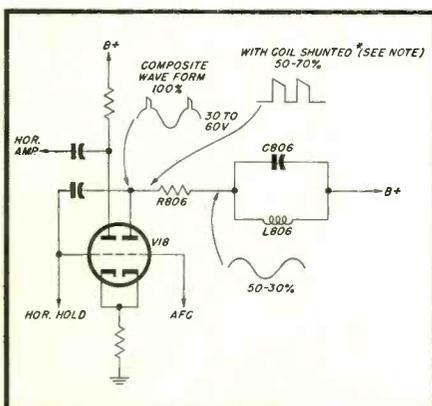


Fig. 4—Incorrect value of plate resistor caused poor horizontal sync.

ACROSS the service bench of every TV service dealer, must eventually pass the receiver which was faulty when it left the factory. The fault may be due to an incorrect component, a missing component, faulty wiring, or poor soldering. The fact that the fault had not been detected during factory inspection indicates that the set must have been near standard to have thus evaded detection, and it is because of this near standard condition that these jobs are more difficult to service.

Oftimes the owner recognizes a defective condition in his new receiver by comparing it with a neighbor's. This is a valuable clue, if brought to the attention of the serviceman, that something is wrong, and rather than brush it aside, the serviceman would do well to investigate it further.

The following notes are on sets in the category of "Production Line Fugitives" with four specific instances cited and several other generalized conditions found.

RCA TA129, KSC 41A Chassis With Low Volume

This set, according to the owner, had had intermittent sound, and while another service shop had apparently corrected that condition, it had been returned with a "low volume" condition. When tube substitution proved ineffective it was decided that an alignment was in order. After carefully aligning the sound *if's*, which considerably improved the condition, the set was tuned to a station. The set played at good volume but the cutting out returned. On closer observation it was noted that the audio would cut out following an unusually loud passage of voice or mu-

Production Line Fugitives

by Allan Kinckiner

Missing components, wrong values, unsoldered connections, and other "built in" troubles cause headaches to set owners and T.V. servicemen alike.

sic. A scope reading showed a signal at the 6AV6 grid (see Fig. 1) but none at the plate, and with a new tube the condition was the same. Further examination revealed the absence of R201, and from the looks of things, the resistor had never been wired into the set. The trouble was traceable to grid-blocking of the 6AV6 by the contact bias built up on the grid condenser. Normally, if R201 were present, it would have kept down this bias to the correct voltage.

RCA KCS40 Delayed Video

The picture came on anywhere from 2 to 10 minutes after the raster, the latter appearing in the normal time. Measurements with a probe and scope proved that the signal came through the first and second *if* stages in normal time, but was delayed in the third *if* stage. Voltages and parts were checked, but revealed no apparent defect. The set was then turned off and allowed to cool. Putting a fixed bias on the *agc* line and turning the set on again resulted in normal operation. Close scrutiny of the wiring of the

third *if* stage revealed that the resistor and choke (Fig. 2), supposed to be connected from the *agc* line to the grid of the third *if* tube, had never been wired to the tube socket, missing its mark by a full one quarter of an inch. Dressing the wire to the socket and then soldering the connection completed the repair on this set.

Analyzing the action here the following explanation is given: With the signal failing to get through, no *agc* was developed. Thus, the first and second *if* tubes were at full gain, which was enough to block the third *if* grid. After a slight delay the charge on this grid leaked off internally, passing enough signal to develop *agc*, which decreased the gain through the first and second stages allowing for further reduction of charge and a return to normal operation. In this case the customer was not even aware of a fault, thinking the delay was normal as the set had always worked that way.

Caphart CX33A, M or K

This set had many faults. First, the set had considerable snow, which was



Fig. 5A—Oscilloscope photo of wave form at the plate of the horizontal mutivibrator. (Fig. 4)

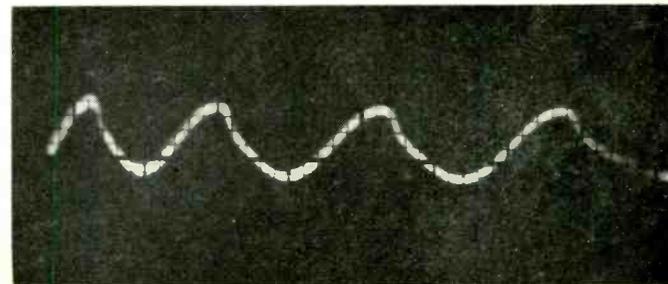


Fig. 5B—Oscilloscope photo of wave form at the B end of R806. (See Figure 4)

look what **\$24⁵⁰** buys
in test equipment!



**HEATHKITS
GIVE YOU
TWICE AS MUCH
equipment for
every dollar
invested**


The famous model V-7A Vacuum-Tube-Voltmeter is a perfect example of the high-quality instruments available from Heath at 1/2 the price you would expect to pay! Complete, only **\$24⁵⁰**



Get the most out of your test equipment budget by utilizing HEATHKIT instruments in your laboratory or on your production line. Get high quality equipment, without paying the usual premium price, by dealing directly with the manufacturer, and by letting engineers or technicians assemble Heathkits between rush periods. Comprehensive instructions insure minimum construction time. You'll get more equipment for the same investment, and be able to fill your needs by choosing from the more than 100 different electronic kits by Heath. These are the most popular "do-it-yourself" kits in the world, so why not investigate their possibilities in your particular area of activity! Write for the free Heathkit catalog now!



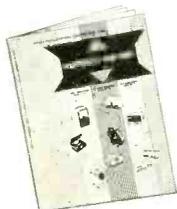Contains detailed descriptions of Heathkit models available, including VTVM's, scopes, generators, testers, bridges, power supplies, etc.



Also describes Heathkit ham gear and hi-fi equipment in kit form. 100 interesting and profitable "do-it-yourself" projects!

FREE catalog

Mail coupon below for
your copy—Now!

HEATH COMPANY
A SUBSIDIARY OF DAYSTROM, INC.,
BENTON HARBOR 29, MICHIGAN

Name _____

Address _____

City & Zone _____

State _____

Servicing Intermittents

by George Kravitz

Westinghouse Elec. Corp.
Metuchen, N. J.

Helpful hints for finding and repairing annoying, intermittent troubles in TV sets are given in this article.

ONE of the most difficult types of repair involves the intermittent—the TV set or radio that works, then quits, then works again. When the receiver becomes defective, tapping the cabinet, or turning the set off and on, may temporarily result in normal operation. Or, the receiver may return to normal by itself. The receiver may fade slowly or cut off sharply. Its return to normal may be gradual or sudden, all of which leads to the question: How do we fix this type of dog? Unfortunately, there is no simple answer. This article provides suggestions, however, based on methods used by experienced servicemen.

Causing the Trouble

To find the cause of intermittent receive failure, the defective part must break down when the receiver is being serviced. When the breakdown occurs, voltages can be measured, or oscilloscope patterns can be observed to isolate the defective stage. Because most receivers are "uncooperative" (they perform perfectly when you want them to fail), a number of methods are used to cause breakdown of the intermittent part. Commonly used methods are: probing and tapping suspected parts, applying heat, and increasing operating voltages.

Probing and Tapping


Tapping suspected parts to cause the

faulty condition requires skill, care, and patience. Your objective is to cause only the suspected part to vibrate. This type of test may be deceptive because many parts may vibrate, leading to suspicion of the wrong part. Parts should be tapped carefully, with a pencil eraser, in an effort to vibrate only one suspected part at a time. This topic is discussed later in this article in connection with specific parts.

Frequently, one strand in an insulated wire may protrude to cause an intermittent short. Or, where a wire is dressed around a tube socket lug, or other terminal, the insulation may be worn; the wire may short intermittently to the lug or terminal. Probing, with an insulated rod, may lead to the detection of this type of trouble. It is advisable to suspect any insulated wire which presses against a terminal. Tapping a terminal strip may reveal a broken terminal; tapping a variable tuning capacitor may reveal a loose or intermittently shorting capacitor plate.

Applying Heat

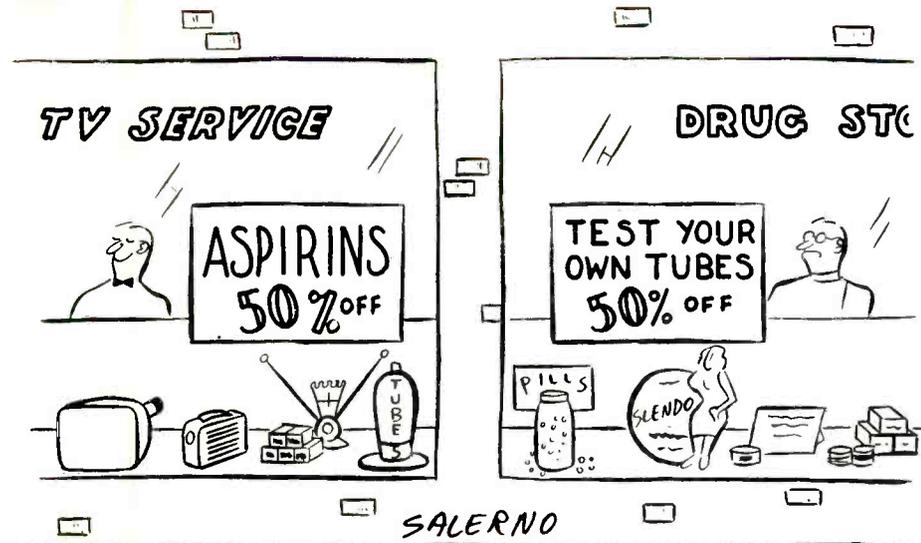When a receiver is bench-tested, its normal operating conditions are *not* being simulated. The ventilation is too good. For this reason, a common practice is to apply heat externally in an effort to bring about the defect. A heating lamp, directed at suspected parts, is frequently used. To apply heat to one part, a funnel can be placed over the



heating lamp with the wide opening covering the bulb, the narrow opening directed at the part under suspicion. Another method of localizing trouble, via the heat treatment, is to hold a hot soldering iron near the part. Where heat is transferred to a suspicious part, remember that the attempt is to cause electrical breakdown under operating conditions, and not to demolish the part with heat.

Increasing Operating Voltages

An intermittent or border-line part will often break down when it receives a higher than normal voltage. A variable line transformer may be used to raise the ac input voltage to about 130 volts. To prevent damage to good components, this method should be tried only for a brief interval. In parallel filament receivers, a tube can be pulled out to increase voltage in a plate circuit. In series filament receivers, a dummy tube (one with only filament prongs) may be substituted to produce the same (high plate voltage) condition.

Tubes

A tube, capacitor, resistor, coil, or transformer may be the culprit causing intermittent operation. Each potential offender is discussed below.

Tube filaments may open intermittently. Where filaments are in parallel, the trouble can be seen in glass tubes. With metal tubes, the trouble may show up in a tube tester. Intermittent

shorts within the tube is another trouble source. Careful tapping of the tube with a pencil eraser may bring about failure. If the trouble can be caused by tapping, but tapping almost *anything* causes trouble, it may be advisable to test each tube. In the tube tester, each tube can be tapped gently, then clunked a little harder to see if it acts up. A picture tube, of course, should never be handled roughly. It can be tapped gently, however, to look for arcing within the tube or an intermittent filament.

Capacitors

Capacitors often open intermittently at a point inside the capacitor where the lead is connected to the foil. This type of defect can frequently be located by gently pulling and nudging the capacitor lead with an insulated probe.

A capacitor may change value when warm. This type of defect should be suspected in frequency drift problems.


Resistors

Wire wound resistors tend to open; carbon resistors tend to change value. The application of heat may cause resistor trouble. Nudging the resistor with an insulated probe may also bring about the defect.

Coils and Transformers

A common cause of trouble is an intermittent open at the point where
[Continued on page 33]

MALLORY Clippings

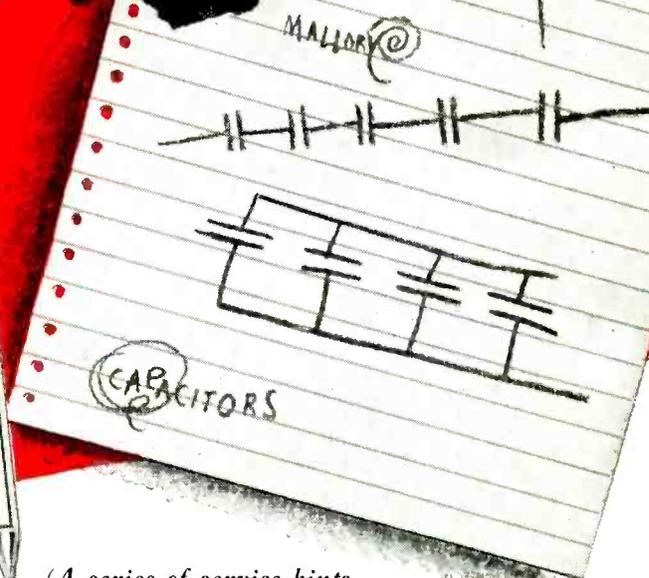

(A series of service hints gleaned from the notebooks of Mallory design and application engineers)

Sometimes you can't find exact-replacement capacitors, especially for some of the older or less popular equipment. Here are a few rules regarding simple substitutions. Obviously, some of these call for physically larger or slightly more expensive capacitors—but that's better than throwing away perfectly good equipment.

In virtually all radio and TV applications, higher voltage ratings or higher capacities can be used at any time.

Individual sections of multiple units can be connected together in parallel to obtain needed capacity, even though they are of different voltage ratings. The lowest voltage rating of all capacitors connected in parallel applies.

Two like capacitors may be connected in series to provide a capacitor with a voltage rating twice as high. The capacity of each section must be twice the actual capacity required. Insulate lead between units and case of capacitor above ground potential. Equalizing resistors are not required.

Regardless of the circuit—you can count on Mallory capacitors to do any service job—right. See your Mallory Distributor, today, and lay in a working replacement stock.

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

Capacitors • Controls • Vibrators • Resistors • Switches • Rectifiers
Power Supplies • Filters • Mercury and Zinc-Carbon Batteries

Outboard Motorboat Electronics

Basic principles in the operation of outboard motor ignition systems, generators, and starting systems are treated in this installment

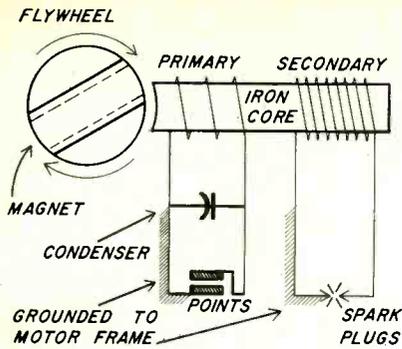


Fig. 1—Basic ignition circuit for magneto fired outboard motor.

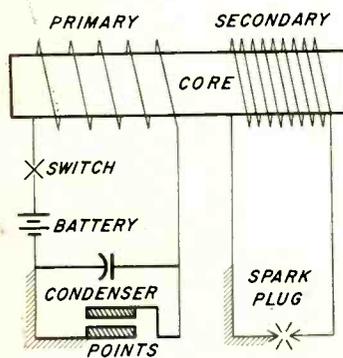


Fig. 2—Ignition system shown here is similar to that used in autos.


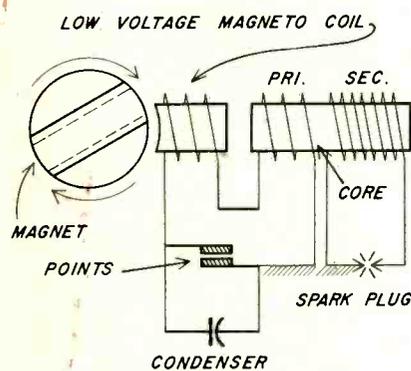


Fig. 3—The new Oliver motors use this variation of the basic system.

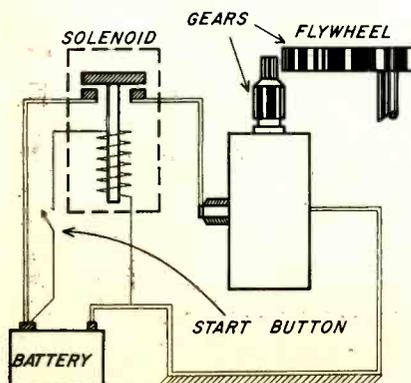

A FEW years ago an outboard motorboat was simply an open skiff with a "kicker" on the stern and fish scales on the seats. But today, outboard motorboats are capable of cruising with the entire family aboard, and of traveling great distances, even far offshore. The recent development of motors with electric starting batteries and charging generators has brought a new era to outboarding, by making it possible to install almost any kind of electrical or electronic gear manufactured for pleasure-boat use. Since outboarders outnumber inboard boats by about ten to one and represent the fastest growing form of marine life today, they represent a market for which the alert marine electronics agency must soon be fully prepared. Already, a number of outboard boats have been fitted with radiotelephones, direction finders, and depth sounders, and their number is sure to increase rapidly in the near future. A knowledge of outboard electrical systems is a coming necessity in the marine electronics business.

The outboard-motor electrical system is divided into three separate parts, each of which varies considerably among motors of different manufacture. Circuits are classified as ignition, starting, and battery-charging. These will be taken up in turn.

Ignition Systems

Figure 1 shows the basic ignition circuit of the usual magneto-fired outboard motor. A primary and secondary

coil are wound concentrically on a laminated iron core and are excited by a rotating field magnet. The system is timed so that at the moment of desired ignition, maximum current flows through the primary winding and the breaker points. At the instant of engine firing, the points open (any arc being absorbed by the shunt capacitor) and the resultant rapid collapse of the magnetic field through the secondary winding induces the necessary high voltage to jump the gap in the spark plug. Note that one side of both the primary and the secondary circuits are, as in automobile ignition systems, grounded, the circuit being completed through the engine frame itself.

As a matter of mechanical convenience and economy, the magneto coils and points assembly are located under the flywheel of the engine, and the field magnet is an integral part of, or attached to, the flywheel.

The circuit shown in Fig. 1 is for a single-cylinder motor, and since most outboard motors use a two-stroke cycle, the magneto furnishes a burst of high voltage once for every revolution of the engine. Two-cylinder engines have two complete magnetos and sets of points under the flywheel, and the cylinders are fired alternately.

Multi-cylinder engines, such as the Mercury four-cylinder models, may have external magnetos driven by gears or a notched belt, with a distributor to route the high tension to the proper cylinders in their firing order.

The first Evinrude put on the market, almost fifty-years ago, had an ignition system using principles somewhat similar to those of our automobiles, as shown in Fig. 2. Here, a conventional

type of high-tension coil is excited by an ignition battery. At the time of firing, the points open, again causing a rapid collapse of the magnetic field through the multi-turned secondary winding and generating high voltage for the spark plug. For many years this system was in discard, but the last couple of years have seen its return in motors such as the *Fageol* and the largest *Mercury* motor. Distributors are used to route the high-tension to the cylinders in firing sequence.

The circuit of Fig. 3, which is used in the new *Oliver* motors, is a variation on the battery system where an external high-tension coil is excited by current induced in a low-voltage magneto winding under the flywheel. The purpose here is to keep the high-voltage circuits to the minimum possible length and out in the open where they can be easily serviced.

These, then, are the basic circuits used for ignition in all of our modern motors. However, individual designs have, of course, a number of variations. For example, motors such as the Scott-Atwater, Evinrude, and Johnson have idling cut-out switches, which disable one of their two cylinders at idling speed so that the motor will slow down satisfactorily. The cut-off switch is actuated by crank-case pressure, and when this drops to a predetermined level, one of the primary coils is grounded. A sidelight on this particular form of switch is that the terminal is a convenient one to use for the installation of an electric tachometer, which must be connected to the primary of the ignition circuit.

Other cut-out switches are used to prevent the motor from being started

Fig. 4—The basic starting system is also similar to that of autos.



by Elbert Robberson

with the transmission in gear, or at high speed throttle settings. This is to safeguard the operator and make it impossible for him to start the engine and have the boat race away from under him. These switches may be either of the mercury or mechanical types.

Starters

The principles of the basic starting circuit are shown in Fig. 4, and are quite similar to those in automotive use. A heavy lead connects from the battery to the motor-starting solenoid, which is physically located on the starter motor itself. The ground return is through the motor block and a heavy cable back to the battery. A relatively low current, flowing when the start button is depressed, actuates the solenoid, closing the starting contacts. A Bendix-type gear engages the starting motor with the flywheel only while the motor is actuated. The choke lever is also actuated by a solenoid, energized by a push-button switch.


Generators

Two systems of battery charging are used. That shown in Fig. 5 is the generator and regulator scheme used on Evinrude and Johnson motors. Here, a miniature automotive type *dc* generator, which is driven by a belt from the flywheel, supplies battery-charging current through a miniature voltage regulator and a dashboard ammeter. On these particular motors there are power-take-off terminals, supplied on a terminal box, for the connection of low-drain external circuits, such as lights, etc.

[Continued on page 26]

Here's How ONE Service Job
Creates Continuing Profit!

Electro-Voice POWER-POINT

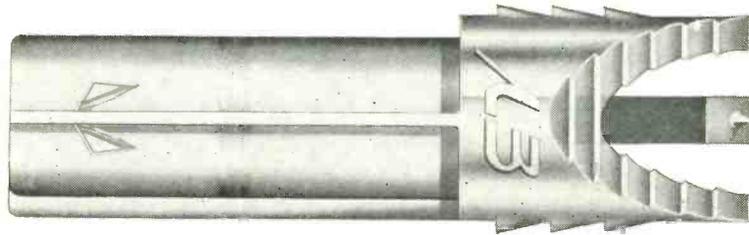

Here's the answer to a serviceman's problem—a way to end cartridge-replacement headaches for all time and still look good on the profit report! Power-Point Mounts fit virtually all phonographs!

YOU install Power-Point Mounts just ONCE and after that, just keep on profiting. Without strain you'll still get the replacement business selling Power-Points—cartridge plus needles in a single unit. You or YOUR CUSTOMER can install a Power-Point in seconds! Strictly profit for you through and through!

What's more, Power-Points end your inventory problems. They're color-coded. You stock just three styles of mounting mechanisms and seven types of Power-Points to service ALL popular-brand phonographs!

Your customers will love you for it! Point out that they'll never need to leave their unit for cartridge/needle service; that THEY install needle and cartridge in seconds once you've attached the mount; that they pay less for a fresh Power-Point cartridge with two needles than they're used to paying for the needles alone! And the color is all they need to remember to get an exact replacement! *Push Power-Points — it's good business!*

Ask your E-V Distributor about Power-Point Mounts

3 POWER-POINT MOUNTS

Model PFT-1, fixed mount, 50¢ list
Model PT-1, turnover mount, \$1 list
Model PT-2, turnunder mount, \$1 list

E-V POWER POINTS



Model 51-1 (red) two 1-mil sapphire tips, \$3.95 list
Model 52-2 (green) two 2-mil sapphire tips, \$3.95 list
Model 53-3 (black) two 3-mil sapphire tips, \$3.95 list
Model 56 (blue) one 1-mil, one 3-mil sapphire tip, \$3.95 list
Model 56DS (orange) one 1-mil diamond, one 3-mil sapphire tip, \$21.50 list
Model 76S (white) one 1-mil, one 3-mil sapphire tip, \$4.20 list
Model 76DS (pink) one 1-mil diamond, one 3-mil sapphire tip, \$21.50 list

Electro-Voice®

ELECTRO-VOICE, INC.

BUCHANAN, MICHIGAN

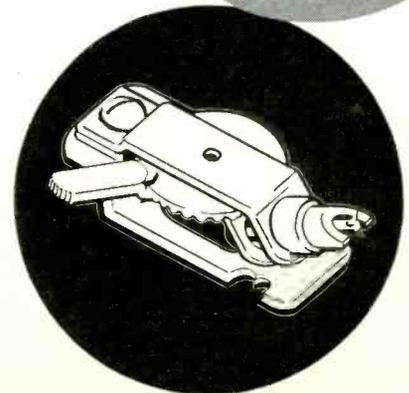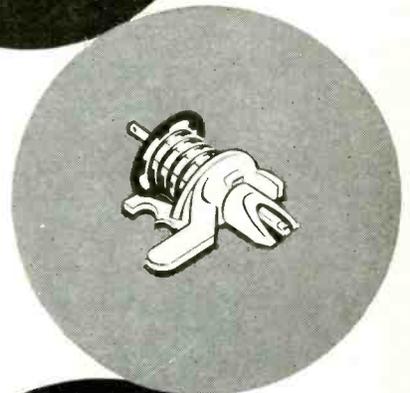Export: 13 East 40th Street, New York 16, U.S.A. Cables: ARLAB



ELECTRONIC SERVICE FIRMS ANALYSIS

by San D'Arcy

TABLE 1

Type of Servicing Done by Radio TV Service Dealers

In this classification only service firms reporting that 53% or more of their annual volume accrued from repairing radios and/or television are included. Firms reporting that over 50% of their service volume accrued from Industrial Electronics and/or Commercial Communications servicing are covered under the Industrial Service classification analysis.	23.4% or 9,945 shops do Radio/TV servicing exclusively
	42.1% or 17,892 shops say Radio/TV servicing is 90-100% of their gross
	28.1% or 11,942 shops say Radio/TV servicing is 80-90% of their gross
	1.6% or 724 shops say Radio/TV servicing is 70-80% of their gross
	4.8% or 1,997 shops say Radio/TV servicing is 53-70% of their gross

Analysis of \$ Service Volume In % of Average Service Shop

Radio-TV Service %	Mobile 2-Way Radio Service %	Hi-Fi - P.A. Intercom Service %	Teletype & Office Mach. Service %	Industrial Electronics Prod. Equip. %	Industrial Electronics Research Equipment %
100 %	—	—	—	—	—
95.5%	1. %	3. %	.06%	.38%	.04%
85.6%	3.4%	6.5%	1. %	3.4 %	—
53.3%	9.9%	19.7%	1.5 %	8.6 %	7. %

NOWADAYS there are 5 basic types of Electronic Service Firm, to wit: 1) the firm that does Radio-TV servicing exclusively; 2) the firm that does *some* Industrial Electronic servicing as well as Radio-TV servicing; 3) the firm that does Industrial Electronic servicing exclusively; 4) the Industrial Electronic service specialists who also do *some* Radio-TV servicing; 5) the service departments of industries, or municipalities, or utilities, which use electronics devices and which only service their own equipments whether it be closed-circuit TV or Counters or 2-way mobile radio.

During April 1957 we sent to every tenth service firm name on our list a questionnaire relating to their present and planned future activities, etc. Exactly 4,998 questionnaires were sent out, and within one month 582 replies were received. Our records indicate there are 44,500 radio-TV service firms and 4,750 Industrial Electronic and/or Commercial Communications service firms in the USA. Thus our survey was rather comprehensive and reached a representative cross-section of servicers in each category in all 48 states, the District of Columbia and US Territories.

For the edification of you subscribers who did not receive a questionnaire, here it is in detail.

You'll note that we did not ask participants to give their name or company affiliation, nor did we ask "loaded or trick" questions because we sought optimum accuracy.

In analyzing and evaluating the replies we broke them into two distinct groups comprising those service firms whose gross income (55% or more) is derived from radio-TV servicing, and

those service firms, who because less than 50% of their income is derived from radio-TV servicing, must be categorized as being Industrial Electronic servicers.

An outstanding fact brought to light by our survey, and it should be stressed strongly, is this: Only a small percentage of the Industrial Electronic Service Firms purport to do any radio/television servicing now—and in the main they make it very clear that they do not intend to go after any additional radio-TV service business in the foreseeable future. By the same token, a relatively high percentage of the firms that now are primarily engaged in radio-TV servicing state that they do intend to extend their activities into Industrial Electronic Servicing at some future date. At present, 93% of the nation's radio-TV service firms derive 70% or more of their gross from radio-TV servicing, whereas only 7%

derive as much as 30% of their income from Industrial Electronic servicing. Yet the survey indicated that in the near future upwards of 25% of the radio-TV service firms anticipate that their gross from Industrial Electronic Service activities will increase anywhere from 10% to 30% over present levels.

Stated another way, radio-TV service firms need not expect any great competition from Industrial Electronic Service firms insofar as the home market is concerned, but by the same token industrial electronic service firms can expect more and more competition from their radio-TV service contemporaries. In truth, the Industrial Electronic Service firms will not "feel" this competition because they can hardly handle the volume of business currently available. There's a very serious manpower shortage of technicians competent to service the myriad of industrial installations now extant.

Getting back to the survey itself—you can see that in effect it allowed us to differentiate between firms that specialize in radio-TV servicing as contrasted to firms that basically are engaged in doing industrial electronics or commercial communications servicing. For example, if any reply to the second sentence in question "IV—SPECIAL" indicated that over 53% of the replier's business is radio/TV repairing, we automatically knew that that particular firm was *not* to be classified as an Industrial Electronic Service Firm.

Now if you are a radio/TV service shop owner you can evaluate your status against "average" by referring to the adjacent *Table 1* which breaks down the "types of servicing done." For example, you know whether 90 to 100% of your income is derived from radio/TV servicing or whether 80 to 90% comes from radio/TV servicing. If, for example, 90 to 100% comes from radio/TV work, then, if yours is an "average shop"—1% of your income is from servicing mobile 2-way radios, 3% from servicing Hi-Fi and P.A., .06% from servicing electronic office machines, etc.

Likewise, if 80 to 90% of your volume is from radio/TV, then 3.4% of your business probably is derived from Mobile 2-way work and 6.5% from Hi-Fi-P.A. if your operation is "average." You can use our other statistical findings as a guide should your operations be dissimilar to an "average" shop.

Of the 9,945 shops now engaged solely in radio/TV servicing, 71% say they do not expect to broaden out into industrial electronic servicing in the near future while 21% report that they are contemplating that move and 8%

are still indecisive. Of the 17,892 shops who report that at present over 90% of their business is now derived from radio/TV servicing, 80% report that they intend to expand and make a stronger effort to obtain Industrial Electronic servicing business soon, while 20% report, in effect, that they will go along on their present basis. Of the 11,942 shops reporting that radio-TV servicing now constitutes over 80% of their income, almost 94% report that they intend to concentrate more and more intensely on Industrial servicing while 6% will hold to the status quo. Almost every one of the 724 shops who now do 70%-80% in radio/TV servicing and almost every one of the 1,997 shops who now do from 53% to 70% of their volume in radio/TV servicing report that they plan much more aggressive efforts to obtain Industrial service work. In fact, 12% of the latter group report that they are gradually giving up radio/TV servicing in order to concentrate 100% in the Industrial service business.

Years In Business

The average Radio-TV Service Dealer has been in business 11 years 2 months.

2,975 or	7% in business	1 year or less
850 or	2% in business	1 to 2 years
13,175 or	31% in business	3 to 5 years
9,350 or	22% in business	5 to 10 years
4,250 or	10% in business	10 to 20 years
11,900 or	28% in business	20 years or more
42,500 or	100%	(total)

Recapitulation of the 42,500 firms engaged in Radio/TV servicing

44.8% or	19,040 shops	are operated as 1 man shops
29.2% or	12,410 shops	have 1 employed technician besides owner
8.7% or	3,697 shops	have 2 employed technician besides owner
13.8% or	5,865 shops	have 3 employed technician besides owner
3.5% or	1,488 shops	have 5 employed technician besides owner

The average (of the 42,500 service shops), has 1.55 employed technicians in addition to the owner-serviceman.

\$ Investment

44,500 Radio-TV Service Firms have \$162,169,550 invested in stock consisting of tubes, components, instruments and fixtures, but not including receivers, Hi-Fi, etc.

Shops have investments ranging from a low of \$250 to highs exceeding \$20,000. The average shop investment is \$4,273.

3% or	1,275 shops	have \$ 500 or less invested
11% or	4,675 shops	have \$500-1000 invested
40% or	17,000 shops	have \$1000-3000 invested
24% or	10,200 shops	have \$3000-5000 invested
13% or	5,525 shops	have \$5000-10,000 invested
9% or	3,825 shops	have \$10,000 or more invested

What test equipment is owned and used by the average Radio-TV service shop?

(To simplify this analysis—the following figures show approximately how many of the respective instruments are in use per 100 service shops.)

Tube Testers	109.9	Yoke-Flyback	
VTVM	102.2	Tester	11.3
'Scopes	88.8	Dot-Bar Generator	11.3
VOM's	73.7	Wheat Bridge	7.6
Signal Generators	54.8	Audio Generator	5.7
Alignment & Sweep Generators	49.1	Color-Bar Generator	5.6
Condenser Checkers	35.9	Square Wave Gen.	5.6
Power Supplies & Batt. Eliminators	35.9	Variac	5.5
CRT-Tester-Rejuv.	22.7	Isolating Transf.	5.4
Signal Tracer	17.0	Field Strength Int.	
Frequency Meter	13.2	Meter	5.4
Marker-Generator	13.2	Grid Dip Meter	3.8
		Transformer	
		Checker	2.2
		Vibrator Tester	2.0

Now let us review the data provided by Industrial Electronic Service Firms.

Industrial Electronics Service Firms Years in Business

The average Industrial Electronic Service Firm has been in business 15 years 6 months.

910 or 20%	have been in business	3 years or less
636 or 14%	have been in business	3 to 5 years
1000 or 22%	have been in business	5 to 10 years
1136 or 25%	have been in business	10 to 20 years
865 or 19%	have been in business	20 years or more
4547	100%	

7% or	318 shops	are operated as 1 man shops
20% or	909 shops	have 1 empl. tech. bes. owner
27% or	1227 shops	have 3 empl. tech. bes. owner
26% or	1582 shops	have 5 empl. tech. bes. owner
19% or	864 shops	have 10 empl. tech. bes. owner
1% or	37 shops	have 20 empl. tech. bes. owner
100%	4547	

The average Industrial Electronic Service Firm has 4.9 technicians employed.

* Of the 222 replies received (from 498 questionnaires sent) 110 were from public utilities, city, state police; airlines, etc., who indicated that their prime service activities relate to servicing their own mobile 2-way radio-communications systems. 86 replies were from Independent Industrial Electronic service firms, many of which report that they are also engaged in servicing mobile, aviation and marine 2-way radio besides servicing Industrial Production and Industrial Electronic Research Equipment.

TABLE II

Analysis of Servicing Done By Industrial Electronics & Commercial Communications Service Firms

The classification "Industrial Electronics Service Firm" has been used in its broadest terms. For example, a Railroad's electronics service department is responsible for servicing: the electronic safety devices along the right-of-way;

the 2-way and 3-way radio-phone equipment from caboose to engineer, or engineer to signal tower; the 2-way radio phone gear used on trucks by line-maintenance crews; the closed circuit TV installations at main ticket reservation branches; the public address installations at railroad stations; the radio and TV systems aboard trains, etc., etc. In like manner the electronics serviceman working for an industrial manufacturing plant maintains the firm's 2-way radio-phone equipment; the electronic

counters, checkers or sorters; the automation or "systems" devices; office machinery, etc.

39%	are engaged in Indus. Com. Serv.	100%
20%	are engaged in Indus. Com. Serv.	90-99%
18%	are engaged in Indus. Com. Serv.	70-89%
12%	are engaged in Indus. Com. Serv.	50-69%
11%	are engaged in Indus. Com. Serv.	30-49%
0%	are eng. in Ind. Prod. Equip. Serv.	100%
1%	are eng. in Ind. Prod. Equip. Serv.	90-99%
1%	are eng. in Ind. Prod. Equip. Serv.	70-89%
1%	are eng. in Ind. Prod. Equip. Serv.	50-69%
6%	are eng. in Ind. Prod. Equip. Serv.	30-49%
91%	are eng. in Ind. Prod. Equip. Serv.	under 30%

[Continued on page 23]



TWO-WAY RADIO

communications equipment

VHF-FM FOR:
MOBILE
AIRCRAFT
MARINE
MOTORCYCLE
PORTABLE
BASE

VHF-AM FOR:
AIRPORT VEHICLES
GROUND STATIONS
POINT-TO-POINT

VHF
ANTENNAS
REMOTE CONTROLS
ACCESSORIES



FLEETCOM Sr.

MODEL 300-6/12 SERIES

The FLEETCOM Sr. is rugged, compact, universal 6/12, VHF-FM two-way mobile communications equipment for the Public Safety, Industrial, Land Transportation and other radio services.

COMCO'S 17 years experience in design leadership and production "know-how" is engineered and built into every FLEETCOM Sr. unit.



Model 300-AB-6/12 Chassis

POWERFUL! COMPACT! EFFICIENT!



Model 300-FG-6/12 mobile package

Features:

- 55 Watts output in low band
- Front or rear mounts
- Case size 14" x 13 1/2" x 6"
- Maximum output with minimum battery drain.
- UNIVERSAL!** Instantly convertible for 6 or 12 volt operation.
- COMPLETE!** Ready for installation and operation.
- QUALITY!** Exceptional value/price ratio.

ATTENTION DEALERS!
Write for available territories.




DESIGNERS AND MANUFACTURERS OF RADIO COMMUNICATIONS EQUIPMENT

COMMUNICATIONS COMPANY, Inc.

FOUNDED 1938 CORAL GABLES, MIAMI 34, FLORIDA

BEST BUY IN SCOPES

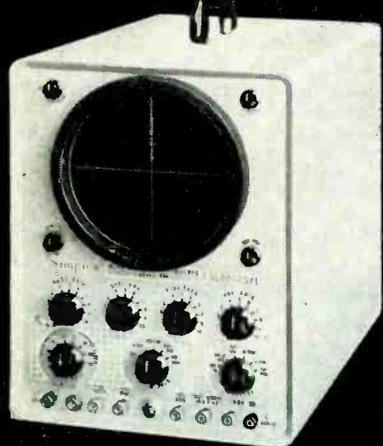

new!
Simpson
COLORSCOPE
MODEL 458

Compare the new Simpson Colorscope Model 458 with any oscilloscope on the market. It is an advanced, seven-inch, high-gain, wide-band scope especially designed for color-TV service. Ideal for black and white, too.

100% RESPONSE at 3.58 mc color-burst!

DUAL bandwidth—narrow or wide!
FLAT FREQUENCY RESPONSE, within 1 db to 4.5 mc!

RISE TIME less than 0.05 microsecond (wide band)!

FULL RANGE compensated vertical attenuator!

Price complete with shielded input cable and Operator's Manual ... **\$229.95**

Four accessory probes are available to provide the Simpson Colorscope with still greater utility.

See your distributor for details or write—

SIMPSON Electric Company
WORLD'S LARGEST MANUFACTURER
OF ELECTRONIC TEST EQUIPMENT

5200 W. Kinzie St., Chicago 44, Illinois
Phone: ESTebrook 9-1121

In Canada: Bach-Simpson Ltd., London, Ont.



1957 Philco TV-part 2.

by H. S. King
Supervisor, Electronic Training Dept.
Philco Corporation

This second installment deals with the Philco chassis 7L40 series with emphasis placed on automatic and remote control tuning, UHF adapters, and circuitry.

7L40 Chassis Series

The 7L40 chassis series are all vertically mounted types designed for installation to one side of the picture tube as shown in Fig. 5. Variations in the chassis of this series include facilities for *uhf*, phonograph connections, automatic tuning with remote control, and changes in the output deflection circuits for various size picture tubes.

All of the chassis that are equipped for automatic tuning also contain provisions for connecting one of the two remote control units available, the RC-10A and RC-30. A 12-contact receptacle is provided on the back of the receiver cabinet for remote control connections.

Top-Touch-Tuning System

The automatic tuning system, known as "Top-Touch-Tuning" consists of a 12 volt motor driven stepper assembly mounted on the rear of the *uhf* tuner.

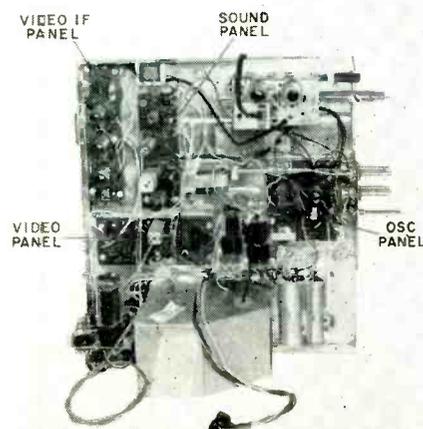


Fig. 5—View of 7L40 vertically mounted chassis.

A momentary contact switch, mounted on the top of the cabinet activates the system permitting consecutive channel selection or selection of only those channels receivable. A selector rod on the cabinet rear provides the means of adjusting the system to select only those channels that can be received in the area or to stop on every channel consecutively.

The RC-10A remote control is a small plastic-case hand unit with a push-button switch and 30 feet of two-conductor control cable and plug. When the plug is inserted into the receptacle on the cabinet rear, the switch of the remote control is in parallel with the top-touch-tuning switch on the receiver and activates the automatic channel selector system in the same manner.

The RC-30 is a deluxe remote control unit. It consists of the hand control, a 30-foot, five-conductor, flat-ribbon cable and a sub-chassis, illustrated Fig 6. This unit permits remote selection of the desired channel, control of volume and also turns the receiver power on and off. The hand unit contains a volume control, an on-off contact switch

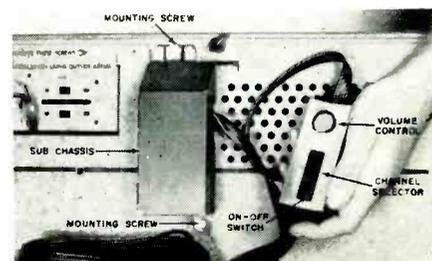


Fig. 6—Photo of RC-30 remote control tuning assembly.

and the automatic tuning contact switch. The sub-chassis contains a step-down transformer (117v-12v), a relay, relay switch and connecting plug. The sub-chassis plugs directly into the receiver's 12-contact receptacle on the cabinet rear.

Circuitwise, the automatic-tuning contact switch on the remote control unit connects in parallel with the top-touch-tuning button on the receiver and permits remote channel selection automatically. The volume control is connected in series with the B-plus voltage applied to the sound *if* stage to control audio volume. It is independent of the receiver's volume control in operation but its maximum range is dependent upon the level to which the receiver's volume control is adjusted. The step-down transformer is continuously powered as long as the receiver is connected to the power line. The remote unit activates the relay switch through the step-down transformer. The relay switch alternately opens or closes each time the on-off button is depressed and the relay is energized, thus opening or closing the power line circuit. The RC-30 remote control circuits are illustrated in Fig. 7.

7L40 Chassis Circuitry

The tuners in the 7L40 chassis series are either 12 position or 13 position incremental types. The 13 position tuner has facilities for the installation of a *uhf* tuner adapter. The output of these tuners is a 45.75 mc *if* signal. The *if* printed wire panel contains 3 stagger tuned *if* amplifiers and the video detector. Maximum interference rejection is obtained in this system by the use of three traps in the input stage, two of which are tuneable to 47.25 mc while

[Continued on page 35]



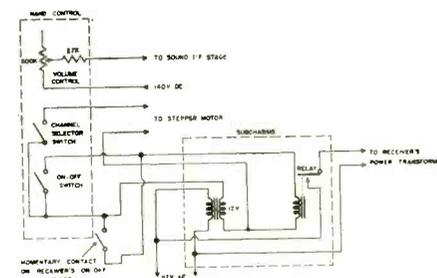



Fig. 7—RC-30 remote control tuning assembly circuitry.

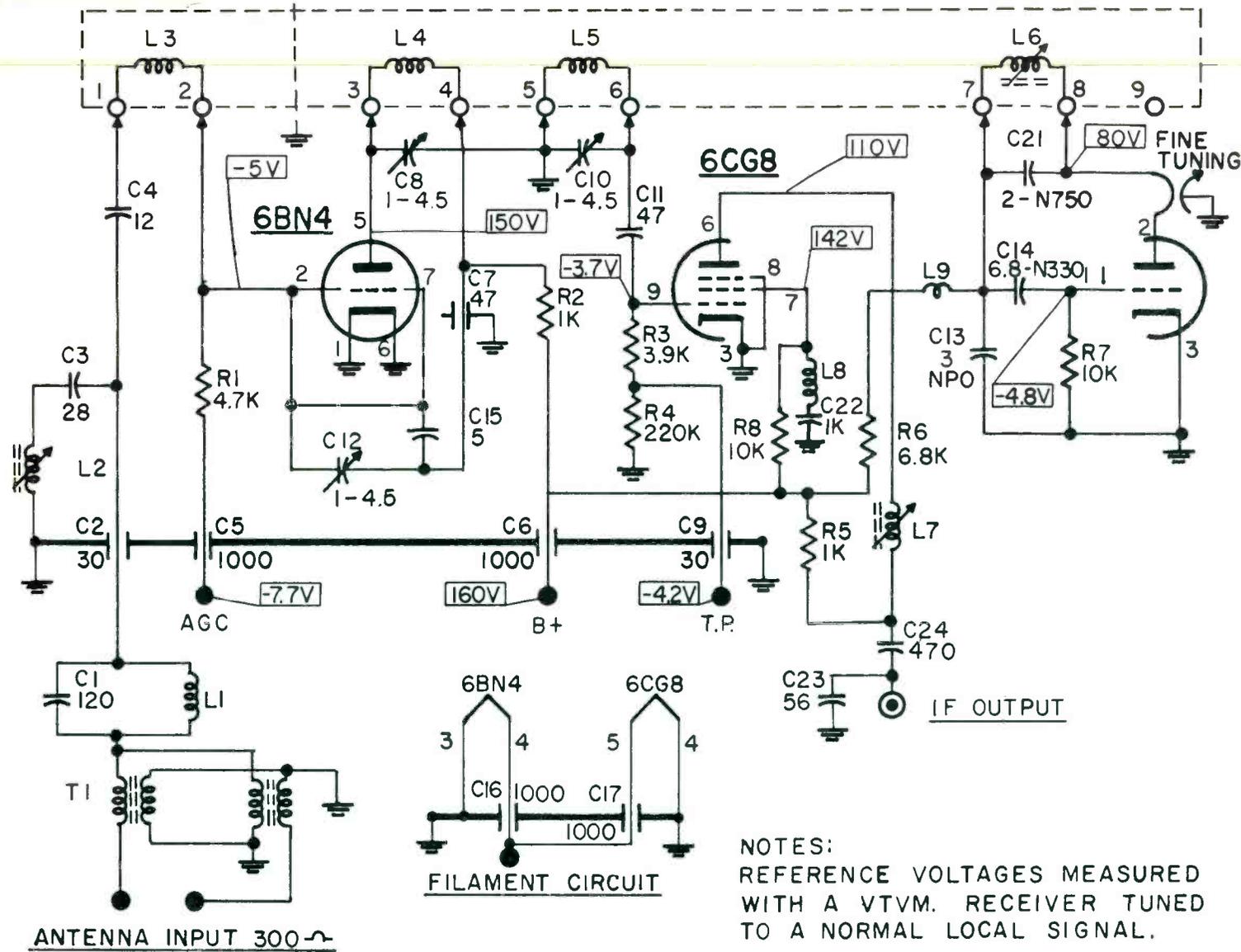

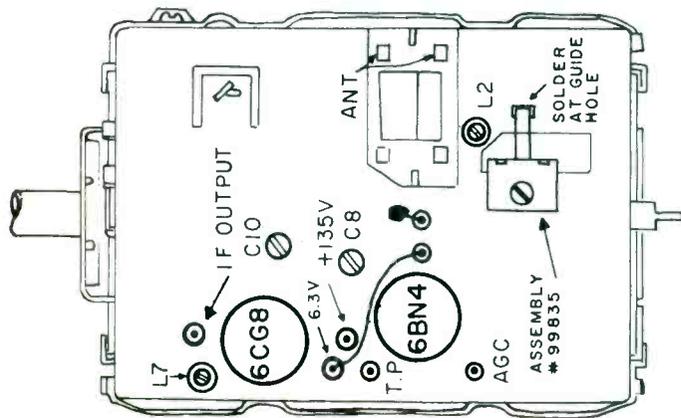
SCHEMATIC DIAGRAM FOR TUNERS 710001 & 710003




TOP VIEW OF TUNERS 710001 & 710003

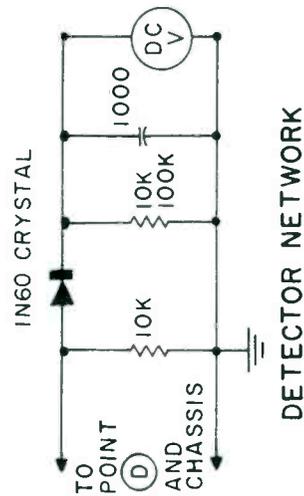


DETECTOR NETWORK

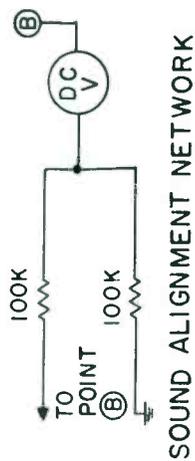


SOUND ALIGNMENT NETWORK

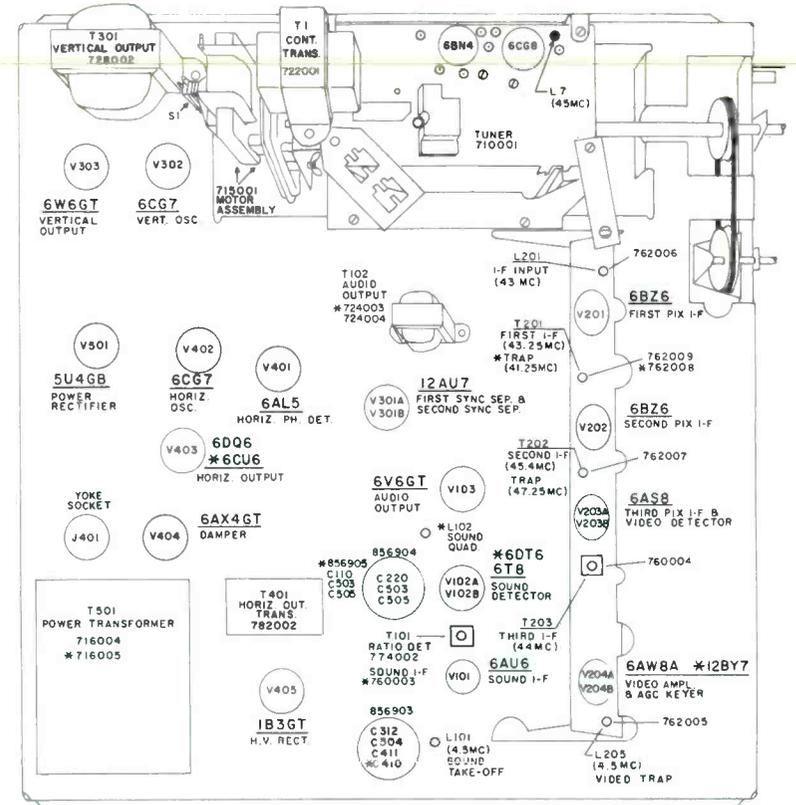

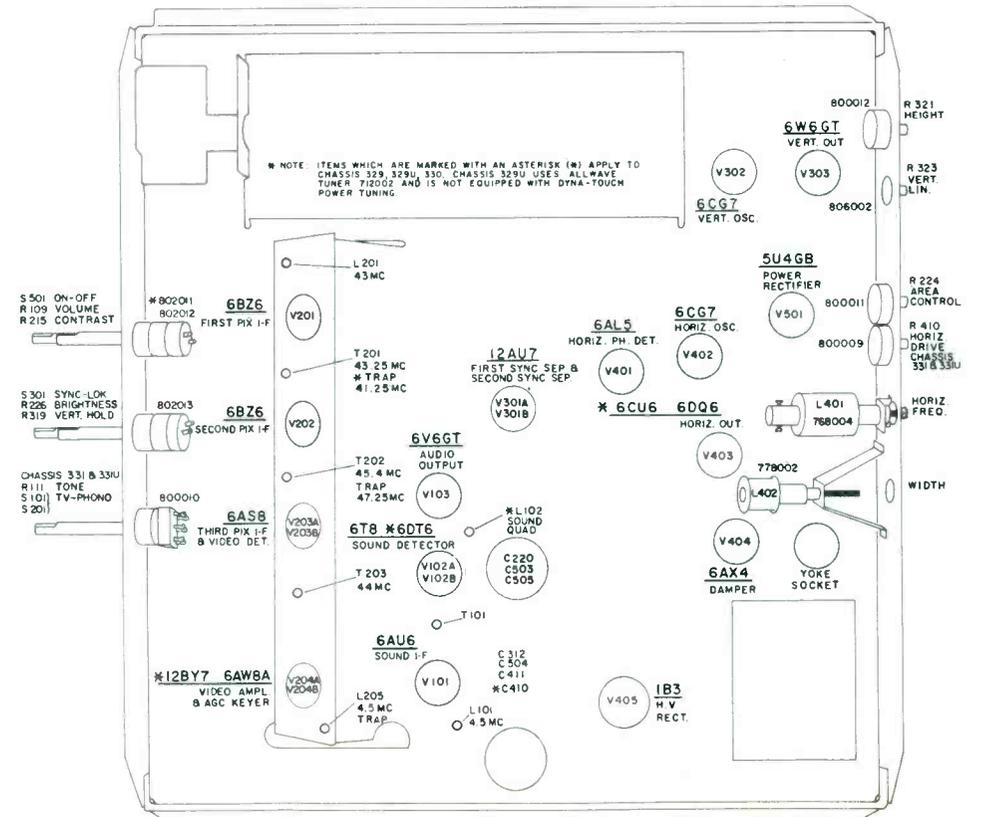
TOP VIEW OF CHASSIS 329, 329U, 330, 331, 331U




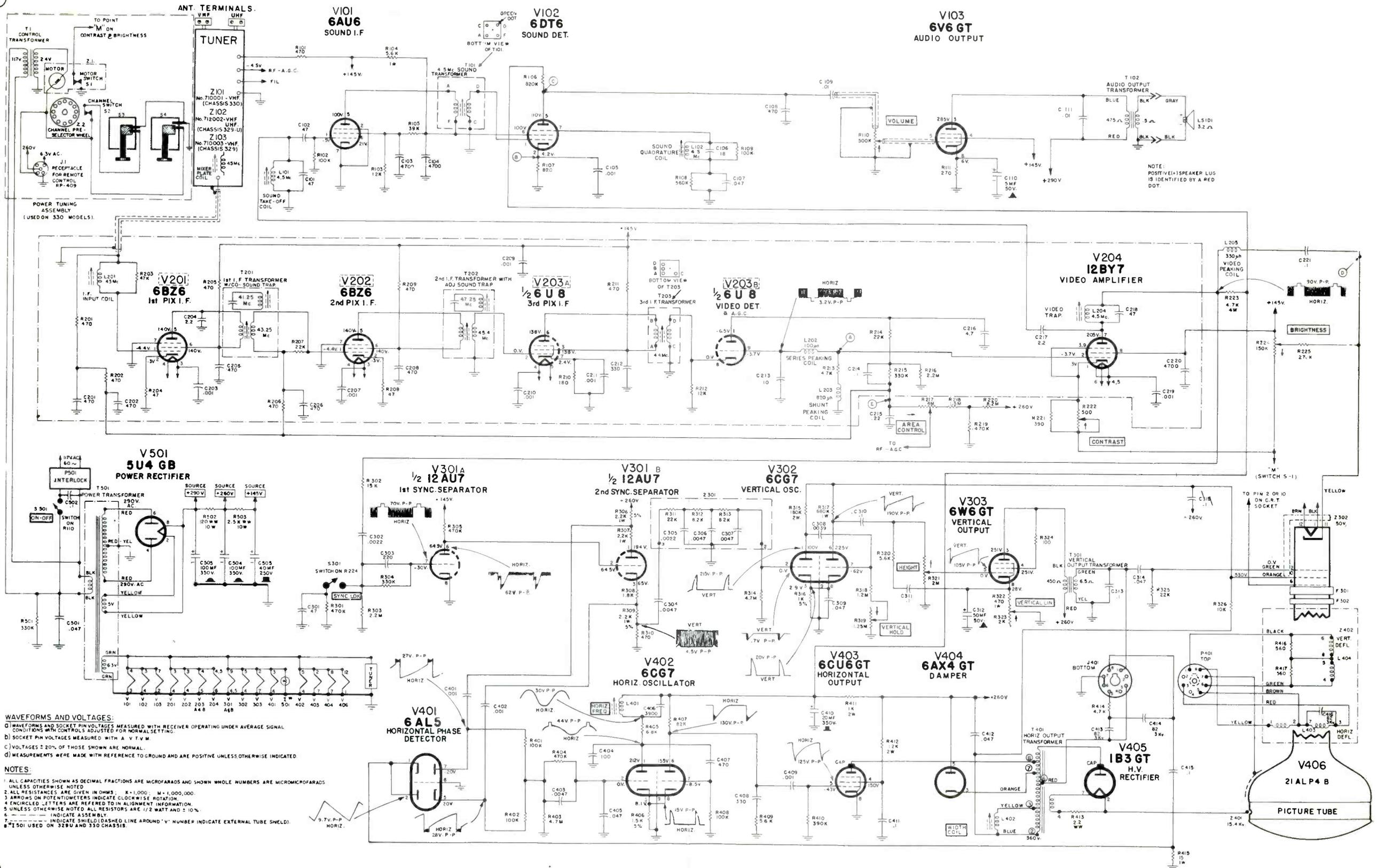BOTTOM VIEW OF CHASSIS 329, 329U, 330, 331, 331U




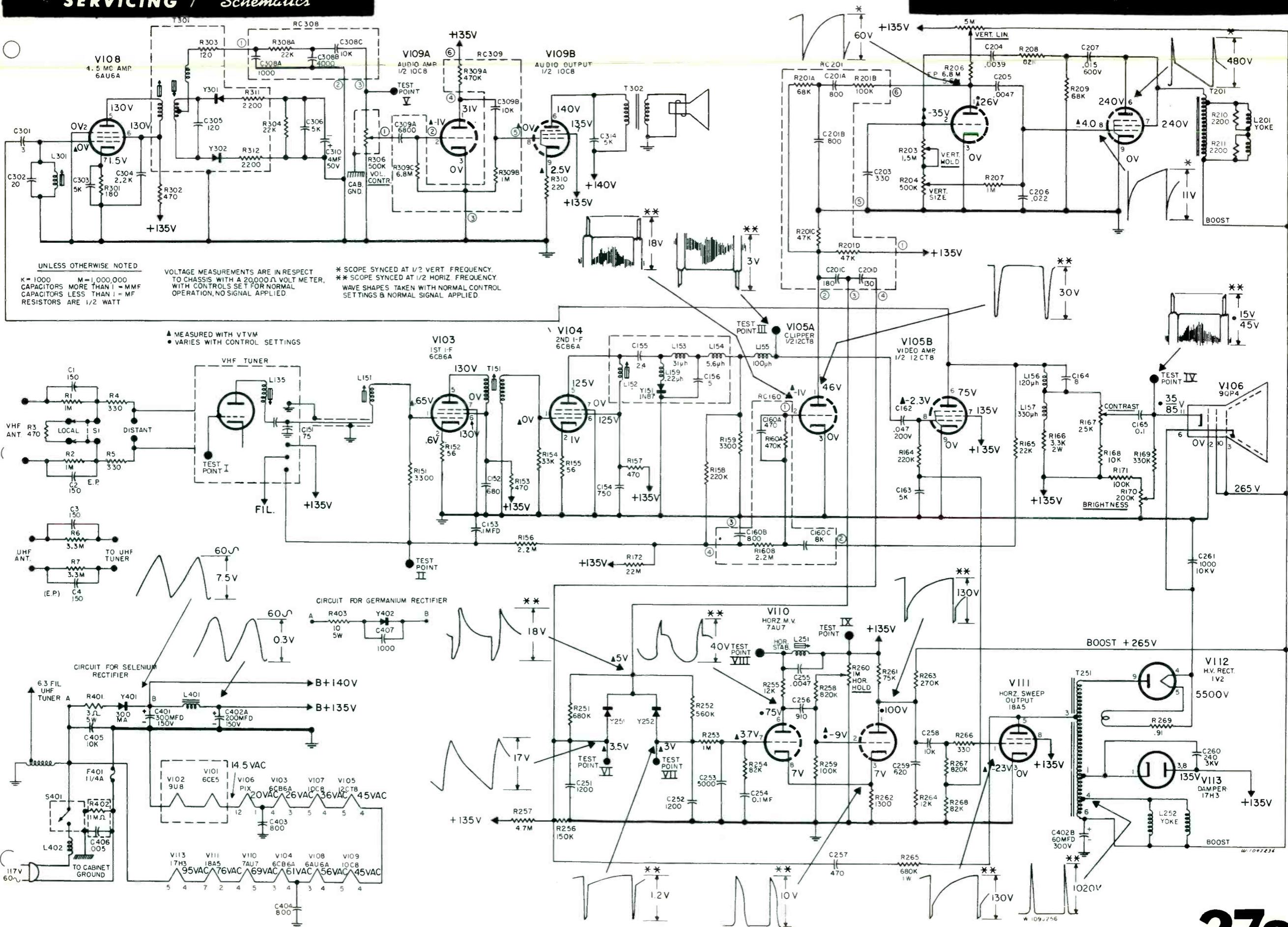SCHEMATIC DIAGRAM FOR HOFFMAN MARK 10 CHASSIS 329, 329U, 330




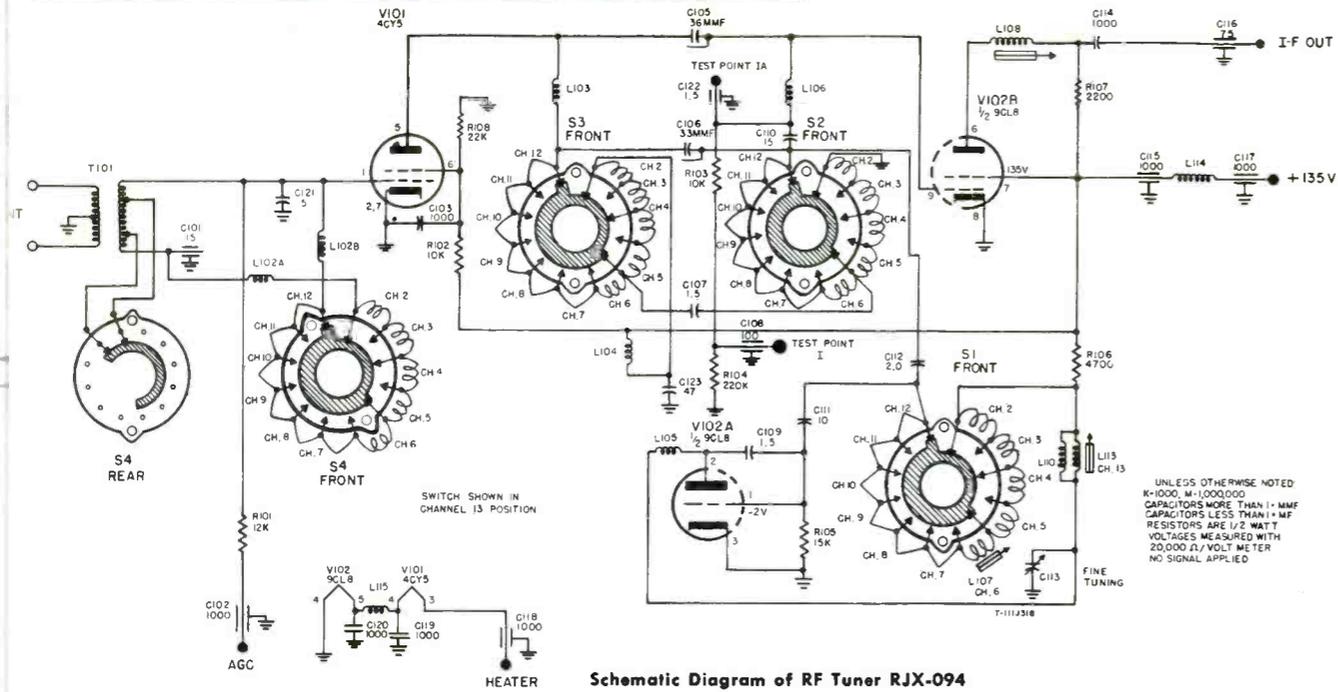


Schematic Diagram of RF Tuner RJX-094

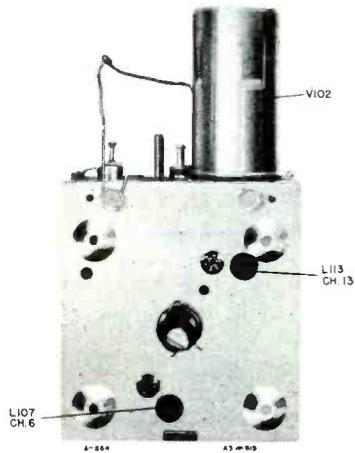


Oscillator Adjustments (RJX-094)

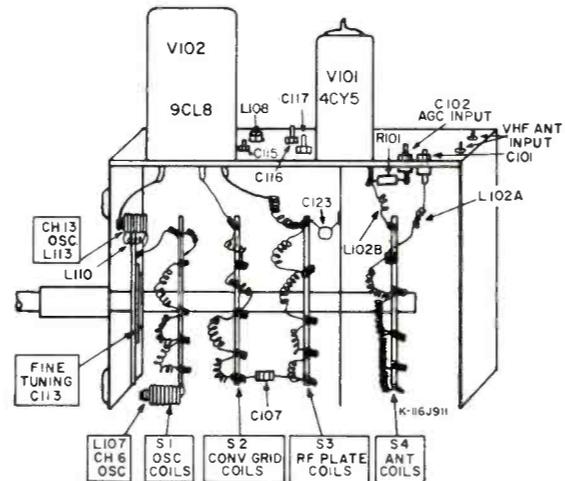


RJX-094 Adjustments

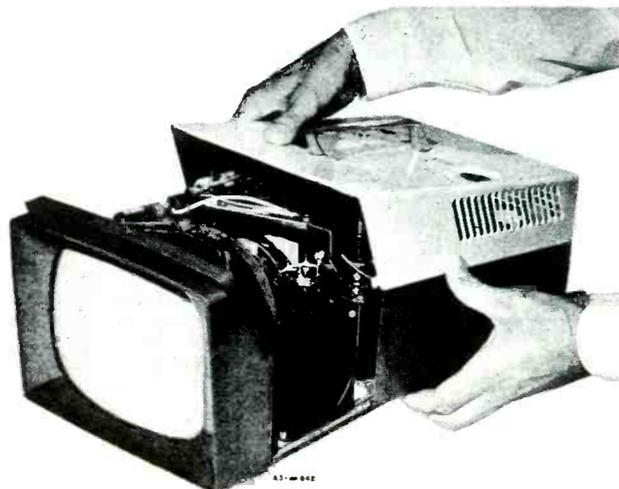

Removing the Cabinet

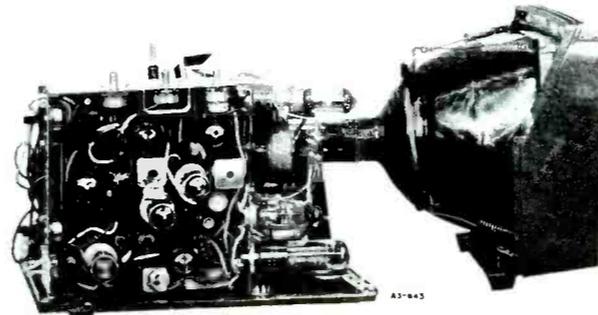

Removing Cabinet Front and Picture Tube

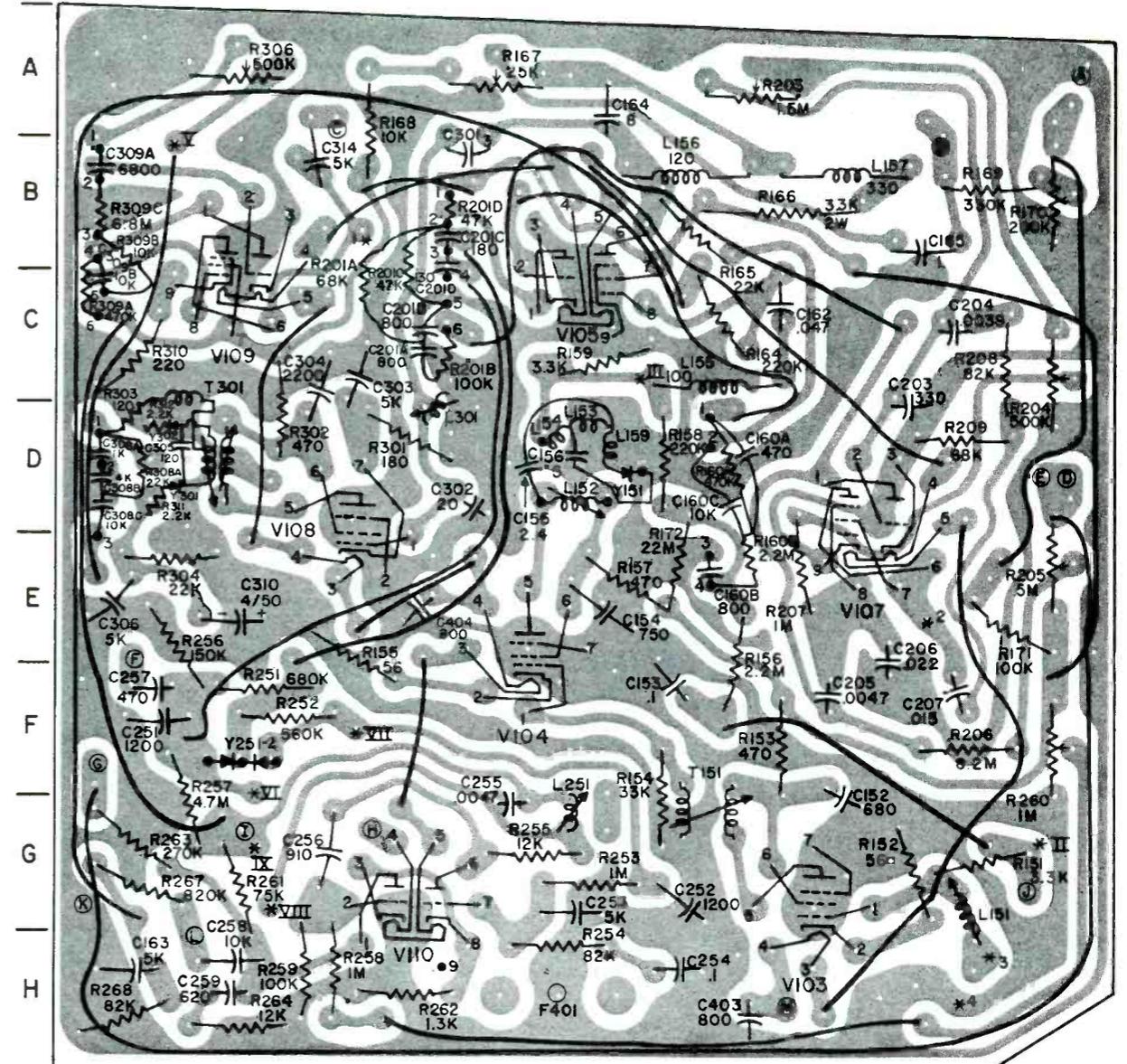

VIEW SHOWS COMPONENT AS VIEWED FROM PRINTED WIRING SIDE OF BOARD P-125J534



CIRCLED (A) LETTERS

REPRESENTS INTERCONNECTING WIRES FROM OTHER COMPONENTS.

- A PIN 2 OF V106
- B PIN 11 OF V106
- C TO Y401
- D PIN 10 OF V106
- E PIN 3 OF V106
- F TO R265
- G TO PIN 6 OF T251
- H TO PIN 2 OF VIII
- I TO PIN 8 OF VIII
- J TO VHF TUNER-AGC
- K TO PIN 3 OF VIII
- L TO R266
- M TO PIN 1 OF V106

ASTERISKED (*) NUMBERS

REPRESENT WIRE WRAP TERMINALS MOUNTED ON COMPONENT BOARD FOR CONNECTING WIRES FROM OTHER COMPONENTS

- * 1 TO T302
- * 2 TO T201
- * 3 FROM VHF TUNER-IF OUTPUT
- * 4 GRD FOR I-F INPUT CABLE SHIELD

UNLESS OTHERWISE NOTED

K=1000 M=1,000,000
 CAPACITORS MORE THAN 1 MF
 CAPACITORS LESS THAN 1 MF
 RESISTORS ARE 1/2 WATT
 INDUCTANCES IN μH

ASTERISKED (*) ROMAN NUMBERS

REPRESENT TEST POINTS ON COMPONENT BOARD

AD LIBS

[from page 3]

cation for a license as a television serviceman and tendered a \$33 check in payment. Preliminary to acting upon the application, the city license department asked for a police report, a formality which usually brings a statement of 'no police record.' In this case, however, the report said: 'In 1946, drunk, 15 days in the workhouse; 1947, disorderly conduct, 15 days in workhouse; disorderly conduct again, 30 days suspended; suspected forgery and suspected auto theft, released; 1948, second degree forgery, sentenced to St. Cloud reformatory; 1949 (and apparently out again) indecent assault and placed on probation; 1955, leaving the scene of an auto accident, 5 days in the workhouse; 1956, disorderly conduct, 10 days suspended; driving after suspension of his driver's license, 30 days; 1957, once again, driving after suspension of his driver's license, 30 days.'

"To add to the insult, the \$33 check which accompanied his request for a city permit bounced for lack of funds. The license committee recommended and the City Council promptly voted to deny the application. Without such a restrictive ordinance, this man might have gone his merry way as a self-styled television repairman, entering homes where women were alone or where only children were present, or where opportunities were wide open for theft or more serious crimes. Some time back when the City Council gave consideration to this type of ordinance, it was agreed that a tight ordinance should be adopted as a safeguard for all in St. Paul. Obviously, that viewpoint is paying off.

"It shouldn't be necessary to point out that persons at home would do well to insist upon proper identification from any person arriving with a tale of offering service. Reputable servicemen welcome such queries and are willing to show their credentials; they know that such questions and evidence of their reliability are protection against the no-goods and the fly-by-nights."

In every walk of life, in every industry or profession there are "sinners" who

have on occasion run afoul of the law. (I've paid fines for overtime parking. My physician tells me that last month he was arrested for speeding. A neighbor of mine recently was hauled into court for burning grass clippings on the street). The mere fact that one has broken some law does not make him a hardened criminal, nor does it justify depriving him of the right to earn a living in his chosen profession. But, there are chronic offenders of law whose past records, like in the case cited by Mr. Langland, justify and require that they be barred from free access to homes where temptation can, and undoubtedly will, induce them to take advantage of the unwary. If licensing of radio/TV servicemen (and other in-the-home servicemen) does nothing less than prevent scoundrels and hardened criminals from having easy access to homes, licensing is justifiable and warrants support of all parties concerned. Servicemen, situated where licensing is required, can hold their heads erect and say with pride, "I have been tried. My record has been scrutinized. I have not been found wanting." This would be a giant-step forward—one in which we would all take enviable pride.

Our Format Change Next Month

Early last year the majority of our subscribers, when asked whether or not they preferred to have ELECTRONIC SERVICING change its format to "King Size - 11 x 11 inches," voted for that change which was put into effect with our May 1956 issue. Since then many subscribers have reversed their opinion and now suggest that we revert to the "Standard Size" with text pages 7 x 10 inches. Many readers suggest that we sectionalize the magazine, too, keeping radio-TV articles apart from industrial service articles so that tear-outs and filing for future reference can be done more easily.

A magazine publisher must respect the wishes of his subscribers. Accordingly, next month ELECTRONIC SERVICING's format will be changed back to its former style. ■ ■

ELECTRONIC FIRMS ANALYSIS

[from page 13]

1% are eng. in ser. Ind. Elec. Res. Equip. 100%
1% are eng. in ser. Ind. Elec. Res. Equip. 90-99%
2% are eng. in ser. Ind. Elec. Res. Equip. 70-89%
3% are eng. in ser. Ind. Elec. Res. Equip. 50-69%
2% are eng. in ser. Ind. Elec. Res. Equip. 30-49%
91% are eng. in ser. Ind. Elec. Res. Equip. under 30%

Test Equipment Reported Owned & Used by Industrial Electronic Service Firms

The huge amount of various specialized instruments owned and used by Industrial Electronic Servicers in addition to the more popular types made it unfeasible to break this classification down.

Commonplace instruments used are: Tube Testers, VTVM's, VOM's, Signal Generators, Alignment and Sweep Generators, Power Supplies and Battery Eliminators, Condenser Checkers, Grid Dip Meters, etc., etc.

The specialized types of instruments include: Frog meters, Thru-line and End Volt-

meters, Modulation and Frequency Meters, Audio signal generators and analyzers, Microvolts, Microwave panoramic analyzers, distortion meters, sound level meters, enlargers, vibrotesters, wavemeters, radiation detectors, etc., etc.

\$ Investment


4,547 Industrial Electronic Service Firms have \$34,874,900 invested in stocks consisting of tubes, components, instruments, fixtures and accessories.

Shops have investments ranging from a low of \$505 to highs approximating \$200,000. The average shop investment is \$7,672.

24% or 1094 shops have \$1000 or less invested
10% or 455 shops have 1,000- 3,000 invested
10% or 454 shops have 3,000- 5,000 invested
23% or 1045 shops have 5,000-10,000 invested
29% or 1318 shops have 10,000-20,000 invested
4% or 181 shops have 20,000 or more invested
100% 4547

Analysis in % Showing Types of Industrial Electronic Equipment That Is Serviced

Industrial Communications Mobile 2-Way Radio	P.A. and Intercom.	Teletype & Office Mach.	Industrial Production Equipments Automation, sorting, Indust. Elect. counting, selection devices, etc.	TV/Radio Research
69.8%	4.5%	2.0%	14.4%	4.6%
				4.7%

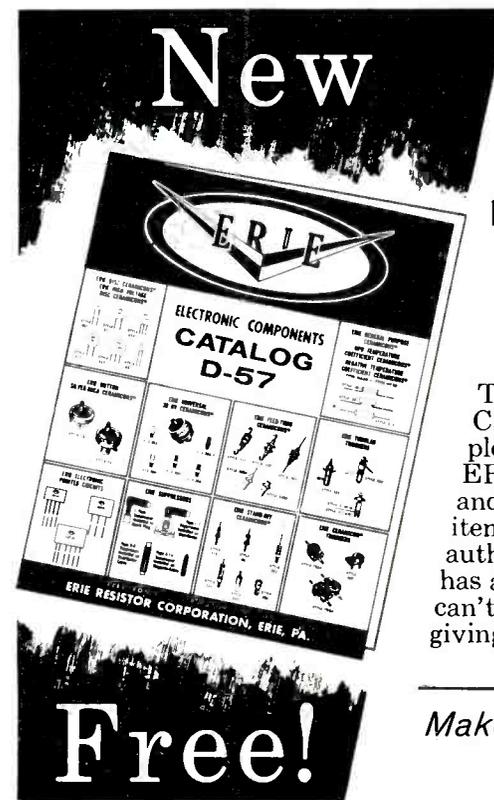

D-57 CATALOG at your Authorized ERIE DISTRIBUTOR

The new ERIE D-57 Catalog, including the complete and enlarged line of ERIE Electronic Components and Corning Glass Works items, is ready. Your authorized ERIE Distributor has a copy for you. If he can't supply you, write us, giving his name.

Make the ERIE Catalog
Your Catalog

Free!

ERIE

Electronics Distributor
DIVISION
ERIE RESISTOR CORPORATION
ERIE, PA.

BEST BUILT



YET

That's our claim—backed up by a solid majority of independent set makers who use them. Built to one standard of quality—Blue Chip Quality—Magic Mirror Aluminized Picture Tubes mirror twice the light to create a picture twice as bright. Tell your supplier you'd rather have Tung-Sol!

Blue Chip Quality

TUNG-SOL®

Magic Mirror Aluminized
PICTURE TUBES

trade

Radio Receptor Co., Inc., a pioneer in electronics, is completing installation of imported equipment to manufacture a line of selenium rectifiers it claims will be smaller yet more efficient. The new rectifiers, to be trade named "Petti-Sel," represent an investment of more than \$500,000 and more than a year of negotiations and planning. Production, under a process developed by the Siemens companies of West Germany, will get under way in about a month, according to Hugo Cohn, president of Radio Receptor.

Sprague Products Company, North Adams, Mass., recently received its fourth Friends of Service Management Award from the National Alliance of Television and Electronic Service Associations. Sidney L. Chertok, Sprague Sales Promotion Manager, left, is shown re-



ceiving the bronze and marble plaque from Harrol O. Eales, NATESA West Central Vice President, at the recent association conference in New Orleans. The plaque compliments Sprague for "outstanding service in creating better customer relations" between set owners and the Television-Radio Service industry.

Manufacturers' sales of receiving and TV picture tubes increased in May over the preceding month, RETMA reported. A decline was recorded, however, in cumulative sales this year compared with the first five months of 1956. Producers sold 32,836,000 receiving tubes worth \$28,995,000 in May compared with 27,970,000 units valued at \$25,384,000 sold in April and 33,015,000 worth \$27,145,000 sold in May 1956. Cumulative receiving tube sales for the first five months of this year totaled 185,847,000 valued at \$159,147,000 compared with 188,619,000 units worth \$152,680,000 sold during the same period last year.

Philco distributors report "no difficulty" in getting dealers with service facilities and independent service shops to sign service agreements with Philco to provide free service to Philco radio and phonograph owners during the 90-day free warranty period, reported Henry T. Paiste, Jr., Vice President-Service of Philco Corporation. The program, announced at the Company's June distributor convention is designed to enroll 10,000 "Gold-plate!" independent service operators and servicing-dealers to give broad national coverage.

A practical and timely Transistor Home-Study Course especially for electric service technicians has just been announced by the CBS tube division. Proclaimed to be an industry first, the course is designed to help the independent service-dealer take advantage of extra profits now available from servicing transistorized equipment. Profusely illustrated, the course is written in an easy "learn by using" manner. What the technician learns he remembers," a company spokesman said, "because he does it himself. . . by making several practical transistor devices he can keep and use."

Formation of a nine-man group of promotion specialists to concentrate solely on color television activities was announced recently by Joseph P. Bannon, General Sales Manager, RCA Victor Television Division, Radio Corporation of America. Heading the new group as Manager, Color Television Market Development, is Roger S. Drew who has had an extensive background in promotion and merchandising. Mr. Drew will have a representative in each of RCA's eight regions.

Two completely new and comprehensive promotion campaigns were announced recently to Raytheon Receiving and Industrial Tube Distributors by Raytheon's Distributor Sales Department. One, a personalized and sales stimulating promotion program for Raytheon Tube Distributors and the second, a business building program for service dealers. Continuance of the popular Raytheon Bonded Electronic Technician Program was also announced to Raytheon Sponsoring Bonded Distributors. The Raytheon Business Building Program for service dealers provide a collection of window displays and streamers, indoor and outdoor signs, sales helps, advertising aids, shop aids,

flashes

business supplies and service help. The Raytheon Business aids and service helps have been designed to assist service dealers in building business and boosting profits.

Transistor sales during the first five months of this year increased substantially over the corresponding 1956 period, RETMA announced. Sales of the semiconductor device during May also showed an increase over April and May of last year. Factory sales of transistors in May totaled 2,055,000 units with a dollar value of \$5,636,000 compared with 1,774,000 transistors sold in April valued at \$4,880,000. Cumulative sales of these devices during the first five months of this year totaled 8,954,300 valued at \$25,128,000 as against 3,628,000 transistors worth \$10,082,000 sold during the corresponding period of 1956.

The first comprehensive exposition covering every phase of the making and the reproducing of sound and pictures opens September 17, 1957 in Chicago's famed International Amphitheatre. Slated for a six day run, the show will unify, under one roof, all industries such as television, radio, hi-fidelity reproducers and recorders, tape, musical instruments, recordings, organs, sheet music, pianos, electronic parts and components, and other allied products.

The TV industry is a competitive morass of too many low-cost, poorly styled, stripped down receivers according to David T. Schultz, president of Allen B. DuMont Laboratories, Inc. He spoke recently before a group of editors and writers at the unveiling of the firm's new television receivers and high fidelity phonographs. "I think most executives in the industry agree," Mr. Schultz said, "that manufacturers have gone too far in trying to outdo each other price-wise in order to get volume. There is now considerable upgrading of merchandising in the new lines being introduced this spring, and I think it's a healthy trend which can and will return TV manufacturing to a profitable business."

Norman Ackerman, President of the Perma-Power Company, Chicago manufacturer, announces that the company has just completed a two week move to its own new and larger building which increases its production five times over its former headquarters. New

equipment, extended assembly lines, better facilities to expedite orders more rapidly, plus additional key production personnel at the new plant assure continued high quality and service. This move marks the first step of the company's expansion program.

A state organization of independent radio-television service groups was created at a recent meeting held in Cambridge by delegates from six Massachusetts cities. The organization is chartered as the Electronic Technicians Guild Of Massachusetts. Among the more pressing problems of the industry



Seated: Nicholas A. Averinos. L-R: Remo DiNicola, Albert N. Giddis, Gilbert P. Clark, L. J. McEvoy.

has been the need of uniform service charges and standard business practices, and public recognition of the electronic service industry as a high skilled technical profession having a unique part to play in 20th century technological society.

Blonder-Tongue Laboratories is now offering to all its distributor's personnel and system installers a factory training course in the installation, operation and maintenance of Closed-Circuit TV and Master TV Systems. The courses are handled on an individual basis to permit consideration of actual wired systems and to concentrate on the major fields of each distributor or operator. Certificates are awarded upon completion of the two and three day courses.

Intensified plans for manufacturer participation in the promotion of National Television Week, Sept. 8-14, have been endorsed unanimously by the nation's leading TV set makers, RETMA announced recently.

BEST FOR



EVERY SET

All Tung-Sol radio, TV or Hi Fi tubes are engineered to one standard of quality—Blue Chip Quality. Whether they're for famous set makers or leading service dealers, Tung-Sol Tubes are identical in design and performance. Tell your supplier you'd rather have Tung-Sol!

Blue Chip Quality

TUNG-SOL[®]
RECEIVING TUBES

TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

OUTBOARD MOTORBOAT ELECTRONICS

[from page 11]

Figure 6 shows the circuit of the other battery-charging system, used on motors such as the *Scott-Atwater*, *Mercury*, *Oliver*, and *Fageol*. Here, alternator windings on a laminated core are installed under the flywheel which contains a magnet. On engines that also have under-the-flywheel ignition magnetos, these windings may be grouped around the ignition windings and excited by the same magnet. Current output from the alternator coils is fed to a bridge-connected selenium rectifier, providing the battery with full-wave

rectified alternating current for charging.

The *dc* generators are rated for a current output of 10-amperes, while the alternators are nominally rated at from 4 to 8 or 9-amperes of *dc* output. Most outboard motors today employ a 12-volt system with the exception of the 4-cylinder *Fageol*, which has 6-volts. Contrary to automotive practice, where different manufacturers use a different ground polarity, the outboard motor people have apparently standardized on using a negative ground.



STOP CB* WITH C-D

*STOP PROFITLESS CALL BACKS by using C-D "BLUE BEAVERS"® The tubular electrolytic that actually improves original factory performance. The built-in extra "factors of safety" insure call-back-free servicing, customer satisfaction and money in your pocket. "BLUE BEAVERS" are made exclusively for the service trade.

SPECIAL! "BLUE BEAVER SERVICE KIT"—a practical assortment of "every day" tubular electrolytics in all-plastic dispenser. You pay only for the capacitors. Ask your distributor salesman to show you the "BLUE BEAVER KIT" or write for details to Dept. RT-67 Cornell-Dubilier Electric Corp., South Plainfield, New Jersey.



stop call backs...insist on
CORNELL-DUBILIER CAPACITORS

SOUTH PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER & CAMBRIDGE, MASS.; PROVIDENCE & HOPE VALLEY, R. I.; INDIANAPOLIS, IND.; SANFORD, FUQUAY SPRINGS & VARINA, N. C.; VENICE, CALIF.; & SUB.: THE RADIART CORP., CLEVELAND, O.; CORNELL-DUBILIER ELECTRIC INTERNATIONAL, N. Y.

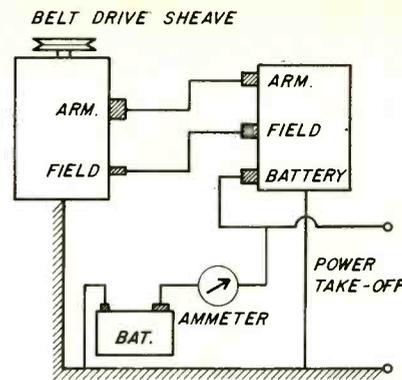


Fig. 5—Charging system used by Evinrude and Johnson motors.

Complete Electrical Systems

Details of the complete *Evinrude* battery and charging system are shown in Fig. 7. *Johnson* motors also use the same circuit. These motors have separate under-the-flywheel magnetos for ignition, which are not shown in this diagram. Although power-take-off terminals are supplied on the junction box, it should be noted that the current to these terminals passes through a rather lengthy cable up to the ammeter, and back to the battery. High-current or voltage-sensitive devices, such as a radiotelephone, might not be expected to do their best if connected to these terminals, especially where an additional long run of wire must be used to connect to the set. However, these terminals are convenient for connecting up any non-critical load circuits. In oper-

ating a radiotelephone, less voltage drop will be experienced if the telephone power circuits are connected to the solenoid switch "hot" terminal and the grounding stud, or bolt, on the motor. These connections are preferable to connecting to the battery directly, where wires might possibly become reversed, causing damage to the boat and/or equipment, and where they would possibly deteriorate from any stray acid.

Figure 8 shows the circuit used in the 4-cylinder *Fageol* outboard motor. Note here that battery, coil, and distributor type ignition is used, while the battery charger is an under-the-flywheel alternator and a rectifier.

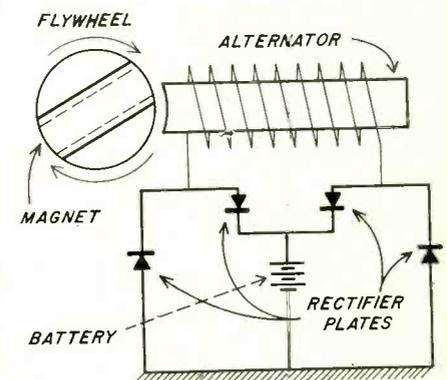


Fig. 6—Charging system used on Scott-Atwater, Mercury, and others.

The circuit of the *Mercury* "Mark 75" 6-cylinder motor is shown in Fig. 9. This motor uses battery, coil, and distributor-type ignition, but with a varia-

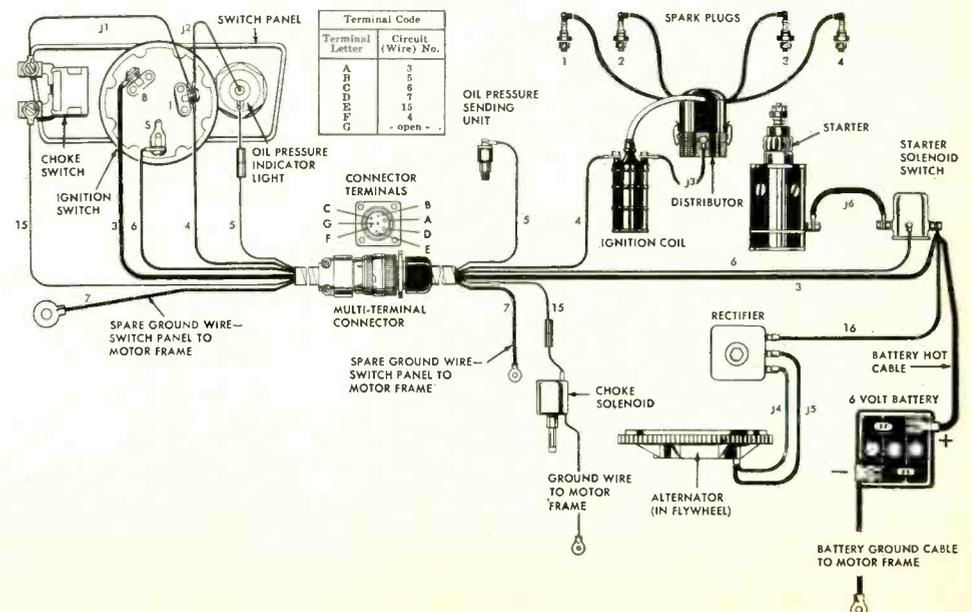


Fig. 8—Wiring diagram for the 4-cylinder *Fageol* outboard motor.

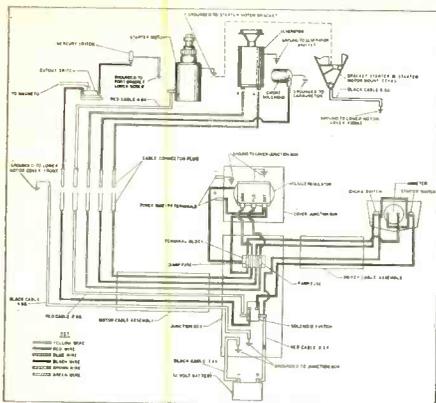


Fig. 7—Wiring diagram of the Johnson and Evinrude electrical systems.

tion from usual practice, in that two coils and sets of points are used. This is due to the fact that at its rated operating speed of 5800-rpm., a single coil and set of points would be called upon to deliver 580 sparks per-second to feed the 6 cylinders—too much to expect. So the job is therefore given to two separate coils and sets of points which fire alternately. A single distributor routes the output from both coils to the cylinders in firing sequence.

The battery-charging system uses an under-the-flywheel alternator and an ex-

ternal rectifier, bridge-connected, giving full-wave rectified *ac* to the 12-volt battery.

The starting circuit of the Mercury "Mark 75" is also a little out of the ordinary. This is due to the fact that "Mark 75" has no reverse gears. Instead, the motor itself is designed to run either backward or forward at the will of the operator. So, naturally, the starter motor must be able to run in either direction to start the engine going ahead or going astern. To accomplish this, a special generator is required with ahead and astern connections which are fed current by one of two solenoids, actuated by switches in the operator's control handle.

The Mercury people recommend the connection of external circuits directly to the battery terminals.

Figure 10 shows the under-the-flywheel circuits of the Oliver ignition and alternator system. One coil with two pairs of "point" contacts is used to supply primary current to either of the two external high-tension coils in sequence. Additional under-the-flywheel coils generate alternating current which is fed to the external selenium rectifier.

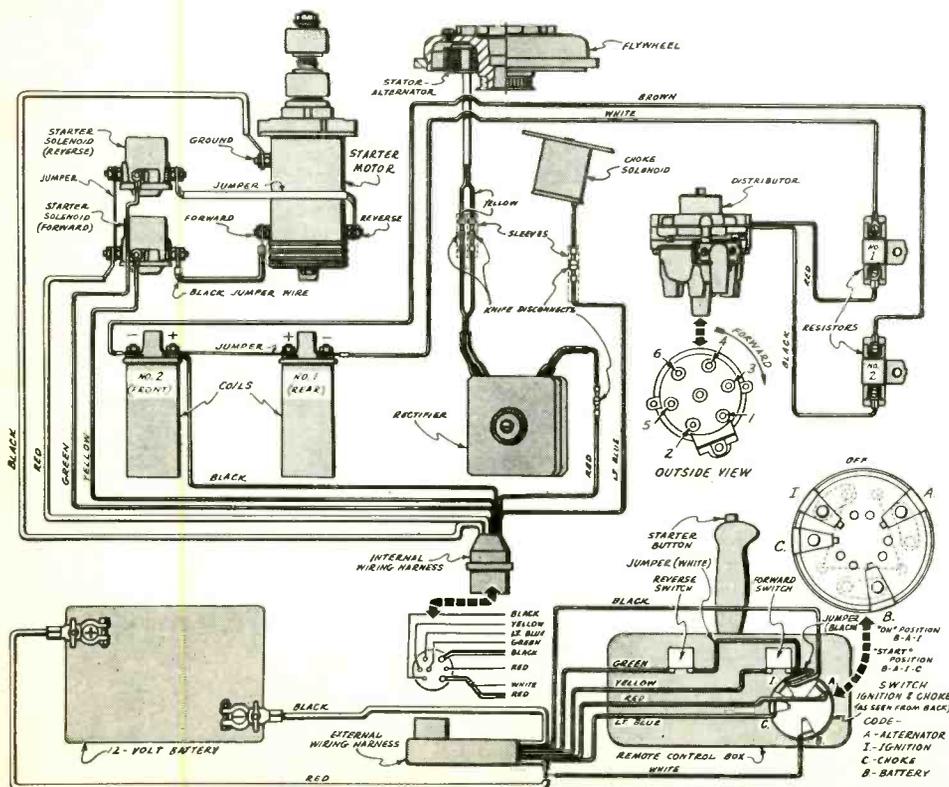


Fig. 9—Electrical system of the Mercury, "Mark 75" 6-cylinder motor.

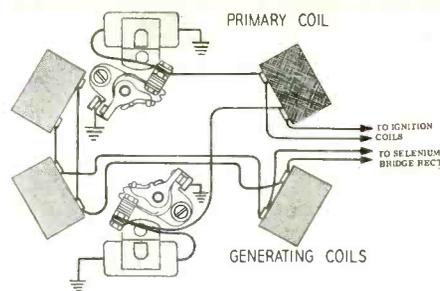


Fig. 10—A single coil and two sets of points are used in this system.

Installation of Accessories

In installing electronic gear on out-board boats, the same cautions regarding current consumption that apply to inboard boats should be followed. Since power availability from the battery charger may range from an approximate low of about 24 watts for one motor to 120 watts for others, care should be taken before selling or attempting to

[Continued on page 31]

Make August Your BIG Phono And Recorder Fix-It Month!

PHONO & RECORDER DRIVE KIT

Specially Priced
For A Limited
Time!

**CONTAINS 9 DRIVES
TO SERVICE ALL RCA
MODEL PHONOGRAPHS
AND RECORDERS**

Pick up extra work... extra
sales... during the summertime
TV lull... by repairing your
customers' phonographs, record
players, tape and wire re-
corders. Exact factory replace-
ments in clear plastic storage
box. Buy now while you save!

P-500 KIT

SPECIAL THIS MONTH

ONLY \$6³⁹

DEALER
NET

SEE YOUR G-C JOBBER NOW!

GENERAL CEMENT MFG. CO.

Division of Textron Inc.

400 South Wyman Street
Rockford, Illinois

FOR HOUSE CALLS

— it's

HEXA CON

FEATHERWEIGHT

INSTANT SOLDER GUN

FITS TUBE CADDY—Takes Half
the Space of Transformer Guns

SMALLEST SOLDER GUN
WEIGHS ONLY 8 OUNCES

— but

POWER-PACKED AT 150 WATTS
and

SOLDERS IN SECONDS


No heavy bulky transformer —
sturdy lifetime tip—never wears or
bends—effective spotlight

Model G14 with ¼" tip — \$7.95
Order from your distributor today

HEXA CON ELECTRIC COMPANY

593 W. CLAY AVE., ROSELLE PARK, N. J.

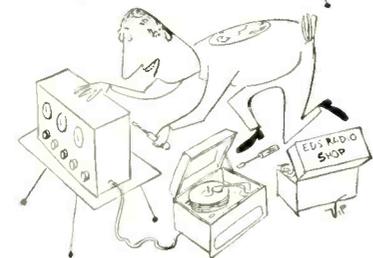SERVING INDUSTRY AND CRAFTSMEN
FOR A QUARTER OF A CENTURY



"There's nothing wrong with
you, doctor, that a new
JENSEN NEEDLE
won't fix up."

THE WORK BENCH

Service Problems And Their Solutions

by **PAUL GOLDBERG**
Service Manager

THE following are a few odd troubles that occur in television receivers. Methodical trouble shooting is of the utmost importance in solving these problems.

Philco RF 41-D-1

The receiver was turned on and it was observed that there was insufficient vertical size. The vertical oscillator, ½ 7N7, and vertical output tube were replaced individually but had no effect. The diagram was then studied. This receiver utilizes ½ the 7N7 as an ordinary blocking oscillator. The vertical output section uses a 6BQ6. This tube is normally used in a horizontal output stage and its characteristics prevent the use of a cathode vertical linearity control. Thus you will note the vertical linearity control is located in the grid circuit of the 6BQ6. The screen voltage required for this tube in this circuit is somewhere around 85 volts. Thus we see the use of resistors R709 and R708 in a voltage dividing network. Knowing these facts, voltage checks were made at

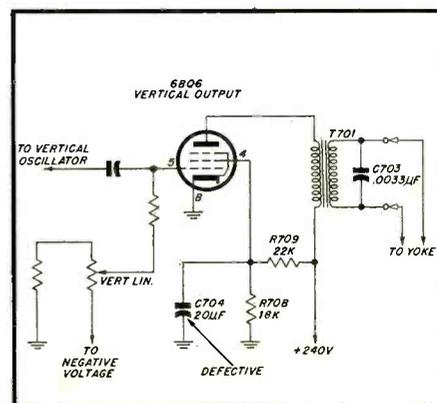


Fig. 1—Open condenser caused reduced height in Philco RF-D-1.

the plate and screen of the 6BQ6, but the voltages were found to be about the correct value. The vertical linearity of the picture seemed normal so we eliminated the possibility of a leaky coupling condenser. Condenser C703 across the secondary of the vertical output transformer was checked for leakage but was found to be satisfactory. Resistors R819, R818, R702 and the height control R706 were all checked for value and found to be correct. Before going so far as to replace the vertical output transformer or the yoke, filter condenser C704 was bridged with a new filter. When C704, the screen bypass condenser was bridged, the height became normal. The defective C704, 20 mf, was then replaced with a new 20 mf, filter. The receiver then functioned properly.

When the defective capacitor was checked it was found to be open. This open bypass condenser caused the screen grid to act in a degenerative fashion, thus lowering the output current of the 6BQ6.

DuMont RA-112

The receiver was turned on and it was seen that the video was very weak and on some stations was barely visible. The sound however, was satisfactory. The diagram was then studied and it was observed that the sound was taken off at the plate of the second video *if*, V206. Thus, because the sound was normal we eliminated the possibility of trouble in the tuner or first and second video *if* circuits. The third video *if* tube V207, fourth video *if* tube V208, video detector V209A, 6AL5, and the video amplifier, V210, 6AC7, were all replaced individually but had no effect. The scope was set up and a wave form check was

made at the plate of V210, 6AC7, the video amplifier. The signal was much too weak and barely distinguishable. The signal was also weak at the grid of V210 and at the diode plate of V209A. Next, voltage checks were made at the plate, screen, and cathode of V207, 6BA6 and V208, 6BC5 and found to be approximately correct. The ohm-meter was next set up and resistance checks were made, starting at the plate of the video detector circuit V209A. The peaking coils L219, L205, L201, and L203 were all measured and checked correctly. A resistance check was next made from pin 7 of V209A to ground. Here the ohm-meter measured about 6 ohms to ground. This was the trouble. The circuitry was examined and C220, 2.5 mmf. was clipped off its ground connection. When this was done the ohm-meter no longer measured 6 ohms to ground, but now measured 3900 ohms to ground which was correct. When the shorted C220 was removed and a new 2.5 mmf. was installed the receiver then functioned properly. ■ ■

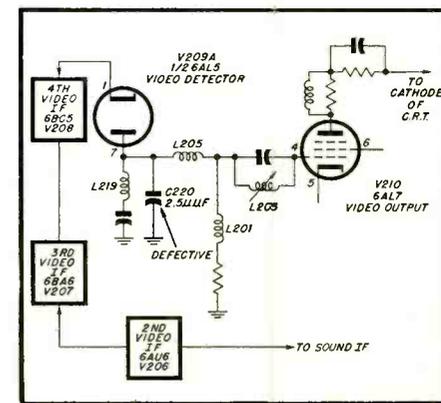


Fig. 2—A weak picture in this DuMont was caused by short in C220.

YOUR AEROVOX
TV
ELECTROLYTIC
CAPACITOR
REPLACEMENTS



**TYPE AFH (85°C)
TWIST-PRONG
ELECTROLYTICS...**

the most complete line in the industry, more exact-duplicate replacements than anyone else. All AFH units offer improved hermetic-sealing, sturdy terminals and mounting prongs; hi-purity aluminum foil construction throughout.



**TYPE PRS (85°C)
TUBULAR
ELECTROLYTICS...**

compact capacitors in aluminum cans with cardboard insulating sleeves. Available in a complete selection of singles, duals, triples and multiples. Insulated, stranded copper wire leads standards on all units.



**TYPE PR WAX-
FILLED TUBULAR
ELECTROLYTICS...**

popular and economical units in cardboard tubes manufactured to the same high standards as more expensive metal-cased types. These are exact-duplicate replacements for TV receivers and antenna rotating devices.



**TYPE SRE
"BANTAM"
ELECTROLYTICS...**

small in size but big in performance. Hermetically sealed in aluminum cans and furnished with cardboard insulating sleeves. Perfect for limited space assemblies and miniaturized low voltage circuits.

All these popular Aerovox TV electrolytic capacitors are always carried in stock by your local Aerovox Distributor. Ask him for your free copy of the complete Catalog with detailed listings and information on all Aerovox components.



AEROVOX CORPORATION

**DISTRIBUTOR SALES DIVISION
NEW BEDFORD, MASS.**

In Canada: AEROVOX CANADA LTD., Hamilton, Ont.
Export: Ad Auriemo, Inc., 89 Broad St., New York, N. Y.
Cable: Auriemo, N. Y.

Mfr: CBS Chassis No. 1601/1602


Card No: CBS 1601-1

Section Affected: Sync.

Symptoms: Horizontal pulling. Unstable horizontal hold.

Cause: Leaky C7-1.

What To Do:
Replace C7-1, .022 mf.

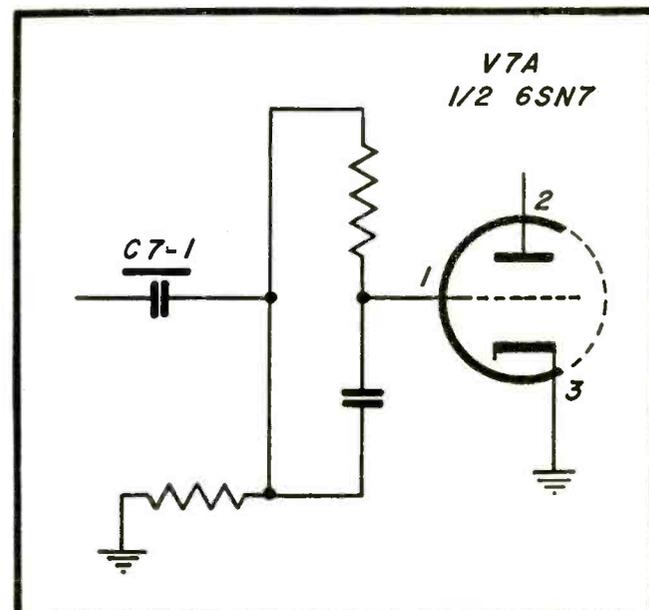

Mfr: CBS Chassis No. 1601/1602


Card No: CBS 1601-2

Section Affected: Sound

Symptoms: Sound buzz.

Cause: Shorted winding in L5-2.

What To Do:
Replace L5-2.

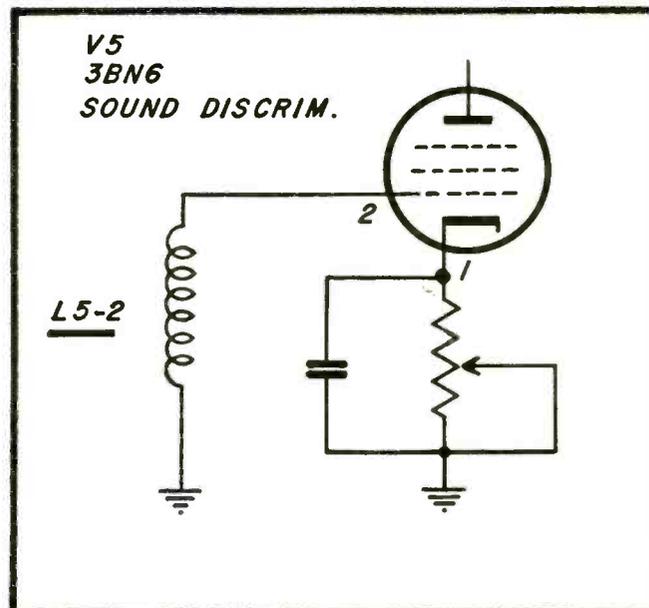

Mfr: CBS Chassis No. 1601/1602


Card No: CBS 1601-3


Section Affected: Raster

Symptoms: Lack of width. Blooming.

Reason For Change: Circuit improvement.

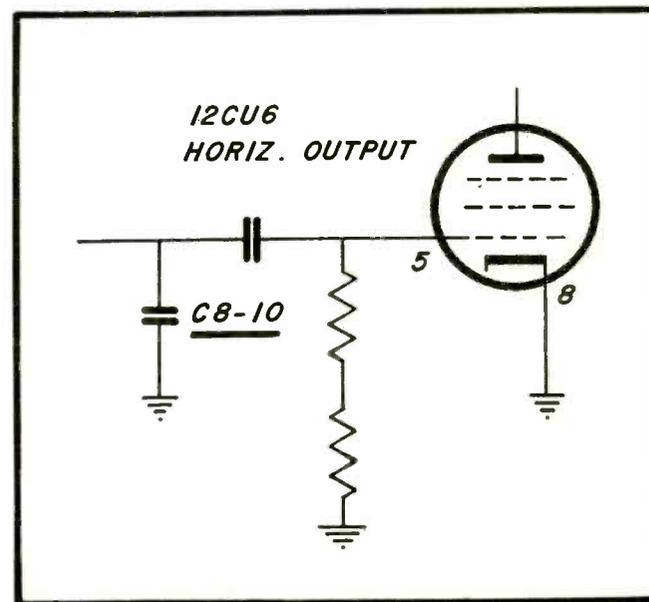What To Do:
Change: C8-10 (1500 mmf) to 1200 mmf.



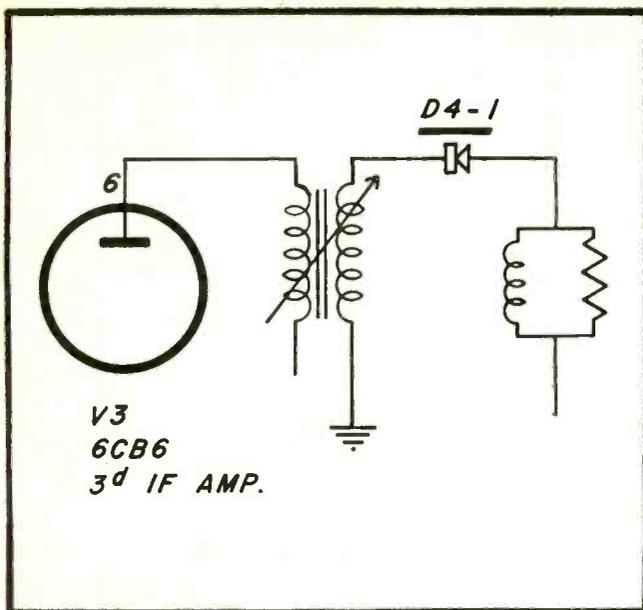

Mfr: CBS

Chassis No. 1601/1602

Card No: CBS 1601-4


Section Affected: Sync.

Symptoms: Horizontal pulling at low contrast levels.

Cause: Defective video detector crystal.

What To Do:

Replace D4-1 1N64.

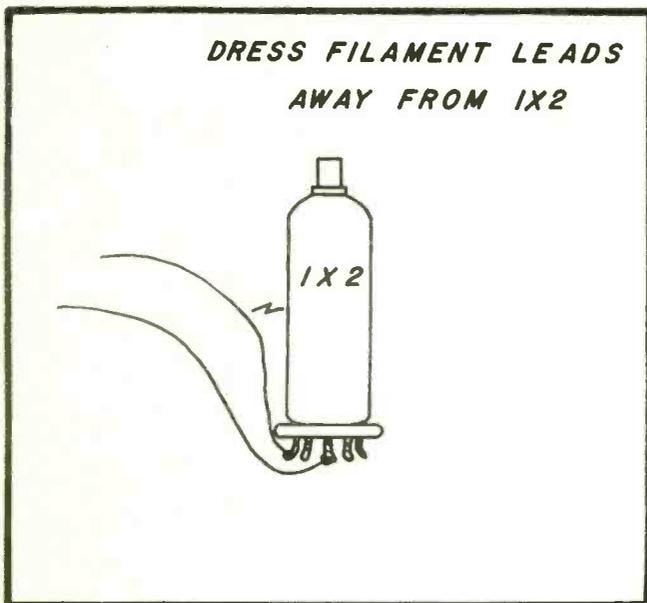

Mfr: CBS

Chassis No. 1601/1602

Card No: CBS 1601-5


Section Affected: High Voltage.

Symptoms: No high voltage. Repeated failure of 1X2B due to arcing.

Reason For Change: Circuit improvement.

What To Do:

Dress filament leads away from 1X2.

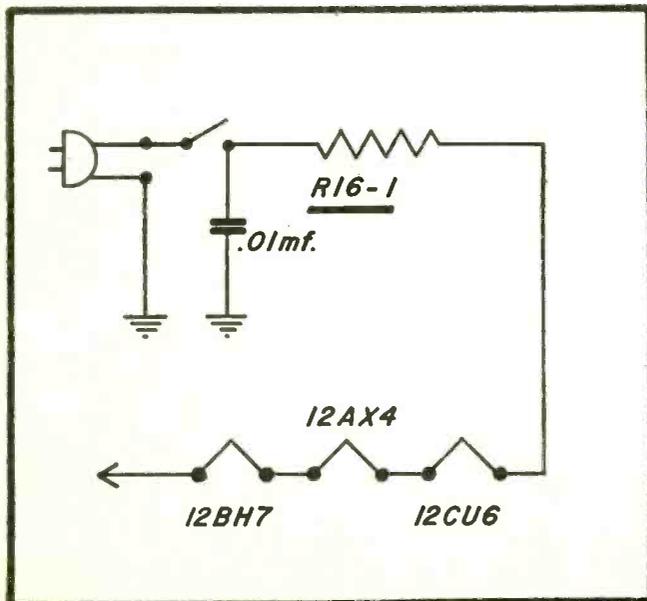

Mfr: CBS

Chassis No. 1601/1602

Card No: CBS 1601-6

Section Affected: Raster

Symptoms: Lack of width. Pix blooming.

Cause: R16-1 has changed value changing filament voltage of 12CU6 horizontal output.

What To Do:

Replace R16-1; 46 ohms, 25W.

Antenna TOWERS

for TV-AMATEURS
COMMUNICATIONS

... from Aermotor Company—since 1888 leaders in the manufacture of Steel Windmill Towers.

Check these features—they're found in all Aermotor Towers.

SELF SUPPORTING — no cumbersome guy wires.

HEAVILY GALVANIZED AFTER FABRICATION—completely protected against rust.

EASILY ASSEMBLED

STRONG—towers safely sustain loads of 1500 lbs.—safe in winds to 85MPH.



TYPE MI-98

For TV Antenna up to 6 square feet of projected area. Heights to 100'.

TYPE MP-5

For Amateur Beams up to 20 square feet of projected area. Heights to 97'3".

TYPE MP-9


(Not illustrated)
Meets "RETMA" Standard TR-116 Specifications. Heights to 123'5".

Write today for complete information on Aermotor Steel Antenna Towers and an Aermotor Franchise in your territory.

AERMOTOR COMPANY

2500 W. Roosevelt Road Chicago 8, Illinois

Dept. ES-8

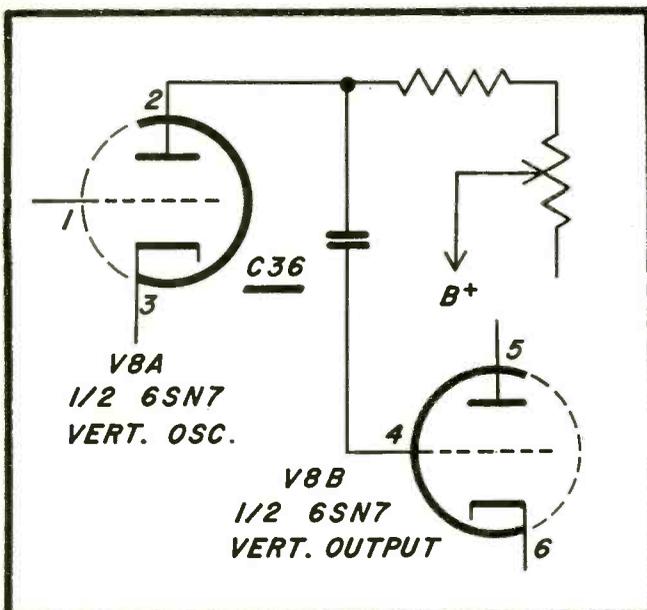

Mfr: Firestone

Model No. 13-G-168


Card No: F13G-168-4

Section Affected: Raster

Symptoms: Poor vertical linearity. Fold over at bottom.

Cause: Leaky or shorted C36.

What To Do:
Replace C36, .1 mf.

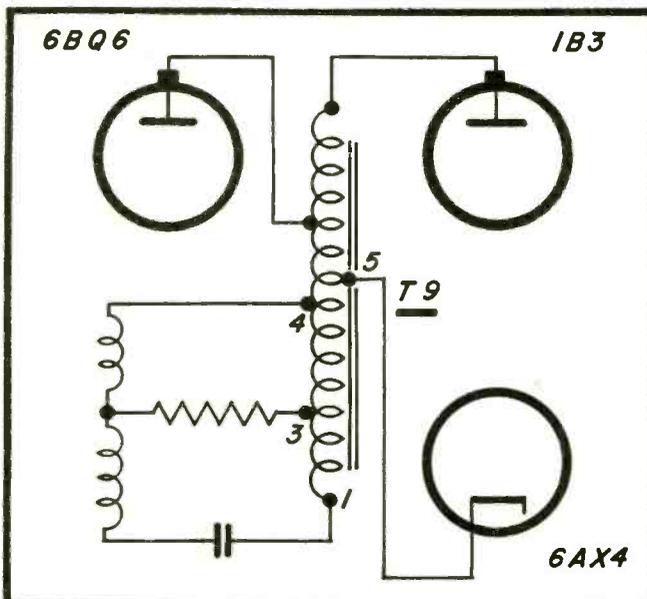

Mfr: Firestone

Model No. 13-G-168


Card No: F13G-168-5

Section Affected: Raster

Symptoms: No raster—6AX4 overheating.

Cause: Shorted flyback transformer, T9.

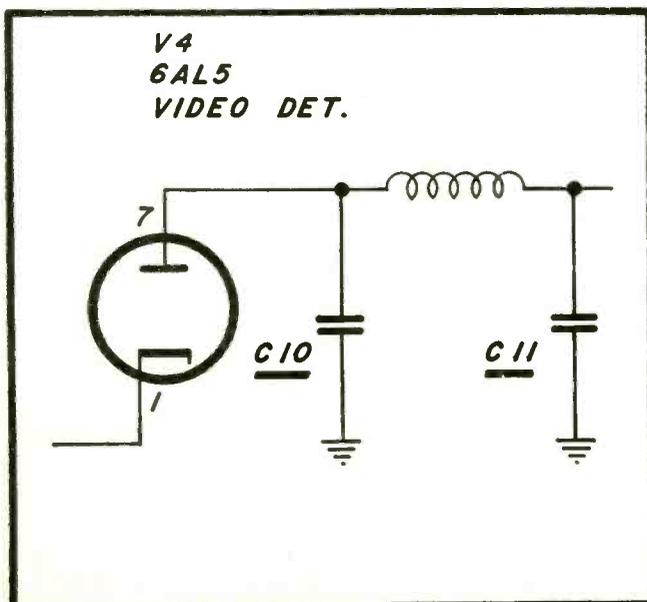What To Do:
Check terminals #1, 3, 4 and 5 of transformer T9 for low resistance to chassis. Replace T9 if defective.



Mfr: Firestone

Model No. 13-G-168

Card No: F13G-168-6

Section Affected: Pix.

Symptoms: Poor resolution.

Cause: Leaky C10 and C11.

What To Do:
Replace C10 and C11, 5mmf each.

OHMITE®

DEPENDABLE RESISTANCE UNITS

INSURE quality replacement
BUILD customer satisfaction.
INCREASE your industrial
and home electronic
servicing business



AXIAL-LEAD RESISTORS

Vitreous-enameled, power-type units designed to withstand high temperatures.



Be Right with

OHMITE®

OHMITE MANUFACTURING CO.

3640 Howard Street, Skokie, Illinois

PRODUCTION LINE FUGITIVES

[from page 7]

Some manufacturers use a 50-50 ratio and one in particular uses a 70-30 ratio, but with the latter the hold and lock-in is quite critical.

The following troubles are less specific and are most often intermittent so far as set operation is concerned.

Philco C-1. Deflection Chassis Using 7N7 Final Sync & Vertical Oscillator

Several of these sets were found with unsoldered connections on the 7N7 tube socket, and on one set the only leads soldered were the filament leads. The result was intermittent sync or vertical deflection. One or the other would cease to operate with the slightest tapping of chassis.

Teleking—Extremely Sensitive to Tapping

Visual inspection revealed a seven lug terminal strip with about fifteen wires connected to it, and not a drop of solder on any of the lugs.

GE "K" Line—Intermittent Video

This set using the component board assembly common to GE had fading video. It was found that if the board

containing the video components was pressed slightly, the pix would come and go. A close examination of all connections on and to the board revealed nothing, but after sweat soldering the entire board the trouble cleared. The component board consists of a fiber board with hollow rivets through it. The component leads are inserted in the rivets and the entire assembly is dip soldered, thus the solder to each lead is not visible to inspection.

One other set with a built-in fault was an RCA 12 inch picture tube set. The customer had purchased the third picture tube for this set in less than four years. Now with the new tube no raster was obtainable. Voltage checks to the picture tube socket showed the tube to be biased beyond cutoff, and a wiring check turned up a resin joint in the brightness control wiring.

This discussion of factory made faults does not include the faults of circuitry in receivers which operate improperly in the field, and for which circuit changes were recommended. It is suggested however when a stubborn fault is encountered, that a review of factory notes be made, to discover if subsequent changes are recommended to cure these faults. ■■

SERVICING INTERMITTENTS

[from page 9]

the lead is connected to the coil. A slight pull on the lead may cause the faulty condition to develop. Trouble within *if* cans is especially annoying and deceptive. When an *if* appears defective, double-check your conclusions by means of voltage or resistance measurements. In fact, *any* apparently defective part should be double-checked because false conclusions are common when the trouble is an intermittent.

It is often possible to repair a defective coil or transformer, if the break can be seen and is accessible. A delicate and patient touch is required. Clean the insulation off the coil wire where it is to be soldered. Use a small soldering


iron. Where necessary, secure the wire with tape to prevent pulling at a vulnerable point.

Miscellaneous Troubles


A cold soldered connection often causes intermittent operation (as well as permanent failure). The connection may appear to be properly soldered, yet may be held together through the adhesive property of rosin, making only mechanical contact. It is often necessary to resolder many connections, all of which appear normal, to resolder the cold connection causing trouble.

A tube, loose in its socket, can cause intermittent receiver failure. The holes,

There
is a
faster
way

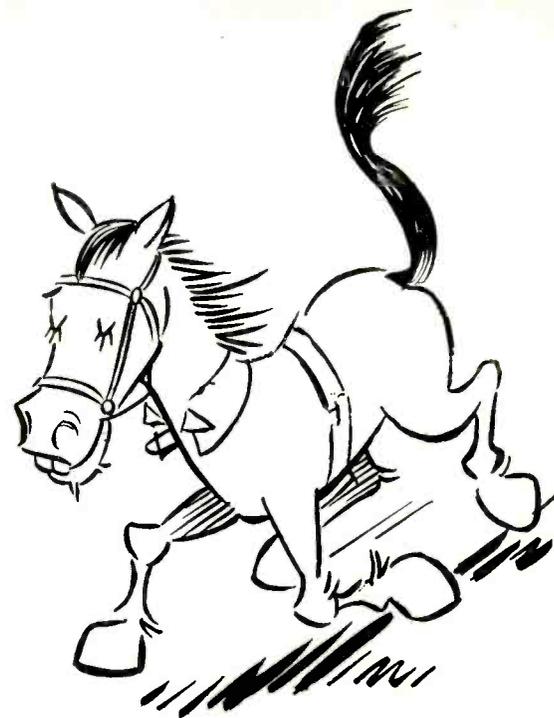

to **SPEED SERVICING!**

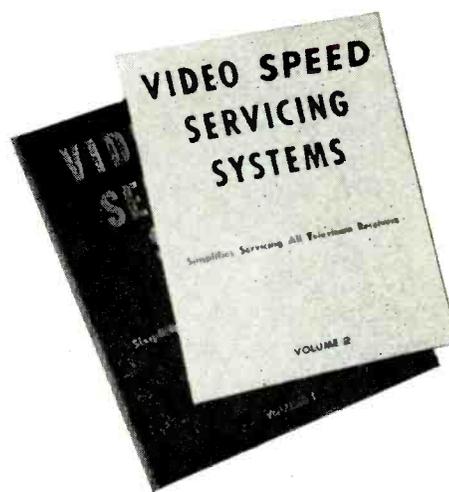

Time is money to servicemen. Thousands of servicemen who have bought Vol. 1 VSSS report that it is a time-saver which helps them pinpoint their trouble-shooting so they can service sets more efficiently.

A compilation of specific receiver service repairs, "bugs," chronic troubles, field circuit changes, manufacturers' production revisions, etc. The compilation enables the service technician to pinpoint what is wrong with any given TV set and to correct the fault in the shortest possible time.

Video Speed Service Systems is guaranteed to simplify servicing all TV sets. Contains over 600 service items representing over 2500 of the most serviced TV models now in use. Over 25 different manufacturers' lines are covered.

CUT OUT AND MAIL

COWAN PUBLISHING CORP., 300 WEST 43rd STREET, NEW YORK 36, N. Y.

Please send me postpaid Video Speed Servicing Systems

Vol. 1 in Paper Bound Edition for \$2.95

Vol. 1 in Hard Cover Ring-Binder Edition for \$4.95

Vol. 2 in Paper Bound Edition for \$2.95

My Check for \$..... is enclosed.

Name.....

Address.....

City..... Zone..... State.....

8 NEW



PRODUCTS

... just a few of the many new B-T precision engineered products



FIELD STRENGTH METER Model FSM-1

A portable precision instrument for accurate measurement of RF signals. Continuous tuning from 54 mc to 216 mc covering VHF-TV, FM, mobile, aircraft, ham, industrial and CD. Use of B-T UHF converter extends range to entire UHF band. **\$310 net**



3 MASTERLINE CRYSTAL-CONTROLLED CONVERTERS

Model MVC: Hi-to-Lo channel VHF converter.

Model MLC: Lo-to-Lo channel VHF converter.

Model MUC: UHF to VHF converter.

Extremely stable, self-powered with two matched 75 ohm outputs. All channel VHF mixing network. Flat within 1/2 db over full 6 mc output. For color and black and white TV.

4 INDOOR TV SYSTEM TAPOFFS

Easy to install, matched low cost tapoffs

Model TO1-75: single isolated tapoff for recessed mounting. For RG-11/U or RG-59/U, with 75 ohm jack.

Model TO1-300: has 300 ohm terminals.

Model TO2-75: two 75 ohm outlets from RG-11/U or RG-59/U cable. List \$9.00

Model TO2-300: two 300 ohm isolated outlets from RG-11/U or RG-59/U cable.

sold by electronic parts distributors for further information use coupon below

BLONDER-TONGUE LABS, INC. SD-8
9-25 Alling Street, Newark 2, N. J.

Please send me literature covering:

Field Strength Meter Masterline Converters
 Indoor TV System Tapoffs

Name.....

Address.....

City..... Zone..... State.....

in which the tube prongs fit, may be too large, causing poor contact. Or the holes or tube prongs may be tarnished.

Tarnished switch contacts, or worn contacts, are a frequent cause of trouble. Recurrent trouble may be due to a poor ground through a rivet or screw. When a wire or part is grounded with a rivet or screw, paint or corrosion may cause trouble, although the connection appears proper.

In the home, a defective antenna lead-in (corrosion at the antenna, at the lead-in point of entrance into the house, or a broken lead-in), or a badly rusted or corroded antenna, are common causes of intermittent TV operation, breaking down of the picture and sound, and recurrent loss of sync. If rabbit-ears are substituted for the antenna, to check this type of trouble, sync troubles may persist due to a weak signal being picked up by the rabbit-ears. This fact should be kept in mind, to prevent false conclusions; the sync

may be normal when a good outdoor antenna and good lead-in are provided.

Conclusion

Few servicemen enjoy fixing intermittents. Such repairs are often exasperating and unprofitable, yet necessary to maintain customer good will. It is a good idea to make a note of information on intermittent conditions likely to develop in certain receivers, and the part likely to be defective. Such information is found in *Video Speed Servicing Systems Data Sheets*, published in each issue of *ELECTRONIC SERVICING*. New data sheets are published monthly. Systematic study of this data will enable you to fix intermittents, as well as other troubles, more quickly and more profitably.

Servicing intermittents, and other types of elusive troubles, requires a great deal of knowledge and considerable patience. ■ ■

HORIZONTAL RETRACE BLANKING

[from page 5]

horizontal retrace a negative pulse developed across $C83$ is applied to the first anode of the CRT to cancel the B plus applied through $R35$ thus accomplishing blanking.

The Olympic 21CV16 employs the circuit shown in Fig. 7. This circuit makes use of a resistive type voltage divider. Resistors $R80$ and $R35$ act as the voltage divider to reduce the intensity of the pulse taken from the flyback while $C66$ is a blocking condenser that prevents the B plus from reaching the control grid of the CRT. The negative pulses coupled through $C66$ cut the CRT off during retrace. Notice that the vertical blanking pulse is also fed to the control grid.

If a set exhibits the need for horizontal retrace blanking any of these circuits may be used. The circuit selected should be the one most easily adapted to the set. That of Fig. 5 is the least practical since it requires the addition of a triode. The circuits shown in Figs. 6 and 7 are more practical since they require only a few additional components and slight circuit modification. A simple horizontal blanking circuit suitable for most sets is shown in Fig. 8. Re-

sistors $R1$ and $R2$ are connected across the deflection yoke. The first anode is connected to the mid-point of the two resistors. The voltage at this point contains the negative pulse which occurs during retrace. The pulse voltage applied to the first anode may be controlled by varying the value of $R2$. A good starting value is about 330,000 ohms. As the value of $R2$ is reduced the ac component is lowered and the amount of blanking is reduced. Excessive blanking is indicated by a shadow encroaching upon the left side of the

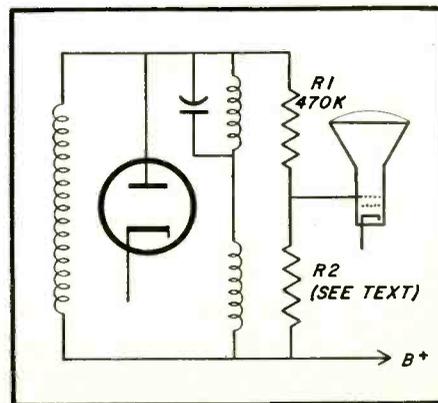




Fig. 8—Simple circuit for providing horizontal retrace blanking pulses.

ALL-CLEAR TV PICTURES

with the new

B-T LABS ANTENNA BOOSTER

(BROADBAND VHF)

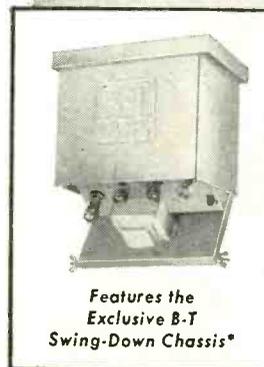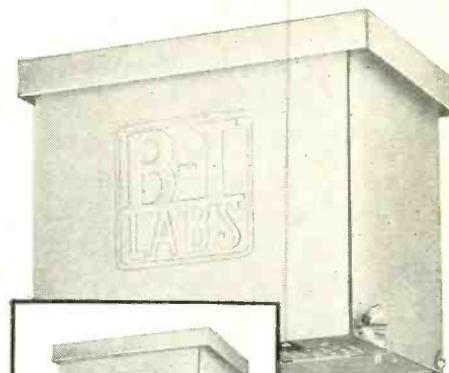

Features the Exclusive B-T Swing-Down Chassis*

MODEL AB

4 TUBES

25DB

GAIN

\$99.50

LIST

WITH

MULTI

VOLTAGE

POWER

SUPPLY

- Low-noise, all-triode circuit
- Easy mast-mounting
- Automatic 'on/off' from set
- 24 and 110v AC available plus step-ups for long-line drop
- Single lead line carries power 'up' and signal 'down'

*For Servicing and Maintenance... chassis swings down - trap door fashion - for easy handling and tube replacements.

For complete details, use this coupon



BLONDER-TONGUE LABORATORIES, INC.
9-25 Alling St., Newark 2, N. J.

Please send complete specs of your new Antenna Booster. I am also interested in:

TV Amplifiers UHF Converters
 Master TV Systems

Name.....

Address.....

City..... Zone..... State.....

Dept. SD-8

picture. $R1$ and $R2$ should be $\frac{1}{2}$ watt resistors.

Service Problems

The service problems that may arise in horizontal blanking circuits are for the most part, routine in nature. There are three major defects which may occur. These are: 1—Loss of raster; 2—Loss of brightness control action; 3—Excessive blanking (shadow on left side of screen).

In the circuit shown in Fig. 5, leakage in $C278$ would impair the action of the brightness control because of the introduction of positive voltage to the control grid. This would cause a constant raster and the CRT could not be cut

off. The circuit shown in Fig. 6 may develop several defects. The raster would be lost if $C83$ shorted, due to the grounding of the first anode. Should $C83$ open, the ac voltage divider action would no longer take place and the full pulse voltage would be applied to the first anode. This would result in excessive blanking and appear as a vertical shadow encroaching upon the extreme left portion of the picture. The circuit of Fig. 7 could produce a problem similar to that mentioned for the circuit shown in Fig. 5. If $C66$ develops leakage, it will reduce the effectiveness of the brightness control, making it progressively less effective as the leakage increases. ■ ■

1957 PHILCO TV

[from page 14]

the remaining trap provides reduction of the associated sound signal at 41.25 mc . The latter is necessary to assure the proper ratio of sound to video carriers for the 4.5 mc intercarrier system.

One stage of video amplification is used, with the output coupled to the CRT cathode. Sound is taken from the output of the video amplifier stage by means of a transformer, whose primary is a 4.5 mc trap in the video output circuit. The sound system contains a sound *if* amplifier (4.5 mc), dynamic limiter, dual crystal-diode discriminator, first audio and audio output stages. Certain chassis of these series contain a duo-diode tube in place of the crystals in the discriminator stage. Composite video from the video amplifier output is coupled to a conventional triode sync-separator stage from which is obtained composite negative-going sync pulses. The *agc* voltage is developed partially in the video detector output circuit and also from the grid current of the sync-separator stage. This voltage is supplied to the tuner and to the first and second *if* stages.

Sweep Circuits

The output of the sync separator feeds both the horizontal and vertical sweep circuits. A duo-triode tube in the vertical section is employed as a modified blocking oscillator and vertical output stage to feed the vertical deflection cir-

cuits. The vertical sync signal is applied to the cathode tap of the autotransformer of the oscillator. The inductive action of the transformer places a high positive overshoot on the sync pulse which by the action of the transformer is applied to the grid of the oscillator for synchronizing purposes. An $R-C$ network from one side of the vertical output transformer to the CRT grid provides vertical retrace suppression.


A phase comparer employing dual selenium diodes controls the frequency of the horizontal oscillator, a cathode-coupled multivibrator. The horizontal output stage, high voltage and deflection circuits are conventional. Horizontal width in this chassis series is obtained by a width link in the screen circuit of the horizontal output tube. The width link shorts out a portion of the voltage divider network in the screen circuit to provide width variation. On 24-inch models the width link is replaced by a width coil.

Power Supply

The transformer-operated power supply provides full-wave rectification. The transformer contains a 12 volt center tapped winding. Filament supply voltages are obtained from the center tap to either side of the winding. The entire 12 volt winding is used to power the stepper motor for the automatic tuner system.

FREE by subscribing to **ELECTRONIC SERVICING** now on this special order form you will get **FREE!** **FREE**

96 PAGE TV SCHEMATIC PACKET

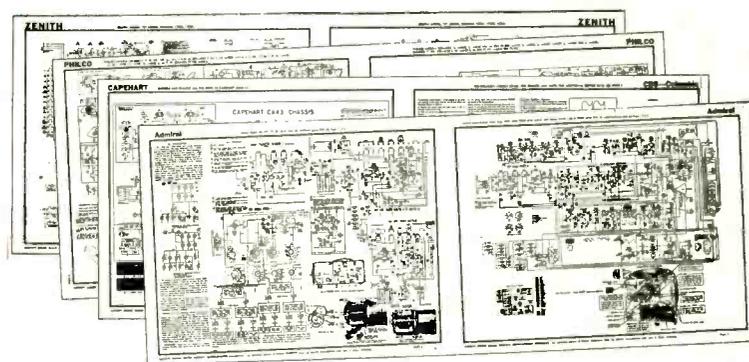

You get 16 more pages of new schematics in every issue

Every issue of **ELECTRONIC SERVICING** now carries 16 pages of new TV schematics. Many of these will not be available from any other source for months. Each schematic is crystal clear and accurate — (prepared by John F. Rider) — ready for immediate use and easy filing for future reference. The schematics include Alignment Data, Waveforms, Operating Voltages, Tube Location Guide, Essential Parts Numbers, etc.

In addition you'll get 4 more new pages of VIDEO SPEED SERVICING SYSTEMS Data Sheets in each issue

HURRY . . . HURRY . . . This Special Offer Good Only While The Present Supply of Schematic Packets Last

— — — **TEAR OFF — MAIL TODAY — GET YOUR FREE 96-PAGE TV SCHEMATIC PACKET FREE!** — — —

ELECTRONIC SERVICING, 300 W. 43rd St., New York 36, N. Y.

I accept your **FREE OFFER . . .** a complete **96 PAGE TV SCHEMATIC PACKET** together with a 2-year subscription to **Electronic Servicing**. Here is my **\$5.00**

CHECK YOUR CLASSIFICATION

- | | |
|---|---------------------------------------|
| <input type="checkbox"/> Independent Radio-TV Serviceman | <input type="checkbox"/> Owner |
| <input type="checkbox"/> Radio-TV Service Organization | <input type="checkbox"/> Employee |
| <input type="checkbox"/> Retail Store having Service Department | <input type="checkbox"/> Service Mgr. |
| <input type="checkbox"/> Industrial Electronic Service Firm | <input type="checkbox"/> Student |
| <input checked="" type="checkbox"/> Firm having electronic equipment which I service and maintain | |

If some other type of company describe: _____

- Check if New Subscriber
 Check if this is to renew or extend your present subscription when it expires

(Please Print)

Name _____

Address _____

City _____ Zone _____ State _____

Name of firm _____

Firm's business address _____

City _____ Zone _____ State _____

SPRAY it or DROP it



the NEW
**QUIETROLE
Spray-Pack**

or the
QUIETROLE
Bottle with the
Eye Dropper Cap

Now QUIETROLE offers you both types of containers. Either way assures you of the same unfailing results that QUIETROLE is known for.

Make your next purchase QUIETROLE, get both and learn the difference between quality and poor substitutes. QUIETROLE is the original product of its kind, it is a FIRST of the industry and you can depend on it to end your noisy control and switch troubles.



manufactured by
**QUIETROLE
COMPANY**
Spartanburg, South Carolina



Pat. No.
2757316

RESTORES PICTURE TO DEFECTIVE
PICTURE TUBE OF ANY TV SET —

Model K-101
\$550
List Price



LOCATES AND CORRECTS FOR

- Open Cathode
- Heater-Cathode Short
- Open Control Grid
- Control Grid-Cathode Short
- Low Emission
- Combinations of above

Perma-Power COMPANY
3100 N. ELSTON AVE. • CHICAGO 18, ILLINOIS
There's Always Something NEW Being Developed by Perma-Power

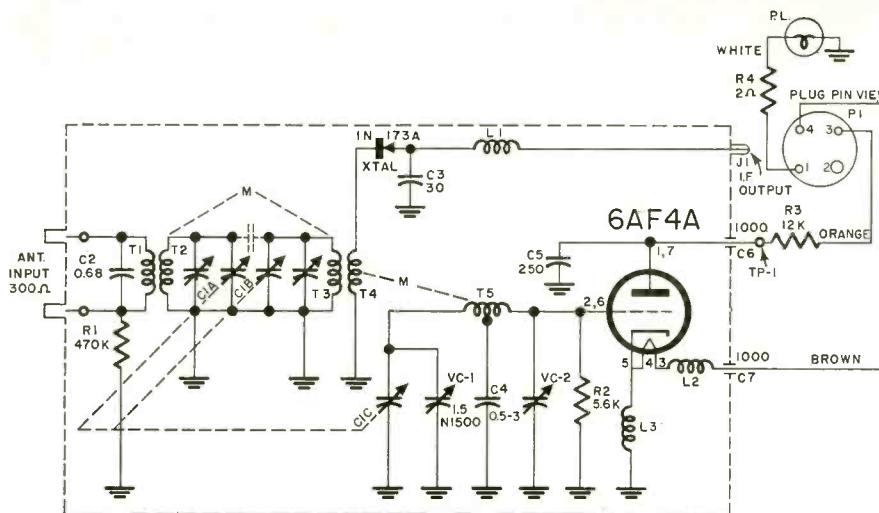


Fig. 8—Schematic of the Model UT-27 *uhf* tuner. This tuner is used in the chassis of the 7L40 series and tunes through all *uhf* channels.

UHF Tuner

The *uhf* tuner used in the chassis of the 7L40 series is the UT-27. This unit tunes through all *uhf* channels. It contains a *vhf-uhf* change-over switch which provides power to the unit and connects the unit into the *vhf* tuner circuit. It is also provided with a jack and a test point for operational checks.

The circuit of the tuner is illustrated in Fig. 9. The incoming *uhf* signal is coupled through a 300 ohm antenna input line to the antenna coupling inductor, *T1*, and transferred to the antenna tank circuit. Mutual coupling of *T2* and *T3* with the stray capacitances existing in the tank assemblies couples the signal to the mixer tank *T4*. A 6AF4 tube is used in the oscillator circuit, the output of which is coupled by mutual inductance of *T4* and *T5* to the mixer circuit which employs a 1N173A crystal. The output of the mixer, a 45.75 *mc* video *if* carrier signal, is coupled by coaxial cable to the *uhf* input of the *vhf* tuner.

In *uhf* position, the local oscillator in the *vhf* tuner is inoperative due to the switching arrangement and the *rf* amplifier and the mixer of the *vhf* tuner operate as *if* amplifiers.

The purpose of the antenna and mixer tank circuits is to pass only frequencies of desired incoming signals (selectivity) and to prevent possible feedback of the oscillator signal to the antenna where radiation might cause possible interference with other receivers.

The mechanical coupling arrangement of the UT-27 tuning assembly permits fast tuning of a desired *uhf* channel along with vernier tuning for precise adjustment of the *uhf* channel. An antenna crossover network panel is available with these tuners for *uhf* and *vhf* signal reception with single antenna lead-in. The crossover panel provides a high-pass filter to the input of the *uhf* tuner adapter for *uhf* signals and a low-pass filter to the *vhf* tuner on *vhf* signals, thus isolating the inputs of both tuners one from the other.

UHF Tuner-Adapter Operational Check

The operation of the crystal mixer stage can be checked by connecting a milliammeter, with a *dc* resistance of 25 ohms or less, from the crystal output test point, J1 of Fig. 9, to ground. The current should be within 0.5 to 5.0 *ma*. Should the crystal be found defective, it is easily accessible for replacement. A test lug is available on the tuner to check the oscillator plate voltage. This test point is TP-1 in Fig. 8 at which point the voltage should be approximately 60 volts to ground.

Replacement of the *uhf* oscillator tube may cause a detuning affect. To avoid the necessity of realigning the unit, a number of tubes may be tried until the most satisfactory substitute for the original is found.

[To be continued]



LINE VOLTAGE ADJUSTORS



Anchor
Model LA 350

Gives
Instant
4-Way
Selection

- 10 Volt Boost
 - 10 Volt Down
 - Normal Line Voltage
 - Current Off
- Model LA 350 List Price Only \$6.75

Model LA 300, economy unit, provides:
10-Volt Boost • Normal Line Voltage.
List Price Only \$6.25

BOTH MODELS ARE 300 WATT AND
OF HEAVY DUTY CONSTRUCTION.
AT YOUR DISTRIBUTOR

anchor products co.
ELECTRONIC COMPONENTS
2712 W. Montrose • Chicago 18, Ill.

the **ALL NEW**
SENCORE
Align-O-Pak
TV
BIAS SUPPLY

Another
Sencore
Time-
Saver

For
BLACK and WHITE
and **COLOR**

Just Dial any DC Voltage from 0 to 18 volts positive or negative—For AGC trouble shooting and alignment—Do away with messy bias batteries.

Completely isolated. Recommended by TV manufacturers. Wire wound control for calibration accuracy. For AGC trouble shooting, connect to AGC buss and vary voltage from 0 to 18 volts negative. If picture stabilizes at any voltage, AGC is defective. Complete with test leads.

MODEL BE3
\$785
Dealer Net
Leather Carrying
Case...\$2.95

Mfg by
SENCORE

**POPULAR
SENCORE
PRODUCTS**


- Transistor Tester
- Leakage Checker
- Filament Tester
- Handy "36" Vibra-Dapter

SERVICE
INSTRUMENTS CORP.
171 OFFICIAL RD. ADDISON, ILL.

Advertisers' Index

Aermotor Company	30
Aerovox Corporation	29
Amphenol Electronics Corp.	1
Anchor Products Company	36
Belden Manufacturing Co.	5
Blonder-Tongue Laboratories, Inc.	34
Busmann Manufacturing Co.	7
Communications Company, Inc.	13
Cornell-Dubilier Electric Corp.	26
Electro-Voice, Inc.	11
Erie Resistor Corp.	23
General Cement Mfg. Co.	27
Heath Company	8
Hexacon Electric Company	28
Hotpoint Company	2
Jensen Industries	28
Mallory, P. R. & Co. Inc.	9
Ohmite Manufacturing Co.	32
Perma-Power Company	36
Pyramid Electric Company	Cover 3
Quietrole Company	36
RCA Batteries	Cover 4
Radiart Corporation	Cover 2
Raytheon Manufacturing Co.	3
Service Instruments Corp.	36
Simpson Electric Company	14
Tung Sol Electric, Inc.	24, 25

BURTON BLOWNE, New York

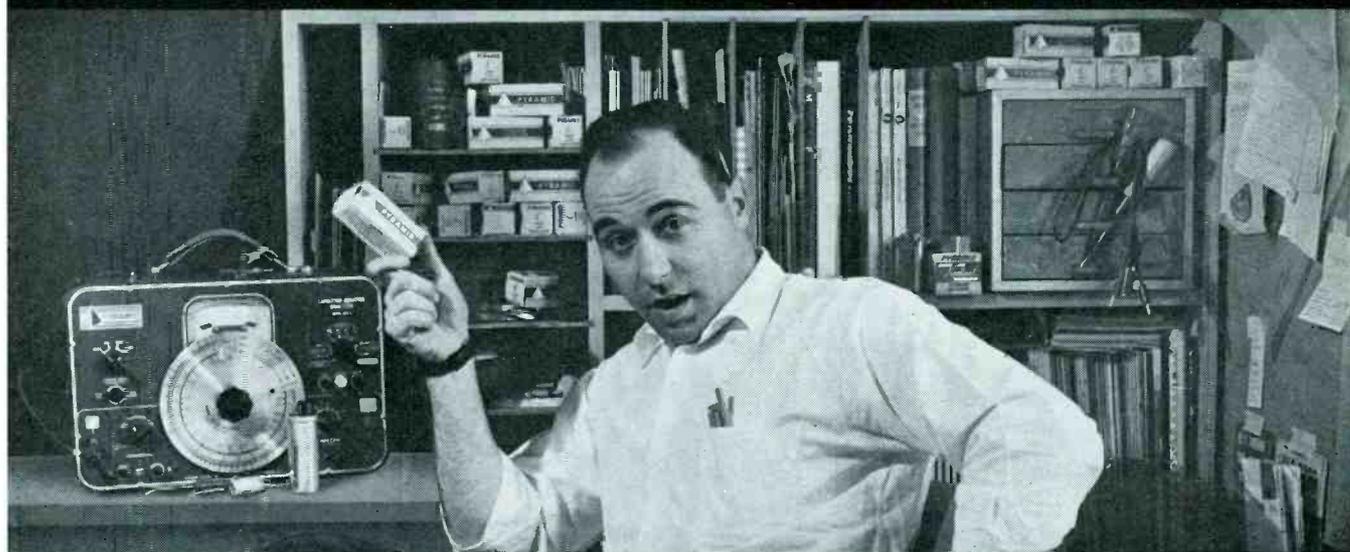

**FOR
RELIABILITY...
WHICH
CAPACITOR
DO YOU
PREFER?**

**PYRAMID...
SAID
4.6
OUT OF
EVERY 6
SERVICEMEN**

CAPACITORS—RECTIFIERS
FOR ORIGINAL EQUIPMENT—FOR REPLACEMENT



PYRAMID ELECTRIC COMPANY

1445 HUDSON BLVD., NORTH BERGEN, NEW JERSEY

Get in the swim...



...with refreshing profits from
RCA BATTERIES!

"Cool" profits are yours when you stock and sell popular RCA Batteries during these summer dog days. Right now the portable radio season is at its height. So what is more natural than to display and merchandise RCA Batteries if you want your profits to soar as high as the temperatures.

To "get in the swim," contact your local distributor and order *your* complete stock of RCA Batteries . . . right now the hottest items under the sun!

(Portable illustrated is RCA Victor Model 7BX9.)



RADIO CORPORATION of AMERICA
COMPONENTS DIVISION

CAMDEN, N. J.

RCA BATTERIES...THE BRAND THAT COMMANDS PUBLIC DEMAND!

COWAN PUBLISHING CORP., 300 West 43rd Street, New York 36, N. Y.

**ELECTRONIC
SERVICING**

IA 6F 244 16 SEP 57A
HERB'S TV
H A KAURANEN PROP
11666 HUBBELL
DETROIT 27 MICH