

40 Construction Projects • SWL • Ham Radio

RADIO-TV EXPERIMENTER

By the Editors of Science and Mechanics

75c
SPRING
1960

*build this
TRF PORTABLE
for less than \$20*



VARIABLE PS FOR
TRANSISTOR CKTS

MEMORIZE MORSE
IN 20 MINUTES

TRANSISTOR
TESTER-VOM

TV-FM ANTENNAS

TELEPHONIC
REMOTE CONTROL

ELECTRIC GUITAR

MINIATURE
MULTIMETER

6-METER CONVERTER

ELECTRONIC
TACHOMETER

ELIMINATING TVI

JACOB'S LADDER

10 20-METER
SW RECEIVER

PLUS

**WHITE'S
RADIO
LOG**



500 Changes · New, Up-to-Date
AM-FM-TV STATIONS
WORLD-WIDE SHORT WAVE

HOW TO GET A GOOD PAYING JOB IN RADIO-TELEVISION



Build this equipment while learning . . . it's yours to keep!



EARN WHILE YOU LEARN AT HOME IN SPARE TIME

I'll prove to you that I can prepare you to become a trained Radio and Television Serviceman in a few months' time . . . ready to step into a good paying job with a real future! Mail coupon-postcard NOW!



MASON R. WARNER,
President

Only \$6 starts you "Learn by Doing" Training Plan

Men by the thousands . . . trained Radio-Television Service Technicians . . . are needed at once! Perhaps you've thought about entering this interesting, top paying field, but lack of ready money held you back. Now—just \$6 enrolls you for America's finest, most up-to-date home study training in Radio-Television! This offer is made because Radio-Television must have the additional men it needs as quickly as possible. We are willing to do our part by making Sprayberry Training available for less money down and on easier terms than ever before. This is your big opportunity to get the training you need . . . to step into a fine job or your own Radio-Television Service Business.

Get Practical Experience with 25 Kits of Radio-TV Parts

In addition to modern lessons, you train with actual parts and equipment. Build the famous Sprayberry Training Television Set, Multi-Range Tester, 2-Band Radio, other Test Equipment—all yours to keep. Get latest training on Color TV, Transistors, Hi-Fi and UHF Conversions to make your training more valuable.

Radio-TV Needs You Now! Get all the facts . . . FREE!

Radio-Television needs you! See how and why Sprayberry Radio-Television home training offers you *more*. Three training plans to suit your exact needs. Low payment . . . only \$6 starts you. Backed by over 27 years of distinguished training experience. Rush special postcard—reply coupon for catalog and free sample lesson.

The Radio-Television industry is begging for trained men for interesting, profitable service work . . . get set now!

✂ **WRITE NAME AND ADDRESS—Cut out card and mail.** ✂

YOUR NAME _____
 ADDRESS _____
 TOWN _____ STATE _____



BUSINESS REPLY MAIL
 First Class Permit No. 34316, Chicago, Ill.

SPRAYBERRY ACADEMY OF RADIO-TELEVISION

Dept. 212-F 1512 Jarvis, Chicago 26, Ill.

FREE
 new 60 page catalog and actual sample lesson



This coupon needs no stamp or envelope. Just write name in upper left corner, cut out along dotted line and drop in any mail box. Pay no attention to printing on back of the card. By return mail you'll receive our big 60 page catalog and free sample lesson.

SPRAYBERRY

ACADEMY OF RADIO-TELEVISION
 Dept. 212-F
 1512 Jarvis, Chicago 26, Ill.

RADIO-TV EXPERIMENTER

Spring 1960 Edition

Terrific TRF Portable	23	Electronic Black Magic	88
Six-Meter Amateur Band Converter	27	Extra Uses for Table Radios	90
Two-Transistor Utility Amplifier	30	Tuned Antenna Coupler	91
SM-FP Unit	33	Learn by Doodling	92
Miniature Multimeter	37	Tube Tester Kit Report	95
Three-Transistor Portable	41	Loop Crystal Set	97
Noise Limiter for Ham Station	44	Printed Circuit Know-How	99
Wave Traps	45	DXing the World	102
Precision Stroboscope	47	Electronic Color Wheel	105
10-20 Short-Wave Receiver	52	VHF Station	107
Telephone Actuated Switch	55	Radio-TV Sound Dimmer	116
Compass Galvanometer	61	Using an Oscilloscope	118
Variable Power Supply	62	Soldering Iron Stand	123
Eliminating TVI	64	The Tunnel Diode	125
Car Battery Adaptor for Radio	68	Electronic Tachometer	127
DC Meter Amplifier	69	Repair That Old Meter	132
Transistorized Photo-Cell Control	72	Why Wait for Air Safety?	134
What to Listen for on Short-Wave	74	TV and FM Aerials	136
How to Memorize Morse Code	77	Learning Electronics	139
Demagnetizer	80	Portable Earphone Plug Box	145
High-Voltage Traveling Arc	82	Electric Guitar	146
Volt-Ohmmeter and Transistor Tester	85	25 Years Ago in Radio	156

WHITE'S RADIO LOG 161

Cover by Harold R. Stluka

Curtis L. Johnson, Handbook Editor
Herb Siegel, Associate Editor, Handbooks
Bill Watkins, Assistant Art Director, for Handbooks

Published and Copyrighted 1960 by
SCIENCE AND MECHANICS PUBLISHING COMPANY
 A Subsidiary of Davis Publications, Inc.

450 East Ohio Street

Chicago 11, Illinois

The Radio-TV Experimenter contains a selection of the most popular electronics projects and radio and TV maintenance articles that have appeared in *Science and Mechanics Magazine*, plus a number of projects and helpful articles on the same subjects appearing for the first time.

Science and Mechanics Handbook Annual No. 2, 1960—No. 565

B. G. DAVIS
 Publisher

JOEL DAVIS
 Assistant Publisher

Editorial Board

DON DINWIDDIE
 Editor

ART YOUNGQUIST
 Home Workshop Editor

P. D. URBAIN
 Associate Editor

F. M. EISENZOPH
 Art Director

Advertising Offices: Chicago: 450 E. Ohio St., WH 4-0530; New York: 527 Madison Ave., PL 3-0377; Los Angeles: The Maurice A. Kimball Co., Inc., 2550 Beverly Blvd., DU 8-6178; San Francisco: The Maurice A. Kimball Co., 681 Market St., EX 2-3363.

The **AMERICAN BASIC SCIENCE CLUB** offers this

Exciting New Hobby for Everyone

Low Cost **SCIENCE LABORATORY**
Over 100 Fascinating Projects with



COMPLETE LABORATORY COMES IN 8 KITS . . . ONE A MONTH
SUPPLIES ALL THE EQUIPMENT FOR ALL THE FOLLOWING:

<p>ELECTRICAL EXPERIMENTS Educational fun with Electro-Magnets, Transformer, Galvanometer, Rheostat, Relay, Voltmeter, Wheatstone Bridge, and other electric equipment.</p>	<p>RADIO RECEIVER A sensitive three tube Regenerative Radio that has its own DC power supply. Plugs into regular 115 volt AC outlet. Complete with Head Set.</p>	<p>SPECTROSCOPE Fascinating optical instrument used to identify and analyze substances by observing the spectrum of their flame. Spectrum charts are included.</p>
<p>PHOTOELECTRIC EYE Photoelectric Cell, Exciter lamp — and Electronic Relay. Everything you need to control motors, bells, alarms, and do other light beam experiments.</p>	<p>MICROPHONE A sensitive carbon-button microphone that greatly amplifies unsuspected noise. Also adaptable for use with your radio transmitter.</p>	<p>ELECTRONIC EXPERIMENTS Explore functions of vacuum tubes and other electronic components. Build an Electronic Switch—Amplifier, and other experimental circuits.</p>
<p>CODE PRACTICE SET Signal Oscillator, Key and Flasher — the complete outfit to learn to receive and transmit the Morse Code — the first step to a Ham License.</p>	<p>STROBE LIGHT A variable pulse neon light. "Freezes" motion of rapidly vibrating or rotating objects for close study and checking frequencies, RPM.</p>	<p>BROADCAST TRANSMITTER Sends clear transmissions of both code and voice to nearby radios. Can be used with your microphone, record player, or code oscillator.</p>
<p>RADIO SERVICE EQUIPMENT All the parts to build your own Radio Signal Tracer and a Probe Light Continuity Tester. Both pieces are invaluable in radio servicing.</p>	<p>SOUND EXPERIMENTS Laboratory demonstration of sound waves, resonance and pitch. Includes Variable Frequency Oscillator, Sonometer and Loud Speaker.</p>	<p>TELESCOPE A mounted astronomical telescope. High quality ground lens enables you to examine details of the moon's surface and distant objects.</p>
<p>PHOTOGRAPHY LAB Complete dark room equipment: Printer—Enlarger—Electronic Timer — Safe Light — Developing Trays and supply of paper and chemicals.</p>	<p>SLIDE PROJECTOR Takes 16mm and 35mm slides, sharp focusing, conversion cooled, G.E. Projection Lamp included. Also adaptable as a Projection Microscope.</p>	<p>MICROSCOPE High and low power, precision ground lens. Substage Light and Polarizer. Adaptable for photomicrography in connection with Photo Lab.</p>
<p>ATOMIC RADIATION EXPM. Check radioactivity of ores and do radiation experiments with sensitive Electroscope. Sample radioactive sources of Radium, Uranium included.</p>	<p>SPINTHARISCOPE Gives you a blown up ringside view of the brilliant explosions of disintegrating radium atoms ejecting alpha particles at 11,000 miles per second.</p>	<p>ATOMIC CLOUD CHAMBER See illuminated tracks of speeding nuclear particles emanating from radioactive Alpha source and mysterious cosmic rays from outer space.</p>
<p>ULTRAVIOLET LAMP Produce dazzling color effects with invisible "black light". Used extensively for crime detection, mineralogy and science and industrial research. Fluorescent Tracer Chemical included.</p>	<p>HEAT EXPERIMENTS Study the Molecular Theory of heat using 2 Thermometers, Thermostat, 3 foot Gas Thermometer and special Microscope arrangement that shows the effect of Molecular Movement.</p>	<p>WEATHER STATION Aneroid Barometer, Cup Anemometer that electronically measures wind speed, Sling Psychrometer, Humidity Gauge, Cloud Speed Indicator, Cloud Chart and Weather Map.</p>

These kits were developed with famous **SOUTHWEST RESEARCH INSTITUTE**

and are a **TRUE BASIC SCIENCE COURSE**

- The 8 instruction manuals are expertly written, clearly illustrated — exciting, interesting.
- WITHOUT PREVIOUS EXPERIENCE you can complete every project and gain a valuable, comprehensive science background.

EASY - FUN - EDUCATIONAL



Analyzing Glowing Gases with the **SPECTROSCOPI**

Trouble Shooting with the **SIGNAL TRACER**

PHOTOMICROGRAPH of a Fly's Wing made with Microscope and Photo Lab (Actual Size 5" diameter)

ALL THE EQUIPMENT FOR ALL THE ABOVE—only \$29.60

SEND **\$2.00** WITH ONLY **COUPON** PAY **\$3.45** ONLY FOR EACH KIT YOU RECEIVE (ONE A MONTH FOR 8 MONTHS) **FREE** **SOLDERING IRON** with second Kit

Your Satisfaction or Your Money Back... AND you may cancel at any time without obligation.

These "no risk" assurances because we know you will be...

SURPRISED! AMAZED! DELIGHTED!

These 8 Kits Make Up a Valuable, Versatile Science Laboratory Containing Standard Parts by:

- SYLVANIA, MALLORY, G. E., PYRAMID, STACKPOLE, TRIM AND OTHER RELIABLE MANUFACTURERS

Retail value of parts alone is over **FIFTY DOLLARS**

FOR SAFETY!

Circuits are low voltage supplied by isolation transformer that comes with first kit.



FREE! These 6 Auxiliary Textbooks

MEMBERS ARE ENTHUSIASTIC!

I wish I could provide each of my Physics students with all of your enjoyable kits. You are doing a wonderful job.

Designing and offering this complete laboratory to the public at such a low price is a notable service to our society.

R. M. Helm Professor of Physics East Carolina College Greenville, N. C.

Allen T. Ayers Physics Dept. Jamestown High School Jamestown, New York

AMERICAN BASIC SCIENCE CLUB, Inc. San Antonio, Texas

AMERICAN BASIC SCIENCE CLUB, Inc.
501 East Crockett, San Antonio 6, Texas

Start sending me A.B.S.C.'s "Home Science Lab" in eight kits, one each month. If not satisfied on inspection of first kit I may return it for immediate refund. (I choose plan check-krit.)
(1) I enclose \$2.00 and will pay \$3.45 plus COD postage on arrival of each kit. I may cancel un-shipped kits at any time.
(2) I enclose \$29.60 as full payment, *Postage Paid*, for all 8 kits. I may cancel any time and get full refund on unshipped kits.

NAME _____
STREET _____
CITY _____ STATE _____
MAIL COUPON TODAY


These men are getting practical training in **NEW Shop-Labs of**

ELECTRICITY

ELECTRONICS

ON REAL

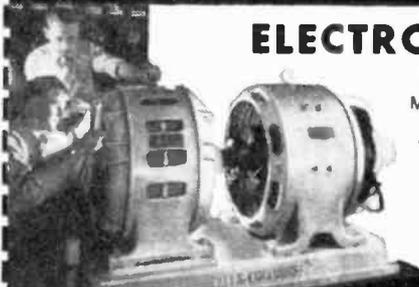- Motors—Generators
- Switchboards—
- Controls—Modern
- Appliances—
- Automatic
- Electronic
- Control Units



TELEVISION

RADIO ELECTRONICS

ON REAL

- TV Receivers—
- Black and White
- and Color
- AM-FM and
- Auto Radios
- Transistors
- Printed Circuits
- Test Equipment



COYNE

In Chicago—prepare for today's **TOP OPPORTUNITY FIELD**. Train on real full-size equipment at COYNE where thousands of successful men have trained for over 60 years—largest, oldest, best equipped school of its kind. Professional and experienced instructors show you how, then do practical jobs yourself. No previous experience or advanced education needed. Employment Service to Graduates.

START NOW—PAY LATER—Liberal Finance and Payment Plans. Part-time employment help for students. **GET FREE BOOK**—"Guide to Careers" which describes all training offered in **ELECTRICITY** and **TELEVISION-RADIO ELECTRONICS**—no obligation; **NO SALESMAN WILL CALL**.

Coyne Electrical School, 1501 W. Congress Parkway
Chartered Not For Profit • Chicago 7, Dept. 30-9C

MAIL COUPON OR WRITE TO ADDRESS BELOW

COYNE ELECTRICAL SCHOOL
Dept. 30-9C—New Coyne Building
1501 W. Congress Pkwy., Chicago 7, Ill.

Send **BIG FREE** book and details of all the training you offer. However, I am especially interested in:

- Electricity Television Both Fields

Name _____

Address _____

City _____ State _____



COYNE offers
LOW COST

TELEVISION

RADIO - COLOR TV

Training in
Spare Time **AT HOME**



The future is **YOURS** in **TELEVISION!**

A fabulous field—good pay—fascinating work—a prosperous future in a good job, or independence in your own business!

Coyne brings you **MODERN-QUALITY** Television Home Training; training designed to meet Coyne standards at truly lowest cost—you pay for training only—*no costly "put together kits."* Not an old Radio Course with Television "tacked on." Here is **MODERN TELEVISION TRAINING** including **Radio, UHF and Color TV**. No Radio background or previous experience needed. Personal guidance by Coyne Staff. **Practical Job Guides** to show you how to do actual servicing jobs—*make money early in course*. Free Lifetime Employment Service to Graduates.

Send Coupon or write to address below
for **Free Book**

and full details,
including easy
Payment Plan.
**No obligation, no
salesman will call.**



COYNE Television Home Training Division

Dept. 30-H9, New Coyne Building
1501 W. Congress Pkwy., Chicago 7, Ill.

Send **Free Book** and details on how I can get Coyne Quality Television Home Training at low cost and easy terms.

Name _____

Address _____

City _____ State _____

COYNE

ELECTRICAL SCHOOL

CHARTERED AS AN EDUCATIONAL INSTITUTION
NOT FOR PROFIT

1501 W. Congress Parkway • Chicago 7, Dept. 30-H9



B. W. COOKE, Jr., President

Coyne—the Institution behind this training... the largest, oldest, best equipped residential school of its kind. Founded 1909.



The Beautiful *Schober* CONSOLETTA
—only small organ with two full 61-note keyboards and 22 stops. Requires only 2x3 1/2" floor space! Commercial value approximately \$1600 or more.

BUILD THIS SUPERB *Schober* ORGAN FROM SIMPLE KITS and save over 50%!

Give Your Family A Lifetime of Musical Joy With A Magnificent Schober Electronic Organ!

Now you can build the brilliant, full-range Schober CONSOLETTA or the larger CONCERT MODEL with simple hand tools! No skills are needed; no woodworking necessary. Just assemble, clearly marked electronic parts guided by step-by-step instructions. You build from kits, as fast or as slowly as you please... at home, in your spare time — with a small table serving as your entire work shop.

THE GREAT CONCERT MODEL meets specifications of American Guild of Organists

ment you assemble is as fine, and technically perfect, as a commercial organ... yet you save over 50% on quality electronic parts, high-priced labor, usual store mark-up!

Free Booklet

Send for 16-page booklet in full color describing Schober organs you may build for home, church or school, plus articles on how easy it is to build your own organ and how pleasant it is to learn to play. Also available is 10" LP demonstration record (price \$2.00 — refundable on first order). Send for literature. No obligation and no salesman will call.

Pay As You Build!

Start building your organ at once, investing just \$18.94! The superb instru-

Mail This Coupon For FREE Schober Literature And Hi-Fi Demonstration Record TODAY!



The Schober Organ Corp., Dept. RX-1
2248 Broadway, New York 24, N. Y.
 Please send me FREE full-color booklet and other literature on the Schober organs.
 Please send me the 10" hi-fi Schober demonstration record. I enclose \$2.00 (refundable on receipt of my first kit order)

Name
Address
City Zone State



send for this **FREE** **EICO** Electronics Catalog

you save 50% on Top-Quality Test Instruments Hi-Fi • Ham Gear **KITS AND ASSEMBLED** Ready-to-use for professional and home use

- TEST INSTRUMENTS**
battery eliminators
bridges
decade boxes
electronic switch
flyback tester
oscilloscopes
probes
signal and sweep generators
tube testers
transistor tester
vacuum tube voltmeters
volt-ohm-milliameters
- HI-FI stereo and monaural**
tuners
preamplifiers
power amplifiers
integrated amplifiers
speaker systems
- HAM GEAR**
cw transmitter
modulator-driver
grid dip meter
- OVER 1 MILLION EICO instruments in use throughout the world.

LIFETIME service and calibration guarantee. IN STOCK at your neighborhood EICO dealer. Send now for FREE catalog RTE-3



33-00 N. Blvd., L. I. C. 1, N. Y. ... praised by the experts as BEST BUYS IN ELECTRONICS

© 1960 ELECTRONIC INSTR., CO., INC.



.22 Cal NEW 7 SHOT REPEATER AUTOMATIC. The skilled hands of the German gunsmith is responsible for this .22 caliber 7 shot repeater automatic with self-ejecting empty shells. Just 4 inches long. Fits easily into pocket or purse. Ideal for sporting events. Boating. Stage use. (Not available to Calif. residents). No permit needed. Money back guarantee. Comes for \$6.95 from Best Values Co., Dept. F-86, 403 Market St., Newark, New Jersey

INVENTORS

PROTECT YOUR PATENT

With NEW PATENT SALES AGREEMENT

Now you can sell your patent and be SURE you are protecting your interests 100 percent. Prepared by the Dean of a leading law school, this S&M Patent Sales Contract will help you protect yourself and make sure you or your attorney overlooks no detail. Not a blank, but a true, TESTED Sales Contract that will protect your earnings and interests. Send today for a copy of our Patent Sales Agreement.

Only \$100

SOLD EXCLUSIVELY BY SCIENCE & MECHANICS MAGAZINE
450 East Ohio Street, Dept. 411, Chicago 11, Illinois

In Spare Time at Home—Prepare for a Better Job—or
Your Own Business in One of the Many Branches of

ELECTRONICS

You build and keep this valuable Vacuum Tube VOLTMETER

You build and keep this 5-inch COLOR OSCILLOSCOPE—almost a "must" for TV servicing.

COLOR TV
DeVry Tech's program also includes training in Color Television

HOME MOVIES . . .
... make important points crystal clear. Speeds your learning. It's almost like having an instructor at your side!

MILITARY SERVICE
If you are subject to military service, the information we have should prove very helpful. Mail coupon today.

RADIO - TELEVISION - RADAR

If you are seeking a better job or a business of your own, the appealing field of Television-Radio-Electronics offers **REAL PROMISE!**

In this fast-growing field, trained Electronic technicians find many good-paying, interesting jobs in manufacturing, installing, operating, servicing. Equally important is the fact that these are **GOOD JOBS**—offering the kind of a future that an untrained man often dreams about.

No previous technical experience or advanced education needed. Prepare for this profitable field in your spare time at home, or in our modern Chicago or Toronto Laboratories. Nothing else like it! Send for **FREE** details.

EARN WHILE YOU LEARN
After you get part of DeVry Tech's training with equipment at home, you may then in your spare time, begin to earn real money servicing Radio and Television sets.



21 INCH

Build and keep this BIG DeVry Engineered TV set—easily converted to U.M.F. (DeVry offers another home training, but without the TV set.)

Your GUIDE

to Profitable Job Opportunities

- TV-Radio Broadcast Technician
- Color Television Specialist
- Radar Operator • Laboratory Technician
- Airline Radio Man • Computer Specialist
- Quality Control Manager
- Your Own Sales & Service Shop
- . . . PLUS MANY OTHERS

YOU GET THE SAME EMPLOYMENT SERVICE

that has helped thousands of our graduates toward fine careers in Electronics.



Send for **FREE BOOKLET TODAY!**

Accredited Member of National Home Study Council

"One of North America's Foremost Electronics Training Centers"



DeVRY TECHNICAL INSTITUTE

CHICAGO 41, ILLINOIS



You work over **300** Learn-By-Doing projects


Build over 300 practical projects from many shipments of Radio-Electronic parts. You build and operate TV-Radio circuits . . . wireless microphone . . . and many other major projects—all designed to provide outstanding practical experience at home.

ACT NOW! Get information-packed publication **FREE!** Mail coupon today.

DEVRY TECHNICAL INSTITUTE
4141 Belmont Ave., Chicago 41, Ill., Dept. RTE-3-Q
Please give me your **FREE** booklet, "Electronics in Space Travel," and tell me how I may prepare to enter one or more branches of Electronics.

Name _____ Age _____
PLEASE PRINT
Street _____ Apt. _____
City _____ Zone _____ State _____
2044 Canadian residents address DeVry Tech of Canada, Ltd.
626 Roselawn Ave., Toronto 12, Ontario

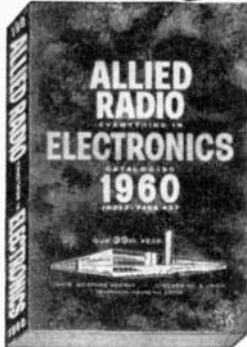k **BUILD THE BEST!**
 build quality money-saving
knight-kits[®]
 A PRODUCT OF ALLIED RADIO



see them all in
ALLIED'S
 1960 ELECTRONIC
 SUPPLY CATALOG

FREE

build your own...
 it's easy...it's fun!
SAVE UP TO 50%

HI-FI
 KITS



INSTRUMENT
 KITS



HOBBY KITS



HAM
 KITS

world's
 largest
 stocks



EASIEST TERMS
 only \$2 down on
 orders up to \$50

FREE
 catalog

ALLIED RADIO

100 N. Western Ave., Dept. 64-C, Chicago 80, Ill.

Rush FREE 1960 ALLIED Catalog

Name _____

Address _____

City _____ Zone _____ State _____

ELLERY QUEEN'S 1960 ANTHOLOGY

A Who's Who of Whodunits!

"The Queen volume contains twenty-three stories . . . none has appeared in an earlier Queen anthology, and only two have been anthologized anywhere. You will, I'm sure, join me in hoping that this new kind of Queen anthology will become (as its title should indicate) an annual event."

—Anthony Boucher, *The New York Times*

HOURS OF THRILLING READING . . .

collects in one volume the finest stories which have appeared in *Ellery Queen's Mystery Magazine* over the past 18 years—selected by Ellery Queen himself. Stories by such famous mystery writers as:

Agatha Christie
 Erle Stanley Gardner
 Mary Roberts Rinehart
 Rex Stout
 John Dickson Carr

Tales of mystery and of crime by such famous literary figures as:

W. Somerset Maugham
 Ben Hecht
 John van Druten
 Mackinlay Kantor

And much, much more . . . a book everyone will be proud to add to his library—3 short novels, 20 short stories, 320 pages. If your local newsstand dealer is sold out, fill in the coupon below and we will mail your copy of this mystery treat.

Davis Publications, Inc., Dept. 565A
 527 Madison Ave., New York 22, N. Y.

Please send me copies of
 ELLERY QUEEN'S 1960 ANTHOLOGY.

I enclose \$1.00 for each copy.

I am an EQMM subscriber.

NAME _____

ADDRESS _____

CITY _____ ZONE _____


STATE _____



ON LAND·IN THE AIR and ON THE SEA..

BIG MONEY

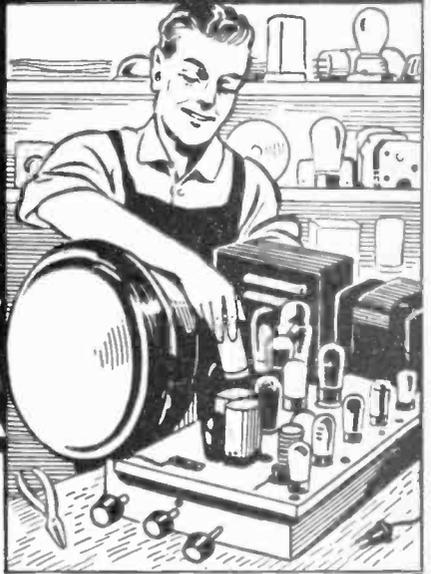awaits
**TRAINED
 TECHNICIANS**
in
**TELEVISION·RADIO·
 ELECTRONICS·RADAR**



EARN *As You Learn*

Christy Shop-Method Home Training makes you a more valuable and desirable technician, assures you of more money, faster progress and greater success. This practical step-by-step training makes everything interesting and easy, makes learning fun. You don't have to leave home or quit your job to learn this simple, easy way. A few hours of your spare time each week soon prepares you for earning while learning and later for a big-pay job or profitable business of your own in this fabulous, fast-growing new industry.

3 new books contain complete information. Describe the course and many opportunities in this fantastic new field. Send for your 3 free books today!

**19 TRAINING
 INSTRUMENTS
 INCLUDED**

In a few months you learn what used to take years of hard work to master, reach your goal sooner and are better prepared to make maximum progress. Send for complete information today!

CHRISTY TRADES SCHOOL
 Dept. T-211
 3214 W. Lawrence Ave.
 Chicago 25, Ill.

C.T.S.'s Complete Course!

C.T.S. training covers every phase of this fascinating new subject. You get this comprehensive training starting with your first lesson. You learn Radar, Sonar, Television, Radio and Electronics in C.T.S.'s Complete course. This broader knowledge and greater understanding means more jobs and higher pay for you. Why be satisfied with less? You learn faster and better with Christy Shop-Method Home Training. It gives you all the training you need in a clear, simple, easy-to-understand way.

Big pay, interesting work, immediate success, await those thoroughly trained in all branches of electronics. And the C.T.S. Master Shop-Method Home Training Course is the only complete course in Radar, Sonar, Television, Radio and Electronics.

MAIL COUPON TODAY!

CHRISTY TRADES SCHOOL
 Dept. T-211, 3214 W. Lawrence Ave., Chicago 25, Ill.

Gentlemen:
 Please send me, without cost or obligation, two FREE Lessons and the new 24-page illustrated book telling all about the C.T.S. Master Shop-Method Home Training Course in Radar, Sonar, Television, Radio and Electronics, and the many opportunities this new field offers.

Name Age

Address

City State



prepare for your career in

ELECTRONICS RADIO-TV COMPUTERS

and other fields of
ELECTRICAL ENGINEERING

At MSOE, you can equip yourself for a career in many exciting, growing fields: **MISSILES • RADAR • AVIONICS AUTOMATION • RESEARCH DEVELOPMENT • ELECTRICAL POWER • ROCKETRY**

When you graduate from the Milwaukee School of Engineering, you are prepared for a dynamic career as an Electrical Engineer or Engineering Technician. Under a faculty of specialists, you gain a sound technical education in modern, completely equipped laboratories and classrooms. As a result, MSOE graduates are in great demand and highly accepted by industries nationally.


At MSOE, you will meet men from all walks of life and all parts of the country — some fresh out of high school or prep school, others in their twenties — veterans and non-veterans.

You can start school in any one of four quarters and begin specializing immediately. Engineering technicians graduate in 2 years with an Associate in Applied Science degree. For a Bachelor of Science degree in Engineering, you attend 4 years. A 3-month preparatory course also is available.



FREE CAREER BOOKLET!

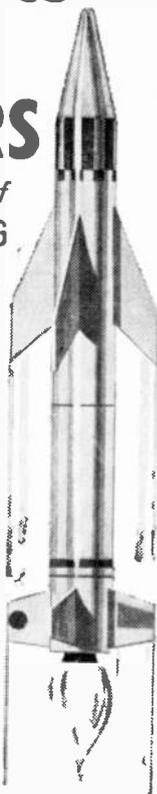If you're interested in any phase of electronics, radio or television, be sure to look into the programs of study offered by the Milwaukee School of Engineering. Just mail the coupon.



MILWAUKEE SCHOOL OF ENGINEERING

Dept. RTVE-60, 1025 N. Milwaukee St., Milwaukee, Wisconsin

Please send FREE Career Booklet. I'm interested in
 Electronics Electrical Power Television
 Mechanical Engineering Radio Computers
 Electrical Engineering Industrial Electronics

PLEASE PRINT

Name Age

Address

City Zone State

I'm eligible for veterans education benefits

MS-125

Experimenters!

BACK-ISSUE BARGAINS!

**Two for \$1.00
Four for \$2.00
\$2.50 for Six**

These back issues of the **RADIO-TV EXPERIMENTER** are still available:



538 Contains over 40 projects. Radio direction finder, hidden metal detector, low-cost speedlight, remote control fireboat, shortwave receivers, radiotelephone station, radio-controlled garage door opener. Single copy, 50¢



551 Includes sun-cell TRF receiver, plans for experimenter's test bench, decade ohm box, electronic tie-tac-toe, split-powered oscillator, photoelectric controls, signal tracer, portable hi-fi record player, single-tube organ. Single copy, 75¢



559 Has 43 different project plans including 15-meter ham rig, simple signal mixer, electronic moisture tester, finger-clip radio, telethermoscope, portable phonograph, hi-fi tone arm, strobe-flash unit. Single copy, 75¢



562 Contains 53 make-it-yourself projects: transistorized intercom, Citizens Band 2-way radio, 7-tube FM tuner, 6-meter ham rig, sun-elled motor, stereo music center. Single copy, 75¢

**Two for \$1.00
Four for \$2.00**

Also available, these **SCIENCE EXPERIMENTERS**



557 Plans for 40 projects including Van de Graaff generator, Tesla coil, Wimshurst static machine, cloud chambers, light ray tracer, satellite scope, solar furnace. Single copy, 50¢

563 Contains over 50 science projects including repulsion coil, satellite camera, tone generator, atmospheric voltmeter, infrared detector. Single copy, 75¢

RUSH COUPON TODAY
Satisfaction guaranteed

SCIENCE and MECHANICS, Dept. 333
450 East Ohio St., Chicago 11, Illinois

Enclosed is \$..... Please send me:

- All SIX of the Experimenters for \$2.50.
- The TWO RADIO-TV Experimenters circled for \$1.00.

538 551 559 562

- All FOUR RADIO-TV Experimenters for \$2.00.
- Both SCIENCE Experimenters for \$1.00.
- The circled issues at single copy prices:

538 551 559 562 557 562

NAME

ADDRESS

CITY ZONE

STATE

NOW! McGraw-Hill's Low-Cost Home Course Shows

HOW TO FIX TV Radio and Record Changers RIGHT AWAY

— even if you've never looked inside a set before!



AT LAST! at Amazing **LOW COST** — the Most Complete TV-Radio Repair Course Ever Published. **TELLS** and **SHOWS** how to do Every Job Quickly and Easily — Make **GOOD MONEY**, Full or Spare Time, in the **BOOMING** Repair Business

How would you like to be boss of a nice TV-radio-record changer repair business — making \$50 to \$75 spare time, or \$150 and up in your own shop?

Now, thanks to McGraw-Hill's new 6-volume Course, you can get started right away! This Course brings you **EVERYTHING** you need to "cash in" on the TV-Radio-Changer boom. Over 2,350 pages of money-making ideas and techniques by top factory engineers and electronics experts. **TWO HUGE TROUBLESHOOTERS** tell exactly **WHERE** to begin, **WHAT** tools to use. **THREE GIANT REPAIR MANUALS** tell and show how to **FIX** every trouble the easy way, "polish off" every job like a whiz. Complete Home Study Volume guides you every step of the way, tells how to build your business into a spare- or full-time **MONEY-MAKER!**

EARN While You Learn

Tested — and now used in repair shops and by electronics instructors — Course volumes are simple enough for green beginners, amaze "pros" with quick, easy methods. Start your doing simple repairs — and earning money — from very first chapter. ABC pictures and directions make tougher jobs a "snap." Before you finish you earn many times Course's low cost.

NO previous training needed; TV repair business pays well in good times or bad. **NO** complicated formulas. **PLAIN ENGLISH** pictures and directions cover **ANY** job on **EVERY SET** — tubes, circuits, speakers, new ac/dc, am/fm/shortwave portables, Color TV, even *what to charge for every job and how to get customers!*

Age and Education No Barrier

Age doesn't matter. Past experience doesn't matter. Your formal education isn't important. Over **40 MILLION** TV sets, **130 MILLION** radios — and the shortage of repairmen — mean big money for you. Course makes it easy to cash in, start your own secure, profitable business.

SEND NO MONEY


Try Course 10 days **FREE**. (We pay shipping!) If you don't agree it can get you started in a money-making repair business — return it, pay nothing. Otherwise keep it, earn while you learn; and pay the low cost on easy terms. Mail coupon **NOW**. McGraw-Hill Book Co., Dept. SMA-4, 327 W. 41st St., New York 36, N. Y.

Free 4 Valuable Repair Aids: TV, RADIO, CIRCUIT and TRANSISTOR Detect-O-Scopes (Total Value \$4.00)



FREE — whether you keep Course or not — **FOUR DETECT-O-SCOPE** Charts. TV and RADIO Scopes enable you to spot tube troubles in a jiffy. **CIRCUIT** and **TRANSISTOR** Scopes spot circuit and transistor troubles. Make fix-it jobs easier, faster. 16 x 21 inches each. **ALL FOUR** (worth \$4.00) yours **FREE**.

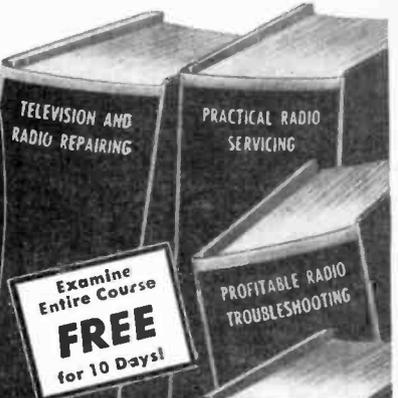New **FREE EXTRA**
New 1960 Transistor
Detect-O-Scope



PARTIAL CONTENTS

- 1** Television and Radio Repairing — Testing, repairing, replacing parts, 566 pages. 700 "This-is-How" pictures, diagrams. By John Markus, Feature Ed., Electronics Magazine.
- 2** Practical Radio Servicing — Easy-to-follow directions, diagrams, drawings — with job sheet for every repair job. 599 pages. 473 illus. By William Marcus, Alex Levy, Electronic Training Experts.
- 3** Profitable Radio Troubleshooting — **WHERE** to look and **WHAT** to do for every trouble. How to avoid costly mistakes, handle customers profitably. 330 pages. 153 "how-to" illus. By William Marcus, Alex Levy.
- 4** Profitable TV Troubleshooting — Short-cuts to **SPOT** and **FIX** every trouble—fast, for big profits. By Eugene A. Anthony Service Consultant, General Elec. Co.
- 5** Repairing Record Changers — Step-by-step pictures and directions — how to set up service bench, etc. 278 pages. 202 A-B-C pictures. By Eugene Ecklund, Eng. DuMont Lab., Inc.
- 6** Complete Home Course Outline — Getting started in television and radio servicing. How to get the most out of your Course. How to get ahead **FAST**. By John Markus.

This Amazing Offer Saves You **\$12.85**

6 BIG VOLUMES

Including Home Course Outline! Shows How to Get Ahead Fast

THIS COUPON SAVES YOU \$12.85

McGraw-Hill Book Co., Dept. SMA-4
327 West 41st St., New York 36, N. Y.

Send me — postpaid — for 10 DAYS' **FREE** TRIAL the 6-Vol. McGraw-Hill TV, Radio and Changer Servicing Course. If okay, I'll remit \$4.95 in 10 days; then \$5.00 monthly for 5 months. (A total savings of \$12.85 on the regular price of Course and Detect-O-Scopes.) Otherwise, I'll return Course in 10 days, pay nothing.

ALSO send **FREE** (to **KEEP** whether or not I keep Course) the TV, RADIO, and CIRCUIT DETECT-O-SCOPE CHARTS, plus up-to-the-minute 1960 Transistor Detect-O-Scope — total value \$4.00.

Name.....
(Please Print Clearly)

Address.....

City..... Zone No. State.....
(If any)

CHECK HERE if you prefer to enclose first payment of \$4.95 with coupon. Same easy pay plan; same 10-day return privilege for full refund. SMA-4

TRANSISTORIZED POCKET FM RADIO AND CONVERTOR KIT



Fun for the youngster or the veteran in the electronic field . . . A 3-way transistorized pocket FM radio and tuner which tunes the complete FM band from 88 to 108.6 megacycles plus aircraft band from 109 to 145 megacycles. This fantastic set can be used in your car, home, or pocket, and needs no antenna or ground wires. Completely non-directional, this compact FM radio and tuner will play where all other radios have failed. Set has been demonstrated under an X-ray beam and near other electrical devices without any static or distortion. Featuring a two-stage circuit, this FM radio and tuner will produce music of top quality from stations located many miles from the receiver. Kit comes complete with easy-to-build instructions.

KIT, Complete with Special Hi-Fi Earpiece with earmold, cord, and plug, \$29.95 postpaid. (less Earpiece, \$26.95)

TWO-STAGE TRANSISTOR AMPLIFIER OR PRE-AMP KIT



You can build a powerful two-stage amplifier or pre-amp which can be used as a phonograph amplifier or amplifier for a crystal set, and as a pre-amp for crystal or magnetic pick-up. Kit comes complete with two transistors, volume control with switch, attractive plastic case with a snap bottom, and is powered with a single penlight cell with an output of nearly $\frac{1}{2}$ of a watt. Complete with easy-to-follow instructions. \$6.95 postpaid.

RADIO-TV SERVICING AID



Powerful 7-power magnifying glass mounted on 3" tweezers. Excellent tool for

getting into difficult and hard-to-see places. Ideal for radio kit builders, model craftsmen and for the Radio-TV service technician. Special low price, \$2.25 postpaid . . . A REAL SERVICE AID BARGAIN!


SPECIAL SECTION for RADIO BEGINNERS

Crystal-Set Kit \$1.25 p p
Headphones (double) \$2.25 p p
Ball Bearing Tuning Condenser with Metal Dial and Knob \$1.50 p p
(Free Crystal with each \$10.00 order)

Beginners all Wave Kit Two Stage Circuit with Transistor, High Frequency Tube, Drilled Chassis and all Clips and Wire—\$7.95 less batteries. Many users report up to 12,500 miles on short wave plus the Broadcast Band. Tunes from 16 meters to 160 meters.

WORLD'S SMALLEST TWO BAND RADIO

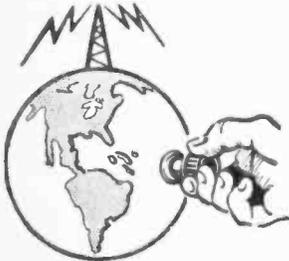TUNE IN THE WORLD OF EXCITEMENT WITH THE WORLD'S FIRST THREE STAGE TRANSISTORIZED TWO BAND RADIO KIT FOR ONLY \$5.00 FULL PRICE—READ CAREFULLY




This set tunes the broadcast band and a click on the band switch lets you enjoy exciting police calls, ship to shore, aircraft, both commercial and military, amateur phone stations, code and foreign stations from all over the world. (It's the best electronic buy ever offered.) Tunes as many stations as sets costing up to \$100.00. Kit includes the following parts: Min-Tube, Min-Tube Socket, a special detector, printed circuit plate, a band switch, a battery switch, a tuning knob, a two band coil, an (Ekeradio) electronic wand, four condensers, two resistors, two phone clips, antenna trimmer, four rubber mounting feet, hookup wire, a coil mounting clip, and a sheet of easy-to-follow instructions. A 722 or a 107 transistor can be used for the third stage (Not furnished). Any phones will work with this set. Two small batteries furnish the power (Not furnished). This can be mounted on your small board or small plastic box. Send only \$5.00, a self-addressed gummed label to facilitate shipping of this fantastic kit, and ten cents in stamps to the address below. If the above instructions are not followed, your order may be delayed several months, so read carefully.

EKERADIO ELECTRONIC DEVELOPMENTS

Dept. E • 650 North Fair Oaks Avenue
In Calif. add State Tax—No C.O.D.

• Pasadena, California
U. S. Orders Only

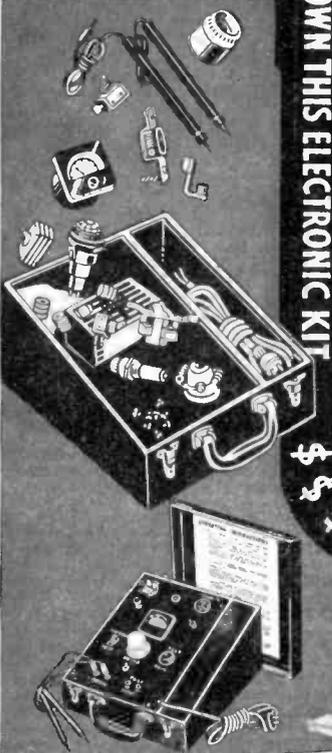Let me send you this amazing- ELECTRONIC KIT!



OWN THIS ELECTRONIC KIT

ASSURE YOURSELF OF FINANCIAL SECURITY—INDEPENDENCE

Imagine being able to fix anything electrical from the tiniest home electric shaver to large industrial motors! Having a training that makes you command a better job with higher wages or a business of your own. You do not need previous special schooling. Just the ability to read and be mechanically inclined. We furnish you with everything! One of the kits sent to you is our famous ELECTRONIC KIT, an all-purpose trouble detector which shows you where the trouble lies. Training kits whose assembly will give you practical shop training at home during your spare time!



You learn practical electricity by using your hands. Best of all, these kits are yours to keep and use forever!




FRAZER

REPAIR ELECTRICAL EQUIPMENT!

ILLUSTRATED COURSE SHOWS EVERYTHING

The Christy maintenance and repair course is written in simple, easy-to-understand language. Each section is profusely illustrated by photographs and drawings and shows you what troubles to look for and then how to correct them. In addition, our course shows you how to build power tools at low cost. Also teaches you welding, nickel plating, general repairing (saw filing, bicycle and gas stove repairing, etc.). Should complicated technical problems arise or the need for a special repair part, simply call on us. We offer YOU our FREE Advisory Service for LIFE! We teach you how to solicit business get repeat orders and what to charge. The Christy Course plus our home-shop training kits make a combination that will go a long way toward ASSURING YOUR SUCCESS.

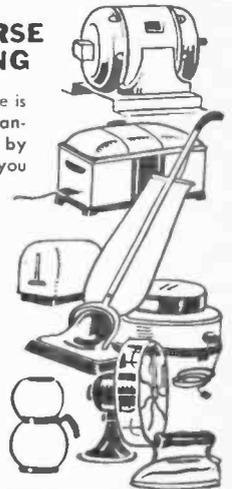

3 EASY STEPS TO SUCCESS

- ① WE SEND YOU AN ELECTRIC KIT
- ② WE TEACH YOU ELECTRICAL APPLIANCE REPAIRING
- ③ WE GIVE YOU LIFE-TIME ADVISORY SERVICE

RUSH THIS COUPON TODAY!

CHRISTY TRADES SCHOOL, Dept. A-511
3214 W. Lawrence Ave., Chicago 25, Ill.


Please send me your FREE book on Electric Equipment Servicing and instructions for paying later from EARNINGS WHILE LEARNING!

Name.....Age.....

Address.....

City.....Zone.....State.....

FARM TELEPHONE CABINETS

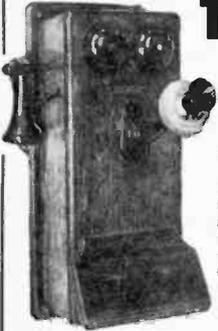

Slightly used crank style CABINETS (once used everywhere) for Home Hobby Shops. Complete with transmitter, receiver, bells, crank and shelf (Less Generator). Has all of the outside parts. Make beautiful, unique Radio Cabinets, Liquor Chests, Spice Cabinets, Flower Planters, etc. Immediate deliveries assured. \$7.00, F.O.B. Chicago.

TELEPHONES


TALK ROOM TO ROOM

to the house across the road, etc. Enjoy your own private telephone system!

Reconditioned e r a d l e phones Guaranteed!

2 for only \$5.00 **\$300** Each

We can supply everything you need.

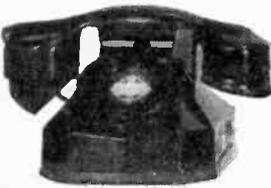

WRITE FOR ILLUSTRATED BULLETIN BB-4 MICROPHONE, Dept. BB-4, 1760 W. Lunt Ave. Chicago 26, Ill.



YOU NEED THIS

FREE GIANT 1960 B-A CATALOG



204 KING-SIZED PAGES
EVERYTHING IN RADIO TV AND ELECTRONICS
100'S OF NEW ITEMS LISTED HERE FOR 1ST TIME
21 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

BURSTEIN-APPLEBEE CO.

Dept. RE, 1012 McGee St., Kansas City 6, Mo.

Send Free 1960 B-A Catalog No. 601.

Name.....

Address.....

City..... State.....

SEND FOR IT TODAY



SO EASY IT'S SHOCKING, IF YOU USE ENLARGED PLANS

to build electronic projects. Enlarged size, step-by-step craft print plans—complete with detailed materials lists—are available for the following:

- 191. TESLA COIL. Produces 70,000 volts at 500,000 cps. Spectacular but safe.....\$1.00
- 227. REPULSION COIL. Defies law of gravity—electromagnetically.....\$1.00
- 243. DEMO ELECTRIC MOTORS. Plans for both windmill and engine types.....\$1.50
- 251. SOLAR BATTERY AND MOTOR. Battery's volt at 180 ma drives motor.....\$1.50
- 258. SUN-POWERED RELAY. Light-activated control with a variety of practical applications.....\$1.00
- 264. HI-FI FM RECORD PLAYER. Phono oscillator, arm and turntable for hi-fi reproduction.....\$1.00
- 265. ELECTRICAL COIL-WINDING MACHINE. Motor-powered with foot-controlled reactor.....\$1.00
- 279. WIMSHURST STATIC MACHINE. Constant source of static electricity.....\$1.50
- 283. VAN DE GRAAFF GENERATOR. Costs \$30 to build. Produces up to 250,000 volts.....\$1.50
- 301. VAN DE GRAAFF GENERATOR. Produces up to 400,000 volts. This is the apparatus that can stand your hair on end!.....\$1.50

... SAVE MONEY! If you order two or more craft prints, deduct 25¢ from the regular price of each print. Thus, for two prints, deduct 50¢; three prints, 75¢, etc. Use handy coupon below. Satisfaction guaranteed or money back.

SCIENCE and MECHANICS, Dept. 227
 450 East Ohio St., Chicago 11, Illinois

Enclosed is \$..... Please send me the circled plans.

These plans are \$1.00 each

191	227	258	264	265
-----	-----	-----	-----	-----

These plans are \$1.50 each

243	251	279	283	301
-----	-----	-----	-----	-----

NAME.....

ADDRESS.....

CITY & ZONE.....

STATE.....

Here's 20¢. Please send me your illustrated catalog of 196 craft print plans.




LET RCA TRAIN YOU IN ELECTRONICS


RCA Institutes, one of the world's largest electronic technical schools, offers a Home Study Course in . . .

ELECTRONICS FOR AUTOMATION

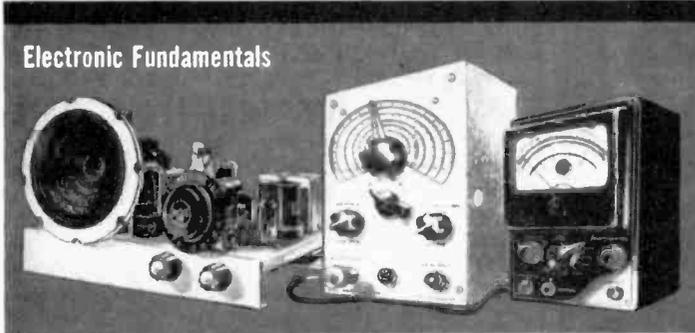
. . . Now you have *four* comprehensive courses for your electronic training . . . from basic electronic theory to the more advanced principles of color TV and Automation.



Electronic Fundamentals

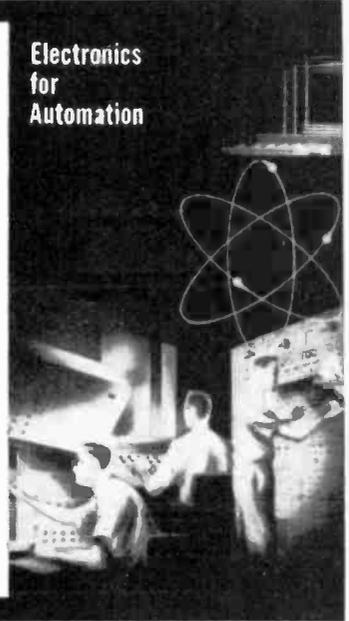

Electronics for Automation

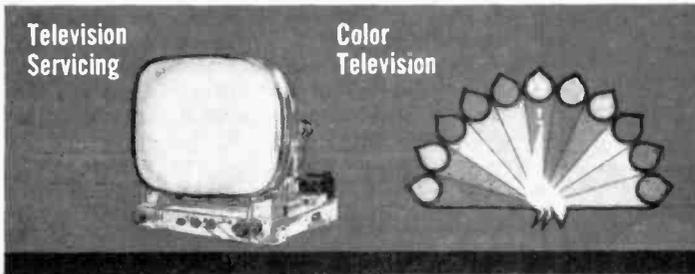

Television Servicing


Color Television

Send for our 64 page Home Study Catalog

FREE!

RESIDENT SCHOOL offers Technical Institute and Vocational School Courses in Electronics. Day and Evening classes start 4 times each year. Resident School Catalog sent free on request.

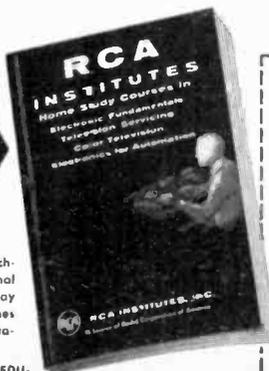ANOTHER WAY RCA SERVES EDUCATION THROUGH ELECTRONICS



Practical work with the very first lesson. Pay-as-you-learn. You need pay for only one study group at a time.

RCA INSTITUTES, Inc. Home Study School, Dept. RTVE-20

A Service of Radio Corporation of America

350 West Fourth Street, New York 14, N. Y.

Without obligation, send me the FREE catalog of Home Study Courses. No salesman will call.

Name Age

Address

City Zone State

Veterans: Enter discharge date

CANADIANS — Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to: RCA Victor Company, Ltd., 5001 Cote de Liesse Rd., Montreal 9, Quebec
To save time, paste coupon on postcard.

New Isotronic Training Method!

**LEARN TV REPAIR
IN ONE SHORT WEEK**

Now, after 5 years research—a dynamic TV training technique that makes others obsolete! If you've waited for a chance to have your own prosperous business, here's an opportunity to make up to \$150 weekly, *almost immediately!*
NO EXPENSIVE TRAINING - NO LONG STUDY!

You want to get started *servicing* TV sets - not building them! So, why pay up to \$250 for high-priced lessons and equipment - study long months? Our revolutionary ISOTRONIC method qualifies you to handle any make TV set right away! All the complicated technical theory is already taken care of by our Scientists! This new technique - hailed the most *practical* in the field - was developed by two of the industry's most respected scientists, in cooperation with every major American TV manufacturer!

PUT YOUR "KNOW HOW" TO WORK FOR PROFIT!

In addition to the most *streamlined* training program of its type, you also benefit from a complete Business Plan that explains fully how to *start, conduct, and expand* your own TV Service business. Written by expert business consultants. Packed solid with practical know-how instead of theory! Yes, a complete "Business Package" designed to quickly bring you the good things in life that come with your own successful business.

FREE LESSON PROVES ISOTRONIC METHOD WORKS!
For conclusive proof, send now for full details and FREE SAMPLE LESSON. Apply it to your own ailing set or a friend's - *repair it without a single tool or testing device* - convince yourself that the amazing Isotronic method can put you in a profitable TV business of your own, *in one short week!*

Write today - *free lesson supply limited!* (No obligation, no salesman will call.)
TV SERVICING SYSTEMS, Dept. D-872
1038 So. La Brea, Los Angeles 19, California

**FREE!
Sample
Lesson**



*** FREE**

Fill in coupon for a FREE One Year Subscription to OLSON RADIO'S Fantastic Bargain Packed Catalog — Unheard of LOW, LOW, WHOLESALe PRICES on Brand Name Speakers, Changers, Tubes, Tools, Hi-Fi's, Stereo Amps, Tuners and other Bargains.

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

If you have a friend interested in electronics send his name and address for a FREE subscription also.

**OLSON RADIO
CORPORATION**

102 S. Forge St., Akron 8, Ohio

INVENTIONS WANTED!

**140 Wealthy Manufacturers
Ready to Pay Top Prices**

WHEN you get an idea you think may be worth thousands of dollars—a brand-new product wanted by everybody; a way to improve a product already in use; a lower-cost, easier method of servicing, making, or doing something—you can know exactly HOW and WHERE to cash in on it and make big profits.

Our book, HOW TO FIND A BUYER FOR YOUR INVENTION, reveals hundreds and hundreds of needed inventions in every type of business. Lists 140 manufacturers who are eager to buy inventions (patented or unpatented) . . . and pay top cash. Tells you WHO to contact and HOW to sell—helps you get the most cash or royalties for your ideas or inventions!

WHY SO MANY INVENTORS FAIL

Few inventors know how to cash in on their ideas. Some spend their entire lives literally sitting on a gold mine without ever getting to the right man in the right firm. The secret of selling your invention—and your short-cut to success as an idea man—is in knowing WHERE your ideas are actually needed, and HOW to contact the man who will say "Yes—BUY!"

That is exactly what the editors of SCIENCE and MECHANICS have now made easy for you to do. Their brand-new guide helps you get the right contact in the right firm. It lists hundreds of inventions urgently needed by top manufacturers. Tells you the name and title of the man to contact in each firm to make a quick sale!

SEND NO MONEY

Examine Guide FREE for 5 Days!

Just mail coupon below and we will rush you a copy of "How to Find a Buyer for Your Invention" to examine FREE for five days. If not convinced that it is worth many times its low cost, simply return it and owe nothing. You don't risk a penny.


**SCIENCE and MECHANICS, Dept. 412
450 East Ohio St., Chicago 11, Illinois**

Please send me—for 5 days' FREE EXAMINATION a copy of "How to Find a Buyer for Your Invention." Unless completely satisfied with book I may return it in 5 days and owe nothing. Otherwise I will keep it and send you \$2.95, plus 25¢ to cover postage and handling.

NAME
ADDRESS
CITY ZONE
STATE

SAVE Money! Enclose only \$2.95 WITH this coupon. Then we prepay delivery charges. Same 5-day return privilege for full refund applies.

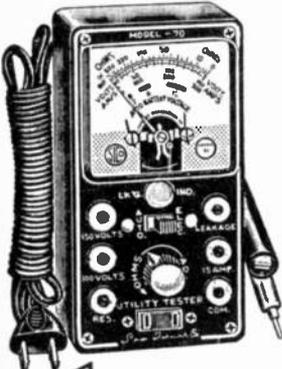Superior's New Model 70 UTILITY TESTER® FOR REPAIRING ALL ELECTRICAL APPLIANCES and AUTOMOBILE CIRCUITS



As an electrical trouble shooter the Model 70:

- Will test Toasters, Irons, Broilers, Heating Pads, Clocks, Fans, Vacuum Cleaners, Refrigerators, Lamps, Fluorescents, Switches, Thermostats, etc.
- Measures A.C. and D.C. Voltages, A.C. and D.C. Current, Resistances, Leakages, etc.
- Will measure current consumption while the appliance under test is in operation.
- Incorporates a sensitive direct-reading resistance range which will measure all resistances commonly used in electrical appliances, motors, etc.
- Leakage detecting circuit will indicate continuity from zero ohms to 5 megohms (5,000,000 ohms).

As an Automotive Tester the Model 70 will test:

- Both 6 Volt and 12 Volt Storage Batteries • Generators • Starters • Distributors • Ignition Coils • Regulators • Relays • Circuit Breakers • Cigarette Lighters • Stop Lights • Condensers • Directional Signal Systems • All Lamps and Bulbs • Fuses • Heating Systems • Horns • Also will locate poor grounds, breaks in wiring, poor connections, etc.



INCLUDED FREE This 64-page book—practically a condensed course in electricity. Learn by doing.

Just read the following partial list of contents: What is electricity? • Simplified version of Ohms Law • What is wattage? • Simplified wattage charts • How to measure voltage, current, resistance and leakage • How to test all electrical

appliances and motors using a simplified trouble-shooting technique.

• How to trace trouble in the electrical circuits and parts in automobiles and trucks.

Model 70 comes complete with 64 page book and test leads. **Only \$15⁸⁵**

Superior's New Model 82A A truly do-it-yourself type



TUBE TESTER

TEST ANY TUBE IN 10 SECONDS FLAT!

- ① Turn the filament selector switch to position specified.
- ② Insert it into a numbered socket as designated on our chart (over 600 types included).
- ③ Press down the quality button—

THAT'S ALL! Read emission quality direct on bad-good meter scale.

FEATURES:

- Tests over 600 tube types.
- Tests OZ4 and other gas-filled tubes.
- Employs new 4" meter with sealed air-damping chamber resulting in accurate vibrationless readings.
- Use of 22 sockets permits testing all popular tube types and prevents possible obsolescence.
- Dual Scale meter permits testing of low current tubes.
- 7 and 9 pin straighteners mounted on panel.
- All sections of multi-element tubes tested simultaneously.
- Ultra-sensitive leakage test circuit will indicate leakage up to 5 megohms.

Production of this Model was delayed a full year pending careful study by Superior's engineering staff of this new method of testing tubes. Don't let the low price mislead you! We claim Model 82A will outperform similar looking units which sell for much more—and as proof, we offer to ship it on our examine before you buy policy.

Model 82A comes housed in handsome, portable Saddle-Stitched Texon case. **\$36⁵⁰**
Only
(Picture Tube Adapter available for \$5.50 additional)

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.

Try any of the above instruments for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. **No Interest or Finance Charges Added!** If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC, INC.

Dept. D-707 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.

Name

Address

City Zone State.....

All prices net. F.O.B., N.Y.C.

- Model 70 Total Price \$15.85 \$3.85 within 10 days. Balance \$4.00 monthly for 3 months.
- Model 82A Total Price \$36.50 \$6.50 within 10 days. Balance \$6.00 monthly for 5 months.
- Include Model 82A Picture Tube Adapter at \$5.50

Dr. BRUNO FURST'S

*School of Memory
and Concentration*

WILL SHOW YOU HOW TO

Remember

**NAMES, FACES, FACTS,
FIGURES & BLUEPRINTS**

For Details See The Article On
Page 77 In This Issue.



**School of Memory
and Concentration**

365 West End Avenue,
New York 24 • Schuyler 4-8299

15 One-Evening Projects



And 63 Other Toys and Games You Can Make

OUR 192-page book TOYS AND GAMES YOU CAN MAKE gives detailed plans for making 78 action toys, thrilling games and fascinating playthings (15 of the projects can be completed in just one evening). Only ordinary hand tools are needed, and our simple, easy-to-follow plans show you exactly HOW to proceed. The detailed drawings, photographs, materials lists and step-by-step instructions make it easy as A-B-C.

IT'S EASY! IT'S FUN! SAVE MONEY, TOO!

This giant collection of plans for toys ranges from those for pull toys for tiny tots to those for a suitcase-size powercycle for teenagers—it includes something for every child or young adult. You'll have fun, and you'll pocket substantial cash savings by making these projects yourself.

ORDER YOUR COPY—NOW!

Ordinarily a book like this would sell for \$3.00 or more, but while our first edition lasts we will send you a copy for only \$1.95. The quantity is limited, so act now. Attach your check or money order to the coupon below. We guarantee complete satisfaction or your money will be refunded.

NO MORE SMASHED FINGERS!

Atlas NAIL DRIVER and SCREW STARTER

Drives nails safe and straight into wood, concrete, metal or brick — in corners, hard-to-reach places — anywhere. No more lost tempers, bent nails or damaged surfaces due to hammer "misfiring". Ideal for Do-It-Yourselfers, Housewives — anyone who uses a hammer.

MONEY
BACK
GUARANTEE



Special Introductory Price **\$1** Each, Postpaid

Send cash, check or money order. No C.O.D.'s, please.

K-J COMPANY


1423 S. 2nd St. • Milwaukee 4, Wis.

HYPNOTISM RECORD & HAND DISC



Use For
Hypnotizing
Others and
Self-Hypnosis

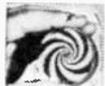Use our Hypnotism Record on groups or individuals. Ends by passing hypnotic control to you. Ride two—for Self-Hypnosis. Has fascinating Electric Metronome, Echo Chamber, background, Free Eye Fixation Spots & instructions. Unbreakable 78 rpm Extended Play Record. Satisfaction Guaranteed or Money Back. Only **\$4.95** ppd.



New Invention
Has Hypnotic
Revolving
Lens

Hold the Hypnotic lens in front of the person you want to Hypnotize. Vibrate the Coin. This sets the hypnotic lens into motion. It captures and holds your subject's gaze. Get this amazing hypnotic aid complete with secrets and instructions. Money Back if not d-lighted. Only **\$1.00** ppd.

HYPNOTIC-AIDS, Dept. RX-1, 1133 Broadway, N. Y. C. 10

Enc. \$1.00 — send "Hypno-Coin" Name

Enc. \$4.95 — send "Record Kit" Address

City State

SCIENCE and MECHANICS MAGAZINE, Dept. 506
450 East Ohio Street, Chicago 11, Illinois

Enclosed is \$1.95, for which send me, all charges prepaid, a copy of the deluxe edition of your 192-page handbook, TOYS AND GAMES YOU CAN MAKE. If I am not completely satisfied, I may return the handbook within 5 days for full refund. I take no risk.

NAME

ADDRESS

CITY ZONE STATE

NOW!
at a price
you can afford!

MAKE MORE MONEY in TELEVISION RADIO-ELECTRONICS

**BETTER... MORE COMPLETE... LOWER COST...
WITH NATIONAL SCHOOLS SHOP-METHOD
HOME TRAINING!**

BETTER... Training that is proved and tested
in Resident School shops and
laboratories, by a School that is
the **OLDEST** and **LARGEST** of
its kind in the world.

MORE COMPLETE... You learn **ALL PHASES** of
Television-Radio-Electronics.

LOWER COST... Other schools make several courses
out of the material in our **ONE
MASTER COURSE**... and you
pay more for less training than
you get in our course at **ONE
LOW TUITION!**



These
two FREE books will
show you how!

You get all information
by mail... You make
your own decision... at
home! **NO SALESMAN
WILL CALL**

TOP PAY... UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry!
Trained technicians are in growing demand at excellent pay—in
ALL PHASES, including Servicing, Manufacturing, Broadcasting and
Communications, Automation, Radar, Government Missile Projects.

**NATIONAL SCHOOLS SHOP-METHOD HOME
TRAINING**, with newly added lessons
and equipment, trains you in your
spare time at home, for these unlimited
opportunities, including many more
technical jobs leading to supervisory
positions.

**YOU LEARN BY BUILDING EQUIPMENT WITH
KITS AND PARTS WE SEND YOU.** Your
National Schools course includes
thorough *Practical* training—**YOU
LEARN BY DOING!** We send you
complete standard equipment of profes-
sional quality for building various
experimental and test units. You advance
step by step, perform more than
100 experiments, and you build a
complete TV set from the ground up,
that is yours to keep! A big, new TV
picture tube is included at no extra
charge.

EARN AS YOU LEARN. We'll show you
how to earn extra money right from
the start. Many of our students pay
for their course—and more—while
studying. So can you!

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident
School at Los Angeles, the world's TV capital,
start **NOW** in our big, modern Shops, Labs and
Radio-TV Studios. Here you work with latest
Electronic equipment—professionally installed
—finest, most complete facilities offered by
any school. Expert, friendly instructors. Personal
attention. Graduate Employment Service. Help
in finding home near school... and part time
job while you learn. Check box in coupon for
full information.

**LESSONS AND INSTRUCTION MATERIAL ARE
UP-TO-DATE, PRACTICAL, INTERESTING.**
Every National Schools Shop-Method
lesson is made easy to understand by
numerous illustrations and diagrams.
All instruction material has been de-
veloped and tested in our own Resi-
dent School Shops, Laboratories and
Studios.

SEND FOR INFORMATION TODAY... It can
mean the difference between **SUCCESS**
and failure for you! Send for your
FREE BOOK "Your Future in
Television-Radio-Electronics" and
FREE Sample Lesson. Do it **TODAY!**
while you are thinking about your
future. It doesn't cost you anything to
investigate!

GET THE BENEFITS OF OUR OVER 50 YEARS EXPERIENCE

Approved for
GI Training



NATIONAL SCHOOLS

Los Angeles 37, Calif.

YOU GET...

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

**SHOP-METHOD HOME TRAINING
COVERS ALL PHASES OF INDUSTRY**

1. Television, including Color TV
2. Radio AM & FM
3. Electronics for Guided Missiles
4. Sound Recording and Hi-Fidelity
5. FCC License
6. Automation and Computers
7. Radar & Micro-Waves
8. Broadcasting and Communications

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

MAIL NOW TO
NATIONAL SCHOOLS, Dept RKK-40
4000 S. FIGUEROA ST. LOS ANGELES 37, CALIF.
Rush free TV-Radio "Opportunity" Book and sample
lesson. No salesman will call.


NAME _____ AGE _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

Check if Interested **ONLY** in Resident School training at Los Angeles
VETERANS: Give date of Discharge _____



You are invited to become a charter subscriber to

MOBILEHOME Journal

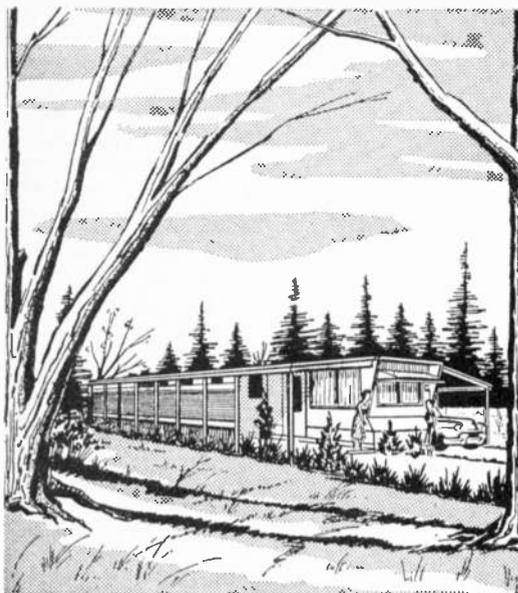

MOBILEHOME JOURNAL, unlike any other publication in its field, recognizes that the mobilehome living story has two sides—male and female. Thus it will include information not only for the head of the house, but also for the heart of the house—features on subjects of vital interest to women as well as articles for the men of the family.

ON SALE APRIL FIFTH

You are cordially invited to become a charter subscriber to MOBILEHOME JOURNAL, the first publication in its field dedicated to serving the interests and needs of the complete family unit. You will find features such as these in each exciting issue:

- HOW TO SELECT YOUR NEW MOBILEHOME—a wealth of information for the veteran mobilehomer—and for the novice.
- THE CASE FOR AIR CONDITIONING—a complete analysis of what this essential feature can mean to the typical mobilehomer.
- WHY THEY RELAXED THEIR ZONING—this hard-hitting article explains why a town that once fought tooth and nail against "those gypsies in the trailer camp" has done a complete about-face.
- LET'S HIT THE ROAD—pointers for travel trailer fans on how to enjoy a camp-out in high style—high in everything but cost.

The first issue of MOBILEHOME JOURNAL goes on sale April 5th. It will be an issue you won't want to miss. You can assure yourself of receiving it and the succeeding five issues—six in all—at the special *half-price* charter subscription rate, by filling in the coupon below and mailing it today. Reserve your copy of the first issue now!

HALF-PRICE CHARTER SUBSCRIPTION COUPON

MOBILEHOME JOURNAL, Dept. 565C
527 Madison Ave., New York 22, N. Y.

Please enter my Charter Subscription to Mobilehome Journal at the special, half-price rate, six issues for \$1.00.

- Cash enclosed
 Please bill me

NAME _____ (PLEASE PRINT)

ADDRESS _____

CITY _____ ZONE _____ STATE _____

(THIS OFFER EXPIRES APRIL 4, 1960)

BECOME A RADIO TECHNICIAN For Only \$22.95

BUILD 16 RADIO

Reg. U. S. Pat. Off.

CIRCUITS AT HOME

All Guaranteed to Work!

Progressive Radio "Edu-Kit"®

PRACTICAL only HOME RADIO COURSE \$22.95



NOW INCLUDES

- ★ 12 RECEIVERS
- ★ TRANSMITTER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR
- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed

Unconditional Money-Back Guarantee

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc. for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.

YOU DON'T HAVE TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. **THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL.**

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio, Electronics Tracer and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for Televising, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth more than the price of the "Edu-Kit" of \$22.95. The Signal Tracer alone is worth more than the price of the entire Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a Professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer, and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools; a professional electric soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator. In addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive study materials with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

FREE EXTRAS

- SET OF TOOLS
- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRENCH-SET
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE • QUIZZES
- TELEVISION BOOK • RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • FCC AMATEUR LICENSE TRAINING • PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Stalilis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

FROM OUR MAIL BAG

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Snuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of radio work. The Troubleshooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.

ORDER DIRECT FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7

- Send "Edu-Kit" postpaid. I enclose full payment of \$22.95.
- Send "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
- Rush me FREE descriptive literature concerning "Edu-Kit."

Name

Address

PROGRESSIVE "EDU-KITS" INC.

Progressive Building, Dept. 506 NN, 1184-86 Broadway, Hewlett, N. Y.

Do YOU Like a Good Mystery?

Connoisseurs of the *best* in mystery stories read

ELLERY QUEEN'S Mystery Magazine

The World's Leading Mystery Magazine

Here are some of the reasons why it's the leader—here and abroad (six separate foreign editions):

- **WORLD'S BEST MYSTERY STORIES** selected and edited each month by Ellery Queen, the finest mystery editor in the business, able to secure the best mystery and suspense stories written. Since its inception in 1941, EQMM has published stories by no less than seven Nobel Prize and twenty Pulitzer Prize authors.
- **BEST MYSTERIES OF THE MONTH** reviewed by the famed critic Anthony Boucher, plus a complete listing of all new mystery and suspense hardbounds and paperbacks.
- **SPECIAL SUBSCRIBER COVER** conservatively designed for the home, not available on newsstands.
- **SPECIAL "INVENTORY" PRICES** on paperback titles—big savings on topflight thrillers; big savings on hardbound books, too; and a mail book shopping service that enables you to order mystery books not available at local stores.
- **THREE SPECIAL ISSUES** each year—these sell for 50¢ on the newsstands; subscribers get them at no extra cost.
- **MONEY-BACK GUARANTEE.**

These exclusive features make *every* issue of *Ellery Queen's Mystery Magazine* a special treat to everyone who enjoys stories of suspense, crime and mystery. To start receiving your copy every month, send in the coupon below today!



ELLERY QUEEN'S MYSTERY MAGAZINE, Dept. 565B, 527 Madison Ave., New York 22, N.Y.

Please enter my subscription to *Ellery Queen's Mystery Magazine* for:

- | | | |
|---|--|--|
| <input type="checkbox"/> 5 years, \$15.00 | <input type="checkbox"/> 2 years, \$7.00 | <input type="checkbox"/> Cash enclosed |
| <input type="checkbox"/> 3 years, \$10.00 | <input type="checkbox"/> 1 year, \$4.00 | <input type="checkbox"/> Please bill me |
| | | <input type="checkbox"/> Extend present subscription |

NAME _____ (please print)

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Learn Electronics

PREPARE FOR YOUR F. C. C. LICENSE—YOUR TICKET TO A BETTER JOB AND HIGHER PAY!



F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radiotelephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a **FIRST CLASS F.C.C. license**, and it does this by **TEACHING** you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand. The organization of the subject matter is such that you progress, step-by-step, to your specific objective—a first class F.C.C. license.

CORRESPONDENCE OR RESIDENCE CLASSES

Grantham training is available by correspondence or in resident classes. Either way (residence or correspondence), we train you quickly and well—no previous training required. Even a beginner may qualify for his first class license in a relatively short time.

FOUR COMPLETE SCHOOLS: To better serve our many students throughout the entire country, Grantham School of Electronics maintains four complete Divisions—located in Hollywood, Calif., Seattle, Wash., Kansas City, Mo., and Washington, D.C. All Divisions of Grantham School of Electronics offer the same rapid courses in F.C.C. license preparation, either by home study or in resident classes.

Get your First Class Commercial F.C.C. License Quickly

GRANTHAM SCHOOL OF ELECTRONICS

HOLLYWOOD CALIF.

1505 N. Western Ave. (HO 7-7737)
Hollywood, Calif.

SEATTLE WASH.

408 Marion Street (MA 2-7737)
Seattle, Wash.

KANSAS CITY MO.

3123 Gillham Road (JK 1-4370)
Kansas City, Mo.

WASHINGTON D.C.

821 - 19th Street, N.W. (ST 2-2614)
Washington, D.C.

This booklet **FREE!**



This free booklet gives details of our training and explains what an F.C.C. license can do for your future.

Upgrade Your Income with a First Class F. C. C. LICENSE

In resident classes or by home study, Grantham training is the easy way to learn more quickly and to prepare more thoroughly for F.C.C. examinations. And your first class F.C.C. license is the quick, easy way to prove to your employer that you are worth more money.

If you already have practical experience in radio-electronics, the Grantham course can add a knowledge of theory and an F.C.C. license to that practical experience. This is most important in qualifying you for higher pay and greater job security.

Our free booklet gives details of how you can prepare quickly for a better job in the rapidly expanding electronics industry. Clip the coupon below and mail it to the Grantham School nearest you.

MAIL COUPON TO SCHOOL NEAREST YOU

(Mail in envelope or paste on postal card)

TO: GRANTHAM SCHOOL OF ELECTRONICS

1505 N. Western • 408 Marion • 3123 Gillham Rd. • 821-19th, NW
Hollywood • Seattle • Kansas City • Washington



Gentlemen:

Please send me your free booklet telling how I can get my commercial F.C.C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____


Address _____

City _____ State _____

I am interested in: Home Study, Resident Classes E-OC

for a fascinating hobby, join the **ROCKHOUNDS!**

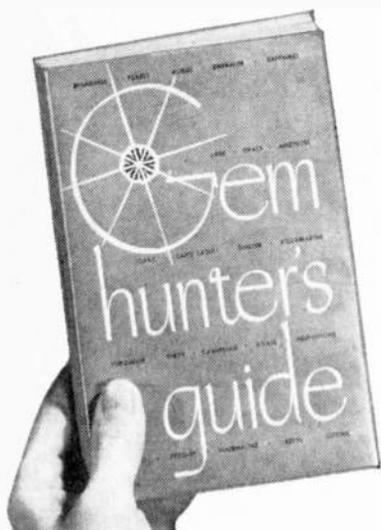get your copy of
the **GEM HUNTER'S GUIDE**
the all-time best-selling
guide to gem hunting



The **GEM HUNTER'S GUIDE** contains:

- 1034 ACTIVE GEM MINERAL LOCATIONS** verified and confirmed by regional experts or personal exploration. This is the most comprehensive, detailed listing of North American gem locations available to the hobbyist—or specialist.
- 81 MAPS OF HARD-TO-FIND AREAS**, the largest group of such pin-point accuracy maps ever published.
- 53 FULL-COLOR PHOTOS OF GEMS**—precious and semi-precious gemstones and minerals shown as they occur in nature.

The **GEM HUNTER'S GUIDE** also has:

- 1) Chapters on how to hunt for gem material and how to recognize it when you find it.
- 2) Chapters on how to identify gem material through field testing by checking color, hardness, crystal formation, transparency and other characteristics.
- 3) Special chapters, complete with lists of important discoveries, on diamonds and pearls.
- 4) A chapter on the fascinating and popular hobby of collecting and displaying fluorescent minerals under black light, including a complete table of fluorescent minerals.
- 5) A complete list of state mining and geological bureaus from which maps and publications may be obtained.
- 6) A complete list of museums having mineral displays and the cities in which they are located.
- 7) A complete list of colleges and universities equipped to help the gem seeker.
- 8) A complete bibliography of books and periodicals of importance to the gem hunter.

Order Now! Get your copy in time for the vacation season!

SCIENCE & MECHANICS MAGAZINE, Dept. 110

450 East Ohio Street, Chicago 11, Illinois

Please send me—for 5 days' **FREE EXAMINATION**—a copy of the "Gem Hunter's Guide" packed with pictures, maps, charts, expert advice telling where gems may be found. Unless completely satisfied with the book at the end of 5 days' examination, I may return it and owe nothing. Otherwise, I will keep it and send you \$3.95, plus 50¢ to cover postage and handling charges.

Name

Address

City, Zone & State

Save 50¢ postage and handling charges . . . by enclosing only \$3.95 WITH this coupon. Then WE will prepay ALL delivery charges. Return book within 5 days for full refund if not completely satisfied.

SEND NO MONEY

Examine FREE For 5 Days

SEND NO MONEY. Just fill out and mail this coupon and we will send the "Gem Hunter's Guide" to examine Free for 5 days at our risk. If you decide to buy the book, it may be the richest investment—in enjoyment and, perhaps, in cash returns—you ever make. So rush coupon for 5 days Free examination in your own home.

Terrific TRF Portable

You'll find the Terrific outstanding from the standpoints of sensitivity, selectivity, tone and volume—and it costs less than \$20

By FORREST H. FRANTZ, Sr.

IF YOU want a portable broadcast band receiver, but wish to avoid the cost and complexity of a superhet, the Terrific is the portable for you.

The first transistor, T1 (see Fig. 3.) performs the dual function of RF amplifier and first audio amplifier. The audio signal is introduced to T1 through capacitor C4. The audio output signal of T1 appears across R4 and is transferred to driver transistor T2 through capacitor C6. The RF signal is introduced to the base of T1 and appears across L2 after amplification. The high-Q tuning circuits C1A-L1 and C1B-L2 assure sharp tuning and high gain. Diode D is the detector. It rectifies the RF signal, and capacitor C7 smooths the peaks of the signal to provide an audio signal across volume control R7.



Transistor T2 is the audio output stage driver. The closed circuit jack between the driver and output stage permits headphone reception. The output stage (transistor T3) drives




The Terrific has a reflexed RF-audio stage, transformerless loudspeaker operation, and is laid out for growth to a superhet or communications receiver.


the loudspeaker directly. This stage is operated class A, but current consumption has been minimized. Current drain for the entire set is approximately 20 ma. A 45-ohm voice coil intercom-type speaker permits direct drive. Although this arrangement results in a comparatively low efficiency output impedance match, it eliminates the need for a space-consuming transformer or a miniature transformer which would compromise the frequency response and result in poor tone.

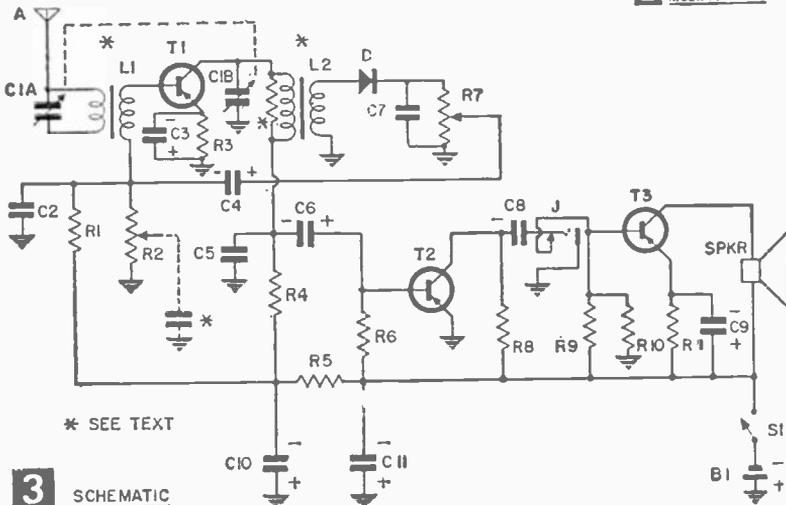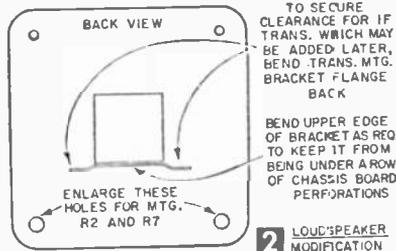Construction. Cut off the shaft of on-off switch S1 at the groove nearest the switch. Cut the shaft of tuning capacitor C1 to a 13/16-in. length. Cut the shafts of the volume control R7 and the control R2 to 7/16-in. lengths. Enlarge the speaker mounting holes on the voice coil connection side of the speaker to 1/4 in. and mount R2 and R7 in these holes. Bend out-



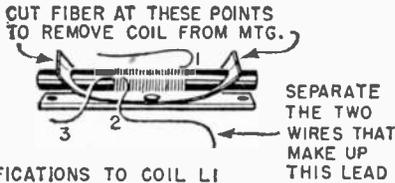

4 MODIFICATIONS TO COIL L1

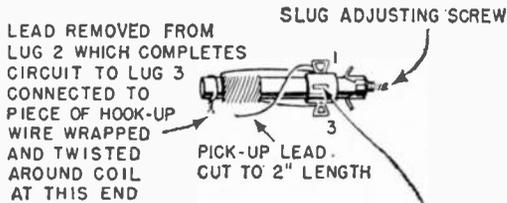

MODIFICATION AND DETAILS L2

LOOSEN LEADS CONNECTED TO LUG 2. LEAD WHICH COMPLETES CIRCUIT TO LUG 1 IS RECONNECTED

5

put transformer mounting flanges on the speaker up toward R2 and R7 slightly as shown in Fig. 2.

Remove the antenna loopstick coil L1 from its mounting board by cutting into the fiber strip that holds it on the board (Fig. 4). Separate the two leads that are soldered together to form the tap on L1. The wire on this coil is litz wire. Try not to break any of the strands, but if you do, apply solder further back on the lead ends.

Now disconnect the two leads connected to lug 2 of the interstage coil L2 (Fig. 5) and separate them. The loose lead which makes a complete circuit to lug 1 is reconnected to lug 2. Connect the other lead (which makes a continuous circuit to lug 3) to a piece of hook-up wire twisted around the end of the coil as shown. Cut the antenna pick-up lead soldered to lug 1 of the coil to a length of 2 in. for connection to the stator of C1B when the radio is assembled. Set the slug adjusting screw to protrude $\frac{1}{4}$ to $\frac{3}{8}$ in. out of the coil.

Next cut out and drill the panel and cabinet sides. These should not be metallic since complete metallic enclosure would shield the antenna coil from radio signals. Perforated Masonite was used for the top panel of the original model to simplify construction. Solid or perforated Masonite may be used for the sides. Although the Masonite perforations in front of the speaker are utilized for sound

transmission, other perforations must be blocked. A cardboard backing sheet was used to prevent front to back speaker sound interference; Fig. 6 shows the layout. Use a taper reamer to make the larger holes in the Masonite. The metal cabinet back is part of a commercially available cabinet, but you may cut and bend your own if you wish.

Cut the perforated Bakelite chassis board with a hacksaw and pocket knife (see Fig. 7). (Cut-outs A, B and C mount IF transformers if the set is converted to a broadcast superhet or a communications superhet, a procedure to be described in a future issue. They may be omitted if you do not wish to have conversion capability.)


Fasten the cardboard baffle to the perforated cabinet top with Duco cement. Mount the speaker, phone jack, tuning capacitor, and antenna coil as shown in Fig. 8. The side of the speaker on which the volume controls are mounted is held in place by a small metal clamp. This may be made from a strip of metal or by rebending a small bracket. Place

enough washers between the tuning capacitor and the Masonite board to obtain a $\frac{1}{4}$ -in. space between them. Fasten the Masonite cabinet front side to the tuning capacitor with a machine screw. Join the two pieces of Masonite to a bracket at the other end. Fasten the antenna coil to the cardboard with Duco cement in the position shown in Fig. 8.

One small piece of perforated Bakelite should be fastened to the antenna coil with Duco, another should be fastened above the speaker clamp with a nut to provide necessary lead tie-down points. Fas-

ten the Bakelite chassis board to the speaker with a machine screw in one of the tapped holes on the back of the speaker. If the output transformer mounting flange on the speaker projects into the chassis board cut-outs, bend it further to allow clearance. The chassis screw also fastens a strip of metal $\frac{1}{2} \times 1\frac{1}{2}$ -in. cut from a tin can. This strip is the common ground tie-down point. Cut gashes into the strip along all four sides so that you can crimp wires in place.

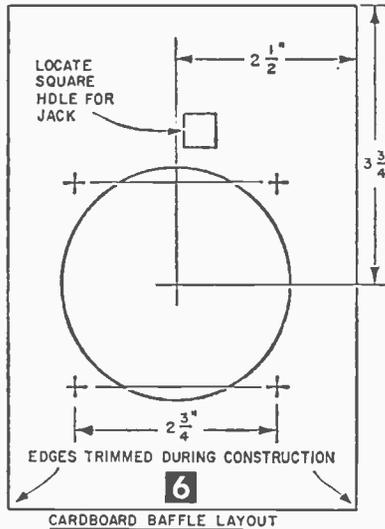Try to make your wiring and parts placement conform as nearly as possible to that shown in Fig. 8 if you wish to convert the set later. Make connections on the chassis board by passing the parts pigtailed and wire lead ends through perforations. The tight mechanical fit that results when two or three



CARDBOARD BAFFLE LAYOUT


parts pigtails are passed through one hole are very reliable electrically, but solder them for extra assurance. Cut excess lead lengths protruding through the bottom of the chassis board to about 1/16 in. Be careful to avoid passing leads through perforations so situated that leads can short circuit to the speaker frame.

Most of the resistors and capacitors mount above the chassis board as viewed from the back of the set. The transistors mount underneath. Leave transistor T1 pigtails at least an inch long for easy conversion to a superhet receiver later.

Mount the interstage coil, L2, near the back of the tuning capacitor. The resistor shown connected across the primary in the circuit diagram should be connected only if the set oscillates after it has been placed in the cabinet and aligned. It's value will be between 10K and 100K. Orient the coil approximately as shown in Fig. 8. Fasten a piece of aluminum foil 1 1/4 x 3 in. to the cardboard beneath the coil with Duco cement and make a ground connection to the ground tie-down strip from the bracket at the rear of the panel. Make battery leads about 9 in. long.

Three sections of the on-off switch are unused in this project. (They will be used if the set is expanded.) Set the on-off knob pointing straight up and down when the switch is "off." Then, when the switch is turned "on" it will point to the machine screw adjacent to it. Paint the head of this screw red to make it obvious when the set is "on."

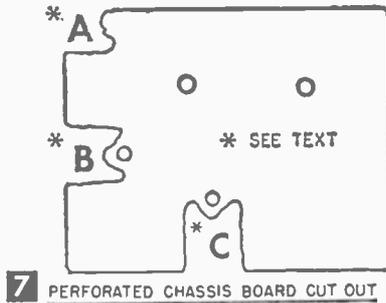The shaft of the tuning capacitor specified is slotted for a spring type push-on knob. If you wish to use a set-screw type knob, build the shaft up to full round with sol-



7 PERFORATED CHASSIS BOARD CUT OUT

der. Regardless of the knob you use, a plastic pointer may be fastened to it. The fine black line on the pointer is made by scratching the line into the plastic with an ice pick and flowing India ink into the scratch.

One of the controls, R2, is used only as a fixed resistance in this circuit. It may be replaced with

a fixed resistance of 10K if you don't intend to change the set to a communications superhet receiver later. Or, you may use it as a tone control of sorts by connecting a capacitor of 0.1 to 1 mfd to it as shown in dotted lines on the circuit diagram.

The battery B1 consists of six large penlite cells connected in series to provide 9v. To fasten the six cells together, lay them side by side on a smooth surface and drop a quantity of Duco cement between them. The negative ends of the batteries should be cleaned with a small file before the battery connections are soldered. Use as little heat as possible to solder these connections.


Drill two 1/4-in. holes in the metal cabinet back adjacent to the carrying handle to provide access to the antenna and RF trimmers, and drill a hole in the bottom to provide access to the RF coil-adjusting screw.

A whip-type antenna (see Materials List) was used on this set. The antenna is furnished with a jack and plug. Mount the jack and solder the plug into it. The antenna may be screwed onto the plug for non-portable use. For portable use, the antenna is left fastened in the two fuse clips provided on the outside of the Masonite back as shown in Fig. 9. The clip nearest the antenna coil is used for the connection.

To place the radio in the cabinet, place a piece of thin cardboard 2 1/2 x 8 1/2 in. along the rear of the metal cabinet and extending about 1/2 in. up the sides. Place the 9-v. battery on the cardboard against the cabinet back and ends. Place a strip of wood 1/4 in. thick and about 6 3/4 in. long over the battery. Clamp the strip to the metal cabinet with a screw through the cabinet hole between the batteries. Push the battery leads back into the cabinet so that they won't interfere with the operation of the tuning capacitor. Ease the radio into the cabinet and fasten with self-tapping screws.

Since the radio may be used in the "handle up" or "flat on its back" positions, provide rubber feet for both positions to avoid scratching furniture. (Fasten grommets to the cabinet with rubber-to-metal cement.) Paint or ink the tuning dial calibration on the cabinet front.


Alignment. Since there's no IF alignment

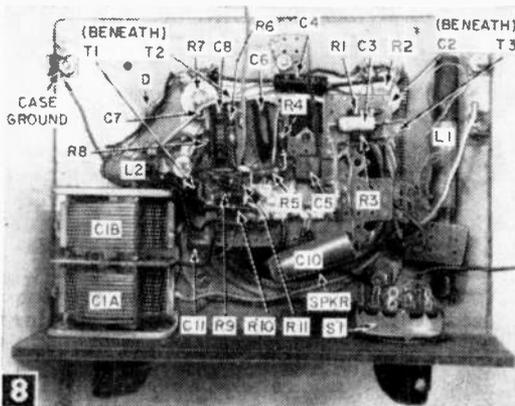

8 Parts layout of the Terrific.

MATERIALS LIST—TERRIFIC	
Desig.	Description ($\frac{1}{2}$ Watt Carbon Resistors)
R11	270 ohms
R5	470 ohms
R3, R8	1 K
R4, R10	2.2 K
R9	3.3 K
R1	47 K
R6	68 K
R2, R7	10K volume control (Lafayette VC-34)
C2, C7	.001 mfd. subminiature capacitor (Lafayette C-609)
C5	.01 mfd. subminiature capacitor (Lafayette C-612)
C4, C6	4 mfd., 6v. subminiature capacitor (Lafayette CF-101)
C8	10 mfd., 15v. electrolytic capacitor (Lafayette CF-122)
C3, C9	30 mfd., 6v. subminiature capacitor (Lafayette CF-104)
C10	100 mfd., 15v. electrolytic capacitor (Lafayette CF-126)
C11	160 mfd., 15v. electrolytic capacitor (Lafayette CF-127)
C1A-B	2 gang 365 mmf. variable capacitor (Lafayette MS-142)
T1	Texas Instruments 2N252 transistor
T2	Raytheon CK722 transistor
T3	Texas Instruments 2N185 transistor
O	Sylvania 1N 34A germanium diode
B1	battery, 9 volts (6 Ray-O-Vac 7R, Burgess Z or Eveready 915 penlite cells in series)
J	miniature closed circuit phone jack (Telex JPM-01)
L1	antenna coil—see text for modification (Miller 2001)
L2	interstage coil—see special instruction in text (Miller 2002 antenna coil)
S1	4P, 2T switch and knob—use one section for on-off switching (Mallory 32 42J)
SPKR	$3\frac{1}{2}$ " speaker, 45-ohm voice coil (Quam 3A07Z45)
1	perforated Bakelite chassis board (Lafayette MS-305)
1	perforated Masonite board (Lafayette ML-81)
2	miniature knobs (Lafayette MS-185)
1	knob for tuning dial
1	metal cabinet back (Use back of ICA 29343 or make)
1	handle for cabinet (available in hardware or variety store)
A	whip antenna (Lafayette F-440)

or mixer tracking to worry about, alignment procedure is extremely simple. The preliminary adjustment of L2 described in the construction procedure will cause the set to be nearly in alignment at the low end of the broadcast band when construction is completed. The set should be mounted in the cabinet for final alignment. Align the high-frequency end of the band by tuning in a weak station between 1400 and 1550 kilocycles and adjusting the trimmer capacitors on the side of the tuning capacitor C1 for maximum output. The antenna trimmer will

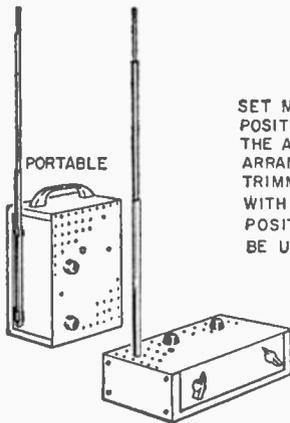


SET MAY BE USED IN EITHER OF POSITIONS SHOWN BY CHANGING THE ANTENNA MOUNTING ARRANGEMENT. THE ANTENNA TRIMMER SHOULD BE TUNED WITH THE ANTENNA IN THE POSITION IN WHICH IT WILL BE USED MOST FREQUENTLY

9

seem to have the greatest effect on tuning. Adjust it till the station comes in at a point on the dial where the RF trimmer tunes the signal to maximum without being all the way in or out. Then tune the set to a weak station between 600 and 700 kilocycles and adjust the tuning slug of the interstage coil L2 for maximum output. Reset the tuning dial to the high frequency end of the broadcast band and readjust the RF trimmer for maximum output.

Out of the metal cabinet the receiver may oscillate at the higher frequency tuning capacitor settings. If it doesn't oscillate when you fasten it in the cabinet and align it, this doesn't matter. But, if the set oscillates when fastened in the cabinet, you'll have to take remedial measures. First, check to be sure that the lead from L2 to the collector of T1 is as short as possible and is dressed against the speaker frame. The same applies to the lead to C1B. If the set still oscillates when it's fastened in the cabinet, connect a 100K resistor across the primary of L2 as shown in the circuit diagram. If oscillation still occurs, try 47K, 33K, and 10K, in turn till oscillation is eliminated. In the original receiver, the 100K resistor did the trick.

Iron Does Double Duty

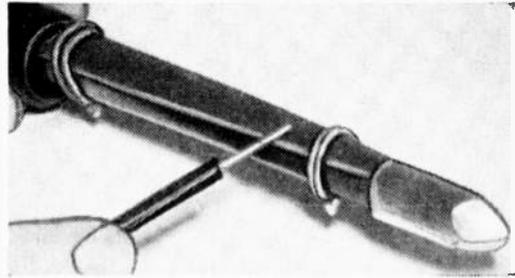

• Quite often a small file is needed to file corroded parts and wires clean before the application of solder. If you want to eliminate the necessity of hunting up such a file every time you have a soldering job to do, attach one to your iron's barrel with heavy solid wire. (You may have to break off the file's tang if it is longer than your iron's barrel.)—J.A.C.


Extending Radio Battery Life

• Many portable battery-operated receivers tend to cease operation long before the batteries have terminated their useful life. This is usually due to the set's oscillator shutting off because of reduced voltages on the tube elements. By increasing the signal feed-back voltage however, the oscillator will continue operation even on reduced voltages. A few extra turns of wire added to the "tickler" winding of the oscillator coil will boost the feedback enough to insure a longer battery life, and considerable saving in replacement dollars.

SIX-METER Amateur Band Converter

If you're a Technician or General Class Amateur interested in six-meter operation, this simple low-cost converter will prove a boon to you for either fixed or mobile use

By JOE A. ROLF,
K5JOK

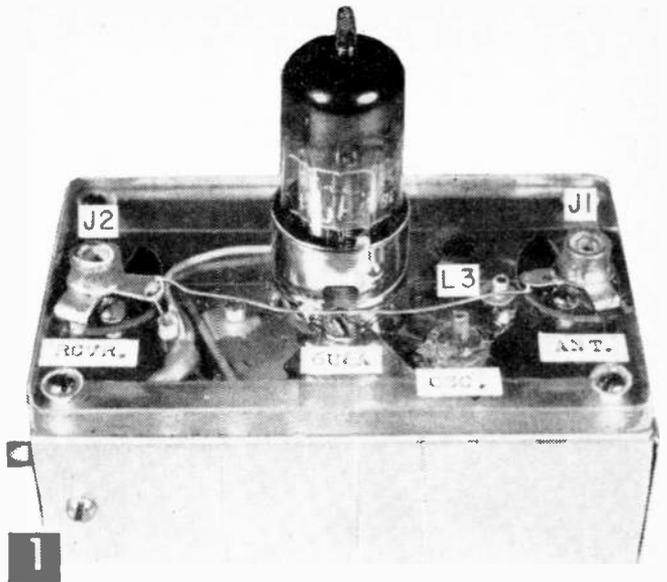

THIS converter can be constructed with parts from most ham scrap-boxes, but even with new parts its cost will not run much over \$5! Naturally, with only one tube, it is not as hot as many commercial multi-tube units, but it will generally hold its own with crystal-controlled converters costing much, much more.


A 6U8 triode-pentode is used—the pentode section as a mixer, the triode as a tunable local oscillator. Tuning is done with the receiver to which the converter is connected, as with a crystal-controlled unit. But with the local oscillator tunable from 47 Mc. to 54 Mc., a number of different intermediate frequencies can be employed.

With a home broadcast or car radio, for example, the oscillator can be set at 49.4 Mc. so that 49.9 Mc. to 51 Mc. is received when the receiver is tuned across the broadcast band. With a simple screwdriver adjustment, the oscillator frequency can be changed for coverage of any desired 1-megacycle segment of the band. When used with a communications receiver, the oscillator can be set at 48 Mc. and the entire six-meter band covered by tuning from 2 Mc. to 6 Mc. This higher IF not only gives continuous tuning, but provides better image rejection than the commonly used lower IF.

A 2½ x 4-in. piece of ¼-in. Plexiglas, available at hobby shops and many radio supply houses, is used for the chassis. This material can be worked with simple hand tools and greatly simplifies construction. Construction, however, can be modified to allow the use of a mini-box or similar metal box.

Details of the chassis are shown in Fig. 2. Screw holes for the tube socket and antenna

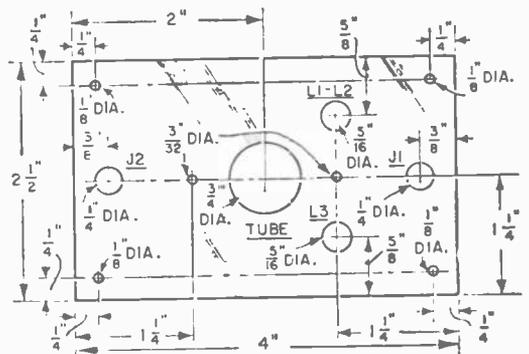
low in cost and simple in construction, the six-meter converter measures only 2½x4 in. when placed in its homemade 1/32-in. aluminum cabinet. With the tube shield in place it is less than 3½ in. high. The cabinet is made in one piece with the exception of the removable end-plate through which the power card passes.



2 CHASSIS (¼" PLEXIGLAS)

jacks, J1 and J2, are not shown and should be positioned for the particular sized component used; 1/8 x 1/4-in. machine screws mount all parts. By using a 3/32-in. hole, the screws will tap themselves into the soft Plexiglas. The four 1/8-in. holes are for mounting the chassis to its cabinet with 1/8 x 1/2-in. screws.

The tube socket is placed in the middle of the chassis, the input and output jacks are centered at each end of the chassis, 3/8-in. from the edge. Phono jacks are used and are mounted on top of the chassis with the solder lugs extending through a 1/4-in. hole in the chassis. One jack is designated "Antenna Input", the other, "Converter Output." If the converter is intended primarily for mobile use, auto radio antenna jacks should be used in place of the phono jacks for direct connec-

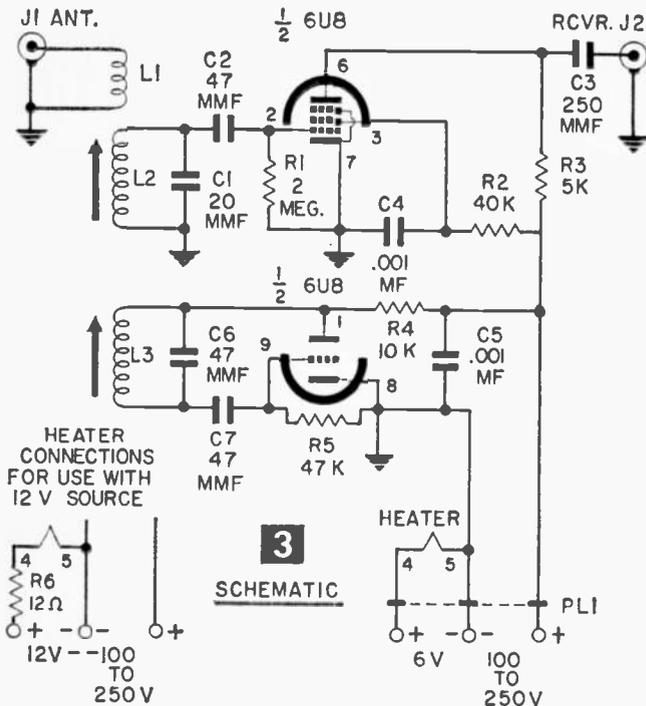

tion to the auto radio, or auto antenna.

Mount a three-lug terminal strip on the underside of the chassis between the output jack and tube socket. The ground (B-minus) and B-plus leads of the power cord and R3 connect to this strip. Capacitor C3 connects from the plate lead end of R3 to the lug on the output jack.

The oscillator and mixer coil forms are mounted midway between the tube socket and the antenna jack. It should be noted that two different types of slug-tuned forms were used. These were 1/4-in. dia. scrap-box components, one from a discarded BC radio, the other from a TV set. The form for the oscillator coil had a press-in type mounting and was pressed into a 5/16 in. chassis hole and secured with Duco cement. The other, a plastic form, had no mounting clip and was glued to the chassis with the slug screw pointing downward. A hole in the bottom of the cabinet permits adjustment of the slug.

Two dissimilar coil forms were used to illustrate the two methods which can be employed in mounting the coils, depending upon the forms available. In the event your scrap-box does not contain suitable slug-tuned forms, they can be obtained from a radio service shop for only a few cents. Most servicemen save discarded coil forms and you'll probably have several dozen to choose from.

For simplest construction, lay out the converter as shown in Figs. 1, 2 and 4. However, the only critical placement (besides keeping leads short) is in the positioning of the RF coils. The mixer and oscillator coils should

be about 1 1/4-in. apart as there is no oscillator voltage injection other than by the coil coupling, tube capacity, and stray circuit capacity. Any form of direct coupling of the oscillator to the mixer circuit will result in excessive pulling (a change in oscillator frequency when the mixer is tuned). The oscillator has sufficient output for good conversion efficiency without direct connection to the mixer.

The cabinet is a three-sided box of 1/32-in. aluminum (see Fig. 5). The power cord of the unit passes through the removable end of the cabinet without unsoldering the power cord plug. As with the chassis, the 1/8-in. machine screws tap themselves into 3/32-in. holes.

The converter is powered by the receiver with which it is used. Requirements are low; 100 to 250v for the plate supply and 6.3 (at 450 ma.) for the filament. These voltages are obtainable from most receivers with the aid of their schematic. A power cord

from the shack's receiver or the auto radio will also prove handy for powering other equipment.

The only difficulty that might be encountered will be with a receiver having 12-v heaters or with an ac-dc set. In the case of a 12-v BC receiver or auto radio, the filament dropping resistor (R6) should be added to the circuit as shown.

If used with an ac-dc type receiver, B-plus voltage for the converter can be taken from

MATERIALS LIST—6-METER CONVERTER

Desig.	Description
C1	20 mmf. ceramic or mica
C2	47 mmf. mica
C3	250 mmf. mica
C4	.001 mmf. disc ceramic
C5	.001 mmf. disc ceramic
C6	47 mmf. ceramic or mica
C7	47 mmf. mica
J1, J2	standard phono jacks
L1	3 turns #28 DCC wire, close-wound next to grid end of L2
L2	4 turns #28 DCC wire, close-wound on 1/2" slug-tuned form
L3	3 turns #22 DCC or enamel wire, close-wound on 1/4" slug-tuned form (see text)
PL1	3-contact power plug (Cinch-Jones P-303-FHT & S-303-FHT)
R1	2 megohm, 1/4 watt
R2	40,000 ohm, 1/2 watt
R3	5,000 ohm, 1/2 watt
R4	10,000 ohm, 1/2 watt
R5	47,000 ohm, 1/4 watt
R6	(for 12-v heater source only) 12 ohm, 4 watt
1	6U8 tube
1	small button 9-pin socket, with shield
10	1/8 x 1/4" machine screws
4	1/8 x 1/2" machine screws
1 pc	1/4" Plexiglas, 2 1/2 x 4"
1 pc	1/2" (.0312) aluminum sheet, 6 x 7"

An underside view of the Plexiglas chassis showing the placement of components. Three-conductor cable passes through the chassis end-plate.

the receiver, but the ground connection of the converter's antenna coupling coil (L1) should be made with a .001 mfd. capacitor. Filament voltage will have to be supplied by an external 6.3-v filament transformer, or a 6-v battery.

A 2-ft. piece of 52-ohm coax connects the output of the converter to the receiver antenna terminals. This lead can be any convenient length, though an excessively long lead will result in some loss of output. The input lead will depend upon the type of antenna used. Both leads should be fitted with phono plugs.



Alignment of the converter is best done with the aid of a grid dip meter. Since this is a popular piece of equipment with hams, you should have no trouble borrowing one if you don't already have one. With power applied to the converter, check the oscillator output with the meter. Output should be from 47 Mc to 54 Mc, or can be adjusted over this range by changing the coil spacing. Once the oscillator is working, adjust its frequency for the desired IF. If the converter is to be used with a BC receiver, for instance, the oscillator should be set 550 Kc below 50 Mc, or at 49.45 Mc. You will not be able to adjust the oscillator to the exact frequency with the meter, but accurate adjustment can be made later.

Next, adjust the mixer to about 52 Mc with the meter.

With a low IF (such as 550 Kc) some pulling will be noted. This, however, is to be expected at 50 Mc. After the mixer frequency has been adjusted, readjust the oscillator frequency again.

Once the converter has been roughly aligned with a grid dip meter, accurate alignment can be made with the aid of a six-meter transmitter.

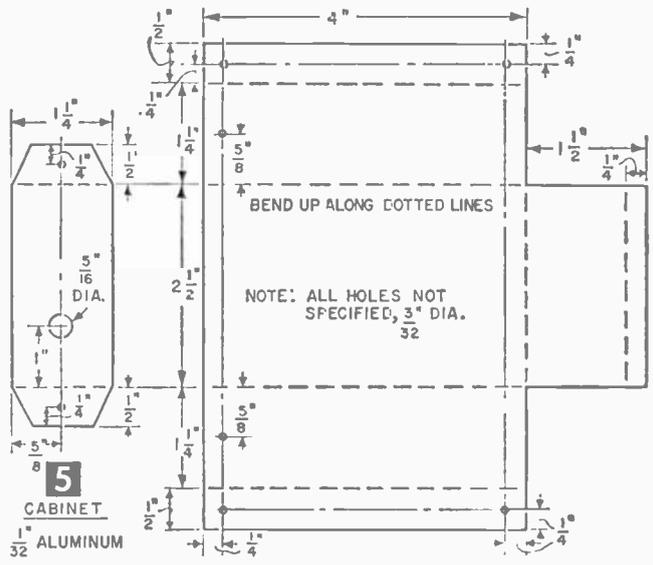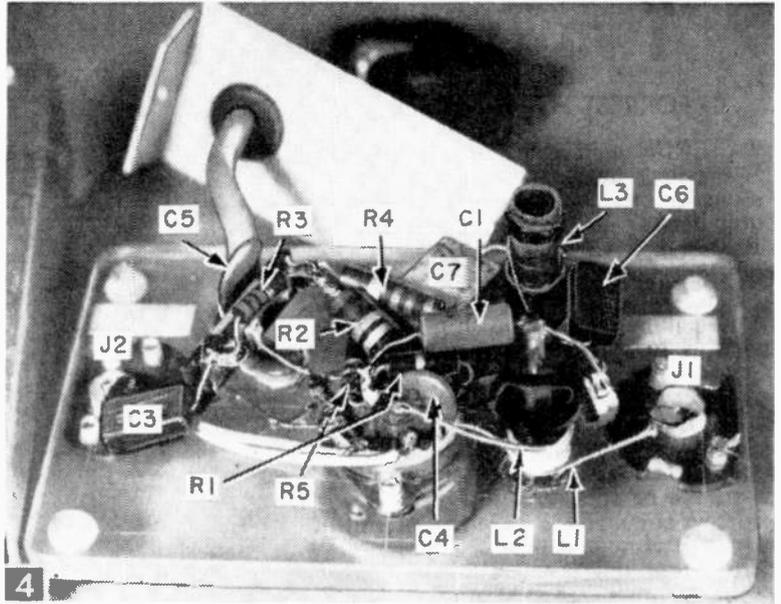While receiving a known, crystal-controlled frequency, adjust the oscillator until the sig-



nal is tuned at the proper frequency by the IF receiver. A 50.1 Mc signal should be read at 650 Kc if a BC receiver is used, or at 2.1 megacycles with a 2 megacycles intermediate frequency.

With fixed operation, excellent performance has been obtained with a simple folded dipole, while the use of a two-element beam has shown that the converter has only slightly less gain and sensitivity than a multi-tube converter using a similar antenna system. For mobile operation, the converter has been used with a 51-in. BC-type antenna and has given very good performance on both ground-wave and skip reception.

Two Transistor Utility Amplifier

By FORREST H. FRANTZ, Sr.

SCIENCE and electronic experimenters need an audio amplifier as a basic piece of laboratory equipment. An audio amplifier is useful for amplifying low audio signals, detecting and measuring low audio and ac voltages, signal tracing electronic equipment, and as an auxiliary amplifier to bring earphone equipment signals up to loudspeaker level.

This amplifier will cost about \$15 to build. It is a compact, self-contained unit that has its own batteries and loudspeaker; it needs no external power source or speaker. The input impedance is sufficiently high to permit its use with vacuum-tube circuits. Output terminals are provided for connection to an external meter so that a multimeter may be used in conjunction with the amplifier for measuring very small ac voltages and for audio signal tracing. An RF-IF probe which extends its use for signal tracing is also described.

Circuit Operation. The circuit is shown in Fig. 2. The input signal is introduced at the jack J. Capacitor C1 isolates any dc components which may accompany the signal from the amplifier, but passes audio signals. The signal is presented across R1 and R2. Resistor R1 is in the circuit to keep the input impedance high. This introduces some loss, and if the amplifier is to be used with transistor circuits exclusively, R1 may be eliminated, with a direct connection from J to R2 for increased gain. R2 is the volume control, coupled to T1 through transformer TR1. The primary impedance of TR1 is 10,000 ohms, and the secondary impedance is 2,000 ohms. Thus, the input impedance of T1 is reflected back to the amplifier at 5 times its value.


Resistors R3 and R4 bias the base of T1. Capacitor C3 bypasses audio frequency signals. Resistor R5 biases the emitter of T1 and stabilizes operation over a wide range of temperature. Capacitor C4 bypasses audio signals. Without C4, gain would be reduced considerably. Capacitor C5 bypasses high-frequency signals in the collector circuit of T1 which might otherwise



1 The utility amplifier can be used with a microphone as above or as a voltmeter audio amplifier.

cause the amplifier to oscillate. Transistor T1 is coupled to T2 through TR2, an impedance matching transformer. Resistors R6 and R7 set base bias for T2, and C6 bypasses audio frequencies. Resistor R8 provides temperature stabilization for T2.

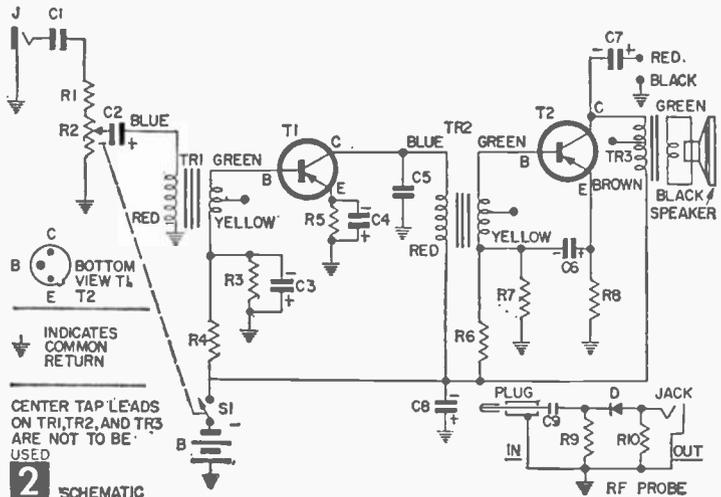The collector of T2 is coupled to the speaker through the output transformer TR3. This transformer matches the relatively high collector load requirement (500 ohms) to the much lower (3.2 ohms) speaker impedance. Capacitor C7 carries the output signal from



the collector of T2 to an output terminal. An ac voltmeter or an oscilloscope may be connected from this terminal to monitor the output voltage of the amplifier.

Construction. The amplifier may be con-

structed in the smallest amount of time if all parts are available when construction is begun (see Materials List), and if this work sequence is followed: 1) Prepare circuit board; 2) prepare panel board; 3) mount components on circuit board; 4) wire circuit board; 5) mount components on panel board; 6) wire panel board; 7) mount circuit board on panel board, and make interconnections.

The circuit board as purchased is the right size, but eight of its perforations must be enlarged to $\frac{1}{8}$ in. (layout is shown in Fig. 3).


Panel board layout is shown in Fig. 4. The volume and tone of the unit will be improved if a piece of cardboard with a $2\frac{3}{8}$ in. dia. hole for the speaker opening is cemented to the back of the panel board. Trace dimensions from the panel board. The center for the speaker hole center is located by tracing the board onto the cardboard and drawing straight lines through diagonally opposite hole location marks.

Next, mount transformers TR1, TR2, and TR3 (see Fig. 5). Then, mount and wire the remaining components, making wiring connections on the bottom of the circuit board.


Now mount the components on the panel board and wire as shown in Fig. 6. Cut R2's shaft to a length of $\frac{3}{4}$ in. before you mount it. Fill the contact eyelets on the battery holder with solder to avoid later battery contact trouble.

Note that two machine screws (Fig. 6) are $1\frac{1}{4}$ in. long. These are fastened to the panel board with nuts and lock-washers. One of these machine screws serves for speaker mounting, but both are provided to support the circuit board. A nut is placed on each screw with the top of the nut $\frac{7}{8}$ in. from the panel. The circuit board is mounted on these and fastened with a nut on each screw. Don't turn them tight initially. You may want to loosen the circuit board to make inter-connections between circuit and panel board. Interconnections are:

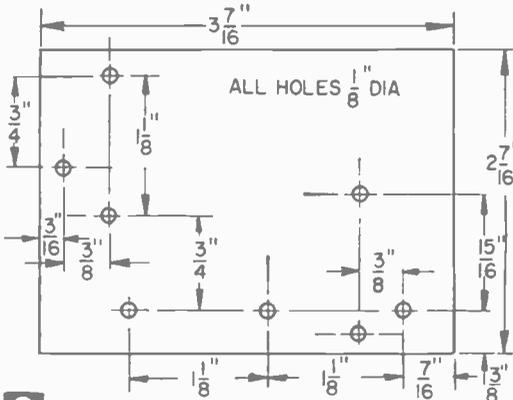
- 1) TR3 secondary to loudspeaker;
- 2) C7 (negative) to T2 Collector;
- 3) S to circuit board negative bus;
- 4) center terminal R2 to C2 negative;
- 5) battery plus to circuit board common return.



3 CIRCUIT BOARD LAYOUT (TOP VIEW)

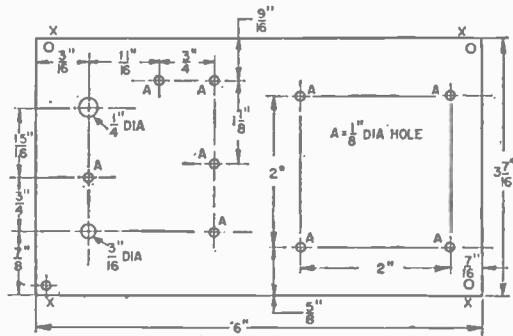

4 PANEL BOARD FRONT VIEW

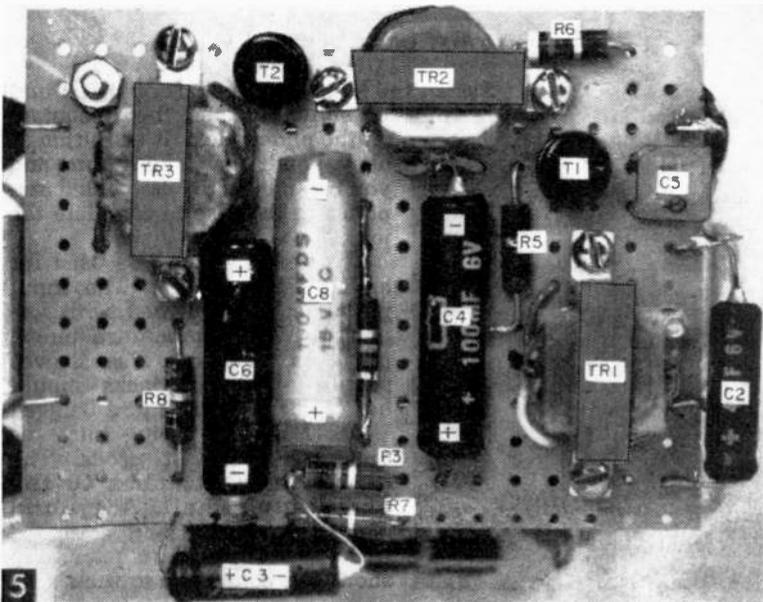


5

Circuit board mountings.

MATERIALS LIST—UTILITY AMPLIFIER


Desig.	Description	Desig.	Description
	$\frac{1}{2}$ watt carbon resistors, 10% plus or minus		
R8	100 ohms	SPKR	$2\frac{1}{2}$ " 3.2-ohm PM speaker (Lafayette SK-65)
R5, R7	1K	B	6v battery—four RCA VS074 or Ray-O-Vac pen-lite cells series connected
R6	4.7K	J	miniature jack (Lafayette MS-282)
R3	10K		binding posts (H. H. Smith 220 Red and 220 Black)
R1, R4	47K		battery holder (Lafayette MS-170)
R2, S1	25K miniature volume control with switch (Lafayette VC-25)		$2\frac{7}{16} \times 3\frac{3}{4}$ " miniature perforated board (Lafayette MS-304)
C5	.01 mfd, 75v Ultraminiature capacitor (Lafayette C-612)		$3\frac{1}{16} \times 6\frac{3}{4}$ " miniature perforated board (Lafayette MS-305)
C1	.1 mfd, 400v tubular capacitor (Aerovox type P822)		$2 \times 3\frac{3}{4} \times 6\frac{1}{4}$ " case (Lafayette MS-216)
C2	4 mfd, 6v miniature electrolytic capacitor (Lafayette CF-101)		knob (Lafayette MS-185)
C7	10 mfd, 6v miniature electrolytic capacitor (Lafayette CF-103)	RF Probe Parts:	
C3	30 mfd, 6v miniature electrolytic capacitor (Lafayette CF-104)	R9, R10	15K, $\frac{1}{2}$ watt carbon resistors (10%)
C4, C6	100 mfd, 6v miniature electrolytic capacitor (Lafayette CF-106)	C9	100 mmfd mica capacitor (Aerovox CM-20B-101)
C8	100 mfd, 15v miniature electrolytic capacitor (Lafayette CF-126)	D1	Germanium diode (RCA or Sylvania IN34A)
TR1, TR2	10K to 2K driver transformer (Lafayette TR-96)		miniature plug-plug set (Lafayette MS-370)
TR3	500 ohm to 3.2 ohm output transformer (Lafayette TR-95)		small plastic bottle approximately $\frac{1}{2}$ " diameter by 2" long (available at drug store prescription counters)
T1, T2	2N321 transistor (General Electric)		(Use Lafayette MS-281 plugs and about 2' of Belden 8411 shielded microphone cable for the input audio test lead)

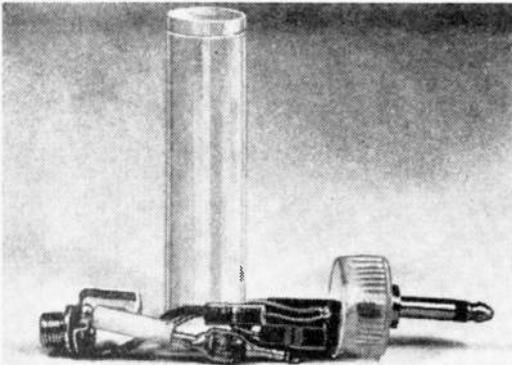All components for this project may be obtained from Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, New York



8

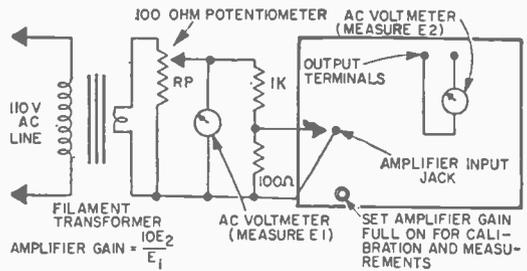
The RF probe fits in the small plastic tube standing behind it. Below, front panel mountings.



7 CIRCUIT FOR CALIBRATION

Fasten the knob on the shaft of R2-S1 and turn on to full volume. Touch the tip contact on the phone jack. If everything's okay, you'll hear a faint hum, and you can mount the assembled amplifier in the case to complete the job.

The amplifier may be used for audio signal tracing. The input probe lead is shielded with Lafayette MS-281 miniature phone plugs on each end. The sleeves supplied with the jacks should be replaced with more rugged $\frac{3}{8}$ -in. Bakelite tubing such as that used on test prods. The center lead attaches to the phone plug shell. A ground lead about 5 in. long equipped with a Mueller Minigator clip should be connected to the shield

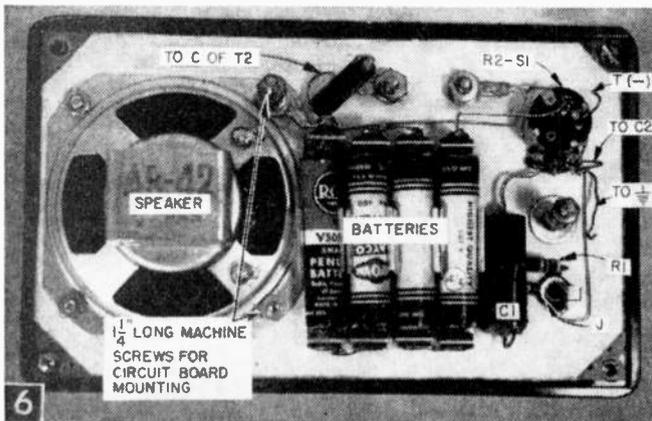

6

at one of the plug ends. These plugs are used at both ends to allow easy attachment of the RF probe.

The utility amplifier will drive an ac voltmeter. The red and black terminals on the front panel have been provided for connecting an external ac voltmeter. This allows the unit to be used for the measurement of small ac voltages and to check amplifier gain. To calibrate, use the circuit of Fig. 7. Set the meter to the lowest ac scale and adjust RP till the meter reads full scale. Now disconnect your meter and measure E1 with it. The full scale range of the amplifier-meter combination is 10% of E1. Since transformer

coupling has been employed without feedback, the amplifier gain varies with frequency. The full scale sensitivity at 60 cycles is less than the full scale sensitivity at 1000 cycles. Be sure to calibrate at the frequency you plan to measure.

The simple RF probe shown in Fig. 8 can be quickly attached to or detached from the input probe lead (described earlier) to trace RF and IF signals. The circuit for the RF probe is shown in Fig. 2. The level of the signal from the RF probe is low, so best results will be obtained if earphones are connected to the red and black terminals on the front panel of the amplifier.

SM-FP UNIT

Increases Value of Receivers

SM-FP unit mounted on
Heathkit AR-3 receiver.






By FORREST H. FRANTZ, Sr.

THE SM-FP ("S" Meter-Front Phone) unit increases the utility of your receiver by providing a visual indication of relative signal strength for tuning, logging and comparison purposes.

An earphone jack (regular or miniature size) on the front panel of the SM-FP unit allows you to connect earphones at the front of the receiver. No more groping around the rear of the receiver where phone jacks (and hot tubes) are frequently located. I don't know of any receivers with "S" meters which sell for less than \$100. The addition of an "S" meter, therefore, adds considerable value to your inexpensive communications receiver. All of these advantages can be yours for less than \$10.

The SM-FP unit "S" meter circuit connects to any receiver which has automatic volume control (AVC) without having to make any changes in the receiver circuit; simply tie the input terminals across the outer terminals of the receiver volume control. The secret of this simple universal type of connection? A transistor amplifier for the "S" meter.

The unit is housed in a Bud CU-2104 Minibox, 2 $\frac{1}{4}$ x 2 $\frac{1}{4}$ x 5 in. and finished in grey hammertone. (The same size is available in natural aluminum as Bud CU-3004.) The hole layout for the front of this box is shown in Fig. 4. A $\frac{3}{8}$ -in. dia. hole should be drilled in the center of the Minibox back and two small holes (about $\frac{1}{8}$ -in. dia.) should be drilled in one side of the back. Location of these holes is not critical; they are provided for the connecting cable and top of set mounting re-

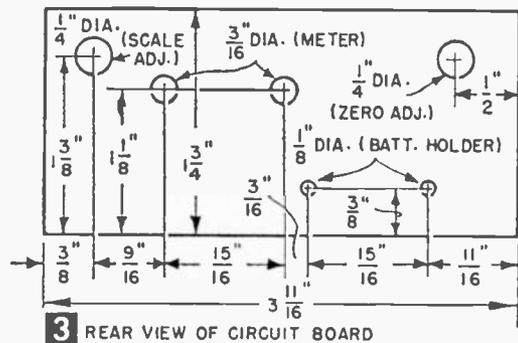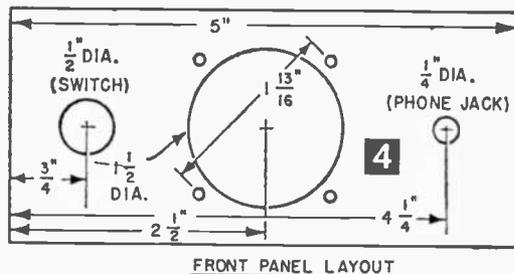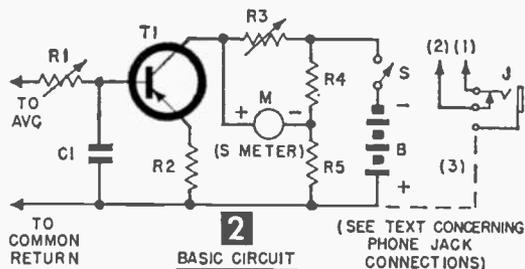

spectively. Mount the meter on the front of the Minibox.

The perforated Bakelite circuit board should be prepared next. Layout for it is shown in Fig. 3. Use a hacksaw to cut out the circuit board and smooth the edges with a file. All hole centers coincide with perforations.

Mount R1, R3, and the battery holders on the circuit board. Carbon resistors, transistor, and capacitor are fastened to the board by passing the pigtail leads through the perforations. When junctions between parts occur—as with R2 and the emitter of T1—the pigtails pass through the same perforation.

The common bus from the plus terminal of the battery is the long wire running the length of the circuit board in Fig. 5. This bus is returned through the connecting cable to receiver ground. The pigtails of components which return to this common bus are bent back against the board and soldered to the bus. The meter soldering lugs, the switch and the jack are connected while board wiring is in progress. The switch and jack leads should be about 2 in. long to allow positioning in the Minibox mounting holes.

When circuit wiring has been completed, make up a four-lead cable of flexible wire for connection to the receiver. Keep the cable reasonably short. I used a 16-in. cable. It helps to use different colored leads. The leads connect to the plus battery bus, R1 and the phone jack. Since the phone jack shell connection returns to the plus battery bus, three of the four connections may be made to the phone jack as shown in Fig. 5 if your receiver is ac operated (has a power trans-

former). Connections for ac-dc receivers are discussed below.


The circuit board is held in place against the back of the meter by the meter connection screws. To assure a good fit and good electrical connections, place cardboard shims between the meter and circuit board as required to elevate the circuit board above the meter binding post studs. Then fasten the binding post screws in place. Fasten the jack and switch on the front panel to complete construction of the SM-FP unit.

To fasten the unit to the receiver, place cardboard shims or use washers to obtain $\frac{1}{8}$ -in. clearance between the receiver top and the bottom side of the Minibox back. The front of the SM-FP unit slides onto the mounted back. Insert two of the self-tapping screws furnished with the Minibox in the appropriate holes on the top of the case to complete the assembly.

The basic connection scheme for all receivers is the same, but the details obviously may differ. The Heathkit AR-3 receiver to which this unit was attached will be used as an example. The Heathkit AR-3 has an octal accessory socket on the rear of the chassis. Pin 1 of this socket is connected to receiver ground. Pins 2, 4, 5, 6, and 7 are unused. I connected a lead from socket pin 2 to the high side of the volume control of the AR-3. This is my detector voltage pick-up point which feeds to R1, the "S" meter input.

The volume control of the receiver is part of the diode load, and AVC voltage is taken from its upper terminal, the audio component being filtered off by a 3.3 Meg resistor and a .01 mfd capacitor. The correct connection point on practically any receiver may be found by locating the detector load and an RC filter with a 1 to 5 Meg resistor and a .01 to .1 mfd capacitor connected to the load. In most receivers, the volume control is part of the detector load and AVC is taken to the filter from this point. In any event, the detector voltage pick-off may be made without changing any wiring; you simply tap on.

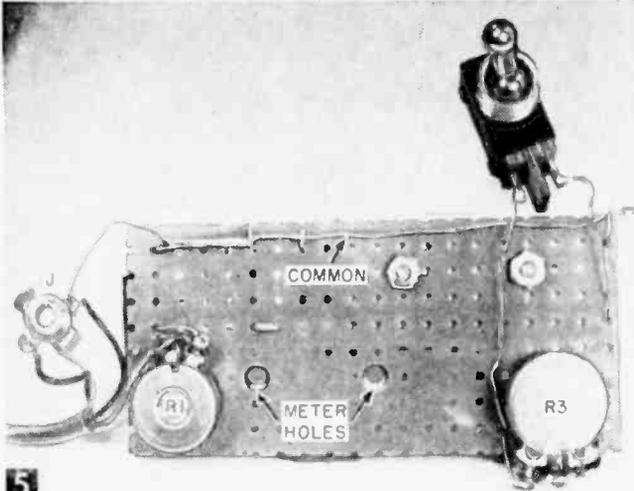The earphone jack on the Heathkit AR-3 is connected across the output transformer secondary. The third terminal on the jack is connected to the speaker voice coil and feeds the output signal to the speaker. Insertion of the phone plug breaks the connection to the




5

Front view of perforated board.

in Fig. 7. If your receiver has an arrangement of this type, you may have to shield the AVC pick-off lead in the cable to prevent audio feedback. This feedback may occur whenever the phone jack is in a high impedance circuit. But it will rarely ever occur when the phone jack is in the low impedance output transformer secondary circuit as it is in the Heathkit AR-3.

A note regarding the ground connection is in order since most inexpensive receivers other than the Heathkit AR-3 are ac-dc operated. Chassis ground on ac-dc receivers is usually isolated from the dc ground which is the common negative return of the set. If you're connecting the SM-FP unit to an ac-dc receiver, provide a fifth wire in the connecting cable.

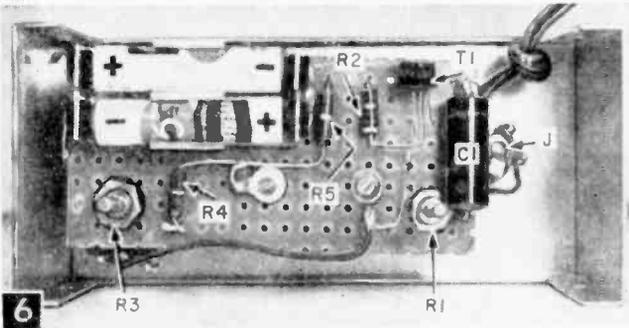Eliminate the connection between the phone jack and "S" meter common on the SM-FP and insulate the phone jack from the Minibox. This may be done by enlarging the jack mounting hole and using fiber insulating washers. The "S" meter common connects to the dc common of the receiver which is usually connected to the negative terminal of



6

Rear view of wired SM-FP unit.

speaker. The phone jack on the SM-FP unit is simply an extension jack.


I disconnected the speaker lead from the jack in the receiver and ran this lead to pin 5 on the accessory socket. I ran another lead from the high side (tip connection) of the phone jack to pin 6 of the accessory socket. These pin connections are connected through a mated plug on the connecting cable to their counterparts on the SM-FP panel jack. I used a defunct octal tube for the cable plug.

Some receivers have the phone jack located between audio stages. A typical arrangement and the required change is shown

the electrolytic filter capacitor or to the "low side" of the volume control terminal. The shell of the SM-FP phone jack connects to the shell of the phone jack on the receiver which is usually at chassis ground. The connections for the other three cable wires remain unchanged.

Adjustment of the SM-FP is simple. Turn the receiver on and tune to a point on one of the short wave bands where there's no station or noise pick-up. Turn the SM-FP on and adjust R3 for zero meter reading. Then tune the receiver to the strongest station you can find. If the "S" meter circuit is working properly, the meter needle will be deflected. Adjust R1 for a meter reading just above the plus 30 db point if you're in a good signal pick-up area, or for an S-9 meter reading if you're in a relatively poor area. Now tune off station to a quiet point and readjust R3 for zero reading. You may want to readjust R1 after you get a better feel for the kind of S readings to expect.

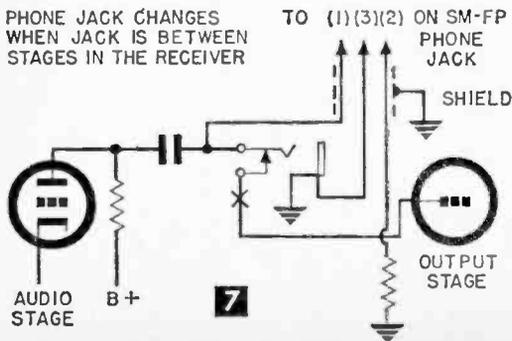Readings are relative and are influenced by your antenna, the sensitivity of your receiver, the band and the place in the band at which stations are received. The important thing is that the S meter allows you to tune your receiver for maximum input and gives



7

PHONE JACK CHANGES WHEN JACK IS BETWEEN STAGES IN THE RECEIVER

MATERIALS LIST—SM-FP UNIT


Desig.	Description
R4	100 ohm, 1/2 w carbon resistor (10%)
R2	470 ohm, 1/2 w carbon resistor (10%)
T1	2.2K, 1/2 w carbon resistor (10%)
R5	10K miniature potentiometer (Lafayette VC-32)
R3	1 Meg miniature potentiometer (Lafayette VC-38)
R1	.02 mfd, 200 v capacitor (Cornell-Dubilier Cub)
C1	2N508 transistor (GE)
J	phone jack (Lafayette MS-282 for miniature plug or Switchcraft 11 for standard phone plug)
B	two 1.5 v penlite cells series connected (Eveready 912)
M	S meter, 0-1 ma movement (Lafayette TM-11)
S	SPST toggle switch (Arrow-Hart and Hegeman 20994-BF)
	two-cell battery holder (Lafayette MS-138)
	Minibox case (See Text)
	perforated miniature Bakelite board (Lafayette MS-305) knob (Lafayette MS-185)

you a better estimate of signal strength than you would otherwise have. I point this out to emphasize that critical calibration of the meter is not required. After you've experimented with the S meter and your receiver for 30 minutes or an hour, you'll be able to set R1 for satisfactory meter deflections.

If the zero signal meter reading changes after the receiver has been operating for a few minutes, it's probable that heat from the receiver is causing the drift. Bend the transistor as near as possible to the center of the Minibox to minimize temperature drift. As

Eliminating Tape Recorder "Click"

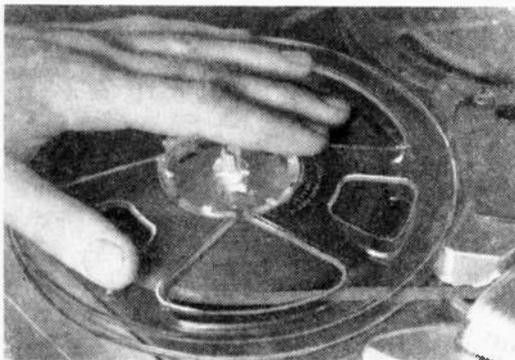• Does your tape recorder leave an audible "click" on the tape every time you depress the stop button while recording? Instead of clipping click from tape while editing, eliminate



it beforehand by manually rewinding an inch or so of the tape back on the supply spool before starting to record again.—JOHN A. COMSTOCK.

Preventing Shorts on Breadboard

To prevent short circuits on a breadboard circuit, tape the wire leads to the chassis with masking or plastic tape. This will also improve the appearance of the layout and permit easier tracing of the wires.—JOHN A. COMSTOCK.

an additional measure, the distance between the top of the receiver and the bottom of the Minibox may be increased to 1/4 in. Of course, you can mount R3 on the panel of the SM-FP unit if you wish, but this permits accidental displacement from the zero setting. This extreme should not be necessary. I might add that I didn't encounter noticeable zero drift with my Heathkit AR-3, but it has a wooden cabinet. I call attention to the possibility because it might occur if your receiver has a metal cabinet.

The "S" meter works in this way: The detection voltage of the receiver is fed through R1 to the base of transistor T1. R1 is an adjustable meter sensitivity control. The combination of R1 and C1 filters audio from the signal and passes only the negative dc level of the detection voltage (which depends on received signal strength) to the base of T1.

Transistor T1 is a dc amplifier. A very small change of current to the base of T1 is amplified to values as great as 1 ma to drive the S meter. Resistors R3, R4, R5 and the meter form the transistor collector load and meter zero (null) set circuit. Resistor R2 provides dc stabilization for transistor T1 to minimize drift and also increases the base input circuit impedance.


Signal Boosters for Portables

• In many portable radios there is no antenna loop of the conventional type, only a "loop stick." Signal sensitivity on such sets can be appreciably increased by winding two to three turns of insulated wire around the stick, one end of this added wire connected to an outside antenna. No ground is needed. You can also, if the set has a loop, wind a one- or two-turn primary over the loop, giving a step-up in voltage. Finally, if you don't wish to incorporate either of these primaries in the set's cabinet, you can make a one-turn loop of heavier insulated or bare wire stapled to a wood block and hung upside-down over the receiver as close as possible to the set's loop and in the same plane, one end of this heavy-wire loop going to an outside antenna as before.—P. M. ARMSTRONG.

Russia Gaining "Hams"

• If they can crack the language barrier, American ham radio operators may have 25,000 new correspondents by 1961—in the USSR. *Radio*, a Soviet magazine published in Moscow, reports that more than 50 radio clubs in Russia now claim 100 transmitters or more. It said that a drive is in progress to reach a goal of 25,000 Russian radio amateurs by 1961. Russian amateurs will operate in the frequency ranges 3.5 to 3.65, 7 to 7.1, 28 to 29.7, 114 to 146, and 420 to 435 mcgacycles.

Miniature Multimeter

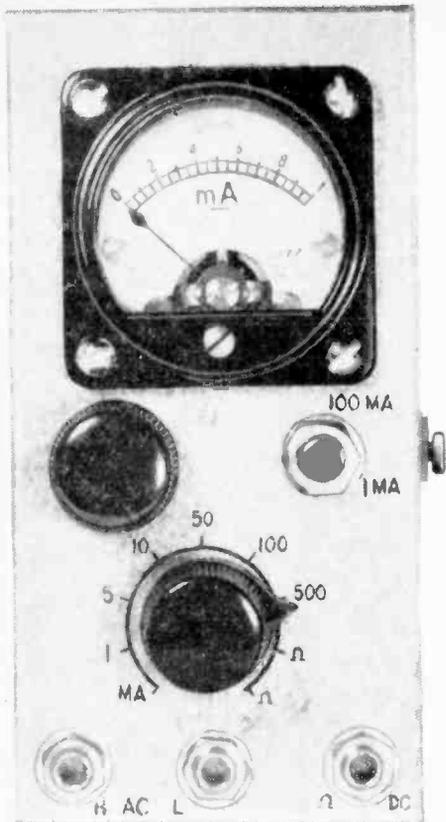

This multimeter fits in a coat pocket, has a special meter protection feature and you can build it for about \$10

IF ALLOWED only one instrument, most technicians would select a multimeter.

With it, you can shoot trouble, learn how electronics equipment operates, evaluate the performance of electronic gear. You can check for shorts or opens, measure ac and dc volts and milliamperes; and measure ohms. And from these measurements you can compute power, capacitance, and inductance.

This miniature multimeter is designed to measure a wide range of electrical quantities. Accuracy on the dc voltage, milliampere, and ohm ranges is good; accuracy on the ac ranges is not quite as good—unless you calibrate the ac ranges—but it's adequate for most purposes. The limitations of the meter are reasonable in view of its low cost and small size. These are its ranges:

dc volts: 1, 5, 10, 50, 100, 500


ac volts: 10, 50, 100, 500

dc ma: 1, 100

ohms: 0-50K (1.5K at meter mid-scale)

0-100K (3K at meter mid-scale)

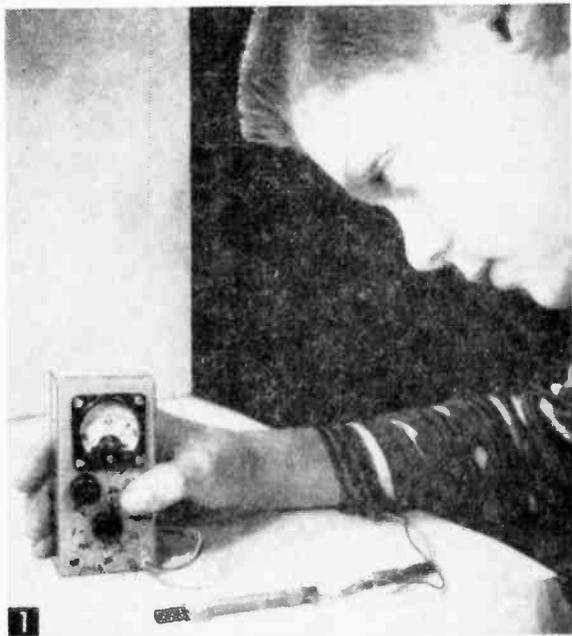Scale switching is accomplished with range




A worthwhile and gratifying construction project for beginning experimenters, this miniature multimeter is also an exceedingly practical piece of test equipment.


switch S1, the push button switch S2, and by the input jack circuit made up of J1, J2, and J3.

If you buy 1% precision resistors for R1 thru R6, the total cost will be slightly over \$10. You can save close to \$2 by selecting resistors R1 thru R6 from standard tolerance resistors. Use a Wheatstone Bridge to measure resistance (Wheatstone bridges are available in the science departments of most high schools and the physics departments of most colleges), or use the ohmmeter ranges on a good vacuum tube voltmeter (VTVM) such as the Heathkit V-7A. If you set the zero adjust and the ohms adjust controls carefully for zero and full-scale deflection of the meter, you can select resistors within plus or minus 2% very easily, and you can expect to get close to 1% if you're careful. This method is most accurate near meter center scale.

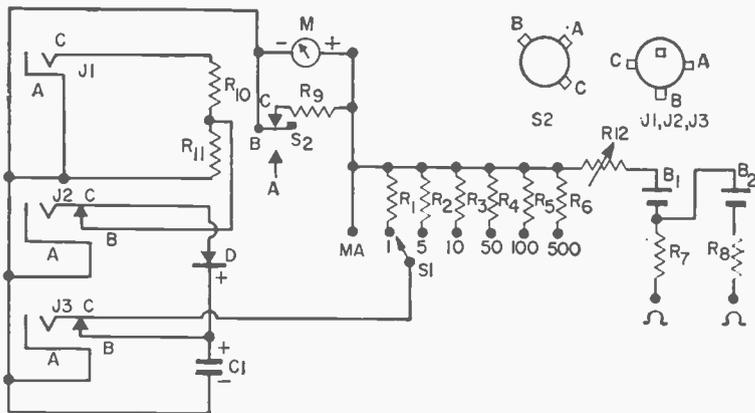
After you have all of the parts together, drill the chassis box (Fig. 3). Next, letter the front panel with India ink. Wash the box in warm sudsy water, rinse, and dry thoroughly before marking. A piece of thin plastic or clear celluloid cut to fit over the panel markings will assure permanence. Trim the holes with a pocket knife, and while you have



2 SCHEMATIC

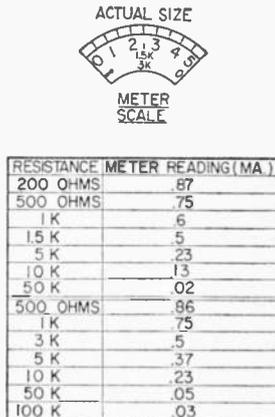

4 OHMMETER TABLE

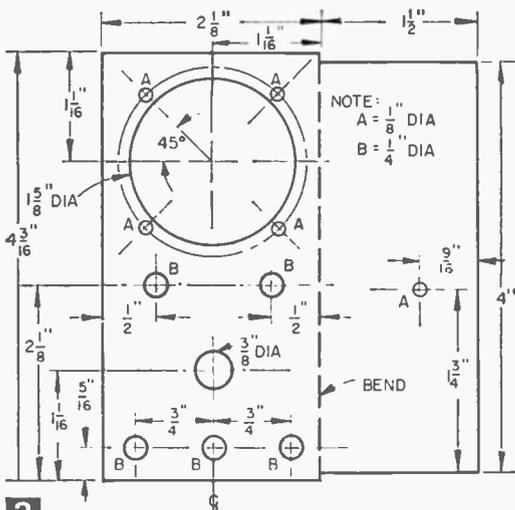

3 LAYOUT

MATERIALS LIST—MINIATURE MULTIMETER

Desig.	Description
R9	0.67 ohm resistor (6 $\frac{1}{2}$ ' of #30 insulated wire)
R1	935 ohm resistor, $\frac{1}{2}$ w, 1%
R2	4,935 ohm resistor, $\frac{1}{2}$ w, 1%
R3	10K resistor $\frac{1}{2}$ w, 1%
R4	50K resistor, $\frac{1}{2}$ w, 1%
R5	100K resistor, $\frac{1}{2}$ w, 1%
R6	500K resistor, $\frac{1}{2}$ w, 1%
R7	1K resistor, $\frac{1}{2}$ w, 10%
R8	2.7K resistor, $\frac{1}{2}$ w, 10%
R11	58K resistor, $\frac{1}{2}$ w, 10%
R10	100K resistor, 2 w, 10%
R12	1K miniature volume control (Lafayette VC-32)
C1	10 mfd, 150 v miniature electrolytic capacitor (Aerovox SRE type)
J1, J2, J3	miniature phone jacks (Lafayette MS-282)
S1	single pole, 10-position miniature switch (Grayhill 5001-10)
S2	miniature push button switch (Lafayette MS-449)
M	0-1 ma miniature panel meter (Lafayette TM-400)
D	selenium rectifier (Sarkes Tarzian 50)
B1, B2	1.5 v penlite cell (Burgess #7)
	1 $\frac{1}{8}$ x 2 $\frac{1}{8}$ x 4" aluminum chassis box (LMB-00)
	miniature knob (Lafayette MS-185)
	small standard knob (Lafayette KN-19)
	miniature phone plug (Lafayette MS-281)

the rubber cement handy, cut out and fasten the meter scale (Fig. 4) on the front of the meter glass.

Next, assemble resistors R1 thru R8 on the rotary switch as shown in Fig. 5. This portion of the wiring is shown inside the dotted line on the schematic, Fig. 2. The numbers indicated on the switch contacts correspond to the numbers on the back of the Grayhill rotary switch (S1). Switch position #9 is not used.


Check push button switch S2 to be sure that it makes good contact in the normally "ON" position. If you can detect any resistance at all between these contacts on the low ohm scale of a VTVM, clean and bend them to provide a low resistance contact. Since this switch is in series with R9, the shunt for the 100-milliampere meter range, contact resistance can impair accuracy.

Cut the shaft of potentiometer R12 so that it extends $\frac{1}{4}$ in. beyond the potentiometer

bushings, and mount R12, S2, J1, J3, the meter and the S1-R1 through R8 range switch assembly (see Fig. 6).

Wire from the meter plus terminal to the middle terminal of R12 and from there to terminal 10 on switch S1. Connect a wire to the upper terminal of R12 and let it hang loose for the moment. Connect a wire from the switch arm of S1 to the contact of J3 designated as "C" in the schematic. Connect a 2 $\frac{1}{2}$ -in. length of wire from contact "B" on J3 to the plus terminal of rectifier D. Connect the other terminal of rectifier D to terminal "C" of jack J2.


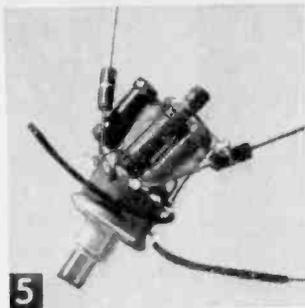
Next, mount J2 on the chassis, positioning rectifier D as shown in Fig. 7. Note that the terminals are bent to avoid the possibility of a short. The connecting wires hold the rectifier in place. Run a wire from contact "B" on S2 to the minus terminal of the meter. Connect another lead from the meter minus terminal to contact "A" on J3. Now connect the minus lead of C1 to the meter minus ter-



minal and the plus lead of C1 to the plus terminal of rectifier D. Place the negative lead of C1 under the negative terminal screw and solder the other two leads to the negative C1 lead. Connect one end of R9 to contact "C" of S2. Resistor R9 is made by folding 6½ ft. of #30 insulated copper wire on itself till it is 1 in. long. Insulate R9 with tape, and tape it to the meter case.

Next, connect R11 from A on J3 to B on J2. Connect R10 from "B" on J2 to "C" on J3. Connect the loose end of R9 to the junction of R1 thru R6 on the switch assembly (Fig. 8). Connect R7 to the terminals at the upper end of the battery holder to form a junction. Connect the loose end of the wire previously connected to the upper terminal of R12 to the remaining plus battery terminal. Connect the loose end of R8 to the remaining negative battery terminal. Then insert the batteries in the holder and fasten the holder to the chassis with a self-tapping screw. If the screw is long enough to threaten the batteries, use washers under its head. Completed construction is shown in Fig. 9. Putting the knobs on completes the work on the front side.

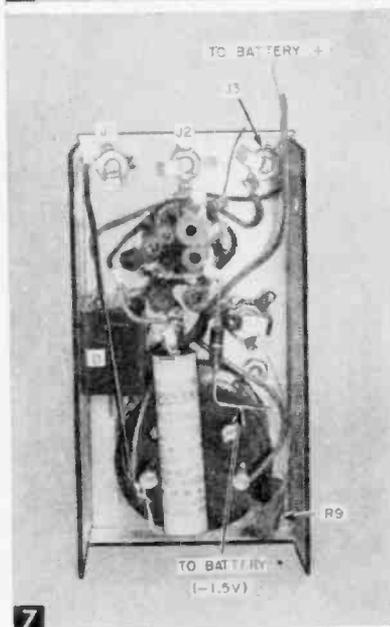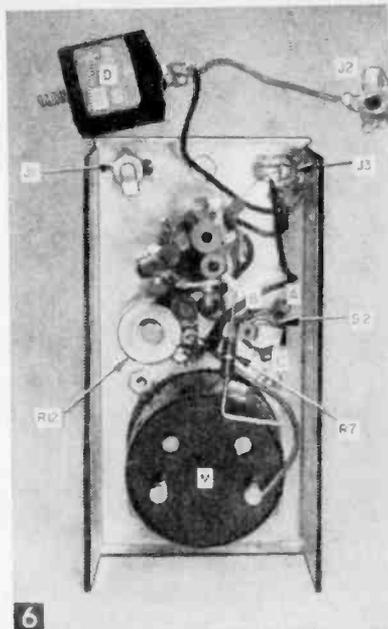The "A" terminals of jacks J1, J2 and J3 are grounded to the chassis case and therefore connect to each other through the chassis. The test leads connect to a single jack plug. You'll have to ream out the back end of the plastic plug handle to pass the wire through it. I used #20 solid hook-up wire for my test leads. Don't strip more of the wire than you must to solder to the jack ter-



Step-by-step construction of multimeter (see text).

minals, and provide tape insulation if necessary to protect against shorts. The test leads are terminated with Mueller Minigator clips at the other end. A wooden matchstick taped to the clip end of the positive lead stiffens it and allows you to use this lead as a probe.

To measure dc volts or ohms, plug the test leads in the ohm-dc jack (J3) and choose the range with S1. Use R12 to zero-set the ohmmeter with the leads shorted when you want to make the resistance measurements. You must depress S2 to get the correct reading. When S2 is not depressed, R9 shunts the meter to protect it against burnout if you should accidentally select too low a range. When you depress S2 to take a reading, the natural reaction to a pegging needle is to release the button. You're warned of very severe overloads that could damage the meter if S2 were quickly depressed and released by higher than usual readings before S2 is depressed. To measure milliamperes, select milliamperes with S1. The range is 100 ma if S2 is not depressed, 1 ma if it is depressed.

To measure ac volts up to 100, plug the test leads into the ac low jack (J2) and use the 10, 50 or 100 volt positions of S2. Again, you must depress S2 to get the appropriate reading.

You can use the 1 and 5 volt positions on S2, but they're very inaccurate on ac. To measure voltages between 100 and 500 volts, plug the leads into the high ac jack (J1) and set S1 to the 100 volt setting. Depress S2 to take the reading. Don't change jack plug-in positions with the test clips connected to a voltage!

When you feel sufficiently confident that you won't be jeopardizing the meter by picking a wrong scale or overloading it in some other way, you can change the connection on terminal "C" of S2 to terminal "A." Then the meter will read properly without depressing

S2. If this change is made, S2 is depressed only when the 100 ma range is desired. When S2 is not depressed, the 1 ma range is connected if the range switch is set to ma after the change has been made.

For current measurements, the meter is connected in series with voltage source and load as shown in Fig. 10A. For voltage measurements the meter is connected in parallel with the voltage source or dropping element as shown in Fig. 10B. To determine power, measure current thru the load and voltage across the load. The power in watts is equal to volts times amperes.


To determine capacitance or inductance use the arrangement of Fig. 10C. Adjust the variable resistor till the ac voltage across the capacitor or coil equals the voltage across the resistance. Then, measure the resistance. For a capacitor,

$$C = \frac{2650}{R}$$


where C is the capacitance in microfarads and R is the resistance in ohms. For a coil:

$$L = .00265R$$


where L is the inductance in henries and R is the resistance in ohms. This method is approximate. The accuracy is good for all types of capacitors 0.1 mfd or greater except for low-voltage electrolytics. This measurement method should not be used on electrolytic capacitors rated under 100 volts. The scheme is not as accurate for lower than 0.1 mfd capacitance because the capacitive reactance is much greater than the meter impedance. The accuracy of inductance measurements is not too good because of the resistance inherent in the coil which this method assumes as neg-

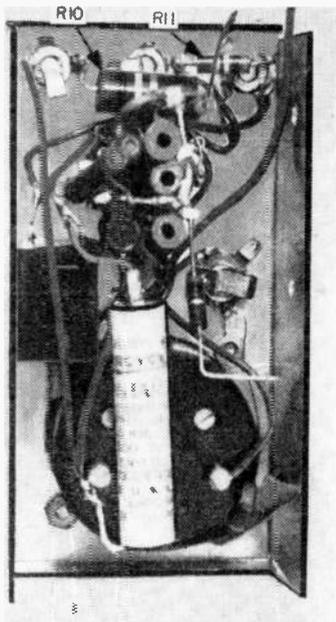

8

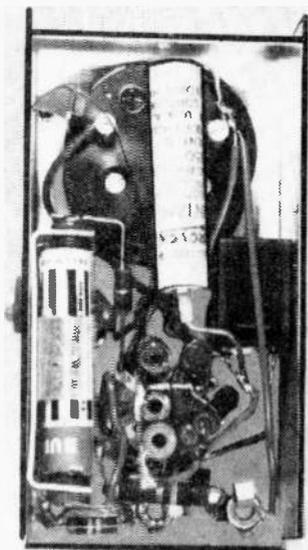


9

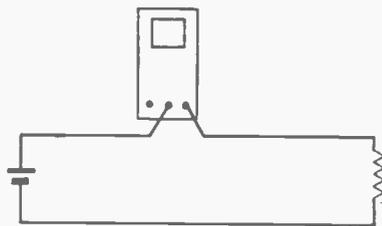

10 A CURRENT



B VOLTAGE

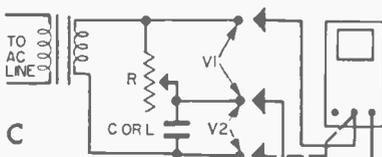

C CAPACITANCE OR INDUCTANCE (ADJUST "R" UNTIL V1 = V2)

ligible. It isn't reasonable to use this scheme for coils with inductances of less than 100 millihenries. But filter chokes and audio coils may readily be measured using this method.


Can the scheme be extended to take in lower inductances and lower capacitances under any circumstances? Yes, but you'd need a higher frequency source than the ac line 60-cycle frequency and you'd need a more sensitive meter.

Jacks J2 and J3 perform some of the switching requirements. Contact "B" is connected to "C" in any jack if the plug isn't inserted. If the test lead jack plug is inserted, "B" is disconnected from "C" in that jack. If the jack plug is inserted in J3, dc can pass directly into the switch arm of S1. If the jack is inserted in J2, the ac input is rectified by D, filtered by C1 and applied to the switch arm of S1 via contacts "B" and "C" on J3. For economy reasons, a half-wave selenium rectifier was employed in this miniature multimeter. This rectifier can't handle voltages much greater than ac line voltage. Therefore, the divider consisting of R10 and R11 was provided to reduce the voltage on inputs up to 500 volts for use with the 100 volt range switch position when the jack plug is inserted in J1.—FORREST H. FRANTZ, SR.

Three-Transistor Portable

This receiver, in spite of its simplicity and low cost, has high sensitivity and selectivity

By FORREST H. FRANTZ, Sr.

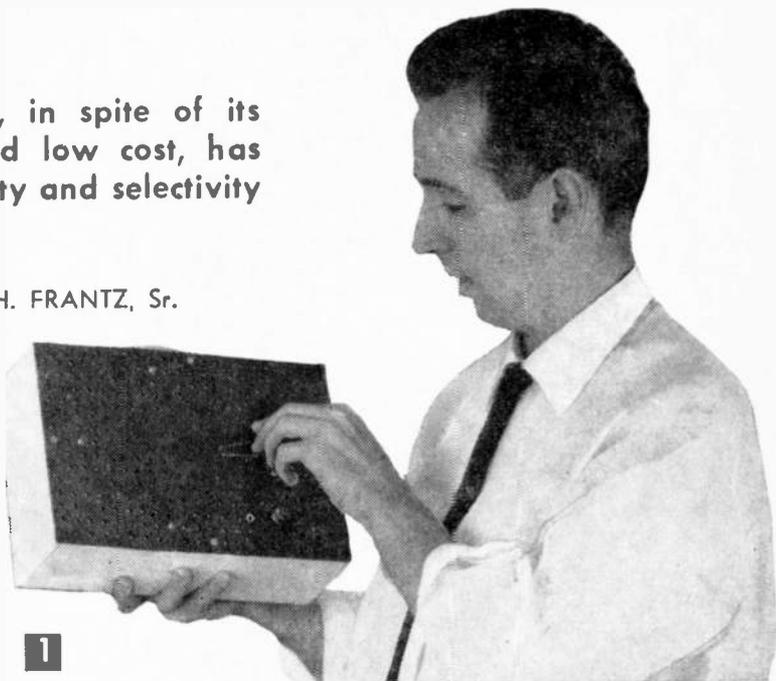


1

Tone of this simple portable is better than that of most small, commercial transistor receivers.



HERE'S a simple receiver that will pick up plenty of stations with loud-speaker volume. The circuit (Fig. 2) is novel in several respects. Transistor T1 is employed as a combination regenerative RF stage and stabilized audio amplifier, with base and collector circuit tuned to provide high RF gain and selectivity. The selectivity and gain characteristics are enhanced by capacitive feedback and the hi-Q ferrite antenna coil.

The amplified RF signal is detected by diode D, and the resulting audio signal is fed via capacitor C3 to the base of T1 for a second trip through. Coil L2 looks like a short circuit to the amplified audio signal and the signal appears across volume control R5. Transistor audio amplifier stages T2 and T3 build the signal up to loudspeaker driving level.

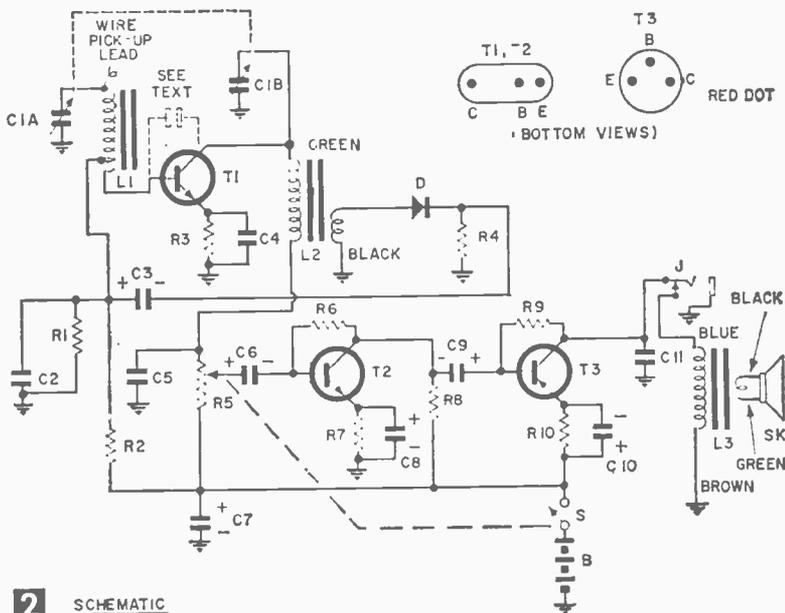Construction. The original three-transistor portable was housed in a "do-it-yourself" case constructed from a length of 1 x 4 with a perforated Masonite front and back (see Materials List). Shave the front edges of the cabinet on the left-hand side to clear for the edges of the loudspeaker and fasten a 1/2 x 1/2



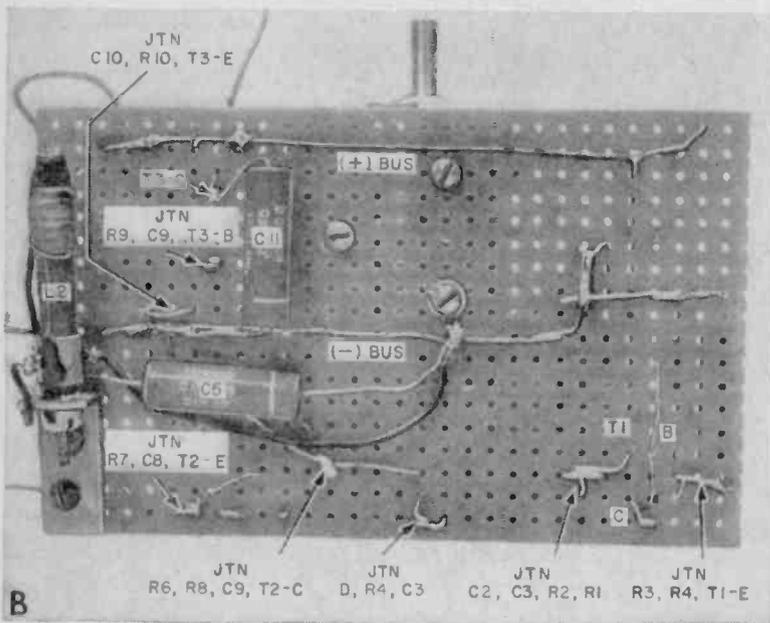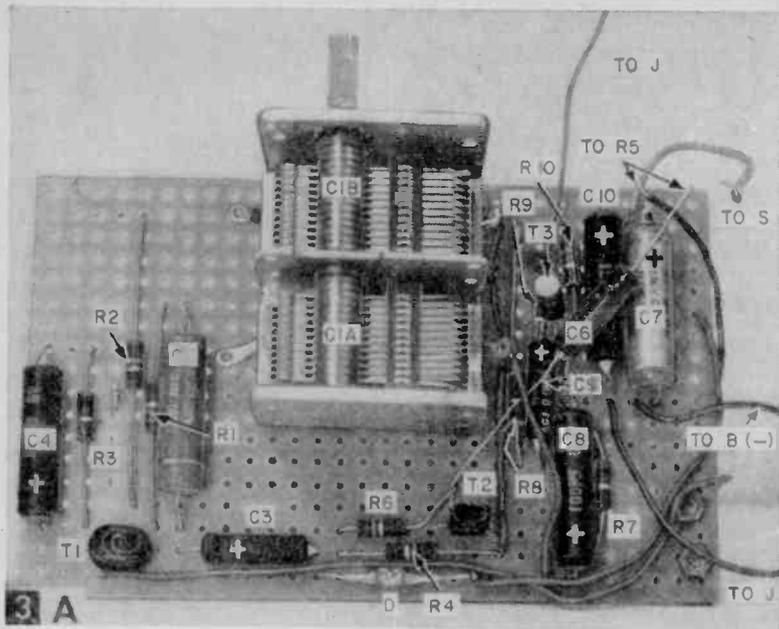x 7 in. wood strip to the bottom of the cabinet to hold the batteries. Fasten a piece of Masonite 2 1/4 x 8 1/4 in. with a 3/4 x 1 1/4 in. triangle cut from the front right corner (to allow



Circuit board layout, top (above) and bottom (below).

clearance for the volume control) to the side of the case with a small screw and bracket, and to the bottom of the case with a 1 $\frac{1}{4}$ -in. screw through a scrap block to complete battery holder.

The receiver proper is constructed in two basic units: circuit board (Fig. 3); and front panel (Fig. 4). The circuit board contains most of the components and fastens to the front panel with two machine screws and nuts terminating on the tuning capacitor

frame. The volume control and switch (R5-S), the phone jack (J), the loudspeaker (SK) and ferrite antenna loop (L1) mount on the front panel.

Cement a piece of cardboard to the front panel, making holes as required for mounting parts with a pocket knife. Draw a 5 $\frac{1}{2}$ -in. dia. circle on the cardboard with center at approximate speaker center. Punch holes in the cardboard within this circle with an ice pick, entering from the perforations on the front.


Cut the shaft of R5-S to a length of $\frac{3}{8}$ in., and mount R5-S, SK, L1, and J. Cut a square hole, $\frac{3}{8}$ in. on a side into the cardboard around the panel hole for J; the jack collar isn't long enough to accommodate the extra thickness of the cardboard. Mount L1 on two 1 $\frac{1}{2}$ -in. right-angle brackets fastened to the front panel, and fasten the output transformer (L3) on the loudspeaker (SK) by soldering at the mounting flanges. Connect the transformer leads and provide a ground lead from the speaker frame to the ground terminal on the jack.

Next, cut the shaft of C1 to $\frac{3}{4}$ -in. length and mount C1 on the board with 6-32 x $\frac{1}{4}$ in. machine screws.

Modify L2 by disconnecting one of the connections to the center-tap (unmarked) lug. Heat the lug and shake off the solder. Then, with heat applied to the lug, use needle nose pliers to loosen the lead with several gentle tugs. Be careful not to damage the litz wire. This modification changes the coil from a single-winding tapped coil to a two-winding coil. Fasten the coil on the small right angle bracket and mount on the circuit board. Proceed with circuit board wiring. Determine correct pairing of the windings on L2 with

MATERIALS LIST—THREE-TRANSISTOR PORTABLE

Desig.	Description
1/2 Watt Carbon Resistors, 20% Tolerance	
R10	270 ohms
R3, R7	1K
R8	2.7K
R1	6.8K
R4	22K
R9	47K
R2, R6	68K
R5-S	1K miniature volume control with switch (Lafayette VC-26)
C1A,B	2-gang 365 mmt. tuning capacitor (Lafayette MS-142)
C2, C5, C11	.01 mfd., 600-v tubular capacitor (Cornell-Dubilier "Tiny Chief")
C9	6 mfd., 15-v miniature electrolytic capacitor (Lafayette CF-104)
C3, C6	30 mfd., 6-v miniature electrolytic capacitor (Lafayette CF-104)
C4, C8, C10	100 mfd., 6-v miniature electrolytic capacitor (Lafayette CF-106)
C7	100 mfd., 15-v miniature electrolytic capacitor (Lafayette CF-126)
L1	transistor loop antenna (Miller 2000)
L2	transistor antenna coil; see text for modification (Lafayette MS-299)
L3	500:3.2 ohm transistor output transformer (Lafayette TR-95)
T1	2N168A NPN RF transistor (General Electric)
T2	2N214 NPN AF transistor (Sylvania)
T3	2N408 PNP AF transistor (RCA or Sylvania)
D	diode (RCA 1N54A)
J	miniature phone jack (Lafayette MS-282)
SK	6" PM loudspeaker, 3.2 ohm (Lafayette SK-27)
B	six 1.5-v flashlight batteries, series connected (RCA VS036)
3 1/16 x 6 3/4" miniature perforated wiring board (Lafayette MS-305)	
two 7 3/4 x 11 1/8" perforated Masonite boards (cut from two Lafayette ML-81 boards)	
two 1 1/8" lengths from 1 x 4	
two 6/8" lengths from 1 x 4	
miniature knob (Lafayette MS-185)	
tuning capacitor knob (made from standard size surplus knob and thin plastic)	
earphones of 500-1000 ohms impedance	
handle, bracket screws	

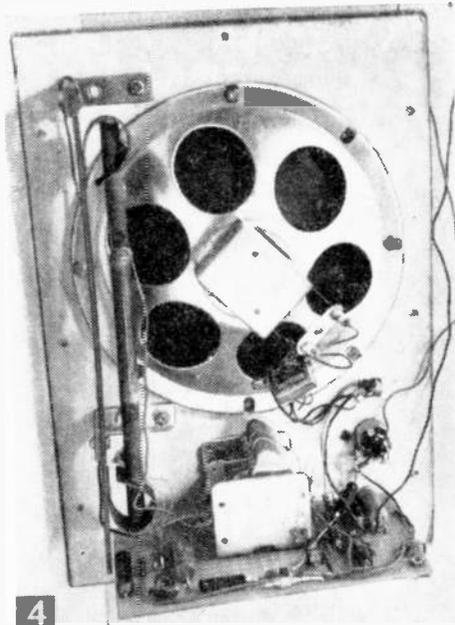

4

Back view of completely assembled front panel.

C1A trimmer considerably or to add turns to L1 by winding some of the "high-end" lead on the ferrite core. The plates of C1A may be bent to improve tracking. The important things are to be sure that you can tune the entire broadcast band, and that you have the greatest possible sensitivity over most

of the band. Don't overlook the fact that this receiver is very directional!

If you wish to miniaturize this set, use a Miller 2001 or 2004 for L1, a Lafayette SK-65 (2 1/2 in.) for SK, and six penlite cells for B. Coil L1 should make a right angle with L2 (but keep L1 horizontal), and these two coils should be separated as much as possible. Coil L1 should be kept away from the speaker or other metal surfaces.


an ohmmeter or a continuity checker.

Fasten the wired circuit board to the front panel and complete the wiring. The antenna pickup lead is a 10-in. length of hook-up wire fastened mechanically (but not electrically) to the ferrite antenna loop (L1) mounting board. Fastening the knobs to the front panel completes receiver construction.

Set the L2 slug screw to extend about 3/8 in. beyond the end of the coil. Turn the trimmer on C1A all the way in, and then release it about 1/4 turn. The trimmer on C1B should be turned all the way in and then released 2 turns. When you feel sure everything is right, solder in the batteries (using as little heat as possible), and try the set.

If the set squeals, move the lead to the stator lug of C1B away from the stator lug and associated surface of C1A. This lead provides the collector to base capacitance shown in Fig. 2. Tune to a station around 1400 kc, and adjust the C1B trimmer for maximum signal. Then tune to a station around 600 kc and adjust the slug of L2 for maximum signal. Now adjust the position of the C1B stator lead relative to the C1A stator for maximum sensitivity without oscillation.

You may find it advantageous to open the

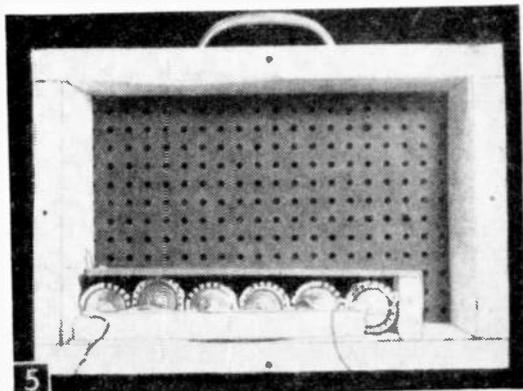


5

Looking into opened case from front.

The Little Muter

A Noise Limiter For The Ham Station

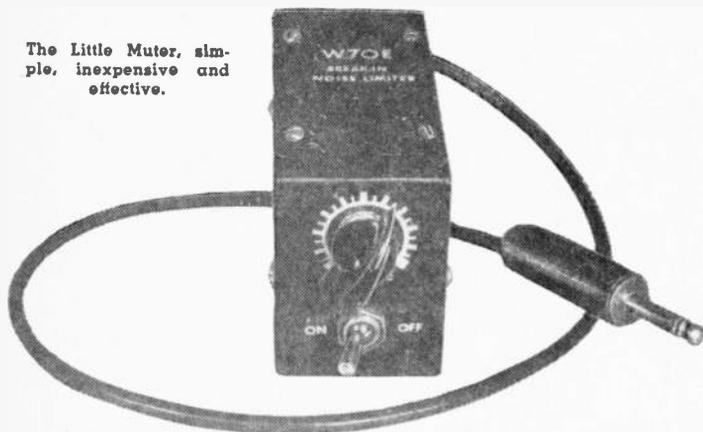
The Little Muter, simple, inexpensive and effective.



By HOWARD S. PYLE,

W7OE

Photos by John F. Hoyt

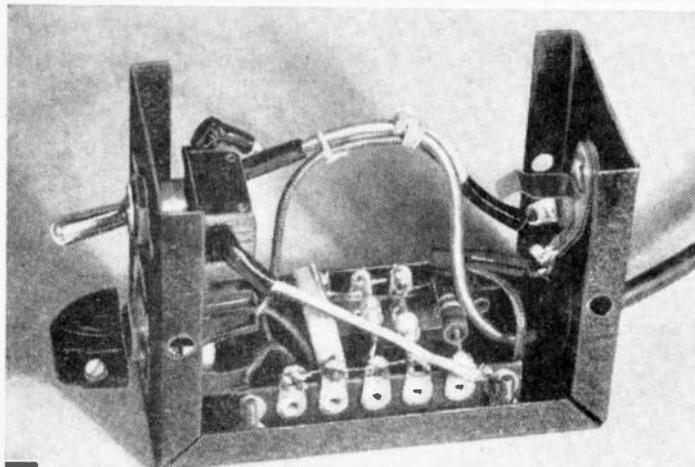

2

Internal view of noise limiter showing component mounting on tie points.

DISSATISFIED with the rather dubious noise-limiting circuits usually built into the average communications receiver, I conducted a number of experiments with the hope that they would lead to a better signal-to-noise ratio than conventional designs seemed to offer. I wanted a noise-reducing device, rather than something that took hold when the noise reached a certain level. In addition, my aim was to attempt to make such a circuit function as an audio noise reducer, with no attempt to reduce the noise pick-up in the antenna circuits, and to make such a device an accessory to the receiver, requiring no modifications or changes in receiver circuitry.


I came up with an extremely simple limiter,

or reducer, as you please, which required no battery or other source of power, was small and compact and could simply be inserted in the headphone or speaker leads from the receiver. I have used this device in CW traffic net message exchange for several years . . . I would be completely snowed under without it! While I do not habitually work in the phone bands, the listening I have done there indicates that this little limiter is every bit as effective on phone signals as with CW. Were all parts for this unit to be purchased new, the total cost would be less than \$5. With the possible exception of the crystal diodes, everything is readily available in your own station's scrap-box.

The unit is completely contained in a Bud Minibox which measures just $2\frac{1}{4} \times 2\frac{1}{4} \times 4$ in. Figure 3 gives the schematic. In my own unit

(see Fig. 2), I mounted capacitor C1, the two crystal diodes X1-X2, and the fixed resistor R1 between two Birnbach #1388 lug terminal strips (tie-points) which were in turn secured to the inside of the Minibox at a spacing of 1 in. Volume control R2 mounts on one end of the cabinet with the toggle switch S1 directly below it. The opposite end of the Minibox mounts the "Phones" jack near the bottom and, near the top center, a rubber grommet in a suitable hole to take the cord from the phone plug. Small decals, available at any radio supply store, mark the controls and add the professional's touch.

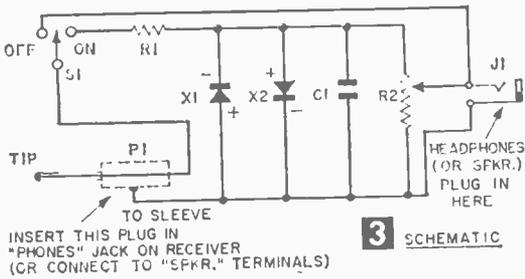Use caution in wiring the two diodes. Make sure that their polarities are in opposition—positive to negative at each end, as shown



3 SCHEMATIC

MATERIALS LIST—NOISE LIMITER


Desig.	Description
S1	SPDT toggle switch
R1	15 megohm 2-watt resistor
X1, X2	Sylvania 1N34 crystal diodes
C1	.0025 mfd. fixed capacitor
R2	10 megohm volume control (Mallory \pm U-20)
J1	open circuit phone jack
P1	phone plug Bud Minibox (CU-3003)

in the schematic. Use care, too, in soldering to the pig-tails of the diodes since they are easily damaged by too much heat. Solder quickly, but be sure it's soldered.

To install, plug the phone plug into the "Phones" jack on your receiver and plug your headphones into the jack under R2 on the *Little Muter*. That's it! If you prefer speaker operation, insert the *Muter* in the same way in the speaker leads.


You'll find that *Little Muter* will cut your audio output, but no matter—with the excessive gain available in modern receivers, this merely means compensating for any loss of audio by running the audio gain control at a slightly higher setting. BUT, you'll find that while the signal comes up, the noise does not come with it in the same ratio! That what you want? I did, and *Little Muter* gave it to me! When you find conditions such that you don't need it, flip switch S1 to *Off* and you are conventionally connected to the receiver through your headphone or speaker.

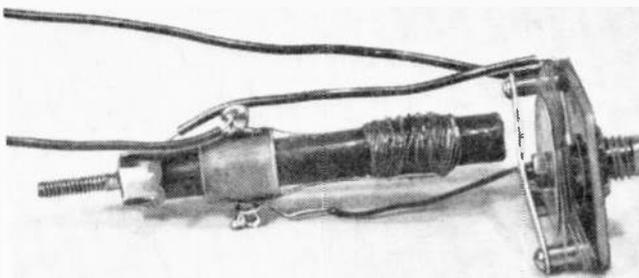Wave Traps Eliminate Station Interference



1

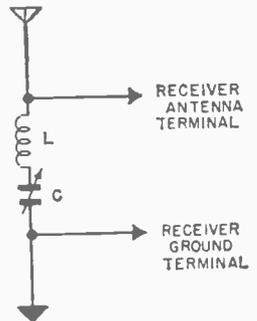Broadcast band wave traps can be connected across receiver loop antenna if coil's axis is vertical. If trap is enclosed in a metal shield (tin can), orientation is not necessary.



2


SERIES RESONANT WAVE TRAP "SHORTS" SIGNAL AT ITS RESONANT FREQUENCY

By FORREST H. FRANTZ, Sr.


A STRONG local radio station can interfere with reception of other radio stations in several ways. One type of interference that can affect any type of receiver circuit is adjacent-channel interference. If the strong local station is on 790 kc, it may affect stations from 700 to 900 kc in TRF receivers. The interference may cover a wider spread on the receiver tuning dial in the case of a crystal detector-amplifier type receiver. Adjacent channel interference in the more selective

superhet circuit is not severe, but it can be troublesome on closely adjacent stations (for instance, 780 kc and 800 kc when the interference local is on 790 kc).

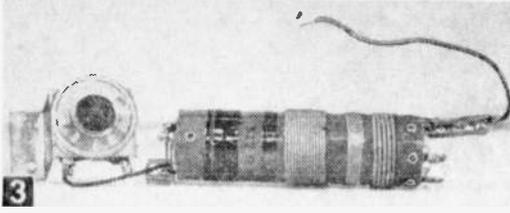Another type of local radio station interference that can affect any type of receiver circuit is harmonic interference. Although FCC regulations require radio stations to keep signal harmonics low, harmonics of strong locals can cause interference. (The second harmonic of a station on 600 kc, for



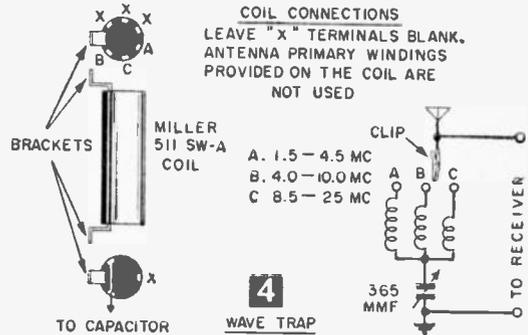Short-wave trap can be mounted on chassis at rear of set if capacitor is mounted on a bracket. Ground connection for capacitor is made through the bracket. The end of the clip lead connects to the antenna terminal of the receiver.



example, would be received at 1200 kc.)

Local radio stations can produce interference in superhet receivers that is peculiar to the superhet circuit. This type of interference occurs because the superhet employs a fixed intermediate frequency. The incoming signal is mixed with the local oscillator to produce the IF (usually about 455 kc in AM receivers), and the mixing process produces a number of signal frequencies at the output of the mixer tube. The desired IF signal is the oscillator frequency minus the received signal frequency. Thus, if the receiver is tuned to receive a station on 1500 kc, the local oscillator frequency is 1500 plus 455 or 1955 kc. If the receiver is tuned to 1500-2 (455) or 590 kc, the local oscillator frequency is 1045 kc. If the 1500 kc station is a strong local, the amount of its signal that appears at the input to the mixer tube even when the receiver is tuned to 590 kc may be very large. One of the signals at the mixed tube output is the received frequency *minus* local oscillator frequency, in this case, 1500-1045, or 455 kc., the IF frequency of the receiver. There is interaction between the 590 kc signal to which the receiver is tuned and the 1500 kc local signal; 590 kc. is the "image" frequency of 1400 kc.

Eliminating Interference. The basic wave trap configuration shown in Fig. 2 is a series resonant wave trap. It is connected across the antenna-ground terminals of the receiver. This wave trap effectively short-circuits the signal frequency to which it is tuned, but has very little effect at other frequencies. The higher the Q of the coil, the more effective the wave trap is. This type of wave trap can be connected across a loop antenna within a broadcast receiver or across the transmission line in the case of a TV receiver. This type of wave trap is recommended for any type of receiver because it will function effectively even if the ground to the receiver is poor.

A wave trap which will suppress frequencies in the broadcast band may be most easily constructed by using a commercially available coil, the Miller #6300 high-Q ferrite antenna coil. This coil has a Q of over 250 and will provide good rejection. The coil is adjustable and will tune the broadcast band

with any capacitor having a maximum capacitance between 250 and 500 mmf.

The wave trap shown in Fig. 1 uses the Lafayette MS-445 365 mmf. tuning capacitor. This capacitor was chosen for its small size and low cost. It was housed in a tin can. The leads to the receiver antenna and ground terminals should be as short as possible. The antenna pickup lead on the coil must be unwound and may be shortened to form one of the connecting leads. The screw adjustment on the coil may be set so that the capacitor will tune the broadcast band. Or, by setting the screw for maximum inductance, the trap can tune down to about 450 kc. when the tuning capacitor is fully closed. If the screw is set for minimum inductance, the trap will tune up to about 2.5 megacycles with the capacitor fully open.

The short wave trap shown in Fig. 3 can tune the frequency range from 1.5 to approximately 25 megacycles. The coil is a Miller 511-SW-A, three-band short-wave antenna coil. The capacitor is the Lafayette MS-445, the same as for the broadcast trap. The windings on the coil cover 1.5 to 4.5, 4.5 to 10, and 10 to 25 megacycles respectively. The coil which covers the frequency to be suppressed must be connected in the wave trap circuit. A Mueller Minigator clip permits quick selection of the required coil, but this clip can be omitted and the coil may be soldered in the circuit for a more permanent installation. The schematic (Fig. 4) shows the connections. This wave trap may be fastened directly to the back of the receiver chassis. If you wish to make this wave trap easy to get at, so that it can be used to improve receiver tuning at all frequencies, house components in a metal cabinet and provide a switch for changing connections to the coil.

Save Those Dirty Radio Parts

• When dirty tube sockets, insulators, knobs, tuning capacitors and other metal, bakelite or ceramic radio parts won't come clean in ordinary cleaning solutions, try this idea. Allow the parts to soak a minute or two in a pan of boiling hot water to which a capful of liquid dishwashing detergent has been added, then brush them with a vegetable brush.—J.A.C.

Precision Stroboscope for Only \$21

This accurate "motion stopper" will enable you to analyze motor operation and trouble shoot flaws in mechanisms

By W. F. GEPHART

Adjust the frequency control to synchronize the flashing strobe lamp with the speed of the fan. The blades will appear as though stationary.

WINKING at up to 6,000 flashes per minute, this easily built portable unit will show you fast moving mechanism "stopped," or in slow motion in order to spot wear, vibration or faulty design in power tools, fans, belts, motors, and reciprocating parts.

A simplified version of equipment widely used in industry, this strobe circuit, uses only about \$21 in parts and performs as well as commercial instruments costing over \$100. The rate of flashing is adjustable between 600, and 6,000 rpm, and by doubling up, you can measure any speed above or below this range. Unlike mechanical tachometers, the stroboscope absorbs no power from a direct connection to the moving mechanism itself.

How It Works. The basic principle of the stroboscope is simple. You might, for example, want to examine a fan blade rotating at about 300 rpm, (5 times a second). The blades will be in the same place every successive fifth of a second; therefore, if you could blink your eyes that fast, you would see the fan as though it were standing still. By means of the frequency control, Fig. 1, the rate of flashing is adjusted until it synchronizes exactly with the moving part. Adjust the control to flash slightly faster, or slower, and you can see the movement in slow motion. Reciprocating motions, such as the action of a pump, or the teeth of a high speed jig saw are clearly stopped in action.

If you calibrate your unit against a standard, you will be able to use it as a tachometer to make measurements of the rpm of high speed motors,



MATERIALS LIST—STROBOSCOPE

Desg.	Description
R1	27 ohm 1 watt 10% carbon resistor
R2	1 megohm 1 watt 10% carbon resistor
R3	7,000 ohm 5 watt wirewound resistor
R4	560K 1/2 watt 10% carbon resistor
R5	1 M 1/2 watt 10% carbon resistor
R6	2M potentiometer (linear taper)
R7	10M 1/2 watt 10% carbon resistor
R8	100K 1/2 watt 10% carbon resistor
R9	5K 5 watt wirewound 5% resistor
R10	10K 5 watt wirewound 5% resistor
R11	2K 5 watt wirewound 5% resistor
C1	8 mfd 450 V electrolytic capacitor
C2	8 mfd 150 V electrolytic capacitor
C3	8 mfd 450 V electrolytic capacitor
C4	.05 mfd 200 V electrolytic capacitor
C5	.033 mfd 200 V paper capacitor
C6	1 mfd. 400 V paper (Sprague 4TM-M1)
C7	20 mfd 450 V (Ill. Cond. IHTe 2045)
SW1	DPST toggle switch
SW2	SPST toggle switch (for range switch)
SR1, SR2, SR3	75 ma 130 RMS selenium rectifiers (IT&T Federal #1003A)
V1, V2	RCA 0A2 150 volt voltage regulator tubes
V3	Sylvania 1021/SN4 Strobotron tube
Misc.	Bud Minibox CU-2114 (12 x 2 1/2 x 2 1/4" aluminum box and cover)
	2 ea. 7 pin miniature sockets, 1 4-prong socket, 1 knob, terminal strips, line cord, reflector, decals, misc. hardware. Walsco Stroboscopic Disc #949

Note: See text and drawing for auxiliary trigger switch parts.

phono turntables, and even of dental drills. Hobbyists have used strobe lights to check the speed of model gas engines vs. various fuel mixtures. And if your model railroad engine is balky, your strobe may quickly indicate the trouble, in a part that is vibrating at certain speeds.


Building the Case. The stroboscope is completely enclosed in a compact aluminum minibox. Mount the strobotron tube socket at one end, and drill the holes for the switches and frequency control in the back, as in Fig. 2. Make the sub chassis of scrap aluminum, and mount all parts including tube sockets, and tie points before starting the wiring. The reflector shown in Fig. 1 is from a used Heiland photo flashgun, and can be obtained in most camera stores. Since the design of the

bracket will depend on the kind of reflector that you obtain, exact dimensions are not given. Simply bend a piece of hardened aluminum strap, $\frac{1}{2} \times \frac{1}{8}$ -in. to focus the center of the reflector directly behind the flashing area of the strobron tube, which centers about $\frac{3}{4}$ in. down from the top of the tube. Since the power supply, and the regulator tubes generate heat, drill ventilating


holes near these parts in each side of the cover as in Fig. 2.

Wiring the Circuit. Begin by wiring and testing the power supply, as in Fig. 3. It consists of a selenium rectifier tripler, with an output of about 430 volts, which is subsequently reduced to 300 volts for both the timing and strobe pulse circuits. Since one side of the power supply is connected directly to the a-c power line, be sure to isolate all interior circuits from the metal case, with the exception of the case ground resistor, which acts as a bleeder to discharge voltages which might otherwise remain stored in the capacitors when the unit was not in use. Make all connections to B- to a bus running through the strobe circuit. Check the output voltage of the power supply before connecting R3 to the regulator tubes. It should be 450 volts or less. If it is higher, increase the value of R3.

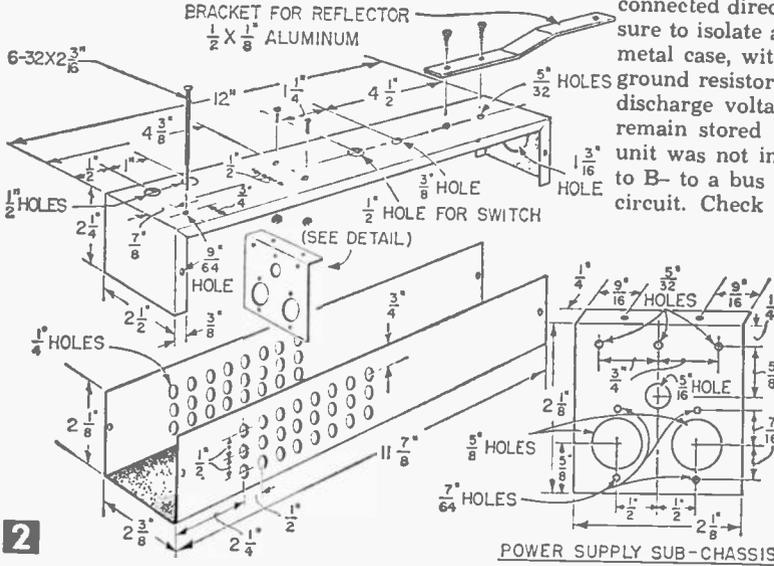
CAUTION: High voltages in the power supply, and charges stored in the capacitors can be hazardous. Use extreme care to avoid shock in handling the chassis



2

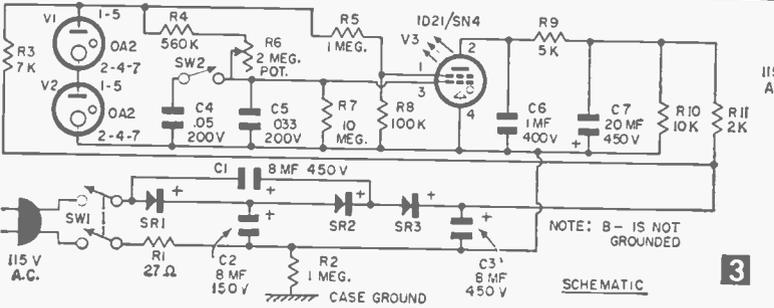

3

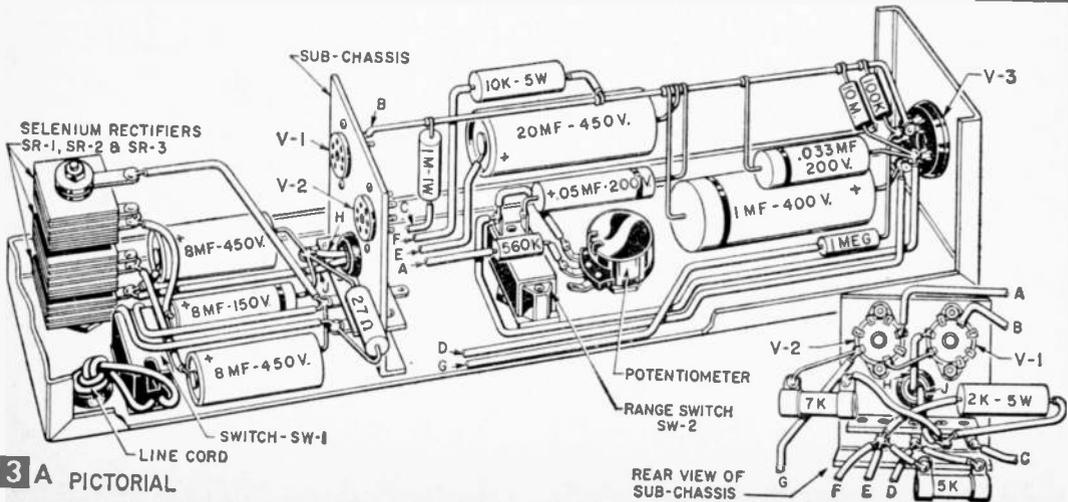

3A PICTORIAL


when power is on. Never touch any live parts, or non-insulated tools, clips, etc., with bare hands.

Next wire the regulator tubes, and the stroboscope section as in the schematic and the pictorial view, taking care to connect the adjustable frequency control R6, so that it has minimum resistance when fully clockwise. Cover all bare wires with spaghetti tubing, and keep the leads to the larger capacitors, C6 and C7, short, so their leads will support them firmly in position.


After wiring, check your work carefully against the schematic. Then, turn the unit on. The strobotron tube should start firing immediately, with the flashing rate increasing as R6 is turned clockwise. The low and high ranges should overlap slightly; with R6 turned all the way clockwise on low, the flashing rate should be slightly faster than with R6 fully counter clockwise on high. The strobe tube makes a slight cracking sound as it fires on low rates, and normally makes a steady buzz at higher flashing rates.

The strobotron tube operates on the principle of placing a high positive potential on the plate with the cathode grounded. When the difference in voltage between the two grids reaches approximately 100 volts, the gas between the grids ionizes, which in turn "ignites" the gas between the cathode and plate. Once the grid voltages "fire" the tube, the plate takes over control, and the gas remains ionized, with a high current flowing between plate and cathode, until the plate voltage is lowered, even though the voltage difference on the grids is removed.

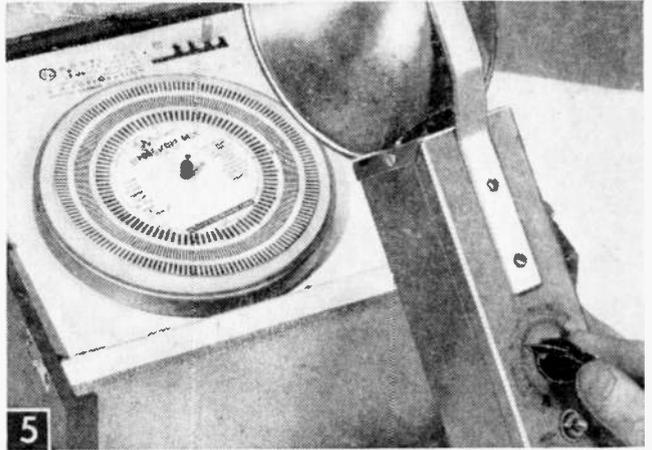In this circuit (Fig. 3) the plate resistor and capacitor are used only to prevent the tube from "firing" continually, and the timing between flashes is controlled by changing the grid voltages. The time constant of R9 and C6 is about




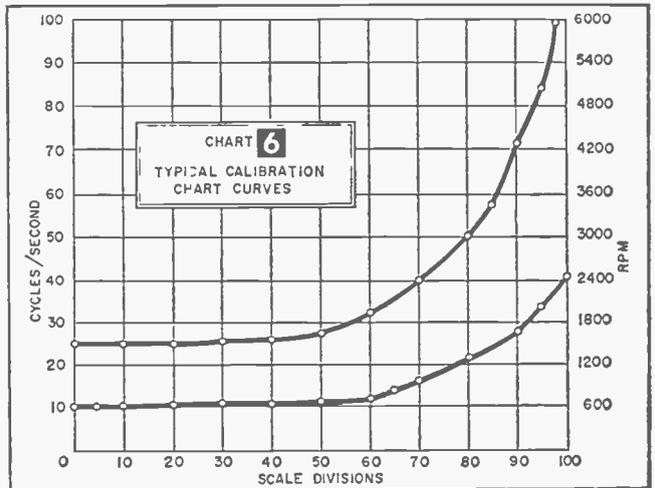
5 An ordinary record turntable and stroboscopic disc are used to calibrate your strobe light.




.005 second, which is the duration of each flash. The grid voltage difference is controlled by a variable R-C charging circuit consisting of R4, R6, C5, SW2, and C4. When a capacitor charges through a resistor, the voltage across the capacitor increases, as shown in Fig. 4A, until it reaches the charging voltage. Notice that the voltage increases rapidly at first, and then tapers off as it approaches the charging voltage.

If arrangements are made to discharge the capacitor rapidly before it reaches the full charging voltage, a sawtooth wave, as shown in Fig. 4B is formed, and if this voltage "Y" is substantially below the full charging voltage, the curve will be more linear. Repeated charging and rapid discharging gives a series of evenly-spaced peaks, Fig. 4B. Charging of the plate and grid capacitors immediately after firing places a heavy load on the power supply, which would tend to drop the supply voltage from X to X1 as in Fig. 4C if this tendency was not minimized by the voltage regulator tubes, V1 and V2.

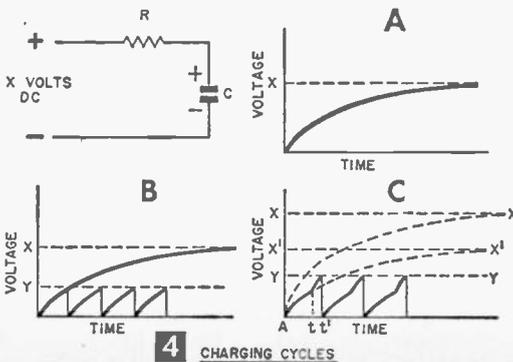

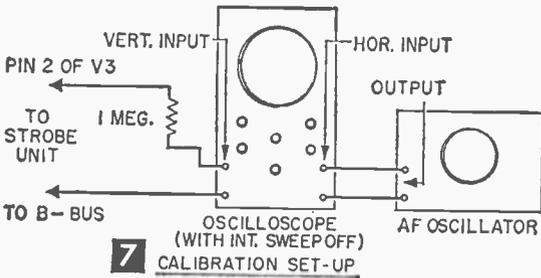

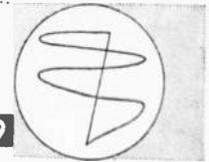8 SINGLE CYCLE PATTERN, WHERE FLASHING RATE EQUALS OSCILLATOR FREQUENCY. USE FOR 20-100 C.P.S.



9 DOUBLE CYCLE PATTERN, WHERE FLASHING RATE IS TWICE OSCILLATOR FREQUENCY. USE FOR 10-20 C.P.S.


The time between the peaks of the grid capacitor charging cycle is dependent on the time constant of the capacitor and the related resistor. The range switch SW2 provides additional capacity for the low frequency range, and R6 makes it possible to vary the time constant for each range. Wired as in the schematic, your strobe unit will have a low range of 10 to 40 cycles per second (600 to 2,400 rpm) while high will cover 25 to 100 cps, (1,500 to 6,000 rpm). You can change the coverage of the unit by altering the value of the grid circuit resistance and capacitance. Reducing the values increases the charging rate, which can be increased up to the maximum flashing rate of the tube, which is 240 pulses per second, (14,400 rpm).

It is however impractical to use flashing rates below 15 cycles per second for eye observation, since persistence of vision, the principle which makes it possible for us to see a series of still pictures as a movie, would tend to blur the image. Complete construction by applying the decals to identify the controls, and protect them with a coat of lacquer, or plastic spray.

Calibrating Your Strobe. While the stroboscope will be very useful at this point, calibration will enhance its uses in measuring exact speeds. Rather than calibrate the frequency dial on the back of the case directly, it is suggested that you make a chart (Fig. 6). Two methods of calibrating can be used; the latter requires an oscilloscope, and is somewhat more accurate.

The simpler method is to use a 33 $\frac{1}{3}$ and 78 rpm phono turntable, and a stroboscopic disc available at record stores (Fig. 5). Since the accuracy depends on the turntable, check it first, by watching the disc, with a fluorescent lamp, or neon bulb, which will flash at exactly the 60 cycle frequency of your power line. If your turntable is not equipped with a speed adjustment, you can slow it down by loading it with records.

Now, plug in the stroboscope, and allow it to warm up a few minutes. Set the range switch on high, with the control turned clockwise to the maximum flashing rate. Watching the disc, as in Fig. 5, turn the control counter clockwise until the 78 rpm ring appears to stop. Mark this dial reading on your chart, as 60 cycles per second (equal to 3600 rpm). Continuing to turn the dial counter clockwise, the ring will "stop" again at five lower points on your dial corresponding to 2400, 1800, 1440, and 1200 rpm. Repeating these

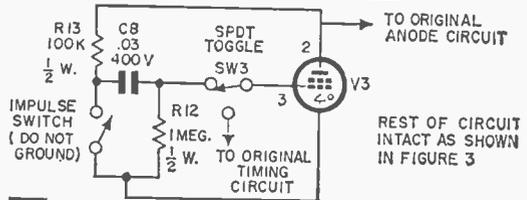

10 AUXILIARY TRIGGER CIRCUIT

steps on low range, you will be able to obtain four calibration points representing 1200, 900, 720, and 600 rpm. With all of these points plotted on your graph, you will obtain curves indicating in-between speeds, as in the graph shown in Fig. 6.

CAUTION: Avoid looking directly at the flashing stroboscopy for more than a few moments. The light can be harmful.

The second method of calibrating requires an oscilloscope and an audio oscillator, connected according to Fig. 7, with a 1 megohm resistor input attenuator. Provided that you have constant line voltage, and warm up your equipment beforehand, it will provide more accurate results. Set the oscillator to 100 cps (equal to 6000 rpm) and adjust the strobe control to get a pattern similar to the one shown in Fig. 8. Since rpm is equal to cycles per second times 60, reduce the oscillator frequency in steps and take note of the dial settings, on your graph, required to obtain the scope pattern shown.

At frequencies below 20 cps, adjust the strobe for a two-cycle pattern (Fig. 9) since most oscillators will not go below 20 cps. To calibrate the low range, start with the high end of the scale, with the oscillator set at 40 cps, and adjust the strobe dial for the two cycle pattern. The strobe is then flashing at 20 cps, or 1200 rpm. Establish your curve points downward, using the two cycle pattern.

Accessory External Switch. If you wish to observe a motor or mechanism in stopped motion, which is changing speed, you can do it by continuously adjusting the dial, or more conveniently by means of an external switch, and the simple circuit addition shown in Fig. 10. The external switch can operate on a cam, or flattened portion of a shaft. A miniature switch with a nylon contact button which will operate at up to 9,600 rpm, without bounce is offered by Licon Division of Illinois Tool Works (Switch #16-4041).

Tips On Strobe Use. Using the stroboscope, you will notice that often you can "freeze" motion

at several different flashing rates which are multiples of the true speed. High speeds above your top flashing rate can be measured as harmonics. Generally the true speed will produce the sharpest image. When measuring motor speeds, engrave or paint a fine line out from the center of the shaft. Harmonic speeds will cause the line to appear at several points.

When adjusting the flashing rate for the true

speed of an object, the object will appear to move slowly in its true direction when the lamp is flashing too slowly, and seems to move slowly in the opposite direction when the lamp is flashing too rapidly. If a motor for example, is running at a true speed of 1800 rpm, and your strobe is set at 1801, the image will appear to be rotating slowly at 1 rpm in the direction of the motor rotation.

AMATEUR RADIO PUZZLE

By JOHN A. COMSTOCK

Do you like ham radio? Then here is an anagram puzzle on your favorite hobby. This puzzle contains many of the words, terms and abbreviations that

(For Solution, See Page 89.)

ACROSS:


- 1) A ham meeting.
- 7) A call acknowledging card.
- 9) Traffic (CW).
- 10) Code.
- 11) A ham radio outfit.
- 13) What a (.) sounds like.
- 15) Generator of frequencies.
- 17) A ham radio conversation.
- 18) One-million cycles.
- 21) A vacuum tube.
- 22) A short-wave listener.
- 24) Mutual conductance.
- 26) A circuit that is charged electrically.
- 28) A bunch of interconnected parts.
- 29) Type of tube base having eight pins and an aligning key.
- 30) No connection made.
- 33) Resistance is expressed in _____ (supply missing letters).
- 34) Break.
- 36) Call for all stations.
- 38) A bunch of frequencies.
- 39) A positive-potential grid.
- 40) A class of amateur operator license.
- 41) An effect connected with antennas.
- 43) Unit of inductance.

- 44) What is the correct time?
- 50) A radio amateur.
- 51) Class of ham license.
- 53) Reversing current.
- 54) Current flow.
- 55) A meter band used by amateurs.
- 56) A type of antenna named after its inventor.
- 61) After-all.
- 63) Medium of radio wave transmission.
- 64) Opposite of signal gain.
- 65) A type of battery cell.

DOWN:

- 1) These are troublesome to some amateurs.
- 2) One-million cycles, ohms, etc.
- 3) Di-di-di-dah, di-dah.
- 4) Safety signal (CW).
- 5) An oscillator coupled by its electron stream.
- 6) Double cotton covered (wire).
- 8) Distress call (CW).
- 12) Vacuum tube cathode current.
- 14) Plate current flow.
- 16) A carrier of intelligence in communications.
- 17) A rig's location.

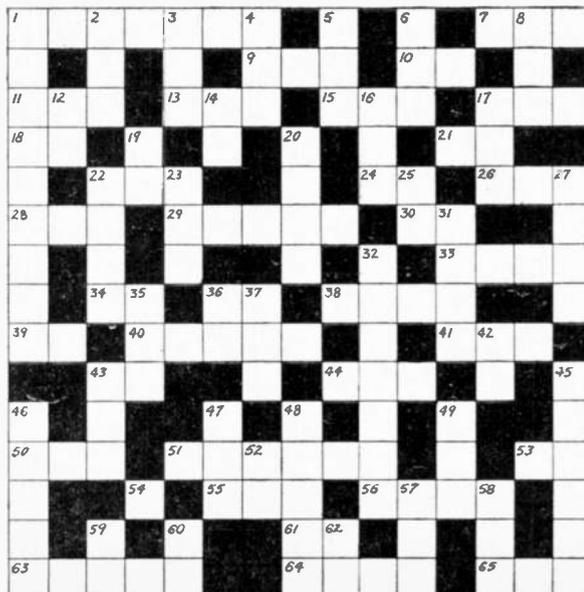
- 19) A wave that is continuous.
- 20) A type of transmission line used by hams.
- 22) Matching transformer.
- 23) An amateur radio station record book.
- 25) Minute.
- 27) To check equipment for proper operation.
- 31) Something you must learn to send and receive before you can obtain your ham license.
- 32) Type of oscillator circuit having a tapped inductance.
- 35) Ham radio operators often pound one.
- 36) Mid-tap (abbr.).
- 37) Shall I send more slowly?
- 42) Neon.
- 43) It's not good for a modulator to do this.
- 45) A ham license.
- 46) An inductance used to limit the flow of ac.
- 47) Potentiometer.
- 48) Last amplifying stage of a ham transmitter.
- 49) Something current does in an inductive circuit.
- 52) Di-di-di-dah, dit.
- 57) Address.
- 58) Continuous waves that are interrupted.
- 59) Watt-hour.
- 60) Regulates voltage.
- 62) Unmodulated carrier wave.




Ten-Twenty Short-Wave Receiver

By HOMER L. DAVIDSON

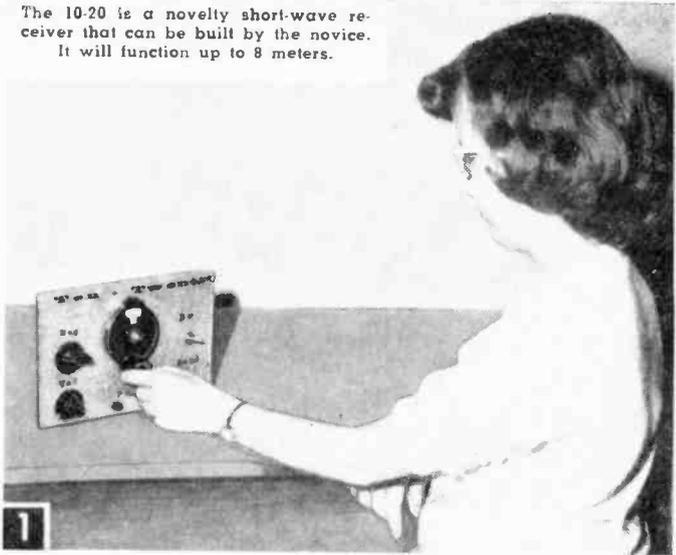The 10-20 is a novelty short-wave receiver that can be built by the novice. It will function up to 8 meters.





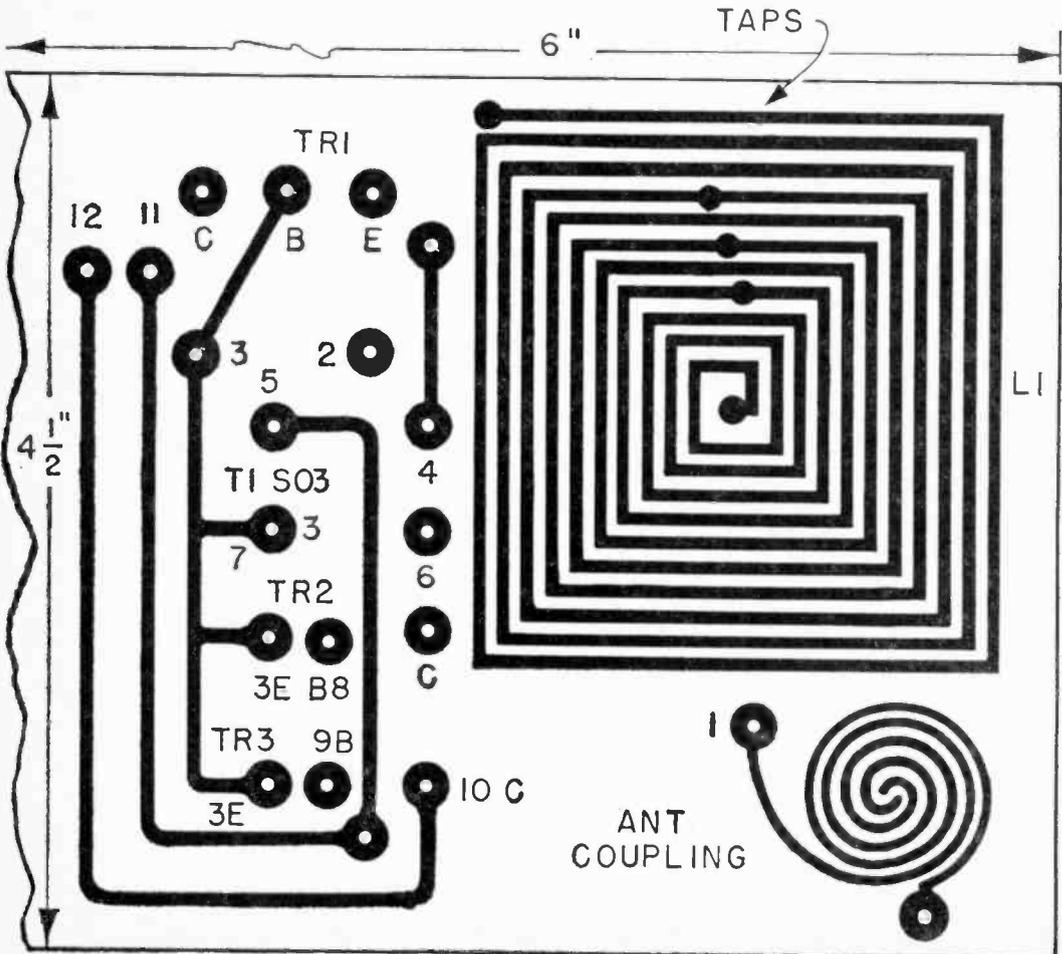HERE is a small, transistorized short-wave receiver—that the beginning experimenter can put together—that provides good short-wave listening on the 10- and 20-meter bands. And if you get a good specimen of a surface-barrier transistor, it will actually operate up to 8 meters.



2 PRINTED CIRCUIT BOARD

ACTUAL SIZE

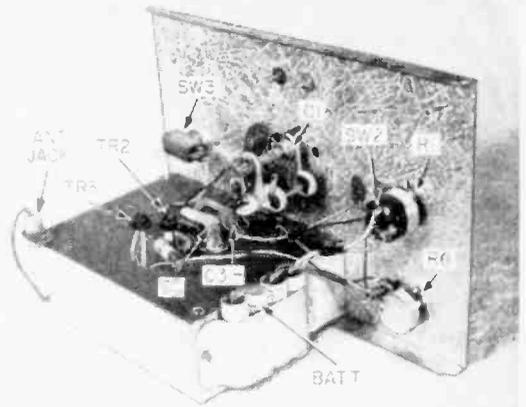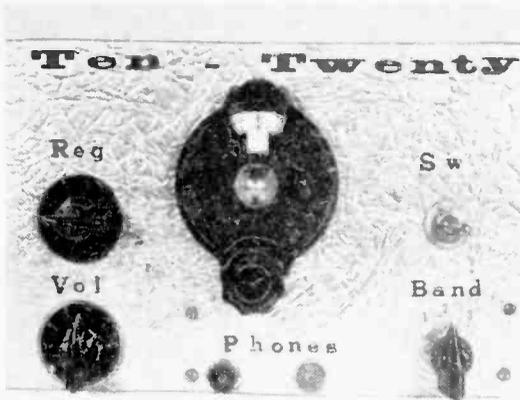

Transistor TR1, a Philco surface-barrier type, is the critical transistor. It is used as a super-regenerative detector.

The chassis for the transistor and parts is a printed circuit board (Fig. 2). Also on this board is coil L1. There is nothing complicated about laying out this coil. Follow Fig. 2, laying out 1/16-in. resist tape on the lines. Be sure the resist-tape has a spacing of its own width between each turn of the coil (a total of 10 turns). The coupling capacitor to the antenna jack and switch is also printed on the board. It is drawn with a ball point resist paint.


A homemade RF choke is wound with 35 turns of No. 28 cotton-covered wire over a 1/4-in. dowel.


The regeneration control R1 and C3 form a time constant creating another oscillation that increases the sensitivity of the small receiver. Use of diode D-1 is optional. On the 10-meter band the fixed crystal band the fixed crystal diode seems to strengthen the signal and sharpens the regeneration point of oscillations. But on the lower, 20-meter band there isn't too much improvement. If you have a fixed diode on hand, solder it into the circuit. Otherwise, omit it.

There are two stages of audio incorporated here with a small volume control in the input circuit of TR3. The output of TR3 is fed directly into an earphone. Battery supply B1 furnishes voltage to the regenerative circuit. Regeneration is very smooth with this

type of operation. Battery supply B2 furnishes voltage to the collector side of TR1 and to both audio transistors.

Printed Circuit Layout. Trace the printed circuit directly on the printed copper board from Fig. 2. Place a carbon paper beneath this drawing and transfer it with pencil to the board. (Wash the printed copper side with soap and water to remove any finger marks or grease that might be on it.) A sharp pocket knife will be needed to cut off the tape at the joints. A ball point pen will make coupling loop and all round connection joints. If the paint runs into another circuit, let it dry and then take the pocket knife and cut or scratch out a separation. (This can

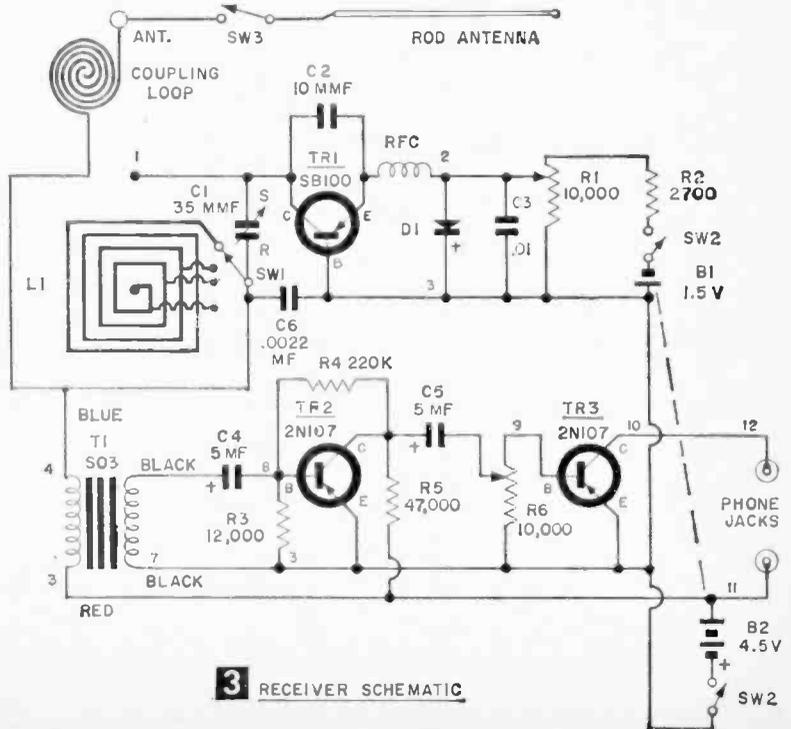

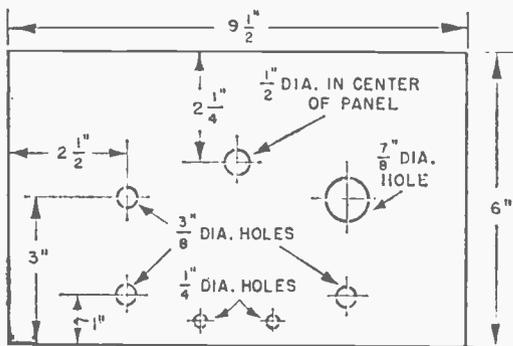

4 FRONT PANEL LAYOUT

also be done after the circuit has been etched by cutting or scratching out the jointed copper circuits.)

After the circuit has been traced on the copper board, lay down the tape resist and pen point in the rest of the circuits. Let the paint dry several hours, then pour enough etching solution into a small tray or flat dish to just cover the printed board. Rock the tray back and forth for quicker etching. It will take about an hour to complete the process.

Wash the board in clear water and pour the etching solution back into its container. (The solution can be used over and over again.) Now remove the resist material. Use a small knife point to pull off the tape and scratch off the paint resist. Drill all small holes before mounting any parts.

Set Operation. All of the small parts are mounted on the printed circuit board as they are wired into the circuit. Cut the front panel (Fig. 4) from Reynolds aluminum stock, available in

MATERIALS LIST—10-20—SHORT-WAVE RECEIVER

Desig.	Description
C1	35 mmfd Hammarlund variable capacitor MC 35-5
C2	10 mmfd fixed disc capacitor
C3	.01 mfd 200-V paper capacitor
C4-C5	5 mfd 25V elec. capacitor
C6	.0022 mfd disc capacitor
R1, R6	10,000-ohm variable resistors
R2	2700 ohm, 1/4-watt fixed resistor
R4	220,000-ohm, 1/4-watt fixed resistor
R5	47,000-ohm, 1/4-watt fixed resistor
SW1	4 position, single throw rotary switch
SW2	DPDT switch on rear R1
SW3	SPST toggle switch
D1	1N64 or 1N34 fixed crystal
T1	S-03 transformer or equivalent (standard transformer)
TR1	SB100 Philco transistor
TR2-TR3	2N107 GE transistors
B1	1 1/2-v penlite cells
B2	three 1 1/2-v penlite cells
RFC	35 turn scramble wound over 1/4" form
L1	see text description


PRINTED CIRCUIT MATERIALS

Techniques Kit—Technicians #5003P obtainable from Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, N. Y.

Alternate Kit

1-pt	PE-5 liquid etchant
1	PRLT liquid resist ball point pen
1	PCB XXXP copper Lam., 1 side 4 1/2 x 6"
1	PRT-2 tape resist 1/16 x 320"
	Also obtainable from Lafayette Radio

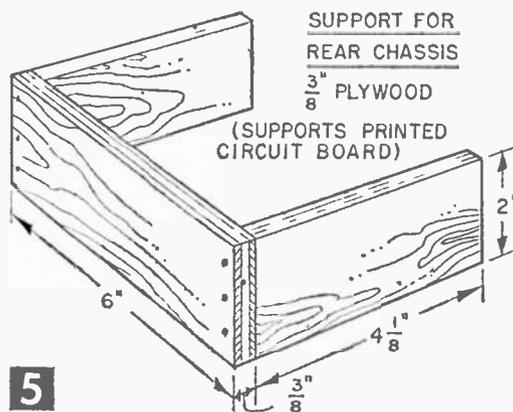sheets at the local hardware store. Figure 5 gives dimensions of the PC board support. Check correct battery polarity before throwing the on-off switch, plug in a pair of earphones and the unit is ready to go. Turn on the regeneration control in the earphone. Hook up the antenna and rotate




5

the tuning dial. Stations and whistles will be heard throughout the bands. When a station is located, turn the regeneration control down until the station is audible.

This little receiver has plenty of volume for earphone operation and some strong short-wave stations can be heard with the earphones laid beside the set. Not only will this small short-wave receiver bring in the 10- and 20-meter amateur bands but also aircraft signals and police bands.

Modified Screwdriver Lifts Tube

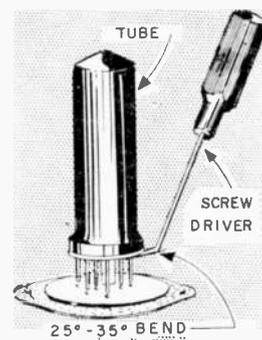• A long-stemmed screwdriver with the bit bent at a 25 or 35° angle makes a handy tube lifter for extracting tight-fitting tubes. To make the bend, heat the tip to a cherry red and let it cool slowly to remove the temper. Bend, then reheat the tip and plunge it into oil. The modified tool also makes a handy offset screwdriver for reaching into inaccessible places on a chassis.—JOHN A. COMSTOCK.




Phono Turntable Repair

• Poor reproduction from a phonograph having the rim-drive type turntable mechanism is usually caused by slippage of the rubber-tired drive wheel. To renew the grip of the rubber tire, sand it lightly with sandpaper. A non-slip dial compound (such as General Cement's *Non-Slip*) applied to the wheel will also cure slippage.

Telephone Actuated Switch For Remote Control

By W. F. GEPHART

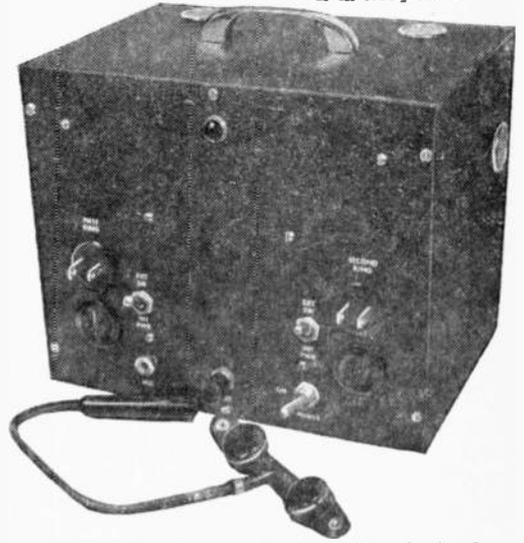Front-panel view of telephone switch remote control unit. Note circular vents in cabinet. Throat microphone is in foreground.



A TIMER will turn on a device at some future time, but it doesn't permit a change in plans. For example, it's nice to have the air conditioner on when you get home after a summer outing, but only if it's needed. With this telephone switch, you can be sure it turns on *only* when needed, because you turn it on by telephoning your home. The only requirement is that you have a dial telephone and the type of service where your telephone rings only when your number is called. Most metropolitan telephone service is of this type.


Switch operation is based on the timing relationship between ringing signals, and minor circuit modifications may have to be made to fit the ringing sequence of your telephone system. The circuit shown here is based on a system of one-second rings, spaced at five-second intervals. If your system operates on a different sequence, an understanding of the circuit is required to make the necessary, and minor, changes.

Tube V1 in Fig. 2 is an amplifier which closes relay Ry1 when the telephone ring is picked up by the microphone plugged into jack J1. Since this "connection" to the telephone is acoustic, it does not violate telephone company rules against devices attached to telephone lines "directly or by induction." Every time Ry1 closes, the "pulse" coil (Ry2A) energizes, moving the stepper relay arm one position. Tube V2 is a timing circuit that closes Ry4 for a given period of time when capacitor C4 is momentarily shorted out.

To operate the switch you dial your telephone number, let it ring just once, and hang up. You wait a few seconds, then dial your number again. Let it ring once to turn on the first device, twice to turn on a second device, etc. Ten seconds after you hang up on the second call, the device plugged into the proper outlet will come on.

The ring on the first call closes Ry1 momentarily and moves Ry2 to Position 1. This completes the circuit to the heaters of thermal relays Ry3 and Ry5, which require 12 and 25 seconds, respectively, to close. During the dialing time for the sec-

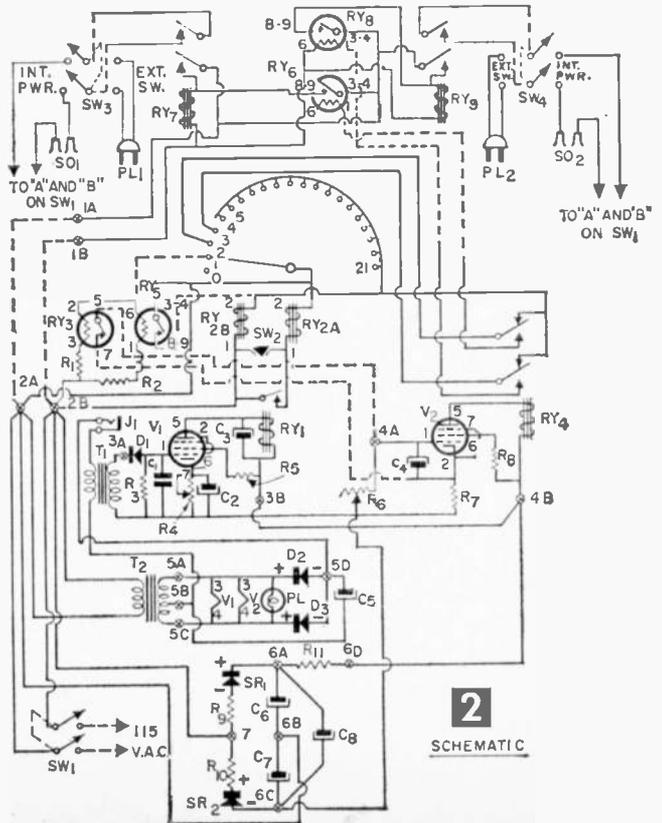ond call, Ry3 closes, shorting C4, which closes Ry4. The first ring of the second call moves Ry2 to Position 2, which removes the voltage to the heaters of Ry3 and Ry5. Ry3 opens and




Ry5 starts cooling, having had insufficient time to close. If you hang up after the first ring on the second call, Ry2 remains on Position 2, which completes the circuit to the heater of thermal relay Ry6.

After ten seconds, this relay closes, closing control relay Ry7, which turns on the device plugged into SO1. The control relay is then held closed by holding contacts.

Now the device is turned on, but the stepper relay (Ry2) is on Position 2 and Ry6 is still heated. After a time interval in the V2 circuit, Ry4 opens, removing the voltage to the heater of Ry6 and completing the circuit to the re-set coil (Ry2B) of the stepper relay. The stepper re-sets to zero position, Ry6 cools and opens, but Ry7 remains closed through its holding contacts. The unit is then back to the original condition, except that the first remote-controlled device is now turned on.

As shown here, the unit has two controlled circuits. Additional circuits for Positions 4, 5, 6, etc., could be incorporated for use by adding additional thermal and control relays. In such case, the time interval of V2 would have to be increased.

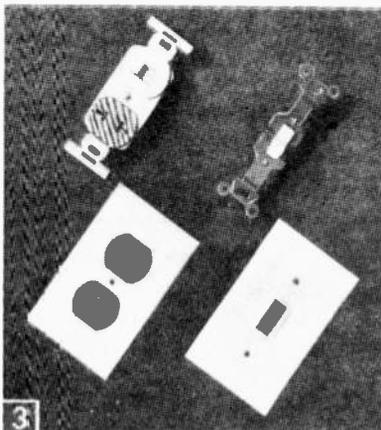Proper timing is the key to successful operation. The timing of the thermal relays can be extended somewhat by resistance in the heater circuit, such as R1 and R2. Relay Ry3 is rated to close in 5 seconds, but closes at 12 seconds, due to R1, while R2 delays Ry5 from its rated 15



Switch-outlet at left replaces regular switch at right (see text) when appliance controlled by wall switch is to be remote-controlled by telephone.


seconds to about 25 seconds. This use of resistors provides non-standard intervals and speeds up cooling (and therefore opening) time. A 25-second relay could be used for Ry5, but its normal opening time is about 90 seconds, as compared to the 15-20 seconds of Ry5 (as used here). Also, the octal version is used for Ry3, as it cools and opens faster than the miniature version. The timing of the V2 circuit is set by R6, whose adjustment will be discussed later.

Other Calls. Let's assume another caller than yourself lets your telephone ring a number of times before he hangs up. On each ring, Ry1 closes, the first ring moving the stepper relay arm to Position 1. The second ring occurs


five seconds later, so neither Ry3 or Ry5 can heat up or close. This second ring moves the stepper to Position 2, which closes the circuit to the re-set coil (Ry2B) through the contacts of Ry4 (since this relay is still open), and the stepper re-sets. The third ring moves the stepper to Position 1, the fourth to Position 2, which resets it, and the sequence continues.

When the caller finally hangs up, the stepper will either be at zero position or Position 1. At zero position, the unit is at normal position, so no further action is required. If ringing stops with the stepper on Position 1, Ry3 closes after 12 seconds, closing Ry4. Some 12 seconds later, Ry5 will close, completing the circuit to re-set coil Ry2B, and returning the stepper to zero position. In another 10-12 seconds, Ry4 will open, and the unit will be back to normal.

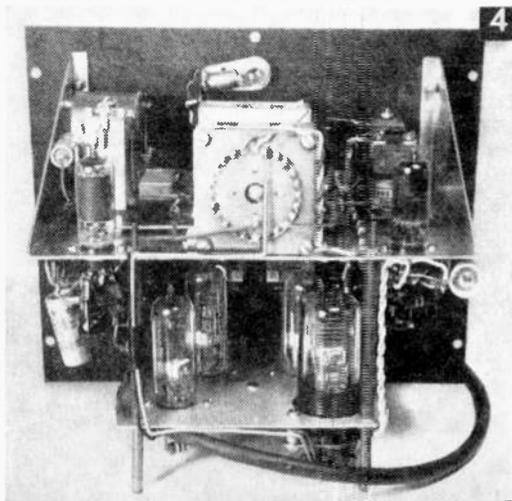If, during the above, another call comes in after Ry4 closes, but before Ry5 can close and re-set the stepper, the first ring will move the stepper arm to Position 2. Since Ry4 is closed, the circuit to Ry6 will be completed, but the next ring



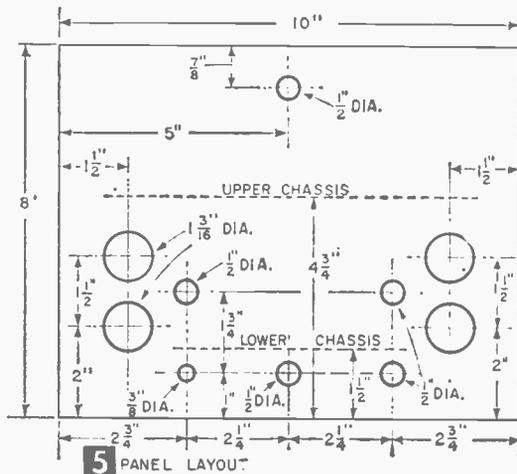Back view of unit showing dual chassis construction.



on this second call will move the stepper to Position 3 before Ry6 can close. The third ring will move the arm to Position 4 before Ry8 can close, and the stepper will then be re-set even if Ry4 is still closed.

If your telephone rings just once (as often happens), Ry3 and Ry4 will close, but the unit will be re-set as mentioned above. If a second call comes in within the 30-odd seconds while Ry3 and Ry4 are closed, nothing will be turned on unless this second call consists of only one or two rings. Essentially, then, the unit is foolproof.


Use. In Fig. 1, the first ring controlled device is plugged into the socket on the left; the second-ring controlled device is plugged in on the right-hand socket. Switches SW3 and SW4 determine whether the unit is to control the external device by furnishing it with power or simply by closing a circuit.

A light or fan normally controlled by a wall switch can be handled by this unit without radically altering the house wiring. Remove the wall switch and substitute a combination switch-outlet, wiring switch and outlet in parallel and connecting the regular wiring to the terminals. The light or fan can then be operated by the new wall switch (as before with the old) or by "jumpering" the outlet. The telephone switch does this "jumpering" when SW3 or SW4 are set on "External Switch" and an ordinary extension cord is connected between the "External Switch" plug on the unit and the new outlet. The old and new items involved are shown in Fig. 3, with stripes painted on the outlet to distinguish it from a power outlet.

By using impulse relays instead of regular relays for Ry7 and Ry9, the unit can be used to turn things "off" or "on" or both. The impulse relays are wired the same as Ry7 and Ry9, except that holding contacts are not used. The first call throws the relay arm to one position and the second call, using the same code, throws it to the other position.

The "Test" button (SW2) on the front panel parallels the contacts on Ry1 and advances the stepper relay each time it is pressed. It can be used for checking the timer circuits and—when impulse relays are used—can be used to turn things "off" or "on" manually. When regular control relays are used, a device that has been turned on by a telephone call can be turned off only by unplugging it or turning the entire unit off for a moment.

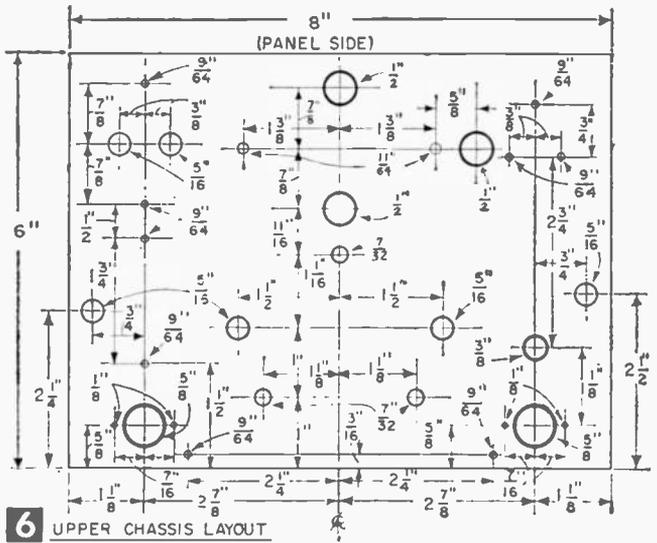Filament transformer T2 provides filament voltage and with D2 and D3, approximately 3.5 volts dc for the carbon microphone. Plate voltage is provided by a voltage doubler (SR1, SR2, C6, C7 and C8) which connects directly to the power line, requiring that no connection be made




6 UPPER CHASSIS LAYOUT


to the metal chassis or cabinet.

Construction. Figure 4 shows a back view of the unit. Dual chassis construction is used both to secure adequate room and to minimize the heating effect on the thermal relays. All heat generating items (tubes, pilot lights, etc.) are mounted on the well-ventilated upper chassis, and the thermal relays and control relays are mounted on the lower chassis.

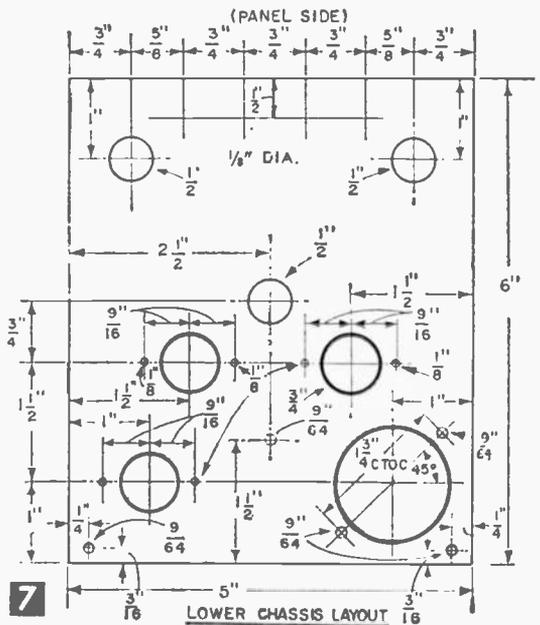Layouts for the panel, upper and lower chassis are shown in Fig. 5, 6, and 7. The upper and lower chassis are made of scrap aluminum, attached to the panel with aluminum angle. The side sections on the upper chassis are not absolutely necessary, as the connecting bolts between



7 LOWER CHASSIS LAYOUT

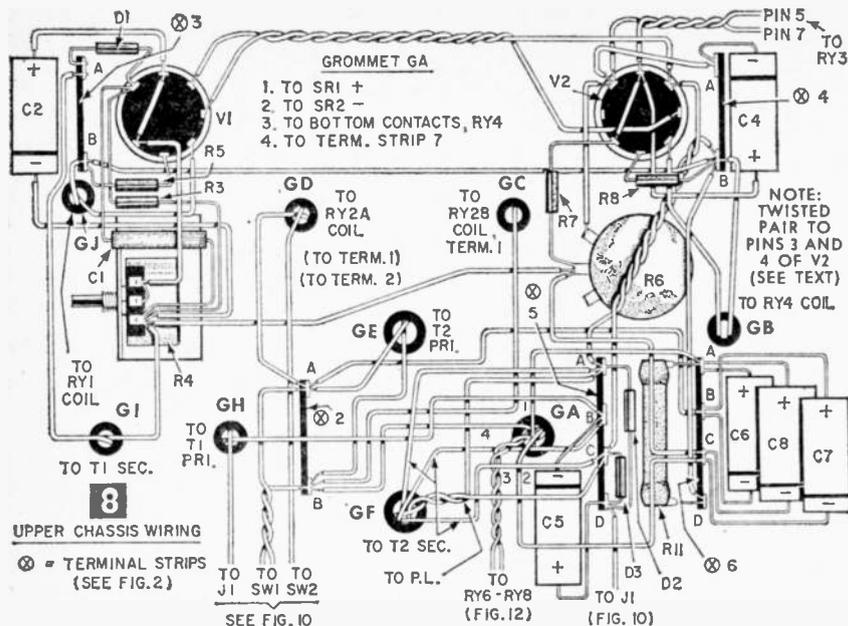

the two chassis (which rest on the bottom) will properly support the upper chassis. If scrap aluminum is not on hand, a $3\frac{1}{2} \times 6 \times 8$ -in. "Minibox" (Bud CU-3009 or CU-2109) will provide all that is required. The flanged side of this box will make the upper chassis merely by cutting the ends of the box to make the side supports, and the other half of the box will make the lower chassis and the 2×2 -in. mounting for R4.

After the panel and chassis sections have been drilled and punched, mount components on all three and attach the upper chassis to the panel. The upper chassis and panel must be wired before the lower chassis is attached to the panel, and the heavy lines in the schematic (Fig. 2) show this initial wiring. As it proceeds, hold the lower chassis (with components mounted) in place from time to time, to check for clearance.

Figures 8, 9, 10 and 11 show wiring. In Fig. 8 a twisted pair is shown to pin 3 of V2 and terminal 4B of the terminal strip, upper right. The twisted pair leads should be shown to pins 3 and 4 of V2; the lead now going to terminal 4B should be shown to V2's pin 4. Filament and pilot light wiring is done first, followed by the carbon microphone voltage supply. The dc power supply is wired next, and then the relay wiring. In wiring between SO1, SO2, PL1, PL2, SW3, SW4 and the contacts on Ry7 and Ry8, be sure to use at least #14 wire. The tube circuits are wired last.

Testing. Before attaching the lower chassis, temporarily attach ac leads to SW1 and make sure that filament, microphone and plate voltages are available. The filament voltage should be 6.3 v ac, the microphone voltage about 3.5 v dc, and the plate voltage around 260-280 v dc. Next, put V1 in its socket and adjust sensitivity control R4.

This adjustment is very critical and must be


set to your telephone. If your telephone has an adjustable bell, turn the bell to its loudest point to minimize the sensitivity required. Also, allow the unit to warm up 5 minutes before making adjustment.


Insert a milliammeter in the B+ lead of V1 at Tie Point 3B. Using R4 to vary the plate current, adjust the relay spring so that the relay closes at about 5.8 ma. With this adjustment, the relay should open at about 4.4

ma. Then set R4 so that the tube draws about 4 ma.

To test this adjustment, place the microphone under the telephone with the two buttons resting against the bottom of the instrument as close to the ringer openings as possible, to utilize both sound and vibration. Have a friend call you and see if Ry1 closes on each ring, and what current is drawn by V1 during the ring. The dc voltage across R3 during ringing ought to be about 6 v, increasing the plate current to over 6 ma. There is a fraction of a second delay in the relay closing, due to the charging of the capacitors in the V1 circuit, but this minimizes accidental triggering of the relay when the telephone is touched or the receiver raised. If the plate current of V1 drops during the ringing, check the polarity of D1.

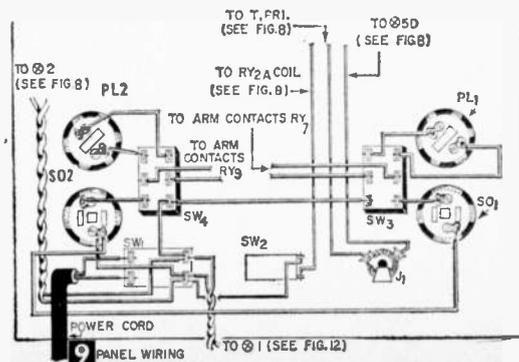
After this adjustment has been made, put V2 in its socket and set R6 at mid-resistance point. As V2 warms up, Ry4 will close and reopen after a short interval. This is caused by plate current flowing as C4 charges up. After Ry4 opens, set R6 to maximum resistance and mo-



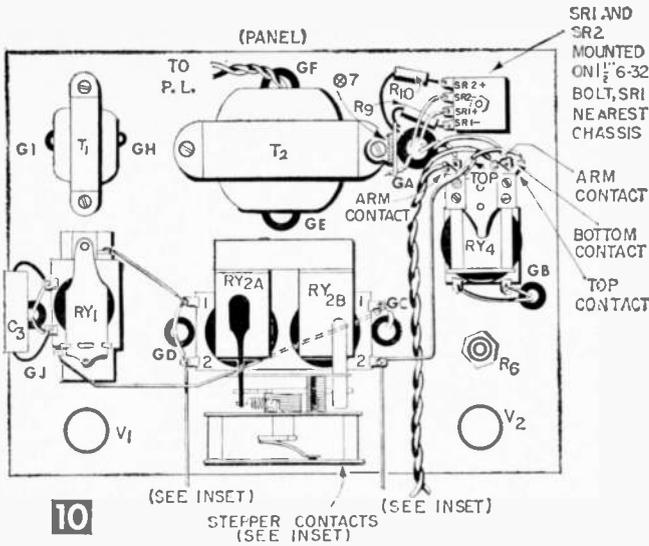

mentarily short Pins 1 and 2 of V2. The relay should close for over a minute with R6 at full resistance. Later, R6 can be adjusted for the exact time interval required.

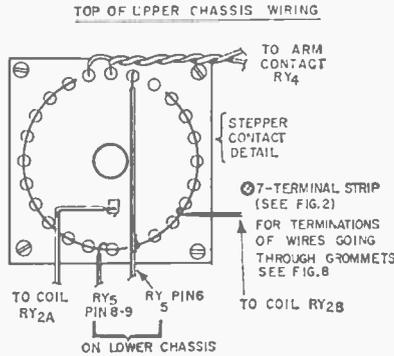Check the ringing amplifier again when Ry4 is closed (and V2 drawing current) to make sure that Ry1 will close properly on a ring when the supply voltage is reduced by the load of V2.



Before attaching the lower panel, pre-wire it to the extent possible, as shown in Fig. 11 and in the light lines in the schematic, Fig. 2. Then fasten it to the panel and bolt the two chassis together with two 5-in. 6-32 bolts and spacers. The spacers are made of 1/4-in. copper tubing, the ones between the chassis being 3 3/4-in. long, the lower ones 1 1/2-in. long. The wiring is then completed as shown by the dashed lines in Fig. 2, running some wires from one chassis to the other along the spacers.

To check final wiring and thermal relay timing, plug in both tubes and Ry3, and press the "Test" button once. The stepper relay should move to Position 1, and after about 12 seconds Ry4 should close, indicating that Ry3 has closed. This interval was selected as the average time required to hang up after the first call, re-dial a seven letter-digit number, and get the first ring. If this time is too long, or Ry3 doesn't close, reduce the size of R1, by trial and error. If the interval is too short, increase R1.


Next, remove V2, re-set the stepper manually, and plug Ry5 in. Press the "Test" button once, advancing the stepper to Position 1. After about 25 seconds the stepper should re-set, indicating that Ry5 has closed. If this timing interval is off, adjust with Ry3.

For final checks, replace V2, set SW3 and SW4 to "Internal Power," and plug a table lamp (or night light) with the lamp switch "on" into SO1 and SO2. Press the "Test" button once and as soon as Ry4 closes, press it again. After 10 seconds, Ry7 should close, turning on the lamp plugged into SO1. Repeat this test, but press the button twice after Ry4 closes to see if Ry9 and the lamp plugged into SO2 goes on. To release control relays (Ry7 and Ry9), turn the unit off momentarily.



Before adjusting timing control R6, have a friend call you so you can time the length of the rings and the interval between them. The time Ry4 stays closed must be equal to the total ring-interval time that it takes to move the stepper relay to the last control position (in this case, Position 3), plus 10 seconds. For example, in the unit shown (with two control positions) with a ringing pattern of one second rings spaced five seconds apart, the total time for Ry4 to be closed would be:

- 1 second for ring that moved Ry2 to Position 2
- 5 seconds interval between rings
- 1 second for ring that moved Ry2 to Position 3
- 10 seconds for Ry8 to close
- or a total of 17 seconds, plus 5 seconds leeway for a total of 22 seconds

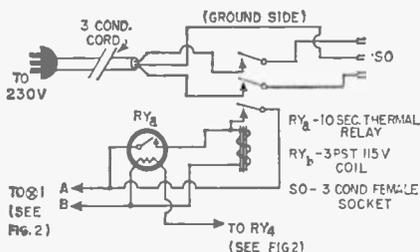Set the time on Ry6 by shorting Pins 1 and 2



12 230 V CONTROL RELAY WIRING

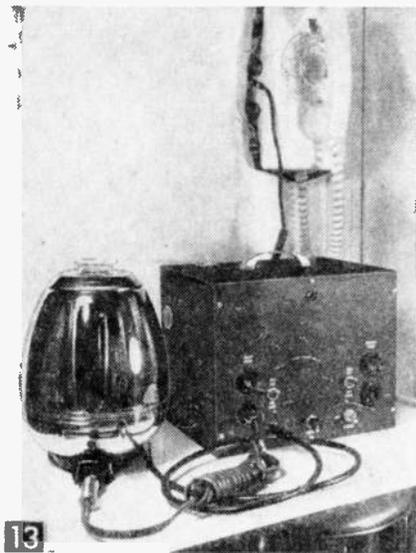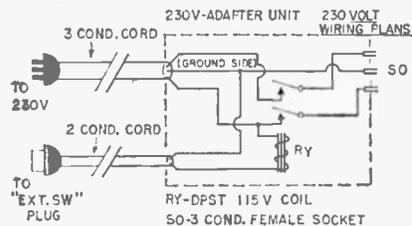

13 Unit in operation. Throat mike on wall telephone will turn on coffee maker—black box, black magic, black coffee.

of V2 together repeatedly until the desired time is reached.

Final tests consist of having a friend call to check operation under actual conditions. With table lamps plugged into SO1 and SO2, and SW3 and SW4 on "Internal Power," have your friend call, let the phone ring once, re-dial and let ring once again. If the first ring on the second call comes in before Ry4 has closed and your friend's dialing speed is average, decrease the time for Ry3 to close. If Ry4 had closed before the first ring of the second call came in, the lamp plugged into SO1 should go on about 10 seconds after the second call. Repeat this test, but let the telephone ring twice on the second call. Lamp 1 will remain on, and 10 seconds after the second ring, Lamp 2 should go on, the stepper relay re-setting shortly after. If Ry4 opens (re-setting the step-

MATERIALS LIST—TELEPHONE SWITCH

Desig.	Description
R1	1200 ohm, 1 watt
R2	2000 ohm, 1 watt
R3	.27 meg. 1/2 watt
R4	2000 ohm potentiometer
R5	27K, 1 watt
R6	5 meg potentiometer
R7	3000 ohm, 1 watt
R8	12K, 1 watt
R9, R10	27 ohm, 1/2 watt
R11	3000 ohm, 10 watt
C1	.02 mfd, 200 v
C2	10 mfd, 25 v
C3	25 mfd, 25 v
C4	50 mfd, 15 v
C5	50 mfd, 6 v
C6, C7	20 mfd, 150 v
C8	20 mfd, 450 v
Ry1	SPDT, 2500-ohm coil (Potter & Brumfield LM-5)
Ry2	midget 21 pos. stepping relay (Guardian MER-115)
Ry3	5-sec. thermal relay, normally open (Amperite 115M05)
Ry4	4PDT, 5000 ohm coil (Guardian Series 200 coil, and Type 200-M5 contacts)
Ry5	15-sec. thermal relay, normally open (Amperite 115N015T)
Ry6, Ry8	10-sec. thermal relays, normally open (Amperite 115N010T)
Ry7, Ry9	4PDT, 115-v ac coil (Guardian Series 200 coil & Type 200-M5 contacts)
T1	microphone transformer (Merit A-2929)
T2	filament transformer, 6.3 v @ 2 amp. (Merit P-2945)
SW1	DPST 15-amp. toggle switch (Carling 2FB54-73)
SW2	SPST push button
SW3, SW4	DPDT 15-amp. toggle switches (Carling 2GL-53-73)
J1	open circuit jack
D1, D2, D3	1N66 or 1N34 diodes
SR1, SR2	65 ma., 130-v selenium rectifiers
PL1, PL2	male chassis plug (Amphenol 61-M)
SO1, SO2	female chassis socket (Amphenol 61-F)
PL	6.3-v pilot lamp and jeweled socket
V1	6AU6
V2	6CB6

per) before Lamp 2 comes on, lengthen the time interval of the V2 circuit, by adjusting R6.

Adaptations.

This unit can be used for switching 230-v circuits by altering either or both control relays (Ry7 and Ry9) or by building separate 230-v adapters.

Both means are shown in Fig. 12. Either alteration requires a power lead to a 230-v source. With relay modification, this lead can be brought out of the cabinet at the point normally used for SW3 or SW4.

The control relays specified have 8-amp. contacts. If additional capacity is required, either heavier relays (requiring additional chassis space and heavier internal wiring) or external power relays will be required. In the latter case, the external relay used to turn the device on should have a 115-v ac coil. It would be plugged

into SO1 or SO2. When using unit with air conditioners or other heavy-duty appliances, use a portable cord and other connected wiring from an outside relay that has adequate size to carry the current of the appliance safely. Relay contacts should also be capable of carrying the required current.

Figure 13 shows the unit in operation—using the throat microphone strapped to a wall telephone—set up to turn on an automatic coffee maker. Whenever using the unit with a telephone with a separate bell, the microphone should be strapped to the bell box, near the bells.

In operation, there are several points to keep in mind:

- 1) Let the unit warm up five minutes before using.
- 2) Place the microphone as near the bells as

possible, and tight against the bottom (or side) of the telephone or bell box, to get both sound and vibration. Where adjustable bells are available, set to loudest setting.

3) Keep in mind that, when calling, the sound you hear is not the actual bell ringing; it is a ringing "signal" indicating that ringing current is being placed on the line. If the sound is a short, fractional part of a full ring, the bell may have merely "tinkled," and Ry1 may not have closed. In such case, complete the calling procedure, and if there is any doubt in your mind, repeat it a minute later. Unless impulse relays

are used (to turn "on" and "off"), repeated calls on the same code won't hurt.

4) You can turn on the circuits in any sequence; that is, Number 2 first, followed by Number 1, or vice-versa.

5) If there is repeated difficulty in Ry1 closing on rings, check your line voltage regulation. In areas of high line-voltage variation, the plate voltage to V1 may vary enough to require different settings for R4. In such case it may be necessary to put two voltage regulator tubes (an OA2 and OB2, series-connected) in the doubler power supply circuit.

Compass Galvanometer

MANY electrical measuring instruments are based on the design of the d'Arsonval String Galvanometer, but substitute a needle-suspended coil riding on jeweled bearings for the hanging coil employed in the original precise lab instrument.



The galvanometer is usually used to indicate the polarity and presence of small currents by comparison methods.

The d'Arsonval instrument suspends a small coil between the poles of a permanent horseshoe magnet. When a current flows through the coil it becomes an electromagnet and its like poles repel the like poles of the horseshoe magnet, thus causing the coil to turn or twist on the metallic string or ribbon by which it is suspended (Fig. 2). The strength of the current determines the extent of the coil's rotation.

A small pointer attached to the moving coil registers on a curved dial, or a tiny mirror is attached to the galvanometer string. A beam of concentrated light is aimed at the mirror, bouncing the beam off to a wall screen or chart to give great magnification of tiny current changes.

Making a Simple Galvanometer. A small amount of insulated magnet wire, any pocket compass and a 2 1/4 x 3 1/2-in. scrap of plywood is what you need to make the simple galvanometer shown in Fig. 1. Cut a strip of cardboard 3/4 in. wide and 3 3/4 in. long. Score the cardboard 3/4 in. from each end, with a dull knife blade and crease so the cardboard resembles a C or bridge shape. Now glue the cardboard to the edges of the wood base.

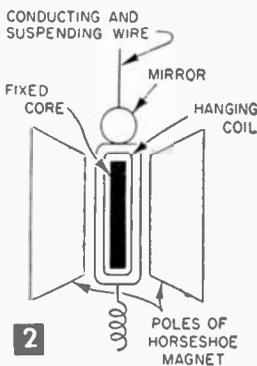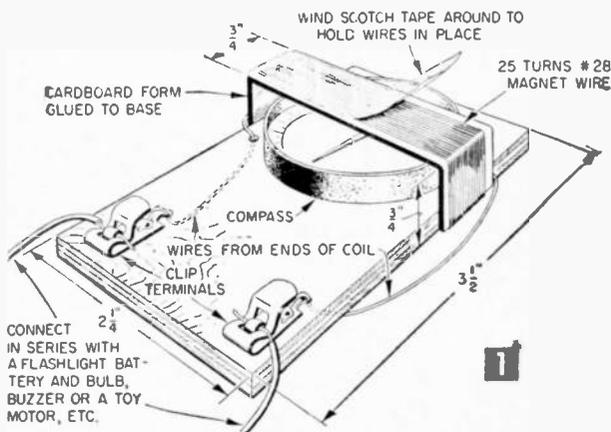Bind the cardboard with a rubber band until glue or cement dries. We wound 25 turns of #28 magnet wire around the cardboard, but heavier



wire and fewer turns will work, too, with a slight drop-off in sensitivity.


Scotch tape is wound around the finished coil to keep the wire turns in place. Connect the ends of the coil to screw terminals or clips. Slip the compass under the coil in a position where its needle comes under the coil and parallel to the coil turns.

Connect the galvanometer in series with a flashlight battery and bulb, a buzzer or a toy motor, etc. When the circuit is closed the compass needle will be drawn so that it is at right angles to the coil (Fig. 1). A


slow swing of the needle indicates the circuit is drawing little current. A rapid swing denotes an increase in current flow.

To show how sensitive this simple galvanometer is, connect what appears to be a dead flashlight cell across the terminals, immediately breaking the circuit. The compass needle will spin at a merry clip.

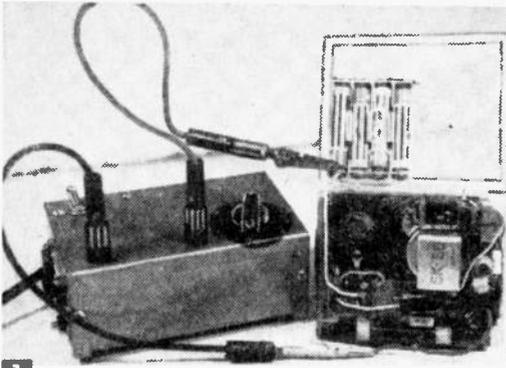The compass galvanometer's needle would be the horseshoe magnet in the d'Arsonval instrument. But, here we cause the magnet to turn with the coil remaining in a stationary position. However, the end result is the same no matter how the galvanometer is constructed.



1

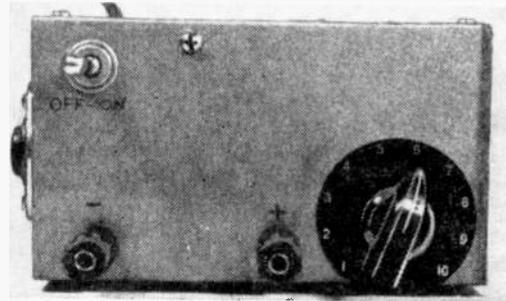


One of the handiest instruments the serious transistor experimenter can own, this regulated power supply has variable voltage control from zero to 10 volts dc.

transistor circuit, a variable output voltage control, and regulation that will keep the output voltage from varying due to changes in line voltages or changes in equipment current demand. Cost of components for this unit is approximately \$15.

Operating Principles. The common collector transistor circuit configuration (Fig. 2A) performs the regulation task in this power supply. This circuit, sometimes referred to as an "emitter follower circuit," is the transistor counterpart of the vacuum tube cathode follower. The circuit has 100% current feedback and is extremely stable under temperature variations. The voltage from emitter to ground is nearly equal to the applied voltage from base to ground. The emitter voltage remains constant in spite of relatively large fluctuations in the collector voltage or variations in the emitter to ground load resistance. The emitter current is equal to the base current times the Beta of the transistor. Thus, a battery may be used to set the base potential.

The circuit of the regulated variable power supply is shown in Fig. 2B. The transformer is a 12.6 v, 1 amp filament unit. A General Electric 1N1115 silicon rectifier is employed in a half-wave circuit with a 1,000 mfd filter capacitor. This basic dc power supply provides collector voltage for transistors T1 and T2, and in turn, voltage at relatively high currents for the load.

Base voltage for transistor T1 is supplied by a reference supply consisting of the 12-v battery B and the 5K potentiometer R1. R1 may be adjusted to present any voltage from 0 to 12 to the base of emitter follower T1. Transistor T2 is another emitter follower directly coupled to T1. The current gain of the cascaded emitter followers is so great that for reasonable power loads, the current demand on the battery (beyond the current required by R1) is negligible (R1 draws 2.4 milliamperes from the battery). The battery switch SB and the line switch SA are ganged to prevent battery current flow when the power supply is turned off. Resistor R2 permits adjustment of the

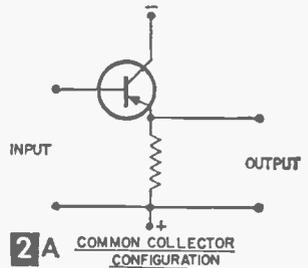


For Transistor Circuits— A Regulated Variable Power Supply

By FORREST H. FRANTZ, Sr.

POWERING experimental transistor circuits with batteries is expensive and exasperating. It's difficult to keep a supply of fresh batteries on hand, and the variation of voltage requirements from one circuit to the next means frequent changes in a battery supply lash-up. Voltages that aren't multiples of single cell voltage can't be obtained from batteries without wasting some battery power, and the voltages of the cells themselves tend to drop quickly.

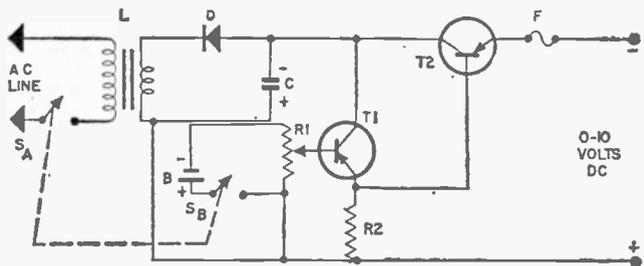The obvious answer is a power supply that operates from the ac line. The power supply described in this article has extremely low ripple—good enough for the most crucial



2B CIRCUIT OF REGULATED POWER SUPPLY







Eliminating TV Interference

How simple filters can cut out annoying TVI from home appliances, neon lights, aircraft, ham broadcasts or other sources

By W. F. GEPHART

TELEVISION interference (TVI) comes from a number of sources, and to eliminate it we must first determine the type and, if possible, the source (Figs 1, 2 and 3).

For best results, the interference should be filtered out at the offending device; if that is not possible, it probably can be eliminated at your TV set. Interference is classified into two types as in Table A, (1) broad-band, where the source consists of many frequencies and harmonics; and (2) narrow-band, where the source has one fundamental frequency and normal harmonics. Most narrow-band inter-

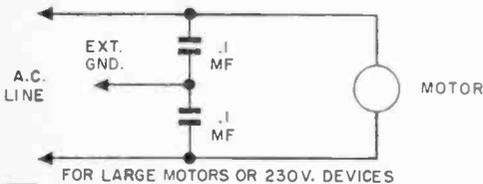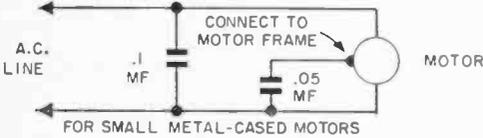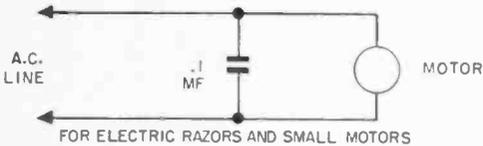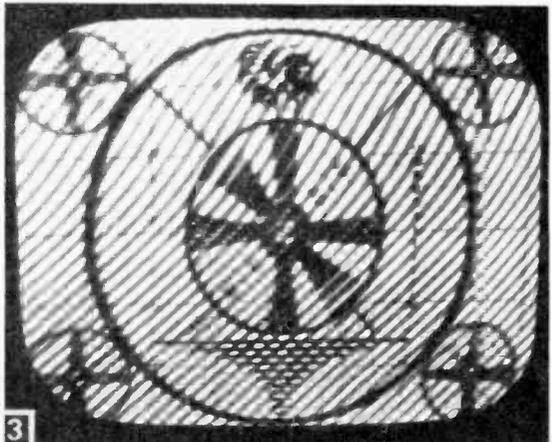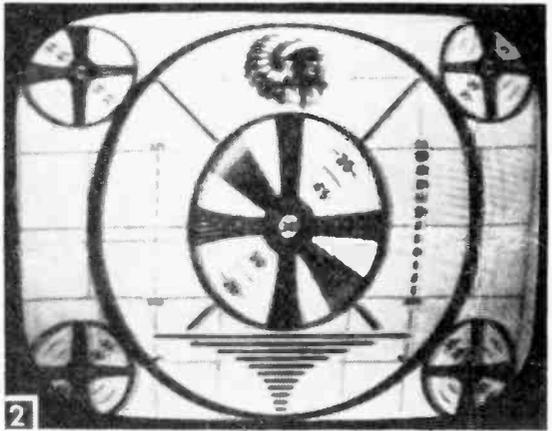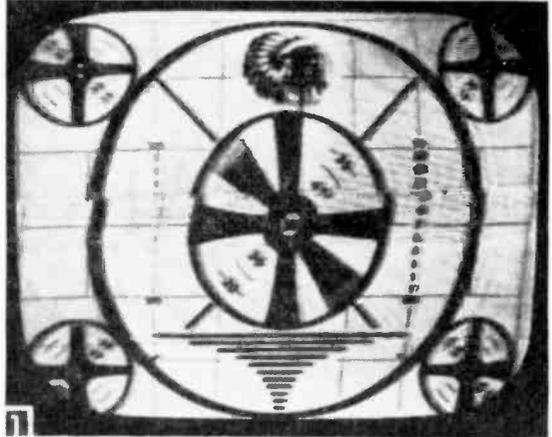


4 SIMPLE POWER LINE FILTERS

1 Ignition or "spark" interference is characterized by multiple bands of "hash" moving up and down the screen, displacement of picture and often a popping noise in the speaker.

2 A-C interference caused by small motor results in a single unchanging band of "hash."

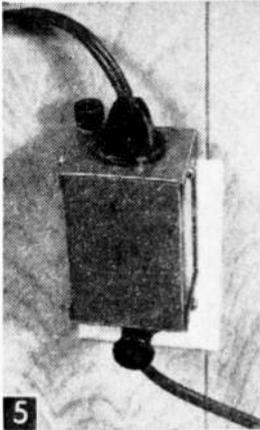3 Diagonal lines (sometimes a herringbone or chicken-wire pattern) indicate R.F. or oscillator interference.



5

A-C line filter plugged into outlet, with TV set plugged into top. Other half of outlet can be utilized.

ference is due to other radiating electronic equipment.

Many cases of broad-band, a-c motor interference can be traced by noting what appliances in your home are operating when the interference is present. Cure by connecting one of the line filters detailed in Fig. 4 to the troublesome motor or device itself to eliminate the interference before it gets into your TV set through the power lines or through the antenna's picking up the radiated interference from power lines.

If you can't install the filter at the trouble source, plug a line filter made as in Figs. 5 and 6 into the wall outlet, and plug the TV set into the filter. Connect the binding post on the top to a good ground such as a water pipe. Mount the male chassis-type plug in one side of the filter chassis as near the bottom as possible as in Fig. 6, and the female socket in the top, slightly off-center to allow for binding post. The coils should not touch the metal case; the wire is stiff enough to make

TABLE A—COMMON TYPES OF TVI SOURCES


Broad-band Interference

Type	Enters Set Thru	Remedy
Ignition & spark noise Fig. 1 (most common type)	Usually through A-C lines; sometimes thru antenna if interference is near and intense	Wide-band A-C line filter on set or filter on trouble causing device
Electric Motor noise Fig. 2	A-C line	Filter at motor or on set; Wide-band A-C line filter on set
Non-communication electronic equipment such as neon lights, diathermy units, infra-red heat drying equipment, etc. (characterized by wide bands of curved lines across picture)	A-C line	Same as electric motor

Narrow-band Interference

(Entering through antenna)

Type	Appearance	Remedy
Oscillator radiation from another TV set Fig. 3	Diagonal black lines or herringbone or chickenwire pattern across screen	Shield offending set (line cabinet with foil or screening) ground receiver (if designed for it), wave trap
Low frequency radio (B.C., police, Hams, etc.)	Diagonal black lines, lines across the screen, usually shifting and moving	Line filter or wide-band R.F. antenna filter
Medium frequency radio (S.W., Hams, aircraft, etc.)	Same as low frequency radio	Specific frequency high-pass filter, wide-band R.F. antenna filter, re-orient antenna
High frequency radio (F.M., aircraft, T.V., etc.)	Same as low frequency radio	Wave trap (stub), re-orient antenna


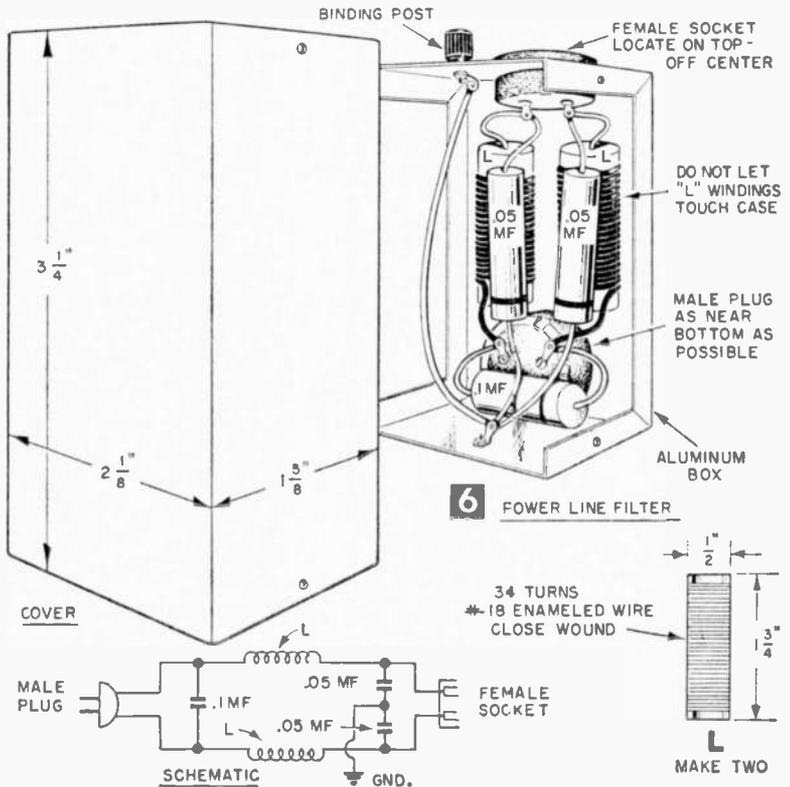


6 POWER LINE FILTER


them self-supporting.

Sometimes turning (re-orienting) the antenna slightly, or moving it to another location eliminates narrow-band radio frequency (R.F.) interference without affecting the signal. If moving within 20 ft. doesn't improve the signal, further moving probably won't help.

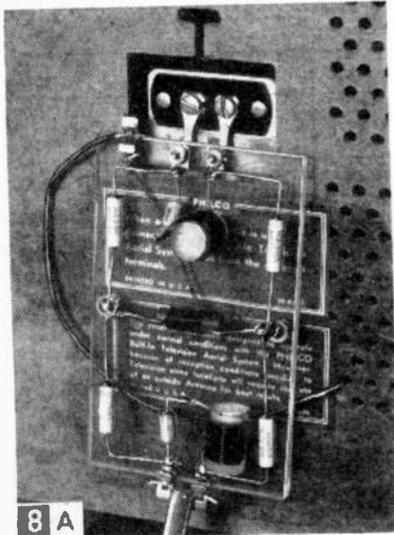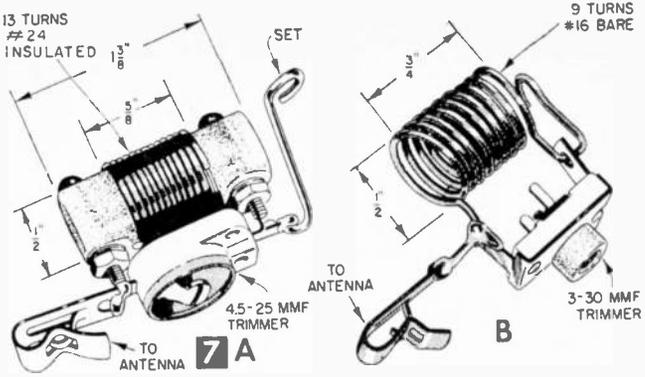Other types of R.F. interference such as FM transmissions, hams or aircraft are eliminated by simple high-pass filters in the antenna leads which allow high frequency TV signals to pass readily but tend to



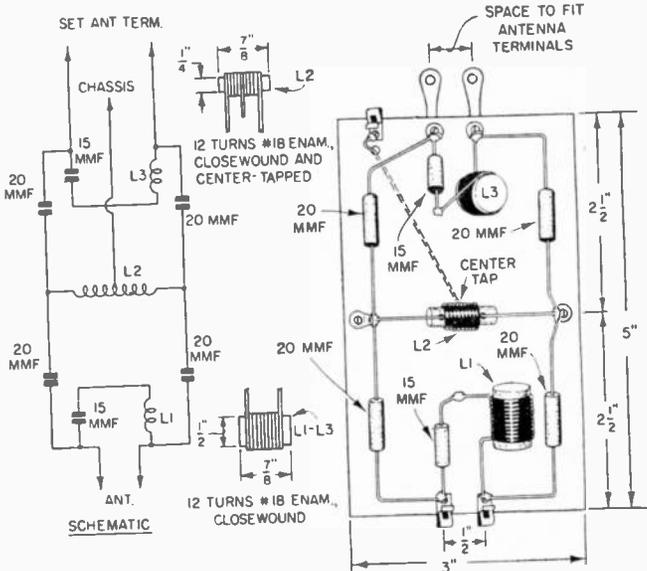Wide band R.F. filter attached to set. Wire from top clip goes to chassis.



WIDE-BAND R.F. FILTER


MATERIALS LIST—TVI FILTERS

Amt.	Description
	A-C Line Filter (Figs. 5 and 6):
2	1/2" dia. x 13/8" long coil rods
1	.1 mf. 400 volt condenser
2	.05 mf. 400 volt condenser
1	male chassis plug (Amphenol 61-M)
1	female chassis socket (Amphenol 61-F)
1	binding post (not insulated)
1	1 3/8 x 3/4 x 2 1/8" aluminum box (Bud CU-2101)
9' (approx.)	#18 enameled wire
	10-32 mc. Antenna Filter (Fig. 7A):
1	1/2" dia. x 1 3/8" long coil rod
1	4.5-25 mmf ceramic trimmer (Centralab 822-AZ)
1	Fahnestock clip
20" (approx.)	#24 insulated wire
	30-120 mc Antenna Filter (Fig. 7B):
1	3-30 mmf mica trimmer
1	Fahnestock clip
15" (approx.)	#16 bare wire
	Wide-band R.F. Antenna Filter (Figs. 8A and B):
2	1/2" dia. 7/8" long coil rods
1	1/4" dia. 7/8" long coil rod
4	20 mmf ceramic condensers
2	15 mmf ceramic condensers
3	Fahnestock clips
1 pc	3 x 5" plastic
5' (approx.)	#18 enameled wire

block out low frequency signals. If the interfering frequency is known, make a "tuned" filter (Figs. 7A or B) that will cover the signal frequency, connecting one to each antenna terminal at the set in such a way that the coils are at right angles to each other, and adjust the capacitors with an insulated screwdriver for best results. If tightening the capacitor on the filter does not eliminate interference, install the other filter shown in Figs. 7A and B.

If the interfering frequency is unknown, or if several frequencies may be involved, install the wide-band R.F. filter in Fig. 8A and B. While not as efficient for any single frequency as a "tuned" filter, it does weaken all frequencies below the TV frequencies. The filter must be made the size shown so the coils are separated to prevent interaction and are at right angles to each other. While it's best to enclose the unit in a metal case, with the side of the case at least 3/4 in. from any coil, and the case grounded, you can assemble the unit on a piece of plastic as in Fig. 8A.

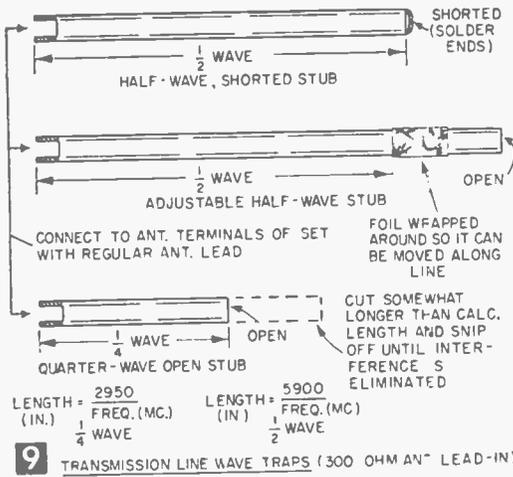If the frequency of the interfering signal is so



close to a TV channel frequency that an antenna filter might also filter out the desired signal, connect a simple filter or trap to the antenna terminals of the TV set (with the regular antenna lead). If you know the TVI frequency, make the filter of a section of 300-ohm antenna lead-in cut to exactly $\frac{1}{2}$ the wavelength of that signal as in Fig. 9; solder the free ends of the stub together. If you don't know the TVI frequency, cut the

lead-in somewhat longer than the calculated length (around 30 in.) and tightly wrap a 2-in. section of aluminum foil around the end (Fig. 9) as a short. Move the foil until best results are obtained, then fasten with cellophane tape. Somewhat less efficient is the simply made $\frac{1}{4}$ -wavelength trap. Cut the lead-in longer than needed, fasten in place and snip off sections until the interference disappears.

If the TVI source is so close that even with the antenna lead filtered, wiring within the TV set picks up the signal, shield the set by lining the cabinet with aluminum foil or copper screening and connecting this shield to the chassis. Also connect the chassis to a good ground, provided the set is designed to have a grounded chassis. Where chassis is not grounded, set should be so labeled according to U.L. standards. Speaking of shielding, check all shields, such as those on tubes, within your TV set, as omission of or loosely-connected shielding can cause interference on your set or your neighbor's.

Eliminating TVI is often a relatively simple matter, but there is no single remedy. Sometimes in apartments or industrial areas, complete elimination is virtually impossible though some improvement can usually be made by the right combination of antenna orientation, shielding, filtering and wave traps.

Try a Lemon or Tomato Battery

THE principles of dry cell battery operation involve the use of two dissimilar materials such as zinc and carbon, placed in an electrolyte, usually a moist mixture of charcoal or gypsum, zinc chloride and ammonium chloride (or sal ammoniac). The electrolyte acts more strongly on the zinc, slowly consuming it in the process. The zinc is the negative side of the cell and the carbon is usually used for the positive or other material.

Another action that takes place is that hydrogen is released with a load, from the action of the current on the electrolyte. The hydrogen bubbles released tend to collect around the carbon and act as an insulator, thus increasing the cell's internal resistance. This would normally cause a voltage drop were it not for another chemical element that is added, called a depolarizer, which may be powdered carbon and manganese dioxide.

To demonstrate a simple cell and its action, cut a lemon or tomato in half; the half will be the cell container and its juice the electrolyte. Then break up an old flashlight cell to recover the carbon rod and a piece of the outer zinc container (Fig. 2). (Use a cell that is not decomposed to the extent that the zinc is destroyed).


Wash the carbon rod and the zinc container from the battery in hot water. Then cut a $\frac{1}{2}$ in. wide strip from the zinc container, press the carbon rod in one side of a cut lemon, and the zinc strip in the opposite side.

By connecting the carbon and zinc terminals

to a high resistance voltmeter, we can then obtain about a 1.2 volt reading (Fig. 2) which is pretty good for a lemon! However, switching the meter switch to the 10 mil scale shows us that the current capacity is small, for a maximum of about .5 mils will be recorded. Now, put salt on the lemon; the current will rise.

If you put a light load on the cell, however, it will quickly polarize, since it has no depolarizer, and a second check on the voltmeter scale will show a decided drop in voltage. This will slowly rise again and come back practically to its original value.

How Does It Work?

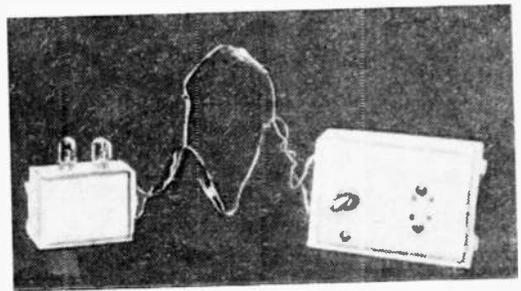

★ Two cases, a pair of wires, one switch, two lamps—Throw switch left and the left lamp turns on; throw switch right and the right lamp turns on, left lamp turns off.

How does it work? The secret is revealed on page 88 together with full details on how to build the unit.

Car Battery Adaptor Operates Portable Transistor Radio


By THOMAS A. BLANCHARD

YOU'LL never have to worry about your portable transistor radio batteries going dead when on a car outing or camping trip if you have this tiny car-battery adaptor tucked away in the glove compartment of your car.

Simply plug the adaptor cord into your car's cigaret lighter or map light socket, attach the cord clips to the radio battery terminals and tune in your favorite program. In this way you save the radio batteries for times when you really need them.


The adaptor will supply power to sets designed for either 6 or 9-volt operation having NPN or PNP transistors. It can be used with 6 or 12-volt car batteries grounded positive or negative to the car chassis.

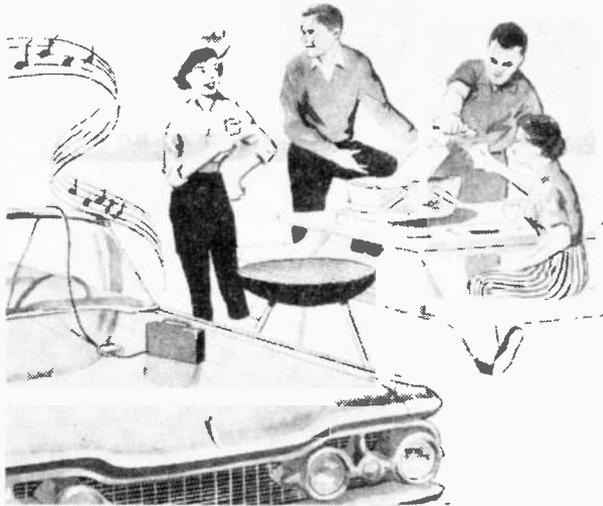The plastic box into which the adaptor was




assembled will be familiar to many of you radio experimenters since a leading line of radio hardware items are packed in these $\frac{3}{4} \times 1\frac{1}{8} \times 2\frac{1}{2}$ -in. slide-cover containers. Drill or ream three holes in the side of the box and install three phone tip or banana jacks as in Figs. 1 and 2. Mount a 2-lug tie-strip to the bottom of the box with a 6-32 $\times \frac{1}{4}$ -in. screw for securing the various components. These consist of a 25 ma. instrument fuse with pigtail leads, a 600 and 300 ohm 1-watt resistor and wire components.

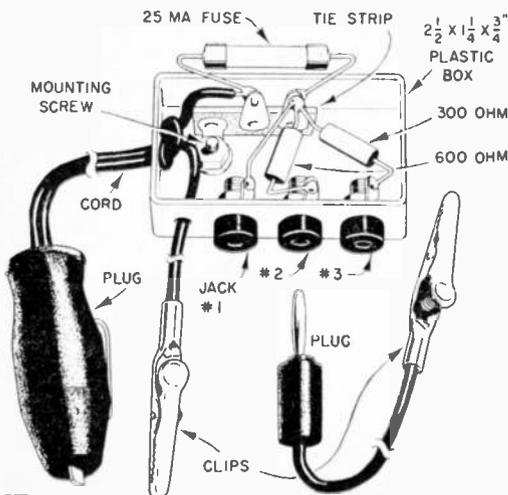To connect the adaptor to the car in the side of the a cord and plug



1 PICTORIAL DIAGRAM

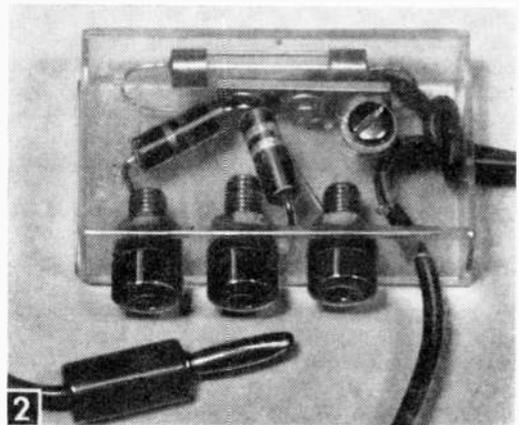

2 Complete adaptor, not including extension wire, fits into $\frac{3}{4} \times 1\frac{1}{8} \times 2\frac{1}{2}$ -in. box and may be stored in car glove compartment.

from an inexpensive trouble light designed to plug into the dash cigaret lighter socket or a suitable length of light fixture cord and fit it with a plug made from the base of a burned-out dash or dome lamp. If you use the latter, break the glass around the lamp base and scrape the base shell clean. Solder the cord leads into the base and fill the base with sealing wax. The wax can be melted by applying a heated soldering iron until wax flows into shell.

In the event that an instrument fuse is not

readily available, get one of the midget fuses your local service station stocks for auto clock circuits. With a little care, pigtail leads can be

soldered to the ends of any regular glass cartridge fuse with a low current rating.


The output leads of the adaptor are fitted with small clips. One clip lead is fitted with either a phone tip or banana type plug for connecting to the desired output jack. Jack #1 should be used for operating either a 6 or 9-volt transistor set from a 6-volt car battery. Jack #2 is used when operating a 6-volt set from a 12-volt car battery. Jack #3 is used for operating a 9-volt set on a 12-volt car battery.

Because of the several variable factors previously mentioned, polarity indications cannot be shown in the wiring plan. To determine which lead is positive, which is negative, attach the adaptor to the dash socket and connect the clip leads into the set. If set fails to work, simply reverse the clips and the radio will play.

However, do not expect to sit in the car and play the radio unless the vehicle has a fabric convertible top. As most experimenters well know, loop radios do not work in hardtop automobiles unless an external antenna is used.


MATERIALS LIST—CAR BATTERY ADAPTOR

No. Req.	Size and Description
1	plastic box 3/4 x 1 3/8 x 2 1/2-in. or larger
12 ft	light plastic extension cord
3	phone tip or banana jack
1	phone or banana jack
1	3-lug tie strip
2	small test clips
1	300 ohm, 1-watt composition resistor
1	600 ohm, 1-watt composition resistor
1	25 ma. pigtail instrument fuse
1	plug—see text

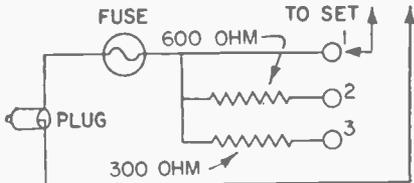

3 SCHEMATIC DIAGRAM

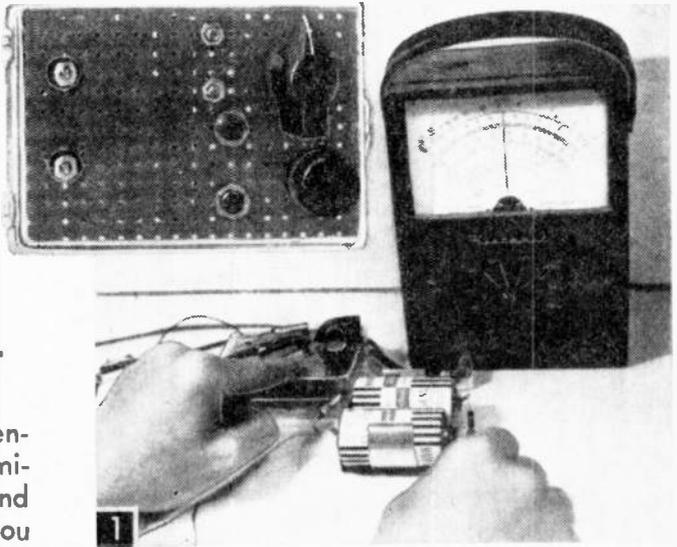Meter amplifier (front panel view shown inset) in use with Heathkit volt-ohm-meter.




1

Sensitive Direct Current Meter Amplifier

This amplifier increases the sensitivity of a milliammeter or microammeter many times! And it can be built from parts you probably have on hand—

By FORREST H. FRANTZ, SR.

TRANSISTORS are basically current amplifiers (in contrast to vacuum tubes which are voltage amplifiers). This characteristic of a transistor makes it a natural as a current amplifier for a meter. With a current amplifier, a low cost milliammeter can be made as sensitive as an expensive microammeter, and microammeters can be made more sensitive. Extremely small currents can be measured; and, if series resistors are employed with the transistor amplifier-meter combination, the result is a sensitive voltmeter which draws very little current from the circuit under measurement. Here is an amplifier unit which can be built from about \$5 worth of parts.

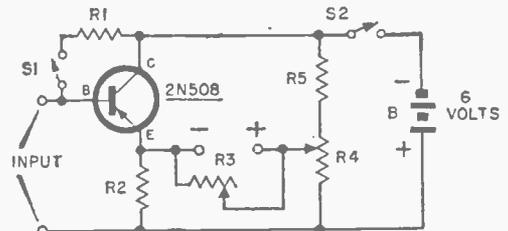

2 SCHEMATIC

Construction. The circuit is shown in Fig. 2. Miniature perforated board layout is shown in Fig. 3. The entire assembly is housed in a plastic case (See Fig. 4).

First, prepare the circuit board. The board on the Materials List is the exact size required, the hole centers coincide with perforations. Drill a $\frac{1}{8}$ -in. hole for each hole position (back the board with a wood block to prevent breakage). The larger holes may be made with a taper reamer or with drills of appropriate size.

Place the finished circuit board against the face of the plastic case for use as a guide in making the case pilot holes. Use a heated ice pick to make pilot center holes, enlarging these to size with a taper reamer. The battery holder holes on the case must be of about $\frac{3}{16}$ in. dia. since the mounting nuts are placed on the front of the circuit board.

Cut the shaft of R3 to a length of $\frac{3}{8}$ in., the shaft of R4 to a length of $\frac{1}{2}$ in. By placing the unwanted end of the shaft in a vise and cutting to desired length with a hacksaw, you do not place any stress on the shaft bushing which could damage the control.


Fasten the battery holder, potentiometers (R3 and R4), switches (S1 and S2), terminals and soldering lugs (plus and minus) on the circuit board. Retaining nuts for all parts (except the battery holder) fasten from the front of the plastic case in the final assembly.

Turn battery holder connection lugs to the side as required to contact adjacent lugs for connecting the cells in series and solder the appropriate lugs together. Then fill the battery contact eyelets on the holder with solder.

Next make connections between the mounted components and wire R1, R2, and R5 into the circuit. (The value of R1 depends on the meter to be used with the amplifier.) Connect the input leads and slip $1\frac{1}{4}$ in. lengths of spaghetti on the transistor leads and solder it into the circuit.

Now remove the nuts which retain R3, R4, S1, S2, and the terminals (plus and minus). Place the circuit board in the plastic case and refasten the component retaining nuts on the front side of the case. Fasten the knobs on R3 and R4, and place the penlite cells in the battery.

Operating Principles. The number of times a given base current change appears to be amplified in the collector circuit of a transistor is commonly called the Beta. Another way to say this is: Beta equals change in collector current divided by the change in base current that started the process. The Beta of the 2N508 transistor is better than 100. It would therefore seem that a current of 10 microamperes on the base of this transistor could cause full scale deflection of a 0-1 millimeter. Actually, however, the Beta of a transistor isn't constant. Generally, meter current amplifiers are operated without a base biasing resistor and the Beta is lower under these conditions than under the test conditions for which a numerical Beta is given. Another factor

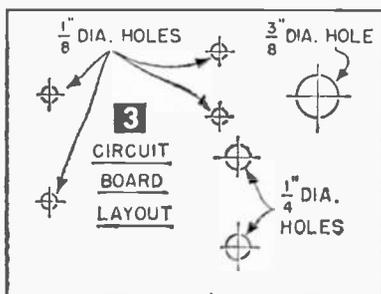

DC METER AMPLIFIER

Table A—Sensitivities and Calibration Points for Various Meter-Transistor Combinations

Value of R1 (Megohms)	Meter Range	Meter-Amp Sensitivity (Micro Amperes)	Beta of Transistor	Calibration Point
.58	1 ma.	20 full scale	50 or more	mid-scale
5.8	100 μ a	2 full scale	50 or more	mid-scale
.116	1 ma.	50 full scale	20 or more	full-scale
1.16	100 μ a	5 full scale	20 or more	full-scale
1.16	200 μ a	10 full scale	20 or more	mid-scale

which tends to reduce the amount of useful current amplification the transistor has in a meter amplifier application is the leakage current (I_{co}) which flows although the base is open.

The current in the emitter circuit of a transistor is nearly equal to the collector current. The meter connects into a bridge circuit consisting of the transistor and resistors R2, R4, and R5. R4 functions as a "zero" control. With S2 depressed, R4 is adjusted for zero deflection of the meter. If a current flows through the input leads, the meter deflection is proportional to this current.

The potentiometer R3 which shunts the meter is a scale adjustment; its setting determines the amount the meter will be deflected for a given base input current. It is set in the following manner: First, depress S2 and adjust R4 to zero the meter. Then S1 is depressed (with S2 still depressed) and R3 is adjusted for a predetermined scale meter deflection. This calibrates the meter.

The value of R1 is chosen to provide a calibration current which is equal to the meter current calibration point divided by 50. Thus, for a 1-ma meter, if the predetermined calibration points is to be full-scale reading, the calibration current is 1 ma divided by 50, or 20 microamperes. The voltage difference from base to emitter is approximately 0.2 v. The battery voltage is 6 v. R1 will have a voltage drop of 6 minus 0.2, or 5.8 volts and the current through it is to be 20 microamperes. Its resistance ($R = V/I$) is (5.8/20) Megohms. The computed value is .29 Megohms or 290K. A 270K resistor that is high in value or a 330K resistor that is low in value can be selected from ordinary 10% or 20% tolerance carbon resistors.

An alternate approach is to let the predetermined meter calibration point be mid-scale. The current through R1 should then be 20/2 or 10 microamperes, and $R1 = (5.8/10)$ Megohms = .58 Megohms; 560K is near enough to this value to use. The battery voltage can be expected to be a few tenths of a volt below 6 anyway, so that 560K

should be more correct than the computed value of 580K. Table A shows the value of R1 for various basic meter ranges, the predetermined

meter calibration point and the base current that will cause full-scale meter deflection.

After the meter amplifier has been zeroed (R4) and the scale adjustment (R3) has been made, the amplifier input leads are connected into the circuit in which a measurement is to be made and S2 is depressed. The meter reading divided by 50 is the amplifier input current. The conversion may be performed mentally by multiplying the meter reading by two, taking the proper unit conversion into account.

MATERIALS LIST—DC METER AMPLIFIER


Desig.	Description
R5	470 ohm, 1/2 watt, 10% carbon resistor
R2	2.2K, 1/2 watt, 10% carbon resistor
R1	see text and Table A
R4	100 ohm wirewound potentiometer (Clarostat Series 43-100)
R5	10K dime-size potentiometer (Lafayette VC-34)
T	2N508 transistor (GE)—text gives information for using other transistors
S1, S2	miniature push button switches (Lafayette MS-449)
B	4—1.5 v penlite cells series connected (RCA VS074)
	2-cell Battery Holder (Lafayette MS-170)
	2 7/16 x 3 3/8" miniature perforated bakelite board (Lafayette MS-304)
	1 x 2 3/8 x 3 3/8" plastic case (Lafayette MS-159)
	miniature knob (Lafayette MS-185)
	pointer knob (Lafayette KN-41)

Alternatives. Suppose you want to use a transistor other than the 2N508 which you may have on hand, say a CK722 or a 2N107. They'll work, but their current gains are low and they have appreciable leakage. To use other transistors, use a single 1K pot in place of R4 and R5. The zero adjustment will be more critical since no padding resistor is provided, but you'll be able to zero the meter.

Resistor R1 is computed as described earlier, but the assumptions are different. Assume the input base current to be the meter reading divided by 20. Thus for a 0-1 ma meter, figure 1/20 ma or 50 microamperes of input current for full-scale deflection. Then R1 is (5.8/50) Megohms or 116K for full-scale deflection (110K is the nearest common value).

If transistors of better quality than the experimenter types are used, current amplification scale factors greater than 20 may be assumed. Even experimenter grade transistors which you might have may have Betas of 50 or more. The reduced values were assumed because Betas vary widely between transistors of a given type. Thus, although some readers may get transistors with low Betas, very few will get transistors with Betas below those assumed for the types covered in this discussion.

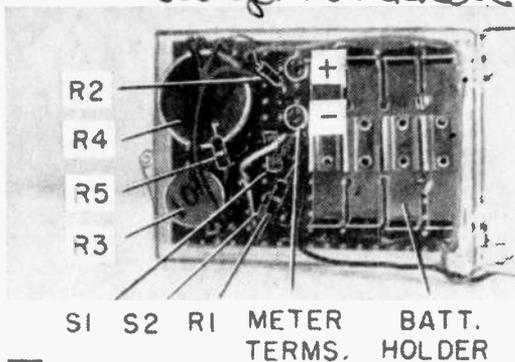The physical construction of the meter amplifier may be varied if you prefer different construction. The amplifier and a basic meter move-



Back view of meter amplifier unit.


ment may be incorporated in a single case, for example. Shunt multipliers may be provided at the amplifier input if several various low current ranges are desired.

Voltmeter. A resistor connected in series with the input lead and the base of the transistor converts the amplifier-meter combination into a high-sensitivity voltmeter. Assume the current sensitivity of the combination is 20 microamperes for full-scale meter deflection (the case for the model described in this article when employed with a .01 ma meter), and the meter is to read full-scale when the measured voltage is 50 v. Then the required series resistor is (50/20) Megohms or 2.5 Megohms. The nearest standard values are 2.2 and 2.7 Megohms. However, standard values of 1 and 1.5 Megohms are available. Connect these in series.

Since this voltmeter arrangement only draws 20 microamperes from the circuit under test, it may be used to make measurements in most vacuum tube equipment without upsetting circuits and introducing loading error in measured values.

Nail Clipper Strips Wire

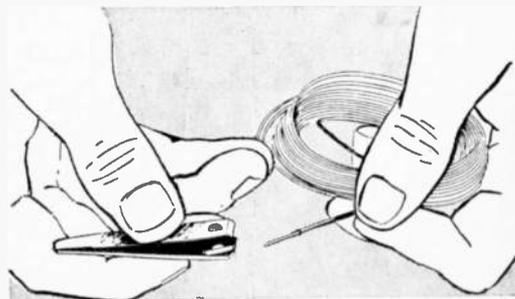- A nail clipper makes an excellent tool for radio and TV hobbyists, to use for removing insulation from small-gage wiring. First, however, remove



the pressure-handle to avoid exerting too much force and cutting right through the wire.—R. J. DeCRISTOFORO.

Transistorized Photo-Cell Control

A beam of light can be a handy workman
around the home

By THOMAS A. BLANCHARD

WHEN this photoelectric-cell switch is placed so its activating light beam shines across a doorway, hall or porch, a person passing through will break the light beam and cause a door chime to sound, a light to turn on or a burglar alarm to ring.


The switch may be wired across any existing 115-volt switch to control lights, a bell, etc., not exceeding 2 amps., or about 130 watts. It is battery operated and therefore portable and completely independent of the house current which it controls. The entire unit is housed in a $2\frac{1}{8} \times 2\frac{1}{4} \times 2\frac{3}{4}$ -in. radio utility box. All components are mounted on $2\frac{1}{2} \times 2\frac{1}{2}$ -in. perforated plastic panel.

Place the components on the panel and mark and drill holes for mounting the parts as in Fig. 2. Make the battery brackets as in Fig. 3C and bolt them to the panel with 3-48 x $\frac{1}{4}$ -in. screws. Also drill three $\frac{5}{32}$ -in. holes for the 6-32 x 1 in. mounting screws. Make the fiber tube spacers for the mounting screws for the same length that the photocell projects through the perforated panel. Transfer the location of these holes and holes for potentiometer and photocell to the front of the box and drill.


The cadmium sulphide photocell is a Clairex CL-2 which is about the size of a small composition resistor. This tiny unit has the general characteristics of a vacuum tube photocell. It is a photo-conductive device like the phototube. It has the unique property of having a very high resistance in darkness, but as it is exposed to light the resistance drops from the megohm range to 10,000 ohms in bright light.

To actuate the control, only a small light change is required so that sufficient current passes

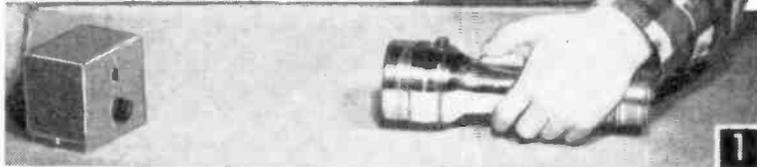
Front and rear views of panel showing placement of parts.



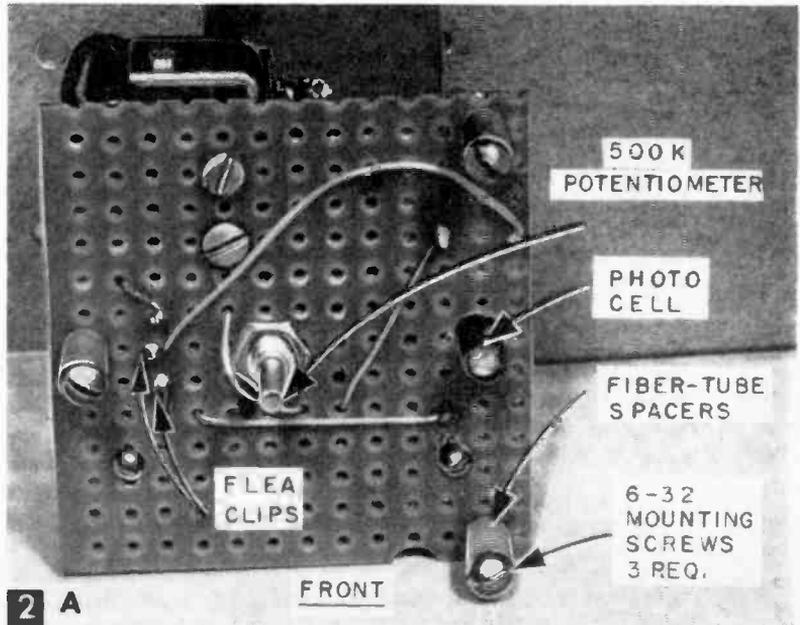
Tiny self-contained photoelectric control being test-actuated at close range with flashlight. Unit is sensitive enough to respond to feeble daylight at surprisingly long distances.



FRONT

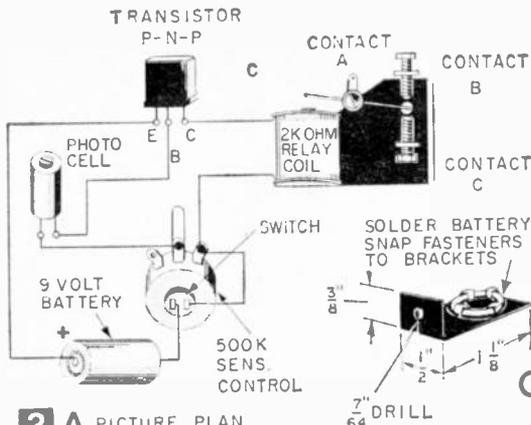

3 A PICTURE PLAN

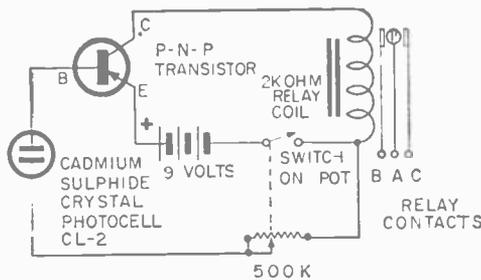

C BATTERY BRACKETS
2 REQ. 1/16 BRASS

B SCHEMATIC PLAN

MATERIALS LIST—PHOTOCELL SWITCH

No. Req.	Size and Description
1	2 1/8 x 2 1/2 x 2 3/4" aluminum radio utility box
1	Sigma sensitive relay type 4F with 200 ohm coil
1	Clairex photocell type CL-2
1	2 1/2 x 2 1/2" perforated phenolic (Bakelite) (Lafayette)
1	500K miniature potentiometer with switch
1	P-N-P transistor (type 2N107, 2N34, CK722, etc.)
5	Lafayette "flea clips"
1	1/16 x 1/2 x 3" brass for battery clips
1	9v transistor battery
3	3/16 I.D. x 3" long fiber tube for mounting screw spacers
3	6-32 x 1" rh machine screws for mounting panel
2	3-48 x 1/4" rh machine screws for battery clips
	Hookup wire and misc. hardware

through it to provide a base return negative voltage to the transistor, thus causing a large flow of current through transistor to the relay coil. The cadmium cell should not be confused with the short-lived selenium cell which is a

photovoltaic device.


Connect the leads from the photocell and transistor to flea clips and insert them through the holes in the perforated panel. Solder hookup wire to the flea clips on the other side of the panel as in Figs. 2 and 3.

The use of a sensitive plate relay is most important. Fixed relays are set up at the factory with predetermined pick-up and drop-out relay contact specifications. Altering these adjustments is difficult and sometimes impossible. The relay employed is the fully adjustable Sigma 4F with a variable hairspring armature adjustment and screw gapped contacts. The coil resistance of the unit is 2000 ohms.

In this application we adjusted armature tension and contacts so that relay picked up at 700 microamps and dropped out at 500 uA. The relay coil with photo cell in darkness draws just 200 uA and only 1.6 mil-liamps in brightest light.

While the life of conventional transistor batteries is limited, those desiring a battery good for 10,000 hours of service may employ the rechargeable nickel-cadmium cells now on the market. Many of these batteries are designed expressly for transistor service and will fit nicely into limited space.

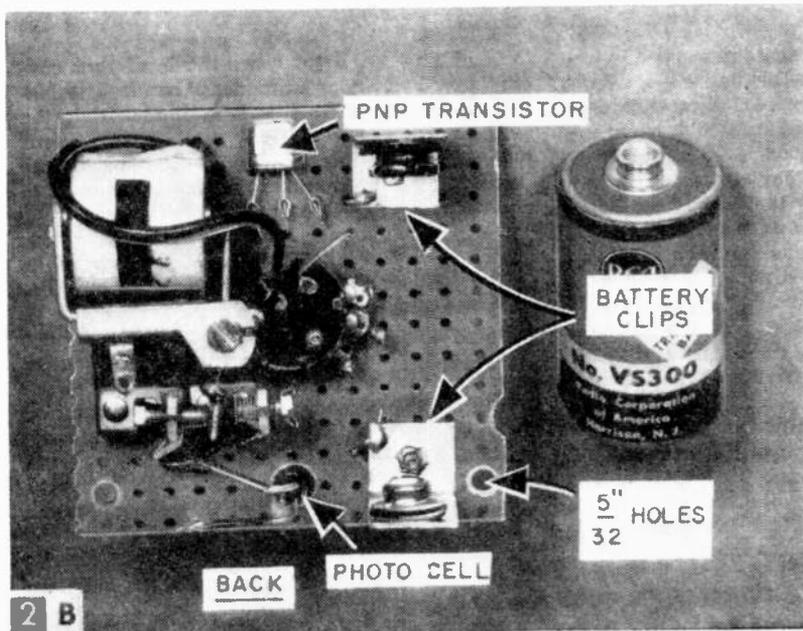Sensitivity of the photo control can be regulated by adjusting the miniature 500,000 ohm linear potentiometer which is wired in series with the photo control so that the desired pick-up and drop-out of relay switch contacts may be adjusted to meet existing light conditions.



2 B

What To Listen For On Short Wave, Spring and Summer, 1960

By C. M. STANBURY II



L R A
RADIO NACIONAL

Agradecido Su atenta carta del 24
11-58- que contenía un informe
correcto de nuestra transmisión
de esa fecha.-

FRECUENCIA 9690 KC/S
POTENCIA 100 KW


PALACIO DE CORREOS REPUBLICA ARGENTINA BUENOS AIRES

QSL (verification card) from Radiodifusión Argentina al Exterior. Note that on globe map Argentina includes the Falkland Islands (held by the British) and a large portion of Antarctica. RAE covers South American news from a different point of view. For details on this and other easily received SW broadcasts see Table B.

AN international broadcast is worth the expense only if you—the listener—can receive it and—for one reason or another—also enjoy the program. (Admittedly, your interests as a short-wave listener and the interests of a SW broadcaster may not always coincide.) Let's look into the factors that affect reception and then analyze the programs themselves to discover which make for enjoyable listening.

Shortwave signals are weak compared to local broadcasting but this is unimportant, as there is little static on the shortwaves. The serious problems for the broadcaster are finding a clear wave-length, since scores of countries are broadcasting, and choosing a wave length that will be reflected by the ionosphere, a region of ionized air 60 and more miles above the earth upon which all short-wave broadcasting depends. The broadcaster must choose a wave-length which is short enough to escape absorption characteristic of lower frequencies and yet not too short for reflection via the ionosphere. If he's going to stick within the internationally authorized shortwave bands (see Table A), this summer he will be limited to a

TABLE A—
BEST SHORTWAVE BANDS,
SPRING AND SUMMER, 1960

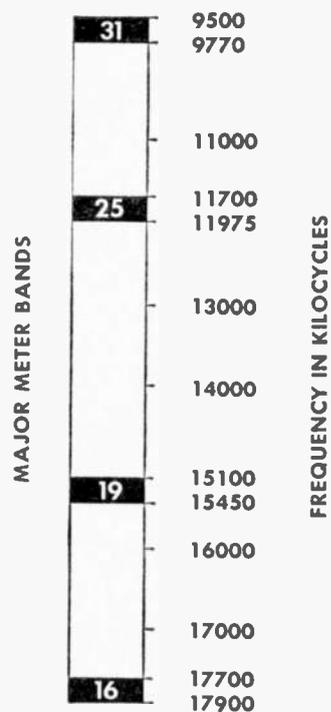

*To convert to megacycles,
divide by 1000

total of 1100 kc, a total two-thirds of that covered by the standard broadcast band. The National Bureau of Standards estimates that the average shortwave listener will tolerate four times as much interference as he will on the broadcast band. This compromise is a matter of necessity.

During the summer, every summer, absorption of radio waves by the ionosphere increases, while in the top layer of the ionosphere ionization decreases. This means that the longer 49 and 40 meter waves will not escape absorption (only the Communists use the latter for North America anyway) and therefore will be unsuitable for consistent transoceanic broadcasting, and due to decreased ionization in the top layer of the ionosphere, 13 meters at the top end of the dial will be reflected only sporadically. Which leaves 16, 19, 25 and 31 meters—and of these the 16-meter band is on the doubtful side. During the past few summers 16 meters has been "Open" (reflected) but with a dropping sunspot count (sunspots increase reflection); international broadcasters will be able to count on this one less and less.

Taking it by regions, daytime European signals will be received best on 19 meters with some on 16 meters, especially in the afternoon. Then evenings these signals will be heard on 25 and 31 meters with 19 also open several hours past sunset. Similar conditions hold for Africa except you probably won't hear any on 19 while dark. Asiatics will first appear around sunset or shortly before on 16 and 19 meters and because it is a peak listening period, such stations having North American broadcasts will transmit them during this period. However during the early *am* hours of darkness many Asiatic signals should be audible from 19 thru 31 meters. Pacific islands will also be heard during the *am* hours on 19, 25 and 31 meters.

Latin American stations, with the exception of

Argentina and Chile, can be received much more easily; they will be received in the summertime all the way down to 6 megacycles (49 meters) and—when static permits—even lower.

The Human Element. As international broadcasting is directed by human beings, for human motives, it is of course far from perfect. And as in any other of man's endeavors, these services range from good, such as the quality program put out by the Swiss Broadcasting Corporation, to the absolute lowest as epitomized by Radio Peking. However there is always one constructive way to judge any shortwave station. Does it provide something worthwhile not readily obtainable elsewhere?

In this connection there are two common practices which, in varying degrees, lessen short-

TABLE B—STATIONS TO START WITH

COUNTRY	FREQUENCY OR WAVE-LENGTH	TIME* (EASTERN STANDARD)	BROADCASTER AND DETAILS
SWITZERLAND	11865 and 9535 Kc/s	2030-2215 and 2315-2400	Swiss Broadcasting Corporation. Swiss news (neutrality and more neutrality), commentary from Swiss newspapers (not so neutral). Good source of factual information about this, one of the world's first republics. You might say it was pro-Swiss but then the Voice of America is pro-U. S. and you really wouldn't want anything else. An interesting little touch with S.B.C.: on each broadcast they give the weather for Switzerland. Finally of note are special international features such as rates of exchange for world's currencies.
NETHERLANDS	15220 Kc/s (16 meters) 11730 and 9590 (9715)†	1615-1705 2130-2210	Radio Nederland. International news from a democratic West European viewpoint. Usually concludes program with a topical talk. These probably reflect quite accurately the general Dutch viewpoint.
SPAIN	9363 Kc/s	2215-2250, 2315-2350 and 0015-0050	The Voice of Spain. This one operates off regular broadcast frequencies to avoid interference. Features a reasonable quantity of Spanish folk and popular music. Too bad the entire program doesn't consist of same.
ISRAEL	9009 (11845) Kc/s	1530-1600	The Voice of Zion. Another off-hand operation and that time is a little early for 31M but with a clear channel it should get through. Interesting source of Israeli news from a Zionist point of view. Also Israeli folk and popular music, but not enough.
CONGO REPUBLIC	11725 Kc/s	2015-2100	Radio Brazzaville (French government radio). African news from, primarily, a French point of view. Certainly better than none at all.
JAPAN	17855 and 15325 Kc/s	1930-2030	Radio Japan. News from Asia's leading democracy. Some Japanese folk and popular music; as usual, not enough.
ARGENTINA	9690 (15345) Kc/s	2200-2300 and 2400-0100	Radiodifusion Argentina al Exterior. South American news from a different if not unbiased point of view. Rest of program consists of Argentine popular music, more polished than most Latin American music and probably less interesting. Compare with the Voice of Spain.
GREAT BRITAIN	16 thru 31 meters	1600-2200	General Overseas Service, British Broadcasting Corporation. This is general programming intended for the entire English speaking world and not any one specific area. Time given is best for North America, but G.O.S. can usually be heard throughout the day on many frequencies. The G.O.S. is an excellent example of British programming and conservative English thought. Covers international affairs, theatre, literature and music. Also international sports but the latter would be of little interest to the average American.
AUSTRALIA	11810 Kc/s	0714-0845 and 1014-1145	Radio Australia. Australian news—the continent has an area of almost 3,000,000 square miles, remember. Remainder of program is mostly entertainment. These broadcasts have twice been voted most popular by the world's short-wave listeners.
CANADA	15195 (11900 or another 25 meter frequency)	2000-2045	Radio Canada. Good source of international and Canadian news. Because of the nation's proximity, the latter is of special interest to U. S. citizens.

* Time is given on the 24-hour clock. 1200 is 12 noon, 1300 is 1 pm, 2400 is midnight, and so on. In other words, for times past noon subtract 1200 to get Eastern Standard Time.

† Frequencies listed in brackets are alternate possibilities. If you fail to hear a program on the channels listed first, try these.

wave's usefulness. First, many stations play classical music. Of course if the transmission is intended for an area where shortwave is the only kind of broadcasting, such a feature is certainly justified. But when beamed to North America, it is a waste of time and frequency. As explained, shortwave is anything *but* a hi-fi media and the classical music fan would do far better on FM, or in some areas, even on the standard broadcast band.

Second, most SW broadcasters when attempt-

ing to give a view of their country, tend to over-emphasize institutions and material things, passing by the real human values. While this is a fault common to most governmental undertakings, it is quite understandable here as these values are quite intangible and obviously difficult to put into words.

I have listed in Table B ten broadcasts which I think you'll find interesting. The chart tells which have been picked for all-round excellence and which for only one or two special features.

Easy Transistor Class Identification

• It's almost impossible to determine whether a transistor is of the NPN or PNP variety just by looking at it in a circuit. However, an easy clue to identification lies in the fact that the middle letter of the transistor class designation indicates which terminal of the battery is connected to the collector element. Thus, in the case of the PNP type, the *negative* terminal of the battery is connected to the collector; similarly, the *positive* terminal of a battery is connected to the collector element of a transistor of the NPN variety. Either by checking the polarity of the potential on the collector element, or by tracing out wires to the battery, it is a relatively simple matter to determine correctly the class of a given transistor.—JOHN A. COMSTOCK.

Wire Scraper from Old Blade

• An old piece of hacksaw blade can be used for cleaning wires when soldering. It will not cut the strands as will a knife.—FRANK A. JAVOR.



Transistors Wired in Tandem

• When building direct-coupled amplifiers using transistors, wiring can be simplified and space saved by connecting matched pairs of transistors together. Cement or tape the two transistors together back-to-back, and solder the emitter lead of one unit to the base lead of the other.



Art Huhta

"This circuit has a response of 20-20,000 cps—practically no harmonic distortion up to 25 watts . . ."

memorize morse in 20 minutes!

By Dr. BRUNO FURST

THE International Morse Code is a language of sound used for radio-telegraphy communication. In it, short and long pulses of sound (*dits* and *dahs*) are combined to indicate the 26 letters of the alphabet, the 10 numerals, punctuation marks, and other information. Table A gives the phonic sounds of International Morse as well as the written designations of the pulses, a dot for a short pulse (*dit*), a dash for a long pulse (*dah*). Except when it is the final syllable of a character, a dit is contracted to *di*, the *t* becoming lost in the *d* of the following syllable.

A brief depression of the telegraph key sends a dot signal; a depression three times as long, a dash. Between signals forming the same letter, there is a pause equal to one dot; the pause between two letters within a word is equal to three dots (a dash); the pause between two words is equal to seven dots.

If the letter *a* were represented by one dot, *b* by two dots and so, no help in memorizing the code would be necessary. However, the distribution of dots and dashes is completely irregular (except that the most commonly used characters have the simplest signal combinations) and help is necessary. There is no uniformity in sequence. There is no pattern. Taken all in all, the code presents a confusing picture, difficult to memorize. Here then is a method which has been tested over and over again that enables everybody (even those without previous experience) to learn the International Morse Code in 15 to 20 minutes.

Since the code consists of dots and dashes, the dots are replaced by vowels (a-e-i-o-u-y), the dashes by consonants. For each letter of the alphabet, a specific word which begins with the letter that it stands for is substituted. For example, the cue word *Air* is substituted for the letter *a*. The cue words (or cue word combinations) at right above represent the entire alphabet:

A ir	J ust now	S uzie
B ruise	K odak	T ot
C hina	L ydia	U sual
D ray	M onk	V isua:
E sso	N ote	W ith
F iery	O n top	X -rays
G lobe	P arty	Y okels
H is essay	Q -Club	Z ombie
I ssue	R eno	

In order to make easier the task of remembering which word belongs to which letter, memorize this five-sentence story (in it, the cues are used in consecutive order):

"A shell burst in the *Air*, causing a *Bruise* to a soldier in *China*, who was riding in a *Dray*.
"The soldier, Private *Esso*, wrote about the *Fiery Globe*. *His Essay* is an *Issue Just Now*.

"With his *Kodak* he took pictures of *Lydia* and a *Monk* writing a *Note On Top* of a hill.

"Then he went to a *Party* at the *Q-Club* in *Reno*, taking *Suzie* and her *Tot* along as *Usual*.

"At the club, *Visual With X-rays* were *Yokels* drinking a *Zombie*."

Because of its very oddity, this story—read once or twice—is easy to remember. So also, because of it, are the cue words, since they appear in it in alphabetical order; each cue word acts as an association for the succeeding cue word. Thus each brings the next to mind. (But if you learn the signals mechanically, by rote, and forget one, there is no way in which to recall it.)

Having learned the cue words, apply the following rules: The first letter of each word is used only to indicate the letter of the alphabet being coded. (If the first letter of each word were included in the decoding, many exceptions would be necessary because the Morse Code signs for several consonants start with a dot—F, H, R, etc.—whereas the vowel O starts with a dash.) For the succeeding letters, substitute a dot for each vowel, a dash for each consonant (for example A ir · — or C hina — · — ·).

Because there are no words in the English language consisting *only* of four vowels (as

for an amateur license you must demonstrate ability to send and receive the morse code. here's how you can learn the code - quickly

TABLE A—INTERNATIONAL MORSE CODE

LETTER	SIGNALS	PHONIC SOUND
A	· —	di DAH
B	· · · ·	DAH di di dit
C	— · — ·	DAH di DAH dit
D	— · ·	DAH di dit
E	·	dit
F	· · — ·	di di DAH dit
G	— · ·	DAH DAH dit
H	· · · ·	di di di dit
I	· ·	di dit
J	· — — —	di DAH DAH DAH
K	— · — ·	DAH di DAH
L	· — · ·	di DAH di dit
M	— —	DAH DAH
N	— ·	DAH dit
O	— — — —	DAH DAH DAH
P	· — — ·	di DAH DAH dit
Q	— — · —	DAH DAH di DAH
R	· · ·	di DAH dit
S	· · ·	di di dit
T	—	DAH
U	· · —	di di DAH
V	· · · —	di di di DAH
W	· — —	di DAH DAH
X	· · · —	DAH di di DAH
Y	— · — —	DAH di DAH DAH
Z	— — · ·	DAH DAH di dit

NUMBER	SIGNALS	PHONIC SOUND
1	· — — — —	di DAH DAH DAH DAH
2	· · — — —	di di DAH DAH DAH
3	· · · — —	di di di DAH DAH
4	· · · · —	di di di di DAH
5	· · · · ·	di di di di dit
6	— · · · ·	DAH di di di dit
7	— · — · ·	DAH DAH di di dit
8	— · — · ·	DAH DAH DAH di dit
9	— · — · ·	DAH DAH DAH DAH dit
0	— — — — —	DAH DAH DAH DAH DAH

PUNCTUATION MARKS & SIGNS	SIGNALS	PHONIC SOUND
PERIOD	· · · · —	di DAH di DAH di DAH
COMMA	— · · · · —	DAH DAH di di DAH DAH
QUESTION MARK	· · · · ·	di di DAH DAH di dit
ERROR	· · · · ·	di di di di di di di dit
DOUBLE DASH	— · · · ·	DAH di di di DAH
WAIT	· · · · ·	di DAH di di dit
END OF MESSAGE	· · · · ·	di DAH di DAH dit
INVITATION TO TRANSMIT	· · —	DAH di DAH
END OF WORK	· · · · —	di di di DAH di DAH
FRACTION BAR	· · · · ·	DAH di di DAH dit
EXCLAMATION	— · · · · —	DAH DAH di di DAH DAH
COLON	— — · · · ·	DAH DAH DAH di di dit

needed for H) or of three consonants (as needed for O), one exception is necessary: For the letters *s* and *o* a dot or dash is substituted only when they appear at the end of a cue word or cue word combination. In all other positions they are disregarded.

the author

Dr. Bruno Furst teaches the art of improving the efficiency of memory. He is director of the School of Memory and Concentration in New York City (the school was 20 years old last fall), professor of law at McGeorge College and instructor at Brooklyn College, Adult Education. His system of memory training has been introduced by many business firms, at the U.S. Army Intelligence School in Washington, and at many Army and Air Force installations.

Aside from his resident classes in New York and other cities in the United States, South America, Africa and Australia, he conducts a correspondence course as well as a self-study course. Readers interested in further developing their memory and powers of concentration can write to Dr. Furst in care of the School of Memory and Concentration at 365 West End Avenue, NYC 24.

Remember this exception by thinking of S.O.S. For example, H is essay · · · · and R eno — · · .

The *s* in His is ignored because it is not at the end of the cue word combination. The *o* in Reno has a dot substituted for it because it is at the end of the cue word.

The entire alphabet is thus transposed as follows:

ir	ote
A · —	N — ·
ruise	n top
B · · · ·	O — — —
hina	arty
C — · — ·	P · — — ·
ray	Club
D — · ·	Q — · · · —
sso	eno
E ·	R — ·
lery	usle
F · · · ·	S · · ·
lobe	ot
G — · —	T —
is essay	sual
H · · · ·	U · · —
ssue	lsual
I · ·	V · · · —
ust now	ith
J · — — —	W — —
odak	rays
K — · —	X — · · —
ydia	okels
L · · · ·	Y — · — —
onk	ombie
M — —	Z — · · ·

For learning numbers in the International Morse Code, no memory help is needed. The signs follow a uniform, progressive pattern (see Table A). The numbers from 1 to 5 start with from 1 to 5 dots; the numbers from 6 to 0 start with from 1 to 5 dashes. All are supplemented by the opposite symbol to a total of five.

Besides the International (Continental) Morse Code, there is an American Code which deviates in several instances from the International Code (see Table B). Considerable auditory skill is needed to read this code because of the irregular spacing used within certain letters (irregular in comparison to International Morse spacing). It is therefore rarely used in radio applications. To apply my method to the American Code, simply change some of the cue words and construct a story of your own. With understanding of the method that I suggest, these changes are easily done, and a story that *you* construct is even easier for you to remember than a story that I or someone else constructs for you.

Of course, knowing the signals will not make you immediately proficient in sending and receiving the Code. Proficiency requires practice. Your ear must grow accustomed to the *sound* of the Code. But the highest hurdle—the memorization of the Morse Code signals—need not take you more than 20 minutes.

Almost everything that we have to learn and to remember in school, in college and in later life can be made easier and retained longer by using more efficient methods. Whenever you face something new that must be


TABLE B—AMERICAN MORSE CODE

LETTER	SIGNALS	LETTER	SIGNALS	NUMBER	SIGNALS
A	· —	N	— ·	1	· — — ·
B	— · · ·	O	· ·	2	· · — · ·
C	· · · ·	P	· · · · ·	3	· · · — ·
D	— · ·	Q	· · — ·	4	· · · · —
E	·	R	· · ·	5	— — — —
F	· — ·	S	· · ·	6	· · · · · ·
G	— — ·	T	—	7	— — · · ·
H	· · · ·	U	· · —	8	— · · · · ·
I	· ·	V	· · · —	9	— · · · —
J	— · · · ·	W	· — —	0	—
K	— · —	X	· · · · ·		
L	—	Y	· · · ·		
M	— —	Z	· · · ·		

learned, do not plunge immediately into parrot-like memorization. Give some thought to the question: Can I find a short-cut which simplifies the task and makes learning and remembering more interesting and more exciting? Invariably the answer is yes.

Lifesaver for Components

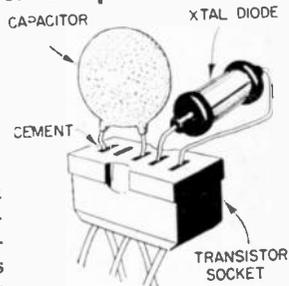• Building a compact transistor circuit? You can save heat-sensitive component parts from being ruined by using transistor sockets not only for transistors, but also for ceramic capacitors, crystal diodes and other parts easily damaged by too much heat from a soldering iron. Just insert the leads into the socket, then add a touch of service cement to the lead where it enters the socket.



Hi-Fi Speaker Improvement

• Where two separate speakers are used in a hi-fi system to reproduce the high and the low frequencies, apply one or two coats of lacquer to the cone of the larger speaker. This will stiffen the cone and improve its response to the lower frequencies.—JOHN A. COMSTOCK.


File Used as Reamer

• When a rat-tail file breaks, don't throw it away—break it up into a number of 2-in. lengths and use them in your power drill to enlarge radio chassis holes. They cut very rapidly and are ideal for enlarging tube socket holes and for similar radio work.—J. A. C.



"I don't remember whether I made that change or not, but I do remember making a mental note to do it."

MEL MILLAR

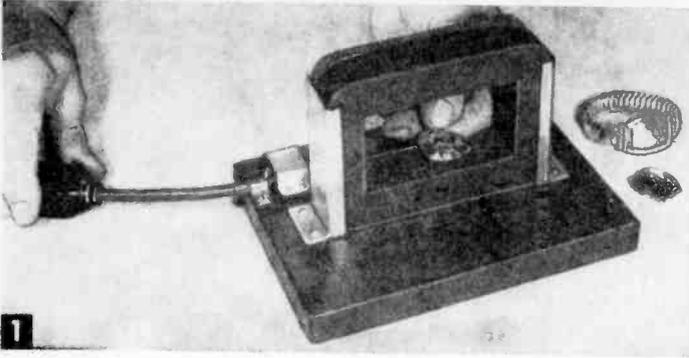

Demagnetizer for Watches and Small Tools

By HAROLD P. STRAND

THE next time your watch starts to lose time or stops because it is magnetized, you can save yourself a trip to the jeweler's by using this demagnetizer (Fig. 1). With the 115 volt 60 cycle power turned On, the alternating current field, created by passage of current through the wound coil, quickly knocks out all magnetism by simply passing the watch movement through the coil opening. Small screw drivers or punches may also be demagnetized with this device.

The hairspring of the balance wheel of a watch has a tendency to accumulate a permanent magnetism, since it is tempered spring steel. This may happen for no apparent reason, or it may occur while you are wearing the watch around electrical equipment, especially where direct current is used. Magnetized turns of the hair spring will stick together or result in an erratic action of the watch movement.




Remember, when using this device, to turn on the power *before* placing the piece in the opening and turn off the power *after* its removal. Otherwise, the sudden switching off of the power while the watch or tool is in place, may result in increasing rather than removing magnetism.


The demagnetizer consists of a rectangular coil, a base board, line cord and switch. To wind the coil, first make up a wooden form which is a permanent part of the unit (Fig. 2). The coil may be wound on a lathe at slow speed, or on a winding machine equipped with a turn counter, but you can handwind the coil by carefully counting the turns. Press a block into the opening of the form, and use a $\frac{1}{4}$ -20 machine screw, nut and washer in a bored hole in the block to provide a stud that can be held in the chuck for turning (see Fig. 4). Solder a flexible #20 lead wire to both start and finish ends of the coil, and bring

out for connection with the line and the switch.

The resulting coil, when energized with 115-volt alternating current, will have sufficient resistance and inductance so that only a small current will flow. If a small tool is placed in the coil opening, a light pull and vibration will be felt from the effects of the magnetic field produced. Since the current in the coil is reversing constantly through 60 cycles or 120 alternations a second, the magnetic field also is in a constant state of reverse, and this causes a complete elimination of the original magnetic polarity in the piece or neutralizes it to zero.

Fig. 3 shows the start of

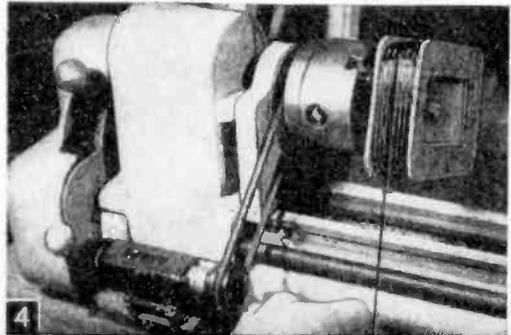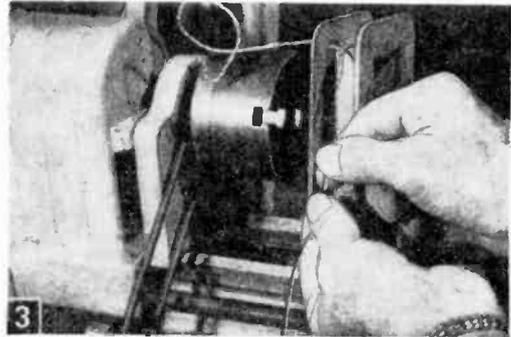
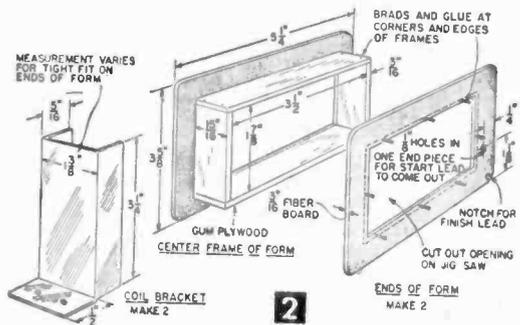


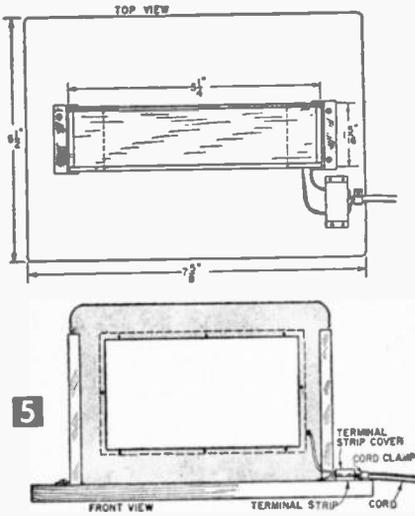

winding the coil in a small lathe, with the flexible lead wire passed through a small hole in the form and soldered to the starting end of the magnet wire. A short piece of plastic tubing will be slipped over the splice to insulate it. A turn counter has been fixed up on this lathe bed, with a rubber vacuum cleaner belt to drive it. Wind 2500 to 2800 turns (Fig. 4) and then solder on the other flexible lead to the finish end. Wrap a turn of electrical or adhesive tape around the winding to bind it in place and then remove the form from the chuck and tap out the block.


Make the base of the demagnetizer from a piece of maple or birch and sand smooth (Fig. 5). The coil is held in position by two side brackets (Fig. 2) which can be made from any soft aluminum or brass sheet stock about 1/32 in. thick. Their width should be such as to tightly grip the sides of the coil form. Use two small round head screws to secure them to the base (Fig. 6).

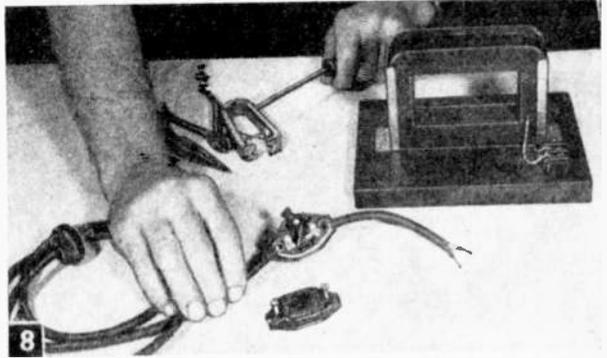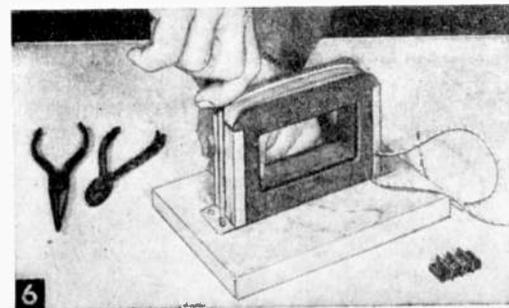The next step is to install a cord switch about 4 in. from one end of a 6 ft. length of rubber line cord (Fig. 8). Connect a regular attachment



MATERIALS LIST—DEMAGNETIZER

Amt. Req'd.	Description	Use
1 pc.	maple or birch 7 1/2 x 5 1/2 x 3/4"	base
1 pc.	3/16" birch or gum plywood, 12 x 1 1/16"	inner frame for coil
1 pc.	3/16" Masonite fiber board, 8 x 6"	sides of coil form
1 pc.	1/32" soft aluminum or brass, 8 x 2"	bracket supports
1 pc.	1/32" soft aluminum or brass, 2 1/2 x 1 1/16"	cover over terminal strip
1	Jones terminal strip, #140, 2 terminal	
1	cord-type toggle switch	
6 ft.	rubber vacuum cleaner cord	
1	attachment plug cap	
1 pc.	sheet brass, 1 x 3/8 x 1/32 thick (bend up to make cord clamp)	
1 lb.	#30 or #29 Formex magnet wire	
4	3/8" #4 rh brass wood screws	
4	1/2" #3 rh brass wood screws	
1	1/4" #5 rh brass wood screw	
2 pcs.	#20 flexible insulated lead wire, 6" long	

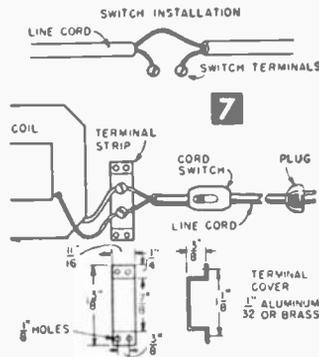


plug cap to the other end. Connect cord to the terminal screws of the terminal strip and make a small clamp to hold cord securely. Place a small cover piece over the live terminals of the terminal strip as protection against accidental shock, screwing through holes in the cover and also down through holes in the terminal strip, to hold the assembly to the base, taking care to

avoid contact between cover and live terminals.

Finish the wood base and the coil unit as desired. A coat of mahogany stain was used in the original, and two thin coats of shellac were then applied as final finish. Sand lightly with 6/0 garnet paper and apply one coat of satin varnish which will complete this project.

Dam for Soldering Lug


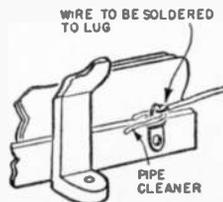


• For a neater job of soldering a wire or cable to a lug, build a dam around it with a pipe cleaner as shown. This idea is particularly good for automotive or radio jobs, where precision is necessary.—V. H. LAMOY.

High-Voltage Traveling Arc

Favorite laboratory background for the movies' "mad scientist" is the Jacob's Ladder or traveling arc. Make your own for about \$25

By HAROLD P. STRAND

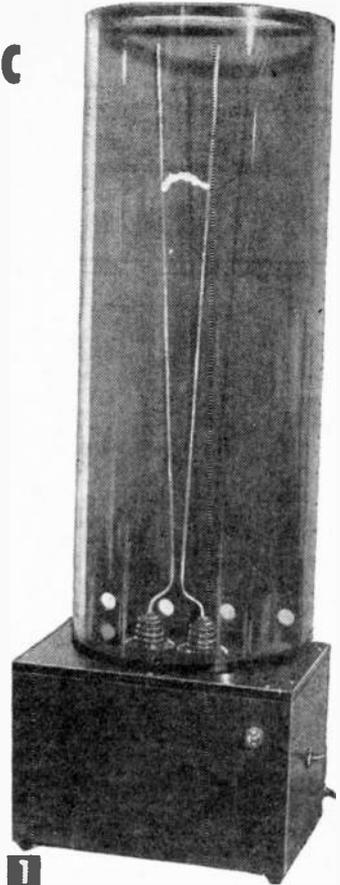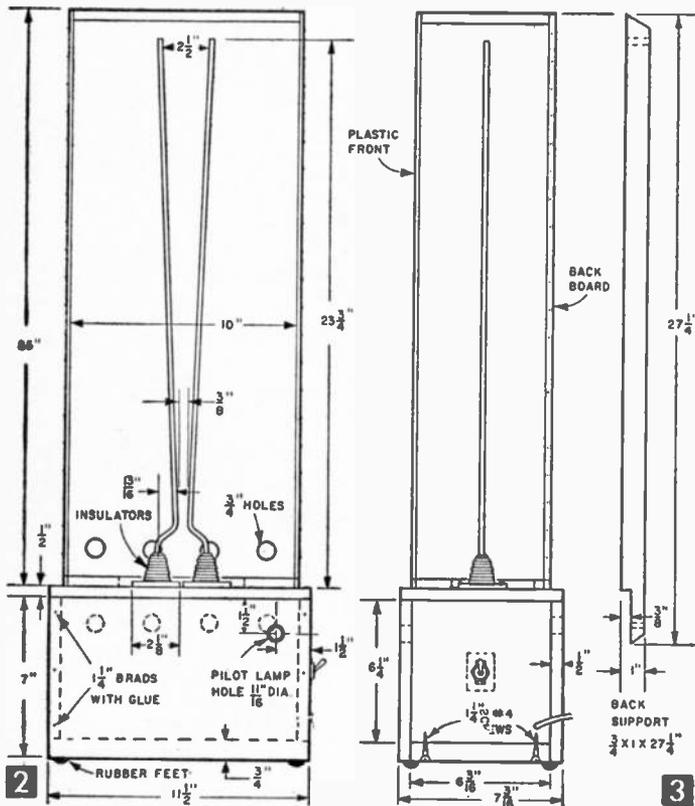


1 A continuous series of flaming arcs will move up the electrodes of this device, which is similar to one shown at the Boston Museum of Science.

REMEMBER when you saw a movie scientist working in his laboratory with the powerful crackle of an electrical arc slowly moving upward between two V-shaped rods in the background? These "Jacob's Ladders" pack a lot of drama into usually dull laboratory equipment and are sure-fire attention getters. You can build your own for experimenting and display—like the one in Fig. 1. As you switch it On, a heavy flaming arc jumps between the wires at the short gap above the insulators. Immediately it starts rising to the top getting longer as the distance between rods increases until it dies out near the top. As soon as one arc is extinguished, another one starts. The process is continuous as long as you keep the switch closed.


vicinity of the arc and, as heated air naturally rises, it pulls the arc up with it. As a 15,000 volt transformer is used in the base, an arc of considerable intensity results and you need the protection against accidental contact that is provided by the enclosure.

You can amuse yourself and your friends with this high-voltage traveling arc, and it makes a good electrical display at shows and exhibits to attract attention to a particular booth. The transformer, from an obsolete Timken oil burner, was purchased secondhand from an oil burner service shop for \$15. Be sure to have the transformer tested before purchasing, which can be done by arranging two well-insulated wires from the secondary terminals to form a gap for the arc

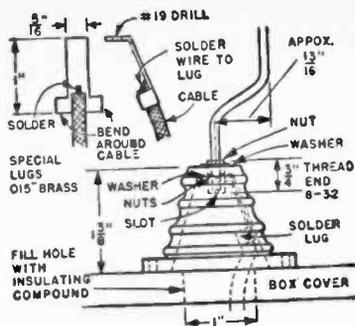
Attach the porcelain insulators to the stained and shellacked cover over 1-in. diameter holes provided.



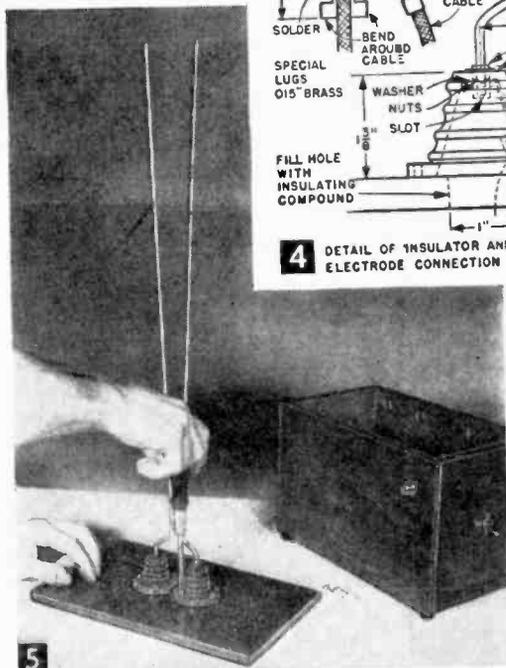4 DETAIL OF INSULATOR AND ELECTRODE CONNECTION



5

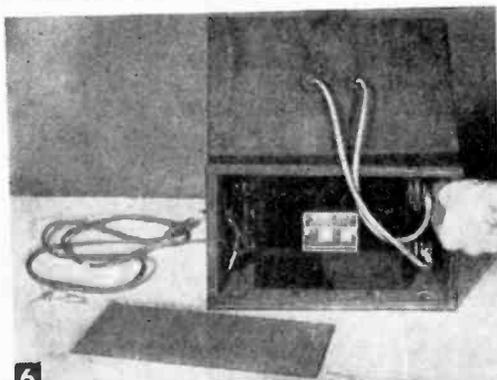

6

With the transformer mounted in the cabinet and the primary connections made with #18 insulated wire, the high-voltage leads of the automotive ignition cable are attached to the secondary terminals. Note that the holes under the insulators on the cover have been sealed with sealing compound.

to jump across. If the unit is in good condition, a heavy arc about 1-in. long should be obtained. Defective windings will produce a weak and short arc, or no arc at all. (CAUTION: Take extreme care in working around such a transformer, as it packs a charge of electricity that can be dangerous or even fatal.) Other makes of oil burner transformers may be used if the rating is about the same, but the dimensions of the box or cabinet given here may have to be modified to suit the size.

Start by making the box from 1/2 and 3/4 in. birch plywood, cutting the parts about 1/16 inch oversize to allow for dressing down to final size on the sanding disc.

Bore the required holes in the cabinet, including four 3/4-in. ventilating holes at the back (Fig. 8A). Assemble sides and ends with a good grade of cabinet glue and 1/4-in. brads, then screw bottom onto the end pieces. Carefully sand all surfaces by hand, slightly rounding the corners. Set the brads and fill the holes with Plastic Wood.


The box can now receive its finish. Apply a coat of walnut oil stain and allow this to dry about ten minutes. Wipe off the surplus stain with a cloth, bringing out the grain. Allow the stain to dry for several hours and then apply a coat of shellac which has been thinned somewhat with denatured alcohol. After drying, lightly rub the surface with #4/0 sandpaper and apply a second coat of shellac, a bit heavier than the first, or with less alcohol. Lightly rub this coat with fine steel wool, taking care to avoid rubbing through the finish at the corners. Apply another coat or two if sufficient shellac has not been built up on the surface. Finish the cover in the same way. Equip the cabinet with rubber knobs or feet at the bottom corners and install a pilot lamp to warn that the power is on and a toggle switch to control the flow of power to the primary. However, a push-button switch can be used instead if desired for momentary operation.

Shape the electrode wires from 5/32 or 3/16 in.

MATERIALS LIST—TRAVELING ARC

- 2 1/2 x 7 x 11 1/2", Birch Plywood
- 2 1/2 x 6 3/4 x 6 3/4", sides, cabinet
- 1 1/2 x 7 3/4 x 11 1/2", ends, cabinet
- 1 3/4 x 6 3/4 x 11 1/2", top, cabinet
- 1 3/4 x 6 3/4 x 11 1/2", bottom, cabinet
- 1 3/4 x 10 x 25", back board, enclosure
- 2 3/4 x 6 x 10", end pieces, enclosure
- 1 3/4 x 1 x 27 1/4", (birch or maple), back support, enclosure
- 1 Miscellaneous
- 1 15,000 volt, 30 milliamperes oil burner ignition transformer for 115 volts 60 cycles (Timken Model A-R Spec. #638-291 or equiv.)
- 2 porcelain stand-off insulators, 1 3/8" high, about 2" diameter bases
- 1 S.P.S.T. toggle switch, 6 amperes at 115 volts, with ON-OFF plate
- 1 pilot lamp assembly for 115 volts, clear lens (Dialco #95408-937, Allied Radio #52E507)
- 1 NE-51 neon lamp
- 8 ft #18 or #16 rubber lamp cord for primary connections
- 1 attachment plug cap
- 1 sheet rubber 1/8 x 5 1/2 x 10" (rubber floor tile will do)
- 2 1/2 or 3/16" dia. x 25" long hard aluminum rod for electrodes, from metal products supply company (see local phone directory). Cut to length after bending
- 4 rubber knobs or cabinet feet with wood screw threaded center studs
- *1 sheet clear rigid vinyl plastic .030 x 17 3/4 x 25"
- 2 solder lugs, .015 x 3/4 x 1 1/2" brass or copper
- 2 solder lugs to fit transformer secondary terminals
- high tension automotive ignition cable
- Misc. stain, shellac, screws, nuts, washers

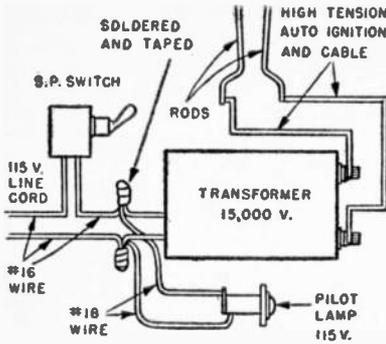*The Forest Products Co., 131 Portland, Cambridge, Mass., will supply the plastic in a .030 x 20 x 25" piece for \$2.75 ppd in U.S.



7 PICTORIAL WIRING DIAGRAM

dia. hard aluminum rod stock so they will be about $\frac{3}{8}$ in. apart at the bottom end and about $2\frac{1}{2}$ in. apart at the top (Figs. 2 and 4). The exact spacing will depend on the diameter of the bases of the insulators obtained, since if they are larger than those we used, greater offset will have to be put in wires to get required spacing. Cut #8-32 to 10-32 threads on wires, depending on rod size, so nuts and washers can be used as in Fig. 4.


Attach the porcelain insulators with the attached electrodes to the box cover (Fig. 5).

Secure the transformer to the cabinet bottom, using four wood screws at its base. Complete the primary connections with two soldered and taped joints (Figs. 6 and 7). Connect the high-voltage cables to the secondary terminals, using solder lugs on the cables (Fig. 4). Seal the holes in the cover through which the cables pass with a sealing compound, which can be any insulating type of hard-setting cement capable of being melted and poured in the holes (Figs. 4 and 6). Place a piece of rubber (shown on the bench, Fig. 6) on top of the transformer to prevent possible leakage of current to that metal surface.


Attach the cover, using roundhead brass screws. Give the unit a preliminary test in this condition, standing 3 or 4 feet away for safety. The arc should form at the bottom and rise, but not in a proper manner as it will when the enclosure is provided.

Construct the enclosure from $\frac{3}{8}$ -in. birch plywood (Fig. 8). Make the openings in the two curved end pieces on the jigsaw and attach to the back board with glue and flathead screws. Fit the back brace to the board. Bore four $\frac{3}{4}$ -in. diameter holes through the back board at the lower end to admit air. Apply walnut oil stain and finish exactly the same as the cabinet.

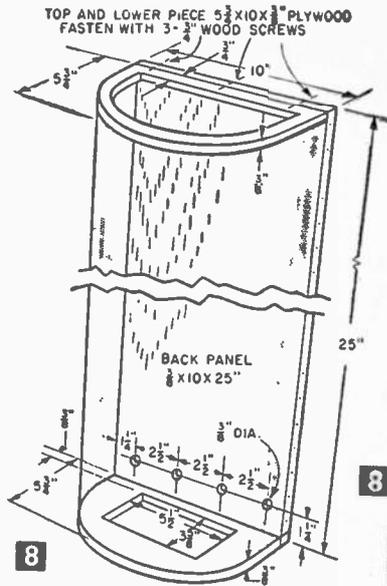Cut the .030-in. clear vinyl plastic front to size with sharp scissors, taking care to avoid cracking, and install to the edges of the unit in a simple manner, using small brads with heads or very small tacks along the two sides



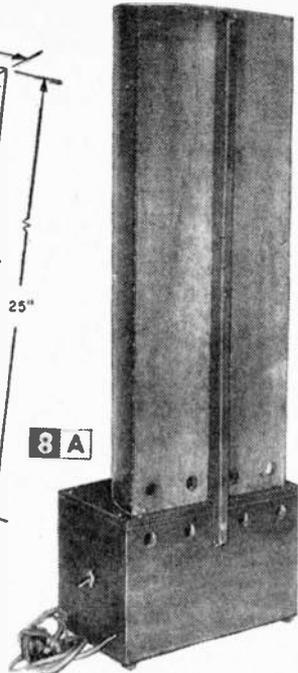8 A view of the finished job from the back side. The author built the device in slightly more than two evenings at a cost of about \$25.



(Figs. 8 and 8A). Apply shellac to the edges first, and allow to dry until tacky. Then place the plastic in position on one edge and secure. Bend the material around the curved end pieces, pull it tight and secure it at the other edge. Be sure to drill a small hole for each brad, since this plastic is quite brittle and may crack if you try to drive a brad through it. Avoid the use of plastic that will support combustion, such as some of the cellulose variety. Vinyl plastic will soften if given too much heat, but will not burn easily.

Long testing has proved that the plastic front was sufficiently far enough away from the arc to keep out of trouble. However, if you want added fire safety, cement or tack a strip of sheet asbestos around the inside edge of the top opening, where the intensity and flame of the arc are the greatest.

Drop the completed enclosure down over the wires and secure to cabinet with a single screw through the supporting brace (Figs. 3 and 8A).

While the unit can probably be operated continuously for quite some time without damage, it is well to use it intermittently or for special demonstrations, since the wire electrodes become quite hot due to the moving arc stream. Print a sign or name plate on the front of the cabinet, reading "CAUTION—15,000 volts," as a general warning to persons who may tend to get careless.

If used properly, however, there should be no danger to anyone.

A Volt-Ohmmeter and Transistor Tester For The Experimenter


By C. F. ROCKEY

If you do much serious radio or electronic experimental work, you will frequently need to make voltage and resistance measurements within your circuitry. And the present intense interest in transistors makes a simple transistor tester increasingly valuable. Why deny yourself these essential measurements when you can build a unit to perform both of these functions in a single Saturday afternoon? One for which the cost will be well below that of currently available, American-made instruments of equivalent utility.

Experience indicates that 99% of all routine electronic circuit tests are those of dc voltage and resistance. While ac voltage and dc current scales would be occasionally useful, the added cost and complexity involved does not justify including them within this device.

The only expensive item is the meter itself. Good meters cost money, poor ones are not worth the little they do cost. But the 0-1 milliampere meter used here is one of the most useful of instruments, and it is well worth its approximate \$10 cost. (You will find plenty of future use for it, long after you have electronically outgrown this project.) Surplus 0-1 milliammeters are available, we understand, at something like one-half new-meter price. But be careful. It is easy for the beginner to get stung. Make sure that the meter you use is of the correct current rating, has not been damaged by shock or mishandling, and is of the moving-coil (D'Arsonval) type. The cost of the remaining parts in this project is small.

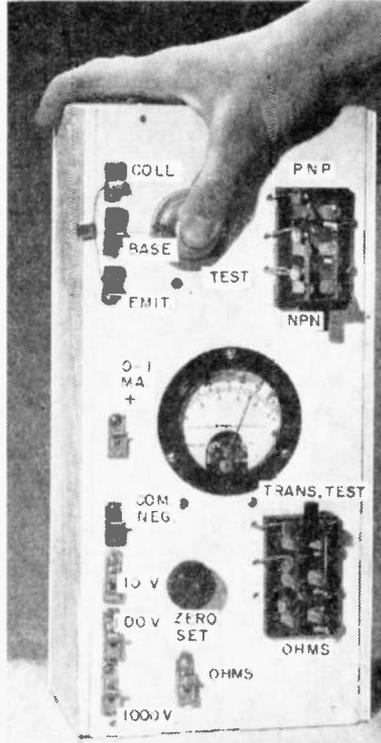This project is big; the writer does not believe in miniaturization in home projects. First, I'm not a jeweler and secondly, miniaturization is costly and subject to difficulties in maintenance. You can redesign this job to fit in a much smaller space. But you will sacrifice ease of construction and maintenance thereby.



1 Not a "black box," but a white one that is inexpensive and useful.

Begin by building the case and panel, a simple plywood box 4 x 6½ x 13½ in. Nail the sides and bottom together to form the cabinet, but leave the top loose. This will be the panel (see Figs. 3 and 5) upon which all parts will be mounted. Quarter-inch plywood scraps were used by the author for the panel, sides, and bottom. The ends are three-quarter inch pine stock. Sand the base and panel for a neat job, but do not finish until all holes have been drilled. Then give the panel a final sanding and finish as you prefer. I used some semi-gloss wall paint I had on hand, but orange shellac is acceptable, and dries much faster.

Cut the meter hole squarely in the center of the panel. A hole of 2¾ in. dia. will fit most modern meters. (The old Weston, vintage of the thirties, used in the writer's job, took a 2½-in. hole.) If you have a suitable expansion bit, use this to cut the hole. If not, draw a circle in the right place and drill all around its circumference with a ½-in. drill. This is the hard way, but it works. The rim of the meter will neatly cover any misses.

Next, drill ⅛-in. holes to mount the two DPDT switches. Use a switch as a template. These switches are available at many chain hardware stores, "dime" stores, etc., throughout the country. Drill a ⅜-in. hole for the zero-set potentiometer. Finish the drilling with the ⅛-in. holes for the Fahnestock clips, the mounting holes for panel, and pushbutton lead holes.

If you consider Fahnestock clips old-fashioned, substitute pin jacks. But you'll find, as the writer did, that they'll lose their grip much sooner, despite their prettier looks.

With all the holes drilled, sand and finish. When finish is dry, mount all parts except the meter. Then wire the circuitry according to Fig. 6. Mount the voltmeter multiplier resistors between two tie-lugs, as shown in Fig. 5. Finally, insert and connect the meter. When the wiring is


completed, check it again.

Why is the flashlight cell soldered into the circuit and allowed to lounge upon the bottom of the case, instead of being fitted into clips? Because of the long anticipated-life of the cell; under normal conditions it will last over a year. Since a really effective battery clip is tricky to build, the writer did not consider it worth the trouble. (A poor clip, found, alas, in many "store-bought" instruments will cause no end of vexation. So, unless you can build a good one, solder the cell in and forget about it for a year.)

Put a knob on the zero-set potentiometer, and turn it to its counter-clockwise extremity. Short-circuit the "ohms" and the "com. neg." terminals (with the switch in "ohms" position) and adjust the pot to make the meter read exactly full-scale. This is the zero on the ohms scale. If this seems strange, remember that, by Ohm's law, maximum current flows when the resistance is minimum. Use this same setting for transistor tests.

In normal use, one of your tests leads is connected to the "com. neg." terminal, while the other is placed in the clip representing the measuring range you wish to use. The number of volts measured is the meter reading times ten, one hundred, or one thousand, depending upon the range in use. This makes the mental arithmetic easy, and covers voltages found in most radio and electronic projects. For obvious safety reasons, do not attempt to measure voltages above one thousand volts with this instrument.

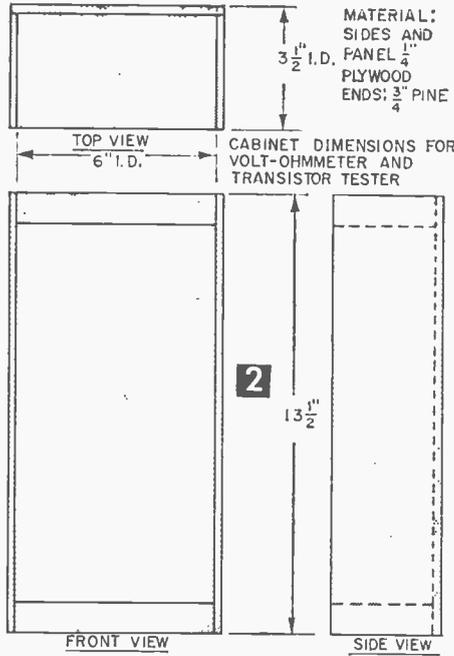Be sure to observe polarity when using the voltmeter, otherwise the meter will swing backwards, which may seriously damage it. Also be sure to unplug all power or remove all batteries from apparatus being



tested before using the "ohms" scale. Otherwise the meter may be irreparably damaged; more test equipment is probably damaged through this kind of neglect than any other.

You may accurately determine any resistance from the ohm-meter reading by using the following formula:

$$R = \left(\frac{1500}{I} \right) - 1500$$

Where: R=Resistance of the unknown or measured resistance, in ohms.


I=Meter reading, milliamperes.

Or, if you wish to carefully place resistance calibrations upon the scale of your meter, as the writer has done, you may use the following table (K= one thousand):

10K ohms	0.130 milliamperes
5K ohms	0.23 milliamperes
3K ohms	0.33 milliamperes
1.5K ohms	0.50 milliamperes
1K ohms	0.60 milliamperes
500 ohms	0.75 milliamperes
100 ohms	0.95 milliamperes

Use a sharp steel pen and black ink. Be sure to disassemble the meter carefully, and in a clean, dry place. Airborne grit is very bad for its insides.

While it is quite impossible to thoroughly test a transistor, in the scientific sense, without several thousand dollars worth of laboratory equipment and much experience, one can obtain a significant check by using this simple unit. Since the maximum applied voltage is $1\frac{1}{2}$ v, all but the most delicate and specialized transistors may be checked without fear of damaging them. This is more than one can say of some of the commercial testers on the market. Like all simple transistor testers, and many tube testers also, this device gives only a comparison test, but this is usually sufficient. It will always reveal a bad

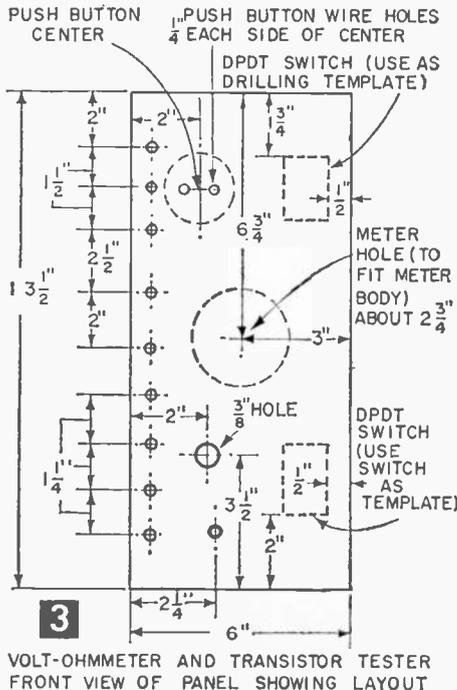

MATERIALS LIST—VOLT-OHMMMETER AND TRANSISTOR TESTER

No. Req'd	Description
1	0 to 1 ma. milliammeter, 3" size (Weston, Triplett, Simpson, or other good make)
2	DPDT. plastic base knife switches
1	push-button, flush mounting
9	Fahnestock clips
1 set	test leads, ICA
1	1000 ohm potentiometer, (Mallory, IRC, or any other good make)
1	knob for potentiometer
1	flashlight cell, large size
1	single-point tie-lug
1	double-point tie-lug
1	triple-point tie lug
1	1 Megohm, 1-watt carbon 5% resistor
1	100K, 1-watt carbon 5% resistor
1	10K, 1-watt carbon 5% resistor
1	1K, 1-watt carbon resistor
1	47 ohm, 1-watt carbon resistor
1	200K, 1-watt carbon resistor
1	9.1K, 1-watt carbon resistor
1	6-32 rh machine screws, 3/4" with nuts, #6 x 3/4" rh wood screws, hookup wire, rosin-core solder, finish
2 pcs	1/4 x 6 x 13 1/2" plywood
2 pcs	1/4 x 3 3/4 x 13 1/2" plywood
2 pcs	3/4 x 3 1/2 x 6" pine stock

transistor's amplifying ability, its "dc beta." The greater the change, the more the potential amplification. One would normally consider a change in current of 0.4 milliamperes to be about the minimum to be expected of a good transistor, as sold today. For a quick check, then, the current should swing up to at least 0.6 ma. when the button is pressed if the transistor is to develop satisfactory gain in the usual circuit.

Experience with this tester will reveal the great variability of characteristics found in transistors of the same type sold on the market today. Even with the tremendous strides being made in semiconductor technology, it is economically impossible to hold the tolerances within the 10% or so, one finds in vacuum tubes. This is especially so in the case of the cheaper units which most of us are economically forced to use. But with a tester like the one described here, you can pick and choose from your stock, selecting the highest-gain units

In-circuit testing of resistors is possible, but watch out for those parallel circuits and make sure circuit is dead.

transistor, but no simple test can definitely assure of a good one, since too many factors are involved. All currently-available types may be significantly checked with it, and the result will be found valid and reliable.

Practically, a transistor has two properties which will determine whether it is usable or not. These are:



1. The open-base, emitter-collector leakage.

2. The grounded-emitter dc voltage gain, or "dc beta."

This device gives a comparative indication of both of these properties.

Place the "PNP-NPN" switch in the appropriate position for the transistor you wish to test. Connect transistor leads to correct terminals. Then throw the "ohms—trans. test" switch into the "trans. test" position. The reading you now observe upon the meter is a function of the open-base, emitter-collector leakage. (This is before the test button is pressed.) The lower the meter reading under these conditions, the better the condition of the transistor. In every case, the meter reading should be less than 0.1 milliamperes, preferably closer to 0.05 milliamperes. If the reading exceeds 0.2 milliamperes it is a sure sign that the transistor has been electrically mistreated, and should be considered questionable, if not downright bad.

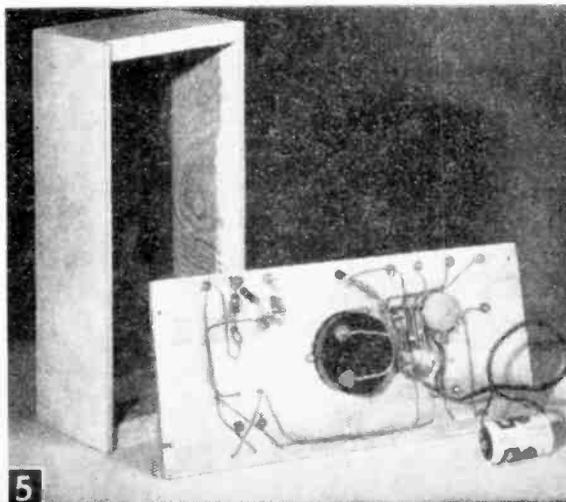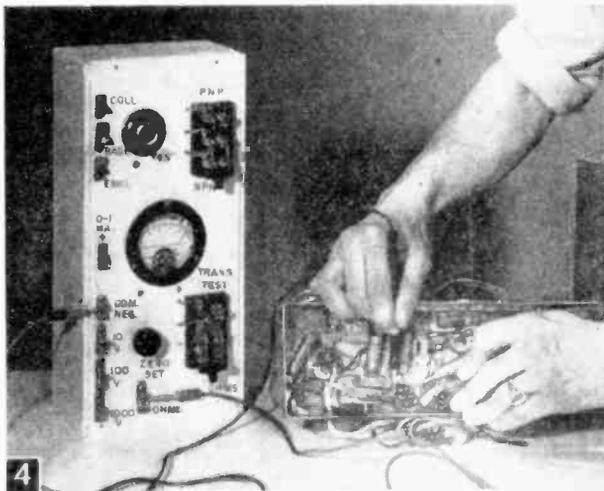
If the transistor passes the above test, press the button. The current indication should increase sharply, at least to 0.6 milliamperes. It is the change in current observed which gives the measure of the



Back view of front panel of case, showing simple wiring.

for the most critical parts of the circuit. If you do this, you will soon see the improvement in performance of the gear you build. (Incidentally, do not leave switch in "trans. test.")

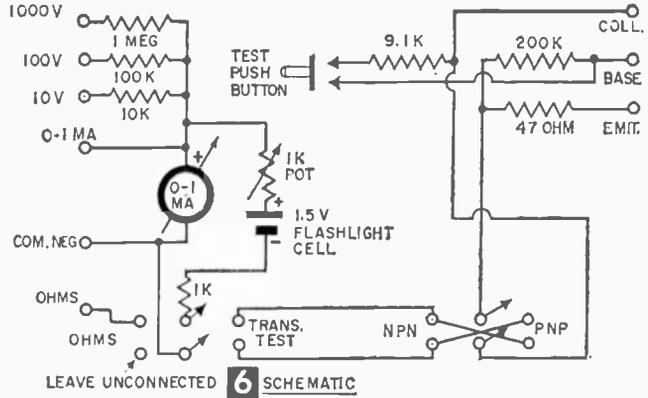You can also use this device for comparative checks of semiconductor, "crystal" diodes. Connect the diode from the "emit" to the "coll" terminals, with the meter switch in "trans. test" position. Switching the "PNP-NPN" switch back and forth *slowly* should reveal a current difference of at least 0.6 of a milliamperere, if the diode is usable. The greater this difference, the better.



Electronic Black Magic

How does it work? Only two wires connect the switch to the lamps, yet throwing the switch in one direction lights one lamp, throwing it in the opposite direction turns the first lamp off, the second on


By FORREST H. FRANTZ, Sr.

FOR every lamp that is to be controlled separately by a single switch throw, two wires are required from lamp to switch—usually. Here, however, one switch and only two wires control two lamps. Extra conductors in the two wires? Hidden wires? Hair-thin connecting wires? Those you demonstrate this device to will look for all of these possibilities. That's one reason connecting clips are used between the switch and lamp cases: to allow observers to convince themselves that the insulation over each lead covers only one wire.

After the observer is convinced that no hidden wires exist, he may take a guess that wireless radio is involved. This goes out the window when you tell him that the entire outfit costs only about \$2, and at that price radio isn't involved. Magnetic coupling, then? To kill this theory, separate the cases by several feet. Point out that the light bulb intensity remains constant no matter what the physical separation between units.

How does it work then? Electronic black magic.

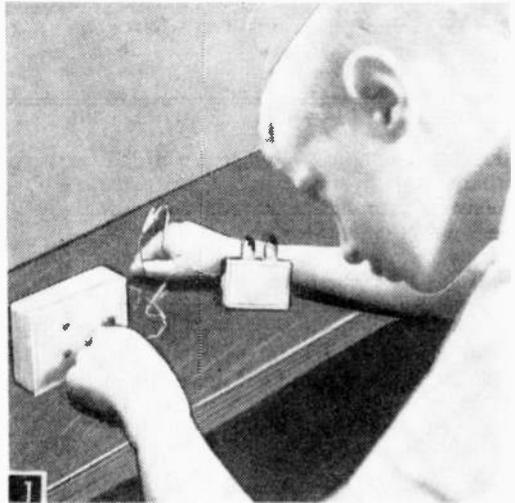Construction. Layouts for switch and lamp cases are shown in Fig. 2. The smaller holes, and pilots for the larger holes, are made with a heated ice pick. Plastic that accumulates around the sides of the holes may be trimmed off with a pocketknife after the material has cooled. Larger holes are finished with a hand taper reamer.



Black magic from white boxes. A single switch and a single pair of wires control two lamps.

MATERIALS LIST—ELECTRONIC BLACK MAGIC

Design.	Description
SWITCH UNIT	
B	four 1.5-v penlite cells, series connected (RCA VS074)
S	DPDT toggle switch (Carling 316-25)
	battery holder (Lafayette MS-170)
	1 x 2 $\frac{5}{8}$ x 3 $\frac{5}{8}$ " plastic case (Lafayette MS-159)
LAMP UNIT	
D1, D2	1N54A diode (RCA)
L1, L2	#48 miniature lamp (RCA)
	1 x 1 $\frac{5}{8}$ x 2 $\frac{1}{8}$ " plastic case (Lafayette MS-156)
	2 Minigator clips (Mueller 30)


Components for this project may be obtained from Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, New York.

When you make the holes for the lamps, work slowly and ream the holes just large enough so that the lamps fit into them tightly.

When all of the holes have been made in the cases, wash them with soap and water, rinse and dry with a lintless cloth. Then paint the insides any color you wish. I used white because this encourages the observer to hold the cases up to the light to try to determine their contents. Although he'll be able to see the switch and battery, he won't be able to see enough to determine the


secret. Use two coats of paint if necessary.

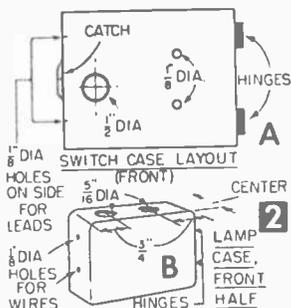Now mount the battery holder and the switch in the switch case (see Fig. 3). Connect the battery holder terminals so that the four penlite cells will be in series. Fill the battery contact holes on the holder with solder. This assures reliable contact. Don't allow the clips to cut the paper covering on the batteries when you insert them. Complete the wiring as shown in Fig. 5.




The inside view of the lamp case is shown in Fig. 4. Wire the lamp case, making sure you observe diode polarities. Don't apply heat to the diodes for a long period of time when you solder them into the circuit. Too much heat will damage them.

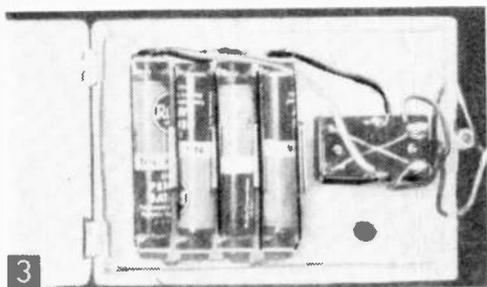
With construction completed, connect the units



3 Inside view of switch case.

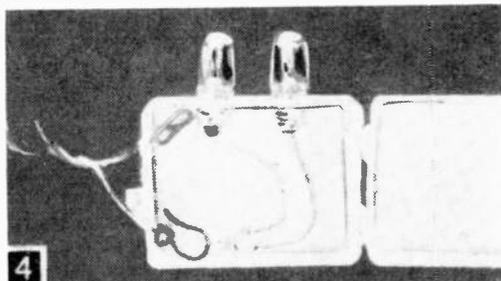

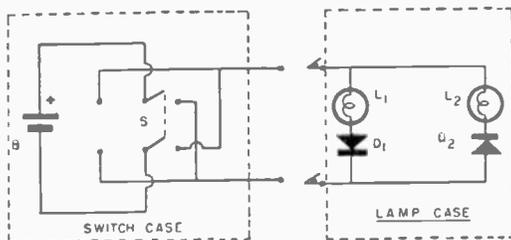
4 Inside view of lamp case. Disconnect two cases when not in use to prevent unnecessary drain on batteries.



5 CIRCUIT DIAGRAM

together and try your handiwork. By now you probably know the electronic black magic that's involved, but for the gadgeteer without electronic experience, an explanation is in order.

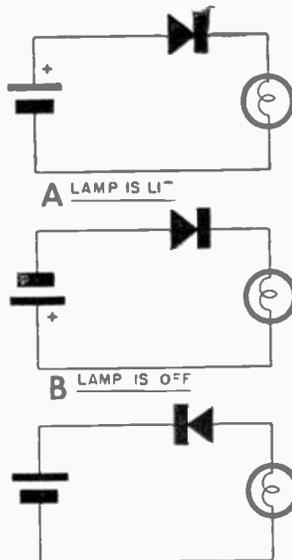A diode will conduct in one direction only. A diode connected in series with a lamp and battery as shown in Fig. 6A will conduct and allow the lamp to light. But if the battery polarity is reversed (Fig. 6B), the diode will not pass current, the lamp will not light. By the same token, if the battery is left as shown in Fig. 6A, but the diode is reversed as in Fig. 6C, the lamp will not light.



6 A LAMP IS LI^T
B LAMP IS OFF
C LAMP IS OFF

Now, referring to Fig. 5, it is apparent that throwing the switch causes the battery polarity to be reversed. Since the diodes



are oppositely connected to the respective lamp bulbs, one—and only one—of the lamps will light, the position of the switch determining which one will. No black magic after all.

Crystals Like It Cool

• The crystal elements of microphones and phonograph pickups and crystal diodes and transistors are sensitive to high temperatures. All these crystal and semiconductor elements are enclosed in a case or shell. If exposed to strong sunlight, the temperature inside may rise far higher than that outside the case or shell, damaging the elements so they no longer work and may actually melt. To prevent damage, be sure to shade the pickup arm of a portable phono pickup or shelter a transistor radio being carried or used on a picnic during the summer. And never leave a pickup unit in its case in the window.—JAMES A. McROBERTS.

SOLUTION TO
AMATEUR
RADIO
PUZZLE
Page 51

H	A	M	P	E	S	T	E	D	Q	S	L
A	E	N	T	F	C	C	W	O			
R	I	G	D	I	T	O	S	C	Q	S	O
M	C	C	P	C	J	V	T				
O	S	W	L	O	G	M	H	O	T		
N	E	T	O	C	T	A	L	N	C	E	
I	U	G	X	H	O	H	M	S			
C	B	K	C	Q	B	A	N	D	I		
S	G	E	X	T	R	A	R	E	N	D	I
H	Y	S	O	T	R	E	T				
C	H	U	P	F	L	L	I				
H	A	M	N	O	V	I	C	E	A	A	C
O	I	T	E	N	Y	A	G	I	K		
K	W	V	A	A	D	C	E				
E	T	H	E	R	L	O	S	S	W	E	T

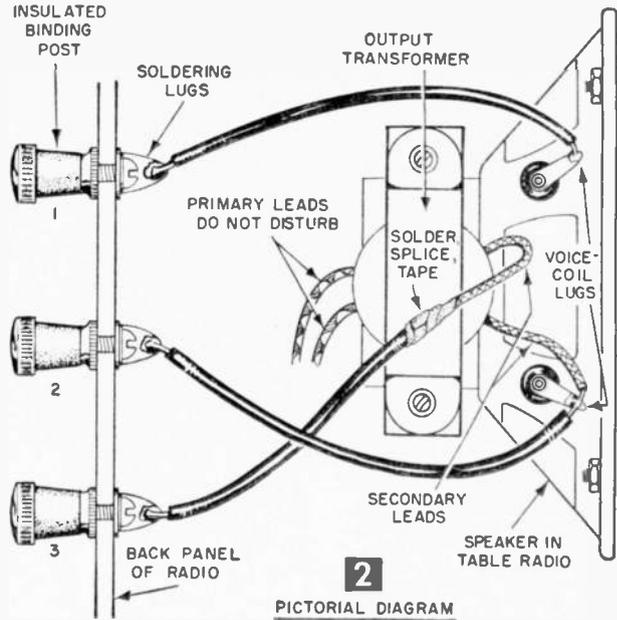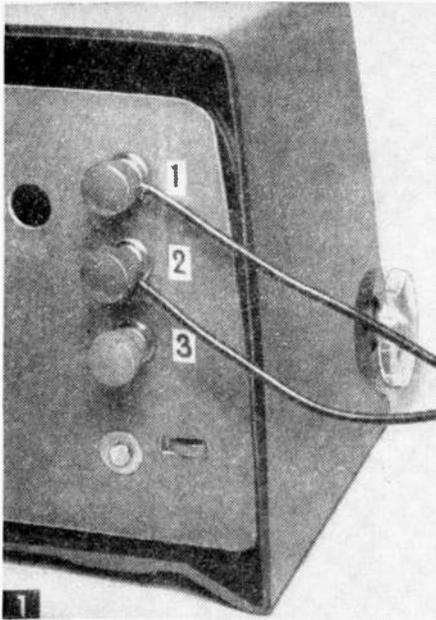

PICTORIAL DIAGRAM

Four Extra Uses for Table Radios

BY making a few wiring changes and adding three insulated binding posts to the back of your table radio as shown in Figs. 1 and 2 you can:


1. Use the speaker only for an experimental dynamic microphone, or speaker can be connected to a code practice set for group instruction or testing a radio you are building by connecting the latter to posts 1 and 2. If the speaker has a permanent magnet, pull out the line cord plug; if it uses a field coil, turn the set on to energize the speaker magnet.

2. Add a small extension PM speaker to the radio for use in other rooms, connecting it to posts 1 and 3 if both speakers are to operate or posts 2 and 3 if only the extension speaker is to be used.

3. Boost the radio fidelity by connecting a large PM speaker housed in a good baffle to posts 2 and 3.

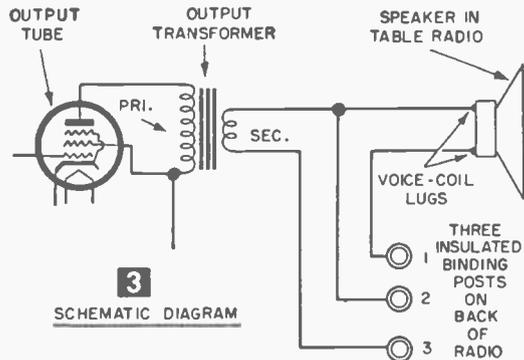4. Use the radio speaker as a "tweeter" and a large PM speaker connected, in series, to posts 1 and 3, as a "woofer." Place the radio on top of the woofer cabinet. If you want the speakers in parallel, connect the woofer to posts 1 and 2 and a wire jumper from post 1 to 3. In either case the speakers should be in phase (their cones moving in the same direction at the same time) to give the best tone quality. If they are out of phase, reverse the woofer connections for better sound.

The radio still can be used as its designer intended by connecting a wire jumper to posts 1-3.



SCHEMATIC DIAGRAM

How to Wire. Fig. 1 shows the installation on an FM table radio; Figs. 2 and 3 furnish the wiring info. Do not disturb the two wire leads, usually red and blue, on the primary side of the output transformer. If you cannot find a place for the posts on the rear panel where they won't interfere with the loop antenna, if any, mount the posts on a strip of insulating material and fasten with an angle bracket to the back of the cabinet.

Caution: If one side of the speaker voice-coil and one of the output transformer's secondary leads are grounded to the chassis of an ac-dc radio, remove these leads from the chassis and connect the latter directly to the voice-coil. This will by-pass a possible hot chassis, and there will be no danger when handling the binding posts. If the radio has a power transformer, there is no danger and no change need be made.—ART TRAUFFER.

"Hop-Up" That Small Radio with a Tuned Antenna Coupler



1

You'll be surprised at how well your small receiver performs when coupled to an outdoor antenna with a tuned antenna coupler.

Do you want to listen to that distant 250-watt station despite a 5000-watter blasting away nearby? Do you live so far from the nearest transmitter that even your local reception is weak and full of noise? If so, this simple gadget is for you.

A long, outside antenna seldom proves satisfactory with the usual small broadcast receiver, since it often spoils the selectivity of the front-end. A simple antenna tuner, such as this unit, used with an outside antenna, will restore this selectivity and couple the circuits more effectively. Result: No more "birdies," or local station smear, and the little ones from far away stick their heads above the mud.


Obtain a cardboard mailing tube, or a core from a bathroom tissue roll about 1½ in. in diameter and at least 3½ in. long. (The dimensions are not critical, and may vary ½ in. either way.) Carefully close-wind on this tube 150 turns of No. 24 copper magnet wire. Cotton-covered wire is best but enamelled wire will do. Arrange for taps on this coil at 50 and 100 turns (see Fig. 2).

Connect this coil in series with a variable capacitor of 360-mmf maximum capacitance. Any variable capacitor having this capacitance will work satisfactorily. (If you use a two-gang unit, salvaged from the junkpile, use only one section.) Mount the capacitor and coil upon a ¾ x 4 x 4 in. softwood board (see Fig. 2), and your antenna tuner is complete.

There are two ways to connect this tuner to


your radio, depending upon the impedance of its input circuit. Try both connections, the one giving the sharpest tuning and the greatest signal boost will be immediately evident. The connection shown in Fig. 3A is for high-impedance, 3B for low impedance inputs.

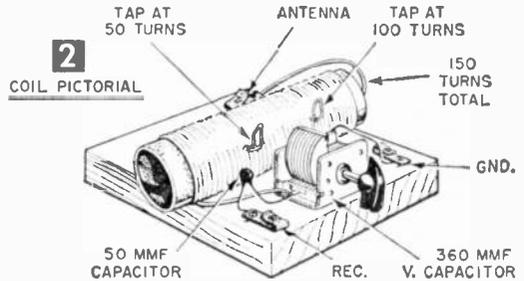Use a well-insulated outdoor antenna with a total length of 60 to 150 ft. A good cold-water pipe ground should also be used. Set the radio dial to the frequency of the weak station you wish to hear and rotate the variable capacitor knob until it peaks to maximum volume. Then readjust radio tuning for best signal quality. Clip the antenna clip on the coil tap that gives best results.—C. F. ROCKEY.



MATERIALS LIST—ANTENNA COUPLER

No. Req'd	Description
1	variable capacitor, 360 mmf. max.
1	Mueller spring battery clip, miniature size knob, for variable capacitor
1	No. 24 magnet wire, cotton-covered or enamelled
¼#	0.01 mfd., 200 w.v. paper capacitor
1	50 mmf., disc-type ceramic capacitor

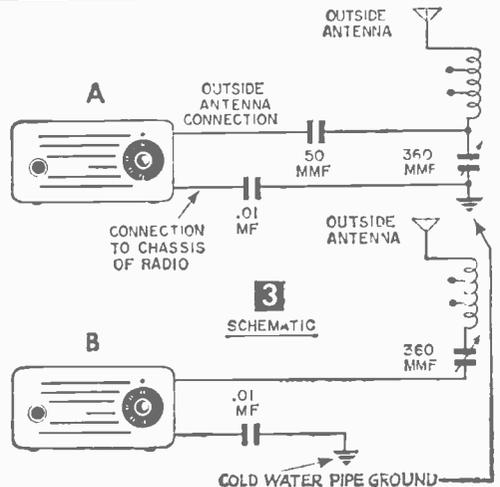

Learn By Doodling

By ROBERT W. LUEBKE

HERE'S an easy way to test your knowledge of amateur radio circuits. The six circuits given on these two pages are some of those you'll find it essential to know about when working toward an Amateur Radio Operator's General Class license. We publish them by special permission of The American Radio Relay League, publishers of the *Radio Amateur's License Manual*.


The connecting wires have been removed, but all the components are shown. Cover the

outlines on these pages with onion-skin or any other translucent paper and "doodle" in the missing connecting lines. Check your doodling for errors by comparing with the complete circuit diagrams on page 94.

If you find your first doodle in error, study the circuit carefully and try again. Use a new sheet of paper each time rather than doodling directly on these pages. Soon you will be able to draw the entire circuit without using the outline at all.


1. Draw a schematic diagram of a full-wave single-phase power supply using a center-tapped high-voltage secondary with a filter circuit for best regulation, showing a bleeder resistor providing two different output voltages and a method of suppressing "hash" interference from the mercury-vapor rectifier tubes. Give the names of the component parts and approximate values of filter components suitable for either amateur radiotelephone or radiotelegraph operation.

1

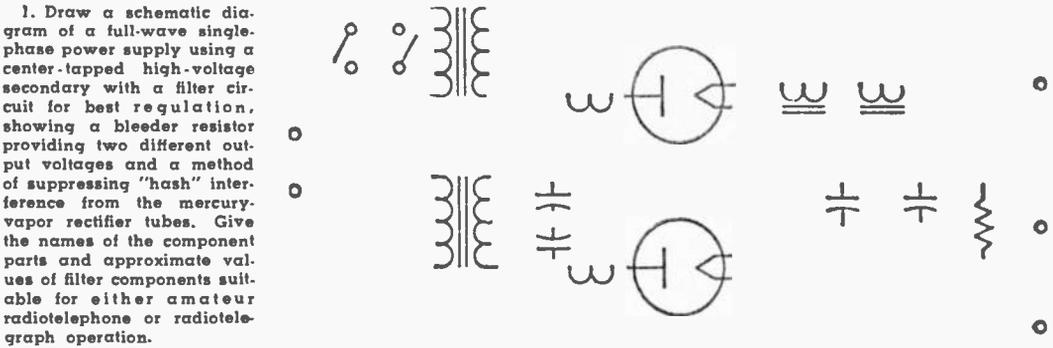

2. Draw a simple schematic diagram of a plate-neutralized final RF stage using a triode tube coupled to a Hertzian antenna, showing the antenna system and a Faraday screen to reduce harmonic radiation.

2

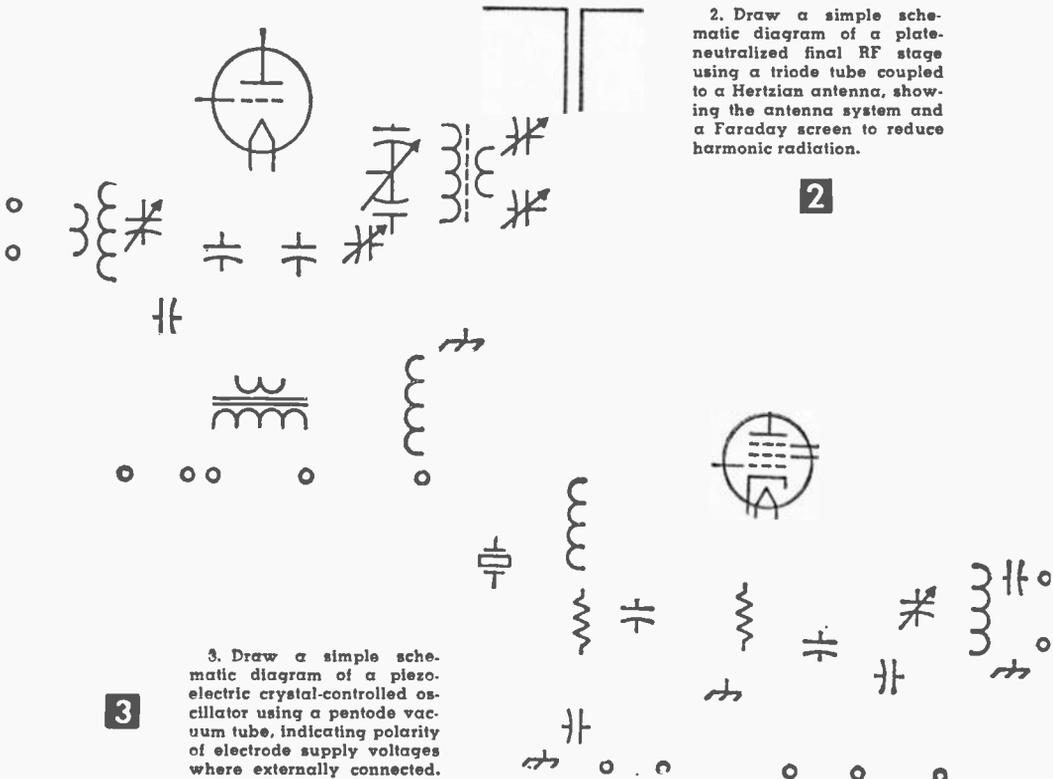


3. Draw a simple schematic diagram of a piezoelectric crystal-controlled oscillator using a pentode vacuum tube, indicating polarity of electrode supply voltages where externally connected.

3


4. Draw a simple schematic diagram of a half-wave rectifier with a filter which will furnish pure dc at highest voltage output, showing filter capacitors of unequal capacitance connected in series, with provision for equalizing the dc drop across the different capacitors.

4

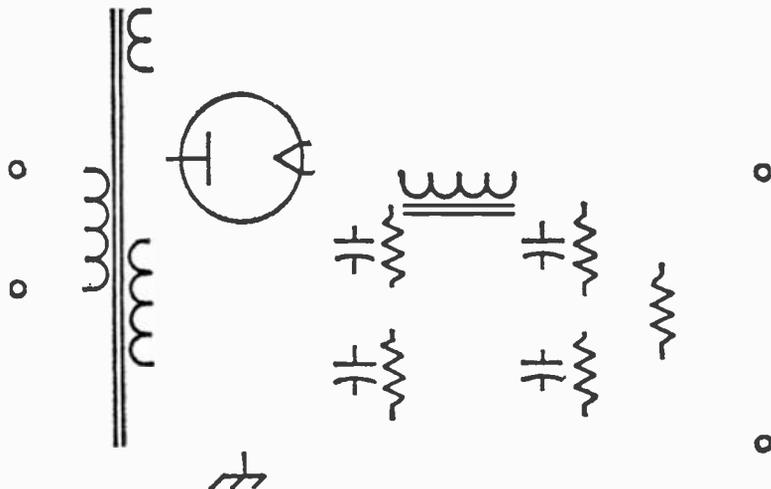


5. Draw a schematic diagram of a pentode audio power-amplifier stage with an output coupling transformer and load resistor, showing suitable instruments connected in the secondary for measurement of the audio-frequency voltage and current, and naming each component part.

5

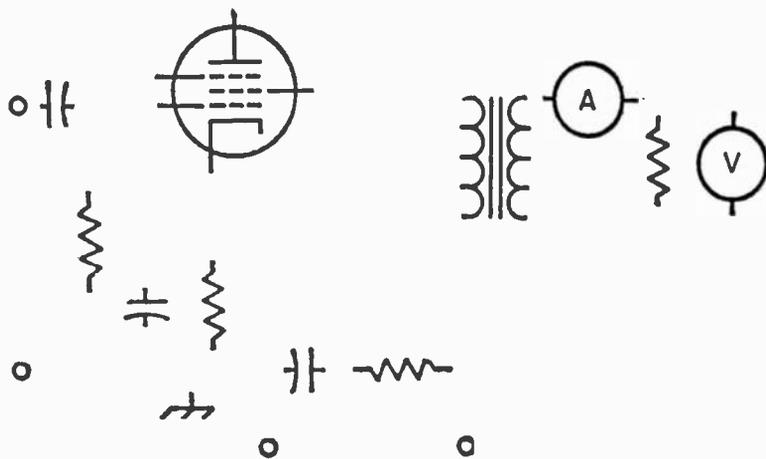


6. Draw a simple schematic diagram of two RF amplifier stages using triode tubes, showing the neutralizing circuits, link coupling between stages and between output and antenna system, and a keying connection in the negative high-voltage lead including a key-click filter.


6

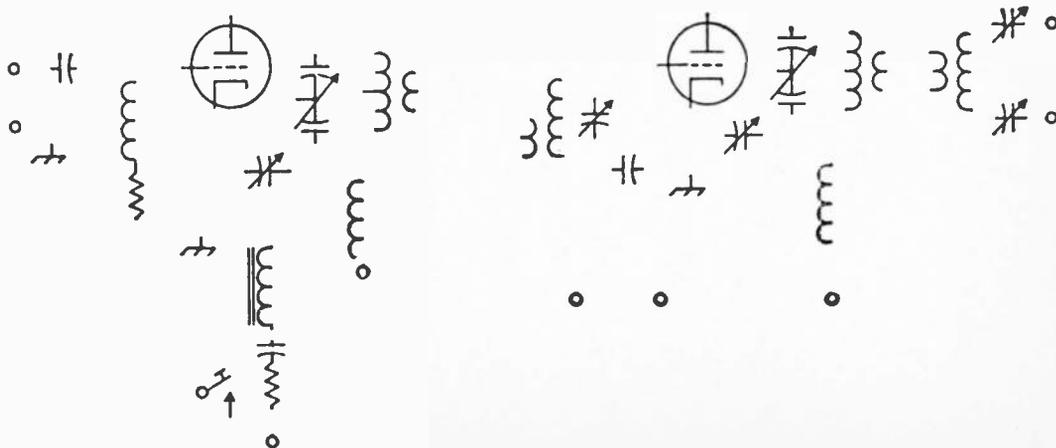


Completed
Circuit
Diagrams

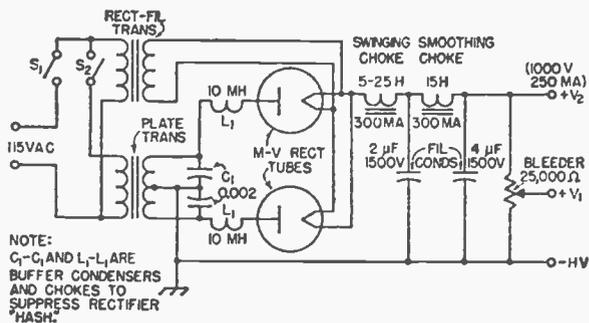


1

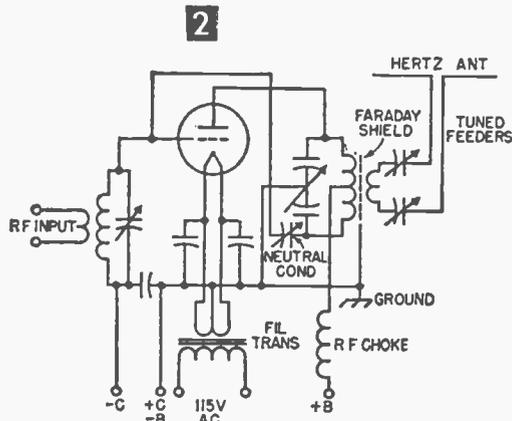


2

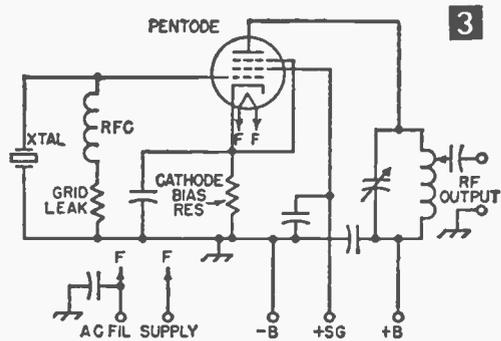


3

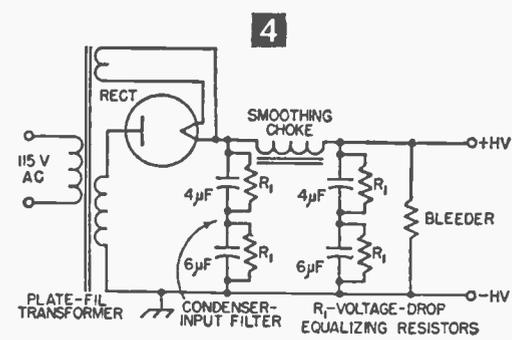


4

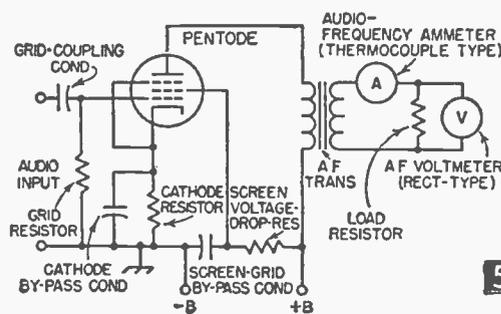

5

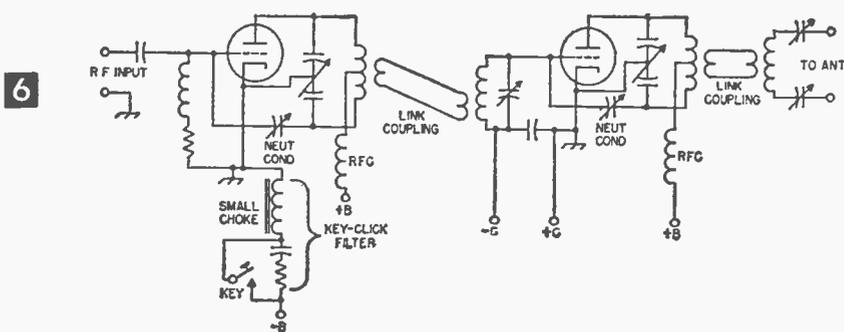

6

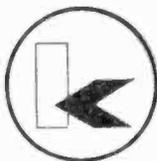

• Knight Tube Checker KIT REPORT

THE KNIGHT-KIT 400 tube checker is an excellent construction project—and it is the lowest priced cathode emission checker on the market.

The 400 tests for filament continuity, for short-circuits and for cathode emission. The most important of these tests is the cathode emission test. In this test full line voltage is applied between the control grid of the tube and ground through the meter. The resulting electron emission from heater to grid is measured, and this is assumed to be the same as if current from heater to plate (as occurs in actual tube use) were being measured.

Seven filament voltages are available on the unit, although in actual use a tube would require a specific filament voltage, of which there are at least a dozen in common use. Presumably there is no possibility of damage to the grid as the result of carrying line voltage during this test.


We ordered our test kit by mail. It arrived by parcel post, in a sturdy carton. The parts were well padded with corrugated, and all of the small parts were in polyethylene bags—screws in one bag, washers in another, and so on. Transformer, meter and wafer switch were individually boxed and padded. Resistors were mounted on a card, each of them

designated by a number, keyed to the instruction booklet. All hook-up wire was cut to the lengths required for the project. Instructions call for a certain color wire—that color is pre-cut to the right length, nine different colors, nine corresponding lengths.

Panel and case of the checker were of heavy-gage steel, well constructed, neatly and accurately punched to receive the four tube sockets, meter, load resistor and 13 slide

KNIGHT 400 TUBE CHECKER

- Checks cathode emission, shorted elements, filament continuity of 400 tube types.
 - Has sockets for 7-pin miniature, 9-pin miniature, octal and loctal-base tubes.
 - Meter has red-green "Replace-Good" Scale, special scale for diodes.
 - Slide-out metal drawer has flip-type tube charts in loose-leaf binding.
 - For operation from 110-125 v, 50-60 cycle ac; has "Hi-Lo" line-voltage compensator switch.
 - Carrying weight: 5¼ lbs.; size: 2¾ x 8 x 9½ in.
 - Allied Radio (100 N. Western Ave., Chicago 80) catalog # 83Y707. Price: \$19.95.
-

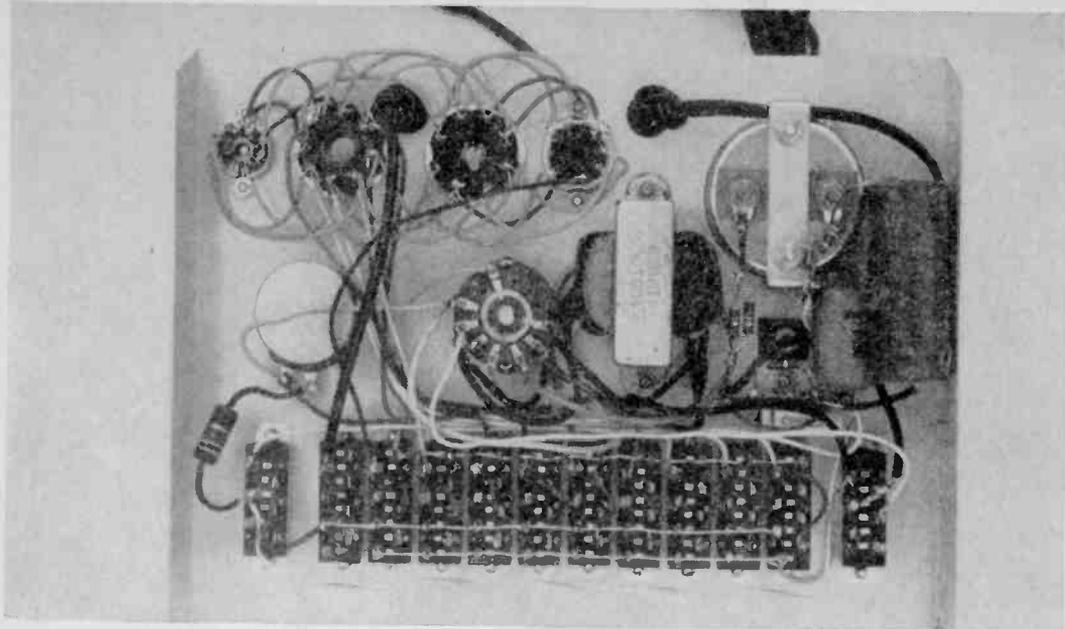

This underside view of the completed panel shows trim parts placement and design.

switches. The panel was handsomely enameled in white, grey and black; all dial markings were clear and distinct. The line cord appeared to be of good quality and plentiful solder was supplied.


Of the 25 tubes that we tested for cathode emission, all but three registered perfect on the meter—so perfect that the needle banged the meter housing in most instances. The tubes tested varied in age from two to 15 years. Of the three that did not register perfect, two registered zero, and were, indeed, burned-out. For one of the tubes that was

tested, an error in the flip-type tube chart data accompanying the checker caused the tube to test *shorted*. In testing for shorts in miniature tubes on this tester—as on all other testers—it is necessary to make each test as brief as possible to avoid the possibility of causing a short in the tube due to the relatively high voltage used in the test.


This kit makes an enjoyable construction project, and when used in conjunction with a tube manual, provides a good introduction to some of the ailments that beset tubes and the diagnosis of those ills.—H. SIEGEL.

Shield Spring for Soldering

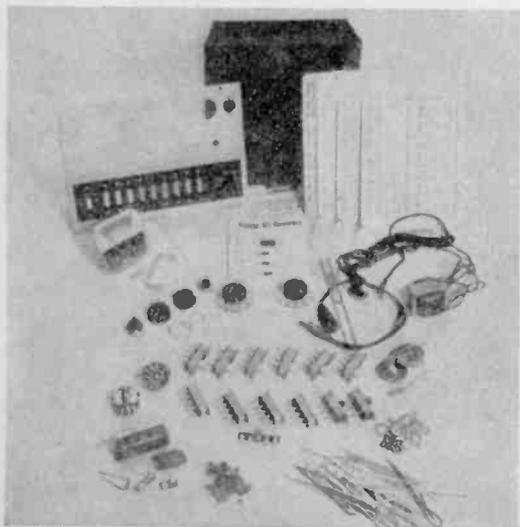• A spring removed from a miniature tube shield makes a handy gadget to hold parts or wires still while you solder them. By tacking the spring down to a scrap piece of wood as shown and clamping the work between the spring's turns, it makes a welcome partner for any electronic hobbyist's bench.—J.A.C.



The components of the tube checker.

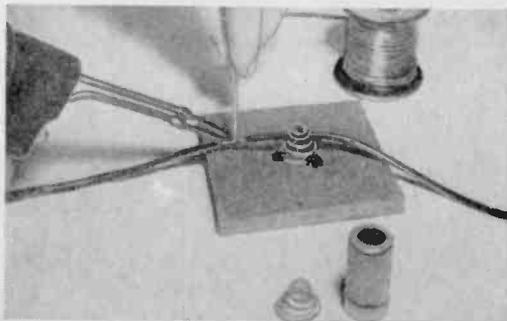

Loop Crystal Set

Just aim the loop at the station you want, and then enjoy yourself

By ARTHUR TRAUFFER







watt stations, no conventional antenna or ground is needed. The loop crystal set can be carried around playing, and used anywhere in the house; just aim the loop at the desired station.


Interfering stations, which are at right-angles to the desired station, can be greatly reduced in volume simply by pointing the loop at the desired station with the loop broadside to the interfering station. In some cases, a loop crystal set will prove to be more selective

IN THESE days of powerful transmitters, sensitive germanium diodes, and sensitive earphones, a loop crystal set for local stations is practical and sometimes a distinct advantage. For example, for those living within about 4 miles of 5,000 watt stations, and 5 or 6 miles from 50,000

than most crystal sets using a conventional antenna and ground, but don't expect the same sensitivity with a loop that you will get with a long outside antenna and a cold water pipe ground. A binding post on the side of the cabinet provides for an additional antenna for those living outside the range of the loop, and for those desiring to pick up more distant stations after the locals have signed off for the night.

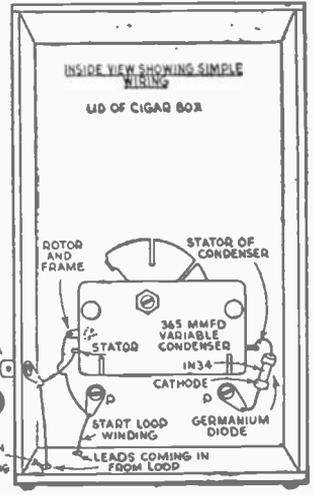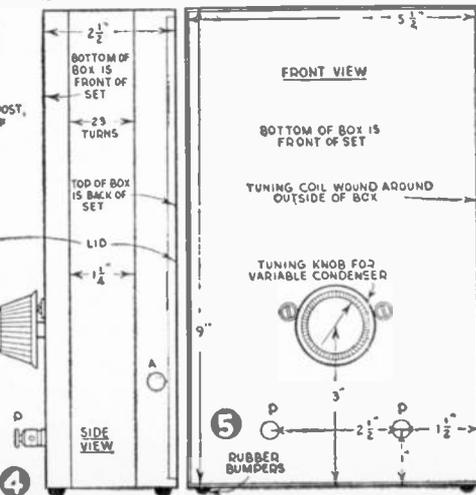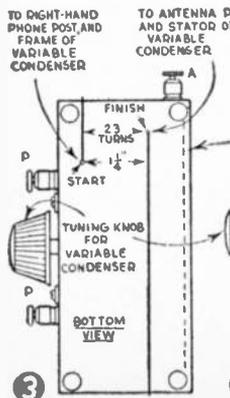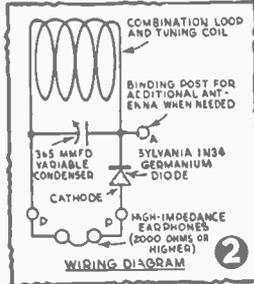
The extreme simplicity of this set is demon-



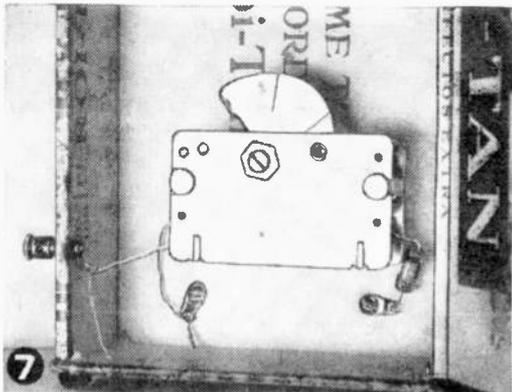

strated by the fact that the set shown (Fig. 1) was assembled and wired by a child under the supervision of the author.

This set differs from other crystal sets in that the tuning coil is wound around the outside of a cigar box to form a loop antenna (Fig. 2), instead of on a small Bakelite or cardboard tube inside the set. Figs. 5 and 6 show the simple layout for the 365 mmfd. variable condenser, the 3 post-type binding posts, or Fahnstock clips for the earphones, and the extra antenna connections. Fasten a soldering lug under the head of each binding post screw. Wind the loop, consisting of 23 turns of #24 gage enameled or double-cotton covered magnet wire, around the outside of the cigar box (Figs. 3 and 4). To start loop winding, connect to right-hand phone post (as seen from front view of set) and to variable condenser rotor and frame (Figs. 3 and 6). Then wind 23 turns clockwise around outside of box and connect the other end of loop

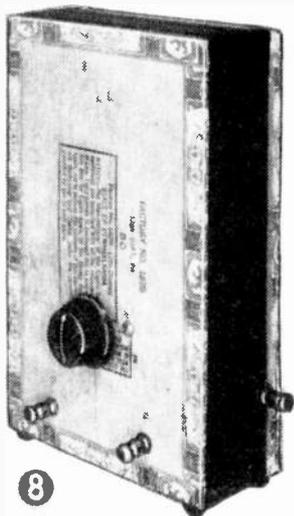

to antenna post and stator of variable condenser. The width of loop winding will be about $1\frac{1}{4}$ in. with the turns spaced the diameter of the wire apart. Connect germanium diode cartridge from another variable condenser stator lug to left-hand phone binding post (Figs. 6 and 7). Mount a pointer knob or a graduated turning dial, on the variable condenser shaft, and tack or glue 4 small rubber bumpers onto the bottom of the cabinet. The set is now completed (Fig. 1).


Wind a few turns of Scotch tape over the loop wires to protect the wires (Fig. 8), or brush a couple of coats of shellac over the loop wires. The writer tried shunting a small by-pass capacitor across the phone terminals, but no improvement was noted. This loop crystal set will give you slightly more volume indoors than outdoors, due to RF energy picked up by induction from the house wiring circuit. There will be some variation in signal strength in different parts of the room and different rooms in the house, due also to the house wiring circuit.

Glue a disc of heavy white paper or thin white cardboard onto the panel under the pointer knob on the tuning condenser so you can log your stations. When an additional antenna is used, however, the log will shift somewhat due to the added capacity introduced into the tuning circuit by the antenna. A water pipe or gas pipe connected directly to the antenna post makes a very efficient antenna for picking up distant stations. To obtain better results on distant stations connect a water pipe to the antenna post and use a bed spring as a counterpoise. Connect the bed spring to the right-hand phone post, which is the other side of the loop.

If you use a variable condenser larger than the one specified, you may have to remove 1 or 2 turns from the loop in order to cover the entire broadcast band. If you use a smaller capacity condenser you may have to add 1 or 2 turns to the loop. It is best to use a condenser not smaller than 365 mmfd., which is a standard size for the broadcast band. A little experimenting will give the desired results.

Auxiliary Auto Aerial

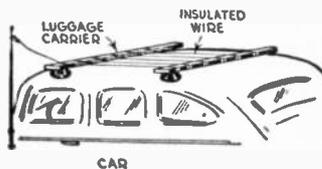• An auxiliary aerial for trips, when you are a way from broadcasting stations, can be added to your car radio if you have a luggage carrier on top of your car. String an insulated wire back and forth between carrier crossbars and attach one end to regular aerial with a small clip.—W. H. McCLAY.



MATERIALS LIST—LOOP CRYSTAL SET

- 1 $5\frac{1}{2}$ " x 9" x $2\frac{1}{2}$ " cigar box
- 1 365 mmfd. variable condenser, single gang, any good make. The one used by the writer was made by Insuline
- 1 Sylvania 1N34 germanium diode, or any other sensitive crystal
- 60 ft. No. 24 or 26 enameled or double-cotton-covered magnet wire
- 3 post-type binding posts or Fahnstock clips
- 3 soldering lugs
- 4 small rubber bumpers
- 1 Bakelite knob or tuning dial for $\frac{1}{4}$ " shaft

Draftsman's Tape Holds Tight

• Draftsman's tape makes an excellent "third hand" to hold electronic components together during assembly or soldering. Due to its high insulation, the tape can be left on permanently.

What Every Young Man Should Know—

About Printed Circuits

AS THE radio and TV industry turns more and more to the use of printed circuitry, the experimenter will eventually have to tinker with, or repair, such sets.

Figure 4 shows a popular four-tube superhet table receiver using a circuit that is more or less standard with the industry. Figure 5 shows a hand-wired set which employs the identical circuit. Note the confusion the latter presents compared to the neat underside of the set with the printed circuit board.

A printed circuit starts on the drawing board. First the positions and mounting holes for the individual components are determined, then a drawing resembling a modified peg board is sent to the tool and die maker who creates a punch and die set which will pierce the necessary holes in the panel of phenolic plastic.


Using a copy of the initial drawing, the draftsman next draws in a series of heavy lines connecting the various component holes. This drawing resembles a puzzle maze. Note in Fig. 4 that no paths cross each other on the underside

As more and more manufacturers turn to high-speed production, where radios almost wire themselves, you may wonder how it's done. Or worse—how it can be redone. Despair is changed to easy repair with these tips

By THOMAS A. BLANCHARD



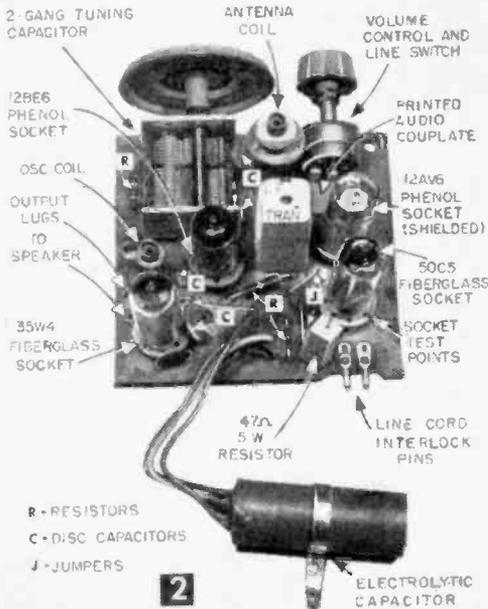Many printed sets are vertically mounted in cabinet and slide out for quick circuit repair. Note that a fine-tip pencil iron, not over 40 watts, is used to prevent wiring damage.




A typical "printed" circuit four-tube superheterodyne showing top of chassis. Note set is complete except for attachment of speaker and line cord. Strap of electrolytic capacitor is secured to a speaker mounting screw in cabinet.

of the board. Where a B- lead must cross a B+ path, a small wire jumper is inserted on the top of the board to complete the circuit.

The drawing is turned over to a photographer for copying. The photographer first produces a regular negative. This film is then printed on another film or reversed in development, to get a positive transparency. This positive copy goes to the silk screen printer.

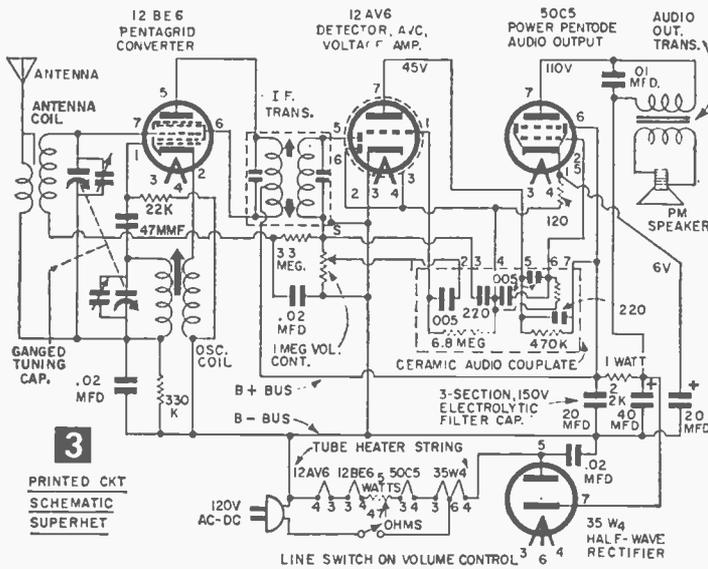The printer mounts a piece of fine Swiss silk in a printing frame, coats the stretched silk with a photographic light sensitive emulsion and al-




lows the silk to dry in the dark. Next the positive film is placed in contact with the sensitized silk and exposure made in a bright light, then the silk is developed just the same as a photograph.

Development creates the printed wiring image on the silk screen. The emulsion has washed out of the silk where maze lines appeared, the background has filled in solid. The silk screen is now mounted in a suitable press and a phenolic wiring board is placed underneath. A squeegee now passes over the silk screen forcing a special conductive paint through the tiny weave openings in the silk. When the silk screen is lifted the plastic panel bears an exact reproduction of the draftsman's original drawing.

The conductive paint is graphite in a suitable vehicle. Experimenters can purchase this paint in any radio parts house under the trademark "Tube Coat" (General Cement Div., Textron, Inc., Rockford, Ill.)

When the phenolic board has dried, it is transferred to a copper electroplating bath. Here a thin film of metal is deposited on the graphite paint, while the rest of the board remains blank. (In some instances the vapor vacuum plating technique is employed to deposit the copper, but the end result is the same.)

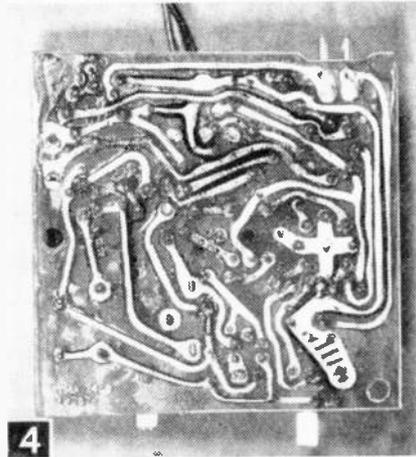The printed circuit is now finished. The plate may be buffed or blast-tumbled with sawdust to



4
A single dipping into molten solder secures all components to wiring board and establishes the printed wiring paths which resemble a puzzle maze.

the receiver is immediately ready for shipment to the dealer.

Servicing a printed circuit is easier than working on the old metal chassis construction. Hidden breaks in hookup wire have been eliminated. All wiring is in clear sight, moreover many circuit boards have voltage measurement points and other identifying data printed along with the circuit. Cold circuit joints are practically unheard of. Failure of the set will be in an easily accessible component located on top of the board.

In regular wiring, wafer sockets carrying rectifier and output tubes often char because of the intense heat such tubes produce. The printed circuits employ wafer sockets fitted with eight supporting pillars. Because the sockets provided for hot tubes such as the 35W4 and 50C5 are a fiberglass laminate, socket charring is eliminated.

polish the copper image. Next the board is fluxed and protected from damage at the same time by spraying with rosin dissolved in alcohol. The printed boards may now be moved on to the assembly department. The assemblers are sometimes human, but more often automat.

Resistors and capacitors in printed circuitry are identical to those used in usual radio assembly. Items such as coils are fitted with tubular pins instead of the spade type soldering lugs. Tubular pins replace lugs on IF transformers, tube sockets, etc. Since the wiring board has been punched, assemblers simply push each component into its proper position on the "peg board" layout.

With all components in place, the board is dipped into a tray (soldering pot) of molten solder consisting of 60% tin and 40% lead. It is removed immediately and given a momentary blast with a CO₂ (liquid carbon dioxide) gun which instantly sets the solder. In one fell swoop all parts have been rigidly secured to the wiring board and all connections and conductive paths completed.

There now remains only the matter of sliding the printed chassis into the cabinet, attaching knobs, and hand soldering the output transformer which is mounted on the speaker frame. Because of uniformity of design, tuning capacitor, oscillator coil and IF transformers are often prealigned so that

These pillars serve a dual function, since measurements can be made from the top of the socket without removing the tube from the set (see Fig. 2).

Most printed circuit receivers contain printed circuits within printed circuits. For example the complete resistance/capacitor network for the audio amplifier is contained in a small ceramic plate fitted with seven pigtail leads or soldering pins. A breakdown of a component in such a couplate or audet does not always require replacement of the entire unit unless the trouble is a short circuit. Locating the open capacitor or resistor, you need only jump it with a disc capacitor or small composition resistor as the case may be. Dotted area of schematic Fig. 3 shows the tiny couplate and its built-in components.


To replace a defective part on the circuit board, here is a simple and sure method: If a disc capacitor or composition resistor is involved, clip the pigtail leads as close to the component body as possible. Small diagonal wire cutters are the best tool for this. Because circuit boards may contain unused holes, and since some components contain more than two leads, apply a drop of nail polish or model plane dope to the wiring board prior to cutting out the defective part, to identify the holes from which the bad part is being removed. A toothpick makes a good applicator.

With the defective components removed, apply a pencil type soldering iron to the underside of the board and pull out the clipped pigtail from the top of the board with flat or needle-nose pliers. With all pigtails removed, the next step is to open the clogged solder holes in the printed circuit.

For this you'll need a metal probe to which radio solder will not adhere. One such metal is stainless steel. Now, while you can buy a probe for \$1 from any parts supplier, you can get six probes for a dime at your local hardware or dime store. These bargain probes are "Fowl Lacers" used to keep the stuffing in the Thanksgiving turkey.

Again applying the pencil soldering iron to the underside of the board, insert one of the stainless steel pins into the clogged hole and twist as the solder softens. Remove the iron and slowly remove the pin. A neat open hole is the result.

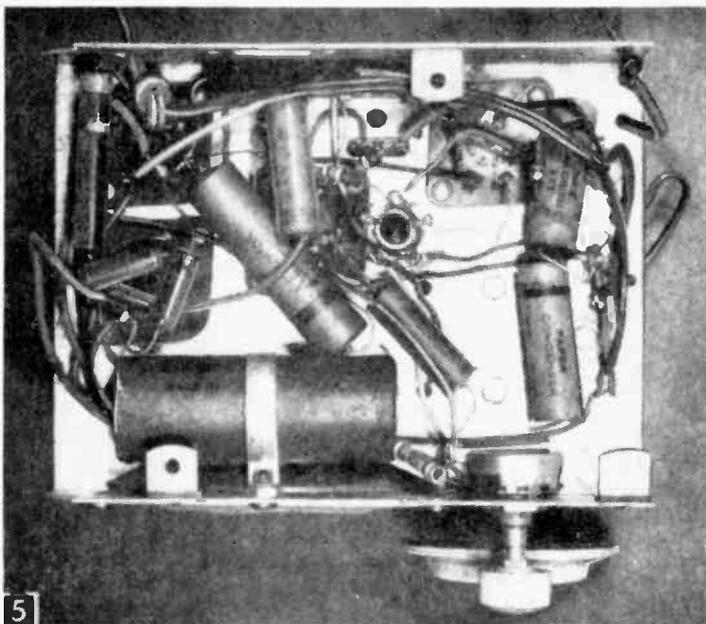With all holes cleared in this manner, you need only insert the new component and resolder the underside of the circuit board. Here a word of caution is in order. Do not use dime store solder, nor use a soldering gun, nor any other heavy-duty iron. You need a 60 tin-40 lead solder alloy



Underside of a four-tube set with hand-wired components and conventional metal chassis. Its circuit is identical to that of the printed set, but note the "jungle" of parts.

such as Kester's "Resin-Five" or Alpha's "Tri-Core." The iron should have a fine tip.

Since solder carries most of the current load in a typical printed radio circuit, you want to melt only the center of the circuit path. When a new part is being installed, hold the iron steady, allowing the solder to form a molten puddle at the joint. At this point, merely lift the iron away from the connection and allow the joint to cool while avoiding any jiggle of the component which could result in a "cold" bond.

Most printed circuits feature interlock cord sets such as are found on TV sets. This is to insure safety since all ground returns may be *live* except for the tuning capacitor and volume control shafts which are kept at a safe potential through a capacitor/resistor ground return. With so much exposed wiring, plus a direct ground on the IF transformer cans and detector tube shield, never work on line-powered sets on a metal table, or in rooms with concrete floors, since dangerous or fatal shock could result through carelessness.

When chassis is connected to line, be sure the bench or table is clear of small tools, wire, or solder. Such items shorting on the printed circuit can result in its utter ruin before the power line fuse has a chance to blow.

Removing Lock-In Tubes

- To remove a "Lock-In" or local tube with ease, push against the side of the tube with a thumb while pulling gently upward, so as to un-snap the locking arrangement. Sockets for these tubes have spring catches which prevent tubes from falling out during shipping or rough use in portable receivers.



Tune in on the World

By C. M. STANBURY II

THE development of radio has given us a wonderful medium for vicarious travel. However, the average listener hears only what his local AM, FM and TV stations care to broadcast. Only when you make full use of your equipment and ears does the *magic* dimension of radio come into play. Such application of ears and equipment is known as *DXing*—distant reception.

Via DX you can move throughout the country learning about people and happenings. The only price is patience and a reasonable amount of equipment and know-how. Your table radio will do for a start; once you decide what you want you may purchase or build more.

There is an element of skill in DXing. In 1920 the reception of KDKA Pittsburgh in New York was a feat. A few years later the same listener was shooting for the Pacific Coast and beyond. He didn't stop until the globe was circled, and today this same pioneer is tuning for the moon. There are as many challenges as there are bands. Colombia on the standard broadcast band is DX. On the short-wave band it's routine. If you saw it on your TV, you'd be one tremendous DXer. Table B shows all the bands of the radio spectrum. However, most of the dividing lines are purely arbitrary, one band shading into the next. Major exceptions are the medium-wave broadcast band and the FM and TV broadcast bands. Like conventional means of travel, each band has its own advantages. And for every individual personality, taste and temperament, there is at least one that is "right."

Early Broadcasting. Radio broadcasting became possible when De Forest invented the vacuum tube, although earlier there had been the dots and dashes of *spark-gap* transmitters. It was just one step from the vacuum tube to voice transmissions, broadcasting and KDKA. Both KDKA in Pittsburgh and WWJ Detroit claim the first broadcast, but KDKA was first licensed. With the licensing of these stations in 1920, the dash into broadcasting was on and radio's golden era had begun. The twenties were an era of newness for the sake of newness, and radio was of a piece with the era. It caught the public's fancy, and its continual expansion kept its fans enthusiastic, even rabid. Every radio listener was a DXer—even those with local stations to listen to hunted distant calls. Stations took on the character of their locale. Those like WEAf New York acquired sophistication, while rural broadcasters took on a neighborly air. A famous rural broadcaster was Henry Field's KFNF Shen-

endoah, Iowa. Field, realizing the great selling power of his battery-operated pioneer, transformed it into a general store of the air. "I don't know if they're any good but you try them out and let me know," he would say, and whether the product was dried prune or automobile tires, the entire shipment would be sold within 48 hours. The DXer was soon able to shoot for the West Coast, for in 1920 California boasted of KNX and KGER; Seattle, of KTW.

Like everything else in the Jazz Age, radio was wild. The Federal Radio Commission licensed, but the stations chose their own frequencies. Many stations tried several channels before settling on one, only to find that some nearby competitor was camping on the same wave-length. Station WHT in Chicago used two channels, switching from one to the other at 9 p.m. Adding to the complexity and confusion of the game were outlaw stations which were hard to trace. In 1928 the chaos was complete as the FRC was declared null and void. During that year every station did as it pleased.

Despite the anarchy, many stations were on the air to stay. In California, KNX, KFI, KGO, KLX, KYA, KMJ, KXO and KFSD; in Washington, KTW, KHQ, KJR and KGY; in Iowa, KFNF. Some of the eastern pioneers were Baltimore's WCBM, WGY Schenectady, WOR New York, WNAC Boston and WSM Nashville. Also founded in 1927 was the Newark News Radio Club, sponsored by the *Newark Evening News*. In 1928, Irving Potts, president then, as now, of the NNRC,

TABLE A—RADIO CLUBS

American Ionospheric Propagation Association, 360 Zimmerman Blvd., Kenmore 17, N. Y., Covers TV only.
 National Radio Club, 325 Shirley Ave., Buffalo 15, N. Y. Covers standard broadcast band only. Publishes *DX News* which is issued weekly during fall, winter and early spring. Annual dues are \$4.
 Newark News Radio Club, 215 Market St., Newark 1, N. J. Monthly bulletin contains sections on all branches of DXing. Annual dues are \$4.
 Universal Radio DX Club, 109 Mesa St., Vallejo, California. Devoted primarily to short-wave. Annual dues are \$4. Publishes *Universalife*, which includes experimental space section.

inaugurated a series of DX programs over WOR attracting widespread attention to the club.

The party was over in 1930. The nation had a king-sized hangover. The effect on radio should have been catastrophic, but it wasn't. Despite the fact that numerous stations went broke, radio hung on. For with a twist of the dial, a man could become top dog, champion. For a few hours the depression ceased to exist.

DXers competed in trying to log the most stations. Of the many radio clubs organized during this period only two remain: the National Radio Club and the Universal Radio DX Club. Normally, standard broadcast band (BCB) stations are not heard at a great distance, but on a morning in 1932 scores of night-owls heard a cricket match. Some logged it as *Poste Parisien* while others claimed it to be Rockhampton, Australia.

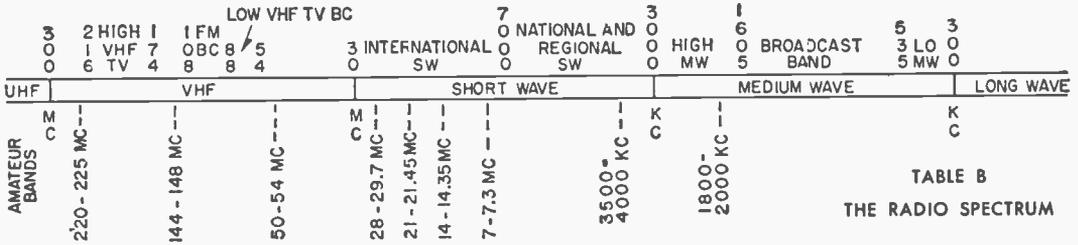


TABLE B
THE RADIO SPECTRUM

Verifications were received from both stations—at first Poste Parisien had been heard carrying a wire broadcast of the match. Later when the European station had faded out, Australia was heard with an on-the-spot description of the same match. When verification of reception established the validity of both sides' claims, the practice of collecting verification cards and letters became almost universal—the cards evidenced the listener's accomplishments and provided the souvenirs that every "tourist" collects. Completing the winter of 1932-33, DX's greatest season, the NNRC scheduled its second historic DX broadcast, a test from LR5 in Buenos Aires. It was a great success—every listener who tried heard LR5.

The Broadcast Band Today. DX permits you to escape the limits of your local stations. If you're a sports fan, the number of baseball, football and basketball broadcasts available to you will be tripled via DX. Those interested in American folk music will be trying for such stations as WAOK in Atlanta, Georgia. Most of the music played by WAOK is the folk or popular music of the southern Negro, sometimes referred to as rhythm and blues. Similarly, many stations such as WVOK Birmingham specialize in hillbilly tunes. When disasters occur, stations in the disaster area reflect the emergency. DXers are able to listen in.

Examples of broadcast band DX, and others, may be heard on an ordinary radio. Some BCB DX may be had around sunset and during the evening. The first period will produce brief reception from a large number of stations. This is accomplished by tuning to a channel used primarily by daytime stations and catching them as they sign off. Such a procedure will boost total of stations heard and verified, but it doesn't provide very interesting listening.

For best results you should listen between 1 and 6 a.m. Most stations are off during this period leaving four excellent sources of DX: 1) a number of stations operating all night and, because of the comparatively clear channels, easily heard at a distance; 2) stations further west which sign off later; 3) stations conducting equipment tests and frequency checks; 4) and stations which sign on before others of their channel.

A greater challenge is offered by attempting reception of foreign stations on the broadcast-band. BCBers have battled static, interference from U. S. and Canadian stations and ridiculously weak signals, to come up with such faraway locations as French West Africa, Russia and Aus-

This chart shows the frequencies allocated to all the commercial broadcasting media. From right to left, these allocations are: Standard Broadcast, 535-1605 kc.; National and Regional Shortwave, 3000-7000 kc.; International Shortwave, 7000 kc. to 30 megacycles; Very High Frequency Television, 54-88 mc. and 174-216 mc.; Frequency Modulation (FM), 88-108 mc. The Ultra High Frequency Television band begins at 473 mc., off the left side of the chart. Amateur band frequencies are also shown.

tralia. Best listening periods here are the early evening and after midnight. Ordinary receivers will usually not do—a communications type set is needed for best results.

International Broadcasting. Like the pioneer international wireless telegraphy, the first international broadcast stations used long-wave. The first was at Daventry, England on 187 kc. This station might compete with KDKA and WWJ as first broadcaster (however regular transmissions were not scheduled until 1922). The British Broadcasting Corporation attempted a North American service with the Daventry transmitter but reception was unsatisfactory.

Short-wave was known in the twenties but was not considered of practical use. In India and the islands which now comprise Indonesia, frequencies just above 3000 kc were used for local broadcasting. In this part of the world, static renders the broadcast band almost useless. Short-wave was carried on by experimental stations and culminated in a regular service by the BBC. Enhanced by the broadcasts of King George V, interest grew rapidly, enough to make it an unqualified success. Today, stimulated by World War II and world tensions, international short-wave broadcasting has greatly increased in scope. For more on this, see page 74.

International broadcasting plays a part in improving understanding among peoples. However, many short-wave services are carried on for political, religious or economic (sometimes an appeal to the tourist trade) reasons and are thus necessarily limited in depth and frankness. Similar to commercial broadcasting, there are both far-sighted and narrow-minded sponsors. As on the broadcast-band, you may use comparison but there are never two contrasting stations within the same country to compare. Thus, you can

TABLE C—BEST SEASONS FOR THE BANDS
Long Wave: Late fall and winter
Medium Wave: Fall, Winter and early spring
Short Wave: All year round
Very High Frequency (VHF) and Ultra High Frequency (UHF):
Late spring, summer and fall

TABLE D—VERIFICATIONS

In order for a station to verify your reception, you must give enough broadcast details so that your report can be checked. In reporting to *broadcast* stations, there must be a complete general description of the program heard. Much better than the general description, however, is the definite item system. Commercials, program name and announcer's name would all be definite items. Song titles will usually not do, however, since many stations keep no record of them. In verifying TV stations, visual descriptions are, of course, important. Always enclose return postage.

In reporting to *utility* stations you may *not* repeat specific details of communications heard. Instead, list date/time, frequency, station contacted or called and, in the case of a mobile facility, position if known. Many utility stations require the DXer to submit a prepared card for them to sign and mail back to him.

obtain a general picture of Europe or Asia but only a comparatively stilted view of individual countries and their people. You can get closer to a country by tuning in on programs intended for home consumption (usually below 7000 kc) or for nationals abroad. Unless you have command of a second language, however, you'll be limited to English-speaking countries. Another way of penetrating the gloss is by concentrating on programs featuring folk music. The imperfections of short-wave are countered by its availability—you can hear stations at any hour of the 24.

Police and Other Utilities. Broadcasting stations occupy only a tenth of the short-wave bands and only two-fifths of the medium-waves. With the exception of a few narrow amateur bands, the rest of the bands are assigned to *utility* radio services—ships, aircraft, airports, police and coast guard. This is the most potentially revealing of all radio listening. The authentic bits of life you overhear come straight. These are men going about the business of living, and you are a completely invisible observer. The aeronautical channels are a source of rare countries—8845 kc will produce such places as Kuwait and Bahrain, Arabia. Other faraway countries can be heard via aircraft passing over them.

VHF and UHF. Distant reception on medium-wave and short-wave is made comparatively consistent by the ionosphere, a layer of gases extending from 50 to 250 miles above the earth which are affected by ultra-violet radiation from the sun. The ionosphere reflects and refracts medium and short-waves back to earth thus making distant communications possible. As frequencies above 30 mc aren't normally reflected by the ionosphere, reception over 30 mc does not extend much beyond the horizon. Occasionally, however, DX is made possible via an upward extension of ionospheric effects, or special conditions in the troposphere. The long periods of nothingness punctuated by bursts of exciting reception give this brand of listening a flavor all it's own. For high-frequency DX you need the proper antenna—it should be the right length, directional, and mounted on a rotor. To find the proper length

for FM antennas see the article on page 136.

America's pioneer FM station, in Alpine, N. J., went on the air in 1938. The first commercial FM station on the air was WSM-FM in 1941, now off the air. Cultural offerings are standard on FM. FM, a high fidelity sound system, is ideal for the reproduction of classical music and this music is widely broadcast on FM. Because of the audience it attracts, other intellectual features such as literary reviews are made commercially feasible. During a DX opening you will have your choice of many stations.

Television. Almost simultaneous with the discovery of radio itself, men became fascinated by the prospect of transmitting pictures to distant points. The first commercial VHF TV station WNBT (now WRCA-TV) opened in 1941. Because of high production costs, most broadcasters



TABLE E—RECEIVERS

For best results on any band, a communications type receiver should be used. These are priced from \$75 up. The major manufacturers selling to the general public are as follows:


- Hallicrafters Company, 4401 West 5th Ave., Chicago 24, Illinois
- Hammarlund Manufacturing Co., 460 W. 34th St., New York 1, N. Y.
- National Company Inc., Malden 48, Massachusetts

These companies will furnish information upon request. When purchasing a receiver, these features should be considered: Frequencies covered and in how many bands (the more the better), sensitivity and selectivity, including crystal selectivity. (The latter is essential in foreign CCB DXing.)

stick closely to established program formula, as gambling or experimenting is too expensive. A few misses and the broadcaster would be out of business. Thus 95% of American TV stations have similar programming. The polish possessed by the CCB outlet does not compare to that of his video cousin. The DX results of this are unmistakable: In comparison with the other broadcasting forms, the number of DX viewers is small, only FM attracts less. The largest TV DX club has 100 members. While most DXers have at one time or another tried for a distant TV station, usually their interest has been only a passing one.

The European TV scene is in startling contrast to the North American. With numerous different nationalities and national customs in close proximity, DX is very popular and the number of such viewers far exceeds those on this side of the Atlantic. This is surprising when you consider not only the language barrier, but that four different TV systems are used in Europe—which means a DX viewer has to make numerous modifications in his set.

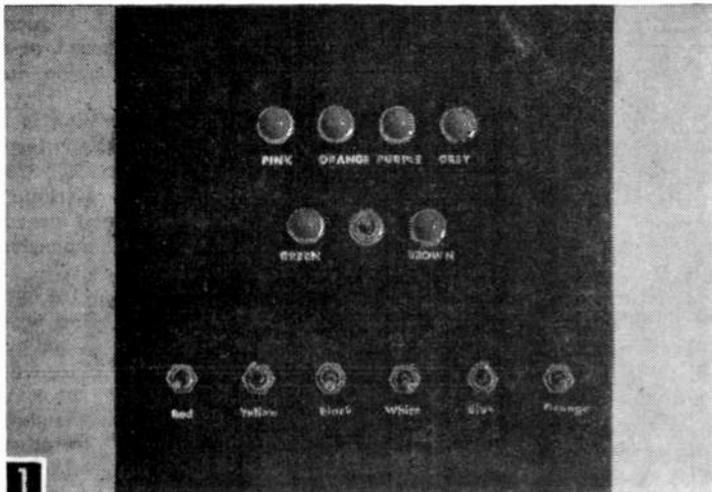Despite it's present inadequacies, TV's potentialities are obvious. The possible uses and human benefits are endless. DX-wise, the future holds unlimited promise. As technological advances multiply, such potentialities will convert an increasing number of DX listeners to DX viewers.



Electronic Color Wheel

By D. X. FENTEN and J. SCHACHNER

THE Electronic Color Wheel is entertaining, educational, inexpensive, and easily built. To light a lamp, two correct switches must be thrown. The lighted lamp is the color that would result if the colors indicated on the switches were mixed. If, for example, the *red* and *yellow* switches were thrown, the orange lamp would light. However, if two color switches are thrown that have no definite color combination, (*red* and *green*) nothing happens.

Single- and double-pole, double-throw toggle switches are used to build the color wheel circuit. The second throw on each switch is used to prevent improper readings in the event that more than two switches are closed. However, despite the fact that the DPDT switches are incorporated to prevent incorrect readings, they are not infallible. Errors can occur. By closing a few select special combinations of three switches, for example, a lamp can be lit.

Consider the situation when the *red*, *yellow*, and *blue* switches are closed. Normally, no lamp should light. However, when the *red* switch is closed, its "lo" contacts close, (see Fig. 2), applying ground to both wiper arms on the blue switch. In effect, this jumps out the red 2c contacts. If the *blue* and *yellow* switches are now closed, the *green* lamp will light. In this manner, an erroneous indication is given. The possibility of an erroneous indication can be overcome in either of two ways—expensive, complex circuitry, or following a simple set of rules of play. As:


Most commercially produced toys are either entertaining or educational, rarely both. Here's a toy you can make that is both, and inexpensive to boot.

- 1) Set On-Off switch to the Off position.
- 2) Set two color switches to the On position.
- 3) Set the On-Off switch to On. If the proper colors have been selected, the mixed color lamp will light.


How to Build. In a piece of 1/4-in. plywood, or other suitable material, bore all the holes necessary to mount the indicator lamp sockets and the toggle switches. Using the Fig. 3 layout as a guide for hole positioning, bore seven 1/2-in. holes to accommodate the toggle switches, and six 1 1/16-in. holes for the indicator lamp sockets.

Mount the indicator lamp sockets in the 1 1/16-in. holes so that all the terminals are aligned horizontally (see Fig.

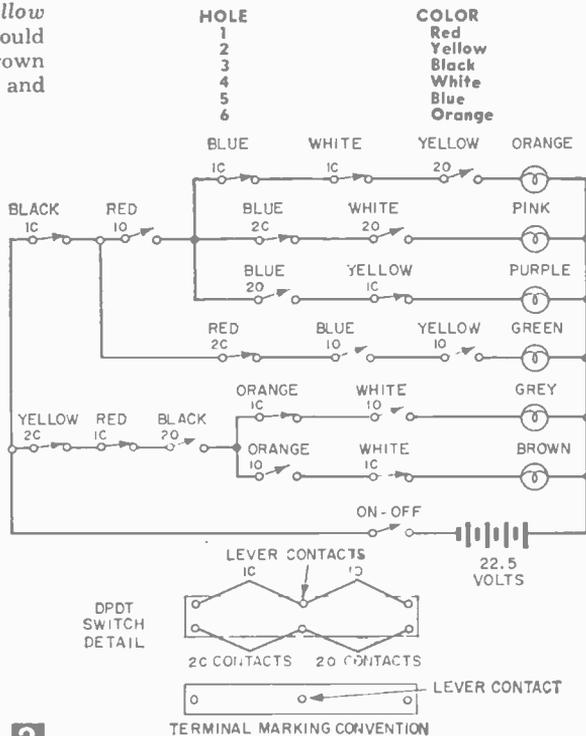4) to facilitate wiring. Mount the SPST switch in the middle row between the two lamps, the remaining switches in the six remaining holes on the bottom row. Reading from right to left, as in Fig. 2, the switches mount in this order:



2 SCHEMATIC

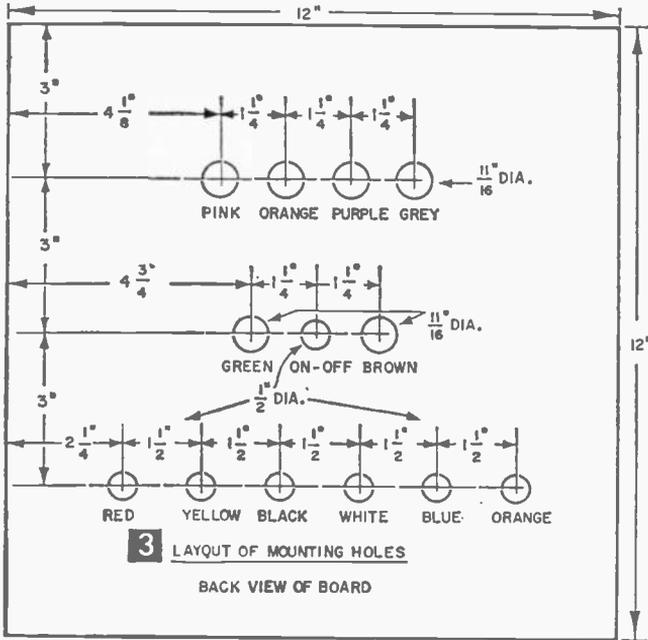

The switches, unlike the lamp sockets, mount vertically. This will place the "o" terminals on the top and the "c" terminals on the bottom, the "1" switch on the left, and the "2" switch on the right.

Now mount the battery on the lamp board. The mount will vary according to the size and type of battery used. Each of the many standard size battery holders has its own mounting

MATERIALS LIST—COLOR WHEEL

No. Reqd.	Description
1	1/4" x 1 x 1' plywood
6	DPDT toggle switches, without center Off position
1	SPST toggle switch
7	indicator lamp sockets and lamps
6	indicator lamp jewels of the following colors: orange, pink, green, purple, grey, brown.
1	battery (can be either of several normally available, but battery voltage and the required lamp voltage must be the same; 6-v. lamps and a 6-v. battery, 22.5-v. lamps and a 22.5 battery, etc.)


method, so a holder which is most easily installed should be used, or a home-made, improvised version designed and used.


The battery shown in Fig. 4 is a standard 22.5-v hearing aid battery. Simply mounted with two #6-32 x 3/4-in. screws and a strip of friction tape, it is easily replaced if necessary, and the mount is inexpensive and easily fabricated.

Solder the negative side of the battery to the On-Off switch and wire the 2c terminals of the red, yellow and black switches to the other side of the On-Off switch. Solder the common side of all the lamps to the positive side of the battery. The other terminal of each lamp is wired to the correct terminal of the color switches. When this has been completed, the control circuit—the switch terminals—is wired, completing the assembly.

Nothing remains but to turn a youngster loose on the wheel.

Wiring in the switches.

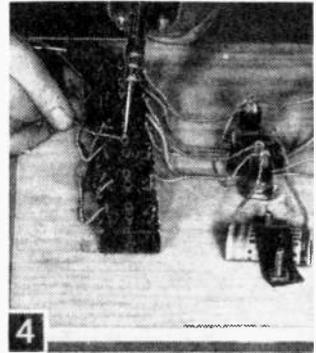

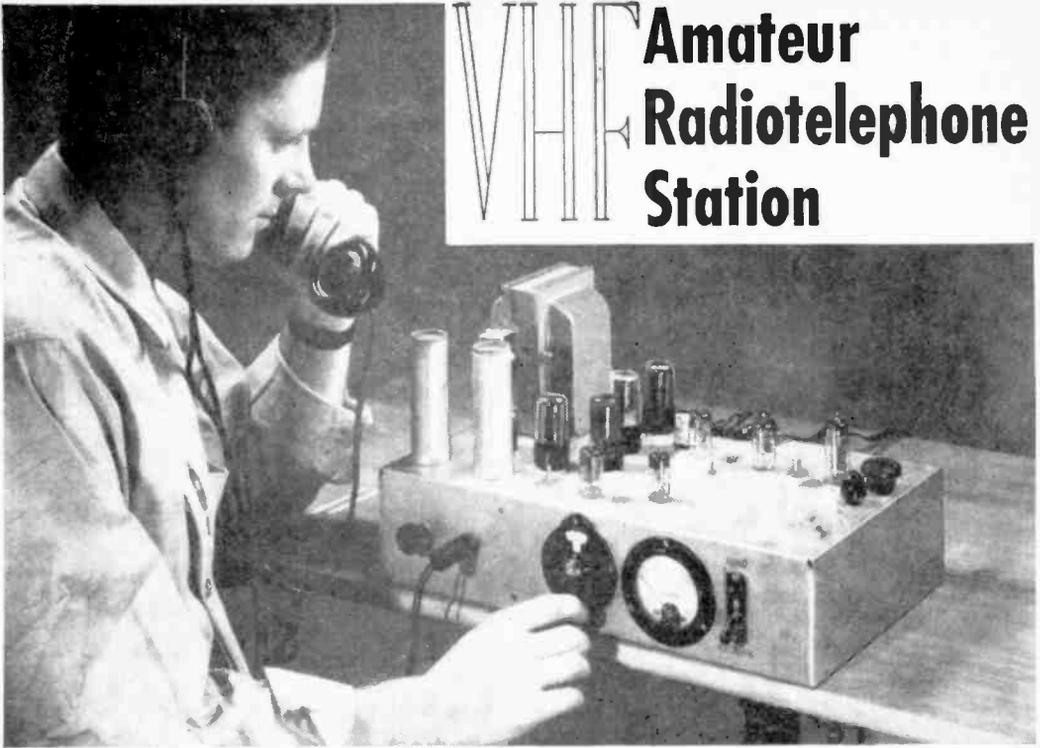

VHF Amateur Radiotelephone Station

By C. F. ROCKEY,
W9SCH

SELF-CONTAINED in a single chassis—except, of course, for antenna, microphone and headphones—this Very High Frequency transmitter-receiver operates in the 144 megacycle, two-meter amateur band. Probably as straightforward—and simple to construct—as a VHF station can be, its cost runs under \$60, less than one-fourth the cost of comparable, commercially made equipment. The receiver, tube for tube, develops maximum gain, has maximum sensitivity. It will easily receive signals from within and beyond the range of the transmitter; also, its efficiently engineered R.F. stage greatly reduces signal-radiation interference during reception. And, since all three stages of the transmitter are tuned to a different frequency, self-oscillation of a transmitter stage (with attendant off-frequency operation) is virtually impossible. No tricky “overtone” oscillator circuit, requiring hand-picked crystals, is used; no neutralization is necessary; there is no spurious signal output from the push-push final amplifier.


Construction of Power Supply and Receiver. On the 4 x 10 x 17-in. chassis, punch socket holes (Figs. 1 and 2) with $1\frac{3}{16}$ -in. dia. and $\frac{3}{4}$ -in. dia. socket punches (obtainable at electronics supply store) and mount the power trans-

The VHF amateur radiotelephone station in action. The operator is listening for an answer to a two-meter CQ.

former, rectifier tube socket, filter capacitors, filter choke coil, terminal strip, and volume control-power switch. (Mounting holes for the transformer are drilled from the data supplied by the manufacturer; tube sockets, filter choke and other station circuit components, except where otherwise indicated, are fastened to the chassis with 6-32 x $\frac{3}{8}$ -in. machine screws and nuts.)

Wiring for the power supply is shown in Fig. 3. (Figure 6 gives a pictorial wiring diagram for both receiver and transmitter sections.) Solder all connections with rosin core solder, checking connections at each step. When the wiring has been double-checked, connect a line cord to the proper terminals on the terminal strip (Fig. 1), insert the 5Z3 rectifier tube in its socket, plug the line cord into a power outlet and turn on the power switch. Now connect a d-c voltmeter from B+ to chassis; it should read between 300 and 400 volts. If it doesn't, check for faulty wiring or a defective tube and remedy or replace.

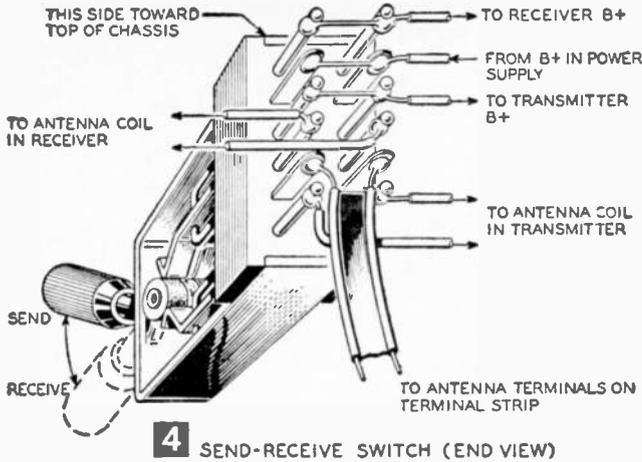With the power supply working, mount and wire the send-receive switch (mount according to manufacturer's instructions; see Fig. 4 for wiring), the receiver's 6AG5 and 12AT7 sockets (with rh 4-36 x $\frac{1}{4}$ -in. screws) and the sockets for the receiver section's two 6SN7's. Then mount and wire the receiver's main tuning capacitor's



4 SEND-RECEIVE SWITCH (END VIEW)

ter), keep all leads as short and direct as possible. A lead 1 in. long is considered short enough for ordinary broadcast and shortwave equipment, but at 144 megacycles it is far too long. Also, use a minimum amount of solder; use ceramic bypass and coupling capacitors; and establish one ground point for each stage, returning all chassis grounds for the stage to that point.

In Fig. 5, RFC1 designates an Ohmite Z-144 VHF R.F. choke, the plate load of the 6AG5 R.F. amplifier. The tuning coil in the 6AG5's


grid circuit consists of three turns of #14 tinned copper wire. Wind this coil on a 1/2-in. dia. form (we used a 1/2-in. drill shank) and then remove the form, leaving an "air-wound, air-spaced" coil. To properly adjust this coil, a grid-dip meter is needed. (With it, also align second detector to 29 megacycles.)

With the 6AG5 and the meter in the circuit (instructions for the use of the grid-dip meter are supplied by the manufacturer), spread apart or squeeze together the three turns of the coil until the meter indicates that the circuit is resonant to about 146 megacycles. For our receiver, this condition occurred when the coil was about 1/2 in. long.

Wind and adjust the coil in the grid circuit of the 12AT7 mixer in the same manner, but with both the 6AG5 and the 12AT7 in their sockets and all other connections properly made.

The small, home-made capacitor, labelled "Gimmick" in Fig. 5, consists of two pieces of ordinary hook-up wire (insulation left on) twisted together three times. It couples the signal from the oscillator to the mixer.

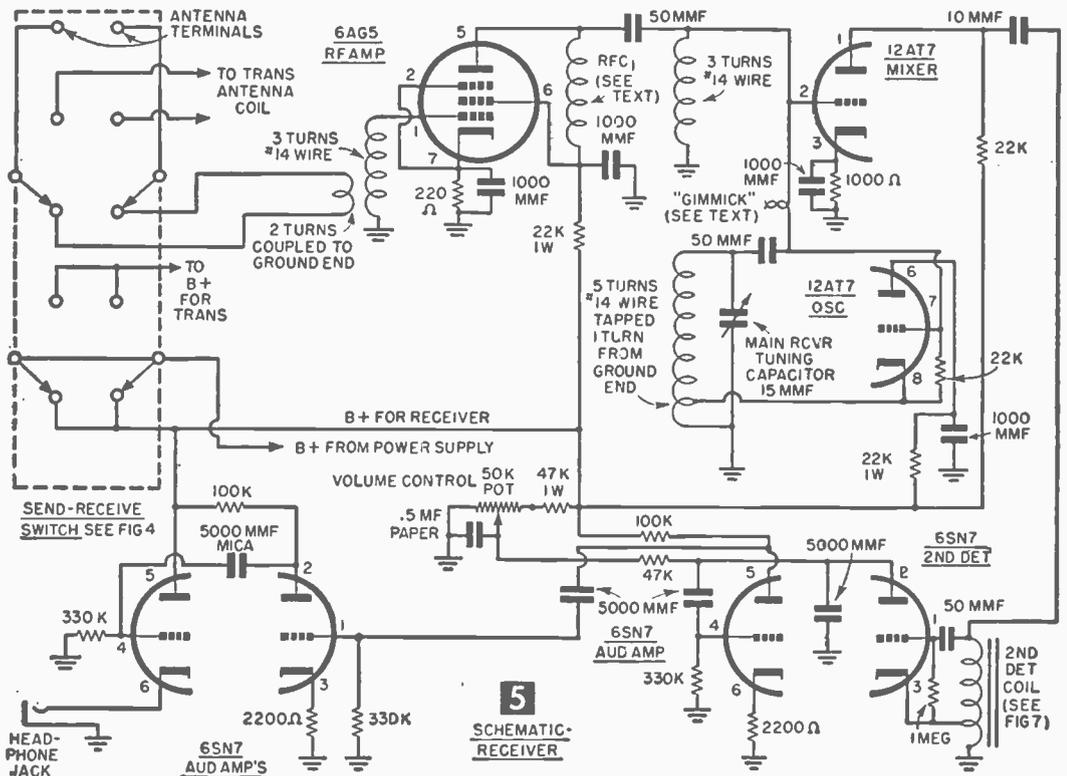
The oscillator coil consists of five turns of #14 wire wound as were the three-turn grid coils. The cathode lead from the oscillator sec-



5 SCHEMATIC-RECEIVER

6

LEGEND			
A- 10MMF	D-5000MMF	G- 47K	K- 330K
B- 50MMF	E- 2.2K	H- 100K	L- 1MEG.
C- 1000MMF	F- 22K	J- 220K	

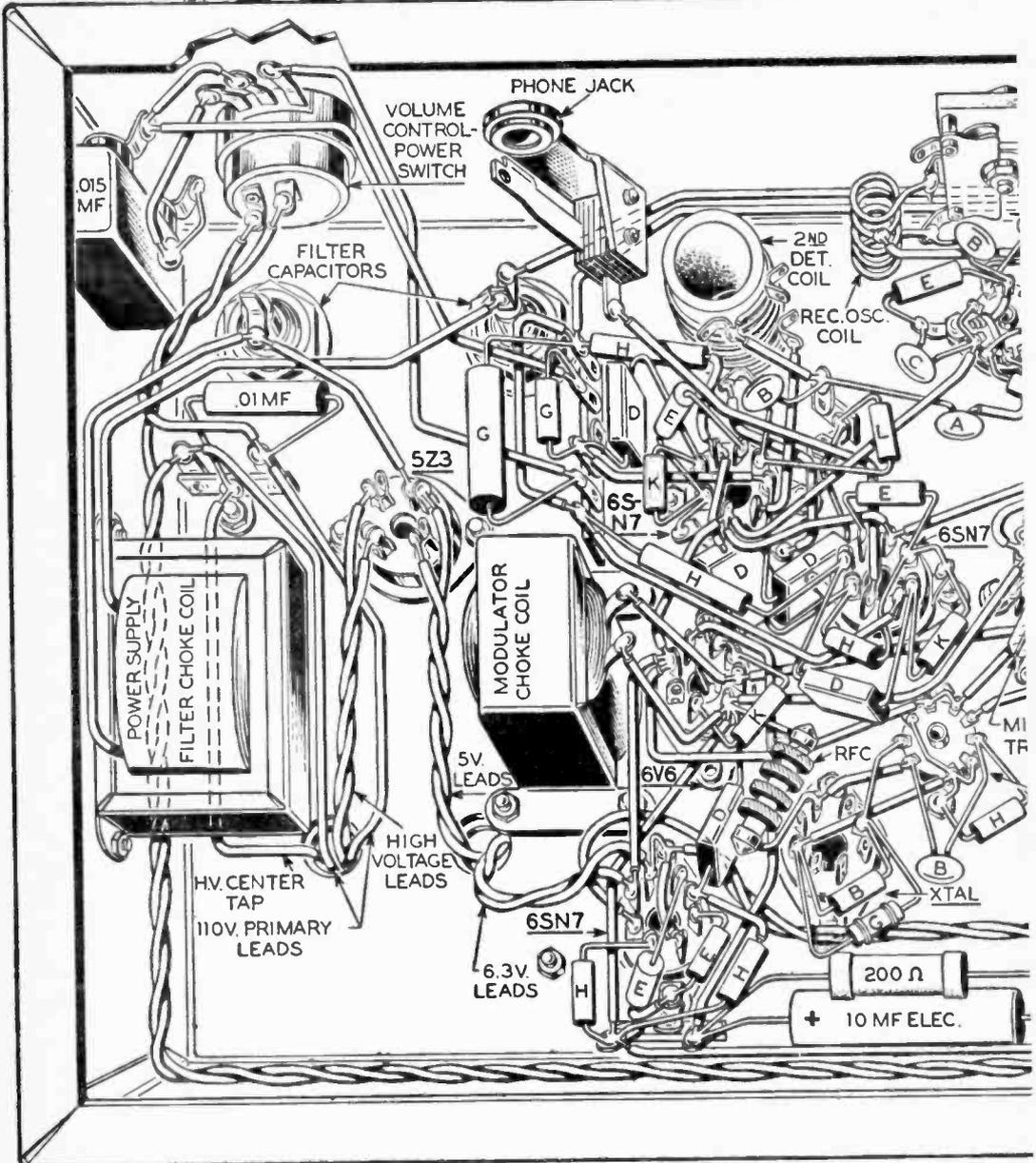


tion of the 12AT7 is soldered to the coil one turn from the ground end. When the R.F. amplifier, mixer and oscillator circuits are completed, apply power and throw the send-receive switch to the receive position. The tuning range for the oscillator, as indicated by a grid-dip meter, should be from within about 115 to about 132 megacycles. If the oscillator is not oscillating, look for shorts between tube pins or try a dif-

ferent 12AT7. If the oscillator's tuning range is incorrect, squeeze or spread the oscillator coil turns slightly until the correct range is obtained.

When the oscillator is working correctly, plug the headphones into their jack, adjust the volume control for a good, strong hiss, set the grid-dip meter for 145 megacycles and place it about 10 ft. from the set. Now tune the main tuning dial on

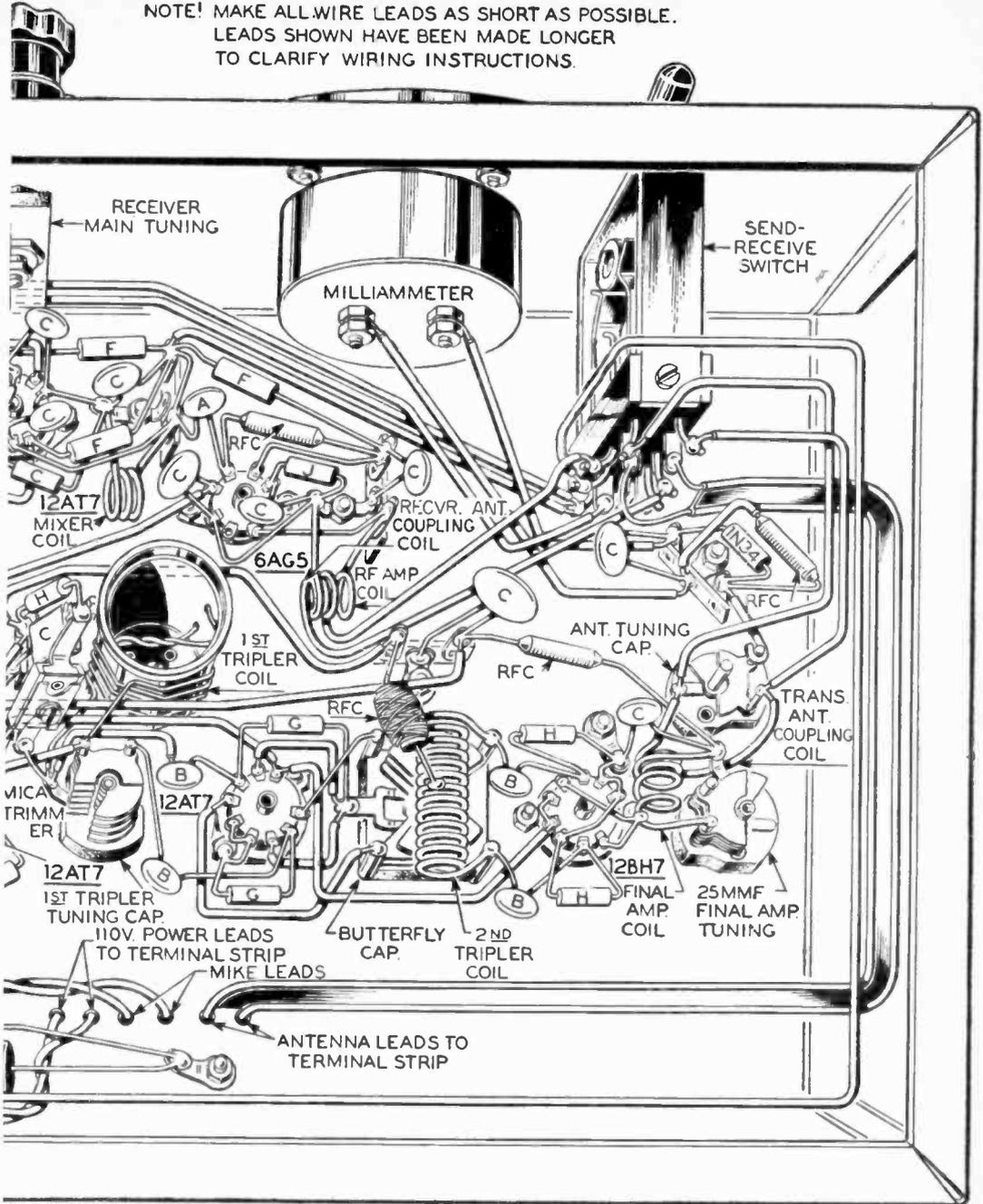NOTE! MAKE ALL WIRE LEADS AS SHORT AS POSSIBLE.
LEADS SHOWN HAVE BEEN MADE LONGER
TO CLARIFY WIRING INSTRUCTIONS.




the receiver throughout its range. At some point on the dial the hiss should disappear. Turning the grid-dip meter off should cause it to reappear. If it does, the receiver is operative. If it doesn't, you'll need to recheck the wiring in the mixer and R.F. amplifier circuits only; the oscillator has been checked.

For test purposes, couple a dipole antenna (see Fig. 8) to the 6AG5 R.F. amplifier grid coil

by means of one turn of wire inserted between the two turns at the ground end of the grid coil. With the volume turned up, tune the main receiver tuning dial through its range. If there are radio-equipped taxicabs, mobile radio telephones, or other 144-megacycle amateurs operating within range of you, you should hear them.

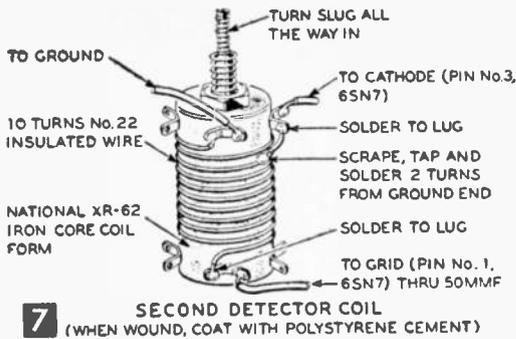Note that when a signal is tuned in, the hiss from the receiver tends to disappear and the



voice signal takes its place. The stronger the signal, the more completely the hiss will disappear. Slight readjustment of the volume control and slight retuning will often do wonders to clear up a weak signal.

Finish work on the receiver section by connecting the antenna coil leads of the 6AG5 directly to the appropriate connections of the send-receive switch (Fig. 4). Then run a short length of 300 ohm "twin-lead" TV lead-in line from the proper switch connections to the antenna terminals on the Jones terminal strip and connect antenna lead-ins to these terminals.

Construction of the Transmitter. Fasten tube sockets for the 12AT7's, 12BH7 and crystal (use 6-32 screws for the crystal socket, 4-36 for tube sockets) and mount the 50 mmf first-tripler tuning capacitor, the "butterfly" second-tripler tuning capacitor, and the 25 mmf final amplifier tuning and antenna tuning capacitors. Be sure that the 50 mmf and the 25 mmf capacitors are mounted with shafts insulated from the chassis. (Drill the shaft hole large enough to give the shaft ample clearance.)

First wire the crystal oscillator (see Figs. 6 and 9), wiring to any two *alternate* pins desired on the crystal socket. In the oscillator's plate circuit, RFC2 (Fig. 9) designates a National R-100 2½ mh R.F. choke.

Choose your crystal frequency according to the class of amateur license you hold. If you hold a general class license, any crystal frequency between 8.000 and 8.210 megacycles will do. If you are a novice, choose a crystal frequency between 8.032 and 8.132 megacycles.

When the crystal oscillator circuit wiring is completed, plug the crystal into the socket pins that are connected to the oscillator circuit. Apply power and throw the send-receive switch into the *send* position. Now, *holding it by its glass envelope*, touch the base of a 2-watt neon bulb to the plate connection (pin #1) of the 12AT7 oscillator tube. A faint but definite bluish-red glow of the neon bulb indicates satisfactory operation of the oscillator circuit. If no glow is observed, recheck the wiring or substitute a different crystal.


Next, wire the first tripler circuit. The first tripler coil is wound as shown in Fig. 10.

With the first tripler wired, apply power and

set grid-dip meter to about 24 megacycles. Hold the grid-dip meter coil near the tripler coil and adjust the 50 mmf capacitor until maximum output from the tripler is observed on the meter. This adjustment must be made with an *insulated* screwdriver to avoid shocks and to insure accurate tuning.

When a good, strong indication is secured on the grid-dip meter, insert the loop of the transmitter tuning lamp (see Fig. 11) into the first-tripler coil with the loop of the lamp parallel to the turns of the coil. When the lamp is inserted all the way into the coil, and the 50 mmf capacitor is readjusted for maximum tripler output, a noticeable glow of the lamp filament should be observed.

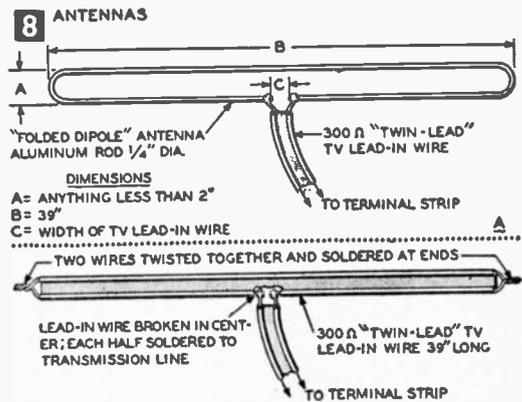Now, wire the second-tripler 12AT7. The second-tripler coil consists of 12 turns of #14 tinned copper wire wound on a ½-in. dia. form. Space the turns carefully to make the entire coil about 1¾-in. long, then remove the form. Connect this



A is superior for outdoor installations.

B is suitable for indoor or temporary use.


RULES FOR ERECTING ANTENNA

- (1) Keep it horizontal.
- (2) Keep it broadside to the directions you wish most to work.
- (3) Erect it as high above ground as possible.

coil between the two stationary sets of plates of the "butterfly" capacitor. Keep leads as short as possible.

The R.F. choke (RFC3) connected to the center tap of the second-tripler coil is made by scramble-winding 100 turns of magnet wire equal to or smaller than #22 around a 1 megohm, 1 watt carbon resistor. Solder the ends of the coil to the resistor leads, dope liberally with polystyrene cement, and solder RFC3 into the circuit.

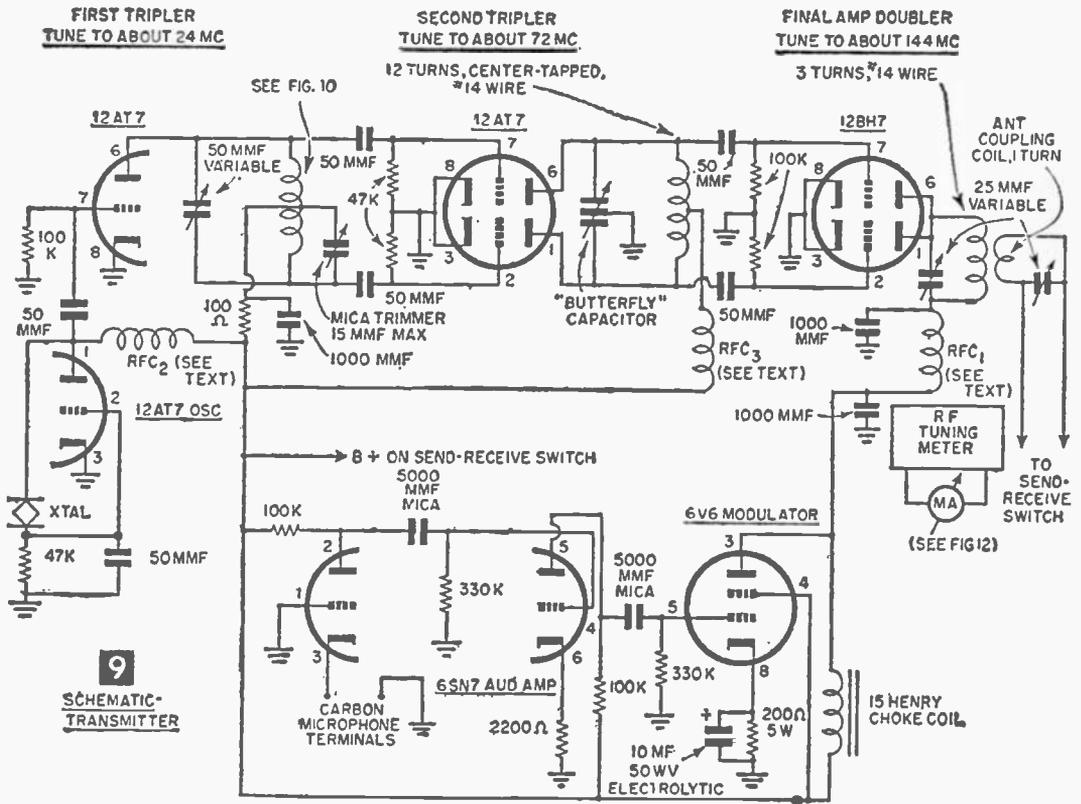Insert the 12AT7 in its socket and apply power. Tune the grid-dip meter to about 72 megacycles and adjust the "butterfly" capacitor for maximum second-tripler output. Then insert the loop of the tuning lamp between the middle turns of the second-tripler coil and readjust the "butterfly" capacitor for maximum second-tripler output. Then, using an insulated screwdriver, read-



9
SCHEMATIC-
TRANSMITTER

just the first-tripler 50 mmf tuning capacitor until the tuning lamp (still in the second-tripler circuit) glows brightly. Now, adjust the first-tripler 15 mmf mica trimmer capacitor and the first-tripler 50 mmf tuning capacitor alternately, until the tuning lamp glows at nearly full brilliance.

The final stage of the transmitter's R.F. section to be wired is the push-push doubler final amplifier. It operates at the output frequency of 144 megacycles, so make every lead as short as possible. The final-amplifier tank coil consists of three turns of #14 tinned copper wire 1/2-in. in diameter. Space out the turns until the length of the entire coil is about one in., remove the form, and connect the coil across the final amplifier tuning capacitor. Keep leads to minimum length.


When the final amplifier is completed, tune the grid-dip meter to about 144 megacycles, insert the 12BH7 tube in its socket and, after the tube has heated, apply B+ by throwing the send-receive switch to *send*. Using the insulated screwdriver, adjust the 25 mmf final-tuning capacitor for maximum indication on the grid-dip meter and readjust the "butterfly" capacitor for maximum output at the final amplifier. Then insert the tuning lamp between the turns of the final amplifier coil. It should gleam brilliantly.

Finally, wire the audio amplifier and modulator. (RFC1 designates an Ohmite Z-144 VHF R.F. choke.) To test the audio amplifier-modu-

lator system, temporarily replace the 15 henry choke coil in the modulator plate circuit with the primary of any loudspeaker output transformer and loudspeaker. With the microphone connected and the send-receive switch in the *send* position, speaking into the microphone should produce a loud, clear signal from the loudspeaker.

Now insert a single-turn antenna coupling coil into the final-amplifier tuning coil at the end farthest from the 12BH7 socket. Push it well down into the final-amplifier coil to obtain tight coupling and run its leads directly to the 25 mmf antenna tuning capacitor. From there, run leads directly to the proper terminals of the send-receive switch (see Fig. 4).

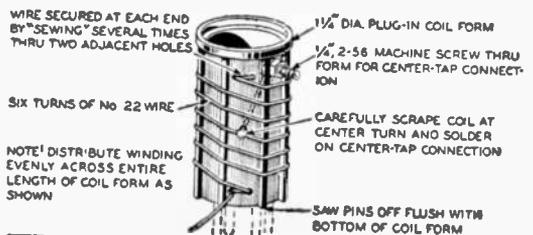Give the entire transmitter a final test by connecting a #48 dial lamp bulb directly across the antenna terminals on the terminal strip. With every component in the circuit and with the




10 FIRST-TRIPLER COIL

send-receive switch in *send* position, the lamp should glow brightly. Touch-up the various tuning adjustments for maximum brilliance of the lamp and then speak clearly and directly into the microphone. The lamp should flicker noticeably, indicating that modulation is taking place.


MATERIALS LIST—AMATEUR RADIOTELEPHONE STATION

- | | |
|--------|---|
| | Receiver and Power Supply |
| Req'd. | |
| 1 | 10 x 17 x 4" aluminum chassis |
| 1 | knob, 1/4" shaft |
| 1 | terminal strip, 6 terminal (Jones barrier 6-140) |
| 6 | 8-prong sockets (Amphenol type MIP) |
| 4 | 9-prong sockets (Amphenol, 59-410) |
| 1 | 7-prong miniature socket (Amphenol, 147-505) |
| 1 | power transformer (Stancor type PC-8410 or equivalent) |
| 1 | filter choke coil (Stancor type C-1001 or equivalent) |
| 2 | can type electrolytic capacitors, 16 MFD 450 v.w. (Cornell-Dubilier, Type KR-516A or equivalent) |
| 1 | single circuit phone Jack |
| 1 | Vernier dial, 0-100-0 scale (National type BM) |
| 1 | 4PDT anti-capacity switch (Federal #1424) |
| 1 | 50K linear taper potentiometer, with switch (50,000 ohms) |
| 1 | pair 2000 ohm headphones (Trimm "Dependable" or equiv.) |
| 1 | phone plug |
| 5 ft. | power line cord with plug |
| 1 | .01 mf, 400 volt paper capacitor |
| 1 | Ohmite Z-144 R.F. choke |
| 8 | 1000 mmf disk type ceramic capacitors |
| 8 | 50 mmf disk type ceramic capacitors |
| 1 | 10 mmf disk type ceramic capacitors |
| 1 | 1000 ohm, 1/2 watt composition resistor |
| 1 | 220 ohm, 1/2 watt composition resistor |
| 1 | 100K ohm, 1/2 watt composition resistors (100,000 ohms) |
| 1 | 47K ohm, 1 watt composition resistor (47,000 ohms) |
| 3 | 47K, 1/2 watt composition resistors (47,000 ohms) |
| 2 | 22K, 1/2 watt composition resistors (22,000 ohms) |
| 2 | 22K, 1 watt composition resistors (22,000 ohms) |
| 5 | 330K, 1/2 watt composition resistors (330,000 ohms) |
| 3 | 2200 ohm, 1/2 watt carbon resistors |
| 1 | 100 ohm, 1/2 watt carbon resistor |
| 1 | 1 meg., 1 watt carbon resistor |
| 1 | 0.5 mf paper capacitor |
| 6 | 5000 mmf mica capacitors, "postage stamp" type ceramic, iron core coil form (National type XR-62) |
| 1 | 15 mmf midget variable capacitor (Hammarlund type HF15 or equivalent) |
| 1 | 5Z3 tube |
| 2 | 6SN7GTB tubes |
| 1 | 12AT7 tube |
| 1 | 6AG5 tube |
| 25' | #14 tinned copper wire |
| | hook-up wire, solder |
| | tube polystyrene cement |
| | tiepoints |
| | screws |
| | miscellaneous hardware |
| 10" | 300 ohm twin lead TV antenna lead-in wire |
| 12" | #22 insulated magnet wire |
| | antenna materials, as desired |
| | Transmitter |
| 2 | knobs, 1/4" shaft |
| 1 | choke coil (Stancor type C-1002 or equivalent) |
| 1 | 0-1 milliammeter (Triplett) |
| 1 | 0.5 mf, 200 v. paper capacitor (Sprague or equivalent) |
| 1 | 10 mf, 50 v. electrolytic capacitor (Sprague or equivalent) |
| 2 | Ohmite type Z-144 VHF RF chokes |
| 1 | 2 1/2 mh RF choke (National R-100) |
| 1 | 1/4" ribbed plastic coil form (ICA) |
| 3 | 25 mmf midget variable capacitor (Hammarlund type APC 25 or equivalent) |
| 1 | 50 mmf midget variable capacitor (Hammarlund type APC 50 or equivalent) |
| 1 | "Butterfly" type midget variable capacitor, 10 mmf per section (Johnson 11MB11) |
| 1 | 1 1/2-15 mmf mica trimmer capacitor |
| 1 | 1N34 crystal diode |
| 1 | quartz transmitting crystal, about 8 megacycles, see text (Petersen radio "PR" type Z2 or Biiley type AX-2) |
| 1 | 6SN7GTB tube |
| 2 | 12AT7 tubes |
| 1 | 12BH7 tube |
| 1 | 6V6GT tube |
| 2 | #48; 2 v., 60 MA dial lamps |
| 1 | 2 watt neon bulb |
| 1 | single-button, telephone-type microphone |
| 1 | 2-lug tiepoint |

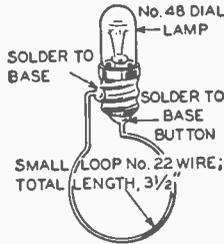The R.F. output meter (Fig. 12) assures proper tuning of the transmitter under all conditions. Fasten the 1N34 crystal diode, the RFC1 choke (an Ohmite Z-144) and the 1000 mmf capacitor to a two-lug tiepoint strip mounted near the transmitter antenna tuning capacitor. The 1 1/2-in. pickup lead should be brought within about 1/2 in.



11 TRANSMITTER TUNING LAMP

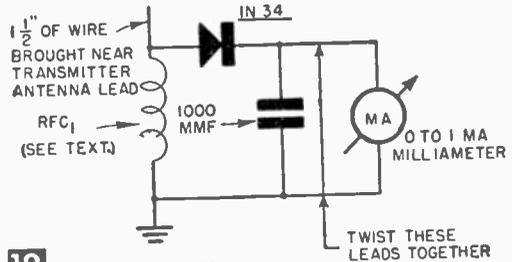

12 RF TUNING METER


of the transmitter 25 mmf antenna tuning capacitor and a twisted pair of wires run to the 0-to-1 milliammeter on the front of the chassis. Apply power, and throw send-receive switch to *send*. If the meter reads backwards, reverse the leads to it. Position the pickup lead so that when


the transmitter is operating and the antenna is properly loaded the meter reads about mid-scale. The transmitter may now be easily adjusted by tuning for the greatest meter reading.

Connect the transmitter to one of the antennas shown in Fig. 8, put the antenna as high and in the clear as possible and you're ready to go on the air. With a dipole antenna 25 ft. high, your range of communication will be around 10 miles; with a dipole antenna 50 ft. high, it will be about 15 miles; 100 ft. high will get you out 20 miles. With a high-gain directional antenna system, you can get out in excess of 100 miles under special atmospheric conditions.

Weatherproofing TV's Lightning Arrestor

• Does your TV picture get snowy nearly every time it rains? If your TV's lightning arrestor is located outdoors where it is exposed to the elements, signal loss may result when the arrestor becomes covered with rain. To prevent this, install an arrestor in a plastic box with a tight-fitting lid. Cut holes in the side of the box to accept the lead-in wire; drill holes in the bottom to fit the arrestor's mounting screws.—JOHN A. COMSTOCK.

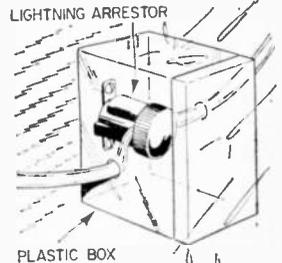

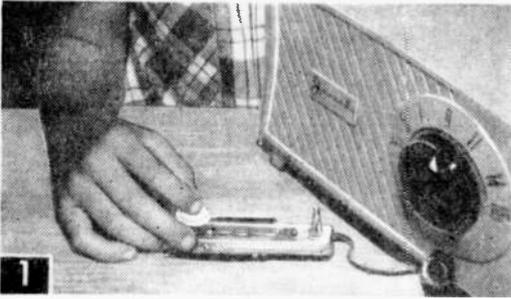

Press the key, and the signal plays through the radio speaker. When plug connecting accessory oscillator is removed (not shown in photo) radio functions normally.

Loudspeaker Code Practice Oscillator

For 50¢

Stealing power from a superhet radio, and playing through the speaker, this unit will also double as a tone generator

ONLY two main parts, a neon lamp and a resistor, plus the key and plug, are all that you need to build this oscillator. Not only is it handy for code practice, it also provides two full octaves of tone, for testing and experimental purposes.

The oscillator's operation is based on the neon glow relaxation circuit, principle of which is shown in Fig. 2. Such a circuit, while it has been popular for years, requires many more parts, and provides only earphone volume and tone. Our circuit (Fig. 3) actually drives a loudspeaker with lusty volume.

The minimum 90 volt d-c current required to excite the neon glow lamp in the oscillator circuit is obtained from the plate lug of the output tube of any small ac-dc radio. The other lead of the oscillator is connected to the first diode of the radio's detector tube. Since this diode is also the input of the voltage amplifier, the weak oscillator signal is therefore automatically amplified by the set's two audio stages and reproduced by the speaker. The wiring plan (Fig. 3) shows how to make the connections to the tube sockets of most popular radio sets. If you want to use an

MATERIALS LIST—CODE PRACTICE OSCILLATOR

No. Reqd.	Description
1	NE-2 Neon Lamp
1	220,000 ohm 1/4 or 1/2-watt composition resistor
1	3 5/8" long, 3/4" wide, 3/8" deep plastic box
1 pc.	spring brass, steel, etc.
1	7/8" dia. plastic garment button
4	3-48 x 3/8" long rh machine screws and nuts
1	subminiature phone plug & jack (Lafayette MS-281 & 282)

earlier model receiver, simply check the respective diode and plate pins of the input and output tubes on a tube chart, and connect according to the tube base outlines.

The miniature phone plug and jack allow the oscillator to be connected to the radio set at will. When the plug is removed from the jack, the set again functions in normal fashion. Leads from the tube sockets to this jack should be as short as possible, and the jack must be fully insulated from the metal chassis of the radio, or a short circuit will result. On some sets, you may find that the hardboard back, to which the loop antenna is attached, is a convenient place for the jack, or drill a hole in plastic cabinet.

As a novelty, the code practice oscillator shown in Fig. 3, was built into a small plastic box, such as is used to package emery boards. The key was homemade of spring brass. The serious radio amateur practicing code for license examinations is advised to use a conventional type of sending key, since the "feel" of a solid key under the hand is important in learning speed.


Drill a hole in the plastic just large enough to pass the NE-2 neon glow lamp, cementing it in place with Duco cement. Shape the key by bending a strip of spring brass according to the plan.

The knob is a 7/8-in. dia. garment button.


The tone of the oscillator is determined by the setting of the receiver's volume control. If the key is held down, and the volume control rocked back and forth, an electronic siren effect will result.

If, instead, you alternately close the key, and vary the volume control setting, a musical tune will result, much in the manner of the "Uke-A-tron." This is an electronic musical instrument, described in S&M Radio-TV Experimenter, Volume 3 (#538—50 cents). And it demonstrates the basic principle of electronic organs.

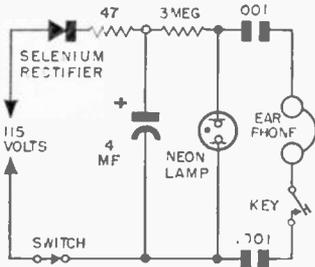Another interesting feature of the relaxation oscillator is that it not only provides an audible signal, but also a visual signal. Every time the key is pressed, the lamp fires with a bright orange glow.—
THOMAS A. BLANCHARD




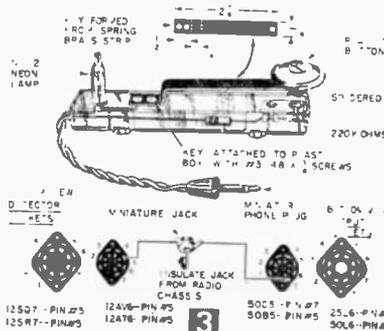2 SCHEMATIC DIAGRAM (TYPICAL RELAXATION OSCILLATOR CIRCUIT)




Sound Down

By BERNARD DICKMAN
and
ALFRED LUCAS

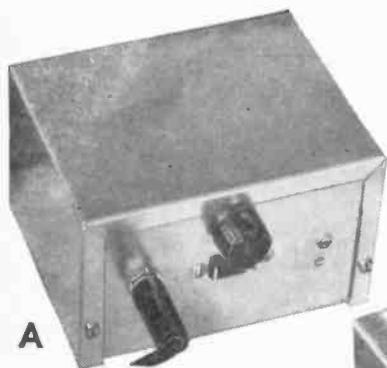

A

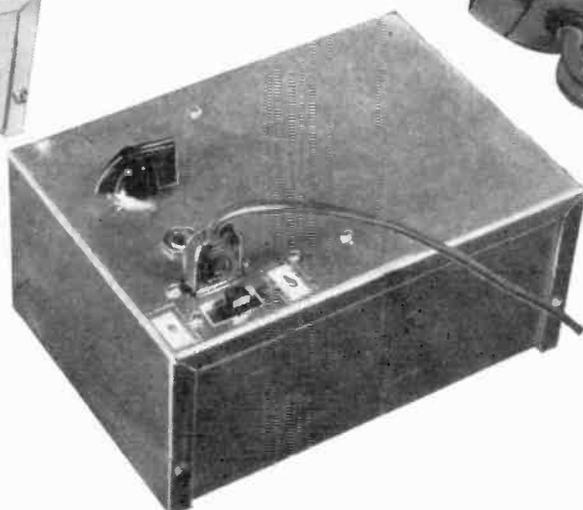

B

Micro-switch mounted at back of phone cradle controls sound dimmer on either version one (A) or two (B) of sound-down unit.




1

Below, parts placement in Version One.


HERE'S a device which will automatically turn down the sound on your television or radio set when you lift the telephone receiver. There are two versions, one of which can be built for less than \$10, the other for less than \$15. The first version (Fig. 1A), while it is the less expensive of the two, draws current from the battery all the time the telephone is in use. The second version (Fig. 1B), will draw current only the moment the telephone is lifted from or returned to its cradle.

Part layouts for the two versions are shown in Figs. 2 and 3. The value of the potentiometer is not critical; almost any good junk-box unit will do. Schematics are shown in Figs. 4 and 5. Note particularly the wiring of the micro-switch (S2). In both schematics it is shown with the phone in use. Switch S1, on the schematic for the second version (Fig. 5) is shown in position for use in turning the TV or radio completely off.

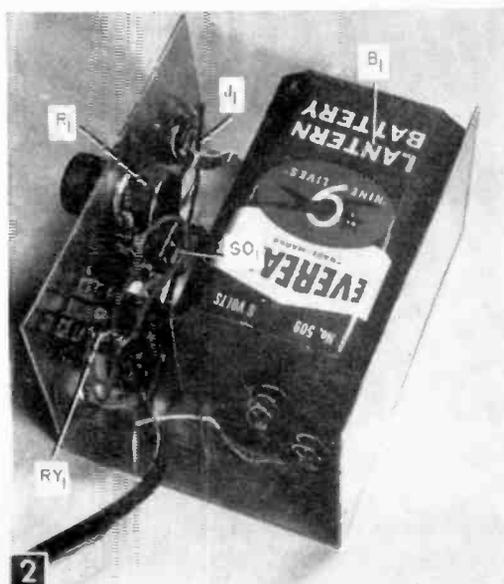After the unit has been wired, connect the micro-switch (Fig. 6) to the telephone. Press it tightly into position under the lip of the handhold of the telephone as is shown in Fig. 1. Pull




2

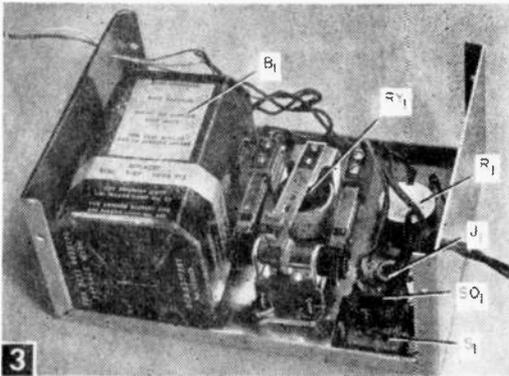


Parts placement in Version Two.

the radio turned on, adjust potentiometer R1 to the desired difference in sound from the TV or radio set. Then, when the telephone receiver is returned to its cradle, the sound will automatically return to normal listening volume. If either unit is plugged into the wall socket with the TV or radio line plug inserted into the ac chassis socket on the unit, the radio or TV will be turned off when the telephone receiver is off the cradle. The first version, in other words, can control a radio and a television set simultaneously; the second version can only be used for one function at a time. The first version controls in these two

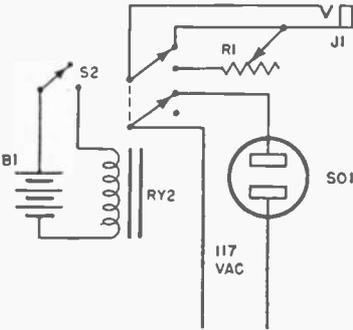

4 VERSION ONE SCHEMATIC

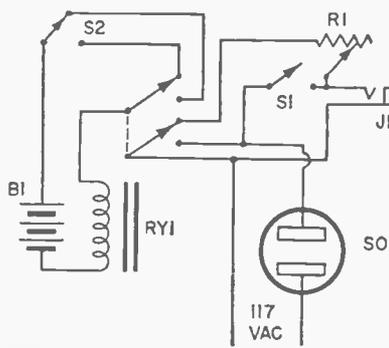


5 VERSION TWO SCHEMATIC


ways: 1) with several ac chassis sockets added, several sets can be turned on and off; 2) with one set connected so that sound will be turned down and one set so that sound will be turned off, both radio and TV can be controlled simultaneously.

cotter pins tight while holding switch in position. Bend the leaf of the micro-switch around the arm rest. Test to see if switch makes and breaks contact when telephone receiver is lifted from and returned to cradle, then cut cotter pins to suitable length.

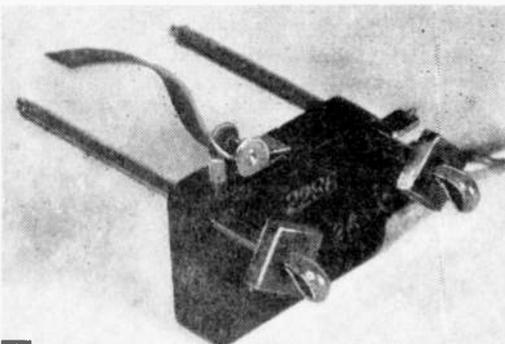To connect either of the versions so that they turn down the sound on a radio or TV, connect the phone plug in series with one of the speaker terminals of the set. The second version must never be plugged into the 117-v wall socket when it is being used with the phone plug. After turning switch S1 on, insert the phone plug into the jack on the unit. With the phone off its cradle and



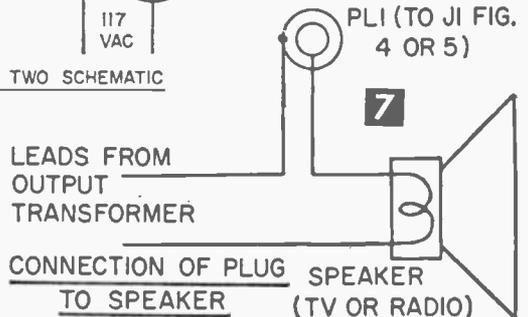6 Micro-switch with cotter pins and nuts ready for mounting on phone.



MATERIALS LIST—VERSION ONE	
Desig.	Description
B1	6-v lantern battery
J1	standard phone jack
PL1	standard phone plug
R1	0-100 ohm linear potentiometer (see text)
RY2	6-v dc, DPDT relay (Advance GHA/2C/6VD; Allied Radio 76 P 461)
S2	leaf actuated micro-switch (Acro 2CMD1-2AXX-A24; Allied Radio 35 B 030)
SO1	ac chassis socket
	aluminum case 3 x 4 x 5" (Bud Minibox CU-3005; Allied Radio 80 P 365)
	screws, grommet, line cord and plug, cotter pins, nuts (for cotter pins)
VERSION TWO	
B1	6-v lantern battery
J1	standard phone jack
PL1	standard phone plug
R1	0-100 ohm linear potentiometer (see text)
RY1	6-v dc, DPDT ratchet relay (Potter and Brumfield AP11D; Allied Radio 76 P 585)
S1	Single pole, single throw slide switch
SO1	ac chassis socket
S2	leaf actuated micro-switch (Acro 2CMD1-2AXX-A24; Allied Radio 35 B 030)
	aluminum case 3 x 5 x 7" (Bud Minibox CU-3008; Allied Radio 80 P 368)
	screws, grommet, line cord and plug, cotter pins, nuts (for cotter pins)



1 Oscillogram pattern of a full-wave, battery charger rectifier showing lower half-cycle, (lost in Fig. 4) inverted and above horizontal centerline, indicating it is being used.

Using an OSCILLOSCOPE

For diagnosing troubles in electronic circuits, the oscilloscope is as useful to the experimenter as the X-ray machine is to a physician

By HAROLD P. STRAND

THE oscilloscope is probably the most useful of all test apparatus commonly employed by electronic technicians and engineers. It can actually give you a moving picture of what is going on in a circuit by means of waveforms and traces on the face of a cathode ray tube. It can be used for many varieties of test, teaching and research work, such as signal tracing, peak-to-peak measurements, frequency measurements, and servicing radio and television receivers. One interesting application is for testing and watching the operation of microphones. The voice produces a varying wave-form on the scope in step with the intensity and type of sounds delivered to the microphone.

It is commonly believed that an oscilloscope is too complex, and too difficult for an experimenter to construct himself. Actually, however, kits are available from electronic supply houses that belie this belief. The scope used for the experiments discussed in this article, for instance, was made from an Allied Radio kit with printed circuit board, that makes the job of building a good, general-purpose oscilloscope quite simple.

This scope is designed for viewing waveforms to 1.5 megacycles. It has built-in regulated cali-

brator to measure exact amplitude of the waveform appearing on the screen, by the flick of a switch. The sweep covers from 15 cycles to 150 kilocycles. These specifications are usually adequate for most general use. The vertical amplifier has a sensitivity of .025 volts (r.m.s) per inch and the input impedance is 3.3 megohms shunted by 45 mmfd. The horizontal amplifier has a sensitivity of .07 volts per inch and an impedance of 2.2 megohms shunted by 30 mmfd. The kit is supplied by Allied Radio, 100-A N. Western Ave., Chicago 80, Ill., under Cat. No. 83YU146, \$44.95 complete. Laced cables, printed circuit board and pre-cut hook-up wires all trimmed, plus easy-to-follow assembly instructions make its construction simple for anyone having some electronic experience.

The wiring of the printed circuit board of this kit especially simplifies its construction.

Those of you who have never used this marvel of circuitry, will be pleasantly surprised at the time saved over conventional wiring. The complex part of the circuit will be already wired for you; it is only necessary to insert the sockets and the resistor and capacitor leads in punched holes and solder them on the back to the silvered copper foil pattern. The top side of the board is lettered and marked to help in quickly identifying the parts to be installed.

Soldering to the printed circuit is not difficult if care is taken to apply just the right amount of heat and all excess solder is eliminated. For use on the connections where small diameter wire is involved, an Ungar soldering pencil was found to be very satisfactory. For use at the other terminals, where larger wire is found, such as with the 1 and 2 watt resistors and large capacitors, you use a 60-watt iron. When you have completed assembly and tests, you can begin your experiments.


The first should be the production of a 60-cycle sine wave on the screen. A 6.3-volt filament transformer mounted on a small piece of board, with insulated line terminals and a terminal strip for the low-voltage secondary leads, is made up

for quick connections to the scope with either 6.3 volts or 3.15 volts. You can obtain either voltage by using the two outside or the center and one outside terminal and many experiments can be conducted at a safe, low voltage. This test unit is shown in Fig. 3, connected to the vertical input terminals of the scope.

Set the V. Input Atten. to .1, the Sync Selector to +INT and the Sweep Selector between 15 and 150. Turn on the power to both the scope and the transformer and after the former warms up a few minutes, you should get a sine waveform on the screen by adjusting the V. Gain, H. Gain and the Sweep Vernier controls. The latter is a vernier on the sweep selector and a point will be found where a single cycle wave will appear and the Sync Lock control will hold the trace stationary. The sine wave is adjusted on the screen so as to be equally divided and below the center horizontal line. This represents a good wave-form




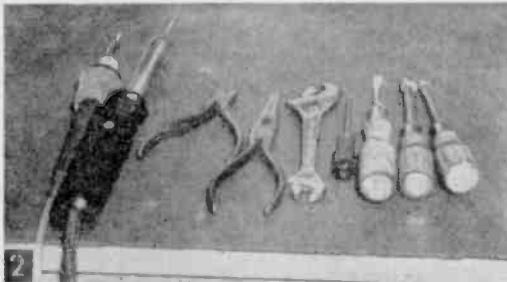Testing the completed oscilloscope with a small step-down filament transformer. The sine wave shown in the above photograph is one cycle or two alternations of the 60 cycle current.




Tools needed to assemble the kit.

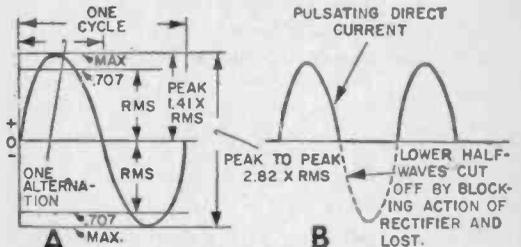Oscilloscope pattern quickly identifies a half-wave rectifier. Note that lower half wave has been cut off and lost.




A SINE WAVE VOLTAGE VALUES
PEAK TO PEAK VALUE IS THE TOTAL AMPLITUDE FROM POSITIVE MAXIMUM TO NEGATIVE MAXIMUM. RMS (ROOT MEAN SQUARE) VALUE IS ORDINARILY READ BY VOLTMETERS.

B HALF-WAVE RECTIFIER WAVEFORM

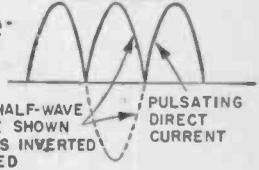


C FULL-WAVE RECTIFIER WAVEFORM

PLASTIC SCREEN RULED 10 LINES PER INCH

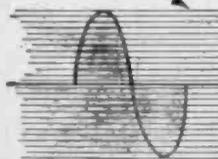

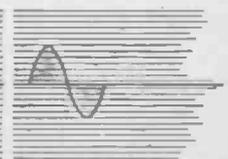
SINE WAVE FROM 18 VOLTS RMS (KNOWN VOLTAGE)



SINE WAVE OF $\frac{1}{2}$ AMPLITUDE 9 VOLTS RMS

VOLTAGE MEASUREMENTS, BY COMPARISON WITH KNOWN VOLTAGE

FILTERED DC

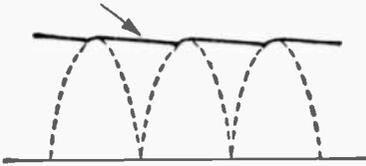

SHOWING THE EFFECT OF FILTERING
A FULL-WAVE RECTIFIER OUTPUT


a negative direction, from where it returns to 0. This is one cycle or two alternations. This sine wave is shown in Fig. 5A for further study and the relation of peak voltage to r.m.s. (root-mean-square) voltage as ordinarily measured by voltmeters, is indicated.

The oscilloscope can be used to measure voltage by comparison of the amplitude of the waveform from a known voltage with an unknown voltage. A plastic screen ruled with 10 lines to the inch (Fig. 5C) and applied to the face of the tube is a convenient method of calibration. The waveform from the known voltage can be adjusted between a certain number of lines and without touching the vertical gain control, the unknown voltage is applied, using the same vertical input terminals of the scope. If the trace has a peak to peak amplitude from the unknown voltage that is twice as great as that from the known voltage, the voltage is twice as great. Knowing the value of one signal applied, is quite easy to calculate other voltages.

To get familiar with the scope controls, turn the Sync Selector to the -INT position and it will be found that the trace is shifted 180 electrical degrees, indicating that synchronization is being effected through the use of the negative half-cycles. If moved to the EXT position, the trace will start to drift, as in this position it requires the use of an external synchronizing source to be connected to the Ext. Sync. terminal.

Further experiments with the controls should include the V. Input Atten. When on the .01 position, the signal voltage connected to the V. Input terminals is divided by a factor of 100 and the trace will be considerably reduced in vertical gain from that shown when the switch is on the 1 position. The .1 marker divides the input signal by 10. This allows some control over the value of the input voltage to the scope and therefore, when applying an unknown voltage or one known to be quite high, always place the attenuator on the .01 position first, advancing the switch later to the other positions if required.

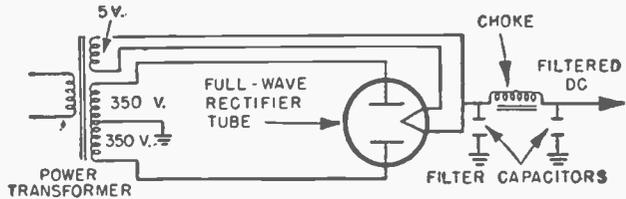
The oscilloscope is useful for indicating either half-wave or full-wave rectification. Such recti-




6

FILTERED POWER SUPPLY

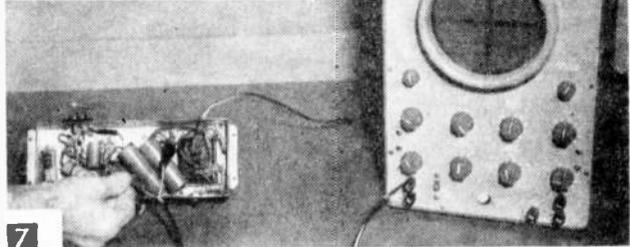Oscilloscope is connected across choke of a phonograph amplifier to show how filtering smooths out the pulsating current of a rectifier.



7

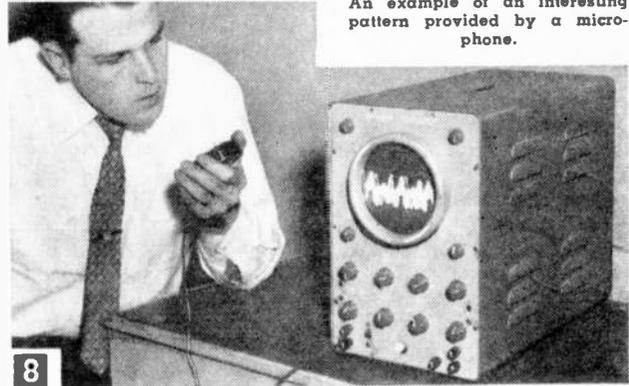


An example of an interesting pattern provided by a microphone.

8

fiers are used in battery chargers, radio and television power supplies and many other types of electrical apparatus.

For the demonstration of half-wave rectification (Fig. 4) a selenium stack has been connected in series with one side of the secondary of the 6.3 volt test transformer and a dummy resistance load connected across the resulting line, with leads to the V. Input scope terminals. A half-wave vacuum tube would show approximately the same waveform.

A half-wave rectifier uses but one of the half-waves of the 60 cycle sine wave shown in Fig. 5A, the other half being lost or wasted. The half-wave that has been cut off is indicated by dotted lines (Fig. 5B) and represents the action of the blocking effect of the rectifier, so that D.C. pulsating current is produced from an alternating current source. An oscillogram of a half-wave rectifier, showing two half-waves above the cen-

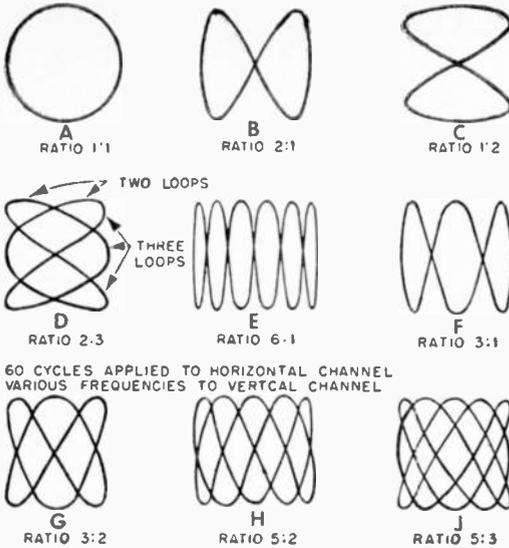

60 CYCLES APPLIED TO HORIZONTAL CHANNEL
VARIOUS FREQUENCIES TO VERTICAL CHANNEL

$$\frac{\text{NUMBER OF LOOPS TANGENT TO A HORIZONTAL LINE}}{\text{NUMBER OF LOOPS TANGENT TO A VERTICAL LINE}} = \text{RATIO OF FREQUENCY}$$

9

VARIOUS LISSAJOUS FIGURES FOR DETERMINING FREQUENCY

ter line with a space between is shown in Fig. 4. In full-wave rectifiers, both half-waves are used for better efficiency, the lost half-wave of the first case being inverted and used to pass unidirectional current. Rectifiers may be either of the dry disc or vacuum tube types.


An example of full-wave rectification in a battery charger is shown in Fig. 1. A dummy resistance load, of a value to show a small amount of current on the meter, has been connected across the spring clips, with leads connecting to the scope. It will be seen that the half-wave lost in the first subject has now been inverted to the space between the half-waves above the line and we have a full-wave rectifier. The pattern has been adjusted by the Vertical Position control so its lower points are on the horizontal line of the screen to get the correct picture. Full wave is obtained from either a bridge type rectifier stack or two half-wave stacks in a circuit with a center-tapped transformer. A full-wave vacuum tube rectifier also delivers this type of current.

The rectifiers illustrated produce pulsating direct current which is unidirectional but is not steady enough for some applications such as electronic power supplies. To smooth out the ripple to an extent as required for the purpose, a filter is added. This usually consists of a choke and two electrolytic capacitors (Fig. 6).

An example of a filtered power supply (Fig. 7) shows the scope connected across the choke in a phonograph amplifier. While the trace on the screen is not exactly a straight line, it has far less ripple than would be the case with the unfiltered rectifier shown in Fig. 1 or in other

words, it now takes the peaks of the waves only with just a slight dip between. Such an oscillogram allows the designer to check the effect of more or less inductance and capacitance so as to result in as little ripple as possible. (Care should be taken while working around apparatus employing high voltage, such as power supplies, since such voltage can deliver dangerous shocks if the worker gets careless and comes in contact with live terminals.)

An interesting demonstration of voice modulation on the oscilloscope is possible with a crystal microphone. Connect the microphone leads to the vertical input terminals, attaching the insulated center wire of the shielded cable to the red terminal (V. Input) and the braid to the ground terminal. When connecting any apparatus always connect the lead from the ground to the GND. terminal where one of the leads does represent

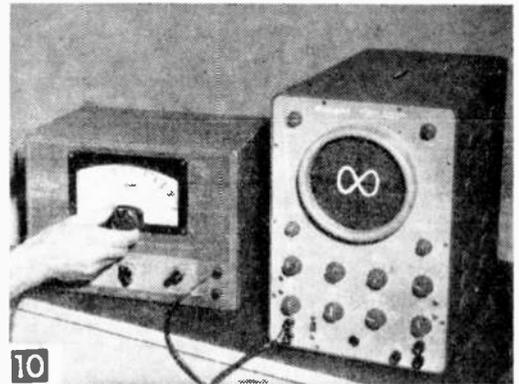


Frequency measurements are made with 60 cycles applied to the horizontal channel, by placing the Sweep Selector on this point and applying the unknown frequency to the vertical channel. Here an audio oscillator is being used to obtain a pattern of 120 cycles.

ground such as with microphones and many radio and TV test connections. Also, use shielded leads to prevent stray pick-up. Various sounded words and letters, as well as whistling will produce a wide variety of interesting patterns one of which is shown in Fig. 8. Musical notes sounded are especially effective. By this means, a good test for the condition or quality of a microphone is provided. A good unit in sensitive condition will respond to very low tones, while a cheap unit or one in bad condition will usually require loud signals in order to get comparable traces or the same gain on the screen. A dead microphone can be quickly identified, since it will have no response.

For use with a crystal microphone, the oscilloscope controls should be set somewhat generally as follows The V. Input Atten is on 1, the Vertical Gain about 3/4 advanced clockwise, the Horizontal Gain about 1/2 advanced clockwise, the Sweep Selector between 15 and 150, Sync. Selector on +INT. The controls are further adjusted as required in a test.

Frequency measurements are another possi-

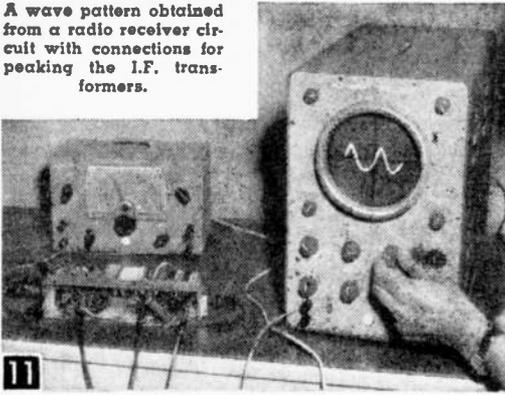A wave pattern obtained from a radio receiver circuit with connections for peaking the I.F. transformers.



bility open to the owner of an oscilloscope. It is often necessary to determine the frequency of some power source and this can be done quite easily by what are known as Lissajous figures. By this method a known frequency is applied to the horizontal channel and the unknown to the vertical channel to produce a variety of patterns that can be interpreted to indicate the frequency of the unknown signal. Fig. 9 shows some of the Lissajous patterns obtained.

The Sweep Selector is set to the 60 cycle position which allows a portion of the 60 cycle line to be applied for the horizontal sweep. For demonstration of various frequencies, which can be taken as the unknown frequency source, an audio oscillator is connected to the vertical input terminals of the scope as in Fig. 10. By adjusting a knob and a range switch, frequencies from 20 to 20,000 cycles are possible; 120 cycles are being delivered to the scope and the pattern shown has two top loops and one side loop. The Sweep Vernier has been adjusted to get the figure shown in Fig. 10. The calculation for frequency of the unknown signal is made by considering the ratio of the loops at the top of the pattern, which represents the unknown frequency, to the loop or loops at the side. In this case the ratio is 2:1. The actual frequency is determined by dividing the loops tangent to an imaginary horizontal line by those tangent to a vertical line or in this case $2/1=2$ and multiplying this ratio by that of the standardizing frequency or 60 cycles to get 120 cycles. If the unknown frequency source happened to be 30 cycles, for another example, there would be one loop at the top to two at the side, as indicated in Fig. 9C. It will be noted that there is but one loop at the top, with two at the side or a ratio of 1:2. Therefore, $1/2=.5$ or the frequency would be $1/2$ that of 60 cycles or 30 cycles. This can be carried out for a great variety of unknown frequency measurements up to a point where it will be difficult to count the number of loops or perhaps up to ratios of 8:1 maximum. In many cases the figures will not remain very stationary due to phase differences in the two signals, but in other cases where they are exactly in phase, the patterns will be quite stationary.

Radio and television service men often use an oscilloscope to get wave patterns in various parts of circuits and also for lining up the I.F. transformers in a superheterodyne radio receiver. For locating trouble in the audio stage the oscilloscope is often connected across the speaker output leads. Where oscillograms are desired in some parts of the I.F. or R.F. sections, an extra accessory is required, called a demodulator probe. In Fig. 11 the Allied oscilloscope is being employed for peaking the I.F. transformers. A signal generator, shown at the left, produces the necessary 456 kc signal to the grid of the mixer tube through a .001 capacitor. The scope is connected across the detector load resistor. The controls on the scope are adjusted to get a pattern showing the frequency response curve of single-peaked I.F. transformers. This output waveform can be used in combination with the tone from the signal generator to make the adjustments at the I.F. transformers. It is usually necessary to shunt out the oscillator section of the variable tuning condenser to accomplish this work.

There are so many possible applications of the oscilloscope in electronics and industry that it would be impossible to try and describe them here. In general the operator should have some background knowledge of electricity and electronics in order to handle the instrument properly. There are several good books on the subject which are suggested for study, among them being the following—


Modern Oscilloscopes and Their Use by Jacob H. Ruitter, Jr., Rinehart & Company, 232 Madison Avenue, New York 16, N. Y.


Obtaining and Interpreting Test Scope Traces by John F. Rider, John F. Rider Publisher, Inc., 480 Canal St., New York 13, N. Y.

The Oscilloscope by George Zwick, Gernsback Publications, Inc., 25 West Broadway, New York 7, N. Y.

Cleaning Fuse Clips

• When tubular fuse-holding clips in electrical equipment become corroded, contact resistance increases and the fuse and its holder effectively become a "resistor," thus impairing the fuse's original purpose. To prevent this, place the fuse in the center of a strip of crocus cloth, with the abrasive side out, and force this into the fuse clip holder. Move the fuse and cloth back and forth several times to burnish the overall insides of the clips and expose fresh metal. This will assure a positive contact when the fuse is replaced. If this process tends to make the fuse fit loosely in the clips, pinch them together slightly, then replace the fuse.—JOHN A. COMSTOCK.

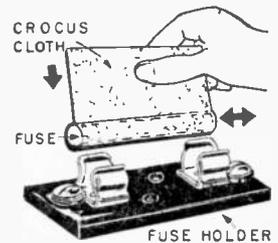

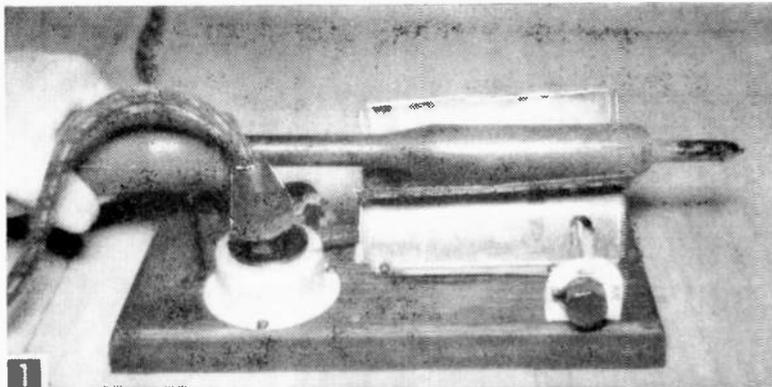

1 Thermostatically controlled stand regulates heat of iron through three levels— saves on electric bills!

Thermostatically Controlled Soldering Iron Stand

A thermostatically controlled soldering iron stand prolongs element life, prevents "frozen" tips and provides the right iron temperature for a variety of jobs. It is one of the few appliances that saves current while working instead of consuming it

By W. McCORMICK



for or the thermostat will regulate poorly.



Now, snip out the thermostat armature blades, one of tin-can steel, the other of brass shim stock (Fig. 4A). Scribe the location of all holes on each blade, centerpunch and drill. Deburr blades, flatten them and rivet them together with $\frac{1}{16}$ -in. diameter eyelet rivets *only* at holes "C" and "D." Ream hole "E" and force-fit a $\frac{1}{4}$ -in. x 2-56 r/h machine screw into it with the screw head on the armature's brass side. Run a hex nut on the screw, tighten it and snip off the excess screw shank. File screw shank flush with the nut, make sure nut is still tight, and file the screw head flat.

Now set one of the brackets (Fig. 3A) before you with its foot behind it and its $\frac{1}{2}$ -in. dimension in the vertical plane. Place the brass side of the armature against the back side of the vertical bracket leg, approaching the bracket

HERE'S a thermostatically controlled soldering iron stand you can make, mostly of junk, that will control any iron from 80 to 600 watts. The temperature sensing element is a bi-metal thermostat. When two strips of metal having different expansion co-efficients, such as steel and brass, are fastened together and heated, the compound strip will bend, with the more expansive metal, the brass, on the convex side. If one end of the strip is held fast, a swinging motion occurs at the free end. This motion can open and close electrical contacts.

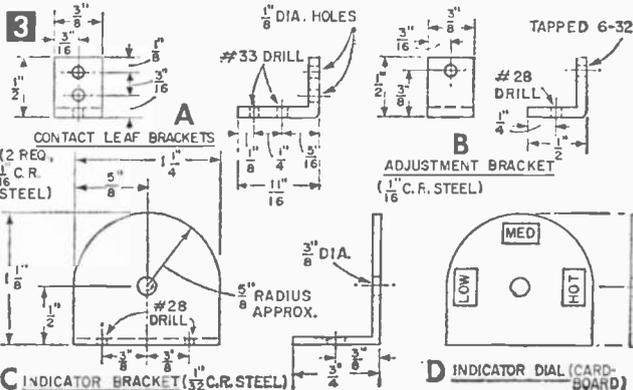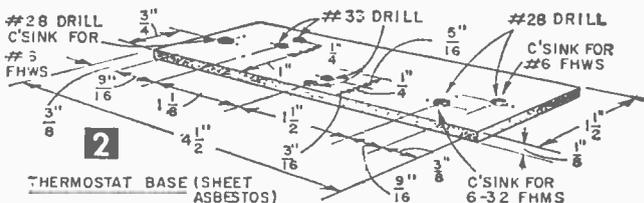To use this principle to control soldering iron temperature, first make the sheet asbestos thermostat base, Fig. 2. Next, make the brackets shown in Figs. 3A and 3B, and the indicator bracket, Fig. 3C, and indicator dial, Fig. 3D, and cement the dial to the face of the bracket. Do not use material heavier than called



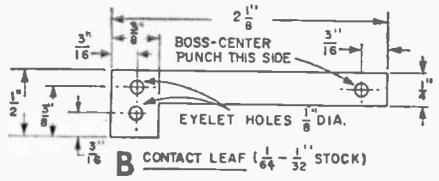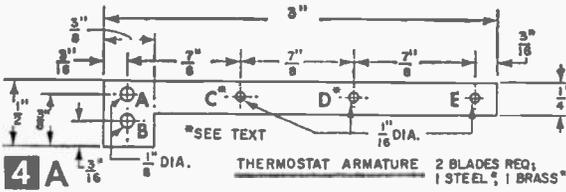


with the brass side of the armature from behind, and rivet the armature and bracket *lightly* together with $\frac{1}{8}$ -in. diameter eyelets. Mount the armature assembly on the thermostat base with $\frac{1}{4}$ -in. x 4-40 fh machine screws. Adjust the armature blades parallel with the armature base, and set the eyelets.

Next, make the contact leaf shown in Fig. 4B. Place the second bracket with its foot toward you and its $\frac{1}{2}$ -in. dimension in the vertical plane. Rivet the contact leaf *lightly* to the far side of the vertical leg, with the leaf's boss facing from you. Use $\frac{1}{8}$ -in. diameter eyelets.

Check the contact leaf for parallelism with the

thermostat base, and set the eyelets and mount this assembly on the thermostat base with $\frac{1}{4}$ -in. x 4-40 fh machine screws. The boss on the contact leaf should face the flat screw head in the armature. Center up the contact leaf's boss with the screw head in the armature, leaving about $\frac{1}{32}$ -in. between the boss and screw head. Spring the armature a little if necessary. Tighten all the bracket mounting screws.


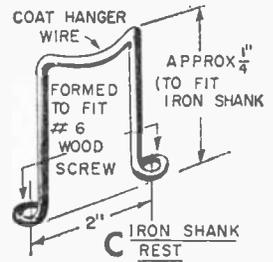


Now mount the adjustment bracket (Fig. 3B) with its tapped hole facing the back side of the contact leaf's boss, and in alignment with the armature's screw-head contact. (Foot of bracket toward you.) Snip the red tip off the fiber aligning tool, and cut the fiber shaft, leaving the tool 3 in. long, overall. Thread $\frac{1}{2}$ in. of the fiber shaft with a 6-32 thread. (The bracket hole thread will do this if the fiber shaft is made slightly pointed.) Slip the compression spring on the threaded end of the alignment tool and screw the threaded shaft into the tapered bracket hole one or two turns—not enough to force the contact leaf boss against the screw head in the armature. Put a soldering lug and nut on the screw-end nearest the upright of both the armature bracket and the contact leaf bracket. Tighten nuts.

Next, make the thermostat cover and iron pan (Fig. 5). Cut both ends out of a #303 tin can and snip cylinder lengthwise into two half-round sections. Form and drill. Rivet finished pieces together with $\frac{1}{8}$ -in. diameter eyelets and blue over a flame. Form the iron-shank rest (Fig. 4C) from a 6-in. length of coat hanger wire.

Now, chamfer the top edges of the hardwood base $\frac{1}{4}$ in., and give it a coat of thinned black enamel. Drill a $\frac{5}{16}$ -in. hole in the shell of the 110-v outlet and insert the grommet. Then place all the completed parts on the wood base and make a trial layout. The thermostat assembly mounts with #6 x $\frac{1}{2}$ -in. fh wood screws. The

- MATERIALS LIST—SOLDERING IRON STAND**
- | No. Req'd. | Description |
|------------|---|
| 1 pc | sheet asbestos, $\frac{1}{8}$ x $1\frac{1}{2}$ x $4\frac{1}{2}$ " (linen-base Bakelite can be used for irons under 200 watts) |
| 1 pc | cold rolled steel, $\frac{1}{16}$ x $3\frac{1}{2}$ x 5" |
| 1 pc | phosphor bronze, spring steel, spring brass or beryllium copper, $\frac{1}{2}$ x $2\frac{1}{8}$ x $\frac{1}{4}$ to $\frac{1}{32}$ " |
| 1 pc | brass shim stock, $\frac{1}{64}$ x $\frac{1}{2}$ x 3" |
| 1 pc | cold rolled steel, $\frac{1}{32}$ x $1\frac{1}{4}$ x $1\frac{1}{8}$ " or two thicknesses tin can steel sweated together |
| 6 | $\frac{1}{16}$ " O.D. x $\frac{1}{8}$ " eyelet rivet |
| 2 | $\frac{1}{16}$ " O.D. x $\frac{1}{8}$ " eyelet rivet |
| 1 | 2-56 x $\frac{1}{4}$ " rh machine screw and hex nut |
| 4 | 4-40 x $\frac{3}{8}$ " fh machine screw and hex nut |
| 1 | 6-32 x $\frac{1}{4}$ " fh machine screw and hex nut |
| 13 | #4 x $\frac{1}{2}$ " rh wood screws |
| 2 | #6 x $\frac{1}{2}$ " fh wood screws |
| 2 | #6 x $\frac{1}{2}$ " rh wood screws |
| 1 | rubber grommet $\frac{3}{16}$ " mtg. hole (Walsco 7023F) |
| 1 | cable clamp $\frac{1}{4}$ to $\frac{3}{8}$ " cable (Walsco 7505F) |
| 1 | assort. comp. spring $\frac{1}{32}$ x $1\frac{1}{2}$ " (Walsco 7440F) |
| 1 | instrument knob $\frac{1}{4}$ " shaft (Burstain Applebee 12A122) |
| 1 | alignment tool (General Cement #8247) |
| 1 | Amphenol 61F receptacle (outlet) |
| 1 | Amphenol 231S receptacle shell |
| 1 | electric iron cord, asbestos wrapped heavy duty |
| 2 | soldering lugs (Walsco 7150F) |
| 1 | compression spring, $\frac{3}{32}$ " I. D. x $1\frac{1}{2}$ " approx. (from old ball point pen or Walsco 7440F) |
| 1 | 2 x 2" piece white-faced cardboard |
| 1 | #303 tin can |
| 1 | tin can (any size) |
| 1 | 10" length #14 ga. stranded hook-up wire |
| 1 | hardwood base 4 x $8\frac{1}{2}$ x $\frac{3}{4}$ " thick |

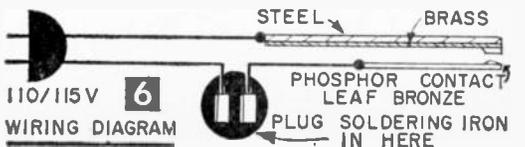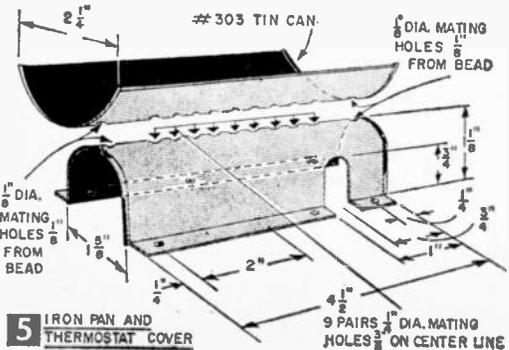


indicator bracket, 110-v outlet and the iron-shank bracket mount with #4 x 1/2-in. rh wood screws. The cord clamp takes a #6 x 1/2-in. rh screw.

Wire as shown in Fig. 6. Wrap solder lugs around the connections to the thermostat, and crush lug loops on the wires. Trim wire ends, and tape the appliance cord where it passes under the cable clamp. Mount the thermostat cover and iron pan assembly over the thermostat.


To calibrate unit, plug a lamp into the solder-

ing iron outlet and plug the iron stand cord into a 110/115-v outlet. Turn the aligning tool clockwise until the bulb just lights without flickering. Put the adjusting knob on the 1/4-in. diameter end of the aligning tool, set it to point to "LOW" on the indicator dial and tighten its set screw. The unit is now fully calibrated and will read "MEDIUM" and "HOT" temperatures correctly. Unplug the lamp, plug in your soldering iron in its place.

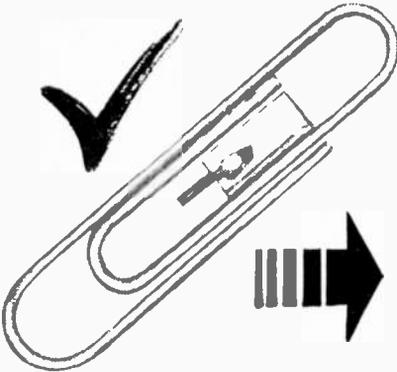Unique Circuit Simplifier the Tunnel Diode



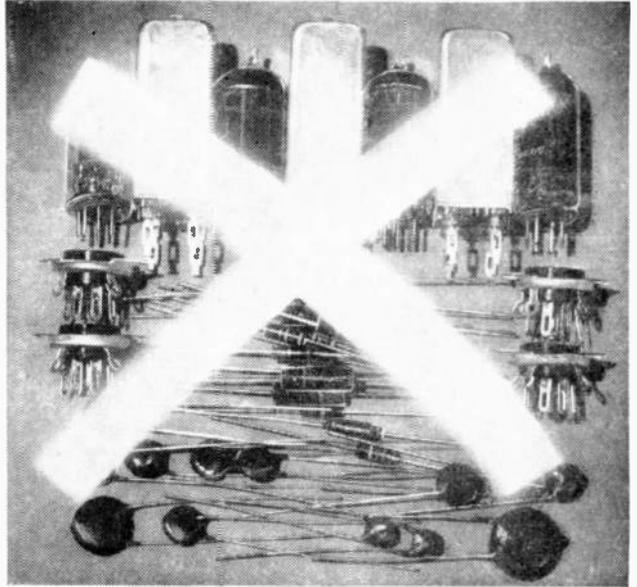Nestled inside this paper clip—with room to spare—is a tunnel diode, one of last year's most startling electronics developments. If an FM receiver were rebuilt using one of the new diodes, all the conventional components shown at the right could be omitted.




THE tunnel diode—newest baby in the fast-growing family of semiconductors—may soon be giving its first cousin, the transistor, an inferiority complex.

So small that a radio transmitter the size of a 50¢ piece has been built with it, the fantastic tunnel diode can perform almost all the functions of a standard low-power transistor and could lead to enormous savings in cost and complexity of electronic circuits.

A few of its features that have electronics engineers most intrigued are: An amplification noise figure of about one decibel, power requirements as low as one millionth of a watt and operation frequencies as high as 10,000 megacycles.

In some instances, the new diode may replace conventional components. In others, it might be used to improve their performance by working with them.

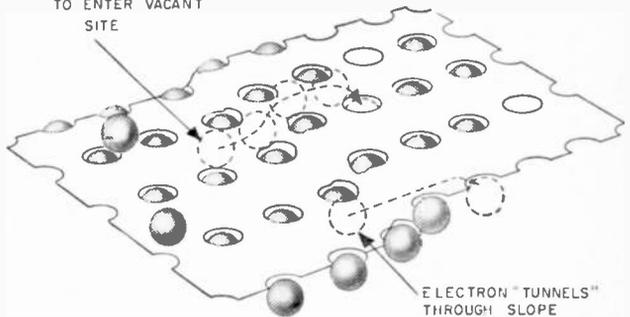ELECTRON "ROLLS UP" SLOPE TO ENTER VACANT SITE



ELECTRON "TUNNELS" THROUGH SLOPE

Here—in an extremely simplified diagram—is how the tunnel diode operates. Drawing represents a structure similar to a Chinese checkerboard, with one side slightly raised. Holes on the left side (which represents an n-type semiconductor) are filled with marbles, with a few left over and sitting on top. Right side (representing a p-type semiconductor) has a few holes vacant. The slope represents the potential barrier. A marble (or electron) from the left, can—after being given a push—enter a hole on the right by rolling up the slope and dropping in. Or, without the push, it can miraculously "tunnel" through the board and appear in a hole. The former process is used in conventional diodes and transistors. The latter represents what happens in tunnel diodes.

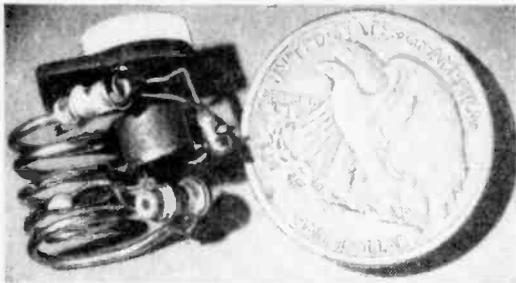


Photo compares transmitter with 50¢ piece. It consists of one variable and two fixed ceramic capacitors, tuning coil and the diode itself—inside can in center of transmitter.

The tunnel diode was first reported by a Japanese scientist—Dr. Leo Esaki—in 1958, and although its construction is very similar to an ordinary rectifying diode's, it works on an entirely different principle.

It takes its name from the phenomenon that makes its operation possible: quantum-mechanical tunneling.

As with transistors, it depends on the transfer of an electrical charge across a p-n junction. This is the region between a p-type semiconductor, which has an excess of positive carriers or "holes" (empty electron states), and an n-type, which has an excess of free electrons.

The opposite sides of this junction take on a charge which resists the movement of the "holes" and electrons across it. In the transistor, a charge carrier must be emitted into a region where its energy can be boosted by an outside voltage. It is then collected on an output electrode. The speed of this process is limited by the time it takes the charge carrier—having left the emitter—to traverse the control region and appear on the collector. This time limits the frequency at which the device can function and is quite long compared to, say, the time needed for a signal to travel an equivalent distance along a copper wire. The reason: in the wire, each electron moves only a microscopic distance, and those coming out the other end aren't the same ones that went in as a signal.

The quantum-mechanical theory says there is another way in which the particles can pass the barrier: an electron has a small, but definite, probability of disappearing from one side of the potential barrier and re-appearing simultaneously on the other—even though it does not have enough energy to surmount the barrier. It is as though the particles "tunnel" under the barrier, setting up almost instantaneous surges of current. Thus, in the tunnel diode, the signal moves with the same speed as it would in a copper wire—the speed of light.

The construction of the amazing device gives it some other interesting characteristics.

Its p-n junction is made of materials more heavily loaded—or doped—with impurities than

conventional diodes (semiconductor materials are doped to form either p-types or n-types), and made so that the barrier between p and n sections is extremely thin, less than a millionth of an inch thick.

So long as no outside voltage is applied across the p-n junction, there is no net current—since the electrons tunnel back and forth easily through the barrier in both directions. Apply a small voltage, however, and current appears. Add still more voltage, and current decreases. Add more, and current increases again.

In the range where an increase in voltage results in a fall-off of current, the tunnel diode is said to have "negative" resistance—making it suited for use as an amplifier or oscillator.


This negative resistance quality, combined with speed-of-light operation, makes possible a very high frequency response. Oscillation frequencies higher than 2000 megacycles have already been obtained—matching advanced transistor performance—and engineers confidently expect frequencies of more than 10,000 megacycles in the near future.

Some other outstanding features:

- It is smaller than a transistor and, because of its simplicity, ultimately will be just a fraction of its present size.
- It is affected very little by environment. The tunnel diode can operate at the near-absolute zero temperature of liquid helium or—at the other end of the thermometer—at temperatures up to 650°F, while conventional silicon diodes won't operate above 400°F.
- It has a low noise level, only parametric amplifiers and masers competing closely with it. And of these, only the tunnel diode can operate directly from a battery.
- Because it is less dependent on the structural perfection of its crystal than is the transistor, the tunnel diode is less affected by the damage that nuclear radiation can do to such crystal structures.

Soldering Flux Can Carries Vise

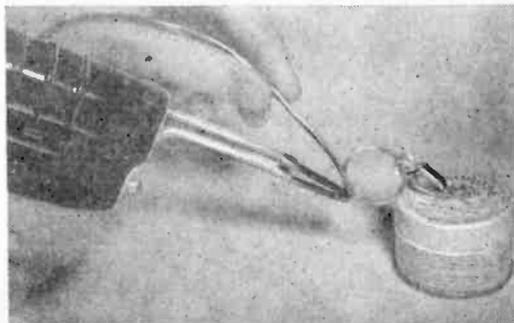- Attach a test-clip to the lid of a can of soldering flux to use as a handy vise for holding small



parts while applying solder. Enlarge hole in clip slightly with a drill and attach to can with a small self-tapping metal screw.—JOHN A. COMSTOCK.

Less bulky than conventional units, complete tachometer clamps to steering column for handy visibility. Instrument can also be installed on dash or used as portable test device.

THE Speed of an engine is the key to its performance. A standard item on the dash panels of many sports cars, the "tach" makes it possible to select the best engine speeds for gas economy. Also it advises the driver when the engine is turning over at just the right speed for shifting—thus cutting down unnecessary clutch and transmission gear wear. And it is essential in making proper carburetor and distributor tune-up adjustments in the garage.

This tachometer is designed to operate on either 6 or 12 volt ignition systems, positive or negative ground. Provided that you change one part, which depends on the number of cylinders, you can use this tachometer on any kind of engine from a "one lung" 2 stroke outboard motor up to an 8 cylinder 4 stroke engine. The photo shows the dial calibrated 0-5000, which is sufficient for most purposes, but it can also be arranged to read the range, 0-10,000 rpm. With an accessory switch, it can even be used to measure the speeds of rotating shafts in appliances and power tools. And unlike conventional tachometers which are bulky and difficult to install, it is compact, and hooks up without costly special cables and switch assemblies. Cost for all parts should be under \$25.

Construction. The meter, M1, shown in Fig. 1, is inexpensive, but has an accurate 50 micro-ampere movement. With the attached circuitry the entire assembly extends only 2 3/8 in. deep behind the panel. Begin construction by cutting Discs A and B (Fig. 2), of 1/8-in. sheet bakelite with either a jig saw or circle cutter. If you use a circle cutter, drill the center hole for a #6 screw, and reverse the cutter blade so that the cutting edge is inside. Rotate the cutter counterclockwise, and work through from both sides of the bakelite sheet to obtain neat discs. Make the spacer, C, from a piece of 1/4-in. brass bar stock, and thread it through with a 6-32 tap.

Parts layout is not critical, but it is necessary to be careful to avoid crowding the wiring in some spots. Cut out the two templates (Fig. 3), and fasten them to the bakelite sheets with tape or rubber cement. Turret type terminal lugs can be used for easier and neater construction, however if you prefer, you may choose to use 4-40





Electronic Tachometer

Dependable transistor circuit counts ignition pulses. Readings indicate proper speeds for operating and tuneup of cars, outboards, truck, marine and stationary engines

By JAMES E. PUGH JR.


machine screws instead. Either way, drill the holes carefully for a tight fit. Fasten solder lugs to the bottom of disc B and making connections to the meter. Drill two 3/16-in. holes in this disc for the meter terminal screws. A 6-32 screw fastens disc A to the threaded spacer later and also connects the positive solder lug at the center (Fig. 8), and thus brings the positive terminal through to the back of disc B.

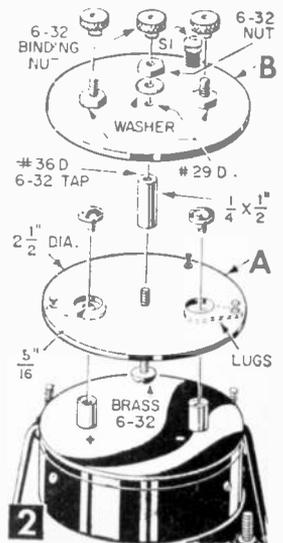

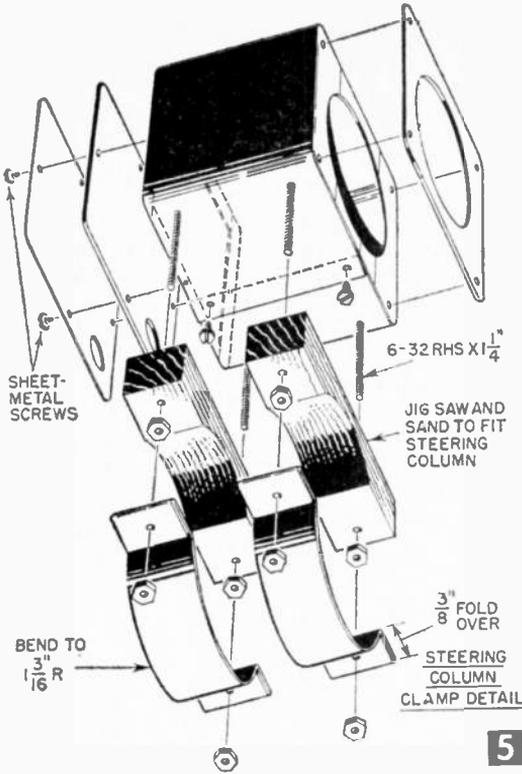


5

CALIBRATION SWITCH (SI) 6

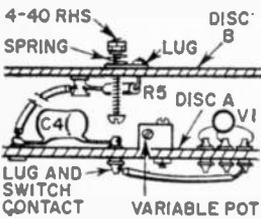

signed to pass the maximum number of pulses from an 8-cylinder engine operating at 10,000 rpm. Frequencies above this range and other "hash" elements are eliminated by the filter, to eliminate the possibility of error in the meter readings.

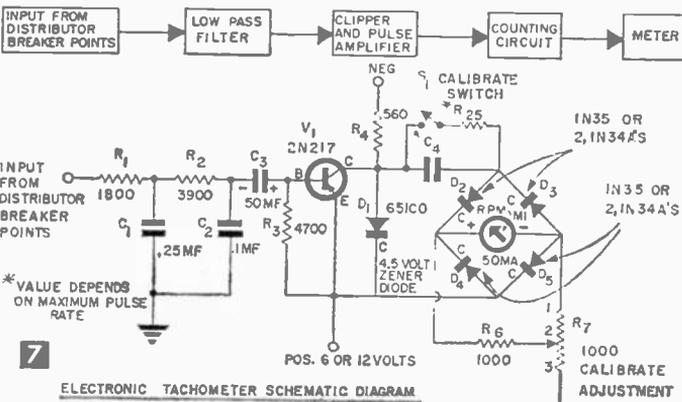Then the output of the filter circuit is fed to transistor V1, where the wave shape is clipped



7

ELECTRONIC TACHOMETER SCHEMATIC DIAGRAM

TABLE A. Calibration data for tachometer using 0-50 meter scale. 5000 rpm at full scale reading.

Number of cylinders		Pulses per second	60 cps calibration	optimum C4
2-stroke	4-stroke			
	1	41.7	36+	.20 uf.
1	2	83.3	36	.10 uf.
2	4	166.7	18	.068 uf.
	6	250	12	.04 uf.
4	8	333	9	.03 uf.

+ at 30 cps

and shaped into a square pulse, and amplified. The Zener diode, (D1) is next in the circuit line-up, and it keeps the pulses at a constant level, regardless of changes in battery voltage. It makes it possible to use the tachometer on either 6 or 12 volt systems, without changing any parts, and with only a minor calibration adjustment.

Next in the counting circuit, the capacitor C4 with the resistive part of the rectifier and meter circuit, convert the square pulses into negative and positive spikes. The electronic enthusiast may enjoy observing these wave shapes on an oscilloscope.

Finally, the diodes D2, D3, D4 and D5, wired as a full wave bridge rectifier, change all the spikes to one polarity to produce a meter current that is directly proportional to the number of pulses coming from the engine.

Calibration. When you have finished the wiring of your tachometer, connect the flexible ground link to correspond to whether your car is wired negative (Fig. 9), or positive ground (Fig. 10). Connect the tachometer to the car battery, or to one of corresponding voltage. Next, connect an audio signal generator to the tachometer ground and input terminals, and set it to 60 cycles per second (or to 30 cps for a 1 cylinder 4 stroke engine).

Adjust potentiometer R7 to give the meter reading listed in Table A for your kind of engine. Note that if you set the audio signal generator to multiples of 60 cps, the meter reading will increase proportionately, for example for calibrating a 6-cylinder 4-stroke engine, the reading at 60 cps will be 12; at 120 cps it will be 24; at 180 cps, 36, etc.

If you have no signal generator, you may be able to borrow one from a radio ham, or use one at a radio service shop. Otherwise you can calibrate without it, by using the output from a 6 or 12 volt filament transformer. Connect the transformer to the tachometer ground and input terminals, and adjust the meter reading, by means of trimmer pot R7, to the desired point as listed in Table A.

MATERIALS LIST—ELECTRONIC TACHOMETER

- M1 0-50 DC Microammeter (Lafayette Radio Co., 165 Liberty Ave., Jamaica 33, N. Y. Cat. #TM-70)
- D1 4.5 volt voltage regulator Zener Diode (Texas Instrument 651 C0)
- D2, D3, D4, D5—Two 1N35 diodes (paired type) or four 1N34A single diodes Sylvania crystal diodes
- V1 2N217 Transistor, RCA

CAPACITORS

- C1 .25 mfd. 200 volt metallized-paper tubular capacitor, Aero-vox P 82Z
- C2 .1 mfd. 200 volt metallized-paper tubular capacitor, Aero-vox P 82Z
- C3 50 mfd. 25-volt ultra miniature electrolytic capacitor, Barco P25-50 (Lafayette Radio)
- C4 100 volt capacitor Elmenco tubular, Type DP (See table A for value)

RESISTORS

- R1 1800 ohm 1/2 watt 10% Carbon resistor
- R2 3900 ohm 1/2 watt 10% Carbon resistor
- R3 4700 ohm 1/2 watt 10% Carbon resistor
- R4 560 ohm 1/2 watt 10% Carbon resistor
- R5 See Table A 1/2 watt 10% Carbon resistor
- R6 1000 ohm 1/2 watt 10% Carbon resistor
- R7 1000 ohm miniature trimmer potentiometer Bourns Wire-wound Trimit 273

HARDWARE

- 1 Threaded bushing, 1/4 inch x 1/2 - 6-32
- 1 dz. ea. Turret terminals, Keystone Electronics Corp. Type 1532 single end; Type 1522 double end (Allied Radio)

MISCELLANEOUS

terminals, screws, nuts, decals, plastic spray, or varnish, 3/16 soft aluminum sheet metal

Next, disconnect the signal generator, close S1, and select a resistor for R5 that will give a convenient reading near the top of the scale. The value of this resistor, will of course, vary for different tachometers. In the one illustrated in this article, a 47,000 ohm resistor gives a reading of 48. Solder the resistor in place and write the meter reading, with S1 switch closed, on a small piece of white tape. By means of this switch, you can easily check the calibration after the tachometer is installed, simply by closing the switch (with the ignition on, but engine off).


Table A lists the pulses per second that are obtained from various engines at 5,000. To calibrate

your tachometer to read 0 to 10,000 maximum, simply double the PPS value, and divide the C4 value and 60 cycle calibration point by two. The formula for calibrating the tachometer for use on any engine is: $PPS = \frac{C \times R}{60 \times N}$

which PPS is the number of pulses per second; C is the number of cylinders, R is the revolutions per minute, and N is the number of revolutions per each cylinder firing.

The value of N will be 1 for a 2 stroke cycle, and 2 for a 4-stroke cycle engine.

The stability of the tachometer circuit is excellent, and your meter readings should be linear with .5% at 70° F.



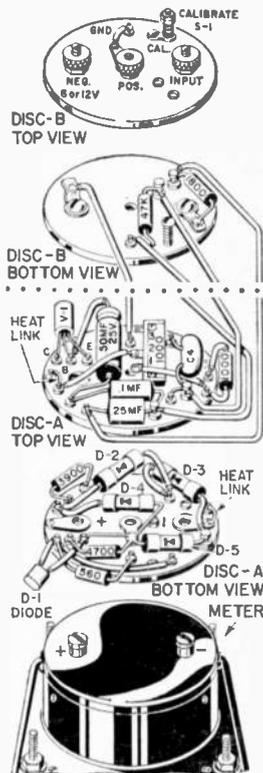


PICTORIAL 8

Installation. Use small diameter test prod wires for connecting to the engine, and be sure to follow the following precautions to avoid damaging the meter and transistor:

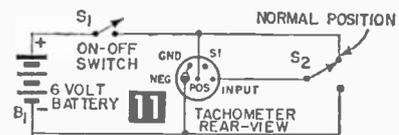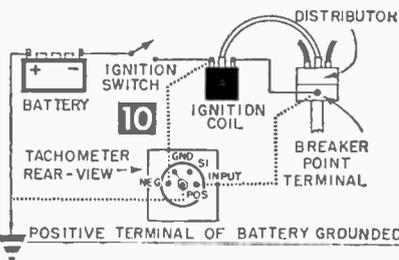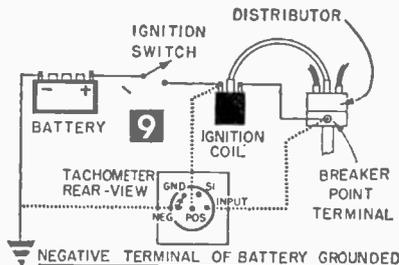1. Make sure that the flexible ground link is connected to the correct ground position for your car, as shown in Figs. 9 or 10.
2. Be sure that the tachometer terminals are connected to the correct battery terminals, with the "hot" tachometer terminal connected to the coil side of the ignition switch.
3. Never start the engine with the calibrate switch (S1) on.

Using Your Tachometer. The tachometer, installed on your car, will not only add to driving pleasure, but will save you money as well. For example, gas consumption is higher at both low and high rpm, therefore, shift and drive with the engine operating in the middle range as much as possible for maximum gas mileage.



CONNECTION FOR MOTORS, DRILL PRESSES, LATHES, ETC. WHERE PULSE IS SUPPLIED BY SHAFT-ACTUATED SWITCH.

S.P.D.T. SWITCH ACTUATED BY MOTOR SHAFT

When piston speed exceeds 2500 feet per minute, ring and cylinder wear go up fast. Calculate the engine speed, at which the piston speed is about 2500 fpm, and use your tachometer as a reminder to operate below this range, to minimize wear.

Best gear shifting is obtained when the teeth of the driving and driven transmission gears are moving at about the same speed. Synchronesh transmissions in standard cars reduce some of the strain when the speeds are unequal, but with your tachometer you can practically eliminate this wear. And on trucks etc., which have no synchronesh, the tach is even more useful. Driving and driven gear speeds can easily be calculated. Synchronize your gears, simply by adjusting your motor speed to the best speed while in neutral and then shift.

If you own a sports car, or one of the smaller foreign cars, never start, pull a heavy load, or travel uphill at low rpm. To do so causes heavy wear on the connecting rod and main bearings. The tachometer will remind the driver to avoid such abuse. Since maximum torque is developed over a narrow band of engine speeds, the tachometer will help you to select the best rpm for fast passing and pulling heavy loads.

Tuneup With Tachometer. To adjust your carburetor, set the low speed adjustment (air to gas ratio) for maximum tachometer reading at idle speed. Then set the idle adjustment to the recommended value, usually between 400 and 600 rpm.

Adjust your distributor setting for maximum rpm, and then back it off slightly to compensate for the grade of gas being used. It should be adjusted for highest rpm without ping. Generally, the adjustment that yields the highest rpm gives the highest economy, power and speed.

Checking Tool Speeds. You can use the tool to measure speeds in checking performance and servicing of electric motors, drill presses, etc. Often, the rpm especially of metal working machines, is the guide to selecting or grinding tools that will cut at the proper rate of feed. Figure 11 shows the circuit needed to hook up your tachometer, with a switch to supply the pulses, and a dry cell battery. An old distributor will work fine as a switch, or you can use a snap action leaf switch, equipped with a roller. Make a cam for the shaft, or simply file a flat spot, and use a 6 volt dry cell, or low voltage rectifier for a power supply.

Using the switch as in Fig. 11, will result in the same readings as for a 1 cylinder, 2 stroke engine, since one pulse will be obtained for each revolution.

It should be noted that if you install an ordinary contact switch, as in Fig. 11, for continuous service on a rotating machine, that the life of the switch will be limited. Many makes of roller, leaf and snap switches are available; however, Switch #11-104, offered by Licon Division of Illinois Tool Works, will operate for many hours at up to 3500 rpm, and is available through distributors.


Compass Making

A MAGNETIZED sewing needle, a cork or round wood disc and a small bowl of water form this simple magnetic compass.

Take a fair-sized steel sewing needle and magnetize it by stroking it along its length with the South pole of a small permanent magnet, either horseshoe or bar type as in Fig. 2. You use the South pole of the magnet because a piece receiving induced magnetism from contact with a permanent magnet will assume the opposite polarity when separated. Thus a South pole will leave a North pole at the point of the needle and this end will point towards the North, provided that you end your magnet-rubbing strokes in the direction of the point.

Some permanent magnets are marked N and S for identification. If not, use an ordinary pocket compass to test it; the end which attracts the North pole of the pocket compass will be the South pole of the magnet (unlike poles attract), and you can mark this end with an S.

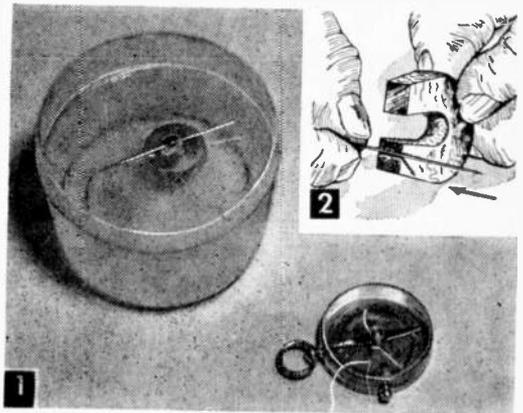The float for the needle is a $\frac{3}{8}$ in. long piece cut off from a hardwood $\frac{3}{4}$ in. diameter dowel. For the water container, use a small plastic, glass or china dish or saucer. Do not use metal. After magnetizing the sewing needle, place it on the



float and melt a drop of wax over it in the approximate center.

Checking the complete magnetic compass with a standard pocket compass (Fig. 1) shows that the needle is pointing due North. The closer you move the two compasses together, the more you will notice a slight interference between the two magnetized needles. Of course, compasses should be kept away from any iron or steel objects which might cause stray magnetic fields and result in an error.

You can arrange a cardboard ring on the top of the dish with N, S, E and W markings.—H.P.S.



Voltmeter accuracy may be checked within reason by dry cell giving 1.5 volt readings.

Repair That Old Meter!

Simple repairs on meters can easily be made by the home craftsman in his own workshop

By J. B. DEVEREAUX

BECAUSE of the delicacy of such instruments, many home shop mechanics, electrical and radio experimenters hesitate to attempt repairs of any sort on electric meters. Such timidity is perhaps justified in many cases where major repairs are required and where extensive dismantling would impose problems that would finally wind up in brushing the parts off the bench and into the waste can.

On the other hand, there are many simple ailments that can be remedied with a little patience and care and many otherwise good meters may often be restored to serviceable condition with a half-hour's tinker-




ing. We are here dealing only with moving coil meters inasmuch as they are by far the most common type in use today for direct current. For A.C. we have the moving iron meter which is also relatively simple and can be easily repaired in many instances. Where major damage has been done, and this is evident by examination, then the owner of the meter had best give up the job or send the meter back to its maker for rehabilitation.


The simple ailments that may be cured at home are frictional retardation, bad balance, overthrow and sticky needles. All other troubles are usually hopelessly beyond home tinkering without the knowledge of design and the special assembly tools and skill available to the manufacturer of the meter only.

The meter that requires tapping with the fingers to bring full reading has frictional trouble of some sort. The needles of such meters move to a certain point depending upon the current and there they stop. Thereafter if agitated by tapping, the needle will move forward for another scale unit or two. Such meters are usually troubled with dull

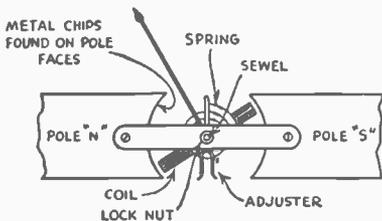Use only very small screw drivers in taking meter out of case.



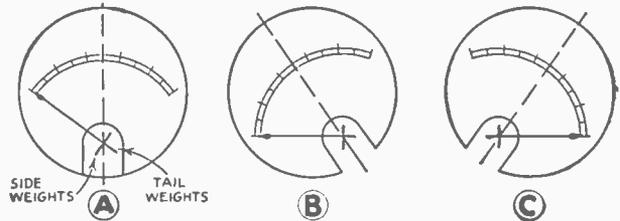1 VITAL PARTS OF MOVING COIL VOLT METERS AND AMMETERS



2 HOW TO BALANCE METER POINTER,


pivots, cracked jewels, dirty points or lint. Cracked jewels may result from dropping or other rough handling and the manufacturer only can remedy such ailments. That also goes for dull pivots. Lint may be removed by the aid of a toothpick or a piece of sharp-pointed wood smeared with a bit of light adhesive material. One must be careful, however, to see that the wood is clean and that he does not deposit more in the meter than is carried away.

Workers on meters of any kind must provide a scrupulously clean bench covered with a piece of glazed cardboard. This should be wiped clean with a moist cloth before the meter case is opened. Linty clothes on the worker should also be avoided, it being best to roll up the sleeves. Such precautions may sound a bit silly to amateurs until it is recalled that the barest piece of foreign matter in a milliammeter or milli-volt meter can produce readings inaccurate by as much as 50%.

The meter should be uncased using the right sized miniature screw driver so that the screw slots will not be ruined. If a shunt is present, it should be left soldered in place. Removal may interfere with readings. Should the repairman find that the moving coil has been burned out by heavy current, he will know that so far as the home repair is concerned, the meter is beyond recall. The same holds true if the pivots are found to be dull. Special machinery would be required to sharpen them and a manufacturer would prefer to replace them with new ones. If the coil, spring, pivots and jewels appear sound then the meter is simply troubled with friction.


Should an examination under a magnifier reveal lint, then the stick moistened with the light adhesive may be tried. Inasmuch as these meters

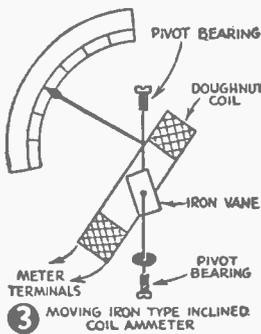have powerful magnets, they often accumulate bits of iron or steel and these often introduce frictional factors. Their removal may usually be effected with the sharpened end of a paper clip. One must make sure, however, that all metal filings are removed from the end of the paper clip wire before it is introduced into the



meter to pry off any metal chips that may already be there adhered to the magnet. Great care should be exercised in the use of this simple tool to make sure that one does not touch the coil of the sensitive spring.

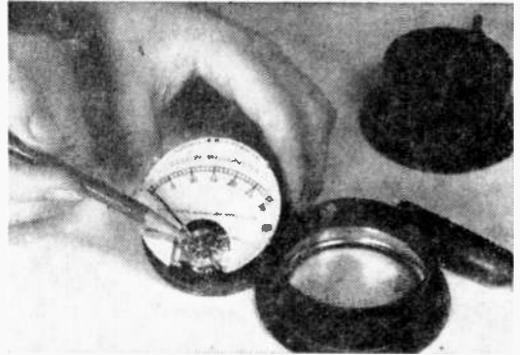If the pointer is found to be touching the dial, often the case with rough usage or dropping, then the pointer may be straightened with a small pair of tweezers but here a very steady hand will be required.



Pointing to pivot bearings, which, if broken, makes factory repair imperative.



An ammeter removed from case.

Oftentimes, especially in the case of the cheaper meters, frictional losses are introduced by tight pivots. In such a case, the jewel screw may be given a half turn or so.

The meter is given a final examination before being replaced in the case. One watches especially for a hair which may have dropped in. With a really sensitive meter, this is like introducing a telegraph pole into the works.

An unbalanced meter is brought into balance by means of the simple steps, 1, 2, and 3 shown in drawing number 2. First the pointer or needle is set on zero by means of the zero adjustment screw while the meter is held in a normal or horizontal position. Then the position of the meter is shifted to that shown at B. The tail weight is then adjusted until meter pointer rests on zero. The side weight is then adjusted until pointer is on zero while holding meter in vertical position. This operation is a very delicate one and the meter may be very easily damaged, especially the pointer, if a steady hand is not used. Overthrow is often due to a bent pointer, that is, bent to the right. Sometimes in the cheaper meters a flexible tail weight is used and this must be bent one way or another to restore balance. Daubs of shellac are used at times.

Old meters that have been used near heavy transformers will usually have badly weakened magnets and these are always factors in inaccu-

racy. The only hope here is for re-magnetization or replacement with a new magnet.

A.C. meters with moving iron are treated in much the same manner. In the case of a vane moving in a close fitting chamber, lint or tiny particles of iron may cause great trouble, making the meter practically useless at times.


With such meters, the soft iron vane should not be bent since all meters of this type depend upon proper relationship here for accuracy. Any change in the position of the coil around the vanes will also result in inaccuracy.

The accuracy of small meters runs plus or minus 2% of the full scale deflection. In the case of a small voltmeter of a few volts range, simple tests for ordinary accuracy may be run

by connecting to two or more (depending upon voltage of meter) new dry cells in series, each cell adding 1½ volts. A potentiometer may also be used so that the pointer of the meter may be run up and down the scale.

A multimeter such as is used by radio repairmen may be used to calibrate such meters inasmuch as extreme accuracy can never be had with inexpensive instruments. The multimeter type of check will be quite sufficient. If the repairman does not have such an instrument then he may be asked for assistance. Calibration may be only a matter of a few minutes. In such cases, the multimeter is used with a potentiometer, the former serving as the standard for determining the calibration.

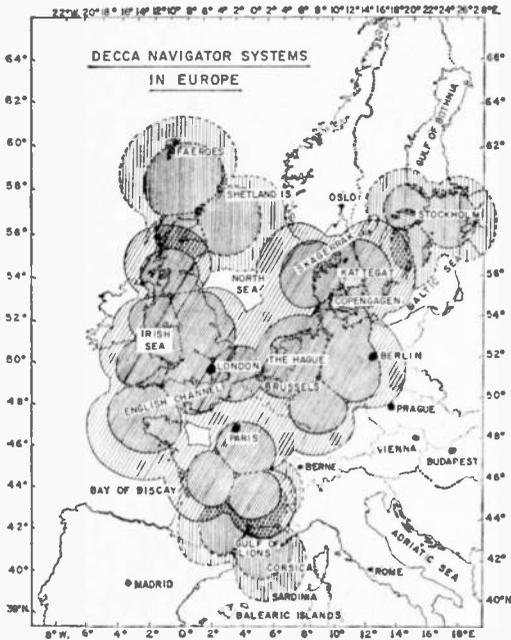Why Wait For Air Safety? By C. M. STANBURY



in three, cutting the required vertical separation in half, and reducing the distance between high speed aircraft flying the same course from 100 to 10 miles. It could do all this in the future.

DECCA cuts the width of the air lane by only half; vertical separation remains unchanged. But separation between aircraft flying the same course is, within 60 miles of the terminal, cut to a mere two miles. The effective airspace is multiplied 100 times. As the distance increases from the terminal, the Master DECCA station and the congested area around them, the system gradually becomes less effective. But at the same time, the air traffic density and danger of air collisions is also diminished.

So DECCA is usually as accurate as radar will be. More important, DECCA is ready now. It has done all these things in Europe for several years and is now doing them in Eastern Canada which is the western terminus for all major North Atlantic routes.

VOR and DME Systems. The Federal Aviation Agency is not, of course, sitting on its hands waiting for this advanced radar to become operational. The FAA is spending millions of dollars for the construction of these comparatively new VHF and UHF navigation devices. A VOR (VHF Omni Range) automatically indicates the aircraft's bearing in relation to the VOR station. It is accurate to within 4 degrees. DME measures the distance from the plane to the facility. A system such as VORTAC which combines VOR and DME, can indicate for the aircraft its position so long as it is within range. Sounds like a match for DECCA, but let's look beneath the surface.

At a distance of 30 miles, VORTAC has a potential accuracy of 1 mile which would permit a minimum separation between aircraft of 2 miles. That's just what DECCA has already obtained at twice that distance. Further we haven't told you about DECCA's potential accuracy, 10 yards within 50 miles.

IS THE U. S. doing anything to improve air safety? Is Washington taking steps to alleviate air traffic congestion? Yes. If you've read any of the magazines in the radio field, you're already familiar with numerous research projects in this field, including radar which, in the future, could increase the effective air space as much as 60 times.

But why wait when the world already has a well established navigational system, a system which in many ways is more effective than even the most advanced radar? This system is DECCA.

DECCA vs. Radar. In the future radar could increase effective air space 60 times. It would do this by dividing the present 10-mile-wide airway

ICAO Turns Its Back on DECCA

At a special meeting in Montreal, the International Civil Aviation Organization voted to adopt DME as a standard short range navigational aid to go along with VOR. The action, spearheaded by the FAA, was bitterly opposed by Great Britain, Canada (previously neutral) and Australia. After the resolution had been pushed through, the head of the British delegation indicated that his country would continue to use and develop DECCA. He elaborated: "Our belief is that the need

for a high accuracy, hyperbolic system will arise much more quickly than many here today believe. Before long we will have to get together and adopt such a system." But probably the most telling objection was that of Australia, which has used DME since the war: On the basis of their unequalled length of experience, they concluded that DME, especially DME allied with VOR, could *not* meet the needs of the jet age. Time will tell who is right.


However, let's be generous and assume both systems to be equally accurate. DECCA can serve any number of aircraft simultaneously, DME only 50. When this number is exceeded, the system automatically accepts the 50 strongest and rejects the rest. How would you like to be riding in the 51st?

Worst of all, VOR and DME systems, because they utilize VHF and UHF frequencies, are limited to line-of-sight reception. DECCA is not. Nor for practical aeronautical purposes is DECCA affected by natural barriers such as hills or mountains. The new U. S. system is. In one month in 1958, some 40 VOR/DME navigation facilities were either inoperative, partially out of order, or in some way operating imperfectly. And this figure does not include those being relocated or re-

Every moment wasted on VOR and DME systems, when the U. S. should be building DECCA chains, costs us money and lives. In 1958 the *Electra* disaster brought this out with sickening emphasis. LaGuardia Field is equipped with the newest VOR/DME system—VORTAC—but Flight 320 still wound up in the East River. Nor was tracking via radar enough.

Speaking conservatively, if there'd been DECCA it might not have happened. The American manufacturer of DECCA, Bendix Aviation, has developed RAILS (Remote Area Instrument Landing System) which can be used where conventional ILS is inadequate. By combining DECCA, the aircraft's own absolute altimeter and a computer, the pilot is furnished with glide path guidance, distance to touch down and ground speed.

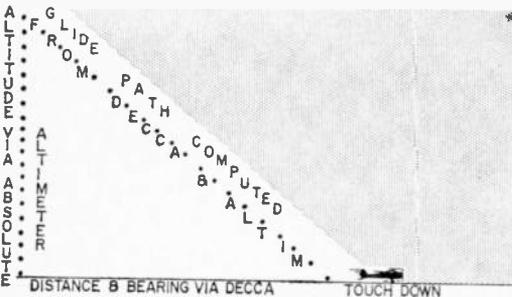Maybe Flight 320 was destined to miss the runway and no amount of technology could have saved her. But DECCA could have made her chances for survival better, while VORTAC was powerless. And there'll be more 320's. How many? That depends upon how much time we waste with VOR/DME, how long we ignore DECCA.



A control system incorporating DECCA—RAILS (Remote Area Instrument Landing System). Although the accuracy of this system is still being evaluated, chances are good it will enhance DECCA's overall superiority. At present it's only commercial use is in conjunction with the Bell helicopter service in the Dallas-Fort Worth area.

constructed. What hope has this system in such mountainous regions as the Rockies or the Alleghenies?

The Handwriting on the Sky. I have no desire to sell radar short. The radar of today, although it does not equal DECCA as a navigational aid, is already an important navigational device. In the future it will be on a par with DECCA. Most probably, they will complement each other. Radar, under those circumstances, would be an airborne system providing data on other nearby aircraft. DECCA would act as the overall, stable ground-based system. They would continually provide a cross-check on each other.


But why wait? Why fool around with VOR and DME which, considering DECCA's obvious superiority, are no better than interim measures when no interim measures are necessary. DECCA is here now.

How DECCA Works


A DECCA chain normally consists of 4 stations, a master and 3 slave stations designated red, green and purple. By measuring the phase difference between radio waves from the master station and any two of the slaves, a navigation fix is obtained and automatically plotted on a gridded chart. Because it utilizes lightweight receiving equipment and is extremely simple to operate, DECCA is suited to all types of aircraft, big or small, commercial or private.

Tap Tube Handle

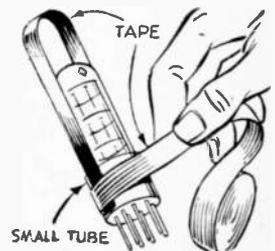• Pulling miniature and sub-miniature tubes from their sockets in crowded electronics hookups will be much easier if you provide each tube with a handle. Use a strip of masking or *Mystik* tape looped over the top of the tube and secured



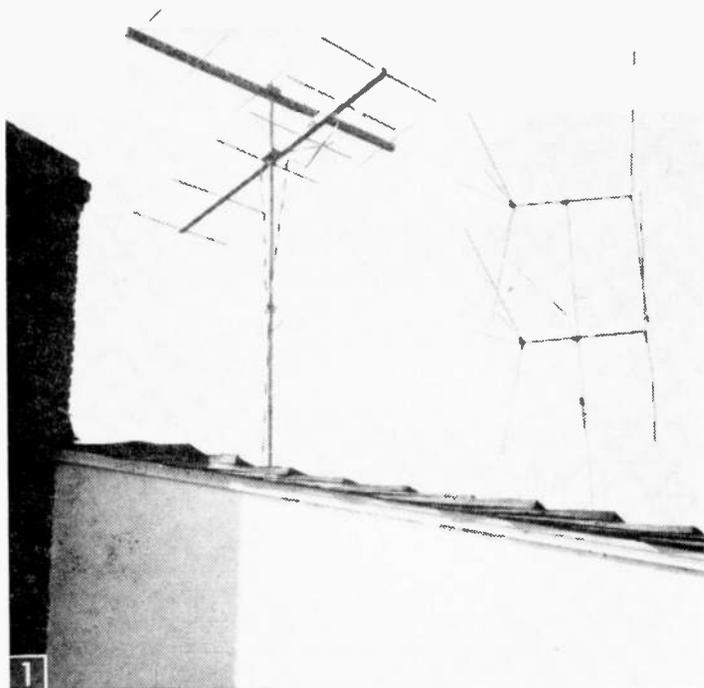around the bottom with another strip of tape. Don't use tape on tubes that heat up excessively, because of the possible danger of fire due to tape igniting. *Never* use plastic tape for this purpose as it ignites easily.—J. A. COMSTOCK.



Completed aeriels are turned toward their respective transmitters. These aeriels could have been mounted on the same pole as the commercial aeriels in the background.

your attic, if you have a non-metallic roof.

When carefully directed toward the desired TV or FM station transmitter, these Yagi, high-gain type aeriels will give the best single (or dual) channel reception possible with any conventional antenna and are especially useful in the so-called dead or fringe areas. Though usually used to fill in the weak spots in commercial "all-channel" aeriels, these antennas may be used alone or in stacks.

First, calculate the materials needed and the dimensions of the components from the information given in Fig. 2 and Tables A (for TV aeriels) and B (for FM aeriels).

While there are six cross pieces called for in construction of the aeriels in the tables, as many as 10 could be used to improve signal strength. For extreme fringe areas, try adding two to four more directors, cut to the same length and spaced the same distance as the last director (L_6) in the table. If two close TV channels are available locally (other than 6 and 7, since the FM band lies between these channels), an aeriels cut for one of these channels usually will work well for the other. One of these aeriels, successfully bringing in channels 7 and 9, was dimensioned for TV channel 8, unused in the Seattle area where

Custom-Build Your TV and FM Aeriels

By R. W. MONTAGUE


ESPECIALLY tailored to receive tough-to-get channels, one or several of these antennas, cut for the needed channels, can be stacked on your present television mast or mounted in

the antenna is located.

It will be noted from Table A that aeriels for channels 2, 3 and 4 would be quite large, and it may be that another type of aeriels might be more

TABLE A—TV AERIALS

Band	Channel	Spacing Between Cross Pieces					Total Spar Length	Length of Cross Pieces					
		S_1	S_2	S_3	S_4	S_5		L_1	L_2	L_3	L_4	L_5	L_6
		(Inches)					S+4'	(Inches)					
Low VHF Band (54 to 88 mc)	2	41 ¹ / ₂	46 ¹ / ₂	38 ² / ₂	56 ¹ / ₂	55 ¹ / ₂	243 ¹ / ₂	96 ³ / ₂	87 ¹ / ₂	83 ³ / ₂	83 ¹ / ₂	81 ³ / ₂	80 ² / ₂
	3	37 ¹ / ₂	42 ³ / ₂	35 ³ / ₂	51	50	220 ³ / ₂	87	79	75 ¹ / ₂	75 ¹ / ₂	73 ¹ / ₂	73
	4	34 ¹ / ₂	38 ¹ / ₂	32 ³ / ₂	46 ¹ / ₂	45 ¹ / ₂	201 ¹ / ₂	79 ¹ / ₂	72 ¹ / ₂	69	68	67 ¹ / ₂	66 ¹ / ₂
	5	30 ³ / ₂	33 ² / ₂	28 ³ / ₂	40 ² / ₂	40	176 ³ / ₂	69 ¹ / ₂	63 ³ / ₂	60 ³ / ₂	60 ³ / ₂	59	58 ¹ / ₂
	6	28	31 ¹ / ₂	26 ¹ / ₂	37 ¹ / ₂	37 ³ / ₂	164 ³ / ₂	64 ¹ / ₂	58 ¹ / ₂	56	56	54 ² / ₂	54
			(Inches)					S+4'	(Inches)				
High VHF Band (174 to 216 mc)	7	13 ¹ / ₂	15 ¹ / ₂	12 ¹ / ₂	18 ¹ / ₂	17 ¹ / ₂	81 ¹ / ₂	31	28 ¹ / ₂	26 ² / ₂	26 ² / ₂	26 ¹ / ₂	26
	8	13	14 ¹ / ₂	12 ³ / ₂	17 ¹ / ₂	17 ¹ / ₂	78 ¹ / ₂	29 ² / ₂	27 ¹ / ₂	26	26	25 ¹ / ₂	25 ³ / ₂
	9	12 ¹ / ₂	14 ³ / ₂	11 ² / ₂	17	16 ² / ₂	76 ¹ / ₂	29	26 ¹ / ₂	25 ¹ / ₂	25 ¹ / ₂	24 ¹ / ₂	24 ¹ / ₂
	10	12 ³ / ₂	13 ² / ₂	11 ¹ / ₂	16 ¹ / ₂	16 ¹ / ₂	73 ¹ / ₂	28 ³ / ₂	25 ¹ / ₂	24 ¹ / ₂	24 ¹ / ₂	23 ³ / ₂	23 ³ / ₂
	11	11 ² / ₂	13 ³ / ₂	11	16	15 ² / ₂	71 ² / ₂	27 ¹ / ₂	24 ¹ / ₂	23 ³ / ₂	23 ² / ₂	23 ¹ / ₂	22 ³ / ₂
	12	11 ¹ / ₂	12 ² / ₂	10 ² / ₂	15 ¹ / ₂	15 ¹ / ₂	69 ¹ / ₂	26 ¹ / ₂	24 ³ / ₂	23	23	22 ¹ / ₂	22 ¹ / ₂
	13	11 ³ / ₂	12 ¹ / ₂	10 ¹ / ₂	15 ³ / ₂	14 ¹ / ₂	67 ¹ / ₂	25 ² / ₂	23 ¹ / ₂	22 ¹ / ₂	22 ¹ / ₂	21 ³ / ₂	21 ³ / ₂
Partial UHF Band	14	5 ¹ / ₂	5 ³ / ₂	4 ¹ / ₂	6 ² / ₂	6 ¹ / ₂	32 ¹ / ₂	11 ¹ / ₂	10 ¹ / ₂	10 ¹ / ₂	10 ¹ / ₂	9 ² / ₂	9 ² / ₂
	15	4 ³ / ₂	5 ¹ / ₂	4 ³ / ₂	6 ¹ / ₂	6 ¹ / ₂	32 ³ / ₂	11 ³ / ₂	10 ³ / ₂	9 ¹ / ₂	9 ¹ / ₂	9 ¹ / ₂	9 ¹ / ₂
	16	4 ¹ / ₂	5 ¹ / ₂	4 ¹ / ₂	6 ² / ₂	6 ¹ / ₂	32 ³ / ₂	11 ³ / ₂	10 ³ / ₂	9 ² / ₂	9 ² / ₂	9 ¹ / ₂	9 ¹ / ₂

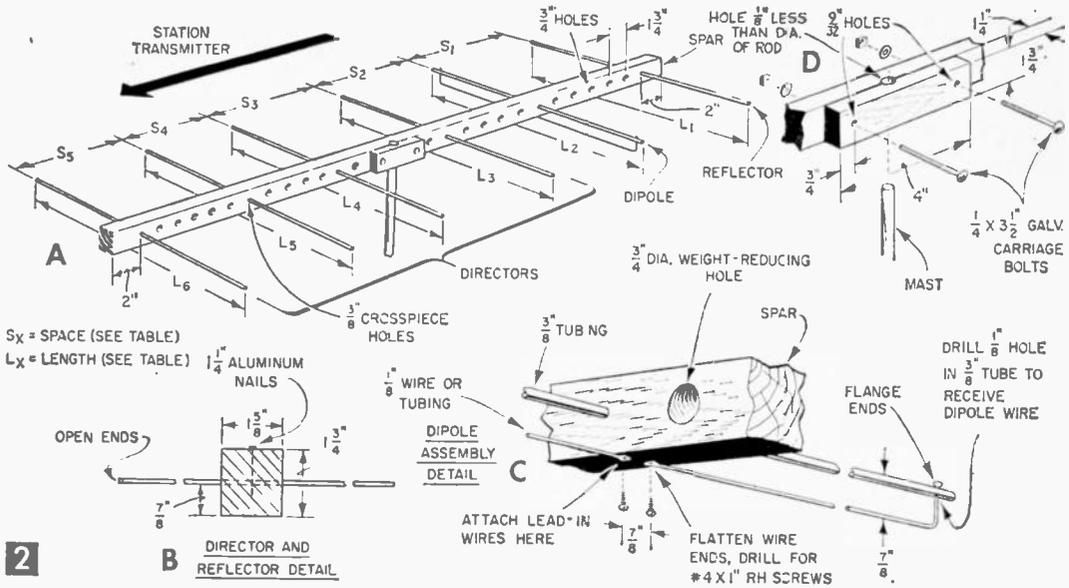

2

TABLE B—FM AERIALS

Calculate FM aerial dimensions as follows:

1. Learn the frequency of the particular FM station desired.
2. Calculate wave length in in. (W_i), using the following formula:

$$W_i = \frac{11,070}{\text{frequency (mc)}}$$

3. Prepare a table for the aerial desired, similar to those in TV aerial Table A:

S_1	S_2	S_3	S_4	S_5	L_1	L_2	L_3	L_4	L_5	L_6
$.215W_i$	$.240W_i$	$.20W_i$	$.290W_i$	$.285W_i$	$.495W_i$	$.450W_i$	$.430W_i$	$.430W_i$	$.420W_i$	$.415W_i$

EXAMPLE

A station operating on a frequency of 98 mc would have a W_i of: $\frac{11,070}{98}$ or 112.9 (112 $\frac{2}{3}$). Following the formula above would produce these specifications for an antenna:

S_1	S_2	S_3	S_4	S_5	L_1	L_2	L_3	L_4	L_5	L_6
24.2"	27.1	22.6	32.7	32.1	55.8"	50.7	48.5	48.5	47.4	46.8

desirable. However, the information is included in the table (which covers all VHF channels in the U. S. and Canada and some UHF) because in extremely bad signal areas this type of aerial would give the highest gain and may have to be used. Mounted in the attic these aeri- als would not be so conspicuous. UHF television channels higher than those given in the table are best received by other types of aeri- als; an extremely small Yagi would be difficult to build.

a number of $\frac{3}{4}$ in. holes as in Fig. 2A to reduce the aerial's weight without loss of strength. Cut cross pieces to length from $\frac{3}{8}$ -in. O.D. aluminum tubing, the size used in commercial TV aeri- als, and available from aluminum supply houses or salvage yards (occasionally it is obtainable free from TV repair shops). If using salvaged tubing, first clean off with fine sandpaper. If the tubing is not available, substitute $\frac{3}{8}$ -in. O.D. copper tubing or the heavier $\frac{3}{8}$ -in. aluminum rod (available from Sears, Roebuck and Co.).

Insert cross pieces, except the dipole, in the proper holes as in Fig. 2. Use paraffin to ease the metal through the tightly-fitting holes. Center the tubes and from the top of the spar, through the tubing, drill a hole for a $\frac{1}{4}$ -in. aluminum nail as in Fig. 2B and fasten securely.

Complete and assemble the dipole parts as in Fig. 2C, and check for fit. Remove one $\frac{1}{8}$ -in. wire section and insert the dipole into its spar hole. Complete the assembly, then flange the ends of the wires where they pass through the tube. In-

MATERIALS LIST—AERIALS

Amt.	Description
1 pc	* $1\frac{1}{2}$ x $1\frac{3}{4}$ " fir, pine or oak
6 pcs	* $\frac{3}{8}$ " O.D. alum. tubing or rod (copper can be substituted)
1 pc	* $\frac{1}{8}$ " (#10) copper or aluminum wire or tubing
1 pc	$1\frac{3}{4}$ x $1\frac{1}{2}$ x 4" fir, pine or oak
6	$1\frac{1}{4}$ " aluminum nails
2	$\frac{1}{4}$ x $3\frac{1}{2}$ " galv. carriage bolts, washers and nuts
2	#4 x 1" rh screws and washers
	varnish or paint
	misc. installation hardware and lead-in wire to match individual installation (see text)

* Length determined by specifications of desired aerial.

It also may be possible to select a frequency in the middle of the FM band and get good reception for the whole band with a single aerial. This depends on individual location problems and must be decided by the wearisome method of trial and error.

Start construction by cutting the $1\frac{1}{2}$ x $1\frac{3}{4}$ -in. wood spar to the length determined as explained above. Drill the $\frac{3}{8}$ -in. cross piece holes as in Fig. 2A, spacing as in Table A or B. Also drill

sert #4 x 1-in. rh screws with washers through holes drilled in the flattened end of the 1/8-in. tubing. These screws must be the same distance apart as the distance between the upper and lower dipole tubes. Lead-in wires will be attached to these screws.


At the center of your aerial, located by measuring and balancing, clamp a 1 3/8 x 1 3/4 x 4-in. piece of wood stock. Center a 1/4-in. hole 3/4 in. from each end of the block (Fig. 2D), insert 1/4 x 3 1/2-in. galvanized carriage bolts, washers and nuts, and draw up tightly. Center a hole in the top of this assembly, sizing it 1/8 in. under the diameter of the roof or attic aerial mast (usually a 1 3/4-in. dia. pole) and drilling with an expansive bit or hole saw. Apply at least three coats of spar varnish or marine quality paint to the now-finished antenna, allowing plenty of drying time between coats.

Install the aerial as in Fig. 2A, with the directors closest to the transmitter of the station desired. Where two stations will be brought in by the aerial, the latter will probably be best directed between the two transmitters. Try it before fastening permanently in place.

There are so many variables involved in aerial installations that it is impossible to describe one lead-in hookup that will work well in each case.

Roll-Up Aerial

• Stronger and clearer radio signals from greater distances are possible with an aerial made from a roll-up steel rule. To mount the rule cut a hole in the top of the radio cabinet and bolt a fiber washer to the hole so that the rule will not ground against the cabinet. Insulate rule housing from the set with friction tape, and fasten the housing to the cabinet with a strip of metal bolted to the cabinet. Solder one end of a length of insulated wire to the rule housing, and connect the other end to the aerial terminal of the set as shown in photo below. Range and volume increase as the rule is pulled out and are reduced as the rule is pushed in.—M. A. TIDD.

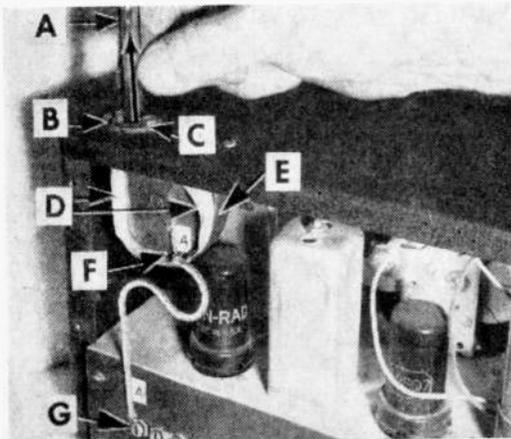


(A) Steel rule, (B) fiber washer, (C) bolts, (D) friction tape, (E) metal strip, (F) solder wire to case, (G) aerial terminal.

The trial and error method must usually be resorted to in the end. It sometimes is possible to just tie lead-in wiring for the new aerial almost any place into the existing lead-in wire to the set (using standard 300 ohm double-strand television wire) if the new aerial is being used to supplement another aerial. If this doesn't give a good picture or interferes with other channels received, a hi-lo coupler may be needed. Low-band channels (2 through 6) will probably have to be led in through a coupler if high band channels (7 through 13) are also received. As a last resort, a completely separate lead-in wire may be used by coupling into an antenna switch (available from TV supply stores, Allied Radio, Dept. SM, 100 N. Western Ave., Chicago 80, Illinois or Sears, Roebuck & Co., Chicago) at the back of the television set. However a 40¢ double-throw knife switch available in hardware stores would serve, though less conveniently. When the aerial is installed and hooked up, make fine direction adjustments by turning the aerial slightly in each direction until the best picture is obtained.


These aerials can be stacked on one roof pole about a foot apart, if desired, although aerials pointing in the same general direction should be two feet or more apart, if possible.

Soldering-Iron Switch

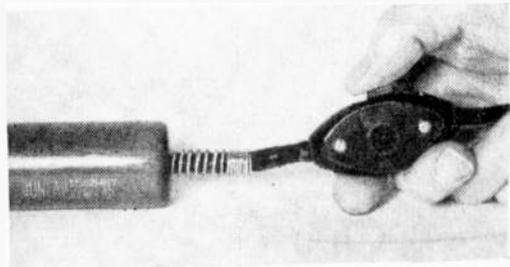• Install a feed-through tumbler switch with "on" and "off" markings on it on the cord of your electric soldering iron close to the handle, as



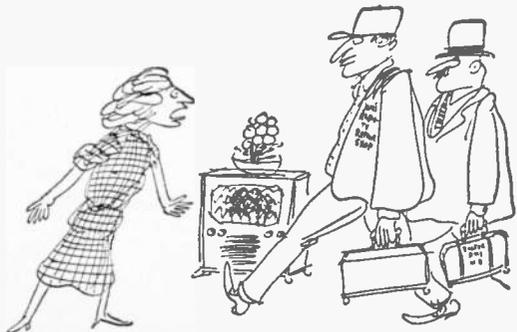shown in the photo. The iron can be kept plugged in while in use and simply turned on or off as needed.—ARTHUR TRAUFFER.



Thank goodness, you're here! My husband is sick in the bedroom—and Jack Paar's all blurry!

Experimenting with a one-stage audio amplifier.


THERE are two possible approaches to follow in obtaining a radio lab kit. One is to acquire the parts yourself and make up your own kit. The second approach, and the approach that I consider best for beginners, is to buy a commercial kit. I tried both approaches.

The home-rolled version was built on a miniature perforated bakelite board. The board layout, component placement and preliminary wiring are shown in Fig. 2 (front) and Fig. 3 (back). Lay out and drill the board first. Shorten the volume control shafts to $\frac{3}{8}$ in. length with a hack-saw. Solder leads about $1\frac{1}{2}$ in. long on the transistor sockets. Mount the parts and complete the wiring to the interconnection lugs (called "flea clips"). Fill the portions of the flea clips that protrude from the front of the board with solder for increased rigidity. The transistor sockets are held in place with Duco cement. Bend the leads tightly against the board as an added precaution.

A separate battery board cut from a piece of perforated Masonite (see Fig. 4) was provided, the batteries held in place with rubber bands. Brackets provided with machine screws make terminal contact. A third bracket provided with a metal spring cut from a tin can makes the connection between the two rows of batteries. The experimental board may be mounted on the battery board with brackets, or it may be used unattached as shown in Fig. 4.

The hook-up of Fig. 4 is the simple one-transistor audio amplifier shown schematically in Fig. 5A. A number of additional, but by no means all of the circuits that can be built with the home-rolled lab kit are also shown in Fig. 5. The resistors and all of the capacitors aren't mounted on the board. They were originally connected by plugging them into the flea clips. However, this wasn't too satisfactory and mini-gator clip leads were adopted for all connections.

The audio one-transistor amplifier of Fig. 5A has very low volume. If another transistor amplifier is connected in front of this amplifier, the two-transistor amplifier of Figure 5B results, with much greater volume. The transistor configuration used is known as the common emitter circuit because the emitters of the transistors are both connected to an input terminal and the common battery terminal. The capacitors between collector of T2 and between the base of T1 and volume control center terminal and base of T2 are provided to allow all audio signals to pass, but to prevent transistor bias voltages from being upset. A capacitor has low impedance for ac voltages, but it has (ideally) infinite impedance

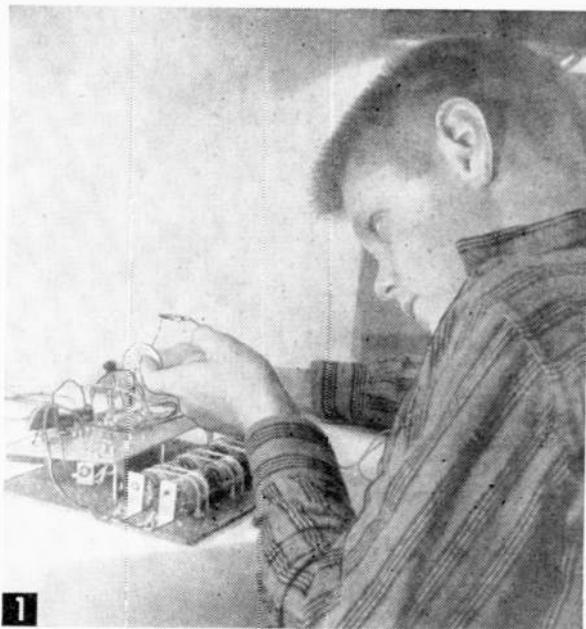


Learning Electronics By Experimenting

"Breadboard" experimentation is a logical way for a beginner to learn electronics, and the approach has considerable merit for the old-timer, too, because it allows him to try his ideas quickly with comparatively conventional parts


By FORREST H. FRANTZ, Sr.

for dc voltages. The resistors in the circuit establish the dc bias voltages on the transistor elements that are required to make the transistors function.

It is apparent then that there are two basic groups of voltages that you are concerned with in any piece of electronic equipment. One is the voltage required to make the transistors or tubes function at all—the dc bias voltages. The other is the signal voltage which is the voltage of interest. The dc bias voltages are somewhat like the gasoline requirement in an automobile and might be thought of as fuel supplied at the right place in the proper amount. The input signal voltage corresponds to the driver's demands of the automobile which he injects at the input in the form of throttle and steering commands. The

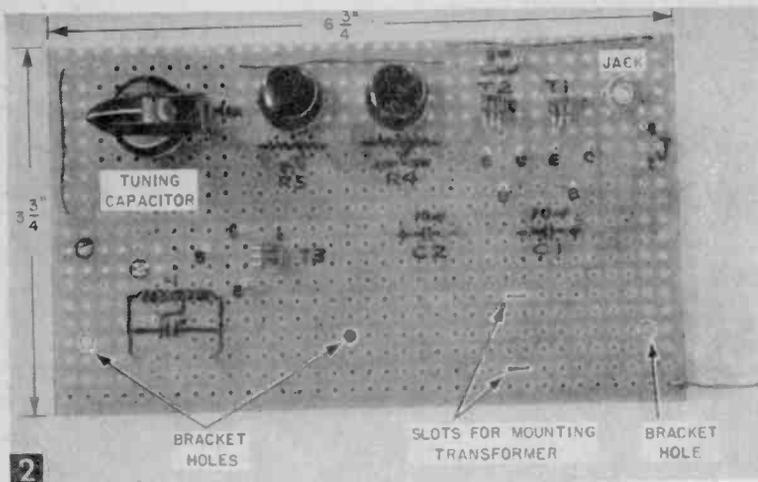


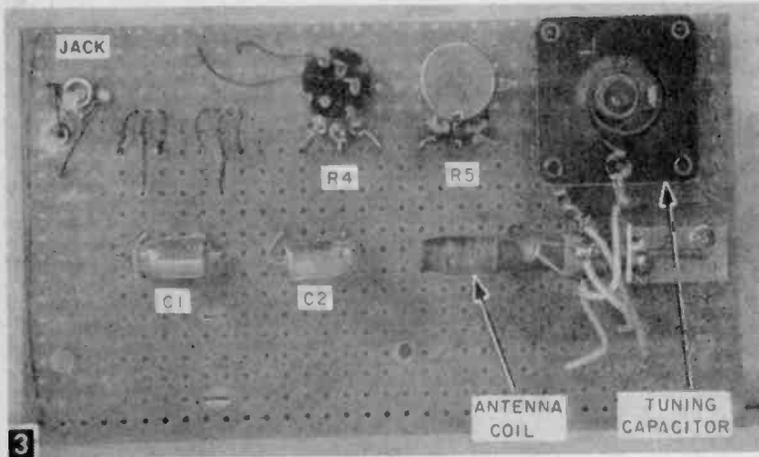Front view of home-made lab kit circuit board.



Back view of home-made lab kit circuit board.

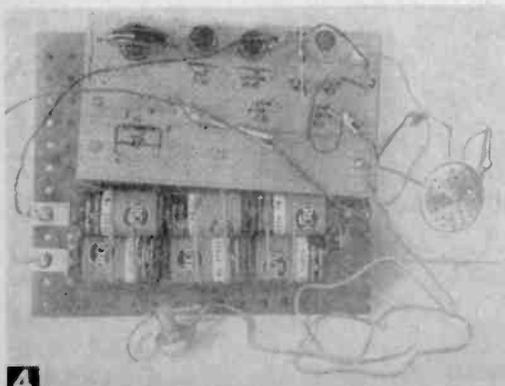input signal is handled by the electronic equipment as required (in this case it's amplified) for the desired output. The mechanical, electrical, and pneumatic systems of an automobile operate on the driver's input signals in an analogous way to provide the required energy and direction at



One-stage audio amplifier hook-up.

the wheels. The two-transistor amplifier may be used with the microphone (as shown) or with a phono pick-up, or with a radio tuner.


If the amplifier output is connected to the amplifier input as shown in Fig. 5C, an audio oscillator is created. An oscillator is a device that converts dc operating voltage into an ac signal. It may be thought of as an ac generator driven by a dc voltage. The advantage of an electronic generator (oscillator) is that the frequency may be varied and controlled very readily. The frequency of the oscillator of Fig. 5C may be varied by adjusting the control that functioned previously as a volume control for the amplifier.

The principle of the oscillator's operation is that a part of the signal at the output is fed back into the input and is continually recirculated. The amplifier action of the basic unit builds the signal at the input back up to the proper level for the output signal continuously.


How do you start it?

Well, all electronic equipment has an amount of noise associated with it. Although this noise is very low, the amplifier will build it up to a point where the transistor characteristics, part values, and dc operating voltage in the circuit limit the output signal size. But at this point, the output signal is high enough to be useful. A key connected in one of the leads from the battery to the amplifier as shown in Fig. 5D would permit quick turn-on and turn-off of the oscillator, and the unit could be used as a code practice set.


Figure 5E is a crystal detector tuner which may be added to the amplifier of Figure 5B to produce a broadcast receiver. The coil-capacitor combination builds up the radio frequency (RF) voltage received from the antenna at a particular frequency determined by the tuning capacitor setting. The tap on the coil permits the signal to be fed to the crystal diode without disturbing the tuning. The crystal diode is a unidirectional device; that is, it passes a signal readily when the anode side is plus, but impedes the signal when it's minus. The waveforms show: A, an RF signal which is the carrier and has the fre-

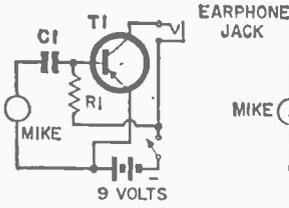


A. 1-TRANSISTOR AUDIO AMPLIFIER

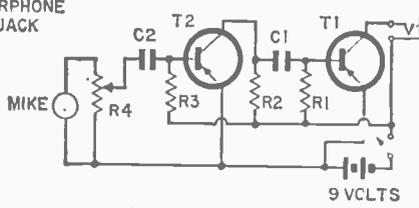


B. 2-TRANSISTOR AUDIO AMPLIFIER

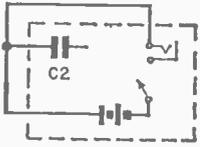

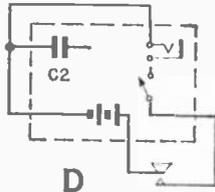C. WITH MIKE DISCONNECTED FROM CIRCUIT 5B AND FEEDBACK CONNECTION SHOWN, YOU'VE CREATED AN AUDIO OSCILLATOR



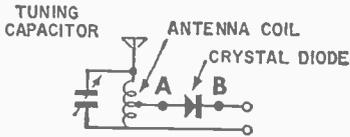D. KEY IN SERIES WITH BATTERY LEAD CONVERTS UNIT OF 5C TO CODE PRACTICE OSCILLATOR



E. SIMPLE TUNER CONNECTED IN PLACE OF MIKE IN 5B CONVERTS UNIT TO SIMPLE RADIO

WAVE FORMS




WITH BY-PASS CAPACITOR FILL-IN

quency of the capacitor-coil tuned combination modulated in height (amplitude) by an audio signal which is the desired signal information; B, the signal rectified (negative excursions chopped off) by the diode as it would appear between the crystal diode cathode and common if no capacitance appeared across these terminals; and C, the audio signal that appears at these terminals due to alternate charging and discharging of a capacitor connected across these terminals. In the case of the simple receiver consisting of this detector and the amplifier of Figure 5B, this fill-in is provided by the capacitance of C2 through the base to emitter circuit of T2 and the stray wiring capacitance of the circuit.

The Commercial Kit. This kit (Knight 10-Circuit Transistor Lab Kit, Allied Radio Catalog No. 83Y299, \$15.75) costs a little more than the basic, home-rolled version just described, but with it you can perform twice as many experiments.

Figure 6 shows the parts and instructions furnished with the kit. There's a preliminary wiring manual which describes the basic assembly in step-by-step and pictorially illustrated detail, and a folder with general soldering and construction information. A set of cards showing how to make plug-in connections between the various parts for each of the 10 circuits is included with the kit. The card for a given circuit fits on the board as shown in Fig. 7, and connections are made with plug leads. There is also a manual of experiments provided in the kit. This manual shows a pictorial and a schematic diagram for each circuit and provides

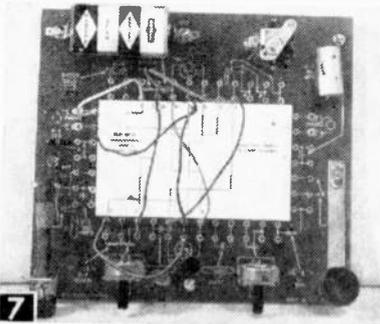

The Knight 10-in-1 Transistor Lab Kit with the Electronic Switch Circuit set up.

Parts and instructions furnished with Knight 10-in-1 Transistor Lab Kit.



6

scale meter deflection will be changed. The transformer primary voltage for full scale meter deflection is calculated with equation 5b on Table A:

$$E_p = 1.5 \sqrt{\frac{750,000}{7,500}}$$

$$E_p = 15 \text{ volts}$$

The new sensitivity of the meter is 750,000 ohms-per-15 volts or 50,000 ohms-per-volt!

For ranges other than 15-v full scale, the multiplier series resistance will be 50,000 times (Voltage Range minus 15). Thus, for the 50-v scale, the multiplier resistance is 50 x (50 - 15) kilohms, or 1.75 megohms.

This can be improved, however, and approached more practically. The lowest range (15 v) has a low dc resistance in spite of its high ac impedance. This might interfere with circuit op-

TABLE B

In Fig. 9, signal generator output is adjusted for full scale deflection of meter "M" at 1,000 cycles. V_1 and V_2 are measured with an audio voltmeter such as the Heathkit AV-2.

Then:

- a) $V_3 = V_1 - V_2$
- b) $I = \frac{V_2}{R}$
- c) $Z_{in} = \frac{V_3}{I}$

For example 2, measured values are:

$R = 1K, V_1 = .75V, V_2 = .15V.$

Then,

- a) $V_3 = .75 - .15 = .6V$
- b) $I = \frac{.15}{1000} = .15MA$
- c) $Z_{in} = \frac{.6}{.15 \times .001} = 4,000 \Omega$

and $\sim V$ sensitivity = $\frac{4000}{.6} = 6,650 \frac{\Omega}{V}$

eration. A capacitor (0.1 mfd or larger) in series with the primary will eliminate this possible source of trouble. A transformer that has the correct impedance used might be difficult to find at a reasonable price. A considerable reduction in transformer impedance can be tolerated if the impedance ratio is unchanged without changing the final ohms-per-volt sensitivity. For this example an impedance ratio of 50,000 ohms to 500 ohms will be satisfactory if the transformer can handle the input signal level linearly.

If the lowest range of the basic meter in our first example had been 5 v, the new lowest ac range would have been 50 v. This would have

MATERIALS LIST—HOME-MADE TRANSISTOR LAB KIT

Desig.	Description
R2	10K, 1/2w resistor
R1, R3	220K, 1/2w resistor
R4	10K miniature volume control with switch (Lafayette VC-28)
R5*	50K miniature volume control (Lafayette VC-36)
C1, C2	10 mfd., 15v. miniature electrolytic capacitors (Lafayette CF-122)
	tuning capacitor (Lafayette MS-215)
	antenna coil (Lafayette MS-299)
T1, T2	transistor (Raytheon CK722 or GE 2N107)
D	diode (GE 1N64)
	three transistor sockets (Lafayette MS-149)
	fla clips (Lafayette MS-263)
	miniature perforated board (Lafayette MS-305)
	two miniature knobs (Lafayette MS-185)
	one pointer knob (Allied 55H074)
	miniature phone jack (Lafayette MS-282)
	minigator clips for connecting leads (Mueller 30)
	perforated Masonite board (Lafayette ML-81)
	brackets
	six batteries (Burgess #1)



* Not used in any of the circuits presented in text, but handy to have for experimental work.

beer, objectionable. Here's an approach that can be applied to a multimeter or even a basic dc meter movement which overcomes this objection. The Heathkit MM-1 meter cited in example 1 has a 150 microampere lowest current range on the selector switch. Set the meter to this range and connect it to a rectifier bridge consisting of 4 Raytheon 1N66 diodes (see Fig. 9). Instrument the circuit as shown in Table B. The input impedance of the rectifier-meter combination was 4,000 ohms for full scale meter deflection. The sensitivity was 6,650 ohms-per-volt.

Next, the meter-bridge combination was connected in the circuit shown in Fig. 10. The transformer, a Microtran M8, was connected for 15,000 ohms primary impedance (red and blue leads), and 600 ohms secondary impedance matching (brown and violet leads). The impedance ratio is 25, and the square root of this ratio is 5. The transformer primary impedance predicted by the theory is 25 x 4,000 or 100,000 ohms, and the sensitivity is predicted as 5 x 6,650 or 33,200 ohms-per-volt. The voltage input to the transformer primary for full scale deflection should be 100,000 ohms divided by the sensitivity, 33,200 ohms-per-volt. The predicted primary voltage is 3 v. The actual voltages measured in the circuit are given in the caption for Fig 10. Using the method shown in Table B, these voltages yield the same results as those predicted above within a reasonable percentage of error.

The linearity of the instrument can be improved by setting the meter pointer about 3% to 5% up scale from zero.

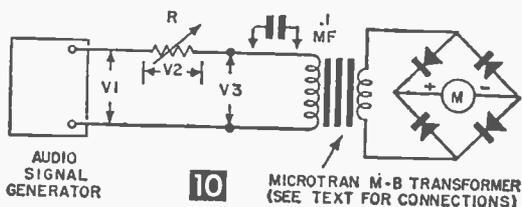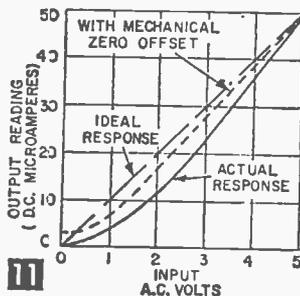The linearity of a transformer-diode-rectifier-meter type ac voltmeter can be improved by off-setting the meter needle from zero and calculating series resistance for exact fit at full scale.



Method used for experimental verification of calculations: $V_1 = 5$ volts; R (60,000 ohms) adjusted for full-scale deflection of M . V_2 was 1.9 volts. Calculated value of Z_{in} is 103 K ohms, sensitivity is 33,400 ohms per volt using the measured values.

Use the mechanical zero set with zero voltage input to do this. Do it before the measurements shown in Fig. 9 are made. This automatically accounts for the upscale dial position in calculations and adjusts the full scale point. The results of the technique are shown in Fig. 11.

It is apparent that the method of the second

example provided a lower bottom ac voltage range than the first method. This improvement resulted from the increased sensitivity of the rectifier-meter combination and the lower impedance ratio of the transformer windings. The decrease in transformer impedance ratio reduced the sensitivity.

ELECTRONICS ANAGRAM

Here is an anagram puzzle that will challenge your knowledge of electronics. To be absolutely sure you do

(For the solution, see page 154.)

ACROSS:

- 1) A point of maximum current or voltage in a stationary wave system.
- 3) Form of phono turntable drive.
- 5) Done with an insulated tool to avoid detuning effects of body capacitance.
- 8) Volt-ampere (abbr.).
- 9) A concentrated number of these will burn the screen of a cathode-ray tube.
- 10) Unit of loudness.
- 11) Volts times amperes.
- 14) Carries electrons in motion.
- 15) Capacitors block it.
- 17) A type of frequency meter.
- 19) The rms value of an alternating current wave.
- 20) One-millionth of an ampere.
- 21) A radiator of electromagnetic waves.
- 22) Inductive opposition to ac (abbr.).
- 23) Done to locate a microphonic tube.
- 24) A particular type of test instrument widely used (abbr.).
- 25) Potential placed on a certain vacuum tube element (letters symbol).
- 27) Done to improve operating characteristics of electronic components.
- 28) An amplifier that handles power (abbr.).
- 29) A TV station's pic-

- ture signal is put on a carrier wave in this manner (abbr.).
- 30) A circuit that can bite.
- 31) Matching transformer.
- 32) A primary color used in color TV.
- 35) Unit of conductance.
- 36) What a volume, gain, or tone control is.
- 37) A coil that opposes RF currents.
- 39) Connection not made (abbr.).
- 41) Figure of merit (letters symbol).
- 42) Transformer, trimmer (letters symbol).
- 43) EMF unit.
- 44) Capacitance (letters symbol).


- 45) Single side band (abbr.).
- 46) A noise made by electrons in vacuum tubes.
- 49) Modulation similar to frequency modulation (abbr.).
- 50) Term connected with 'scopes.
- 51) Main oscillator (abbr.).
- 54) An inert gas (abbr.).
- 56) What a ham calls his radio outfit.
- 57) Controlled by radio (abbr.).
- 58) An antenna system of two or more vertical radiators.

- 4) A particular type of transducer.
- 5) The electron catcher of a vacuum tube.
- 6) Code that is periodically interrupted.
- 7) Number of interconnected stations.
- 12) The kind of signal ordinarily superimposed on a carrier wave (abbr.).
- 13) Captures certain frequencies and disposes of them.
- 16) A positive ion.
- 18) To eliminate audio echoes.

DOWN:



- 1) An electro-acoustic unit of power.
- 2) Fleming invented the first one.
- 3) To send radio waves into space.

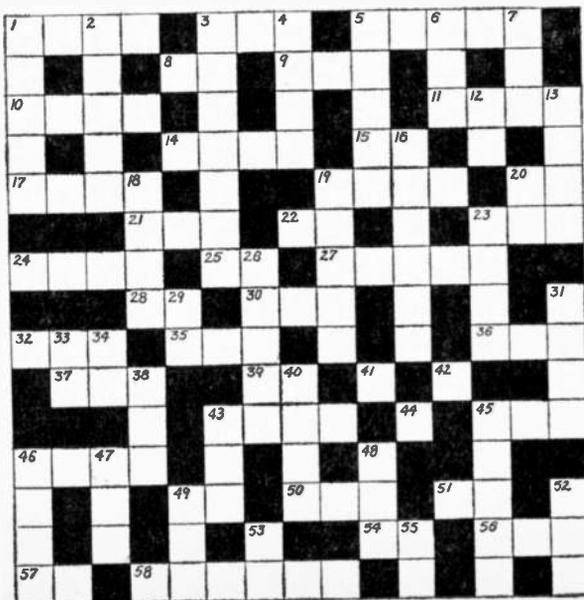- 19) Same meaning as #5 down.
- 20) Same as #20 across.
- 26) Plays recordings.
- 33) Voltage drop measured across a resistor (letters symbol).
- 34) A device that finds directions.
- 38) A tube that utilizes an electron gun (abbr.).
- 40) Temporary connector.
- 43) A meter that measures volts, ohms, and amperes (abbr.).
- 45) Might blow a fuse.
- 46) Emits sound waves (abbr.).
- 47) A meter rating.
- 48) Type of transistor (abbr.).
- 52) A gain compensating circuit (abbr.).
- 53) Output power.
- 55) C-bias (letters symbol).



Portable Earphone Plug Box

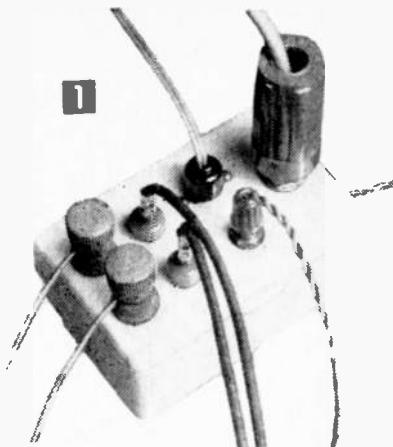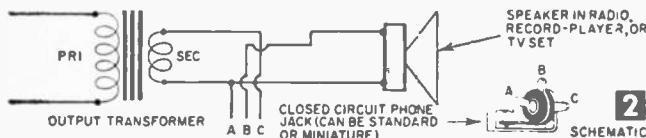You can quickly connect various sizes and types of earphone jacks to your radio, Hi-Fi, recorder or TV set with this versatile "Jack in the Box"



Built in less than an hour, this "Jack Box" accommodates five kinds of non-interchangeable earphone and speaker connections, permitting instant hookup of many combinations.


HERE'S an easy project for you Hi-Fi fans and experimenters who are so often annoyed by the fact that earphones as well as radios, record players, recorders, etc. come with non-interchangeable plugs and jacks.

If you want to plug in earphones that fit one piece of equipment, into another, you may have to either cut the wire and put on a new plug, or make a special adapter—by then, the program you wanted to hear is over. Here is an unusual answer to the problem; a plug box (Fig. 1) that accepts every common kind of plug. Also, it can be used to connect several earphones, or speakers at once, and will come in handy for test work and hi-fi experimenting.

Figure 1 shows a 3 x 2 x 1 1/4" deep hinged plastic box. In its lid are mounted two binding posts, a pair of standard phone tip jacks, and three other commonly used phone jacks. You don't need a blueprint giving sizes and locations of holes. In fact, you may want to modify the layout to fit the special needs of your equipment. Just mount the parts where you please, making sure they are not too crowded. All the holes are quickly made by reaming up to size with the small pointed end of a pen-knife blade.

Wire all the plugs in parallel (Fig. 2), with 20 gage solid copper wire soldered at each connection. If the spring prongs on the large phone jack are too long, bend the ends over to fit. Solder a length of light twin lead, or twisted lead wire to the prongs of the phone jack, and bring it out through a hole in the box side.

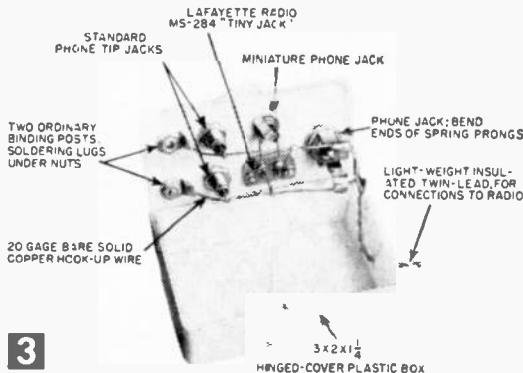The phone box is connected to the radio, record player, or TV speaker through a circuit



Holes in plastic box lid for mounting parts are reamed up to size with small knife blade. The jacks are wired in parallel, with solid copper hook-up wire.

opening jack. When the phone box is plugged in, the speaker is off; remove the plug, and the speaker is automatically reconnected.

Some ac-dc table radios ground one side of the output transformer, and of the speaker coil, directly to the chassis. If there is a wire leading from one side of the speaker coil directly to the metal chassis, your set is this type. With such a set, your earphones would be "hot" when the power plug of the radio is inserted one way into the power outlet. Eliminate the hazard simply by unsoldering the two chassis connections and wiring them directly together without electrically contacting the chassis.

Before touching any chassis parts, especially of TV sets, pull the power plug, and discharge the high-voltage capacitors, which can cause fatal shock.

If you are a stereo fan, you will easily be able to adapt the plug box to a "twin channel" design. A larger plastic box will provide space for mounting two sets of jacks, and the unit will make it easy to experiment.—ART TRAUFFER

MATERIALS LIST—PHONE PLUG BOX

No. Req.	Size and Description
1	3" long x 2" wide x 1 1/4" plastic box with deep-hinged cover (available in 10-cent stores, etc.)
1	Standard single phone jack, Switchcraft #12B (Allied 41H-632)
2	Miniature phone jacks of the type needed to fit your plugs
2	Standard phone tip jacks
2	Standard binding posts, with soldering lugs to fit
1	Short length lightweight insulated twin-lead, or twisted-lead wire
Misc. Machine screws, nuts, washers as required	

Save Over \$90—Build Your Own

ELECTRIC GUITAR

By J. EVANS KNAPP

Craft Print Project No. 277



2




1

Perfect formula for serenading a lovely lady: one electric guitar, playing through the phonograph connection of a table-model radio.

VERY few instruments have enjoyed the meteoric rise in popularity the guitar has in recent years. Long established as an ideal portable instrument for accompanying ballads, country and western singers, the guitar of not so many years ago still had its limitations. One was that its music was too soft to be used in orchestras (or at noisy parties).

That's not true today, thanks to the magic of electronics. For, when you hook up an amplifier to a guitar, you automatically give it the same stature as a piano—and far more versatility. You get, not only a full range of volume, but a complete control of tone—everything from throbbing base for rhythm chords to pure, treble melody notes to lead or back up the singer. You find, suddenly that guitars can “talk” sweet or sassy, soft or sharp, boogie beat or ballad strum.

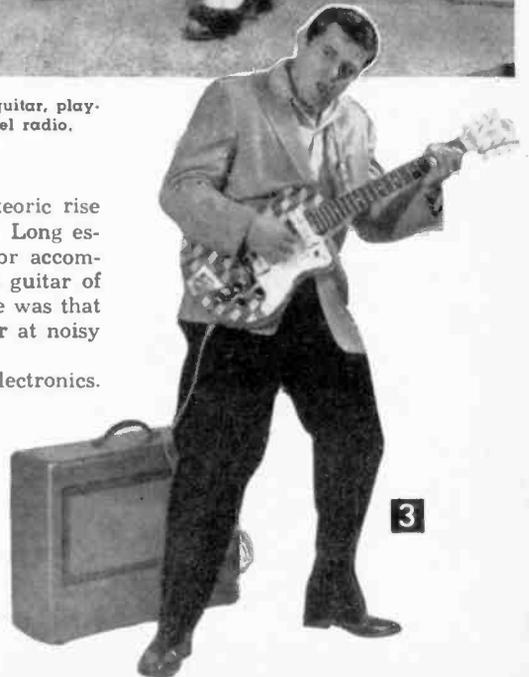A good guitar deserves a good carrying case. Make the box dimensioned in Fig. 20A, using glue and $\frac{3}{4}$ in. nails at all joints. Then, mark a line on the ends and sides 2 in. from the top and saw the box in two parts, making a top and bottom section. Sand all edges, rounding them



3

Electric guitar hooked up to a commercial music amplifier. Looks as if this fellow enjoys his rock-billy crooning.

slightly and cover the outside of both top and bottom sections with leatherette. Use waterproof glue or cement and wrap the leatherette around on the inside surface about 1/2 in.

Next, place 2 1/2 in. thick blocks of balsa along the sides and ends of the bottom section and

place your guitar on top of the blocks. Mark around the guitar forming a pattern or outline of the instrument on the balsa blocks. Allow about 1/16 in. clearance all around for the plush fabric covering. Remove the blocks, cut to shape and replace for testing. Also make up the neck

block and latch, and the compartment sides. With all of the blocks cut to size, place them in the bottom section together with the guitar to see that everything fits well. Make any adjustments needed and cut a 1/16 x 3/8 rabbet along the upper edges of the blocks that contact the box sides. Then glue the blocks to case bottom and sides.


When covering the blocks with the plush fabric, cement the fabric to the tops first. Allowing enough material to fold over the inside edge about 1/2 in. and force the other edge down into the rabbet with a dull knife (Sec. A-A, Fig. 20). Then cement a strip around the vertical sides of the blocks, allowing about 1/2 in. of material to fold flat against the bottom and turn in at the top where it is sewed to the top covering. For the bottom, cut a piece of cardboard the shape of the recess, cover with fabric wrapped around the edges and cement to the bottom of the case. To line the inside of the top or cover, cut pieces of cardboard to cover the sides and underside of top, cover with fabric and cement (Fig. 20).

Fasten the top of the case to the bottom with 1 in. brass butt hinges, install a pair of suitcase catches and suitcase handle to the other side.

Electric guitars are not only more versatile, but they are far easier to play than non-electrics.

But What Will It Cost? The price of guitars ranges from \$15 to \$25 for a second-hand, low cost, non-electric one, up to \$500 or better for a few of the electrics some professionals use. One excellent commercial model electric with four volume and tone controls and about the same size as the one shown in Figure 1, costs around \$136 new, with its case. In contrast, this guitar with its case will cost you about \$40 to \$45 for materials.

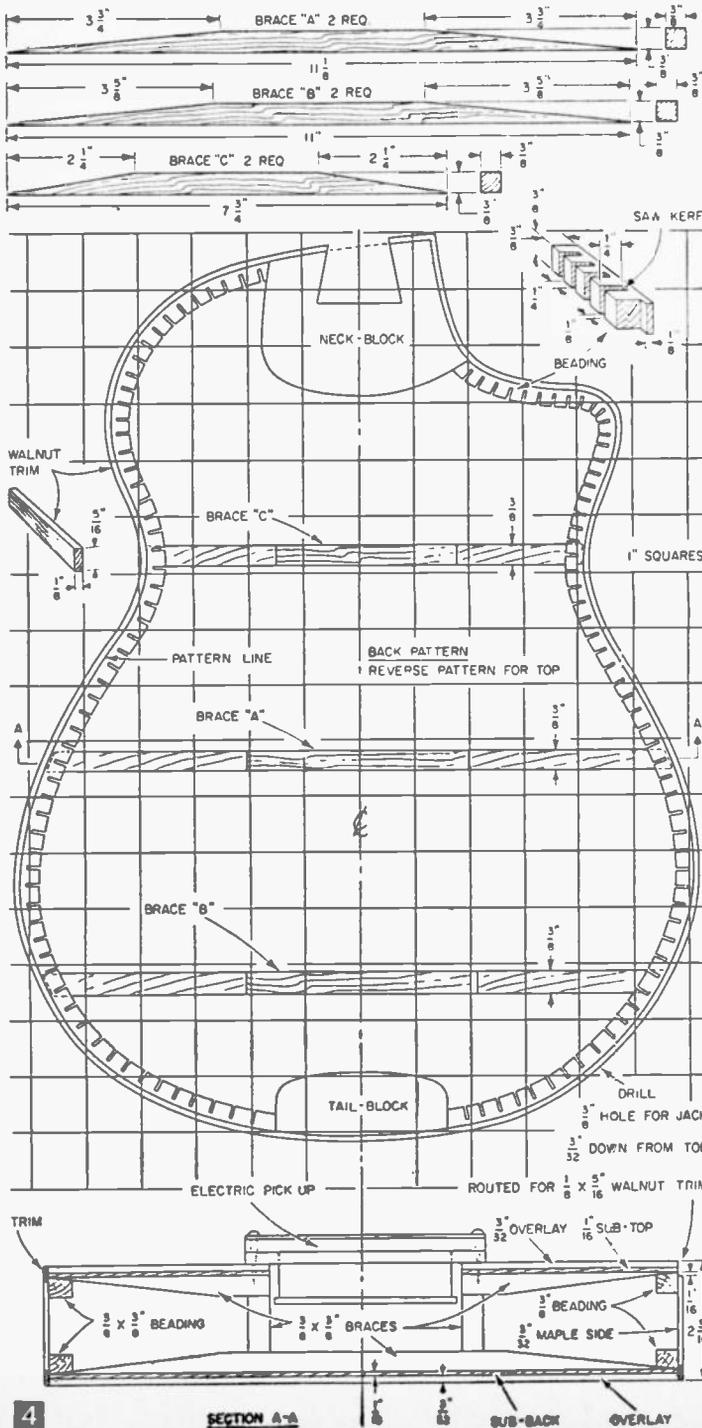You can, of course, use it with a special musical amplifier such as that shown in Fig. 3. But such amplifiers are costly, and a better



4

SECTION A-A

SUB-BACK OVERLAY

solution for the budget-minded, is to play the guitar through a radio (Fig. 1) or an old tape recorder (Fig. 11).

Start construction by making a full-size drawing of the guitar body (Fig. 4), on single weight illustration board. (Because it is impossible to show these parts full size on the magazine page, full-size drawings are available. See box at end

MATERIALS LIST—ELECTRIC GUITAR

No.	Size and Description	Use
2 pc	2 1/4 x 10 x 24" pine or hemlock	side bending form
2 pc	3/4 x 5 5/8" six foot pine	steam box
2 pc	3/4 x 3" six foot pine	steam box
2 pc	1/2 x 16 x 20" plywood	gluing clamp
1 pc	1 1/8 x 2 1/4 x 3 1/2" pine or hemlock	neck-block
1 pc	1 1/8 x 1 7/8 x 2 3/4" pine	tail-block
2 pc	3/16 x 13 1/2 x 39" plywood	case

The above can be purchased from your local lumber yard.

1 pc	3/4 x 1 7/8 x 60" maple	sides
1 pc	3/4 x 4 x 24" maple	overlay
1 pc	3/4 x 4 x 24" walnut	overlay
1 pc	3/4 x 4 x 24" mahogany	overlay
1 pc	2 1/2 x 4 3/4 x 30" maple	neck
2 pc	1/4 x 5 x 39" poplar	case
2 pc	1/4 x 5 x 13" poplar	case
4 pc	1/8 x 8 x 20" pine or poplar	sub-top and back
1 pr	1" butt hinges	case
1 pr	suitcase catches	case
1	suitcase handle	case
1/2 pt	paste wood filler, natural transparent	case
1 pt	clear glass varnish	case

The above can be purchased from Craftsman Wood Service, 2729 So. Mary St., Chicago 8, Ill., or from Albert Constantine & Son Inc., 2058 Eastchester Road, New York 61, N. Y.

12	1/4 x 1/4" Alnico magnets	
Magnets can be purchased from Ronald Eyrich, 12720 Robin Lane, Brookfield, Wisconsin. (12 for \$3.00. postpaid.)		
1/2 lb	#40 Nylclad magnet wire	pickup coils
6 ft	#20 single strand shielded grid wire	hookups
6 ft	varnished spaghetti	hookups
2	1 Meg type 11-137 volume controls	hookups
2	500K type 13-133 tone controls	hookups
4	3/4" walnut knobs	hookups
1	type 11 Little-Jax phone jack	hookups
1	type 1452 2 pole 3 pos. shorting type lever action switch	hookups
2	.001 600 stock 305 Olson capacitors	hookup
1 roll	Scotch #33 plastic backed electrical tape	

The above can be purchased from Allied Radio Co., 100 N. Western Ave., Chicago 80, Ill.

1 pr	#2140W patent or machine heads	
1	#2158 rosewood adjustable bridge	
1	#2172 bone fingerboard nut	
1	#2179 rosewood oval 25 1/4" scale fingerboard	
1	#2160 trapeze tailpiece	
1 set	#3044 Lektro-Magnetic strings for the electric Spanish guitar	

The above numbered parts are from catalog of Continental Music, 717 Chicago Ave., Evanston, Ill., and Atlanta, Ga., (distributors). Purchase from your local music store, or from Carvin Co., Box 287, Covina, Calif.

1 pc	4 x 25 1/2" tooling leather	lanyard
1	5/8" keeper	lanyard
1	5/8" watch band buckle	lanyard
1	No. 3202 swivel lanyard hook	lanyard
1	Lignum Vitae circle (Edgeslicker)	lanyard
1 pt	Neat-Lac beeswax	lanyard


The above can be purchased from Tandy Leather Co., Box 791, Fort Worth, Texas.

1 pc	3/16 x 1 1/2 x 4 1/2" white opaque plastic	pickup
1 pc	1/4 x 3 x 4 1/2" white opaque plastic	pickup
1 pc	1/16 x 6 1/2 x 12" white opaque plastic	pickup and pick guard

The above plastics can be purchased from Cadillac Plastic Co., 727 W. Lake St., Chicago.


2 yds	36" width upholstery fabric	case
3 yds	36" width Duron plastic	case
28	1/4 x 4" carriage bolts	gluing clamp
28	1/4" thumb or wing nuts	gluing clamp
1 box	#18 3/4" wire brads	case

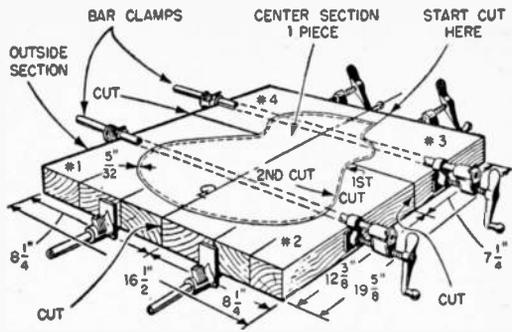The above can be bought from your local Montgomery Ward Co.




5 BENDING FORM

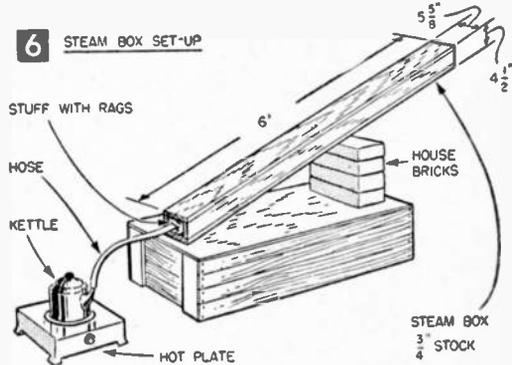SEVERAL PIECES OF 2 1/4" THICK STOCK, GLUED TOGETHER TO MAKE ONE PIECE



6 STEAM BOX SET-UP

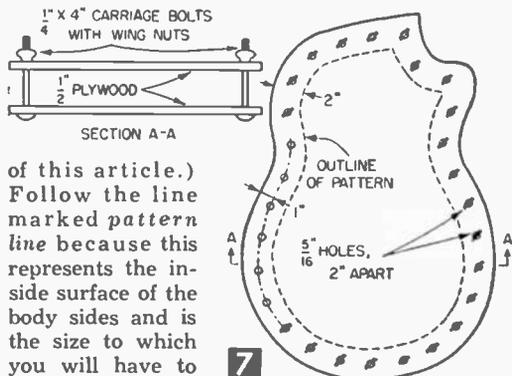

of this article.) Follow the line marked pattern line because this represents the inside surface of the body sides and is the size to which you will have to make the center

portion of the bending form. With a knife, carefully cut out the drawing. Draw in the neck and tail blocks, but do not cut them out at this time.

The bending form (Fig. 5) consists of five sections; one center section, and four outside sections surrounding the center section. Make the form from any soft wood you may have on hand by gluing up 2 1/4 in. thick pieces to make up a block 16 1/2 x 20 in. Use Weldwood or Elmer's Waterproof glue because the part to be bent will be moist from being steamed.


Mark a centerline on the block dividing the 16 1/2 in. width and fasten the pattern on the center of the block with two thumbtacks. With a sharply pointed pencil, draw around the pattern and then, using a compass as a marking

gage, draw a second line around the pattern $\frac{5}{32}$ in. from the first line. Starting at the top of the body design as indicated in Fig. 5, saw the five bending form pieces to shape on a bandsaw or jigsaw. The material between the two lines is waste, so make your saw cuts in this waste material leaving just a trace of the penciled lines on the center and outside form sections. Two saw cuts will be required. With the center portion cut out, rout out a $\frac{1}{2} \times \frac{1}{2}$ in. rabbet around the top corner as shown in sec. A-A of Fig. 4, to provide clearance for the $\frac{3}{8} \times \frac{3}{8}$ in. beading. Then saw the outside form into four sections.


Make the steam box Fig. 6 next. Set it up on a low bench or box and prop up one end with some house bricks or block of wood. To generate the steam, place a tea kettle on a hot plate and attach a short length of hose over the kettle spout. Insert the other end of the hose into the steam box and stuff some rags around the hose to hold it in place.

You are now ready to start the actual construction of the guitar by steam bending and forming the body sides. For this you will need a $\frac{3}{4} \times 1\frac{1}{8} \times 60$ in. piece of maple. Since this thickness cannot be purchased, rip a $\frac{3}{16}$ in. thick strip with a circular saw from the $\frac{3}{4} \times 2\frac{1}{4} \times 60$ in. piece of stock called for in the materials list. Dress this strip down on a thickness planer to $\frac{3}{32}$ in. If you do not have a planer, you can use a jointer by backing the strip with a length of scrap stock to support it while pushing it through the jointer. A belt sander could also be used. However, in this case rip the stock $\frac{1}{8}$ in. thick and sand to $\frac{3}{32}$ in.

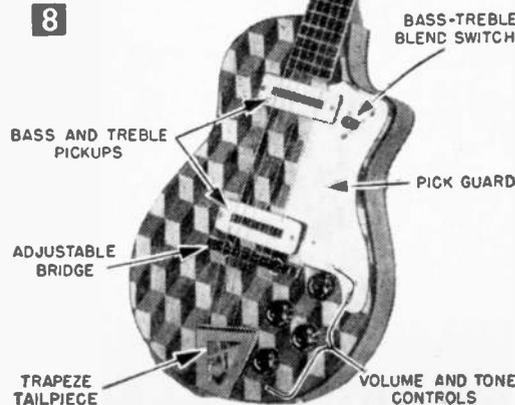
Place the finished piece on edge in the steam box and stuff the top of the box with rags. When the water in the kettle begins to boil steam will fill the box and satu-



8

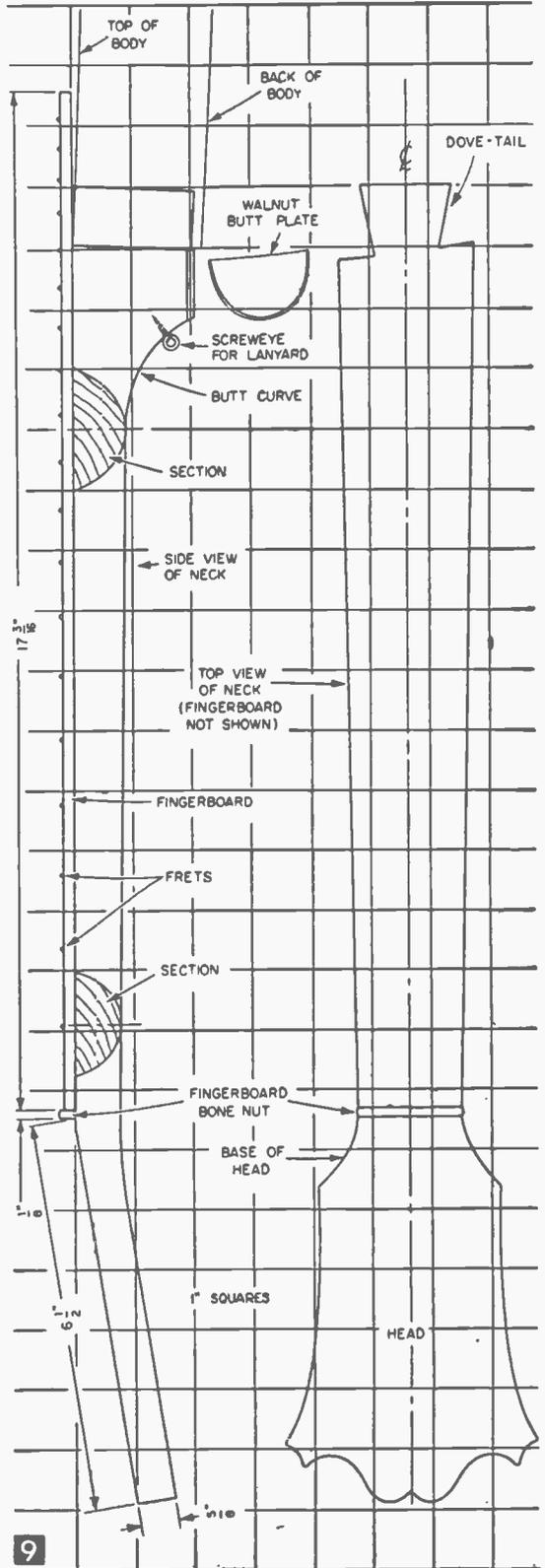

9

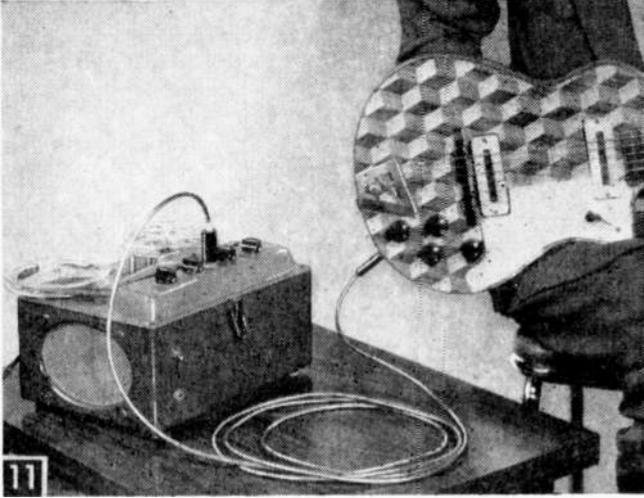

Here a small tape recorder (purchased second-hand for \$40) not only serves as an amplifier for the guitar, but also will record what you play if you want to hear it later—an invaluable method for improving your playing. And, an extension speaker plugged into that jack on the front of the recorder will give you some stereophonic effects.

fitted to the body later. Transfer the shape of the side patterns to the maple stock first and saw from the end of the head to the butt curve at the dovetail end of the neck. Do not cut the scrap piece off, but back out the saw. Then make the other cut, which is the top surface of the head.

Now, using the top pattern of the neck, transfer its shape to the top of the maple stock. Beginning at the dovetail, saw to the location of the nut on both sides, back out the saw on each cut. Then make cuts at right angles to the long cuts you just made at the location of the nut, removing the scrap side pieces. Also cut off the bottom scrap piece. To make the cuts on the sides of the head square with the top surface of the head, turn the neck bottom-side up and transfer the shape of the head on the underside of the neck. When sawing the neck sides, tilt the neck up so that the top surface of the head is flat against the jigsaw table. File the underside of the neck with a coarse wood rasp to the shape of the templates and sand.

Set the neck aside for the moment and remove the center bending form from the guitar body but leave the outside bending form pieces around the body. Then glue the bottom $\frac{3}{8} \times \frac{3}{8}$ in. beading to the lower edge of the body sides. Use masking tape to hold the beading in place. When the glue dries remove the body from the form and carefully sand the edges of the sides and beadings square and flush. Place the sub-top on the body arranging it so the edges of the top project about $\frac{1}{16}$ in. beyond the sides all around. Since the braces on the underside of the sub-top rest against the beading, mark and file the beading to provide clearance for the braces. The underside of sub-top must fit flat against the beading. Glue the sub-top to the body and clamp in gluing clamp (Fig. 7) by tightening all thumb nuts down snug. Remove from clamp when dry

and sand edges flush with body sides. Glue the sub-bottom on later.

Your next step is to overlay the top with contrasting woods as in Figs. 8 and 10. First lay out the centerline from the neck block to the tail block on the sub-top. The three pieces of hardwood (maple or holly, walnut and mahogany) that the overlays are cut from should all be exactly the same width ($\frac{3}{4}$ in.). Using a planer blade in the circular saw, rip the hardwood into $\frac{7}{32} \times \frac{3}{4}$ in. strips. Set the miter gage at 45° and saw 150 diamond-shaped pieces (Fig. 10) from the walnut strips. Then reset the miter gage to $22\frac{1}{2}^\circ$ and cut 150 pieces each from the maple and mahogany strips. Find length A of these pieces (Fig. 10) by measuring length A on the diamond shaped pieces. After cutting six or eight of these pieces make a test assembly with some diamond-shaped pieces to make sure they fit perfectly.


After all the pieces are cut, start the overlay by gluing a line of diamond-shaped walnut pieces on the centerline of the sub-top as in Fig. 10. Ignore the cutouts for the pickups at this time since these openings will be cut later. Continue gluing the other pieces in position, working from center to edges. After the glue dries, trim edges and sand flush with sides. Sand the top.

To install the walnut trim around the outside top edge (Fig. 4), first rout all around the top edge $\frac{7}{32}$ in. deep and to a depth $\frac{1}{16}$ in. below the sub-top (Sec. A-A Fig. 4). Rip saw a strip of $\frac{1}{8} \times \frac{1}{4}$ in. walnut and place it in the steam box. When flexible, bend it around the routed body and secure with masking tape. After the strip has dried, remove the tape and strip, apply glue to the routed edges and again tape the walnut strip in place. When the glue dries, remove the tape and sand the walnut trim strip flush with the top and sides.

Make cutouts in the top for pickups and mixer, and drill the holes for the tone controls. First lay out the cutouts and hole locations as in Fig. 10 and then saw out with a deep-throat coping saw. Use a $\frac{3}{8}$ in. machine-drill for the holes.

Now, set this part aside and take up the previously made neck piece. On the top side of the head, lay out the $\frac{7}{32}$ in. holes and the three diamond-shaped walnut inlay pieces (Fig. 14). Drill the holes and rout or chisel out the head to a depth of $\frac{1}{16}$ in. for the walnut inlays. Glue the inlays in place and sand flush.

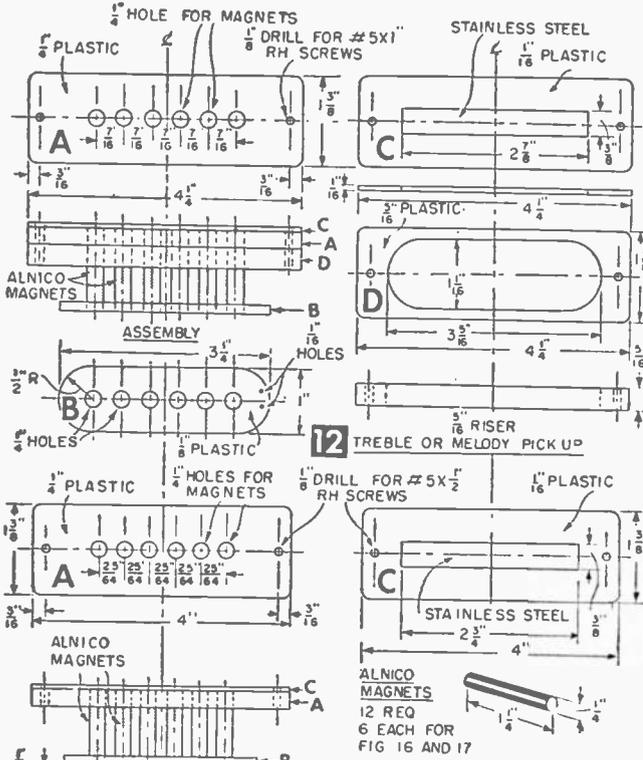Fasten the neck to the body so that the centerline of the neck and the centerline of the body are in perfect alignment. This is very important because a slight discrepancy will throw the strings completely out of alignment and the strings will not come over the fingerboard where they belong. Use a combination coarse and fine rasp to fit the dovetail on the neck to dovetail



of six 1/4 in. dia. magnets 1 1/4 in. long by inserting the magnets through the 1/4 in. holes. Cement magnets in place with household cement.


Now, wrap one turn of Scotch #33 electrical tape around all six magnets forming a core on which to wind a coil. Thread an 8 in. length of #20 shielded grid wire through one of the 1/16 in. holes in piece B and solder the end of a spool of #40 Nylclad heavy magnet wire to the #20 wire. Wind the #40 wire around all of the magnets at once in even layers to form a coil. It will take about 3,500 ft. of magnet wire, or about 6,500 turns on the coil which should test approximately 3,700 ohms on an ohmmeter. If you do not have an ohmmeter, have the coil tested at your local radio repair shop. Complete the coil by soldering the end of the coil to another 8 in. length of #20 shielded grid wire, threaded through the other 1/16 in. hole, and wrap four turns of #33 electrical tape around the entire coil.

Make the top piece (C in Fig. 12) from 1/16 in. thick plastic, cut out the center and tightly fit a piece of stainless steel into the opening. Ce-

in the body.

The top surface of the neck should be a slight angle with the top surface of the body when tested with a straightedge as in Fig. 15. If you file away too much stock, use wooden shims to fill in where needed. When you are satisfied with a good fit, glue the neck to the body with Weldwood glue and let dry.

Before fastening the back of the body in place, make and install the electrical parts that go inside the body. Starting with the treble pickup, make piece A from 1/4 in. plastic and piece B from 1/8 in. plastic according to dimensions given in Fig. 16. When drilling the 1/4 in. holes for the Alnico magnets, center piece B on top of piece A, tape together and drill through both pieces at once. Assemble both pieces at opposite ends

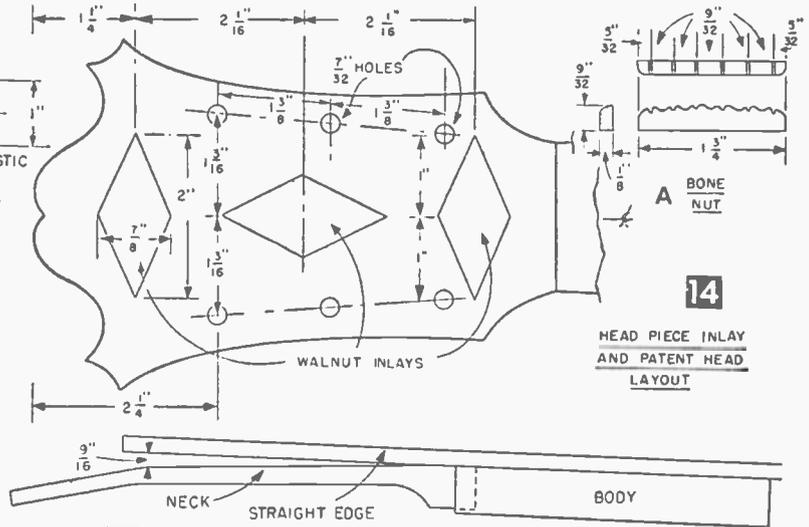

ment in place if necessary. Also make up piece D in Fig. 12 and place over the coil under piece A. Place piece C on top of piece A and tape the three pieces together. Then drill the 1/8 in. holes for the #5 x 3/4 in. rh screws.

The bass or chord pickup (Fig. 13) is similar to the treble pickup with the exception that the magnets project 1/8 in. below the bottom piece B and no riser piece is used. Wind the coil with 6,900 turns of #40 Nylclad magnet wire. The




hole, cut the pieces of inlay to conform to the opening and glue in place. Place a piece of paper between the cut edges of the inlay pieces so that the hand-hole cover will not become glued shut. When finished, fasten cover to body with four #2 x 1/2 in. fh screws, countersunk. Trim and sand the edges of the back flush with the sides and sand the inlay surface flat and smooth. Then rout out the edge for the walnut binding and install the binding as you did around the top.

The fingerboard and bone nut which are purchased parts need only be trimmed to fit as is shown in Fig. 9. The 12th fret should be 12 5/8 in. from the bone nut. Glue in place on the neck. When dry, sand and finish the back, sides and neck as you did the top. Use paste wood filler on the inlay surface only and do not apply any type of finish on the fingerboard or nut. When the first coat of varnish has dried, wet sand the entire instrument, except the fingerboard and nut, and apply two more coats of varnish, sanding between coats. The final coat of varnish can be rubbed down with 2/0 pumice and rottenstone.

You can make the tail piece or purchase one at your local music store. To make one, draw the one shown in Fig. 16B full-size on paper and transfer to 12 gage stainless steel. Saw this out with a metal-cutting blade on a scroll saw. Drill the holes and bend to shape. Also make the tail-piece loop (Fig. 16B). Then mount the tail piece and loop to the guitar body so that the center of the six drilled holes for the strings is exactly in line with the body centerline. The leather lanyard can also be purchased or you can make your own according to the dimensions given in Fig. 19.

Next, install the purchased patent or machine heads to the underside of the neck head as in Fig. 13. To string up your instrument, use *Lektro-Magnetic* strings for the electric Spanish guitar. After stringing, set the rosewood adjustable bridge in place.

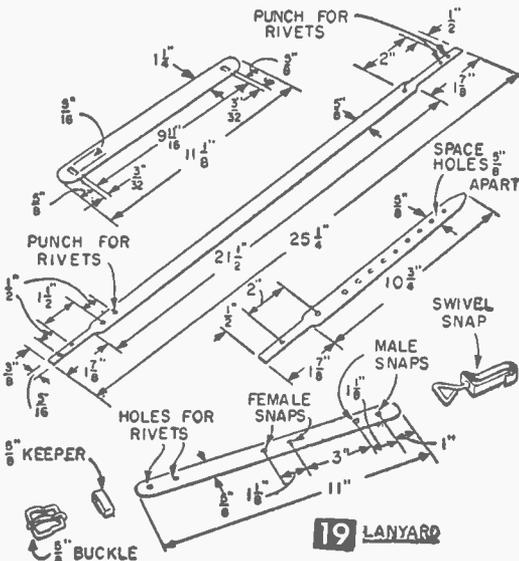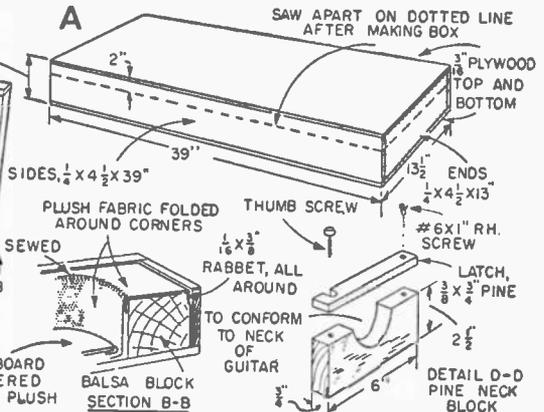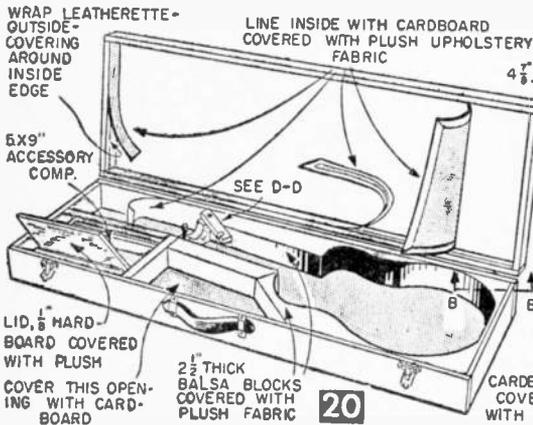Since this instrument is made on the 25-1/4 in. scale, the bridge will be 12 5/8 in. from the 12th fret on the fingerboard. You are now ready to tune your guitar.




● Craft Print No. 277, in enlarged size for building the Electric Guitar is available at \$2. Order by print number. To avoid possible loss of coin or currency in the mails, we suggest you remit by check or money order (no C.O.D.'s or stamps) to Craft Print Dept. 226, SCIENCE AND MECHANICS, 450 East Ohio Street, Chicago 11, Illinois. Please allow three to four weeks for delivery. To obtain our Craft Print Catalog—which contains descriptions of 196 different plans—send us 20¢ (includes 10¢ for postage and handling).

SOLUTION TO ELECTRONICS ANAGRAM
Page 144

N	O	D	E	R	I	M	A	L	I	G	N	
E	I	V	A	I	O	N	C	E				
P	H	O	N	D	K	O	W	A	T	T		
E	D	W	I	R	E	D	C	R				
R	E	E	D	A		P	E	A	K	M	A	
				A	N	T	X	L	T	T	A	P
V	T	V	M	E	P	A	G	I	N	G		
				P	A	H	O	T	O	T	S	
R	E	D	M	H	O	E	N	P	O	T		
				R	F	C		N	G	O	Y	U
				R	V	O	L	T	C	S	S	B
S	H	O	T	O	I	N	H					
P	P	P	M	P	I	P	M	O	A			
K	V	A	P	N	E	R	I	G				
R	C	A	D	C	O	C	K	G	T	C		

Why Does the Lamp Light?

• For an interesting electrical experiment, take a paper capacitor of 2 mfd or larger from your junk-box. Do not use an electrolytic capacitor in this setup as it may explode. Paper capacitors were extensively used in the power units of early radios and are still extensively used in modern amateur transmitters, so such a paper capacitor should not be hard to find. Test the capacitor by connecting an ohmmeter across its terminals. If the capacitor is good, the ohmmeter will indicate (after a quick "kick") an open circuit through the unit.

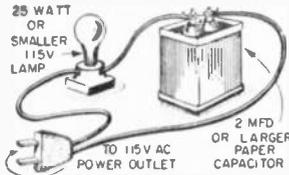

Now connect your capacitor in series with a cleat lamp socket and screw in a 25-watt, or smaller, bulb. When you connect the series combination to the ac power line, you will note that the bulb lights up, although not at full brilliance. Since the ohmmeter had just shown us that the capacitor is an open circuit, how, then, can the lamp light?

A capacitor is made of two separate conducting sheets with a good insulating substance (such as

oiled paper) between them. Practically, no electrons can move through the paper to complete the circuit between the plates, yet an ac current passes

Although the ohmmeter indicated an open circuit through the capacitor, the needle did "kick" when the test leads were first applied. This kick is the clue to our apparent paradox; it represents electrical energy flowing in to charge the capacitor. A good capacitor may thus retain a stored charge for hours. The electrical energy in this charge may be nearly completely recovered from the capacitor.

The voltage across the ac power line periodically reverses itself 60 (50 in some parts of the country) times per second. Now, when a capacitor is connected across such a line it is forced to charge and discharge twice during each complete reversal, or 120 times each second. Each time it charges or discharges, electrons move through its connecting wires. Since our lamp is connected in one of these wires, this charge-discharge current causes it to light.

This principle is universally applied to separate ac from dc (unchanging) currents throughout vacuum-tube and transistor circuits.—C. F. ROCKEY.

Get This Valuable Book *Just For Examining COYNE'S New Set*

FREE

150 PICTURE PATTERNS & DIAGRAMS EXPLAINED

"Applied Practical Radio-Television"

on 7 DAY FREE TRIAL!

NOW! 7 BIG BOOKS IN ONE GREAT SET!

SEND NO MONEY!

Yes, you get our big Diagrams book, FREE! It's like a road-map that shows you the way to easier Radio-TV repair. Needed by every serviceman. Complete 11x22" Schematic Diagrams on many Radio and TV sets help cut servicing time. Includes simple instructions on how to use diagrams and picture patterns. This book is yours FREE for asking to see Coyne's great new 7-book set, "Applied Practical Radio-Television!"

AT LAST! MONEY-MAKING "KNOW-HOW" ON TRANSISTORS, COLOR TV AND SERVICING

Coyne's great 7-volume set gives you all the answers to servicing problems quickly! For basic "know-how" that's easy to understand you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step from fundamentals to installing, servicing and trouble-shooting all types of radio and TV sets. So up-to-date it includes the latest on COLOR TV and UHF. All this plus **Volume 7—TRANSISTOR CIRCUITS**—the most complete book ever published on the applications of Transistors in electronics New! Set has colorful design, washable covers.

EXTRA! 968 Page TV Encyclopedia Included!

For speedy, on-the-job use, you also get Volume 6—famous Coyne CYCLOPEDIA. Answers problems on servicing, alignment, installation etc., in easy ABC order. Use this 7-volume, TV-RADIO LIBRARY FREE for 7 days; get the Servicing Book FREE!

FREE!

5 YEARS OF VALUABLE SUPPLEMENTS

With your set you also get Coyne's annual Supplement Service FREE for 5 years. Keep your set up-to-date on everything that will be new in radio, television, electronics and electricity.

Just max coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. (Cash price, only \$24.95.) Or you can return the library at our expense in 7 days and owe nothing. YOU BE THE JUDGE. Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. 20-RE
1501 W. Congress Pkwy., Chicago 7, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name Age

Address

City Zone State

Where Employed

Check here if you want library sent C.O.D. You pay postman \$24.95 plus C.O.D. postage on delivery. 7-day money-back guarantee.

Educational Book Publishing Division

COYNE

ELECTRICAL SCHOOL

1501 W. Congress Pkwy., Dept. 20-RE Chicago 7, Ill.

25 Years Ago in Radio

A QUARTER of a century ago, *White's Radio Log* was 12 years old and commercial broadcasting itself was not much older. Yet as these pages reproduced from the March 1934 issue of *White's* show, broadcasting was even then a healthy medium of entertainment. Some of the programs popular in 1934 are still on the air (and most of 1934's sponsors are still going

strong). Indeed, the programming of the Thirties may seem to many to have been radio's golden age, flawed possibly by immaturity, but lusty and vital all the same. Here—for those of you old enough to remember—is what you were listening to 25 years ago. And here—for those of you who missed it—is what your fathers heard, and grow nostalgic about today.

NETWORK RADIO PROGRAMS OF MARCH 1934

C., CBS Network Stations. N.F., WEAf; N.Z., WJZ—both NBC Networks. Eastern Standard Time used exclusively. Sponsors' names appear in parentheses.

A & P Gypsies (Great A & P Tea Co.)	Monday, 9:00 p.m., N.F.
Abe Lyman's Orch.: Frank Munn (Sterling Products)	Friday, 9:00 p.m., N.F.
Adventures of Tom Mix and his Ralston Straight Shooters (Ralston Purina Co.),	Mon.-Wed.-Fri., 5:30 p.m., also Wed.-Fri., 6:30 p.m., N.F.
Albert Payson Terhume (Spratts Ptd., Ltd.)	Sunday, 4:00 p.m., N.Z.
Albert Spalding (Fletcher's Castoria)	Wednesday, 8:30 p.m., C.
American Album of Familiar Music (Bayer Co., Inc.)	Sunday, 9:30 p.m., N.F.
American Revue (American Oil Co.)	Sunday, 7:00 p.m., C.
Amos 'n' Andy (Pepsodent Co.)	Daily except Sat. & Sun., 7 p.m., also western, 11:00 p.m., N.Z.
An Evening in Paris (Bourjois Sales Corp.)	Sunday, 8:00 p.m., C.
Armour Program, featuring Phil Baker (Armour Co.)	Friday, 9:30 p.m., N.Z.
Baby Rose Marie (Tasty Yeast, Inc.)	Sunday, 12:15 p.m., N.Z.
Bar X Days and Nights (Health Products Co.)	Sunday, 2:00 p.m., N.Z.
Ben Bernie's Blue Ribbon Orchestra (Premier-Pabst Sales Co.),	Tues., 9 p.m., 12 midnight, N.F.
Benny Meroff's Review (Plough, Inc.)	Wednesday, 10 p.m., N.Z.
Betty and Bob (General Mills, Inc.)	Daily except Sat. & Sun., 4:00 p.m., N.Z.
Betty Moore, Interior Decorator (Benjamin Moore & Co.)	Wednesday, 11:30 a.m., N.F.
Big Ben Dream Drama (Western Clock Co.)	Sunday, 5:00 p.m., N.F.
Big Hollywood Show (Phillips Dental Magnesia)	Sunday, 2:30 p.m., C.
Big Show (Ex-Lax Co.)	Monday, 9:30 p.m., C.
Bill and Ginger (C. F. Mueller Co.)	Monday, Wednesday, Friday, 10:15 a.m., C.
Billy Bachelor (Wheatena Corp.)	Daily except Saturday, 7:15 p.m., N.F.
Bing Crosby, Gus Arnheim's Orch., Mills Bros. (John Woodbury Co.)	Monday, 8:30 p.m., C.
Boake Carter (Philco Radio & Television Corp.)	Daily except Sat. & Sun., 7:45 p.m., C.
Bobby Benson and Sunny Jim (Hecker H-O Co.)	Daily except Sat. & Sun., 6:15 & 8:15 p.m., C.
Broadway Melodies (American Home Products Corp.)	Sunday, 2:00 p.m., C.
Buck Rogers in the 25th Century (Cocomalt)	Mon., Tues., Wed., Thurs., 8:00 & 7:30 p.m., C.
Buick Presents (Buick Motor Co.)	Monday & Thursday, 9:15 p.m., C.
Byrd Expedition Broadcast (General Foods Corp.)	Saturday, 10:00 p.m., C.
Cadillac Concert (Cadillac Motor Car Co.)	Sunday, 8:00 p.m., N.Z.
Camel Caravan (R. J. Reynolds Tobacco Co.)	Tuesday & Thursday, 10:00 p.m., C.
Capt. Henry's Maxwell House Show Boat (General Foods Corp.)	Thursday, 9:00 p.m., N.F.
Carborundum Band (Carborundum Co.)	Saturday, 9:30 p.m., C.
Charm Secrets (Lavoris Co.)	Tuesday & Thursday, 11:15 a.m., C.
Chase & Sanborn Hour (Standard Brands, Inc.)	Sunday, 8:00 p.m., N.F.
Chevrolet Program (Chevrolet Motor Co.)	Sunday, 10:00 p.m., N.F.
Cities Service Program (Cities Service Co.)	Friday, 8:00 p.m., N.F.
Clara, Lu 'n' Em (Colgate-Palmolive-Peet Co.)	Daily except Sat. & Sun., 10:15 a.m., N.Z.
Climalene Carnival (The Climalene Co.)	Tuesday & Thursday, 11:30 a.m., N.F.
Conoco Travel Adventures (Continental Oil Co.)	Wednesday, 10:30 p.m., N.Z.
Contented Program (Carnation Milk)	Monday, 10:00 p.m., N.F.
Cook Travelogues (Thomas Cook & Son)	Sunday, 2:30 p.m., N.F.
Cooking Close-Ups (Pillsbury Flour Mills)	Monday, Wednesday, Friday, 11:00 a.m., C.
Corn Cob Pipe Club of Virginia (Larus & Brothers Co.)	Wednesday, 10 p.m., N.F.
Cruise of the Seth Parker (Frigidaire Corp.)	Tuesday, 10:00 p.m., N.F.
Dangerous Paradise (John H. Woodbury Co.)	Wednesday and Friday, 8:30 p.m., N.Z.
Death Valley Days (Pacific Coast Borax Co.)	Thursday, 9:00 p.m., N.Z.
Del Monte Ship of Joy (California Packing Corp.)	Monday, 9:30 p.m., N.F.
Djer Kias Recital (Vadsco Sales Corp.)	Monday, 8:30 p.m., N.Z.
Don Quixote Dramatization (Jeddo-Highland Coal Co.)	Thurs., Fri., Sat., 7:15 p.m., N.Z.
Easy Aces (Wyeth Chemical Co.)	Tuesday, Wednesday, Thursday, Friday, 1:30 p.m., C.
Eddie Duchin and his Orchestra (Pepsodent Co.)	Tues., Thurs., Sat., 9:30 p.m., N.Z.
Edwin C. Hill (Barbasol Co.)	Daily except Saturday & Sunday, 8:15 & 11:30 p.m., C.
Eno Crime Clues (Harold S. Ritchie & Co.)	Tuesday & Wednesday, 8 p.m., N.Z.
First Nighter (Campana Corp.)	Friday, 10:00 p.m., N.F.
Fitch Program (F. W. Fitch Co.)	Sunday, 7:45 p.m., N.F.


Fleischmann Hour (Standard Brands, Inc.)	Thursday, 8:00 p.m., N.F.
Forty-five Minutes in Hollywood (Borden Co.)	Saturday, 8:00 p.m., C.
Fox Fur Trappers (I. J. Fox, Inc.)	Tuesday, 7:30 p.m., N.F.
Frank Crummit and Julia Sanderson (General Baking Co.)	Sunday, 5:30 p.m., C.
Fred Allen's Sal Hepatica Revue (Bristol-Myers Co.)	Wednesday, 9:30 p.m., N.F.
Fred Waring's Pennsylvanians (Ford Motor Co.)	Sunday, 8:30 p.m., Thursday, 9:30 p.m., C.
Galaxy of Stars (Red Star Yeast & Products Co.)	Tues., Thurs. & Sat., 11:00 a.m., N.F.
Garden of Tomorrow (Tennessee Corp.)	Sunday, 10:30 a.m., N.F.
Gems of Melody (Carleton & Hovey Co.)	Sun., 2:45 p.m., N.F., Wed., 7:15 p.m., N.Z.
Gene Arnold and the Commodores (Crazy Crystals Water Co.)	Sun., Wed., Fri., 2:00 p.m., N.F., Mon. & Thurs., 12 noon, N.Z.
Goldbergs (Pepsodent Co.)	Daily except Saturday & Sunday, 7:45 p.m., N.F.
Grand Hotel (Campana Corp.)	Sunday, 5:30 p.m., N.Z.
Gulf Headliners (Gulf Refining Co.)	Sunday, 9:00 p.m., N.Z.
Hall of Fame (Lehn & Fink Products Co.)	Sunday, 10:30 p.m., N.F.
Happy Bakers (Continental Baking Co.)	Monday, Wednesday & Friday, 8:00 p.m., C.
Hoover Sentinels Concert (The Hoover Co.)	Sunday, 4:30 p.m., N.F.
Horlick's Adventures in Health (Horlick Malted Milk Co.)	Tuesday & Thursday, 8:30 p.m., Tuesday, 11:45 p.m., N.Z.
Household Musical Memories (Household Finance Corp.)	Tuesday, 9:00 p.m., N.Z.
Ipana Troubadours (Bristol-Myers Co.)	Wednesday, 9:00 p.m., N.F.
Irene Rich in Hollywood (Welch Grape Juice Co.)	Sun., 3:15 p.m., Wed., 7:45 p.m., N.Z.
Jack Armstrong, All American Boy (General Mills, Inc.)	Daily except Sun., 5:30 & 6:30 p.m., C.
Jack Frost's Melody Moments (National Sugar Refining Co.)	Monday, 9:30 p.m., N.Z.
Jane Ellison's Magic Recipes (The Borden Sales Co.)	Wednesday, 11:45 a.m., C.
Jack Pearl (Standard Brands, Inc.)	Wednesday, 8:00 p.m., N.F.
Joan Marrow (J. W. Marrow Mfg. Co.)	Tuesday & Thursday, 1:15 p.m., C.
Jergens Program (Andrew Jergens Co.)	Sunday, 9:30 & 11:15 p.m., N.Z.
Josephine Gibson Hostess Council (H. J. Heinz Co.)	Mon., Wed., Fri., 10:00 a.m., N.Z.
Judy and Jane (J. A. Folger & Co.)	Daily except Saturday & Sunday, 2:30 p.m., N.F.
Just Plain Bill (Kolynos Sales Co.)	Daily except Saturday & Sunday, 2:00 & 7:15 p.m., C.
Lady Esther Serenade (Lady Esther Co.)	Sun., 3:00 p.m., Tues. & Wed., 8:30 p.m., N.F.
Lazy Dan, the Minstrel Man (American Home Products Corp.)	Sunday, 1:30 p.m., C.
Leo Reisman's Orch. with Phil Ducey (Philip Morris & Co.)	Tuesday, 8:00 p.m., N.F.
Let's Listen to Harris (Northam Warren Corp.)	Friday, 9:00 p.m., N.Z.
Little Miss Bab-O's Surprise Party (B. T. Babbitt Co., Inc.)	Sunday, 1:00 p.m., N.F.
Little Italy (Delaware, Lack. & Western Coal Co.)	Tuesday & Thursday, 6:45 p.m., C.
Little Orphan Annie (Wander Co.)	Daily except Sunday, 5:45 p.m., 6:45 p.m., N.Z.
Lowell Thomas (Sun Oil Co.)	Daily except Saturday & Sunday, 6:45 p.m., N.Z.
Madam Sylvia of Hollywood (Ralston Purina Co.)	Tuesday, 10:30 p.m., N.F.
Maltex Program (Malted Cereals Co.)	Sunday, 1:30 p.m., N.F.
Manhattan Merry-Go-Round (R. L. Watkins Co.)	Sunday, 9:00 p.m., N.F.
Marie the Little French Princess (Affiliated Prod., Inc.)	Tues., Wed., Thurs., Fri., 1:00 p.m., C.
March of Time (Remington Rand, Inc.)	Friday, 8:30 p.m., C.
Metropolitan Opera Broadcast (American Tobacco Co.)	Saturday, 1:45 p.m., N.F. & N.Z.
Minneapolis Symphony Orchestra (General Household Utility Co.)	Tuesday, 9:30 p.m., C.
Molle Show (The Molle Co.)	Monday, Wednesday, Thursday, 7:30 p.m., N.F.
Music by Gershwin (Health Products Corp.)	Monday & Friday, 7:30 p.m., N.Z.
Music on the Air with Jimmy Kemper (Tide Water Oil Sales Co.)	Mon., Wed., Fri., 7:30 p.m., C.
Myrt & Marge (Wm. Wrigley, Jr., Co.)	Daily except Sat. & Sun., 7:00 & 10:45 p.m., C.
Mystery Chef (R. B. Davis Co.)	Tues. & Thurs., 9:45 a.m., C.; Wed. & Fri., 9:00 a.m., N.Z.
Nat Shilkret and his Salon Orchestra (Smith Bros.)	Sunday, 9:45 p.m., N.Z.
National Barn Dance (Dr. Miles Laboratories)	Saturday, 11:00 p.m., N.Z.
Nestle's Chocolate (Lamont-Corliss & Co.)	Friday, 8:00 p.m., N.Z.
Old Gold Program (P. Lorillard Co.)	Wednesday, 10:00 p.m., C.
Oldsmobile Presents (Old's Motor Works)	Tuesday & Friday, 9:15 p.m., C.
Oxol Feature (J. L. Prescott Co.)	Monday, Tuesday, Wednesday, Friday, 5:45 p.m., C.
Oxydol's Own Ma Perkins (Procter & Gamble Co.)	Daily except Saturday & Sunday, 3:00 & 4:30 p.m., N.F.
Patri's Dramas of Childhood (Cream of Wheat Corp.)	Sunday, 10:00 p.m., C.
Paul Whiteman and his Orchestra (Kraft Phenix Cheese Corp.)	Thursday, 10 p.m., N.F.
Pet Milky Way (Pet Milk Sales Corp.)	Tuesday & Thursday, 11:00 a.m., C.
Philadelphia Orchestra (Liggett & Myers Tobacco Co.)	Daily except Sunday, 9:00 p.m., C.
Playboys (M. J. Breiten-Bach Co.—Pepto Mangan)	Sunday, 10:45 a.m., C.
Plough's Musical Cruiser (Plough, Inc.)	Wednesday, 10:00 p.m., N.Z.
Pond's Program (Lamont-Corliss & Co.)	Friday, 9:30 p.m., N.F.
Pontiac Presents (Buick-Oldsmobile-Pontiac Sales Co.)	Saturday, 9:30 p.m., C.
Princess Pat Players (Princess Pat, Ltd.)	Sunday, 4:30 p.m., Monday, 10:30 p.m., N.Z.
Pure Oil Program (Pure Oil Co.)	Saturday, 9:00 p.m., N.Z.
Real Silk Show (Real Silk Hosiery Mills)	Sunday, 7:00 p.m., N.Z.
Red Davis, Dramatic Sketch (Beech-nut Packing Co.)	Mon., Wed. & Fri., 8:45 p.m., N.Z.
Richard Hudnut Presents Marvelous Melodies (Hudnut Sales Co., Inc.)	Friday, 9:30 p.m., C.
Rin Tin Tin Thriller (Chappel Bros., Inc.—Ken-L-Ration)	Sunday, 7:45 p.m., C.
Rings of Melody (Perfect Circle Co.)	Sunday, 2:30 p.m., N.Z.
Romance of Helen Trent (Edna Wallace Hopper, Inc.)	Daily except Sat. & Sun., 2:15 p.m., C.
Roses and Drums (Union Central Life Ins. Co.)	Sunday, 5:00 p.m., C.
Saturday Night Terraplane Party (Hudson Motor Car Co.)	Saturday, 10:00 p.m., N.F.
Sealed Power Side Show (Sealed Power Corp.)	Monday, 8:00 p.m. & 12 midnight, N.Z.
Seven Star Revue (Corn Products Refining Co.)	Sunday, 9:00 p.m., C.
Silver Dust (Gold Dust Corp.)	Tuesday, Thursday & Saturday, 7:50 p.m., C.

Sinclair Greater Minstrels (Sinclair Refining Co.)	Monday, 9:00 p.m., N.Z.
Singing Lady (Kellogg Co.)	Daily except Saturday & Sunday, 5:30 p.m., 6:30 p.m., N.Z.
Skippy (Phillips Dental Magnesia)	Daily except Saturday & Sunday at 5:00 & 6:00 p.m., C.
Smiling Ed McConnell (Acme White Lead & Color Works),	Sunday, 6:30 p.m., Wednesday & Friday, 12:30 p.m., C.
Soconyland Sketch (Standard Oil Co. of N. Y.)	Monday, 8:00 p.m., N.F.
Songs Your Mother Used to Sing (Wyeth Chemical Co.)	Sunday, 6:00 p.m., C.
Stamp Adventurer's Club (Louden Packing Co.)	Thursday, 5:45 & 6:45 p.m., C.
Sweetheart Melodies (Manhattan Soap Co.)	Thursday, 11:30 a.m., N.F.
Swift Garden Program (Swift & Co.)	Sunday, 3:30 p.m., N.F.
Swift Review (Swift & Co.)	Friday, 10 p.m., C.
Talkie Picture Time (Luxor, Ltd.)	Sunday, 5:30 p.m., N.F.
Texaco Fire Chief Band; Ed Wynn (Texas Co.)	Tuesday, 9:30 p.m., N.F.
Tito Guizar's Mid-day Serenade (Brillo Mfg. Co.)	Sunday, 12:30 p.m., C.
Today's Children (Pillsbury Flour Mills Co.)	Daily except Sat. & Sun., 10:30 a.m., N.Z.
Tony Wons with Keenan & Philips (S. C. Johnson & Son)	Tues. & Thurs., 11:30 a.m., C.
Tower Health Exercises (Metropolitan Life Ins. Co.)	Daily except Sun., 6:45 to 8:00 a.m., N.F.
Trade & Mark (Smith Brothers, Inc.)	Saturday, 8:45 p.m., C.
True Story Court of Human Relations (True Story Pub. Co.)	Sunday, 7:00 p.m., N.F.
Voice of Firestone (Firestone Tire & Rubber Co.)	Monday, 8:30 & 11:30 p.m., N.F.
Voice of Romance (Rieser Co., Inc.)	Saturday, 6:15 p.m., C.
Warden Lawes in "20,000 Years in Sing Sing" (Wm. R. Warner Co.)	Wed., 9 p.m., N.Z.
Ward's Family Theatre (Ward Baking Co.)	Sunday, 6:45 & 7:30 p.m., C.
Waves of Romance (Rieser & Co.)	Sunday, 5:15 p.m., N.F.
Wayne King's Orchestra (Lady Esther Co.)	Monday, 10:00 p.m., C.
White Owl Program (General Cigar Co.)	Wednesday, 9:30 p.m., C.
Wildroot Institute (Wildroot Co.)	Sunday, 4:15 p.m., N.F.
Will Osborne and His Orchestra (Corn Products Refining Co.)	Mon., Wed., Fri., 10:45 a.m., C.
Wizard of Oz (General Food Corp.)	Monday, Wednesday & Friday, 5:45 p.m., N.F.
Vince Program with John McCormack (Wm. R. Warner Co.)	Wednesday, 9:30 p.m., N.Z.
Voice of Experience (Wasey Products, Inc.),	Daily except Sun., 12 noon; also Tues., 8:30 & 11:45 p.m., Thurs., 8:30 p.m., C.
Yeast Foamers (Northwestern Yeast Co.)	Sunday, 3:30 p.m., N.Z.
Ye Happy Minstrel and Tiny Band (Wheatena Corp.),	Mon., Wed., Sat., 6:45 p.m.; Tues. & Thurs., 4:45 p.m., C.
Zoel Parenteau's Orchestra (Worcester Salt Co.)	Friday, 6:45 p.m., C.

For some auditors, listening to a favorite program was a ritual. At 7:00, for example, everyone stopped everything and the country lis-

tened to Amos n' Andy. Here are the programs of a typical 1934 weeknight (Wednesday in this instance), and the times you tuned them in.

6:45 to 8:00 a.m. Tower Health Exercises	N.F.	7:00 p.m. Myrt and Marge	C.
9:00 a.m. The Mystery Chef	N.Z.	7:15 p.m. Billy Batchelor	N.F.
10:00 a.m. Josephine Gibson Hostess Council	N.Z.	7:15 p.m. Gems of Melody	N.Z.
10:15 a.m. Bill and Ginger	C.	7:15 p.m. Just Plain Bill	C.
10:15 a.m. Clara, Lu 'n' Em	N.Z.	7:30 p.m. Buck Rogers in the 25th Century	C.
10:30 a.m. Today's Children	N.Z.	7:30 p.m. The Mollie Show	N.F.
10:45 a.m. Will Osborne and his Orch.	C.	7:30 p.m. Music on the Air with Jimmy Kemper	C.
11:00 a.m. Cooking Close-Ups	C.	7:45 p.m. Boake Carter	C.
11:30 a.m. Betty Moore, Interior Decorator	N.F.	7:45 p.m. Goldberg's	N.F.
11:45 a.m. Jane Ellison's Magic Recipes	C.	7:45 p.m. Irene Rich in Hollywood	N.Z.
12:00 noon. Gene Arnold and the Commodores	N.F.	8:00 p.m. Eno Crime Clues	N.Z.
12:00 noon. The Voice of Experience	C.	8:00 p.m. Happy Bakers	C.
12:30 p.m. Smiling Ed McConnell	C.	8:00 p.m. Royal Gelatin Review with Jack Pearl	N.F.
1:00 p.m. Marie, the Little French Princess	C.	8:15 p.m. Bobby Benson and Sunny Jim	C.
1:30 p.m. Easy Aces	C.	8:15 p.m. Edwin C. Hill, "The Human Side of the News"	C.
2:00 p.m. Just Plain Bill	C.	8:30 p.m. Albert Spalding	C.
2:15 p.m. Romance of Helen Trent	C.	8:30 p.m. Dangerous Paradise	N.Z.
2:30 p.m. Judy and Jane	N.F.	8:30 p.m. Lady Esther Serenade	N.F.
3:00 p.m. Oxydol's Program	N.F.	8:45 p.m. "Red Davis" Dramatic Sketch	N.Z.
4:00 p.m. Betty and Bob	N.Z.	9:00 p.m. Ipana Troubadours	N.F.
4:30 p.m. Oxydol's Program	N.F.	9:00 p.m. Philadelphia Orchestra	C.
5:00 p.m. Skippy	C.	9:00 p.m. Warden Lawes in "20,000 Years in Sing Sing"	N.Z.
5:30 p.m. Adventures of Tom Mix	N.F.	9:30 p.m. Fred Allen's Revue	N.F.
5:30 p.m. Jack Armstrong, All American Boy	C.	9:30 p.m. Vince Program with John McCormack	N.Z.
5:30 p.m. Singing Lady	N.Z.	9:30 p.m. White Owl Program	C.
5:45 p.m. Little Orphan Annie	N.Z.	10:00 p.m. Plough's Musical Cruiser	N.Z.
5:45 p.m. The Oxol Feature	C.	10:00 p.m. Corn Cob Pipe Club	N.F.
5:45 p.m. Wizard of Oz	N.F.	10:00 p.m. Old Gold Program	C.
6:00 p.m. Buck Rogers in the 25th Century	C.	10:30 p.m. Conoco Adventures	N.Z.
6:00 p.m. Skippy	C.	10:45 p.m. Myrt and Marge	C.
6:15 p.m. Bobby Benson and Sunny Jim	C.	11:00 p.m. Amos n' Andy	N.Z.
6:30 p.m. Adventures of Tom Mix	N.F.	11:30 p.m. Edwin C. Hill, "The Human Side of the News"	C.
6:30 p.m. Household Music Box	C.		
6:30 p.m. Jack Armstrong, All American Boy	C.		
6:30 p.m. Singing Lady	N.Z.		
6:45 p.m. Little Orphan Annie	N.Z.		
6:45 p.m. Lowell Thomas	N.Z.		
6:45 p.m. Ye Happy Minstrel & Tiny Band	C.		
7:00 p.m. Amos n' Andy	N.Z.		

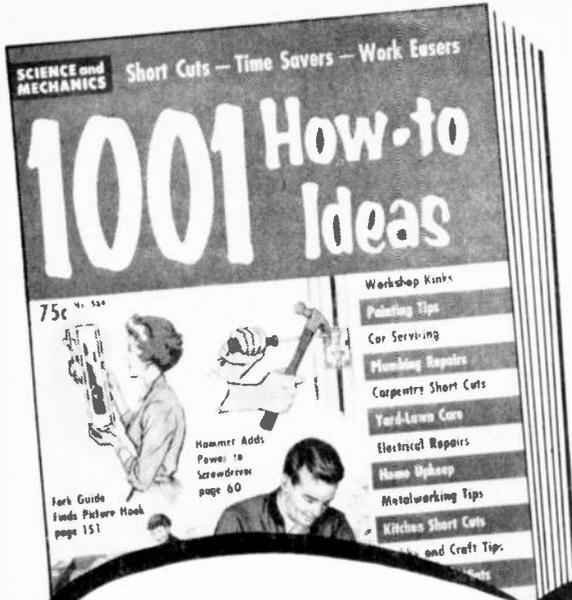

on sale now
get your copy of


1001 How-to Ideas

Kinks like this

on- radio-tv repairs
home decorating
home remodeling
groundskeeping
plumbing repairs
electrical repairs
home maintenance
auto repairs
carpentry
woodworking
masonry
metalworking
power tool use
hand tool use
photography
craft hobbies

Salvaging Flashlights

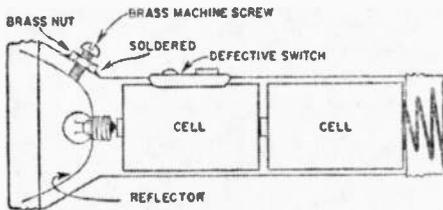• Since a flashlight switch is riveted to the case, and the interior of the case is hard to get at for repairs, it is simpler to ignore the original switch entirely when it is broken or badly worn and install a simple substitute switch. Do this by



drilling a hole in the case close to the reflector, soldering a square or hexagon nut over the hole, and twisting a roundhead machine screw into the nut. To light the lamp, simply turn the screw clockwise until the end of the screw contacts the reflector. This provides the necessary connection from the case to the reflector, as the reflector is usually in contact with the lamp base but not the case. To turn off the lamp, back up the screw.

Only **75¢**

If you do it yourself around the home, you'll want a copy of the 1960 edition of *1001 How-to Ideas* (Vol. 2, No. 564). Compiled by the editors of *Science and Mechanics Magazine*—The Magazine That Shows You How—*1001 How-to Ideas* contains tested tips and shortcuts that will save you

many, many hours on your projects—and dollars, too. Whatever area of do-it- (or make-it-) yourself you're interested in, you'll find at least a score of ideas in this book that will show you faster, easier, thrifter ways to do it.

Get a copy now.

Get your copy of the 1960 edition from your newsdealer, or send 75¢ for a copy to
SCIENCE AND MECHANICS 450 E. Ohio St. Dept. 332 Chicago 11, Illinois

THE FRABIJAN'S BUSTED?

Don't Throw It Away,
Fix It - Subscribe To

SCIENCE and MECHANICS

The Magazine That Shows You How

- Every issue packed with useful, money-saving information on home repairs and upkeep
- Every issue, projects to build—boats, household accessories, workshop and hobby equipment
- Every issue, news on science and industry, car test reports
- Every issue, everything under the sun from satellites to sofas to surfboarding



Science and Mechanics has always been a leader in its field—readers' mail says it's the leader—but the NEW *Science and Mechanics* is bigger and better than ever. Now a Davis Publication, the NEW *Science and Mechanics* has the same solid substance, the same respect for facts it's always had. As before, it publishes the latest news on science and industry (written to relate to your needs and interests), plus completely detailed do-it- and make-it-yourself project articles. But under its new

aegis, *Science and Mechanics* has more editorial content than ever before, and it's presented in new, more entertaining and more attractive ways . . . And in every issue of the NEW S&M there's a big BONUS feature.

For one of the most interesting experiences of your magazine-reading life, and for one of the most useful and practical magazine purchases you'll ever make, subscribe now to the NEW S&M. The first tip you use from the many in each issue will more than repay you.

The April Issue, Now On Sale, Includes:

Fold-Out Blueprints for MINIATURE, BATTERY-POWERED TAPE RECORDER. Can be built for about \$35. Completely portable, compatible—can be played back on ordinary home recorder at 3¾ ips. Equivalent of commercial units costing \$100-\$250.

3-OCTAVE, 120-BASS CHORD ORGAN. Separate balance control for treble and bass. More chord selection (though less tone control) than \$900-plus commercial models. Will cost approximately \$50 to build; easily equivalent of \$250 commercial organs.

Plus Project Articles on ONE-TUBE TIN CAN RECEIVER. Inexpensive broadcast-band receiver pulls in stations 70 miles distant.

TRANSMITTER FOR THE NOVICE. Compact 75-watt transmitter that even a Novice YL can build in a few hours (in fact, one did). The rig puts out a good signal on 40 and 80 meters, features band-switching, and—with suitable power supplies—can be used either at home or in a car.

USE THE COUPON INSERTED OPPOSITE THIS PAGE TO SUBSCRIBE TODAY

WHITE'S RADIO LOG

An up-to-date broadcasting directory
AM, FM, TV and Short-Wave Stations

Vol. 37 No. 1



Every effort has been made to ensure accuracy of the information listed in this publication, but absolute accuracy is not guaranteed and, of course, only information available up to press-time could be included. Copyright 1960 by Science and Mechanics Publishing Co., a subsidiary of Davis Publications, Inc., 450 East Ohio St., Chicago 11, Ill.

QUICK REFERENCE INDEX

U.S. and Canadian AM Stations by Frequency	161
U.S. and Canadian AM Stations by Location	170
U.S. and Canadian AM Stations by Call Letters	178
Canadian Short-Wave Stations	185
World-Wide Short-Wave Stations	186
United States FM Stations	188
Canadian FM Stations	190
United States Television Stations	190
Canadian Television Stations	191

U. S. and Canadian AM Stations by Frequency

U.S. stations listed alphabetically by states within groups, Canadian stations precede U.S. Abbreviations: Kc., frequency in kilocycles; W.P., watt power; d—operates daytime only. Wave length is given in meters

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
540—555.5			560—535.4			580—516.9			630—499.7		
CBK Regina, Sask.	5000		CFRA Ottawa, Ont.	5000		WKBN Youngstown, Ohio	5000		KCSJ Pueblo, Colo.	1000	
KVIP Redding, Calif.	1000d		CJKL Kirkland Lake, Ont.	5000		WNAX Yankton, S.Dak.	5000		WDLF Panama City, Fla.	1000	
KFMB San Diego, Calif.	5000		CFOS Owen Sound, Ont.	1000		WFAA Dallas, Tex.	5000		WPLO Atlanta, Ga.	5000	
WGTO Cypress Gardens, Florida	5000d		WEOF Dethan, Ala.	5000d		WFAP Ft. Worth, Tex.	5000		KGMB Honolulu, Hawaii	5000	
WDAK Columbus, Ga.	5000		KYUM Yuma, Ariz.	1000		KLUB Salt Lake City, Utah	5000		KID Idaho Falls, Idaho	5000	
KBRV Soda Springs, Idaho	5000		KSFO San Fran., Calif.	1000		KVI Seattle, Wash.	5000		WVLK Lexington, Ky.	5000	
KWMT Ft. Dodge, Iowa	1000d		KLZ Denver, Colo.	5000		WMAM Marinette, Wis.	250		WEEI Boston, Mass.	5000	
WDVM Pocomoke City, Md.	5000		WQAM Miami, Fla.	5000		580—516.9			WKZO Kalamazoo, Mich.	5000	
WCNG Canonsburg, Pa.	250d		WIND Chicago, Ill.	5000		CFLG Timmins, Ont.	1000		WOW Omaha, Nebr.	5000	
WDXN Clarksville, Tenn.	250d		WMIK Middleboro, Ky.	5000		CJFX Antigonish, N.S.	5000		WROW Albany, N.Y.	5000	
WRIC Richlands, Va.	1000d		WGAN Portland, Maine	5000		CKEY Toronto, Ont.	5000		WGTM Wilson, N.C.	5000	
550—545.1			WHYN Springfield, Mass.	1000		CKPR Ft. William, Ont.	5000		WARM Scranton, Pa.	5000	
CFNB Fredericton, N.B.	5000		WMIC Monroe, Mich.	5000		CKUA Edmonton, Alta.	1000		WMBS Uniontown, Pa.	1000	
CFBR Sudbury, Ont.	1000		WBCB Duluth, Minn.	5000		CKY Winnipeg, Man.	5000		WYFC Austin, Tex.	5000	
CHLN Three Rivers, Que.	5000		KWTO Springfield, Mo.	5000		WABT Tuskegee, Ala.	5000		KSUB Cedar City, Utah	1000	
CKPG Prince George, B.C.	250		KMON Great Falls, Mont.	5000		KTAN Tucson, Ariz.	5000		WLVA Lynchburg, Va.	1000	
KENI Anchorage, Alaska	5000		WGAI Elizabeth City, N.C.	1000		KUBC Montrose, Colo.	5000		KHQ Spokane, Wash.	5000	
KDY Phoenix, Ariz.	5000		WFL Philadelphia, Pa.	5000		WDBO Orlando, Fla.	5000				
KAFY Bakersfield, Calif.	1000		WIS Columbia, S.C.	5000		WGAC Augusta, Ga.	5000				
KRAI Craig, Colo.	1000		WHBQ Memphis, Tenn.	5000		KFXD Nampa, Idaho	5000				
WGGA Gainesville, Ga.	5000		KFDM Beaumont, Tex.	5000		WILL Urbana, Ill.	5000d				
KMYI Wailuku, Hawaii	1000		KPQ Wenatchee, Wash.	5000		KSAC Manhattan, Kans.	5000				
KFRM Concordia, Kansas	5000d		WJLS Beckley, W.Va.	5000		WLB Topeka, Kans.	5000				
WCBI Columbus, Miss.	1000		570—526.0			WLAG Alexandria, La.	5000				
KSD St. Louis, Mo.	5000		CKEK Cranbrook, B.C.	1000		WTAG Worcester, Mass.	5000				
KOPR Butte, Mont.	1000		CJCK Quesnel, B.C.	1000		WELO Tupelo, Miss.	1000				
WGR Buffalo, N.Y.	5000		CJEM Edmundston, N.B.	1000		WAGR Lumberton, N.C.	5000				
WDBM Statesville, N.C.	5000		WCAS Gadsden, Ala.	5000d		WHP Harrisburg, Pa.	5000				
KFYR Bismarck, N.Dak.	5000		KCON Alturas, Calif.	1000		WKAQ San Juan, P.R.	5000				
WKRC Cincinnati, Ohio	5000		KLAC Los Angeles, Calif.	5000		WRKH Rockwood, Tenn.	1000d				
KOAC Corvallis, Oreg.	5000		WGMS Washington, D.C.	5000d		KDAB Lubbock, Tex.	5000				
WFLM Bloomsburg, Pa.	500		WAEL Waycross, Ga.	5000		WCHS Charleston, W.Va.	5000				
WPAB Ponce, P.R.	5000		WKYP Paducah, Ky.	1000		WKTY LaCrosse, Wis.	5000				
WPAW Pawtucket, R.I.	1000d		WVMI Biloxi, Miss.	1000d		590—508.2					
KTRS Midland, Tex.	5000		KGRT Las Cruces, N.Mex.	1000d		CFAR FlinFlon, Man.	1000				
KTSA San Antonio, Tex.	5000		WMCA New York, N.Y.	5000		CKAR Huntsville, Ont.	1000				
WDEV Waterbury, Vt.	5000		WSYR Syracuse, N.Y.	5000		CKRS Huelter, Que.	1000				
WVA Harrisonburg, Va.	5000		WWNC Asheville, N.C.	5000		VOCM St. John's, N.F.	1000d				
WSAU Wausau, Wis.	5000		WSHE Raleigh, N.C.	5000d		WRAG Carrollton, Ala.	1000d				
						KBHS Hot Springs, Ark.	5000d				
						KFXM San Bernardino, Cal.	1000				

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
WRRZ	Cinton, N.C.	1000d	WWWR	Russellville, Ala.	1000d	WAGM	Presque Isle, Maine	5000	KEAP	Fresno, Calif.	500d
WRFD	Worthington, Ohio	5000d	KARK	Little Rock, Ark.	5000	WORL	Boston, Mass.	5000d	KFWB	Los Angeles, Calif.	5000
890—336.9											
WLS	Chicago, Ill.	5000d	KDES	Palm Springs, Calif.	1000d	WVJ	Detroit, Mich.	5000	KLGN	GlenwoodSprgs., Colo.	1000d
WHNC	Henderson, N.C.	1000d	KVEC	San Luis Obispo, Cal.	1000d	KRSI	St. Louis Park, Minn.	1000d	WSUB	Wroton, Conn.	1000
KBYE	Okl. City, Okla.	1000d	KIUP	Durango, Colo.	5000	WBKH	Hattiesburg, Miss.	5000d	WRC	Washington, D.C.	5000d
900—333.1											
CKTS	Sherbrooke, Que.	1000	KREX	Kort Junction, Colo.	5000	KLIK	Jefferson City, Mo.	5000d	WDVH	Gainesville, Fla.	5000d
CHML	Hamilton, Ont.	5000	KLMR	Lamar, Colo.	1000	WBFB	Rochester, N.Y.	1000	WDTT	Marianna, Fla.	1000d
CHRO	Sudbury, Ont.	1000d	WMEG	Eat. Gailita, Fla.	1000d	WUPA	Utica, N.Y.	5000	WDFP	Pensacola, Fla.	500d
CJBR	Rimouski, Que.	1000d	WGST	Allanta, Ga.	5000	WPET	Greensboro, N.C.	5000	WLDQ	Pompano Beach, Fla.	1000d
CKJL	St. Jerome, Que.	1000	KAHU	Waipahu, Hawaii	1000d	WNCC	Barnesboro, Pa.	500d	WHLK	Hartwell, Ga.	1000d
CJVI	Victoria, B.C.	1000	WMOK	Metropolis, Ill.	1000d	WPEN	Philadelphia, Pa.	5000	WBBN	Perry, Ga.	500d
CKBI	Prince Albert, Sask.	1000d	WBAA	W. Lafayette, Ind.	5000	WSPA	Spartanburg, S.C.	5000	WRIP	Rossville, Ga.	5000
CJGX	Yorkton, Sask.	1000d	KFNF	Shenandoah, Iowa	1000d	KWAT	Watertown, S.Dak.	1000	WUPT	Idaho Falls, Idaho	1000d
WATV	Birmingham, Ala.	1000d	WTCW	Whitesburg, Ky.	1000d	WAGG	Franklin, Tenn.	1000d	KIUY	Danville, Ill.	1000
WGOK	Mobile, Ala.	1000d	WBDX	Bogalusa, La.	1000d	KDSX	Denison, Tex.	500	KDKA	Shreveport, La.	5000d
WDOZ	Ozak, Ala.	1000d	KTCC	Junction, La.	500d	KRBC	Houston, Tex.	5000	WCAP	Lowell, Mass.	1000d
KPRB	Fairbanks, Alaska	1000d	WPIX	Lexington Pk., Md.	5000	KSEL	Lubbock, Tex.	1000d	WAFB	Winnipeg, Minn.	1000d
KHOZ	Harrison, Ark.	1000d	WMLP	Hancock, Mich.	1000d	KJRW	Richmond, Va.	1000d	KMBC	Kansas City, Mo.	5000
KBIF	Centerville, Calif.	1000d	KDHL	Faribault, Minn.	1000d	KWAK	Charleston, W.Va.	5000	KGSM	St. Genevieve, Mo.	500
WJWL	Georgetown, Del.	1000d	KWAD	Wadena, Minn.	1000	WKTL	Sheboygan, Wis.	5000d	KVER	Clovis, N.Mex.	1000
WSWN	Bell Glade, Fla.	1000d	KRAM	Las Vegas, Nev.	1000	960—312.3					
WMOP	Ocala, Fla.	1000d	KOLO	Reno, Nev.	1000	CFAC	Calgary, Alta.	10000	KMIN	Grants, N. Mex.	1000d
WCGA	Calhoun, Ga.	1000d	KQED	Albuquerque, N.Mex.	1000	CHNS	Halifax, N.S.	10000	WTRY	Troy, N.Y.	5000
WCRY	Macon, Ga.	250d	WTIM	Trenton, N.J.	1000	CKWS	Kingston, Ont.	5000	WCLM	Wilmington, N.C.	5000d
WJIV	Savannah, Ga.	1000d	WKRT	Cortland, N.Y.	1000	WBRC	Birmingham, Ala.	5000	WONE	Wm. Salem, N.C.	1000d
KSIR	Wichita, Kan.	250	WGHQ	Saugerties, N.Y.	1000d	WMOZ	Mobile, Ala.	1000	WILK	Wilkes-Barre, Pa.	1000
KYKW	Louisville, Ky.	1000d	WBBB	Burlington, N.C.	5000d	KOD	Phoenix, Ariz.	5000	KDSJ	Deadwood, S.Dak.	1000
WREI	Pikeville, Ky.	1000d	WMMI	Columbus, Ohio	500	KAVR	Apple Valley, Calif.	5000d	WSIX	Rossville, Tenn.	5000
WREB	Oakdale, La.	250d	KGAL	Lebanon, Oreg.	1000d	KNEZ	Lompoc, Calif.	5000	KFRD	Nashberg, Tex.	1000d
WCNE	Brunswick, Maine	500d	WKVA	Lewistown, Pa.	1000d	KABL	Oakland, Calif.	1000	KSVQ	Richfield, Utah	5000
WATC	Gaylord, Mich.	1000d	WJAR	Providence, R.I.	5000	KABL	Oakland, Calif.	1000	WFHG	Bristol, Va.	5000
KTIS	Minneapolis, Minn.	1000d	KEZU	Rapid City, S.Dak.	1000d	WELI	New Haven, Conn.	5000	WWEK	Cheney City, Va.	500d
WDDT	Greenville, Miss.	1000d	WLIV	Livingston, Tenn.	1000	WGRO	Lake City, Fla.	500d	KUTV	Yakima, Wash.	5000
KFAL	Fulton, Mo.	1000d	KELP	El Paso, Tex.	1000	WJCM	Sebring, Fla.	1000d	WHAW	Weston, W.Va.	100d
KJSK	Columbus, Nebr.	1000d	KECK	Odesa, Tex.	1000	WRFC	Athens, Ga.	5000	WCUB	Manitowoc, Wis.	1000d
WOTW	Nashau, N.H.	1000d	KTLL	Texas City, Tex.	1000d	KSRJ	Salmon, Idaho	1000d	WPRE	Prairie du Chien, Wis.	5000d
WBRV	Boonville, N.Y.	1000d	KITN	Olympia, Wash.	1000d	WSBT	South Bend, Ind.	5000	990—302.8		
WSPN	Saratoga Sprgs., N.Y.	250d	KXLY	Spokane, Wash.	5000	KMA	Shenandoah, Iowa	5000	CBW	Winnipeg, Man.	5000d
WAYN	Rockingham, N.C.	1000d	WMNM	Fairmont, W.Va.	5000	KPRT	Prestonsburg, Ky.	1000d	CBT	Grand Falls, N.F.	1000
WIAM	Williamston, N.C.	1000d	WOKY	Milwaukee, Wis.	1000	WBBC	Salisbury, Md.	5000	WWWF	Fayette, Ala.	1000d
WFMG	Fargo, N.Dak.	1000d	930—322.4						WTCB	Flomaton, Ala.	500d
WAND	Canton, Ohio	500d	CFBC	Saint John, N.B.	5000	WHAK	Roger City, Mich.	5000d	RTKT	Tucson, Ariz.	10000d
WFRD	Fremont, Ohio	500d	CJDN	Edmonton, Alta.	1000d	WAGB	Greenwood, Miss.	500d	KRIS	Pittsburg, Calif.	5000
WCPA	Clearfield, Pa.	1000d	WETO	Wetasken, N.F.	1000d	KFVS	Cape Girardeau, Mo.	1000	KLIR	Denver, Colo.	1000d
WFLN	Philadelphia, Pa.	1000d	KTKN	Ketchikan, Alaska	1000d	KNEB	Scottsbluff, Nebr.	1000	WHOO	Worthington, Conn.	1000d
WGBR	Lebanon, Tenn.	5000d	KAPR	Douglas, Ariz.	1000d	KWYK	Farmington, N.Mex.	1000d	WDWD	Dawson, Ga.	1000d
KALT	Allanta, Ga.	1000d	KHJ	Los Angeles, Calif.	5000	WEAV	Plattsburg, N.Y.	5000	WCZA	Carthage, Ill.	100d
KMCO	Conroe, Tex.	500d	KIUP	Durango, Colo.	5000	WFTC	Kingston, N.C.	5000	WJZP	Jasper, Ind.	1000d
KFLD	Floydada, Tex.	250d	WKSB	Milford, Del.	500d	WGST	Woster, Ohio	1000d	KAYL	Storm Lake, Iowa	250d
KCLW	Hamilton, Tenn.	250d	WJAX	Jacksonville, Fla.	1000	KLAD	Klamath Falls, Oreg.	5000d	KJRM	Russell, Kans.	250d
WAFB	Staunton, Va.	1000d	WXNY	Saratoga, N.Y.	5000	WHYL	Carlisle, Pa.	5000d	WJMR	New Orleans, La.	250d
KUEN	Wenatchee, Wash.	500	WNGR	Bainbridge, Ga.	5000d	WADP	Kane, Pa.	1000d	KCLP	Rayville, La.	250d
WATK	Antigo, Wis.	250d	KSEI	Pocatello, Idaho	5000	WATS	Sayre, Pa.	1000d	WRKO	Waynesboro, Miss.	250d
910—329.5											
CJDV	Drumheller, Alta.	1000	WTAD	Quincy, Ill.	5000	WBEU	Beaufort, S.C.	1000d	KSPV	Artesia, N. Mex.	250d
CKLY	Lindsay, Ont.	1000	WKCT	Bowling Green, Ky.	1000	WBCE	McMinnville, Tenn.	500d	WEEB	Southern Pines, N.C.	1000d
CFJC	Kamloops, B.C.	5000	WFMD	Frederick, Md.	1000	KIMP	Mt. Pleasant, Miss.	1000d	WJEH	Gallipolis, Ohio	1000d
CHRL	Rebval, Que.	1000	WREB	Holyoke, Mass.	5000	KGSL	San Angelo, Tex.	5000	WTIG	Massion, Ohio	250d
KPHO	Phoenix, Ariz.	5000	WBCK	Battle Creek, Mich.	1000d	KQVO	Provo, Utah	5000	KABC	Albany, Oreg.	250d
KLCN	Blytheville, Ark.	5000d	WJAC	Jackson, Miss.	5000	WDBJ	Roanoke, Va.	5000	WIBG	Philadelphia, Pa.	5000d
KAMD	Camden, Ark.	1000	WKOC	Poplar Bluff, Mo.	1000	KALE	Richland, Wash.	1000	WPRM	Mayaguez, P.R.	250d
KDEO	El Cajon, Calif.	1000	KWFI	Kaisapi, Mont.	5000d	WTCH	Shawano, Wis.	1000	WAKN	Aiken, S.C.	1000d
KEWB	Oakland, Calif.	5000	KOGA	Ogallala, Nebr.	500d	970—309.1					
KOXR	Oxnard, Calif.	1000d	WNNH	Rochester, N.H.	5000d	CKCH	Hull, Que.	5000	WERH	Hamilton, Ala.	5000d
KPOF	Fr. Denver, Colo.	5000	WPAT	Paterson, N.J.	5000	WTFB	Troy, Ala.	5000	KNSJ	Jonesboro, Ark.	1000d
WHAY	New Britain, Conn.	5000	WBEN	Buffalo, N.Y.	5000	KBIS	Bakersfield, Calif.	1000d	KCHV	Coachella, Calif.	1000d
WPLA	Plant City, Fla.	1000d	WIST	Charlotte, N.C.	5000	KBEF	Modesto, Calif.	1000d	KFEL	Pueblo, Colo.	1000d
WGAF	Valdosta, Ga.	5000	WROR	Rochester, N.H.	5000	WFLA	Tampa, Fla.	5000	WFLA	Tampa, Fla.	5000
WKAKO	Lawrenceville, Ill.	5000	WEOL	Elyria, Ohio	1000	WOP	Viadala, Ga.	5000d	WHIP	Hawaii	5000d
WSUI	Iowa City, Iowa	5000	WKYI	Yukon, N.D.	1000	KHBC	Hilo, Hawaii	5000d	KAYT	Rupert, Idaho	1000d
WBSL	Baton Rouge, La.	5000	KAGI	Oklahoma City, Okla.	5000	WMAY	Springfield, Ill.	1000	WAVE	Louisville, Ky.	5000
WABI	Bangor, Me.	1000	KWGN	Grand Trans, Oreg.	1000	KSYL	Alexandria, La.	1000	WGSB	Portland, Maine	5000
WFDF	Fridt, Mich.	5000	WCNR	Bloomsburg, Pa.	1000d	WAND	Aberdeen, Md.	5000	WESO	Southden, Md.	1000d
WCOC	Meridian, Miss.	5000	KSDN	Aberdeen, S.D.	1000d	WJAN	Ispheming, Mich.	5000d	WKHM	Jackson, Mich.	1000
KOYN	Billings, Mont.	1000d	WSEY	Sevierville, Tenn.	5000d	KOKK	Billings, Mont.	5000	KJLT	No. Platte, Nebr.	5000d
KYSS	Missoula, Mont.	1000d	WDEI	Center, Tex.	1000d	WNTA	Newark, N.J.	5000	WBRB	Buffalo, N.Y.	5000
KBIM	Roswell, N.Mex.	5000d	KENY	Bellingham-Ferndale Wash.	1000d	WCHN	Cheney, N.Y.	5000	WRCS	Ashokli, N.C.	1000d
WLAS	Jacksonville, N.C.	1000d	WSAZ	Huntington, W.Va.	1000d	WBIT	Canton, N.Dak.	1000d	WDAY	Fargo, N.Dak.	5000
CKJB	Minot, N.Dak.	1000d	WLBL	Auburndale, Wis.	5000d	WICA	Ashtabula, Ohio	5000	WATH	Athens, Ohio	1000d
WPFB	Middletown, Ohio	1000	940—319.0						KAKC	Tulsa, Okla.	1000d
KGCL	Miami, Okla.	1000	CBM	Montreal, Que.	5000d	CKNB	Campbellton, N.B.	1000d	KOIN	Portland, Oreg.	5000
KURY	Brookings, Oreg.	500	CJJB	Yorkton, Sask.	1000d	CKBB	Barrie, Ont.	5000	WWSW	Pittsburgh, Pa.	5000
WAVL	Anolio, Pa.	1000d	CJJB	Vernon, B.C.	1000	WRMA	Montgomery, Ark.	1000d	WJMX	Florence, S.C.	5000
WGBI	Seranton, Pa.	1000	KFRE	Fresno, Calif.	5000d	KJK	Forrest City, Ark.	5000d	WJMK	Fort Worth, Tex.	1000d
WSBA	York, Pa.	1000	WNAZ	Miami, Fla.	5000d	KFSA	Fort Smith, Ark.	1000	KREM	Spokane, Wash.	5000
WPRP	Ponce, P.R.	5000	WNAZ	Macon, Ga.	5000d	KAHU	Auburn, Calif.	1000d	WYD	Pineville, W.Va.	1000d
WJRD	Spartanburg, S.C.	5000	WMLX	Macon, Ga.	1000	KIMN	Denver, Colo.	5000	WHA	Madison, Wis.	5000d
WJHL	Johnson City, Tenn.	1000	KIOA	Des Moines, Iowa	1000	WFSB	Ft. Walton Beh., Fla.	1000d	980—305.9		
WEPG	S. Pittsburgh, Tenn.	500d	WYLD	New Orleans, La.	1000	WDFI	Orlando, Fla.	5000	CFPL	London, Ont.	10000
KRIO	McAllen, Tex.	1000	WESA	Charleroi, Pa.	250	WGTA	Summerville, Ga.	1000d	CBV	Quebec, Que.	5000
KRRV	Sherman, Tex.	1000	WIPR	San Juan, P.R.	10000	WGOV	Valdosta, Ga.	5000	CHEX	Peterboro, Ont.	5000
KALL	Salt Lake City, Utah	1000	KIXZ	Amarillo, Tex.	1000	KBOI	Bo. Idaho	5000	CKRM	Regina, Sask.	5000
WRRJ	White River Junction, Vermont	1000d	950—315.6						WKLF	Clanton, Ala.	1000d
WRNL	Richmond, Va.	1000d	CKNB	Campbellton, N.B.	1000	CKNB	Campbellton, N.B.	1000	KINS	Eureka, Calif.	5000
WHYE	Roanoke, Va.	1000d	CKBB	Barrie, Ont.	5000	CKBB	Barrie, Ont.	5000	WHITE'S RADIO LOG 163		
KDRD	Pasco, Wash.	1000d	WRMA	Montgomery, Ark.	1000d	WRMA	Montgomery, Ark.	1000d			
KODE	Renton, Wash.	1000	KJFK	Forrest City, Ark.	5000d	KJFK	Forrest City, Ark.	5000d			
KISN	Vancouver, Wash.	1000	KFSA	Fort Smith, Ark.	1000	KFSA	Fort Smith, Ark.	1000			
WWSM	Hayward, Wis.	1000d	KAHU	Auburn, Calif.	1000d	KAHU	Auburn, Calif.	1000d			
WDRD	Sturgeon Bay, Wis.	500d	KIMN	Denver, Colo.	5000	KIMN	Denver, Colo.	5000			
920—325.9											
CJCH	Halifax, N.S.	10000	WFSB	Ft. Walton Beh., Fla.	1000d	WFSB	Ft. Walton Beh., Fla.	1000d			
CJCH	Woodstock, N.B.	1000	WDFI	Orlando, Fla.	5000	WDFI	Orlando, Fla.	5000			
CJNX	Wingham, Ont.	2500	WGTA	Summerville, Ga.	1000						

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
WSKY	Asheville, N.C.	250	KDEC	Decorah, Iowa	250	WYTH	Madison, Ga.	1000	WTAL	Tallahassee, Fla.	5000
WFAT	Fayetteville, N.C.	250	KBVL	Decorah, Iowa	250	WIZZ	Streator, Ill.	5000	WGBA	Columbus, Ga.	5000
WFR	High Point, N.C.	250	KWBZ	Ditumwa, Iowa	250	WGL	Ft. Wayne, Ind.	1000	WJCC	Commerce, Ga.	1000
WISP	Kinston, N.C.	250	KICD	Spencer, Iowa	250	WRAY	Princeton, Ind.	1000	WTFI	Twin Falls, Idaho	5000
WNCN	Newton, N.C.	250	KIUL	Garden City, Kans.	250	KFKU	Lawrence, Kans.	5000	KEIC	Charleston, Ill.	1000
WCBT	Roanoke Rap., N.C.	250	KAKE	Wichita, Kans.	250	WREN	Topoka, Kans.	5000	WCBF	Rock Island, Ill.	5000
KDIX	Dickinson, N.Dak.	250	WINN	Louisville, Ky.	250	WLCK	Scottsville, Ky.	5000	WHMR	Elkhart, Ind.	500
WCPO	Cincinnati, Ohio	250	WFTM	Maysville, Ky.	250	WGUY	Bangor, Maine	5000	WYCA	Gary, Ind.	1000
WCOL	Columbus, Ohio	250	WPKF	Waynesville, Ky.	250	WARE	Ware, Mass.	5000	WVBC	Waynesport, Ind.	1000
WURO	Ironton, Ohio	250	WFSO	Somerset, Ky.	250	WBCB	Bay City, Mich.	1000	KSRB	Liberal, Kans.	1000
WTOL	Toledo, Ohio	250	KASO	Minden, La.	250	KOTE	Fergus Falls, Minn.	1000	WAIN	Columbia, Ky.	1000
KADA	N. of Ada, Okla.	250	KANE	New Iberia, La.	250	KCUK	Red Wing, Minn.	1000	WFUL	Fulton, Ky.	1000
WBBZ	Ponca City, Okla.	250	WCDO	Lewiston, Maine	250	WHNY	McComb, Miss.	5000	KVCL	Winnfield, La.	1000
KVAS	Astoria, Oreg.	250	WCEN	Cambridge, Md.	250	KVLV	Fallon, Nev.	1000	WSPR	Springfield, Mass.	1000
KRNS	Brown, Oreg.	250	WWEJ	Hagerstown, Md.	250	WMTR	Morrisstown, N.J.	1000	WXYZ	Detroit, Mich.	5000
KDSS	Cross Bay, Oreg.	250	WHAJ	Greenfield, Mass.	250	WIPS	Ticonderoga, N.Y.	1000	KWEB	Rochester, Minn.	5000
KGRD	Gresham, Oreg.	250	WOCB	W. Yarmouth, Mass.	250	WBRM	Marion, N.C.	1000	WLSM	Louisville, Miss.	1000
KYJC	Medford, Oreg.	250	WATT	Cadillac, Mich.	250	WCHO	Washington Court House, Ohio	5000	KLSN	St. Joseph, Mo.	1000
KQIK	Lakeview, Oreg.	250	WCBY	Cheboygan, Mich.	250	WPEL	Montrose, Pa.	1000	WTSN	Dover, N.H.	5000
WBVP	Beaver Falls, Pa.	250	WJPO	Ishpeming, Mich.	250	WPEC	Pittsburgh, Pa.	5000	WGLV	Vineland, N.J.	5000
WEEX	Easton, Pa.	250	WJIM	Lansing, Mich.	250	WNOW	York, Pa.	1000	KRAC	Alamogordo, N.Mex.	1000
WKBO	Harrisburg, Pa.	250	WVFG	Hibbing, Minn.	250	WTMA	Charleston, S.C.	5000	WHLO	Niagara Falls, N.Y.	5000
WCRO	Johnstown, Pa.	250	WJON	St. Cloud, Minn.	250	WKBL	Covington, Tenn.	1000	WDLA	Walton, N.Y.	1000
KHFP	Lock Haven, Pa.	250	WMPA	Aberdeen, Miss.	250	KFTV	Paris, Tex.	5000	WCGC	Belmont, N.C.	1000
WAKK	Arcadio, P.R.	250	WGBM	Grenada, Miss.	250	KRAC	Port Arthur, Tex.	5000	WPMP	Smithfield, N.C.	1000
WERI	Westerly, R.I.	250	WGCM	Gulfport, Miss.	250	KUKA	San Antonio, Tex.	5000	KBOM	Mandan, N.Dak.	1000
WAIM	Anderson, S.C.	250	WMOX	Meridian, Miss.	250	KSMI	Seminole, Tex.	1000	WFLC	Camden, Ohio	1000
WNOK	Columbia, S.C.	250	WMI5	Natchez, Miss.	250	KVEL	Vernal, Utah	1000	KWPR	Claremore, Okla.	5000
WOLS	Florence, S.C.	250	KFMO	Ft. River, Mo.	250	KVDA	Danville, Va.	5000	KAJO	Kansas Pass, Oreg.	1000
KISD	Sioux Falls, S.Dak.	250	KWOS	Jefferson City, Mo.	250	WYSA	Franklin, Va.	1000	WBR	Lebanon, Pa.	1000
WJMT	McMinnville, Tenn.	250	KNEM	Nevada, Mo.	250	WNRG	Grundy, Va.	1000	WBHC	Hampton, S.C.	1000
KXWJ	Corpan, Tex.	250	KBMY	Billings, Mont.	250	KWSC	Pullman, Wash.	5000	KIHO	Sioux Falls, S.Dak.	1000
KDLK	Del Rio, Tex.	250	KLBJ	Cloutier, Mont.	250	KTW	Seattle, Wash.	1000	WLK	Newport, Tenn.	5000
KNUZ	Houston, Tex.	250	KXLL	Helena, Mont.	250	WEMP	Milwaukee, Wis.	5000	KIOX	Bay City, Tex.	1000
KERV	Kerrville, Tex.	250	KFLR	Lincoln, Nebr.	250	1260-238.0			KHEM	Big Spring, Tex.	1000
KLVT	Loveland, Tex.	250	KODY	North Platte, Nebr.	250	CFRN	Edmonton, Alta.	1000	KEPS	El Paso, Tex.	1000
KEEE	Neogoches, Tex.	250	KELK	Elko, Nev.	250	DYVE	Cebu, P.I.	1000	KJZF	Jarvis Worth, Tex.	5000
KOSA	Odessa, Tex.	250	WKBR	Manchester, N.H.	250	WYUO	Newport News, Va.	1000	KCVL	Colville, Wash.	1000
KHHH	Panama, Tex.	250	WSNJ	Bridgeton, N.J.	250	KBAM	Longview, Wash.	1000	WKYR	Keyser, W.Va.	5000
KSEY	Seymour, Tex.	250	KAYN	Baytown, N.Mex.	250	1280-234.2			CJMS	Montreal, Que.	5000
KCMC	Texarkana, Tex.	250	KCLV	Clovis, N.Mex.	250	CFRT	Birmingham, Ala.	5000	KCKV	Quebec, Que.	5000
KSST	Spulphin Sprgs., Tex.	250	WGBB	Freeport, N.Y.	250	KCCB	Corning, Ark.	5000	WPID	Piedmont, Ala.	1000
KWTX	Waco, Tex.	250	WVGA	Geneva, N.Y.	250	KBCB	Nashville, Ark.	5000	WNPT	Tuscaloosa, Ala.	5000
KMUR	Murray, Utah	250	WJTN	Jamestown, N.Y.	250	KGIL	San Fernando, Calif.	1000	KHEP	Phoenix, Ariz.	1000
KOAL	Price, Utah	250	WVOS	Liberty, N.Y.	250	KYA	San Francisco, Calif.	5000	KFOJ	Long Beach, Calif.	1000
WJOY	Burlingame, Vt.	250	WNBZ	Saranac Lake, N.Y.	250	WWDC	Washington, D.C.	5000	KJON	Stockton, Calif.	1000
WBBI	Abingdon, Va.	250	WWSH	Schenectady, N.Y.	250	WFTW	Fort Walton Beach, Florida	1000	WNPJ	Tuscaloosa, Ala.	5000
WCFV	Clifton Forge, Va.	250	WATW	Wartburg, N.C.	250	WMMA	Miami, Fla.	5000	KWEX	Wilmington, Del.	1000
WVFA	Fredricksburg, Va.	250	WPNF	Brevard, N.C.	250	WPPF	Palatka, Fla.	1000	KFOJ	Long Beach, Calif.	1000
WNOR	Norfolk, Va.	250	WSOC	Charlotte, N.C.	250	WHAB	Baxley, Ga.	5000	KJON	Stockton, Calif.	1000
KQTY	Everett, Wash.	250	WCNC	Elizabeth City, N.C.	250	WTJH	East Point, Ga.	5000	WSUX	Seaford, Del.	1000
KLYK	Spokane, Wash.	250	WJAL	Jacksonville, N.C.	250	KIFI	Idaho Falls, Idaho	5000	WDSP	DeFuniak Springs, Florida	5000
KREW	Sunnyside, Wash.	250	WRAL	Raleigh, N.C.	250	KWEJ	Weiser, Idaho	1000	WQIK	Jacksonville, Fla.	5000
WLOG	Logan, W.Va.	250	KDLR	Devils Lake, N.Dak.	250	WFBM	Indianapolis, Ind.	2500	WIPC	Lake Wales, Fla.	1000
WTAP	Parkersburg, W.Va.	250	WHIZ	Zanesville, Ohio	250	KFGQ	Boone, Iowa	2500	WIBB	Macon, Ga.	5000
WHBY	Appleton, Wis.	250	KVSO	Ardmore, Okla.	250	KWHK	Hutchinson, Kans.	1000	WBRD	Aurora, Ill.	2500
WCLO	Janesville, Wis.	250	KBEK	Elk City, Okla.	250	WEZE	Boston, Mass.	5000	WFBV	Evansville, Ind.	5000
WHVF	Wausau, Wis.	250	KBEL	Idabel, Okla.	250	WALM	Albion, Mich.	1000	KSCB	Newton, Iowa	1000
KVOC	Casper, Wyo.	250	KKBL	Kumulge, Okla.	250	WJBL	Holland, Mich.	5000	KDOK	Arkansas City, Kans.	1000

1240-241.8

CFLM	La Tuque, Que.	1000
CFNW	Norman Wells, Northwest Terr.	100
CFPR	Prince Rupert, B.C.	250
CFWH	Whitehorse, Y.T.	250
CJAV	Port Alberni, B.C.	250
CJCS	Stratford, Ont.	250
CJRW	Somersdore, P.E.I.	100
CKKS	St. Hyacinthe, Que.	250
CKLS	LaSarre, Que.	250
WEDJ	Breaux, Ala.	250
WULA	Eufaula, Ala.	250
WQWL	Florence, Ala.	250
WARF	Jasper, Ala.	250
KWJB	S. of Globe, Ariz.	250
KOFA	Yuma, Ariz.	250
KYRC	Arkadelphia, Ark.	250
KAGH	Crown Hill, Ark.	250
KHOZ	Harrison, Ark.	250
KWAK	Stuttgart, Ark.	250
KPLY	Crecent City, Calif.	250
KRDU	Dinuba, Calif.	250
KMBY	Monterey, Calif.	1000
KPPC	Pasadena, Calif.	100
KRKS	Ridgecrest, Calif.	250
KROY	Sacramento, Calif.	250
KRNO	San Bernardino, Calif.	250
KSON	San Diego, Calif.	250
KMSA	Santa Maria, Calif.	250
KRSO	Susanville, Calif.	250
KDUE	Colorado Sprgs., Colo.	250
KDGO	Durango, Colo.	250
KSLY	Monte Vista, Colo.	250
KCRT	Trinidad, Colo.	250
WWCO	Waterbury, Conn.	250
WBGC	Chipey, Fla.	250
WLCO	Eustis, Fla.	250
WINK	Fort Myers, Fla.	250
WMMB	Melbourne, Fla.	250
WFOY	St. Augustine, Fla.	250
WBHB	Fitzgerald, Ga.	250
WDUN	Gainesville, Ga.	250
WLAG	LaGrange, Ga.	250
WBML	Macon, Ga.	250
WNNS	Statesboro, Ga.	250
WPAX	Thomasville, Ga.	250
WTAW	Thomasville, Ga.	250
KANI	Kailua, Hawaii	250
KVNI	Coeur d'Alene, Idaho	250
KWIK	Pocatello, Idaho	250
WCRW	Chicago, Ill.	100
WEDC	Chicago, Ill.	100
WBCB	Chicago, Ill.	250
WBEQ	Harrisburg, Ill.	250
WTAX	Springfield, Ill.	250
WSDR	Sterling, Ill.	100
WHBU	Anderson, Ind.	250

1250-239.9

CHWO	Oakville, Ont.	1000
KKBL	Matane, Que.	5000
CKRB	Ville St. Georges, Que.	5000
CKSB	St. Bonifare, Man.	1000
WZOB	Ft. Payne, Ala.	1000
WETU	Wetumpka, Ala.	5000
KFAY	Fayetteville, Ark.	5000
KAJI	Little Rock, Ark.	1000
KHOT	Madera, Calif.	5000
KTMS	Santa Barbara, Calif.	1000
KXXI	Golden, Colo.	1000
WNER	Live Oak, Fla.	1000
WRIM	Pahokee, Fla.	5000
WDAE	Tampa, Fla.	5000

1270-236.1

CHAT	Medicine Hat, Alta.	1000
CHWK	Chiliwaek, B.C.	1000
JCB	Sydney, N.S.W.	5000
CFGT	St. Joseph d'Alma, Quebec	1000
WGSV	Guntersville, Ala.	1000
WAIP	Priehard, Ala.	1000
KBYR	Anchorage, Alaska	1000
KDJJ	Holbrook, Ariz.	1000
KFAR	Flagstaff, Calif.	1000
KKOT	Yuba City, Calif.	1000
WNOG	Naples, Fla.	5000
WHYI	Orlando, Fla.	5000
KMCM	McMinnville, Oreg.	1000
WERC	Erie, Pa.	5000
WPHB	Phillipsburg, Pa.	1000
WISO	Ponce, P.R.	1000
WUUU	Greenville, S.C.	1000
WJOT	Lake City, S.C.	1000
KWYR	Winner, S.Dak.	5000
WVFS	Chattanooga, Tenn.	1000
WCHN	Chickasaw, Tenn.	1000
WBNK	Dickson, Tenn.	1000
WCLC	Jamestown, Tenn.	1000
KSPJ	Diboll, Tex.	1000
KBLP	Falfurrias, Tex.	5000
KWFR	San Angelo, Tex.	1000
KTUE	Tulia, Tex.	1000
KTAE	Taylor, Tex.	1000
WCHV	Charlottesville, Va.	5000
WBCR	Christiansburg, Va.	1000
KWIK	Moses Lake, Wash.	1000
WVVW	Grafton, W.Va.	5000
WVIS	Black River Falls, Wis.	1000
WEKZ	Monroe, Wis.	1000
KPOW	Powell, Wyo.	5000

WTAL	Tallahassee, Fla.	5000
WGBA	Columbus, Ga.	5000
WJCC	Commerce, Ga.	1000
WTFI	Twin Falls, Idaho	5000
KEIC	Charleston, Ill.	1000
WCBF	Rock Island, Ill.	5000
WHMR	Elkhart, Ind.	500
WYCA	Gary, Ind.	1000
WVBC	Waynesport, Ind.	1000
KSRB	Liberal, Kans.	1000
WAIN	Columbia, Ky.	1000
WFUL	Fulton, Ky.	1000
KVCL	Winnfield, La.	1000
WSPR	Springfield, Mass.	1000
WXYZ	Detroit, Mich.	5000
KWEB	Rochester, Minn.	5000
WLSM	Louisville, Miss.	1000
KLSN	St. Joseph, Mo.	1000
WTSN	Dover, N.H.	5000
WGLV	Vineland, N.J.	5000
KRAC	Alamogordo, N.Mex.	1000
WHLO	Niagara Falls, N.Y.	5000
WDLA	Walton, N.Y.	1000
WCGC	Belmont, N.C.	1000
WPMP	Smithfield, N.C.	1000
KBOM	Mandan, N.Dak.	1000
WFLC	Camden, Ohio	1000
KWPR	Claremore, Okla.	5000
KAJO	Kansas Pass, Oreg.	1000
WBR	Lebanon, Pa.	1000
WBHC	Hampton, S.C.	1000
KIHO	Sioux Falls, S.Dak.	1000
WLK	Newport, Tenn.	5000
KIOX	Bay City, Tex.	1000
KHEM	Big Spring, Tex.	1000
KEPS	El Paso, Tex.	1000
KJZF	Jarvis Worth, Tex.	5000
WYUO	Newport News, Va.	1000
KCVL	Colville, Wash.	1000
KBAM	Longview, Wash.	1000
WKYR	Keyser, W.Va.	5000

1280-234.2

CJMS	Montreal, Que.	5000
KCKV	Quebec, Que.	5000
WPID	Piedmont, Ala.	1000
WNPT	Tuscaloosa, Ala.	5000
KHEP	Phoenix, Ariz.	1000
KFOJ	Long Beach, Calif.	1000
KJON	Stockton, Calif.	1000
WSUX	Seaford, Del.	1000
WDSP	DeFuniak Springs, Florida	5000
WQIK	Jacksonville, Fla.	5000
WIPC	Lake Wales, Fla.	1000
WIBB	Macon, Ga.	5000
WBRD	Aurora, Ill.	2500
WFBV	Evansville, Ind.	5000
KSCB	Newton, Iowa	1000
KDOK	Arkansas City, Kans.	1000
WCPM	Cumberland, Ky.	1000
WDSU	New Orleans, La.	5000
WCLC	Dak Grove, La.	5000
WEIM	Fitchburg, Mass.	5000
WFYC	Alma, Mich.	1000
WTCO	Wrentham, Minn.	5000
KVOX	Moorhead, Minn.	1000
WJSJ	Magee, Miss.	5000
KDKD	Clinton, Mo.	1000
KYRO	Potosi, Mo.	5000
KRNI	Broken Bow, Nebr.	1000
KTOO	Henderson, Nev.	5000
WHBI	Newark, N.J.	2500
KUUN	Uniontown, N.Mex.	5000
KHOB	Hoobs, N.Mex.	1000
WADD	New York, N.Y.	5000
WVET	Rochester, N.Y.	5000
WRSR	Saratoga Sprgs., N.Y.	1000
WSAT	Salisbury, N.C.	1000
WONW	DeFance, Ohio	500
WLMJ	Jackson,	

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
KITO	San Bernardino, Calif.	5000	KOKX	Keokuk, Iowa	1000	KGAK	Gallup, N. Mex.	5000	KNDE	Aztec, N.M.	250
WCCC	Hartford, Conn.	5000	WTTL	Madisonville, Ky.	5000	WEVD	New York, N.Y.	5000	KSIL	Silver City, N. Mex.	250
WTUX	Wilmington, Del.	10000	WDOC	Prestonsburg, Ky.	5000	WFOW	New York, N.Y.	5000	WBGD	Auburn, N.Y.	250
WTMC	Ocala, Fla.	5000	WKKS	Sulphur, La.	500	WEBO	Owego, N.Y.	10000	WEN	Geneva, N.Y.	250
WSCM	Panama City Beach, Fla.	5000	KUZN	W. Monroe, La.	10000	WHAZ	Troy, N.Y.	10000	WJOC	Jamestown, N.Y.	250
WIRK	W. Palm Bch., Fla.	5000	WLOB	Portland, Maine	10000	WFIN	Findlay, Ohio	10000	WUSJ	Lockport, N.Y.	250
WDEC	Americus, Ga.	10000	WORC	Worcester, Mass.	5000	WKVO	Wellston, Ohio	5000	WMSA	Massena, N.Y.	250
WCHC	Canton, Ga.	5000	WKMH	Dearborn, Mich.	5000	KPOJ	Portland, Ore.	5000	WALL	Middletown, N.Y.	250
WTOC	Savannah, Ga.	5000	KRBI	St. Peter, Minn.	10000	WBLF	Bellefonte, Pa.	5000	WIRY	Plattsburg, N.Y.	250
WYFE	Pocatello, Idaho	10000	WXXX	Hattiesburg, Miss.	10000	WICU	Erie, Pa.	5000	WJRI	Lanor, N.C.	250
KIRL	Peoria, Ill.	5000	KFSB	Joplin, Mo.	5000	WLA-T	Conway, S.C.	5000	WTSY	Lumberton, N.C.	250
KBFL	Benton, Ky.	10000	KFBB	Great Falls, Mont.	5000	WBBC	Greenville, S.C.	10000	WQXF	Waxhaw, N.C.	250
KJF	Jennings, La.	10000	WLK	W. Lakes Park, N.J.	250	WAEW	Crossville, Tenn.	5000	WQOW	Washington, N.C.	250
WGR	Houghton Lake, Mich.	5000	WCAM	Camberly, N.J.	250	WTRO	Dyersburg, Tenn.	5000	WGNJ	Wilmington, N.C.	250
WNIL	Niles, Mich.	5000	WVIP	Mt. Kisco, N.Y.	10000	KMIL	Cameron, Tex.	5000	WAIR	Winston-Salem, N.C.	250
WOIA	Saline, Mich.	5000	WTLT	Utica, N.Y.	1000	KSWA	Graham, Tex.	5000	KGPC	Ashtland, N.D.	250
KBMO	Benson, Minn.	5000	WISE	Asheville, N.C.	5000	KINE	Kingsville, Tex.	10000	WNGO	Gratland, Ohio	250
WBLE	Batesville, Miss.	10000	WKTC	Charlotte, N.C.	1000	KDOK	Tyler, Tex.	10000	WDTB	Athens, Ohio	250
KALM	Thayer, Mo.	10000	WTK	Durham, N.C.	1000	WBTM	Danville, Va.	5000	WVTE	Springfield, Ohio	250
KCVG	Missoula, Mont.	5000	KNOX	Grand Forks, N. Dak.	5000	WESR	Tasley, Va.	10000	WSTV	Steubenville, Ohio	250
KOIL	Omaha, Neb.	5000	WFAH	Alliance, Ohio	10000	KFKF	Bellevue, Wash.	10000	KIHN	Hugo, Okla.	250
WKNE	Keene, N.H.	5000	KNPT	Newport, Ore.	5000	WETZ	New Martinsville, Va.	10000	KOCY	Okla. City, Okla.	250
KSRC	Secor, N.H.	5000	WBFD	Bedford, Pa.	10000	WBHL	Sheboygan, Wis.	1000	KLOO	Corvallis, Ore.	250
WGLI	Babylon, N.Y.	1000	WGSA	Ephrata, Pa.	10000	KOVE	Lander, Wyo.	1000	KIHR	Hood River, Ore.	250
WBNF	Binghamton, N.Y.	5000	WNAE	Warren, Pa.	5000	1340-223.7			KFIR	North Bend, Ore.	250
WHKY	Hickory, N.C.	5000	WKD	Kingstree, S.C.	5000	CFGB	Goose Bay, Nfld.	250	WFBG	Altoona, Pa.	250
WEYE	Sanford, N.C.	10000	WDD	Chattanooga, Tenn.	5000	CFSL	Weyburn, Sask.	250	KWV	Conestoga, Pa.	250
WMP	Bakersfield, Calif.	5000	WDJ	Jackson, Tenn.	5000	CFYK	Yellow Knife, N.W.T.	150	WSAJ	Grove City, Pa.	100
WHIO	Dayton, Ohio	5000	WBNT	Oneida, Tenn.	10000	CHAD	Amos, Que.	250	WKRZ	Oil City, Pa.	250
KUMA	Pendleton, Ore.	5000	KZIP	Amarillo, Tex.	10000	CHRD	Yarmouth, N.S.	250	WHAT	Philadelphia, Pa.	250
KLIQ	Portland, Ore.	10000	WRR	Rocky Hill, Conn.	5000	CJQC	Quebec, Que.	250	WRAP	Reading, Pa.	250
WTRN	Tyrona, Pa.	10000	WKOY	Odessa, Tex.	5000	CKAR-I	Parry Sound, Ont.	250	WBRE	Wilkes-Barre, Pa.	250
WICE	Providence, R.I.	5000	KUBO	San Antonio, Tex.	5000	CKOX	Woodstock, Ont.	250	WPA	Williamsport, Pa.	250
WFIG	Sumter, S.C.	1000	WEEL	Fairfax, Va.	5000	WKUL	Cullman, Ala.	250	WKEK	Charleston, S.C.	250
WATO	Oak Ridge, Tenn.	10000	WGH	Newport News, Va.	5000	WJOF	Florence, Ala.	250	WRHI	Rock Hill, S.C.	250
KBT	Big Lake, Tex.	10000	KARY	Prosser, Wash.	10000	WJWG	Selma, Ala.	250	WSSC	Sumter, S.C.	250
KIVY	Crockett, Tex.	5000	WIBA	Madison, Wis.	5000	WFB	Bay Mills, Mich.	250	KIIV	Huron, S.D.	250
KRGV	Westlaco, Tex.	5000	1320-227.1			WJW	Wichita Falls, Tex.	5000	KRSD	Rapid City, S. Dak.	250
KTRN	Wichita Falls, Tex.	5000	CJSO	Sorel, P.Q.	1000	WJWB	Wichita Falls, Tex.	5000	WBAC	Cleveland, Tenn.	250
WPVA	Colonial Hgts., Va.	5000	CKKW	Kitchener, Ont.	1000	KIBH	Seward, Alaska	250	WKRM	Columbia, Tenn.	250
WAGE	Leesburg, Va.	10000	WAGF	Dothan, Ala.	1000	KIKO	Miami, Ariz.	250	WGRV	Greenville, Tenn.	250
WVOW	Logan, W. Va.	10000	WENN	Homewood, Ala.	10000	KKNO	Nogales, Ariz.	250	WGNK	Knoxville, Tenn.	250
WML	Milwaukee, Wis.	10000	KWHN	Fort Smith, Ark.	10000	KZOK	Prescott, Ariz.	250	WHHM	Memphis, Tenn.	250
WCOW	Sparta, Wis.	10000	KRLW	Walnut Ridge, Ark.	10000	KBTA	Batesville, Ark.	250	WCDT	Winchester, Tenn.	250
1300-230.6			KHSJ	Hemet, Calif.	5000	KBRS	Springdale, Ark.	250	KWKC	Abilene, Tex.	250
CBAF	Moncton, N.B.	5000	KUDE	Oceanside, Calif.	500	KENL	Arcata, Calif.	250	KAND	Corsicana, Tex.	250
WAS	Tallahassee, Fla.	10000	KCRA	Sacramento, Calif.	5000	KMK	Greenock, Calif.	250	KSE	St. Paul, Pa.	250
KWCB	Searcy, Ark.	10000	KRY	Rocky Ford, Colo.	10000	KSFE	Needles, Calif.	250	KRAF	Fredericksburg, Tex.	250
KROP	Brawley, Calif.	1000	WATR	Waterbury, Conn.	10000	KATY	San Luis Obispo, Calif.	250	KDUB	Lubbock, Tex.	250
KYNO	Fresno, Calif.	1000	WGMA	Hollywood, Fla.	10000	KIST	Santa Barbara, Calif.	250	KRBA	Lufkin, Tex.	250
KWKV	Pasadena, Calif.	1000	WJHP	Jacksonville, Fla.	5000	KOMY	Watsonville, Calif.	250	KVKM	Monahans, Tex.	250
KVOR	Color. Sprgs., Colo.	1000	WHIE	Griffin, Ga.	10000	KDEN	Denver, Colo.	250	KPDN	Pampa, Tex.	250
WAVZ	New Haven, Conn.	1000	WNEG	Toceca, Ga.	10000	KVRH	Salida, Colo.	250	KOLE	Port Arthur, Tex.	250
WRKT	Cocoa Beach, Fla.	5000	WKAN	Kankakee, Ill.	10000	KVRS	New Haven, Conn.	250	KTXL	San Angelo, Tex.	250
WMTM	Tamiami, Fla.	5000	KMAQ	Maquoketa, Iowa	5000	WOK	Washington, D.C.	250	WTWN	St. Johnsbury, Vt.	250
WML	Moultrie, Ga.	5000	KLWN	Lawrence, Kans.	5000	WTAN	Clearwater, Fla.	250	WSTA	Charlotte Amalie, V.I.	250
WIMO	Winder, Ga.	10000	WBR	Bardonia, Ky.	10000	WRD	Daytona Bch., Fla.	250	WKEY	Covington, Va.	250
KOZE	Lawiston, Idaho	5000	WNGO	Mayfield, Ky.	10000	WDR	Lake City, Fla.	250	WHAP	Hopewell, Va.	250
WTAQ	LaGrange, Ill.	5000	KVHL	Homer, La.	10000	WTVS	Marianna, Fla.	250	WJMA	Orange, Va.	250
WFRX	W. Frankfort, Ill.	10000	WICO	Salisbury, Md.	10000	WQXT	Palm Beach, Fla.	250	KAGT	Anacortes, Wash.	250
WHLT	Huntington, Ind.	5000	WARA	Attleboro, Mass.	1000	WNSM	Valparaiso-Niceville, Fla.	250	KPK	Port Wash., Wash.	250
WMFT	Terre Haute, Ind.	5000	WILS	Lansing, Mich.	5000	WGAU	Athens, Ga.	250	KAPA	Raymond, Wash.	250
KGLO	Mason City, Iowa	5000	WDMJ	Marquette, Mich.	1000	WAKE	Atlanta, Ga.	250	KMEL	Wenatchee, Wash.	250
WBG	Lexington, Ky.	1000	WOPC	Houston, Miss.	5000	WBQA	Augusta, Ga.	250	WHAR	Clarksville, W. Va.	250
WIBR	Brown Rouge, La.	1000	WRJW	Piquette, Miss.	5000	WGAA	Cedartown, Ga.	250	WPCM	Martinsburg, W. Va.	250
KLUE	Shreveport, La.	10000	KXLW	Clayton, Mo.	10000	WOKS	Columbus, Ga.	250	WMON	Montgomery, W. Va.	250
WBR	Baltimore, Md.	5000	KOLT	Scottsbluff, Neb.	5000	WBT	York, Pa.	250	WVOT	Welch, W. Va.	250
WDA	Quincy, Mass.	10000	WHHG	Hornell, N.Y.	5000	WTIF	Tifton, Ga.	250	WLDY	Waltham, Wis.	250
WDD	Grand Rapids, Mich.	5000	WAGY	Forest City, N.C.	5000	KPST	Preston, Idaho	250	WRIT	Milwaukee, Wis.	250
WRBC	Jackson, Miss.	5000	WCOG	Greensboro, N.C.	5000	WSOY	Deatur, Ill.	250	WFHR	Wis. Rapids, Wis.	250
WMO	Marshall, Mo.	10000	KQDY	Minot, N. Dak.	10000	WJPF	Herrin, Ill.	250	KOWB	Laramie, Wyo.	250
KBRL	McCook, Neb.	10000	WJOK	Lanesville, Ohio	10000	WJOL	Joliet, Ill.	250	KWOR	Worldway, Wyo.	250
KPTL	Carson City, Nev.	5000	WKEV	Keokuk, Iowa	10000	WBW	Bedford, Ind.	250	13150-222.1		
WAAT	Trenton, N.J.	2500	WAMP	Allentown, Pa.	1000	WTRB	Peikha, Ind.	250	CHOV	Pembroke, Ont.	1000
WOSC	Fulton, N.Y.	10000	WSCR	Pittsburgh, Pa.	5000	WLB	Muncie, Ind.	250	CJDC	Dawson Creek, B.C.	1000
WGOL	Goldsboro, N.C.	10000	WCSR	Scranton, Pa.	1000	KROS	Clinton, Iowa	250	CHGB	St. John's, Nfld.	1000
WSYD	Mt. Airy, N.C.	5000	WRID	Rio Piedras, P.R.	5000	KLIL	Estherville, Iowa	250	CHG	St. John's, Nfld.	1000
WERE	Cleveland, Ohio	5000	WMSC	Columbia, S.C.	1000	KCKN	Kansas City, Kans.	250	CKLB	Oshawa, Ont.	10000
WVNO	Mt. Vernon, Ohio	5000	KELO	Sioux Falls, S. Dak.	5000	KCKK	Pittsburg, Kans.	250	CKEN	Kentville, N.S.	10000
KOME	Tulsa, Okla.	5000	WKLN	Clinton, Tenn.	5000	WCHM	Ashland, Ky.	250	WELB	Elba, Ala.	10000
KDOV	Medford, Ore.	5000	WMSR	Manchester, Tenn.	10000	WBS	Murray, Ky.	250	WGAO	Gadsden, Ala.	5000
KACI	The Ocales, Ore.	10000	KVME	Colo. City, Tex.	10000	WKEY	Richmond, Ky.	250	KAAB	Hot Springs, Ark.	10000
WTL	Mayaguez, P.R.	1000	KXYZ	Houston, Tex.	5000	WLEW	Bad Axe, Mich.	250	KRMD	Rockfield, Calif.	10000
WTKI	Greer, S.C.	10000	KCPX	Salt Lake City, Utah	5000	WLVG	Grand Rap. Mich.	250	KKRC	San Bernardino, Calif.	5000
KOLY	Mohrville, S. Dak.	10000	WLLY	Richmond, Va.	10000	WAGW	Gardner, Mass.	250	KSRO	Santa Rosa, Calif.	1000
WMTN	Horseshoer, Tenn.	5000	KXRO	Aberdeen, Wash.	10000	WBH	New Bedford, Mass.	250	KGHF	Pueblo, Colo.	5000
WET	Austin, Tex.	1000	KHIT	Wallia Walla, Wash.	10000	WBK	Pittsfield, Mass.	250	WNLK	Norwalk, Conn.	500
KTFY	Brownfield, Tex.	10000	WQMN	Superior, Wis.	10000	WLEW	Bad Axe, Mich.	250	WPCT	Putnam, Conn.	10000
WCL	Seattle, Wash.	5000	1330-225.4			WLVG	Grand Rap. Mich.	250	WOCF	Oade City, Fla.	10000
WOLG	Morgantown, W. Va.	10000	CBH	Halifax, N.S.	100	WCSR	Hillsdale, Mich.	100	WRPB	Waverly, N.Y.	10000
WKLC	St. Albans, W. Va.	10000	WROS	Scottsboro, Ala.	10000	WCTR	Manistee, Mich.	250	KRLC	Idaho Falls, Idaho	5000
1310-228.9			KMOP	Tucson, Ariz.	5000	WAGN	Memphis, Mich.	250	WEEK	Peoria, Ill.	1000
CKOY	Ottawa, Ont.	5000	KFAC	Los Angeles, Calif.	5000	WAGN	Memphis, Mich.	250	WJBO	Salem, Ill.	5000
CJRH	Richmond Hill, Ont.	10000	WARR	St. Pierre, Fla.	10000	WMB	Benning, Mich.	250	WIOU	Kokomo, Ind.	10000
WHEP	Foley, Ala.	10000	WYSE	Lakeland, Fla.	10000	KOLM	Detroit Lakes, Minn.	250	KRNT	Des Moines, Iowa	5000
WJAM	Marion, Ala.	5000	WBEY	Milton, Fla.	5000	WEVE	Evelev, Minn.	250	KMAN	Manhattan, Kans.	5000
KBUZ	Mesa, Ariz.	5000	WMEN	Tallahassee, Fla.	5000	KROC	Rochester, Minn.	250	WLou	Louisville, Ky.	10000
KBOK	Malvern, Ark.	10000	WMLT	Dublin, Ga.	5000	KWLM	Wilmar, Minn.	250	WSMB	New Orleans, La.	5000
KWBR	Oakland, Calif.	10000	WEA	Easton, Ill.	10000	WJMB	Brookhaven, Miss.	250	WDEA	Ellsworth, Me.	10000
KTKR	Taft, Calif.	5000	WRAM	Monmouth, Ill.	10000	WAL	Laurin, Miss.	250	WHMI	Howell, Mich.	500
KFKA	Greeley, Colo.	1000	WRRR	Rockford, Ill.	10000	KXEO	Mexico, Mo.	250	KOIO	Ortonville, Minn.	10000
WICH	Norwich, Conn.	10									

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
WORK	York, Pa.	5000	KSOP	Salt Lake City, Utah	10000	CKRN	Rouyn, Que.	250	WGTN	Georgetown, S.C.	250
WDAR	Darlington, S.C.	5000	WBTN	Bennington, Vt.	5000	CKSW	Swift Current, Sask.	250	WTHE	Spartanburg, S.C.	250
WGSW	Grovespring, S.C.	10000	WHEE	Martinsville, Va.	5000	WMSL	Decatur, Ala.	250	WJZM	Clarksville, Tenn.	250
WRKM	Carthage, Tenn.	5000	WJWS	South Hill, Va.	10000	WXAL	Demopolis, Ala.	250	WHUB	Cookeville, Tenn.	250
KTXJ	Jasper, Tex.	10000	KPOR	Quincy, Wash.	10000	WFPA	Fl. Payne, Ala.	250	WLSB	Copper Hill, Tenn.	250
KGOR	San Antonio, Tex.	5000	WMOD	Moundsville, W.Va.	10000	WLJD	Homewood, Ala.	250	WKPT	Kingsport, Tenn.	250
WBLT	Bedford, Va.	10000	WCCN	Neillsville, Wis.	5000	WJHO	Opelika, Ala.	250	WGAP	Maryville, Tenn.	250
WNVV	Norton, Va.	5000	KVVO	Cheyenne, Wyo.	1000	KSEW	Sitka, Alaska	250	WHAL	Shelbyville, Tenn.	250
WAYP	Plymouth, Va.	5000				KLFL	Clifton, Ariz.	250	KRBN	Ballinger, Tex.	250
WPDOR	Portage, Wis.	10000				KONL	Phoenix, Ariz.	250	KUNO	Spring, Tex.	1000
						KTUC	Tucson, Ariz.	250	KUNO	Corpus Christi, Tex.	250
						KVOY	Yuma, Ariz.	250	KILE	Nr. Galveston, Tex.	250
						KELD	El Dorado, Ark.	250	KGVL	Greenville, Tex.	250
						KCLA	Pine Bluff, Ark.	250	KEBE	Jacksonville, Tex.	250
						KWYN	Wynne, Ark.	250	KIUN	Pecos, Tex.	250
						KRE	Berkeley, Calif.	250	KEYE	Perryton, Tex.	250
						KSDA	Redding, Calif.	250	KVOP	Plainville, Tex.	250
						KCOY	Santa Maria, Calif.	250	KDWF	Stamford, Tex.	250
						KSPA	Santa Paula, Calif.	250	KTEM	Temple, Tex.	250
						KUKI	Ukiah, Calif.	250	KFTS	Texarkana, Tex.	250
						KONG	Visalia, Calif.	250	KVOU	Uvalde, Tex.	250
						KRLN	Canon City, Colo.	250	KIXX	Provo, Utah	250
						KFTM	Ft. Morgan, Colo.	250	WDOT	Burlington, Vt.	250
						KBZZ	La Junta, Colo.	250	WINA	Charlottesville, Va.	250
						WSTC	Stamford, Conn.	250	WLOW	Fort Worth, Va.	250
						WLIL	Williamantic, Conn.	250	WHLF	Sr. Boston, Va.	250
						WFLA	Ft. Lauderdale, Fla.	250	WINC	Winchester, Va.	250
						WIRA	Ft. Pierce, Fla.	250	KWLK	Longview, Wash.	250
						WRHC	Jacksonville, Fla.	250	KRSC	Othello, Wash.	250
						WRBY	Indio, Calif.	250	KTNT	Tacoma, Wash.	250
						WTRR	Sanford, Fla.	250	WBOY	Clarksburg, W.Va.	250
						WCOS	Alma, Ga.	250	WRON	Ronceverte, W.Va.	250
						WSGC	Elberton, Ga.	250	WKWK	Wilmington, W.Va.	250
						WNEK	Macon, Ga.	250	WATH	Williamson, W.Va.	250
						WVGA	Moultrie, Ga.	250	WRDB	Ashland, Wis.	250
						WCOH	Newnan, Ga.	250	WBIZ	Eau Claire, Wis.	250
						WGSJ	Davanna, Ga.	250	WOUZ	Green Bay, Wis.	250
						KART	Jerome, Idaho	250	WRJN	Racine, Wis.	250
						KRPL	Moscow, Idaho	250	WRDB	Reedsburg, Wis.	250
						KSPD	Sandpoint, Idaho	250	WRIJ	Wausau, Wis.	250
						WDWS	Champaign, Ill.	250	KAI	Casper, Wyo.	250
						WGIL	Galesburg, Ill.	250	KODI	Cody, Wyo.	250
						WGOE	Evansville, Ind.	250			
						WBLT	Lafayette, Ind.	100			
						KCOG	Centerville, Iowa	100			
						KVFD	Fort Dodge, Iowa	250			
						KVOE	Emoria, Kans.	250			
						KAYS	Hays, Kans.	250			
						WCYN	Cynthiana, Ky.	100			
						WIEL	Elizabethtown, Ky.	250			
						WFRP	Hammond, La.	250			
						KAOK	Lake Charles, La.	250			
						WRDO	Augusta, Maine	250			
						WIDE	Biddeford, Maine	250			
						WWIN	Baltimore, Md.	250			
						WALE	Fall River, Mass.	250			
						WHLH	Lowell, Mass.	250			
						WHMP	Northampton, Mass.	250			
						WELL	Battle Creek, Mich.	250			
						WJLB	Detroit, Mich.	250			
						WHDF	Houghton, Mich.	250			
						WMAJ	Munising, Mich.	250			
						WSAM	Saginaw, Mich.	250			
						WJSM	St. Joseph, Mich.	250			
						WTOM	Traverse City, Mich.	250			
						KMHL	Marshall, Minn.	250			
						WMIN	Mpls.-St. Paul, Minn.	250			
						WHLB	Virginia, Minn.	250			
						WBPJ	Beonville, Miss.	250			
						WAGJ	Greenville, Miss.	250			
						WFOR	Forrestersburg, Miss.	250			
						WJQS	Jackson, Miss.	250			
						WMBG	Macon, Miss.	250			
						KFRU	Columbia, Mo.	250			
						KSIM	Sikeston, Mo.	250			
						KTTS	Springfield, Mo.	250			
						KXCB	Clarendon, Mont.	250			
						KXLK	Great Falls, Mont.	250			
						KCOV	Alliance, Nebr.	250			
						KLIN	Lincoln, Nebr.	250			
						KBMI	Henderson, Nev.	250			
						KWNA	Winnemucca, Nev.	250			
						WTSJ	Hanover, N.H.	250			
						KGFL	Roswell, N. Mex.	250			
						KTRC	Santa Fe, N. Mex.	250			
						KCHS	Truth or Consequences, N. Mex.	250			
						KTNM	Tucumcari, N. Mex.	250			
						WOND	Pleasantville, N.J.	250			
						WABY	Albany, N.Y.	250			
						WBNB	Buffalo, N.Y.	250			
						WELM	Elmira, N.Y.	250			
						WCLB	Ogdensburg, N.Y.	250			
						WBMA	Beaufort, N.C.	250			
						WGBG	Greensboro, N.C.	250			
						WKDX	Hamlet, N.C.	250			
						WISC	Statesville, N.C.	250			
						WSE	Ashtand, N.C.	250			
						WHCC	Waynesville, N.C.	250			
						KEYJ	Jamestown, N.Dak.	250			
						WPAY	Portsmouth, Ohio	250			
						WPNV	Bartlesville, Okla.	250			
						KTMG	McAlester, Okla.	250			
						KNOR	Norman, Okla.	250			
						KWIN	Wintour, Okla.	250			
						KOMB	Cottage Grove, Okla.	250			
						WEST	Easton, Pa.	250			
						WJET	Erico, Pa.	250			
						WHGB	Harrisburg, Pa.	250			
						WJAC	Johnstown, Pa.	250			
						WBSI	St. Marys, Pa.	250			
						WICK	Seranton, Pa.	250			
						WRAC	Williamsport, Pa.	250			
						WFOA	San Juan, P.R.	250			
						WPCC	Clinton, S.C.	500			
						WCOS	Columbia, S.C.	250			

1380—217.3

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
CFDA	Victoriaville, Que.	1000	CKPK	Brantford, Ont.	10000	CKRN	Rouyn, Que.	250	WGTN	Georgetown, S.C.	250
CKLC	Kingston, Ont.	5000	CKLC	Kingston, Ont.	5000	CKSW	Swift Current, Sask.	250	WTHE	Spartanburg, S.C.	250
WGYV	Greenville, Ala.	10000	WGYV	Greenville, Ala.	10000	WMSL	Decatur, Ala.	250	WJZM	Clarksville, Tenn.	250
KDXE	N. Little Rock, Ark.	10000	KDXE	N. Little Rock, Ark.	10000	WXAL	Demopolis, Ala.	250	WHUB	Cookeville, Tenn.	250
KBVM	Leicester, Calif.	10000	KBVM	Leicester, Calif.	10000	WFPA	Fl. Payne, Ala.	250	WLSB	Copper Hill, Tenn.	250
KGMS	Sacramento, Calif.	1000	KGMS	Sacramento, Calif.	1000	WLJD	Homewood, Ala.	250	WKPT	Kingsport, Tenn.	250
KFLJ	Walsenburg, Colo.	10000	KFLJ	Walsenburg, Colo.	10000	WJHO	Opelika, Ala.	250	WGAP	Maryville, Tenn.	250
WAMS	Wilmington, Del.	1000	WAMS	Wilmington, Del.	1000	KSEW	Sitka, Alaska	250	WHAL	Shelbyville, Tenn.	250
WLIZ	Lake Worth, Fla.	5000	WLIZ	Lake Worth, Fla.	5000	KLFL	Clifton, Ariz.	250	KRBN	Ballinger, Tex.	250
WQXQ	Ormond Beh., Fla.	10000	WQXQ	Ormond Beh., Fla.	10000	KONL	Phoenix, Ariz.	250	KUNO	Spring, Tex.	1000
WLCY	St. Petersburg, Fla.	5000	WLCY	St. Petersburg, Fla.	5000	KTUC	Tucson, Ariz.	250	KUNO	Corpus Christi, Tex.	250
WAOK	Atlanta, Ga.	5000	WAOK	Atlanta, Ga.	5000	KVOY	Yuma, Ariz.	250	KILE	Nr. Galveston, Tex.	250
WRWH	Cleveland, Ga.	5000	WRWH	Cleveland, Ga.	5000	KELD	El Dorado, Ark.	250	KGVL	Greenville, Tex.	250
RFOT	Honolulu, Hawaii	5000	RFOT	Honolulu, Hawaii	5000	KCLA	Pine Bluff, Ark.	250	KEBE	Jacksonville, Tex.	250
WRKH	San Francisco, Ind.	5000	WRKH	San Francisco, Ind.	5000	KWYN	Wynne, Ark.	250	KIUN	Pecos, Tex.	250
KCMJ	Carroll, Iowa	1000	KCMJ	Carroll, Iowa	1000	KRE	Berkeley, Calif.	250	KEYE	Perryton, Tex.	250
WMTA	Central City, Ky.	5000	WMTA	Central City, Ky.	5000	KSDA	Redding, Calif.	250	KVOP	Plainville, Tex.	250
WWKY	Winchester, Ky.	10000	WWKY								

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
KFHA	Lakewood, Wash.	1000d	WGAL	Lanester, Pa.	250	1560—192.3			WPGC	Bradbury Hgts., Md.	1000d
WISM	Madison, Wis.	1000	WBCE	Lancaster, Pa.	250	CFRS	Simcoe, Ont.	250d	WQWE	Allegan, Mich.	250d
1490—201.2											
CFRC	Kingston, Ont.	100	WMRF	Leiston, Pa.	250	KPMC	Bakersfield, Calif.	1000d	KDOM	Windom, Minn.	250d
CKCR	Kitchener, Ont.	250	WMGW	Meadville, Pa.	250	WBYS	Canton, Ill.	250d	WAMY	Amory, Miss.	5000d
CKBM	Montauq, Que.	250	WNBT	Wellsboro, Pa.	250	WDXR	Council Bluffs, Iowa	500d	WGLC	Centerville, Miss.	250d
WANA	Annisson, Ala.	250	WDDD	Fajardo, P.R.	250	WQXR	Paducah, Ky.	1000	WESY	Peland, Miss.	1000
WAJF	Decatur, Ala.	250	WGGC	Chester, S.C.	250	WQXN	New York, N.Y.	5000d	WFMP	Pascagoula, Miss.	1000d
WLRL	Lalet, Ala.	250	WMRB	Greenville, S.C.	250	WTNS	Coshocton, Ohio	1000d	KBIA	Columbia, Mo.	250d
WHBB	Selma, Ala.	250	WORN	Mitchell, S.Dak.	250	WTDJ	Toledo, Ohio	1000d	NLM	Maryville, Mo.	250d
KYCA	Prescott, Ariz.	250	WOPF	Bluff, Tenn.	250	WKCO	Chickasha, Okla.	1000	WCRV	Washington, N.J.	500d
KAIR	Tucson, Ariz.	250	WOXB	Chattanooga, Tenn.	250	WENA	Bayamon, P.R.	250	KHAM	Albuquerque, N.Mex.	500d
KXAR	Hope, Ark.	250	WJXM	Lewisburg, Tenn.	250	KHBR	Hillsboro, Tex.	250d	WFAC	Pathmore, N.Y.	500d
KTLO	Mtn. Home, Ark.	250	WDXL	Austin, Tenn.	250				KZKY	Akron, N.C.	500d
KDRS	Paragould, Ark.	250	KNOW	Lexington, Tex.	250				WTYN	Tryon, N.C.	250d
KOTN	Pine Bluff, Ark.	250	KIBL	Beeville, Tex.	250				WKVO	Columbus, Ohio	1000d
KXRJ	Russellville, Ark.	250	KBST	Big Spring, Tex.	250				KLTR	Clackwell, Okla.	250d
KMAP	Bakersfield, Calif.	250	KNEL	Burger, Tex.	250				WCQY	Columbus, Pa.	500d
KPAS	Banning, Calif.	250	KSAM	Huntsville, Tex.	250				WANB	Waynesburg, Pa.	250d
GLA	Burbank, Calif.	250	KVOZ	Laredo, Tex.	250				WBPD	Orangeburg, S.C.	1000d
KICO	Calexico, Calif.	250	KUCO	Littlefield, Tex.	250				WYCL	York, S.C.	250d
KOWL	Lake Tahoe, Calif.	250	KPLT	Paris, Tex.	250				KGAF	Gainesville, Tex.	250d
KAFP	Petaluma, Calif.	250	KGKB	Tyler, Tex.	250				KIRT	Mission, Tex.	1000d
KBFL	Red Bluff, Calif.	250	KVVC	Vernon, Tex.	250				KTLU	Rusk, Tex.	250d
KDB	Santa Barbara, Calif.	250	KVOG	Vadon, Utah	250				KWED	Seguin, Tex.	1000d
KBYC	Yreka, Calif.	250	KWKE	Wheat, Va.	250				KVFA	Shameck, Tex.	250d
KSQL	Boulder, Colo.	250	WVCA	Culpeper, Va.	250				WILA	Danville, Va.	1000d
KCMS	Manitou Springs, Colo.	250	WVEC	Hampton, Va.	250				WPUV	Pulaski, Va.	5000d
KOLO	Sterling, Colo.	250	WAYB	Waynesboro, Va.	250				WTTN	Watertown, Wis.	250d
WNLC	New London, Conn.	250	KBRO	Bremerton, Wash.	250						
WTOR	Torrington, Conn.	250	KLOG	Kelso, Wash.	250						
WTRL	Bradenton, Fla.	250	KENE	Toppishish, Wash.	250						
WJBS	DeLand, Fla.	250	KTEL	Walla, Wash.	250						
WMET	Miami Beach, Fla.	250	WMSM	Charleston, W.Va.	250						
WSRA	Milton, Fla.	250	WTCS	Fairmont, W.Va.	250						
WCRG	Stark, Fla.	250	WLOH	Princeton, W.Va.	250						
WTTB	Ver Beach, Fla.	250	WGEZ	Beloit, Wis.	250						
WSIR	Winter Haven, Fla.	250	WLX	LaCrosse, Wis.	250						
WMOG	Brunswick, Ga.	250	WIGM	Medford, Wis.	250						
WMJM	Cordele, Ga.	250	WOSH	Oshkosh, Wis.	250						
WMRE	Norroe, Ga.	250	KIML	Glenn, Wyo.	250						
WSFB	Quitman, Ga.	250	KRTR	Thermopolis, Wyo.	250						
WSNT	Sandersville, Ga.	250	KGOS	Torrington, Wyo.	250						
WSYL	Sylvania, Ga.	250									
KTOK	Lihue, Hawaii	250									
KCID	Caldwell, Idaho	250									
WKRO	Cairo, Ill.	250									
WDAN	Danville, Ill.	250									
WAWY	East St. Louis, Ill.	250									
WOPA	Oak Park, Ill.	250									
WKVB	Richmond, Ind.	250									
WNDU	South Bend, Ind.	250									
KBUR	Burlington, Iowa	250									
WBQJ	Dubuque, Iowa	250									
KRIB	Mason City, Iowa	250									
KTOP	Topeka, Kans.	250									
WKFY	Frankfort, Ky.	250									
WKAY	Glasgow, Ky.	250									
WOMI	Owensboro, Ky.	250									
WSP	Paintsville, Ky.	250									
WKIC	Bogalusa, La.	250									
KEUN	Eunice, La.	250									
KCJL	Houma, La.	250									
KBUS	Port Allen, La.	250									
WPOR	Port Orleans, La.	250									
WTVL	Waterville, Maine	250									
WARK	Hagerstown, Md.	250									
WHAV	Haverhill, Mass.	250									
WMRC	Milford, Mass.	250									
WTXL	W. Springfield, Mass.	250									
WABJ	Adrian, Mich.	250									
WCBS	Flint, Mich.	250									
WMDN	Midland, Mich.	250									
KXRA	Alexandria, Minn.	250									
KOZY	Grand Rapids, Minn.	250									
KLGR	Redwd. Falls, Minn.	100									
WLDX	Bloomington, Miss.	250									
WCLE	Cleveland, Miss.	250									
WFOJ	Phlatort, Miss.	250									
WTUP	Tupelo, Miss.	250									
WVIM	Vicksburg, Miss.	250									
KDMO	Carthage, Mo.	250									
KTRR	Rolla, Mo.	250									
KDRD	Sedalia, Mo.	250									
KBOW	Butte, Mont.	250									
WBOB	Omaha, Neb.	250									
WLDB	Atlanta, N.C.	250									
KRSN	Los Alamos, N.Mex.	250									
KRTN	Raton, N.Mex.	250									
WCSS	Amsterdam, N.Y.	250									
WBTA	Batavia, N.Y.	250									
WKNY	Kingston, N.Y.	250									
WIOY	Malone, N.Y.	250									
WDLC	Port Jervis, N.Y.	250									
WOLF	Syracuse, N.Y.	250									
WSSB	Durham, N.C.	250									
WFLB	Fayetteville, N.C.	250									
WLOE	Leaksville, N.C.	250									
WRNB	New Bern, N.C.	250									
WRMT	Rocky Mount, N.C.	250									
WSPF	Salisbury, N.C.	250									
KNDG	Hettinger, N.Dak.	250									
KOVC	Valley City, N.Dak.	250									
WBEX	Chillicothe, Ohio	250									
WJMO	Cleveland Hgts., Ohio	250									
WOHI	E. Liverpool, Ohio	250									
WMOA	Marietta, Ohio	250									
WBRN	Marion, Ohio	250									
KBRW	Guthrie, Okla.	100									
KBIX	Muskogee, Okla.	250									
KBKR	Baker, Okla.	250									
KRNR	Roseburg, Okla.	250									
KBZY	Salmon, Okla.	250									
WESB	Bradford, Pa.	250									
WAZL	Hazleton, Pa.	250									
WARD	Johnstown, Pa.	250									
WFCR	Bradbury Hgts., Md.	1000d	WJBE	Beaufort, N.C.	1000d	1580—189.2			WJBC	Chicotimi, Que.	1000d
WQWE	Allegan, Mich.	250d	WJBT	Beaufort, N.C.	1000d	CBJ	Chicotimi, Que.	1000d	WJHB	Tallahadega, Ala.	1000d
KDOM	Windom, Minn.	250d	WJCH	Chickasha, Okla.	1000d	KPCA	Marked Tree, Ark.	250d	KFPD	Van Buren, Ark.	500d
WAMY	Amory, Miss.	5000d	WJCL	Columbia, S.C.	1000d	KWIP	Macedonia, Cal.	5000d	KWIP	Macedonia, Cal.	5000d
WGLC	Centerville, Miss.	250d	WJCM	Chattanooga, Tenn.	1000d	KPIK	Colorado Spgs., Colo.	5000d	WVIL	Ft. Lauderdale, Fla.	1000d
WESY	Peland, Miss.	1000	WJCN	Cincinnati, Ohio	1000d	WGRC	Green Cove Springs, Fla.	500d	WVIO	Mount Dora, Fla.	1000d
WFMP	Pascagoula, Miss.	1000d	WJCO	Columbus, Ohio	1000d	WVIO	Mount Dora, Fla.	1000d	WVFB	Tallahadega, Fla.	1000d
KBIA	Columbia, Mo.	250d	WJCT	Charlotte, N.C.	1000d	WVLA	Columbus, Ga.	1000d	WVLA	Columbus, Ga.	1000d
NLM	Maryville, Mo.	250d	WJDA	Dallas, Tex.	1000d	WVON	Duquoin, Ill.	1000d	WVON	Duquoin, Ill.	1000d
WCRV	Washington, N.J.	500d	WJDF	Dayton, Ohio	1000d	WVPT	Pittsfield, Ill.	1000d	WVPT	Pittsfield, Ill.	1000d
KHAM	Albuquerque, N.Mex.	500d	WJDR	Dayton, Ohio	1000d	WKID	Urbana, Ill.	1000d	WCNB	Connersville, Ind.	250d
WFAC	Pathmore, N.Y.	500d	WJDU	Dubuque, Iowa	1000d	WVSA	South Bend, Ind.	1000d	WVSA	South Bend, Ind.	1000d
KZKY	Akron, N.C.	500d	WJEA	Elgin, N.C.	250d	WVAM	Washington, Ind.	250d	KCHA	Charles City, Iowa	500d
WTYN	Tryon, N.C.	250d	WJEM	Elgin, N.C.	250d	WVFA	Macon, Ga.	1000d	WVFA	Macon, Ga.	1000d
WKVO	Columbus, Ohio	1000d	WJEM	Elgin, N.C.	250d	WVFN	Denison, Iowa	500d	WVFN	Denison, Iowa	500d
KLTR	Clackwell, Okla.	250d	WJEM	Elgin, N.C.	250d	WVGR	Georgetown, Ky.				

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Brampton, Ont.	CHIC 1090	Cartersville, Ga.	WBHF 1450 M	Clanton, Ala.	WSAI 1360	Cornelia, Ga.	WCRR 1390
Brandon, Man.	CKX 1150	Carthage, Ill.	WCAZ 990	Claremore, Okla.	WKLF 980	Cornor Brook, Nfld.	WCBN 1450
Branson, Mo.	BKHM 1220	Carthage, Mo.	KDMD 1400	Claremont, N.H.	WFSV 1290	Corning, Ark.	WCOB 1260
Brawley, Cal.	WTSA 1450	Carthage, Tenn.	WRKM 1350	Clarksburg, W.Va.	WBGO 1340 M	Corning, N.Y.	WCBS 1350
Breckenridge, Minn.	KROP 1300 A	Carthage, Tex.	KGAS 1590		WHAR 940 M		WCLL 1450 A
Brosenkrige, Tex.	KBTB 1430	Caruthersville, Mo.	KCRB 1370		WPDZ 750	Cornwall, Ont.	CJSS 1220
Bremen, Ga.	WCCD 1440	Casper, Wyo.	KPIN 1260	Clarksdale, Miss.	WROX 1450 M	Corona, Calif.	KBUC 1370
Bremerton, Wash.	KBRO 1490		KATI 1400		WKDL 1600	Corry, Pa.	WCSS 1370
Brenham, Tex.	KWHI 1280		KVOC 1230 A-M	Clarksville, Ark.	KLYR 1360	Corsicana, Tex.	KAND 1340
Brevard, N.C.	WPNF 1240 M-N	Cayce, S.C.	WCAY 620	Clarksville, Tenn.	WJZM 540 M	Cortez, Colo.	KVFC 740
Brewton, Ala.	WEBJ 1240 M	Cedar City, Utah	KSUB 590	Clarksville, Tenn.	WJZN 540	Cortland, N.Y.	WKRT 520
Bridgesport, Conn.	WICG 600 M	Cedar Rapids, Iowa	KCRG 1600 M	Claxton, Ga.	KCR 1350	Corvallis, Ore.	KQAC 950
	WNSJ 1240		KPIE 1450	Clayton, Mo.	WCLA 1470		KFLY 1240
Bridgeton, N.J.	WNSJ 1240		WMT 600 C		KKLW 1320		KLOO 1340
Bridgewater, N.S.	CKBW 1000	Cedartown, Ga.	WGAA 1340		KFOU 850	Coshocton, Ohio	WTNS 1560
Brighton, N.Y.	KBUM 800	Center, Tex.	KDET 930	Cleveland, Ohio	KLMX 1450	Cottage Grove, Ore.	KOMB 1400
Brighton, Colo.	KHIL 800	Centerville, Iowa	KCOG 1400		WCPA 900		KFRM 600
Bristol, Conn.	WBIS 1440	Centerville, Tenn.	WHLP 1570	Cleveland, Tenn.	WATN 1340	Council Bluffs, Iowa	KISL 1560 M-A
Bristol, Tenn.	WOPY 1490 N	Centerville, Utah	KBBC 1600		WCAR 1220		CFWP 1440
Bristol, Va.	WCYB 690 A	Central City, Ky.	WNLS 1600		WHK 420 C	Courtenay, B.C.	CGF 1450
	WNSJ 1240		WMT 1380		WABQ 1540	Covington, Ga.	WGFS 1430
Brockton, Mass.	WBET 1460	Centralia, Ill.	WCNT 1210		WJW 850 N	Covington, Ky.	WZIP 1050 M
Brockville, Ont.	CFJR 1450	Centralia & Chehalis, Wash.	KELA 1470		WCL 1570	Covington, Tenn.	WKBL 720
Broken Bow, Nebr.	KNKI 1280	Centerville, Miss.	WGLC 1580		WJW 850 N	Covington, Va.	WKBY 1340 A
Brookfield, Mo.	KGHM 1470	Chadron, Nebr.	KCSR 1450		WJW 850 N	Cowan, Tenn.	WKAY 540
Brookhaven, Miss.	WCHJ 1470	Chambersburg, Pa.	WBCB 910		WJW 850 N	Craig, Colo.	KRAI 550
	KFY 1340 M		WWS 1450		WJW 850 N	Crane, Tex.	KCRN 1380
Brookings, Ore.	KBRK 1430	Champaign, Ill.	WDWS 1400		WJW 850 N	Creighton, Iowa	KPSB 1520
Brookings, S.Dak.	KBKR 1430	Chanute, Kans.	KCRB 1460		WJW 850 N	Crestview, Fla.	WCNU 1010
Brookline, Mass.	WBOS 1600	Chapel Hill, N.C.	WCHL 1360		WJW 850 N	Crews, Va.	WVBY 800
Brooklyn, N.Y.	WPW 1330	Charleroi, Pa.	WESA 940		WJW 850 N	Crockett, Tex.	KIVY 1290
Brooksville, Fla.	WJIB 1450	Charles City, Iowa	KCHA 1580		WJW 850 N	Crookston, Minn.	KROX 1260
Brownfield, Tex.	KTFY 1300	Charleston, Ill.	WEIC 1270		WJW 850 N	Crossett, Ark.	KAGH 800
Brownsville, Tex.	KBOR 1600 A	Charleston, Mo.	KCHR 1600		WJW 850 N	Crossville, Tenn.	WAEW 1330
Brownwood, Tex.	KBWD 1380	Charleston, S.C.	WCSC 1390		WJW 850 N	Crowley, La.	KSFJ 450 M
	WJIB 1450		WKE 1340 A-M		WJW 850 N	Cuere, Tex.	KCFH 1600
	WJIB 1450		WPAL 730		WJW 850 N	Culman, Ala.	WFLC 1460
	WJIB 1450		WQSN 1450		WJW 850 N		WKLU 1340
	WJIB 1450		WTMA 1250 N		WJW 850 N		WCVA 1490 M
	WJIB 1450		WCWA 1400		WJW 850 N		WCPM 1280
	WJIB 1450		WCS 800		WJW 850 N		WCUM 1230 C
	WJIB 1450		WMS 1490 A		WJW 850 N		WTBO 1450
	WJIB 1450		WKAZ 950 N		WJW 850 N		KUSH 1600
	WJIB 1450		WTIP 1240 M		WJW 850 N		WGTO 540
	WJIB 1450		WCER 1390		WJW 850 N		WCYN 1440 A
	WJIB 1450		WBT 1110		WJW 850 N		WDFC 1350
	WJIB 1450		WAYS 610 A		WJW 850 N		KXIT 1410
	WJIB 1450		WY 1600		WJW 850 N		KPLK 1460
	WJIB 1450		WTKC 1310		WJW 850 N		KRLD 1080 C
	WJIB 1450		WIST 930 M		WJW 850 N		KIXL 1040
	WJIB 1450		WSOC 1240 N		WJW 850 N		KSKY 660
	WJIB 1450		WWOK 1480		WJW 850 N		KLIF 1190
	WJIB 1450				WJW 850 N		WFAA 570 A
	WJIB 1450				WJW 850 N		WFAA 820 N
	WJIB 1450				WJW 850 N		KBOJ 1480
	WJIB 1450				WJW 850 N		WRR 1310 M
	WJIB 1450				WJW 850 N		KACI 1300
	WJIB 1450				WJW 850 N		KY 1440 A
	WJIB 1450				WJW 850 N		WBLJ 1230 M
	WJIB 1450				WJW 850 N		WRCD 1430
	WJIB 1450				WJW 850 N		WLAD 800
	WJIB 1450				WJW 850 N		WDAN 1490 C
	WJIB 1450				WJW 850 N		WITY 980
	WJIB 1450				WJW 850 N		WHIR 1230 M
	WJIB 1450				WJW 850 N		WDVA 1250 M
	WJIB 1450				WJW 850 N		WILA 1580
	WJIB 1450				WJW 850 N		WDAR 1350
	WJIB 1450				WJW 850 N		CKDM 1050
	WJIB 1450				WJW 850 N		WOC 420 N
	WJIB 1450				WJW 850 N		KFMA 1580
	WJIB 1450				WJW 850 N		KSTY 1170 M
	WJIB 1450				WJW 850 N		WDWD 990
	WJIB 1450				WJW 850 N		CFYT 1230
	WJIB 1450				WJW 850 N		CJDC 1350
	WJIB 1450				WJW 850 N		WHIO 1290 C
	WJIB 1450				WJW 850 N		WING 1410
	WJIB 1450				WJW 850 N		WONE 980
	WJIB 1450				WJW 850 N		WVAF 1240
	WJIB 1450				WJW 850 N		WDNT 1280
	WJIB 1450				WJW 850 N		WNBD 1150 M-A
	WJIB 1450				WJW 850 N		WMFJ 1450
	WJIB 1450				WJW 850 N		WRD 1340
	WJIB 1450				WJW 850 N		KDSJ 980
	WJIB 1450				WJW 850 N		WKHM 1310
	WJIB 1450				WJW 850 N		WHOS 800
	WJIB 1450				WJW 850 N		WAJF 1490
	WJIB 1450				WJW 850 N		WMSL 1400 M
	WJIB 1450				WJW 850 N		WGUN 1010
	WJIB 1450				WJW 850 N		WZD 1050
	WJIB 1450				WJW 850 N		WV 1340 C
	WJIB 1450				WJW 850 N		KDEC 1240
	WJIB 1450				WJW 850 N		KLWC 1240
	WJIB 1450				WJW 850 N		WONW 1280
	WJIB 1450				WJW 850 N		WV 1340 C
	WJIB 1450				WJW 850 N		WSP 1280
	WJIB 1450				WJW 850 N		WZP 1460
	WJIB 1450				WJW 850 N		WLS 1360
	WJIB 1450				WJW 850 N		WBS 980
	WJIB 1450				WJW 850 N		WOO 1310
	WJIB 1450				WJW 850 N		KXJ 1010
	WJIB 1450				WJW 850 N		WDF 1420
	WJIB 1450				WJW 850 N		

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Del Rio, Tex.	KDLK 1230	Elba, Ala.	WELB 1350	Fayetteville, Tenn.	WEKR 1240 M	Gaffney, S.C.	WFGN 1570
Delta, Colo.	KOTA 1400	Elberton, Ga.	WSSC 1400	Fergus Falls, Minn.	KOTE 1250 M	Gainesville, Fla.	WVH 980
Deming, N. Mex.	KOTS 1230	El Cajon, Calif.	KDEO 910 A	Fernandina Beach, Fla.	WPAP 1570	Gainesville, Ga.	WGGC 980
Demopolis, Ala.	WXAL 1220	El Campo, Tex.	KULP 1390 M	Ferriday, La.	KFNW 1600	Gainesville, Tex.	WGRF 850 M
Denham Sprgs., La.	WLBI 1200	El Centro, Calif.	KXKO 1230 M	Festus, Mo.	KFEN 1010	Gainesville, Tex.	WWSU 1500
Denison, Iowa	KDSN 1580	El Dorado, Ark.	KDMS 1290	Findlay, Ohio	WFIN 1390	Gallatin, Tenn.	WHIN 1010
Denison, Tex.	KDSX 950	El Dorado, Ark.	KELD 1400 A	Fisher, W.Va.	WELD 690 A	Gallipolis, Ohio	WJEH 990
Denton, Tex.	KDEN 1440	Elgin, Ill.	WRMN 1410	Fitchburg, Mass.	WEIM 1280 M	Gallup, N. Mex.	KGAK 1330 A
Denver, Colo.	KFML 1390	Elizabeth City, N.C.	WCNC 1240	Fitzgerald, Ga.	WBHB 1240 M	Galveston, Tex.	CKGR 1110
	KHOW 630 A	Elizabethton, Tenn.	WBAI 560	Flagstaff, Ariz.	KCLS 600 N	Gander, Nfld.	CBG 1450
	KLIN 950 M	Elizabethtown, N.Y.	WJEL 1400	Flomaton, Ala.	KEOS 1290	Garden City, Kans.	KNCO 1050
	KLIR 990	Elizabethtown, Pa.	WBLA 1450 M	Florence, Ala.	KFMO 1240 M	Gardner, Mass.	KIUL 1240 M
	KLZ 560 C	Elk City, Okla.	KBKX 1240 A	Flint, Mich.	CFAR 590	Gary, Ind.	WGAW 1340
	KICN 710	Elkhart, Ind.	WTRC 1340 N	Florencia, Fla.	WFDF 910 N	Gastonia, N.C.	WGNC 1450 A
	KOA 850 N	Elkins, N.C.	WCMR 1270	Florence, S.C.	WJMI 1440 M	Gate City, Va.	WGAT 1050
	KPof 910	Elkins, W.Va.	WDNE 1240	Floydada, Tex.	WOLS 1320	Gaylord, Mich.	WATC 900
	KFSK 1220	Elko, Nev.	KELK 1240 M	Foley, Ala.	KFLD 900	Geneva, Ala.	WGEA 1150
	KTLN 1280	Ellensburg, Wash.	KXLE 1240	Fond du Lac, Wis.	WFEP 1470	Geneva, N.Y.	WGVA 1240 A
	KDN 1390	Ellsworth, Me.	WDEA 1350	Fordeys, Ark.	KFIZ 1450 M	Georgetown, Del.	WJWL 900
	KOLA 1010	Elmira, N.Y.	WELM 1400 A-C	Forest, Miss.	KBJT 1570	Georgetown, S.C.	WGSR 1240
	KCBC 1390 A	Elmira Heights-Horseheads, N.Y.	WENY 1280 N	Forest City, N.C.	WBBQ 780	Georgetown, S.C.	WGTE 1400 M
	KIOA 940			Forest Grove, Ore.	WAGO 1320	Gillette, Wyo.	KIMI 1490
	KRNT 1350 C			Forest City, Ark.	KGGS 1570	Gilroy, Calif.	KPER 1290
	KSO 1460			Forest City, Ark.	KWTF 950	Gladewater, Tex.	KSJ 1430
	KWY 1150 M			Ft. Bragg, Calif.	KDAC 1230	Glasgow, Ky.	WKAY 1490
	WCAR 1130			Ft. Collins, Colo.	KCOL 1410	Glasgow, Mont.	WGLM 1240
	WJBL 1400			Ft. Dodge, Iowa	KVFD 1400 M	Glendale, Ariz.	KRUX 1360
	WJR 760			Ft. Frances, Ont.	KWMT 540 A	Glendale, Calif.	KIEV 870
	WWJ 950 N			Ft. Knox, Ky.	CFOB 800	Glendive, Mont.	KXGN 1400
	WXYZ 1270 A			Ft. Lauderdale, Fla.	WFLA 1470	Glen Falls, N.Y.	WWSU 1450 A
				Ft. Lauderdale, Fla.	WVIL 1580	Glenwood Sprgs., Colo.	WGLN 980 M
				Ft. Lupton, Colo.	KHIL 800	Globe, Ariz.	KGLN 1240 A
				Ft. Madison, Iowa	KXGI 1360	Gloversville, Va.	WDDY 1420
				Ft. Morgan, Colo.	KFTM 1400	Glovesville-Johnston, N.Y.	WENT 1340 C
				Ft. Myers, Fla.	WYRK 1410	Golden, Colo.	KXXI 1250
				Ft. Payne, Ala.	WZOB 1250	Golden Meadow, La.	KLFT 1600
				Ft. Pierce, Fla.	WARN 1330	Golden Valley, Minn.	KEVE 1440 M
				Ft. Scott, Idaho	KMDD 1600	Goldsboro, N.C.	WFMC 1330
				Ft. Smith, Ark.	KFPW 1230 C	Gonzales, Tex.	KCTI 1450
				Ft. Stockton, Tex.	KFSA 950 A	Goodland, Kans.	KBLR 1340 M
				Ft. Valley, Ga.	KWTF 1470	Goodland, Kans.	CFGB 750 M
				Ft. Walton Beach, Fla.	KWHL 1320	Goshen, Ind.	WVW 1460
					WFBS 950	Grafton, N.D.	KGPC 1340
					WFTW 1260	Grafton, W.Va.	WVWV 1260
					WVW 1250	Graham, Tex.	KSWA 1330
					WVW 1250	Granby, Que.	CHEF 1450
					WVW 1250	Grand Falls, Nfld.	CBT 990
					WVW 1250	Grand Falls, N.D.	KFRD 1360
					WVW 1250	Grand Coulee, Wash.	KFJM 1470
					WVW 1250	Grand Coulee, Wash.	KILD 1440 C
					WVW 1250	Grand Haven, Mich.	KGHN 1310 M
					WVW 1250	Grand Island, Nebr.	KMMJ 750 A
					WVW 1250	Grand Junction, Colo.	KRGI 1430
					WVW 1250	Grand Rapids, Mich.	KREX 920 M
					WVW 1250	Grand Rapids, Mich.	KXEO 1230
					WVW 1250	Grand Rapids, Mich.	KSTR 1230
					WVW 1250	Grand Rapids, Mich.	KXSP 1650
					WVW 1250	Grand Rapids, Mich.	KXSN 750
					WVW 1250	Grand Rapids, Mich.	WJEF 1230 C
					WVW 1250	Grand Rapids, Mich.	WFUR 1570
					WVW 1250	Grand Rapids, Mich.	WGRD 1410
					WVW 1250	Grand Rapids, Mich.	WLAV 1340 A
					WVW 1250	Grand Rapids, Mich.	WMAX 1480 M
					WVW 1250	Grand Rapids, Mich.	WOOD 1300 N
					WVW 1250	Grand Rapids, Minn.	KOZY 1490 M
					WVW 1250	Grangeville, Idaho	KORT 1230
					WVW 1250	Grants, N. Mex.	KMIN 980 M
					WVW 1250	Grants Pass, Ore.	KAJO 1270
					WVW 1250	Gravelbourg, Sask.	CFGR 1230
					WVW 1250	Grayson, Ky.	CFRG 710
					WVW 1250	Gt. Barrington, Mass.	WGOH 1370
					WVW 1250	Gt. Bend, Kans.	WSSB 860 N
					WVW 1250	Gt. Falls, Mont.	KFBB 1310 C
					WVW 1250		KUDI 1450
					WVW 1250		KMON 560 M
					WVW 1250		KXLK 1400 N
					WVW 1250		KFKA 1310
					WVW 1250		KYDU 1450
					WVW 1250		WJPG 1360 C
					WVW 1250		WDUZ 1440 A
					WVW 1250		WGR 1580
					WVW 1250		WGRV 1340
					WVW 1250		WHAI 1240 M
					WVW 1250		WHAI 1240 C
					WVW 1250		WCOG 1320
					WVW 1250		WGBG 1400 A
					WVW 1250		WPET 950
					WVW 1250		WHJB 620
					WVW 1250		WGYV 1890

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	
Greenville, Miss.	WJPR 1330 WDDT 900 WGVN 1260	Hillsboro, Ohio Hillsboro, Ore. Hillsboro, Tex.	WSRW 1590 KUIJ 1360 KHBR 1560	Jacksonville, Fla.	WTJS 1390 A WJAX 930 WJCB 800	Knoxville, Tenn.	KLAD 960 WV 1240 A WVW 850	
Greenville, N.C.	WGTC 1590 M	Hillsdale, Mich.	WCSB 1340		WZOK 1320 A WIVY 1050 WMBR 1460 C		WATE 620 N WGN 1340 M WKKV 900 WNOX 890 C	
Greenville, S.C.	WECB 660 WFG 1330 WMBR 1490 A-M	Hilo, Hawaii	KIPA 1110 KIMO 850 M		WBOB 1360 WPDQ 800 WQIK 1280	Kckomo, Ind.	WIOU 1350 C Kosciusko, Miss. Lacrosse, Wis.	WKOZ 1350 A KPL 1240 A WKBH 1410 N WLXC 1490
Greenville, Tex.	WMMU 1260 WQOK 1440 C KGYL 1400	Hobart, Okla. Hobbs, N. Mex.	KTJS 1420 KWEW 1480 M	Jacksonville III. Jacksonville, N.C.	WRHC 600 C WJNC 1240 M WLAS 910	Lafayette, Ind.	WLFY 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Greenwood, Miss.	WABG 960 A WGRM 1240 N WRS 1450 N	Holbrook, Ariz. Holdrege, Nebr. Holland, Mich.	KHOB 1280 KOUJ 1270 KURV 380 WHTC 1450 WJBL 1260	Jacksonville, Tex. Jacksonville Beh., Fla.	WJWB 1320 WREB 930 KVHL 1320 WSDS 1430 WANO 800 WENN 1320 M	Lafayette, La.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Greer, S.C.	WEAB 800 WCKI 1300 A	Hollywood, Fla. Holyoke, Mass. Homer, La.	WJMA 1320 WREB 930 KVHL 1320 WSDS 1430 WANO 800 WENN 1320 M	Jamestown, N. Dak.	WZRO 1010 KEJY 1400 M	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Grenada, Miss.	WNAG 1400 M	Homestead, Fla. Homestead, Pa. Homewood, Ala.	WJMA 1320 WREB 930 KVHL 1320 WSDS 1430 WANO 800 WENN 1320 M	Jamestown, N.Y.	WJTN 1240 A WJOC 1340 M	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Gresham, Ore.	WGR 1230	Honolulu, Hawaii	WJLD 1400 KGMB 590 C KPOI 1380 KIKI 830 KGO 760 N	Jamestown, Tenn. Janesville, Wis. Jasper, Ala.	WCLC 1260 M WCLO 1230 M WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Gretna, Va.	WMNA 730	Hood River, Ore.	KHIR 340 A	Jasper, Ind. Jasper, Tex. Jefferson City, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C KLIK 950 KWOS 1240 M	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Griffin, Ga.	WKEU 1320 M	Hopewell, Va.	KXAR 1490 WHAP 1340 WHOP 1230 C	Jessup, Ga. Johnson City, Tenn.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C KLIK 950 KWOS 1240 M	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Grinnell, Iowa	WGRN 1410	Hopkinsville, Ky.	WHOP 1230 C WKOA 480 WHTD 800	Johnson City, Tenn.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Groton, Conn.	WSUB 980	Hornell, N.Y.	WJLD 1400 KGMB 590 C KPOI 1380 KIKI 830 KGO 760 N	Johnston, Pa.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Grove City, Pa.	WSAJ 1340	Hot Springs, Ark.	WJLD 1400 KGMB 590 C KPOI 1380 KIKI 830 KGO 760 N	Joliet, Ill. Jonesboro, Ark.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Grundy, Va.	WNRG 1250	Houghton, Mich.	WHDF 1400	Jonesboro, Ark.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Guayama, P.R.	WXRF 1590	Houghton Lake, Mich.	WHDF 1400	Jonesboro, La.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Gulfport, Miss.	WGR 1230	Houlton, Maine	WHGR 1290	Jonesboro, Tenn.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Guntersville, Ala.	WGSV 1270	Houma, La.	WHGR 1290 WHUJ 1340 CKIL 940 N	Jonquiere, Que.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Guthrie, Okla.	WKRWR 1490	Houston, Miss.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Guymon, Okla.	WGYN 1220	Houston, Tex.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hagerstown, Md.	WARK 490 C	Huntington, Pa.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Haleyville, Ala.	WJEJ 1240 A-M	Huntington, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Halifax, N.S.	WJBB 1230 M CH 1330 CHNS 960 CJCH 920	Huntington, N.Y.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hamilton, Ala.	WERH 970	Huntington, W.Va.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hamilton, Ohio	WMOH 1450	Huntsville, Ala.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hamilton, Ont.	CHML 900	Huntsville, Ont.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hamilton, Tex.	CKOC 1150	Huntsville, Tex.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hamlet, N.C.	WKDX 900	Huron, S. Dak.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hammond, Ind.	WJOB 1230	Hutchinson, Kan.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hammond, La.	WFRP 1400	Hutchinson, Minn.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hampton, S.C.	WBHC 1270	Idabel, Okla.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hampton, Va.	WVEC 1490	Idaho Falls, Idaho	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hancock, Mich.	WMP 920	Independence, Kans.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanford, Calif.	KNGS 520	Independence, Mo.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hannibal, Mo.	KHMO 1070	Indiana, Pa.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 1340 CKIL 940 N	Joplin, Mo.	WVWF 1360 WARF 1240 WITZ 990 KTSB 600 C	Lafayette, Tenn.	WVLA 1590 WASK 1450 M WBA 920 KPEL 1420 A	
Hanover, N.H.	WTSL 400	Indianapolis, Ind.	WHGR 1290 WHUJ 134					

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.		
New Bern, N.C.	WNBH 1340 M WHIT 1450 M WRNB 1490	Oceanlake, Oreg.	WHYS 1370 KBCH 1380 KUDE 1320	Park Falls, Wis.	WTAP 1230 A WFPF 1450	Ponca City, Okla.	WL0D 980 WP0M 1470		
Newberry, S.C.	WKOK 1240	Odessa, Calif.	KECK 920 KOSA 1230 KOYL 1310	Parry Sound, Ont.	CKAR-1 1340	Fonce, P.R.	WB2Z 1230 M WFBQ 910 WUC 1420 WPAC 550 WLE0 1170 WIS0 1260 WP0N 1460 KW0C 930 WFOR 1350		
New Braunfels, Tex.	KGNB 1420		KRIG 1410 M	Parsons, Kans.	KLKC 1540 KALI 1430 KPPC 1240				
New Britain, Conn.	WHAY 910 A		KOEL 950	Pasadena, Calif.	KR1A 1110 KJWK 1300 KLVL 1480				
New Brunswick, N.J.	WVCTC 1450	Delweir, Iowa	KOGA 930	Pasadena, Tex.	WPMF 1580 A				
Newburyport, N.Y.	WGNV 1220	Ogallala, Nebr.	KLO 1430 M	Pasceaug, Miss.	KORD 910				
Newburgh, Mass.	WNBP 1470	Ogden, Utah	KSVN 730 KVOG 1490	Pasco, Wash.	KPRK 1340				
New Carlisle, Que.	CHNC 610		WSLB 1400 M	Paso Robles, Calif.	KPRL 1230 M				
Newcastle, N.B.	CKMR 790	Ogdensburg, N.Y.	WKRZ 1340	Patchogue, L.I., N.Y.	WALK 1370 M				
New Castle, Pa.	WKST 1280	Oil City, Pa.	KBIE 880 A		WPAC 1580				
Newcastle, Wyo.	KASL 1240	Okla. City, Okla.	KLPR 1140		WPAT 930				
New Glasgow, N.S.	WVLC 1300		KOMA 1520 N	Paterson, N.J.	KV1L 1470				
New Haven, Conn.	WVZ 1300 WELI 960 WNHC 1340 A KANE 1240 KVM 1360		KTOK 1000 C	Pauls Valley, Okla.	WPAW 550 A				
New Iberia, La.			KTOW 800	Pawtucket, R.I.	KEOK 1450				
New Kensington, Pa.	WKPA 1150		WKY 930	Payette, Idaho	CKYL 650				
New London, Conn.	WNL 1490 M	Okmulgee, Okla.	OKML 1240	Peace Rivr. Alta.	WFLN 400 M				
New Martinsville, Va.		Old Saybrook, Conn.	WLS 1470	Pecos, Tex.	WLA 1420				
		Olean, N.Y.	WMNS 1360	Peekskill, N.Y.	WLV 1420				
			WHOL 1450 A	Pekin, Ill.	WSIV 1140				
Newnan, Ga.	WCOH 1400 M		WV1N 740	Pell City, Ala.	WFHK 1430				
New Orleans, La.	WDSU 1280 N WJBW 1230 WJMR 990 WBOK 800 WDOE 1060 WSMB 1350 A WNPS 1450 WTIX 690 WWL 870 C WYFD 940	Diney, Ill.	WV1N 740	Pembroke, Ont.	CHOV 1350				
		Olympia, Wash.	WV1N 740	Pendleton Oreg.	KKIO 1240 A KUBE 1050 KUMA 1290				
			WV1N 740	Pennington Gap, Va.	WSWV 1570 A				
			WV1N 740	Pensacola, Fla.	WBOP 980 WBRS 1450 C WNVY 1230 A WCOA 1370 N WFFA 790 WFLN 400 M WMB0 1470 C WIRL 1290 C WPEO 1020 WPRY 1400 WBBN 980 WARR 1600 WFL 1490 CHEX 980 WSSB 1240 M WBBN 1340 WPX 1460 A WHOC 1490 WCAU 1210 WDA5 1480 WFL 580 A WFLN 900 WHAT 1340 WIBG 900 WIP 610 M WJM1 540 WEN 1450 WRN 1060 N WTEL 860				
			WV1N 740	Perry, Fla.	WPRY 1400				
			WV1N 740	Perry, Ga.	WBBN 980				
			WV1N 740	Perryton, Tex.	KEYE 1400 M				
			WV1N 740	Peru, Ind.	WARR 1600				
			WV1N 740	Petaluma, Calif.	KMP 1490				
			WV1N 740	Peterborough, Ont.	CHEX 980				
			WV1N 740	Petersburg, Va.	WSSB 1240 M				
			WV1N 740	Peteskoy, Mich.	WBBN 1340				
			WV1N 740	Phenix City, Ala.	WPX 1460 A				
			WV1N 740	Philadelphia, Miss.	WHOC 1490				
			WV1N 740	Philadelphia, Pa.	WCAU 1210 WDA5 1480 WFL 580 A WFLN 900 WHAT 1340 WIBG 900 WIP 610 M WJM1 540 WEN 1450 WRN 1060 N WTEL 860				
			WV1N 740	Philadelpia, Pa.	WCAU 1210 WDA5 1480 WFL 580 A WFLN 900 WHAT 1340 WIBG 900 WIP 610 M WJM1 540 WEN 1450 WRN 1060 N WTEL 860				
			WV1N 740	Philadelpia, Pa.	WCAU 1210 WDA5 1480 WFL 580 A WFLN 900 WHAT 1340 WIBG 900 WIP 610 M WJM1 540 WEN 1450 WRN 1060 N WTEL 860				
			WV1N 740	Philadelpia, Pa.	WCAU 1210 WDA5 1480 WFL 580 A WFLN 900 WHAT 1340 WIBG 900 WIP 610 M WJM1 540 WEN 1450 WRN 1060 N WTEL 860				
			WV1N 740	Philadelpia, Pa.	WCAU 1210 WDA5 1480 WFL 580 A WFLN 900 WHAT 1340 WIBG 900 WIP 610 M WJM1 540 WEN 1450 WRN 1060 N WTEL 860				
			WV1N 740	Philadelpia, Pa.	WCAU				

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
	WPTF 680 N	Rome, N.Y.	WKAL 1450 A		KENS 680 C		C.S. 1050
	WSHE 570	Ronceverte, W.Va.	WRON 1400		KUKA 1250	Seguin, Tex.	KWED 1580
Rapid City, S.Dak.	WRAL 1400	Roseburg, Oreg.	KRNR 1490 C		KUBO 1310	Selma, Ala.	WGWC 1340 C
	KOTA 1300	Rosenberg, Tex.	KRXL 1240 A		KMAC 630 A		WHBB 1490
	KFRD 1300	Rossville, Ga.	KFRD 980		KOND 960		WRWJ 1570
	KEZU 920	Roswell, N.Mex.	WRIP 960		KTSA 550		KSML 1250
Raton, N.Mex.	KRTN 1490 A		KSWS 1230	San Bernardino, Calif.	WOAI 1200	Seminole, Tex.	WSNW 1150
Ravenwood, W.Va.	WMOV 1360		KGFL 1400 M		KKCK 1350	Seneca Township, S.C.	WVEY 930
Rawlins, Wyo.	KRAL 1240 M	Rouyn, Que.	KBIM 910		KFKM 590	Sevierville, Tenn.	KIBW 1340 C-A
Raymond, Wash.	KAPA 1340	Roxboro, N.C.	KCRN 1400		KKNM 1240	Seward, Alaska	WJCD 1390
Raymondville, Tex.	KSOX 1240	Royal Oak, Mich.	WRXO 1430		KITO 1290 M	Seymour, Ind.	KSEJ 1290
Rayville, La.	KCIV 540	Rumford, Me.	WEXL 1340	Sandersville, Ga.	WSNT 1490	Seymour, Tex.	KWJ 1300
Reading, Pa.	WEUW 540 A	Rushton, La.	WRUM 790	San Diego, Calif.	KFBQ 1170	Shamokin, Pa.	WISL 1480
	WHUM 1240 C	Rusk, Texas	KAYT 970		KFSO 600 N	Shamrock, Tex.	KBYP 1580
	WRAP 1340 N	Russell, Kans.	KRUS 1490		KGB 1360 A	Sharon, Pa.	WPIC 960
Redding, Calif.	KRDG 1230 M	Russellville, Ala.	KTLU 1580		KSON 1240	Shawhan, Wis.	WTCH 960
	KPAP 1270	Russellville, Ark.	KRSL 990		KSDO 1130	Shawigan, Que.	CKM 1220
	KSDA 1400	Rutland, Vt.	WWWR 920		KSPD 1050	Shawnee, Okla.	KGFF 1430 A
	KVCV 600		KXJR 1490	Sandpoint, Idaho	KSPD 1050	Sheboygan, Wis.	WHBL 1350 M
Red Bluff, Calif.	KBLF 1490		WVUS 610	Sandusky, Ohio	WLEC 1450 M	Shelby, Mont.	KWTL 950
Red Deer, Alta.	CKRD 850		WHW 1000	San Fernando, Calif.	KGLL 1100	Shelby, N.C.	KSEN 1150 M
Redlands, Calif.	KCAL 1410		WSYB 1380 M	Sanford, Fla.	WTRR 1260		WHOS 730 M
Red Lion, Pa.	WGCB 1440	Saanich, B.C.	CFAX 810		WIOD 1360	Shelbyville, Tenn.	WAOA 1390
Redmond, Oreg.	KPRB 1240	Sackville, N.B.	CBA 1070	Sanford, Me.	KWME 1220	Shenandoah, Iowa	KFNZ 920
Red Wing, Minn.	KCSE 1250	Sacramento, Calif.	KCBA 1320 A	Sanford, N.C.	WEYE 1290		KMA 960 A
Redwood Falls, Minn.	KLGR 1490		KGMS 1380	San Francisco, Cal.	WWGP 1050	Sherbrooke, Que.	CHLT 630
Redwood, Wis.	WVCF 1400		KXDA 470 C		KBFS 740		CKTS 900
Regina, Sask.	WCBK 540	Safford, Ariz.	KGLU 1480 A		KCBS 740	Sheridan, Wyo.	KWYO 1410 M
	CKCK 620	Saginaw, Mich.	WKNX 1210		KCNB 680 N	Sherman, Tex.	KRRY 910 M
Reidsville, N.C.	WFRG 1600 A		WSAM 1400 N		KOBY 1550 M	Show Low, Ariz.	KTKO 1500
	WREY 1220	St. Albans, Vt.	WWSG 790 M		KSAY 1010	Shreveport, La.	KANB 1300
Remsen, N.Y.	WRV 1480	St. Albans, W.Va.	WWSR 1420	San Jose, Calif.	KSAN 1450		KCIJ 1050
Reno, Nev.	KOH 630 N	St. Anne de la	WKLC 1300		KSFD 560		KEEL 710
	KBET 1340 M	Peatieres, Que.	CHGB 1350		KYA 1260		KENT 1550 M
	KOLO 920 C	St. Augustine, Fla.	WFOY 1240 C		KSJO 1590		KJDE 1480
	KONE 1450		WSTN 1420		KEEN 1370		KKOA 1380
	KDOT 1230	St. Boniface, Man.	CKSB 1050	San Juan, P.R.	KXRK 1500		KKRM 1240 A
Renton, Wash.	KQDE 910	St. Catharines, Ont.	CKTB 610		WAPA 680 M	Sidney, Mont.	KGCG 1480 M
Rexburg, Idaho	KRX 1230	St. Charles, Mo.	KADY 1230		WHPA 1400	Sidney, Nebr.	KSID 1340 M
Rhineland, Wis.	WOBT 1240	St. Cloud, Minn.	KFAM 1450 N		WIPR 940	Sierra Vista, Ariz.	KHFF 1420 A
Rice Lake, Wis.	WJMC 1240		WJON 1240		WKAY 580	Sierston, Mo.	KSIM 1400
Richfield, Utah	KSCV 960	St. George, Utah	KDXU 1450		WKAM 1230	Siler City, N.C.	WNGA 1570
Richland, Wash.	KALE 980	St. Helen, Mich.	WMIC 1590		WKYM 1230	Silver Spring, Ark.	WLOA 1400
Richland, Wis.	WRGO 1450	St. Hyacinthe, Que.	CKBS 1240	San Luis Obispo, Calif.	WITA 1140	Silver Sprgs., Md.	WGAY 1050
Richville, Va.	WRIC 540	St. Jean, Que.	CHRS 1090		KATY 1340	Simcoe, Ont.	CFRS 1560
Richmond, Ind.	KWBY 1490 A	St. Jerome, Que.	CHL 900	San Marcos, Tex.	KVCE 920 M	Sinton, Tex.	KTOD 1590
Richmond, Ky.	WEKY 1340	Saint John, N.B.	CFB 930	San Mateo, Calif.	KOFY 1050	Sioux City, Iowa	KCSJ 1360 A
Richmond, Va.	WANT 990		CHSJ 1150	San Rafael, Calif.	KTIM 1510		KHNS 620
	WBBL 1480	St. John's, Nfld.	CBN 640	San Saba, Tex.	KBAL 1410		KKSC 1470
	WEZL 1590		CJON 930	Santa Ana, Calif.	KWIZ 1480		KISD 1520
	WLEF 1480 N		VOAR 1230	Santa Barbara, Cal.	KDB 1490		KELD 1320
	WBEZ 1320		VOCM 590		KIST 1340		KIHO 1270
	WMBE 1380 A	St. Johnsburry, Vt.	WTWR 1400	Santa Cruz, Calif.	KTMS 1250 A-M		KSDO 1140 A
	WRNL 910 M	St. Joseph, Mich.	WWSJ 1400	Santa Fe, N.Mex.	KTRC 1400 A	Sitka, Alaska	KIFW 1230 C-A
	WRVA 1140 C	St. Joseph, Mo.	KFEQ 680		KVSE 1260 C	Skowhegan, Maine	WGEW 1400
	WXGI 950		KRES 1550 M	Santa Maria, Cal.	KCOY 1400	Smithfield, N.C.	WMPM 1270
Richmond Hill, Ont.	CJRH 1310	St. Joseph d'Alma, Que.	CFAT 1270		KSM 1240	Smiths Falls, Ont.	CJET 630
Richwood, W.Va.	WMNF 1280	St. Louis, Mo.	KATZ 1600	Santa Monica, Cal.	KMA 1580	Snyder, Tex.	KSNY 1450 M
Ridgecrest, Calif.	KRC 1360		KMOX 1120 C	Santa Paula, Calif.	KSP 1400	Socorro, N.Mex.	KSRC 1290
	KIS 1400		KSD 550 N	Santa Rosa, Calif.	KSRO 350	Soda Sprgs., Idaho	KBRV 540
Rimouski, Que.	CJBR 900		KSTL 690	Santurce, P.R.	WIAC 740	Somerser, Ky.	WSPC 1240 M
Rio Piedras, P.R.	WRIO 1320		KWK 1380	Saranac Lake, N.Y.	WNBZ 1240 A	Somerser, Pa.	WVC 990
	WWWV 1520		KXOK 630	Sarasota, Fla.	WKXY 930	Sonora, Calif.	KROG 1450
Ripley, Tenn.	WTRB 1570		WEL 770 M	Santa Ana, Calif.	WSPB 1450 C	Sorel, P.Q.	CJSD 1320
Ripon, Wis.	WCWC 1600	St. Louis Park, Minn.	WIL 1430 A	Saratoga Springs, N.Y.	WSPN 900	So. Bend, Ind.	WNDU 1490 A
Riverhead, N.Y.	WRV 1390	St. Mary's, Pa.	KRSI 950		WSPN 900		WVJ 1580 M
Riverside, Calif.	KPRD 1440	St. Paul, Minn.	WKBJ 1400	Sarnia, Ont.	HRSA 1280	Southbridge, Mass.	WBSB 970 C
	KACE 1570		KSTP 1500 N	Saskatoon, Sask.	CFQC 600	So. Boston, Va.	WLHF 1400 A
Riverton, Wyo.	KWRL 1450 M	St. Peter, Minn.	KDWB 1590 M		CFNS 1170	South Daytona Beach, Fla.	WELE 1590
Riviera Beach, Fla.	WHEW 1600	St. Petersburg, Fla.	WFIN 680	Saugerties, N.Y.	CKQM 1420	So. Gastonia, N.C.	WGAS 1420
Riviere du Loup, Que.	CJFP 1400		WSUN 620 A	Sault Ste. Marie, Mich.	WQMG 920	So. Paris, Me.	WKTK 1450
Roanoke, Ala.	WELR 1360		WLCY 1380 M	Sault Ste. Marie, Ontario	CJIC 1050	So. Pittsburg, Tenn.	WEPG 910
Roanoke, Va.	WDBJ 960 C	St. Thomas, Ont.	CHLO 580	Savitona, Ga.	WCCP 1450 M	So. St. Paul, Minn.	WISB 630 M
	WRIS 1410 M	St. Thomas, Ont.	CHLO 580		WJIV 900	So. Williamsport, Pa.	WMP 1450
	WYF 910	St. Thomas, Ont.	CHLO 580		WSA 630 N	Sparta, Ill.	WHCO 1230
	WROY 1240 A	St. Thomas, Ont.	CHLO 580		WSA 630 N	Sparta, Tenn.	WSMT 1050
	WLSL 610 N	Salamanca, N.Y.	WNY 1590		WTOC 1290 C	Sparta, Wis.	WCOW 1290
Roanoke Rapids, N.C.	WCBT 1230 M	Salem, III.	WJBS 1350		WSDK 1230 A	Spartanburg, S.C.	WTHE 1400 M
Roaring Sprgs., Pa.	WKMC 1370	Salem, Ind.	WSLM 1230	Savannah, Tenn.	WORM 1010		WORD 910 N
Roberval, Que.	CHRL 910	Salem, Mass.	WESX 1250	Sayre, Pa.	WBY 1320	Spencer, Iowa	WSP 950 C
Robinson, Ill.	WTAY 1570	Salem, Mo.	KSMO 1340	Schefferville, Que.	CFKL 1230	Spokane, Wash.	KICD 1240
Rochester, Minn.	KROC 1340 N	Salem, Oreg.	KSML 1390 A	Schenectady, N.Y.	WGY 810 N		KGK 1510 A
	KWEB 1270		KSLM 1390 A		WSNY 1240		KLYK 1290
Rochester, N.H.	WNNH 930	Salem, Va.	WBLU 1480		KNEB 960 M		KPEG 1380
Rochester, N.Y.	WBBF 950 M	Salida, Colo.	KVRH 1340 M		KWRI 1050		KKHQ 590 N
	WHAM 1180 N	Salina, Kans.	KSAL 1150 M	Scottsbluff, Nebr.	KNEB 960 M		KKEW 790 M
	WHIC 1460	Salinas, Calif.	KDON 1460		KWRI 1050		KKX 970 C
	WRVM 680		KSMB 1380 M	Scottsboro, Ala.	WCRI 1050		KXLY 920 C
	WSAY 1370	Saline, Mich.	KBWB 1490	Scottsdale, Ariz.	KPKO 1400	Springdale, Ark.	KBRB 1340 A
	WYET 1280 A	Salisbury, Md.	WBOC 960	Scottsville, Ky.	WLCK 1250	Springfield, Ill.	WCVS 1450 A-M
Rockford, Ill.	WRWK 1440 A		WICD 1320	Scranton, Pa.	WARM 590 A		WMAY 970 N
	WRRR 1330	Salisbury, N.C.	WJTY 1470		WEJL 630	Springfield, Mass.	WTAX 1240 C
Rock Hill, S.C.	WRH 1340 M		WSTP 1490 M		WGBI 910 C		WVZA 1030
	WTYC 1150	Salmon, Idaho	WSAT 1280 A		WICK 1400		WHYN 950 C
Rockingham, N.C.	WAYN 900	Salt Lake City, Utah	KALL 910 M		WSCR 1320		WMAS 1450 M
Rock Island, Ill.	WBFH 1270 C		KCPX 1320 N	Seaford, Del.	WSUX 1280	Springfield, Mo.	WSPR 1270
Rockland, Maine	WRKD 1450 A		KLUB 570 A	Seattle, Wash.	KAYO 1150		KICK 1340
Rockmart, Ga.	WPLK 1220 M		KNAK 1280		KING 1090 A		KKTS 1400 C
Rock Springs, Wyo.	KVRS 1360 M		KSL 1160 C		KIRO 710 C		KWTO 560 A
Rockville, Md.	WINX 1600		KSOF 1370		KJR 950		WIZE 1340 A
Rockwood, Tenn.	WRK 580		KWHD 860		KOL 1300		WBLY 1600
Rocky Ford, Colo.	WRGS 1420		KWIC 1570		KOMO 1000 N		KEED 1050
Rocky Mount, N.C.	WCEC 810		KTXL 1340		KTIX 1590		WDBL 1590
	WEED 1390 A		KGKL 960 A		KTW 1250		WCFR 1480
	WRMT 1490		KPEP 1420		KXA 770		WCFB 1460
	WYTI 1570		KWFR 1269	Searcy, Ark.	KWCB 1300		WTOE 1470
Rogers, Ark.	KAMO 1390		KCOR 1350	Sebring, Fla.	WJCM 960	Stamford, Conn.	WSTC 1400 A
Rogers City, Mich.	WHAK 960			Sedalia, Mo.	WJRO 1480	Stamford, Tex.	KDWT 1400
Rogersville, Tenn.	WRGS 1370					Starke, Fla.	WRGR 1490
Rolia, Mo.	KTRR 1490						
Rome, Ga.	WLAG 1410 A						
	WRGA 1470 M						
	WRDM 710						

Yazoo City Miss. WAZF 1230
 Yellowknife, N.W.T. CFYK 1340
 York, Nebr. KAWL 1370
 York, Pa. WNOW 1250
 WORK 1350 N

York, S.C. WSBA 910 A-M
 WYCL 1580
 Yorkton, Sask. CJGX 1440
 Youngstown, Ohio WBBW 920 A
 WFMJ 1390 N

Yreka, Calif. KSYC 1570
 Yuba City, Calif. KUBA 1600
 KAGR 1450
 Yuma, Ariz. KOFA 1240

WKBN 570 C
 KVCY 1400 A
 KYUM 560 N
 WHIZ 1240 N
 WAWZ 1380

Zanesville, Ohio
 Zephareth, N.J.

U. S. and Canadian AM Stations by Call Letters

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
KAAA	Kingman, Ariz.	1250	KBIM	Roswell, N. Mex.	910	KCMR	McCamey, Tex.	1450	KENT	Shreveport, La.	1550
KAB	Hot Springs, Ark.	1350	KBIS	Bakersfield, Calif.	970	KCMS	Manitou Sprgs., Colo.	1490	KENY	Bellingham, Wash.	930
KABC	Los Angeles, Calif.	790	KBIX	Muskogee, Okla.	1490	KCNI	Broken Bow, Nebr.	1280	KEOK	Payette, Idaho	1450
KABL	Oakland, Calif.	960	KBIZ	Ottumwa, Iowa	1240	KCNO	Alturas, Nebr.	1470	KEOS	Postfach, Ariz.	1280
KABQ	Albuquerque, N. M.	1350	KBJT	Fordyce, Ark.	1570	KCNY	San Marcos, Tex.	1280	KEPC	Kennerick, Wash.	610
KABR	Aberdeen, S. Dak.	1250	KBKC	Mission, Kans.	1480	KCOB	Newton, Iowa	1280	KEPS	Eagle Pass, Tex.	1270
KABY	Albany, Oreg.	990	KBKR	Baker, Oreg.	1490	KCOG	Centerville, Iowa	1400	KERB	Kermit, Tex.	690
KACE	Riverside, Calif.	1570	KBKW	Aberdeen, Wash.	1450	KCOH	Houston, Tex.	1430	KERC	Eastland, Tex.	1500
KACI	The Dalles, Oreg.	1360	KBLA	Burbank, Calif.	1490	KCOK	Tulare, Calif.	1270	KERG	Eugene, Oreg.	1280
KACT	Andrews, Tex.	1360	KBLF	Red Bluff, Calif.	1490	KCOL	Ft. Collins, Colo.	1410	KERN	Bakersfield, Calif.	1410
KACY	Port Hueneme, Calif.	1320	KBLI	Blackfoot, Idaho	690	KCON	Conway, Ark.	1230	KERV	Kerrville, Tex.	1230
KADA	Ada, Okla.	1230	KBLH	Hot Springs, Ark.	1470	KCOR	San Antonio, Tex.	1350	KEUN	Uniontown, Tex.	1440
KADO	Marshall, Tex.	1410	KBLR	Goodland, Kans.	730	KCOW	Allamore, Nebr.	1490	KKEV	Perroy, Mo.	1400
KADY	St. Charles, Mo.	1460	KBLT	Big Lake, Tex.	1290	KCOY	Santa Maria, Calif.	1400	KEVE	Minneapolis, Minn.	1440
KAFP	Petaluma, Calif.	1490	KBLM	Henderson, Nev.	1400	KCRA	Sacramento, Calif.	1320	KEVL	White Castle, La.	1590
KAFY	Bakersfield, Calif.	550	KBMN	Bozeman, Mont.	1230	KCRB	Chanute, Kans.	1490	KEVT	Tucson, Ariz.	690
KAGE	Winona, Minn.	1380	KBMO	Benson, Minn.	1290	KCRC	Enid, Okla.	1360	KEWB	Oakland, Calif.	910
KAGI	Crosslet, Ark.	800	KBMW	Breckinrdg., Minn.	1450	KCRG	Cedar Rapids, Iowa	1600	KEX	Portland, Oreg.	1190
KAGJ	Grants Pass, Oreg.	1300	KBMX	Coalinga, Calif.	1470	KCRH	Crane, Tex.	1380	KEXO	Grand Junction, Colo.	1230
KAGT	Anacortes, Wash.	1340	KBNB	Boiling, Mont.	1110	KCRS	Midland, Tex.	1550	KFYD	Dakota, N. Dak.	1220
KAGR	Yuba City, Calif.	1450	KBNB	Band, Oreg.	1110	KCRV	Caruthersville, Mo.	1870	KEYE	Yerkes, Mo.	1490
KAHI	Auburn, Calif.	950	KBNZ	Lajunta, Colo.	1400	KCSI	Pueblo, Colo.	1590	KEYZ	Rapid City, S. Dak.	920
KAHU	Waipahu, Hawaii	920	KBOA	Kennett, Mo.	830	KCSJ	Chadron, Nebr.	1450	KEYJ	Jamesstown, N. Dak.	1400
KAIM	Kaimuki, Hawaii	870	KBOE	Oskaloosa, Iowa	740	KCSR	Chadron, Nebr.	1450	KEYS	Corpus Christi, Tex.	1440
KAIR	Tucson, Ariz.	1490	KBOI	Boise, Idaho	950	KCTA	Corpus Christi, Tex.	1030	KEYV	Provo, Utah	1450
KAJI	Little Rock, Ark.	1250	KBOK	Malvern, Ark.	1310	KCTI	Gonzales, Tex.	1450	KEYZ	Williston, N. Dak.	1360
KAJD	Kanawha, W. Va.	1300	KBOJ	Boulder, Colo.	1270	KCTX	Childress, Tex.	1510	KFAB	Omaha, Nebr.	1110
KAKC	Tulsa, Okla.	970	KBOM	Manda, Okla.	1270	KCTD	Tulsa, Ariz.	1290	KFAD	Los Angeles, Calif.	1330
KAKE	Wichita, Kan.	1240	KBON	Omaha, Nebr.	1490	KCUE	Red Wing, Minn.	1320	KFUL	Fulton, Mo.	900
KALB	Alexandria, La.	580	KBOP	Pleasanton, Tex.	1380	KCVL	Fort Worth, Tex.	1520	KFAM	St. Cloud, Minn.	1450
KALE	Richland, Wash.	960	KBOS	Brownsville, Tex.	1600	KCVL	Colville, Wash.	1270	KFAR	Fairbanks, Alaska	660
KALG	Alamogordo, N. Mex.	1230	KBOW	Butte, Mont.	1490	KCVR	Lodi, Calif.	1570	KFAY	Fayetteville, Ark.	1250
KALI	Pasadena, Calif.	1430	KBOW	Medford, Oreg.	730	KCYL	Lampasas, Tex.	1450	KFBB	Great Falls, Mont.	1310
KALJ	Salt Lake City, Utah	910	KBOX	Dallas, Tex.	1480	KCAD	Ft. Bragg, Calif.	1230	KFCB	Cheney, Wyo.	1240
KALM	Thayer, Mo.	1290	KBRK	Mill, Oreg.	1430	KDAL	Duluth, Minn.	610	KFBI	Wichita, Kans.	1070
KALT	Atlanta, Tex.	900	KBRK	Mt. Vernon, Wash.	1430	KDAB	Earhart, Calif.	790	KFB	Marion, Ark.	1530
KALV	Alva, Okla.	1430	KBRK	Brookings, S. Dak.	1430	KDAA	Lubbock, Tex.	580	KFDA	Amarillo, Tex.	1440
KAMD	Camden, Ark.	910	KBRM	McCook, Nebr.	1300	KDAS	Santa Monica, Calif.	1580	KKDF	Van Buren, Ark.	1580
KAML	Kenedy, Tex.	990	KBRB	Bremerton, Wash.	1490	KDB	Santa Barbara, Calif.	1490	KFDM	Beaumont, Tex.	560
KAMO	Rogers, Ark.	1390	KBRB	Springdale, Ark.	1340	KDBC	Mansfield, La.	1360	KFRD	Grand Coulee, Wash.	1360
KAMP	El Centro, Calif.	1430	KBRV	Soldi Sprgs., Ida.	540	KDBM	Dillon, Mont.	800	KFEL	Pueblo, Colo.	970
KANA	Anaconda, Mont.	1230	KBRV	North Platte, Nebr.	1350	KDD	Dumas, Tex.	800	KFEQ	St. Joseph, Mo.	680
KANB	Shreveport, La.	1300	KBRZ	Freepress, Texas	1460	KDD	Des Moines, Iowa	1240	KFFA	Fort Worth, Tex.	1280
KAND	Corsicana, Tex.	1340	KBSF	Springhill, La.	1460	KDEA	Albuquerque, N. Mex.	1150	KFGG	Boone, Iowa	1260
KANE	New Iberia, La.	1240	KBST	Big Spring, Tex.	1490	KDEF	Albuquerque, N. Mex.	1150	KFHI	Wichita, Kans.	1330
KANI	Kailua, Oahu, Hawaii	1240	KBTA	Batesville, Ark.	1340	KDEN	Denver, Colo.	1340	KFLA	Lakewood, Wash.	1480
KANO	Anoka, Minn.	1470	KBTM	Jonesboro, Ark.	1230	KDEO	El Cajon, Calif.	910	KFLH	Los Angeles, Calif.	640
KANS	Independence, Mo.	1510	KBTN	Neesho, Mo.	1420	KDES	Palm Sprgs., Calif.	920	KFIR	North Bend, Oreg.	1340
KANK	Lake Charles, La.	1400	KBTO	El Dorado, Kans.	1360	KDET	Center, Tex.	930	KFIV	Modesto, Calif.	1360
KAPA	Raymond, Wash.	1400	KBUA	Corona, Calif.	1370	KDEX	Dexter, Mo.	1590	KFIZ	Fond du Lac, Wis.	1450
KAPB	Marksville, La.	1370	KBUA	Athena, Ga.	1410	KDFA	Faribault, Minn.	920	KFLK	Klamath Falls, Oreg.	1150
KAPI	Pueblo, Colo.	690	KBUH	Brigham City, Utah	800	KDIA	Oakland, Calif.	1310	KFLM	Grand Forks, N. Dak.	1370
KAPR	Douglas, Ariz.	930	KBUN	Bemidji, Minn.	1450	KDIO	Ortonville, Minn.	1310	KFJZ	Ft. Worth, Tex.	1270
KARE	Atchison, Kan.	1470	KBUR	Burlington, Iowa	1490	KDKA	Pittsburgh, Pa.	1020	KFKF	Bellevue, Wash.	1330
KARK	Little Rock, Ark.	920	KBUS	Mexia, Tex.	1590	KDKA	Kidsburg, Mo.	1280	KFKL	Livada, Kans.	1250
KARL	Fresno, Calif.	1430	KBUY	Amarillo, Tex.	1010	KDKC	Clinton, Mo.	1490	KFLD	Loyd, Tex.	900
KARS	Sauk Rapids, Minn.	1250	KBUZ	Mesa, Ariz.	1310	KDLD	DeRidder, La.	1010	KFLW	Wadena, Minn.	1360
KART	Jerome, Idaho	1400	KBWA	Lancaster, Calif.	1360	KDLK	Del Rio, Tex.	1230	KFLW	Klamath Falls, Oreg.	1450
KARY	Prosser, Wash.	1310	KBWD	Brownwood, Tex.	1380	KDLM	Detroit Lakes, Minn.	1340	KFLY	Corvallis, Oreg.	1240
KASH	Eugene, Oreg.	1600	KBYE	Okla. City, Okla.	890	KDLR	Devils Lake, N. Dak.	1240	KFMA	Davenport, Iowa	580
KASI	Ames, Iowa	1430	KBYG	Big Spring, Tex.	1400	KDMA	Montevideo, Minn.	1450	KFMB	San Diego, Calif.	1540
KASK	Ontario, Calif.	1510	KBYP	Shamrock, Tex.	1580	KDMO	Carthage, Mo.	1490	KFMI	Tulsa, Okla.	1050
KASL	Newcastle, Wyo.	1240	KBYR	Anchorage, Alaska	1270	KDMS	El Dorado, Ark.	1290	KFML	Denver, Colo.	1390
KASB	Albany, Minn.	1250	KBZY	Salem, Oreg.	1490	KDND	Deer Park, Tex.	1330	KFMO	Flat River, Mo.	1240
KASD	Minneapolis, Minn.	1240	KCAL	Redlands, Calif.	1410	KDNE	Deer Park, Tex.	1330	KFNF	Shenandoah, Iowa	920
KAST	Astoria, Oreg.	1370	KCAP	Helena, Mont.	1340	KDOK	Tyler, Tex.	1490	KFNR	Ferriday, Iowa	1600
KASY	Auburn, Wash.	1220	KCAR	Clarksville, Tex.	1350	KDOM	Windom, Minn.	1530	KFNW	Fargo, N. Dak.	900
KATE	Albert Lea, Minn.	1450	KCBG	Des Moines, Iowa	1390	KDON	Salinas, Calif.	1420	KFNL	Lincoln, Nebr.	1240
KATI	Casper, Wyo.	1400	KCBG	Des Moines, Iowa	1390	KDOT	Reno, Nev.	1260	KFNU	Long Beach, Calif.	1280
KATL	Miles City, Mont.	1340	KCBQ	San Diego, Calif.	1170	KDQV	Medford, Oreg.	1330	KFPW	Ft. Smith, Ark.	1230
KATY	San Luis Obispo, Calif.	1340	KCBS	San Fran., Calif.	740	KDQN	DeQueen, Ark.	1390	KFQD	Anchorage, Alaska	900
KATZ	St. Louis, Mo.	1600	KCCB	Corning, Ark.	1260	KDRS	Paradise, Ark.	1490	KFRB	Fairbanks, Alaska	730
KAUS	Austin, Minn.	1480	KCCO	Paris, Ark.	1460	KDSE	Deadwood, S. Dak.	980	KFRD	Rosenberg, Tex.	940
KAVE	Carlsbad, N. Mex.	1240	KCCR	Pierre, S. Dak.	1590	KDSN	Denison, Iowa	1580	KFRE	Fresno, Calif.	980
KAVI	Rocky Ford, Colo.	1320	KCCF	Corpus Christi, Tex.	1130	KDSE	Denison, Tex.	950	KFRM	Kansas City, Mo.	550
KAVL	Lancaster, Calif.	610	KCEE	Eusebio, Ariz.	790	KDTE	Delta, Colo.	1400	KFRG	Longview, Tex.	1370
KAVR	Apple Valley, Calif.	1370	KCFA	Spokane, Wash.	1330	KDTH	Dubuque, Iowa	1370	KFRU	Columbia, Mo.	1400
KAWL	York, Nebr.	1370	KCFH	Cuero, Tex.	1600	KDUB	Hutchinson, Minn.	1260	KFSA	Ft. Smith, Ark.	950
KAWY	Puyallup, Wash.	1450	KCHA	Charles City, Iowa	1580	KDWB	St. Paul, Minn.	630	KFSG	Joplin, Mo.	1310
KAYL	Storm Lake, Iowa	990	KCHE	Cherokee, Iowa	1440	KDWT	Stamford, Tex.	1400	KFSC	Denver, Colo.	1220
KAYO	Seattle, Wash.	1150	KCHI	Chilliothe, Mo.	1010	KDXE	N. Little Rock, Ark.	1380	KFSD	San Diego, Calif.	600
KAYS	Hays, Kans.	1400	KCHJ	Chillicothe, Mo.	1010	KDXU	St. George, Utah	1450	KFSG	Los Angeles, Calif.	1150
KAYT	Rupert, Idaho	970	KCHR	Chickasha, Okla.	1350	KDYL	Salt Lake City, Utah	1320	KFTF	Ft. Stockton, Tex.	860
KBAL	San Saba, Tex.	1210	KCHS	Truth or Consequences, N. Mex.	1400	KDZA	Pueblo, Colo.	1230	KFTM	Ft. Morgan, Colo.	1400
KBBM	Longview, Wash.	1470	KCHV	Coachella, Calif.	970	KDZB	Keokuk, Iowa	1490	KFTV	Paris, Tex.	1250
KBAN	Bowie, Tex.	1410	KCHY	Cheney, Wyo.	1590	KEAP	Fresno, Calif.	980	KFUN	Las Vegas, N. Mex.	1230
KBAR	Burley, Idaho	1290	KCID	Caldwell, Idaho	1490	KEBE	Jacksonville, Tex.	1400	KFUO	St. Louis, Mo.	850
KBBA	Benton, Ark.	690	KCII	Shreveport, La.	1050	KECK	Odessa, Tex.	920	KFVS	Case Girardeau, Mo.	980
KBBB	Borger, Tex.	1600	KCIL	Houma, La.	1490	KEDD	Longview, Wash.	1400	KFWB	Los Angeles, Calif.	980
KBBC	Centerville, Utah	1600	KCLM	Crail, Iowa	1380	KEDS	Springfield, Oreg.	1050	KFXD	Nampa, Idaho	560
KBBS	Buffalo, Wyo.	1450	KCMB	Comstock, N. Dak.	910	KEEL	Nacogdoches, Tex.	1230	KFXM	San Bernardino, Calif.	590
KBCB	Oceanlake, Oreg.	1380	KCJB	Minot, N. Dak.	1350	KEEL	Shreveport, La.	1370	KFYN	Bonham, Tex.	1420
KBCD	Bossier City, La.	1220	KCKC	San Bernardino, Cal.	1350	KEEP	Twin Falls, Idaho	1450	KFYU	Lubbock, Tex.	790
KBCE	Waxahatchie, Tex.	1390	KCKN	Kansas City, Kans.	1340	KELA	Centralia, Wash.	1470	KFYZ	Bismarck, N. Dak.	550
KBEE	Modesto, Calif.	1490	KCKY	Coolidge, Ariz.	1150	KELD	El Dorado, Ark.	1400	KGA	Spokane, Wash.	1510
KBEK	Elk City, Okla.	1240	KCLA	Pine Bluff, Ariz.	1400	KELE	Elko, Nev.	1240	KGAF	Gainesville, Tex.	1580
KBEL	Idabel, Okla.	1240	KCLE	Cleburne, Tex.	1120	KELO	Sioux Falls, S. Dak.	1320	KGAL	Gallup, N. Mex.	1390
KBEN	Carrizo Sprgs., Tex.	1450	KCLF	Clifton, Ariz.	1490	KELO	Sioux Falls, S. Dak.	1320	KGAS	Gallop, N. Mex.	1390
KBER	Reno, Nev.	1340	KCLG	Clifton, Ariz.	1490	KELO	Sioux Falls, S. Dak.	1320	KGAT	Gallup, N. Mex.	1390
KBFS	Belle Fourche, S. Dak.	1450	KCLH	Clinton, Iowa	1390	KELO	Sioux Falls, S. Dak.	1320	KGAS	Gallop, N. Mex.	1390
KBFC	Washington, Ariz.	1250	KCLJ	Clifton, Ariz.	1490	KELO	Sioux Falls, S. Dak.	1320	KGAS	Gallop, N. Mex.	1390
KBFM	Branson, Mo.	1450	KCLK	Clifton, Ariz.	1490	KELO	Sioux Falls, S. Dak.	1320	KGAY	Salem, Oreg.	1590
KBHS	Hot Springs, Ark.	590	KCLM	Clinton, Iowa	1390	KELO	Sioux Falls, S. Dak.	1320	KGB	San Diego, Calif.	1360
KBIA	Columbia, Mo.	1580	KCLN	Clinton, Iowa	1390	KELO	Sioux Falls, S. Dak.	1320	KGBC	Galveston, Tex.	1540
KBIF	Fresno, Calif.	900	KCLP	Rayville, La.	990	KELO	Sioux Falls, S. Dak.	1320	KGBT	Harrison, Tex.	1530
KBIG	Avon, Calif.	740	KCLS	Flagstaff, Ariz.	600	KELO	Sioux Falls, S. Dak.	1320	KGBX	Springfield, Mo.	1260
			KCLV	Clovis, N. Mex.	1240	KELO	Sioux Falls, S. Dak.	1320	KGCX	Sidney, Mont.	1480
			KCLW	Hamilton, Tex.	900	KELO	Sioux Falls, S. Dak.	1320			
			KVLX	Colfax, Wash.	1450	KELO	Sioux Falls, S. Dak.	1320			
			KCMC	Texarkana, Tex.	1230	KELO	Sioux Falls, S. Dak.	1320			
			KCMJ	Palm Sprgs., Calif.	1010	KELO	Sioux Falls, S. Dak.	1320			
			KCMO	Kansas City, Mo.	810	KELO	Sioux Falls, S. Dak.	1320			

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
KGDN	Edmonds, Wash.	630	KIPA	Hilo, Hawaii	1110	KMBC	Kansas City, Mo.	950	KONE	Reno, Nev.	1450
KGEE	Bakersfield, Calif.	1230	KIRO	Seattle, Wash.	710	KMBL	Junction, Tex.	1480	KONG	Visalia, Calif.	1400
KGEG	Sterling, Colo.	1230	KIRT	Mission, Tex.	1580	KMBY	Monterey, Calif.	1240	KONI	Phoenix, Ariz.	1400
KGEM	Boise, Idaho	1140	KIRX	Kirkville, Mo.	1450	KMCD	Fairfield, Iowa	1570	KONO	San Antonio, Tex.	860
KGEN	Tulare, Calif.	1570	KISD	Sioux Falls, S.Dak.	1230	KMCM	McMinville, Oreg.	1200	KONP	Port Angeles, Wash.	1450
KGFR	Long Beach, Calif.	1390	KISN	Vancouver, Wash.	910	KMCO	Conroe, Tex.	910	KOOK	Billings, Mont.	970
KGKZ	Kalispell, Mont.	600	KIST	Yakima Barbara, Calif.	1340	KMDF	Fort Scott, Kans.	1600	KOOL	Phoenix, Ariz.	960
KGJF	Shawnee, Okla.	1450	KITV	Yakima, Wash.	1400	KMEL	Wenatchee, Wash.	1400	KOOG	Omaha, Nebr.	1420
KGJF	Los Angeles, Calif.	1230	KITI	Chetahis, Wash.	1420	KMEL	Wenatchee, Wash.	1340	KOOS	Mission, S.Dak.	1490
KGFL	Roswell, N.Mex.	1400	KITN	Olympia, Wash.	920	KMHL	Marshall, Minn.	1400	KOPR	Butte, Mont.	550
KGFW	Kearney, Nebr.	1340	KITO	San Bernardino, Calif.	1290	KMHT	Marshall, Tex.	1450	KOPY	Alice, Tex.	1070
KGFX	Pierre, S.Dak.	630	KIUL	Garden City, Kans.	1240	KMIL	Cameron, Tex.	1330	KORA	Bryan, Tex.	1240
KGGF	Coffeyville, Kans.	690	KIUN	Pecos, Tex.	1400	KMIN	Grants, N.M.	980	KORC	Mineral Wells, Tex.	1110
KGGM	Albuquerque, N.Mex.	610	KIUP	Durango, Colo.	930	KMJB	Fresno, Calif.	580	KORD	Pasco, Wash.	910
KGHF	Pueblo, Colo.	1350	KIUR	Prockett, Tex.	1290	KMLB	Monroe, La.	1440	KORE	Eugene, Oreg.	1450
KGHL	Billings, Mont.	790	KIUS	Shreveport, La.	1040	KMLW	Lawrence, Kan.	1400	KORK	Las Vegas, Nev.	1340
KGHM	Brookfield, Mo.	1470	KIXX	Provo, Utah	1400	KMNJ	Grand Island, Nebr.	750	KORN	Mission, S.Dak.	1490
KGIL	San Fernando, Calif.	1260	KIXZ	Amarillo, Tex.	940	KMNS	Sioux City, Iowa	620	KORT	Grangeville, Idaho	1230
KGIV	Alamosa, Colo.	1450	KJAN	Atlantic, Iowa	1220	KMNS	Sioux City, Iowa	620	KOSA	Odesa, Tex.	1230
KGKB	Tyler, Tex.	1490	KJAT	Henderson, Tex.	1000	KMO	Tacoma, Wash.	1360	KOSE	Oseola, Ark.	860
KGKL	San Angelo, Tex.	960	KJAX	Santa Rosa, Calif.	1150	KMON	Great Falls, Mont.	560	KOSI	Aurora, Colo.	1430
KGKC	Miami, Okla.	910	KJAY	Topeka, Kans.	1440	KMOP	Tucson, Ariz.	1330	KOSY	Texasarkana, Ark.	790
KGLE	Glenwood Sprngs., Colo.	980	KJLD	Midland, Tex.	1150	KMOX	St. Louis, Mo.	1120	KOTA	Rapid City, S.Dak.	1280
KGLO	Wesson City, Iowa	1300	KJLW	Shreveport, La., Calif.	1420	KMRC	Los Angeles, Calif.	1430	KOTE	Fergus Falls, Minn.	1500
KGLU	Safford, Ariz.	1480	KJCK	Junction City, Kans.	1290	KMRS	Morris, Minn.	1570	KOTN	Elm Bluff, Ark.	1490
KGMB	Honolulu, Hawaii	590	KJEF	Jennings, La.	1290	KMUL	Muleshoe, Tex.	1380	KOTS	Deming, N.M.	1230
KGMC	Englewood, Colo.	1150	KJET	Beaumont, Tex.	1380	KMUR	Murray, Utah	1570	KOVC	Valley City, N.Dak.	1490
KGMS	Cape Girardeau, Mo.	1220	KJFW	Webster City, Iowa	1570	KMUS	Muskogee, Okla.	1230	KOVE	Lander, Wyo.	1330
KGMS	Sacramento, Calif.	1380	KJIM	Ft. Worth, Tex.	870	KMVS	Muskogee, Okla.	1230	KOVO	Provo, Utah	960
KGNC	New Braunfels, Tex.	1420	KJLT	North Platte, Nebr.	970	KMWI	Walluku, T. H.	550	KOWB	Laramie, Wyo.	1340
KGNB	Amarillo, Okla.	710	KJNO	Juneau, Alaska	630	KMYS	Marysville, Calif.	1410	KOWH	Omaha, Nebr.	660
KGND	Dodge City, Kans.	1370	KJNS	Shreveport, La.	1480	KNAF	Fredericksburg, Tex.	1480	KOWL	Lake Tahoe, Calif.	1490
KGDN	San Francisco, Calif.	810	KJOY	Stockton, Calif.	1290	KNAK	Salt Lake City, Utah	1280	KOWM	Escondido, Calif.	1450
KGON	Dregon City, Oreg.	1520	KJRS	Seattle, Wash.	950	KNAL	Victoria, Tex.	1410	KOXR	Ormaiztegui, Calif.	1010
KGOS	Torrington, Wyo.	1490	KJRW	Newton, Kans.	950	KNBA	Vallejo, Calif.	1190	KOYP	Phoenix, Ariz.	550
KGPC	Grafton, N.Dak.	1340	KJSC	Columbus, Nebr.	900	KNBC	San Francisco, Calif.	680	KOYE	El Paso, Tex.	1150
KGPN	Grinnell, Iowa	1410	KKEY	Vancouver, Wash.	1150	KNBX	Kirkland, Wash.	1050	KOYL	Odesa, Tex.	1310
KGRO	Gresham, Oreg.	1230	KKID	Pendleton, Oreg.	1240	KNBY	Newport, Ark.	1280	KOYN	Billings, Mont.	910
KGRT	Las Cruces, N.Mex.	570	KKIS	Pittsburg, Calif.	990	KNCK	Concordia, Kans.	1390	KOZI	Lewiston, Idaho	1300
KGST	Fargo, N.Dak.	1600	KKLN	Lincoln, Neb.	1270	KNCM	Meribyr, Tex.	1240	KZL	Chelan, Wash.	1220
KGU	Honolulu, Hawaii	760	KKSN	Grand Prairie, Tex.	730	KNCD	Garden City, Kans.	1050	KZM	Grand Rapids, Minn.	1490
KGVL	Greenville, Tex.	1400	KLAC	Los Angeles, Calif.	570	KNDC	Hettinger, N.Dak.	1490	KZP	Palm Springs, Tex.	1250
KGVO	Missoula, Mont.	1290	KLAD	Klamath Falls, Oreg.	960	KNDE	Aztec, N.Mex.	1340	KPAC	Grand Rapids, Tex.	1450
KGWV	Belgrade, Mont.	630	KLAK	Lakewood, Colo.	1450	KNDY	Marysville, Kant.	1570	KPAM	Pain Springs, Calif.	1450
KGW	Portland, Oreg.	620	KLAK	Cordova, Alaska	1450	KNEA	Jonesboro, Ark.	970	KPAM	Portland, Oreg.	1410
KGWA	Enid, Okla.	960	KLAS	Las Vegas, Nev.	1230	KNEB	Scottsbluff, Nebr.	960	KPAP	Hereford, Tex.	860
KGWY	Olympia, Wash.	1240	KLBM	La Grande, Oreg.	1450	KNEC	McAlester, Okla.	1150	KPAS	Banning, Calif.	1490
KGYN	Guymon, Okla.	1220	KLBN	Lawton, Okla.	1220	KNEE	Brady, Tex.	1240	KPAY	Chico, Calif.	1060
KHAM	Albuquerque, N.Mex.	1580	KLCN	Blitheville, Ark.	910	KNEV	Nevada, Mo.	1240	KPBK	Clinton, Ark.	1590
KHAS	Hastings, Nebr.	1230	KLCN	Poteau, Okla.	1280	KNET	Pelastine, Tex.	1450	KPBM	Castroville, N.Mex.	740
KHAT	Phoenix, Ariz.	1480	KLEA	Lovington, N.Mex.	630	KNEU	Provo, Utah	1450	KPCA	Marked Tree, Ark.	1580
KHBC	Hilo, Hawaii	970	KLEE	Ottumwa, Iowa	1480	KNEW	Spokane, Wash.	790	KPDN	Pampa, Tex.	1340
KHBM	Monticello, Ark.	1430	KLEM	LeMars, Iowa	1410	KNEX	McPherson, Kans.	1540	KPDP	Portland, Oreg.	800
KHBR	Hillsboro, Tex.	1560	KLEN	Killeen, Tex.	1050	KNEZ	Lompo, Calif.	960	KPEG	Spokane, Wash.	1380
KHEM	Big Springs, Tex.	1270	KLEO	Wichita, Kans.	1480	KNGS	Hanford, Calif.	620	KPEL	Lafayette, La.	1420
KHEN	Henryetta, Okla.	1590	KLER	Orofino, Idaho	950	KNIM	Maryville, Mo.	820	KPEP	San Angelo, Tex.	1420
KHEP	Phoenix, Ariz.	1280	KLEX	Lexington, Mo.	1570	KNM	Abilene, Tex.	1080	KPEP	Gilroy, Calif.	1280
KHEY	El Paso, Tex.	690	KLFD	Litchfield, Minn.	1410	KNOC	Natchitoches, La.	1450	KPEP	El Paso, Tex.	680
KHFH	Sierra Vista, Ariz.	1420	KLFT	Golden Meadow, La.	1600	KNOE	Monroe, La.	1390	KPHO	Phoenix, Ariz.	910
KHHH	Pampa, Tex.	1230	KLGA	Algona, Iowa	1600	KNOG	Nogales, Ariz.	1340	KPIG	Cedar Rapids, Iowa	1450
KHIL	Brighton-Fort Lupton, Colorado	800	KLGN	Logan, Utah	1390	KNOK	Ft. Worth, Tex.	970	KPIK	Colorado Sprgs., Colo.	1580
KHIT	Walla Walla, Wash.	1320	KLGR	Redwood Falls, Minn.	1490	KNOR	Norman, Okla.	1400	KPIN	Casa Grande, Ariz.	1260
KHJ	Los Angeles, Calif.	930	KLKR	Dallas, Tex.	1190	KNOR	Prescott, Ariz.	1450	KPKW	Paso, Wash.	1340
KHMO	Hannibal, Mo.	1070	KLKI	Jefferson City, Mo.	950	KNOW	Aurora, Colo.	1340	KPLC	Lake Charles, La.	1470
KHOB	Hobbs, N.Mex.	1280	KLIL	Estherine, Iowa	1340	KNOX	Grand Forks, N.Dak.	1310	KPLD	Dallas, Tex.	1460
KHOG	Fayetteville, Ark.	1450	KLIN	Lincoln, Nebr.	1400	KNPT	Newport, Ore.	1310	KPLY	Crescent City, Calif.	1420
KHOT	Madera, Calif.	1250	KLII	Portland, Oreg.	1290	KNUJ	New Ulm, Minn.	860	KPMC	Bakersfield, Calif.	1560
KHOW	Denver, Colo.	630	KLIR	Denver, Colo.	990	KNVJ	Houston, Tex.	1290	KPMG	Port Neches, Tex.	1150
KHOZ	Harrisburg, Ark.	600	KLIR	Denver, Colo.	990	KNWS	Waterloo, Iowa	1090	KPOA	Honolulu, T.H.	620
KHQ	Spokane, Wash.	590	KLIX	Twin Falls, Idaho	1310	KNX	Los Angeles, Calif.	1070	KPOC	Pocahontas, Ark.	1430
KHSJ	Hemet, Calif.	1320	KLK	Brainerd, Minn.	1380	KOAC	Corvallis, Oreg.	550	KPOF	Denver, Colo.	910
KHSL	Chico, Calif.	1290	KLKC	Parsons, Kans.	1540	KOAL	Price, Utah	1370	KPOH	Honolulu, Hawaii	1490
KHUB	Fremont, Nebr.	1340	KLKA	Leesville, La.	1570	KOAM	Pittsburg, Kans.	860	KPOJ	Portland, Oreg.	1380
KHUZ	Borger, Tex.	1490	KLLE	Lubbock, Tex.	1460	KOAB	Albuquerque, N.Mex.	1030	KPOK	Scottsdale, Ariz.	1440
KHVN	Honolulu, Hawaii	1040	KLMO	Longmont, Colo.	1050	KOBE	Las Cruces, N.Mex.	1450	KPOL	Los Angeles, Calif.	1020
KIEE	Palo Alto, Calif.	1210	KLMS	Lamar, Colo.	920	KOBY	San Francisco, Calif.	1550	KPOP	Los Angeles, Calif.	1020
KIBB	Sawax, Alaska	1340	KLNR	Lincoln, Nebr.	1480	KOCA	Albino, Tex.	1450	KPOR	Quincy, Wash.	1370
KIBL	Beaville, Tex.	1490	KLNO	Keosauqua, N.Mex.	1430	KOCB	Albino, Tex.	1450	KPOW	Powell, Wyo.	1260
KIBS	Bishop, Calif.	1230	KLOG	Kelso, Wash.	1490	KOCY	Okmulgee, Okla.	1340	KPOX	Omaha, Neb.	1420
KICA	Clovis, N.Mex.	980	KLOH	Pipestone, Minn.	1050	KODJ	Joplin, Mo.	1230	KPQ	Wenatchee, Wash.	560
KICO	Spencer, Iowa	1240	KLOK	San Jose, Calif.	1170	KODI	Cody, Wyo.	1400	KPRB	Redmond, Oreg.	920
KICK	Springfield, Mo.	1340	KLOS	San Jose, Calif.	1170	KODL	The Dalles, Oreg.	1440	KPRC	Houston, Tex.	1240
KICN	Denver, Colo.	710	KLOO	Corvallis, Oreg.	1340	KODY	North Platte, Nebr.	1240	KPRK	Livingston, Mont.	1340
KICQ	Calexico, Calif.	1490	KLOU	Albuquerque, N.Mex.	1450	KOFA	Yuma, Ariz.	1240	KPRL	Paso Robles, Calif.	1230
KIDD	Idaho Falls, Idaho	690	KLOV	Lake Charles, La.	1590	KOFE	Pullman, Wash.	1150	KPRS	Riverside, Calif.	1440
KIDO	Boise, Idaho	590	KLOV	Loveland, Colo.	1570	KOFI	Kalispell, Mont.	930	KPSD	Kansas City, Mo.	1590
KIKD	Monterey, Calif.	630	KLPL	Lake Providence, La.	1050	KOFO	Ottawa, Kans.	1220	KPST	Fairfax, Tex.	1260
KIKO	Eureka, Calif.	1480	KLPM	Minot, N.Dak.	1390	KOFS	Ottawa, Kans.	1220	KPST	Preston, Idaho	1340
KIEV	Glendale, Calif.	870	KLPR	Okla. City, Okla.	1140	KOFT	San Mateo, Calif.	1050	KPTL	Carson City, Nev.	1300
KIFJ	Idaho Falls, Idaho	1260	KLPW	Union, Mo.	1220	KOGA	Dgallala, Nebr.	930	KPUG	Bellingham, Wash.	1170
KIFN	Phoenix, Ariz.	860	KLRA	Little Rock, Ark.	1010	KOGT	Orange, Tex.	1600	KPVA	Camas, Wash.	1480
KIFW	Sitka, Alaska	1280	KLRS	Mountain Grove, Mo.	1360	KOH	Reno, Nev.	630	KQOE	Renton, Wash.	910
KIFX	Hugo, Okla.	1340	KLRT	Little Falls, Minn.	1580	KOHU	Hermiston, Oreg.	1570	KQDI	Bismarck, N.D.	1350
KIHO	Stout, Falls, S.Dak.	1240	KLTV	Viola, Okla.	1240	KOIA	Omaha, Neb.	920	KQDM	Midot, N.Dak.	1320
KIHR	Hood River, Oreg.	1370	KLTZ	Glasgow, Mont.	1240	KOJN	Portland, Oreg.	910	KQEO	Shawnee, N.Mex.	1490
KIJV	Huron, S.Dak.	1340	KLUB	Salt Lake City, Utah	570	KOJM	Havre, Mont.	670	KQIK	Lakewood, Wyo.	1230
KIKK	Bakersfield, Calif.	800	KLUK	Longview, Tex.	1280	KOKA	Shreveport, La.	980	KQTE	Missoula, Mont.	1340
KIKI	Honolulu, Hawaii	830	KLUE	Evanston, Wyo.	1240	KOKA	Austin, Tex.	1370	KQTY	Everett, Wash.	1240
KIKO	Miami, Ariz.	1340	KLUV	Haynesville, La.	1580	KOKL	Dkmuige, Okla.	1240	KQV	Pittsburgh, Pa.	1410
KIKS	Sulphur, La.	1310	KLVC	Leadville, Colo.	1230	KOKO	Warrensburg, Mo.	1450	KRAC	Alamogordo, N.M.	1270
KIKW	Galveston, Tex.	1400	KLVI	Denver, Colo.	1600	KOKR	Sturgis, Iowa	1400	KRAI	Craig, Colo.	550
KILO	Grand Forks, S.Dak.	1440	KLVY	Passadene, La.	1480	KOKY	Little Rock, Ark.	1400	KRAL	San Angelo, Calif.	1490
KILT	Houston, Tex.	610	KLWL	Levelland, Tex.	1230	KOLD	Seattle, Wash.	1320	KRAL	Rawlins, Wyo.	1240
KIMA	Yakima, Wash.	1460	KLWN	Lawrence, Kans.	1320	KOLE	Tucson, Ariz.	1450	KRAM	Las Vegas, Nev.	920
KIMB	Kimbali, Nebr.	1260	KLWT	Lebanon, Mo.	1230	KOLP	Port Arthur, Tex.	1340	KRAY	Amarillo, Tex.	1360
KIML	Gillette, Wyo.	1490	KLYD	Bakersfield, Calif.	1350	KOLJ	Quannah, Tex.	1150	KRBA	Lufkin, Tex.	1340
KIMO	Hilo, Hawaii	850	KLYK	Spokane, Wash.	1230	KOLL	Libby, Mont.	1230	KRBC	Billene, Tex.	1470
KIMN	Denver, Colo.	650	KLYR	Clarksville, Ark.	950	KOLR	Reno, Nev.	920	KRBI	St. Peter, Minn.	1310
KIMP	Mt. Pleasant, Tex.	960	KLZ	Denver, Colo.	1600	KOLS	Pryor, Okla.	1570	KRBO	Las Vegas, Nev.	1050
KIND	Independence, Kans.	1010	KMAA	Shenandoah, Iowa	980	KOLY	Scottsbluff, Nebr.	1320	KRCS	St. George, Utah	1360
KINE	Kingsville, Tex.	1330	KMAE	McKinney, Tex.	1600	KOLY	Mobridge, S.Dak.	1300	KRCO	Prineville, Oreg.	690
KING	Seattle, Wash.	1090	KMAF	Fresno, Calif.	1340	KOMA	Okla. City, Okla.	1520	KRCT	Baytown, Tex.	650
KINS	Eureka, Calif.	980	KMAK	Tulosa, N.Mex.	1590	KOMB	Cottage Grove, Oreg.	1400	KRDE	Redding, Calif.	1230
KINT	El Paso, Tex.	1590	KMAP	Manhattan, Kans.	1350	KOME	Tulsa, Okla.	1520	KRDO	Colorado Springs, Colo.	1240
KINY	Juneau, Alaska	800	KMAQ	Bakersfield, Calif.	1490	KOMS	Seattle, Wash.	1000	KRDU	Dinuba, Calif.	1240
KIOA	Oak Grove, Iowa	940	KMAB	Wasson, Iowa	1320	KOMW	Omaha, Neb.	680			
KIOX	Bay City, Tex.	1270	KMAR	Winnboro, La.	1570	KOMY					

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
KRE	Berkeley, Calif.	1400	KSOX	Raymondville, Tex.	1240	KUGN	Eugene, Oreg.	590	KWKH	Shreveport, La.	1130
KREH	Oakdale, La.	900	KSPA	Santa Paula, Calif.	1400	KUIK	Hillsboro, Oreg.	1360	KWKW	Pasadena, Calif.	1300
KREI	Farmington, Mo.	800	KSPJ	Stillwater, Okla.	780	KUJ	Walla Walla, Wash.	1420	KWKY	Des Moines, Iowa	1150
KREM	Spokane, Wash.	970	KSPD	Dibell, Tex.	1260	KUKI	Ukiah, Calif.	1400	KWLC	Decorah, Iowa	1240
KRED	Indio, Calif.	1400	KSPF	Sandpoint, Idaho	1400	KUKO	Post, Tex.	1370	KWLM	Willmar, Minn.	1540
KRES	St. Joseph, Mo.	1550	KSRA	Salmon, Idaho	960	KUKU	Willow Springs, Mo.	1330	KWMT	Ft. Dodge, Iowa	540
KREW	Sunnyside, Wash.	1230	KSRO	Secorro, N.Mex.	1290	KULA	Honolulu, Hawaii	690	KWNA	Winnemucca, Nev.	1400
KREX	Grand Junction, Colo.	920	KSRQ	Santa Rosa, Calif.	1350	KULE	Ephrata, Wash.	730	KWNO	Winona, Minn.	1230
KRFQ	Owatonna, Minn.	1300	KSRP	Spring, Oreg.	1580	KUM	Idaho Falls, Idaho	1380	KWPA	Worthington, Minn.	730
KRFS	Superior, Ariz.	1600	KSSS	Colorado Springs, Colo.	740	KUMA	Pendleton, Oreg.	1290	KWRB	Glaremore, Mo.	930
KRG	Grand Island, Neb.	1430	KSTT	Sulphur Springs, Tex.	1230	KUNO	Corpus Christi, Tex.	1400	KWDE	Clinton, Okla.	1320
KRGV	Westlake, Tex.	1290	KSTA	Coleman, Tex.	1000	KUOA	Siloam Springs, Ark.	1290	KWEO	Bartlesville, Okla.	1400
KRHD	Duncan, Okla.	1350	KSTB	Breckenridge, Tex.	1430	KUOM	Minneapolis, Minn.	270	KWOR	Worland, Wyo.	1340
KRIB	Mason City, Iowa	1490	KSTL	St. Louis, Mo.	690	KUPI	Idaho Falls, Idaho	980	KWJS	Jefferson City, Mo.	1240
KRIC	Beaumont, Tex.	1450	KSTN	Stockton, Calif.	1420	KURA	Moab, Utah	1450	KWOW	Pomona, Calif.	670
KRIG	Odessa, Tex.	1410	KSTP	St. Paul, Minn.	1500	KURL	Billings, Mont.	730	KWPC	Muscateine, Iowa	860
KRID	McAllen, Tex.	1230	KSTR	Grand Junction, Colo.	1270	KURJ	Edinburg, Tex.	710	KWPM	West Plains, Mo.	1450
KRIZ	Phoenix, Ariz.	1290	KSTV	Davenport, Iowa	1170	KURY	Brookings, Oreg.	910	KWRP	Glaremore, Mo.	1270
KRKC	King City, Calif.	1570	KSTW	St. Joseph, Mo.	1510	KUSD	Vermillion, S.Dak.	690	KWRD	Henderson, Tex.	1470
KRKO	Los Angeles, Calif.	1150	KSUB	Cedar City, Utah	590	KUSH	Cushing, Okla.	1600	KWRE	Warrenton, Mo.	730
KRKO	Everett, Wash.	1380	KSUW	Susanville, Calif.	1240	KUSN	St. Joseph, Mo.	1270	KWRF	Warren, Ark.	860
KRKS	Ridgecrest, Calif.	1240	KSUM	Fairmont, Minn.	1370	KUTI	Yakima, Wash.	980	KWRL	Riverton, Wyo.	1450
KRLA	Pasadena, Calif.	1110	KSUM	Bisbee, Ariz.	1230	KUTY	Palmdale, Calif.	1470	KWRO	Coquille, Oreg.	1450
KRLC	Lewiston, Idaho	1350	KSWA	Richfield, Utah	980	KUVR	Holdrege, Neb.	1380	KWRT	Boonville, Mo.	1370
KRLD	Dallas, Tex.	1080	KSWV	Artesia, N.Mex.	990	KUZN	W. Monroe, La.	1310	KWRW	Guthrie, Okla.	1490
KRLN	Canon City, Colo.	1400	KSWY	Granger, Tex.	1480	KWJ	Wolf Point, Neb.	1240	KWS	Washburn, Wash.	1250
KRLW	Wauwat Ridge, Ark.	1400	KSWJ	Council Bluffs, Iowa	1560	KVCL	Winfield, La.	1270	KWSD	Mid. Shasta, Calif.	620
KRMD	Shreveport, La.	1340	KSWD	Lawton, Okla.	1380	KVCC	Redding, Calif.	600	KWSH	Wetoka-Seminole, Okla.	1260
KRMG	Tulsa, Okla.	740	KSWS	Roswell, N.Mex.	1230	KVEC	San Luis Obispo, Calif.	920			
KRMO	Monett, Mo.	990	KSYC	Yreka, Calif.	1490	KVEL	Vernal, Utah	1250	KWSK	Pratt, Kans.	1570
KRMS	Osage Beach, Mo.	1150	KSYL	Wichita Falls, Tex.	990	KVEN	Ventura, Calif.	1450	KWSO	Waseo, Calif.	1050
KRNO	San Bernardino, Calif.	1240	KSYD	Alexandria, La.	970	KVET	Austin, Tex.	1300	KWST	Barstow, Calif.	1230
KRNR	Roseburg, Oreg.	1490	KTAC	Tacoma, Wash.	850	KVFP	Cortez, Colo.	740	KWTF	Springfield, Mo.	1230
KRNS	Burns, Oreg.	1230	KTAE	Tucson, Ariz.	1260	KVFD	Ft. Dodge, Iowa	1400	KWTV	Waverly, Iowa	1470
KRNS	Des Moines, Iowa	1350	KTAN	Tucson, Ariz.	580	KVGB	Great Bend, Kans.	1590	KWVW	Waterloo, Iowa	1330
KRNY	Kearney, Neb.	1460	KTAR	Phoenix, Ariz.	620	KVHL	Homer, La.	1320	KWKY	Farmington, N.Mex.	960
KROC	Rochester, Minn.	1340	KTAT	Frederick, Okla.	1570	KVSI	Seattle, Wash.	570	KWYN	Wynne, Ark.	1400
KROD	El Paso, Tex.	600	KTBB	Tyler, Tex.	600	KVIC	Victoria, Tex.	1340	KWYD	Sheridan, Wyo.	1410
KROF	Abbeville, La.	960	KTBC	Austin, Tex.	590	KVIM	New Iberia, La.	1360	KWYR	Winner, S.Dak.	1260
KROG	Sonora, Calif.	1450	KTCD	Malden, Mo.	1470	KVIN	Vinita, Okla.	1470	KXSA	Pullman, Wash.	1400
KROP	Brawley, Calif.	1300	KTCE	Porterville, Calif.	1480	KVKM	Monahans, Tex.	1340	KXAR	Hope, Ark.	1490
KROS	Clinton, Iowa	1260	KTCF	Fort Smith, Ark.	1410	KVLC	Cleveland, Tex.	1410	KXEL	Waterloo, Iowa	1540
KROX	Crookston, Minn.	1240	KTCG	Fort Smith, Ark.	1410	KVLC	Little Rock, Ark.	1050	KXFN	Festus, Mo.	1010
KROY	Sacramento, Calif.	1260	KTEE	Carmel, Calif.	1410	KVLG	Alpine, Tex.	1240	KXGE	Mexico, Mo.	1340
KRPL	Moscow, Idaho	1400	KTEE	Walla Walla, Wash.	1490	KVLG	LaGrange, Tex.	1570	KXGI	Ft. Madison, Iowa	1380
KRRV	Sherman, Tex.	910	KTEM	Temple, Tex.	1570	KVLH	Pauls Valley, Okla.	1470	KXGN	Glendive, Mont.	1400
KRSC	Othello, Wash.	1400	KTER	Terrill, Tex.	1570	KVLH	Pauls Valley, Okla.	1470	KXGO	Fargo, N.D.	790
KRSD	Rapid City, S.Dak.	1400	KTFI	Twin Falls, Idaho	1270	KVFA	Fallon, Nev.	1250	KXHA	Helena, Mont.	1400
KRSI	St. Louis Park, Minn.	950	KTFB	Texarkana, Tex.	1480	KVFM	Madonia, Ark.	680	KXIB	Dalhart, Tex.	1410
KRSL	Russell, Kans.	950	KTFE	Brawley, Calif.	1300	KVFN	Flagstaff, Ariz.	690	KXJK	Forrest City, Ark.	950
KRSM	Los Alamos, N.Mex.	1490	KTFH	Thermopolis, Wyo.	1240	KVNC	Winslow, Ariz.	1010	KXLE	Portland, Oreg.	720
KRTN	Raton, N.Mex.	1490	KTHS	Little Rock, Ark.	1090	KVNI	Coeur d'Alene, Idaho	1240	KXLF	Butte, Mont.	1370
KRTR	Thermopolis, Wyo.	1490	KTHT	Houston, Tex.	790	KVNU	Logan, Utah	610	KXLL	Helena, Mont.	1240
KRUN	Ballinger, Tex.	1400	KTHB	Thibodaux, La.	630	KVOC	Casper, Wyo.	1230	KXLM	Great Falls, Mont.	1400
KRUS	Ruston, La.	1490	KTIL	Tillamook, Oreg.	1590	KVOP	Emporia, Kans.	1400	KXLS	Missoula, Mont.	1450
KRUX	Glendale, Ariz.	1360	KTIM	San Rafael, Calif.	1510	KVOL	Lafayette, La.	1330	KXLR	No. Little Rock, Ark.	1150
KRYN	Lexington, Neb.	1010	KTKN	Porterville, Calif.	1450	KVON	Napa, Calif.	1440	KXLL	Clayton, Mo.	1320
KRWQ	Forest Grove, Oreg.	1230	KTKS	Seattle, Wash.	1590	KVOT	Tulsa, Okla.	1170	KXLO	El Centro, Calif.	1230
KRXL	Roseburg, Oreg.	1230	KTKH	Hobart, Okla.	1420	KVOR	Corpus Springs, Colo.	1300	KXOA	Sacramento, Calif.	1470
KRYS	Corpus Christi, Tex.	1360	KTKN	Ketchikan, Alaska	930	KVOS	Odessa, Tex.	1400	KXOL	Ft. Worth, Tex.	1360
KSAC	Manhattan, Kans.	580	KTKR	Taft, Calif.	1310	KVOX	Littlefield, Tex.	1490	KXOX	Sweetwater, Tex.	1240
KSAL	Salina, Kans.	1150	KTKT	Tucson, Ariz.	990	KVOY	Moorhead, Minn.	1280	KXRA	Alexandria, Minn.	1490
KSAM	Huntsville, Tex.	1490	KTKL	Tululuth, La.	1360	KVOZ	Yuma, Ariz.	1400	KXRB	Russellville, Ark.	1490
KSAN	San Francisco, Calif.	1450	KTKM	Tululuth, La.	1360	KVPC	Laredo, Tex.	1490	KXRD	Abbeville, Wash.	1320
KSBB	Salina, Okla.	1380	KTKN	Mtn. Home, Ark.	1450	KVRC	Arkadelphia, Ark.	1220	KXRX	San Jose, Calif.	1500
KSCB	Liberia, Kans.	1270	KTKL	Mtn. Home, Ark.	1450	KVUD	Uvalde, Tex.	1400	KXSG	Golden, Colo.	1250
KSCJ	Sioux City, Iowa	1360	KTKL	Rusk, Tex.	1580	KVUW	Uvalde, Tex.	1400	KXSL	Sioux Falls, S.Dak.	1450
KSCO	Santa Cruz, Calif.	1080	KTKL	Texas City, Tex.	920	KVOX	Littlefield, Tex.	1490	KXSY	Houston, Tex.	1290
KSD	St. Louis, Mo.	530	KTKM	McAlester, Okla.	1400	KVOZ	Laredo, Tex.	1490	KXTC	Clayton, Mo.	1320
KSDA	Redding, Calif.	1400	KTKS	Santa Barbara, Calif.	1230	KVPI	Ville Platte, La.	1050	KXUX	San Jose, Calif.	1500
KSDN	Aberdeen, S.Dak.	930	KTKC	Salta City, Neb.	1400	KVRC	Arkadelphia, Ark.	1220	KXVJ	Golden, Colo.	1250
KSEW	San Diego, Calif.	1450	KTKM	Tacoma, Wash.	1400	KVRE	Edinburg, Tex.	710	KXVL	Sioux Falls, S.Dak.	1450
KSEK	Pocatello, Idaho	930	KTKN	Tacoma, Wash.	1400	KVRS	Rock Springs, Wyo.	1360	KXVY	Houby, Kans.	790
KSEK	Pittsburg, Kans.	1340	KTKO	Jonesboro, La.	920	KVSA	McGehee, Ark.	1220	KXW	Clayton, Mo.	1320
KSEL	Lubbock, Tex.	950	KTKD	Sinton, Tex.	1420	KVSE	Santa Fe, N.Mex.	1260	KYCA	San Francisco, Calif.	1260
KSEM	Moses Lake, Wash.	1470	KTKO	Mankato, Minn.	1590	KVSO	Ardmore, Okla.	1240	KYCA	Prescott, Ariz.	1490
KSEN	Shelby, Mont.	1150	KTKO	Lihue, Hawaii	1490	KVVC	Vernon, Tex.	1480	KYCD	Medford, Oreg.	1230
KSEO	Durant, Okla.	750	KTKO	Oklahoma City, Okla.	1000	KVVM	Show Low, Ariz.	1050	KYME	Boise, Idaho	740
KSET	El Paso, Tex.	1400	KTKD	Henderson, Tex.	1280	KVWD	Cheyenne, Wyo.	1370	KYND	Freshwater, Calif.	630
KSEW	Sitka, Alaska	1400	KTKD	Denver, Colo.	900	KVWE	Washburn, Wash.	1400	KYNG	Bay, Oreg.	1420
KSEY	Seymour, Tex.	1230	KTKD	St. Joseph, Mo.	1510	KVWK	Waukegan, Ill.	1240	KYNT	Yankton, S.Dak.	1450
KSFA	Neacoches, Tex.	860	KTKD	Tulsa, Okla.	1260	KVWL	Wallace, Idaho	620	KYOK	Houston, Tex.	1590
KSFE	Needles, Calif.	1340	KTKD	Tulsa, Okla.	1260	KVWM	Memphis, Tenn.	990	KYOT	Blythe, Calif.	1450
KSFO	San Francisco, Calif.	560	KTKD	Tulsa, Okla.	1260	KVWT	Watertown, S.Dak.	950	KYOS	Merced, Calif.	1480
KSJM	St. Genevieve, Mo.	980	KTKD	Tulsa, Okla.	1260	KWBA	Baytown, Tex.	1360	KYDU	Greely, Colo.	1400
KSIB	Creston, Iowa	1320	KTKD	Tulsa, Okla.	1260	KWBB	Wichita, Kans.	1410	KYFD	Fotosi, Idaho	1280
KSID	Sidney, Neb.	1340	KTKD	Tulsa, Okla.	1260	KWBC	Boone, Iowa	1590	KYGN	Manitou, Minn.	740
KSJ	Crowley, La.	1450	KTKD	Tulsa, Okla.	1260	KWBD	Boone, Iowa	1590	KYNS	Colorado Sprgs., Colo.	1460
KSJG	Gladewater, Tex.	1430	KTKD	Tulsa, Okla.	1260	KWBE	Hutchinson, Kans.	1450	KYSS	Missoula, Mont.	910
KSIL	Silver City, N.Mex.	1340	KTKD	Tulsa, Okla.	1260	KWCB	Searcy, Ark.	1300	KYTE	Pocatello, Idaho	1290
KSIM	Sikeston, Mo.	1400	KTKD	Tulsa, Okla.	1260	KWCL	Oak Grove, La.	1280	KYUM	Yuma, Ariz.	560
KSIR	Wichita, Kans.	900	KTKD	Tulsa, Okla.	1260	KWCO	Chickasha, Okla.	1560	KYVA	Gallup, N.Mex.	1230
KSIS	Sedalia, Mo.	1050	KTKD	Tulsa, Okla.	1260	KWCB	Chickasha, Okla.	1560	KYWC	Cleveland, Ohio	1140
KSIV	Woodward, Okla.	1450	KTKD	Tulsa, Okla.	1260	KWCD	Chickasha, Okla.	1560	KYWD	Windsor, N.C.	1220
KSJW	Corpus Christi, Tex.	1230	KTKD	Tulsa, Okla.	1260	KWCE	Wesley, Idaho	1260	KZEY	Tyler, Tex.	690
KSJB	Jamestown, N.Dak.	600	KTKD	Tulsa, Okla.	1260	KWEL	Midland, Tex.	1600	KZIN	Coeur d'Alene, Idaho	1050
KSJO	San Jose, Calif.	1590	KTKD	Tulsa, Okla.	1260	KWEM	Hobbs, N.Mex.	1480	KZJP	Amarillo, Tex.	1310
KSJY	Dallas, Tex.	660	KTKD	Tulsa, Okla.	1260	KWFR	San Angelo, Tex.	1260	KZOL	Prescott, Ariz.	1340
KSJL	Salt Lake City, Utah	1160	KTKD	Tulsa, Okla.	1260	KWFT	Wichita Falls, Tex.	620	KZML	Mulshoe, Tex.	1570
KSJM	Salem, Oreg.	1390	KTKD	Tulsa, Okla.	1260	KWST	Stockton, Calif.	1230	KZNF	Farmington, N.Mex.	1280
KSLO	Opelousas, La.	1230	KTKD	Tulsa, Okla.	1260	KWTH	Brenham, Tex.	1280	KZON	Opportunity, Wyo.	850
KSJV	Monte Vista, Colo.	1240	KTKD	Tulsa, Okla.	1260	KWTK	Hutchinson, Kans.	1450	KZWA	Winstonsalem, N.C.	940
KSNA	Santa Maria, Calif.	1240	KTKD	Tulsa, Okla.	1260	KWUN	Fort Smith, Ark.	1320	WAAB	Worcester, Mass.	940
KSML	Seminole, Tex.	1250	KTKD	Tulsa, Okla.	1260	KWWD	Salt Lake City, Utah	860	WAAC	Chicago, Ill.	1550
KSNN	Mason City, Iowa	1010	KTKD	Tulsa, Okla.	1260	KWVH	Altus, Okla.	1450	WAAG	Adel, Ga.	1470
KSNO	Salem, Mo.	1340	KTKD	Tulsa, Okla.	1260	KWVW	Salt Lake City, Utah	1570	WAAT	Trenton, N.J.	1300
KSNY	Snyder, Tex.	1450	KTKD	Tulsa, Okla.	1260	KWVX	Pocatello, Idaho	1240	WAAY	Huntsville, Ala.	1550
KSO	Des Moines, Iowa	1460	KTKD	Tulsa, Okla.	1260	KWVY	Albany, Oreg.	790	WABA	Aquadilla, P.Rico	820
KSOA	Arkansas City, Kans.	1280	KTKD	Tulsa, Okla.	1260	KWVZ	Albany, Oreg.	790	WABD	Greenbale, Ala.	780
KSON	San Diego, Calif.	1240	KTKD	Tulsa, Okla.	1260	KWVZ	Albany, Oreg.	790	WABN	White Sulphur Springs, N.Y.	770
KSOO	Sioux Falls, S.Dak.	1140	KTKD	Tulsa, Okla.	1260	KWVZ	Albany, Oreg.	790	WABG	Wagonwheel, Miss.	960
KSP	Salt Lake City, Utah	1370	KTKD	Tulsa, Okla.	1260	KWVZ	Albany, Oreg.	790	WABJ	Bangor, Maine	910
			KTKD	Tulsa, Okla.	1260	KWVZ	Albany, Oreg.	790	WABP	Adrian, Mich.	1490
			KTKD	Tulsa, Okla.	1260	KWVZ	Albany, Oreg.	790	WABL	Amite, La.	1370
			KTKD	Tulsa, Okla.	1260	KWVZ	Albany, Oreg.	790	WABM	Waynesboro, Miss.	990
			KTKD	Tulsa, Okla.	1260	KWVZ	Albany, O				

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WABV	Abbeville, S.C.	1590	WAVE	Louisville, Ky.	970	WBRM	Marion, N.C.	1250	WCNT	Centralia, Ill.	1210
WABW	Annapolis, Md.	810	WAVF	Dayton, Ohio	1210	WBRN	Big Rapids, Mich.	1480	WCNU	Crestview, Fla.	1010
WABY	Albany, N.Y.	1400	WAVL	Apollo, Pa.	910	WBRT	Waynesboro, Ga.	1310	WCNX	Middletown, Conn.	1150
WABZ	Albemarle, N.C.	1010	WAVM	Stillwater, Minn.	1220	WBRO	Bardonia, Ky.	1320	WCOA	Pensacola, Fla.	1370
WACA	Camden, S.C.	1590	WAVO	Avondale Estates, Ga.	1420	WBRY	Boonville, N.Y.	900	WCOG	Meridian, Miss.	910
WACB	Kittanning, Pa.	1380	WAVP	Avon Park, Fla.	1390	WBXX	Berwick, Pa.	1280	WCOG	Greensboro, N.C.	1320
WACE	Chicopee, Mass.	730	WAVU	Albertville, Ala.	630	WBRY	Waterbury, Conn.	1590	WCOP	Newnan, Ga.	1400
WACK	Newark, N.Y.	1420	WAVY	Partsmouth, Va.	1530	WBSC	Bennettsville, S.C.	1550	WCOT	Covington, Ohio	1420
WACL	Wayne, Pa.	1300	WAVZ	New Haven, Conn.	1800	WBST	Westfield, Mass.	1500	WCOW	Columbus, Ohio	1290
WACO	Waco, Tex.	1460	WAWK	Kendallville, Ind.	1570	WBSR	Pensacola, Fla.	1450	WCOR	Cornelia, Ga.	1450
WACR	Columbus, Miss.	1050	WAWX	Zarephath, N.J.	1380	WBTA	Charlotte, N.C.	1110	WCOP	Boston, Mass.	1150
WACT	Tuscaloosa, Ala.	1420	WAXE	Vero Beach, Fla.	1370	WBTA	Batavia, N.Y.	1490	WCOR	Lebanon, Tenn.	1900
WADA	Shelby, N.C.	1390	WAXX	Chippewa Falls, Wis.	1150	WBTH	Williamson, W.Va.	1400	WCOS	Alma, Ga.	1300
WADC	Akron, Ohio	1350	WAYB	Waynesboro, Va.	1490	WBTH	Farmville, N.C.	1050	WCOW	Lewiston, Maine	1240
WADE	Wadesboro, N.C.	1210	WAVE	Oundak, Md.	860	WBVM	Danville, Va.	1390	WCOW	Montgomery, Ala.	1170
WADK	Newport, R.I.	1540	WAVN	Rockingham, N.C.	900	WBVN	Bennington, Vt.	1370	WCOW	Sparta, Wis.	1290
WADD	New York, N.Y.	1280	WAWB	Charlotte, N.C.	610	WBTO	Linton, Ind.	800	WCOW	Columbia, Pa.	1580
WADP	Kane, Pa.	960	WAYX	Waycross, Ga.	1230	WBUD	Trouton, N.J.	1260	WCPC	Clearfield, Pa.	900
WADS	Ansonia, Conn.	690	WAYZ	Waynesboro, Pa.	1380	WBUT	Butler, Pa.	1050	WCPC	Houston, Miss.	1320
WAEB	Allentown, Pa.	790	WAZA	Bainbridge, Ga.	1380	WBUX	Doylestown, Pa.	1570	WCPC	Etowah, Tenn.	1210
WAEL	Mayaguez, P.Rico	600	WAZF	Yazoo City, Miss.	1230	WBUX	Lexington, N.C.	1440	WCPC	College Park, Ga.	1570
WAEW	Crossville, Tenn.	1330	WAZL	Hazelton, Pa.	1490	WBUZ	Fredonia, N.Y.	1570	WCPC	Cumberland, Ky.	1280
WAFG	Staunton, Va.	900	WBAE	West Lafayette, Ind.	920	WBVL	Barboursville, Ky.	1250	WCPO	Cincinnati, Ohio	1230
WAGC	Chattanooga, Tenn.	1490	WBAJ	Bayton, N.Y.	1440	WBVF	Beaver Falls, Pa.	930	WCPS	Tarboro, N.C.	760
WAGE	Leesburg, Va.	1290	WBAC	Charlotte, N.C.	1340	WBVE	Cary, N.C.	1290	WCRC	Elmhurst, Ill.	1090
WAGF	Dothan, Ala.	1320	WBAL	Baltimore, Md.	1090	WBVS	Canton, Ill.	1560	WCRC	Birmingham, Mass.	1330
WAGG	Franklin, Tenn.	950	WBAM	Montgomery, Ala.	740	WBZ	Boston, Mass.	1030	WCRC	Wareham, Mass.	1420
WAGM	Presque Isle, Maine	1450	WBAP	Ft. Worth, Tex.	570, 820	WBZA	Springfield, Mass.	1030	WCRI	Scottsboro, Ala.	1050
WAGN	Menominee, Mich.	1340	WBAR	Bartow, Fla.	1460	WBZZ	Torreyton, Conn.	990	WCRC	Morrisville, Tenn.	1150
WAGR	Lumberton, N.C.	580	WBAT	Marion, Ind.	1400	WCAC	Northfield, Pa.	1250	WCRL	Ooneota, Ala.	1570
WAGS	Bishopville, S.C.	1380	WBAX	Wilkes-Barre, Pa.	1240	WCAL	Northfield, Minn.	770	WCRO	Johnstown, Pa.	1230
WAGY	Forest City, N.C.	1320	WBAY	Warwick, S.C.	740	WCAM	Canton, N.J.	1310	WCRR	Corinth, Miss.	1380
WAIK	Gatesburg, Ill.	1590	WBAY	Bay, Wis.	1360	WCAN	Baltimore, Md.	1800	WCRR	Clinton, S.C.	1260
WAIL	Baton Rouge, La.	1460	WBBA	Pittsfield, Ill.	1580	WCAP	Lowell, Mass.	980	WCRT	Birmingham, Ala.	1260
WAIM	Anderson, S.C.	1230	WBBB	Burlington, N.C.	920	WCAR	Detroit, Mich.	1190	WCRT	Washington, N.J.	1580
WAIN	Columbia, Ky.	1270	WBBC	Rochester, N.Y.	950	WCAS	Gadsden, Ala.	1570	WCRT	Chicago, Ill.	1240
WAIP	Prichard, Ala.	1270	WBBI	Abingdon, Va.	1230	WCAT	Orange, Mass.	1390	WCRT	Macon, Ga.	1900
WAIR	Winston-Salem, N.C.	1340	WBBL	Richmond, Va.	1480	WCAU	Philadelphia, Pa.	1210	WCSC	Charleston, S.C.	1390
WAIT	Chicago, Ill.	820	WBBM	Chicago, Ill.	780	WCAW	Charleston, W.Va.	1300	WCSP	Portland, Maine	970
WAJF	Decorah, Ala.	1540	WBBO	Chicago, Ill.	980	WCAX	Guttenberg, Vt.	620	WCSP	Columbus, Ind.	1010
WAJR	Morgantown, W.Va.	1440	WBBO	Forest City, N.C.	780	WCAY	Cayce, S.C.	820	WCSP	Wilmington, N.C.	1040
WAKE	Atlanta, Ga.	1340	WBBO	Augusta, Ga.	1340	WCAZ	Carthage, Ill.	990	WCSS	Amsterdam, N.Y.	1490
WAKN	Aiken, S.C.	990	WBBL	Lyons, Ga.	1340	WCBA	Corning, N.Y.	1350	WCST	Berkeley Springs, W.Va.	1010
WAKO	Lawrenceville, Ill.	910	WBBS	Youngstown, Ohio	1240	WCBB	Anderson, Ind.	1470	WCST	Andalusia, Ala.	920
WAKR	Akron, Ohio	1590	WBBS	Ponca City, Okla.	1230	WCBB	Chambersburg, Pa.	1590	WCST	New Brunswick, N.J.	1450
WAKU	Latrobe, Pa.	1570	WBBC	Bay Minette, Ala.	1150	WCBI	Columbus, Miss.	550	WCST	Corbin, Ky.	680
WAKY	Louisville, Ky.	790	WBBC	Levittown, Pa.	1490	WCBL	Benton, Ky.	1290	WCST	Wiscasset, Wis.	880
WALA	Mobile, Ala.	1410	WBCC	Chickasha, Okla.	1380	WCBO	Freemont, Mich.	1490	WCUE	Akron, Ohio	1150
WALB	Albany, Ga.	1590	WBCC	Battle Creek, Mich.	930	WCBS	New York, N.Y.	1480	WCUM	Cumberland, Md.	1250
WALD	Waterboro, S.C.	1220	WBCC	Bay City, Mich.	1440	WCBS	New York, N.Y.	1480	WCVA	Culpeper, Va.	1490
WALE	Fall River, Mass.	1400	WBCC	Christiansburg, Va.	1260	WCBT	Roanoke Rapids, N.C.	1230	WCVI	Connettsville, Pa.	1340
WALK	Pathogue, N.Y.	1370	WBCC	Union, S.C.	1460	WCBY	Cheboygan, Mich.	1240	WCVP	Murphy, N.C.	600
WALL	Middletown, N.Y.	1340	WBCC	Pittsfield, Mass.	1420	WCCE	Hartford, Conn.	1290	WCVS	Springfield, Ill.	1450
WALL	Albion, Mich.	1260	WBCE	Harvey, Ill.	1570	WCCL	Lawrence, Mass.	800	WCVC	Wichita, Wis.	1040
WALM	Humas, P.R.	1240	WBCE	Belleville, Tenn.	1240	WCEN	St. Louis, Mo.	930	WCVC	Crystal Lake, Ill.	690
WALT	Tampa, Fla.	1110	WBCE	Beloit, Wis.	1380	WCEN	Minneapolis, Minn.	830	WCVC	Bryant, Va.	1400
WALY	Herkimer, N.Y.	1420	WBEN	Buffalo, N.Y.	930	WCEN	Savannah, Ga.	1450	WCVC	Chattanooga, Ky.	1400
WAMD	Aberdeen, Md.	970	WBET	Brookton, Mass.	1460	WCEN	Cardanole, Pa.	1440	WCVC	Indiana, Pa.	1450
WAME	Miami, Fla.	1260	WBET	Beaufort, S.C.	960	WCEN	Edenton, N.C.	1260	WCVC	Tampa, Fla.	1250
WAMI	Opp, Ala.	860	WBET	Beaver Dam, Wis.	1430	WCEN	Winchester, Tenn.	1310	WCVC	Kansas City, Mo.	610
WAML	Laurel, Miss.	1340	WBEX	Chillicothe, Ohio	1490	WCEN	Rocky Mount, N.C.	810	WCVC	Columbus, Ga.	540
WAMN	Flint, Mich.	1410	WBEX	Hartford, Pa.	1410	WCED	DuBois, Pa.	1420	WCVC	Rock Hill, S.C.	1380
WAMR	Homestead, Pa.	860	WBEX	Chickasha, Okla.	1370	WCED	Hawkinsville, Ga.	1410	WCVC	Danville, Va.	1490
WAMP	Pittsburgh, Pa.	1320	WBGR	Jessup, Ga.	1240	WCEN	Cambridge, Md.	1240	WCVC	Darlington, S.C.	1550
WAMS	Wilmington, Del.	1380	WBHB	Fitzgerald, Ga.	1240	WCEN	Met Pleasant, Mich.	1150	WCVC	Philadelphia, Pa.	1480
WAMV	E. St. Louis, Ill.	1490	WBHC	Hampton, S.C.	1270	WCER	Charlotte, Mich.	1390	WCVC	McRae, Ga.	1410
WAMW	Washington, Ind.	1580	WBHF	Cartersville, Ga.	1450	WCFL	Chicago, Ill.	1000	WCVC	Fargo, N. Dak.	970
WAMY	Amery, Miss.	1580	WBHU	Huntsville, Ala.	1230	WCFR	Springfield, Vt.	1480	WCVC	Escanaba, Mich.	680
WANA	Ansonia, Ala.	1490	WBIA	Augusta, Ga.	1230	WCFT	Clifton Forge, Va.	1230	WCVC	Delray Beach, Fla.	1420
WANB	Waynesboro, Pa.	1580	WBIB	Bay, Wis.	1360	WCFC	Galveston, Tex.	960	WCVC	Wilmington, Mich.	1490
WAND	Canton, Ohio	900	WBIG	Greensboro, N.C.	1470	WCFC	Belmont, N.C.	1270	WCVC	Springfield, Tenn.	1590
WANE	Ft. Wayne, Ind.	1450	WBIL	Leesburg, Fla.	1410	WCFA	Chambersburg, Pa.	800	WCVC	Statesville, N.C.	550
WANN	Annapolis, Md.	1910	WBIP	Booneville, Miss.	1400	WCHE	Instker, Mich.	1440	WCVC	Oriando, Fla.	580
WANS	Anderson, S.C.	1280	WBIR	Knoxville, Tenn.	1240	WCHE	Chillicothe, Ohio	1350	WCVC	Dubuque, Iowa	1490
WANT	Richmond, Va.	990	WBIS	Bristol, Conn.	1440	WCHE	Brookhaven, Miss.	1470	WCVC	Dade City, Fla.	1350
WANU	Albany, Ky.	1390	WBIV	Bedford, Ind.	1360	WCHE	Canton, Ga.	1290	WCVC	Tarpon Springs, Fla.	1470
WAPA	Altoona, Pa.	1340	WBIV	Bedford, Wis.	1490	WCHE	Washington Court House, Ohio	1250	WCVC	Wilmington, Del.	1150
WAQV	Vincennes, Ind.	1450	WBKH	Hattiesburg, Miss.	950	WCHE	Washington Court House, Ohio	1250	WCVC	Greenville, Miss.	900
WAPA	San Juan, P.R.	680	WBKN	Newton, Miss.	1410	WCHE	Chapel Hill, N.C.	1360	WCVC	Gloucester, Va.	1420
WAPF	Jacksonville, Fla.	690	WBKV	West Bend, Wis.	1470	WCHE	Norwich, N.Y.	970	WCVC	Ellsworth, Me.	1350
WAPG	McComb, Miss.	980	WBLE	Elizabethtown, N.C.	1450	WCHE	Charleston, W.Va.	580	WCVC	Americus, Ga.	1290
WAPF	Arcadia, Fla.	1480	WBLE	Batesville, Miss.	1290	WCHE	Charlottesville, Va.	1260	WCVC	Chattanooga, Tenn.	1370
WAPL	Birmingham, Ala.	1070	WBLE	Bellefonte, Pa.	1330	WCHE	Carbondale, Ill.	1020	WCVC	Highland, Tenn.	800
WAPL	Apex, Wis.	1570	WBLO	Lexington, Ky.	1300	WCHE	Cincinnati, Ohio	1480	WCVC	Wilmington, Del.	1150
WAPD	Chattanooga, Tenn.	1150	WBLO	Dalton, Ga.	1290	WCHE	Columbia, Miss.	1450	WCVC	Waterbury, Vt.	550
WAPX	Montgomery, Ala.	1800	WBLO	Evergreen, Ala.	1470	WCHE	Dunn, N.C.	780	WCVC	Westfield, Mass.	1570
WAQE	Towson, Md.	1570	WBLO	Batesburg, S.C.	1430	WCHE	Kear, S.C.	1300	WCVC	Minneapolis, Minn.	1130
WARA	Attleboro, Mass.	1320	WBLO	Bedford, Va.	1350	WCHE	Miami, Fla.	1610	WCVC	Memphis, Tenn.	1070
WARB	Covington, La.	730	WBLO	Salmon, Va.	1480	WCHE	Cincinnati, Ohio	1530	WCVC	Dothan, Ala.	1450
WARD	Johnstown, Pa.	1490	WBLY	Springfield, Ohio	1600	WCHE	Claxton, Ga.	1470	WCVC	Orangeburg, S.C.	1150
WARE	Ware, N.J.	1250	WBLY	Springfield, N.C.	1400	WCHE	Jackson, Ga.	1420	WCVC	Clinton, Tenn.	1280
WARF	Jasper, Ala.	1240	WBMC	Memphis, Tenn.	960	WCHE	Camden, S.C.	1260	WCVC	Dickson, Tenn.	1260
WARK	Hagerstown, Md.	1490	WBMD	Baltimore, Md.	750	WCHE	Cleveland, Miss.	1490	WCVC	Walton, N.Y.	1270
WARL	Arlington, Va.	780	WBMK	West Point, Ga.	1310	WCHE	Cleveland, Tenn.	1570	WCVC	Marshallfield, Wis.	1450
WARM	Seranton, Pa.	590	WBML	Macon, Ga.	1240	WCHE	Morgantown, W.Va.	1350	WCVC	Port Jervis, N.Y.	1490
WARN	Ft. Pierce, Fla.	1330	WBML	Conway, N.H.	1050	WCHE	Corning, N.Y.	1450	WCVC	Indianola, Miss.	1380
WARU	Peru, Ind.	1600	WBML	Boonville, Ind.	1540	WCHE	Janesville, Wis.	1230	WCVC	Parma City, Fla.	580
WASA	Hartsville, Grace, Md.	1330	WBML	Columbus, Ohio	1460	WCHE	Columbus, Ga.	1580	WCVC	Burlington, N.C.	1490
WASK	Lafayette, Ind.	1450	WBML	Union, S.C.	1310	WCHE	Chickasha, Okla.	1430	WCVC	Wilmington, N.C.	860
WATA	Boone, N.C.	1450	WBNN	New York, N.Y.	1380	WCHE	Mansfield, Ohio	1370	WCVC	Marquette, Mich.	1320
WATC	Gaylord, Mich.	900	WBNU	Buffalo, N.Y.	1400	WCHE	Corinth, Miss.	1230	WCVC	Durham, N.C.	620
WATE	Knoxville, Tenn.	620	WBON	Galax, Va.	1380	WCHE	Harrisburg, Pa.	1430	WCVC	Elkins, W.Va.	1240
WATH	Athens, Ohio	970	WBOS	Salisbury, Md.	960	WCHE	Wildwood, N.J.	1260	WCVC	Ansonia, Ala.	1450
WATK	Antigo, Wis.	900	WBOS	Virginia Beach, Va.	1600	WCHE	Brunswick, Maine	900	WCVC	Clinton, Tenn.	1280
WATM	Altoona, Pa.	1240	WBOS	New Orleans, La.	800	WCHE	Ashtland, Ky.	1340	WCVC	Canton, Ga.	1370
WATN	Watertown, N.Y.	1240	WBOS	Marion, N.C.	980	WCHE	Arden, N.C.	1280	WCVC	Prentissburg, Ky.	1310
WATP	Oak Ridge, Tenn.	1290	WBOS	Brookline, Mass.	1800	WCHE	Pine City, Minn.	1350	WCVC	Chattanooga, Tenn.	1310
WATQ	Marion, S.C.	1430	WBOS	Terre Haute, Ind.	1230	WCHE	Elkhart, Ind.	1270	WCVC	Dunkirk, N.Y.	1410
WATR	Waterbury, Conn.	1320	WBOS	Bogalusa, La.	920	WCHE	Norfolk, Va.	1050	WCVC	Marine City, Mich.	1590
WATS	Sayre, Pa.	960	WBOS	Clarksburg, W.Va.	1400	WCHE	Martin, Tenn.	1410	WCVC	Cleveland, Ohio	1260
WATT	Cadillac, Mich.	1240	WBPD	Orangeburg, S.C.	1580	WCHE	Camden, Ohio	1060	WCVC	Athens, Ga.	1470
WATV	Birmingham, Ala.	900	WBPD	Lock Haven, Pa.	1230	WCHE	Ottawa, Ill.	1430	WCVC	Wheaton, Md.	1540
WATW	Wilmington, N.C.	1400	WBPD	Chickasha, Okla.	1380	WCHE	Ashtland, Ky.	1340	WCVC	Sturgeon Bay, Wis.	910
WATZ	Alpena, Mich.	1450	WBRC	Birmingham, Ala.	960	WCHE	Chickasha, Okla.	1430	WCVC	New York, N.Y.	730
WAUC	Wauchaula, Fla.	1310	WBRO	Bradenton, Fla.	1420	WCHE	Elizabeth City, N.C.	1240	WCVC	Dorchester, Va.	1400

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WDDV	Dover, Del.	1410	WETZ	New Martinsville, West Virginia	1330	WGEE	Indianapolis, Ind.	1590	WHIM	E. Providence, R.I.	1110
WDM	Duquoin, Ill.	1580	WEUC	Ponce, P.R.	1420	WGEH	Quincy, Ill.	1440	WHIN	Gallatin, Tenn.	1010
WDRC	Hartford, Conn.	1560	WEUP	Huntsville, Ala.	1600	WGEC	Chicago, Ill.	1390	WHIO	Dayton, Ohio	1260
WDRF	Chester, Pa.	1590	WEVA	Emporia, Va.	860	WGET	Gettysburg, Pa.	1450	WHIP	Mooreville, N.C.	1550
WDSC	Dillon, S.C.	800	WEVD	New York, N.Y.	1930	WGEZ	Beloit, Wis.	1490	WHIR	Danville, Ky.	1230
WDSG	Dyersburg, Tenn.	1450	WEVE	Evelet, Minn.	1340	WGFS	Covington, Ga.	1430	WHIS	Bluefield, W.Va.	1440
WDSK	Cleveland, Miss.	1410	WEW	St. Louis, Mo.	770	WGG	Gainesville, Ga.	550	WHIT	New Bern, N.C.	1450
WDSM	Superior, Wis.	1210	WEWO	Laurinburg, N.C.	1080	WGGH	Gainesville, Fla.	1230	WHY	Orlando, Fla.	1270
WOSP	DeFuniak Springs, Florida	780	WEWU	Wayne, Mich.	1340	WGGI	Marion, Ill.	1150	WHZ	Zanesville, Ohio	1240
WDSR	Lake City, Fla.	1340	WEY	Sanford, N.C.	1290	WGO	Salamanca, N.Y.	1510	WHJB	Greensburg, Pa.	820
WDSU	New Orleans, La.	1280	WEZB	Bessemer, Ala.	1450	WGOA	Newport Nws, Va.	1310	WHJC	Catawba, W.Va.	150
WDTV	St. John, V.I.	1190	WEZE	Boston, Mass.	1260	WGHM	Skowegan, Maine	1150	WHK	Cleveland, Ohio	1420
WDUN	Gainesville, Ga.	1240	WEZI	Williamsburg, Ky.	1440	WGHN	Grd. Haven, Mich.	1370	WHKK	Akron, Ohio	640
WDX	Waupaca, Wis.	800	WEZL	Richmond, Va.	1590	WGHQ	Saugerties, N.Y.	920	WHKP	Hendersonville, N.C.	1450
WDZ	Green Bay, Wis.	1400	WEZN	Elizabethtown, Pa.	1600	WGI	Brunswick, Ga.	1440	WHKY	Hickory, N.C.	1290
WDVA	Danville, Va.	1250	WF	Cocoa, Fla.	1480	WGL	Galesburg, Ill.	1400	WHLB	Virginia, Minn.	1400
WDVH	Gainesville, Fla.	980	WFA	Dallas, Tex.	570, 820	WGM	Manchester, N.H.	610	WHLF	Niagara Falls, N.Y.	1270
WDVL	Vineland, N.J.	1270	WFAH	Alliance, Ohio	1310	WGN	Charlotte, N.C.	1600	WHLS	South Boston, Va.	1400
WDVM	Pocomoke City, Md.	540	WFAI	Albany, N.Y.	1470	WGA	Atlanta, Ga.	1600	WHLL	Hempstead, N.Y.	1100
WDWD	Dawson, Ga.	990	WFAJ	White Plains, N.Y.	1230	WGV	Charleston, W.Va.	1300	WHLM	Wheeling, W.Va.	600
WDWS	Champaign, Ill.	1400	WFAK	Augusta, Me.	1340	WGL	Fort Wayne, Ind.	1250	WHLN	Bloomburg, Pa.	1550
WDXB	Chattanooga, Tenn.	1490	WFAZ	Falls Church, Va.	1220	WGLC	Centerville, Miss.	1580	WHLP	Harlan, Ky.	1410
WDXE	Lawrenceburg, Tenn.	1370	WF	Greenville, S.C.	1330	WGLD	Babylon, N.Y.	1290	WHLS	Port Huron, Mich.	1450
WDXL	Jackson, Tenn.	1310	WFB	Albany, N.Y.	1390	WGMA	Hollywood, Fla.	1320	WHLT	Huntington, Ind.	1300
WDXM	Jacksoning, Tenn.	1480	WFB	Syracuse, N.Y.	1390	WGMG	Washington, D.C.	370	WHMA	Anniston, Ala.	1390
WDXN	Clarksville, Tenn.	540	WFBM	Indianapolis, Ind.	1260	WGN	Chicago, Ill.	720	WHMC	Hartford, Conn.	1450
WDXP	Paducah, Ky.	1560	WFB	Baltimore, Md.	1300	WGN	Wilmington, N.C.	1450	WHMP	Northampton, Mass.	400
WDZ	Decatur, Ill.	1050	WFB	Flt. Walton Beh., Fla.	950	WGN	Murfreesboro, Tenn	1450	WHMS	Charleston, W.Va.	490
WEAB	Greer, S.C.	800	WFD	Flint, Mich.	910	WGO	Walhalla, S.C.	1460	WHNC	Henderson, N.C.	890
WEAG	Alcoa, Tenn.	1470	WFD	Manchester, Ga.	1370	WGOH	Grayson, Ky.	1370	WHNY	McComb, Miss.	1250
WEAM	Arlington, Va.	1390	WFD	St. Helen, Mich.	1590	WGH	Mobile, Ala.	900	WHOD	Des Moines, Iowa	1040
WEAN	Providence, R.I.	790	WFE	St. Albans, Vt.	1340	WGO	Goldboro, N.C.	1300	WHOA	San Juan, P.R.	400
WEAQ	Eau Claire, Wis.	790	WFE	St. Albans, Vt.	1340	WGO	Georgetown, Ky.	1590	WHOP	Hawley, Mich.	1380
WEAT	W. Palm Beach, Fla.	850	WFE	Miami, Fla.	1220	WGP	Valdosta, Ga.	950	WHDK	Ladwell, Ohio	1320
WEAV	Plattsburgh, N.Y.	960	WFG	Fitchburg, Mass.	960	WGP	Bethlehem, Pa.	1100	WHOL	Allentown, Pa.	600
WEAW	Evanston, Ill.	1330	WFG	Gaffney, S.C.	1570	WGPC	Albany, Ga.	1450	WHOM	New York, N.Y.	1480
WEBC	Baltimore, Md.	1360	WFH	Bristol, Va.	980	WGR	Buffalo, N.Y.	550	WHOO	Orlando, Fla.	990
WEBS	Duluth, Minn.	560	WFH	Pell City, Ala.	1430	WGR	Cairo, Ga.	790	WHOP	Hopkinsville, Ky.	1230
WEBJ	Brewton, Ala.	1240	WFH	Wis. Rapids, Wis.	1340	WGR	Green Cove Springs, Florida	1580	WHOS	Decatur, Ohio	800
WEBL	Dwago, N.Y.	1240	WFI	Philadelphila, Pa.	560	WGR	Grand Rapids, Mich.	1410	WHOT	Campbell, Ohio	1570
WEBC	Harrisburg, Ill.	1240	WF	Findlay, Ohio	1330	WGR	Aguadella, P.R.	1340	WHOU	Waukegan, Ill.	1410
WEBR	Buffalo, N.Y.	970	WF	Fountain Inn, S.C.	1600	WGR	Greenwood, Miss.	1240	WHOW	Clinton, Ill.	1520
WEBY	Milton, Fla.	1330	WF	Fairfield, Ill.	1390	WGR	Lake City, Fla.	960	WHPP	Harrisburg, Pa.	580
WECL	Eau Claire, Wis.	1050	WF	Franklin, Ky.	1220	WGR	Greeneville, Tenn.	1340	WHPE	High Point, N.C.	1070
WECC	Chicago, Ill.	1240	WF	Franklin, Ky.	1220	WGR	Greeneville, Tenn.	1340	WHPT	Belton, S.C.	1390
WECD	McKeesport, Pa.	810	WF	Tampa, Fla.	970	WGR	Greeneville, Tenn.	1340	WHRE	Hartsville, Ala.	860
WEDE	Birmingham, Ala.	1220	WFL	Fayetteville, N.C.	1490	WGS	Savannah, Ga.	1400	WHRV	Ann Arbor, Mich.	1600
WEDE	Southwest, N.C.	1220	WFL	Philadelphia, Pa.	900	WGS	Huntington, N.Y.	740	WHRW	Bowling Green, Ohio	730
WEED	Rocky Mount, N.C.	1390	WFL	Farmville, Va.	870	WGS	Millen, Ga.	1570	WHSA	Hawley, Mich.	1380
WEEL	Boston, Mass.	590	WFL	Dundee, N.Y.	1570	WGS	Atlanta, Ga.	920	WHSM	Hayward, Wis.	910
WEEL	Peoria, Ill.	1350	WFL	Monticello, Ky.	1360	WGS	Guntersville, Ala.	1270	WHSY	Hattiesburg, Miss.	1250
WEEM	Fairfax, Va.	1310	WFL	Waldorf, Md.	730	WGS	Greenwood, S.C.	1350	WHTC	Holland, Mich.	1430
WEEN	Lafayette, Tenn.	1460	WFM	Frederic, Md.	930	WGT	Summerville, Ga.	950	WHTE	Eatontown, N.J.	1410
WEEP	Plattsburgh, Pa.	1080	WFM	Cullman, Ala.	1460	WGTC	Greenville, N.C.	1590	WHU	Cookeville, Tenn.	1400
WEER	Warrenton, Va.	1570	WFM	Youngstown, Ohio	1390	WGTL	Kannapolis, N.C.	870	WHUC	Hudson, N.Y.	1230
WEEX	Reading, Pa.	1230	WFM	Fairmont, N.C.	860	WGTN	Georgetown, S.C.	1400	WHUD	Reading, Pa.	1340
WEU	Easton, Pa.	1230	WFM	Madisonville, Ky.	730	WGTN	Georgetown, S.C.	1400	WHUN	Huntington, Pa.	1150
WEGD	Concord, N.C.	1410	WFNC	Fayetteville, N.C.	1390	WGT	Cypress Gardens, Fla.	540	WHVF	Wausau, Wis.	1250
WEHH	Elmira Heights-Horseheads, N.Y.	1590	WFNS	Burlington, N.C.	1150	WGUN	Deatur, Ga.	1010	WHVH	Henderson, N.C.	1430
WEIC	Charleston, Ill.	1270	WFO	Wreston, Ohio	1430	WGUS	North Augusta, S.C.	1600	WHVR	Hanover, Pa.	1280
WEIC	Fitchburg, Mass.	1280	WFO	Marietta, Ga.	1230	WGU	Bangor, Maine	1250	WHWB	Rutland, Vt.	1000
WEIR	Weymouth, Va.	630	WFD	Hattiesburg, Miss.	1400	WGV	Geneva, N.Y.	1240	WHYE	Roanoke, Va.	910
WEJL	Seranton, Pa.	630	WFO	Milwaukee, Wis.	860	WGV	Greenville, Miss.	1250	WHYL	Carlisle, Pa.	960
WEKR	Fayetteville, Tenn.	1240	WFD	St. Augustine, Fla.	1240	WGW	Selma, Ala.	1340	WHYM	Reading, Mass.	1340
WEKY	Richmond, Ky.	1340	WFP	Fort Payne, Ala.	1450	WGW	Asheboro, N.C.	1260	WHYS	Ocala, Fla.	1370
WEKZ	Monroe, Wis.	1260	WFP	Atlantic City, N.J.	1450	WGY	Schenectady, N.Y.	810	WIAC	San Juan, P.R.	580
WELE	Elba, Ala.	1350	WFR	Fort Riley, Ga.	1150	WGV	Greenville, Ala.	1380	WIAM	Williamston, N.C.	900
WELC	Welch, W.Va.	1150	WFR	Hammond, La.	1400	WHA	Madison, Wis.	970	WIB	Madison, Wis.	1310
WELF	Fisher, N.Y.	690	WFR	Franklin, Pa.	1430	WHAB	Baxley, Ga.	1260	WIBB	Macon, Ga.	1280
WELE	S. Daytona, Fla.	1590	WFR	Frostburg, Md.	740	WHAG	Greenfield, Mass.	1240	WIBC	Indianapolis, Ind.	1070
WELI	New Haven, Conn.	960	WFR	Reidsville, N.C.	1600	WHAL	Rosier City, Mich.	930	WIBD	Midlandville, Pa.	950
WELK	Charlotteville, Va.	1010	WFR	Freeport, Ill.	600	WHAM	Shelbyville, Tenn.	1400	WIBM	Wilmington, Pa.	1300
WELL	Battle Creek, Mich.	1400	WFR	Fremont, Ohio	900	WHAP	Hopewell, Va.	1340	WIBU	Baton Rouge, La.	990
WELM	Elmira, N.Y.	1400	WFR	West Frankfort, Ill.	1300	WHAR	Hopewell, Va.	1340	WIBV	Poynette, Wis.	1240
WELP	Tupelo, Miss.	580	WFS	Franklin, N.C.	1050	WHAS	Louisville, Ky.	840	WIBW	Belleville, Ill.	1260
WELT	Easley, S.C.	1360	WFS	Caribou, Maine	600	WHAT	Philadelphia, Pa.	1340	WIBX	Topeka, Kans.	580
WELU	Roanoke, Va.	1360	WFT	Kinston, N.C.	960	WHB	Philadelphia, Pa.	1340	WIBY	Utica, N.Y.	950
WELS	Kinston, N.C.	1010	WFT	London, Ky.	1400	WHB	Wilmington, Mass.	1490	WICA	Ashtabula, Ohio	970
WELY	Eiv, Minn.	1450	WFT	L. Landerdale, Fla.	1400	WHB	Weston, W.Va.	980	WICB	Wilmington, Conn.	600
WELZ	Belzoni, Miss.	1460	WFT	Front Royal, Va.	1450	WHAY	New Britain, Conn.	910	WICE	Providence, R.I.	1290
WEMB	Erwin, Tenn.	1420	WFT	Front Royal, Va.	1450	WHAZ	Troy, N.Y.	1330	WICH	Norwich, Conn.	1310
WEMP	Milwaukee, Wis.	1250	WFTW	Fl. Walton Beach, Florida	1260	WHB	Kansas City, Mo.	710	WICR	Seranton, Pa.	1400
WENA	Bayamon, P.R.	1560	WFUL	Fulton, Ky.	1270	WHBB	Selma, Ala.	1490	WICU	Salisbury, Md.	1320
WENC	Whiteville, N.C.	1220	WFUN	Huntsville, Ala.	1450	WHBC	Canton, Ohio	1480	WICU	Erie, Pa.	1390
WEND	Baton Rouge, La.	1360	WFUN	Huntsville, Ala.	1450	WHBD	Rock Island, Ill.	1270	WICU	Malone, N.Y.	1490
WENE	Endicott, N.Y.	1430	WFR	Grand Rapids, Mich.	1570	WHBI	Newark, N.J.	1350	WIDU	Wilmington, R.I.	1600
WENK	Union City, Tenn.	1240	WFR	Fredonia, Va.	1460	WHBL	Sheboygan, Wis.	1330	WIEF	Fayetteville, N.C.	1600
WENN	Home Wood, Ala.	1320	WFG	Quincy Sprngs, N.C.	1460	WHBL	Sheboygan, Wis.	1330	WIEL	Elizabethtown, Ky.	1400
WENO	Madison, Tenn.	1430	WFW	Camden, Tenn.	1220	WHBN	Harrodsburg, Ky.	1420	WIFM	Elkin, N.C.	1540
WENT	Gloversville, N.Y.	1340	WFC	Alma, Mich.	1280	WHBO	Tampa, Fla.	1050	WIGM	Medford, Wis.	1490
WENY	Elmira, N.Y.	1230	WFC	Alma, Mich.	1280	WHBQ	Memphis, Tenn.	560	WILA	Atlanta, Ga.	970
WENL	Evansville, Ind.	1480	WFC	Mineola, N.Y.	1340	WHBT	Harrisman, Tenn.	1600	WIKB	Iron River, Mich.	1230
WENK	Poughkeepsie, N.Y.	1390	WGA	Csdartown, Ga.	1340	WHBU	Anderson, Ind.	1240	WIKC	Bogalusa, La.	1490
WEOL	Elyria, Ohio	930	WGC	Augusta, Ga.	580	WHB	Appleton, Wis.	1400	WIKD	Wilton, Vt.	1490
WEPG	S. Pittsburg, Tenn.	910	WGA	Gadsden, Ala.	1350	WHCC	Waynesville, N.C.	1400	WIKY	Evansville, Ind.	820
WEPM	Martinsburg, W.Va.	1340	WGA	Valdosta, Ga.	910	WHCO	Sparta, Ill.	1230	WIL	St. Louis, Mo.	1430
WERE	Cia, Pa.	1260	WGA	Elizabeth City, N.C.	560	WHCU	Ithaca, N.Y.	870	WILA	Danville, Va.	1580
WERD	Atlanta, Ga.	860	WGL	Lancaster, Pa.	1490	WHDF	Houghton, Mich.	1400	WILD	Boston, Mass.	1090
WERE	Cleveland, Ohio	1800	WGAN	Portland, Maine	560	WHDH	Boston, Mass.	850	WILE	Cambridge, Ohio	1270
WERH	Hammonton, N.J.	970	WGAP	Maryville, Tenn.	400	WHDI	Olean, N.Y.	1450	WILL	Williamsville, Conn.	980
WERI	Westerly, R.I.	1230	WGAT	Cleveland, Ohio	1220	WHDK	McKean, Tenn.	1400	WIMK	Wilmington, Del.	1280
WERT	Van Wert, Ohio	1220	WGCM	Washington, N.C.	1420	WHEB	Portsmouth, N.H.	750	WILL	Urbana, Ill.	580
WESA	Charleroi, Pa.	940	WGCT	Gate City, Va.	1050	WHEC	Rochester, N.Y.	1460	WILM	Wilmington, Del.	1450
WESB	Bradford, Pa.	1490	WGAU	Athens, Ga.	1340	WHEN	Rochester, N.Y.	1460	WILF	Frankfort, Ind.	1570
WESC	Greenville, S.C.	660	WGAU	Gardner, Mass.	1340	WHES	Syracuse, N.Y.	620	WILS	Lansing, Mich.	1320
WESO	Southbridge, Mass.	970	WGAU	Silver Spring, Md.	1050	WHER	Memphis, Tenn.	1430	WILZ	St. Petersburg Beach, Florida	1590
WESQ	Tasley, Va.	1380	WGB	Columbus, Ga.	1270	WHF	Wewertha Beach, Fla.	1600	WIMA	Lima, Ohio	1490
WEST	Easton, Pa.	1010	WGBB	Freeport, N.Y.	1240	WHG	Millington, Tenn.	1320	WIMO	Winder, Ga.	1300
WESX	Salem, Mass.	1230	WGB	Freeport, N.Y.	1240	WHG	Benton Harbor, Mich.	1450	WIMS	Michigan City, Ind.	1420
WESY	Leland, Miss.	1580	WGBG	Greensboro, N.C.	1400	WHG	Cleora, Ill.	1450	WINA	Charlottesville, Va.	1400
WETR	Johnson City, Tenn.	790	WGBI	Seranton, Pa.	910	WHG	Harrisburg, Pa.	1400	WINC	Winchester, Va.	1400
WETO	Gadsden, Ala.	930	WGBR	Goldboro, N.C.	1150	WHG	Houghton L., Mich.	1290	WIND	Chicago, Ill.	560
WETU	Wetumpka, Ala.	1250	WGBS	Miami, Fla.	710	WHH	Warren, Ohio	1440	WINK	Kenmore, N.Y.	1080
			WGB	Red Lion, Pa.	1400	WHY	Montgomery, Ala.	1440	WINF	Manchester, Conn.	1230
			WGCD	Chester, S.C.	1490	WHM	Memphis, Tenn.	1340	WINE	Dayton, Ohio	1410
			WGCM	Gulfport, Miss.	1240						

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WINK	Fort Myers, Fla.	1240	WIPS	Evansville, Ind.	1330	WKWF	Key West, Fla.	1600
WINN	Louisville, Ky.	1240	WJQS	Jackson, Miss.	1400	WKWK	Wheeling, W.Va.	1400
WINQ	Tampa, Fla.	1010	WJR	Detroit, Mich.	760	WKXJ	Concord, N.H.	1450
WJNR	Binghamton, N.Y.	680	WHD	Tuscaloosa, Ala.	1150	WKXV	Knoxville, Tenn.	900
WINS	New York, N.Y.	1010	WRI	Lenoir, N.C.	1340	WKXY	Sarasota, Fla.	930
WINT	Winter Haven, Fla.	1200	WJBS	Crestview, Fla.	1050	WKY Oklahoma City, Okla.	900	
WIX	Reckton, Md.	1600	WJO	Jonesboro, Tenn.	1590	WKYB	Paducah, Ky.	570
WINZ	Miami, Fla.	940	WJTN	Jamestown, N.Y.	1240	WKYR	Keyser, W.Va.	1270
WIOD	Sanford, Fla.	1360	WJUN	Mexico, Pa.	1220	WKYU	Louisville, Ky.	900
WION	Jonia, Mich.	1430	WJVA	South Bend, Ind.	1580	WKOZ	Kalamazoo, Mich.	590
WIDS	Tawas City, Mich.	1480	WJWC	Cleveland, Ohio	850	WLAC	Nashville, Tenn.	1510
WIOU	Kokomo, Ind.	1350	WJWL	Georgetown, Del.	900	WLAD	Nashbury, Conn.	800
WIP	Philadelphia, Pa.	610	WJWS	South Hill, Va.	1370	WLAF	Lafayette, Tenn.	1430
WIPC	Lake Wales, Fla.	1260	WJKN	Jackson, Miss.	1450	WLAG	La Grange, Ga.	1240
WIPR	San Juan, P.R.	940	WJZM	Clarksville, Tenn.	1400	WLAK	Lakeeland, Fla.	1400
WIPS	Ticonderoga, N.Y.	1250	WKAB	Mobile, Ala.	840	WLAM	Leviston, Maine	1470
WIRA	Fort Pierce, Fla.	1400	WKAI	Macomb, Ill.	1510	WLAN	Lancaster, Pa.	1390
WIRB	Enterprise, Ala.	600	WKAL	Rome, N.Y.	1450	WLAP	Lexington, Ky.	630
WIRC	Hickory, N.C.	630	WKAM	Goshen, Ind.	1460	WLAR	Rome, Ga.	1410
WIRE	Indianapolis, Ind.	1430	WKAN	Kankakee, Ill.	1320	WLAR	Athens, Tenn.	1350
WIRI	Humboldt, Tenn.	740	WKAP	Allentown, Pa.	1320	WLAT	Conway, S.C.	1450
WIRK	W. Palm Beach, Fla.	1290	WKAQ	San Juan, P.R.	1480	WLAU	Laurel, Miss.	1500
WIRL	Peoria, Ill.	1290	WKAR	East Lansing, Mich.	870	WLAV	Grand Rapids, Mich.	1340
WIRO	Ironton, Ohio	1230	WKAT	Miami Beach, Fla.	1360	WLAW	Lawrenceville, Ga.	1360
WIRY	Plattsburg, N.Y.	1340	WKAY	Glasgow, Ky.	1490	WLAY	Muscle Shoals, Ala.	1450
WIS	Columbia, S.C.	560	WKAZ	Charleston, W.Va.	950	WLBA	Gainesville, Fla.	580
WISE	Asheville, N.C.	1100	WKBC	N. Wilkesboro, N.C.	810	WLBB	Carrollton, Ga.	1100
WISH	Indianapolis, Ind.	1310	WKBB	La Crosse, Wis.	1410	WLBC	Muncie, Ind.	1340
WISL	Shamokin, Pa.	1480	WKBI	St. Mary's, Pa.	1400	WLBE	Leesburg, Va.	790
WISM	Madison, Wis.	1480	WKBJ	Winn, Minn.	1600	WLBF	Bangor, Me.	1160
WISN	Milwaukee, Wis.	1150	WKBK	Keene, N.H.	1220	WLBH	Watton, Ill.	870
WISO	Ponce, P.R.	1260	WKBL	Covington, Tenn.	1250	WLBI	Denham Springs, La.	1220
WISP	Kinston, N.C.	1230	WKBN	Youngstown, Ohio	570	WLBJ	Bowling Green, Ky.	1410
WISR	Butler, Pa.	680	WKBO	Harrisburg, Pa.	1230	WLBK	DeKalb, Ill.	1360
WIST	Charlotte, N.C.	930	WKBR	Manchester, N.H.	1240	WLBL	Auburndale, Wis.	930
WISV	Virouqua, Wis.	1360	WKBV	Richmond, Ind.	1490	WLBN	Lebanon, Ky.	1520
WITA	San Juan, P.R.	1140	WKBW	Buffalo, N.Y.	1490	WLBR	Lebanon, Pa.	1590
WITH	Baltimore, Md.	1230	WKCB	Buffalo, N.Y.	1220	WLBT	Bartlett, Mo.	1170
WITI	Lewisburg, Pa.	1010	WKCB	Muskegon, Mich.	850	WLCK	Scottsville, Ky.	1250
WITY	Danville, Ill.	980	WKCB	Berlin, N.H.	1230	WLCL	Lancaster, S.C.	1380
WITZ	Jasper, Ind.	990	WKCC	Bowling Green, Ky.	930	WLCD	Eustis, Fla.	1240
WIVI	Christiansted, V.I.	1040	WKDA	Nashville, Tenn.	1240	WLCS	Baton Rouge, La.	910
WIVK	Knoxville, Tenn.	860	WKDK	Newberry, S.C.	1240	WLCC	LaCrosse, Wis.	1490
WIVV	Vieques, P.R.	1370	WKDL	Clarksdale, Miss.	1600	WLCT	St. Petersburg, Fla.	1380
WIVY	Jacksonville, Fla.	1050	WKDN	Camden, N.J.	800	WLDB	Atlantic City, N.J.	1400
WIZE	Springfield, Ohio	1340	WKDO	W.C. N.C.	800	WLDC	Laurel, Ill.	1340
WJAC	Syracuse, N.Y.	1250	WKEE	Huntington, W. Va.	800	WLDY	Ladysmith, Wis.	1450
WJAG	Johnstown, Pa.	1400	WKEI	Kewanee, Ill.	1450	WLEA	Hornell, N.Y.	1450
WJAH	Norfolk, Nebr.	780	WKEN	Dever, Del.	1600	WLEC	Sandusky, Ohio	1480
WJAK	Jackson, Tenn.	1460	WKEU	Griffin, Ga.	1450	WLEE	Richmond, Va.	1450
WJAM	Marion, Ala.	1310	WKEY	Covington, Va.	1340	WLEM	Emporium, Pa.	1250
WJAN	Ishpeming, Mich.	970	WKGK	Knoxville, Tenn.	930	WLEP	Pence, P.R.	1170
WJAR	Providence, R.I.	1200	WKHM	Jackson, Mich.	1370	WLET	Teococ, Ga.	1420
WJAS	Pittsburgh, Pa.	1320	WKID	Urbana, Ill.	1390	WLEU	Erie, Pa.	1450
WJAT	Swainboro, Ga.	800	WKID	Urbana, Ill.	1580	WLEW	Bay Axe, Mich.	1340
WJAX	Jacksonville, Fla.	930	WKIK	Leonardtown, Md.	1370	WLFA	Lafayette, Ga.	1590
WJAY	Mullins, S.C.	1280	WKIN	Kingsport, Tenn.	1320	WLFB	Little Falls, N.Y.	1190
WJAZ	Albany, Ga.	1050	WKIP	Poughkeepsie, N.Y.	1450	WLFB	New York, N.Y.	1230
WJBB	Haleyville, Ala.	1230	WKIS	Orlando, Fla.	740	WLIC	Newport, Tenn.	1270
WJBC	Bloomington, Ill.	1230	WKIX	Raleigh, N.C.	850	WLIL	Lenoir, Tenn.	730
WJBD	Salem, Ill.	1350	WKIZ	Kittanning, Pa.	1370	WLIN	Kingston, Wis.	1400
WJBE	Detroit, Mich.	1000	WKJB	Mayaguez, P.R.	710	WLIS	Old Saybrook, Conn.	920
WJBL	Holland, Mich.	1260	WKJC	Fort Wayne, Ind.	1380	WLIV	Livingston, Tenn.	1420
WJBO	Baton Rouge, La.	1150	WKKO	Cocoa, Fla.	860	WLIZ	Lake Worth, Fla.	1380
WJBS	DeLand, Fla.	1490	WKKS	Vanceburg, Ky.	1570	WLJL	Lowell, Mass.	1400
WJBW	New Orleans, La.	1230	WKLA	Ludington, Mich.	1450	WLJM	Richmond, Va.	1320
WJCD	Seymour, Ind.	1390	WKLC	St. Albans, W.Va.	1300	WLKJ	Jackson, Ohio	1280
WJCM	Seymour, Ind.	1390	WKLE	Kingston, Ga.	1370	WLKA	Peekskill, N.Y.	1420
WJCN	Quincy, Mass.	1400	WKLF	Canton, Ala.	980	WLKB	York, Pa.	1350
WJDB	Thomasville, Ala.	630	WKLG	Cloquet, Minn.	1230	WLKD	Bradford, Pa.	1550
WJDC	Jackson, Miss.	620	WKLM	Wilmington, N.C.	980	WLOR	Portland, Maine	1310
WJDF	Salisbury, Md.	1470	WKLO	Louisville, Ky.	1080	WLDP	Pompano Beach, Fla.	980
WJEF	Grand Rapids, Mich.	1230	WKLV	Blackstone, Va.	1440	WLEO	Leaksville, N.C.	1490
WJEH	Gallipolis, Ohio	990	WKLY	Paris, Ky.	1440	WLOF	Lorain, Fla.	950
WJEA	Hagerstown, Md.	1240	WKLY	Paris, Ky.	980	WLOG	Logan, W.Va.	1280
WJEL	Valdosta, Ga.	1150	WKLZ	Kalamazoo, Mich.	1470	WLOU	Portsmouth, N.Wa.	1400
WJER	Dever, Ohio	1450	WKMC	Roaring Springs, Pa.	1370	WLOI	LaPorte, Ind.	1540
WJET	Erie, Pa.	1400	WKMF	Flint, Mich.	1470	WLOK	Memphis, Tenn.	1480
WJGD	Columbia, Tenn.	1280	WKMG	Dearborn, Mich.	1310	WLOL	Minneapolis, Minn.	1330
WJHB	Talladega, Ala.	1580	WKMI	Kalamazoo, Mich.	1360	WLOM	Lincolnton, N.C.	1050
WJHL	Johnson City, Tenn.	910	WKMT	Kings Mts., N.C.	1220	WLOS	Asheville, N.C.	1380
WJHO	Opelika, Ala.	1400	WKNB	New Britain, Conn.	1290	WLOU	Louisville, Ky.	1350
WJIG	Tulahoma, Tenn.	740	WKNE	Keene, N.H.	1290	WLOW	Portsmouth, N.H.	1400
WJIM	Lansing, Mich.	1240	WKNS	Saginaw, Mich.	1210	WLOX	Bluff, Miss.	1490
WJIV	Savannah, Ga.	900	WKNY	Kingston, N.Y.	1490	WLPM	Suffolk, Va.	1450
WJJC	Commerce, Ga.	1270	WKOA	Hopkinsville, Ky.	1480	WLPO	LaSalle, Ill.	1220
WJJD	Chicago, Ill.	1160	WKOK	Sunbury, Pa.	1240	WLS	Chicago, Ill.	890
WJJE	Niagara Falls, N.Y.	1440	WKOP	Binghamton, N.Y.	1360	WLSB	Copper Hill, Tenn.	1400
WJJK	Lewisburg, Tenn.	1490	WKOV	Wellston, Ohio	1330	WLSL	Loris, S.C.	1570
WJKD	Springfield, Mass.	1070	WKOW	Windsor, Wis.	1070	WLSM	White Stone Gap, Va.	1400
WJKE	Hammond, Ind.	1400	WKOX	Framingham, Mass.	1190	WLSW	Wallace, N.C.	1400
WJLD	Homewood, Ala.	1400	WKDY	Bluefield, W.Va.	1450	WLSH	Lansford, Pa.	1410
WJLK	Asbury Park, N.J.	1310	WKDZ	Kosciusko, Miss.	1350	WLSI	Pikeville, Ky.	900
WJLS	Beckley, W.Va.	560	WKPA	New Kensington, Pa.	1150	WLSM	Louisville, Miss.	1270
WJMA	Orange, Va.	1340	WKPT	Kingsport, Tenn.	1400	WLSN	Escanaba, Mich.	600
WJMB	Brookhaven, Miss.	1340	WKRC	Cincinnati, Ohio	550	WLSV	Wellsville, N.Y.	790
WJMC	Rice Lake, Wis.	1240	WKRR	Murky, N.C.	1390	WLTC	Gastonia, N.C.	1370
WJMD	Philadelphia, Pa.	1540	WKRT	Mobile, Ala.	710	WLTG	Spring Hill, Ga.	1450
WJME	Cleveland Hts., Ohio	1490	WKRM	Columbia, Tenn.	1340	WLW	Cincinnati, Ohio	700
WJMR	New Orleans, La.	990	WKRO	Cairo, Ill.	1490	WLYC	Williamson, Pa.	1050
WJMS	Ironwood, Mich.	630	WKRS	Waukegan, Ill.	1220	WLYN	Lynn, Mass.	1360
WJMX	Athens, Ala.	730	WKRT	Cortland, N.Y.	920	WMAA	Munising, Mich.	1400
WJMX	Florence, S.C.	970	WKRT	Oil City, Pa.	1340	WMAF	Madison, Fla.	1230
WJNC	Jacksonville, N.C.	1240	WKSB	Wilford, Del.	930	WMAF	Forest, Miss.	860
WJND	W. Palm Beach, Fla.	1230	WKSC	Jefferson, N.C.	1600	WMAH	Spring Hill, Ga.	1450
WJNB	Hammond, Ind.	1230	WKST	Pulaski, Tenn.	1420	WMAK	Nashville, Tenn.	1300
WJOC	Jamestown, N.Y.	1340	WKSR	New Castle, Pa.	1280	WMAJ	Washington, D.C.	630
WJOE	Ward Ridge, Fla.	1570	WKTC	Charlotte, N.C.	1310	WMAK	Marionette, Wis.	570
WJOI	Florence, Ala.	1340	WKTF	Warrenton, Va.	1420	WMAN	Mansfield, Ohio	1400
WJOL	Joliet, Ill.	1340	WKTG	Thomasville, Ga.	730	WMAP	Monroe, N.C.	1060
WJON	St. Cloud, Minn.	1240	WKTL	Sheboygan, Wis.	950	WMAQ	Chicago, Ill.	670
WJOA	Lake Waukegan, S.C.	1050	WKTN	Waukegan, Ill.	1260	WMAK	Spring Hill, Mass.	1450
WJOY	Burlington, Pa.	1230	WKTO	South Paris, Maine	1450	WMAX	Grand Rapids, Mich.	1470
WJPA	Washington, Pa.	1450	WKTX	Atlantic Beach, Fla.	1600	WMAZ	Macon, Ga.	940
WJPD	Ishpeming, Mich.	1240	WKTY	LaCrosse, Wis.	580	WMB	Aubridge, Pa.	1460
WJPF	Herrin, Ill.	1340	WKUL	Cullman, Ala.	1340	WMB	Macon, Miss.	1400
WJPG	Green Bay, Wis.	1400	WKVA	Lewisport, Pa.	920	WMBD	Peoria, Ill.	1470
WJPR	Greenville, Miss.	1330	WKWN	San Juan, P.R.	810			
WMBQ	Richmond, Va.	1380						
WMBH	Joplin, Mo.	1450						
WMBI	Chicago, Ill.	1100						
WMBL	Morhead City, N.C.	740						
WMBM	Miami Beach, Fla.	830						
WMBN	Peteska, Mich.	1340						
WMBR	Auburn, N.Y.	1340						
WMBU	Jacksonville, Fla.	1460						
WMBT	Uniontown, Pa.	590						
WMC	Memphis, Tenn.	790						
WMCB	New York, N.Y.	570						
WMCB	Church Hill, Tenn.	1260						
WMCB	McKeesport, Pa.	1360						
WMCB	Miami Beach, Fla.	1400						
WMCB	Hazlehurst, Miss.	1220						
WMD	Fajardo, P.R.	1490						
WMD	Mount Dora, Fla.	1580						
WMDN	Midland, Mich.	1490						
WMEG	Eau Gallie, Fla.	920						
WMEK	Chase City, Va.	980						
WMEK	Tallahassee, Fla.	1390						
WMEC	Miami Beach, Fla.	1400						
WMEV	Marion, Va.	1010						
WMEF	Boston, Mass.	510						
WMEF	Monroeville, Ala.	1360						
WMEF	Wilmington, N.C.	630						
WMEF	Hibbing, Minn.	1240						
WMEF	Daytona Beach, Fla.	1450						
WMEF	High Point, N.C.	1230						
WMEF	Charlottesville, Va.	1260						
WMEF	Terre Haute, Ind.	1300						
WMEG	Moultrie, Ga.	1400						
WMEG	New York, N.Y.	1050						
WMEG	Bainbridge, Ga.	930						
WMEG	Meadville, Pa.	1490						
WMEG	Montgomery, Ala.	800						
WMEC	St. Helen, Mich.	1390						
WMEC	Hamlet, N.C.	1400						
WMEI	Miami, Fla.	1140						
WMIK	Middlesboro, Ky.	560						
WMLI	Milwaukee, Wis.	1290						
WMIN	Mpls.-St. Paul, Minn.	1400						
WMIQ	Iron Mountain, Mich.	1450						
WMIK	Natchez, Miss.	1240						
WMIK	Mt. Vernon, Ill.	1490						
WMIK	Arden, N.C.	1450						
WMLF	Pineville, Ky.	1230						
WMLP	Milton, Pa.	1570						
WMLS								

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WNAD	Norman, Okla.	640	WOSU	Columbus, Ohio	820	WRCD	Dalton, Ga.	1430	WSKY	Asheville, N.C.	1230
WNAE	Warren, Pa.	1310	WOTR	Corry, Pa.	1970	WRCO	Richland, Wis.	1450	WSLB	Oakdale, N.Y.	1400
WNAG	Grenada, Miss.	1400	WOTW	Nashua, N.H.	1300	WRCS	Ashokic, N.C.	970	WSLJ	Jackson, Miss.	930
WNAH	Nashville, Tenn.	1360	WOUB	Athens, Ohio	1340	WRCV	Philadelphia, Pa.	1060	WSLM	Salem, Ind.	620
WNAK	Nanticoke, Pa.	730	WOVE	Welch, W.Va.	1340	WRDB	Reedsburg, Wis.	1400	WSLS	Roanoke, Va.	1100
WNAM	Neenah, Wis.	1280	WOW	Omaha, Nebr.	590	WRDO	Augusta, Maine	1400	WSM	Nashville, Tenn.	650
WNAR	Norristown, Pa.	1110	WOWE	Alleghen, Mich.	1580	WRDW	Augusta, Ga.	1480	WSMB	New Orleans, La.	1850
WNAT	Natchez, Miss.	1450	WOWV	New Albany, Ind.	1570	WREB	Holyoke, Mass.	950	WSME	Sanford, Maine	1220
WNAU	New Albany, Miss.	1470	WOWL	Florence, S.C.	1240	WRFB	Memphis, Tenn.	1240	WSMI	Litchfield, Ill.	1540
WNAV	Annapolis, Miss.	1430	WOWO	Ft. Wayne, Ind.	1190	WREL	Lexington, Va.	1450	WSMN	Madison, Wis.	1580
WNAX	Yankton, S.Oak.	570	WOXF	Oxford, N.C.	1340	WREM	Remsen, N.Y.	1480	WSMT	Sparta, Tenn.	1050
WNBF	Binghamton, N.Y.	1290	WOZK	Ozark, Ala.	900	WREN	Topeka, Kans.	1250	WSNJ	Nr. Bridgeton, N.J.	1240
WNBH	New Bedford, Mass.	1340	WPAB	Poncha, P.R.	550	WREY	Reidsville, N.C.	1220	WSNT	Sandersville, Ga.	1490
WNBP	Newburyport, Mass.	1470	WPAC	Patchogue, N.Y.	1580	WRFB	Tallahassee, Fla.	1580	WSNW	Seneca Twnshp., S.C.	1150
WNBS	Murray, Ky.	1340	WPAD	Paducah, Ky.	1450	WRFC	Athens, Ga.	960	WSNY	Schenectady, N.Y.	1240
WNBT	Wellsville, Pa.	1480	WPAG	Ann Arbor, Mich.	1050	WRFD	Worthington, Ohio	880	WSOC	Charlotte, N.C.	1240
WNBSZ	Saraz Lake, N.Y.	1240	WPAL	Palatka, S.C.	730	WRGA	Alexander City, Ala.	1050	WSOC	Savannah, Ga.	1230
WNCA	Siler City, N.C.	1570	WPAM	Pottsville, Pa.	1450	WRGR	Rome, Ga.	1470	WSOM	Tampa, Fla.	1360
WNCC	Barnesboro, Pa.	950	WPAN	Fernandina Beach, Fla.	1570	WRGR	Starkie, Fla.	1490	WSOJ	Henderson, Ky.	860
WNCO	Ashland, Ohio	1340	WPAQ	Mount Airy, N.C.	740	WRGS	Rogersville, Tenn.	1370	WSOO	St. Ste. Marie, Mich.	1230
WNBO	Daytona Beach, Fla.	1150	WPAP	Parkersburg, W.Va.	1450	WRHC	Jacksonville, Fla.	1400	WSOT	Decatur, Ill.	1340
WNBR	Syracuse, N.Y.	1260	WPAT	Paterson, N.J.	930	WRHI	Rock Hill, S.C.	1340	WSPA	Spartanburg, S.C.	950
WNBU	South Bend, Ind.	1490	WPAT	Paterson, N.J.	930	WRIB	Providence, R.I.	1220	WSPB	Sarasota, Fla.	1450
WNBU	Worcester, Mass.	1230	WPAT	Paterson, N.J.	930	WRIC	Richmond, Va.	1340	WSPD	Toledo, Ohio	1370
WNEG	Tacoma, Wash.	1200	WPAX	Watucket, R.I.	550	WRIC	Memphis, Tenn.	1240	WSPF	Sarasota, Fla.	900
WNER	Liver Oak, Fla.	1250	WPAX	Waterville, Me.	1240	WRIM	Pahokee, Fla.	1250	WSPR	Springfield, Mass.	1270
WNES	Central City, Ky.	1600	WPATZ	Portsmouth, Ohio	1400	WRIO	Rio Piedras, P.R.	1320	WSPR	Springfield, Mass.	1270
WNEW	New York, N.Y.	1130	WPBC	Portsmouth, Pa.	1370	WRIP	Rossville, Ga.	980	WSPR	Stevens Pt., Wis.	1010
WNEX	Macon, Ga.	1400	WPBC	Minneapolis, Minn.	980	WRIS	Rossville, Ga.	980	WSRA	Milton, Fla.	1490
WNGO	Mayfield, Ky.	1320	WPCC	Clinton, S.C.	1400	WRIS	Roanoke, Va.	1410	WSRC	Durham, N.C.	1410
WNHC	New Haven, Conn.	1340	WPCC	Clinton, S.C.	1400	WRIT	Milwaukee, Wis.	1340	WSRO	Marlborough, Mass.	1470
WNHA	Chesterboga, N.Y.	1230	WPCT	Putnam, Conn.	1590	WRIV	Riverhead, N.Y.	1390	WSRW	Hillsboro, Ohio	1590
WNIA	Arabic, Pa.	1230	WPCT	Putnam, Conn.	1590	WRJA	Rocky Mt., N.C.	1490	WSRW	Warren, N.C.	1480
WNIL	Niles, Mich.	1290	WPDP	Potsdam, N.Y.	1470	WRJW	Picayune, Miss.	1320	WSSC	Sumter, S.C.	1490
WNJR	Newark, N.J.	1430	WPDP	Potsdam, N.Y.	1470	WRKD	Rockland, Maine	1450	WSSO	Starkville, Miss.	1230
WNKY	Neon, Ky.	1480	WPDP	Portage, Wis.	1350	WRKH	Rockwood, Tenn.	580	WSSP	Petersburg, Va.	1240
WNLC	New London, Conn.	1490	WPDX	Clarkburg, W.Va.	750	WRKM	Carthage, Tenn.	1350	WSTA	Charlotte Amalie, V.I.	1340
WNLK	Norwalk, Conn.	1350	WPDX	Clarkburg, W.Va.	750	WRKT	Cocoa Beach, Fla.	1300	WSTC	Stamford, Conn.	1400
WNLE	Evansville, Ill.	1590	WPEL	Montrose, Pa.	1250	WRLD	Lanit, Ala.	1490	WSTK	Woodstock, Va.	1230
WNLC	Newton, N.J.	1360	WPEL	Montrose, Pa.	1250	WRMA	Montgomery, Ala.	1050	WSTM	Eminece, Ky.	1600
WNNT	Warsaw, Va.	690	WPEL	Peoria, Ill.	1020	WRMF	Titusville, Fla.	1050	WSTB	St. Augustine, Fla.	900
WNOC	New Orleans, La.	1060	WPEF	Taunton, Mass.	1570	WRMN	Elgin, Ill.	1410	WSTP	Salisbury, N.C.	1490
WNOG	Naples, Fla.	1270	WPEF	Taunton, Mass.	1570	WRMT	Rocky Mount, N.C.	1490	WSTR	Sturgis, Mich.	1230
WNOK	Columbia, S.C.	1230	WPGA	Greensboro, N.C.	780	WRNB	New Bern, N.C.	1490	WSTS	Masena, N.Y.	1050
WNOP	Newport, Ky.	740	WPF	Park Falls, Wis.	1450	WRNL	Richmond, Va.	910	WSTU	Suart, Fla.	1450
WNOR	Norfolk, Va.	1230	WPGC	Bradbury Hgts., Md.	1580	WROR	Gulfport, Miss.	1390	WSTV	Steubenville, Ohio	1340
WNOS	High Point, N.C.	1590	WPGW	Portland, Ind.	1440	WROR	Waukegan, Ill.	1450	WSTB	Greenvale, Conn.	960
WNOW	York, Pa.	1250	WPBH	Phillipsburg, Pa.	1260	WROR	Daytona Beach, Fla.	1340	WSTC	St. Charles, Mo.	1340
WNDX	Knoxville, Tenn.	990	WPID	Plant City, Fla.	1280	WROK	Rockford, Ill.	1440	WSUI	Iowa City, Iowa	910
WNPS	New Orleans, La.	1450	WPIK	Piedmont, Ala.	790	WROM	Rome, Ga.	710	WSUN	St. Petersburg, Fla.	620
WNPT	Tuscaloosa, Ala.	1280	WPIN	St. Petersburg, Fla.	680	WRON	Ronoverte, W.Va.	1400	WSUX	Seaford, Del.	1280
WNRG	Grandy, Va.	1250	WPIT	Pittsburgh, Pa.	730	WROS	Scottsboro, Ala.	1330	WSV	Palatka, Fla.	800
WNRI	Woonsocket, R.I.	1380	WPKE	Pikeville, Ky.	1240	WROV	Roanoke, Va.	1240	WSVA	Harrisonburg, Va.	550
WNRW	Narrows, Va.	960	WPKO	Waverly, Ohio	1380	WRW	Warren, N.Y.	580	WSVA	Greene, Va.	800
WNSL	Laurel, Miss.	1260	WPKY	Princeton, Ky.	1380	WRX	Clarksville, Miss.	1040	WSWV	Pennington Gap, Va.	1570
WNSM	Valparaiso-Nieville, Florida	1340	WPLH	Huntington, W.Va.	1470	WRWB	Warner Robbins, Ga.	1350	WSWB	Pittsfield, Wis.	1590
WNTE	Newark, N.J.	970	WPLK	Rockmart, Ga.	1220	WRR	Dallas, Tex.	1310	WSYD	Mt. Airy, N.C.	1300
WNZA	Talladega, Ala.	1230	WPLM	Plymouth, Mass.	1390	WRRF	Washington, N.C.	930	WSYL	Sylvania, Ga.	1490
WNZA	Norfolk, Va.	1230	WPLA	Atlanta, Ga.	590	WRRZ	Clinton, N.C.	680	WSYR	Syracuse, N.Y.	370
WNZY	Pensacola, Fla.	1230	WPLY	Plymouth, Wis.	1420	WRSA	St. Albans, N.Y.	1280	WSTAB	Wattsburg, N.C.	1040
WNYC	New York, N.Y.	830	WPME	Punxsutawney, Pa.	1540	WRSW	Warsaw, Ind.	1480	WTAC	Flint, Mich.	600
WNYS	Salamanca, N.Y.	1590	WPME	Punxsutawney, Pa.	1540	WRTA	Altoona, Pa.	1240	WTAD	Quincy, Ill.	930
WNXT	Portsmouth, Ohio	1260	WPMP	Pascagoula, Miss.	1580	WRUF	Gainesville, Fla.	850	WTAG	Worcester, Mass.	580
WOAI	San Antonio, Tex.	1200	WPNC	Plymouth, N.C.	1470	WRUM	Rumford, Maine	790	WTAL	Tallahassee, Fla.	1270
WOAP	Owosso, Mich.	1080	WPNF	Brevard, N.C.	1240	WRUN	Utica, N.Y.	1150	WTAN	Clearwater, Fla.	1340
WOAY	Oak Hill, W.Va.	860	WPNX	Phenix City, Ala.	1470	WRUS	Russellville, Ky.	610	WTAD	Cambridge, Mass.	740
WOBS	Jacksonville, Fla.	1240	WPOM	Pompano Beach, Fla.	1470	WRVA	Richmond, Va.	1450	WTAP	Petersburg, W.Va.	1460
WOBT	Rhinelande, Wis.	1240	WPON	Portia, Mich.	1460	WRVK	Mt. Vernon, Ky.	1460	WTAR	LaGrange, Ill.	1300
WOC	Davenport, Iowa	1420	WPOP	Hartford, Conn.	1410	WRVM	Rochester, N.Y.	680	WTAR	Norfolk, Va.	790
WOCB	W. Yarmouth, Mass.	1240	WPOR	Portland, Maine	1490	WRWH	Cleveland, Ga.	1380	WTAW	Bryan, Tex.	1150
WOCI	North Vernon, Ind.	1460	WPOW	New York, N.Y.	1330	WRWJ	Selma, Ala.	1570	WTAX	Springfield, Ill.	1240
WOHI	E. Liverpool, Ohio	1490	WPFA	Pottsville, Pa.	1450	WRXO	Roxboro, N.C.	1430	WTAY	Raynham, Ill.	1570
WOHO	Toledo, Ohio	1470	WPRC	Perry, Pa.	990	WSAC	Fort Knox, Ky.	1470	WTBC	Tuscaloosa, Ala.	1230
WOHS	Shelbyfontaine, Ohio	1380	WPRE	Prairie Du Chien, Wis.	980	WSAL	Cincinnati, Ohio	1360	WTBF	Froy, Ala.	970
WOHS	Shelby, N.C.	730	WPRN	Butler, Ala.	1220	WSAJ	St. Joseph, Mo.	1490	WTBF	Springfield, Md.	1040
WOI	Ames, Iowa	640	WPRT	Prestonsburg, Ky.	960	WSAL	Logansport, Ind.	1230	WTCB	Floydton, Ala.	990
WOIA	Saline, Mich.	1290	WPRO	Providence, R.I.	630	WSAN	Saginaw, Mich.	1400	WTCH	Shawano, Wis.	960
WOIC	Columbia, S.C.	1470	WPRS	Ponca, P.R.	910	WSAN	Allentown, Pa.	1470	WTCT	Tell City, Ind.	1230
WOKB	Winter Garden, Fla.	1600	WPRS	Ponca, P.R.	910	WSAR	Fall River, Mass.	1480	WTCT	Traverse City, Mich.	1400
WOKC	Charleston, S.C.	1340	WPRV	Princeton, Va.	1440	WSAT	Nr. Salisbury, N.C.	1280	WTCT	Minneapolis, Minn.	1280
WOKK	Meridian, Miss.	1450	WPRY	Perry, Pa.	990	WSAV	Wausau, Wis.	1420	WTCC	Campbellsville, Ky.	1450
WOKJ	Jackson, Miss.	1460	WPTF	Raleigh, N.C.	1480	WSAV	Savannah, Ga.	630	WTCC	Chattanooga, Tenn.	1490
WOKO	Albany, N.Y.	1460	WPTA	Albany, N.Y.	1540	WSAY	Rochester, N.Y.	1370	WTCS	Fairmont, W.Va.	1490
WOKS	Columbus, Ga.	1340	WPTS	Pittsboro, Pa.	1540	WSAZ	Huntington, W.Va.	930	WTCS	Whitesburg, Ky.	920
WOKY	Milwaukee, Wis.	920	WPTW	Piqua, Ohio	1370	WSB	Atlanta, Ga.	750	WTHA	Philadelphia, Pa.	860
WOKZ	Alton, Ill.	1570	WPX	Lexington Park, Md.	1520	WSBA	York, Pa.	910	WTHS	Spartanburg, S.C.	1400
WOL	Washington, D.C.	1450	WPUV	Pulaski, Pa.	1580	WSBB	New Smyrna Beach, Florida	1230	WTHG	Jackson, Ala.	1290
WOLF	Syracuse, N.Y.	1490	WPVA	Colonial Hgts., Va.	1290	WSBC	Chicago, Ill.	1240	WTHR	Terre Haute, Ind.	1480
WOLG	Florence, S.C.	1490	WPVL	Painesville, Ohio	1460	WSBS	Gt. Barrington, Mass.	860	WTIC	Hartford, Conn.	1080
WOMI	Owensboro, Ky.	1490	WQAM	Miami, Fla.	560	WSBT	South Bend, Ind.	960	WTIF	Tifton, Ga.	1340
WOMP	Bellaire, Ohio	1290	WQBC	Vicksburg, Miss.	1420	WSCM	Panama City Beach, Florida	1290	WTIF	Massillon, Ohio	900
WOMT	Manitowoc, Wis.	1240	WQDY	Calais, Maine	1230	WSCR	Scranton, Pa.	1320	WTIK	Durham, N.C.	1310
WONA	Winona, Miss.	1570	WQIC	Meridian, Miss.	1390	WSD	Homestead, Fla.	1430	WTIM	Mayaguez, P.R.	1800
WOND	Pleasantville, N.J.	1400	WQIK	Jacksonville, Fla.	1240	WSDN	Sterling, Va.	1280	WTIM	Taylorville, Ill.	1410
WONE	Dayton, Ohio	980	WQMN	Superior, W.Va.	1320	WSEN	Baldwinsville, N.Y.	1050	WTIN	Charleston, N.C.	1280
WOLF	Oneda, N.Y.	1600	WQOK	Greenville, S.C.	1440	WSEV	Sevierville, Tenn.	930	WTIX	New Orleans, La.	690
WONN	Lakeland, Fla.	1280	WQSN	Charleston, S.C.	1450	WSEV	Sevierville, Tenn.	930	WTJH	East Point, Ga.	1260
WONW	Defiance, Ohio	1280	WQTE	Monroe, Mich.	560	WSEB	Quitman, Ga.	1490	WTJS	Jackson, Tenn.	1390
WOOD	Grand Rapids, Mich.	1300	WQUA	Moline, Ill.	1230	WSFC	Somerset, Ky.	1240	WTKM	Hartford, Wis.	1470
WOOF	Dothan, Ala.	560	WQXI	Atlanta, Ga.	790	WSFT	Thomaston, Ga.	1220	WTKO	Ithaca, N.Y.	1540
WOOK	Washington, D.C.	1340	WQXQ	Ormond Beh., Fla.	1380	WSGA	Savannah, Ga.	1400	WTLB	Utica, N.Y.	1310
WOOD	Deland, Fla.	1310	WQXR	Rockford, N.Y.	1560	WSGC	Elberton, Ga.	1400	WTLC	Somerset, Ky.	1450
WOOW	Washington, N.C.	1340	WQXT	Palm Beach, Fla.	1490	WSGN	Birmingham, Ala.	610	WTLS	Louisville, Ky.	1300
WOXA	Oak Park, Ill.	1490	WRAC	Racine, Wis.	1460	WSGW	Saginaw, Mich.	790	WTMA	Charleston, S.C.	1250
WOPI	Bristol, Tenn.	1490	WRAD	Radford, Va.	1460	WSHE	Raleigh, N.C.	570	WTMC	Ocala, Fla.	1290
WOR	New York, N.Y.	710	WRAG	Carrollton, Ala.	590	WSIC	Statesville, N.C.	1400	WTMJ	Milwaukee, Wis.	620
WORA	Mayaguez, P.R.	1150	WRAJ	Anna, Ill.	1440	WSID	Baltimore, Md.	1010	WTMP	Tampa, Fla.	1150
WORC	Worcester, Mass.	1310	WRAL	Williamsport, Pa.	1400	WSIG	Mount Jackson, Va.	790	WTMT	Louisville, Ky.	920
WORD	Spartanburg, S.C.	910	WRAL	Raleigh, N.C.	1240	WSIR	Painesville, Ky.	1490	WTNC	Winston-Salem, N.C.	1280
WORK	York, Pa.	1350	WRAM	Wilmington, N.C.	1330	WSIR	Winter Haven, Fla.	1490	WTND	Dayton, Ohio	1290
WORL	Worcester, Mass.	850	WRAP	Norfolk, Va.	850	WSIV	Pekin, Ill.	1140	WTNS	Coletton, Ohio	1560
WORM	Savannah, Tenn.	1010	WRAY	Reading, Pa.	1340	WSIX	Nashville, Tenn.	980	WTNT	Tallahassee, Fla.	1450
WORX	Fulton, Ind.	1270	WRBC	Princeton, Ind.	1250	WSJC	Magee, Miss.	1280	WTOB	Winston-Salem, N.C.	1890
WOSC	Madison, N.Y.	1300	WRBL	Jackson, Miss.	1400	WSJM	St. Joseph, Mich.	1400	WTOC	Savannah, Ga.	1280
WOSH	Oshkosh, Wis.	1490	WRBL	Columbus, Ga							

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WTON	Staunton, Va.	1240	WWL	New Orleans, La.	870	CFCW	Camrose, Alta.	1230	CION	St. John's, Nfld.	930
WTOP	Washington, D.C.	1500	WWNC	Asheville, N.C.	570	CFCY	Charlottetown, P.E.I.	630	CJOR	Vancouver, B.C.	600
WTOR	Torrington, Conn.	1980	WWNH	Rochester, N.H.	930	CFDA	Victoriaville, Que.	1340	CIOY	Quebec, Que.	1450
WTOT	Marianna, Fla.	1500	WWNB	Backus, W.Va.	620	CFGB	Goose Bay, Nfld.	1340	CIQC	Quebec, Que.	1340
WTPR	Paris, Tenn.	710	WWNS	Statesboro, Ga.	1240	CFGP	Grand Prairie, Alta.	1050	CJRH	Richmond Hill, Ont.	1310
WTRA	Latrobe, Pa.	1480	WWNY	Watertown, N.Y.	790	CFGR	Gravelbourg, Sask.	1230	CJRL	Kenora, Ont.	1220
WTRB	Ripley, Tenn.	1570	WWOD	Lynchburg, Va.	1390	CFGT	St. Joseph d'Alma, Que.	1270	CJRW	Summerside, P.E.I.	1240
WTRC	Elkhart, Ind.	1340	WWOK	Charlotte, N.C.	1480	CFJC	Kamloops, B.C.	910	CJSO	Sereb, Que.	1320
WTRL	Bradenton, Fla.	1490	WWOL	Buffalo, N.Y.	1120	CFJR	Broekville, Ont.	1450	CJSP	Vancouver, Ont.	710
WTRN	Tyrone, Pa.	1290	WWON	Woonsocket, R.I.	1240	CFKL	Schoffville, Que.	1380	CJST	Cornwall, Ont.	1220
WTRD	Wyersburg, Tenn.	1390	WWPA	Williamsport, Pa.	1340	CFLN	London, Ont.	1240	CJVI	Victoria, B.C.	900
WTRP	LaGrange, Ga.	620	WWPF	Palatka, Fla.	1260	CFML	Cornwall, Ont.	1110	CKAC	Montreal, Que.	730
WTRR	Sanford, Fla.	1400	WWRI	W. Warwick, R.I.	1450	CFNB	Fredericton, N.B.	550	CKAR	Huntsville, Ont.	590
WTRU	Muskegon, Mich.	1600	WWRJ	White River Lunc., Vt.	910	CFNS	Saskatoon, Sask.	1170	CKAR-1	Parry Sound, Ont.	1340
WTRW	Two Rivers, Wis.	1590	WWRL	Woodside, N.Y.	1600	CFOB	Fort Frances, Ont.	1600	CKBB	Barrie, Ont.	950
WTRX	Floyt, Mich.	1330	WWSC	Glens Falls, N.Y.	1450	CFOR	Orillia, Ont.	1570	CKCB	Bathurst, N.B.	1400
WTRY	Troy, N.Y.	980	WWSS	St. Albans, Vt.	1420	CFOS	Owen Sound, Ont.	560	CKCI	Prince Albert, Sask.	900
WTSA	Brattleboro, Vt.	1450	WWST	Weoster, Ohio	960	CFPA	Port Arthur, Ont.	1230	CKCL	Matane, Que.	1260
WTSB	Lumberton, N.C.	1340	WWSW	Pittsburgh, Pa.	970	CFPR	Prince Rupert, B.C.	1240	CKCM	Montmagny, Que.	1490
WTSL	Hanover-Lebanon, N.H.	1400	WWVA	Wheeling, W.Va.	1170	CFQC	Saskatoon, Sask.	600	CKBS	St. Hyacinthe, Que.	1240
WTSN	Dover, N.H.	1270	WWVB	Jasper, Ala.	1360	CFRA	Toronto, Ont.	560	CKBW	Bridgewater, N.S.	1000
WTSV	Claremont, N.H.	1230	WWWF	Fayette, Ala.	990	CFRB	Toronto, Ont.	1010	CKCH	Hull, Que.	970
WTTB	Vero Beach, Fla.	1490	WWWR	Rio Piedrae, P.R.	1520	CFRC	Kingston, Ont.	1490	CKCK	Regina, Sask.	620
WTTN	Port Huron, Mich.	1380	WWXL	Manchester, Ky.	1450	CFRG	Gravelbourg, Sask.	710	CKCL	Truro, N.S.	800
WTTM	Madisonville, Ky.	1310	WWYM	Geneville, W.Va.	970	CFRN	Edmonton, Alta.	1240	CKCQ	Quebec, B.C.	570
WTTN	Trenton, N.J.	920	WXA	Demois, Ala.	1400	CFRS	St. Simons, Ont.	1560	CKCR	Kingston, Ont.	1490
WTTN	Watertown, Wis.	1580	WXG	Richmond, Va.	950	CFRY	Portage la Prairie, Man.	1570	CKCV	Quebec, Que.	1280
WTRR	Westminster, Md.	1470	WXL	Dublin, Ga.	1440	CFSA	Saskatoon, Sask.	600	CKCW	Moncton, N.B.	1220
WTTT	Arlington, Ind.	1370	WXLW	Indianapolis, Ind.	950	CFSE	Weyburn, Sask.	1340	CKCY	Sault Ste. Marie, Ont.	1400
WTUG	Tuscaloosa, Ala.	790	WXK	Guayama, P.R.	1590	CFUN	Vancouver, B.C.	1410	CKDA	Victoria, B.C.	1220
WTUP	Tupelo, Miss.	1490	WXKX	Hattiesburg, Miss.	1310	CFWH	Whitehorse, Yukon T.	1240	CKDH	Amherst, N.S.	1400
WTUX	Wilmington, Del.	1290	WXX	Wilmington, Del.	1270	CFYK	Yellowknife, N.W.T.	1400	CKDM	Dauphin, Man.	730
WTVB	Caldwate, Mich.	1590	WYCL	York, S.C.	1580	CFZ	London, Ont.	1230	CKE	Kingston, Ont.	1490
WTVL	Waterville, Maine	1490	WYDE	Birmingham, Ala.	850	CHAB	Moose Jaw, Sask.	800	CKEK	Granby, B.C.	570
WTVN	Columbus, Ohio	610	WYFE	New Orleans, La.	600	CHAD	Mos, Que.	1340	CKEN	Kentville, N.S.	1350
WTWA	Thomson, Ga.	1240	WYLD	New Orleans, La.	940	CHAT	Medicine Hat, Alta.	1240	CKEY	Toronto, Ont.	580
WTWB	Auburndale, Fla.	1570	WYMB	Manning, S.C.	1410	CHCE	Edmonton, Alta.	1080	CKFH	Toronto, Ont.	1430
WTWN	St. Johnsbury, Vt.	1340	WYNG	Warwick-East, Vt.	1400	CHED	Granton, Que.	1450	CKGB	Timmins, Ont.	680
WTXL	W. Springfield, Mass.	1150	WYRN	Louisburg, N.C.	1590	CHEX	Peterborough, Ont.	820	CKGR	Galt, Ont.	1110
WTYC	Rock Hill, S.C.	1150	WYSE	Lakeland, Fla.	1430	CHFC	Churchill, Man.	1230	CKH	St. Jerome, Que.	900
WTYM	East Longmeadow, Mass.	1600	WYSR	Franklin, Va.	1250	CHG	St. Anne de la Pecosatiere, Que.	1350	CKLB	Shawano, Ont.	1380
WTYN	Tryon, N.C.	1580	WYTH	Madison, Ga.	1250	CHIB	Brampton, Ont.	1090	CKLC	Oshawa, Ont.	1350
WTYS	Marianna, Fla.	1340	WYTI	Rocky Mount, Va.	1570	CHLN	Three Rivers, Que.	550	CKLD	Thetford Mines, Que.	1230
WULA	Eufaula, Ala.	1240	WYUO	Newport News, Va.	1270	CHLO	St. Thomas, Ont.	800	CKLG	N. Vancouver, B.C.	730
WUSJ	Lockport, N.Y.	1340	WYVE	Wytheville, Va.	1280	CHLT	St. Thomas, Ont.	800	CKLN	Nelson, B.C.	1390
WUST	Bethesda, Md.	1120	WYFE	Atlanta, Ga.	1480	CHMT	Sherbrooke, Que.	680	CKLS	LaSarre, Que.	1240
WVAM	Altona, Pa.	1430	WZEP	Defunk Springs, Fla.	1460	CHND	Hamilton, Ont.	900	CKLW	Windsor, Ont.	800
WVCG	Coral Gables, Fla.	1070	WZIP	Covington, Ky.	1050	CHNO	New Carlisle, Que.	910	CKLP	Midland, Ont.	1230
WVCH	Chester, Pa.	740	WZKY	Albemarle, N.Dak.	1580	CHNS	Sudbury, Ont.	600	CKMR	Newcastle, N.B.	790
WVEC	Hampton, Va.	1490	WZOB	Ft. Payne, Ala.	1250	CHOK	Sarnia, Ont.	1070	CKNB	Campbellton, N.B.	950
WVET	Rochester, N.Y.	1280	WZOK	Jacksonville, Fla.	1320	CHOV	Pembroke, Ont.	1350	CKNW	New Westminster, British Columbia	980
WVIM	Vicksburg, Miss.	1490	WZRO	Jacksonville Beach, Fla.	1010	CHOW	Welland, Ontario	800	CKNX	Wingham, Ont.	920
WVJP	Mid. Kisco, N.Y.	1310	WZYX	Cowan, Tenn.	1440	CHRW	Welland, Ontario	800	CKOC	Hamilton, Ont.	1150
WVJP	Canajoharie, N.Y.	1110				CHRM	Toronto, Ont.	1070	CKOD	Penticton, B.C.	800
WVJS	Owensboro, Ky.	1420				CHRD	Drummondville, Que.	1340	CKOM	Saskatoon, Sask.	1420
WVKO	Columbus, Ohio	1580				CHRL	Roberval, Que.	910	CKOT	Tillsonburg, Ont.	1510
WVLD	Valdosta, Ga.	1450				CHRS	St. Jean, Que.	1090	CKOV	Kelowna, B.C.	630
WVLK	Lexington, Ky.	590				CHSJ	Saint John, N.B.	1590	CKOX	Woodstock, Ont.	1340
WVLN	Oney, Ill.	740				CHUB	Nanaimo, B.C.	1570	CKOY	Ottawa, Ont.	1310
WVMC	Mt. Carmel, Ill.	1360				CHUC	Port Hope, Ont.	1240	CKPC	Kingston, Ont.	1380
WVMI	Bloom, N.S.	570				CHUM	Toronto, Ont.	1050	CKPG	Prince George, B.C.	550
WVNA	Tusculum, Ala.	1590				CHVC	Niagara Falls, Ont.	1600	CKPR	Fort William, Ont.	580
WVNI	Newark, N.J.	620				CHWK	Chilliwack, B.C.	1270	CKRB	Ville St. Georges, Que.	1250
WVOK	Birmingham, Ala.	690				CHWO	Oakville, Ont.	1250	CKRC	Winnipeg, Man.	630
WVOL	Nashville, Tenn.	1470				CHJW	Woodstock, Que.	800	CKRD	Red Deer, Alta.	850
WVOP	Vidalia, Ga.	970				CJAT	Trail, B.C.	610	CKRM	Regina, Sask.	980
WVOS	Liberty, N.Y.	1240				CJAB	Port Alberni, B.C.	820	CKRN	Rouyn, Que.	1400
WVOT	Wilson, N.C.	1420				CJBC	Toronto, Ont.	1240	CKRS	Shawano, Que.	590
WVOV	Logan, W.Va.	1290				CJBB	Belleville, Ont.	900	CKSA	Lloydminster, Alta.	1150
WVOX	New Rochelle, N.Y.	1460				CJCB	Rimouski, Que.	800	CKSB	St. Boniface, Man.	1050
WVPO	Stroudsburg, Pa.	840				CJCA	Edmonton, Alta.	930	CKSL	London, Ont.	1290
WVSC	Somerset, Pa.	990				CJCB	Sydney, N.S.	1270	CKSM	Shawinigan, Quebec	1220
WVVW	Grayton, W.Va.	1260				CJCH	Halifax, N.S.	820	CKSO	Sudbury, Ont.	790
WVWB	Bray City, Mich.	1250				CJCK	Woodstock, N.B.	1240	CKSW	Swift Current, Sask.	1400
WVWB	Bamora, N.C.	790				CJCL	Stratford, Ont.	1240	CKTB	St. Catharines, Ont.	610
WVWB	Vineland, N.J.	1360				CJCM	Dawson Creek, B.C.	1350	CKTR	Three Rivers, Que.	1150
WVWC	Gary, Ind.	1270				CJCN	Edmundston, N.B.	570	CKTS	Sherbrooke, Que.	900
WVWC	Bremen, Ga.	1440				CJCT	Smiths Falls, Ont.	630	CKUA	Edmonton, Alta.	580
WVWC	Waterbury, Conn.	1240				CJCF	Riviere du Loup, Que.	1400	CKVD	Val d'Or, Que.	1230
WVWC	Washington, O.C.	1260				CJFX	Antigonish, N.S.	580	CKVL	Verdon, Que.	850
WVWP	Sanford, N.C.	1050				CJGB	Yorkton, Sask.	940	CKVM	Ville Marie, Que.	710
WVWS	Tifton, Ga.	1420				CJJB	Verona, B.C.	340	CKWS	Kingston, Ont.	960
WVWG	Hornell, N.Y.	1320				CJJC	Sault Ste. Marie, Ont.	1050	CKWX	Vancouver, B.C.	1130
WVWL	Ft. Lauderdale, Fla.	1580				CJJK	Kirkland Lake, Ont.	560	CKX	Brandon, Man.	1150
WVIN	Baltimore, Md.	1400				CJLR	Quebec, Que.	1060	CKXL	Calgary, Alta.	1140
WVIS	Black River Falls, Wis.	1260				CJLS	Yarmouth, N. S.	1340	CKY	Winnipeg, Man.	580
WVWJ	Canton, N.C.	970				CJMT	Montreal, Que.	1280	CKYL	Peace River, Alta.	630
WVWZ	Lorain, Ohio	1380				CJNE	Chicoutimi, Que.	1420	VOAR	St. John's, Nfld.	1230
WVWJ	Detroit, Mich.	950				CJNF	Battleford, Sask.	1460	VOCM	St. John's, Nfld.	800
WVWJ	Brookville, Fla.	1380				CJNG	Blind Bay, Ont.	730	VOCM	St. John's, Nfld.	800
WVWKY	Winchester, Ky.	1380				CJOC	Winnipeg, Man.	680	VOCM	St. John's, Nfld.	800
						CJOC	Lethbridge, Alta.	1220			

Canada

Canadian Short-Wave—Domestic and International

Abbreviations: Kc., frequency in kilocycles (to change to megacycles, divide by 1000); C.L., call letters

*Transmitter at Sackville, New Brunswick

Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location
5970	CBNX	St. John's, Nfld.	6160	CBUX	Vancouver, B.C.	11720	CBFL	Montreal, Que.*	15320	CKCS	Montreal, Que.*
5970	CKNA	Montreal, Que.*	6160	CHAC	Montreal, Que.*	11720	CHOL	Montreal, Que.*	17710	CKSB	Montreal, Que.*
5990	CHAY	Montreal, Que.*	9520	CBFR	Montreal, Que.*	11760	CBFA	Montreal, Que.*	17735	CKRX	Montreal, Que.*
6005	CFXC	Montreal, Que.*	9585	CKLP	Montreal, Que.*	11760	CKRA	Montreal, Que.*	17820	CKNC	Montreal, Que.*
6010	CJCX	Sydney, N.S.	9610	CBFX	Montreal, Que.*	11900	CKEX	Montreal, Que.*	17865	CHYS	Montreal, Que.*
6030	CFVP	Calgary, Alta.	9610	CHLS	Montreal, Que.*	11945	CKEX	Montreal, Que.*	21600	CKRP	Montreal, Que.*
6060	CKRZ	Montreal, Que.*	9630	CHFR	Montreal, Que.*	15090	CKLX	Montreal, Que.*	21710	CHLA	Montreal, Que.*
6070	CFRX	Toronto, Ont.	9630	CHLR	Montreal, Que.*	15105	CKLU	Montreal, Que.*			
6080	CKFX	Vancouver, B.C.	9710	CHLR	Montreal, Que.*	15190	CBFZ	Montreal, Que.*			
6090	CBFW	Montreal, Que.*	9740	CHFO	Montreal, Que.*	15190	CKCX	Montreal, Que.*			
6090	CKOB	Montreal, Que.*	11705	CFBY	Montreal, Que.*	15255	CKSR	Montreal, Que.*			
6130	CHNX	Halifax, N.S.	11705	CKXA	Montreal, Que.*	15275	CKBR	Montreal, Que.*			

World-Wide Short-Wave Stations

Most international broadcasting is done within frequency limits agreed upon at international conventions. These frequency ranges are listed here, at the right, expressed both in frequency and by meter bands (wave-length).

Not all of the bands are employed at once. In fact, only one or two are usable at any one time. The time of the day and the season (or seasons, since the season is opposite in the southern hemisphere) are the two chief determining factors. Broadcasters beaming programs to the U.S. use the best band for the time. Broadcasts not beamed to the U.S., if heard here at all, will be scattered over the bands. Low frequencies are better heard at night than by day. High frequencies are better heard in summer than in winter.

- 5950 to 6200 kc/s (49 meter band)
- 7100 to 7300 kc/s (41 meter band)
- 9500 to 9775 kc/s (31 meter band)
- 11700 to 11975 kc/s (25 meter band)
- 15100 to 15450 kc/s (19 meter band)
- 17700 to 17900 kc/s (16 meter band)
- 21450 to 21750 kc/s (13 meter band)

The symbol • denotes stations beaming regular evening broadcasts to the United States.

Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location
4768	HJEF	Calli, Colombia	6035	GWS	London, England	6405	TGQA	Quezaltenango, Guat.	9531	COCO	Havana, Cuba
4775	HJGB	Bucaramanga, Col.	6035	Monte Carlo,	Monaco	6450	COCY	Santa Clara, Cuba	9535	HER4	Bern, Switzerland
4783	HJAB	Barranquilla, Col.	6035	XYZ	Rangoon, Burma	6632	HC2RL	Guayaquil, Ecu.	9535	SBU	Stockholm, Sweden
4790	YVQC	Ciudad Bolivar, Vz.	6037	San Jose,	Costa Rica	6660	HROW	Tegucigalpa, Hond.	9540	Munich,	Germany
4797	HJFU	Armenia, Colombia	6040	GSY	London, England	6758	YNPV	Managua, Nic.	9540	VLG9	Melbourne, Aus.
4800	YVME	Maracaibo, Venez.	6040	KCBR	Delano, Calif.	6790	ZJM6	Limassol, Cyprus	9540	ZL2	Wellington, N. Zeal.
4805	ZYSB	Moscow, U.S.S.R.	6040	Tangier,	Tangier	6830	4XB21	Tel Aviv, Israel	9543	XYZ	Rangoon, Burma
4810	YVMG	Maracaibo, Venez.	6040	WLVW	Cincinnati, U.S.A.	6870	PC4EB	Machala, Ecuador	9548	KEFT	Vera Cruz, Mex.
4815	HJBB	Cucuta, Col.	6045	YDF	Djakarta, Indonesia	7105	Paris,	France	9550	HVJ	Vatican City
4820	XEJG	Guadalajara, Mex.	6050	HIIN	Ciudad Trujillo, D.R.	7112	CR4AA	Praia, Cape V. Isls.	9550	Paris,	France
4820	YVNB	Core, Venez.	6050	GSA	London, England	7120	GRM	London, England	9550	OLR3A	Prague, Czechos.
4830	YVVA	San Cristobal, Vz.	6054	HJEX	Calli, Colombia	7135	BE07	Taipei, Formosa	9550	Grenada,	Windward Is.
4835	HJKE	Bogota, Colombia	6055	HER2	Bern, Switzerland	7135	MCM	London, England	9555	OIX2	Peri, Finland
4845	YVDI	Merla, Venez.	6060	GSJ	London, England	7230	GSW	London, England	9555	XETT	Mexico, Mex.
4845	CSA93	Ponta Delgada, Az.	6060	KNBH	(VOA) Dixon, Calif.	7145	Radio Free Europe		9560	IBD2	Kawachi, Japan
4848	HJGF	Bucaramanga, Col.	6060	Tangier I,	Tangier	7150	GRT	London, England	9560	London,	England
4850	YVMS	Barquisimeto, Vz.	6060	WDSI	New York, U.S.A.	7165	Moscow,	U.S.S.R.	9560	Paris,	France
4855	HJFN	Neiva, Colombia	6065	SBO	Motala, Sweden	7175	VUD	Delhi, India	9560	WLVW	Cincinnati, U.S.A.
4860	JKL	Tokyo, Japan	6065	XEXE	Mexico City, Mex.	7180	JOA	Tokyo, Japan	9560	WRCA	New York, U.S.A.
4860	YVPA	San Felipe, Venez.	6069	JB9	Tokyo, Japan	7185	GRK	London, England	9565	Komsomolsk,	U.S.S.R.
4865	PRCS	Belom, Para, Brazil	6070	GRR	London, England	7200	GWZ	London, England	9565	ZYK3	Recife, Brazil
4871	HJFA	Armenia, Colombia	6070	KLWO	Cincinnati, U.S.A.	7210	Warsaw,	Poland	9570	Paris,	France
4871	HJBG	Cucuta, Colombia	6080	Munich III,	Germany	7210	GRW	London, England	9570	GWX	London, England
4880	YVKF	Caracas, Venez.	6081	OAX42	Lima, Peru	7210	HE13	Bern, Switzerland	9570	KCBR	(VOA) Delano, Calif.
4892	YVKB	Caracas, Venez.	6085	ORU	Brussels, Belgium	7222	Budapest,	Hungary	9570	Warsaw,	Poland
4895	HJCH	Bogota, Col.	6085	VP4RD	Port-of-Spain, Trinidad	7230	GSW	London, England	9570	Bucharest,	Rumania
4895	PRF6	Manaos, Brazil				7240	Moscow,	U.S.S.R.	9570	Rome,	Italy
4897	VLX4	Perth, Aust.	6085	ZYK2	Recife, Brazil	7240	Paris,	France	9580	GSC	London, England
4905	YVQE	Maracaibo, Venez.	6090	TWM	London, England	7250	GWJ	London, England	9580	SH9	Shannon, Aus.
4903	HJAG	Barranquilla, Col.	6090	VL16	Sydney, Australia	7255	Prague,	Czechoslovakia	9585	Madrid,	Spain
4907	YVMM	Core, Venez.	6092	Radio Luxemburg		7257	JKH	Tokyo, Japan	9590	Hilversum,	Neth.
4910	JKI	Nazaki, Japan	6095	Horby,	Sweden	7260	GSU	London, England	9590	WABC	New York, U.S.A.
4910	YDB2	Djakarta, Indon.	6095	Radio Free Europe,		7260	Moscow,	U.S.S.R.	9600	GRY	London, England
4915	Acera,	Ghana				7280	GWN	London, England	9600	KCBR	Delano, Cal., U.S.A.
4915	YVKR	Caracas, Venez.	6095	ZYB7	Sao Paulo, Brazil	7285	JKJ	Tokyo, Japan	9600	KRCA	San Fran., U.S.A.
4915	HJGB	Santiago, Dom. Rep.	6100	HJFK	Cerinto, Colombia	7285	TAS	Ankara, Turkey	9600	Leningrad,	U.S.S.R.
4917	VLW4	Brisbane, Aus.	6100	Belgrade,	Yugoslavia	7290	Hamburg,	Germany	9605	HPSJ	Panama, Pan.
4930	HJAP	Cartagena, Col.	6100	WRCA	New York, U.S.A.	7290	VUD	Delhi, India	9605	JKL2	Tokyo, Japan
4940	JKM	Kawachi, Japan	6110	GSL	London, England	7295	Moscow,	U.S.S.R.	9605	Radio Free Europe,	
4940	YVMQ	Barquisimeto, Vz.	6112	HIIZ	Ciudad Trujillo, D.R.	7300	Radio Free Europe,				
4945	HJCV	Bogota, Col.	6115	Berlin,	Germany						
4950	ZQI	Kingston, Jamaica	6120	HC2FB	Guayaquil, Ecu.	7300	SYD2	Athens, Greece	9607	Athens,	Greece
4951	Dakar,	Senegal	6120	ZJ4	Limassol, Cyprus	7315	SD	San Salvador, Salv.	9610	VLX9	Perth, Australia
4960	YVQA	Caracas, Venez.	6120	Tangier	Tangier	7320	GRI	London, England	9610	ZYCO	Rio de Janeiro, Brazil
4967	HJAE	Cartagena, Col.	6120	WRCA	New York, U.S.A.	7335	BE36	Taipei, Formosa	9610	XERQ	Mexico, Mex.
4970	YVLK	Caracas, Venez.	6122	HP5H	Panama, Pan.	7360	Moscow,	U.S.S.R.	9615	Voices of Amer.,	Tangier
4985	YVMO	Barquisimeto, Vz.	6124	HRQ	San Pedro Sula, Hond.	7670	Sofia,	Bulgaria	9615	VLB9	Shepparton, Aus.
4993	HIIA	Santiago, D.Rep.	6125	GWA	London, England	7850	ZAA	Tirana, Albania	9615	WRCA	New York, U.S.A.
5010	Grenada,	Windward Is.	6130	KEU2	Mexico, Mex.	7863	SUX	Cairo, Egypt	9618	WDCR	San Jose, C.Rica
5014	PJCS	Williamstad, Curas.	6130	Radio Spain,		7933	HLKA	Pusan, S. Korea	9620	TIDCR	San Jose, C.Rica
5020	HJFW	Merla, Venez.	6130	GRS	Havana, Cuba	7951	Alicante,	Spain	9620	Horby,	Sweden (Nov. to Febr. only)
5023	HI62	Santiago, O.Rep.	6130	Port Moresby,	New Guinea	8036	FXE	Beirut, Lebanon	9620	Paris,	France
5030	YVKK	Caracas, Venez.	6135	HJED	Calli, Colombia	8664	COJK	Camaguey, Cuba	9620	ZL8	Wellington, N.Z.
5045	ZYP23	Petropolis, Brazil	6140	Munich,	Germany	8825	COCQ	Havana, Cuba	9625	XEBT	Mexico, Mex.
5050	YVKD	Caracas, Venez.	6145	HJDE	Medellin, Col.	9055	COKG	Santiago, Cuba	9625	GW	London, England
5053	HI2L	Ciudad Trujillo, D.R.	6147	PRL9	Rio de Janeiro, Br.	9007	Voices of Zion,	Tel Aviv, Israel	9625	VP4RD	Port-aux-Spain, Trinidad
5053	HJDW	Medellin, Col.	6150	GRW	London, England						
5075	HJKH	Sutatenza, Colom.	6150	WLVW	Cincinnati, U.S.A.	9026	COBZ	Havana, Cuba	9630	HJKC	Bogota, Colombia
5758	PZH5	Paramaribo, Surinam	6160	HJKJ	Bogota, Colombia	9236	COBQ	Havana, Cuba	9630	VUD4/10	Delhi, India
5880	HRN	Tegucigalpa, Hond.	6160	Honolulu,	Hawaii	9252	Bucharest,	Rumania	9630	Rome,	Italy
5920	HRA	Tegucigalpa, Hond.	6160	Munich,	Germany	9290	PRN9	Rio de Janeiro, Brazil	9635	Munich,	Germany
5940	Khabarovsk,	U.S.S.R.	6165	GWK	London, England	9316	LRS	Buenos Aires, Arg.	9635	Voices of Amer.,	Tangier
5940	Moscow,	U.S.S.R.	6165	HER3	Bern, Switzerland	9340	OAX4	Lima, Peru	9640	Acera,	Ghana
5952	TGNA	Guatemala, Guat.	6167	GYCM	Port-aux-Prince, H.	9350	DB	Hawabak, Japan	9640	West Germany	Radio Plogne
5952	HJCF	Bogota, Colombia	6170	GSZ	London, England	9369	Madrid,	Spain	9640	DZH2	Manila, P.I.
5965	Shanghai,	China	6170	KCBR	Delano, Cal., U.S.A.	9380	Khabarovsk,	U.S.S.R.	9640	GVZ	London, England
5969	HVJ	Vatican City	6170	YVKO	Caracas, Venez.	9400	OTM2	Leopoldville, Belgian Congo	9645	Karachi,	Pakistan
5970	HI4T	Ciudad Trujillo, D.R.	6172	ZJM5	Limassol, Cyprus	9410	GRI	London, England	9645	LLH	Oslo, Norway
5981	ZFY	Georgetown, Br. Gui.	6175	XEXA	Mexico, Mex.	9440	Brazzaville,	Fr. Eq. Africa	9645	TIFC	San Jose, C.Rica
5985	Radio Free Europe,		6180	LRM	Mendoza, Argentina	9452	Radio Babel,	Danmark	9646	HVJ9	Vatican City
5990	TGJA	Guatemala, Guat.	6180	GRO	London, England	9463	TAP	Ankara, Turkey	9650	Honolulu,	Hawaii
5995	HO50	Panama, Panama	6182	TGBW	Guatemala, Guat.	9480	Moscow,	U.S.S.R.	9650	Moscow,	U.S.S.R.
6005	Berlin,	Germany	6185	KCBR	(VOA) Delano, Calif.	9490	KUJ39	Agana, Guam.	9650	Tangier,	Tangier
6005	HP5K	Colon, Panama	6185	HJCT	Bogota, Colombia	9500	XEWW	Mexico, Mex.	9650	WDSI	(VOA) Brentwood, N. Y.
6009	HJFC	Armenia, Colombia	6190	Frankfurt,	Germany	9504	OLR3B	Prague, Czechos.	9652	ZJM8	Limassol, Cyprus
6010	GRB	London, England	6190	HIST	Puerto Plata, D.R.	9505	HOLA	Colon, Panama	9654	OTC2	Leopoldville, Belgian Congo
6010	OLR2A	Prague, Czechos.	6190	WLVW	Cincinnati, U.S.A.	9505	YHJ	Barquisimeto, Ven.			
6015	KEU1	Mexico, Mex.	6190	WRCA	New York, U.S.A.	9510	GSB	London, England	9655	JKI2	Nazaki, Japan
6015	PR4E	Recife, Brazil	6195	GRN	London, England	9515	KNBH	(VOA) Dixon, Calif.	9656	4VEH	Cap-Haitien, Haiti
6018	HJCX	Bogota, Col.	6195	Honolulu,	Hawaii	9515	TAT	Ankara, Turkey	9660	EQC	Teheran, Iran
6020	Kiev,	U.S.S.R.	6200	Paris,	France	9520	Colombo,	Ceylon	9660	GW	London, England
6020	Radio Free Europe,		6215	SP13	Warsaw, Poland	9520	HJKF	Bogota, Colombia	9660	VLQ9	Brisbane, Aus.
6020	KNBH	(VOA) Dixon, Calif.	6235	HR2D	La Ceiba, Hond.	9520	WLVW	Cincinnati, U.S.A.	9665	PEU9	Bern, Switzerland
6024	Brazzaville,	Fr. Eq. Africa	6235	Karachi,	Pakistan, U.S.A.	9525	Warsaw,	Poland	9668	HONB	Guatemala, Guat.
6024	Shanghai,	China	6235	Budapest,	Hungary	9525	WLV9	Port Moresby, British New Guinea	9670	Munich,	Germany
6025	Radio Nederland		6285	TGTQ	Guatemala, Guat.	9525	WLVW	Cincinnati, U.S.A.	9670	Voices of Amer.,	Tangier
6025	HI1J	San Pedro, D.R.	6295	OTM1	Leopoldville, Belgian Congo	9525	GWJ	London, England	9675	Moscow,	U.S.S.R.
6030	Stuttgart,	Germany				9525	GWJ	London, England	9675	GWT	London, England
6030	DZH6	Manila, P.I.	6295	TGLA	Guatemala, Guat.	9525	ZBWS	Victoria, Hong Kong	9675	JOB3	Tokyo, Japan
6030	XEKW	Morelia, Mex.	6320	Baden-Baden,	Germany	9527	Warsaw,	Poland	9680	Paris,	France
6030	HP5B	Panama, Pan.	6322	COCW	Havana, Cuba	9530	Honolulu,	Hawaii	9680	XEQQ	Mexico, Mex.
			6335	TGTA	Guatemala, Guat.	9530	Manila,	Philippines	9680	VUD	Delhi, India
			6351	HRP1	San Pedro Sula, Hond.	9530	KCBR	Delano, Cal., U.S.A.	9680	Moscow,	U.S.S.R.
			6374	CSA21	Lisbon, Port.	9530	WABC	New York, U.S.A.	9680	Voices of America,	Tangier

Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location
9680	VL9R/VL9H	Melbourne, Australia	11795	YDF3	Djakarta, Indonesia	15120	Rome, Italy	15405	DMQ15	Cologne, W. Germany	
9685	Paris, France		11795	YDF3	Djakarta, Indonesia	15125	CSA36	Lisbon, Portugal	15410	Moscow, U.S.S.R.	
9685	WLWO	Cincinnati, U.S.A.	11795	WRU1	Boston, U.S.A.	15130	WAO	Voice of America, Tangier	15410	Moscow, U.S.S.R.	
9690	GRX	Buenos Aires, Arg.	11795	WRU1	Boston, U.S.A.	15140	WABC	New York, U.S.A.	15420	Paris, France	
9690	LR London, England		11795	ELWA	Montevideo, Liberia	15130	WLWO	Cincinnati, U.S.A.	15420	Paris, France	
9690	Moscow, U.S.S.R.		11800	JK14	Tokyo, Japan	15130	KCBR	(VOA) Delano, Calif.	15425	Radio Netherlands	
9690	Singapore, Malaysia		11800	GWH	London, England	15130	WBOU	Bound Brook, N.J., U.S.A.	15435	GWE	London, England
9695	JKM2	Kawachi, Japan	11800	Brussels, Belgium		15135	Radio Japan, Tokyo		15440	Moscow, U.S.S.R.	
9700	GWY	London, England	11810	Moscow, U.S.S.R.		15135	PRB23	Sao Paulo, Brazil	15445	Radio Netherlands	
9700	WDSI	New York, U.S.A.	11810	Radio Sweden	(except—)	15140	GSF	London, England	15450	GRD	London, England
9700	Sofia, Bulgaria		11810	Rome, Italy	Nov. to Febr.	15140	YVC	Yokohama, Japan	15395	Brazzaville, Fr. Eq. Africa	
9700	Voice of America, Tangier		11810	VLAI1	Shepparton, Aus. (Morn'g program)	15145	ZYK2	Rice, Brazil	15880	Radio, Spain	
9700	WLWO	Cincinnati, U.S.A.	11815	Warsaw, Poland		15150	OAX4R	Lima, Peru	15880	Peking, China	
9700	KCBR	Delano, Calif., U.S.A.	11820	GSN	London, England	15150	CE1515	Santiago, Chile	17200	GVP	London, England
9700	FZF6	Fl. de France, Mart. Moscov, U.S.S.R.	11820	XEBR	Hermosillo, Mex.	15155	SBT	Motala, Sweden	17710	WRUL	Boston, U.S.A.
9710	Dakar, Fr. W. Africa		11825	XK16	Tokyo, Japan	15156	ZY89	Sao Paulo, Brazil	17715	GRA	London, England
9710	YDF6	Djakarta, Indonesia	11825	Moscow, U.S.S.R.		15160	VUD5/7	Delhi, India	17720	LRA35	Buenos Aires, Arg.
9715	Rome, Italy		11825	YK3	Recife, Brazil	15160	VLD15	Shepparton, Aus.	17730	GVQ	London, England
9715	Cairo, Egypt		11830	FZ54	Salgon, Fr. Indo-C.	15160	TAS	Amara, Turkey	17750	WRUL	Boston, U.S.A.
9716	Moscow, U.S.S.R.		11830	Moscow, U.S.S.R.		15165	WLWO	Cincinnati, U.S.A.	17750	Rome, Italy	
9717	Radio Free Europe, Ger.		11830	Voice of America, Tangier		15165	ZYN7	Fortaleza, Brazil	17760	WGE0	Schenectady, U.S.A.
9720	PRL7	Rio de Janeiro, Brazil	11830	WBOU	(VOA) New York, U.S.A.	15170	LKV	Oslo, Norway	17760	VUD	Delhi, India
9730	French Equatorial Africa		11830	WDSI	(VOA) New York, U.S.A.	15170	TGWA	Guatemala, Guat.	17770	Rome, Italy	
9730	Nanking, China		11835	CXA19	Montevideo, U.S.A.	15170	Moscow, U.S.S.R.		17770	Voice of America, Tangier	
9730	DZ17	Batavia, P.I.	11835	PRAGUE, Czechoslovakia		15175	LLM	Oslo, Norway	17770	Radio Sweden, Stockholm	
9730	Leipzig, Germany		11840	VLW11	Perth, Australia	15180	GSF	London, England	17775	Hilversum, Netherlands	
9735	H12T	Ciudad Trujillo, D.R.	11840	OLR4A	Prague, Czech.	15180	OH2H	Shamlebak, Den.	17780	VUD7	Delhi, India
9741	CSA27	Lisbon, Portugal	11840	LR4A	Prague, Czech.	15180	YDU05	I11 Delhi, India	17780	WBOU	New York, U.S.A.
9745	HCJB	(Missionary Station), Quito, Ecuador	11840	LR4A	Prague, Czech.	15190	O1X4	Pori, Finland	17780	Voice of Amer., Manila, P.I.	
9745	ORU	Brussels, Belgium	11840	LR4A	Prague, Czech.	15195	TAQ	Ankara, Turkey	17784	HER7	Bern, Switzerland
9750	CR7BE	Lourenco Marques, Moz.	11845	LR4A	Prague, Czech.	15200	Moscow, U.S.S.R.		17785	JDA	Tokyo, Japan
9765	TGWA	Guatemala, Guat.	11845	LR4A	Prague, Czech.	15200	Moscow, U.S.S.R.		17790	GSF	London, England
9770	London, England		11850	VLBI1	Shepparton, Aus.	15200	VLA15/VL15		17795	WLWO	Cincinnati, U.S.A.
9770	ORU	Brussels, Belgium	11850	ORU	Brussels, Belgium	15205	Voice of America, Tangier		17800	WRU1	Boston, U.S.A.
9770	PRL4	Rio de Jan., Brazil	11850	TGNC	Guatemala, Guat.	15210	Munich, Germany		17800	WLWO	Cincinnati, U.S.A.
9780	Rome, Italy		11850	VUD11	Delhi, India	15210	GWU	London, England	17800	Radio Australia, Melbourne	
9785	Monte Z. Bata, Mexico		11850	LLK	Oslo, Norway	15210	WBDU	(VDA) New York, U.S.A.	17800	Radio Poland	
9825	GRH	London, England	11855	DZ19	Manila, Philippines	15210	WBDU	(VDA) New York, U.S.A.	17800	KRHO	Honolulu, Hawaii
9833	Budapest, Hungary		11855	Radio Free Europe, Lisbon, Portugal		15210	VLG15	Melbourne, Aus.	17800	Stockholm, Sweden	
9833	COBL	Havana, Cuba	11860	GSE	London, England	15210	VLG15	Melbourne, Aus.	17800	O1X5	Pori, Finland
9865	YDF8	Djakarta, Indonesia	11860	KWID	San Fran., U.S.A.	15220	Hilversum, Neth.		17800	DZ16	Batavia, P.I.
9915	GRZ	London, England	11865	CR6RA	Luanda, Angola	15225	JBD3	Kawachi, Japan	17805	Formosa	Radio, P.I.
9966	Brazzaville, Fr. Eq. Africa		11865	HER5	Bern, Switzerland	15225	Komsomolsk, U.S.S.R.		17810	GSV	London, England
10018	Paris, France		11870	Munich, Germany		15230	GWU	London, England	17810	Moscow, U.S.S.R.	
10220	PSH	Rio de Janeiro, Brazil	11870	KNB8	San Fran., U.S.A.	15230	Moscow, U.S.S.R.		17815	WRUL	Boston, U.S.A.
10258	XRRR	Peiping, China	11870	Voice of America, Tangier		15230	WLD15	Melbourne, Aus.	17820	Colombo, Ceylon	
10780	SDB2	Motala, Sweden	11870	WRUL	Boston, U.S.A.	15230	WRH15	Melbourne, Aus.	17825	LLN	Oslo, Norway
1027	CSA29	Lisbon, Portugal	11875	OLR4C	Prague, Czech.	15230	WRUL	Boston, U.S.A.	17830	TAQ	Ankara, Turkey
1090	CSA92	Ponta Delgada, Azores	11875	Radio Portugal		15235	BD3	Taipei, Formosa	17825	Radio Japan, Tokyo	
11455	Peking, China		11880	Moscow, U.S.S.R.		15235	JOB5	Tokyo, Japan	17830	Moscow, U.S.S.R.	
11475	ZNX5	Batavia, B.W.I.	11880	LRS	Buenos Aires, Arg.	15240	Radio China (Canton)		17830	WDSI	(VOA) New York, U.S.A.
11513	Tangier, Morocco		11880	VLG11/VLH11	Melbourne, Aus.	15240	Belgrade, Yugoslavia		17835	Karachi, Pakistan	
11515	Peking, China		11880	Horby, Sweden		15240	KCA	San Fran., U.S.A.	17840	Radio Sweden	
11630	Leningrad, U.S.S.R.		11880	XEHH	Mexico, Mex.	15240	VLH15	Melbourne, Aus.	17840	Brazzaville, Fr. Eq. Africa	
11640	All India Radio, Delhi		11880	GRE	London, England	15240	WLWO	Cincinnati, U.S.A.	17840	Moscow, U.S.S.R.	
11650	Peking, China		11880	SBP	Stockholm, Sweden	15240	Bucharest, Rumania		17840	VLJ7	Shepparton, Aus.
11670	Bangkok, Thailand		11885	APK3	Karachi, Pakistan	15250	Voice of Amer., Manila, P.I.		17840	HVC1	Vatican City
11680	HJCQ	Quito, Ecuador	11890	Moscow, U.S.S.R.		15250	WLWO	Cincinnati, U.S.A.	17850	Paris, France	
11680	GRG	London, England	11890	GWU	London, England	15250	Voice of Amer., Tangier		17860	DRU3	Brussels, Belgium
11685	Peking, China		11890	KZFJ	Manila, P.I.	15250	GSF	London, England	17865	Damascus, Syria	
11695	HP5A	Panama, Panama	11890	WBOU	New York, U.S.A.	15260	Karachi, Pakistan		17870	CSA19	Batavia, P.I.
11700	GWU	London, England	11895	FHE3	Dakar, Fr. W. Af.	15270	KCBR	Delano, Calif., U.S.A.	17870	HCJB	(Missionary Station) Quito, Ecuador
11702	Paris, France		11895	Radio Portugal		15270	Munich, Germany		17910	Grenada, Windward Is.	
11705	JOA4	Tokyo, Japan	11895	Manila, Philippines		15270	WBOU	(VOA) New York, U.S.A.	18250	TFTO	Paris, France
11705	SBP	Mexico, Sweden	11900	CE1180	Santiago, Chile	15270	Sverdlovsk, U.S.S.R.		18450	United Nations Radio, Geneva, Switzerland	
11710	Voice of America, Tangier		11900	HCJB	Calvary Radio Ministry	15280	Munich, Germany, U.S.S.R.		20088	Moscow, U.S.S.R.	
11710	VUD5/7	Delhi, India	11900	XEXE	Mexico City, Mex.	15280	ZL4	Wellington, N.Z.	21460	KNB8	(VOA) Dixon, Calif.
11710	WLWO	Cincinnati, U.S.A.	11900	Rome, Italy		15280	Moscow, U.S.S.R.		21470	GSH	London, England
11714	ZJM7	Limassol, Cyprus	11910	Budapest, Hungary		15280	Voice of Amer., Tangier		21480	Hilversum, Netherlands	
11715	HE15	Bern, Switzerland	11910	Budapest, Hungary		15285	CR7BG	Lourenco Marques, Mozambique	21490	Paris, France	
11718	Athena, Greece		11915	Radio Netherlands		15285	WBOU	(VOA) New York, U.S.A.	21500	WRCA	New York, U.S.A.
11720	PRL9	Rio de Janeiro, Brazil	11915	Damascus, Syria		15285	WBOU	(VOA) New York, U.S.A.	21510	VUD5	Delhi, India
11720	Radio Portugal		11915	HCJB	Quito, Ecuador	15290	LRU	Buenos Aires, Arg.	21520	WRU1	Boston, U.S.A.
11720	OTM4	Leopoldville, Belgian Congo	11915	Radio Portugal		15290	VUD5/9	Delhi, India	21520	WLWO	Cincinnati, U.S.A.
11720	ORY2	Brussels, Belgium	11918	BD4	Taipei, Formosa	15295	Voice of Amer., Tangier		21530	GSJ	London, England
11724	HNG	Baghdad, Iran	11924	FZ54	Salgon, Vietnam	15300	DZ18	Manila, P.I.	21540	VLB2	Shepparton, Aus.
11725	COCY	Havana, Cuba	11930	GWU	London, England	15300	Singapore, Malaysia		21550	GST	London, England
11730	GVV	London, England	11935	Warsaw, Poland		15305	HER6	Bern, Switzerland	21560	Moscow, U.S.S.R.	
11730	KGEI	San Fran., U.S.A.	11937	Bucharest, Rumania		15305	HER6	Bern, Switzerland	21560	Rome, Italy	
11730	Hilversum, Nether.		11950	Radio Netherlands		15305	Novosibirsk, U.S.S.R.		21570	WDSI	(VOA) New York, U.S.A.
11730	CE1173	Santiago, Chile	11955	YAX	San Salvador, Salv.	15310	KCBR	Delano, Calif.	21580	Horby, Sweden	
11735	BE06	Taipei, Formosa	11955	YAX	London, England	15310	GSP	London, England	21590	WGE0	Schenectady, N.Y.
11735	LK10	Federstadt, Ger.	11960	Moscow, U.S.S.R.		15320	VLG15	Melbourne, Aus.	21510	WLWO	(VOA) Cincinnati, U.S.A.
11735	Radio Free Europe, Ger.		11970	Brazzaville, Fr. Eq. Africa		15320	Moscow, U.S.S.R.		21520	Colombo, Ceylon	
11740	Moscow, U.S.S.R.		11972	T1H	San Jose, C. Rica	15320	Rome, Italy		21530	GRZ	London, England
11740	Warsaw, Poland		11975	Colombo, Ceylon		15330	KGEI	San Fran., U.S.A.	21530	WLWO	Cincinnati, U.S.A.
11740	WRUL	Boston, U.S.A.	11980	Moscow, U.S.S.R.		15330	WRU1	Boston, U.S.A.	21560	Lisbon, Portugal	
11742	CE1174	Santiago, Chile	11985	CSA32	Lisbon, Portugal	15330	WRU1	Boston, U.S.A.	21670	LLP	Dalo, Norway
11750	GSJ	London, England	11985	CE1180	Santiago, Chile	15335	Brussels, Belgium		21675	GVR	London, England
11755	Radio Portugal		1200	GRV	London, England	15335	Karachi, Pakistan		21680	VL21	Shepparton, Aus.
11760	Moscow, U.S.S.R.		1205	RF	London, England	15340	Moscow, U.S.S.R.		21690	Voice of America, Tangier	
11760	OLR4B	Prague, Czech.	1215	TFJ	Reykjavik, Iceland	15340	KCBR	Delano, Calif., U.S.A.	21700	GSV	London, England
11760	Voice of America, Tangier		14492	Radio Portugal		15340	Voice of Amer., Tangier		21730	WBOU	(VOA) New York, U.S.A.
11760	VLAI1/VLBI1		14690	PSF	Rio de Janeiro, Brazil	15345	Athena, Greece		21740	KCBR	Delano, Calif., U.S.A.
11760	VUD7/II	Delhi, India	15050	ETAA	Addis Ababa, Eth.	15345	Formosa Radio		21740	KGEI	San Fran., U.S.A.
11764	CR7BH	Lourenco Marques, Mozambique	15050	V3USE	Forest Side, Mauritius	15345	Paris, France		21750	WRU1	Boston, U.S.A.
11770	GVU	London, England	15060	Peking, China		15350	WLWO	Cincinnati, U.S.A.	25615	OE18	Linz, Austria
11770	YDE/YDF7	Djakarta, Indonesia	15070	GWU	London, England	15350	VUD8	Dethi, India	25640	HER9	Berne, Switzerland
11775	Radio Poland		15100	CSA39	Lisbon, Portugal	15352	Radio Luxemburg		25650	DM29	Cologne, West Germany
11780	BBC	London, England	15100	Moscow, U.S.S.R.		15360	London, England		25670	Sweden Radio, Stockholm	

Location	C.L. Chan.	Location	C.L. Chan.	Location	C.L. Chan.	Location	C.L. Chan.		
NEW MEXICO				TENNESSEE					
Albuquerque	KGGM-TV 13 KNME-TV 5 KOAT-TV 7 KOB-TV 4 KQV-TV 6 KVER-TV 12 KSWR-TV 8	Youngstown	WTOL-TV 11 WFMJ-TV 21 WKBN-TV 27 WKST-TV 45 WHIZ-TV 18	Chattanooga	WDEF-TV 12 WRGT-TV 3 WUTC 3 WDXI-TV 7 WJHL-TV 11 WATE-TV 10 WBIR-TV 6 WTVK 26	Hampton	WVEC-TV 13		
Carlsbad	KOB-TV 4	Zanesville	WTOL-TV 11	Jackson	WJHL-TV 11	Harrisonburg	WSVA-TV 3		
Clovis	KVER-TV 12	OKLAHOMA				Lynchburg	WLVA-TV 13		
Roswell	KSWR-TV 8	Ada	KTEN-TV 10	Knoxville	WATE-TV 10	Norfolk	WTRF-TV 9		
NEW YORK				Ardmore	KXII-TV 12	Petersburg	WXEX-TV 8		
Albany	WTEN-TV 10	Enid	KCCO-TV 5	Memphis	WHBQ-TV 13	Portsmouth	WAVY-TV 10		
Binghamton	WTRB-TV 10 WINR-TV 40 WNBZ-TV 12	Lawton	KSWO-TV 7	Nashville	WRCT-TV 10 WRCO-TV 3 WVLC-TV 5 WSIX-TV 8 WSM-TV 4	Richmond	WRVA-TV 12		
Buffalo	WBEN-TV 4 WBUF 17 WGR-TV 2 WKBW 7 WCAY-TV 7 WSTZ-TV 18 WABC-TV 7 WNEW-TV 5 WCBS-TV 2 WOR-TV 9 WPIX 11 WRCA-TV 4 WPTZ-TV 5 WHCT-TV 10 WRDC-TV 5 WVET-TV 10 WGRB 6 WHEN-TV 8 WSYR-TV 3 WKTV 13	Oklahoma City	KETA-TV 13 KOKH-TV 25 KWTW 3 WKY-TV 3 KOTV 6 KOED-TV 11 KTUL-TV 8 KV00-TV 2	Abilene	KRBC-TV 9	Roanoke	WDBJ-TV 7 WLSL-TV 10	WASHINGTON	
Carthage	WCAY-TV 7	Tulsa	KOED-TV 11 KTUL-TV 8 KV00-TV 2	Amarillo	KRBC-TV 9 KFDA-TV 10 KGNC-TV 4 KVII 7	Bellingham	KVOS-TV 12		
Elmira	WABC-TV 7	OREGON				Ephrata	KBAS-TV 16		
New York	WABC-TV 7 WNEW-TV 5 WCBS-TV 2 WOR-TV 9 WPIX 11 WRCA-TV 4 WPTZ-TV 5 WHCT-TV 10 WRDC-TV 5 WVET-TV 10 WGRB 6 WHEN-TV 8 WSYR-TV 3 WKTV 13	Corvallis	KOAC-TV 13	Austin	KTBC-TV 7	Passo	KEPR-TV 19		
Plattsburg	WRCA-TV 4	Eugene	KVAL-TV 13	Beaumont	KFDM-TV 6	Seattle	KCTS-TV 9 KING-TV 5 KIRO-TV 7 KOMO-TV 4 KHQ-TV 6 KREM-TV 2 KXLY-TV 4 KTNT-TV 11 KTWV 13 KIMA-TV 29 KNDO-TV 23		
Rochester	WRDC-TV 5	Klamath	KOTI-TV 2	Big Spring	KEDY-TV 4	WEST VIRGINIA			
Schenectady	WVET-TV 10	Medford	KBES-TV 5	Bryan	KBTX-TV 3	Bluefield	WHIS-TV 6		
Syracuse	WVET-TV 10	Portland	KGW-TV 8 KHTV 27 KOIN-TV 6 KPTV 12 KPIC 4	Corpus Christi	KRIS-TV 6 KZTV 10 KRLD-TV 4 WFAP-TV 8 KELP-TV 13 KRDD-TV 4 KTSM-TV 9	Charleston	WCHS-TV 8		
Utica	WKTV 13	Roseburg	KPIC 4	Dallas	KRLD-TV 4 WFAP-TV 8 KELP-TV 13 KRDD-TV 4 KTSM-TV 9	Clarksburg	WBOY-TV 12		
NORTH CAROLINA				TEXAS				Huntington	WHTN-TV 13
Asheville	WISE-TV 62 WLOS-TV 13 WUNC-TV 4 WBT-TV 3 WSOC-TV 5 WTVD 11 WFMY-TV 2 WNCT 9 WRAL-TV 5 WITN 7 WECT 6 WSIS-TV 12	PENNSYLVANIA				El Paso	KRFD-TV 10 KFJZ-TV 11 WBAP-TV 5 KGBT-TV 4 KPRC-TV 2 KHOU-TV 1 KTRK-TV 13 KHUHT 8 KGNB-TV 8 KQUB-TV 11 KTRV-TV 2 KMDV-TV 9 KVMK-TV 7 KOSA-TV 9	Oak Hill	WOAY-TV 4
Chapel Hill	WUNC-TV 4	Altoona	WFBG-TV 10	Ft. Worth	KFJZ-TV 11	Port Arthur-Beaumont	WPAC-TV 4	Parkersburg	WTAP-TV 15
Charlotte	WBT-TV 3	Erie	WICU-TV 12	Harrisburg	WHP-TV 55	San Angelo	KCTV 8	Wheeling	WTRF-TV 7
Durham	WTVD 11	Harrisburg	WHP-TV 55	Johnstown	WARD-TV 56	San Antonio	KCOR-TV 41 KENS-TV 5 KONO-TV 12 WQAI-TV 4 WVIA-TV 6 KCNV-TV 12 KCMC-TV 7 KLTV 7 KWTX-TV 10 KRGV-TV 5 KFDX-TV 3 KSYD-TV 6	Wilmington	WECT 6
Greensboro	WFMY-TV 2	Johnstown	WARD-TV 56	Lancaster	WARD-TV 56	San Antonio	KCOR-TV 41 KENS-TV 5 KONO-TV 12 WQAI-TV 4 WVIA-TV 6 KCNV-TV 12 KCMC-TV 7 KLTV 7 KWTX-TV 10 KRGV-TV 5 KFDX-TV 3 KSYD-TV 6	Winston-Salem	WSIS-TV 12
Greenville	WNCT 9	Johnstown	WARD-TV 56	Lancaster	WARD-TV 56	Sweetwater	WQAI-TV 4	WISCONSIN	
Raleigh	WRAL-TV 5	Johnstown	WARD-TV 56	Lancaster	WARD-TV 56	Temple	KCNV-TV 12	Eau Claire	WEAU-TV 13
Washington	WITN 7	Johnstown	WARD-TV 56	Lancaster	WARD-TV 56	Texarkana	KCMC-TV 7	Green Bay	WBBW-TV 2
Wilmington	WECT 6	Johnstown	WARD-TV 56	Lancaster	WARD-TV 56	Tyler	KLTV 7	WFRV 5	
Winston-Salem	WSIS-TV 12	Johnstown	WARD-TV 56	Lancaster	WARD-TV 56	Waco	KWTX-TV 10	La Crosse	WKBT 8
NORTH DAKOTA				RHODE ISLAND				Madison	WHA-TV 21 WISC-TV 3 WKOW-TV 27 WMTV 33
Bismarck	KBMB-TV 12 KFYR-TV 5 KDX-TV 2 WDAY-TV 5 KXGO-TV 11 KNOX-TV 10 KXNC-TV 13 KMOT 10 KXJB-TV 4 KUMV-TV 8	RHODE ISLAND				Waco	KWTX-TV 10	Marinette	WMBW-TV 11
Dickinson	KBMB-TV 12	Providence	WJAR-TV 10 WPRO-TV 12	SOUTH CAROLINA				Milwaukee	WISN-TV 12 WMVS-TV 10 WTMJ-TV 4 WPIX 18 WSAU-TV 7 WITI-TV 6
Fargo	KBMB-TV 12	Providence	WJAR-TV 10 WPRO-TV 12	Anderson	WAIM-TV 40	Wichita Falls	KFDX-TV 3 KSYD-TV 6	Wausau	WSAU-TV 7
Grand Forks	KBMB-TV 12	Providence	WJAR-TV 10 WPRO-TV 12	Charleston	WCSC-TV 5	UTAH		Whitefish Bay	WITI-TV 6
Minot	KBMB-TV 12	Providence	WJAR-TV 10 WPRO-TV 12	Columbia	WCSC-TV 5	Provo	KLOR-TV 11	WYOMING	
Valley City	KBMB-TV 12	Providence	WJAR-TV 10 WPRO-TV 12	Columbia	WCSC-TV 5	Salt Lake City	KLOR-TV 11 KSL-TV 5 KTV 4 KUED 7 KUTV 2	Casper	KTWO-TV 2
Williston	KBMB-TV 12	Providence	WJAR-TV 10 WPRO-TV 12	Columbia	WCSC-TV 5	VERMONT		Cheyenne	KFBC-TV 5
OHIO				SOUTH CAROLINA				VERMONT	
Akron	WAKR-TV 49	Anderson	WAIM-TV 40	UTAH		Burlington	WCAX-TV 3	Riverston	KWRB-TV 10
Cincinnati	WCET 48 WCPO-TV 9 WCRC-TV 12 WLW-TV 5 WCIN-TV 54 KYW-TV 3 WEWS 5 WJW-TV 8 WBNS-TV 10 WLW-C 4 WDSU-TV 34 WTWV-TV 6	Charleston	WCSC-TV 5	Provo	KLOR-TV 11	VIRGINIA		GUAM	
Cleveland	WCET 48	Charleston	WCSC-TV 5	Salt Lake City	KLOR-TV 11	Bristol	WCYB-TV 5	Agana	KUAM-TV 8
Columbus	WCET 48	Charleston	WCSC-TV 5	Salt Lake City	KLOR-TV 11	VERMONT		PUERTO RICO	
Dayton	WCET 48	Charleston	WCSC-TV 5	Salt Lake City	KLOR-TV 11	Burlington	WCAX-TV 3	Mayaguez	WORA-TV 5
Lima	WCET 48	Charleston	WCSC-TV 5	Salt Lake City	KLOR-TV 11	VERMONT		Ponce	WRIK-TV 7
Oxford	WCET 48	Charleston	WCSC-TV 5	Salt Lake City	KLOR-TV 11	VERMONT		San Juan	WSUR-TV 9
Steubenville	WCET 48	Charleston	WCSC-TV 5	Salt Lake City	KLOR-TV 11	VERMONT		WIPR-TV 6	
Toledo	WCET 48	Charleston	WCSC-TV 5	Salt Lake City	KLOR-TV 11	VERMONT		WKAQ-TV 2	

Canadian Television Stations

Location	C.L. Chan.	Location	C.L. Chan.	Location	C.L. Chan.	Location	C.L. Chan.		
ALBERTA				NEW BRUNSWICK					
Calgary	CHCT-TV 2	Winnipeg	CBWT 3	Elliot Lake	CKSO-TV-1 3	QUEBEC			
Edmonton	CFRN-TV 7	NEW BRUNSWICK				Hamilton	CHCH-TV 11		
Lethbridge	CJLH-TV 7	Moncton	CKCW-TV 2	Kapuskasing	CFCL-TV-1 11	Clermont	CFCV-TV-1 75		
Medicine Hat	CHAT-TV 6	Saint John	CHSJ-TV 4	Kingston	CKWS-TV 3	Estouart	CJES-TV-1 70		
Red Deer	CHCA-TV 6	NEWFOUNDLAND				Jonquiere	CKRS-TV 12		
BRITISH COLUMBIA				NEWFOUNDLAND				Matane	CKBL-TV 9
Dawson Creek	CJDC-TV 5	Argentia	CJQX-TV 10	North Bay	CKGN-TV 10	Montreal	CBFT 2		
Kamloops	CFCR-TV 2	Corner Brook	CBYT 5	Peterborough	CHEX-TV 12	New Carlisle	CHAU-TV 5		
Kelowna	CHBC-TV 2	St. John's	CJON-TV 6	Ottawa	CBOFT 9	Quebec	CFQM-TV 4		
Pentlton	CHBC-TV 13	Stephenville	CFSN-TV 8	Port Arthur	CFJ-TV 2	Rimouski	CKMI-TV 5		
Vancouver	CBUT 2	NOVA SCOTIA				Sault Ste. Marie	CJIC-TV 2		
Vernon	CHBC-TV 7	Halifax	CBHT 3	Sudbury	CKSO-TV 5	Ruyn	CKRN-TV 4		
Victoria	CHBC-TV 7	Inverness	CJCB-TV-1 6	Timmins	CFCL-TV 6	Sherbrooke	CHLT-TV 7		
LABRADOR				Liverpool	CBHT-1 12	Three Rivers	CKTM-TV 13		
Goose Bay	CFLA-TV 8	Shelburne	CBHT-2 8	SASKATCHEWAN					
MANITOBA				Sydney	CJCB-TV 4	Moose Jaw	CHAB-TV 4		
Brandon	CKX-TV 5	Yarmouth	CBHT-3 11	Windsor	CKLW-TV 9	Prince Albert	CKBI-TV 5		
ONTARIO				PRINCE EDWARD ISLAND				Regina	CKCK-TV 2
Barrie	CKVR-TV 3	PRINCE EDWARD ISLAND				Saskatoon	CFQC-TV 8		
Eik Lake	CFCL-TV-2 2	Charlottetown	CFCY-TV 13	PRINCE EDWARD ISLAND				Swift Current	CFJB-TV 5
ONTARIO				PRINCE EDWARD ISLAND				Yerkton	CKOS-TV 3

How to **CRACK** the education barrier



Is there an "education barrier" between you and promotion? Are young college graduates being brought in to fill positions above you?

You can break down that barrier . . . gain real security, responsibility, prestige . . . *surprise fellow employees and win their respect.* You can match yourself against the smartest of the college boys and come out a WINNER. Here's how!

AN HOUR A DAY THE I. C. S. WAY!

If you can spare an hour a day, if you have the determination to make good, if you're willing to invest pennies now for dollars later on—then I. C. S. can help you. You can be a man or woman, young or old, skilled or unskilled. So long as you

can understand simple language and illustrated training manuals, you need have no doubts. The I.C.S. hour-a-day plan is SUCCESS-PROVED. You learn while you earn—anywhere, any time.

Just pick the subject you want!

Only I. C. S. offers you such a wide range of subjects to choose from. Drafting. Engineering. Television. Aeronautics. Business. High School. 258 courses in all. *I. C. S. is the oldest, largest home-study school. It is also the best known in business and industry.*

Free catalog plus free books!

When you mail the coupon below, you get a complete catalog on the subject you check with information about employment opportunities, training requirements, etc. And you get "How to Succeed"—36 pages of valuable tips on winning recognition, pay raises, success. Also, a free sample lesson in basic mathematics.

For Real Job Security—Get an I. C. S. Diploma! I. C. S., Scranton 15, Penna. Accredited Member, National Home Study Council

INTERNATIONAL CORRESPONDENCE SCHOOLS



BOX 62248A, SCRANTON 15, PENNA.

(Partial list of 258 courses)


Without cost or obligation, send me "HOW TO SUCCEED" and the opportunity booklet about the field BEFORE which I have marked X (plus sample lesson):

- | | | | | |
|--|--|--|--|---|
| <p>ARCHITECTURE and BUILDING CONSTRUCTION</p> <ul style="list-style-type: none"> <input type="checkbox"/> Air Conditioning <input type="checkbox"/> Architecture <input type="checkbox"/> Arch. Drawing and Designing <input type="checkbox"/> Building Contractor <input type="checkbox"/> Building Estimator <input type="checkbox"/> Carpenter Builder <input type="checkbox"/> Carpentry and Millwork <input type="checkbox"/> Carpenter Foreman <input type="checkbox"/> Heating <input type="checkbox"/> Painting Contractor <input type="checkbox"/> Plumbing <input type="checkbox"/> Reading Arch. Blueprints <p>ART</p> <ul style="list-style-type: none"> <input type="checkbox"/> Commercial Art <input type="checkbox"/> Magazine Illus. <input type="checkbox"/> Show Card and Sign Lettering <input type="checkbox"/> Sketching and Painting <p>AUTOMOTIVE</p> <ul style="list-style-type: none"> <input type="checkbox"/> Automobile <input type="checkbox"/> Auto Body Rebuilding and Refinishing <input type="checkbox"/> Auto Engine Tuneup <input type="checkbox"/> Auto Technician | <p>AVIATION</p> <ul style="list-style-type: none"> <input type="checkbox"/> Aero-Engineering Technology <input type="checkbox"/> Aircraft & Engine Mechanic <p>BUSINESS</p> <ul style="list-style-type: none"> <input type="checkbox"/> Accounting <input type="checkbox"/> Advertising <input type="checkbox"/> Business Administration <input type="checkbox"/> Business Management <input type="checkbox"/> Cost Accounting <input type="checkbox"/> Creative Salesmanship <input type="checkbox"/> Managing a Small Business <input type="checkbox"/> Professional Secretary <input type="checkbox"/> Public Accounting <input type="checkbox"/> Purchasing Agent <input type="checkbox"/> Salesmanship <input type="checkbox"/> Salesmanship and Management <input type="checkbox"/> Traffic Management <p>CHEMICAL</p> <ul style="list-style-type: none"> <input type="checkbox"/> Analytical Chemistry <input type="checkbox"/> Chemical Engineering <input type="checkbox"/> Chem. Lab. Technician <input type="checkbox"/> Elements of Nuclear Energy <input type="checkbox"/> General Chemistry <input type="checkbox"/> Natural Gas Prod. and Trans. <input type="checkbox"/> Petroleum Prod. and Engr. <input type="checkbox"/> Professional Engineer (Chem) <input type="checkbox"/> Pulp and Paper Making | <p>CIVIL ENGINEERING</p> <ul style="list-style-type: none"> <input type="checkbox"/> Civil Engineering <input type="checkbox"/> Construction Engineering <input type="checkbox"/> Highway Engineering <input type="checkbox"/> Professional Engineer (Civil) <input type="checkbox"/> Reading Struc. Blueprints <input type="checkbox"/> Sanitary Engineer <input type="checkbox"/> Structural Engineering <input type="checkbox"/> Surveying and Mapping <p>DRAFTING</p> <ul style="list-style-type: none"> <input type="checkbox"/> Aircraft Drafting <input type="checkbox"/> Architectural Drafting <input type="checkbox"/> Drafting & Machine Design <input type="checkbox"/> Electrical Drafting <input type="checkbox"/> Mechanical Drafting <input type="checkbox"/> Sheet Metal Drafting <input type="checkbox"/> Structural Drafting <p>ELECTRICAL</p> <ul style="list-style-type: none"> <input type="checkbox"/> Electrical Engineering <input type="checkbox"/> Elec. Engr. Technician <input type="checkbox"/> Elec. Light and Power <input type="checkbox"/> Practical Electrician <input type="checkbox"/> Practical Lineman <input type="checkbox"/> Professional Engineer (Elec) <p>HIGH SCHOOL</p> <ul style="list-style-type: none"> <input type="checkbox"/> High School Diploma | <ul style="list-style-type: none"> <input type="checkbox"/> Good English <input type="checkbox"/> High School Mathematics <input type="checkbox"/> High School Science <input type="checkbox"/> Short Story Writing <p>LEADERSHIP</p> <ul style="list-style-type: none"> <input type="checkbox"/> Industrial Foremanship <input type="checkbox"/> Industrial Supervision <input type="checkbox"/> Personnel-Labor Relations <input type="checkbox"/> Supervision <p>MECHANICAL and SHOP</p> <ul style="list-style-type: none"> <input type="checkbox"/> Diesel Engines <input type="checkbox"/> Gas-Elec. Welding <input type="checkbox"/> Industrial Engineering <input type="checkbox"/> Industrial Instrumentation <input type="checkbox"/> Industrial Metallurgy <input type="checkbox"/> Industrial Safety <input type="checkbox"/> Machine Shop Practice <input type="checkbox"/> Mechanical Engineering <input type="checkbox"/> Professional Engineer (Mech) <input type="checkbox"/> Quality Control <input type="checkbox"/> Reading Shop Blueprints <input type="checkbox"/> Refrigeration and Air Conditioning <input type="checkbox"/> Tool Design <input type="checkbox"/> Tool Making <p>RADIO, TELEVISION</p> <ul style="list-style-type: none"> <input type="checkbox"/> General Electronics Tech. | <ul style="list-style-type: none"> <input type="checkbox"/> Industrial Electronics <input type="checkbox"/> Practical Radio-TV Eng'g <input type="checkbox"/> Practical Telephony <input type="checkbox"/> Radio-TV Servicing <p>RAILROAD</p> <ul style="list-style-type: none"> <input type="checkbox"/> Car Inspector and Air Brake <input type="checkbox"/> Diesel Electrician <input type="checkbox"/> Diesel Engr. and Fireman <input type="checkbox"/> Diesel Locomotive <p>STEAM and DIESEL POWER</p> <ul style="list-style-type: none"> <input type="checkbox"/> Combustion Engineering <input type="checkbox"/> Power Plant Engineer <input type="checkbox"/> Stationary Diesel Engr. <input type="checkbox"/> Stationary Fireman <p>TEXTILE</p> <ul style="list-style-type: none"> <input type="checkbox"/> Carding and Spinning <input type="checkbox"/> Cotton Manufacture <input type="checkbox"/> Cotton Warping and Weaving <input type="checkbox"/> Loom Fixing Technician <input type="checkbox"/> Textile Designing <input type="checkbox"/> Textile Finishing & Dyeing <input type="checkbox"/> Throwing <input type="checkbox"/> Warping and Weaving <input type="checkbox"/> Worsted Manufacturing |
|--|--|--|--|---|

Name _____ Age _____ Home Address _____

City _____ Zone _____ State _____ Working Hours _____ A. M. to P. M.

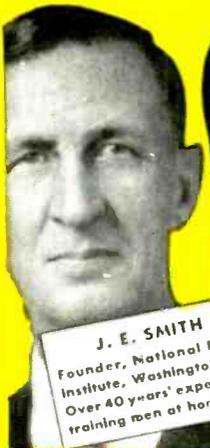Occupation _____ Canadian residents send coupon to International Correspondence Schools, Canadian, Ltd., Montreal, Canada. . . . Special low monthly tuition rates to members of the U. S. Armed Forces.



J. E. SMITH
 Founder, National Radio
 Institute, Washington D.C.
 Over 40 years' experience
 training men at home.

Mail Postage-Free Card for
SAMPLE LESSON FREE
Shows you how easy, practical it is to
**Train at Home for RADIO
 TELEVISION ELECTRONICS**

**Oldest and Largest Home Study Radio-
 Television Training School. N.R.I. has
 Trained Thousands for Good Pay Jobs**

Since 1914 . . . for more than 40 years—N.R.I. has been training ambitious men at home in spare time for Radio-TV. Let us send you a sample lesson to help prove you can keep your job and TRAIN AT HOME in your spare time for better pay and a brighter future. We will also send N.R.I.'s 64-page catalog to show you that Radio-Television is today's field of OPPORTUNITY for properly trained men.



Television Making Good Jobs, Prosperity

The technical man is looked up to. He should be. He does important work, is respected for what he knows, gets good pay for it. There are splendid opportunities for the man well trained in Radio-Television Servicing or Broadcasting. Government, Aviation, Police, Ship, Micro-Wave Relay, Two-Way Communications for buses, taxis, trucks are growing Radio-TV fields, making more good jobs.

N.R.I. is the Tested Way to Better Pay

N.R.I. Training is practical, thorough. You get the benefit of N.R.I.'s 40 years' experience. Many successful N.R.I. men start without any knowledge of Radio, many without high school education. Find out what Radio-Television training can mean to you. Make the first move today toward becoming one of that select group—a Radio-TV Technician. Send postage-free card for Actual Lesson and 64-page Catalog, both FREE. NATIONAL RADIO INSTITUTE, Dept. 0883, Washington 16, D. C.

WHAT N.R.I. GRADUATES DO AND SAY



Has Own Radio-TV Business

"We have an appliance store with Radio-TV servicing. During army service, NRI training helped me get too rated job."—W. M. WEIDNER, Fairfax, S. D.



Chief Engineer with KCCU


"I am Chief Engineer with station and also have my own radio & tube servicing business."—R. BARNETT, Bismarck, N. D.



Paid for instruments from Earnings

"I am doing very well in spare time. Sometimes have three TV jobs, waiting also for car. Radio-TV."—P. BEAMAN, N. Y. N. Y.

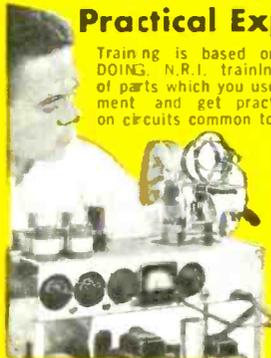**Without Extra Charge
 NRI Sends Equipment for
 Practical Experience**



Training is based on LEARNING-BY-DOING. N.R.I. training includes kits of parts which you use to build equipment and get practical experience on circuits common to both Radio and Television. Shown at left is low-power Broadcasting Transmitter you build as part of N.R.I. Communications Course. FREE Catalog shows other equipment you get, things you learn.

See Other Side

FIRST CLASS
 Permit No. 20-R
 (Sec. 349, P.L. 83)
 Washington, D.C.

BUSINESS REPLY CARD
 No Postage Stamp Necessary If Mailed In The United States

POSTAGE WILL BE PAID BY
NATIONAL RADIO INSTITUTE
 Washington 16, D. C.




Learn Radio Television Electronics

by Practicing at Home

N.R.I. SENDS KITS with which you practice building circuits, common to Radio and Television. You LEARN-BY-DOING. As part of N.R.I. Servicing Course, you build Vacuum Tube Voltmeter and AC-DC Receiver shown here.

2 BOOKS FREE

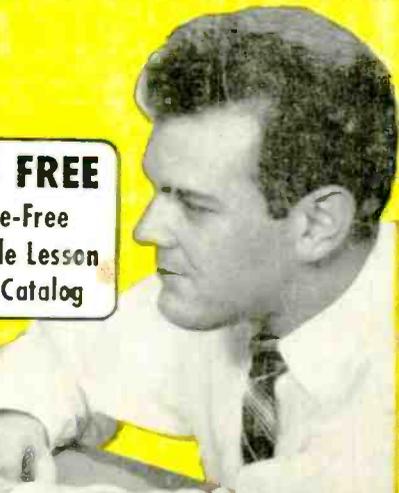Mail Postage-Free
Card for Sample Lesson
and 64 Page Catalog



Fast Growing Field Offers You Good Pay, Success, Bright Future

Bigger than ever and still growing. That's why Radio-Television has special appeal to ambitious men not satisfied with their future prospects. More than 4,000 Radio and TV Stations use trained technicians. 150 million home and auto Radios and 40 million TV sets must be kept in service. Color TV promises added opportunities. There are good jobs, bright futures in Radio-TV Servicing or Communications. Training PLUS Opportunity is the ideal combination for success. Plan now to get into Radio-TV. The technical man is looked up to, does important work, gets good pay. Keep your job while training. With N.R.I. you learn at home in spare time. N.R.I. is the OLDEST and LARGEST home study Radio-TV school. Its methods have proved successful for more than 40 years.



J. E. SMITH,
Founder, N.R.I.



See Other Side

Many Good Jobs in Radio-TV Servicing and Communications for Trained Men



CUT OUT AND MAIL THIS CARD NOW

Sample Lesson & 64-Page Catalog

Both FREE

NO STAMP NEEDED—WE PAY POSTAGE

NATIONAL RADIO INSTITUTE
Dept. 0883, Washington 16, D. C.

Mail me Sample Lesson and 64-page Catalog. (No salesman will call. Please write plainly.)

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL



Start Soon to Make \$10—\$15 a Week Extra in Your Spare Time

Soon after enrolling, many N.R.I. students start to earn \$10, \$15 a week in spare time fixing sets for friends and neighbors. Some make enough to start their own full time Radio-TV shops. Easy-to-understand lessons teach you basic principles. You LEARN-BY-DOING on N.R.I. equipment which "brings to life" things you study.

Find out what N.R.I. offers. Study fast or slow—as you like. Diploma when you graduate. Mail postage-free postcard now. ACTUAL LESSON FREE. Also 64-page catalog that shows opportunities, equipment you get. Cost of N.R.I. courses low. Easy terms. NATIONAL RADIO INSTITUTE, Dept. 0883, Washington 16, D. C.