

LOOP WORKS ANY SET, EVEN CRYSTAL By **Chester Charlton**

RADIO WORLD

Title Reg. U. S. Pat. Off.

VOL. 6. NO. 3. ILLUSTRATED EVERY WEEK

Thirteen Practical Stunts for Home Constructors

By Herman Bernard

The Simplest 3-Tube Set

By Wainwright Astor

Wave's Peak or Bust (Radio-Frequency for the Beginner)

By N. N. Bernstein

A 2-Tube-and-Crystal Reflex


By Byrt C. Caldwell

Photo of Radio Industries' Banquet




REFLEXING THE PANEL—"Lips that touch rouge" make the hard rubber do double duty.

Why it is Better

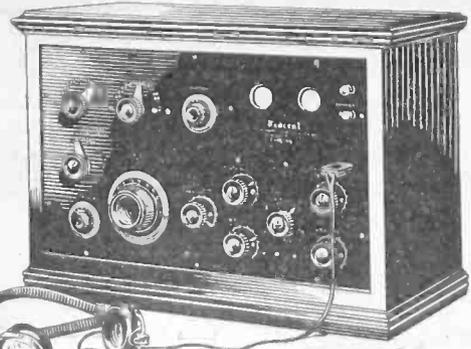

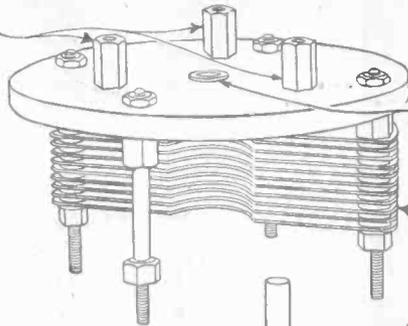Original three point suspension assuring perfect alignment which prevents buckling or short circuiting of plates and affords 7/16 inch air dielectric between condenser head and panel. Template furnished with each condenser.



This is the rotor bearing with extra-long brass bushing, machine centered, true to 1/1000 of an inch.

Both rotor and stator plates are of aluminum of practically constant surface resistance, each held rigidly by large draw-bolts thus eliminating the use of solder and its inherent resistance.

All burrs are automatically removed from plates during a pack annealing process employed to straighten plates after punching.

Plates are micrometer calipered; positively insuring true spacing.

Over-size, hard brass jam nut affording a positive lock for rotor plates.

Special hexagon bearing lock nut.

Full quarter inch circular bakelite heads—die-tapped and jig centered.

Machine ground male cone bearing. Self centering.

Exclusive female cone bearing, machine centered and provided with "star" spring to compensate for wear.

Special jam nut and rotor terminal

Federal 11 plate and 21 plate have minimum capacities never exceeding 10 micro-microfarads, while the minimum capacity of the 43 plate condenser is always less than 15 micro-microfarads.

"Star" spring of special tempered steel to automatically correct alignment and maintain positive electrical contact.

Look for this sign



LOOK at this illustration—see for yourself the eleven distinctive features in the construction of the Federal Condenser. Every feature is a distinct point of superiority—essential to clear, sharp tuning and clear reception. You can get the outstanding advantages of

Federal Tone and Federal Selectivity in your pet hook-up *only by insisting* on Federal Parts. There are over 130 Federal Standard Radio Parts bearing the Federal iron-clad performance guarantee. Use them—for your own protection and enjoyment.


FEDERAL TELEPHONE & TELEGRAPH CO.
BUFFALO, N. Y.

Boston New York Philadelphia Pittsburgh Chicago
San Francisco Bridgeburg, Canada



Federal

Standard RADIO Products

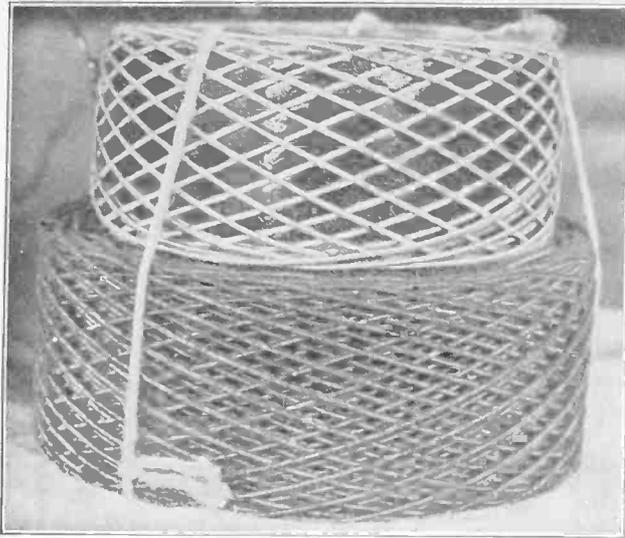

(Foto Topics)

GRAPHIC photo showing the difference between a honeycomb coil and a duolateral coil. The honeycomb coil is on top. Its windings seem to constitute only a single layer, though there are two layers in this 25-turn coil. The reason is that the two layers are wound so that one wire is exactly parallel with and atop of that on the corresponding under layer. But the lower coil, which has 75 turns, is of duolateral design, that is, each succeeding layer is so wound that its corresponding turns of wire are to one side of the turns of the under layer. One wire of a given layer is centered over two wires of the preceding layer. The duolateral coil reduces the distributed capacity present in the honeycomb variety.

It's Easy to Cut and Drill RADION PANELS

No special tools are required. Common house tools will turn out a clean hole and a straight edge, with no chipping.

There are 18 stock sizes to select from—literally a size for every set. This means less cutting and little waste, sometimes a definite saving in real money.

Exhaustive research has shown that RADION excels other insulations in the important electrical and mechanical characteristics. It's worth while to ask for RADION Panels and Parts. Be sure to get only the genuine.

Do not accept inferior so-called hard rubber panels that are not RADION and that do not have the insulating values of RADION.

American Hard Rubber Co.
11 Mercer Street New York

18 STOCK SIZES
Mahogany and Black

3/16 x 6 x 7	3/16 x 7 x 21
3/16 x 6 x 10½	3/16 x 7 x 24
3/16 x 6 x 14	3/16 x 7 x 26
3/16 x 6 x 21	3/16 x 7 x 30
3/16 x 7 x 9	3/16 x 7 x 48
3/16 x 7 x 10	3/16 x 8 x 26
3/16 x 7 x 12	1/4 x 8 x 40
3/16 x 7 x 14	1/4 x 10 x 36
3/16 x 7 x 18	1/4 x 20 x 24



Look for this stamp on every genuine RADION panel. Beware of substitutes and imitations!


RADION

Panels, Dials, Knobs, Sockets, Insulators

FRESHMAN MASTERPIECE

It's Easy to Build

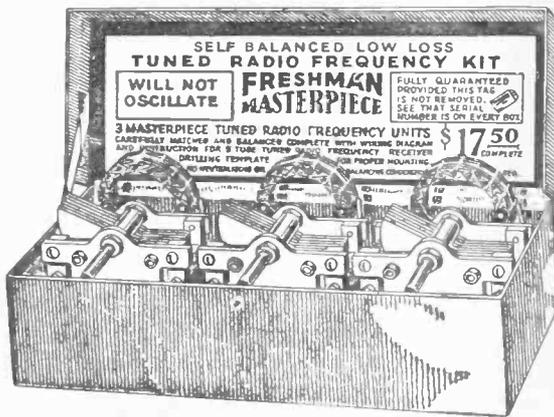a five tube radio frequency receiver when you use the Freshman Masterpiece Kit



No Neutralizing or Balancing Condensers Required

when you build with this kit to produce a radio frequency receiver that will bring in even the most distant stations with the volume and clarity of locals. So selective that stations can be brought in day after day at the same dial settings. A set that will be the equal, if not the superior, to any 5 tube receiver on the market, and what's more, it's the easiest set in the world to operate.

Kit consists of 3 Masterpiece Tuned Radio Frequency Units carefully matched and balanced. Complete with wiring diagram and instructions for building any 5 tube tuned radio frequency receiver and also drilling template for proper mounting....

\$17.50

Each and every Freshman Masterpiece Coil bears a serial number and Trademark—our guarantee of electrical and mechanical perfection. Every genuine Freshman Coil is made of specially insulated wire to prevent short-circuiting, so often caused by inferior coils. For your protection demand only the genuine.

At your dealers, otherwise send purchase price and you will be supplied without further charge.

CHAS. FRESHMAN CO., INC., 106 Seventh Ave., New York.

VOLUME SIX OF
RADIO WORLD

[Entered as second-class matter, March 28, 1922, at the Post Office at New York, N. Y., under the Act of March 3, 1879]

A Weekly Paper Published Every Wednesday and Dated Saturday, by Hennessy Radio Publications Corporation from Publication Office, 1493 Broadway, New York, N. Y. Phones: Lackawanna 6976 and 2063.

Vol. VI. No. 3. Whole No. 133.



October 11, 1924

15c. per copy, \$6.00 a year


Recipes for Cooking Up Some Stunts in Your Home

13 Little Thrills for You


By Herman Bernard

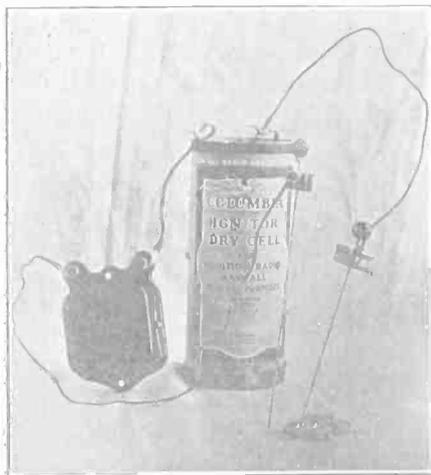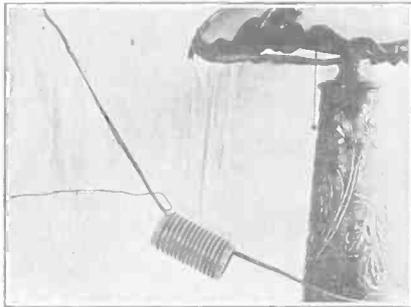

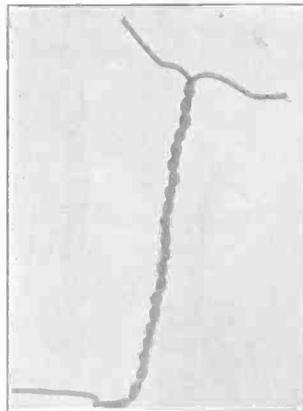TESTING DEVICE—Even the humble hatpin may be used in testing for short or open circuits. In photo the positive A is connected to a clip on the pin, the negative A going to one side of the buzzer, the other side of the buzzer to another pin. The beaded tips are good insulators. A fixed condenser is in foreground, prior to a short-circuit test.



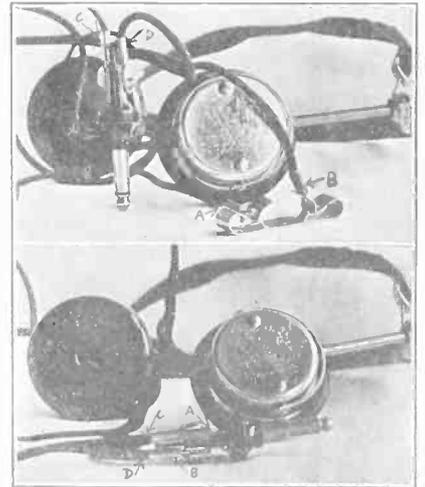SMALL VARIABLE CONDENSER—By twisting two insulated pieces of wire together, as shown, you make a condenser. The insulation and air between turns is the dielectric. Lamp cord or bell wire may be used or any other large-sized wire. By adding more twists the capacity is increased, and by reducing the number it is lowered. This is a serviceable neutralizing condenser.



MULTIPLE PHONES—Top photo shows right way to connect two or more sets of earphones, i. e., in series, which lowers resistance. One of the tips of each phone (C) goes to the plug, as does one tip (D) of the other set of phones. The free tips (A and B) are connected by a clip. Bottom photo shows wrong way, i. e., parallel connections, both tips of both phones going to the plug.

HERE is an assortment of suggestions for solving difficulties or providing substitute means of accomplishing results or introducing novelties that will be gratifying to the experimenter:

1. Two hatpins, wire, a buzzer and two clips provide an excellent testing device handy in hunting for short circuits, etc. The beaded tips of the hatpins are excellent insulation and it is these one should grip in making tests. The buzzer may be bought in any electrical store and is inexpensive. The connected wire should be stranded and insulated, e. g., lamp cord. One wire goes from the positive post of a dry cell to one hatpin, another from the negative to one side of the buzzer and the third from the remaining uncon-

nected side of the buzzer to the other hatpin. A fixed condenser may be easily tested for a short circuit, denoted by the buzzing sound. Here is where silence is gratifying.

2. Two pieces of insulated wire may be twisted together, say 4 or 5" strips of No. 18 insulated. The terminals at one end are connected in a circuit, the other terminals remaining free. By untwining one decreases capacity, but twining more wire one increases capacity. This device may be used as a neutralizing condenser.

3. Phones in multiple connection should be in series; for lower resistance, hence better volume, not in parallel. Say two phones are used. Do not

A Baker's Dozen of Tests to Delight Any Experimenter

Who Likes Odd Tricks That Really Work


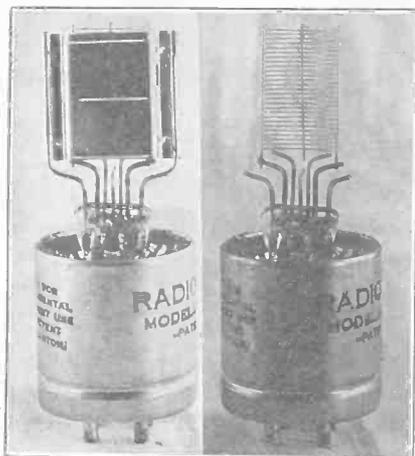
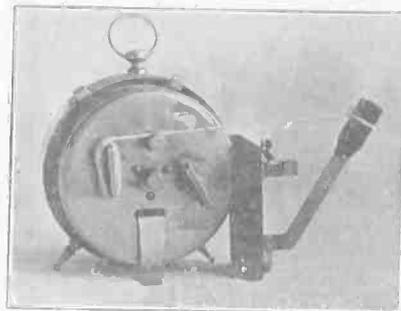


PLATE AND GRID of a vacuum tube. The plate, at left, is solid. The grid is a thin zig-zag wire, thus accounting for the familiar circuit symbol.

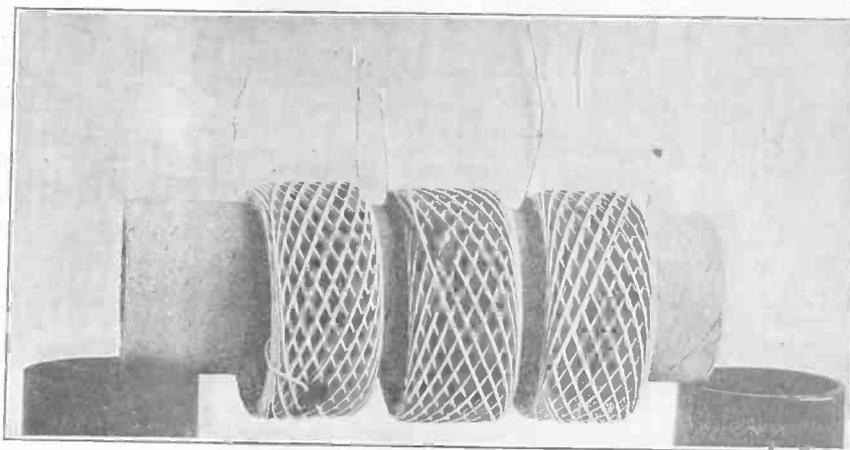

AN RF TRANSFORMER may be made of honeycomb coils. A good way is to put a 25-turn coil in the middle of a cardboard tubing and two 35-turn coils at the ends. Connect the outside coils in series. The coupling may be as shown or may be closer.

place one tip of each phone in the plate lead and the remaining tips in the B+ lead, but connect only two tips in the plug, one tip of each phone going to plate and B+ respectively, the two remaining tips being connected together, preferably by a clip.

4. A radio-frequency transformer for a tuned stage may be made of three honeycomb coils. A 25-turn coil is placed in the center of a 2" cardboard tube. At either end is a 35-turn coil. The terminal of one 35-turn coil (the wire emerging on the outside of the winding) is connected to the beginning of the other 35-turn coil (the wire emerging from under the winding). The middle coil is the primary. The free leads of the 35-turn coils go to the variable 23-plate condenser. Distance between coils should not exceed 3/8". Close coupling is all right. The tubing may be omitted and the coils tied together with linen thread.


5. One may learn much about the vacuum tube by carefully breaking the glass from a burnt-out tube, the plate is solid metal. The grid is zigzagged thin wire. The electrons flow from the negative grid to the positive plate.

6. The frame of an audi-frequency transformer may be grounded to rid a set of AF howls caused by magnetic feedback or inter-capacity action or eddy currents. These are short-circuited to the ground.

7. As electrons in a tube flow from negative to positive, if a magnet is placed against the tube glass, at the plate side, the attraction of electrons is greater, that is, the flow increases. Greater signal strength and sensitivity are obtained.

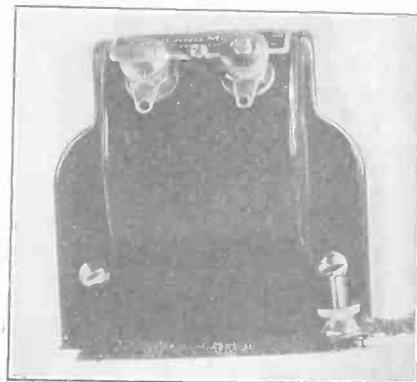8. A burnt-out tube may be utilized by breaking away all the glass and elements and attaching a

GROUNDING the frame of an audio-frequency transformer often has the effect of ditching stray impulses, such as those arising from magnetic coupling between the secondary and other inductive parts of the set, and preventing capacitive feedback which may be the cause of audio howls in a set. In some makes of audio-frequency transformers the laminations on which the core is built may be grounded instead of the frame. Often greatly improved results in clarity are obtained.



flashlight bulb socket to the base. Two wires connect the socket terminals to the filament leads in the base. Thus, is 1 1/2-volt A batteries are used, an A battery circuit may be tested. If a tube "goes" it will be only a cheap flashlight one, not a radio tube.

9. A fixed condenser in parallel with a coil boosts the wavelength. Thus if your set fails to reach the higher waves you have that remedy. A small variable condenser may be used. This gives vernier effect. If an untuned primary is to be boosted a .001 mfd. fixed condenser will set your dial readings back about 5 degrees. If a tuned primary is to be shunted the condenser should be .0001 or less, or the twisted wire device may be used.

10. A battery clips are handy, especially on storage batteries, for then you do not soil your hands with corrosion. The leads may be soldered to the

Hints for Home Consumption

end of the clips and the clips clipped to the battery terminals. Mark one clip + and join it to the red post of the storage battery.

11. A vernier may be made from a dowel (a small round wooden stick) and a circle of rubber such as is used to prevent a pencil from falling out of your




ELECTRONS are supposed to flow from negative to positive, hence the positively charged plate attracts them from the grid. By placing a magnet, as shown, on the plate side of the bulb the electronic flow is facilitated. This device was popular several years ago, but it draws laughs nowadays from newcomers in radio who do not think such a thing possible.



A TEST LAMP may be used in this fashion, the lamp socket being placed on the base of a destroyed tube

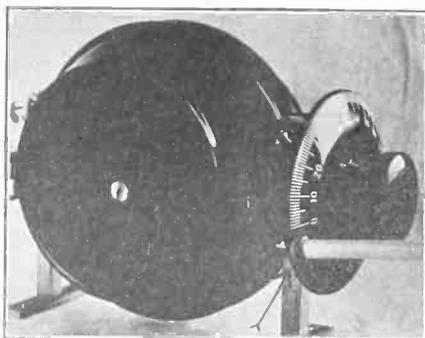A VERNIER effect may be successfully obtained by using a dowel at the end of which is a circular band of rubber, such as is used most commonly for keeping a pencil or fountain pen from falling out of your pocket. The dowel is a short wooden rod. The rod is rotated, with the rubber held against the periphery of the dial. Thus a much finer control is obtained than is possible from the unaided hand




pocket. Slip the rubber collar on the end of the stick and turn the dial by rotating the stick, with the rubber collar against the dial rim.

12. If you want to be awakened in time to tune in the 7:30 A. M. setting-up exercises broadcast from some enterprising station, you can be awakened by an alarm clock (that is, I hope you can) and the alarm clock can get your set going. Tune in to the station the night before, disconnect your A battery switch, connect the switch to the winding arm of the alarm clock with string, and when the arm turns, on account of the bell ringing, it will pull the switch and—get up, you lazy bones!

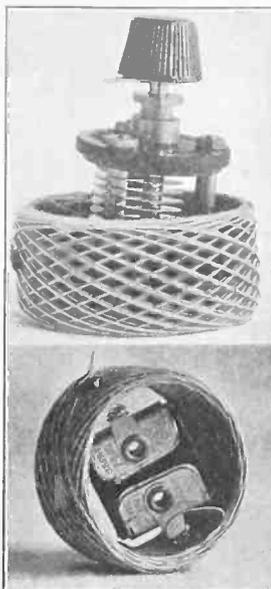
13. For an aerial, put 20 or 30 turns of wire on a tubing and slide the tubing over the electric lamp cord. Connect one end of the wound wire to the set.

The C Battery Is No Panacea

SOME fans believe that a C battery always will improve results. The efficiency of an audio frequency amplifier is not always improved by a C battery. If the plate voltage is not high a C battery will produce no improvement, but is likely to cause distortion. The advantage of a C battery is that it makes it possible to use a higher B battery voltage, giving an increased volume with minimum distortion. The chief purpose of a C battery is to reduce distortion. It also reduces consumption of the B battery current.



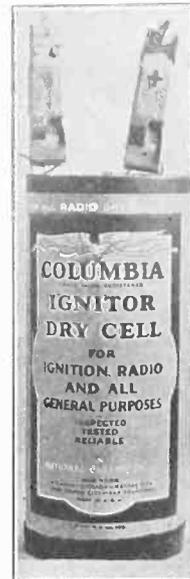INCREASING WAVELENGTH may be accomplished with a fixed or small variable condenser across the coil terminals, i. e., in parallel with the coil. The small variable condenser really serves as a vernier



CLIPS may be attached to A battery terminals to facilitate connections. This is most important when storage batteries are used.

Why Coil Never Is Pure Inductance


IN each turn of wire wound in the form of a coil with insulation between the windings there exists an electrical quality known as "distributed capacity." When there are a great number of parallel turns the capacity is greater. Two electrical conductors which are at different potentials have capacity between them. The electrical energy is stored up in the insulating material between the turns of wire. The turns of wire act as two plates of a small condenser. This results in a series of small capacities distributed along the length of the coil, and these capacities added up make the total or "distributed capacity" of a coil. Therefore, a coil is not a pure inductance because it has capacity across the terminals equal to its distributed capacity. In calculating the wavelength of a coil not only the amount of wire must be considered but also the resistance and distributed capacity.

Sodion Tube Needs No Grid Leak

A **NEGATIVE** charge of electricity does not accumulate around the grid of the Sodion tube as it does on the grid of ordinary vacuum tubes. The purpose of a grid leak in connection with vacuum tubes is to serve as a path for the negative charges to leak off the grid automatically. Since there is no tendency for negative charges to gather on the grid of the Sodion tube, a grid leak is not required. If the Sodion tube is used in a standard circuit the grid leak should be removed. If it is left in the circuit the operator should reverse the A battery connections so that the grid return connects to the negative terminal of the socket. This wire generally connects to the positive filament terminal in ordinary vacuum tube detector sets.

1-Dial DX Set Works Speaker

FIG. 1.—Wiring diagram for a single-dial set, operating a loud speaker. As it is regenerative it is good for DX. It is a simple circuit to wire and may be accommodated on a 7x7" panel. It is an inviting circuit for any one who desires to make his first 3-tube set. The veteran would prefer something fancier. The circuit was devised by Colpitts and named for him. Regeneration is controlled by the rheostat R2. R1 is the grid leak, which should be variable for 199 or 299 tubes, 1/2 to 10 megohms.

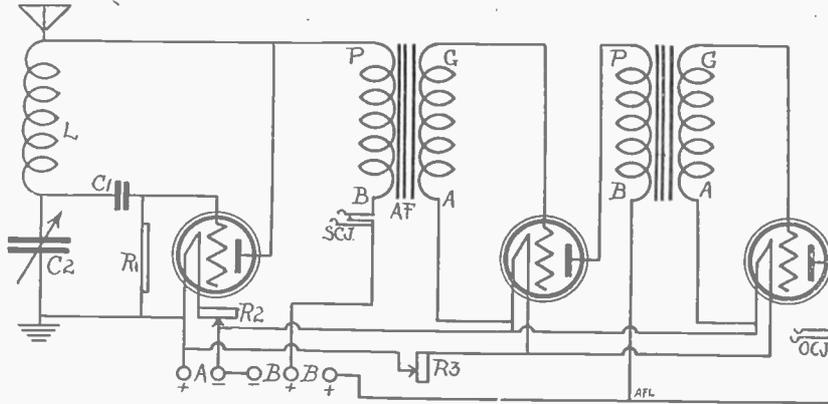

THE A+ and A- are shown, with the B- and the A- connected (lower left of diagram). Then, reading to the right, are two B+ posts. The first is the B+ for detector, the last the B+ for amplifier. Two 45-volt batteries are connected, the - of one to the + of the other. The remaining minus goes to A-, the remaining plus to OCF and B of the second AFT (at right, top). The tap for the detector is taken from one + post of the B battery whose - lead goes to A-. B- may go to A+ instead.

By Wainwright Astor

THE simplest possible 3-tube set, comprising a detector tube and two stages of transformer-coupled AF, is still a very efficient one. A single dial is used. As the circuit is regenerative, and as all regenerative circuits must have some method of varying the regeneration, the rheostat, R2, is used for that purpose. The set is selective enough for all ordinary needs, produces good signal quality and considerable volume, especially if 201A, or 301A type tube is used. The set works well with 199 or 299 tubes, also with the 11 and 12 tubes. As the rheostat R3 controls the two audio-frequency tubes, those at extreme right in Fig. 1, its resistance should be about half as much as would be necessary if only one tube were controlled thereby.

The coil L is a 100-turn honeycomb or duolateral.

Notice that the grid leak R1, instead of being connected as usual across the grid condenser C1, goes from the grid post of the detector socket to the A+. This is to keep the high voltage of the plate circuit off the grid, where it might paralyze the tube. The connection may be made from socket post to socket post. The leak normally would be 2 megohms, but if 199 or 299 tube is used as detector it must be above 3 megohms and a variable one, going up to 5 or more, should certainly be used.

Properly wired, this set is capable of good DX work, 500 miles being obtained on the loudspeaker without trouble, in cold weather.

Panel Layout

The detector rheostat is mounted at left, under the variable condenser dial, and the AF rheostat at right, on the panel, as shown (Fig. 2). The mounting holes are for fastening the baseboard to the panel with wood screws. The jacks are placed at right and left, near the top of the panel. The diagram gives the dimensions. The jack at left is for the detector circuit, so that earphones may be used.

Assembly Plan

A terminal strip is used for connecting the leads from the set to the aerial and ground and the batteries. Holes are bored in the back of the cabinet to let these insulated leads emerge, and they should be preferably stranded insulated wire, like lamp cord. The position of the three sockets are shown (Fig. 3), with 199 or 299 tubes used. If other tubes are to be employed the sockets would be placed in the same relative position, only the filament posts on the sockets would be on the same plane, instead of diagonally opposite, which is a 199 and 299 characteristic.

The coil is mounted in back of the variable condenser, preferably more than 1" away, to prevent interplay of currents between coil and condenser. AFT represents the audio-frequency transformers, which are merely symbolized, as they would take up more relative room than shown. However, all the parts fit on the baseboard, which is 6 1/2" wide by 7" deep. The rheostat at left is for the detector, the one at right for the amplifiers.


Wiring Directions

1. Connect the A- to one terminal of the detector rheostat, R2, the other leg of the rheostat going to the F- post of the detector tube socket, the socket at extreme left in Figs. 1 and 3. Connect the positive A battery post directly to the F+ post on the detector socket, then to one side of the amplifier


2. Connect the battery negative post directly to the F- posts of the amplifier tube sockets and join the remaining unconnected side of R3 to the F+ posts on these two sockets. Join the B- and A-. This completes the A battery wiring. Be careful that the F+ goes direct from the battery to the F+ post on the detector socket and that the negative A goes direct from battery to the F- posts of the amplifier sockets.

3. Connect the aerial to the beginning of the winding of the coil L. The beginning emerges from under the winding, the end from the top or outside layer of the winding. The aerial also goes to the plate of the detector tube and to the P post of the first AFT. All audio-frequency transformers are marked with either or both of the following sets of designation: P or P1, B or P2, G or S1, F or S2. P represents the primary and S the secondary, where numerals are used. Otherwise P means plate, B means B battery plus, G means grid and F means filament minus. Now connect the B of the first AFT to one side of the single closed-circuit jack. The other side of the jack, the side to which the spring connects when the plug is out, goes to the B+22 1/2 volts.

(Concluded on next page)

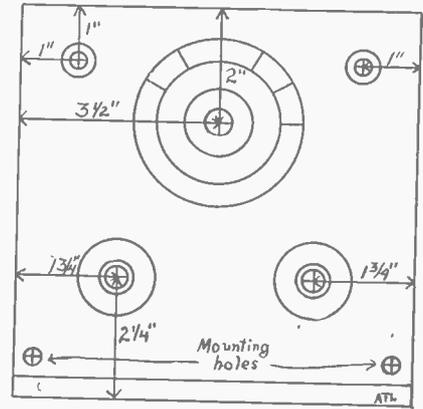


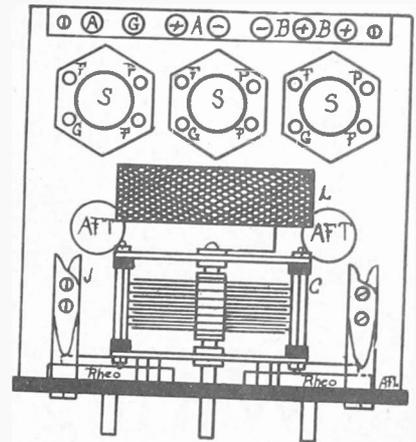PANEL LAYOUT, showing also holes for mounting the baseboard to the panel.



ASSEMBLY PLAN, with the audio-frequency transformers designated in the circles.

Loop Makes Any Set Work

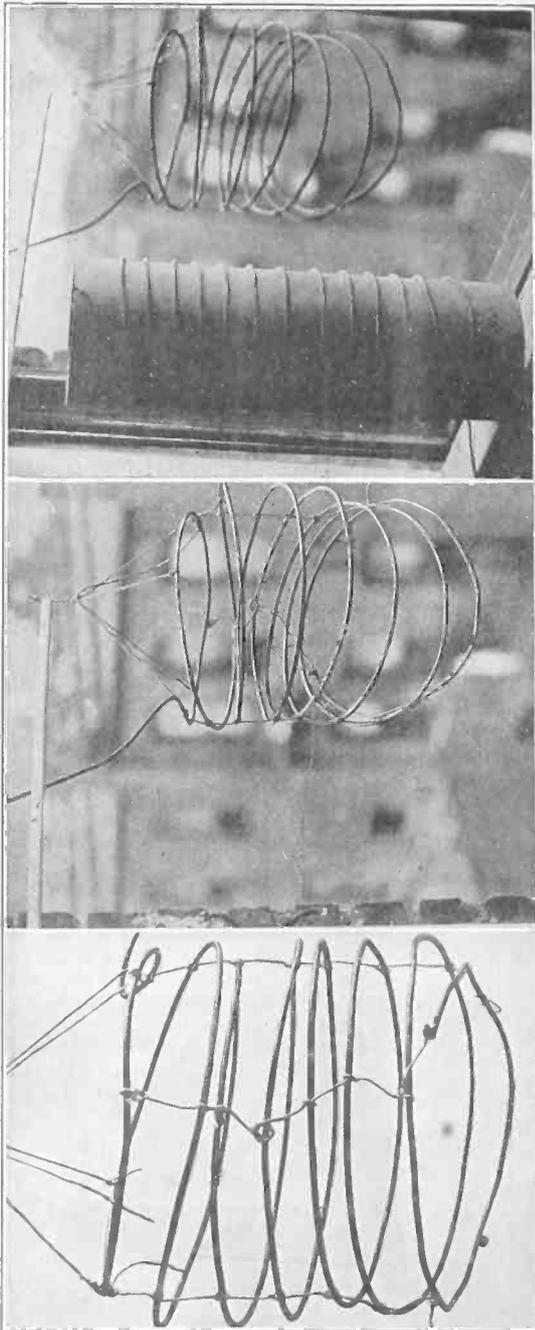

BOTTOM to top, Figs. 1, 2 and 3.



FIG. 4—Fan tuning in non-loop set that nevertheless worked well with Chester Charlton's loop method.

By Chester Charlton

YOUR aerial need not be conductively coupled to your set. If you follow my tip you can even get a crystal set to percolate—on a loop!

Fig. 1 shows a coil of No. 14 insulated wire, and how it is tied together with twine. The lead at left is from the regular aerial lead-in. Fig. 2 shows the inductance, mounted on a pole and held by the twine at right, attached to the coping or window ledge above. The lead-in is at left. Fig. 3 shows a $3\frac{1}{2}$ " diameter tubing in the foreground, giving an idea of how the energy is transferred by induction from the outside coil to the one on the tubing. This tubing coil is connected to your set, just as if it were the aerial lead-in. The ground connection may remain. Now, as for the loop. It is simply used instead of the tubing coil, if you have a loop in your home. The loop terminals may go to aerial and ground posts of your set (aerial and ground removed), or just one loop terminal to the set is aerial post, the other loop tip remaining free, and the ground connection remaining on your set. A fan is shown tuning in a regenerative set that would not operate on a loop alone, but which worked well my way.

Wiring Astor's 7x7" Circuit

(Concluded from preceding page)

If 199 or like tube is used bring this lead to B+45 volts. Connect the end of L to the stator or immovable plates of C2 and to one side of the grid condenser C1, the other side of C1 going to the grid post of the detector socket. (This lead goes to one side of the grid leak, R1, the other side of the grid leak going to A+) The ground is connected to A+ and also to the rotor or movable plates of the variable condenser. The wiring of the detector circuit is now complete.

3. The G post of the first AFT goes to the grid socket post, also marked G, and the F goes to the battery side of A—. As A— does not go through a rheostat in the amplifier circuit this connection may be made to the F— post of the first amplifier tube socket, the second tube from left in Figs. 1 and 3. The plate of this tube goes to P of the second AFT, the B of this AFT going to B+90 volts, i.e., the B battery lead at right in Fig. 1, bottom. This same 90-volt lead goes to the spring of the single open-circuit jack, OCJ. The G of the AFT goes to the grid post of the last tube socket and the F to the F— post of that socket. The plate of the third tube goes to the frame or right-angle of OCJ.

LIST OF PARTS

- One 100-turn honeycomb or duolateral coil (L).
- One 17-plate variable condenser (C2).
- One grid condenser, .00025, if fixed, but preferably of the variable type (C1).
- One grid leak, 2 megohms if fixed, but preferably of the variable type, from 1 to 5 megohms or higher (R1).
- Two audio-frequency transformers (AF).
- One rheostat to match the detector tube (R2).
- One rheostat of about half the value of that used for the detector, granting the same tubes are used in the AF (R3).
- One single closed-circuit jack, for detector (SCJ).
- One single open-circuit jack, for amplifier (OCJ).
- One storage battery, if that type tube is used, or if dry cells are used, 3 dry cells, each of the voltage required for running one tube.
- Two 45-volt B batteries.
- One 7 x 7" panel.
- One cabinet to fit.
- One $6\frac{1}{2}$ " wide by 7" deep baseboard.
- One 3" dial.
- One terminal strip with binding posts attached.
- 100 feet of aerial wire, 50 feet of No. 14 insulated lead-in wire, stranded No. 18 connecting wire, a brass angle or bus bar for mounting coil to condenser, screws, nuts, solder.

The 3-Circuit Regenerator, All Circuits Tuned, Is MY FAVORITE RECEIVER

Because—

"Its Tone Quality Is Superb"
"Its Volume Is Immense"

"Its Selectivity Is All One Needs"
"Its DX Powers Are Great"
—"That's All I Ask."

By Herbert E. Hayden


WHEN you ask a man what is his favorite receiver he usually has to stop awhile to think. But I can tell you right off the bat that mine is the 3-circuit tuner, with all circuits tuned. A variocoupler is used as the aerial tuning element and two variometers are used besides, one to tune the grid and the other to tune the plate. The regeneration is supplied through the action of the plate variometer, which when tuned to the same wave as the aerial inductance causes the transfer of energy from plate to grid to be accomplished capacitively, through the tube elements. Regeneration may be controlled, and thus radiation avoided. The plate variometer is left at zero while a station is tuned in by the aerial inductance and the grid variometer. By tightening the coupling of the plate variometer ever so gradually the point of maximum volume, soon easily recognized, is reached and the set is left tuned as it then stands. Occasionally some slight readjustment of the two other tuning elements may be necessary, however.

In any regenerative set one should tune in a station by the voice or music then being broadcast, and not by the whistle which one would hear by virtue of excess regeneration present while the tuning is being accomplished. Tune first and regenerate afterwards.

I like regeneration because it gives more volume and greater distance. It is about the equal of a stage of radio-frequency amplification ahead of a non-regenerative detector tube, hence you get the value of two tubes out of one tube, without reflexing. You cannot be so certain of making a good reflex set as you can of this one, for many experimenters do not find it easy to make a reflex reflex. It is easier to make a reflex regenerate, which it should not do.

Let us consider first the detector circuit, then two stages of audio-frequency amplification.

Use a 21" long panel, radion or bakelite. Many prefer radion, because it is easier to drill and cut. If you desire to include the two AF stages, use a 26" panel. These sizes are recommended because of the extreme desirability of keeping the variometers far apart. The variocoupler should be mounted in the center and the variometers with center shafts 8" from the coupler shaft. The detector rheostat may be placed between the variocoupler and the plate variometer, which is at right. If a terminal strip is used it should be in the rear of the set. A 20" baseboard should be used for a 21" panel and a 25" baseboard for a 26" panel. The strip would be affixed to the baseboard and the leads carried to the posts on the strip, outside connections being made with insulated wire carried from the posts through holes to be bored in the back of the cabinet. A

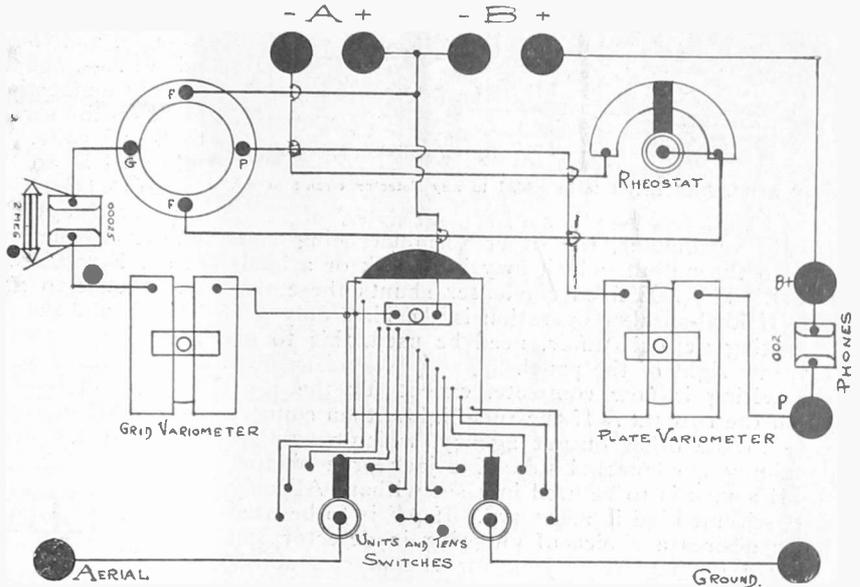

THE DETECTOR CIRCUIT (Fig. 1) of the variocoupler-two-variometer set, a favorite that has stood the test. The tube socket is at left, top. The aerial goes to one tap switch, the ground to the other. This circuit is selective and produces good quality of signal. It gets DX well. Dry cell tubes like 11 or 12 type, with 1½-volt A battery, may be used, or 199 or 299, with 4½-volts. Storage battery tubes work well.


double tap switch may be employed on the coupler stator or two separate home-made switches used. The commercial double product is inexpensive and more convenient, as only two holes need be drilled to secure it to the panel.

The aerial and ground leads enter the cabinet either through the rear of the cabinet or from a panel binding post, as you prefer. Each lead goes to a metal connecting strip on each switch. This connecting strip connects with the movable switch arm and thence to the switch points, the points being connected to the tap loops on the coupler stator. Get a coupler that is tapped in units and tens, that is, tapped every turn for the first eight turns or so, then one every ten turns thereafter. The unit taps are those made to the aerial switch and the tens taps to the ground switch. The energy is transferred from the stator to the rotor of the coupler by mutual inductance. The beginning of the rotor goes to one terminal of the grid variometer and the end of the rotor to the A+. The remaining unconnected terminal of the grid variometer goes to one side of the grid condenser, the other side of that condenser going to the grid post (G) on the socket. (Fig. 1.) Across the condenser is a 2-megohm grid leak. The only other condenser used in the circuit is the .002 mfd. fixed condenser across the phones. Hence all tuning is by inductance, which is to be preferred as against capacity, because of the effect of inductance in building up the signal.

The A wiring consists of connecting the A- to one side of the rheostat, the other side of the rheostat to the F- post on the socket, and the A+ directly to the F+ post on the socket. B- and A+ are joined.

The P post on the socket goes to one terminal of

Wiring Two Stages of AF

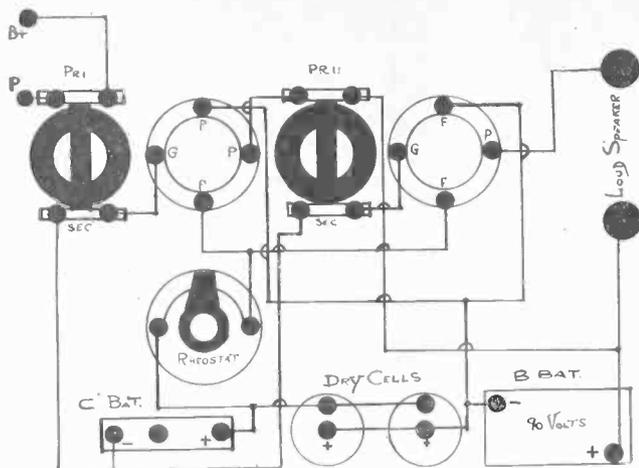

THE AF AMPLIFIER circuit to be added to any detector circuit at all.

the plate variometer, the other terminal being connected to the output, which may be a jack or a binding post. The .002 fixed condenser shunts these two leads. If loud-speaker operation is the idea, only one jack, a single-circuit affair, need be used, this to go at extreme right of the panel.

The wiring is now complete, except for the B+. Turn on the rheostat. If the tube lights, then connect the B+ to the other output agency, which would be a remaining unconnected side of a jack or a binding post. If a jack is to be used in a set without AF only a single-circuit kind is necessary. If AF is to be used and one desires a choice of plugging in detector and AF, use a double-circuit jack for the phones and a single-circuit one for the speaker. An examination of the jacks you buy will reveal how they operate and how the connections are to be soldered to them. The set at this stage is ready for earphone reception, DX included.

As for the AF (Fig. 2), one rheostat controls the two AF tubes. The rheostats depend on the type of tube used. If the 11 or 12 type tube is used, 20 ohms for the detector and 10 or 15 ohms for the amplifier circuit suffice.

The parts for the amplifier should be arranged as shown in Fig. 2. The primaries and secondaries of the AF transformers are so marked; also the posts of

the sockets are designated F, G and P. Note that a C battery is inserted. The C+ goes to the A- and the C- to the F or S² post of each of the transformers. P¹ and P, P² and B, S¹ and G, S² and F are corresponding designations on AF transformers. P stands for primary and S for secondary.

The output of the detector, marked P and B in Fig. 1, go to the P and B leads in Fig. 2. The connections are as follows: The plate output of the detector goes to P¹ of the first AFT, the one at left, Fig. 2. The AFT may be recognized also by the heavy black circles, with thick black diameters. The P² is connected to B 22½ volts. G goes to the grid of the first AF tube and the F to the C-. C+ goes to the battery side of A-, not to the side of the rheostat opposite the battery connection. The P of the first AF tube goes to P¹ on the second AFT, P² of the second AFT going to B+ 90 volts. S¹ or G goes to the grid of the last tube and S² to the C-. Two dry cells are connected in parallel for the AF circuit, i. e., the like posts are connected together, plus to plus, minus to minus. The plus then goes direct to the F+ post on each of the two AF sockets. The A- goes through the rheostat and thence to the F- socket posts as in the detector. The B- and the A+ are connected. The output is taken from the P post on the last socket and from the B+ 90 volts. These two leads may go to one of each of the terminals of a single-circuit jack. The P goes to the frame or right angle of the jack, the B+ 90 volts to the spring or blade.

Efficiency from Separate B Cells

HOWLS in a radio-frequency amplifier can sometimes be attributed to a common B battery, because the wiring of one tube is mixed with that of another and interaction begins. If a radio-frequency amplifier is used it is a good idea to use separate B batteries for each tube. A common B battery can be used with the detector and audio amplifiers. Efficient Super-Heterodyne sets generally employ an individual B battery for the oscillator; another unit for the first detector and intermediate amplifier and another set for the second detector and audio amplifiers.

Fixed Condensers Short-Circuited by Using Too-Hot Iron

Most Common Cause of Failure Company Finds After Making Many Trouble-Shooting Tests—Tubes That Light But Don't Amplify Is Second Most Frequent Difficulty

A MANUFACTURER with a large service department that undertakes trouble-shooting reports that the outstanding result of the experiment has been to reveal that the troubles are not found in the large units of sets, like transformers and variable condensers. Usually the difficulties discovered are such things as short circuited fixed condensers, caused by the set-builder using an extremely hot soldering iron when soldering a wire to the condenser. This was the

commonest source of trouble. Next to it was using tubes which would light but could not amplify. These defective tubes when tested were found not giving any electron emission, hence no results therefrom were possible.

Another source of trouble was caused by taking liberties with the circuit itself and incorporating some of the builder's own ideas. Not infrequently trouble is experienced through using discarded parts from other sets in making a new one.

Many times these old parts were smeared with solder or dirt which made them unsuitable for further use.

High losses in variable condensers which had no cover to exclude dust explained difficulties in many instances. Some builders, too, did not realize that condensers should not be oiled. High losses also are caused by poorly soldered joints in jacks, or by using acids for soldering. One such joint when measured in the laboratory showed several hundred thousand ohms resistance. A joint like this would cause a high pitched whistle and other noises which would be blamed incorrectly to inter-transformer action.

The success attending the operation of service stations has resulted in a decision by the company to continue them permanently.

Non-Radiating Regeneration

2-Tube Set, with RF tube reflexed for an audio stage, and a tube serving as detector—Neutralization used with compensating coils

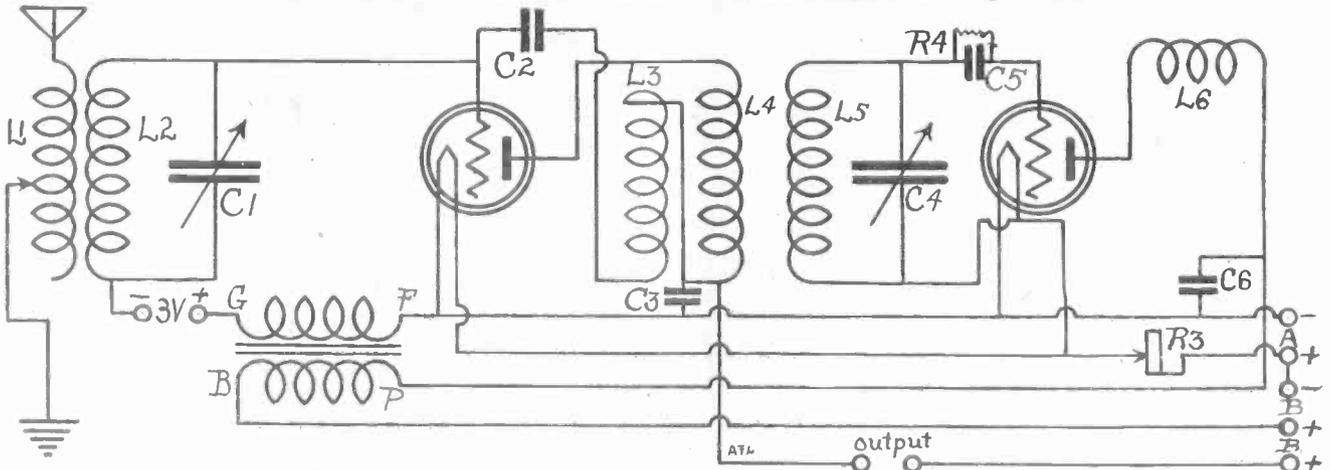


FIG. 3—Wiring diagram of the neutralized reflex. Two tubes are used, the first is the RF tube, then the detector, and the signal is passed back through the audio-frequency transformer to be amplified in the first tube at audio frequencies.

By Brewster Lee

MOST reflex circuits, unless made by experts, oscillate undesirably, due to inter-circuit coupling. This reflex circuit employs regeneration and also neutralized radio-frequency amplification. The neutralizing principle is basically the same as that used in the Neutrodyne.

All the coils are spider-webs and, wound on a 13-spoke form, 5½" diameter. L1 consists of 30 turns of No. 22 DCC wire with a tap taken from every fifth turn. L2 has 45 turns of the same size wire. Coils L3 and L4 are the self-balancing or compensating windings of the primary of the coupler. Both these windings are made at the same time, in the following manner. Measure off two lengths of 55 feet of No. 26 wire, place the two lengths side by side and wind them together as one wire on a spider web form, making 22 turns. Connect one of the outside leads to one of the inside leads, thus making in effect a 44-turn coil. L5 is the same as L2, having 45 turns of No. 22 wire. L6, the tickler coil, consists of 20 turns of No. 22 wire. Five spider web coils are used. To obtain maximum selectivity over all the broadcasting wavelengths, the tickler coil is made variable. This is done by passing a rod through a supporting bushing on the panel, and fastening coil L6 thereto as shown in the assembly plan, Fig. 1. Coils L3, L4 and L5 are fastened parallel to the baseboard. L1 L2 are mounted upright and to the right of C1 and the audio-frequency transformer. The radio-frequency tube is placed immediately behind the rheostat, and the detector tube placed behind the RF tube. The spider-web coupler just fits in nicely be-

tween the rear of variable condenser C4 and the binding post strip at the back of the baseboard.

Coils L1 L2, the RF coupler, may be moved back from the panel enough to provide room for the jack as shown in the panel diagram, Fig. 2. The five taps from L1 will be a little longer in this case. The rheostat is placed underneath the switch knob, and the knob controlling the tickler coupler is directly to the right. The jack is at the corresponding left hand position of the rheostat knob. The panel should be drilled exactly in accordance with the dimensions given on the diagram.

In assembling the set, first mount the condensers jack, rheostat, switch lever and tickler coupling rod onto the panel. Next place the audio-frequency transformer, sockets and fixed condensers. The spider-web coils are next put in place, and remember firmly to fasten the tickler coil to the rod. Use as little metal here as possible, preferably tying the coils tightly to the rod with thread. The binding post strip is placed at the rear of the baseboard and has marked binding posts. The panel is 16"x7"x3/16".

The wiring diagram, Fig. 3, shows the end of L3 connected to the neutralizing condenser C2 and the beginning of L4 connected to the plate. This may not be followed exactly as there is no difference which coil is connected to C2. It is important, however, to have L6 connected right, and the builder will have to reverse the leads of that coil if the circuit does not oscillate. Condenser C2 should be a small 3-plate condenser, as a higher capacity than that used for ordinary Neutrodyne circuits is necessary here. A 3-volt C battery is connected from the G post of the AF transformer to the outside end of L2. One rheostat, R3, regulates the filament temperature of both tubes. Careful neutralization of the RF tube is necessary for best results.

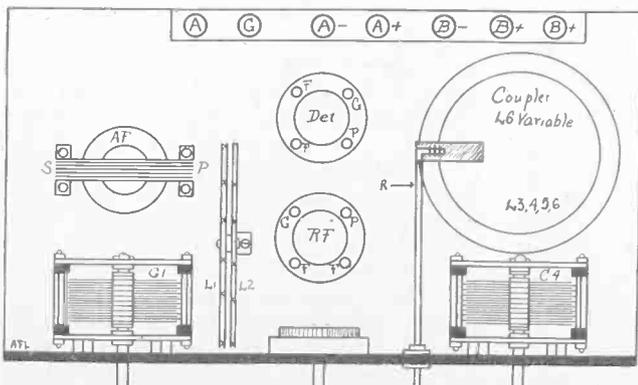


FIG. 1—Assembly plan of Lee's set. Rod R may be either a thin dowel stick or a length of ¼ inch hard rubber or bakelite round rod.

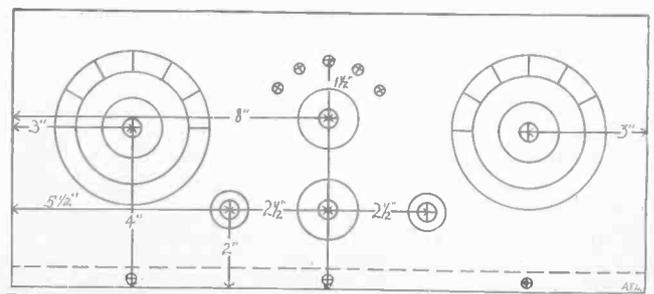


FIG. 2—Panel layout, 16"x7". The antenna tuning condenser dial is at the left, and the secondary condenser at the right. The rheostat is placed underneath the tap switch, and the tickler knob to the right of the rheostat.

Wave's Peak or Bust


A Discussion of Radio-Frequency for the Beginner by a Noted Expert

By N. N. Bernstein

AFTER the beginner in radio has had some experience with the single-tube circuits as described in the October 4 issue of *RADIO WORLD* the desire is always present to increase the range and volume of the receiver. To this end amplification is necessary. Merely to increase the volume would not bring in greater distance. To obtain greater sensitivity the signal must be amplified before it is rectified by the detector tube. One or more vacuum tubes are required to do this, and the process is called radio-frequency amplification, because the signal is still inaudible. It is only after the signal is rectified in the detector tube that it can be heard in the earphones. The circuit for amplifying at radio-frequency is the same, in many respects, as the single detector circuit. In Fig. 1, P represents the primary and S the secondary of a fixed radio-frequency transformer. The fixed type of RF transformer usually has an iron core. The iron core has the effect of broadening the amplification peak of the transformer, thereby causing the transformer to function over a fairly large wave band. This is the necessary makeshift due to absence of a tuning control. The antenna is connected to one side of the primary, the ground to the other. One end of the secondary is connected to the grid and the other end to the negative A battery lead. In detector circuits the grid return, that is, the electrical lead going from the grid of the tube to the filament post of the same tube, is to the A+, but in all amplifiers that lead goes to the negative post. The binding posts in Fig. 1 marked "out," are connected to the detector tuning circuit, where the antenna and ground posts are. Of course, when using the radio-frequency amplifier the antenna and ground are not connected to the detector tuner. As the transformer in Fig. 1 will not cover all the broadcast wavelengths efficiently, it is desirable to tune this circuit variably. In that way your RF amplifier functions at a peak on almost all wavelengths, instead of only in a few.

In Fig. 2 we have a tuned radio-frequency circuit. The coil may be 60 turns of No. 22 wire, single or double cotton cover, and the condenser the variable type, say 17 plates, if the low-loss type is used. As in the simple detector circuit, the signal is tuned by the condenser, which allows only the wavelength of a desired station to pass on to the grid of the tube. A unit, such as represented in Fig. 2, will increase the ordinary range of a detector circuit as much as 100%. This form of RF is known as impedance, since no primary-and-secondary combination is used.

Fig. 3 is two stages of tuned radio-frequency amplification. The coils are what is popularly known as Neutroformers. The combination of a Neutroformer and a variable condenser makes a tuned radio-frequency unit. This transformer is different from the one represented in Fig. 1 because there is no iron core, the coils of wire simply being wound on $3\frac{1}{2}$ " diameter tubes. The primary and secondary windings may go side by side or one on top of the other. The ten turns are the primary of the first Neutroformer and are untuned. The signal passes through this primary circuit and is induced through air to the secondary circuit, where the tuning takes place. The .00035 mfd. condenser (17-plate) tunes the grid of the first tube to respond to the desired wave. A high B battery volt-

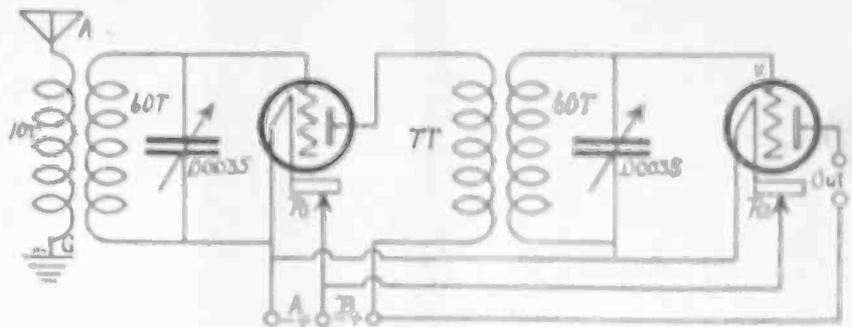

TWO STAGES of transformer-coupled tuned RF, such as used in the commercial Neutrodyne. The output in from the plate of the second tube, this lead going to the B+90 volts, through the primary, of the RF transformer used in the detector circuit. The secondary is coupled inductively to the primary, that is, there is no metallic contact. The tuning element of the detector is an RF transformer, too.


age, usually from 67½ to 90 volts, on the plate of the RF tubes effects a fairly high rate of amplification. This circuit increases the strength of the signals in the first tube. This amplified radio-frequency signal passes on to the second coil, which is composed of seven turns for the primary and sixty turns for the tuned secondary. This low number of primary turns is sufficient to induce the proper amount of energy into the sixty turns secondary. The number of turns in this primary may be increased, but in that case the circuit will have a tendency to oscillate, due to bringing the grid and plate circuits into resonance. The second condenser is tuned the same as the first one, thus tuning the signal again as in the first stage. The weak signal, so originally picked up and amplified by the first tube, goes through the same process again in the second tube with a correspondingly higher rate of amplification. Two steps of radio-frequency amplification, such as described, are the standard used in commercial Neutrodyne sets. The output of these tubes goes directly to the tuning element of the detector circuit, where the greatly increased signal is then rectified and brought out very loud indeed. A curious fact about radio-frequency amplification is that a strong signal from a nearby local station will not be amplified as much as a weak signal from a distant station. Therefore the weaker signal will have a greater amplification factor than a correspondingly strong signal. This is the reason for the great distance records made by tuned radio-frequency sets.

In matching coils and condensers for RF and detector stages it must be remembered that low-loss condensers of say 17 plates cover as effective a capacity range as a 23-plate condenser not of the low-loss type, and that low-loss coils give a greater amount of induction for the same number of turns.

This accounts for the failure of some experimenters to cover the broadcast band, although turn for turn and plate for plate the inductance directions and the capacity ratings seemingly were followed as given by the author. The fact is they were not.


Many wonder just what the Neutrodyne circuit is, since it is described as two stages of RF, detector and two stages of audio-frequency amplification. There is some debate as to whether the Neutrodyne is entitled to rank as a circuit. The fact is that it is mainly a device for preventing the currents from running back and forth among tubes, this truancy playing havoc with stability so greatly desired in any circuit. The device is a neutralizing condenser, which is an ordinary condenser of small capacity. It is variable and is adjusted to the proper capacity, governed by the type of tube used and other considerations, and connected usually between the grid of one tube and

Chaos vs. Neatness at Workbench

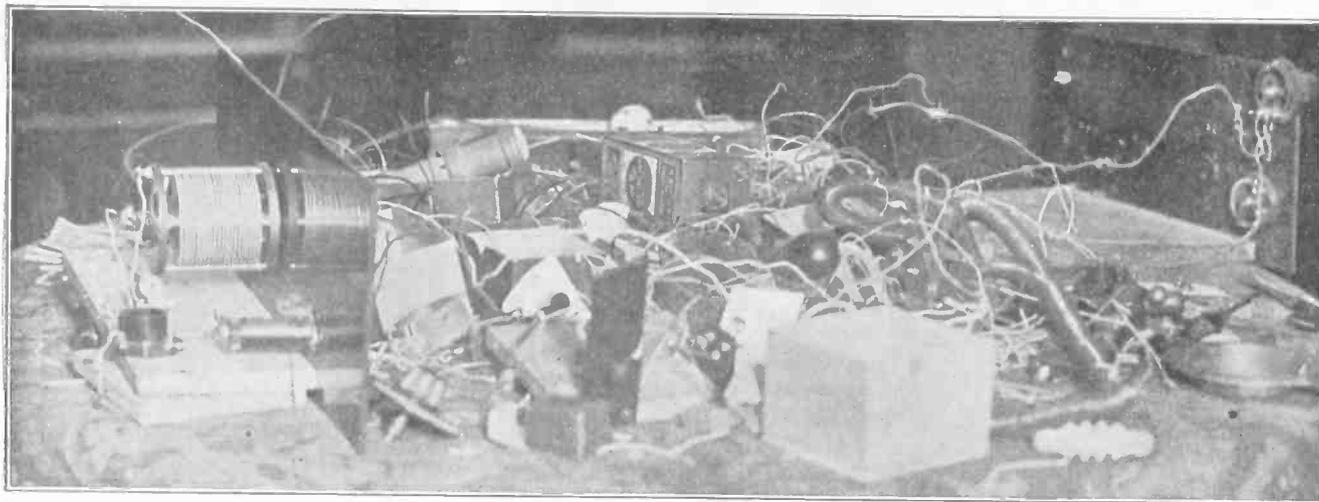


(Foto Topics)

THIS IS NO WAY to keep your parts, apparatus, equipment and wire, as if they were a lot of junk. When possible shelving should be used and your parts and equipment stored in regular places for ready access. By leaving things all jumbled up, as shown in this photo, considerable time is lost in hunting for what you want, your patience is sorely tried, and you do not get the fun out of home construction that is your due. It converts your hobby into a task. The careless fellow responsible for the above outrage even left a dollar bill on the table, extreme left background.

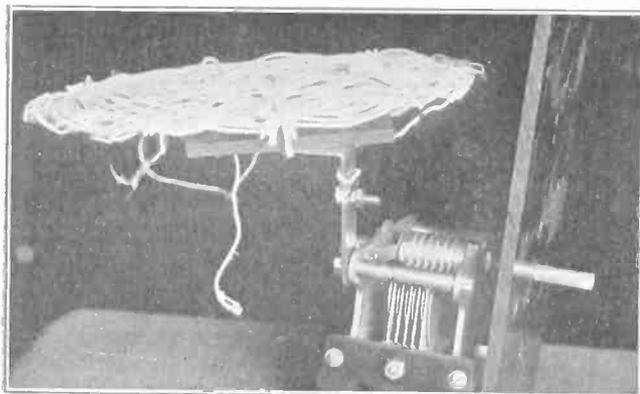

(Foto Topics)

A RADIO-FREQUENCY TRANSFORMER may be wound on a spider-web coil, the primary consisting of 12 feet, wound first, and the secondary of 50 feet, wound next, No. 20 double cotton covered wire being used. Linen thread or cord may be used to bind the windings of both coils, one such piece of thread circumscribing the apertures between spokes of the spider-web form. Then the form may be cut away. The secondary is connected to the variable condenser. The coil may be mounted as shown, a brass angle being fastened by one of the screws on the end plate of the condenser. The brass angle has holes in it that pass the machine screws most frequently used in radio, and corresponding holes are bored in the hard rubber so that the screws are passed through both the rubber and the brass angle, nuts securing the two together. The coil is then tied to the hard rubber strip. The coil is kept more than 1 inch away from the back of the panel and also more than 2 inches above the condenser plates. This is to conserve the signal strength. Both coil and condenser are low-loss.

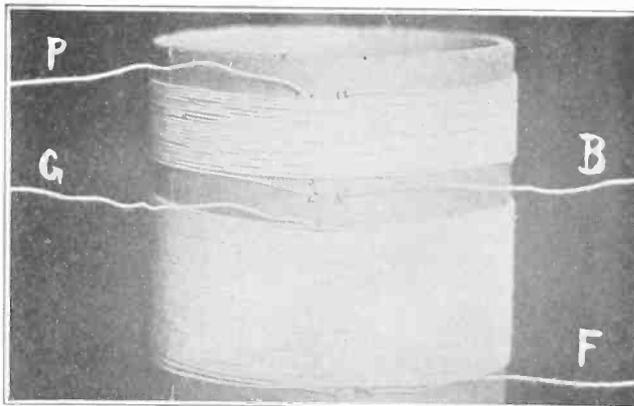


(Foto Topics)

ON A CARDBOARD TUBING a radio-frequency transformer may be easily wound. The winding is begun at top, $\frac{1}{2}$ " or less from the rim. The beginning is P and the end is B. This winding constitutes the primary. If used in a radio-frequency stage, P goes to the plate of the preceding tube and B goes to B+90 volts. If the transformer is used for tuning the aerial circuit, P goes to aerial and B goes to ground. The secondary winding is begun $\frac{1}{2}$ or $\frac{3}{4}$ " from the end of the primary. The beginning of the secondary is G, because it goes to the grid of the tube upon which the transformer functions. The end of the secondary is F, because, in amplifier circuits this lead, called the grid return, goes to the filament minus post on the socket. P is the only lead that ever goes to the preceding tube. The number of turns will vary with the purpose and the capacity of the condenser. Used as the detector tuning element in a reflex set, 20 turns of No. 20 double cotton covered wire will function as the primary.

Taking the IF Out of RF


(Concluded from preceding page)

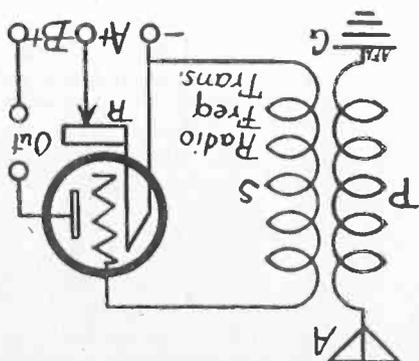grid coil of the succeeding tube. This balancing effect may be obtained without the use of neutralizing condensers, by preventing the magnetic fields from exchanging their charges and keeping unwanted capacity out of the coils. Phusi-formers, low-loss coil - and - condenser combinations, direction of coil winding and



THE PRIMARY and secondary of a fixed radio-frequency transformer are shown here, hooked up to a tube as the first RF stage, i. e., aerial and ground connected to the primary. Note that there is no tuning element, i. e., variable condenser, variometer, etc. An iron core in this small commercial device broadens the tuning

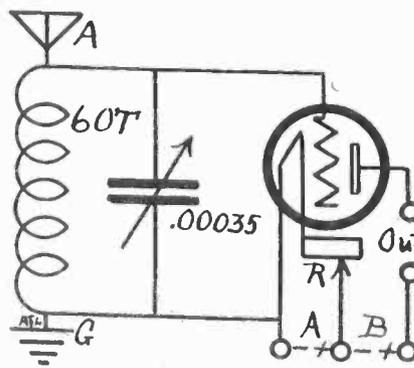the use of a potentiometer are ways in which these results are attempted. Some of these ways are good, others not so good, and the Neutrodyne so far is holding its own. In the Neutrodyne and in some of its competitor circuits that use no external balancing device the coils are mounted at an angle to avoid or minimize the interplay of the currents so disastrous to fine results.



TUNED IMPEDANCE RF consists of a coil and variable condenser.

Boxing Coil for Outdoor Loop

The Radio University

A Question and Answer Department conducted by RADIO WORLD for its Readers by its Staff of Experts. Address Letters to Radio University Department, RADIO WORLD, 1493 Broadway, New York City.

PLEASE show me in a diagram how to put a honeycomb coil inside a doubly-protected box arrangement, so I may use my outdoor antenna as a loop and gain selectivity, as described in RADIO WORLD, issue of October 4.—Thomas Waldkind, Albany, N. Y.

A 25-turn honeycomb or duolateral coil (LI in Fig. 43) is placed inside a small wooden box, the leads being brought out through two holes bored in the box as shown. These holes are sealed with sealing wax. This contraption is placed in a slightly larger wooden box, where the process is repeated. Thus the coil is protected from the weather. The leads A and G go, respectively, to the end of the aerial farthest from the set and to the ground at that same point.

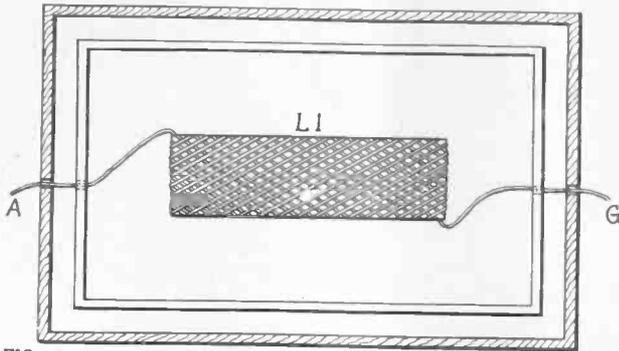


FIG. 43 (above) Showing how a coil is placed inside two boxes and sealed, for using your antenna as a loop.

THE ARTICLE in RADIO WORLD for August 2, dealing with the Ideal Loop, does not specify the capacity of the condenser to be used to cover the range from 20 to 600 meters. What capacity condenser should be used? Concerning B. J. Bongart's 4-tube Super-Heterodyne, I should like to know if the loop and condenser specified is absolutely required or will any loop tuned by the proper condenser do the work?—Bernard C. McGee, 1829 Eye St., N. W., Washington, D. C.

The condenser to be used with this loop is .001 mfd., and should be of the low-loss type. This condenser will cover the wavelengths desired. Any loop and condenser that is designed for the broadcast wavelengths is suitable for Super-Heterodyne work. Suggest you wait for new data being prepared on this circuit.

I WOULD LIKE to construct one of the low-loss radio-frequency amplifier coils as recommended by Neal Fitzalan in the September 6 issue of RADIO WORLD, but cannot get a form to wind it on. Where can I purchase such a form or coil?—Earnest Knight, 1802 Dean St., Brooklyn, N. Y.

That form of coil you refer to is the basket weave type and may be purchased at almost any radio shop or in some chain stores.

I BUILT the Superdyne as described in RADIO WORLD for May 17, 24 and 31. I get good results, the stations coming in loud and clear, but I had a little trouble with the coils. I had wound them on cardboard tubing. I dismantled this set and bought a complete set of ready-made coils and I find that they are quite different. The coupler stator has only 25 turns of wire and the plate coil 25 turns. I have been told this will not cover the broadcast wavelengths. I would very much like to use these low-loss coils in place of the others as I want this set to stay put.—J. Woods, 14 Stanley St., Montreal, Can.

The low-loss coils you refer to do not need the same number of turns as the old type coils, because the wavelength range is greater when insulation is absent from the field. Undoubtedly they will be satisfactory when used with 23-plate low-loss condensers. The tuning should also be much improved.

I HAVE just completed the Monodial 3-tube set as described in RADIO WORLD. I used a commercial coil and Hammarlund 23-plate low-loss condensers and auto transformers from an old Tuska receiver. It works splendidly on the detector, but when I switch on the loudspeaker there is not enough volume, and if I turn the detector rheostat up high enough to get volume on the loudspeaker it is full of foreign noises and distortion. Could you suggest what might be my trouble? I get DX fine by using the headphones on the detector tube, but cannot use amplifiers.—W. L. Whitehurst, Coneto, N. C.

Your trouble lies in the audio-frequency transformers or the audio-frequency wiring. Go over the connections carefully, and also test the transformers with a battery and headphones. Be sure to connect them properly in the circuit. It is important to get the plate and grid leads right.

IN THE July 26 issue of RADIO WORLD an article by Herman Bernard showed how to add a stage of RF to a 3-circuit tuner. I built this up and had several radio men test the same and all tell me that everything is properly connected. Still I fail to get any reception at all. What can the trouble be?—John O'Donnell, 783 East 156th St., Bronx, N. Y.

Since all the connections are in order, the trouble must be located in some of the parts used. Suggest you thoroughly examine the socket and condensers, and test other tubes in that part of the set. You will probably find your trouble is purely mechanical.

INFORMATION is desired on how to make low-loss variocouplers, as I believe they are better than the others. I would also like to get details about the Dynocoils that have proven so popular.—Will Morrell, 1402 Oregon Ave., Cleveland, O.

The method of making variocoupler low-loss is described in RADIO WORLD for July 5, and that article also tells how to make your condensers low-loss. The Dynocoils are described in detail in the August 9 issue.

I AM a regular reader of RADIO WORLD and have built a lot of the circuits published therein. I have never had trouble with any of them until I built the low-loss Neutrodyne. I have built this circuit and the lowest wavelength I can reach is WJZ on 455 meters. Anything above this wave I can receive all right. The trouble may be in the coils, as the antenna worked fine with other sets. What can be done to reach the lower wavelengths?—Roy C. Bagley, 34 Whiting St., Roxbury, Mass.

You have probably wound too many turns on the secondaries of the coils. So reduce the number of turns on each coil, one or two turns at a time, until you get down to 200 meters. You will be able to reach up to the higher wavelengths, about 600 meters, with ease.

1. DOES THE feedback through two stages of RF increase the signal strength or is the use of the ordinary variometer preferred? 2. Set does not have much volume over 400 meters. 3. Effect of regeneration not pronounced on higher wavelengths. 4. Adjustment of potentiometer has

little effect on operation of set.—Carl H. Lambach, Davenport, Iowa.

1. The variometer in the detector plate circuit is to be preferred unless the superdyne principle is utilized. 2 and 3. Try connecting a variometer in series with the tickler and plate. This will boost the inductance in this circuit and raise the wavelength, allowing full regeneration in the higher wavelengths. 4. Disconnect the ground connection from the grid return. The potentiometer with the suggested changes will be of little use.

I WOULD LIKE to have some advice about the connections of the Ultra-Reflex by Neal Fitzalan in RADIO WORLD for June 28.—A. E. Hicks, Mt. Washington, Mo.

Posts B and P are shunted with a .001 mfd. condenser. The primary B and A—are connected together. The top side of the coupler should go to the RF transformer. It would be proper to ground in on the minus A post or anywhere on this lead.

I WOULD like to build a 3-tube set having exceptional volume, using 199 tubes. What is your advice?—Murray Hemler, 876 New Lots Ave., Brooklyn, N. Y.

The Reflexed Neutrodyne, by N. N. Bernstein, described in the September 13 issue of RADIO WORLD, is just the thing for you.

CAN I BUY the coils for the Reflexed Magnadyne, as I do not want to wind them myself? Wm. Boulden, 132 West 79th St., New York City. These coils may be purchased or some very nearly like them. Advertisers in RADIO WORLD or your radio store would be glad to help you out.

I HAVE an Aeriola, Sr., set to which I would like to add one step of RF amplification. Please tell me how this should be done.—Lucy Smith, Box 61, Bowling Green, Ky.

Refer to the May 3 issue of RADIO WORLD, "Adventures with the Neutrad Unit," solves your problem efficiently.

I WOULD like to have a 1-tube hookup which is a good DX getter, which is simple to operate.—J. Dryden, 147 Linden Ave., East Kildina, Manitoba.

Refer to the June 28 issue of RADIO WORLD. The article, "A Non-Squealing Regenerative Set," by Herman Bernard, will be "Eureka" to you.

I WOULD like to get some information regarding the Magnadyne, published in RADIO WORLD, issues of August 16 and 23.—F. H. Cooper, P. O., Drawer G, Johnstown, Pa.

The condensers used in this set are low-loss and have what are known as grounded rotors. The layout shows the outside of the inductances to the stators and from thence should go to the grid. The angle of the Dynocoils may be reversed and this would shorten the leads somewhat.

I HAVE BEEN a reader of RADIO WORLD since almost its first number, and have built many of the sets described in the various numbers. In the article on the low-loss Superdyne, by N. N. Bernstein, in the August 23 and 30 issues, what is the resistance of R3 and R7?—Fred L. Hunkins, 71 Center St., Laconia, N. H.

R3 and R7 are .5 meg., that is, 500,000 ohms.

I NOTE that the tuning coil is sometimes referred to as a radio-frequency transformer, when consisting of primary and secondary. Is this correct?—Jackson Hall, Memphis, Tenn.

Yes. The fact that the inductance is not used for inter-stage coupling does not alter the fact that it is a radio-frequency transformer.

THE REFLEXED MAGNADYNE, A 3-TUBE NEUTRODYNE, by N. N. Bernstein, Technical Editor, issue of Sept. 13. Send 15 cents or start your subscription with that number. Radio World, 1493 Broadway, N. Y. C.

Join RADIO WORLD'S University Club

And Get Full Question and Answer Service for the Coming 52 Weeks. RADIO WORLD, 1493 Broadway, New York City:

Enclosed find \$6.00 for RADIO WORLD for one year (52 Nos.) and also consider this as an application to join RADIO WORLD'S University Club, which gives me free information in your Radio University Department for the coming year.


Name

Street

City and State


Telegraphed queries will be answered collect the same day as received. Be sure to direct in your query that the answer be sent collect.

Chaos vs. Neatness at Workbench

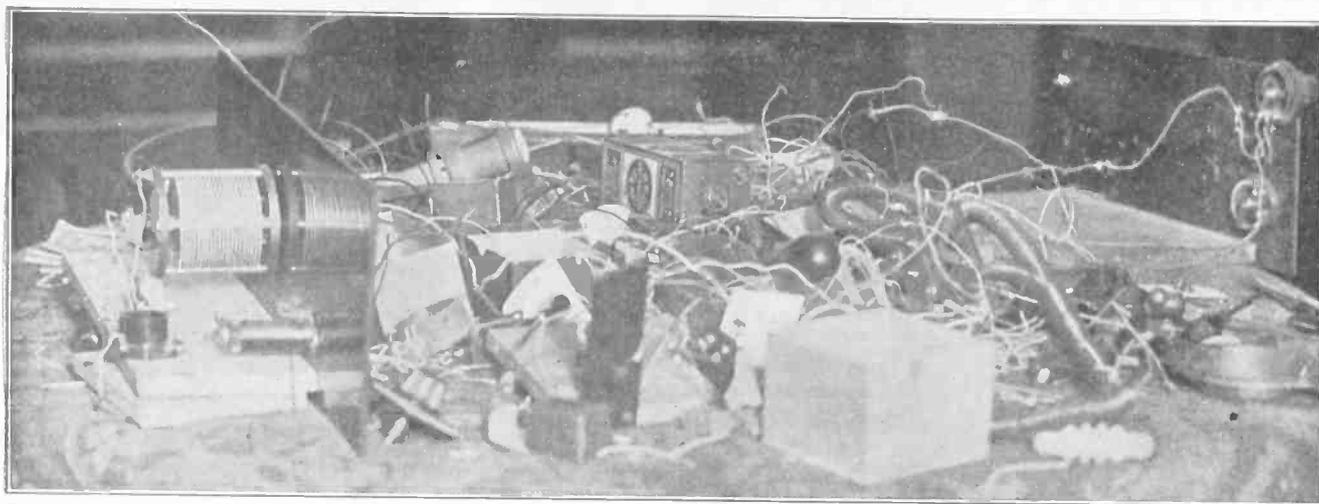


(Foto Topics)

THIS IS NO WAY to keep your parts, apparatus, equipment and wire, as if they were a lot of junk. When possible shelving should be used and your parts and equipment stored in regular places for ready access. By leaving things all jumbled up, as shown in this photo, considerable time is lost in hunting for what you want, your patience is sorely tried, and you do not get the fun out of home construction that is your due. It converts your hobby into a task. The careless fellow responsible for the above outrage even left a dollar bill on the table, extreme left background.

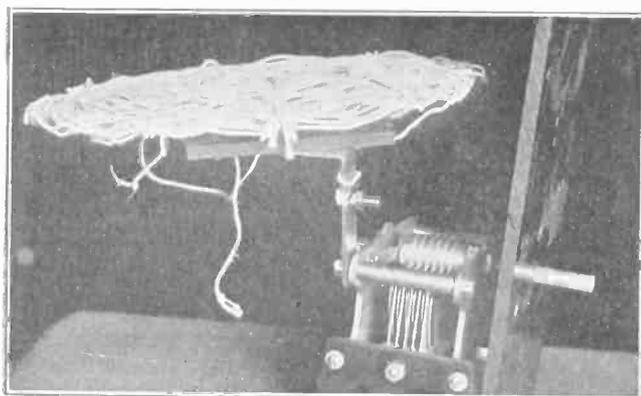

(Foto Topics)

A RADIO-FREQUENCY TRANSFORMER may be wound on a spider-web coil, the primary consisting of 12 feet, wound first, and the secondary of 50 feet, wound next, No. 20 double cotton covered wire being used. Linen thread or cord may be used to bind the windings of both coils, one such piece of thread circumscribing the apertures between spokes of the spider-web form. Then the form may be cut away. The secondary is connected to the variable condenser. The coil may be mounted as shown, a brass angle being fastened by one of the screws on the end plate of the condenser. The brass angle has holes in it that pass the machine screws most frequently used in radio, and corresponding holes are bored in the hard rubber so that the screws are passed through both the rubber and the brass angle, nuts securing the two together. The coil is then tied to the hard rubber strip. The coil is kept more than 1 inch away from the back of the panel and also more than 2 inches above the condenser plates. This is to conserve the signal strength. Both coil and condenser are low-loss.

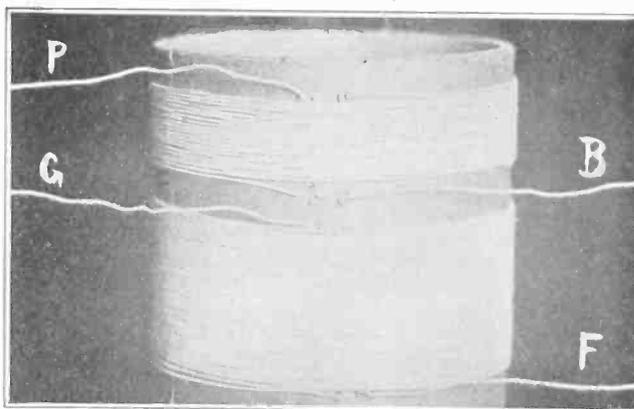


(Foto Topics)

ON A CARDBOARD TUBING a radio-frequency transformer may be easily wound. The winding is begun at top, $\frac{1}{2}$ " or less from the rim. The beginning is P and the end is B. This winding constitutes the primary. If used in a radio-frequency stage, P goes to the plate of the preceding tube and B goes to B+90 volts. If the transformer is used for tuning the aerial circuit, P goes to aerial and B goes to ground. The secondary winding is begun $\frac{1}{2}$ or $\frac{1}{4}$ " from the end of the primary. The beginning of the secondary is G, because it goes to the grid of the tube upon which the transformer functions. The end of the secondary is F, because, in amplifier circuits this lead, called the grid return, goes to the filament minus post on the socket. P is the only lead that ever goes to the preceding tube. The number of turns will vary with the purpose and the capacity of the condenser. Used as the detector tuning element in a reflex set, 20 turns of No. 20 double cotton covered wire will function as the primary.

Taking the IF Out of RF


(Concluded from preceding page)

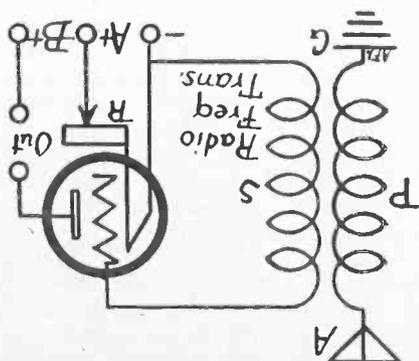grid coil of the succeeding tube. This balancing effect may be obtained without the use of neutralizing condensers, by preventing the magnetic fields from exchanging their charges and keeping unwanted capacity out of the coils. Phusi-formers, low-loss coil - and - condenser combinations, direction of coil winding and



THE PRIMARY and secondary of a fixed radio-frequency transformer are shown here, hooked up to a tube as the first RF stage, i. e., aerial and ground connected to the primary. Note that there is no tuning element, i. e., variable condenser, variometer, etc. An iron core in this small commercial device broadens the tuning

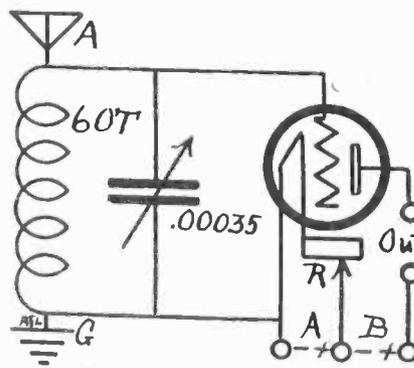the use of a potentiometer are ways in which these results are attempted. Some of these ways are good, others not so good, and the Neutrodyne so far is holding its own. In the Neutrodyne and in some of its competitor circuits that use no external balancing device the coils are mounted at an angle to avoid or minimize the interplay of the currents so disastrous to fine results.



BALANCED IMPEDANCE RF consists of a coil and variable condenser.

Boxing Coil for Outdoor Loop

The Radio University

A Question and Answer Department conducted by RADIO WORLD for its Readers by its Staff of Experts. Address Letters to Radio University Department, RADIO WORLD, 1493 Broadway, New York City.

PLEASE show me in a diagram how to put a honeycomb coil inside a doubly-protected box arrangement, so I may use my outdoor antenna as a loop and gain selectivity, as described in RADIO WORLD, issue of October 4.—Thomas Waldkind, Albany, N. Y.

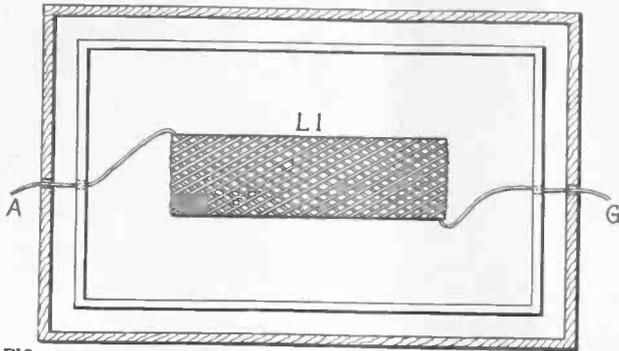


FIG. 43 (above) Showing how a coil is placed inside two boxes and sealed, for using your antenna as a loop.

A 25-turn honeycomb or duolateral coil (LI in Fig. 43) is placed inside a small wooden box, the leads being brought out through two holes bored in the box as shown. These holes are sealed with sealing wax. This contraption is placed in a slightly larger wooden box, where the process is repeated. Thus the coil is protected from the weather. The leads A and G go, respectively, to the end of the aerial farthest from the set and to the ground at that same point.

THE ARTICLE in RADIO WORLD for August 2, dealing with the Ideal Loop, does not specify the capacity of the condenser to be used to cover the range from 200 to 600 meters. What capacity condenser should be used? Concerning B. J. Bongart's 4-tube Super-Heterodyne, I should like to know if the loop and condenser specified is absolutely required or will any loop tuned by the proper condenser do the work?—Bernard C. McGee, 1829 Eye St., N. W., Washington, D. C.

The condenser to be used with this loop is .001 mfd., and should be of the low-loss type. This condenser will cover the wavelengths desired. Any loop and condenser that is designed for the broadcast wavelengths is suitable for Super-Heterodyne work. Suggest you wait for new data being prepared on this circuit.

I WOULD LIKE to construct one of the low-loss radio-frequency amplifier coils as recommended by Neal Fitzalan in the September 6 issue of RADIO WORLD, but cannot get a form to wind it on. Where can I purchase such a form or coil?—Earnest Knight, 1802 Dean St., Brooklyn, N. Y.

That form of coil you refer to is the basket weave type and may be purchased at almost any radio shop or in some chain stores.

I BUILT the Superdyne as described in RADIO WORLD for May 17, 24 and 31. I get good results, the stations coming in loud and clear, but I had a little trouble with the coils. I had wound them on cardboard tubing. I dismantled this set and bought a complete set of ready-made coils and I find that they are quite different. The coupler stator has only 25 turns of wire and the plate coil 25 turns. I have been told this will not cover the broadcast wavelengths. I would very much like to use these low-loss coils in place of the others as I want this set to stay put.—J. Woods, 14 Stanley St., Montreal, Can.

The low-loss coils you refer to do not need the same number of turns as the old type coils, because the wavelength range is greater when insulation is absent from the field. Undoubtedly they will be satisfactory when used with 23-plate low-loss condensers. The tuning should also be much improved.

I HAVE just completed the Monodial 3-tube set as described in RADIO WORLD. I used a commercial coil and Hammarlund 23-plate low-loss condensers and auto transformers from an old Tuska receiver. It works splendidly on the detector, but when I switch on the loudspeaker there is not enough volume, and if I turn the detector rheostat up high enough to get volume on the loudspeaker it is full of foreign noises and distortion. Could you suggest what might be my trouble? I get DX fine by using the headphones on the detector tube, but cannot use amplifiers.—W. L. Whitehurst, Conetoe, N. C.

Your trouble lies in the audio-frequency transformers or the audio-frequency wiring. Go over the connections carefully, and also test the transformers with a battery and headphones. Be sure to connect them properly in the circuit. It is important to get the plate and grid leads right.

IN THE July 26 issue of RADIO WORLD an article by Herman Bernard showed how to add a stage of RF to a 3-circuit tuner. I built this up and had several radio men test the same and all tell me that everything is properly connected. Still I fail to get any reception at all. What can the trouble be?—John O'Donnell, 783 East 156th St., Bronx, N. Y.

Since all the connections are in order, the trouble must be located in some of the parts used. Suggest you thoroughly examine the socket and condensers, and test other tubes in that part of the set. You will probably find your trouble is purely mechanical.

INFORMATION is desired on how to make low-loss variocouplers, as I believe they are better than the others. I would also like to get details about the Dynocoils that have proven so popular.—Will Morrell, 1402 Oregon Ave., Cleveland, O.

The method of making variocoupler low-loss is described in RADIO WORLD for July 5, and that article also tells how to make your condensers low-loss. The Dynocoils are described in detail in the August 9 issue.

I AM a regular reader of RADIO WORLD and have built a lot of the circuits published therein. I have never had trouble with any of them until I built the low-loss Neutrodyne. I have built this circuit and the lowest wavelength I can reach is WJZ on 455 meters. Anything above this wave I can receive all right. The trouble may be in the coils, as the antenna worked fine with other sets. What can be done to reach the lower wavelengths?—Roy C. Bagley, 34 Whiting St., Roxbury, Mass.

You have probably wound too many turns on the secondaries of the coils. So reduce the number of turns on each coil, one or two turns at a time, until you get down to 200 meters. You will be able to reach up to the higher wavelengths, about 600 meters, with ease.

1. DOES THE feedback through two stages of RF increase the signal strength or is the use of the ordinary variometer preferred? 2. Set does not have much volume over 400 meters. 3. Effect of regeneration not pronounced on higher wavelengths. 4. Adjustment of potentiometer has

little effect on operation of set.—Carl H. Lambach, Davenport, Iowa.

1. The variometer in the detector plate circuit is to be preferred unless the superdyne principle is utilized. 2 and 3. Try connecting a variometer in series with the tickler and plate. This will boost the inductance in this circuit and raise the wavelength, allowing full regeneration in the higher wavelengths. 4. Disconnect the ground connection from the grid return. The potentiometer with the suggested changes will be of little use.

I WOULD LIKE to have some advice about the connections of the Ultra-Reflex by Neal Fitzalan in RADIO WORLD for June 28.—A. E. Hicks, Mt. Washington, Mo.

Posts B and P are shunted with a .001 mfd. condenser. The primary B and A—are connected together. The top side of the coupler should go to the RF transformer. It would be proper to ground in on the minus A post or anywhere on this lead.

I WOULD like to build a 3-tube set having exceptional volume, using 199 tubes. What is your advice?—Murray Hemler, 876 New Lots Ave., Brooklyn, N. Y.

The Reflexed Neutrodyne, by N. N. Bernstein, described in the September 13 issue of RADIO WORLD, is just the thing for you.

CAN I BUY the coils for the Reflexed Magnadyne, as I do not want to wind them myself?—Wm. Boulden, 132 West 79th St., New York City. These coils may be purchased or some very nearly like them. Advertisers in RADIO WORLD or your radio store would be glad to help you out.

I HAVE an Aeriola, Sr., set to which I would like to add one step of RF amplification. Please tell me how this should be done.—Lucy Smith, Box 61, Bowling Green, Ky.

Refer to the May 3 issue of RADIO WORLD, "Adventures with the Neutrad Unit," solves your problem efficiently.

I WOULD like to have a 1-tube hookup which is a good DX getter, which is simple to operate.—J. Dryden, 147 Linden Ave., East Kildina, Manitoba.

Refer to the June 28 issue of RADIO WORLD. The article, "A Non-Squealing Regenerative Set," by Herman Bernard, will be "Eureka" to you.

I WOULD like to get some information regarding the Magnadyne, published in RADIO WORLD, issues of August 16 and 23.—F. H. Cooper, P. O., Drawer G, Johnstown, Pa.

The condensers used in this set are low-loss and have what are known as grounded rotors. The layout shows the outside of the inductances to the stators and from thence should go to the grid. The angle of the Dynocoils may be reversed, and this would shorten the leads somewhat.

I HAVE BEEN a reader of RADIO WORLD since almost its first number, and have built many of the sets described in the various numbers. In the article on the low-loss Superdyne, by N. N. Bernstein, in the August 23 and 30 issues, what is the resistance of R3 and R7?—Fred L. Hunkins, 71 Center St., Laconia, N. H.

R3 and R7 are .5 meg., that is, 500,000 ohms.

I NOTE that the tuning coil is sometimes referred to as a radio-frequency transformer, when consisting of primary and secondary. Is this correct?—Jackson Hall, Memphis, Tenn.

Yes. The fact that the inductance is not used for inter-stage coupling does not alter the fact that it is a radio-frequency transformer.

THE REFLEXED MAGNADYNE, A 3-TUBE NEUTRODYNE, by N. N. Bernstein, Technical Editor, issue of Sept. 13. Send 15 cents or start your subscription with that number. Radio World, 1493 Broadway, N. Y. C.

Join RADIO WORLD'S University Club

And Get Full Question and Answer Service for the Coming 52 Weeks.

RADIO WORLD, 1493 Broadway, New York City:

Enclosed find \$6.00 for RADIO WORLD for one year (52 Nos.) and also consider this as an application to join RADIO WORLD'S University Club, which gives me free information in your Radio University Department for the coming year.

Name
Street
City and State.....

Telegraphed queries will be answered collect the same day as received. Be sure to direct in your query that the answer be sent collect.

Mix Reports

Radio Industries Give Mac



(Foto Topics)

THE BOWDOIN, Capt. Donald H. MacMillan's exploration ship, being back from the North Pole, Donald Mix (above), the ship's radio operator, perforce is back, too. In New York City Mix told how those aboard had not only listened to jazz and classical compositions when fourteen degrees from the North Pole, but also had heard and recognized the voices of their loved ones at home. Frequently they listened in to Station POZ in Germany, he said. Amateurs in various parts of the United States have copied Mix's Polar messages. (Foto Topics.)

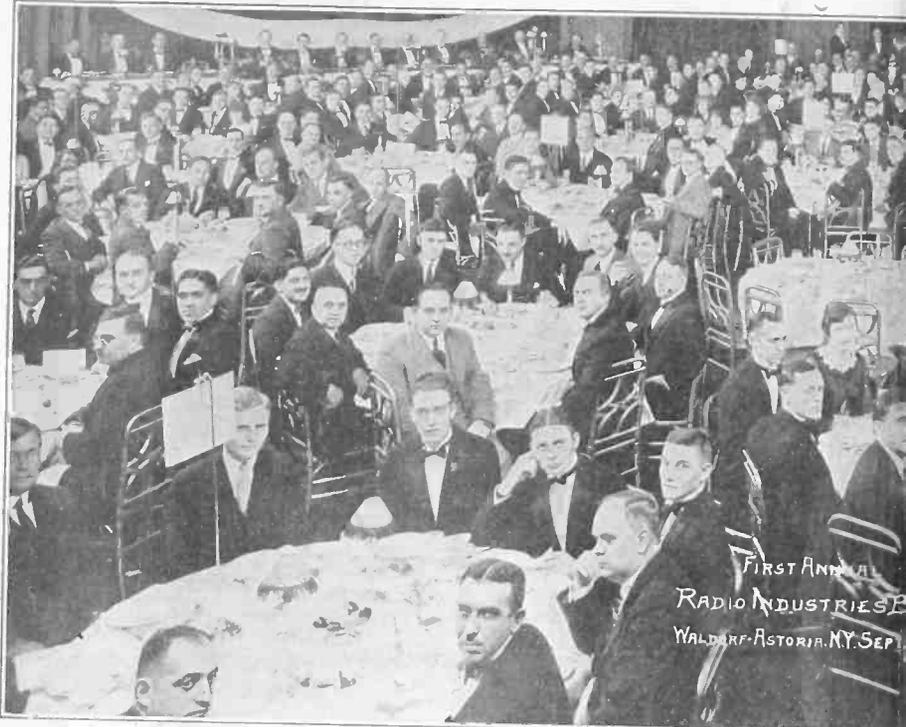



PHOTO OF DINER Hotel Waldorf-Astoria table at rear in the drew White, the fam from the right is Do ovation, all the diner returned to the city the National Associati Radio Corporation of Bernard, managing er the guests brought t 500 persons attending.



HOUSE THAT JACK BUILT is really an RF set, using crystal detector. It looks like a house and works like a charm. The constructor was John Neis, of 1533 Wolfram Street, Chicago. (Foto Topics.)



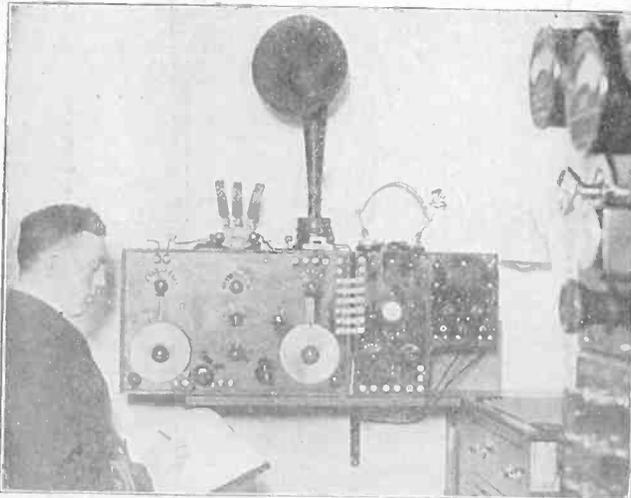THE SENDING ROOM at Madison Square Garden, used in broadcasting political speeches. The first of the candidates for President to speak at the Garden was Robert M. LaFollette, and this operator saw to it that the speech got on the air properly. (Fotograms.)




THE LATEST TYPE commercial receiver, with three stages of AF, is used aboard the SS. Republic, formerly the President Grant, broadcasting stations 3,000 miles away being heard on the speaker. (Kadel & Herbert.)




HERE is a handy way sockets on on

Millan Ovation at Banquet

Animal Tests

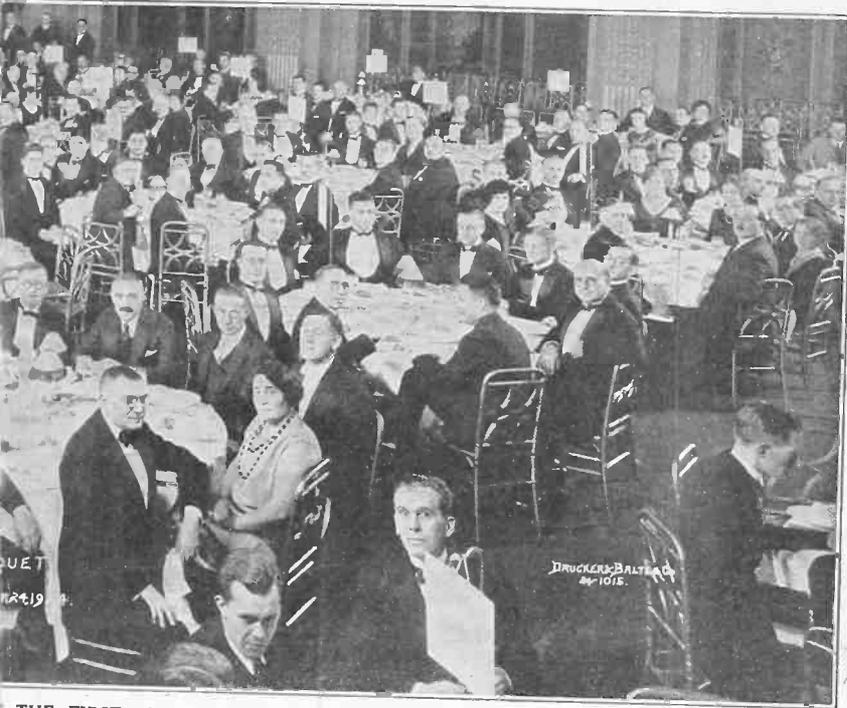

THE FIRST ANNUAL BANQUET OF THE RADIO INDUSTRIES, held in the ballroom of the New York City, during the week of the first annual Radio World's Fair. Sitting at the dais, the photo, are the guests, including the speakers. At extreme right at that table sits J. Announcer, an official of the Haynes-Griffin Radio Service, Inc., New York City retailers. Fifth B. MacMillan, the noted Arctic explorer, who, when he got up to speak, was given a two-minute and applauding all the while. He was the guest of honor. Only a few days before he had a four-year quest in the Arctic. At MacMillan's right sits Paul B. Klugh, executive chairman of Broadcasters, who was toastmaster. At Klugh's right sits David Sarnoff, vice-president of the Radio. RADIO WORLD was represented at the banquet by Fred S. Clark, manager, and Herman but their photographic identities are submerged in the shadowed background at right. Some of the women folk, who added to the attractiveness of the scene. The banquet was a great success, about every one of them remaining to the bitter end. (Drucker & Baltes, 106 W. 43d St., N. Y. C.)

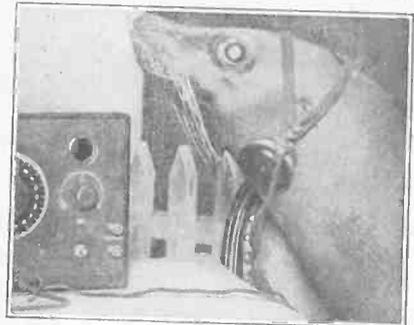

emble a Super-Heterodyne, with the eight and the transformers beneath.



THE RADIO is used as a means of applying intelligence tests to animals. Nobody, however, has been able to convince these noble beasts that speech and music actually come over the air. Animals seem to think we're trying to fool 'em. At top, right, is a bear, using earphones, as is the trained seal in the photo below that one. Above we see a dog listening to a speaker. The tests proved that the dog is radio's best friend, as he is man's, and that an uneducated bear has even more intelligence than a trained seal. (Photos by Underwood & Underwood.)

Mix Reports

Radio Industries Give Mac



(Foto Topics)

THE BOWDOIN, Capt. Donald H. MacMillan's exploration ship, being back from the North Pole, Donald Mix (above), the ship's radio operator, perforce is back, too. In New York City Mix told how those aboard had not only listened to jazz and classical compositions when fourteen degrees from the North Pole, but also had heard and recognized the voices of their loved ones at home. Frequently they listened in to Station POZ in Germany, he said. Amateurs in various parts of the United States have copied Mix's Polar messages. (Foto Topics.)

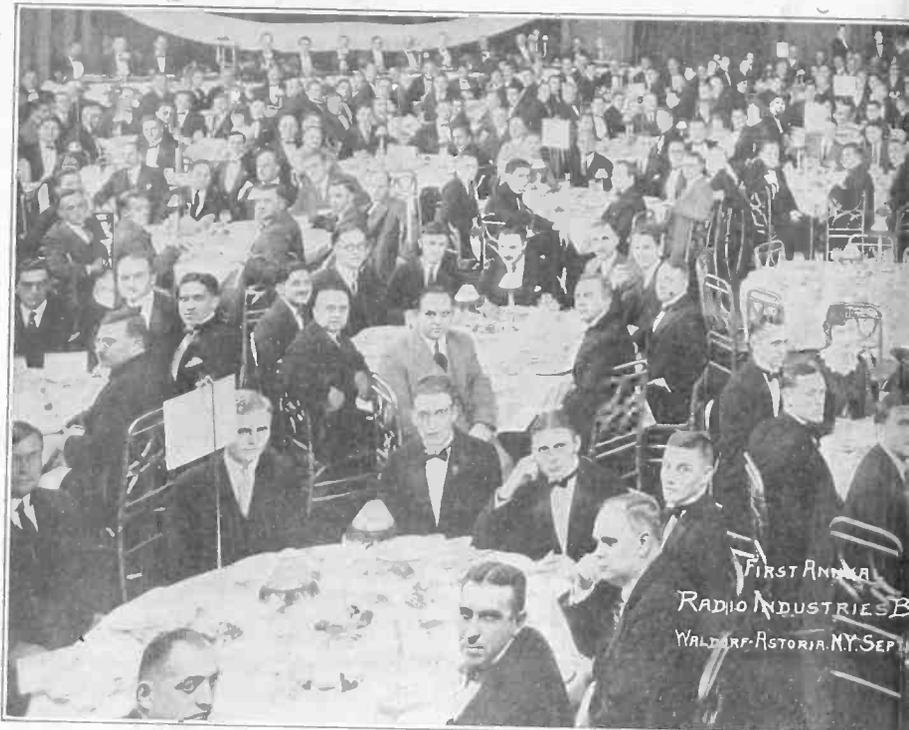



PHOTO OF DINERS at Hotel Waldorf-Astoria. The man at table at rear in the foreground is Fred White, the famous radio engineer. From the right is Dr. J. H. D. ... returned to the city ... the National Association of Broadcasters, managing editor of the guests brought to the city. 500 persons attending.



HOUSE THAT JACK BUILT is really an RF set, using crystal detector. It looks like a house and works like a charm. The constructor was John Neis, of 1533 Wolfram Street, Chicago. (Foto Topics.)



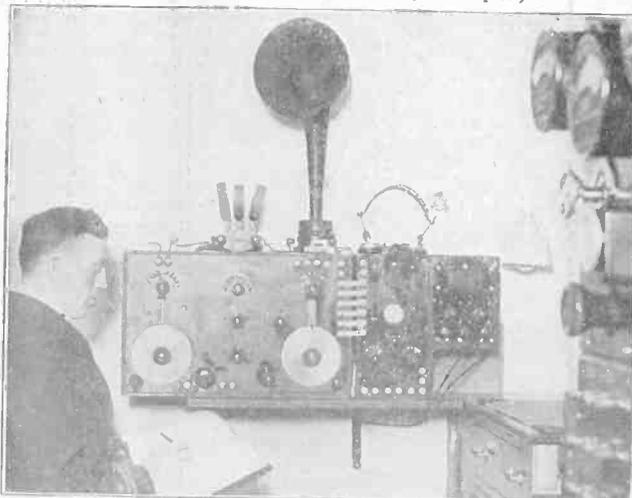THE SENDING ROOM at Madison Square Garden, used in broadcasting political speeches. The first of the candidates for President to speak at the Garden was Robert M. LaFollette, and this operator saw to it that the speech got on the air properly. (Fotograms.)



THE LATEST TYPE commercial receiver, with three stages of AF, is used aboard the SS. Republic, formerly the President Grant, broadcasting stations 3,000 miles away being heard on the speaker. (Kadel & Herbert.)




HERE is a handy way to connect sockets on one...

Millan Ovation at Banquet

Animal Tests



THE FIRST ANNUAL BANQUET OF THE RADIO INDUSTRIES, held in the ballroom of the New York City, during the week of the first annual Radio World's Fair. Sitting at the dais, the guests, including the speakers. At extreme right at that table sits J. Announcer, an official of the Haynes-Griffin Radio Service, Inc., New York City retailers. Fifth B. MacMillan, the noted Arctic explorer, who, when he got up to speak, was given a two-minute and applauding all the while. He was the guest of honor. Only a few days before he had a four-year quest in the Arctic. At MacMillan's right sits Paul B. Klugh, executive chairman of Broadcasters, who was toastmaster. At Klugh's right sits David Sarnoff, vice-president of ca. RADIO WORLD was represented at the banquet by Fred S. Clark, manager, and Herman but their photographic identities are submerged in the shadowed background at right. Some of women folk, who added to the attractiveness of the scene. The banquet was a great success, about every one of them remaining to the bitter end. (Drucker & Baltes, 106 W. 43d St., N. Y. C.)

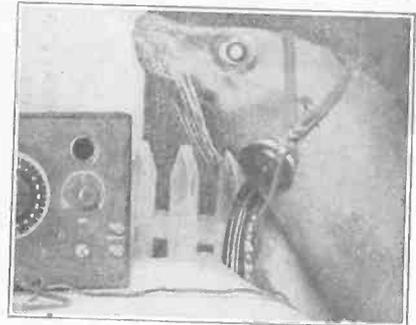

semble a Super-Heterodyne, with the eight and the transformers beneath.



THE RADIO is used as a means of applying intelligence tests to animals. Nobody, however, has been able to convince these noble beasts that speech and music actually come over the air. Animals seem to think we're trying to fool 'em. At top, right, is a bear, using earphones, as is the trained seal in the photo below that one. Above we see a dog listening to a speaker. The tests proved that the dog is radio's best friend, as he is man's, and that an uneducated bear has even more intelligence than a trained seal. (Photos by Underwood & Underwood.)

BROADCAST PROGRAMS

Thursday, October 9

WRC, Washington, D. C., 469m—5:15 P. M., code instruction. 6:00 P. M., children's hour by Peggy Albion. 7:45 P. M., motoring talk. 8:00 P. M., Georgada Macfarlane, mezzo-soprano. 8:15 P. M., dance program, Better Ole Club Orchestra; J. E. S. Kinsella, baritone. 9:15, to be announced. 9:55 P. M., time signals.

KFNF, Shenandoah, Ia., 266m—7:30 P. M., concert, Riverview Club of Neb. City, Neb.

WWJ, Detroit, 517m—8:00 A. M., setting-up exercises. 9:30 A. M., "tonight's dinner" and a special talk by the Woman's Editor. 9:45 A. M., Public Health Service bulletins. 10:25 A. M., official weather forecast. 11:55 A. M., Arlington time. 12:00 Noon, music. 3:00 P. M., the Detroit News Orchestra. 3:45 P. M., weather forecast. 3:55 P. M., market reports. 8:30 P. M., Detroit News Orchestra; Graeme Gillies, bass. 10:00 P. M., dance music by Jean Goldkette's Orchestra, from Graystone ballroom. 11:00 P. M., Detroit News Orchestra.

KHJ, Los Angeles, 395m—12:30 to 1:15 P. M., Coy Barkley and Palace Ballroom Orchestra. 2:30 to 3:30 P. M., musical. 6:00 to 6:30 P. M., Hickman's Concert Orchestra. 6:30 to 7:30 P. M., children's program. 8:00 to 9:00 P. M., program of Radio Corporation of Southern California. 9:00 to 10:00 P. M., birthday program for Queen Titania. 10:00 to 11:00 P. M., Hickman's orchestra.

WABM, Saginaw, Mich., 254m—10:15 A. M., news items, market quotations. 11:30 A. M., vocation and shopping talk, "Tonight's Dinner" weather forecast. 2:30 P. M., weather forecast, talks for women. 6:00 P. M., news items, Saginaw market quotations, weather forecast. (The above broadcast every day except Sunday.) 8:00 to 10:00 P. M., orchestra.

WDAR, Philadelphia, 395m—11:45 A. M., daily almanac; organ recital; Arcadia Concert Orchestra. 2:00-3:00 P. M., orchestra; recital. 5:00 P. M., question period in series of educational talks, Peirce School of Business Administration; Samuel H. Alman, "Where Does Your Money Go?" 5:45 P. M., sporting results. 7:30 P. M., Dream Daddy.

KSD, St. Louis, Mo., 546m—Silent.

WQJ, Chicago, 448m—11:00 A. M. to 12 Noon, Home Economics of Helen Harrington Downing; Erna Bertrams, "One Dish Meal"; Eleanor Chalmers, "Dressing Your Children." 3:00-4:00 P. M., Cora Beeman, "Deep Fat Frying." 7:00-8:00 P. M., Ralph Williams and His Rainbo Garden Orchestra; Manuel Rodriguez, tenor; Kathryn Snyder, reader. 10:00 P. M. to 2:00 A. M., Ralph Williams and His Rainbo Skylarks; jazz songs.

WBZ, Springfield, Mass., 337m—11:55 A. M., time signals; weather reports; Springfield market report. 6:30 P. M., songs. 6:40 P. M., Leo Reisman, Hotel Brunswick Orchestra. 7:00 P. M., market report. 7:10 P. M., "At the Theatres," with A. L. S. Wood, dramatic editor. 7:30 P. M., Uncle Dave Cory's Jack Rabbit story. 7:45 music by Charles R. Hector, St. James Theatre Orchestra. 8:15 P. M., music from the Hotel Brunswick, Boston. 9:15 P. M., Jessie M. French, contralto; Maud Middleton, accompanist. 9:55 P. M., music from the Hotel Kimball studio, Springfield.

KYW, Chicago, 536m—6:30 A. M., morning exercises. 9:30 A. M., financial and commercial markets. 10:30 A. M., farm and home. 11:35 A. M., table talk by Mrs. Anna J. Peterson. 2:35-4:00 P. M., "Afternoon Frolic." 6:02-6:18 P. M., news, financial and final markets. 6:35-7:00 P. M., children's bedtime story, told by "Uncle Bob" (Walter Wilson). 7:00-7:30 P. M., concert from Congress Hotel. 7:00-7:10 P. M., Joska De Babary's Orchestra. 7:10-7:20 P. M., Paul Whiteman's "Collegians," direction A. V. Gauthier. 7:20-7:30 P. M., DeBabary's Orchestra. 8:00-8:20 P. M., "Twenty Minutes of Good Reading" by Rev. C. J. Perrin, S. J., Loyola University. 8:20-9:15 P. M., music; Marguerite Gotthardt, soprano; George D. Horne, baritone; Ruth McBride, pianist. 9:15 P. M., "Safety First" talk. 10:00-11:30 P. M., studio program.

KDKA, East Pittsburgh, Pa., 326m—9:45 A. M., markets; agricultural items. 11:55 A. M., time signals. 12:00 Noon, weather forecast; reports of Pittsburgh livestock market and wholesale produce markets. 12:15 P. M., Scalzo's Orchestra. 6:30 P. M., KDKA Little Symphony Orchestra, Victor Saudek, conductor. 7:15 P. M., the children's period. 7:30 P. M., late news. 7:40 P. M., livestock and wholesale produce markets. 8:00 P. M., program by National Stockman and Farmer. 8:30 P. M., Little Symphony Orchestra; Irma Carpenter, soprano; Mrs. Elme Sulzner, contralto. 9:55 P. M., Arlington time signals; weather forecast. 11:00 P. M., Pittsburgh Post studio concert.

WOC, Davenport, Ia., 484m—10:00 A. M., opening market quotations. 10:05 A. M., household hints. 10:55 A. M., time signals. 11:00 A. M., weather and river forecast. 11:05 A. M., market quotations. 12:00 Noon, chimes concert. 12:15 P. M., weather forecast (repeated). 2:00 P. M., Closing stocks and markets, including weekly report of wool markets. 6:45 P. M., sport news and weather forecast. 7:00 P. M., bedtime stories by Val McLaughlin. (1 hour), Palmer school radio orchestra. Erwin Swindell, conductor.

WEAF, New York City, 492m—11:12 A. M.,

music, talk market and weather reports. 4:5 P. M., Pauline Fierstein, soprano. Other music.

WMAQ, Chicago, 447.5m—4 P. M., sport results. 4:10 P. M., household hour, Mrs. Elizabeth O. Hiller. 4:30 P. M., music. 6 P. M., Chicago Theatre organ recital. 6:30 P. M., Hotel LaSalle orchestra. 8 P. M., railway talk. 8:45 P. M., automobile trails. 9 P. M., University of Chicago. 9:15 P. M., Whitney trio.

WIP, Philadelphia, 509m—1 P. M., Gimbel Tea Room orchestra, Ray Steen, director. 1:30 P. M., weather forecast. 3 P. M., artist students from the Philadelphia Musical Academy, David Sokolove, pianist; Cecil Sigelski, violinist, and Lena Weber Brocker, contralto; Flora Ripka, accompanist. 6 P. M., weather forecast. 6:05 P. M., music under Charles Sansone, featuring Richard Brothers. 6:45 P. M., livestock and produce market reports. 7 P. M., Uncle Wip's bedtime stories, Kiddie Klub. 8 P. M., "Timely Talks to Motorists," Gene Hogle. 8:15 P. M., Philadelphia police band, direction Lieut. J. Kiefer. 9 P. M., "Horse Show," by A. K. Johnson. 9:15 P. M., Eleanor Moore Shute, contralto; Louis Shenk, baritone; Flora Ripka, accompanist. 10:05 P. M., Harvey Marburger, vaudeville orchestra.

WHN, New York City, 360m—12:30-1:00 P. M., Strickland's orchestra. 2:15-3:15, Bob Schaefer entertainers. John DeDroit's orchestra. 4:00 P. M., Alfred Dulin, pianist. 4:14 P. M., Madeline Groff, soprano. 4:30 P. M., Victor Wilbur, baritone. 4:45 P. M., Loretto C. Lynch, "Tea Time Talk." 5:00 P. M., Hickey Hickson's jazz artists. 6:30-7:00 P. M., Olcott Vail, violinist; Stephen Balogh, piano. 7:00-7:30 P. M., Specht's orchestra. 9:30 P. M., Flo Williams, songs. 9:45 P. M., Melody male quartette. 10:00 P. M., Spear's orchestra. 10:30 P. M., Romano's Roseland dance orchestra. 11:00 P. M., Gene Austin, own songs. 11:15-12:00 P. M., Loew's vaudeville. 12:00-12:30 P. M., Parody Club orchestra.

WOO, Philadelphia, 509m—11:00 A. M., organ. 11:30 A. M., weather forecast. 11:55 A. M., time signals. 12:00, Tea Room orchestra. 5:15 P. M., organ, trumpets. 7:40 P. M., Sports results, police reports. 9:55 P. M., time signals. 10:02 P. M., weather forecast.

KFI, Los Angeles, 469m—5:00-5:30 P. M., news. 5:30-6:00 P. M., Examiner news bulletins. 6:45-7:30 P. M., Y. M. C. A. lecture, Bon Ton orchestra. 7:30-8:00 P. M., Harry Porter, baritone, Sylvia Marotta. 8:00-9:00 P. M., Los Angeles Grand Opera association, "Romeo and Juliet" with Thalia Sabanieva. 11:00 P. M., Beniamino Gigli, Millo Picco.

WEEL, Boston, 303m—7:00 P. M., Boston Edison Big Brother club. 7:30 P. M., musicale. 9:00 P. M., program from N. Y. studio.

WJZ, New York City, 455m—10:00 A. M., menu, Mrs. Julian Heath. 10:20 A. M., "The Progress of the World," talk. 10:50 A. M., Eleanor Gunn's fashion talk. 1:00 P. M., Nathan Abas' Hotel Pennsylvania orchestra. 4:00 P. M., specialty numbers. 5:30 P. M., agricultural reports; closing quotations N. Y. Stock Exchange. 7:00 P. M., Bernhard Levitow's Hotel Commodore orchestra. 7:55 P. M., John B. Kennedy. 8:00 P. M., Wall Street review. 8:10 P. M., N. Y. Univer. Air College; Prof. Charles V. D. Magoffin, "Facts, Fancies and Figures of Archaeology." 8:30 P. M., to be announced. 10:00 P. M., Hotel St. George trio. 10:30 P. M., Waldorf-Astoria dance orchestra.

WJY, New York City, 405m—7:30 P. M., Weekly French lesson. 8:00 P. M., organ recital. 9:00 P. M., Al Reiser's orchestra.

WEBB, Chicago, 370m—7:8 P. M., concert. 9-10, dance; Sidney Ellstrom, baritone; musical bits; Nick Lucas, songs. 11-12 P. M., dance; Harry Davis, baritone; trio; late revue.

WNYC, New York City, 526m—7:30 P. M., police alarms. 8:30 P. M., Rose Maza, pianist. 9 P. M., Navy band. 10:10 P. M., "The Book of the Hour—Old New York," by Edith Wharton; speaker, Professor Carter Troop. 10:30 P. M., police alarms. 10:30 P. M., Sam Perry and Herbert Clair, piano. 11 P. M., weather. 2 P. M., Ada Bessie Swan, cooking. 2:30 P. M., market prices. 2:40 P. M., music. 3 P. M., J. B. Bayley, "Rabies or Hydrophobia."

WLAG, Minneapolis, 417m—10:45 A. M., "Hallow'en Party." 2 P. M., world series. 4 P. M., magazine reading, "The Mazurka." 5:30 P. M., children's hour. 6 P. M., baseball. 6:30 P. M., Heiman's orchestra. 7:30 P. M., talk. 9 P. M., weather. 10 P. M., Hoo Hoo orchestra; glee club.

Friday, October 10

KFNF, Shenandoah, Ia., 266m—7:30 P. M., program by Thurman Iowa, direction Fred F. Flatt.

KFI, Los Angeles, 469m—5:00-5:30 P. M., news bulletins. 5:30-6:00 P. M., news bulletins. 6:45-8:00 P. M., organ recital. 8:00-9:00 P. M., Carl Edward Hatch. 9:00-10:00 P. M., program from Examiner Studio. 10:00-11:00 P. M., John Smallman night. 11:00-12:00 P. M., Ambassador Hotel Coconut Grove Orchestra.

WWJ, Detroit, 517m—8:00 A. M., setting-up exercises. 9:30 A. M., "tonight's dinner" and a special talk by the Woman's Editor. 9:45 A. M., Public Health Service bulletins. 10:25 A. M., weather forecast. 11:55 A. M., Arlington time. 12:00 Noon, music. 3:00 P. M., Detroit News Orchestra. 3:50 P. M., weather forecast. 3:55 P. M., market reports. 8:30 P. M., Detroit News Orchestra; Donald Pratt, baritone; Deora Wolfe, pianist.

WRC, Washington, D. C., 469m—3:00 P. M., fashion development. 3:00 P. M., Arthur McCormick, baritone. 3:20 P. M., "Beauty and Personality" by Elsie Pierce. 3:25 P. M., Current Topics. 3:35 P. M., piano recital. 3:50 P. M., The Magazine of Wall Street. 4:00 P. M., song recital. 5:15 P. M., time signals and

weather forecasts. 6:00 P. M., stories for children by Peggy Albion.

KHJ, Los Angeles, 395m—12:30-1:15 P. M., news and music. 2:30-3:30 P. M., music. 6-6:30 P. M., Art Hickman's concert orchestra from the Biltmore Hotel; Edward Fitzpatrick, director. 6:30-7:30 P. M., children's program, Prof. Walter Sylvester Hertzog on American history; Richard Headrick, screen juvenile; bedtime story, Uncle John. 8-10 P. M., Mullen & Bluet program. 10-11 P. M., Hickman's orchestra.

WDAR, Philadelphia, 395m—11:45 A. M., daily almanac. 12 Noon, organ; Arcadia concert orchestra. 2-3 P. M., concert orchestra; playlet. 4:30 P. M., dance. 5:45 P. M., sporting results. 7:30 P. M., Dream Daddy. 8 P. M., book review, Arnold Abbott; studio artists. 10 P. M., Morning Glory Club; Lanin's dance orchestra; studio artists.

KSD, St. Louis, Mo., 546m—8 P. M., Sixth U. S. Infantry band.

WQJ, Chicago, 448m—11 A. M. to 12 Noon, Mann and his Sunday dinner. 3-4 P. M., J. Downing, "Hallow'en Doughnuts"; Mrs. F. T. Sanger, "Rainier National Park." 7-8 P. M., dinner concert by Williams orchestra; Do. Schubert, soprano; Arthur W. Ward, tenor; Harry Geise, piano. 10 P. M.-2 A. M., a. a. p. Williams and Skylarks, songs and specialties.

WBZ, Springfield, Mass., 337m—11:55 A. M., time signals; weather; market report. 6 P. M., Westinghouse Philharmonic Trio. 7 P. M., market reports. 7:10 P. M., book review. 7:20 P. M., "What Types of Lighting Fixtures Give Best Service." 7:30 P. M., bedtime story. 9:55 P. M., time; weather. 10 P. M., J. K. Murray, tenor; Clara Lather, soprano. 10:30 P. M., to be announced. 11 P. M., Westinghouse Philharmonic Trio; Alwyn E. W. Bach; Katherine Gravelin, accompanist. 11:30 P. M., dance, McEnelly's singing orchestra.

KYW, Chicago, 536m—6:30 A. M., exercises. 9:30 A. M., news, financial and commercial markets. 11:35 A. M., table talk by Mrs. Anna J. Peterson. 12:30 P. M., "The Progress of the World," talk. 6-6:30 P. M., news, financial markets review of Chicago trade. 6:35-7 P. M., bedtime story by "Uncle Bob." 7-7:30 P. M., dinner concert from Congress Hotel. 7:10-7:20 P. M., DeBarbary's orchestra. 7:10-7:20 P. M., Whiteman's "Collegians." 7:20-7:30 P. M., DeBarbary's orchestra. 7:30-8 P. M., program from studio. 8:20-8:45 P. M., speeches, American Farm Bureau Federation. 9:30-10:30 P. M., revue. 10:30-10:45 P. M., stage revue. 10:45 P. M.-12:30 A. M., continuation of midnight revue. 12:30 A. M., organ solo, W. Remington Welch.

KDKA, East Pittsburgh, Pa., 326m—9:45 A. M., reports on markets; agricultural items. 11:55 A. M., time. 12 Noon, weather; reports Pittsburgh live stock and wholesale produce markets. 12:15 P. M., concert by Daugherty's orchestra. 6:30 P. M., organ, Paul E. Freeger. 7:15 P. M., children's period. 7:30 P. M., news. 7:40 P. M., reports primary livestock and wholesale produce markets. 8 P. M., "What Types of Lighting Fixtures Give Best Service," talk; "Football Coaching," Guy M. (Chalky) Williamson, University of Pittsburgh. 8:30 P. M., Westinghouse band, T. J. Vastine, conductor; Alice Smith, soprano; F. Robert Coe, baritone. 9:55 P. M., time; weather.

WHAS, Louisville, Ky., 400m—4-5 P. M., Alamo Theatre orchestra; police bulletins; weather; news. 4:55 P. M., local livestock, produce and grain market reports. 5 P. M., time. 7:30-9 P. M., "Dix Bluegrass Serenaders"; contralto solos, Mrs. M. E. Burchett, accompanied by Mrs. Harry Long; international Sunday school lesson; welfare talk; news; time announced at 9 o'clock.

WOC, Davenport, Ia., 484m—10 A. M., market quotations. 10:05 A. M., household hints. 10:55 A. M., time. 11 A. M., weather. 11:05 A. M., market. Noon, chimes. 12:15 P. M., weather (repeated). 2 P. M., stocks and markets. 6:45 P. M., sport news and weather. 7 P. M., Sandman. 7:20 P. M., "Girls Club Work," by Lulu Trengone. 8 P. M., musical (1 hour)—Ralph Jaenicke and his orchestra.

WEAF, New York City, 492m—11 A. M.-12 Noon, musical and talks; market and weather reports. 4:5 P. M., program for women, musical. 6-10 P. M., music from the Waldorf-Astoria; children's story by Blanche Elizabeth Wade; Edith Bailey, soprano; The Happiness Boys; Minnie Weil, pianist; Astor Coffee dance orchestra.

WMAQ, Chicago, 447.5m—4 P. M., sport results. 4:10 P. M., items for women. 4:30 P. M., musical. 6 P. M., organ. 6:30 P. M., orchestra. 8 P. M., Wide-Awake club, Mrs. Francis M. Ford. 8:30 P. M., musical geography, by Mr. and Mrs. Marx E. Oberndorfer. 9 P. M., program from Waukegan, Ill.

WGY, Schenectady, N. Y., 380m—11:55 A. M., time. 12:30 P. M., stock market. 12:40 P. M., produce market. 12:45 P. M., weather. 12:50 P. M., farm movement of lettuce. 2 P. M., music, "Hints for the Home Maker," courtesy Society of Electrical Development. 6 P. M., markets; news. 6:30 P. M., stories for children. 7 P. M., Sunday school lesson. 7:45 P. M., health talk. 7:50 P. M., Remington Typewriter band. 10:30 P. M., music by Remington Typewriter band.

WHN, New York City, 360m—2:15 P. M., songs. 2:30 P. M., songs. 2:45 P. M., Hitter's orchestra. 3:45 P. M., Uncle Robert's chat to children. 3:50 P. M., Mabel Livingston, children's poet. 4 P. M., Arthur Ball, tenor. 4:15 P. M., Joseph C. Wolfe, baritone. 4:30 P. M., recital, Genevieve Williams, soprano; Charles Strickland, pianist; Sam Steinberg, violinist. 5 P. M., Chas. B. Allen orchestra. 6:30-7 P. M., violin, Olcott Vail, accompanied by Stephen Balogh, piano. 7:30 P. M., Specht's orchestra. 9:30 P. M., Gregory's orchestra. 10 P. M., baseball statistics by Al Munroe Elias.

05 P. M., Cogert's revue, Sol. Hirsch, pianist; Deck Motta, Lillian Pitt, Ed. Bridges, Stella Weck. 10:20 P. M., Bob Emmerich, jazz pianist. 10:30 P. M., Henderson's orchestra. 11 P. M., Jack Morrisse, tenor 11:15 P. M., vaudeville. 11:30 P. M., Wooding's orchestra. 12-12:30 A. M., Parody Club orchestra.

WIP, Philadelphia, 509m.—1 P. M., music by Tea Room orchestra. 1:30 P. M., weather. 3 P. M., popular music, direction Harry Link. 4 P. M., "The Psychopathic Child," talk by Dr. N. W. Winkleman. 6 P. M., weather. 6:05 P. M., Jordan-Lewis dance orchestra. 6:45 P. M., livestock and produce reports. 7 P. M., Uncle Wip's bedtime stories; Kiddie Klub; Wallace Root, Honor Boy Scout, experiences at the Jamboree, Copenhagen.

WJZ, New York City, 455m.—10 A. M., menu, Mrs. Julian Heath. 10:20 A. M., arts and decorations talk. 10:50 A. M., fashions. 1 P. M., Zantio. 4:30 P. M., Leo Riggs, organist. 5:30 P. M., agricultural reports; closing quotations of N. Y. Stock Exchange; foreign exchange; 7 P. M., Lafayette Hotel orchestra. 8 P. M., all Street review. 8:10 P. M., N. Y. University. 9 P. M., Prof. Charles V. D. Magofan, president, Archaeological Institute of America, "Facts, Fancies and Figures of Archaeology." 8:30 P. M., May Singhi Breen, banjo. 8:50 P. M., "Chats with the Editor," Earnest A. Zadig. 9 P. M., Breen, banjo. 9:15 P. M., Army Night, "Bonny," by Gen. Robert B. Davis; music, 16th Inf. band.

WJY, New York City, 405m.—7:30 P. M., Wynne's orchestra. 8:30 P. M., current topics, W. H. Allen. 8:55 P. M., "Income Taxes," Frank Shevit. 9:15 P. M., Democratic National Committee talk.

WEEI, Boston, 365m.—1 P. M., Chamber of Commerce luncheon. 7 P. M., Boston Edison Big Brother Club. 7:30 P. M., music. 11 P. M., dance. Dok Eisenburg and his Sifonians.

WAAM, Newark, N. J., 263m.—2 P. M., market prices. 2:10 P. M., Jimmy LaSelle. 2:40 P. M., American Radio Relay League. 2:45 P. M., music. 8 P. M., sports talk. 8:45 P. M., Ethel West, soprano. 9 P. M., Rosedale orchestra. 9:30 P. M., Imperial quintette, melodies. 10 P. M., Catellos dance orchestra, entertainers. 10:45 P. M., Harry Greenwood, stories.

WLAG, Minneapolis, 417m.—10:45 A. M., "Eat and Keep Young," Betty Crocker. 2 P. M., talk. 2:30 P. M., world series. 4 P. M., magazine reading. C. G. Milham. 5:30 P. M., children's hour, Ellen Nye. 6 P. M., baseball scores and sport hour. 6:30 P. M., Heiman's orchestra. 8 P. M., fire prevention talk. 8:30 P. M., Barrett's band. 9 P. M., weather.

WNYC, New York City, 526m.—7:30 P. M., police alarms. 8:30 P. M., Creighton Allen, pianist. 8:45 P. M., Arthur Baecht, violin. 9 P. M., Creighton Allen. 9:15 P. M., Arthur Baecht. 9:30 P. M., a talk on the Board of Estimate, by Peter McGowan. 9:40 P. M., recital. 10:10 P. M., "Arneo," by Col. H. Edmund Bullis. 10:30 P. M., police alarms. 10:35 P. M., Ward orchestra. 11 P. M., weather. 11:05 P. M., Ward orchestra. 11:30 P. M., Vaughan and Leath. 12 P. M., Martin orchestra from 'Ill Say She Is."

WEBA, Chicago, 370m.—7-8 P. M., concert; La Ponsa Musical College. 9-10 P. M., dance; Marann Manship, soprano; Nick Lucas, songs. 11-12 P. M., dance; Winter Garden Four; Pdererick Agard, songs; Edgewater Beach trio.

Saturday, October 11

WLAG, Minneapolis, 417m.—10:45 A. M., girl's club. 2 P. M., Haskell Indians and U. of M. football game. 6 P. M., baseball and sport hour. 8 P. M., fire prevention talk. 8:30 P. M., Imperial quartet. 9 P. M., weather. 11 P. M., Heiman's orchestra.

WNYC, New York City 526m.—6:30 P. M., Wooding's Club Alabama orchestra. 7:30 P. M., police alarms. 7:35 P. M., Chateau Four. 8:30 P. M., Nazarene Chorus. 9:20 P. M., vocal program. 10:10 P. M., the screen—season's new plays, in- WEBH, Chicago, 370m.—7-8 P. M., Edgewater 10:30 P. M., police alarms. 11 P. M., weather, including "Conscience" and "Havoc," Ada Sterling, Beach Oriole orchestra; Helen Snyder, soprano; Radio Sunday School lesson. 9-10 P. M., dance; musical bits. 11-12 P. D., dance selections; Hawaiian Guitars; Marie Kelly, reader; Tom Malie and Jack Little, songs.

KHJ, Los Angeles, 395m.—12:30-1:15 P. M., program, Atwater Kent Radio Co., Uncle Remus. 2:30-3:30 P. M., music. 6-6:30 P. M., Hickman's orchestra. 6:30-7:30 P. M., children's program, Prof. Walter Hertzog, stories of American history; Maud Haskins, harp; bedtime story, Uncle John. 8-9 P. M., program of the Continental National Bank. 9-10 P. M., program of Greater Westlake Business Association. 10-11 P. M., Hickman's dance orchestra.

WDAR, Philadelphia, 395m.—11 A. M., organ. 11:45 A. M., daily almanac. 12 Noon, organ; features from studio; concert orchestra. 2-3 P. M., Arcadia concert orchestra. 4:30 P. M., studio artists. 5 P. M., Samuel H. Talman, "Where Does Your Money Go?" 5:45 P. M., sporting results. 7:30 P. M., Dream Daddy. 7:45 P. M., news for farm folks. 8 P. M., concert orchestra; E. E. Schermerhorn, "Fire Preventions." 8:15 P. M., Edwin Mathews, "Flowers and the Garden." 9:20 P. M., movie review. 9:30 P. M., Stanley Theatre, overture. 10 P. M., Arcadia Cafe dance orchestra; vaudeville, Fay's Knickerbocker Theatre.

KDKA, East Pittsburgh, Pa., 326m.—9:45 A. M., livestock markets; general market review; agricultural items. 11:55 A. M., time. 12 Noon, weather; Pittsburgh live stock and wholesale produce markets. 12:15 P. M., Daugherty's orchestra. 3 P. M., Pitt-West Virginia football game from Forbes Field, Pittsburgh. 6:30 P. M., concert. 7:15 P. M.,

children's period. 7:30 P. M., news. 7:45 P. M., Sunday school lesson, by Carman Cover Johnson. 8 P. M., sport review. 8:15 P. M., Heinz program. 9:55 P. M., time; weather.

KSD, St. Louis, Mo., 546m.—7 P. M., orchestral music and specialties from Missouri Theatre. WQJ, Chicago, 448m.—11 A. M.-12 Noon, H. F. West, "Pressure Cookers"; other speakers. 3-4 P. M., "Coffee" Klatsch, 300 ladies will be entertained in Rainbo Gardens. 7-8 P. M., Otis P. Jester, soprano; Mary House, pianist; William Molnaire, tenor. 10 P. M.-2 A. M., Ralph Williams and Skylarks; Jerry Sullivan; The Melodians; Geo. A. Little and Larry Shay; Marion Morgans, prima donna; Malie and Little; Lew Butler.

WBZ, Springfield, Mass., 337—11:55 A. M., time; weather. 6:30 P. M., Brunswick orchestra. 7 P. M., market report. 7:30 P. M., bedtime story. 7:40 P. M., Hotel Kimball trio, Jan Geerts, violinist and director; Arnold Janser, cellist; Lloyd Stoneman, pianist. 8:30 P. M., Women's Philharmonic orchestra. 9 P. M., Weltman Conservatory Jr. orchestra. 9:55 P. M., time; weather. 10 P. M., Albert Edwards, baritone.

KYW, Chicago, 536m.—6:30 A. M., exercises 9:30 A. M., news and comment financial and commercial markets. 10:30 A. M., farm and home service. 11:35 A. M., table talk by Mrs. Anna J. Peterson of Peoples Gas Co. 6:02-6:10 P. M., news, financial and final markets. 6:35-7 P. M., children's bedtime story, "Uncle Bob." 7-7:30 P. M., dinner concert from Congress Hotel. 7-7:10 P. M., DeBabry's orchestra. 7:10-7:20 P. M., Whiteman's "Colleagians." 7:20-7:30 P. M., DeBabry's orchestra. 8-8:58 P. M., music; Adeline Keller, soprano; Mildred Pike, contralto; George Morosoff, tenor; Sallie Menkes, accompanist. 9:05 P. M., Youth's Companion. 9:35-11:30 P. M., show.

WGY, Schenectady, N. Y., 389m.—11:55 A. M., time. 12:30 P. M., stock market. 12:40 P. M., produce market. 12:50 P. M., farm movement of lettuce. 8:30 P. M., dance; popular songs; football results.

WOC, Davenport, Ia., 484m.—10 A. M., opening market quotations. 10:05 A. M., household hints. 10:55 A. M., time. 11 A. M., weather. 11:05 A. M., market. 11:10 A. M., agricultural bulletins. 12 Noon, chimes concert. 12:15 P. M., weather. 12:17 P. M., closing markets. 6:45 P. M., sport news and weather. 7 P. M., Sandman's Visit. 9 P. M., orchestra (1 hour); Ralph W. Fuller, baritone.

WMAO, Chicago, 447.5m.—4 P. M., sport results 6:30 P. M., Hotel LaSalle orchestra. 8 P. M., Salvation Army band. 8:40 P. M., lecture, Dr. Max Heinius, Scandinavia. 9 P. M., theatre review.

WEAF, New York City, 492m.—1:45 P. M., play by play description of the Columbia-Wesleyan football game direct from Baker Field. 4 P. M., Clifford Lodge dance orchestra. 6-12 P. M., music from Waldorf-Astoria; stories for boys, by Fred J. Turner; Charles Wold, musical glasses; Josiah B. Free, baritone; Nancy McCord, soprano; Virginia Masselink, pianist; Rubi Davis, violinist; L. Wolfe Gilbert, pianist, and Abner Silver, singer; Count de Martini and his Hotel St. George concert orchestra; Vincent Lopez and his orchestra from Hotel Pennsylvania.


WHN, New York City, 360m.—2:15 P. M., Bert Dixon and Elmo Russo, songs. 2:30 P. M., Samuel Weber, blind pianist. 2:45 P. M., Blue Ridge entertainers. 3:45 P. M., Ellen Montague Cross Concert Company. 4:15 P. M., Elias Cohen, violinist; Ruben Kroll, pianist. 4:30 P. M., Kathryn Connelly, soprano. 4:45 P. M., boy's period. 5 P. M., Johnston-Davison orchestra. 6:30-7 P. M., violin solos by Olcott Vail; Stephen Balogh at piano. 7-7:30 P. M., Specht's orchestra. 7:30 P. M., Hotel Carlton Terrace orchestra. 8 P. M., "Personal Chats of Screen Life," by E. S. Colling. 8:15 P. M., Arthur Stone, blind pianist. 8:30 P. M., "Goodnight Children," by Elizabeth Morrison-Jones. 8:45 P. M., Tom Bracken and Bob King. 9 P. M., Pergola Brothers, accordion and banjo. 9:15 P. M., Jimmy Flynn, tenor. 9:30 P. M., "Columbus Day," by Jos. A. Lawson. 9:45 P. M., Fitzpatrick Bros., old-time medleys. 10 P. M., baseball statistics by Al. Munroe Elias. 10:05 P. M., Lillian Havel, soprano. 10:15 P. M., Victor Wilbur, baritone. 10:30 P. M., Chas. Degele, violinist; Segerer Brothers, zither. 11 P. M., Jimmy Clarke and his entertainers. 11:30 P. M., Henderson's Roseland dance orchestra.

WIP, Philadelphia, 699m.—1 P. M., organ, Karl Bonawitz. 1:30 P. M., weather. 3 P. M., play by play description of the football game Univ. of P. and Sfarthmore, from Franklin Field. 6 P. M., weather. 6:05 P. M., Hotel St. James dance orchestra. 6:45 P. M., livestock, and produce 7 P. M., Uncle Wip's bedtime stories, Kiddie Klub. 8 P. M., "The Ballet and Its Development in America." Florence Cowanova. 8:15 P. M., Zernsay orchestra, dance. 9 P. M., Mason-Heffin male quartet. Roy MacClellan, Frederick Aime, Albert Hirst, Henry L. Booth, Natalie Heider, pianist; Flora Ripka, accompanist. 10:05 P. M., dance Hotel St. James orchestra. 11:05 P. M., organ, Karl Bonawitz.

WJZ, New York City, 455m.—4 P. M., music. 5:30 P. M., agricultural reports; closing quotations N. Y. Stock Exchange. 7 P. M., Waldorf-Astoria dance orchestra. 8 P. M., to be announced. 9 P. M., "The Cost to Business of Stolen Mail," by Owen A. Keen. 10:30 P. M., Hotel Astor dance orchestra.

WWJ, Detroit, 517m.—8:00 A. M., setting-up exercises. 9:30 A. M., "tonight's dinner" and a special talk by the Woman's Editor. 10:25 A. M., weather forecast. 11:55 A. M., Arlington time. 12:00 Noon, music. 3:00 P. M., Detroit News Orchestra. 3:50 P. M., weather forecast. 3:55 P. M., market reports and football scores. 5:00 P. M., football scores.

MAGNAVOX
Radio Products

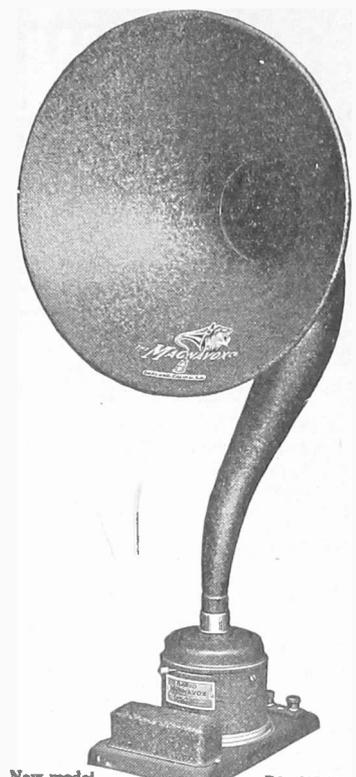

New model R3—\$35.00

Current consumption in the new Magnavox Reproducer R3 is so low that it is an unimportant factor.

This feature, combined with the new Volume Control, makes the new R3 indispensable for use with every radio receiving set.

- Magnavox Reproducers**
- R2 with 18-inch curvex horn \$50.00
 - R3 with 14-inch curvex horn \$35.00
 - M1 with 14-in. curvex horn. Requires no battery for the field. \$30.00
 - M4 Latest Magnavox Reproducer. Requires no battery. \$25.00

- Magnavox Combination Sets**
- A1-R consisting of electro-dynamic Reproducer with 14-inch curvex horn and 1 stage of amplification \$59.00
 - A2-R consisting of electro-dynamic Reproducer with 14-inch curvex horn and 2 stages of amplification \$85.00

Magnavox Power Amplifiers

One, two and three stage . . . \$27.50 to \$60.00

Magnavox Vacuum Tubes

Type A—six volt storage battery tube with standard base; requires no circuit changes . . . \$5.00

Magnavox products are sold by reliable Dealers everywhere. Write for catalogue.

The Magnavox Company
Oakland, California
New York and San Francisco
Canadian Distributors
Perkins Electric Limited
Toronto Montreal Winnipeg

Conference Paves Way for Better Programs All Over U. S.

RADIO WORLD

The Mag. U. S. Pub. Off.



TELEPHONE: LACKAWANNA 6976. 2068
PUBLISHED EVERY WEDNESDAY

(Dated Saturday of same week)

FROM PUBLICATION OFFICE

HENNESSY RADIO PUBLICATIONS CORPORATION
ROLAND BURKE HENNESSY, President
M. B. HENNESSY, Vice-President
FRED S. CLARK, Secretary and Manager
1493 BROADWAY, NEW YORK, N. Y.

European Representative: The International News Co.,
Breams Bldgs., Chancery Lane, London, Eng., Paris,
France. Brentano's, 38 Avenue de l'Opera.

EDITOR, Roland Burke Hennessy
MANAGING EDITOR, Herman Bernard

SUBSCRIPTION RATES

Fifteen cents a copy. \$6.00 a year. \$3.00 for six months. \$1.50 for three months. Add \$1.00 a year extra for foreign postage. Canada, 50 cents.

Receipt by new subscribers of the first copy of RADIO WORLD mailed to them after sending in their order, is automatic acknowledgment of their subscription order. Changes of address should be received at this office two weeks before date of publication. Always give old address also. State whether subscription is new or a renewal.

ADVERTISING RATES

RATES—Page, 7 1/2 x 11", \$200.00; half page, 8 1/2 D. C. or 5 1/2 x 13" col., \$100.00; quarter page, 4 1/2 D. C., \$50.00; one col., 2 1/4 x 11", \$66.66. \$7.00 per inch. Per agate line, 50c. Times Discounts: 52 Consecutive Issues, 20%; 26 Times Consecutive, or E. O. W. One Year, 15%; 4 Consecutive Issues, 10%.

CLASSIFIED ADVERTISEMENTS

Ten cents per word. Minimum, 10 words. Cash with order.

Entered as second-class matter, March 28, 1922, at the Post Office at New York, N. Y., under the act of March 3, 1879.

OCTOBER 11, 1924

The Health of the Industry

THE fact that final figures show more than 150,000 persons attended the First Radio World's Fair during its seven-day run at Madison Square Garden, New York City, shows the splendid health of the industry. Public interest is the gauge and that interest ran high. What a winter this will be for the industry! The big Fall season already is well under way, and the trade is sending in enthusiastic reports.

It is well to remember that although the automobile industry is ten years older than the radio industry, no one yet has succeeded in running an automobile show in New York City from which it was necessary to close the doors each night against 5,000 to 10,000 persons, on account of a capacity house. And as for the phonograph trade—oh, well!

Hoover's Address Impresses Gathering—Interference, Advertising and Wavelengths Discussed

THE Third National Radio Conference, held here at the instance of Secretary of Commerce Hoover, grappled with the problems of making all stations a part of a national chain, wavelength allocation, interference, "indirect advertising," and other subjects brought up by Secretary Hoover in his address to the convention. He stressed the voluntary nature of the conference and the desire for solutions by agreement rather than by compulsion.

Concerning the chain idea, he said:

"Experimental broadcasting upon a national scale during the past year has now brought us to the stage where we know it can be done. The local material available for the local program is not in my view enough to maintain assured interest, and therefore maintain the industry, or to adequately fulfill the broadcasting mission. So far as the art has developed, I think we all agree that for accuracy and regularity of reception we can depend only upon the local broadcasting stations. My proposition is that the local stations must be able to deliver every important national event with regularity. The local station must be able to bring to its listeners the greatest music and entertainment of the nation, but far beyond this it must be able to deliver important pronouncements of public men, it must bring instantly to our people a hundred and one matters of national interest. To this it must add its matters of local interest. This can only be accomplished by regularly organized interconnection on a national basis with nationally organized and directed programs for some part of the day in supplement to more local material. The greatest advance in radio since our last conference is the complete demonstration of the feasibility of interconnection.

Monopoly Inconceivable

It has been possible to broadcast many national events over three-quarters of the United States during the past year, and the whole country has been covered twice. The service deserves the appreciation of the public, for it has demonstrated this great thing to be practicable.

"It is our duty to consider the possibilities and potentialities of interconnection as a regular daily routine of the nation. Unless it be systematically organized we cannot expect its continuation.

"It would be unfortunate indeed if such an important function as the distribution of information should ever fall into the hands of the Government. It would be still more unfortunate if its control should come under the arbitrary power of any person or group of persons. It is inconceivable that such a situation could be allowed to exist. But I am not now dealing with monopoly."

On the subject of broadcast ads, he said:

"I believe that the quickest way to kill broadcasting would be to use it for direct advertising. The reader of the newspaper has an option whether he will read an ad or not, but if a speech by the President is to be used as the meat in a sandwich of two patent medicine advertisements, there will be no radio left. To

what extent it may be employed for what we now call indirect advertising I do not know and only experience with the reactions of the listeners can tell."

As for a tax on receiving sets or other financing, he said:

"I do not believe there is any practical method of payment from the receivers. I wish to press for consideration the possibility of mutual organization by broadcasters of a service for themselves similar to that which the newspapers have for their use in the press associations, which would furnish programs of national events and arrange for their transmission and distribution on some sort of a financial basis just as the press associations gather and distribute news among their members."

Regarding congestion of the air, Secretary Hoover mentioned the 32 possible solution of assigning present Class C wavelengths to Class B stations, and other methods.

5,000 Watts and Up

Concerning power of stations he said: "Another question of importance is the limit of power to be used in broadcasting. Most Class B stations are now operating on 500 watts. A limitation of 1,000 watts is imposed in the license. I understand there are several stations erected or in course of construction which contemplate the use of power up to 5,000 watts, and I am aware of the suggestions of those who would go beyond even this. There is opposition to the plan. Its advocates tell us of the great advantages in the way of louder signals and more distant transmission, while opponents complain of interference and the drowning out of other stations. The latter fear is particularly acute when the powerful station is located in a congested receiving center. From the viewpoint of nation-wide broadcasting, the question becomes as to whether we should aim to cover a large territory through a single powerful station, or through a number of interconnected smaller ones. We must not stifle progress in any direction. We must not do anything that will interfere with the programs of local stations on which many of our people depend, nor with the wide selective range which they now have. It may be that both purposes may be accomplished without loss to either.

Regarding interference:

"One matter that must be dealt with sometime, but over which there is no means of control at present, is the interference from non-radio sources. We listeners have all experienced frequently and to our great disgust the squeals and roars which we are told come from electrical devices of various sorts in which there is no purpose to cause audible disturbance. Some branch of our radio industry certainly should investigate and study them. Harmonics, too, are troublesome."

On sticking to the assigned wave he said:

"It is useless to assign a station to a definite wave length if its signals go out not only on that one but on three or four others. Our amateurs, who make up by far the largest element in the radio family outside of the listeners as a whole, are particular sufferers since the harmonics from many stations have an especial tendency to invade the amateur band. Accurate and sharp transmission must be insisted upon."

Trade Review

New Rotor Control

ONE of the best vernier adjustment controls is marketed by Manufacturers' and Inventors' Electric Co., 29 Gold Street, New York City. It is called the Microtor and it provides refinement of rotor control. It gives infinite adjustment that brings in distance and gives the utmost clarity on local stations. It also has these advantages: Infinitesimal control of any rotor part, universal application to all standard dials up to and including 4", permits usual adjustment of dial by hand, enabling quick setting which is then refined by the Microtor; easy application by any one to all sets using dials.

(Tested and approved by RADIO WORLD)

Tri-Coil Transformer

THE Tri-coil radio-frequency transformer, manufactured by the Brooklyn Metal Stamping Company, 718 Atlantic Ave., Brooklyn, N. Y., is used extensively by great numbers of amateur and commercial set builders who use a straight radio-frequency amplifying circuit. This transformer uses a compensating coil arrangement on the primary which balances the plate circuit in which it is used. It is an effective product.

(Tested and approved by RADIO WORLD)

Uncle Sam Coil

THE Uncle Sam Coil Company of Plainfield, N. J., make a 3-circuit coil used in the popular

(Concluded on next page)

Coming Events

OCT. 14 TO 19, INCLUSIVE—Southwestern Radio & Electrical Exposition, Parkmoor Building, Dallas, Texas. Mailing address, Adolphus Hotel, Dallas.

NOV. 3-8—Third Annual National Radio Exposition, Grand Central Palace, New York City, under auspices of American Radio Exposition Co., 522 Fifth Ave., N. Y. C. Annual National Radio Convention in conjunction with show.

NOV. 11-14—Wisconsin Radio Exposition, Milwaukee.

NOV. 18-23—Chicago Radio Fair.

NOV. 24 TO 30, INCLUSIVE—International Radio Week.

DEC. 1-7—Newark Radio Fair.

DEC. 1 TO 6, INCLUSIVE—Boston Radio Exposition, Mechanics Building, Boston.

Business Opportunities Radio and Electrical

Rates: 40c a line; Minimum, 3 lines.

RADIO FACTORY ORGANIZED \$25,000, needs additional working capital; wants financial backing; consider services office or sales manager record; references; money secured. Box 1, RADIO WORLD.

WILL SELL GOING RADIO MANUFACTURING business, nationally established; very lucrative; \$25,000; wonderful opportunity; reason for selling. BOX 2, RADIO WORLD.

RADIO DISTRIBUTION AGENCY—Valuable exclusive sales rights for high-class sets, Eastern territory; incorporated; literature printed ready to start; price \$2,500. Box 3, RADIO WORLD.

RADIO "B" BATTERY FACTORY and business, well situated for Eastern markets; fully equipped; efficient staff; output contracted for by reputable dealers in key cities of East; outright sale, which will include formulas which have proven their superiority by yearly increased demand for product; reasonable terms can be arranged; a superlative opportunity and one that will stand closest investigation; banking and business references exchanged; quick action essential, as busy season at hand. Box 4, RADIO WORLD.

RADIO PARTS, STAMPINGS, SCREW machine parts, tools and dies manufactured, quantity production. Write or call Kings Manufacturing Co., Bush Terminal, Brooklyn, N. Y.

FOR RENT—RADIO STORE.

Best location in New York, in the centre of the radio market; visited by thousands of radio fans daily; act quickly. Box D. E. F., Radio World.

DELIVERY SERVICE FOR INDIVIDUAL corporation, will supply truck best fitted for clients' needs, under contract. Nolte, 312 West 21st, N. Y. C.

Sales at World's Fair Put at \$3,000,000

IRVING HOFFMAN MADISON SQUARE GARDEN

THE FAIR AFFORDED A FINE OPPORTUNITY FOR MANUFACTURER AND DEALER TO MEET AND DISCUSS THEIR PROBLEMS.

STATIONS WEAF, WJZ, WHN, AND WAHG, BROADCAST THE PROCEEDINGS.

COMMISSIONER MILLS REPRESENTED MAYOR HYLAN.

JAS. F. KERR WAS THE MANAGER OF THE RADIO WORLD'S FAIR.

IT WAS ESTIMATED THAT 150,000 PEOPLE ATTENDED DURING THE SEVEN DAYS.

JUST WITNESS THE PLIGHT OF MR. EMERSON WHITE, HE TRIED TO TAKE HOME ALL HIS CIRCULARS ONE NIGHT.

OF COURSE NO RADIO SHOW WOULD BE COMPLETE WITHOUT THOSE FREAK SETS.

THE actual count of admissions to the first annual Radio World's Fair, held jointly in Madison Square Garden and the 69th Regiment Armory, nearby, places the number at 175,000 for the seven days it lasted. It is estimated 25,000 saw the show twice, hence 150,000 individuals visited it. Calvin Harris, of the show's executive staff, reports:

"Over \$3,000,000 worth of orders were booked by the exhibitors during the first six days of the show. Four companies succeeded in disposing of their entire 1924-1925 output, while three others actually oversold their maximum factory production for the coming year from ten to thirty per cent. Also, 3,600 radio dealers and jobbers from the United States and Canada attended the fair and close to 500 more came from South America, Europe and the Orient. General Manager James F. Kerr and Managing Director U. J. Herrmann have already completed arrangements for the 1925 Radio World's Fair which will be held in the New Garden soon to be erected by John Ringling and Tex Rickard. Although the new building will be twice the size of the present structure, Manager Kerr reports that 80 per cent. of the available exhibiting space already has been contracted for.

5 Neutrodyne Licensees in New Finance Plan

THE Independent Radio Manufacturers, Inc., announced that a number of Neutrodyne patents have adopted a new method for handling the financing of sales on the instalment plan. The arrangement was made with the Com-

mercial Investment Trust, Inc., of New York City. The Commercial Investment Trust makes collections direct. The dealer is required to obtain a minimum down payment equal to one-third the total value of the set and its accessories. This obviates the necessity of demanding cash for tubes and batteries. The Neutrodyne licensees who have already adopted the plan are F. A. D. Andrea, Inc., Freed Eisemann Radio Corp.; Garod Corporation; Wm. J. Murdock Co., and the Workrite Mfg. Company.

TRADE REVIEW

(Concluded from preceding page)

3-circuit regenerative circuit. The aperiodic primary is wound on the same tube as the secondary, and the tickler coil, which is wound on a

**S-U-P-E-R-D-Y-N-E
SPECIALISTS**

Our Own Coils—guaranteed \$6.50
KIT (Fluwelllag Condensers, Coils and Diagram) 19.50
Complete Parts, Assembled with Diagram 65.00
Superdyne Advice Free. Mail Orders Solicited.

WALLACE RADIO COMPANY, Inc.
135 LIBERTY STREET NEW YORK CITY

WANTED

Representatives, jobbers, dealers in every City, County, State and Country (correspondence confidential), to handle our new line of radio receiving sets—The Ultra Synchronyne VII and The Stracyn VIII. Something worth your while. Stanley's Perpetual Radio Bulb Fuse.

THE STANLEY RADIO COMPANY
2947 Lorain Avenue Cleveland, Ohio

ST. MARK'S RADIO CO.

A money order for \$5.95 will bring you a crystal set complete—including "Scientific" headphones, aerial wire, aerial clamp, lead-in wire and neat, substantial cabinet.

All Standard Radio Parts in Stock
Mail Orders Solicited

ST. MARK'S RADIO CO.
29 THIRD AVE. NEW YORK

Bankrupt Stock

Cunningham Regenerative one tube long range sets

\$10.50 each

Prepaid While They Last
Formerly Sold at \$32.50

No Circulars. Order from This Ad.

S. A. TWITCHELL CO.

1930 Western Ave. Minneapolis, Minn.

New! **Metallic
Grid Leak
DURHAM**

ANOTHER important advance in radio—the development of a practical METALLIC high resistance for grid leak and resistance coupling! This is the invention of two professors in chemistry and electricity at a large eastern university.

The new DURHAM Metallic Resistance Unit is a rare metal deposited on glass by means of a complicated process developed after months of scientific research.




Accurate-Permanent-Noiseless
Tested and guaranteed accurate, every DURHAM unit is noiseless and non-inductive. You can depend upon them absolutely. They are the biggest little things in radio.

DURHAM Fixed or Variable Resistance Units (grid leaks) fit standard holders. But you will find the new style base more convenient. Three styles take care of plain mounting, grid leak and condenser mounting and double base for resistance amplifiers.

PRICES:—

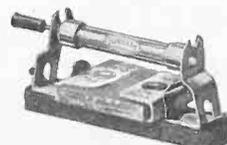Fixed, 28 sizes
50c-75c
Variable 75c
Mounts
30c-40c



**GET THIS
RESISTANCE AMPLIFIER BOOKLET**

Complete details for construction of the most perfect type of amplification. Coupling resistances and grid leaks for detector and two stages cost less than one good transformer. Send 10c for this useful booklet about the "biggest little thing in radio"

DURHAM & CO., Inc.
1930 Market St., Philadelphia,

rotor, is placed at the top of the tube near the end of the secondary. The coil is efficient for both local and DX reception.

(Tested and approved by RADIO WORLD)

**New and Selective
Tuning Unit**

A NEW tuning unit, called the Ever-Ready Tuning Unit, is being marketed by the Ever-Ready Radio Co., of 1861 86th St., Brooklyn, N. Y. The Unit will make a complete set with 3 tubes, sockets and transformers. The engineers who have worked to perfect the Ever-Ready Tuning Unit are among the best known in the country. The Ever-Ready Tuning Unit will bring in long distance stations without interference, while local stations are in operation with much volume.

(Tested and approved by RADIO WORLD)

100 Will Exhibit at Dallas

THE Southwestern Radio & Electrical Exposition, to be held in the Parkmoor Building, Dallas,

WANTED

Factory Distributors. Tremendous profits in distributing newly invented, much needed Radio device. Patented. Sells for only 50 cents retail. Market several million yearly. Big repeats. Nationally advertised. Write at once for new sales plan.

RADIO EQUIPMENT COMPANY
20-W Stuart St. Boston, Mass.

Clear-O-Dyne

Four and Five Tube Sets

No set of an equal number of tubes will do more, yet the price is very moderate.

The Clearstone Radio Co.
Essex Place and McMillan St.
CINCINNATI, OHIO

WE REPAIR

RADIO TUBES

WD-11 .. \$2.50	DV-2 .. \$2.50
WD-12 .. 2.50	DV-5A .. 2.50
UV-200 .. 2.50	UV-199 .. 2.50
UV-201 .. 2.50	C-299 .. 2.50
C-300 .. 2.50	UV-201A .. 2.50
C-301 .. 2.50	C-301A .. 2.50
DV-6 .. 2.50	Marconi .. 2.50
DV-1 .. 2.50	Doorhead .. 2.50
UV202 Transmitter .. \$4.00	
G302 Transmitter .. \$4.00	

Mail orders solicited and promptly attended to.

Dealers and agents write for special discounts.

H. & H. RADIO CO.
P. O. Box 22-B

Clinton-Hill Station Newark, N. J.

PETER J. CONSTANT, Inc.

91 Seventh Ave., New York
Chelsea 0665

Distributors for
Well Known Radio Manufacturers
Standard nationally advertised radio merchandise always on hand for prompt delivery.

**In Constant Service—There is
Constant Satisfaction**

**RICHARDSON
SUPERHETERODYNE KIT**

The Richardson "Self Evident" wiring system makes it possible for a 10-year-old child to build a 9 tube Superheterodyne.

And other Products of Merit

**fits Grid Leak
any mounting**

FRESHMAN PLUNGER

TYPE VARIABLE GRID LEAK
was designed especially for the non-technical set owner who can replace in an instant the fixed grid leak with this new, efficient cartridge type Variable Grid Leak: without requiring the change of a single wire.

At your dealer
or by mail post-
paid. Write for
free catalogue.



65c
106-7th Ave.
New York

Texas, October 14 to 19, inclusive, under the direction of the Southwestern Radio Jobber's Association, will have approximately a hundred exhibitors, many of whom have already reserved their space, representing every type of radio receiving set, as well as the various accessories and batteries that are now on the market.

NEW TUBES

Exchanged or Repaired

FOR OLD

\$2.25

Send any type or make of tube in any condition 199, 201A, 12, 200.....

We will replace your old Burnt-out or Bad Tube with another of similar type and guarantee it to function as well as any Standard Tube made.

Our Tubes are made in all types—201A, 200, WD 12, WD 11, 199, etc. Any tube that does not oscillate and amplitly will be replaced Free of Charge if Filament is not burned out.

CRESCENT SALES CO.

985 Third Avenue New York, N. Y.
Mail Orders Promptly Filled.

**HARP
TUBES
\$1.00**



REGULAR PRICE

\$3.75

6 V., 1/4 Amp. Det.

Royal Mfg. Co.

206 BROADWAY
cor. Fulton St., N. Y.

The New Type 54

**Sleeper
MONOTROL**

Reg. U. S. Pat. Off.

Grimes Inverse Duplex System

The only set that has 3 stages of tuned radio frequency on one tuning dial.

23 other important improvements.

Write for booklet "W." It's FREE.

SLEEPER RADIO CORPORATION
434 Washington Street Long Island City, N. Y.

S. HAMMER RADIO CO.
303 Atkins Ave., Brooklyn, N. Y.

SPECIAL!!

**5 TUBE NEW COCKADAY
4 CIRCUIT TUNER with
Resistance Coupled Amplifier KIT**

FREE GENUINE BAKELITE PANEL
Drilled and engraved, worth \$8.00, with all orders for this Kit received up to January 1st, 1925.

PARTS In this Kit are exactly as specified and recommended by Mr. Cockaday in the October issue of Popular Radio, also featured in our new catalog.

WIRED This set wired complete in **\$85.00**
genuine mahogany cabinet...

We specialize in Cockaday Kits

WRITE FOR OUR NEW CATALOG
containing 28 pages, unexcelled bargains in standard nationally advertised radio accessories, parts, sets, kits.

Orders over \$5.00 will be shipped prepaid. Money orders or C. O. D. Not insured unless insurance charges included. Write for Price List.

ANY "DYNE" YOU WANT

The Dynoflex, one stage of tuned RF, crystal detector and one stage of reflexed AF, Aug. 9 issue.

The Magnadyne, a Low-Loss Neutrodyne. Issues of Aug. 16 and 23.

A Low-Loss Superdyne, 5 tubes, including 3 stages of resistance-coupled AF. Issues of Aug. 23 and 30.

Literature Wanted

THE names of readers of RADIO WORLD who desire literature from radio jobbers and dealers, are published in RADIO WORLD, on request of the reader. The blank below may be used, or a post card or letter will do instead.

Service Editor,
Radio World,
1493 Broadway, New York City.
I desire to receive radio literature.

Name

City or town

State

- Alfred Frank, 1565 Ellis St., San Francisco.
- Ralph Mellon, Pottstown, Pa.
- Ed. L. Campbell, RFD 1, Waterbury, Conn.
- Harry E. Newton, 504 E. 7th Ave., Tarentum, Pa.
- Twin City Cycle Shop, Lewiston, Me. (Dealer.)
- J. P. Lamb, Jonesboro, Ark.
- Jas. H. Openshaw, 628 E. 10 1/2 St., Houston, Tex.
- Harold E. Miller, 108 W. 141st St., Apt. 34, N. Y. C.
- Earl A. Jackson, 4811 Forestville Ave., Chicago.
- William Johnson, 705 Virginia St., Gary, Ind.

- Wilco Products Co., 1011 Kimball Bldg., Chicago. (Dealer.)
- Will E. Johnson, 301 Minor Bldg., Kansas City, Mo.
- E. L. Strebe, Tonawanda, N. Y.
- Edmund Gardner, 6751 S. Pauling St., Chicago.
- L. F. Brunl, 159 Waverley St., Palo Alto, Cal.
- Maurice Stone, Box 15, West Bend, Ia.
- A. E. Bailey, Geneva, O.
- J. E. Hartnett, Pomeroy, Wash. (Dealer.)
- E. M. Zabel, Creosote, Wash.
- Henry V. Zarak, Maynard, Mass.
- Geo. M. Crampton, 192d St., W. Riverside, Spokane, Wash.
- Chas. McDermott, 527 So. Olden Ave., Trenton, N. J.
- Wm. H. Rumpf, 719 Miner St., Ann Arbor, Mich.
- Wm. H. Figg, 320 Governor St., Paterson, N. J.
- John W. Murray, 80 Webster Ave., Jersey City, N. J.
- Herbert J. Scott, 611 Columbus Ave., N. Y. C.
- H. S. Meily, Jr., 211 Hill St., Huntington Park, Cal.
- W. M. Near, Shelby, Mich.
- P. W. Motola, 9845 Corona Ave., Corona, N. Y.
- O. E. Freeman, 162 Brownwood Ave., Atlanta, Ga.
- W. Roland Grover, 261 Aldrich Rd., Portsmouth, N. H.
- Geo. H. Laing, Saginaw, Mich.
- Arthur O. Carlson, Portland, N. D.

B. J. Spotts, Jr., 1534 Race St., Philadelphia.
J. A. Burton, Union Bridge, Md.
A. E. Dickinson, 14 Newport St., Dorchester, Mass.

The Standard of the World



The base-type Freshman Variable Grid Leak

is the standard for those who build their own sets. It is the most compact and being entirely sealed it always remains unaffected by any climatic conditions. Complete with either .00025 or .0005 Freshman Condenser—\$1.00 without condenser75

At your dealer's, otherwise send purchase price and you will be supplied postpaid

Chas. Freshman Company, Inc.
106-7th Ave., New York

Burnt-Out Tubes Replaced for \$2.50



A Wonderful Tube for Your Superdyme.

GUARANTEE

Burnt-out, Defective or Broken Tubes of any brand or make whatsoever will be replaced by a brand new (not refilled) Royaltron Tube, at a cost of only \$2.50.

It is with the Object of Advertising the MERITS of ROYALTRON Tubes, that we make the above unusual offer.

- ROYALTRON TUBES
- Royaltron Tubes TYPES
- 100 (.66 Amp.)
 - W12 (1/2 Amp.)
 - 208 (1/2 Amp.)
 - 200A (1/2 Amp.)

Every ROYALTRON Tube is accompanied by the above money-back guarantee.


Approved by the Radio News and World Laboratories

ROYAL MANUFACTURING CO.
Department W. O.

206 BROADWAY NEW YORK
Dealers, distributors and agents, write or wire immediately for unusual proposition.

Complete Building Parts for 5-Tube NEUTRODYNE Set, Only

\$39.49

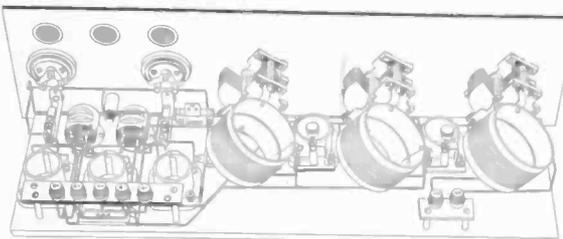

Build Your Own Low-Loss 5 TUBE NEUTRODYNE At Half The Price

You know that the expensive part about building a receiving set is the wiring and assembling. The labor charges of radio builders run into big money. You can save all this, and get the same volume, tone, and distance as a factory set you would pay \$100 to \$150 for. You get all the screws, wires, parts, drilled panels, sockets and a chart and directions to wire and assemble the set. So simple you can't go wrong.

In this knocked-down, 5-tube, Coast-to-Coast, De Luxe Neutrodyne outfit, you get genuine licensed Hazeltine parts; synchronized and matched. Gather in broadcasts from coast to coast. Loud, clear, powerful. Delicate tuning. The superlative realization of months of preparation with new low-loss parts.

You don't need to send a penny in advance to get this outfit. Just put your name and address on the coupon and mail it. Then when the outfit arrives merely pay your postman only \$39.49 plus carrying charges. If you are not entirely delighted with it return the outfit as sent to you and your money cheerfully refunded. THE RADIO SHACK, 55 Vesey Street, Dept. K152, New York, N. Y.

\$39.49

WHAT THE SET CONSISTS OF

- 1 Drilled Mahogany Panel, polished mahogany effect, engraved in gold.
- 3 Four-inch Mahogany Dials, gold engraved. Gold Plated Jacks.
- 3 Genuine Hazeltine Neuroformers mounted on the famous Brunswick Low Loss Condenser, Positively the only Neutrodyne Kit including them.
- 2 Hazeltine Neurodons.
- 5 Heavy Bakelite Sockets.
- 1 6-Ohm Rheostat with gold plated knob to match panel.
- 1 30-Ohm Rheostat with gold plated knob to match panel.

- 2 Genuine Hegehog, Completely Shielded, Audio Transformers.
 - 1 Baseboard.
 - 20 Feet Tinned Bus-bar.
 - 1 .00025 Freshman Grid Condenser.
 - 1 Tubular Glass Grid Leak.
 - 1 Set Engraved Binding Posts.
 - 1 .002 Micon Condenser.
 - 1 .006 Micon Condenser.
- Exact size special panel—base, blue print and instructions.

BUILDING KIT COMPLETE

\$39.49 C.O.D.

OPERATING OUTFIT

- 5 Tested Tubes (Type 201A) \$17.25
- 2 45-volt Extra Large Variable "B" Batteries for Neutrodyne 6.50
- 1 60-Ampere Hour Storage Battery, guaranteed 2 years 11.25
- 1 pr. 3000-Ohm Head Phones and Cord 3.75
- 1 Phone Plug, double90
- 1 Antenna Equipment 1.50

COMPLETE OPERATING OUTFIT

\$41.15 C.O.D.

(Parts Also Sold Separately)

Mail This Coupon Now—Send No Money

RADIO SHACK—Dept. K152,
55 Vesey St., New York, N. Y.

Please send me the Neutrodyne outfit I have marked, when it arrives I will pay postman the amount. If I am not satisfied I will return it in 5 days, as sent to me, and you agree to refund my money instantly. Mark in square outfit wanted.

(A) Complete Building Kit, \$39.49

(B) Operating Outfit - - - \$41.15

Name

Address

City

State

FREE FINE MAHOGANY FINISH CABINET

If you order Building Kit and Operating Outfit both together, we will include Fine Mahogany Finish CABINET FREE.

\$3.75

SPECIAL

On August 13, 1924, the United States Patent Office issued patents for the protection and manufacture of the world's greatest storage "B" battery. The new battery gives an extra long service and lasts much over five years—gives good, clear and loud reception and sets distance very well.

A New Kind of Plate

The battery is absolutely noiseless and gives over 8,000 milli ampere hours of service per charge. The new plate is graphite treated, size 2 1/2 x 1 1/2 inches, and can be recharged in a few hours from any charger lamp socket or farm outfit. Five batteries cost only five cents per charge.

Container is Genuine Hard Rubber

The new battery is built in a one piece, unbreakable, neat hard rubber container as illustrated, with vent caps large enough for hydrometer readings. Each battery is called a unit of 22 1/2 volts. Add units for higher voltage.

Most for Your Money

This is the largest size battery for your money. Built under patents, thus you get the very best. The battery can be bought assembled or knockdown. Units come with full directions printed very clear. Units can be assembled by any one in a few minutes' time. Don't waste more money on dry batteries—send today for the new patented battery. A set of them will last indefinitely.

Price Assembled \$4.50
Knock down 3.75
A-C Rectifier75

SIDBENEL RADIO MFG. CO.
Licensed Manufacturers
89 WEST MT. EDEY AVE., NEW YORK CITY
BIG CATALOG ON REQUEST

A. B. C. Editor, RADIO WORLD,
1493 Broadway, New York City.
Please enroll me as a member of
the American Broadcast Club.
Name
Address
City or Town.....
State

Join the A. B. C. NOW

THE American Broadcast Club, formed under the auspices of RADIO WORLD, has for its object the promotion of the welfare of the broadcast listeners of the United States, Canada and Mexico. Membership is open to all interested in radio in any way, either as broadcast listener, dealer, manufacturer, wholesaler or jobber.

A novel feature of the A. B. C. is that membership entails no duties or obligations whatever. There are no dues. All you have to do is enroll. That will signify your interest in radio and make you one of the thousands unselfishly united in a common interest.

NEW MEMBERS

- F. E. Mattson, Oak Grove Hotel, Minneapolis, Minn.
- Frank Holetsky, R4, c/o Searight, Uniontown, Pa.
- John F. Shea, dealer, 3330 Hickory St., St. Louis.
- W. L. Deremiah, 4514 A Enright Ave., St. Louis.
- H. A. Sparks, 156 Day Ave., Toronto, Ont.
- Eugene Morsan, 74 des Prairies, Quebec, Can.
- Charles W. Anderson, 2136 Stansbury St., St. Louis.
- Joseph Giaquinto, 117 Madison Ave., Paterson, N. J.
- A. C. Peed, dealer, Mt. Sterling, Ky.
- F. C. Arnold, 104 No. West St., Waukegan, Ill.
- Alfred Frank, 1365 Ellis St., San Francisco.
- Alfred E. Ritter, 250 Crocus Ave., Floral Park, N. Y.
- P. W. Moteola, 9845 Carona Ave., Carona, N. Y.
- Ernest Knight, 1802 Dean St., Brooklyn, N. Y.
- S. J. Fedor, 1229 E. 62d St., Los Angeles, Cal.
- James Englander, 16 W. 8th St., N. Y. C.
- Alton Bailey, 20 Prospect St., Geneva, Ohio.
- Chas. McDermott, 527 So. Olden Ave., Trenton, N. J.
- Roland Hinckley, 133 Court St., Portsmouth, N. H.
- Wm. H. Rumpf, 719 Minder St., Ann Arbor, Mich.



Jiffy Blow Torch

**Good Soldering—
Good Reception!**

You know how essential good soldering is to the working of your set. A "Jiffy" Blow Torch will give you a real professional job. Self-blowing—absolutely safe! "Jiffy" complete outfit, Copper Soldering Iron, String Solder, "Jiffy" Non-corrosive Flux and "Jiffy" Blow Torch with accessories, **\$2.50.**

At your dealer's or direct

Apex Stamping Company
Dept. 18 Riverdale, Ill.

Dealers! Write for proposition

SWEEPING THE COUNTRY—Superdyma Circuit in RADIO WORLD July 5, August 23 and 30. Send 45c or start your subscription with any number.

FALL BUYERS' NUMBER OF RADIO WORLD dated September 27 sent on receipt of 15c.

TOWER'S

TOWER'S Scientific

WEIGHS ONLY 8OZ

Perfect Tone Makes

\$2.95

Plus a few cents postage

Buy a Headset you'll be proud of

OUR \$200,000.00 COMPANY STANDS SQUARELY BACK OF EVERY HEADSET

now \$2.95, with Notable Improvements

Longer Cord (full 5 feet), Stronger Magnets, Higher Resistance, Increase of Sensitivity, Perfect Tone Mates

EVERY SET TESTED BY LICENSED RADIO OPERATORS

Send no money - Order on a Post-Card

THE TOWER MFG. CO. Dept. D-98 BROOKLINE AVENUE, BOSTON, MASS.

Scientific

Eskimo Children in Alaska Stay Up to Hear Oakland

WHEN an interesting KGO radio program is being received in their home, Eskimo children are just as hard to keep in bed as any other children.

Discovering this in an orphanage for Es-

kimo children at Teller, Alaska, the matron has reported to KGO, Oakland, Cal., that during a recent broadcast of KGO she found "several of the girls out of bed with their ears to the floor just above the loud speaker, enjoying the program."

New Installations Are for 500 Watts

MOST of the new installations being made are the latest 500-watt Western Electric set. There are now ten of these sets in operation and fifty of the old-type 500-watt sets. The new equipment consists of four 250-watt vacuum tubes and one 50-watt tube. The tubes are mounted in the upper part of the framework of the transmitter, to provide adequate ventilation. The current for heating the filaments is supplied from a constant potential generator. The filament current is adjusted and held constant by means of a rheostat.

The radio transmitter is essentially an oscillation generator with means for modulating or molding its output in accordance with current variations produced by a microphone which is operated by the speech or music. The oscillator comprises a tuned circuit coupled to the antenna system. This tuned circuit determines the frequency and wavelength of the radiated energy.


MAHOGANITE and BLACK RADION PANELS

DIALS, KNOBS, TUBING, SOCKETS MAHOGANITE BINDING POSTS

"THAT SPECIAL SIZE" FOR YOUR PHONOGRAPH, PORTABLE OR SUPER

ALL STOCK SIZES
WHOLESALE RETAIL
Send for Complete Price List
New York Hard Rubber Turning Co.
212 Centre Street New York City

"ROLLS ROYCE" RADIO TUBES

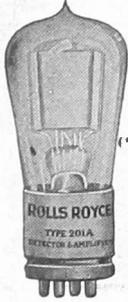

Like their name, significant of quality, durable and powerful. Bring in distance with a maximum of volume and clearness.
Type 200—5 volts, 1 ampere Detector Tube
Type 201A—5 volts, .25 ampere Amplifier and Detector
Type 199—3-4 volts, .08 ampere Amplifier and Detector
Type 198—3-4 volts, .04 ampere With Standard Base—Amplifier and Detector
Type 12—1 1/2 volts, .25 ampere Platinum Filament—Amplifier and Detector

ALL TYPES of Radio Tubes \$2.50

Type 202 Five (5) Watt Transmitter.....\$8.00
EVERY TUBE GUARANTEED to work in Radio Frequency. Especially adapted for Neutrodyne, Reflex and Super Neutrodyne Sets. Shipped Parcel Post U. S. D. When ordering mention type.
Rolls Royce Tube Co.
21 Norwood Street Dept. W Newark, N. J.

Record Your Radio Stations On RADEX Log Cards to Match Your Set

Copyright 1924 by S. T. Aston & Son
Telephone Franklin 2189

\$3.00
Complete Postpaid

100 Cards, Mahogany Finish or Oak Cabinet, and Index Dividers. A Useful Accessory to Any Set. Give Name of Set or Sketch of Dial Arrangement. Postpaid on Receipt of Cash or Money Order. Dealers Write for Terms.
S. T. ASTON & SON
114 WORTH STREET NEW YORK CITY

PATENT
Four Ideas. Good on a sketch or simple model of your invention. **FREE** advice. **FREE** booklet. Write for **FREE** BOOKLET
MANUFACTURERS PATENT CO., INC.
79 WALL STREET, NEW YORK

The "Goode" Two-o-One



Le Ton d'argent



BY MAIL ONLY
\$2.39
Postpaid

QUARTER AMPERE AMPLIFIER-DETECTOR RADIO TUBE

GUARANTEED SATISFACTORY

All "GOODE" Tubes Sold Direct to the Consumer—No Dealer Profits.

ONE—"Goode" Detector-Amplifier. **\$2.39**
THREE—"Goode" Detector-Amplifiers **\$6.42**


(All Postage Prepaid)

The "Goode" Two-o-One A Tube amplifies or detects. It is a quarter ampere, six volts, standard base silvered tube.

Send express or postal money order or New York draft to—

The Goode Tube Corporation
Incorporated
EVANSVILLE INDIANA

Ward's Radio Catalogue

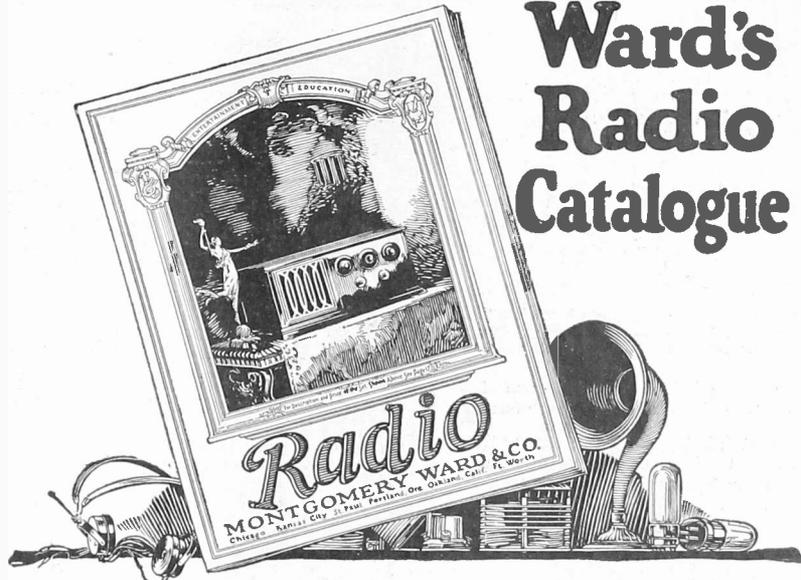

Write for your FREE copy

We want you to have a copy of Ward's new Radio Catalogue.

You will find it a storehouse of information—a dependable guide to the newest and most important radio developments.

It shows all improved parts and diagrams of the best hook-ups for the man or boy to build his own set, as well as the very best ready-built sets at surprisingly low prices.

Montgomery Ward & Co. are Headquarters for *everything* in Radio. And this Catalogue

shows complete—everything in Radio equipment. Remember we sell only standard goods—direct to you by mail, and without the usual Radio profits.

For 52 years, "Satisfaction guaranteed or your money back," has stood behind every Ward sale. At Ward's, quality is never sacrificed to make a low price.

Write for your copy of this 68-page Radio Catalogue. See for yourself the low prices. You may as well profit by the savings it offers. Address our house nearest you: Dept. 42-R

ESTABLISHED 1872 Montgomery Ward & Co.

The Oldest Mail Order House is Today the Most Progressive

Chicago Kansas City St. Paul Portland, Ore. Oakland, Calif. Ft. Worth

Programs

Saturday, October 11, Continued from page 19

WEEL, Boston, 246m—Silent Night.
KFNF, Shenandoah, Ia., 266m—7:30 P. M., program by John G. Woodard Candy Co., Council Bluffs. 10:30 P. M., seedhouse frolic
KFI, Los Angeles, 469m—2:00 P. M., Los Angeles Grand Opera Company, "Amico Fritz," with Tito Schipa, Thalia Sabanieva and Giuseppe de Luca, and "Gianni Schicchi" with Giuseppe de Luca, Myrtle Donnelly and Jose Mejica. 5:00-5:30 P. M., news bulletins. 5:30-6:00 P. M., news bulletins. 6:45-8:00 P. M., dance orch. and Basil Webb lecture on India. 8:00-9:00 P. M., Raymond Instrumental Trio. 9:00-10:00 P. M., program

THOUSANDS OF BARGAINS
FACTORY GUARANTEED MDS. BY MAIL
 Genuine New Radiotron or Cunningham Tubes
 UV-199—200—201A—WD-11—12..... **\$3.39**
 C299—300—301A—C11—12.....
 Fresh Burgess or Eveready "B" Batteries
 22 1/2 Volt large size \$1.68—45 Volt \$5.00 size \$3.33
 Write for Free new Complete Catalog on Sets and Parts.
STONE ELECTRIC CO., 714 Pine St., St. Louis, Mo.
 All Mds. F.O.B. St. Louis, Mo. Dept. W

Baldwin Phones Free
 For best long distance record on my hook-up. Other prizes too. Particulars free.
LEON LAMBERT
 562-K Kaufman Bldg. Wichita, Kansas



Write Today For Descriptive Folder of the

NEW HOWARD 5-TUBE NEUTRODYNE

This Remarkable Set has Created a Sensation Among Radio Enthusiasts.

Beautiful Walnut Cabinet with Special Howard Neuroformers, Tube Sockets and Rheostats.

Licensed by Independent Radio Manufacturers, Inc. Reg. U.S. Pat. Off.
NEUTRODYNE
 Pat. March 27, 1923 and April 1, 1924
 Machine Nos. 1450, 080 and 149, 226
 Other Patents Pending

HOWARD MFG. COMPANY
 4248 No. Western Ave. Chicago, Ill.

from Examiner Studio. 10:00-11:00 P. M., Packard Radio Club. 11:00-12:00 P. M., Ambassador Hotel Cocoanut Grove Orchestra.
WRC, Washington, D. C., 469m—5:15 P. M., code instruction. 6:00 P. M., children's hour by Peggy Albion. 8:00 P. M., song recital by Fany Shreve Heartsill, soprano. 8:15 P. M., to be announced. 8:30 P. M., Francis P. Heartsill, bass. 8:45 P. M., to be announced. 9:35 P. M., time signals.

Sunday, October 12

WLAC, Minneapolis, 417m—8 P. M., Mrs. Mel-accompanist; Elsie Wolf, piano; Marion Bernstein violin A. Campbell, contralto; Eleanor Freemantel, Bearman, violin. 9 P. M., weather.
WBAP, Fort Worth, Tex., 476m—11 A. M., church services. 4 P. M., concert from Rialto Theatre. 11-12 P. M., concert.
WQJ, Chicago, 448m—10:30 A. M., Dr. Preston Bradley's sermon and services People's Church. 8-10 P. M., Williams orchestra in concert; Iandon Bros., guitar; Lancaster Smith, basso; Mrs. Lancaster Smith, accompanist; The Premier quartet; James Whalen, tenor.
WHO, Des Moines, Ia., 526m—7:30-9 P. M., music. The Bankers Life radio orchestra, W. L. Marsh, dir.; Kathryn Fletcher, Helen Birmingham, Mrs. La Vere Brauchet, Gladys McMahon.
WDAF, Kansas City, Mo., 411m—Baseball scores at 3:30, 4, 4:30 and 5 P. M. 4-5 P. M., music.
KGO, Oakland, Cal., 312m—11 A. M., service First Baptist Church. 3:30 P. M., Little Symphony orchestra. 7:30 P. M., service of First Baptist Church.
WHAS, Louisville, Ky., 400m—9:57 A. M., organ. 10 A. M., church service, Broadway Baptist Church; H. U. Goodwin, organist; Mrs. O. W. Edinger, Miss Angeline McCrocklin, Charles H. Barnes, Jr., William Cornwall. 4-5 P. M., Vesper song service.
KPO, San Francisco, 423m—11 A. M. to 12 Noon, undenominational and non-sectarian church services; Dr. William P. Bentley, pastor First Christian Church; Wm. Edward Johnson, soloist; organ by Theo. J. Irwin. 8:30-10 P. M., concert by Seiger's orchestra.
KFI, Los Angeles, 469m—10:45 A. M., L. A. Church Federation service. 6:45-7 P. M., Paul Reese musical talks. 7-8 P. M., Metropolitan Theatre program. 8-9 P. M., Ambassador Hotel concert orchestra. 9-10 P. M., program, studio. 10-11 P. M., Packard Six orchestra.
WIP, Philadelphia, 509m—7:30 P. M., Holy Trinity Church service. 9:30 P. M., concert by Ben


Stad symphony orchestra; Karl Bonawitz, organ.
WGY, Schenectady, N. Y., 380m—10:45 A. M., service First Methodist Church, Schenectady, N. Y., sermon by the Rev. Dr. Philip L. Frick. 7:30 P. M., service of the First Methodist Church, Schenectady.
KFNF, Shenandoah, Ia., 266m—3:00 P. M., sacred concert. 6:30 P. M., song service.
WWJ, Detroit, 517m—11:00 A. M., services at St. Paul's Episcopal Cathedral, broadcast from the cathedral. 2:00 P. M., Detroit News Orchestra.
KGW, Portland, Ore., 492m—6:00 P. M., church services, by Portland Council of Churches.
WEEL, Boston, 246m—4:00 P. M., organ recital; Boston Chamber of Commerce; musicale. 7:30 P. M., Mark Strand Theatre program, New York City.
WOAW, Omaha, Neb., 526m—9:00 A. M., radio chapel service by Rev. R. R. Brown. 9:00 P. M.,



Little Wonder!!!
SOLDERLESS LUG
 Holds Bus Wire Like Oil!
 Connect or Disconnect Wires
 Without Disturbing Terminal!
 Price 10 for 5c. Ask your dealer.
 Distributors Wanted
 Mfd. by PAUL GLAMZON
 203 Lafayette Street New York



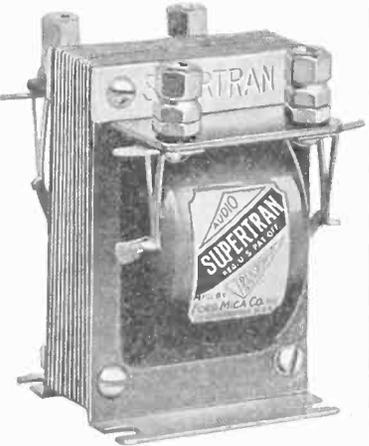Supertran
 Registered U. S. Patent Office
SHIELDED!
 The Ideal Audio for Neutrodyne



Every Neutrodyne Receiver requires audio transformers which are especially built for this circuit. Build right by selecting SUPERTRAN'S first! Greatest volume. Least distortion.

The Supertran is shielded to prevent damage to the coil in mounting.

Price \$6.00

At your dealers or by mail postpaid on receipt of purchase price. Write for our free literature.

Distributed by
WETHORE-SAVAGE CO., Boston
THE BECKLEY-RALSTON CO., Chicago
COAST RADIO SUPPLIES CO., San Francisco
RADIO, LIMITED, Montreal
EXCEL-ALL RADIO CO., Bloomfield, N. J.

Manufactured by
Ford Mica Company
 33 East 8th Street New York



World Battery
 Saves You 50%

Famous Guaranteed Quality and Service—Backed by Years of Successful Manufacture and Thousands of Satisfied Users.

Prices That Save and Satisfy

Auto Batteries	Radio Batteries
6-Volt 11 Plate, \$12.25	6-Volt 60 Amps. \$ 8.50
6-Volt 13 Plate, 14.25	6-Volt 100 Amps. 12.50
12-Volt 7 Plate, 17.00	6-Volt 120 Amps. 14.50
	6-Volt 140 Amps. 16.00

Special 2-Volt Storage Battery for W.D.11 and 12 tubes. Will run 200 hours on one charge. Rechargeable. **\$5.00.**
 Special 4-Volt Storage Battery for U.V.199 tubes. Same features as 2 Volt. **\$8.00.**
 Shipment express C.O.D. subject to examination. 6% Discount for cash in full with order.

2-Yr. Guarantee Bond in Writing With Each World Storage Battery
 proves satisfactory World performance. Mail this ad with your name and address and we will ship battery day order is received; and give you a 45-Volt "B" Battery and Hydrometer Free with each battery purchased. Write today.

World Battery Company
 Dept. 17, 321 S. Wash St. CHICAGO, ILL.

FREE
 45 V. B-BATTERY and HYDROMETER

STATEMENT OF THE OWNERSHIP, MANAGEMENT, CIRCULATION, ETC., REQUIRED BY THE ACT OF CONGRESS OF AUGUST 24, 1912.

Of Radio World, published weekly at New York, N. Y., for October 1, 1924.

State of New York, County of New York, ss:

Before me, a Notary Public, in and for the State and County aforesaid, personally appeared Roland Burke Hennessy, who, having been duly sworn according to law, deposes and says that he is the Editor of the Radio World, and that the following is, to the best of his knowledge and belief a true statement of the ownership, management (and if a daily paper, the circulation), etc., of the aforesaid publication for the date shown in the above caption, required by the Act of August 24, 1912, embodied in section 443, Postal Laws and Regulations, printed on the reverse of this form, to wit:

1. That the names and addresses of the publisher, editor managing editor, and business managers are: Publisher, Hennessy Radio Publications Corporation, 1493 Broadway, N. Y. C.; editor, Roland Burke Hennessy, 1493 Broadway, N. Y. C.; managing editor, Herman Bernard,

1493 Broadway, N. Y. C.; business manager, Fred S. Clark, 1493 Broadway, N. Y. C.

2. That the owners are: (Give names and addresses of individual owners, or, if a corporation, give its name and the names and addresses of stockholders owning or holding 1 per cent. or more of the total amount of stock): Hennessy Radio Publications Corp., 1493 Broadway, N. Y. C.; Roland Burke Hennessy, 1493 Broadway, N. Y. C.; Mrs. Mary McArthur, Statler Hotel, Cleveland, Ohio.

3. That the known bondholders, mortgagees, and other security holders owning or holding 1 per cent. or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.) None.

4. That the two paragraphs next above, giving the names of the owners, stockholders, and security holders, if any, contain not only the list of stockholders and security holders as they appear on the books of the company but also, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, is given; also that the said two paragraphs contain statements embracing affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear on the books of the com-

pany as trustees, hold stock and securities in a capacity other than that of a bona fide owner; and this affiant has no reason to believe that any other person, association, or corporation has any interest, direct or indirect in the said stock, bond or other securities than as so stated by him.

5. That the average number of copies of each issue of this publication sold or distributed, through the mails or otherwise, to paid subscribers during the six months preceding the date shown in the caption of this form, is weekly. (This information is required from daily publications only.)

ROLAND B. HENNESSY, Editor.

(Sworn to and subscribed before me this 26th day of September, 1924.

KARL E. GOTTFRED, Notary Public, New York County, New York County Clerk's No. 180, New York Co., Register's No. 6165, Term expires March 30, 1926.

Note.—This statement must be made in duplicate and both copies delivered by the publisher to the postmaster, who shall send one copy to the Third Assistant Postmaster General (Division of Classification), Washington, D. C., and retain the other in the files of the post office. The publisher must publish a copy of this statement in the second issue printed next after its filing.

Programs, Continued

musical chapel service, North Presbyterian Church; Rev. James M. Hamilton, pastor; Hugh E. Wallace, choir director; Mrs. Deyo Crane, organist.

WCBD, Zion, Ill., 345m-8:00 P. M., vocal and instrumental sacred music, Glen R. Sparrow, Paul Stewart, Gerald Mason, Wm. C. Dunn, Daniel Mascor.



RADIO EXPERTS EARN BIG MONEY

Thousands of big pay opportunities open to the radio trained man. Success easily won in the fastest growing industry of all time. From land and sea comes the urgent call for men who can construct, install, operate, repair, maintain and sell radio equipment.

CASH for Your Spare Time!

Take orders from your neighbors for radio sets. Get big fees for your services and advice. Home study qualifies you in short course, low cost, easy terms, money back guarantee.

Wonderful tube receiving set of latest design. Range over 1000 miles. Write today for FREE copy of "Radio Facts".

A. C. MOHAUFY, Radio Engineer
RADIO ASSOCIATION OF AMERICA
4513 Ravenswood Ave., Dept. 918, Chicago

Monday, October 13

WFAA, Dallas, Tex., 476m-10:30 A. M., weather report and forecast; highway condition bulletin; produce market report and Wall Street review. 12:30 P. M., Dr. Ellis W. Shuler, Southern Methodist University, on "Texas History in the Rocks." 2:30-3 P. M., Dallas livestock market, late general markets, sports, news. 3:30-4, 4:30-5 P. M., Agriograms, health bulletins, Texas market news, sports, news. 5:30-6 P. M., bedtime story and fairy tale by Mary C. Toomey. 8:30-9:30 P. M., Mozart Choral Club, Earle D. Behrends directing. 6:45-7 P. M., sport news and information bulletins. 9:30 P. M., weather report and forecast.

The above is substantially every-day program for WFAA. Only night programs are published for remaining dates of week.

WQJ, Chicago, 448m-11 A. M.-12 Noon, Earle Hart Miller, "Furnishing the Small House or Apartment"; Agnes May Allen, "Your Favorite Restaurant Recipes"; Marcia Meadows, "Furnishing the Living Room." 3-4 P. M., Helen Harrington Downing, "Three Meals a Day"; silent night for Chicago.

KPO, San Francisco, 423m-12 Noon, time; scripture. 1-2 P. M., Seiger's orchestra. 4:30-5:30 P. M., Seiger's orchestra. 5:30-6:30 P. M., children's hour. 7-7:30 P. M., Seiger's orchestra. 8-9 P. M., organ, Theodore J. Irwin. 9-10 P. M., contralto, Mrs. Mark T. H. Shwayder; piano, A. M. G. Vermaas; tenor, Gwynn Jones; book review, George Douglas. 10-11 P. M., Bradford's band.

WHO, Des Moines, Ia., 526m-Sciota McAdow Herndon, soprano; Charlotte Van Ginkle Dye, acc.; D. H. Welis, tenor; Jennie Hines, acc.; Scotch Kiltie band; also artists from the Drake Conservatory, direction Dean Holmes Cowper. 11:15-12 Noon, organ, by L. Carlos Meier.

WDAF, Kansas City, Mo., 411m-baseball scores at 3:30, 4, 4:30 and 5 P. M. 3:30-4:30 P. M., trio. 5-5:30 P. M., Boy Scout program. 5:50-6 P. M., marketgram, weather, time. 6-7 P. M. (School of the Air), piano tuning in number; The Tell-Me-a-Story Lady; Fritz Hamein's Trianon Ensemble. 8-10 P. M., minstrels and orchestra. 11:45 P. M.-1 A. M. (Nighthawk Frolic), The "Merry Old Chief" and the Plantation Players.

WGY, Schenectady, N. Y., 380m-Earl Rice, piano; Isabelle Franklin, soprano; Frederick A. Clinkick, cornet; Walter Reagles, tenor.

WHAS, Louisville, Ky., 400m-4-5 P. M., selections by the Alamo Theatre orchestra; police bulletins; weather; humor; readings; news. 4:55 P. M., livestock, produce and grain market re-

ports. 5 P. M., time. 7:30-9 P. M., WHAS is silent on Monday nights.

KFI, Los Angeles, 469m-5-5:30 P. M., news. 5:30-6 P. M., news. 8-11 P. M., Los Angeles Grand Opera, "Traviata," with Claudia Muzio, Jose Mojica, Giuseppe de Luca.

KGO, Oakland, Cal., 312m-1-30 P. M., N. Y. and S. F. stock reports and weather. 3 P. M.,

(Continued on next page)



12 Cells
24 Volts
Solid Rubber
Case

\$4.00 C.O.D. SPECIAL INTRODUCTORY PRICE

For a limited time only, and to introduce this new and superior Storage "B" Radio Battery to the Public, we are selling it for \$4.00. Regular Retail Price is \$6.00. You save \$2.00 by ordering NOW. A finer battery cannot be built than the World Storage "B" Battery

(12 CELLS-24 VOLTS)
To ten million homes with Radio Sets—and to countless millions of prospective buyers—this WORLD Storage "B" Battery brings a new era of battery economy and performance. Here is a battery that pays for itself in a few weeks—will last for years and can be recharged at a negligible cost. And you save \$2.00 by ordering now.

A Superior Battery Equipped With Heavy Duty Solid Rubber Case
Has heavy duty 2-1/8 in. x 1 1/2 in. x 1-1/4 in. plates and plenty of acid circulation. Extra heavy glass jars allow ready observation of charge and prevent leakage and seepage of current. It holds its charge, while idle, at constant voltage. You will find this battery a boon to long distance reception. If, due away with a great many noises so often blamed on "static," still your order today.

SEND NO MONEY
Just state number of batteries wanted and we will ship day order is received. EXTRA OFFER: 4 batteries 2 series (24 volts), \$16.00. Pay Expressman after receiving battery. 6 per cent discount for cash in full with order. Send your order NOW and save \$2.00.

WORLD BATTERY COMPANY
Makers of the famous World Radio "A" Storage Battery
1219 S. Wabash Ave., Dept. 82, Chicago, Ill.
SAVE \$2.00 BY ORDERING NOW!



LEGO WONDER FIXED DETECTOR
For REFLEX & CRYSTAL SETS
Something Entirely New!
100% SENSITIVE

10 IMPORTANT FEATURES READ THEM CAREFULLY

- 1—No parts to replace or wear out.
- 2—The use of a NEW MATERIAL that effectively eliminates distorted and interrupted reception, and substitutes clarity and increased volume.
- 3—Absolutely 100% sensitive. No searching for sensitive spot.
- 4—Glass encased, it is immune from sun and dust.
- 5—Especially designed to withstand high voltage in reflex circuits.
- 6—Solidly constructed throughout, it is practically everlasting.
- 7—It is ALWAYS READY—no adjustments of ANY kind needed.
- 8—As good looking as it is efficient. High nickel-plated throughout, and attractively designed. It enhances the appearance of any set.
- 9—Constructed so that it is thoroughly VIBRATION-PROOF.
- 10—Carefully tested, approved and unconditionally guaranteed by its makers.

For Sale by All Dealers 90c. or Sent Postpaid Insured \$1.00
LEGO CORP., 225 W. 77th St., N. Y. C.

THAT GREAT SUPERDYNE CIRCUIT

The Editors decided recently to bring RADIO WORLD'S Superdyne articles strictly up-to-date, and the Superdyne Circuit was, therefore, fully covered in descriptive story and diagrams in RADIO WORLD dated Aug. 31 and 30, 1924. These two copies sent on receipt of 20 cents. Also the July 5 issue contained an article about "Trouble Shooting for the Superdyne," mailed on receipt of 15 cents or start your subscription with any number. RADIO WORLD, 1493 Broadway, New York City.

The Nation's Largest RADIO Mail order House.

WE DEFY COMPETITION ON MAIL ORDERS
Our Prices Are Lower Than Any Other House in the Country—Every Item in Stock Has the Stamp of Highest Quality

Allow us to quote on any parts or standard sets. Send 5c in stamps for catalogue.

PHONES	Hosick Falls, Panel Mtg. \$0.75	Amsco, 4 in. \$0.79
Ditograph \$3.89	Patent 199 .40	DeForest, 3 in. .35
Brandes \$4.95	Federal .79	DeForest, 4 in. .40
Baldwin Type C \$7.85	General Radio .89	Pathe, 2 in. .30
Ambassador \$3.25	Workrite, 199 .60	Pathe, 3 in. .40
N. & K. \$6.50	TRANSFORMERS—PUSH PULL	Pathe, 4 in. .55
Scientific \$2.90	Como Duplex \$9.90	VARIABLE CONDENSERS
LOUD SPEAKERS	All American \$9.00	General Instrument Lo-Loss, all sizes \$4.50
Pathe \$12.98	TRANSFORMERS—AUDIO	Heath Lo-Loss, all sizes \$3.85
Muscle Master \$24.50	Star \$2.95	Heath Vernier Lo-Loss, all sizes \$5.00
Spartan \$9.25	Modern \$4.25	All other lines in stock.
Firth Adjustable \$9.98	Acme \$3.50	VOLT METERS
Sonora \$27.50	All American \$3.35	Jewel, 0-80 Volts \$2.25
New Ditograph \$24.50	Federal No. 65 \$4.90	Sterling, 0-80 Volts \$1.75
Magnaphone \$23.50	Thordarson \$3.98	Sterling, 0-35 Amp. .89
CHARGERS	Amertran \$4.55	Sterling, 0-35 Amp., 0-50 Volts, combination \$3.00
Westinghouse, 2 Amp. \$15.40	Erla \$3.95	Sterling, 0-120 Volts \$4.50
Westinghouse, 5 Amp. \$23.40	Federal No. 226 \$3.98	FRESHMAN PRODUCTS
Ward Leonard, D. C. \$7.75	TRANSFORMERS—RADIO	We carry a complete line of new Freshman Products. Let us quote you on your wants.
RHEOSTATS	Acme R-2, 3, 4 \$3.50	CRYSTALS
Fada \$0.60	Acme 30-K Super-Het. \$4.20	Lego Wonder Fixed Crystal \$0.80
Amsco (all styles) .85	Tri-Coil \$3.50	Erla Fixed .79
C. Hammer, 6 Ohm. .79	Erla Reflex \$3.95	DeForest Crystal \$1.39
P-cent .89	Rasla \$3.00	Pyretok Fixed \$1.10
Federal No. 18 .79	UV 1714 \$3.60	
Arrow Knob .69	RR 1716 (Super-Het) \$6.75	
SOCKETS	DIALS	
Fada \$0.79	Amsco, 2 in. \$0.30	
DeForest .50	Amsco, 3 in. .50	

Ultradyne, Complete, 8-Tube, Parts, \$85.00, with Blue Prints and Connecting Wires
Ultradyne Kit \$26.00 Ultradyne Book \$5c

THE BROOKLYN RADIO SERVICE
577 Myrtle Avenue
Brooklyn, N. Y.

Programs

Monday, October 13, Continued from preceding page

music; Parent-Teacher Association speaker. 4:53-5:30 P. M., Halstead's dance orchestra. 5:30-6 P. M., Aunt Betty stories and Kiddies Klub. 6:45 P. M., stock reports, weather, S. F. produce news, baseball scores, news. 8 P. M., educational pro-

COAST TO COAST
Every Turn **STAR** No
A Tap **COIL** Soldering
SEND FOR LITERATURE
STAR RADIO PRODUCTS CO.
711 S. DEARBORN ST. CHICAGO, ILL.

You "R. F. Monkeyers"

Same panel, same layout, fewer parts than a "Neut"—but, oh! how she steps out. Selectivity with deep, resonant volume. If you've been thro the embarrassing vicissitudes of "Neut" making, there's "Welcome" on your door mat for this very circuit. No one else has it. Necessary stabilizer, 22 feet gold sheathed wire, lithographed white print of circuit and complete, simple instructions—prepaid anywhere, cash or stamps—\$8.00. Nothing else to buy. Satisfaction guaranteed. Data about this circuit section for 10c. New radio catalog, thousands unusual items for stamp.


Kladag Radio Laboratories
KENT, OHIO



Save 1/2 Cost of New Tube

Guaranteed Vacuum Tube Repairs at Popular Prices
We try to maintain 24-hour service.
All repairs guaranteed. Tubes satisfactory or money refunded.
Special discounts to dealers.
Send broken and burned out tubes parcel post. Repaired tubes returned parcel post, C.O.D.

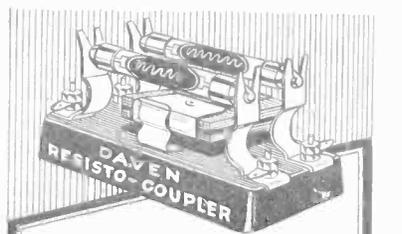HARVARD RADIO LABORATORIES
200 Old Colony Avenue
SO. BOSTON, MASS.



Imitation Is the Sincerest Flattery

—and is inevitable with so fine and worthy a product. But an imitation rarely satisfies.

The discriminating fan will insist upon the original and only **RESISTO-COUPLER**. Price, \$1.25 Sold everywhere.

Get from your dealer the **DAVEN "RESISTOR MANUAL,"** a practical handbook on Resistance Coupled Amplification. By Zeh Bouck. Price 25c

DAVEN RADIO CORP.
"Resistor Specialists"
Newark, N. J.

A DX SET ON 8" x 8" PANEL, 1-Tube Regenerator, by Herman Bernard. Sept. 13 issue of Radio World. Send 15 cents or start your subscription with that number. Radio World, 1493 Broadway, N. Y. C.

gram; courses in agriculture, music, economics and literature; music by Arion Trio. 10-11 A. M., dance by Halstead's orchestra; soloists.

WBAP, Fort Worth, Tex., 476m—10 A. M., 10 A. M., opening market quotations. 11 A. M., weather forecast; livestock reports; cotton and grain quotations. 12 Noon, market. 1 P. M., market. 2 P. M., close on cotton, grain and cottonseed oil; Dun's and Bradstreet's financial reviews. 6 P. M., Port of Missing Men; baseball scores. 6:30 P. M., sport review. (The above part of the program applies to all week days, except Saturday.) 7:30-8:30 P. M., artists from the Majestic Theatre. 9:30-10:45 P. M., concert by the Foster Merrill Music House, Hereford, Texas.

WHAZ, Troy, N. Y., 380m—9:00 P. M., concert by Columbus Club Italian Band; solos. 12:00 P. M., transcontinental and international program by the Campus Serenaders, Rensselaer Polytechnic Institute students' dance orchestra. **WMC, Memphis, Tenn., 500m—12:30 P. M.,** noon-day programme by the Skyline Serenaders playing at the Shrine Roof Cafe. 8:30 P. M., Monday evening request programme by the Gayoso Hotel Orchestra.

WOAW, Omaha, Neb., 526m—6:00 P. M., half-hour or dramatics. 6:30 P. M., Randall's Royal Orchestra. 9:00 P. M., program from vocal studio of Walter B. Graham, baritone; Regina Franklin, accompanist. 10:00 P. M., Wow! dance program, Pat's Melody Boys.

KFNF, Shenandoah, Ia., 266m—Silent Night.
KGW, Portland, Ore., 492m—11:30 A. M., weather forecast. 5:00 P. M., children's program. 7:15 P. M., markets, weather, news bulletins and police reports. 8:00 P. M., Elks Quartet; Ernest Crosby, Ross Fargo, Charles Thomson, Walter Hardwick, Matt Howard, piano; also Elsie Cramer, Margaret Notz, Marie Chapman McDonald, violinist.

WCB, Zion, Ill., 345m—8:00 P. M., Zion Band, assisted by Dorothy Bull, Ralph Bull, Erma Reynolds, Evelyn Uhlík, Mark Whiteside, Bessie Wiedman, Lillian Detienne.

Tuesday, October 14

WBAP, Fort Worth, Tex., 476m—7:30-8:30 P. M., concert. 9:30-10:45 P. M., concert of old-time music by the Tom Bean Fiddle Band. (See WBAP, Oct. 13)

WDAF, Kansas City, Mo., 411m—Baseball scores at 3:30, 4, 4:30, 5 and 6 P. M. 3:30-4:30 P. M., trio. 5-5:30 P. M., child talent. 5:50-6 P. M., marketgram, weather, time. 6-7 P. M. (School of the Air), piano tuning-in number; The Tell-Me-A-Story Lady; Hanlein's Trianon Ensemble. 11:45 P. M.—1 A. M. (Nighthawk Frolic), The "Merry Old Chief" and the Plantation Players, Hotel Meuhlebach.

KGQ, Oakland, Cal., 312m—N. Y. and S. F. stock reports and weather. 4-5:30 P. M., concert orchestra. 6:45 P. M., stock reports, weather, S. F. produce news, baseball scores, news. 8 P. M., "E. M. S. Pinafore," the KGO Opera Company, direction Carl Anderson; Arion Trio. 10 P. M.—1 A. M., dance, Halstead's orchestra.

WGY, Schenectady, N. Y., 380m—7:45 P. M., Chinese night, music, tour through New York Chinatown of quarter of a century ago by Edward H. Smith. 11:20 P. M., organ recital by Stephen E. Boisclair.

KFI, Los Angeles, 469m—5-5:30 P. M., news. 5:30-6 P. M., news. 6:45-8 P. M., organ. 8-9 P. M., Hotel Ambassador orchestra. 9-10 P. M., studio. 10-11 P. M., Don Meaney motion picture night.

KFO, San Francisco, 423m—12 Noon, time; scripture. 1-2 P. M., Seiger's orchestra. 2:30-5:30 P. M., Seiger's orchestra. 5:30-6:30 P. M., children's hour. 7-7:30 P. M., Seiger's orchestra. 8-10 P. M., Jack I. Thomas, tenor. 10-11 P. M., Bradford's band.

WHAS, Louisville, Ky., 400m—4-5 P. M., Alamo Theatre orchestra; police bulletins; weather; humor; readings; news. 4:55 P. M., livestock, produce and grain reports. 5 P. M., time. 7:30-9 P. M., Happy Hoosier Harmonists, Charles Harris, director; Carson Bard, Stumpe Meyer, Emil Stein, Kenneth Robison, Albert Koehler; news, time at 9 o'clock.

WFAA, Dallas, Tex., 476m—12:30-1 P. M., address, DeWitt McMurray. 8:30-9:30 P. M., Elizabeth Gay Jones, pianist; Dallas artists. 11-12 P. M., Adolphus Hotel orchestra, dance. (See WFAA, Oct. 13)

WQJ, Chicago, 448m—11 A. M.—12 Noon, John Mehan, "What Football Will Do for Your Boy";

MAILED ABSOLUTELY GUARANTEED



D-201A, D-209, D-199, D-13 in standard sizes to fit any socket. The internationally famous

DUTCH RADIO VALVE

will be mailed, fully guaranteed to you, for \$2.25 plus postage.

Three **DUTCH RADIO VALVES** (any type) will be sent for \$6.50 plus postage.

D. R. V. Importing Co.
515 Orange St., Newark, N. J.

FOR ANY CIRCUIT IN ANY SET YOU CAN'T BEAT THE DUTCH

Mr. L. J. Andrus, "The Care of Canaries." 3-4 P. M., Cora Beeman, "Croquettes for Supper"; Col. Alexander M. Damon, Salvation Army talk. 7-8 P. M., concert by Williams' orchestra; James Mitchell, baritone; Merrie Boyd Mitchell, soprano. 10 P. M.—2 A. M., Williams' orchestra; Otis Pike Jester, soprano; Mary House, pianist; Harry Geise; Edna Solosom, contralto; Paul Lougher, tenor; Will Rossiter, Nubs Allen, contralto; Malie and Little.

KFNF, Shenandoah, Ia., 266m—7:30 P. M., concert, Henry Field Seed Co.

WOAW, Omaha, Neb., 526m—5:00 P. M., "Advice to Lovelorn," by Cynthia Grey. 6:25 P. M., dinner program from WOAW's Studio, Shenandoah, Ia.

KGW, Portland Ore., 492m—11:30 A. M., weather forecast. 12:30 P. M., concert. 5:00 P. M.,

RADIO RECORD

Keep a permanently bound record of all stations you have received and how you received them. Radio Record 5 1/2" x 14"—500 lines. All broadcasting stations listed, and indexed with space for new stations—\$1.00 Postpaid.

THE BEADLE PRINTING CO.
MITCHELL SOUTH DAKOTA
Applause Cards 60 for \$1.00 Postpaid

ACME

for amplification

READ MICRODENSER

The perfect equalizing capacity for Radio Frequency circuits.



Microdenser adjustment—sturdy construction. Dust proof. No tools needed for adjustment. Once adjusted it cannot change.

J. M. READ & CO.

3289 Washington Blvd. Cleveland, O.
Dealers write for prices.

"GET HASTINGS, NEB."

We Will Mail Free the Hook-up of "Killoch Kilo Koupler"

Most Wonderful Coil

A CIRCUIT WELL WORTH WHILE!
Build a two-tube set, one stage of R. F., using neodymium principle and detector. Full details in Radio World, issue April 12. Send 15 cents.

David Killoch Company

Dodge Building, 45 West Broadway
Corner Park Place, New York City

Mail This Coupon NOW for FREE RADIO CATALOG



No set-builder or radio fan should be without this big catalog. It is full of wonderful radio bargains which have not and can not be equalled elsewhere. Our unrivaled buying power means a worth while savings for you.

Chicago Salvage Stock Store,
Dept. W-8, 509 S. State St., Chicago, Ill.

Gentlemen: Please send me a copy of your new radio catalog.

Name

Postoffice State

Rural Route..... Box No.....

Street and No.....

Programs, Continued

children's program. 7:15 P. M., markets, weather, news bulletins and police reports. 8:00 P. M., agricultural lecture. 8:30 P. M., concert by Civic Music Club.

Wednesday, October 15

WHO, Des Moines, Ia., 526m—7:30-9 P. M., Bankers Life Orchestra; Margaret Leech, soprano; Jack Eberhart, baritone.

WFAA, Dallas, Tex., 476m—12:30-1: P. M., Musicale by the Red-Headed Girl. Station WFAA will be silent for the remainder of the day. (See WFAA, Oct. 13.)

WBAP, Fort Worth, Tex., 476m—7:30-8:30 P. M., musical concert by the Hemphill Heights Masonic Lodge No. 1164. 9:30-10:45 P. M., dance music by the Texas Hotel Orchestra. (See WBAP, Oct. 13.)

WDAF, Kansas City, Mo., 411m—3:30, 4, 4:30, 5 and 6 P. M., baseball scores. 3:30-4:30 P. M., trio. 5:50-6 P. M., marketgram, weather, time signals. 6-7 P. M., (School of the Air); piano; address, health; address, meat; the Tell-Me-a-Story Lady; Hanlein's Ensemble. 8:15 P. M., Federated Music Clubs. 11:45 P. M.—1 A. M., (Nighthawk Frolic). The "Merry Old Chief" and Bobbie Kuhn's K. C. A. C. Orchestra.

KGO, Oakland, Cal., 312m—1:30 P. M., N. Y. and S. F. stock reports and weather; music. 4-5:30 P. M., concert orchestra, Hotel St. Francis. 6:45 P. M., stock reports; weather; S. F. produce news; baseball scores, and news items. Silent night.

WHAS, Louisville, Ky., 400m—4-5 P. M., Alamo Theatre orchestra; police bulletins; weather; humor; readings; news. 4:55 P. M., livestock; produce and grain market. 5 P. M., time. 7:30-9 P. M., concert by Keith Kammard and his Kentucky Ramblers; news at 9 P. M.

WGY, Schenectady, N. Y., 380m—6:30 P. M., adventure story.

KFI, Los Angeles, 469m—5:53-30 P. M., news. 5:30-6 P. M., news. 6:45-7:30, detective stories and concert. 7:30-8 P. M., 1-act play, "The Stranger." 8-9 P. M., studio. 9-10 P. M., studio. 10-11 P. M., Hollywoodland orchestra. 1-12 P. M., Ambassador Hotel orchestra.

KPO, San Francisco, 423m—Noon, time signals. 1-2 P. M., Seiger's orchestra. 2:30-3:30 P. M., Fisher's Amphians. 4:30-5:30 P. M., Seiger's orchestra. 5:30-6:30 P. M., children's hour. 6-7:30 P. M., Seiger's orchestra. 8-11 P. M., Bradfield's band; songs by Woolley sisters.

KNF, Shenandoah, Ia., 266m—7:30, Harmonica concert.

KGW, Portland, Ore., 492m—11:30 A. M., weather forecast. 12:30 P. M., Bill Darby's Orchestra. 5:00 P. M., children's program. 7:15 P. M., markets, weather, news bulletins and police reports. 8:00 P. M., program, courtesy Elizabeth Hoben. 10:00 P. M., George Olsen's Metropolitan Orchestra (two hours).

WMC, Memphis, Tenn., 500m—12:30 P. M., program by the Skyline Serenaders. 8:30 P. M., Silent Night.

Thursday, October 16

WBAP, Fort Worth, Tex., 476m—7:30-8:30 P. M., concert. 9:30-10:45 P. M., Dot Echols Frolics. (See WBAP, Oct. 13.)

WFAA, Dallas, Tex., 476m—12:30-1 P. M., Charles E. Osborne, "Fit for Every Fight." 8:30-9:30 P. M., Walter J. Fried, violinist, and Dallas artists. 11-12 P. M., organ with orchestra. (See WFAA, Oct. 13.)

WDAF, Kansas City, Mo., 411m—3:30, 4, 4:30, 5 and 6 P. M., baseball. 3:30-4:30 P. M., trio. 5:50-6 P. M., marketgram; weather; time signals. 6-7 P. M., (School of the Air); piano; Edgar Allan Linton, talks on world travels; reading, Miss Cecile Burton, poems and essays; the Tell-Me-a-Story Lady; Hanlein's Trianon Ensemble. 8:15 P. M., 1 A. M., (Nighthawk Frolic). The "Merry Old Chief" and the Plantation Players, Hotel Muehlebach; Eddie and Bobbie Kuhn's K. C. A. C. orchestra.

KGO, Oakland, Cal., 312m—1:30 P. M., N. Y. and S. F. stock reports and weather. 4-5:30 P.

M., concert orchestra, Hotel St. Francis. 6:45 P. M., stock reports; weather; S. F. produce news; baseball scores; news. 8:00 P. M., Mid-Pacific Hawaiian quartet; address, "The Bolshevism of the Bee," by Rev. George W. Phillips; songs; music. 10 P. M.—1 A. M., dance music program by Henry Halstead's orchestra and soloists, Hotel St. Francis, San Francisco.

WGY, Schenectady, N. Y., 380m—7:45 P. M., new books, by William F. Jacobs. 8:00 P. M., radio drama, "The Path of Glory," by Rabbi Goodman Lipkind, presented by WGY writers; WGY orchestra. 11:20 P. M., organ. **KFI, Los Angeles, 469m—5:53-30 P. M.,** Evening

Herald news bulletins. 5:30-6 P. M., news. 6:45-7:30 P. M., Y. M. C. A. lecture. 7:30-8 P. M., Harry Porter, baritone, and Sylvia Marotta. 8-9 P. M., concert orchestra. 9-10 P. M., studio. 10-11 P. M., Spanish program.

RADIO CABINETS

Shipped knock-down. Each joint fitted. Hinges attached. Oak cabinets unsoldered. Guaranteed perfect. Add parcel post charges to remittances. Send for literature.

7 x 12..	\$1.80
7 x 14..	1.80
7 x 18..	1.80
7 x 21..	2.10
7 x 24..	2.35
7 x 26..	2.60

Radio Cabinet Co.
1804 Vine St., Philadelphia, Pa.
DEALERS' DISCOUNT

FAHNESTOCK CLIPS

"Popular Wherever Radio Is Used"

14 Sizes in Beautiful Display Case

Dealers write for big money-making proposition.

FAHNESTOCK ELECTRIC CO.
Long Island City, L. I.

How to Build ULTRADYNE
The Improved SUPER-HETERODYNE

32 page illustrated book with detailed instructions on drilling, wiring, assembling and operating Model L-2 Ultradyne Receiver. Latest R. E. inventor of the Ultradyne—the most selective receiver known. Write for descriptive circular.



Phenix Radio Corp.

5-9 Beekman Street
New York

THE FRANK SUPER-KIT

For 8 Tube Super-Heterodyne

Contains Complete Parts



Sells for Only \$85.00

When completed, the Frank Super-Set can be mounted in a standard 7 x 26 inch or beautiful console cabinet, making a Super-Heterodyne set, unsurpassed by others for extreme distance reception, volume, selectivity and wonderful tone quality. Rightfully named the Rolls Royce of radio at a reasonable price. In New York on demonstration at all Perfection Radio Stores.

Sent on receipt of money order or check.

All orders are sent out within 24 hours.

DEALERS WRITE OR WIRE FOR DISCOUNTS

Everlast Radio Products Co.

27 Park Place

New York City

KHJ, Los Angeles, Cal.

We are glad to confirm your report of reception of our program.

John S. Daggett,
"Uncle John,"
Mgr., Times Radio Staff.

GENERAL ELECTRIC COMPANY

Pacific Coast Broadcasting Station
5555 E. 14th St. Oakland, Cal.
KGO
Sept. 11, 1924.

Mr. T. J. Kennedy,
1300 University Ave., New York, N. Y.
We are glad to confirm your reception of KGO on the evening of Sept. 6 as we were broadcasting the opera "Carmen."

We always appreciate hearing from our radio listeners and hope that you will be able to pick up KGO regularly.

Yours very truly,
Jennings Pierce,
Radio Broadcasting Pub. Dept.

KLZ, Denver, Colo.

We are pleased to acknowledge receipt of your report of reception of our phone station. We have placed a tack in our map for you.

Reynolds Radio, Inc.

DX Fans! Confirmations Stop All "Doubting Thomases"

Confirmations of Stations Received from New York, N. Y., with

KENNEDY TUNER

DX Fans! If you want real results, get a KENNEDY TUNER AND HAVE THE WHOLE U. S. A. AT YOUR FINGER TIPS.

Only one dial to get stations and the other to increase or decrease volume. Kennedy Tuner is used in place of variometer, variometer and honeycomb coils, saving the cost of over \$3.00 worth of unnecessary junk that is in most receiving sets, and no dead end losses.

Kennedy 5.00 Tuner Including Globe Trotter Diagram

GUARANTEE:
If not satisfied after 30 days, we will cheerfully return your money.

Send for Free Diagram

T. J. KENNEDY

RADIO GLOBE TROTTER
1360 University Ave., New York, N. Y.

KFI, Los Angeles, Cal.

Thanks for your letter received. Yes, "The Minuet," by Louis Parker, was broadcast from the Anthony station during the late program.

Yours Radio, KFI

GENERAL ELECTRIC COMPANY

Pacific Coast Broadcasting Station
5555 E. 14th St. Oakland, Cal.
KGO
Sept. 4, 1924.

Mr. Vincent T. Kenney,
124 W. 96th St., New York, N. Y.

We are glad to confirm your reception of our late program from the Hotel St. Francis on the morning of August 27th.

We are always glad to answer any questions of our radio friends and hope you write in often with your comments.

Yours very truly,
Jennings Pierce,
Radio Broadcasting Pub. Dept.

2-LO, London, Eng.

We beg to acknowledge your reception of our program.

Yours faithfully for the
British Broadcasting Co., Ltd.,
Jr. Director, London Station, C. C. H. King.

DeForest Imperils R. C. A.

PHILADELPHIA.

CHARGES of infringement and conspiracy made in applications for injunctions sought by Dr. Lee De Forest were joined in a series of suits against the Westinghouse Electric and Manufacturing and Westinghouse Lamp companies. The applications were filed in the Federal

Court by the De Forest Radio Telephone and Telegraph Company. Similar actions making the same general charges were filed in Delaware against the Radio Corporation of America.

The complaints allege the generic patents of Dr. De Forest on oscillators, detectors, amplifiers, the three electro audio or vacuum tube and certain other of his essential radio inventions have been infringed upon in equipment made or sold by the three defendants. Further charges concerning an alleged trade agreement now in force, under which the Westinghouse interests manufacture 40 per cent. of the transmitting, receiving and miscellaneous equipment sold by the Radio Corporation, much of which embodies alleged infringements on De Forest letters patents, are made. Samuel E. Darby, Jr., of Darby and Darby, New York, counsel for the De Forest interests, said that the actions were based on previ-

ous decisions which had upheld the inventor's patents. He said: "We have asked for an accounting of all profits accruing to the three defendant corporations and injunctions that will prevent future infringement."

20% OFF Manufacturers' Prices

Select most any standard advertised set or part and remit to us the advertised manufacturers' price, LESS ONE-FIFTH, and we will immediately ship you the goods, fully guaranteed, and in most cases in original packages as received from the manufacturer.

Send check or money order, or pay upon delivery. We pay transportation on all orders of \$4.00 or over.

*Satisfaction Absolutely
Guaranteed*

ALEXANDER RADIO CO.

640 Broadway New York City

INSIDE-AERIAL

Hang between walls close to ceiling—Copper—Fluxless inside—Copper
DISTANCE-SELECTIVE-NOT A LOOP
 but a full size aerial with 132 feet stranded copper wire in a compact form
NOT AFFECTED BY WIND, RAIN, SNOW OR LIGHTNING
 CERTIFICATE OF APPROVAL by one of the largest RADIO LABORATORIES
 after a RIGID TEST sent on request, also with each coil.
 PRICE \$7 Postpaid or \$5 and a address of set owners.
 See ad about our 100% 2227 75 75 75

INTERSTATE SIGNAL CO., Dept. 2, COLUMBUS, OHIO

CROSLEY
 RADIO CATALOG FREE

Describes fully the complete line of radio frequency sets, regenerators and sets (licensed under Armstrong U. S. Patent Nos. 1,113,149) and parts.

Write for Catalog Today

THE CROSLEY RADIO CORPORATION
 POWEL CROSLEY, Jr., President
 10402 Alfred Street Cincinnati, Ohio

RADIO MONEY SAVING
 CATALOG SENT
FREE
TIMES SQUARE AUTO SUPPLY CO., INC.
 BROADWAY at 56th St. New York

PRE-AMPLIFIER



Makes Distant Stations Sound Like Local Ones

THE TWITCHELL PRE-AMPLIFIER is a Powerful Radio Frequency Amplifier attachable to any make of receiving set. It brings in many distant stations which you cannot hear without it. Brings in with tremendous volume those you now hear only faintly. Makes your set selective. Prevents re-radiation.

Price, complete with tube, prepaid

\$25.00

Diagram of circuit, \$1.00

S. A. TWITCHELL CO.
 1930 Western Ave. Minneapolis, Minn.

RADIO WORLD'S QUICK-ACTION CLASSIFIED ADS.

10 CENTS A WORD. 10 WORDS MINIMUM. TELEPHONE YOUR CLASSIFIED IF IN A HURRY.

SPOKEN ESPERANTO for beginners — for groups—1 cloth or 2 paper, \$1.00. Norman Frost, 12 Ash Place, Cambridge, 38, Mass.

RAILWAY POSTAL CLERKS start at \$133 month. Railroad pass, expenses paid; questions free. Columbus Institute, V16, Columbus, Ohio.

FOR SALE—One-tube radio set and few parts. For information send to W. Hemry, 523 So. Beech, Casper, Wyo.

NEW AMRAD RF 4-TUBE SET, Brandes Talker, Separate Load Coils, dual jack and radiator for set. Value \$162.25. Will sell for \$80.00. J. M. Ragsdale, Jr., Columbus, Mont.

SUPERHETRODYNE FILTER. Eliminates noises and distortion. An essential finishing touch. Consists of choke coil, non-inductive resistors and diagram, \$6.25. RADIO CENTRAL, Abilene, Kan.

AMPLIFY YOUR SET with Flint Audio Transformers, \$3 each, postpaid. All tubes—all circuits—guaranteed. The Flint Radio Co., 1816 Wilson Avenue, Chicago, Ill.

EARN \$110 TO \$250 monthly, expenses paid, as Railway Traffic Inspector. Position guaranteed after completion of 3 months' home study course or money refunded. Excellent opportunities. Write for Free Booklet G-161. Standard Business Training Inst., Buffalo, N. Y.

BE A DETECTIVE—Earn big money; easy work; we show you all; free particulars. Write National Headquarters, 188 East 79th Street, New York.

FOR SALE—Fully equipped Radio Broadcasting Station. Standard make of parts. Two generators 500 and 250 watts. Ready for operation. Reasonable terms to responsible parties. Hardy Sanitarium, Ardmore, Okla.

HOOK-UPS FOR EVERYBODY—Henley's 222 Radio Circuit Designs, \$1.00, postpaid. The Columbia Print, 1495 Broadway, N. Y. C.

A REMARKABLE TWO-FOR-PRICE-OF-ONE

Subscription Offer

for

NEW RADIO WORLD Readers

Radio World has made arrangements

- to offer a year's subscription for
- any one of the following publications
- with one year's subscription for

- RADIO WORLD:
- RADIO NEWS or
- POPULAR RADIO or
- RADIO BROADCAST or
- WIRELESS AGE or
- RADIO DEALER or
- RADIO (San Francisco).

This is the way to get two publications

- for the price of one:
- Send \$6.00 today for RADIO WORLD
- for one year (regular price
- for 52 numbers)
- and select any one of the other
- six publications for twelve months
- Add \$1.00 a year extra for
- Canadian or Foreign postage.
- Present RADIO WORLD subscribers
- can take advantage of this offer by
- extending subscriptions one year NOW.
- Or order thru your newsdealer.

RADIO WORLD'S SPECIAL TWO-FOR-PRICE-OF-ONE SUBSCRIPTION BLANK

RADIO WORLD, 1493 Broadway, New York City
 Enclosed find \$6.00, for which send me RADIO WORLD for twelve months (52 numbers, beginning.....
 and also without additional cost, Radio News, or Popular Radio, or Radio Broadcast, or Wireless Age, or Radio Dealer, or Radio for twelve months, beginning..... Put a circle around the other publications you want. Or send \$10 for two yearly subscriptions.

Indicate if renewal. Offer Good Until Oct. 20, 1924. Name Street Address City and State

**GETS THE STATION
MICROTOR**
Infinitesimal Control of Condensers and Rotors
1 Division of MICROTOR Knob turns Rotor
1-5400 Revolution.
Controls standard dials to and including 4" dia.
Easy, Universal application.
50c Postpaid, on receipt of cash.
**MANUFACTURERS' & INVENTORS' ELECTRIC
COMPANY**
Distributors write for terms.
29-31 Gold Street Dept. RW New York City

RADIO CRYSTALS
MOUNTED, UNMOUNTED, BULK
Packed under your own label if desired.
Dealers and Jobbers—Write us for lowest
prices on Quality Crystals.
MELODIAN CO. OF AMERICA
INDEPENDENCE, MISSOURI

**COSMOPOLITAN
PHUSIFORMER**
Send Fifty Cents for Manual
15-17 West 18th St., New York

\$15 Set Gets 2,000 Miles
The Essex Radio Special, the receiving set with a
concealance, gets you more distant stations clearer and
easier than sets costing ten times its price. \$15
Set complete with cabinet, without tube or batteries.
\$20 Set complete with cabinet, tube and batteries.
ESSEX RADIO SERVICE
617 West 125th St. New York
Detailed information on request.

Just Out! Second Year!
The
**RADIO DEALER
YEAR BOOK**
Season 1924-1925

A complete directory and cata-
logue of the entire radio in-
dustry.
Listing manufacturers of radio
parts, sets and accessories by
their products, showing full ad-
dress and list prices.
The most complete compilation
of radio information ever made.
Single copies \$1.00 or FREE with a
year subscription to The Radio
Dealer, the trade monthly.
Send all orders to the
publishers.
THE RADIO DEALER
1133 Broadway New York City

**DID YOU GET RADIO WORLD'S
FALL BUYER'S NUMBER**
Sept. 27 issue of Radio World contained the follow-
ing important features: "A New 1-Tube Reflex," by
A. I. Peck; "The Best Set for Your Location," by
N. N. Hornstein, Technical Editor; "Three Stages of
Resistance-Coupled AF," by Walworth Ator; "A
2 Tube and Crystal Reflex Using Only One Control,"
etc. Full list of Broadcasting Stations. 10c. per
copy, or start your subscription with that number.
RADIO WORLD, 1493 Broadway, New York

A LOW-LOSS 3-CIRCUIT TUNER, by Neal
Pitzalan, Sept. 13 issue. Send 15 cents or start
your subscription with that number. Radio
World, 1493 Broadway, N. Y. C.

**RADIO WORLD'S
Broadcast University**
*Questions and Answers On
the Air Every Wednesday Eve-
ning at WLS, the Sears-Roebuck
Station, Chicago — Department
Conducted by Mat H. Friedman,
RADIO WORLD'S Chicago Repre-
sentative.*

I AM SURE that many radio fans like myself
are puzzled about the kind of radio-frequency
amplification to use. I understand that the trans-
former type would be desirable if one could get
one to amplify equally well on all wavelengths.
But I also know that a fixed transformer will not
do that. But suppose we should use two stages,
each one with a different wave band, could the
amplification be improved on all wavelengths?
In the tuned type, are the windings of the trans-
formers critical? I note that most of them use
about 20 turns for the primary and about 60 for
the secondary. Could I use 40 turns for the
primary and 50 for the secondary? Are the tuned
type more selective than the transformer kind?—
P. E. Miller, 1252 N. Campbell St., Chicago.

Your method of broadening the peak of the
coupled transformers is not practical, because
should the first stage be under the wave received,
and the second stage be over the wave received,
tuning sharply and efficiently would be defeated.
In the first stage you would not be tuning to the
station properly, and in the second stage the
transformer would be trying to amplify a signal
that is weakened by poor tuning in the first place.
The windings of the tuned type of transformers
are critical to a degree, and when more than one
stage is used the number of turns on each trans-
former should be the same in order that the con-
densers tune to the same dial numbers in step.
Forty turns on the primary of a transformer
would be too much because it would tune the
plate circuit into resonance with the grid circuit
and cause oscillation. Fifty turns on the secondary
would not be enough to enable the circuit to tune
to the higher broadcast wavelengths without the
use of very large condensers. The tuned type of
transformers are much more efficient and are much
sharper tuned than the fixed type.

I WISH to build a separate 2-stage audio ampli-
fier, and I have all the parts necessary for stor-
age battery connections. I would like a diagram
showing how the connections go, and also show a
double circuit-jack after the first stage.—J.
Handwerker, 1624 Park Place, Brooklyn, N. Y.
Fig. 43 is the circuit you ask for. The two bind-
ing posts at the left go to the detector output
posts. Up to 100 volts may be used on the plates
of the amplifiers.

I WAS greatly interested in the article by Lieut.
Harry F. Breckel in the August 30 issue, dealing
with radio-frequency amplification. After reading
many articles on the subject I find that all agree
that tuned RF is the best. They also agree that
the fixed transformer coupled type can be made

to function better by shunting a condenser across
the windings. Lieut. Breckel says a 23-plate
should go across the secondary. Other articles
call for a 5-plate condenser across the primary.
If an untuned transformer is used with a 23-plate
condenser across the secondary, what should the
natural wavelength of the transformer be? When
using two stages of RF amplification, one fixed
and the other tuned, which should be placed in
the first stage?—R. E. Miller, 1252 N. Campbell
St., Chicago, Ill.

By your first question it is understood that
you refer to the fixed transformers which are
usually not tuned, but whose wavelength factor
is predetermined for definite wavelengths. If so,
that transformer, in order to tune upwards, for
the broadcast wavelengths should have a natural
fundamental of 200 meters. The condenser would
then boost the wavelength up close to 600 meters,
provided one with 23 plates is used. The same
applied to the other RF transformers, like the
Neutroformers, which have a fundamental of about
200 meters. Tuning the primary, especially when
that primary is in the plate circuit of the pre-
ceding tube, is poor practice, as it will bring
the plate into resonance with the grid circuit at
times and will cause uncontrollable oscillation. It
is the usual practice to place the untuned RF
stage first, and the tuned stage of RF directly
before the detector when using a combination of
both, but it works either way.

Loud Speaker FREE
with Every Complete Original
NATH. BALDWIN HEADSET
Purchased at \$7.50
WALTER SCOTT & CO.
636 Highland Ave. Newark, N. J.


For Maximum Amplification Without
Distortion and Tube Noises
use the well known
Como Duplex Transformers
Push-Pull
Send for literature.
COMO APPARATUS COMPANY
446 Tremont St. Boston, Mass.

The Ultimate Radio Receiver
THE FLEX-O-DYNE CO.
1674 Broadway (At 52nd St.)
New York, N. Y.
Circle 4569

WINDING A LOOP ON A PHONOGRAPH
RECORD, by Herbert E. Hayden, Sept. 13 issue.
Radio World, 15 cents.

CATALOG OF RADIO & ELECTRICAL BOOKS
sent free on receipt of post card. The Columbia
Print, 1493 Broadway, N. Y.

Presenting the 1925 Operadio
*The Original
Self-Contained Radio Set*
Introduced last year, the Operadio
created a country-wide sensation. Many
thousands are now in use.
In the 1925 model all the former features are
retained—the loud speaker, six tubes, dry cells,
and all parts are fitted into a compact cabinet and
the necessity for aerial and ground is eliminated
by a patented wave-bridge located in the cover.
The new set is marked by extreme beauty of
appearance and efficiency of performance. The
wave band is expanded to include reception from
radiocast stations of all wave lengths. Utmost
simplicity of tuning. Razor-sharp selectivity.
There are many unusual features. Write
at once for particulars about our dealer
proposition.
The Operadio Corp.
8 South Dearborn Street Chicago
OPERADIO

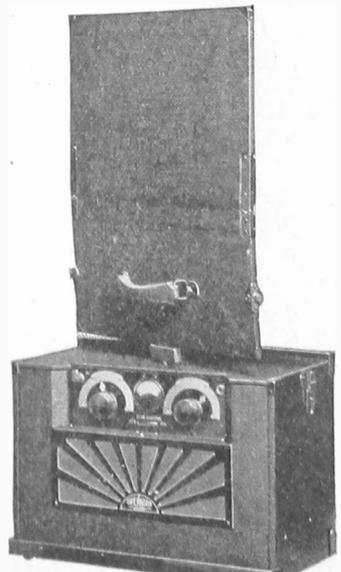



THIS BATTERY WILL MATERIALLY REDUCE YOUR OPERATING COSTS ON HEAVY CURRENT SETS

NEW!

Eveready Heavy Duty "B" Battery, 45 volts. Three Fahnestock Clips. Length, 8 1/2 inches; width, 4 3/4 inches; height, 7 3/4 inches; weight, 13 3/4 pounds.

New low price, \$4.75

New Heavy Duty 45-volt "B" Battery No. 770 Extra Large Cells— Extra Long Service

FOR maximum "B" Battery economy, use this *New Eveready Heavy Duty 45-volt "B" Battery*, in the following general cases:

- 1—On all receiving sets operating at 90 volts or more, having four tubes without a "C" Battery, and all sets having five or more tubes, with or without a "C" Battery.
- 2—On all power amplifiers.
- 3—On all sets that pull heavy currents from the "B" Battery.

Under the above conditions, the *New Eveready Heavy Duty 45-volt "B" Battery* will give much longer service than the 45-volt "B" Battery of usual size.

If your receiving equipment falls under any of the above classifications, you can make a big saving in "B" Battery costs by using this *New Eveready Heavy Duty 45-volt "B" Battery No. 770*. Buy it and you get the biggest battery value on the market to-day!

Manufactured and guaranteed by
NATIONAL CARBON COMPANY, INC.
Headquarters for Radio Battery Information
New York—San Francisco

Canadian National Carbon Co., Limited, Toronto, Ontario

If you have any battery problem, write to Mr. G. C. Furness, Manager, Radio Division, National Carbon Co., Inc., 200 Orton St., Long Island City, New York.

EVEREADY
Radio Batteries
—they last longer

No. 7111
Eveready Radio
"A" Dry Cell
Specially
manufactured for
use with dry cell
tubes



Eveready 6-volt Storage
"A" Battery

No. 766
Eveready "B"
22 1/2 volts. Six
Fahnestock Spring
Clip Connectors



No. 772
Vertical 45-volt, large
size "B" Battery

No. 771
Eveready "C" Battery
Clarifies tone and
prolongs "B" Battery
life



No. 764
Vertical 22 1/2-volt
"B" Battery