

May 11th, 1929


15 Cents

RADIO WORLD

REG. U.S. PAT. OFF.

The First and Only National Radio Weekly

372d Consecutive Issue—Eighth Year

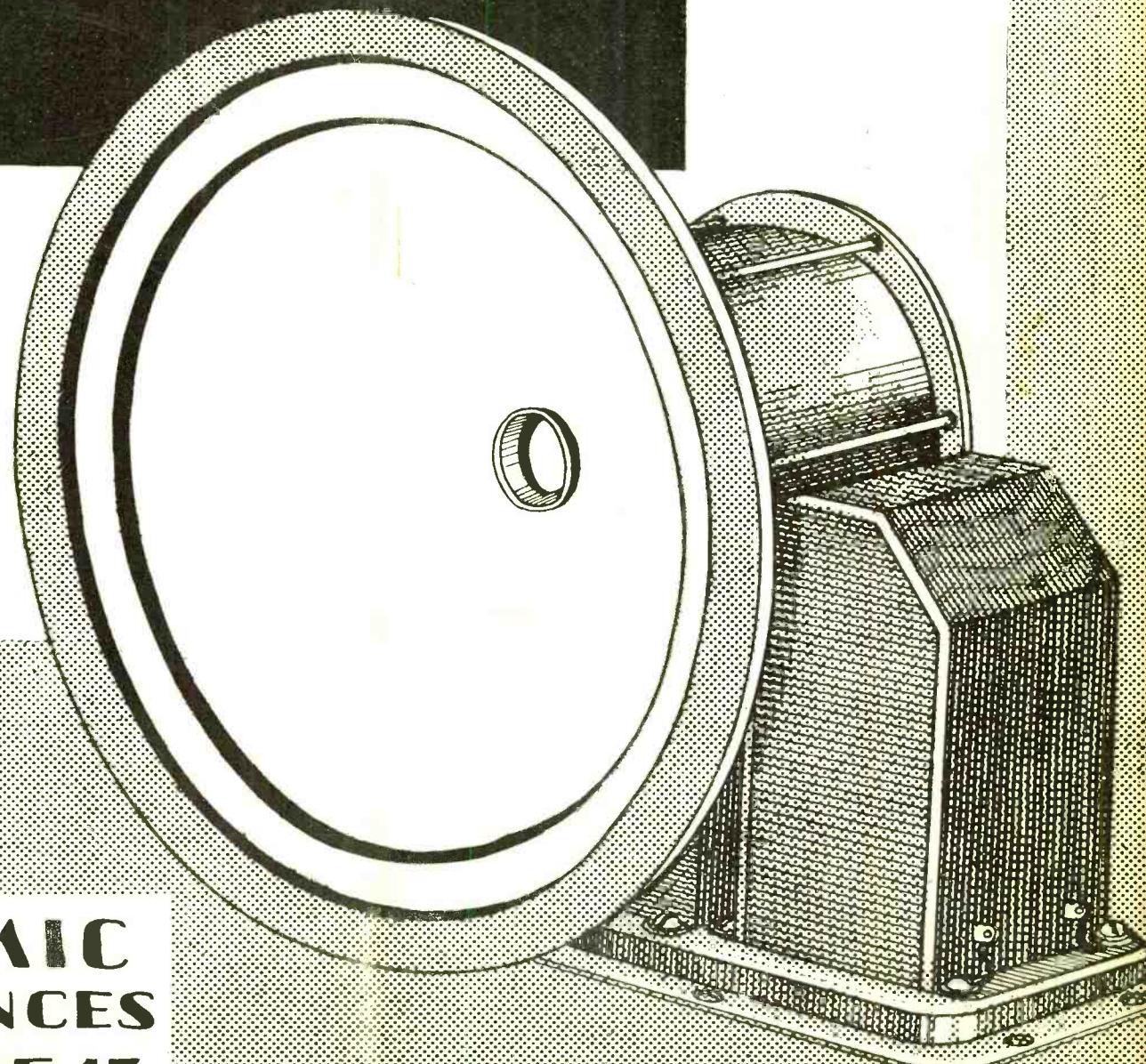

DYNAMIC
IMPEDANCES
SEE PAGE 17

THE LATEST RADIO MAGAZINE



REGULAR SUBSCRIPTION RATES
\$2.50 in U. S., 25c a copy;
\$3.00 in Canada and foreign.

Special Rate for Readers of Radio World, \$2.00 a Year

RADIO-CRAFT—the latest and most up-to-date Radio magazine. Edited only for the set-builder, the radio-constructor, the experimenter and the radio enthusiast who believes in radio craftsmanship.

Published every month. Large size 9 x 12 in. Cover in full 4 colors.

TECHNI-CRAFT PUBLISHING CORP.
R. W., 98 Park Place
New York, N. Y.

Enclosed find \$2.00 (check, money order) for which enter my subscription to your new monthly magazine RADIO-CRAFT. Please mail all copies to address below:

Name

Address

City and State.....

Most Selective Diamond Follow Blueprint

THIS IS THE BATTERY MODEL

Here is the circuit of circuits—the design that makes a neighboring cleared-channel, high-power broadcaster snap out of audibility at a slight turn of the dial.

No need to worry about the selectivity requirements imposed on receivers by the reallocation.

Volume "to fill the house"—even on distance. Tone quality excellent.

Get the official blueprint of the laboratory model of the new SG 4-tube Diamond, exactly as built by Herman Bernard, the designer.

RADIO WORLD
145 W. 45th St., N. Y. City
(Just E. of B'way)
 Enclosed please find \$1.00 for which please send at once the official blueprint of the new highly selective 4-tube screen grid Diamond of the Air battery model.
 60 cents extra for the February 9th, 18th 23rd and March 2nd (1929) issues of Radio World, containing Bernard's articles on the construction of this receiver.

\$3.00 for 6 months (26 numbers) subscription for Radio World. Send Diamond blueprint and four Diamond issues FRHE. In addition to 26 current issues.

Name

Address

City

"Look for the Green Box"



**The Only Tubes with
5-Day Money-Back
Guarantee in Each Box**

222 Screen Grid Tube \$3.50



AFTER having tried many screen grid tubes, many specialists have made Kelly 222 their choice. Our 222 stands up! Filament is not critical, but 3.3 volts work best. Plate voltage may be from 90 to 180, but negative bias of 1.5 volts remains the same. The screen grid voltage, G post of socket, may be 22 to 45 volts, depending on how much amplification you want. A working amplification of 60 is easily obtainable (80 mu.).

The plate current is virtually independent of plate voltage in the recommended range, 90 to 180 volts. This aids stability.

The cap at top of the tube is for familiar grid connection.

This tube is for battery or A-eliminator operation.

240 High Mu Tube \$1.25

Great for Detector or in audio channels where a resistor or impedance coil is in the plate circuit. Fil. 5 volts DC, plate 90 to 180 volts.

POWER TUBES

| | | | |
|-----------|--------|-----------|--------|
| 250..... | \$6.00 | 210..... | \$4.50 |
| 171A..... | 1.50 | 112A..... | 1.50 |

OTHER TYPES

| | | | |
|-----------|--------|----------|--------|
| 280..... | \$2.50 | 281..... | \$3.50 |
| 227..... | 2.25 | 226..... | 1.25 |
| 201A..... | 1.00 | 199..... | 1.25 |

KELLY TUBE COMPANY
Walter J. McCord, Manager
57 DEY STREET, NEW YORK CITY
Tel. BARclay 8459
Suite 6

SCREEN GRID COILS for the

4-tube SG Universal

Antenna coil, Model RF5
for .0005 mfd. \$1.50

Antenna coil, Model RF3
for .00035 mfd. 1.75

Coupler, Model TP5, for
.0005 mfd. 2.00

Coupler, Model TP3, for
.00035 mfd. 2.25

SCREEN GRID COIL CO.

143 West 45th Street
New York City
Immediate Delivery and
10-Day Money-Back Guarantee

RCA Radiola 28

**8-Tube Super-Heterodyne,
Always Sold at \$260.00
Our Price While They Last \$75!**



Radiola 28, an 8-tube Super-Heterodyne, of the Radio Corporation of America, in solid mahogany cabinet, with RCA solid mahogany loop and eight RCA Radiotron tubes; solid mahogany table is included. Everything exactly as illustrated. Always sold at \$260.00. All in factory-sealed cartons at our special price of \$75.00.

Guaranty Radio Goods Co., 145 West 45th St., N. Y. City.
(Just East of Broadway.)

Please send me at once one 8-tube Radiola 28 Super-Heterodyne, in solid mahogany cabinet, with solid mahogany table affixed; RCA loop, seven RCA Radiotrons UX199, and one Radiotron power tube UX122. All in a factory-sealed carton, at only \$75.00.

Please find remittance of \$75.00 enclosed. You are to pay carriage.

Please ship C.O.D. I will pay carriage.

One 0-6 volts plug-in type tip jack voltmeter for Radiola 28, at \$2.00 extra.

Name

Address

City..... State.....

THIS OFFER REVOCABLE WITHOUT NOTICE!

If your remittance arrives too late we will return money the day after receipt.

See All You Get for Only \$75.00

WHEN you purchase a Radiola 28 eight-tube Super-Heterodyne, with R. C. A. loop, eight tubes and table included, you are buying at almost 70 PER CENT OFF the previous price of \$260, and are buying the product of the world's leading radio and acoustical engineers, a product in which the talents of R. C. A., Westinghouse and General Electric are combined. Here's what you get:

- (1) An 8-tube Radiola 28 Super-Heterodyne, in beautiful solid mahogany two-tone cabinet.
- (2) A solid mahogany table that is an integral part of the cabinet construction.
- (3) An R. C. A. loop especially designed for this receiver, with solid mahogany frame.
- (4) Eight R. C. A. Radiotrons, consisting of seven UX199 tubes and one UX120 power tube.

ALL IN A FACTORY SEALED CARTON!

EVERYBODY wants a Super-Heterodyne because it is so selective that you do not have to worry about separating stations—10 kc. separation is yours at last.

You are almost ready to demonstrate this set to your admiring family and friends the moment it is received, since only the A and B supplies and the speaker are necessary for operation.

And when you turn on the set—oh, what a thrill! The most sensitive receiver design is yours, and how proud you are of your smart "buy"! In all the length and breadth of the United States—indeed, all the world over—there is no bigger or better radio bargain than this! A Super-Heterodyne! Eight tubes! Self-contained operation! (No outdoor aerial needed!) You

can move this receiver, with the self-contained A and B sources and speaker you furnish, into any room—so conveniently—and there she plays, beautifully, clearly!

You will need 135 volts maximum B supply, 22½ volts maximum C bias and a 4½-volt A source, plus speaker, to operate the set. The B supply may be a B eliminator or B batteries. The A supply may be a 4½-volt storage battery. Or you may use a 6-volt storage battery with 5 ohms in series with the negative A battery post. Or you may use six No. 6 dry cells connected three each in series, and the two series pair in parallel. There is plenty of room in the compartment for A battery, dry cells, B batteries and C battery. Another option is a 4½-volt A eliminator and a 135-volt B eliminator to make the set electrified (except for C batteries).

You can check up on the filament voltages by using a 0-6 volt tip jack voltmeter (price, \$2 extra). The voltmeter jacks are on the front panel. The filament voltage for the tubes should be from 3 to 3.3 volts.

The Thirteen Lucky Features!

1 Radiola 28 uses the famous RCA 8-tube Super-Heterodyne circuit which gives remarkable sensitivity, selectivity, volume and quality of reproduction.

2 Unusual selectivity is provided which permits the separation of powerful broadcast stations even when the Radiola 28 is located in their immediate vicinity, this selectivity having been carried to an extremely fine degree by the employment of two stages of tuned radio frequency amplification ahead of the oscillator circuit. Only one control is required for these two tuned circuits, illustrating the extreme manufacturing precision employed on RCA Radiolas.

3 The extreme sensitivity of Radiola 28 makes it possible to receive over great and unusual distances under favorable conditions.

4 Audio frequency transformers have uniform acoustical properties.

5 Ideal for country clubs, lodges, auditoriums or living rooms in the home.

6 The "Uni-Control" tuning mechanism has been grouped in the center of the sloping panel, and is surrounded by a bronze escutcheon plate of fascinating appearance.

7 The rotating loop gives additional selectivity in that it may be turned at right angles to undesired, interfering signals. The loop fits into a specially designed socket.

8 The set is extremely easy to operate. Tuning is accomplished by moving the "Station Selectors," which takes the form of two drums, calibrated in kilocycles. For most purposes, local or distant stations can be tuned in by operating both drums together as a unit, with a finger. The two drums may also be operated separately for extremely fine tuning. Thus we have a radio receiver with true uni-control.

9 Radiola 28 can be readily moved from room to room as no external connections for batteries, aerial or ground are necessary.

10 Station call letters may be marked on the Station Selector Drums.

11 The "Volume Control" provides regulation without detuning.

12 All the parts are enclosed and sealed in a strong metal case or "catacomb."

13 Radiola 28 is equipped with "straight line frequency" condensers. The figures of the station selector drums are spaced 10 kilocycles apart. Each division on the drums corresponds to a broadcast station.

GUARANTY RADIO GOODS CO.

145 West 45th St.

Just East of Broadway

N. Y. City

**GET
RADIO STATIONS
YOU NEVER HEARD
USE THE
CE-LECTOR
A TRUTONE PRODUCT**

**THE ORIGINAL
STATION SEPARATOR**

The Ce-Lec-Tor enables you to tune sharply and get any station regardless of its wave length. It also reduces static and stops aerial interference.

\$6.50 AT ALL DEALERS
If not at your dealer's, write us for circular.

Trutone Radio Sales Co., 114 Worth St. New York City

For Best Results With Your GIANT SIX-1 Receiver

Tune With the HAMMARLUND CONDENSERS

Specified by the Designer



VICTOREEN Super Coils

Write for Free Blueprints of
New Victoreen Circuits

Geo. W. Walker Co.
2825 Chester Avenue
Dept. B Cleveland, O.

Grid Biasing the 250

Here's a real radio engineering job. No use guessing at the resistance value. Use skimp resistors. But apply a 200-100,000 ohm POWER CLAROSTAT and adjust it for best tone quality, and you're all set!

And there are thousands of uses for this and other Clarostats. Ask for literature.

CLAROSTAT MFG. CO., Inc.
291 N. 6th St., Brooklyn, N. Y.

CLAROSTAT

REG. U. S. PAT. OFF.

FAMOUS NATIONAL

Velvet B Eliminator \$16.13
180 Volts (with 230 Tube)



Latest Model National Velvet-B, Type 3580, in handsome crackle finish black metal casing, for use with sets up to and including six tubes. Input 105-120 volts AC, 50 to 60 cycles. Output 180 volts maximum at 35 milliamperes. Three variable output intermediate voltages. (Det., RF, AF). Eliminator has excellent filter system to eliminate hum, including 30 henry choke and 18 mfd. Mershon condenser. No motorboating! (Eliminator Licensed under patents of the Radio Corporation of America and associated companies.)

Guaranty Radio Goods Co.

145 W. 45TH STREET
(Just East of Broadway)
NEW YORK CITY

GUARANTY RADIO GOODS CO. 145 W. 45th St., N. Y. City

Please send C. O. D. on 5-day money-back guarantee, one National Velvet B (180 volts maximum with three variable intermediate voltages), with 230 tube, at \$16.13.

Enclose find \$16.13. Please send above. You are to pay carriage.

Name

Address

City..... State.....

5-DAY MONEY-BACK GUARANTY

Recent Issues of RADIO WORLD, 15 cents each. Any number published in 1928 available for a short while. Six issues 75 cents, 10 issues \$1.00. Send stamps, coin or money order NOW, before the issues are sold. RADIO WORLD, 145 West 45th Street, New York City.

RADIO
BLUEPRINT LIBRARY
AC
HOOK UPS

1929 EDITION

6 Tube Single Control Set
6 Tube Tuned Radio Frequency Set
4 Tube Popular Model Set
6 Tube Screen Grid Set
3 Tube All Wave Set (\$20 to \$50)
B-Eliminator for A-C Current

LYNCH

Television Experimenters: Build a resistance coupled amplifier with the Lynch Audio Amplifier Kit. \$9.00 complete.

ARTHUR H. LYNCH, INC.
1775 Broadway New York City

Send for free book on Resistance in Radio

NEWS to Set Builders


LATEST RADIO GUIDE

Barawik offers set builders bigger bargains—bigger opportunities to make money this season. New sets, new kit ideas, all the leading parts, dynamic speakers, supplies, etc. Lowest rock-bottom prices. Bigger stocks, quicker service. Send for Big Bargain Book today—*free*.

BARAWIK CO., 135A Canal St., CHICAGO, U. S. A.

WHAT RADIO COMPANIONSHIP DO YOU ENJOY?

HIGH RESISTANCE VOLTMETERS

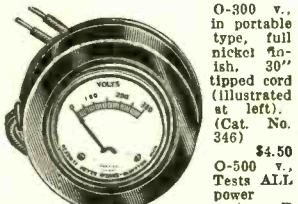

O-300 v. in portable type, full nickel finish, 30" tipped cord (illustrated at left). (Cat. No. 346) \$4.50
O-500 v. Tests ALL power packs. B eliminators. Same casing as above. (Cat. No. 347) \$5.00
Just the thing for service men, custom set builders, home experimenters.

GUARANTY RADIO GOODS CO.
145 W. 45th St., N. Y. City

ARE you meeting weekly the best minds of radio? Do you keep abreast of all the new circuits, the intimate details on perfecting existing sets, and get the inside track on sensitivity, distance reception, tonal quality, and how to achieve them? Do you keep fully abreast of the news of radio, technical and non-technical? If not, here is your chance to enjoy the writings of Dr. Lee De Forest, McMurdo Silver, J. E. Anderson, Herman Bernard and a host of others. You can find no magazine that better caters to your needs than Radio World, which specializes in most intimate revelations of the ins and outs of the best circuits, with technical accuracy second to none. Enjoy the weekly companionship of Radio World's famous contributors, and glean the news of radio, from the four quarters of the earth. Short waves? Radio World will tell you all about them. Extremely sensitive broadcast receivers? Their construction and operation are fully discussed with confident regularity. Power supplies—push-pull or otherwise? AC receivers? Screen grid tubes? Large receivers that give a super-abundance of performance—small, economical receivers that give performance out of all comparison to their size? Are you interested in these? Then you're interested in Radio World. Send \$1.00 now for a ten-week subscription for Radio World (regularly \$1.50), and in addition you will be sent FREE any one of the following panel meters:

- | | |
|--|---|
| <input type="checkbox"/> 0-6 Voltmeter D.C. | <input type="checkbox"/> 0-10 Amperes D.C. |
| <input type="checkbox"/> 0-50 Voltmeter D.C. | <input type="checkbox"/> 0-25 Milliamperes D.C. |
| <input type="checkbox"/> 6-Volt Charge Tester D.C. | <input type="checkbox"/> 0-50 Milliamperes D.C. |

Put a cross in the square next to the meter you desire, and return this slip with one dollar, whereupon we will send you Radio World by mail each week for ten weeks. Present mail subscribers may renew their subscription under this remarkably generous offer by putting a cross in this square. □

15c per copy
\$6 per year

RADIO WORLD
145 West 45th St., New York City

Published
Weekly



Vol XV, No. 8 Whole No. 372

May 11th, 1929

15c per Copy \$6.00 per Year

[Entered as second-class matter, March, 1922, at the Post Office at New York, N. Y., under Act of March, 1879.]

RADIO WORLD

Latest News and Circuits
Technical Accuracy Second to None

EIGHTH YEAR

HOOVER PICKS STARBUCK FOR RADIO BOARD

Washington.

President Hoover has appointed William D. L. Starbuck, patent attorney and engineer, to fill the vacancy in the Federal Radio Commission created on February 23d by the resignation of Orestes H. Caldwell. Mr. Starbuck would represent the First Zone, comprising Maine, New Hampshire, Vermont, Connecticut, Rhode Island, New York, New Jersey, Delaware, Maryland, the District of Columbia, Porto Rico, and the Virgin Islands.

Mr. Starbuck, who is forty-three, lives in Sound Beach, Conn., and practices patent law in New York City. He is a friend of Col. William L. Donovan, former Assistant Attorney General, and was a classmate of Donovan's at Columbia University. Col. Donovan is a warm friend of President Hoover and helped manage the Hoover campaign in New York.

The Senate is expected to confirm the appointment of Mr. Starbuck, Democrat, and also that of Maj.-Gen. Charles McK. Saltzman, Republican, named by President Hoover to fill the vacancy caused by Sam Pickard's resignation as Commissioner. Mr. Pickard went with the Columbia Broadcasting System. With these two appointments filled the Board membership of five would be complete again.

Engineers Preferred

President Hoover by his two appointments to the Board showed a preference for men with engineering training. Saltzman was chief of the Signal Corps, the chief signal officer of the Army, a military engineering post.

Starbuck, born in New York City, attended Drisler and Horace Mann schools and got his master's degree in engineering at Columbia University.

In 1908, Mr. Starbuck began the practice of mechanical engineering in New York, going later to the Middle West, where he continued in that work until December, 1917, when he enlisted in the army as First Lieutenant in the Ordnance Department. He was in France from May, 1918, to March, 1919.

Specialized in Radio

From 1919 to 1921 Mr. Starbuck was connected with the firm of Starbuck & Clapp, New York, and later with several manufacturing companies. In 1921 he began the study of patent law and was admitted to the Federal, New York City and New York State bars in 1925. Since that time he has been engaged in patent law work, specializing in radio.

He is a member of the American Society of Mechanical Engineers, the Royal Society of Mechanical Engineers, London, and the American Legion.

Bill Prohibits Program Piracy

Washington.

Representative Darrow (Rep.), of Philadelphia, Pa., introduced a bill to amend the Radio Act to forbid interception and re-transmission of radio programs without authority of the originating station. The bill, which also prohibits sending of false distress signals, was referred to the Committee on Merchant Marine and Fisheries.

The full text of the amendment:

Section 28. No person, firm, company, or corporation within the jurisdiction of the United States shall knowingly utter or transmit or cause to be uttered or transmitted any false or fraudulent signal of distress or communication relating thereto; nor shall any such person, firm, company, or corporation intercept in the process of transmission and rebroadcast or in any manner retransmit by wire or wireless or by any means record, for the purpose of reproduction, the program, or any part thereof, of another station without the express authority of the originating station."

2 ACTS BECOME CORPORATIONS

Chicago.

WBBM made the following announcement:

"The copyright laws, made to protect the author and artisan of the printed word from having his work stolen by unscrupulous competitors, overlooked radio entirely.

"The broadcaster's spoken word can be repeated at will by other radio announcers, even if an idea or a phrase has been originated and popularized by the first station. There is no protection offered under the copyright laws because they were in existence long before radio was regarded as anything but visionary.

"To protect two very popular features given regularly over the WBBM air Theater, Chicago, they have been incorporated under the laws of the state of Illinois. Officers and a board of directors have been elected for each corporation and they hold regular meetings and must stay on the air in order to maintain their charters.

"The two features are the Nutty Club and the Old Grey Mare Club."

PROSKAUER BROADCASTS

Over WKBQ, Starlight Park, the Bronx, New York City, every Monday night from 8 to 9 o'clock, a series of interesting talks is given on curing noises and other interference. These talks are by Julian J. Proskauer, Associate Member, Institute of Radio Engineers, head of the Trutone Laboratories, 114 Worth Street, New York City.

FOUR STATIONS OUSTED AND 29 ON PROBATION

Washington.

Four stations were ordered off the air by the Federal Radio Commission for failing to justify their existence. The stations were WHBW, Philadelphia; WSMD, Salisbury, Md.; WSRO, Middletown, O., and WAAD, Cincinnati, O. The Commission found that public interest, convenience and necessity would not be served by granting a renewal of their licenses.

Fourteen stations were put on probation for forty-six days for serious frequency deviation, and fourteen others were treated likewise because of creating interference.

The twenty-ninth station put on probation was WOBU, Charleston, W. Va., this one for 30 days, for removing its transmitter without first having obtained permission.

All the other stations—about 600—obtained unconditional renewal of licenses for 90 days, or until July 31st. The conditional or probationary renewals carry a threat of license forfeiture if the situation complained of is not remedied or perfect conduct proven to exculpate a past violation.

Four Cancellations

Licenses were outright refused to:

WHBW, operated by D. R. Kienzle, Philadelphia, Pa., on 1500 kc with 100 watts power, sharing time with WALK and WPSW.

WSMD, operated by Tom Little, Salisbury, Md., on 1310 kc with 100 watts power.

WSRO, operated by Harry W. Fahrlander, Middletown, Ohio, on 1420 kc with 100 watts power, sharing time with WAAD.

WAAD, operated by Ohio Mechanics Institute, Cincinnati, Ohio, on 1420 kc with 25 watts power, sharing time with WSRO.

14 Wave Wobblers

Serious deviation from frequency, with failure to correct after warning, brought a conditional renewal for 46 days of the licenses of the following:

KFWI, Radio Entertainments, Inc., San Francisco, Calif.

KGFJ, Ben S. McGlashan, Los Angeles, Calif.

KFQW, Inc., Seattle, Wash.

KGER, C. Merwin Bobyns, Long Beach, Calif.

KGGC, Golden Gate Broadcasting Co., San Francisco, Calif.

KOL, Seattle Broadcasting Co., Seattle, Wash.

KMO, Inc., Tacoma, Wash.

KPQ, Archie Taft & Louis Wasmer, Seattle, Wash.

KGA, Northwest Radio Service Co., Spokane, Wash.

WAGM, Robert L. Miller, Royal Oak, Mich.

KWTC, Pacific-Western Broadcasting Federation, Santa Ana, Calif.

WICC, Bridgeport Broadcasting Station, Easton, Conn.

WOKO, Harold E. Smith, Mt. Beacon, N. Y.

KFBL, Leese Bros., Everett, Wash.

POLL OPPOSES USE OF TAINTED TESTIMONIALS

The National Better Business Bureau has conducted a poll among national advertisers and advertising agencies regarding the use of purchased testimonials. These endorsements are not only used in printed advertisements but in occasional instances are read over the air. The advertising agencies arrange those parts of the program having to do with the reading of purchased testimonials, and also place the contract for time on the air, for which they are paid a commission by the stations that receive the contract.

The poll gave the following results:

| | Against | For |
|---------------------------|---------|-----|
| National advertisers..... | 700 | 41 |
| Advertising agencies..... | 149 | 14 |
| Totals | 849 | 55 |

Practice Widespread

An analysis by the Bureau showed that purchased testimonials were widely used through the scope of advertising and were not limited to one advertiser or to a single industry.

"The promptness of reply and the large percentage of returns from our questionnaire," says the Bureau, "very definitely demonstrated the seriousness with which the abuse of purchased testimonials was criticized."

"A summary shows an overwhelming percentage who disapprove. The opinion as expressed is added to by trade and newspaper comment, supplemented by cartoons and wise cracks from professional jesters."

"Add to that the sleeve-laughing that is going on by many well-paid testifiers who, from their own experience, must believe that the advertising business is dependent upon deception for success and supplies these insincere testifiers with a lucrative 'racket.'

Food Men Attack Practice

The National Food Protective Committee recently petitioned the Federal Radio Commission to revoke the licenses of thirty-eight stations on the National Broadcasting Company's chain that broadcast the "Lucky Strike" program each Saturday night, one ground being that "tainted testimonials" were read over the air, the testifiers being heroes and heroines in the eyes of youth, and their testimonials being calculated to make young boys and girls become cigarette addicts.

The petition also said that lists of names of famous persons are available, with the price of a testimonial after each name, and that all an advertiser has to do is to pay the price and obtain a testimonial for any product. It was hinted Lucky Strike cigarette manufacturers simply bought endorsements in this way.

RCA QUITS VICTOREEN SUIT

Cleveland, O.

The injunction suit of Radio Corporation of America against the George W. Walker Company, of 2825 Chester ave., Cleveland, merchandisers of Victoreen products, alleging infringement of patents involving the Super-Heterodyne manufacture parts for use in a circuit which is famous as the Victoreen.

The George W. Walker Company manufacturers parts for use in a circuit which is famous as the Victoreen.

Esquimo Wants Arctic Shoe Store

Chicago.

A shoe company broadcast programs from WBBM and asked listeners to answer the question: "Why I want a store in my neighborhood," intended for Chicago people.

Out of 8,000 letters from listeners there were some from practically every State in the Union, and some from Canada. Also, an Esquimo asked where the nearest store was, so he could buy a pair of snow shoes.

50,000 WATTS GIVEN TO WTAM

Washington.

Authority to construct a broadcasting station capable of using the maximum allowable power of 50,000 watts was granted by the Federal Radio Commission to WTAM, at Cleveland, Ohio.

The Commission, it was stated, has granted the station a construction permit to erect the new station outside of Cleveland, and to "reconstruct," and "move" as well as to increase its power. WTAM, operated by WTAM & WEAR, Inc., at present is authorized to use 3,500 watts on the 1,070 kilocycle channel. Station WEAR, which it also owns, operates on the same channel with 1,000 watts.

There are now only half a dozen 50,000 kilowatt stations in operation in the United States, it was explained, although construction permits have been issued to a number of stations to build transmitters of this output. The authority to WTAM to construct a transmitter of 50,000 watts does not include authorization to broadcast with this power. Under Commission regulations, a separate order must be issued.

Ohio has one 50-kilowatt transmitter in operation. WLW, operated by the Crosley Radio Corporation at Cincinnati. Commission records show that since this station has used the maximum power it has been heard practically throughout the country, says "The United States Daily."

Commission regulations also specify that the maximum actually allocated power to a broadcasting station must be 25,000 watts but provides that additional power up to 25,000 watts may be authorized experimentally.

Victor-RCA Merger Goes Into Effect

The Radio-Victor Corporation of America has been formed as a wholly-owned subsidiary of the Radio Corporation of America.

The new company, incorporated under the laws of Maryland, will take over the sales activities of the radio corporation and the Victor Talking Machine Company.

More than 99 per cent of the common stock of the Victor Talking Machine Company has been deposited by Victor stockholders pursuant to the unification plan announced last January.

On the board of directors are representatives of the General Electric Company, Westinghouse Company, and Radio Corporation of America, including H. P. Davis, General Harbord, Owen D. Young, Gerald Swope and David Sarnoff.

MOVES CHICAGO OFFICE
The Chicago office of the DeJur-Amsco Corporation has been moved from 77 West Washington Street to the Wrigley Building. William E. Burgoyne is in charge.

9 MORE SEEK LICENSES FOR NEW STATIONS

Washington.

Applications as follows were received by the Federal Radio Commission, including nine applications for new stations:

New station. Idris J. Jones, Birmingham, Ala. Requests authority to erect a station using 6,000 or 5,000 kilocycles (short waves) with 15 to 150 watts power.

New station: Proffer Bros. Battery Station (H. R. and C. R. Proffer), Dexter, Mo. Requests authority to erect a station using 967 kilocycles, 75 watts power and daylight hours only specified.

New station, Abe Cohen, Lynchburg, Va. Requests authority to erect a station using 1,000 kilocycles with 100 watts power and to operate from 1 p. m. to 12 p. m.

New station, Harold Ralph Jones, Chanute, Kans. Requests authority to erect a station using 250 watts power, 1,200 kilocycles and unlimited time.

College Seeks Station License

New station, Radio College of California, Los Angeles, Calif. Requests authority to erect a station using 1,500 kilocycles, 250 watts and unlimited time. (Radio College of California, owned by H. A. McGougal and J. A. Finney).

WRBJ, Woodruff Furniture Co., Inc., Hattiesburg, Miss. Requests change in frequency from 1,500 kilocycles to 1,420 kilocycles, increased power from 10 watts power to 100 watts power.

WREN, Jenny Wren Company, Lawrence, Kans., requests permission to move from Lawrence, Kans., to outskirts, and increased power from 1 kilowatt to 5 kilowatts.

New station, Robert Allyn Sapp, Denton, Texas. Requests authority to erect a station using 100 watts power, 1,240 kilocycles, and unlimited time.

New Station, Symons Broadcasting Company, Great Falls, Mont. Requests authority to erect a station using 1 kilowatt power, 570 kilocycles, full time for day, divide with KXA after sunset each half hour.

New Station, The Gas Engine & Elec. Co., Inc., Columbia, S. C. Requests authority to erect a station using 1,310 kilocycles with 150 watts power and daytime hours specified. This station filed a previous application in the name of Station Radio Distributors Radio Branch of the Gas Engine & Electric Co., Charleston, S. C.

Alabama Petition

New Station, Reynald's Music House Co., Mobile, Ala. Requests authority to erect a station using 1,200 kilocycles with 50 watts power and four hours daily and one evening hour.

WIOD, Isle of Dreams Broadcasting Co., Miami Beach, Fla. Requests increase in power from 1 kilowatt to 2½ kilowatts on 560 kilocycles and unlimited time were granted on April 12, 1929, also 1 kilowatt day, 500 watts night and 500 watts night additional for experimental purposes.

KIDO, Boise Broadcasting Station, Boise, Idaho. Requests change in frequency from 1,250 to 1,220 kilocycles.

Stations Barred from the Argentine Cities

A decree passed in Argentina prohibits broadcasting stations within city limits.

Stations now within cities must move outside within nine months. Special provisions regarding wavelengths and other changes have also been adopted.

A. P. TO PROBE SENDING NEWS OVER STATIONS

Newspaper publishers are at odds over the broadcasting of news. Some think it should be prohibited, as the public learns the latest news more quickly by radio than from the press, and, satisfied that it has been sufficiently informed, is discouraged from reading newspapers.

Other publishers contend that the broadcasting of news merely whets the appetite for complete details, which the stations do not furnish, but which are published in the newspapers.

Discussed at Meeting

The question came up at the twenty-ninth annual business meeting of the Associated Press. On motion of Josephus Daniels, of the "News and Observer," Raleigh, North Carolina, the directors of the Associated Press were called on to make a general survey of conditions and report to the 1930 meeting. Mr. Daniels was Secretary of the Navy in the Wilson administration.

Victor F. Ridder, speaking as publisher of the "St. Paul Dispatch," moved that the directors, who had authorized limited chain broadcasting, be asked to eliminate from the chain all stations in any city in which an Associated Press member objected to the broadcasting. This motion was lost and Mr. Daniels' motion, offered as an amendment, was carried.

Public News-Hungry

The afternoon newspapers were particularly interested in the subject, as they feature "flash" news in many instances as circulation pullers, these "flashes" or "bulletins" often not being much more comprehensive than the broadcast details of the same news.

Kent Cooper, general manager of A. P., said there had never been such a hungering for news on the part of the public as there is to-day.

Two New Volumes

by Rider Published

Two books by John F. Rider for the radio service man are announced by the Radio Treatise Co., 1440 Broadway, New York City. They constitute a series entitled "The Service Man's Manual."

The first volume entitled "The Mathematics of Radio" explains radio phenomena in a practical manner, with examples of calculation.

The second volume, entitled "The Trouble Shooting Manual," contains the diagnosis of receiver systems, RF amplifiers, eliminators, etc. Trouble shooting in these systems with commercial set testers and analysis of symptoms.

It Can't Be Accidental!

Radio World sells each month more copies than are sold in the same period of time by any other radio publication in the world—bar none.

Radio World's subscription list has increased faster during the past four months than during any other period of its existence.

One company controlling a few hotel and railroad newsstands in the West has added 495 copies to its order.

Son Born as Papa Plays Piano on Air

San Francisco.

Lon Protteau, one of "The Three Boys of KGO," learned he had just become a father while playing over the station the other morning. He became so excited when Charles Park, KGO announcer, whispered the glad tidings to him that he didn't know which end of the piano was the bass.

"I'm Walking Around in a Dream" was played over the air by Protteau for his wife, who was separated from her husband by the San Francisco Bay. A loudspeaker along the side of the bed at home enabled mother and son to listen in.

NO MISTAKES BY ANNOUNCER?

The National Broadcasting Company will expand its efforts to perfect the art of announcing.

George Engles, vice-president, director of the Program Department, said that experts in various specialized subjects will be called in to assist in this effort. Authorities on art, music, science and the like will supplement the general knowledge of announcers, so that absolute accuracy in the use and pronunciation of technical terms may be insured.

"The requirements of the company in engaging its announcers are extremely stringent," said Engles. "All of the announcers have more than the average amount of information on many subjects covered by broadcasting. The company demands a high standard of education and culture, as well as the ability to speak correctly.

"However, with the spotlight of public attention focused so strongly upon radio announcers, particularly by the American Academy of Arts and Letters, we realize that absolute perfection is necessary. Radio announcers are now expected to set the standard of public usage. If they are to be entirely worthy of public confidence they must never make a mistake."

"We realize that no one person can be infallible on every subject. It takes an authority on music to know the exact use and pronunciation of all terms relating to music. The same is true in the case of art and science. Even so, authorities themselves sometimes disagree. There must be someone to have the deciding word. Such experts will be engaged to act in an advisory capacity to the announcers."

Engles said that the company has recently inaugurated an intensive training course in speech for its announcers. Each week the entire staff of announcers meets with Miss Vida Sutton for advanced coaching in diction and the use of the voice. Miss Sutton is director of the speech department at the Theater Guild's School for the Young Actor.

"The course," said Engles, "is designed to do away with localisms, individual mannerisms and the metallic quality often existing in American speech. In this connection announcers will be given the opportunity to hear how their voices come over the air—to see just how the quality is recorded by the microphone and loudspeaker. They are given special exercises for resonance, articulation and breath control. Bodily exercises supplement the vocal exercises since coordination of body and voice are so interrelated."

Milton J. Cross, NBC announcer, recently won the Academy's diction medal.

RADIO AFFORDS \$400,000,000 ANNUAL WAGES

Washington.

The status of the radio industry has been assayed by a Commission appointed by President Hoover. It has been found that the industry is, in general, in a healthy condition, that close to 350,000 persons are employed in it, and that the annual turnover is around a billion dollars.

The Department of Labor has made a separate survey that includes the radio industry. The average wage in the industry has been put at \$25 a week. Multiplying the 350,000 employes by the average wage, the total wage for the industry amounts to \$8,750,000 per week, or more than \$400,000,000 a year.

Receivers Popular

The receiving set has become vastly popular. Starting in 1921 with 50,000, the number has increased to around 10,000,000.

The employment in the industry is analyzed on the general basis of activities in or association with radio, and includes not only the factory workers and their executives, but also persons employed in studios, even if in a clerical capacity, and of course includes service men and others employed by retail stores, jobbers, etc.

Greater Stability

In some branches of the radio field the demand is greater than the supply, it has been found, while in other branches a condition of overcrowding exists.

A general trend toward better stability is noted, particularly associated with continued activities during the Summer. Many factories will continue in operation during 1929 without interruption for the first time in their history.

Ce-Lec-Tor Is Newest Station Separator

The Ce-Lec-Tor, the newest and most modern type of station separator, embodying the band-pass filter system together with the best principles heretofore known for the cutting apart of interfering stations, is now ready for immediate shipment. Factory facilities have been expanded to take care of the Ce-Lec-Tor output and there will be no slackening on this account in the production of the Si-Len-Ser, which is in greater demand than ever.

These two devices were designed by Julian J. Proskauer, head of the Trutone Radio Sales Company and director of their laboratories. Further information may be had from this concern by addressing their main office at 116 Worth Street, New York City. Mention RADIO WORLD.—J. H. C.

Lynch Appoints O'Neil

Arthur H. Lynch, Inc., 1775 Broadway, New York City, announced that J. F. O'Neil has become general manager.

Mr. O'Neil was for eight years Superintendent of Agencies for the Curtis Publishing Company before going with a tube company. O'Neil will have charge of a group of Lynch sales experts in all parts of the country.

Mr. O'Neil is well known among New York, New Jersey and Pennsylvania jobbers.

Why Neutralize Audio?

Prevents Plate-Grid Capacity Cutting High Notes

By Herbert E. Hayden

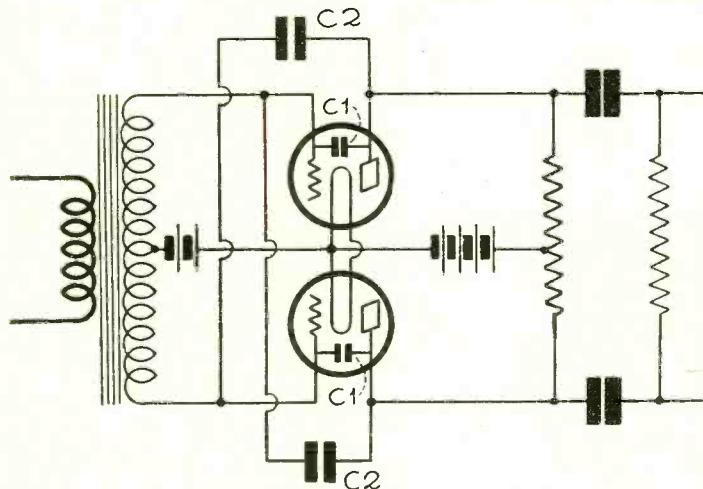


FIG. 1

A PUSH-PULL STAGE USING RESISTANCE COUPLING IN WHICH NEUTRALIZING CONDENSERS C2 ARE USED TO COUNTERACT THE FEEDBACK THROUGH THE GRID-TO-PLATE CAPACITIES C1.

RESISTANCE coupled amplifiers are said to amplify signals of all frequencies equally well. Of course, this is only relatively true. There is a certain amount of discrimination at both ends of the audio scale. At the low frequencies the stopping condensers reduce, and at the high frequencies the plate to grid capacity reduces the amplification.


It is not difficult to design a resistance coupled circuit so that it will amplify the low frequencies as low as required. It is only necessary to increase the size of the coupling condenser, or, for a fixed value of coupling condenser, to increase the resistance value of the grid leak which follows the condenser.

It is not so easy to bring up the amplification at the high frequencies, for the cause of the suppression is not controllable. For a high voltage step-up the plate resistance in the output of the tube should be large. But as this resistance is increased the effective value of the input capacity increases greatly, and the greater is the suppression on the high notes. That is, the increase of the plate output resistance increases only the amplification on the low and medium notes. Hence the larger the value of the plate resistance, the poorer will the quality be.

What happens is that the amplified signal is reflected back from the plate to the grid in such phase as to oppose the input voltage on the grid. The feedback takes place through the grid to plate capacity.

Neutralization in Push-Pull

If the circuit has two tubes or more it is possible to neutralize the feedback by a method used in the early resistance coupled radio frequency amplifiers. A small condenser is connected between the grid of the first tube and the plate of the second. The potential of the plate of the second tube is in the same phase as the grid of the first. Hence the feedback through the grid to plate capacity may be counteracted by the feedback from the second plate to the grid of the first. This condenser must be smaller than the grid to plate capacity, since the signal has been amplified by two tubes. In fact, the condenser would have to be extremely small to prevent oscillation.

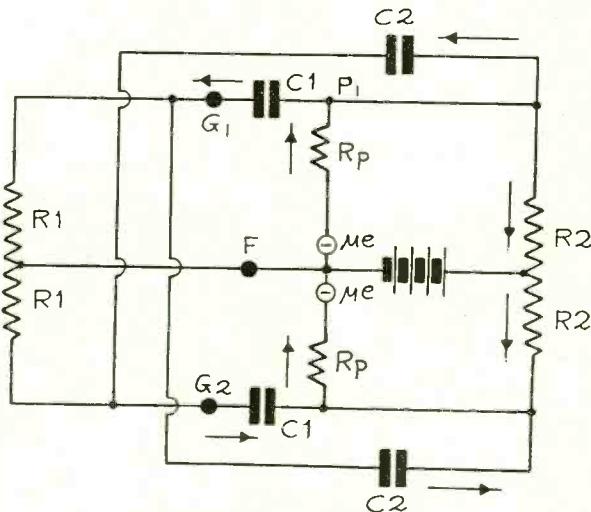

A SIMPLIFIED CIRCUIT DIAGRAM OF A PUSH-PULL RESISTANCE COUPLED AMPLIFIER. MID-TAPPED RESISTOR IS USED FOR INPUT IN PLACE OF THE PUSH-PULL TRANSFORMER SECONDARY.

If the audio amplifier is push-pull, it is possible to neutralize the plate to grid capacity in a single stage. This has been done in many short wave receivers, but not in audio amplifiers. Perhaps the reason is that push-pull resistance coupled amplifiers have not gained much popularity.

Fig. 1, left, shows the first stage of a resistance coupled push-pull amplifier. It is supposed to be adjusted so that it is perfectly symmetrical with respect to the filament. This means that the tubes are exactly the same and that the voltages and the corresponding coupling impedances are equal.

Each tube has its own plate to grid capacity indicated by C1. These capacities work in both tubes so as to reduce the amplification on the high notes. Now, the grids at any instant are at the same absolute potential but in opposite phase. That is, when one is V volts positive with respect to the operating point, the other tube is V volts negative with respect to the same point.

Plates in Opposite Phase

Since the grids are in opposite phase the plates are also in opposite phase. But the potential of the plate of one tube is in the same phase as the potential of the grid of the other. Therefore if two small condensers C2 be connected diagonally across the circuit from grid to plate the effect of the feedback through the plate to grid capacity in either tube will be neutralized.

For example, the plate of the upper tube feeds a certain amount back to the grid of that tube through the upper C1 and at the same time the plate of the lower tube feeds an equal amount to the upper grid through the lower C2. The amounts of voltage fed back to the upper grid are equal, or may be made so, but opposite in phase. Hence the feedback does not change the signal voltage on the grid of the upper tube.

The same applies to the lower tube. In this case the upper C2 and the lower C1 feed voltage to the lower grid.

Simplified Circuit

It will be observed that as far as the feedback is concerned the plate of each tube is connected through a small condenser to both sides of the input device. Therefore there can be no feedback.

The right hand diagram in Fig. 1 shows the same circuit in a simplified form. In this circuit the tubes have been replaced by equivalent elements, namely, the fictitious voltages ue, the internal plate resistances Rp and the plate to grid capacities C1. Grid-to-filament resistances and the inter-element capacities other than C1 have been omitted. Also the secondary of the transformer has been replaced by a center-tapped resistor having a total value of 2R1.

When this type of input is used, another resistance enters into the circuit in parallel with 2R1, and that is the plate resistance of the tube ahead. But that resistor is balanced with respect to the feedback as well as is the center-tapped resistor.

The arrows in the lower circuits indicate the directions of the various currents which establish the potentials across the impedances. When arrows point to an element, such as the grid G1, the potential at that point may be considered to be rising, and when the arrows point away from a point the voltage may be considered as falling. It will be seen that on grid G1 the arrow for C1 points to the grid and the arrow for C2 points away. Thus if the two condensers involved pass the same current, there is no tendency for the potential to change as far as the feedback is concerned.

The push-pull amplifier does not suppress the high notes so much as a single-sided circuit composed of similar elements because the equal grid-to-plate capacities are in series, and therefore only one-half as great, effectively, as in the single tube stage. Hence it is not necessary to neutralize the capacities except when the high audio and superaudible notes must be amplified as well as the low audio notes. Receivers used for television reception require a band about 50,000 cycles. This is much wider than any ordinary audio amplifier is able to cover.


When the neutralizing condensers are used they should be small variable condensers such as are used for trimming tuning circuits in broadcast receivers. The plate-to-grid capacity in an ordinary high mu tube is of the order of 10 mfd., so that the neutralizing condensers should be of this size. That is, condensers which has a lower minimum than this should be used.

A New Self-Stabilizer

Oscillation in RF Channels Efficiently Controlled Automatically

By Herman Bernard

Managing Editor

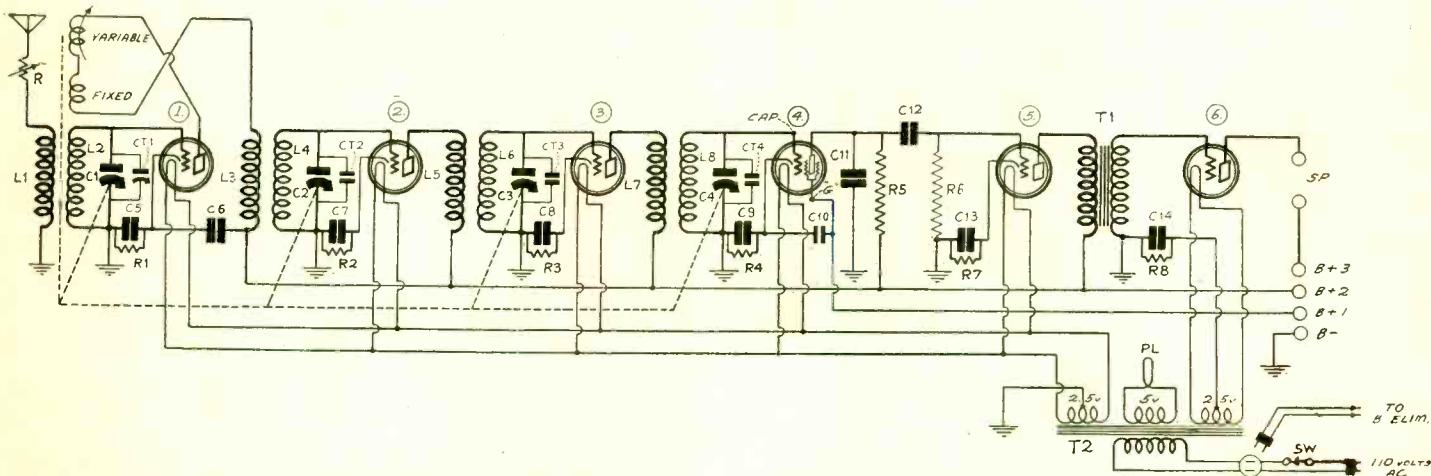

AN AC CIRCUIT, USING THREE STAGES OF TUNED RADIO FREQUENCY AMPLIFICATION, STABILIZED BY MEANS OF NEGATIVE FEEDBACK, VARIED AUTOMATICALLY BY MECHANICALLY COUPLING THE TICKLER SHAFT TO THE CONDENSER SHAFT. IF FEEDBACK IS TOO GREAT IN EITHER POSITIVE OR NEGATIVE DIRECTION THE TICKLER COIL MAY BE ADJUSTED TO COMPENSATE FOR THIS, OR AN EXTRA WINDING MAY BE PROVIDED (MARKED "FIXED"), AND MADE NEGATIVE OR POSITIVE, AS CIRCUMSTANCES REQUIRE.

THE advisability of using multiple stages of tuned radio frequency amplification, for the resultant sensitivity and selectivity, is generally recognized, but some means must be introduced to stabilize the receiver. Every such means introduces some loss, no matter what system of neutralization is used, but it is a gainful loss, since otherwise the receiver would be virtually inoperative. A parallel example is that of a driver of an automobile when he reaches the top of a steep hill with railroad tracks ahead. He puts on the brakes, to avoid nearing the tracks at an uncontrollable speed that might render him and the automobile permanently inoperative. This braking is a loss, but the kind of a loss one is glad to endure, since it enables life. The same is true in the receiver. Without stability it is as good as dead.

Various methods of stabilizing a receiver at radio frequencies work out satisfactorily, including grid suppressors connected from stator of a tuning condenser to grid of a socket, neutralizing condensers that establish a capacity equal to the self-capacity of the tube, but with negative feedback to neutralize the positive feedback caused by that internal capacity, high negative bias on radio amplifiers, and the like.

Interesting Subject

As self-oscillation is usually most troublesome on the higher broadcast frequencies, and as some method of increasing the resistance is always employed, it follows that a receiver balanced for the troublesome frequencies will be a little less sensitive on the lower frequencies (higher wavelengths). Therefore some method that changes the resistance in the right direction, lowering it for the lower frequencies, is an interesting subject of investigation.

The method proposed is a new one, and consists of using a rewound three-circuit coil, so that the primary is in the antenna circuit, the secondary in the grid circuit,

and the tickler in the plate circuit of the first tube, but the tickler is used at least in part for reverse feedback. Either the tickler alone may be used, or a small extra winding may be put on the coil form at the end opposite to the one accommodating the primary or on a separate inside form, and this small winding may be connected in series with the tickler.

The control of self-oscillation becomes complete when the inductances are properly proportioned and the shaft of the rotating coil is coupled to the shaft of the gang tuning condenser. A Hammarlund flexible coupler will do this, if the tuning condenser has a part of its shaft protruding from the far end.

How It Works Mechanically

The mechanical operation then is as follows: As the tuning dial is rotated from lowest to highest frequency in the broadcast band, that is, from 100 to 0 on most dials, the tickler coil turns with the condenser. If the phases are correctly established, by exercise of knowledge and care in connection of coil terminals, the positive feedback will decrease as the frequency increases, due to automatic rotation of the tickler. This change is accomplished through the tuning mechanism itself.

The results will differ depending on how the tickler is originally positioned. If at lowest frequency (100 on the dial) the coupling is made full positive, by paralleling the tickler with the secondary and having equal potentials in relatively the same position, there will be positive feedback. Under some circumstances this will work out well. If the circuit is not keyed up too high, that is, has not a terrific attribute of feedback, the positive regeneration will be useful. As the higher frequencies are tuned in the feedback reverts to zero, at the numerical center of the dial, and then turns negative in the region where the greater incurred resistance is needed.

If this arrangement is properly pro-

portioned, there will be positive feedback to aid the sensitivity and volume on the lower frequencies, thus tending to atone for the rising characteristic of tuned radio frequency amplification where the amplification is greater the higher the frequency, and at the same time contributing a variable resistance factor that spares the loss introduced on the high frequencies from affecting the low frequencies where it is not wanted. In fact, as explained, instead of the loss being merely eliminated for the low frequencies, a gain is actually provided. However, this almost ideal condition is hard to attain, since critical regeneration is a function of both the frequency and the volume, and satisfaction of both requirements introduces technical difficulties of a high order.

Simpler Method

Therefore a simpler method may be used by anybody, and good results obtained, since if the first tube is prevented from oscillating there is seldom any trouble from subsequent tubes in the cascaded chain. This simpler method is to put the tickler in a parallel position with the secondary, when the condenser plates are totally out of mesh, and to join the coil terminals to their destinations in reverse feedback fashion. This consists of noting where the grid is connected on the secondary and then connecting the plate of the first tube to that terminal of the tickler which occupies exactly the opposite position. Assuming both windings in the same direction, this means that if the beginning of the secondary goes to grid, the end of the tickler goes to plate. The other terminal of the tickler may be connected experimentally to the terminal of L3 that otherwise would have gone to plate.

[Further discussion of this interesting method of introducing stability in the radio frequency amplifier without incurring undue losses will be published next week in the May 18th issue.]

New Theory Propounds Calls for Infinite

By J. E.

Technical

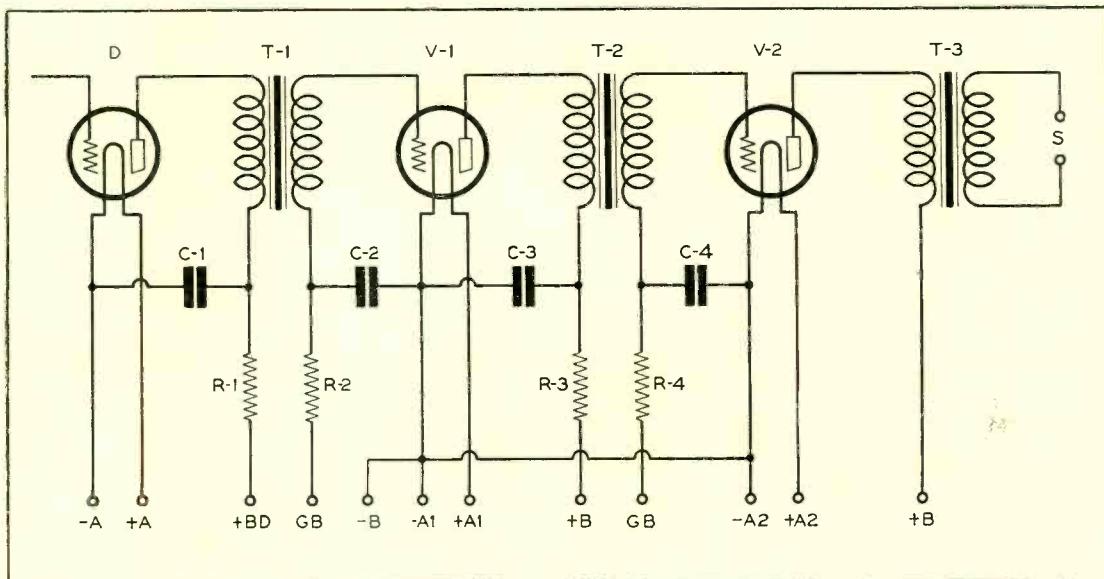


FIG. 1
A DIAGRAM OF A FERRANTI AUDIO AMPLIFIER SHOWING HOW RESISTANCE-CAPACITY FILTERS SHOULD BE USED TO PREVENT REGENERATION.

WHAT are the conditions for obtaining maximum power output from a tube when the speaker is coupled to the tube by means of a transformer? Should the primary impedance of the transformer be equal to the plate resistance of the tube, as has been asserted countless times? Should the primary impedance be equal to twice the value of the plate resistance of the tube, which is asserted to be the condition for maximum undistorted power output? Or should the primary impedance of the transformer be as large as possible, as is asserted by Ferranti engineers? The as-

sertion of these engineers is rather startling and the question is whether it works out in practice.

Problem Complex

The problem is not at all simple, because there are so many factors that enter into the determination of the optimum conditions. Many assumptions have to be made regarding the properties of the transformers, and they are only approximately true. Also, there is much doubt about the impedance of the loudspeaker, for it varies not only with the frequency

but also with the electrical location of the speaker.

It may be shown that the total power, that is, both the active and the reactive, may be expressed $(u E M w)^2 Z^2 / (Z_1 Z_2 + M^2 w^2)$, in which u is the amplification constant of the tube, E the effective value of the input voltage on the grid, M the mutual inductance of the coupling transformer between the tube and the speaker, w the frequency multiplied by 6.28, and Z_2 the total impedance of the secondary circuit.

Assume that there is no leakage inductance, an assumption justified for most

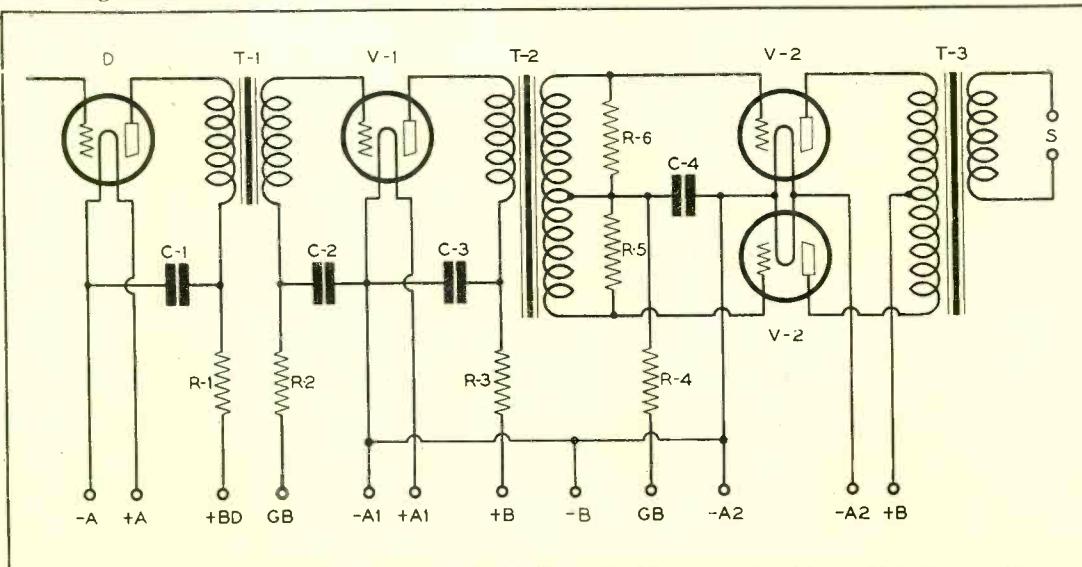


FIG. 2
FERRANTI AUDIO AMPLIFIER CONTAINING A PUSH-PULL STAGE, SHOWING HOW THE RESISTANCE-CAPACITY FILTERS SHOULD BE CONNECTED TO STOP REGENERATION.

ded for AF Transformer Load Impedance

Anderson

Editor

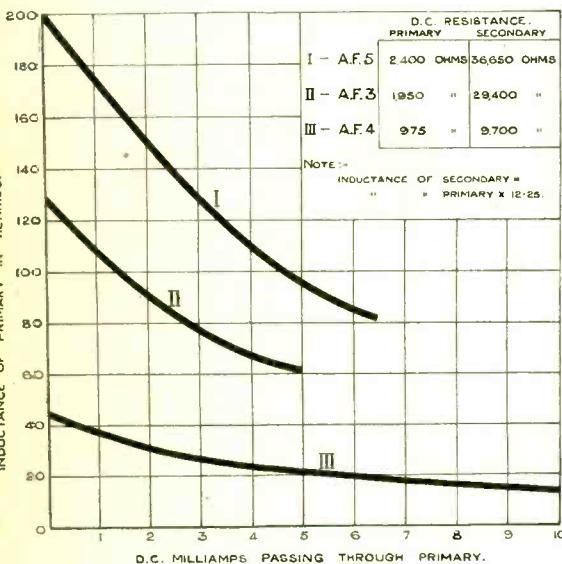


FIG. 3,

HOW THE INDUCTANCE OF THE PRIMARY OF THE FERRANTI TRANSFORMERS VARY WITH THE AMOUNT OF DC.

transformers. Then M_2 may be expressed as $L_1 L_2 w^2$, where L_1 and L_2 are the primary and the secondary inductances. When this value is substituted in the above expression for the power, and noting that Z_1 equals $R_1 + jwL_1$, it will be seen that the power increases as $L_1 w$ increases. This is because as $L_1 w$ increases it becomes large compared with R_1 .

The larger the primary impedance of the transformer, the smaller is the primary current. Thus the losses in the plate resistance decrease, and a greater proportion of the total available power is delivered to the transformer to appear as useful power in the secondary.

Lower Power Loss

As the primary current decreases by virtue of the increase of the primary impedance, the losses in the transformer decrease rapidly, thus leaving more for useful work in the secondary circuit.

A sample of the results obtained by the Ferranti engineers on a dynamic speaker at 50 cycles will suffice to show how the power increases with the increase in the primary impedance. The tube used had a plate resistance of 2,000 ohms, the speaker resistance was 4 ohms and the transformer ratio was 25-to-1. The results at 50 cycles are given:

| Primary impedance in ohms | Secondary impedance in ohms | Speaker power in milliwatts |
|---------------------------|-----------------------------|-----------------------------|
| 2,000 | 3.2 | 128 |
| 4,000 | 6.4 | 135 |
| 19,000 | 30.2 | 136 |
| Infinite | infinite | |

Of course, the infinite impedance condition cannot be obtained, but it is not necessary, for at 19,000 ohms the power is less than one per cent lower than the theoretical maximum.

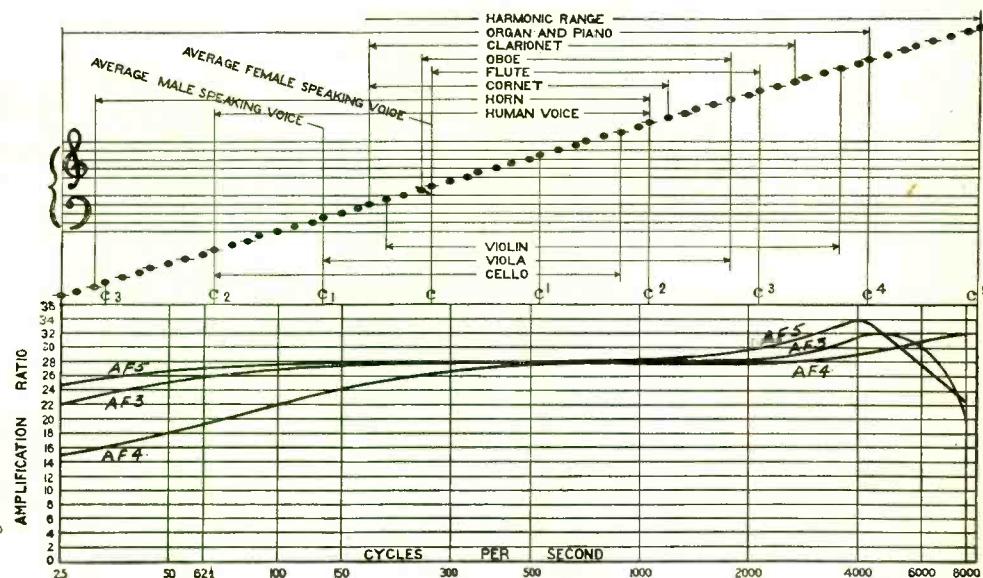


FIG. 4
PERFORMANCE CURVES OF THE FERRANTI TRANSFORMERS COMPARED DIRECTLY WITH THE MUSICAL SCALE.

The ratio of turns also affects the power output. This is due to matching of the loudspeaker impedance with the secondary of the transformer. In the example cited above the ratio of turns is 25-to-1 and the power is 135 milliwatts. If the ratio of turns be decreased to 20-to-1 the power is reduced to 131 milliwatts and if the ratio be increased to 30-to-1 the power drops to 128 milliwatts.

Filtering Well Done

The Ferranti engineers have also delved into the question of regeneration in audio frequency amplifiers and devised methods for rendering it ineffective. One of the circuits recommended by them is shown in Fig. 1. This circuit is for battery operated tubes. It will be noted that there is a resistance-capacity filter in every grid and every plate circuit. The condenser in each instance goes direct to the filament, while the resistor is placed in series with the plate or grid return lead below the condenser. This effectively reduces feedback to a point where it will not cause oscillation or even slight frequency distortion.

While no filter is shown in the last stage, it will not hurt to put a large condenser from the B plus terminal of the output transformer to the negative end of the filament.

In Fig. 2 is shown the filtering treatment given a circuit having a push-pull output stage. The arrangement of the resistors and the condensers is the same.

Condenser C4 serves both the tubes in the last stage. So does resistor R4. In a push-pull stage which is well balanced the need of a filter either in the grid or the plate circuit is not so great as in a single-sided circuit. But it is well to

use filters just the same, for there is often a considerable unbalance in a push-pull stage.

Effect of DC

Coupling transformers having iron cores do not have the same impedance under all conditions. For example, if a direct current is flowing in the primary, the resistance drops to a much lower value than when no direct current is superposed on the alternating current. Fig. 3 shows how the primary inductances of three Ferranti transformers vary with the DC through the winding.

These curves indicate that for low impedance tubes AF-4 is suitable because its inductance does not decrease rapidly with the current. Its low impedance is offset by the low impedance of the tube with which it is used.

For tubes of higher impedance, and for circuits in which the plate current is low, the AF-3 and the AF-5 are superior. The amplification will be much greater than when the AF-4 is used, especially on the bass notes. These facts are clearly shown on the experimental curves in Fig. 4.


The curves are plotted on an octave scale and directly above the curves is plotted the musical scale and the frequency ranges of the various musical instruments. Note that the transformers have practically straight lines over the entire musical scale. The curve for AF-5 is particularly attractive. It shows an amplification of nearly 25 at 25 cycles and a little over 22 at 8,000 cycles. The peak at 4,000 cycles shows an amplification of 34, which is only about .8 decibel above the amplification at 1,000 cycles. The smallest intensity difference the human ear can distinguish is about 1 decibel.

THE choice of an audio frequency amplifying channel is something deserving of thoughtful attention, because no matter how excellent may be the radio frequency channel of a receiver, the reproduction may be impaired or ruined in the audio circuit. No matter how the radio amplifier is made, nor what circuit it is, it can not improve quality of tone. If improperly made, voltaged or operated, it may injure tone quality. It can harm tone, never help it. Therefore if any succor is to be had, it must be in the audio channel.

For selectivity and sensitivity we depend on the radio amplifier. For tone values we look alone to the audio channel. Since all of us are supremely interested in

A Quality A a Sound Investm

By H. B.

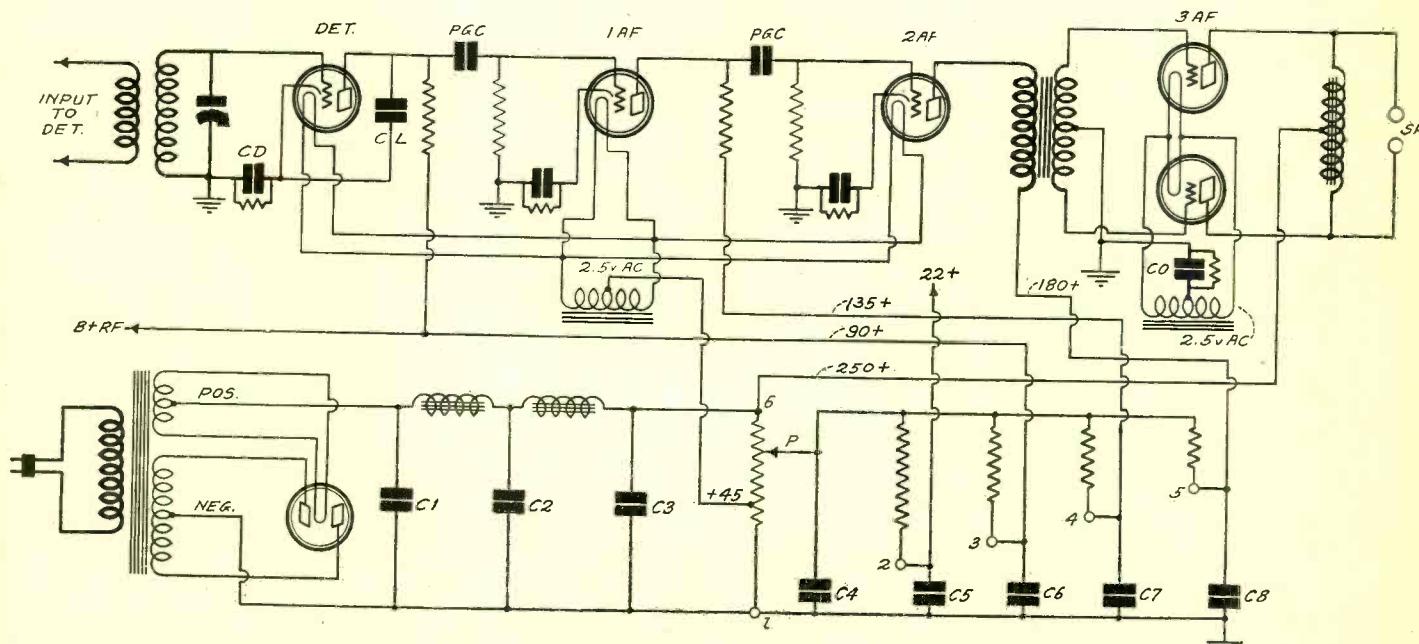

DESIGN OF A TWO-STAGE RESISTANCE-COUPLED AUDIO AMPLIFIER WITH TRANSFORMER-COUPLED PUSH-PULL THIRD STAGE. THE B SUPPLY IS EMBODIED. THE FILTRATION IS ESPECIALLY WELL GUARDED AND STABILITY RESULTS. THIS AMPLIFIER IS TO BE WORKED WITH THREE STAGES OF RADIO FREQUENCY AND DETECTOR, OR LESS.

fidelity of reproduction, we choose whatever radio amplifier and detector is to our liking, or suits our needs best, and proceed to an intense study of the *audio* amplifier for the safeguarding of what the detector delivers.

In a very real sense the best audio amplifiers are merely the best safeguards and protectors of the detector output. Correct design permits a distortionless detector output, in the sense that audio frequency response is virtually impartial throughout the entire range.

Double Wrong

If there are shortcomings in the radio amplifier, as where too great selectivity injures the high notes, a compensating effect may be introduced in the audio circuit for reducing the intensity of the low notes. But this is a makeshift. It proceeds on the basis of an acknowledged error, and instead of correcting the original error, commits another one, perhaps on the theory that two wrongs make a right, a philosophy unacceptable since Caesar stormed Gaul. And in the audio channel the subdiction of low notes to offset the injury previously done to high notes may be in obedience to a theory alone, and not a practical feat, since more than mere balancing of missing high notes against missing low ones is necessary. The result may be simply the absence or deep attenuation of both extremes, to the utter predominance of the middle register. That, indeed is not tone quality. It is the acknowledgment of one

mistake by the commission of another. The net result may be less notorious, but it is still far from that perfection which all of us desire at least to approach in our own home installations.

Can't Progress Much More

The quality of the audio amplifier is determined by complex conditions, including the nature and value of constants used for coupling, the voltages and means of providing them, the tubes and, of course, the speaker. That this quality can approach perfection is indeed a fact in this advanced state of the radio science, and that much improvement ever will be made is impossible, since the margin between the present condition and perfection is too small, and better than perfect it means distortion!

With such an abundant opportunity, therefore, to obtain results that will be approximately standard for all time, it is certainly fitting that the wisest choice be made.

Just what to choose is a subject on which unanimity, fortunately, never can exist. Taking perfection as the theoretical criterion, it is fair to state that any one of the three main methods of coupling—by transformer, impedance or resistance—or combinations thereof may accomplish this. Transformers are few indeed that are excellent, and always the excellent ones are not cheap in price, because costly to manufacture. The Ferranti AF5, for instance, one of the best transformers in the world, lists at \$14. An audio am-

plifier consisting of a pair of these transformers, with proper B supply, well filtered, makes as excellent an audio amplifier as one would want.

Gives Great Enjoyment

If 250 tubes in push-pull are desired as the output, with a built-in B supply, there is something to win any man's heart. There are other good transformers, although probably none quite so good. Even one with an acoustically trained ear will get plenty of enjoyment out of the resultant reproduction.

It is, in general, harder to get as good results from impedance coupling, due to the limitations imposed by coil-winding. The distributed capacity should not be so high across the coil terminals as to bypass the higher audio frequencies, for this would be the same effect as produced by sideband-trimming in an over-selective tuner. Yet the impedance of the coil should be as high as possible—infinity, in fact. The limitations that distributed capacity and excessive DC resistance place upon the coil that should be of infinite impedance are obvious. By a predetermined method of tuning the coupling circuit, that is, introducing regeneration effective at the desired frequencies, a good response may be obtained.

Stability Always Possible

The third method, resistance coupling, is as good as there is, since the resistance equals the impedance at all frequencies

audio Amplifier ent in Happiness

Herman

(whereas coil impedance depends on frequency), although it has proven harder to obtain stability in a resistance-coupled audio amplifier than in any other, with impedance coupling a close second on this score, and transformer coupling last. However, roughly speaking, any audio circuits of the three different types, or combinations thereof, if equally true in reproduction, will give about equal trouble from self-oscillation. This regeneration, taking place at audio frequencies, is due to a common coupling, often through the common impedance of the B supply or batteries, or the unison of plate and grid circuits such as always takes place when biasing resistors are used. However, properly filtered and bypassed, any audio circuit worked within reasonable limits of amplification, may be made stable.

Resistance coupling never has achieved great popularity. Transformer coupling always has been the overwhelming favorite. Most transformers in use are distorters, and the general run of transformers in factory-made receivers, nearly all of which have transformers, is poor indeed.

83 Cents for Audio Transformer

While it is amusing to read advertisements of set manufacturers extolling the tone of their receivers, in only a few instances does realism prove out on actual test, because 83 cents is a fair price for a manufacturer to pay for an audio transformer, or, if he makes his own, the same transformer usually will cost him more. In a two-stage amplifier you therefore get \$1.76 worth of one quality (manufacturers' price), and the advertising copy writers can coin all the fancy tone phrases they want, but they can not thereby change the laws of nature, one of which is the law of magnetic circuits pertaining to effect of the structure upon the frequency response and wave form.

It is pertinent to ask why one manufacturer lists one single audio frequency transformer at \$14 and why another manufacturer, this one a set producer, lists an entire table model receiver for \$60.

If it is pertinent to ask the question, it is not impertinent to answer it.

Radio is being robbed of its very birth-right of brightest enjoyment by the dissemination of bad receivers and the mis-education of the public that these distorting devices deliver tone quality.

Does Deception Hurt?

A small percentage of the total population has a deep appreciation of musical values and acoustical science, and if distorting contraptions are established as the criterion of real tone, the victim will be none the worse off for the deception, if it is true that the ignorant are none the worse off for their lack of education, or the poverty-stricken none the worse off for their lack of money. If price alone is the consideration, then why do not the manufacturers catering to the low-price market, instead of arguing that a low-priced radio set of merely passable or even inferior tone is better than none at all, make a low-priced receiver of excellent tone realism? Rather than cheap transformers of bad quality they could use cheaper resistors of much better tone quality! But that would require solution of the problem of proper filtration, to avoid motorboating or other manifestations of incipient or advanced self-oscillation. A proper distribution of the voltages and currents derived from the B supply, suitable bypass condensers, often not many more of them than are now used in cheap, poor sets, would help a great deal, and the engineering department could complete the work along special lines that a particular manufacturer's receivers might require.

Amplifier of Happiness

But it isn't done that way. The world is being made safe for distortion. You hear it at proud demonstrations of sales-excited manufacturers, you hear it from demonstration receivers operated at radio stores, particularly music stores that are rather proud of these noise boxes, and you

come across it in almost every home that you visit.

There is no need to ask a man why he should go to the pains of building an audio amplifier, or purchasing one of the built-up models that cost more than an ordinary, fully-equipped receiver. He has a good reason, the best reason: he knows tone quality when he encounters it, and knows distortion when he doesn't encounter tone quality. No number of misleading assertions in advertisements can dissuade him. He enjoys realism, not fairy tales. And as knowledge adds to the enjoyment of life, he is willing to go to the pains and expense of obtaining the audio amplifier that will make his life happier.

Realism Starts Blinks


While it is true that many thousands of persons calmly listen to distorted reproduction, and refer to it as realism, tone quality, perfect reproduction, clear, faithful, it is also true that they have ears, and that ears are not so dull as some persons would have them. The opportunity to compare one's distorting receiver with the reproduction of a distortionless amplifier is seldom enjoyed—not one-half of one per cent. of the time.

Even lacking this direct comparison, there is something about realism that sort of makes a startled hearer blink. Listening to a fine amplifier under home conditions has been one of the greatest influences leading otherwise unversed persons to adopt excellent audio as their maxim.

The construction of the audio amplifier, for the heretofore unapproachable results obtainable, should be along lines laid down by those thoroughly familiar with the quality branch of this work—circuits and parts being used such as are recommended in the better-grade technical press, by editorial writers of sound knowledge and practical experience. Every such author will provide excellent filtration, will reduce the common coupling as much as practical, both in circuit formation and in bypassing and filtration, and will spread greater delight than ever among those whose interest and confidence he courts. He will present an audio amplifier designed for quantities of undistorted power output and will consider whether the output of the detector is to be of a high or low order of volume—will provide much greater audio-amplified volume for a simple little tuner than for a multi-stage radio frequency circuit that often feeds as much as 5 or 6 volts to a detector, and, that done, will have served his public well.

* * *

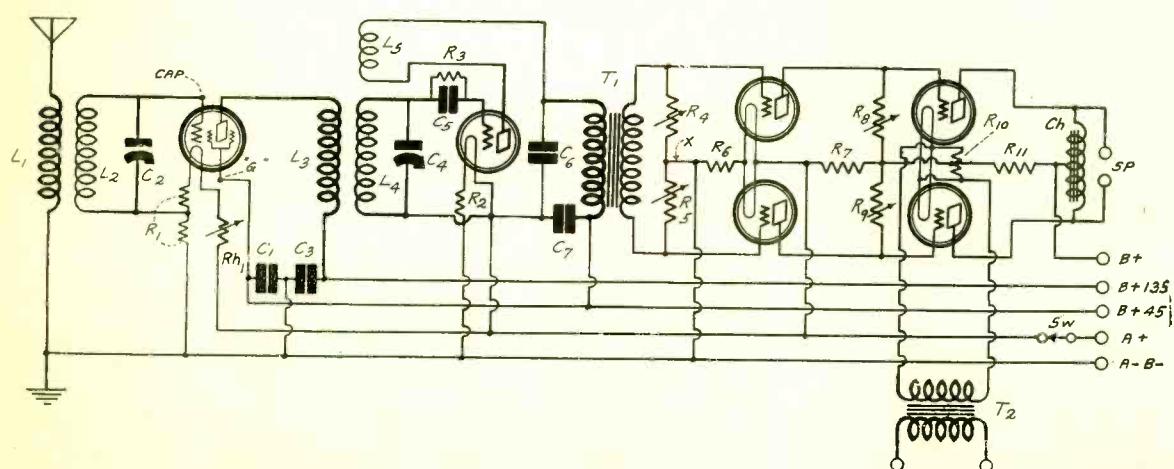[*Audio amplifier and B supply circuits for best toned reproduction will be published in subsequent issues, following designs laid down by the author. One design is diagrammed on the opposite page in advance.—Editor.*]



An interesting attempt to have a push-pull resistance-coupled last stage of audio. This circuit is purely experimental, since the accurate balancing of the resistors is a technical feat.

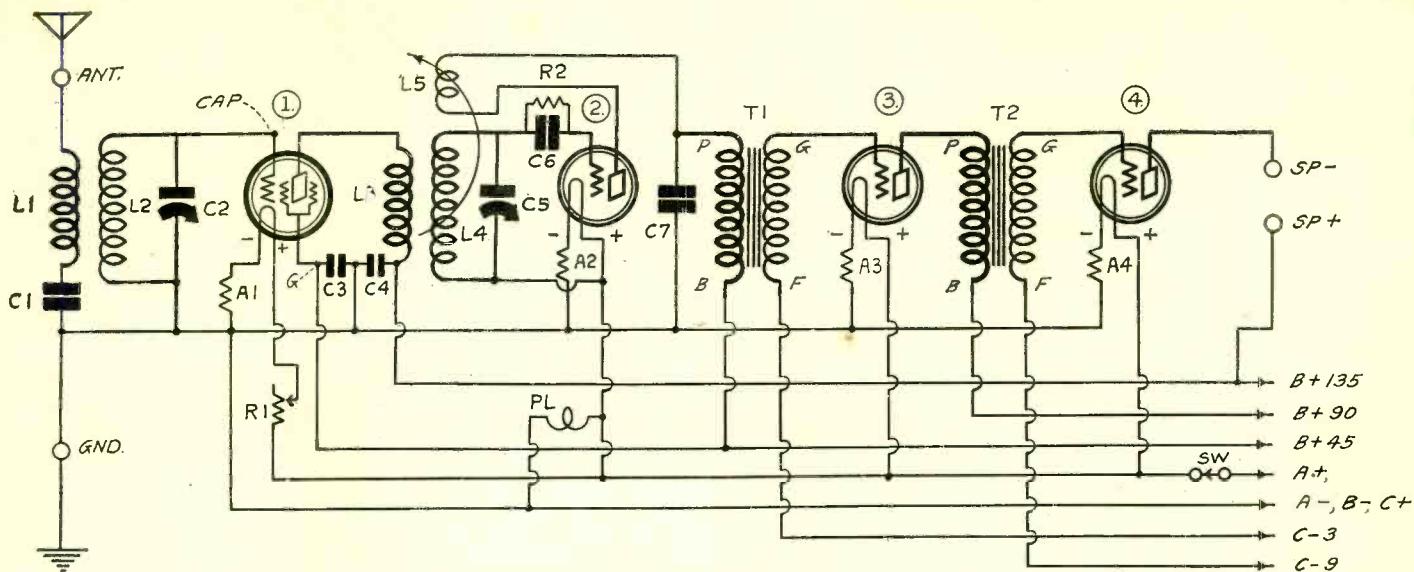


FIG. 751

TO SECURE RADIO FREQUENCY STABILITY WHEN USING ONE OR MORE SCREEN GRID TUBES, BOTH THE SCREEN GRID AND THE PLATE SUPPLY LEADS SHOULD BE BYPASSED, AS SHOWN IN THIS DIAGRAM. C3 AND C4 ARE THE BYPASS CAPACITORS. EACH MAY BE .1 MFD. OR LARGER.

Radio University

When writing for information give your Radio University subscription number.

PLEASE SHOW a circuit diagram indicating how to measure the plate and grid voltages in a receiver using AC tubes.

(2)—Also please show a simple method of measuring the grid bias in a resistance coupled circuit.

AMOS BURT,
Nashville, Tenn.

(1)—See Fig. 750, left. Voltmeter 1 measures the grid bias, meter 2 measures the plate voltage, while meter 3 measures the sun. A high resistance meter must be used.

(2)—The right hand figure in Fig. 750 shows an arrangement for measuring the grid bias on a resistance coupled tube. Throw the grid to the upper point and note the reading on the plate milliammeter. Then throw the grid down to pick up the battery Eg. Adjust this battery until the plate milliammeter reads the same as it did before. The reading on the voltmeter across Eg is the bias sought.

* * *

I HAVE a power tube in which there is a blue glow at all times. Is this harmful to the tube and to the operation of the circuit?

(2)—What is the cause of the glow? How can it be removed?

(3)—If the tube can not be used safely as a power tube could it be used to advantage in some other part of the circuit?

VINCENT LATIMER,
Toledo, Ohio.

(1)—It is not harmful to the tube because that is already defective. It should not be used in the power stage, or in any amplifier stage.

(2)—The glow is caused by residual gases in the tube. It usually appears when the plate voltage is too high. Get a new tube.

(3)—It may be used as a detector. But if the amplification factor of the tube is low it will not function well as a detector.

* * *

CERTAIN BYPASS condensers are provided with spark gaps. What are they for?

(2)—Why are by-pass condensers rated at different operating voltages for alternating and direct voltages?

(3)—Why is the continuous operating voltage lower than the flash voltage?

(4)—What is the difference between a condenser rated at 200 and one rated at 1,000 volts? Why is the size of the 1,000 volt condenser larger than the 200 volt condenser when both have the same capacity?

WILFORD TODD,
Omaha, Neb.

Right or Wrong?

[Answers on page 15]

1.—The apparent quality of a radio receiver depends on the volume intensity even if the tubes are large enough to handle the volume without overloading.

2.—In order to get the maximum volume out of a power tube the primary impedance of the transformer between the tube and the speaker should be equal to the plate resistance of the tube.

3.—For maximum power output the impedance of the loudspeaker should be equal to the impedance of the secondary of the coupling transformer.

4.—The impedance of the dynamic speaker is simply the DC resistance of the voice coil winding.

5.—A low resistance voltmeter does not give the correct voltage when used to measure the output of a power pack because of the drop in the resistors in the network.

6.—The pleasant timbre of music from a harp or a piano is due to the fact that the harmonics produced are exact multiples of the fundamental.

7.—The sound from a drum is not musical because the harmonics are missing.

8.—The harmonics of a carrier frequency produced by overloading of the tubes are exact multiples of the carrier frequency.

9.—The impedance of the primary of an audio transformer or that of a choke coil with iron core does not depend on the amount of direct current in the winding.

10.—Motorboating in a receiver is simply a periodic charging and discharging of the stopping condenser which results when the grid of the tube goes positive.

(1)—The spark gap is for protective purposes. When the voltage across the condenser rises above a certain value determined by the insulation, the condenser discharges across the spark gap and this prevents the condenser itself from breaking down.

(2)—The direct voltage rating is higher because it is steady and contains no peaks. The alternating voltage varies between zero and a value 1.41 times the effective voltage. Hence the alternating voltage rating must be only about .7 of the direct voltage rating.

(3)—A voltage is a stress on the condenser. If this exists for a long time the condenser gradually weakens. When the voltage is alternating there is an alternating current through the condenser. This heats it up and weakens it further.

(4)—The difference between these condensers lies in the thickness of the insulation between the two plates, or between the two layers of tin foil. A low voltage condenser may have a single layer of treated paper between the two plates. Another may have two. A high voltage condenser may have from six to eight layers of the same paper. Usually a condenser has at least two layers in order to minimize short circuits from defects in the paper, such as holes and metal particles. The size increases rapidly with the voltage rating because not only is much more paper used but more tinfoil has to be used to make up for the greater separation of the plates.

* * *

WHAT IS MEANT by the decrement of a radio frequency wave?

(2)—Has the decrement anything to do with the quality of broadcast programs?

(3)—Is the decrement a property of the wave or of the circuit in which the wave is produced?

SEYMORE EVERETT.

Lexington, Ky.

(1)—The decrement is the rate of decrease of the amplitude of a damped wave, and depends on the amplitudes of two consecutive maxima in the same direction.

(2)—The waves used in broadcasting have no decrement. They are undamped. As long as it is unmodulated the amplitude remains constant.

(3)—The decrement is strictly a property of the wave but is caused by a property of the circuit, its effective resistance.

* * *

I HAD a battery-operated receiver that I built myself and operated with much pleasure for two years. Then I moved into a neighborhood that has alternating current, and I decided to build an AC re-

ceiver. My output tube is a 171A. I used grid biasing resistors all through, including one in each stage of radio frequency, one in the detector and one each in the two audio stages. The bypass condensers across all these resistors are .006, mfd., as a friend recommended this large capacity. My complaint is that the circuit does not reproduce the low notes as well as did the battery-operated receiver, although many of the same parts are included in the new outfit, including tuning condensers and radio coils. How can I get the same fine quality out of my new receiver?

ADAM J. MORCHAND,
Rye Beach, N. Y.

The capacity of the condensers used for bypassing the resistors is not large in any sense. For the radio frequency tubes it is passable, although louder signals might result if you increased the capacity to .01 mfd. or .02 mfd. In the detector stage and first audio the biasing resistors, bypassing condensers should be at least .5 mfd., and preferably much larger, say 4 mfd., while the final audio stage never should have anything less than 4 mfd. Above 4 mfd. the improvement in any audio circuit is not noticeable to the ear. The reason for the large capacity of 4 mfd. is that the impedance to audio frequencies of the biasing circuit is reduced greatly, thus improving the general amplification, and particularly the low-note reproduction. With these precautions taken, your AC receiver will give you just as fine tone as did the other.

* * *

IS IT TRUE that a baffle for a dynamic speaker must be large, and that the popular types of cabinets that house them, e. g., walnut, mahogany, spruce, etc., in modernistic and other shapes and finishes, tend to make the loud speaker sound boomy? I am looking for the best reproduction possible, but hesitate to buy one of those good-looking cabinets if tonal results will not be good.

ADOLPH MENGES,
Detroit, Mich.

A baffle for a dynamic speaker should be large, say, three-feet square, and should be well ventilated, preferably consisting of nothing but the baffle board and a bottom on which to rest the speaker. However, this is not attractive to the eye, no matter how made up, hence a box should be simulated, which can be done by using cane for the top, sides and back, or leaving the back open and having the sides and top cane. Still, three feet is quite a size, and the common expert practice is to compromise in favor of appearances, using an 18-inch or smaller baffle. This will give good results. The small box type, although the most handsome and does not give the best tonal results, still affords quality satisfactory to many. The chief objection is not so much boombiness all through the audio lower frequencies but to very strong and false accentuation of certain few low frequencies, particularly one to which the box structure itself is resonant. Therefore the expression "box resonant" has arisen. The speaker may rattle at this resonant frequency. You may compromise, as many others have done, on an 18-inch or 24-inch baffle, acoustically open, but imitating a box in appearance, and will be well satisfied.

* * *

I LIVE in the heart of New York City. My complaint is that WOR comes in so strongly that I have difficulty tuning it out, even 15 dial divisions off resonance. I have tried all kinds of aerials. If I make the aerial short the volume on the high wavelength stations is too low, and WOR is still troublesome. If I make the aerial long, WOR is more troublesome than ever. I like to listen to this station, but I do hate to suffer crosstalk from WOR when listening to WJZ or WEAF,

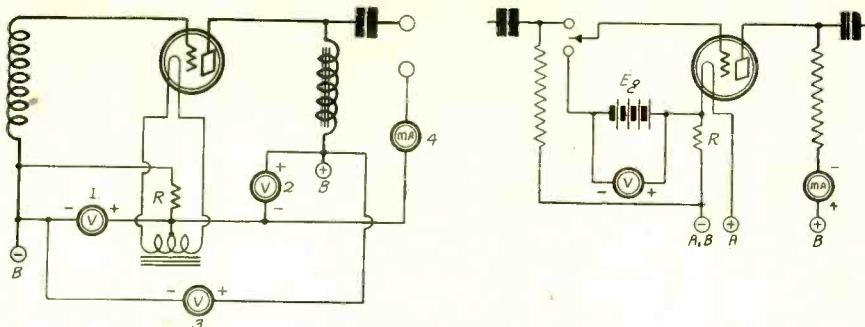


FIG. 750
AT LEFT IS A CIRCUIT SHOWING HOW TO CONNECT VOLTMETERS FOR MEASURING THE PLATE AND GRID VOLTAGES IN AN AC TUBE. AT RIGHT IS SHOWN A CIRCUIT ARRANGEMENT FOR ACCURATELY MEASURING THE GRID BIAS ON A RESISTANCE COUPLED TUBE.

which often have programs I prefer. What remedy do you propose?

HAL BREEN, New York City

Your receiver is not selective enough and there is little you can do to make it more selective, except to introduce regeneration, say, in the detector or stage, if you haven't a regenerative feature already. Even this, however, is unlikely to do you much good, since your case is a severe one. Not only do you need a selective receiver but one that must be ultra-selective to meet an unusual situation. The strength of WOR's signals in parts of the Boroughs of Manhattan and Brooklyn is so great that this ultra-selectivity becomes imperative. You should build a circuit having four tuned stages—

three stages of tuned RF and a tuned detector unit. Put a trimming condenser across the first tuning section of the gang condenser, or tune the first circuit independently of the others, if you want two main tuning controls. By using as a volume control a variable biasing resistor that affects one, two or three RF tubes you will increase selectivity when you reduce volume, which will be another aid in the general direction you desire. With the receiver suggested, a 50-foot aerial will be ample, WOR will be tuned out readily (in about 3 divisions), and still WEAF and other stations on lower frequencies will come in with plenty of volume. Put permanent trimmers across each section of the gang condenser for utmost practical selectivity.

Right or Wrong?

[Question on page 14]

1. —Right. As the volume is decreased the high and the lower frequencies disappear because they are then not strong enough to affect the ear. The ear is more sensitive to sounds in the middle register.
2. —Wrong. The impedance of the primary should be higher than the plate resistance.
3. —Right. This is the only point in the circuit where there should be matching. If the speaker is connected in the plate circuit directly the speaker impedance should be equal to the plate resistance of the tube.
4. —Wrong. The resistance of the voice coil to DC is only a small part of the total effective resistance of the speaker. The resistance of the air against the diaphragm constitutes the greater part, and the only useful part.
5. —Right. The resistors are equivalent to external resistors in the voltmeter.
6. —Wrong. The harmonics are not true multiples of the fundamental but only approximately so. However, the peculiar timbre of each instrument is due to the harmonics.
7. —Wrong. The sound is not musical because there are too many and too strong harmonics and because they are discordant.
8. —Right.
9. —Wrong. The impedance of an iron core inductance of any kind depends very much on the direct current flowing through the winding. The inductance decreases as the current increases.
10. —Wrong. Motorboating is due to feedback from one tube to preceding tubes through the B battery eliminator or the B battery. It is a form of incipient or advanced oscillation, usually of low frequency.

Join RADIO WORLD'S University Club

And Get Free Question and Answer Service for the Coming 52 Weeks
This Service for Yearly Subscribers Only

Have your name entered on our subscription and University lists by special number. Put this number on the outside of the forwarding envelope (not the enclosed return envelope) and also put at the head of your queries. If already a subscriber, send \$6 for renewal from close of present subscription and your name will be entered in Radio University. No other premium given with this offer.

[In sending in your queries to the University Department please paragraph them so that the reply can be written under or alongside of each query. Write on one side of sheet only. Always give your university number.]

RADIO WORLD, 145 West 45th Street, New York City.

Enclosed find \$6.00 for RADIO WORLD for one year (52 nos.) and also enter my name on the list of members of RADIO WORLD'S University Club, which gives me free information in your Radio University Department for 52 ensuing weeks, and send me my number indicating membership.

Name

Street

City and State

The Reduction of Hum

As Applied to the Giant 6-1 AC Circuit

AS for hum, there is little indeed from this receiver, but if you desire to make it almost zero you can do so by using a smaller resistor in the detector plate circuit (R10), provided stability is thereby maintained, and by putting a condenser across the immediate output of the rectifier tube (one side to choke lead going to midtap and other side to ground). The condenser was eliminated from this point and the extra capacity put at the end (C21, C22) to prolong considerably the life of the rectifier tube, but if you'd rather have a little less hum, with shorter rectifier tube life as the price, move the schematic connection at top of C21 over to the choke point previously specified.

Midtap Connection

Hum is kept very low by connecting the midtap of the heater winding to plus 22 volts, more or less. Do not make the mistake of connecting the wrong 2.5 volt winding to B plus. The filament transformer has three windings. The top one at 2.5 volts is used for the heater tubes. The midtap of this goes to the positive B voltage. The middle winding is 5 volts and heats the pilot light PL1, which illuminates the dial. The bottom winding, the second 2.5 volts, does not go to a heater tube but to the power tube, hence if you put the B voltage at that center tap you'd be applying B voltage to the filament.

Tips on 227 Tube

The heaters of the 227 tubes are diagrammed like the filaments of any other tubes. The two terminals on the sockets are marked H and H'. The cathode, or electron emitter, is shown schematically as a hooked element over the heater, and

LIST OF PARTS For The Amplifier

T2—One Silver-Marshall power transformer (S-M Cat. No. 330).
F—One 1 Ampere fuse, 110v.
Ch1, Ch2—One Silver-Marshall Unichoke (S-M. Cat. No. 331).
C20, C21, C22, C23, C24, C25—Aerovox filter-buffer condenser block, Type No. TH-862.
Ro—One Aerovox standard tapped Pyrohm resistor, type A (0.3,000, 2,800, 750, 750 ohms).
 One standard sockets (4-prong).
 One baseboard 34x18 inches.
 One 280 tube.
 One dynamic AC speaker.

on the socket is marked C or K. Grid and plate are standard. The heater tubes require five-spring sockets.

As there is no guiding pin on the base of the tube, and usually none on the socket, either, and as five prongs are to be accommodated, some familiarity must be gained in inserting these tubes or you'll spend some awkward moments trying to fit them in place. An easy way out is to learn the respective positions of the terminal receptacles on the sockets. These constitute a triangle between K, G and P (cathode, grid and plate). The apex of the triangle is G. See the pictorial diagram. So when you pick up a 227 tube, look at the prongs. Immediately you can locate this apex of the equilateral triangle. Put your finger on it. Your eye will tell you then the G post of socket. Insertion can then be made quickly and

without error. The only error possible is that you couldn't insert the tube.

Data on Parts

The layout of parts and the schematic diagram give you sufficient information so you will not require a blueprint. However, some extra information about the parts will assist you.

All four coils are identical. The primary has six turns, $\frac{1}{4}$ -inch space is left, and then 48 turns are wound for the secondary. The wire is No. 24 silk (single or double insulation) and the diameter $2\frac{1}{2}$ -inches. The ends of the windings that adjoin go to B plus and ground respectively.

The SM-331 choke is connected with (1) to center tap of the 280 filament, 2 and 3 united, with C20 here, and 4 as the rectifier's maximum output. On the SM 330 power transformer (1) and (2) represent the AC cable, already built in; (3) and (4) are the $7\frac{1}{2}$ -volt winding and (5) and (7) go to grid and plate posts of rectifier socket. (8) is the frame and is grounded and joined to (6). The voltage across (5) and (6) is 300 volts, also across (6) and (7), so (5) to (7) will read 600 volts AC. If the $7\frac{1}{2}$ -volt winding has no center tap, provide one by putting a 10-ohm center-tapped Clarostat "humdinger" across posts (3) and (4) of the 330.

The condenser bank, Aerovox TH862, has three high voltage condensers of 2 mfd. each (C20, C21, C22) and three of medium voltage (C23, C24, C25). Connect the black wire lead of the bank to B minus and ground, the two blues (respectively to points (2) and (3) of the resistor Ro, the orange to point (4); red to the center of Ch1 Ch2, and both browns to (4) on Ch1.

The Pyrohm resistor Ro has a resistance of 7,300 ohms: The 750-ohm end goes to B minus in this circuit.

Literature Wanted

THE names and addresses of readers of RADIO WORLD who desire literature on parts and sets from radio manufacturers, jobbers, dealers and mail order houses are published in RADIO WORLD on request of the reader. The blank at bottom may be used, or a post card or letter will do instead.

RADIO WORLD,
145 West 45th St., N. Y. City.
I desire to receive radio literature.

Name

Address

City or town

State

Jack B. Kammer, 1531 Andrew St., Fort Wayne, Ind.
 Milton K. Browne, 1st Sgt. 2nd Batt. Hq. Co., 10th Inf., N. Y. Nat'l. Guard, Binghamton, N. Y.
 E. T. Somerset, G-BRS 125, Inholmes Park, Burgess Hill, Sussex, Eng.
 J. E. Wilkes, Forest Gate, Sask., Can.
 Rufro Ramirez, No. 1 Jose M. Fernandez St., Santurce, P. R.
 Joseph Rowe, R. F. D. No. 3, Smithburg, Md.
 Arthur J. Green, 700 Alpha St., Klondyke, Ohio.
 Helmer Romness, R. F. D. No. 4, Zumbrota, Minn.
 Dr. Leo H. Neuman, 194 State St., Albany, N. Y.
 Geo. H. Osgood, care Dole, Osgood & Co., Peabody, Mass.
 D. D. A. Outcalt, Rt. 1, Box 715, Tacoma, Wash.
 C. Burton, 40 Clermont Ave., Brooklyn, N. Y.
 M. S. Perry, 18813 Sloane Ave., Lakewood, Ohio.
 James L. Norris, Cor. F & 5th Sts., N.W., Washington, D. C.
 C. H. Hoblitzel, 433 Bauer St., Hammond, Ind.
 H. B. Bernert, 8718 Ridge Blvd., Apt. 6L, Brooklyn, N. Y.
 H. S. Cooper, 714 Woodland St., Nashville, Tenn.
 A. E. Blakeman, 1946 Clairmount Ave., Detroit, Mich.
 G. E. Hendrickson, Board of Education, Duluth, Minn.
 Chas. Haines, North Bend, B. C., Can.
 F. E. Richter, care Chicago Lumber & Coal Co., Arcade Bldg., St. Louis, Mo.
 Theo. B. Barnes, 308 Frederick Ave., Detroit, Mich.
 W. J. Kotera, care Radio KMMP, City Center, Neb.
 Howard Weikel, 14 So. Anthracite St., Shamokin, Pa.
 Robt. J. On, 149 Rosemont Ave., Coatesville, Pa.
 C. L. Strope, 59 10th St., Providence, R. I.
 F. Forrest Soper, care Civil Service Commission, 435 City Hall, Cleveland, Ohio.
 Wm. J. Maynard, 146 Mill St., Bennington, Vt.
 H. M. Simons, care Merks Cigar Store, 1535 4th Ave., Seattle, Wash.
 J. J. Buckalew, P. O. Box 95, Milford, Del.
 Chas. J. Trual, R. F. D. No. 1, Beverly, N. J.
 Chas. R. Eversfeld, 517 Hamlin St., Watertown, N. Y.
 Carl R. Wittman, Corfu, N. Y.
 R. W. Deck, 409 Center St., Sandusky, Ohio.

Leo M. Haas, 20 Alexander St., Framingham, Mass.
 J. S. Bosher, 301 E. Brookland Blvd., Richmond, Va.
 J. E. Sears, Colfax, Calif.
 J. J. Fleck, 1438 No. 15th St., Philadelphia, Pa.
 Edison Leeds, care Ernest Beyer, 1623 Atlantic Ave., Atlantic City, N. J.
 Radio Den, 1545 East 85th St., Cleveland, Ohio.
 Rex C. Pine, 1428 Vanburen St., Missoula, Mont.
 John Cruite, 119 Cliffe St., Shelton, Conn.
 O. Candy, 33 Chester Ave., Toronto, Ont., Can.
 H. S. Livingston, Livingston, Wis.
 Paul Garman, 2107 Wrocklage Ave., Louisville, Ky.
 J. J. Fleck, 1439 No. 15th St., Philadelphia, Pa.

Melvin Olroyd, 902 S. Richard St., Joliet, Ill.
 Wm. Ericson, 32 Stone St., Concord, N. H.
 R. W. Myers, Box 60, Bay Roberts, Newfoundland.
 G. T. Burch, 3710 Ridgecroft Rd., Gardenville, Baltimore, Md.
 B. Bachman, Box 187, Provo, Utah.
 N. M. Sutterfield, Prop. K. M. A. Barber Shop, Rt. 2, Iowa Park, Tex.
 Jos. Agoglia, 1462 2nd St., Brooklyn, N. Y.
 C. J. McCrea, Bedford, Iowa.
 J. D. Carmen, Magnolia, Md.
 Albert Driver, 199 Collette St., New Bedford, Mass.
 James C. Campbell, 903 Calif. Ave., Oakmont, Pa.
 Edwin C. Watkins, 806 Cornelia St., Flint, Mich.
 W. M. Lee, 159 W. River St., Orange, Mass.
 Curt Bowser, 219 Water St., Freeport, Pa.
 Frank M. Carter, P. O. Box 15, Phoebe, Va.
 Fred Gray, 26 Marten, Wadesboro, N. C.
 Ralph Dyson, 4733 7th Ave., N.E., Seattle, Wash.
 Frank Orcutt, 2108 W. Church St., Orlando, Fla.
 A. J. Ruder, 6246 Lipton Way, Los Angeles, Calif.
 Oscar Segal, 1210 S. Holman Ave., Chicago, Ill.
 Mrs. J. C. Wallace, Southport, Conn.
 A. M. Westover, 102 East Bell Ave., Altoona, Pa.
 A. J. Bellar, 1112 W. Nebraska Ave., Peoria, Ill.
 A. J. Bosseau, Box 161, Avella, Pa.
 Clarence Parker, 2443 8th St., N.W., Washington, D. C.
 Oscar Le Moine, 3018 Vernon St., Duluth, Minn.
 E. Gourdeau, 6310-A De Normanville St., Montreal, P.Q., Can.
 Fred Frisch, 204 Hart St., Brooklyn, N. Y.
 Seth L. Worthing, 233 Montezuma St., Houghton, Mich.
 Dr. Jos. D. McGrath, 302 W. Jefferson St., Fort Wayne, Ind.
 F. I. Woltz, 160 Lincoln Rd., Phillipsburg, N. J.
 Geo. R. Parker, 9719 Woodward Ave., N. E., Cleveland, Ohio.
 W. R. Youmans, 815-5 6th St., Ironton, Ohio.
 A. J. Tripp, 12282 Hartwell Ave., Detroit, Mich.
 Gerard Desparlate, 1827 Gird St., Montreal, Que., Can.
 W. N. Wagar, 1851 Francis Ave., Troy, N. Y.
 P. B. Sanford, Second Presbyterian Church, Grove & Church Sts., Amsterdam, N. Y.
 Geo. R. Furman, 21 W. 4th St., Williamsport, Pa.
 Gordon A. Francis, 430 4th St., N. E., Washington, D. C.
 Allen Carter, 1742 Evansville Ave., Toledo, Ohio.
 Jos. S. Goral, Rt. 2, Box 35, Latrobe, Pa.

Dynamic Impedances

How the Speaker Compares with Magnetic Type

By James H. Carroll

Contributing Editor

WHY are two coils needed in a dynamic speaker? What is the function of the voice coil? What does the field coil do? Why is it necessary to have a step-down transformer between the power tube and the voice coil in the dynamic speaker? These are some of the questions asked by fans who have dynamics who are planning to get them.

In all speakers it is necessary to have a field and an armature. In magnetic and dynamic speakers the field is magnetic. It may be set up by a permanent magnet or by an electro-magnet. While in so-called magnetic speakers the field is usually set up by strong permanent magnets, some of this type have been constructed with electro-magnets. Also, while most dynamic speakers are constructed with electro-magnets, some have also been constructed with permanent magnets.

Only those speakers of either type which employ electro-magnets need a field winding. The difference between the permanent magnet and the electro-magnet is simply in the type of core used. The permanent magnet is made of steel which retains magnetization put into the material by means of an electro-magnet. The electro-magnet is made of iron or steel which does not retain its magnetization. In this type it is necessary to have a current-carrying coil around the core to maintain the magnetization.

In both the magnetic and the dynamic speakers the motion of the armature is due to an interaction between two magnetic fields, the steady field set up by the permanent magnet or the electro-magnet, and the field set up by the current in or around the armature.

In the magnetic speaker the armature coil carrying the signal is fixed. The armature is a little electro-magnet which alternates in polarity. In the dynamic the armature is simply the voice coil which is free to move. It, too, is an electro-magnet, but its core is fixed and is a part of the steady field core. The polarity of this electro-magnet alternates also under the influence of the voice current through the moving coil.

Hence the essential difference between a magnetic and a dynamic speaker is that in one the armature core moves and its coil is fixed, and in the other the coil moves and the core is stationary.

Is Small Coil Essential

Why are dynamic speakers made with a very small armature coil? Could not this coil be made so large as to eliminate the need of a step-down transformer? It has been done. But if the moving coil is made so large that its impedance matches that of a power tube, it will be very heavy. The speaker then would not respond to high frequencies. And if it were wound with very fine wire so that it would be light, it would not carry the current. It would burn out. Even if the direct current were kept out of the coil, it would not carry the voice current without burning out, because there would not be the necessary ventilation of the turns.

So dynamic speakers are generally made with a small voice coil requiring a step-down transformer between the power

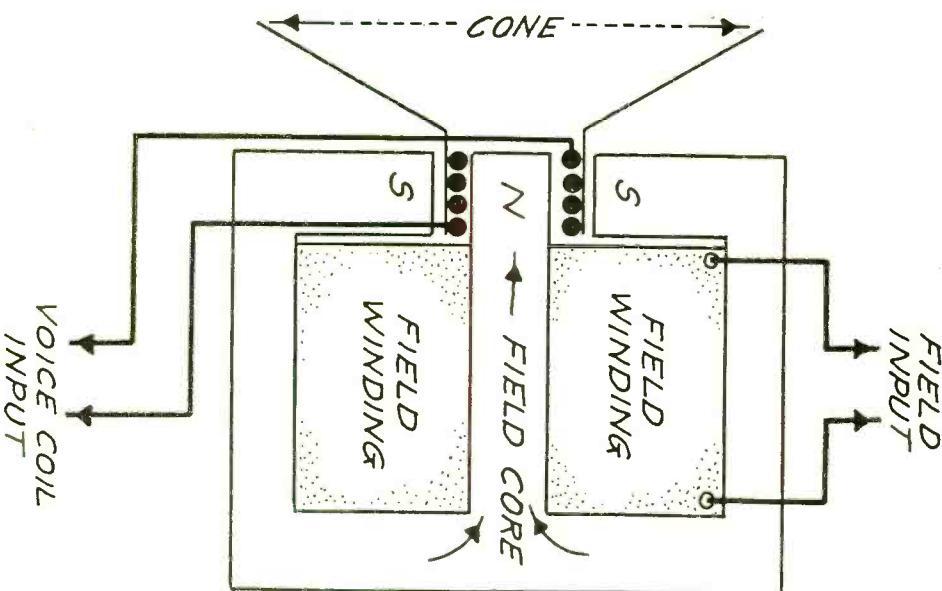


FIG. 1
DIAGRAM OF A CROSS SECTION OF A DYNAMIC SPEAKER STRUCTURE,
SHOWING THE VOICE COIL, THE CORE AND THE FIELD COIL SPACE.

tube and the speaker. The transformer automatically keeps the direct plate current out of the voice coil.

An important consideration is the proper matching of the speaker and the tube. It may be shown that for maximum undistorted output the ratio of the step-down transformer should be the square root of the ratio R_1/R_2 , where R_1 is the plate resistance of the power tube and R_2 the effective resistance of the speaker. This does not mean the resistance of the speaker as measured with DC methods, or with AC methods with the speaker armature clamped down. It means the resistance of the speaker measured with AC methods while the speaker is sounding normally.

Transformer Ratio

Suppose the tube used has an AC resistance of 1,800 ohms in the plate circuit, and that the effective resistance of the speaker is 25 ohms. The above ratio is then $3,600/25$, the square root of which is 12. This should be the ratio of turns of the step-down transformer used.

The ratio $2R_1/R_2$ was derived on the supposition that the primary resistance is negligible in comparison with the plate resistance of the tube and that the secondary winding resistance is negligible in comparison with the effective resistance of the speaker.

The effective resistance of the speaker is not a definite quantity for it varies with the frequency and with the position of the speaker with respect to other objects in the room. Hence it is not possible to match the impedances for all frequencies. But there is a very simple way of attaining the best adjustment.

There are output transformers available which have taps on the secondary winding. By connecting the voice coil across various taps a variation of the output will be obtained. That tap which

gives the loudest response combined with the most pleasing tone should be used.

The output transformer which is found in a dynamic speaker may not be the best for the tube and speaker. If it is desired to substitute another, all that is necessary is to disconnect the voice coil from the transformer built in and to connect them to the external transformer. The voice coil leads are usually connected directly to the cone where access to them may be gained.

Built-In Filter

Practically all dynamic speakers also have low pass filters built in to cut off the high notes, that is, to reduce the tube and battery noises and the excessive response of the speaker on the high notes. The effect of this filter may not be the best from the point of view of the user of the loudspeaker. When the external transformer is connected to the voice coil in place of the built-in transformer, the filter is disconnected also. It is then possible to try other filter combinations, or no high frequency suppressor at all.

There are other reasons why an external transformer may improve the results. Some dynamic speakers have rather small output transformers. They are not built to carry the heavy primary currents which will occur with high power output tubes. When the core of the output transformer is saturated, good quality is impossible. If the external transformer is used, one large enough to handle any requirements may be selected. There is no sense in building a high quality audio amplifier only to have the quality ruined in the output transformer.

Fig. 1 shows a cross section of a dynamic speaker. The shaded portion is the space for the field coil and the white portion is the core. The voice coil is shown by dots in the narrow space between the N and S poles of the magnet.

PARTS FOR THE AC 4

| | |
|---|---------|
| Complete Kit of Parts for the AC4, less B eliminator | \$36.75 |
| Complete Kit of Parts for AC4, with National B eliminator (180 v.) including 280 tube | \$54.75 |
| Complete Kit of Parts for AC4, with National B eliminator, 280 tube, cabinet, three 227 tubes, one 171A tube and Table Model Polo Speaker (nothing else to buy) | \$75.00 |

GUARANTY RADIO GOODS CO.

143 West 45th Street
New York City

Front and Subpanel
for the

AC 4

Front panel, drilled for National Drum Dial, volume control switch, and for "dummy". \$2.35
Subpanel, 6x19", cut milk ladel shape, to permit room for B eliminator; 4 sockets built into subpanel; other holes drilled.....\$3.65

SPECIAL: We carry National Velvet B (type 3580) in stock, also 280 tube. Get our prices on these. Blueprint for AC4.....\$1.00

GUARANTY RADIO GOODS CO.
143 W. 45th St., N. Y. City

COILS FOR THE NEW AC 4


Two AC5 (for .0005 mfd.) @ \$1.50 each....\$3.00
Two AC3 (for .00035 mfd.) @ \$1.75 each,... 3.50

SCREEN GRID COIL CO.
143 West 45th Street
N. Y. City
(Just East of Broadway)

LACAULT'S BOOK

"Super-Heterodyne Construction and Operation," giving the master's most masterful exposition of the theory, performance and construction of this fascinating type of circuit, is a necessity to every serious radio experimenter. More than 100 pages and more than 50 illustrations. Buckram cover. This book by R. E. Lacault. FREE if you send \$1.00 for an 8-weeks subscription for Radio World. Present subscribers may accept this offer. Subscription will be extended.

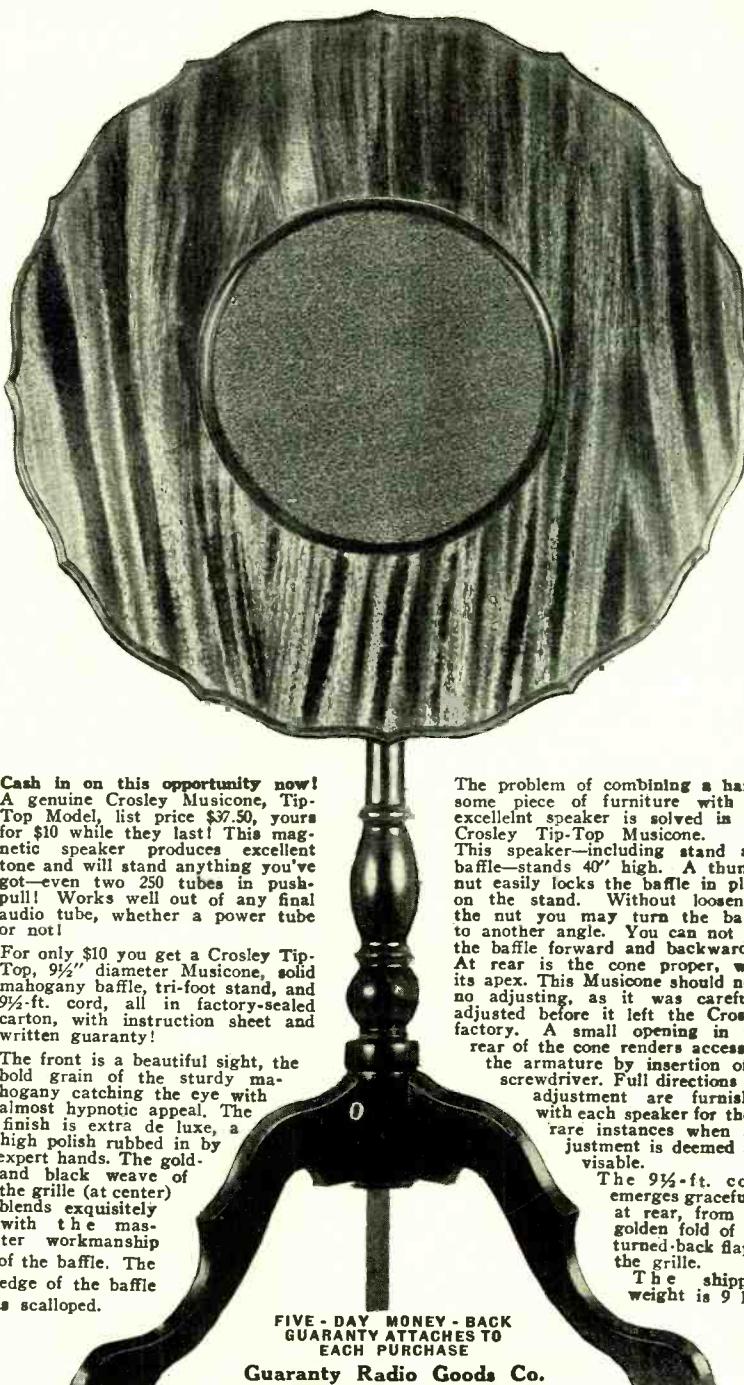RADIO WORLD
145 W. 45th St., N.Y. City
Just East of B'way



Cash in on this opportunity now! A genuine Crosley Musicone, Tip-Top Model, list price \$37.50, yours for \$10 while they last! This magnetic speaker produces excellent tone and will stand anything you've got—even two 250 tubes in push-pull! Works well out of any final audio tube, whether a power tube or not!

For only \$10 you get a Crosley Tip-Top, 9½" diameter Musicone, solid mahogany baffle, tri-foot stand, and 9½-ft. cord, all in factory-sealed carton, with instruction sheet and written guaranty!

The front is a beautiful sight, the bold grain of the sturdy mahogany catching the eye with almost hypnotic appeal. The finish is extra de luxe, a high polish rubbed in by expert hands. The gold-and black weave of the grille (at center) blends exquisitely with the master workmanship of the baffle. The edge of the baffle is scalloped.

FIVE-DAY MONEY-BACK
GUARANTY ATTACHES TO
EACH PURCHASE

Guaranty Radio Goods Co.
145 West 45th Street New York, N. Y.
(Just East of Broadway)

The problem of combining a handsome piece of furniture with an excellent speaker is solved in the Crosley Tip-Top Musicone. This speaker—including stand and baffle—stands 40" high. A thumb-nut easily locks the baffle in place on the stand. Without loosening the nut you may turn the baffle to another angle. You can not tilt the baffle forward and backward. At rear is the cone proper, with its apex. This Musicone should need no adjusting, as it was carefully adjusted before it left the Crosley factory. A small opening in the rear of the cone renders access to the armature by insertion of a screwdriver. Full directions for adjustment are furnished with each speaker for those rare instances when adjustment is deemed advisable.

The 9½-ft. cord emerges gracefully at rear, from the golden fold of the turned-back flap of the grille.

The shipping weight is 9 lbs.

RADIO WORLD, published every Wednesday, dated Saturday of same week, from publication office, Hennessy Radio Publications Corporation, 145 West 45th Street, New York, N. Y., just east of Broadway. Roland Burke Hennessy, President; M. B. Hennessy, Vice-President; Herman Bernard, Secretary. Roland Burke Hennessy, Editor; Herman Bernard, Managing Editor; J. E. Anderson, Technical Editor.

Quick Action Classified Ads

Radio World's Speedy Medium for Enterprise and Sales

10 cents a word — 10 words minimum — Cash with Order

AGENTS AND SALESMEN WANTED

Sell \$5.00 Men's Daily Necessity for 50c. Cost quantities 20c. Sample postpaid 30c. Catalog hundreds household articles free. Mills Sales Co., 901 Broadway, New York.

AMAZING! NEW! Wonder-tone, connects between speaker and set. Gives you that rich, vibrant, mellow tone. Practically eliminates hum, static and other noises. \$2.00 postpaid. Literature on request. Wonder-tone Mfg. Co., 311 Gratiot, Detroit, Mich.

\$25-\$35 WEEKLY. Easy. Address cards at home. Spare time. Experience unnecessary. Everything furnished. Particulars free. Write today. Rol-Kel Company. Dept. F., Greenfield, Ohio.

ARTISTS and Art Students are printing 250 signs or pictures an hour without machinery. Sample and particulars 10c. Straco, 1014 Mulberry, Springfield, Ohio.

RADOS FOR SALE

RADIO FANS—Would you like to purchase the latest electric Coast to Coast Screen Grid Radio for less than the cost of a battery set? If so address Economy Sales Co., Pa. Ave. Sta., Wash. D. C.

ORIGINAL BALDWIN PHONES, tested and guaranteed, \$3.65, postpaid, Blan, the Radio Man, 89 Cortlandt Street, New York City.

RADIO RECEIVING TUBES, by Moyer and Wostrel, first edition just off the press. No radio service man, experimenter or student of radio should be without this authoritative book on the principles and applications of vacuum tubes. It answers all your questions relating to receiving, amplifying and rectifying tubes. Price postpaid, \$2.50 Radio World, 145 W. 45th St., New York.

**CONE ASSEMBLY
WITH DOUBLE MAGNET UNIT**

\$6.00



An excellent magnetic type speaker for installation in any cabinet. The unit is a double-magnet Paratone, with two magnet coils, for utmost sensitivity. Each horseshoe magnet is $\frac{3}{4}$ " thick. The magnet coils are forever protected against dust and other foreign, injurious substances, by special bakelite housings. The pin is reverse drive. The cone frame is metal. The 9" cone is specially treated buckram.

All assembled, with long cord, ready to play, Shipping weight 6 lbs. (Cat. CAS) Net \$6.00

The unit alone (cord included). It will operate any type sounding surface, including paper, cloth, wood, etc. Shipping weight 4 lbs. (Cat. UA) Net \$3.50

Guaranty Radio Goods Co.

145 West 45th St., New York City

BUILD A 36-INCH CONE—LOWEST COST FOR FINEST TONE!



\$6.00

24" KIT, SAME PRICE. Build the speaker. If not overjoyed at results, return the built-up speaker in five days and get ALL your money back!

GUARANTY RADIO GOODS CO.
145 WEST 45TH STREET
N. Y. City Just East of Broadway

**COMPLETE KIT OF PARTS
for the New, Highly Selective**

SCREEN GRID DIAMOND

(Four-Tube Battery Model)


Exactly as Specified by Herman Bernard \$29.00 Net

Guaranty Radio Goods Co.
145 West 45th Street
New York City

Just East of Broadway

SOCKET WRENCH

**F
R
E
E**

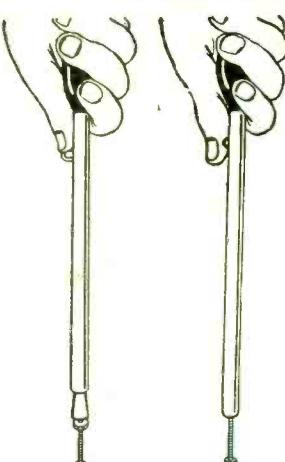

Push out control lever with knob (as at left) and put wrench on nut. Push down on handle only (at right), then turn nut left or right.

ONE of the handiest tools for a custom set builder, service man or home constructor is a BERNARD socket wrench.

It consists of a $\frac{6}{7}$ " long metal tubing in which is a plunger, controlled by a knob. The plunger has a gripping terminal (called a socket, hence the name "socket wrench") that may be expanded or contracted to fit 6/32, 8/32 and 10/32 nuts, the most popular sizes in radio.

Use the knob to push out the plunger, press down on the handle to grip the nut, then turn the nut to left for removal or to right for fastening down. Total length, distended, including stained wooden handle, 10". Gets nicely into tight places. Send \$1 for 8 weeks' mail subscription for RADIO WORLD and get this wrench FREE.

No other premium with this offer. Present subscriber may extend subscription by stating he is one, and entitle himself to this FREE premium, making \$1 remittance.

RADIO WORLD

145 WEST 45TH ST., N. Y. CITY

**BLUEPRINT of the
New, Highly Selective
Screen Grid DIAMOND
(AC MODEL)**

\$1.00

RADIO WORLD

145 West 45th Street New York City
Few Doors East of Broadway

Twice as Much for Your Money!

Send \$6.00 for one year's mail subscription for RADIO WORLD (52 numbers, one each week), and you will be given one full year's subscription for any one of the following six magazines:

Radio News (monthly)
Science and Invention (monthly)
Radio, San Francisco (monthly)

Radio Engineering (monthly)
Youth's Companion (weekly)
Boys' Life (monthly)

SPECIAL TWO-FOR-PRICE-OF-ONE COUPON

RADIO WORLD, 145 West 45th Street, New York City (Just East of Broadway): Enclosed please find \$6.00, for which send me RADIO WORLD each week for one year, 52 numbers, and also send me, without extra cost, for one year ONE of the following magazines as indicated:

- RADIO NEWS
- SCIENCE AND INVENTION
- RADIO (San Francisco)

- RADIO ENGINEERING
- YOUTH'S COMPANION
- BOYS' LIFE

[Put a cross in the proper square above. Fill out coupon and send \$6.00. If you are a subscriber for RADIO WORLD or for the other magazine you select, or both, check off squares below, as left.]

Present RADIO WORLD subscriber may renew under this offer. If renewing, put a cross here

If renewing for the other magazine you select, put a cross here

Name.....

Street Address.....


City..... State.....

THIS OFFER EXPIRES AT NOON ON JUNE 15TH, 1929

YOU MUST GET THIS BOOK!

DRAKE'S RADIO CYCLOPEDIA
(New Edition)

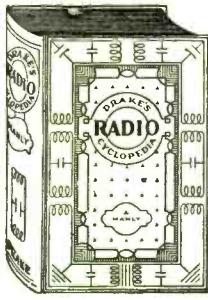has been developed to answer the questions of service men, custom set builders and home constructors, of experimenters, students, salesmen and operators of receiving equipment and to allow all these to have instant access to the information they want. The author, Harold P. Manly, has collected and translated into plain English the material formerly obtainable only from dozens of scattered sources.



BOOK IS 2 $\frac{1}{2}$ " THICK,
WEIGHS 3 $\frac{1}{4}$ LBS., 1,025 ILLUSTRATIONS.

name under which the information might be classed.

This alphabetical arrangement lets the experienced worker refer directly to the one thing in which he is interested at the moment without hunting through non-essentials. The needs of the beginner are cared for.

The important articles deal primarily with receivers and reception. They do not stop with the electrical end, but go also into the mechanics of construction.

Every new thing in radio is covered in detail.
1,680 Alphabetical Headings from A-battery to Zero Beat
1,025 Illustrations, Diagrams, Layouts and Graphs
920 Pages. Each 6 by 9 inches
240 Combinations for Receiver Layouts

OF THE PRINCIPAL ARTICLES

159 Concern service men, 129 help the set builder, 162 help the experimenter, 155 interest the student, 75 assist in sales work, 73 interest set owners.

GARANTY RADIO GOODS CO.
145 W. 45th St., New York, N. Y. (Just E. of 8'way)

Gentlemen: Please mail me at once the new (second) edition of "Drake's Radio Cyclopedias," by Harold P. Manly, just published, with all the latest technical information in it. I will pay the postman \$6.00 plus a few cents extra for postage. If I am not delighted, I may return the book in five days and you will promptly refund my purchase money.

Name.....

Address.....

City..... State.....

5-DAY MONEY-BACK GUARANTY!

DYNAMIC BAFFLE

Completely built up, for any type dynamic chassis. State what make dynamic you want it for. Cane sides, open back. \$12.00
De luxe finish. Size, 24x24 inches.....

GARANTY RADIO GOODS CO.

145 West 45th Street, New York City

HBH Unit

ALL acoustical and radio engineers agree that the balanced armature type of loudspeaker unit is the best, the most sensitive and the most faithful of all magnetic units. But it is only in the HBH unit that superior designing skill, scrupulous care in the selection of the best materials, and extreme accuracy of manufacture have been combined and co-ordinated so as to bring out all the possibilities of the principle of the balanced type unit.

any magnetic speaker requires a strong permanent magnet for its operation. The strength of the HBH unit is assured by the use of a long magnet of large cross-section, made of specially selected, high coercive-force steel, forged under the lowest heat possible, scientifically tempered in oil and aged.

The making of a permanent magnet requires a highly specialized skill. It must be forged, cut and tempered with as few heatings as possible, and no heating must exceed a certain temperature if the magnet is to retain its strength and permanence. Another important feature of the magnet which enhances its strength and permanence is that NO HOLES ARE CUT IN IT. The magnet is one solid piece of steel and the pole pieces are clamped firmly to the steel by screws in the die cast harness holding the pole pieces and the armature.

The sensitivity and efficiency of the unit are enhanced by the use of laminated, properly tapered silicon steel pole pieces. Eddy current losses are thus reduced to a vanishing minimum and all the force is concentrated on the ends of the armature.

The armature itself is made of carefully annealed soft iron, thus eliminating any residual magnetization and reducing eddy currents and hysteresis losses to a very small percentage of the energy involved in the operation of the unit. The armature is made short and heavy to enhance its effectiveness in translating electro-magnetic energy into sound.


Nobody ever returned an HBH unit because of dissatisfaction with its performance! It stands up and delivers and continues to deliver. You can put 150 volts right through the magnet coils, steadily, without danger of the coil breaking. You don't need any extra power to operate this unit—as you do with dynamics—but get full efficiency at lowest cost and greatest economy.

Put this unit in your cone or cloth speaker in place of the unit now there and marvel at the difference! You will then recognize the technical superiority of this unit in terms of tone value and volume. It produces so much more volume than most other units that it makes distant stations sound like locals.

Order a unit today! Send \$4.00. Try the unit ten days. If not overjoyed, return it for full refund. Otherwise take 90 days to pay the extra \$1.95.

10-day money back guaranty!

90 days to pay in full!

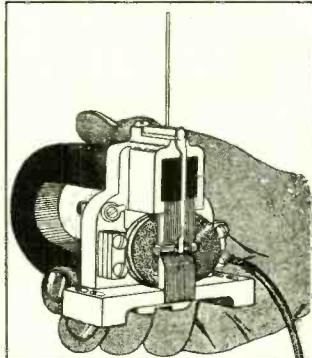

The HBH Unit, representing the most skillful and sturdiest magnetic unit design. Mfgd. under BBL License.

Price \$5.95
Moulded bracket (extra) 65c

Guaranty Radio Goods Co.,
145 West 45th Street, N. Y. City
(Just East of Broadway)

Please ship one HBH Unit only on 10-day money-back guarantee; at \$4.00 down, balance of \$1.95 in 90 days, unless I return the unit in 10 days for full refund of \$4.00.
 Please ship moulded bracket also at 65c.

Name
Address
City
State

New Powertone

Cone or Cloth Diaphragm Speaker Unit

With 5-foot cord, less bracket, \$3.00
ipex, chuck and nut. Cat. PA.

New Moulded tri-foot bracket, fits Powertone, Polo, B.B.L., Brielle, Paratone and other units. Cat. BA 65c
Apex, Thumbscrew and Chuck. Cat. AA 10c
(Note: Cat. AA not sold alone.)

You Cannot Buy a Better Unit at Anywhere Near This Price!

The 1929 Model Powertone Unit, that drives any cone or similar type speaker, is an extremely sensitive and faithful reproducer. The magnet coil (the black ring under the pin in illustration) is wound to higher impedance than is ordinarily encountered. Volume is greater. The unit has an adjustable armature.


Guaranty Radio Goods Co.,
145 West 45th Street, N. Y. City
(Just East of Broadway)

Please mail me at once C.O.D. (Check off).
 One Powertone Unit alone, Cat. PA @ \$3.00.
 One Tri-foot Bracket, Cat. BA @ 65c.
 One Apex, one Chuck, one Thumbscrew, Cat. AA @ 10c.

Name
Address
City State

"BRUNO" COILS

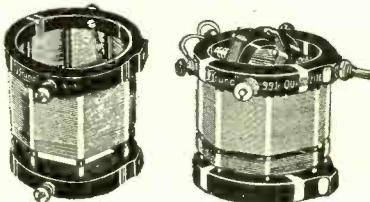Wound on quartzite glass;
low-loss construction; high
gain per stage.



99RF \$2.50
99 TUNER \$3.75

99RF is useful as an antenna coil where high selectivity is desired and as an inter-stage coupler for all tubes, battery or AC, except screen grid tubes. Tunes with .0005 mfd. only.

99 Tuner is a three-circuit coil for any standard circuit using a rotatable winding. Tunes with .0005 mfd. only.

Guaranty Radio Goods Co.
145 West 45th Street, New York City

Blueprint of the AC Diamond

BUILD this 4-tube receiver, using one 222 tube, two 227 and one 112A (or 171A), and enjoy tone quality, selectivity and ease of control. The official blueprint gives the picture diagram life size, both top and bottom views; also schematic diagram and list of parts. You can use your present B eliminator externally, but the filament transformer is a part of the circuit.


Enjoy the convenience of AC operation, and still have just as selective and sensitive receiver, by building the AC Diamond. If you have 110-volt, 50 to 60 cycle AC house current, then this is the circuit for you. Fine performance. No hum.

Radio World, 145 W. 45 St., N. Y. City (Just East of Broadway)
 Inclosed please find \$1.00 for which send at once official blueprint of the 4-tube AC Diamond.
 30c for the March 23d and 30th issues (1929) describing this circuit.
 \$3.00 for 6 months subscription for Radio World. Send blueprint and two AC Diamond issues FREE.

NAME
ADDRESS
CITY STATE

PLUG AND CABLE for any SHORT WAVE ADAPTER

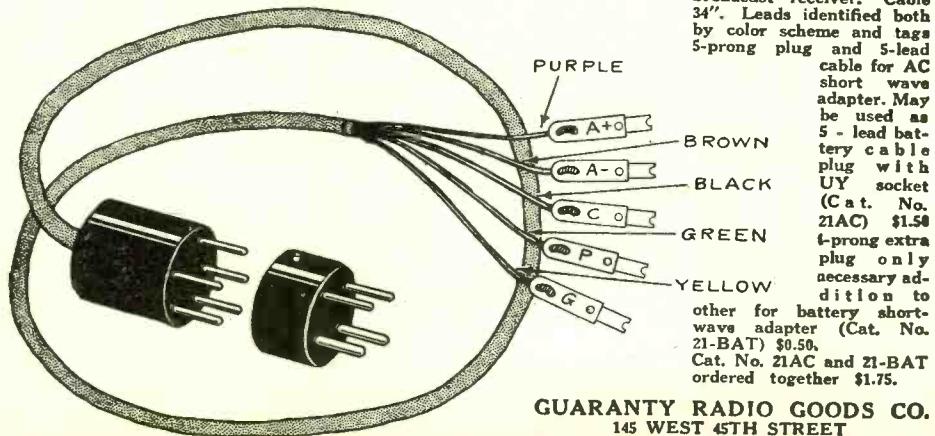May also be used as a 5-Lead Battery Cable and Plug, in conjunction with a 5-prong (AC227) socket.



GUARANTY RADIO GOODS CO.
145 WEST 45TH STREET
New York City Just East of Broadway

SUBSCRIPTION DEPARTMENT
RADIO WORLD
145 WEST 45TH ST., N. Y. CITY


SUBSCRIBERS!

Look at the Expiration Date on Your Wrapper

Please look at the subscription date stamped on your last wrapper, and if that date indicates that your subscription is about to expire, please send remittance to cover your renewal.


In this way you will get your copies without interruption and keep your file complete.

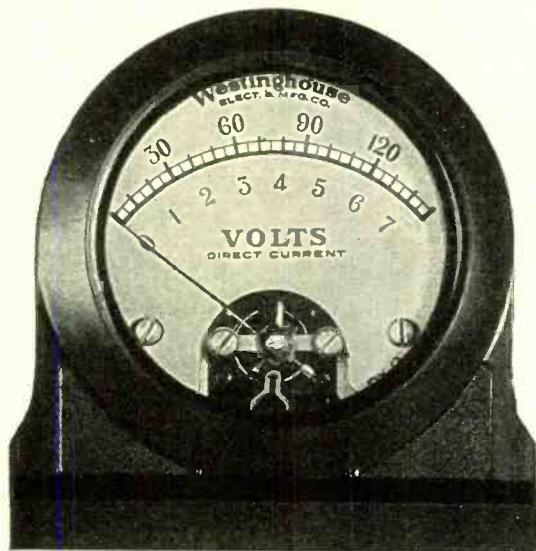Westinghouse 0-7½, 0-150 VOLT-METER FREE!



This beautiful Westinghouse meter given FREE! Read generous offer!

Filament Transformer

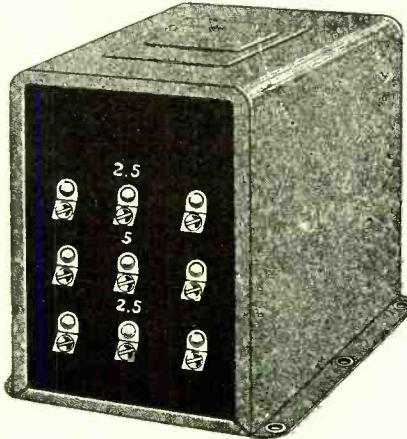

The heater type tube draws 1.75 ampere at 2.5 volts. If several such tubes are used a heavy-duty filament transformer is necessary. The top 2.5-volt winding of this filament transformer easily carries NINE AMPERES, or enough current for five heater type tubes. The bottom 2.5-volt winding stands four amperes, or enough current to heat TWO MORE such tubes, a total of SEVEN TUBES! The power tube, if of the 5-volt type, may be heated from the 5-volt central winding. 5-volt power tubes in push-pull may be heated from this winding.

All three windings are tapped at the exact electrical center. This precision location, made with the aid of an impedance bridge, accounts for absence of hum otherwise caused by the last tube when heated directly with AC. The heater type tubes are indirectly heated by AC, since the filament that glows is fed by AC but communicates heat to the cathode or electron emitter.

The heater type tube is represented by the 227, excellent as radio amplifier and audio amplifier, and the exclusive type of AC detector tube. Also the new AC screen grid tubes, with the same filament voltage and current, are of the heater type.

The transformer is beautifully finished in cracked glossy black, with bakelite front, and comes equipped with 32-inch AC cable with plug. Six riveted mounting holes for baseboard or subpanel. Size, 3 1/4 in. high, 2 1/2 in. wide, 3 in. deep. Shipping weight, 6 lbs.

Cat. F226A, for 50-to-60 cycles, 105-to-120 volts AC, Net Price \$6.00


Guaranty Radio Goods Co.
145 West 45th St.
N. Y. City

Double range direct current meter, 0-7½ volts legible to ¼ volt, and 0-150 volts, legible to 5 volts. The d'Arsonval Movement (dynamic principle) is used. Resistance is about 100 ohms per volt. A mirror strip, for observing the needle so as to hide its own reflection, facilitates closest reading, in conjunction with knife-edge. End-stops are built in. So is a zero corrector. The casing is moulded bakelite. The meter is illustrated full size. At rear are three posts—the common minus and the two positive posts. A connecting cable is furnished with each meter, lugs at one end, tip plugs at other. Send \$6 for year's subscription for Radio World (52 numbers) and get this genuine Westinghouse table model meter FREE! Present subscribers may renew under this offer by stating subscription expiration date and enclosing \$6.

Radio World, 145 W. 45th St.
New York City

O-600 V. AC and DC High Resistance Meter

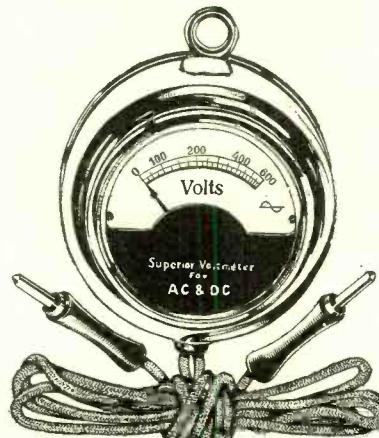Same Meter Reads Both AC and DC
Accurate to 1 per cent.



The O-600 volt AC and DC meter (Cat. No. 600), with 3-ft. cord, de luxe tips and hanger \$7.00.

THE output voltages of all B eliminators, the voltages of all B batteries, as well as the house current line voltage, whether AC or DC, and the voltage across power transformer secondaries, can be accurately measured by this meter. The full scale is 0-600 volts, and this same meter measures both AC and DC. Since it is a high resistance meter, of extraordinary range, and accurate to 1% plus or minus, it is advisable to get this meter for your testing purposes, since it is like two meters in one—AC and DC. You can find trouble more quickly without it you can't tell if a power transformer secondary is delivering voltage. 10-day money-back guarantee.

GUARANTY RADIO GOODS CO.
145 West 45th Street, N. Y. City.
(Just East of Broadway)

Please ship at once one 0-600 volts AC and DC high resistance voltmeter, accurate to 1% plus or minus (Cat. No. 600); meter equipped with 3-ft. cord, moulded tip receptacles, tips and hanger.

[Put cross in proper square below.]


- \$7.00 enclosed
 I will pay postman \$7.00 plus few cents extra for postage

Name

Address

City State

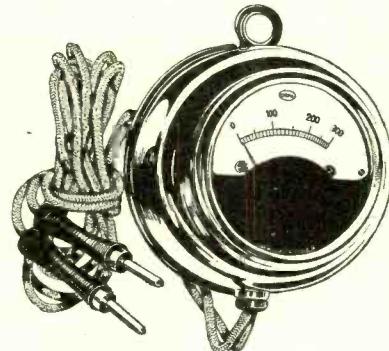Individual METERS For Portable or Panel Use



High resistance 0-300 Voltmeter, accurate to 1%. Measures any DC voltage to 300, including B eliminators. Provided with 30' cord, with luxurious jack tips and hanger. Meter full nickel de luxe finish. No. 346F. Meter, same as above, but 0-500 volts, \$8.00. No. 347F, same as above, but 0-500 volts, \$8.00.

\$4.50

POCKET AND PORTABLE VOLTMETERS

| | |
|--|--------|
| No. 8—For testing A batteries, dry or storage, 0-8 volts DC scale..... | \$1.00 |
| No. 10—For testing A batteries, dry or storage, 0-10 volts DC scale..... | 1.00 |
| No. 13—For testing A batteries, dry or storage, 0-18 volts DC scale..... | 1.00 |
| No. 50—For testing B batteries, dry or storage, but not for B eliminators, 0-50 volts DC scale..... | 1.00 |
| No. 59—For testing B batteries, dry or storage, but not for B eliminators, 0-100 volts DC scale..... | 1.00 |
| No. 40—For testing A and B batteries, dry or storage, but not for B eliminators; double reading, 0-8 volts and 0-100 volts DC scale..... | 1.75 |
| No. 42—For testing A batteries, dry or storage, but not for B eliminators; 0-150 volts DC scale..... | 1.50 |
| No. 348—For testing AC current supply line, portable, 0-150 volts..... | 4.00 |

PANEL AC VOLTMETERS

(Panel meters take 2-5/64" hole)

| | |
|--|--------|
| No. 351—For reading 0-15 volts AC..... | \$2.25 |
| No. 352—For reading 0-10 volts AC..... | 2.25 |
| No. 353—For reading 0-8 volts AC..... | 2.25 |

(See No. 348 under "Pocket and Portable Voltmeters")

PANEL VOLTMETERS

| | |
|--|------|
| No. 335—For reading DC voltages, 0-8 volts, \$1.00 | |
| No. 310—For reading DC voltages, 0-10 volts, 1.00 | |
| No. 318—For reading DC voltages, 0-16 volts, 1.00 | |
| No. 328—For reading DC voltages, 0-8 volts, 1.00 | |
| No. 337—For reading DC voltages, 0-50 volts, 1.00 | |
| No. 339—For reading DC voltages, 0-100 volts, 2.25 | |
| No. 342—For reading DC voltages, 0-150 volts, 2.25 | |
| No. 346—For reading DC voltages, double reading, 1-8 volts, 0-100 volts..... | 1.50 |

VOLTMAMMETERS

| | |
|--|--------|
| No. 18—For testing amperage of dry cell A batteries and voltage of dry or storage A batteries, double reading, 0-8 volts, and 0-40 amperes DC..... | \$1.25 |
| No. 35—For testing amperage of dry cell A batteries and voltage of B batteries (not B eliminators); double reading, 0-50 volts, 0-40 amperes DC..... | 1.50 |

PANEL MILLIAMMETERS

| | |
|--|--------|
| No. 311—For reading 0-10 milliamperes DC..... | \$1.75 |
| No. 395—For reading 0-20 and 0-100 ma. DC..... | 1.50 |

VOLTAGE REGULATOR

| | |
|---|--------|
| No. 218—For preventing excess voltage on the filament and cathode of AC tubes, by compensating for excess line voltage..... | \$5.00 |
|---|--------|

POCKET AMMETER

| | |
|---|-----|
| No. 1—For testing dry cells, 0-50 ampere DC scale pocket meter..... | .75 |
|---|-----|

Immediate Shipment

GUARANTY RADIO GOODS CO.
145 West 45th Street, New York City.
Just East of Broadway

Send me the following individual meters (quantity in square):

- | | | |
|--|--|--|
| <input type="checkbox"/> Cat. No. | <input type="checkbox"/> Cat. No. | <input type="checkbox"/> Cat. No. |
| <input type="checkbox"/> Cat. No. | <input type="checkbox"/> Cat. No. | <input type="checkbox"/> Cat. No. |

NAME

ADDRESS

CITY..... STATE.....

TEN-DAY MONEY-BACK ABSOLUTE GUARANTY!

A COMPLETE CATALOG

containing detailed information on condensers and resistors may be had free on request.

AEROVOX
BUILT BETTER
CONDENSERS AND RESISTORS


74½ Washington St., Bklyn., N. Y.

THE RESEARCH WORKER

will keep you abreast of developments in radio. It may be had free on request.

New Style DeLuxe Leatherette Carrying Case FREE with each Jiffy Tester!

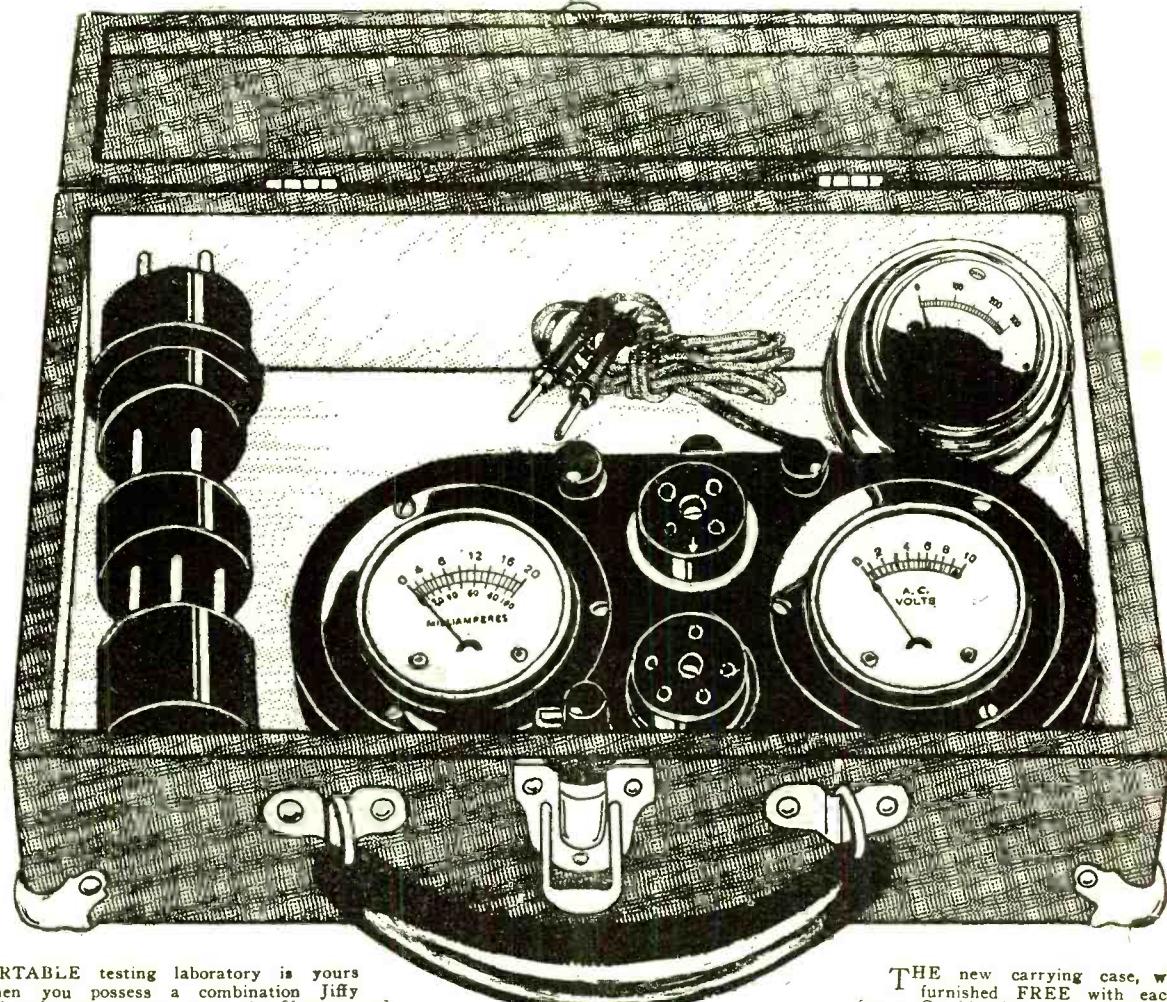This combination of meters tests all standard tubes, including the new AC screen grid tubes and the new 245 tube, making thirteen tests in $4\frac{1}{2}$ minutes! Instruction sheet gives these tests in detail.



A PORTABLE testing laboratory is yours when you possess a combination Jiffy Tester, for then you can measure the filament and plate voltages of all standard tubes, including AC tubes, and all standard battery-operated or AC screen grid tubes; also plate voltages up to 500 volts on a high resistance meter that is 99% accurate; also plate current.

The Jiffy Tester consists of a 0-20, 0-100 milliammeter, with change-over switch and a 0-10 volt AC and DC voltmeter (same meter reads both), with two sockets, one for 5-prong, the other for 4-prong tubes; a grid bias switch and two binding posts to which are attached the cords of the high resistance voltmeter; also built-in cable with 5-prong plug and 4-prong adapter, so that connections in a receiver are transferred to the Tester automatically. Not only can you test tubes, also opens or shorts in a receiver, continuity, bias, oscillation, etc. The instruction sheet tells all about these tests.

In addition you can test screen grid tubes by connecting a special cable, with clip to control grid (cap of tube) and other end of special cable to the clip in the set that went to the cap before the tube was transferred to the tester.

GUARANTY RADIO GOODS CO., 145 W. 45 St., N. Y. City. (Just East of Broadway).

- Please ship at once on 5-day money-back guaranty one "Jiffy 500," at \$14.50, consisting of
- (1) One Two-in-One 0 to 10 voltmeter for AC and DC. Same meter reads both. Scale especially legible at $1\frac{1}{2}$ to $7\frac{1}{2}$ volts. This meter reads the AC and DC filament voltages.
- (2) One DOUBLE reading DC milliammeter, 0 to 20 and 0 to 100 milliamperes, with change-over switch. This reads plate current.
- (3) One 0-500 volts high resistance voltmeter, 99% accurate; with tipped 30' cord to measure B voltages.
- (4) One 5-prong plug with 30' cord for AC detector tubes, etc., and one 4-prong adapter for other tubes.
- (5) One grid switch to change bias.
- (6) One 5-prong socket.
- (7) One 4-prong socket.
- (8) Two binding posts.
- (9) One handsome moire metal case.
- (10) One instruction sheet.
- (11) One de luxe carrying case.
- (12) One screen grid special cable.
- If 0-300 DC high resistance 99% accurate voltmeter is preferred to 0-500, put check here. Price is same, \$14.50.
- Same as above, except substitute a 0-600-volt AC and DC high resistance 99% accurate voltmeter (same meter reads both) for the 0-500 DC meter. Price \$15.50.

NAME

ADDRESS

CITY STATE


FIVE-DAY MONEY-BACK GUARANTY

THE new carrying case, which is furnished FREE with each order for a Combination Jiffy Tester, contains the entire outfit, including the three meters, cable and plug, and three adapters (one for 4-prong tubes, two for 199 tubes). This case is $10\frac{1}{2}$ " $7\frac{1}{4}$ " $3\frac{1}{2}$ " and has nickel corner pieces and protective snap-lock. The case is made of strong wood, with black leatherette overlay.

To operate, remove a tube from the receiver, place the cable plug in the vacant receiver socket, put the tube in the proper socket of the Tester, connect the high resistance meter to the two binding posts, and you're all set to make the thirteen vital tests in $4\frac{1}{2}$ minutes!

The Combination Jiffy Tester is just the thing for service men, custom set builders, experimenters, students, teachers and factories. Order "Jiffy 500." The price is only \$14.50.

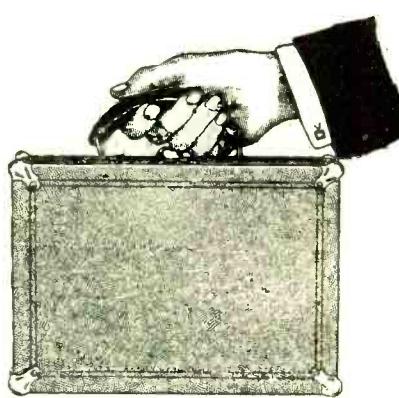If a 0-600 AC and DC high resistance meter (99% accurate) is desired, so house electricity line voltage and power transformer voltages can be measured, as well as plate voltage, instead of the 0-500 DC voltmeter, order "Jiffy 600" at \$15.50.



The new de luxe leatherette carrying case is compact and handy. Size $10\frac{1}{2}$ " long, $7\frac{1}{4}$ " wide, $3\frac{1}{2}$ " deep.

Choose Your Speaker from This Complete Array!

EXPONENTIAL TYPE HORNS




Cat. 200
\$7.50 Net

This horn has a 92-inch air column. No resonance peaks. Front, 18" x 18". Depth, 13½". Weight, 5 lbs.




Cat. 300
\$10.50 Net

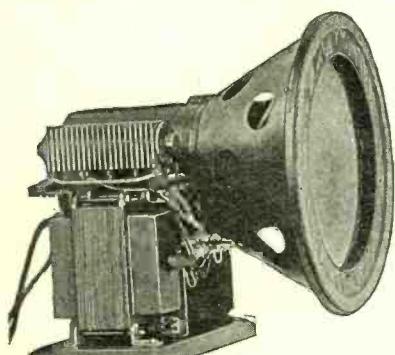The larger horn is preferable, where space permits. Air column, 120". Front, 18" x 18". Depth, 13". Weight, 7 lbs.



Cat. 110 A.C.; Price, \$20.50 Net

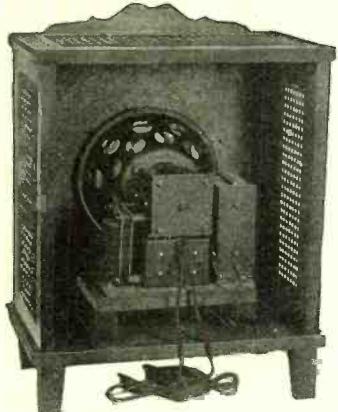

Cat. 111; Price, 11.00 Net


Cat. 110 A.C., shown inside, \$20.50 extra.

DYNAMIC CHASSES and Baffle

The dynamic speaker is the most popular one by far, and here is your opportunity to get a real fine chassis at a low price. Cat. 110 A.C. operates directly from the 110-volt A.C. (alternating current) lamp socket, to which built-in plug is connected, while the tipped cords go to your receiver output. Dry rectifier and output transformer built in this model.


Those whose place is wired with 110-volt D.C. (direct current) should use Cat. 110 D.C. @ \$17.50 net. Those who have no electricity should use the model that works from a 6-volt storage battery. Cat. 6 D.C. @ \$14.75 net.

At left is illustrated an 18" x 18" baffle, Cat. 111, with cane sides and top, for any dynamic speaker. Specify speaker. Walnut 5 ply veneer. Price \$11.00 net.

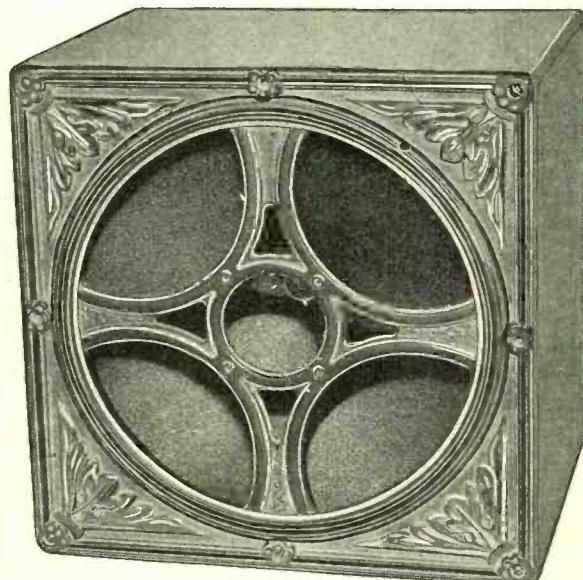


Cat. 113
Price, \$13.50 Net

New Model Polo Speaker, with five-ply veneer walnut housing, moulded, decorated metal front pieces, and containing Polo Twin Magnet Unit and Textile Cone. All ready to play. Stands 180 volts without filtering. Will work fine from any output tube, from 201A to a pair of push-pull 250s, without rattling.

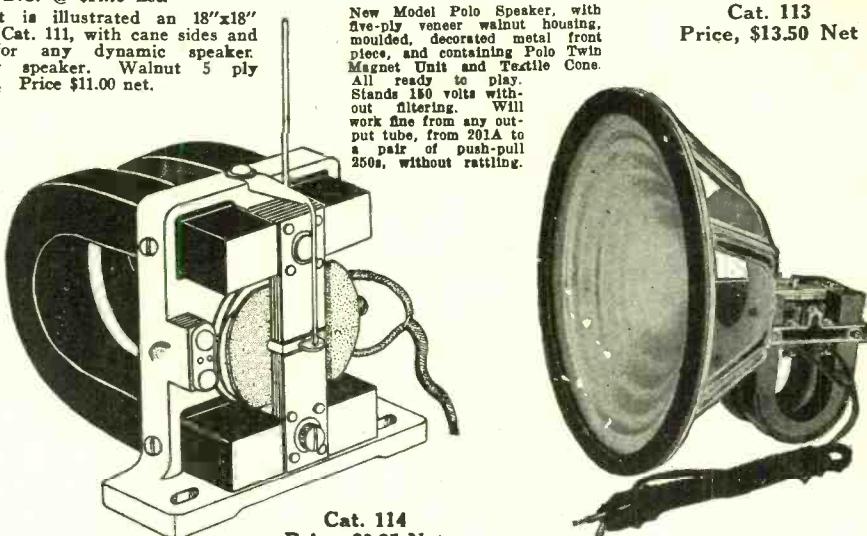

Cat. 114
Price, \$9.25 Net

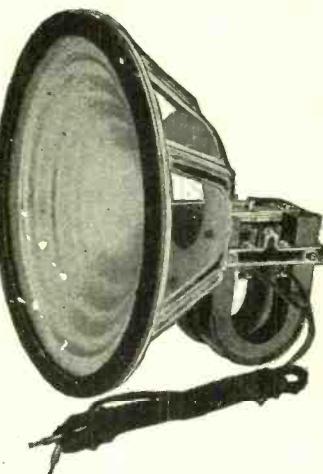Polo Twin Magnet Unit—weight, 3½ lbs., or twice as heavy as ordinary unit. Twin magnetic double sensitivity. This unit gives more volume, clearer tone, and stands the gaff. Supplied with 10-ft. cord. Cat. 114. Tri-foot molded unbreakable metal mounting bracket and apex constitute Cat. 114A @ \$8.75.



Cat. 115; Price, \$11.50 Net

Molded 9" spider, unbreakable metal, with Textile cone and felt ring and spox, and Polo Unit mounted on the assembly, which stands on own feet. Cat. 115.

FILL OUT AND MAIL COUPON

ACOUSTICAL ENGINEERING ASSOCIATES,
143 West 45th Street, N. Y. City

(Just East of Broadway)

Please send me at once on 5-day money-back guarantee the following (check off):

- Cat. No. 200
- Cat. No. 111
- Cat. No. 300
- Cat. No. 113
- Cat. No. 110 A.C.
- Cat. No. 114
- Cat. No. 110 D.C.
- Cat. No. 114A
- Cat. No. 6 D.C.
- Cat. No. 115
- Cat. No. 300
- Cat. No. 203
- Please send C.O.D.
- Please send C.O.D.
- Remittance enclosed. Please send prepaid.

Name

Address

City State

5-DAY MONEY-BACK GUARANTEE