

# SUCCESSFUL Servicing

FEBRUARY 1953

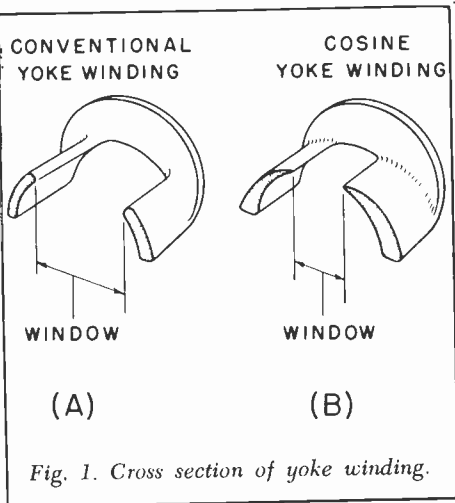


Fig. 1. Cross section of yoke winding.

In physical appearance deflection yokes for tv receivers have changed but little since the early models. However, electrically and magnetically the changes have been considerable.

In size, for instance, the first yokes were about three inches long and were designed to be used with small picture tubes having deflection angles of about 50 degrees. Present-day yokes run a maximum of two and one half inches long and are used for 66-degree and 70-degree tubes.

Electrically the old-style yokes used lower inductance horizontal coils (8 mh) while modern coils have inductances which run from 13 to 30 mh. At the same time, vertical windings have grown somewhat smaller, with inductances of about 30 to 40 mh, against the early 50 mh windings.

Magnetically, modern design employs ferrite cores in a yoke known as the *cosine yoke*. This yoke gives a notable improvement in focusing at the edges of the picture. This deficiency in performance of earlier yokes was generally ignored because of the use of smaller picture tubes. The design of these early yokes was primarily concerned with sensitivity of deflection and toward obtaining a perfectly rectangular raster with no sagging inward or bulging outward of the sides. The sagging inward is called "pincushioning" while the bulging outward is known as "barrelling."

The means employed to construct a cosine yoke involves the correct distribution of the

winding. The cross section of the winding is not uniform as in the case of older yokes (see part A of Fig. 1). The turns near the inside of the winding are in a thin layer, and pile up to successively increasing thickness as the winding progresses away from the window (see part B of the figure). As a result of this type of winding arrangement, the distribution of magnetic flux threading through the neck of the tube is more uniform than with the old-style yokes.

Because of this more uniform field, the focus of the spot toward the edges and the corners of the picture-tube raster is considerably improved.

As the electron beam, which has a definite thickness, passed through the nonuniform field produced by the conventional yoke, different portions of that beam experienced differing amounts of deflection force. As a result, an elongated spot was produced at the raster edges that resulted in an out-of-focus condition. By causing the beam to travel through the more uniform field produced by the cosine yoke, uniform deflection of all parts of the electron beam occur, and a 500 minimum amount of defocusing takes place.

The arrangement of the conventional windings around the picture-tube neck can be seen in part A of Fig. 2. The deflection coils are shown in cross section here. The horizontal windings produce a magnetic field with vertical lines of force. This magnetic field produces horizontal deflection. The vertical windings produce a magnetic field

(Continued on page 10)

## the cosine yoke

by harry e. thomas



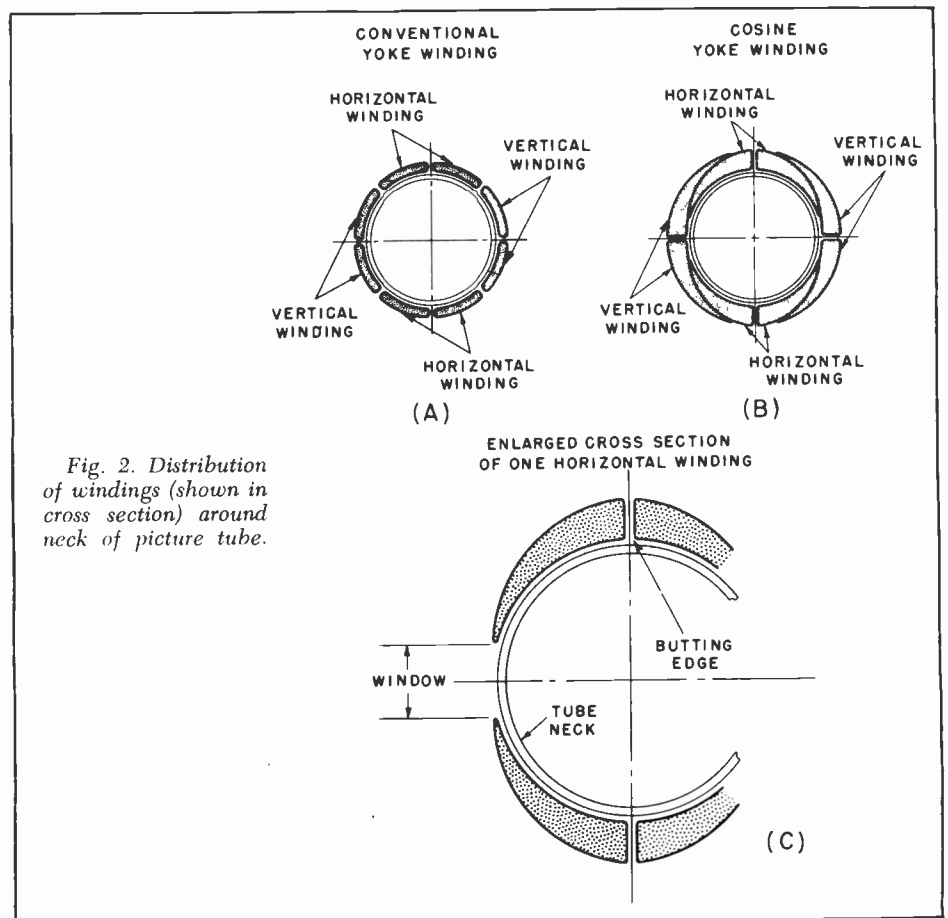


Fig. 2. Distribution of windings (shown in cross section) around neck of picture tube.

# SPRAGUE

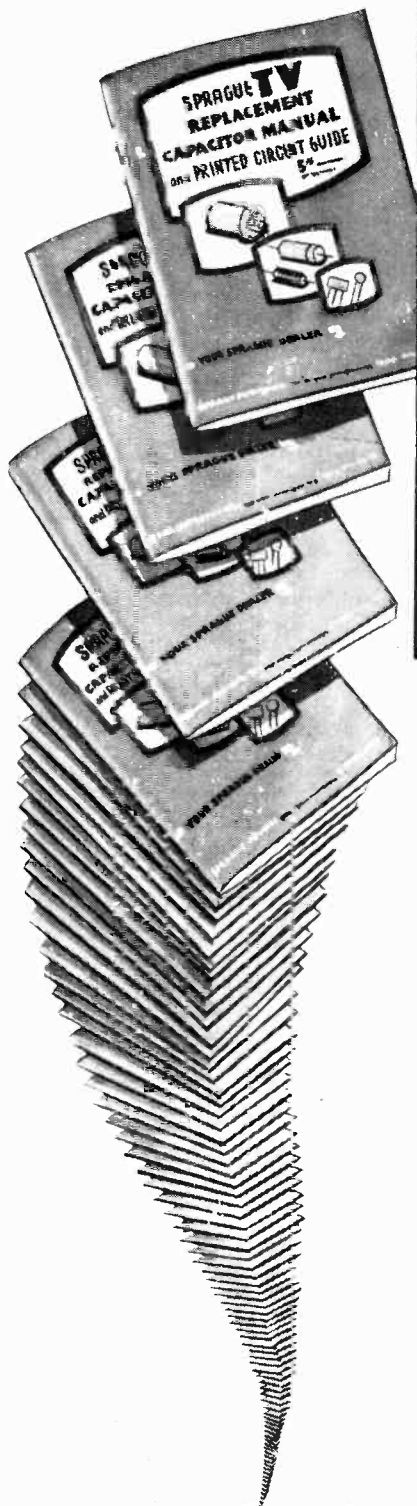

## SERVICEMAN'S DIARY... by Ben Grim

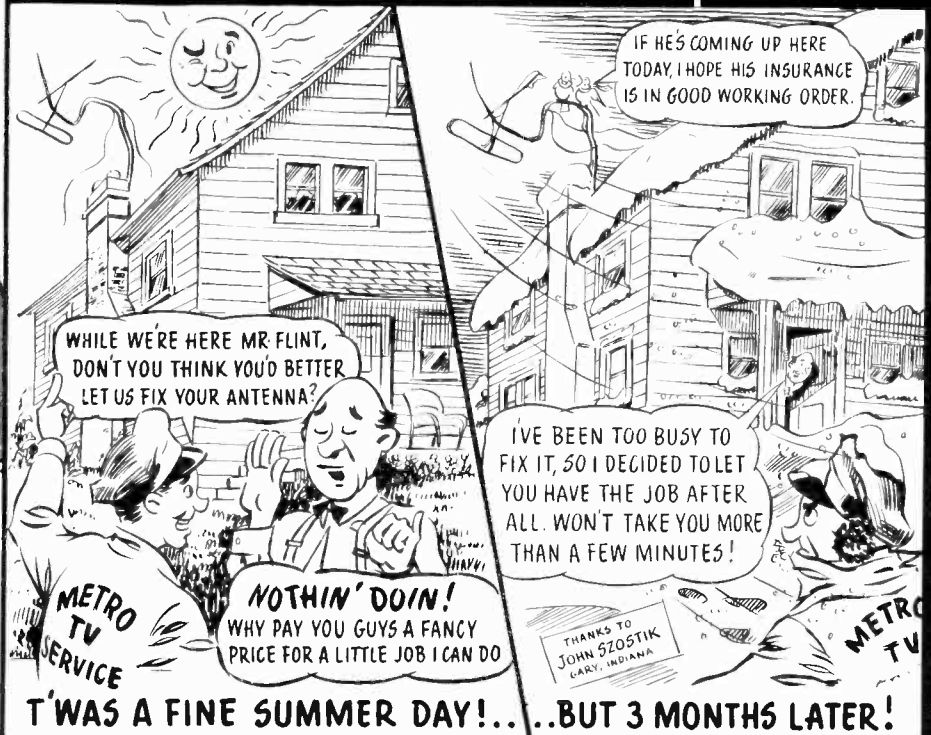

### Do you have the **NEW 5th Edition** of the **SPRAGUE TV REPLACEMENT CAPACITOR MANUAL?**

If not, get your copy from your distributor without delay!

This 44-page reference guide shows the accurate, up-to-the-minute Twist-Lok<sup>☆</sup> and Atom<sup>☆</sup> Electrolytic Capacitor replacements for 2460 receiver models by 78 set manufacturers. It's the most comprehensive of all such manuals and it's yours FREE!


Also included for the first time in this new edition is a Printed Circuit Guide for the resistor-capacitor plates used by 46 manufacturers as well as a complete capacitor color code chart, two extra features to make the Sprague TV Replacement Capacitor Manual even more invaluable to every television technician!

*P.S.* If your distributor is temporarily out of stock, you can also get copies by writing Sprague Products Co., 55 Marshall St., North Adams, Mass. Please enclose 10c to cover handling and postage.


<sup>☆</sup>Trademark

# SPRAGUE

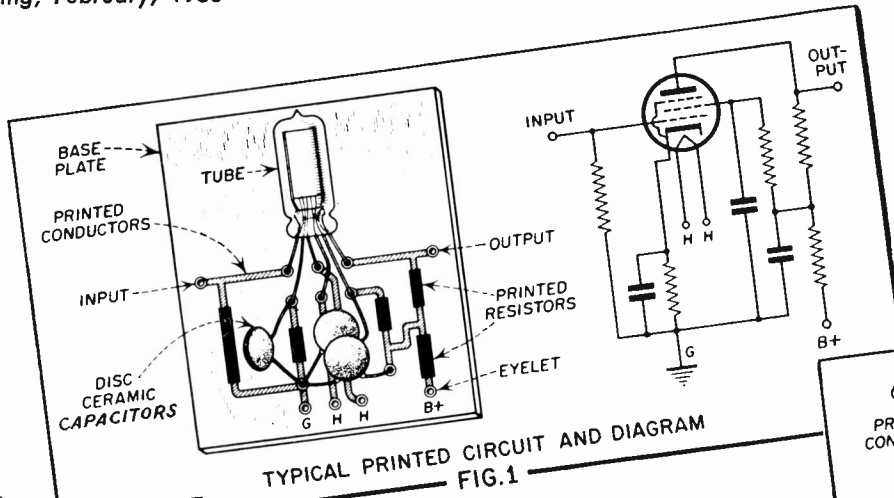
## WORLD'S LARGEST CAPACITOR MANUFACTURER



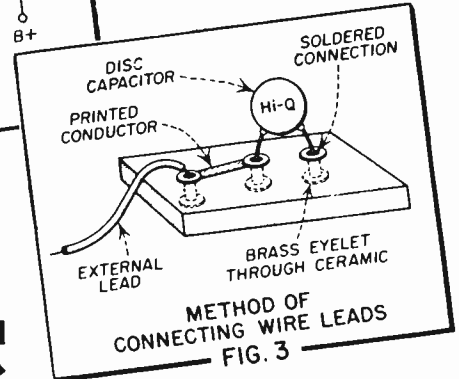TYPICAL PRINTED CIRCUIT AND DIAGRAM  
FIG. 1



METHOD OF CONNECTING WIRE LEADS  
FIG. 3

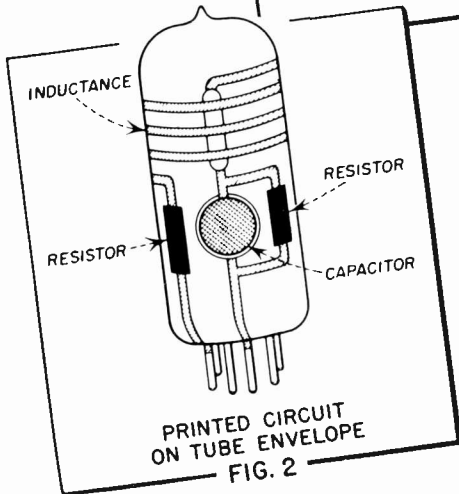

PRINTED CIRCUIT ON TUBE ENVELOPE  
FIG. 2

# PRINTED ELECTRONIC CIRCUITS\*

by the Engineering Department,  
Aerovox Corporation

\*This material appeared originally in "The Aerovox Research Worker".

THE reproduction of electrical circuits on insulated surfaces by various printing techniques has become a standard method of fabricating small, lightweight, economical electronic devices. The increased emphasis placed by the Armed Services and industry on miniaturization and ruggedness of electrical components has caused this innovation to assume vital importance. Printed circuitry is no longer confined to a few military devices and hearing aids, but may now be encountered in a large number of everyday equipments. These include speech amplifiers, portable receivers, citizens two-way radios, television receiver front-ends, f-m receivers, and many others. For this reason, a working knowledge of the design, production, and maintenance of such circuits will be a valuable asset to any worker in the electronics field. This article is concerned with a discussion of the general types of printed circuits, the relative advantages of each, and methods of effecting servicing repairs.

The use of printed circuitry has been revolutionary not only because it permits the fabrication of extremely small and rugged electronic components, but also because it reduces the production of such components to a simple, rapid operation which is almost completely devoid of the

possibility of human error. By this method, a relatively unskilled operator can reproduce literally hundreds of complex units in the time formerly required to make one unit by old-fashioned "wire-by-wire" soldering techniques. In addition to electrical conductors, critical circuit components such as resistors, capacitors, and inductors can be "printed" into the circuit in the same operation and held to close, reproduceable tolerances. Fig. 1 shows a typical printed circuit and its schematic diagram.

Printed circuits are classified according to the method used to reproduce them. There are, at present, six general types. These processes are: painting, spraying, vacuum evaporation, chemical processing, metal stamping, and powdered metal dusting. Each of these general categories will now be discussed in some detail.

## Printing Techniques

Probably the most widely used process for producing printed circuits is the *painting* technique. In this method, the conductors and other components of the circuit being fabricated are painted on the insulating surface which acts as the base for the circuit. The paint may be applied by hand with a brush, although in production operations the silk-screen stenciling process is more frequently used. Thin ceramic or plastic sheets may be employed for the base, or a metallic surface covered with an insulating lacquer may be used. In special instances, the glass envelope of a vacuum

tube has been utilized as a base for its associated printed circuit. See Fig. 2.

The paint used for electrical conductors consists of a powdered metal such as copper or silver in suspension in a liquid binder. This conducting paint is applied to the surface of the insulating base to form the "wires" of the circuit. Other paint, made up of a resistive material such as carbon, may be applied in specific amounts to form resistors. Capacitors may be made by printing the plates on opposite sides of the base plate, if the required capacitance is small. Otherwise, small capacitors (such as the Aerovox Hi-Q BPD type disc ceramic) are connected to the printed circuit as in Fig. 3. It is interesting to note that these capacitors are manufactured by processes which are essentially printed circuit techniques. Inductances are produced by painting spirals of conducting paint on the surface of the ceramic or other base material. "Cross-overs" in the wiring are made by planting one conductor directly over the other with a layer of insulating material such as lacquer between, or by "detouring" one conductor to the other side of the plate for a short distance by means of metal rivets or eyelets through the insulator, as is illustrated in Fig. 4.

When all printed components have been painted in place, the entire assembly is "fired" at an elevated temperature to fuse the metal particles together and bond the circuit to the base plate. Temperatures ranging from room temperature for plastic bases to as high as 800 degrees C. for ceramics are used.


Vacuum tubes, external leads, and other components not printed are soldered to eyelets in the base plate as in Figs. 1 and 3. To take maximum advantage of the space-saving properties of printed circuits, tubes of the subminiature type are usually employed.

(Continued on page 17)
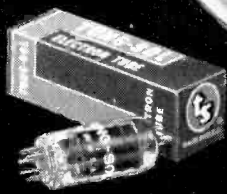
# USE TUNG-SOL TUBES FOR TROUBLE-FREE SERVICE!

TUNG-SOL "QUALITY CONTROL" recognizes but one standard. All Tung-Sol Tubes meet the highest original equipment requirements of leading radio and tv set manufacturers.

TUNG-SOL ELECTRIC INC., Newark 4, N. J.  
Sales Offices: Atlanta • Chicago • Culver City • Dallas  
Denver • Detroit • Newark



No Call-Backs for me, pal

Here's a real lively "stopper" to attract attention to your place of business and emphasize the quality of your service. Colorful—bright red and two shades of blue. 15 inches high. Your jobber salesman will tell you how to get one.

TUNG-SOL MAKES ALL-GLASS SEALED BEAM LAMPS, MINIATURE LAMPS, SIGNAL FLASHERS, PICTURE TUBES, RADIO, TV AND SPECIAL PURPOSE ELECTRON TUBES

Please mention *Successful Servicing* when answering advertising.

# Successful SERVICING

REG. U.S. PAT. OFF.

A house organ of John F. Rider Publisher, Inc., dedicated to the financial and technical advancement of electronic maintenance personnel

VOLUME 14 NUMBER 2

FEBRUARY, 1953

**JOHN F. RIDER, Publisher**  
**ANNETTE M. TRICARICO, Editor**  
 Stuart Flexner, Assistant Editor  
 Milton S. Snitzer, Technical Advisor

*Advertising Representative*

H. J. Olso & Co.  
 3951 Grand Central Terminal  
 New York 17, N. Y.  
 MUrray Hill 6-4670



## *Curtain Time*

### Transistors and Replacement Parts

The last few months have witnessed increased activity in the publicity given to transistors and other semi-conductors. In fact, almost the entire November, 1952 issue of the *Proceedings of the IRE* was devoted to this fabulous device. One manufacturer already is offering one type of transistor for sale to experimenters.

No one has any doubt about the impact of the transistor on the entire electronic industry. This will occur when there are no uncertainties about its reproducibility in large quantities and with consistent performance characteristics — application to all present uses of vacuum tubes over the full gamut of frequencies. When all of this comes to pass, the effect will be the equivalent of a revolution in electronic components and design.

The miniaturization of all equipment will be one manifestation, although this program involving subminiature vacuum tubes and transistors, has been going on for years under the impetus of the Armed Forces equipment requirements. The trend to transistors or some other devices made of materials showing similar behavior will, without question, shrink the physical dimensions of electronic equipment to a small fraction of even the smallest vacuum tube device made today.

Forgetting vacuum tubes for the moment, a tremendous effect seems likely on companion units presently being used to supply operating power to the vacuum tubes. A great portion of the energy supplied to vacuum tubes is wasted in heat. This is not so in transistors; hence those devices which supply operating power to the vacuum tubes in equipment are subject to change to a great degree — if not elimination in their present form.

All of this will not happen overnight. Engineers involved in the research of transistor and similarly behaving materials are very reluctant to forecast when the change from vacuum tubes to some

semi-conductor type of device will take place; estimates range from 4 years to 8 years. But who can tell? In the meantime, present-day designed equipments are still being sold in great quantities to the public. It is not a wild guess to say that before any major engineering change takes place in electronic equipments — television receivers especially — the nation's houses will contain from 40 to 50 million units, if not more. These receivers will require replacement parts for a long time, regardless of what radical engineering change may take place at the end of four or five years.

It is said that color television is on its way. It is highly doubtful if it will be a transistor-equipped receiver when it arrives, despite the fact that such a black and white receiver equivalent to 34 tubes has been shown already. All sound evaluations contend that the arrival of color television in a year or two, will still make use of vacuum tubes and present types of complementary equipments.

All in all, a tremendous market for replacement parts exists — and is destined to increase substantially in the immediate future. The concern which need be felt by those who are producing and selling these parts is a matter of the nature of their planning. How far in the future do they look? The receivers in the field — all kinds of receivers — must be serviced, and they require replacement parts. The table model radio displaced the console radio — but those consoles which were in people's homes were not discarded. They were serviced until television came along to grab the public's interest.

The birth of a "hot" war may change some of this. If past performance is any sort of a barometer, an acceleration of technological development is a certainty. A part of this will be the transistor or its equivalent because of the unbounded interest in miniaturization of electronic devices for military uses. If this occurs, semi-conductor devices will emerge full fledged much sooner than would be the case with just a cold war in progress. But even then, public holding in electronic equipment will not be thrown away; they will require service and so, replacement part production, selling, and installation.

Summarizing the whole thing, there is every reason why all individuals affiliated with the electronic industry should take note of the progress being made in the semi-conductor phase of the art. The tube manufacturers have been doing this for a long time. But we can't see any reason for concern about inventories in parts manufacturing establishments, parts jobbers stocks, or service technician's parts stocks. Everyone will sell what they have, and what they will make and buy, for years to come.

### TV Service

Questions asked here and there among those who are in a position to know indicate a definite improvement in the level of competency being demonstrated by TV service technicians. Taking into account the television receiver sales during 1952, and the total number in use across the nation, the proportion of complaints has decreased. This is especially true in the largely populated areas, where greatest density of receivers prevails.

### Chassis Coding

The matter of chassis coding is still a problem in the field. In view of the practice by many television receiver manufacturers to show different schematics representative of different production runs, especially when changes have been made, it is of the utmost importance that the service technician be able to correlate correctly, with the appropriate schematic, the chassis in for service.

We don't know what the answer is, but isn't it possible to establish some common method of coding and also a common location for the coding symbol on the chassis? The former may be difficult because of the different systems firmly rooted in the factories, but the latter is not faced with the same problems. Even if the entire issue is not settled for some time, taking care of one detail at a time would help.

*John F. Rider*

# Greater than Ever!



Accepted as outstanding... now with the ADDED features this BOOSTER leads the field. The automatic switch makes it possible to shut off the TV set by switching off the booster... the stand-by position keeps the booster in readiness for use... and the extra outlet adds versatility to the booster.

## THE RADIART TV Booster

**with these added features:**

- ★ Automatic On-Off Switch
- ★ Stand-By Position — eliminating "warm-up" time for booster
- ★ EXTRA 110 volt convenience outlet — plug in rotor or any appliance

*and these too: High Signal-to-Noise Ratio ★ Wide Band Amplification ★ Complete Neutralization for Stable Operation ★ Mahogany Grained Polished Finish ★ Completely Enclosed for Dust-Free Operation ★ 15 Degree Tilt for Easier Visibility.*

It's the Perfect Partner to the CDR ROTOR... the TV TWINS



SUBSIDIARY OF **THE RADIART CORPORATION** CLEVELAND 13, OHIO

VIBRATORS • AUTO AERIALS • TV ANTENNAS • ROTORS • POWER SUPPLIES

Please mention *Successful Servicing* when answering advertising.

# Replacement Parts in TV Receivers

## Part I-Capacitors (cont'd)

*This is the fourth in a series of articles on "Replacement Parts in TV Receivers." "Capacitors" will be continued next month.*

by John F. Rider

Preceding paragraphs dealt with the identification of capacitors according to their physical construction. This base gives rise to the major type categories. But in the final analysis the suitability of a capacitor for a particular use is only in part determined by its physical construction. Every capacitor within a major type group is not necessarily suitable for every application even if the function indicates the general category of type from which the selection should be made. Still another basis of selection must be applied in order to establish suitability.

For instance a mica capacitor is generally considered to be a suitable type of capacitor for use in tuned circuits. The same may be said for the ceramic dielectric unit. Yet every version of these two general types of units is not suitable for use in every resonant circuit. The same applies to the paper dielectric and the electrolytic capacitors relative to portions of the TV receiver which contain these types. The final indicator in the suitability of use are the constants of the capacitor.

### Constants of Capacitors

The suitability of a capacitor for a particular application is determined by many factors. Among these are

- a. physical size
- b. capacitance
- c. operating voltage rating
- d. allowable variation in capacitance from rated value
- e. required change in capacitance with temperature
- f. allowable change in capacitance with temperature
- g. maximum temperature for normal operation
- h. permissible electrical losses
- i. insulation resistance
- j. resonant frequency
- k. test voltage rating
- l. leakage current (if applicable)

and several others.

With the exception of the physical dimensions, the other factors express the electrical qualifications of the component, and when stated in particular standardized terms, are the constants of the capacitor. Some of the terminology already listed are examples of terms which are constants, as for instance, items *a, b, c, i, j, k* and *l*. Item *d* is expressed by the constant "capacitance tolerance"; item *e* is "temperature coefficient" and item

*f* is "tolerance in temperature coefficient". Item *g* is expressed by "operating temperature", and item *h* by "power factor" and several others.

Because of the limitations in capabilities imposed by physical construction, or because of the capabilities given to a capacitor by its physical construction, each main type of capacitor has its own set of constants. Some of the constants are common to all types of capacitors because of the very nature of the device. A few examples of these are the physical size, the capacitance, the operating voltage and the electrical losses. When expressed numerically, they may differ widely — again because of the constructional features — but each set of constants does include them.

The selection of a particular capacitor for a particular use is a matter of comparison of the constants of the contemplated capacitor with the requirements of the circuit where it is to be used. At first thought this may seem to be a major problem to the service technician. Actually it is not so, because it already has been done by the individual who designed the circuit. In fact the entire problem is simplified because the receiver manufacturer's service literature contains the electrical specifications for the capacitors required at every point. All of the constants are not given, but a familiarity with the general order of constants applicable to that particular type of capacitor, will,

when added to the details already known, lead to the correct replacement.

In the Rider Replacement Parts Program all the electrical requirements surrounding the original capacitor used in the television receiver are known, and these are compared with the electrical constants of the replacement items; then the suitable replacement is listed, that is, if there is one. A number of different types of capacitors can satisfy some of the original design requirements, but only after consideration of all of the constants is it possible to select which particular type of capacitor is suitable, or in some instances, which types are the equivalent of each other for a particular use. Examples of these will be given in a later article.

### Physical Size

The physical size requirement is listed as one of the constants. Perhaps this is taking some license with the stricter meaning of constants but it does no harm. It is one of those descriptive terms which offers substantial leeway in the selection. At the factory end the physical size relates to most convenient production, satisfying space limitations inside or around other components, electrical performance when operation is at very high or ultra-high frequencies, and finally, to some extent the matter of economy. From the service technician's viewpoint, the physical size requirement is the one with the least problem, providing that when a limitation exists, it is realized.

We have illustrated the range of physical dimensions within which capacitors of different types are generally available. It was seen that each type comes in different sizes. In some categories of units the full range of sizes is available on the replacement market; in others it is not. But fortunately the manner of use of a capacitor in a television receiver does not always demand complete conformance with the physical size specification, assuming that the electrical requirements can be satisfied.

For example, when a capacitor is located inside of some other component with fixed boundaries, such as an i-f or similar transformer can, or a deflection yoke, it is necessary that the replacement be of similar physical dimensions, or smaller, in order to fit within the same space. At the moment we are neglecting the possibility that the technician may not be interested in replacing a capacitor in an i-f transformer; he would rather replace the entire unit, which after all, does make sense when all factors are considered. Another example is the capa-

(Continued on next page)

**New RIDER TEK-FILE Packs**  
with  
**Replacement Parts Listings**  
*available this month!*

Pack 70. Motorola  
Pack 71. Packard-Bell, Philco  
Pack 72. RCA  
Pack 73. Western Auto, Westinghouse  
Pack 74. Radio Craftsmen, RCA, Sears  
Roebuck  
Pack 75. Sentinel, Sparton, Spiegel,  
Starrett, Stewart-Warner  
Pack 76. Stromberg-Carlson, Sylvania  
Pack 77. Westinghouse, Zenith

For the individual models included in these Packs, refer to the TEK-FILE INDEX in the January, 1953 issue. If you do not have the issue, consult your Rider distributor or write to us directly.

citor which is used in a critical circuit where space is at a premium and the distributed capacitance must be kept to a minimum, or when the lead length is important. The larger the unit in these cases, the lesser is the possibility of keeping the lead length to the dimension used for the original component.

It is not beyond the realm of the imagination that a service technician may feel that the replacement of a fixed tuning capacitor inside of a transformer can be accomplished by locating the component outside the can. This is bad practice, and should not be done. The performance of the transformer can be affected adversely and feedback problems may arise.

Finally there is the case of the can type of electrolytic capacitor for which a mounting plate already exists in the receiver. It is conceivable that a new mounting plate suitable for a larger or smaller sized replacement can be used instead of the old one, but this involves the unwarranted expenditure of time and is justified only when the proper replacement is not procurable. Or, it is conceivable that a completely new mounting arrangement will be used, such as locating the replacement beneath the chassis. Of course it can be done, but we feel that in the latter cases, which are not too numerous to begin with, the physical features of the chassis should be retained by procuring the part that fits the chassis properly.

As to capacitors which are located on the underside of the chassis, the physical dimensional requirements are not of major import, providing, as we have said before, that the electrical requirements are satisfied. However, it always is best to duplicate the original size, but if there is to be a difference, it is best and most convenient to work with the smallest physical sizes rather than the reverse.

#### Capacitance and Capacitance Tolerance

In the list of electrical qualifications and in any list of constants of capacitors, these two items are shown individually. In reality they are closely related; hence are treated together here. Moreover, they are associated with all basic categories of capacitors being treated in this replacement parts series.

All capacitors bear some identification which states the capacitance rating of the unit. Sometimes the value is simply stated on the box which contains the unit, as usually is the case with variable capacitors. In the case of fixed units of all kinds, the value is marked on a label attached to the capacitor, or it appears as some form of coding impressed on the unit. Whether the label or coding expresses the capacitance in microfarads or micromicrofarads is unimportant because one is convertible into the other. A more important thing is the realization that the value of capacitance so shown is an *approximate* value. Frequently it is referred to as the *nominal* value.

By approximate or nominal we mean a value corresponding to the standard value within a certain leeway or tolerance. As a matter of convenience, lowest cost, and other production factors, the radio and television industry has agreed upon certain values of capacitance for each type of capacitor as being "standard" values. Design engineers try to build their equipments around these values. Capacitor manufacturers in turn build capacitors to approximate these standard values within a certain tolerance (expressed as a percentage of the rated value) and label them accordingly.

Although the standard values of capacitance are not the same for all basic categories of capacitors, at least do not begin at the same low limit and end at the same high limit, there is a range of capacitance in which the paper dielectric, mica dielectric, and ceramic dielectric afford more or less the same standard values, but not exactly the same. Such a list would begin at about 0.0001  $\mu\text{f}$  and end at about 0.01  $\mu\text{f}$ . It must be understood however that operating voltage ratings will tend to modify the range of standard values in all three types. As an illustration we might point out that the usual lowest standard value of capacitance in paper dielectric capacitors rated below 2000 volts working, is 0.001  $\mu\text{f}$ , and even this is increased to perhaps several times that value when the working voltage is below 600 volts.

Mica dielectric and ceramic dielectric capacitors are available in like standard values from about 1  $\mu\text{f}$  to about 0.01  $\mu\text{f}$ , but even in this group, especially between a fraction of 1  $\mu\text{f}$  and about 70  $\mu\text{f}$ , the preponderant selection of ceramic capacitors for many uses by design engineers has led to the creation of standard values which differ from each other in very small steps, perhaps 2 or 3  $\mu\text{f}$ .

The electrolytic capacitor is in a class by itself as far as standard values are concerned. They begin at about 4  $\mu\text{f}$  and extend up into the thousands of microfarads. But here too the particular type and the working voltage rating sets limits, as for example about 50  $\mu\text{f}$  is the limit at 450 volts, whereas 5000  $\mu\text{f}$  units are available at 6 volts.

**Capacitance Tolerance.** Concerning the association between standard values and tolerance, by definition, tolerance is the acceptable departure from a rated value. In the television industry, for that matter in the entire electronic industry, capacitance tolerance is expressed in two ways. One is in terms of percentage of the rated value, the other is in terms of a certain amount of capacitance. For instance when the capacitance is less than 10  $\mu\text{f}$ , and the unit is a ceramic dielectric capacitor, the + and - tolerance ratings may be 0.1 $\mu\text{f}$ , 0.25  $\mu\text{f}$ , 0.5  $\mu\text{f}$ , 1.0  $\mu\text{f}$  or 2.0  $\mu\text{f}$ , depending entirely on the degree of accuracy required by the circuit involved. As a rule, capacitors of this kind used in television

receivers bear either + or - 0.25 $\mu\text{f}$  or 0.5  $\mu\text{f}$  tolerance ratings.

In the case of mica capacitors up to and including 10  $\mu\text{f}$ , two minimum tolerance ratings exist. For the plain foil mica, the minimum tolerance is 1.0  $\mu\text{f}$ , whereas for the silver mica it is 0.5  $\mu\text{f}$ .

When the capacitance exceeds 10  $\mu\text{f}$ , the capacitance tolerance is expressed in

(Continued on page 20)

### There's a RIDER Book For Every Phase of Radio — Television

|   |  |
|---|--|
| Encyclopedia on Cathode-Ray Oscilloscopes and Their Uses<br>992 pages .....   | \$9.00                                   |
| Vacuum-Tube Voltmeters, 2nd Ed.<br>432 pages .....                            | \$4.50                                   |
| TV and Other Receiving Antennas<br>(Theory and Practice)<br>606 pages .....   | \$6.90                                   |
| TV Installation Techniques<br>336 pages .....                                 | \$4.50                                   |
| TV Master Antenna Systems<br>356 pages .....                                  | \$5.00                                   |
| Receiving Tube Substitution<br>Guide Book, 1st Ed. 224 pages.                 | \$3.00                                   |
| First Supplement, Receiving Tube<br>Substitution Guide Book<br>48 pages ..... | \$ .99                                   |
| TV Picture Projection and<br>Enlargement 192 pages .....                      | \$3.30                                   |
| Television—How It Works<br>203 pages .....                                    | \$2.70                                   |
| FM Transmission and Reception,<br>2nd Ed. 460 pages .....                     | \$4.95                                   |
| Radio Operator's License Q & A<br>Manual, 3rd Ed. 734 pages.....              | \$6.60                                   |
| Broadcast Operator's Handbook,<br>2nd Ed. 440 pages .....                     | \$5.40                                   |
| Radar—What It Is 80 pages.....  | \$1.00                                   |
| Understanding Vectors and<br>Phase in Radio<br>160 pages .....                | Cloth cover \$1.89<br>Paper cover \$ .99 |
| Installation and Servicing of Low<br>Power Pa Systems 208 pages.....          | \$3.00                                   |
| Servicing by Signal Tracing<br>360 pages .....                                | \$4.00                                   |
| Inside the Vacuum Tube<br>424 pages .....                                     | \$4.50                                   |
| Servicing Superheterodynes<br>288 pages .....                                 | \$2.00                                   |
| Servicing Receivers by Means<br>of Resistance Measurement<br>203 pages .....  | \$2.00                                   |
| The Business Helper<br>134 pages .....  | \$2.00                                   |


WE GUARANTEE your satisfaction!  
Make these books PROVE their value  
to you. Examine them at your favorite  
jobber. If he does not have them —  
order from us.

**Order Your Copy Now!**

**JOHN F. RIDER PUBLISHER, INC.**  
480 Canal Street, New York 13, N. Y.

**COMING IN APRIL RIDER'S TV11**



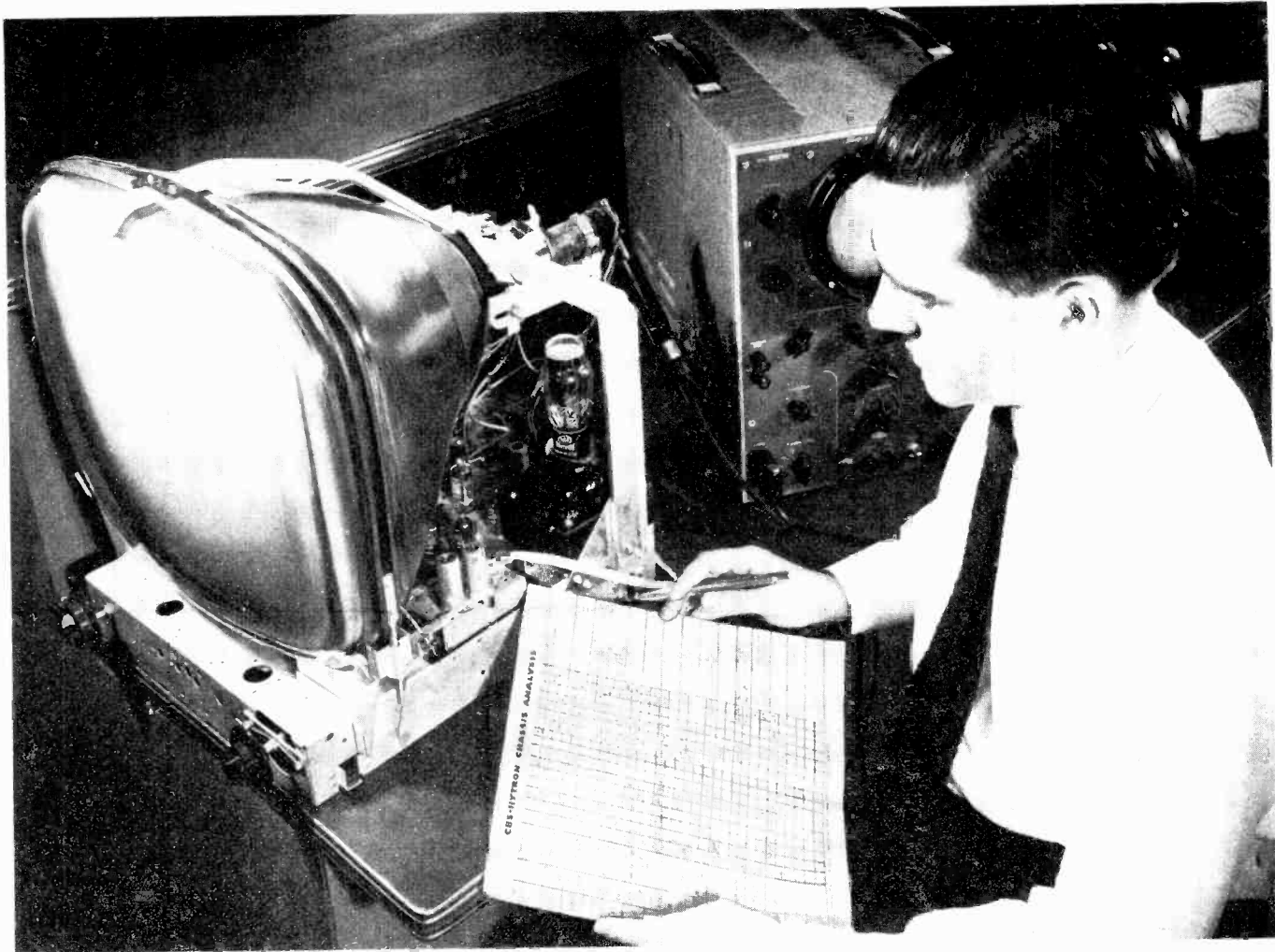

## Bring back that New-Set Sparkle with Performance-Tested Tubes

Meet John Cunningham, a CBS-Hytron Commercial Engineer. John is beginning at the beginning for you. Socket by socket, he is analyzing the tube requirements of a brand-new TV set design.

John knows the superior performance demanded. He concentrates his know-how on insuring top tube operation within standard specification limits. He tests sample tubes . . . checks analysis data. Working hand-in-glove with the set designer . . . and with CBS-Hytron engineers . . . he assures control of the characteristics of all tubes for this new chassis. Finally he achieves . . . from rectifiers to picture tube . . . the perfect performance all of this engineering team (and you) seek.

Constantly CBS-Hytron carries on teamwork like this. Socket by socket analysis. Day in, day out — with 9 out of 10

leading TV set makers. Both tube and set engineers pool their specialized skills. Scores of the nation's foremost TV set engineers help make endless CBS-Hytron improvements. Help assure you of unsurpassed performance in virtually *all* leading TV sets.

Small wonder that your CBS-Hytron replacement tubes recapture that new-set sparkle. Please *your* customers. Cut *your* call-backs. Profit more. Take advantage of CBS-Hytron engineering. Demand CBS-Hytron . . . your logical replacement tube, because it is performance-tested all the way . . . from original to replacement.

**NEW... BIGGER... BETTER**

**FREE!**

**6th Edition**

**CBS-HYTRON  
Reference Guide  
for  
Miniature Electron  
Tubes**



- A CBS-Hytron original . . . it's unique.
- All miniatures, regardless of make.
- 250 miniature types . . . 87 new.
- 111 basing diagrams . . . 34 new.
- Similar larger prototypes indicated.
- 8 packed pages of data you need daily.
- And it's FREE!

Get your copy of this old friend brought up to date now. Ask your CBS-Hytron jobber or write direct . . . today!




MANUFACTURERS OF RECEIVING TUBES SINCE 1921  
**HYTRON RADIO AND ELECTRONICS CO.**

A Division of Columbia Broadcasting System, Inc.  
Main Office: Danvers, Massachusetts
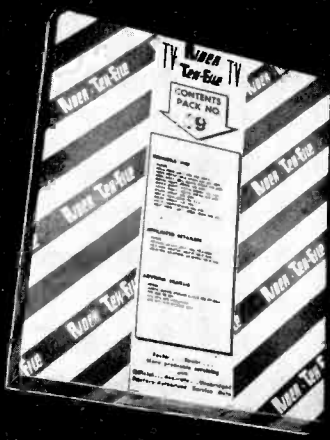
# Why not repair TV the easy way?

**Rider TV MANUALS.** These are the large, bound volumes that come out about 3 times a year. Each volume covers the current production of every receiver brand from A to Z. There are now 10 TV volumes that cover a total of more than 4,650 different models. Each volume has 2,000 or more 8½ x 11" pages of official, factory-authorized information and all contents are clearly indexed for fast and easy use. With a Rider TV Manual, you'll know all about the different production runs and changes, circuits, voltages, trouble cures . . . everything the manufacturer has to tell for easy service.

We don't mean by saying a few magic wands over the set. Before you can do that they'll build a set that just won't break down . . . and we'll all be out of business. We mean that once you know the make and model of the TV receiver, think how easy it would make your job if you knew as much about the set as the company that made it. Impossible? No. Rider servicing information tells you all you need to know to do a permanent repair job. One that really makes the customer happy. This complete and easy-to-use data comes two ways . . .



**TEK-FILE.** Here is the same complete, official factory-authorized Rider information in packaged form. TEK-FILE information is just like the Manuals . . . organized, indexed, easy-to-use. Buy TEK-FILE when you need information for just certain receivers and models. There are now 77 TEK-FILE packs that cover over 2,800 tv models. You can find out what packs are available from the free TEK-FILE indexes at your jobbers, or by writing to us.

Beginning with TV Manual 10 and TEK-FILE Pack 57, you'll find this new feature: a listing — by brand names — of dependable replacement parts. All parts' specifications are checked and rated against original parts. If you can't get TEK-FILE information, let us know. We'll tell you where to buy it . . . or sell you direct. Find out for yourself how easy tv servicing can really be. Try a TEK-FILE Pack — if you're not completely satisfied—return it to us within 7 days and we'll return your money!

**NOTE TO ALL TV 10 OWNERS!** Do yourself and us a favor by filling in and sending to us the registration coupon on the first page of TV 10. This will help us send you additional exclusive information. Thank you.

For Easier Radio Servicing . . . Use Rider's 22 AM-FM Manuals!

## JOHN F. RIDER

PUBLISHER, INC.

480 Canal Street, New York 13, N. Y.

West Coast Office:

4216-20 W. Jefferson Blvd. Los Angeles, California

## The Cosine Yoke

(Continued from page 1)

with horizontal lines of force. This magnetic field produces vertical deflection. Part B of the figure shows a cross section of the windings of the cosine yoke. Windings which produce horizontal and vertical deflections are labeled. Part C is an enlarged view of one of the horizontal windings with the window and butting edge of the winding shown.

Note that the cosine distribution must be designed into both vertical and horizontal windings, but in different amounts. This is true because the deflection components of both magnetic fields are not the same due to the raster being wider than it is high. The size of the window in both horizontal and vertical coil assemblies affects the over-all distribution and hence the spot focusing in the corners of the picture.

The cosine distribution curve is a design detail and has no direct significance to the service man. Suffice it to say that the winding thickness varies in a cosinusoidal manner. Some windings claim to be cosine squared in character, which means that the winding thickness increases faster than in a normal cosine yoke.



In general a cosine yoke can be distinguished from a conventional-style yoke by inspecting the size of the winding window. Cosine yokes have narrow windows. This is natural, since the winding starts nearer to the center line of the assembly, and thus has farther to spread while increasing its thickness. The horizontal winding window can be readily seen, since this winding is on the inside of the yoke and lies along the neck of the tube.

Finally, in checking an old yoke when considering replacement with a cosine yoke, note that the cosine yokes probably have higher horizontal-winding inductance than conventional designs and replacement might result in poor performance and probably give ringing in the picture. Also, another condition to watch out for is whether the shape of the raster has been changed, since better corner focus may have been obtained at the expense of pincushioning of the raster. Some cosine yokes produce pincushioning that must be removed by placing small permanent magnets (held on brackets) around the neck of the tube. These anti-pincushioning magnets must be readjusted in making a replacement. A cosine yoke with such magnets cannot be used with metal picture tubes since the cone may become permanently magnetized and thus distort the raster.

*Rider Tek-File gives you*  
Complete parts lists and values



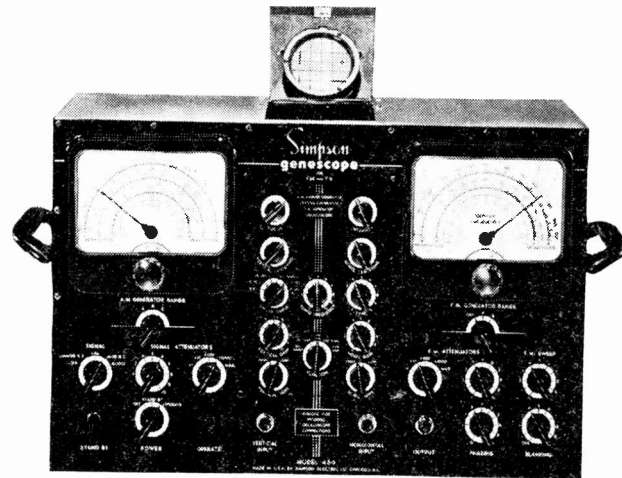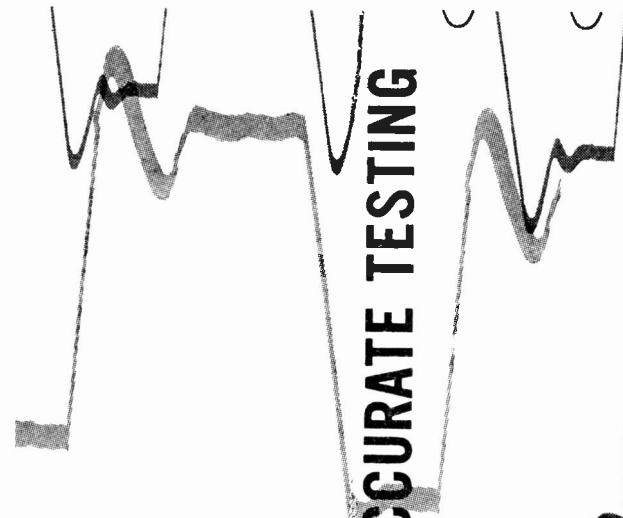**SIMPSON MODEL 480 GENESCOPE FOR ACCURATE TESTING**



*approved by  
service managers of:*

*admiral*

*zenith*



*motorola*

*emerson*

*hoffman*

*hallicrafters*

Provides all the necessary signal sources for proper alignment and servicing of FM and TV receivers • Includes the Simpson High Sensitivity Oscilloscope, complete in every detail and equipped with a high frequency crystal probe for signal tracing • Independent, continuously variable attenuators and step attenuators for both AM and FM units offer complete control of output at all times—from the high level required for front end adjustment to extremely low levels for fringe area peaking operations • Multiple shielding, generous bypassing and adequate line filtering reduces signal leakage to a negligible factor • A 0-15 megacycle sweep is provided by means of a noiseless specially designed sweep motor based on the principles of the D'Arsonval meter movement for fine control and lasting accuracy • The exclusive Simpson output cable (illustrated on the right) includes a variable termination network which is quickly adapted to provide open, 75 or 300 ohm terminations—the addition of a pad provides attenuation and isolation. The use of appropriate resistors across certain terminals will provide any other termination required. A .002 MFD blocking condenser can be added on any termination for use on circuits containing a DC component • The FM generator output voltage is constant within .2 DB per MC of sweep. Model 480 \$395.00

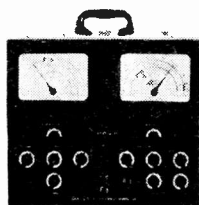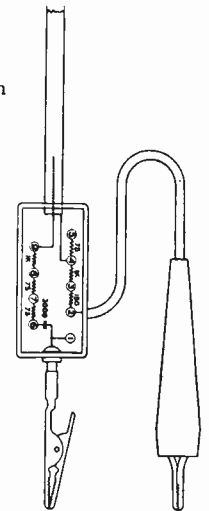


Also available without the oscilloscope as Simpson Model 479 TV-FM Signal Generator. Model 479 \$269.00

Simpson Instruments That Stay Accurate Are Available From All Leading Electronic Distributors

SIMPSON ELECTRIC COMPANY

5200 W. Kinzie St., Chicago 44, Illinois • Phone: COlumbus 1-1221 • In Canada: Bach-Simpson, Ltd., London, Ont.

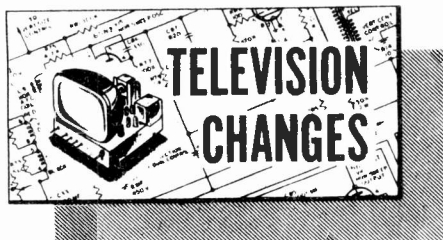Please mention *Successful Servicing* when answering advertising.



In compliance with the many requests we have received from our readers, this and future issues of SUCCESSFUL SERVICING will again contain the feature, TV PRODUCTION CHANGES.

The Rider Manual pages and TEK-FILE pack which include the original data and schematics to which the following production changes apply, appear in the index on page 24 of this issue.

**ANDREA MODEL T-VL12 CHASSIS VL12**

Service Data Addenda (Coil and Transformer Resistances)

Low-Voltage Transformer, T12, Part. No. ST-3033

Primary: .8 ohm

High-voltage secondary: 38 ohms, (center tap)

5v secondary (yellow leads): .1 ohm

6v secondary (green leads): .1 ohm

6v secondary (blue leads): .3 ohm

High-Voltage Transformer, T8, Part No. ST-3018-1

Terminals 1-2: 90 ohms

Terminals 2-3: 180 ohms

Terminals 4-5: 9 ohms

Terminals 5-6: .3 ohm

Vertical-Output Transformer, T7, Part No. ST-3030

Blue-red leads: 600 ohms

Green-yellow leads: 10 ohms

Vertical-Blocking Transformer, T6, Part No. ST-3029

Blue-red leads: 150 ohms

Green-yellow leads: 900 ohms

Horizontal-Oscillator Transformer, L18, Part No. SA-335

Terminals A-F: 75 ohms

Terminals C-D: 43 ohms

Deflection Yoke, L17, Part No. ST-3034

Horizontal winding: 13.5 ohms

Vertical winding: 70 ohms

Focus Coil, L14, Part No. ST-3032

1300 ohms

Horizontal-Linearity Control, L20, Part No. SA-315-1

35 ohms

Width Coil, L19, Part No. SA-336

.5 ohm

Speaker Output Transformer, T11, Part No. SL-4009

Primary: 400 ohms

Secondary: .5 ohm

Filter Choke, L22, Part No. 3031

100 ohms

**MAGNAVOX**

**CHASSIS CT-270, 271, 272, 273, 274**

R-F Unit

These chassis use r-f tuner unit No. 700349.

**GAMBLE-SKOGMO (CORONADO)**

Circuit Changes, Video Amplifier

The following component changes were made in the video amplifier circuit:

| Ref. No. | Old Part Number | New Part Number | Description             |
|----------|-----------------|-----------------|-------------------------|
| R35      | C-9B1-70        | C-9B1-66        | 2,200 ohms, ½ watt, 10% |
| R38      | C-9B2-64        | C-9B-62         | 1,000 ohms, ½ watt, 10% |
| R123     | C-9B4-21        | C-9B2-70        | 4,700 ohms, 1 watt, 10% |
| R127     | new part added  | C-9B4-82        | 47K ohms, 2 watts, 10%  |
| C122     | new part added  | C-8G-11892      | 22 μf, ceramic          |
| L20      | A-16A-18685     | A-16A-19486     | 240 μh peaking coil     |
| L21      | A-16A-18685     | A-16A-19485     | 380 μh peaking coil     |

NOTE: Chassis code numbered 124023 or higher incorporate this change.

**MITCHELL**

**MODELS T16-2KB, T16-2KM, T16-B, T16-M**

Production Change (Tube Substitution)

In some receivers, a 6SN7 is used in place of a 12AU7 for the d-c restorer and sync separator stage. This is done by making the following wiring changes:

1. Filaments: Connect pins 5 and 9 of the 12AU7 to pins 7 and 8 of the 6SN7, respectively. Disconnect pin 4 of the 12AU7.
2. Cathodes: Connect pins 3 and 8 of the 12AU7 to pins 6 and 3 of the 6SN7, respectively.
3. Grids: Connect pins 2 and 7 of the 12AU7 to pins 4 and 1 of the 6SN7, respectively.
4. Plates: Connect pins 1 and 6 of the 12AU7 to pins 5 and 2 of the 6SN7, respectively.

**HOFFMAN**

**MODEL 612 CHASSIS 142**

Hoffman Model 612 is a 24 tube table model with a 6 inch speaker and an audio power output of 3.0 watts. A 12 inch picture tube is used. Its major components are:

Chassis — 142

Speaker — 6" PM (Part No. 9062 voice coil, 3.2 ohms at 400 cps.)

Cabinet — Part No. 7533

Escutcheon Frame — Part No. 2277

Filter Plate Glass — Part No. 734

Picture tube — 12KP4, 12LP4, L2QP4

**SYLVANIA**

**MODEL 74M CHASSIS 1-356(C05)**

Sound I-F Limiter (Circuit Change)

1. Resistor R-104 (120 ohm) is removed from the cathode (pin 7) of the Sound I-F Limiter (V-10, 6AU6) and the cathode is connected directly to ground.
2. Capacitor C-104 (.2μf, 400v), connected from the bottom of T-52 (sound discriminator transformer primary) to ground, is removed from the circuit.
3. Resistors R-105 (33K, ½w) and R-106 (10K, ½w), connected to the screen grid of the Sound I-F Limiter (pin 6 of V-10, 6AU6), are removed from the circuit.
4. Pin 6 of V-10 is connected to the bottom of T-52.
5. Resistor R-107 (33K, ½w), connected between the bottom of T-52 and the +125v supply, is changed to 22K, ½w (Service Part 181-0223).

NOTE: Chassis coded C06 (Serial Nos. beginning 5606-) incorporate this change.

**SYLVANIA**

**MODELS 22M-1, 23B, 23M, 24M-1 CHASSIS 1-387-1**

3rd Video I-F Stage (Resistor Change)

Resistor R-140, in the grid circuit (pin 1) of the 3rd video i-f tube (V-5, 6BA6), is changed from 27K, ½w to 22K, ½w (Service Part 181-02235).

NOTE: Chassis coded C01 (Serial Nos. beginning 87101-) incorporate this change.

**"HIGH FIDELITY Simplified"**  
by H. D. WEILER

Here is the complete story of high fidelity — clearly told, easily understood. This brand new, practical book covers everything from 'what high fidelity is' to the actual selection, purchase and installation of the proper high fidelity equipment. You'll find page after page of detailed, illustrated information concerning record players and changers, amplifiers, loudspeakers and tape recorders . . . it answers your questions on what to buy and do to obtain perfect results. Learn how you can enjoy the most lifelike musical reproduction possible. Order your copy of this valuable, new first edition today at your local bookstore . . . or simply send \$2.50 to —

**John F. Rider, Publisher, Inc.**  
Dep't. T, 480 Canal Street  
New York 13, N. Y.

# DEALERS GETTING WESTINGHOUSE TUBES PROFIT FROM HEAVY LOCAL ADVERTISING AT NO COST

Service dealers are getting powerful local advertising support from new Westinghouse RELIATRON™ Tube Distributors. In cities now served by Westinghouse Distributors, dealers get local newspaper advertising, a complete kit of store display and imprinted mailing material.

All of it—local ads and kits—are designed to build TV-radio service business in the dealer's local area.

Best of all, none of it costs the dealer a penny!

You can get your store listed in two local newspaper ads at no charge, and get a kit to boot. If Westinghouse Tubes are now sold in your area, see your Westinghouse Distributor and take advantage of this \$900-

worth-of-advertising-at-no-cost offer.

**NEWSPAPER ADS**



## COMING YOUR WAY

If Westinghouse Tubes are not yet distributed in your area, be patient. Distributors are being established in all market areas as fast as product availability and good service permit.

You'll soon have the chance to buy RELIATRON Tubes. Keep this tremendous opportunity in mind: you'll get newspaper advertising at no cost! Imprinted material for mailings! Imprinted signs for your window!

All of it is local advertising which sells your service in your own area where it counts.

For the name of your Westinghouse Distributor, or the approximate date when Westinghouse Tubes will be available in your area, drop a postal card to Dept. M-201 or have your regular distributor contact Dept. M-201 for information on how he can better serve you.

YOU CAN BE SURE... IF IT'S  
**Westinghouse**

**RELIATRON TUBES**  
TM

WESTINGHOUSE ELECTRIC CORPORATION, ELECTRONIC TUBE DIVISION, ELMIRA, N. Y.

To All Purchasers of:

# RIDER'S TV 10

Please do not forget to fill in the registration coupon on the first page of your Rider TV 10 Manual and send it to us if you have not done so already. We will forward the replacements parts listing corrections direct to your address. Also, by returning this coupon to us, you will be assured of having your name on our mailing list for exclusive, replacement parts information that will be available to TV 10 owners. Do Not send us the replacement parts pages!

Here are more data that will keep your RIDER'S DEPENDABLE REPLACEMENT PARTS LISTING published in TV Volume 10 up to date.


### ADDITIONS TO PHILCO VARIABLE RESISTANCE CONTROLS SECTION:

| PHILCO Part No. | REPLACEMENTS |         |             |            |           |         |             |            |             |             |            |           |         |             |            |             |             |            |
|-----------------|--------------|---------|-------------|------------|-----------|---------|-------------|------------|-------------|-------------|------------|-----------|---------|-------------|------------|-------------|-------------|------------|
|                 | CLAROSTAT    |         |             |            | IRC       |         |             |            |             |             |            | MALLORY   |         |             |            |             |             |            |
|                 | Cat. No.     | Kit No. | Inner Shaft | Switch No. | Stock No. | Kit No. | Panel Elem. | Rear Elem. | Outer Shaft | Inner Shaft | Switch No. | Stock No. | Kit No. | Panel Elem. | Rear Elem. | Outer Shaft | Inner Shaft | Switch No. |
| 33-5546-41      | A43-10K      |         | FKS 1/4     |            | WK-10000  |         |             |            |             |             |            | M10MP     |         |             |            |             |             |            |
| 33-5546-49      | A10-10K      |         | FKS 1/4     |            | 4WK-10000 |         |             |            |             |             |            |           |         |             |            |             |             |            |
| 33-5563-42      | RTV-345      |         |             |            | QJ-391    |         | W17-111     | WR11-116   | P3-129      | R8-213      |            |           |         |             |            |             |             |            |
| 33-5563-43      | RTV-241      |         |             |            | QJ-302    | K-2     | B11-125     | B11-130    | P1-200      | R1-216      |            |           |         |             |            |             |             |            |
| 33-5563-44      | RTV-380      |         |             |            | QJ-340    | K-2     | B12-141     | B18-139X   | P1-200      | R1-216      | 76-1       |           |         |             |            |             |             |            |
| 33-5563-50      | RTV-358      |         |             |            | QJ-356    | K-2     | B11-123     | B11-130    | P1-200      | R1-216      |            |           | UF54L   | UR25AL      |            |             |             |            |
| 33-5563-51      | RTV-359      |         |             |            | QJ-357    | K-3     | W17-111     | B11-128    | P3-131      | R1-216      |            |           | WF252   | UR15L       |            |             |             |            |
| 33-5564-14      | AT-116       |         | FS-3        | SWA        | Q18-139X  |         |             |            |             |             |            | UT451     |         |             |            |             |             | US26       |
| 33-5565-17      | AG-55-S      |         | FKS 1/4     |            | Q11-130   |         |             |            |             |             |            | SU46      |         |             |            |             |             |            |
| 33-5565-30      | AG-44-S      |         | FKS 1/4     |            | Q11-123   |         |             |            |             |             |            | SU35      |         |             |            |             |             |            |
| 33-5565-31      | AG-85-S      |         | FKS 1/4     |            | Q11-14    |         |             |            |             |             |            | SU67      |         |             |            |             |             |            |
| 33-5565-32      | AG-84-S      |         | FKS 1/4     |            | Q11-239   |         |             |            |             |             |            | SU565     |         |             |            |             |             |            |

### ADDITIONS AND CORRECTIONS TO FIXED CAPACITORS SECTION:

| Set Mfr.          | Set Mfr.'s Original Part No. |  |
|-------------------|------------------------------|--|
| Belmont           | 8C-18487                     | Add AFH4-82 to Aerovox column.   |
| Packard-Bell      | 23936                        | Change BPD-.0015 mf to SI-2-1500 mmf in Aerovox column.                  |
| "                 | "                            | Change K071 to G071 in Cornell-Dubilier column.                          |
| "                 | "                            | Change DC-5215 to UC-5212 in Mallory column.                             |
| "                 | "                            | Change 5HK-D15 to 5GA-D15 in Sprague column.                             |
| "                 | 23955                        | Change K078 to KD077 in Cornell-Dubilier column.                         |
| "                 | "                            | Change UC-5240 to DCD524 in Mallory column.                              |
| "                 | "                            | Change 5DA-D4 to 5HK-2D4 in Sprague column.                              |
| "                 | 23956                        | Change 1468L-HV 47 mmf to HVD30-47 mmf 10% in Aerovox column.            |
| "                 | "                            | Delete 5P20Q47 in Cornell-Dubilier column. No replacement.               |
| "                 | "                            | Delete MCL-447 in Mallory column. No replacement.                        |
| "                 | "                            | Change 60GAB-Q47K to 20GAB-Q47K in Sprague column.                       |
| "                 | 23967                        | Change 1468L-HV-100 mmf to HVD15-470 mmf in Aerovox column.              |
| "                 | "                            | Delete 5P10T47 in Cornell-Dubilier column. No replacement.               |
| "                 | "                            | Delete MCK-347 in Mallory column. No replacement.                        |
| "                 | 23959                        | Change MMA20T5 to MMC-20T5 in Cornell-Dubilier column.                   |
| Philco            | 30-2417-3                    | Add PRS50-10 to Aerovox column.  |
| "                 | "                            | Add BR-105 to Cornell-Dubilier column.                                   |
| "                 | "                            | Add TC-32 to Mallory column.   |
| "                 | "                            | Add TVA-1304 to Sprague column.  |
| "                 | 30-2417-7                    | Add BBR-2-50T to Cornell-Dubilier column.                                |
| "                 | 30-2570-57                   | Add D111 to Cornell-Dubilier column.                                     |
| "                 | "                            | Add FP476 to Mallory column.   |
| "                 | 30-2570-66                   | Add XA004 to Cornell-Dubilier column.                                    |
| "                 | "                            | Add FP117 to Mallory column.   |
| "                 | 30-2584-9                    | Add D111* to Cornell-Dubilier column.                                    |
| "                 | "                            | Add FP344.5 to Mallory column.   |
| "                 | 30-2584-15                   | Add UPT 435 to Cornell-Dubilier column.                                  |
| "                 | "                            | Add FP225-TC72** to Mallory column.                                      |
| Stromberg-Carlson | 111082                       | Change PRS 15/500 to PRS 12/500 in Aerovox column.                       |
| "                 | 111094                       | Change TVL-2764 to TVL-4840*** in Sprague column.                        |
| "                 | "                            | Change FP238 to FP476*** in Mallory column.                              |
| "                 | 111095                       | Change FP476* to FP238 in Mallory column. Delete "Remarks" column.       |
| "                 | "                            | Change TVL-4840* to TVL-2764 in Sprague column. Delete "Remarks" column. |

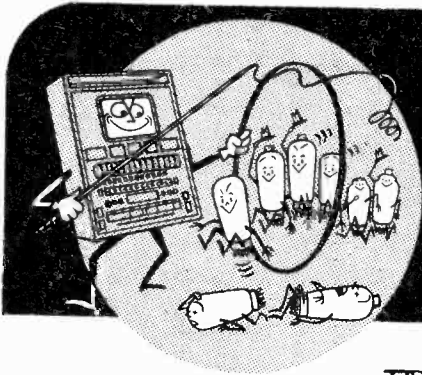\*Parallel 20 mf and one 20mf/3000VDC section to replace original 30 mf section.  
 \*\*TC72 tubular electrolytic used in place of 10mf/450V section of original unit.  
 \*\*\*Omit one 10 mf section.




# THE INSTRUMENT THAT DEMANDS **OVERALL PERFORMANCE** FROM THE TUBE UNDER TEST!

*-PRECISION-* SERIES 10-12
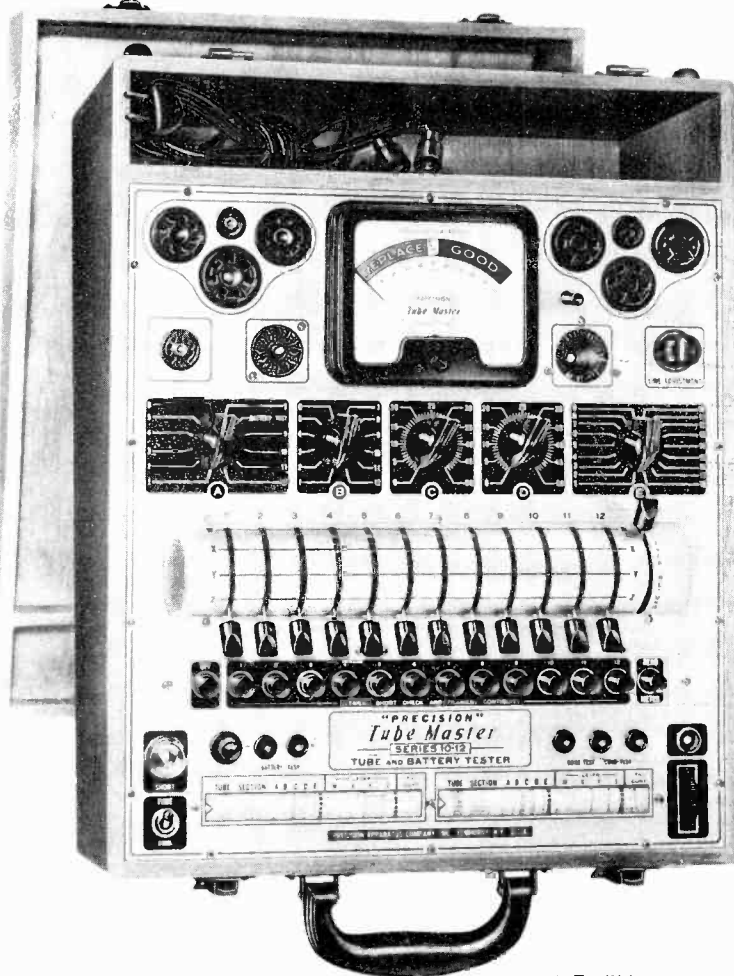
## Electronamic\* Tube PERFORMANCE Tester

with 12 element free-point Master Lever Selector System



MODEL 10-12-P (illustrated): in sloping, portable hardwood case with tool compartment and hinged removable cover. Sizes 13 $\frac{3}{4}$ " x 17 $\frac{1}{4}$ " x 6 $\frac{3}{4}$ ".....\$104.50  
MODEL 10-12-C (Counter Type) \$109.25  
MODEL 10-12-PM (Panel Mount) \$109.25

To test modern tubes for only one characteristic will not necessarily reveal **OVERALL PERFORMANCE CAPABILITIES**. Modern tube circuits look for more than just mutual conductance or other single factor.

It has been conclusively proven that even though a tube may work well in one circuit, it might fail to work in another—simply because different circuits demand different relative performance characteristics, such as amplification factor, plate resistance, power output, emissive capability, etc.

In the PRECISION "ELECTRONAMIC" Circuit, the tube under test is made to *perform* under appropriately phased and selected individual element potentials, encompassing a wide range of plate family characteristic curves. This COMPLETE PATH OF OPERATION is electronically integrated by the indicating meter circuit in the positive performance terms of Replace-Weak-Good.

The efficiency of this "Electronamic" test results from encompassing several fundamental tube characteristics, NOT JUST ONE. Accordingly, when a tube passes this demanding **OVERALL PERFORMANCE** test, it can be relied upon, to a very high degree, to work satisfactorily.

\*REG. U.S. PAT. OFF. T. M. 438,006

### Compare these features

- ★ Facilities to 12 element prongs.
- ★ Filament voltages from  $\frac{3}{4}$  to 117 V.
- ★ Tests Noval 9 pins; 5 and 7 pin acorns; double-capped H.F. amplifiers; low power transmitting tubes, etc., regardless of filament or any other element pin positions.
- ★ Isolates each tube element regardless of multiple pin positions.
- ★ Dual Hi-Lo short check sensitivity for special purpose tube selection.
- ★ Simplified, High Speed, 12 element Short-Check system, uses consecutive push-button switching.
- ★ Battery Tests under dynamic load conditions.
- ★ 4 $\frac{1}{2}$ " Full Vision Meter.
- ★ Built-in Dual-Window, high speed, geared roller chart.
- ★ Free Replacement Roll Charts & supplementary tube test data service.

See the "Precision" Master "Electronamic" Tube Testers at leading Radio Equipment Distributors. Write for new, 1952 "Precision" catalog.

AM • FM • TV •



**PRECISION APPARATUS CO., INC.**

92-27 Horace Harding Boulevard, Elmhurst 12, New York  
Export Division: 458 Broadway, New York 13, U.S.A. • Cables—Morhane  
In Canada: Atlas Radio Corp., Ltd., 560 King Street, W., Toronto 2B

Convenient "PRECISION" Purchase Terms can be arranged with your local and favorite authorized "PRECISION" Distributor.

AM • FM • TV



# PRINTED ELECTRONIC CIRCUITS

(Continued from page 3)


The painting technique has the advantage of requiring a minimum of auxiliary equipment and so has been the most popular type for experimentation and design work with printed circuits. It is also the best method to use in making repairs on printed circuits, as will be discussed later.

The *spraying* method of reproducing printed circuits differs from the painting technique in that the conductors are sprayed onto the surface of the base. Both molten metals and metallic conducting paints may be applied in this manner. In some processes, stencils are used to define the circuit conductors. In others, grooves are machined or molded in the base material where a conductor or other circuit component is desired. Grooves may also be formed by sand-blasting through a stencil. Metal is then sprayed over the entire base plate, filling the grooves and covering the spaces between. The surface is then milled off, removing the excess metal and leaving only that in the grooves. High conductivity is obtained by this method since relatively large conductors are formed in the grooves. Standard

the work. Metal evaporated from a heated filament, or other source of metal vapor, is distilled on the printed circuit plate placed over it. In either type of vacuum processing, it is unnecessary to further heat treat or fire the deposited metal. Only thin films are usually deposited in this manner. If greater conductivity is required, conductors may be built up by electroplating.

In the *chemical-deposition* methods of making printed circuits, the techniques employed are similar to those used in silvering mirrors. A silvering solution, consisting of ammonia and silver nitrate mixed with a reducing agent, is poured on the chemically clean surface to be coated. The confines of the solution are controlled by an adhesive stencil. The metal films obtained are usually too thin to permit direct soldering, but may be built up by repeated coatings or by plating. The chemical processes have not been applied as extensively as those discussed above.

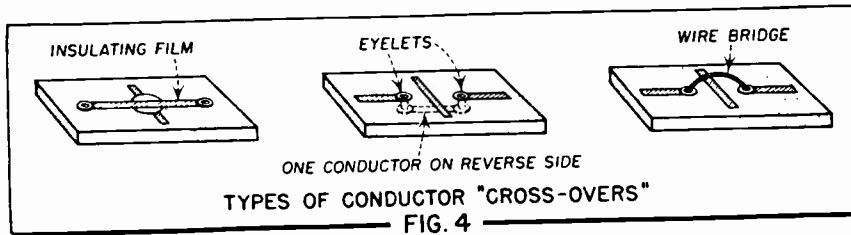The *metal stamping* technique has been used principally to print loop antennas on the back covers of radio receivers. However,



tube sockets and other components are sometimes connected to sprayed circuits by mounting them on the opposite side of the base plate so that the terminals protrude through holes into the grooves. Then, when the circuit is sprayed, connections are automatically made to the conductors. Circuit cross-overs are made in a manner similar to that employed in the painting process. Resistors, capacitors, and inductances may also be formed by spraying.

The *vacuum evaporation* process of circuit printing consists of evaporating a metal such as silver, copper, or nickel onto the surface of the dielectric material by melting the metal in a vacuum. A mask or stencil on the surface of the insulator is used to outline the circuit desired. In one such process, called "cathode sputtering", a high voltage is applied between the source of metal vapor (the cathode) and the work upon which it is to be deposited (the anode). The metal vapor is thus drawn to the work by electrostatic forces. Only a "rough" vacuum, such as can be produced by a good mechanical vacuum pump, is required for this process.

Another vacuum process used is very similar to cathode sputtering except that no voltage is applied between the cathode and

other types of circuit wiring have been produced by this method. A die, bearing the outline of the desired circuit, is used to press a thin metal foil into the surface of a plastic or other insulator. In the same operation the sharp edges of the die cut the metal sheet to the desired shape. The metal sheet may be backed by an adhesive to insure a good bond. Circuits made in this manner have good conductivity.

The last general type of printed circuit is produced by a process known as "dusting". In this method, a powdered metal is dusted onto the insulating base plate and fired in place. The circuit outline is defined either by coating the entire insulator with a sticky substance and applying the metal powder through a stencil, or by applying the bonding substance through the stencil and then dusting on the powder so that it is held in place by the adhesive until fired.

### Servicing Printed Circuits

As was mentioned above, the most convenient method of making repairs and replacements in printed circuits is the brush-applied painting technique. Kits of such paints, including both conductor and resistor mixtures, are commercially available.

(Continued on page 18)

## Brand New RIDER Books

### POSITIVE CURES FOR T.V. TROUBLES

with TV MANUFACTURER'S RECEIVER TROUBLE CURES VOL. 1



First in a brand new series of practical books that will give you the exact directions for correcting TV receiver performance "bugs." Each remedy is the one developed by the receiver's own manufacturer. It is positive! Each cure is official, factory-authorized. It will help correct some of the most difficult faults—picture jitter, hum, instability, buzz, tearing, etc.

If you work in a strong-signal area, a fringe area, an area of high humidity, etc., you have special problems in servicing. The manufacturers' trouble cures given in this book will relieve these troubles when properly applied to the receiver in question. These tried and tested cures will speed up your work, make it easier and more profitable.

For instant reference, a complete index in which trouble cures are listed by brand and chassis or model number, is included.

VOLUME 1 covers 12 prominent brands—ADMIRAL, AIRKING, ANDREA, ARVIN, BELMONT-RAYTHEON, BENDIX, CALBEST, CAPEHART-FARNSWORTH, CBS-COLUMBIA, CERTIFIED, CROSLEY, DUMONT. One service job will more than pay the cost of the book!

Over 120 pages. 5½"x8½" illus. \$1.80

### Out in March

### TV MANUFACTURER'S RECEIVER TROUBLE CURES VOL. 2

... covering 11 prominent brands — EMERSON, FADA, FIRESTONE, FREED, GAMBLE-SKOGMO, GENERAL ELECTRIC, HALLICRAFTERS, HOFFMAN, INDUSTRIAL, INTERNATIONAL, JACKSON.

Over 120 pages. 5½"x8½" illus. \$1.80

### TV SWEEP ALIGNMENT TECHNIQUES by Art Liebscher, Test Equipment Specialist

Never before has there been a book such as this on TV sweep alignment! Here you have techniques set up by an expert in the field — a man who gives you accurate, time-saving methods — and tells you how they work. The new Supermark method of TV sweep alignment is introduced. Learn new uses for your test equipment. Chock-full of sweep curve pictures taken from actual jobs using the test equipment set-ups and techniques discussed. Valuable for servicing in UHF signal areas. Covers TV sweep alignment methods completely from all angles. Know how to check video amplifier response with a sweep generator applied to the antenna input; how to peak align tuned circuits with sweep equipment; how to tune traps rapidly, etc. This book shows you how!

Over 100 pages 5¼"x8¼" illus. \$2.10

Buy these books now at your jobbers... leading bookstores... or —

**JOHN F. RIDER** PUBLISHER, INC.  
460 Canal Street, New York 13, N. Y.

**PRINTED ELECTRONIC CIRCUITS**

*(Continued from page 17)*

Most of these paints require no heat for drying, so that they may be used for repairing circuits having parts which cannot be subjected to high temperatures. This is an important precaution when working with circuits printed on certain types of plastic.

Although subminiature tube sockets are sometimes used with printed circuits, tubes are frequently connected directly to metal eyelets in the base plate, as in Fig. 1. When replacing tubes connected in this manner, care must be exercised to avoid the use of excessive heat during soldering operations. Soldered connections may also be made directly to printed conductors if the base material will stand the heat involved.

A solder containing a small percentage of silver should be used for best results. Where soldering is inadvisable, connections to tube leads and other wires should be made with metallic paint.

Printed resistors which have become defective may be repaired or replaced by the painting technique. Defective resistors are located in the usual manner with an ohmmeter. If it becomes necessary to "disconnect" a printed resistor from the circuit for a resistance check, this may be accomplished by scratching through the printed conductor lead with a sharp instrument. If defective, the resistor may be repaired with resistive paint. It will usually be found to be open or high in value. In such cases, additional resistive paint should be applied over the old resistor to reduce its resistance to the

proper value. Some commercial printed circuits have a protective layer of lacquer over the conductors and particularly over resistors to prevent moisture absorption. This coating must be completely removed before repairing resistors. If attempts to repair defective resistors are unsuccessful, the old coating should be removed completely and a new resistor painted in its place. The proper dimensions may be determined by trial and error, keeping in mind that the resistance is directly proportional to the length, and inversely proportional to width and thickness. The resistance material must make good contact with the printed conductors at the ends. Breaks introduced in the conductors to isolate resistors may be repaired with a bridge of conducting paint.


**the latest!**

**"Quick Service"  
Capacitor Kits in  
handy crystal clear  
plastic cases!**

**CORNELL-DUBILIER - TWIST-PRONG CAPACITOR REPLACEMENT KIT No. 1**

|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| <b>UP 2045</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2345</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2346</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2347</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2348</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2349</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2350</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2351</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2352</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2353</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2354</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2355</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2356</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2357</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2358</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2359</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2360</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2361</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2362</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2363</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2364</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2365</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2366</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2367</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2368</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2369</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2370</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2371</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2372</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2373</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2374</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2375</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2376</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2377</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2378</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2379</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2380</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2381</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2382</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2383</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2384</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2385</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2386</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2387</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2388</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2389</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2390</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2391</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2392</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2393</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2394</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2395</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2396</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2397</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2398</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2399</b><br>20 MFD 450 WVDC<br>List Price \$1.00 | <b>UP 2400</b><br>20 MFD 450 WVDC<br>List Price \$1.00 |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

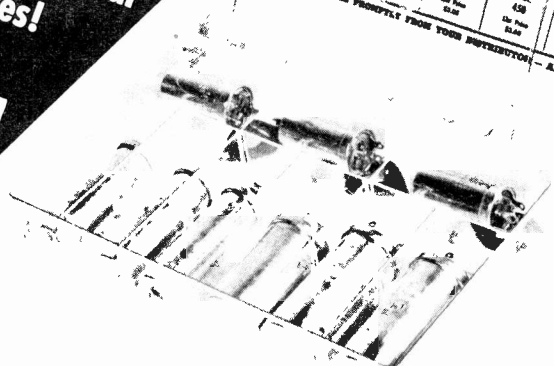ORDER PROMPTLY FROM YOUR DISTRIBUTOR - ALWAYS 1 DAY AHEAD



- KIT #1 - UNIVERSAL
- KIT #2 - FOR RCA SETS
- KIT #3 - FOR PHILCO SETS
- KIT #4 - FOR MOTOROLA SETS
- KIT #5 - FOR GENERAL ELECTRIC SETS
- KIT #6 - FOR ADMIRAL SETS

*A service of*

**CORNELL-DUBILIER**

*world's largest maker of capacitors*

PLANTS IN SO. PLAINFIELD, N. J. • NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASSACHUSETTS • PROVIDENCE, R. I. • INDIANAPOLIS, INDIANA • FUQUAY SPRINGS, NORTH CAROLINA • SUBSIDIARY, RADIART CORP., CLEVELAND, OHIO

And you pay *only* for the capacitors. Case costs you nothing.


6 kits for practically every possible twist-prong electrolytic capacitor replacement. Designed to service most TV sets.

See this new packaging of dependable Cornell-Dubilier electrolytics at your jobber today. Cornell-Dubilier Electric Corp., So. Plainfield, N. J.

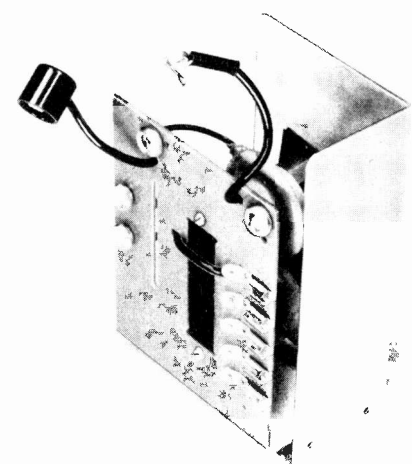**New Horizontal Output Transformer May Be Replaced Easily**

One component with a high mortality rate is the horizontal-output transformer. Not much was done to alleviate the replacement problem. To those who have undertaken such replacement, the tedious and delicate procedure can be well appreciated.

In the new Stewart-Warner 9300 television chassis, a realistic approach has been taken to the problem. The horizontal-output transformer (shown here) is simply mounted



*New Horizontal Output Transformer.*

and connectors are employed rather than soldered leads. With this transformer, it is not necessary to remove the high-voltage rectifier tube socket from the chassis merely to replace the filament leads, nor is it necessary to postpone replacement of the transformer as a last resort because of the work involved.

To replace the horizontal-output transformer, it is only necessary to remove two sheet metal screws and unplug the leads. The entire replacement procedure does not require much more than five minutes, and can be done in the customer's home without removing the chassis and without the use of a soldering iron.

# TV SUPPLEMENTARY SHEET NO. 1

| MODEL & CHASSIS  | PART #   | CATALOG #          | FUNCTION              | DESCRIPTION   | LIST PRICE           | MODEL & CHASSIS   | PART #  | CATALOG #            | FUNCTION  | DESCRIPTION  | LIST PRICE                              |               |
|--|--|--------------------|-----------------------|---|----------------------|---|---|----------------------|---|--|---|---------------|
| ADMIRAL<br>22A2,A<br>22M1<br>22Y1                                  | 75B1-50  | AG-83-5<br>KSS-3   | Tone                  | 2 Meg. $\Omega$ carbon                                      | \$1.25               | AMBASSADOR  | VC-12121C   | AG-84-5<br>FKS-1/4   | Height  | 2.5 Meg. $\Omega$ carbon                               | \$1.24                                  |               |
|  | 75B11-20   | RTV-327            | Contrast/<br>Vol./Sw. | 1500/1 Meg. Tap<br>500K $\Omega$ Conc. Dual<br>carbon--SPST | \$4.30               |   | VC-12127B   | RTV-297              | Contrast/<br>Vol./Sw.                                     | 750 Tap 500/250K $\Omega$<br>Conc. Dual carbon<br>SPST | \$4.30                                  |               |
|  | 75B13-3  | AG-84-5<br>FKS-1/4 | Height                | 2.5 Meg. $\Omega$ carbon                                    | \$1.25               |   | VC-12131C   | AG-44-5<br>KSS-3     | Hor.<br>Hold  | 50K $\Omega$ carbon                                    | \$1.25                                  |               |
|  | 75B13-7  | AG-15-5<br>FKS-1/4 | Vert.<br>Lin.         | 3000 $\Omega$ carbon  | \$1.25               |   | VC-12132C   | AG-83-5<br>KSS-3     | Vert.<br>Hold   | 1.3 Meg. $\Omega$ carbon                               | \$1.25                                  |               |
|  | 75B13-12   | AG-49-5<br>KSS-3   | Bright.               | 100K $\Omega$ carbon  | \$1.25               |   | VC-12135  | AG-49-5<br>FKS-1/4   | Bright  | 100K $\Omega$ carbon                                   | \$1.25                                  |               |
|  | 75B13-13   | AG-40-5<br>KSS-3   | Hor.<br>Hold          | 25K $\Omega$ carbon   | \$1.25               |   | ANDREA<br>2C-VL20   | GRV-812-1            | AG-83-5<br>FKS-1/4  | Height   | 2 Meg. $\Omega$ carbon                  | \$1.25        |
|  | 75B13-14   | AG-61-5<br>KSS-3   | Vert.<br>Hold         | 1 Meg. $\Omega$ carbon                                      | \$1.25               |   |   | GRV-824              | A43-2000<br>FKS-1/4                                       | Vert.<br>Lin.  | 2000 $\Omega$ 2W-W.W.                   | \$1.25        |
|  | 75B13-16   | A43-750<br>KSS-3   | Focus                 | 750 $\Omega$ 2W-W.W.  | \$1.25               |   |   | GRV-830              | AG-60-Z<br>FS-3/SWB                                       | Vol./Sw.   | 500K $\Omega$ carbon--SPST              | \$1.25<br>.60 |
| AMBASSADOR<br>C1720<br>C2020<br>C2420<br>C.D2020<br>T1720<br>T2020 | 131-0001   | AG-19-5<br>FKS-1/4 | Vert.<br>Lin.         | 5000 $\Omega$ carbon  | \$1.25               | CHASSIS<br>VL-20  |   | GRV-831              | RTV-75  | Hor./Vert<br>Hold                                      | 50K/2 Meg. Conc.<br>Dual carbon         | \$3.10        |
|  | 131-0002   | AG-84-5<br>FKS-1/4 | Height                | 2.5 Meg. $\Omega$ carbon                                    | \$1.25               | GRV-834   |   | RTV-300              | Bright./<br>Contrast                                      | 20K/5000 $\Omega$ 4W-W.W/<br>carbon Conc. Dual         | \$4.05                                  |               |
|  | 131-0003   | RTV-1              | Contrast<br>Vol./Sw.  | 10K/1Meg. Tap<br>200K $\Omega$ Conc. Dual<br>carbon--SPST   | \$3.70               | ARTONE<br>AR14L<br>AR17L<br>17CD<br>17CRR<br>17ROG<br>20CD<br>203D<br>1000<br>1001<br>2nd Run |   | P-2                  | AG-19-5<br>FKS-1/4  | Vert.<br>Lin.  | 5000 $\Omega$ carbon                    | \$1.25        |
|  | 131-0012   | AG-44-5<br>KSS-3   | Hor.<br>Hold          | 50K $\Omega$ carbon   | \$1.25               |   |   | P-5                  | AG-84-5<br>FKS-1/4  | Height   | 2.5 Meg. $\Omega$ carbon                | \$1.25        |
|  | 131-0012   | AG-44-5<br>KSS-3   | Bright.               | 50K $\Omega$ carbon   | \$1.25               |   |   | P-7                  | AG-60-Z<br>FS-3/SWB                                       | Vol./Sw.   | 500K $\Omega$ carbon<br>SPST            | \$1.25<br>.60 |
|  | 131-0013   | AG-61-5<br>KSS-3   | Vert.<br>Hold         | 1 Meg. $\Omega$ carbon                                      | \$1.25               |   | P-12  | AG-8-5<br>FKS-1/4    | AM-Rejection  | 1000 $\Omega$ carbon                                   | \$1.25                                  |               |
|  | 131-0014   | RTV-10             | Focus                 | 5000 $\Omega$ 4W-W.W.                                       | \$1.85               |   | PD-5  | RTV-146              | Vert./Hor.<br>Hold  | 1 Meg./50K $\Omega$<br>Conc. Dual carbon               | \$3.10                                  |               |
|  | 14MT, MTS<br>16MT, MTS<br>17MC, MTS<br>MT, MTS<br>20MC, MTS<br>MTS | VC-12120B          | AG-19-5<br>FKS-1/4    | Vert.<br>Lin.   | 5000 $\Omega$ carbon |   | \$1.25  | PD-6                 | RTV-253   | Contrast/<br>Bright.                                   | 2000/100K $\Omega$<br>Conc. Dual carbon | \$3.10        |
|  | VC-12121C  | AG-84-5<br>FKS-1/4 | Height                | 2.5 Meg. $\Omega$ carbon                                    | \$1.25               |   | MST-12<br>MST 14<br>14TR<br>16TR<br>17CD<br>17CRR<br>17ROG<br>20CD<br>20TR<br>112X<br>203D<br>312<br>819<br>3163CR<br>8163CR<br>8193CM<br>1st Run | P-2                  | AG-19-5<br>FKS-1/4  | Vert.<br>Lin.  | 5000 $\Omega$ carbon                    | \$1.25        |
|  | VC-12127B  | RTV-297            | Contrast.<br>Vol./Sw. | 750 Tap 500/250K $\Omega$<br>Conc. Dual--SPST               | \$4.30               |   | P-5   | AG-84-5<br>FKS-1/4   | Height  | 2.5 Meg. $\Omega$ carbon                               | \$1.25                                  |               |
|  | VC-12130   | AG-49-5<br>KSS-3   | Bright.               | 100K $\Omega$ carbon  | \$1.25               | P-6   | A10-1500<br>FKS-1/4   | Focus                | 1500 $\Omega$ 4W-W.W.                                     | \$1.85   |   |               |
|  | VC-12131   | AG-44-5<br>KSS-3   | Hor.<br>Hold          | 50K $\Omega$ carbon   | \$1.25               | P-7   | AG-60-Z<br>FS-3/SWB   | Vol./Sw.             | 500K $\Omega$ carbon<br>SPST                              | \$1.25<br>.60  |   |               |
|  | VC-12132B  | AG-83-5<br>KSS-3   | Vert.<br>Hold         | 1.3 Meg. $\Omega$ carbon                                    | \$1.25               | PD-4  | RTV-145   | Contrast/<br>Bright. | 750 Tap 250/100K $\Omega$<br>2W-W.W./carbon<br>Conc. Dual | \$3.70   |   |               |
| AM-17C,<br>CB, C1M<br>ET, T1M                                      | PT-1002  | RTV-252            | Contrast<br>Vol./Sw.  | 750 Tap 250/250K<br>2W-W.W./carbon<br>Conc. Dual--SPST      | \$4.30               | PD-5  | RTV-146   | Vert./Hor.<br>Hold   | 1 Meg./50K $\Omega$<br>Conc. Dual carbon                  | \$3.10   |   |               |
| AM-20C, T<br>PL-17CB, CG,<br>PG, TM<br>20C<br>23P                  | PT-1004  | AG-19-5<br>FKS-1/4 | Vert.<br>Lin.         | 5000 $\Omega$ carbon  | \$1.25               | ARVIN<br>5175<br>5176   | E22464-17   | RTV-258              | Contrast/<br>Vol./Sw.                                     | 25K/3 Meg. Tap<br>1 Meg. Conc. Dual<br>carbon--SPST    | \$4.30                                  |               |
|  | PT-1005  | AG-84-5<br>FKS-1/4 | Height                | 2.5 Meg. $\Omega$ carbon                                    | \$1.25               |   | E22464-20   | RTV-259              | Vert. Lin./<br>Height                                     | 3000/2.5 Meg.<br>2W-W.W./carbon<br>Conc. Dual          | \$3.10                                  |               |
|  | PT-1007  | AG-49-5<br>KSS-3   | Bright                | 100K $\Omega$ carbon  | \$1.25               |   | CHASSIS<br>TE320  | E22464-34            | AG-49-5<br>KSS-3  | Bright.  | 100K $\Omega$ carbon                    | \$1.25        |
|  | PT-1008  | AG-61-5<br>KSS-3   | Vert.<br>Hold         | 1 Meg. $\Omega$ carbon                                      | \$1.25               |   |   | E22464-35            | Order from<br>MFR.  | Tone/<br>Phono Sw.                                     |   |               |
|  | PT-1009  | AG-44-5<br>KSS-3   | Hor.<br>Hold          | 50K $\Omega$ carbon   | \$1.25               |   |   | E22464-36            | AG-83-5<br>KSS-3  | Vert.<br>Hold  | 1.5 Meg. $\Omega$ carbon                | \$1.25        |
| 20PC<br>20PC5<br>20PC52  | VC-12120B  | AG-19-5<br>FKS-1/4 | Vert.<br>Lin.         | 5000 $\Omega$ carbon  | \$1.25               |   |   | E22464-37            | AG-44-5<br>KSS-3  | Hor.<br>Hold   | 50K $\Omega$ carbon                     | \$1.25        |



This supplementary sheet is for use as an up-to-the-minute addition to your Clarostat RTV Manual. Manuals are available through your distributor or directly from Clarostat. Price \$1.00.

Form No. 751835010-5M-11/52

**CLAROSTAT MFG. CO., INC.**  
**DOVER, NEW HAMPSHIRE**

Please mention *Successful Servicing* when answering advertising.

## Replacement Parts

(Continued from page 8)

percentages, and sometimes in a value of capacitance, whichever is the greater of the two. As to *minimum* tolerances, they vary with the type of component. For example the minimum tolerance generally considered in ceramic dielectric capacitors and in silver mica capacitors is  $\pm 1$  percent. In the plain foil mica dielectric unit it is  $\pm 2$  percent, whereas in paper dielectric capacitors it is  $\pm 5$  percent. In electrolytic capacitors the minimum tolerance is 10 percent.

While on the subject of tolerances it is necessary to comment that the minimum tolerances quoted here are not necessarily the standard tolerances which are used for components in television (and radio) receivers. The high order of accuracy indicated by these minimum tolerances are seldom applied to household electronic equipments. The figures used are much more liberal, but none the less important as far as accomplishing a desired result, hence demanding recognition by the service technician who is making a replacement. It is because of this that television receiver manufacturers frequently list the capacitance tolerance in their service literature, and why the Rider Replacement Parts Program listings of capacitors always state the capacitance tolerance.

Each type of capacitor bears a standard tolerance figure plus and minus. The list shown below indicates the range of tolerances associated with capacitors used in household electronic appliances such as television and radio receivers. Attention is called to the fact that we have omitted the full gamut of capacitance tolerances which are *available* on request from capacitor manufacturers; instead we show only those values which appear in the capacitor specifications set by the receiver manufacturers for capacitors used in their television and radio receivers, and whatever other electronic products they make for public consumption. The list which follows applies to capacitors in excess of 10  $\mu\text{f}$ . Lower values of capacitance have already been dealt with.

It is understandable that every single capacitance tolerance figure which is used in the industry is not listed here. But it can be said that those which represent the vast majority are included.

It also is important to state that the letter code shown on this listing corresponds to the coding in capacitor specifications contained in capacitor manufacturers' catalogs and in *RTMA* as well as *JAN* specifications. We have however omitted the letter coding indicative of 1, 2 and 3 percent capacitance tolerances. These are F, G and H respectively, although the letter H when applied to ceramic units indicates 2.5 percent.

Finally, attention is called to the possibility of confusion between the capacitance tolerance code letters and the Temperature Coefficient as well as the Temperature Co-

efficient Tolerance code letters. While similar code letters apply to all of these, their meanings are completely different.

| Type of Capacitor      | Standard Industry Capacitance Tolerance in Percent | Capacitance Tolerance Values Used in Percent | Letter Code |
|------------------------|--|--|-------------|
| Mica                   |  |  |             |
| (Plain)                | $\pm 20$   | $\pm 20$                                     | M           |
|                        |  | $\pm 10$                                     | K           |
| (Silver)               | $\pm 5$  | $\pm 10$                                     | K           |
|                        |  | $\pm 5$                                      | J           |
| Ceramic                |  |  |             |
| (GP)#                  | $\pm 20$   | $\pm 20$                                     | M           |
|                        |  | $\pm 10$                                     | K           |
|                        |  | $\pm 5$                                      | J           |
| (GMV)*                 | + 100<br>and - 0                                   | + 100 - 0                                    |             |
|                        |  | + 100 - 20                                   |             |
| (TC)**                 | $\pm 10$   | $\pm 10$                                     | K           |
|                        |  | $\pm 5$                                      | J           |
| Paper Dielectric       | $\pm 20$   | $\pm 20$                                     | M           |
|                        |  | $\pm 10$                                     | K           |
|                        |  | $\pm 5$                                      | J           |
|                        |  | + 60 - 25                                    |             |
|                        |  | + 40 - 20                                    |             |
|                        |  | + 40 - 15                                    |             |
|                        |  | + 40 - 10                                    |             |
|                        |  | + 20 - 10                                    |             |
| Electrolytic (Tubular) |  | + 100 - 10                                   |             |
|                        |  | + 150 - 10                                   |             |
|                        |  | + 250 - 10                                   |             |
| (Can)                  |  | + 40 - 10                                    |             |
|                        |  | + 50 - 10                                    |             |
|                        |  | + 100 - 10                                   |             |
|                        |  | + 150 - 10                                   |             |

# General Purpose

\* Guaranteed Minimum Value

\*\* Temperature Compensating

*Applications of Capacitance and Capacitance Tolerance.* How are these two constants used? . . . To begin with, the capacitance required in a circuit is a function of the design of the system which uses it. Among the constants of the circuit is the amount of capacitance required. But seldom, if ever, is this value an absolutely precise one; invariably it is an approximation, although it is stated as a definite amount as that value which most closely approximates the nearest standard value. We refer to it as an approximation because the capacitance value indicated is  $\pm$  a certain amount of capacitance. For instance the capacitance specified by a receiver manufacturer for a circuit may be 0.0022  $\mu\text{f} \pm 10$  percent. Assuming all other conditions satisfied, any value of capacitance between 0.00198  $\mu\text{f}$  and 0.00242  $\mu\text{f}$  seems suitable.

The conclusions accompanying the example are correct except for one additional consideration. Suppose we deal with the 0.0022  $\mu\text{f}$  unit. In order to be a suitable replacement within the stated 10 percent capacitance limits, the value must be a measured value for the replacement unit. If this is not so, but instead a capacitor labelled

(Continued on page 23)



A monthly summary of product developments and price changes supplied by RADIO'S MASTER, the Industry's Official Buying Guide, available through local parts distributors.

COMMENT: Since the last reported period, fewer manufacturers were engaged in "change activity". TV and radio receiving tube manufacturers are continuing their tendency toward increasing prices, while other product group price changes remain spotty with no apparent trend.

### New Items

AEROVOX — Introduced a number of new items including AFH triple and quad electrolytic capacitors.

AMERICAN ELECTRONICS — Added No. 4-01, Code Booklet at \$5.50 dealer net . . . No. 103-01, Advanced Course at \$6.95 dealer net and Individual Records at \$1.40 dealer net.

AMERICAN PHENOLIC — Added Model 114-053, UHF bo-ty antenna at \$3.00 dealer net . . . Model 114-560, UHF bo-ty reflector at \$1.65 dealer net and Model 114-558, UHF bo-ty stacking harness at \$3.36 pr/dealer net.

BELL SOUND SYSTEM — Added Model 372MB, 30 watt mobile amplifier at \$165.00 dealer net.

BRIDGEPORT BRASS — Added plastic spray Model 603 at \$1.95 dealer net.

CLAROSTAT — Added TV replacement controls RTV 384 to 390 inclusive.

CORNELL-DUBILIER — Added Model V-8, VHF antenna at \$25.50 dealer net . . . Model U-4, UHF antenna at \$5.97 dealer net and Model 110T22, vibrator converter at \$47.31 dealer net.

CREST LABS. — Added Model LVB-117, line voltage booster at \$10.08 dealer net.

EBY SALES — Added laminated miniature sockets No. 49-6H at \$1.35 dealer net and No. 49-7H at \$1.80 dealer net.

GENERAL ELECTRIC — Added germanium transistors 4JA1A1 at \$1.95 dealer net . . . 4JA1A2 at \$3.85 dealer net . . . 4JA1A3 at \$4.80 dealer net and 4JA2A4 at \$5.30 dealer net. Also added Model UPX-009, pickup and transcription arm at \$9.33 dealer net . . . Model RPX-051, triple play variable reluctance cartridge at \$5.28 dealer net and Model RPX-042, variable reluctance cartridge at \$4.35 dealer net.

GON-SET — Added No. 1499, UHF line at \$7.08/100 ft. dealer net . . . No. 3027, cascade pre-amplifier at \$19.95 dealer net and No. 3028, signal slicer at \$29.95 dealer net.

ILLINOIS RESEARCH LABS. — Added Silencer in quart size at \$6.50 dealer net and introduced Sta-clear, new chemical solution for keeping static attracted dust from accumulating on picture tube at \$1.00 dealer net. (4 oz. bottle).

KENWOOD ENGINEERING — Added Model 12W, 12" wall bracket and Model 7W, 7" wall bracket.

MERIT TRANSFORMER — Added Model HVO-11, transformer at \$5.40 dealer net.

MINNESOTA MINING — Added 7" (1200') professional reel and box (plastic) at \$1.25 list.

RADIO CITY PRODUCTS — Added a number of new items including Model 345, super vacuum tube voltmeter at \$47.50 dealer net and Model 8873, TV servishop at \$139.95 dealer net.

R.C.A. — Added radio receiving tubes 6AR5 at \$1.65 list . . . 6AX4GT at \$2.40 list and 6K8G at \$3.30 list. Also added electron tubes 3C45 at \$17.80 list . . . 91 at \$30.00 list . . . 5718 at \$8.65 list and 6211 at \$2.95 list.

RAYTHEON — Added 6AH6V, radio receiving tube at \$3.90 list, a miniature sharp cut-off pentode having high transconductance and low input and output capacitances, and is designed specifically for television amplifier applications.

REEVES SOUNDCRAFT — Added soundcraft 45 rpm recording disc at \$6.66 dealer net.

STANDARD TRANSFORMER CORP. — Added deflection yokes Model DY-11A at \$6.00 dealer net and Model DY-12A at \$6.00 dealer net.


STROMBERG-CARLSON — Added a number of new items including No. AP-51, power amplifier at \$157.50 list and TR-13, line transformer at \$3.50 list.

SYLVANIA — Added radio receiving tubes 6T4 at \$3.55 list . . . 1XR8 at \$2.65 list . . . 40B2 at \$2.05 list . . . 6SN76TA at \$2.20 list and sub-miniature tubes 1T6 at \$2.05 list . . . 6BF7 at \$1.85 dealer net and 6BG7 at \$1.85 dealer net.

(Continued on page 24)




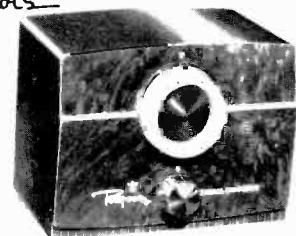Thomas A. White  
president: Jensen Manufacturing Company, Chicago, Illinois  
says: "In every field there's one leader  
---- in boosters it's **Regency**"  
the largest selling booster at any price









Please mention *Successful Servicing* when answering advertising.

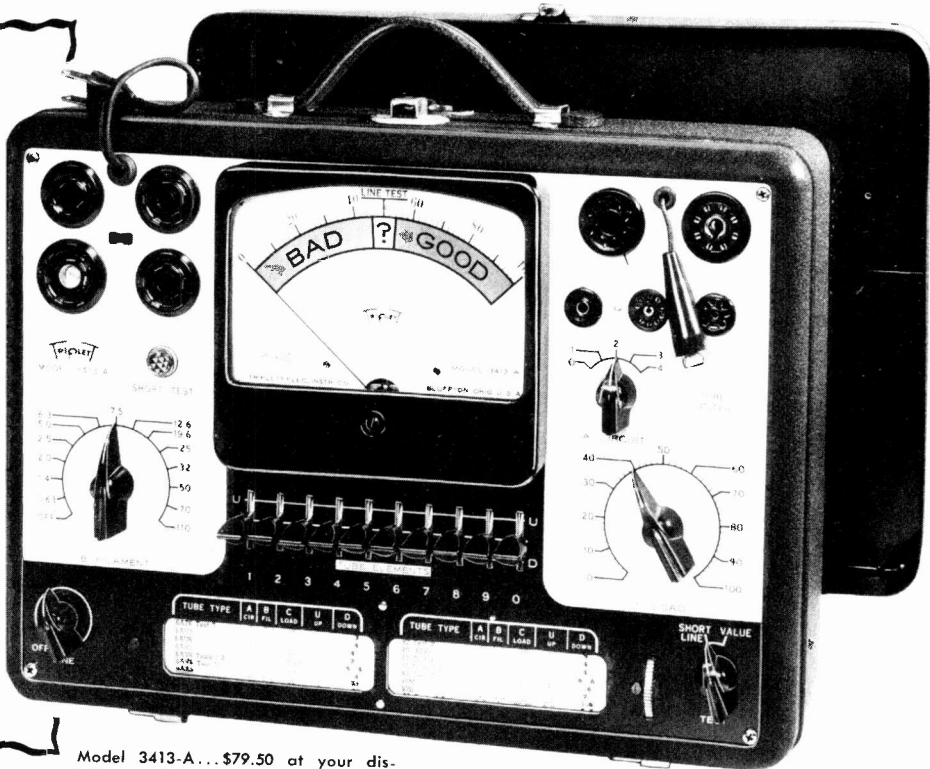For accurate  
flexible and  
quick tube  
testing at  
low cost...  
model 3413-A

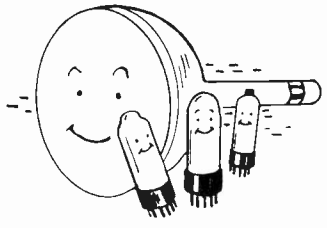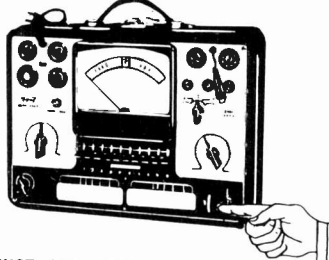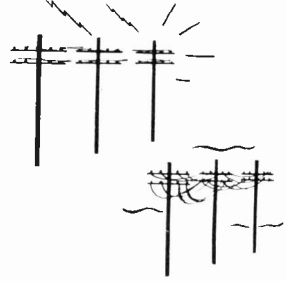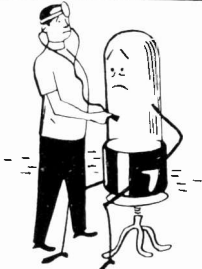

Model 3413-A...\$79.50 at your distributor. (Price subject to change.) BV Adapter, \$7.90 Add'l.

1. **YOU CAN TEST MORE TYPES** of tubes, also appliances for shorts and open circuits. 
2. **JUST SPIN THE KNOB**—for correct, last-minute data, on the speed roll chart. Lists 700 tubes. 
3. **YOU CAN COMPENSATE** for line voltage—just throw snap-action switch. 
4. **YOU CAN TEST EACH ELEMENT** in each tube—by a simple flip of the switch. 
5. **YOU CAN TEST THE NEW TUBES**—including those with low cathode current. 
6. **YOU GET NEW TUBE DATA**—immediately, while it is still news. No waiting. 

*Nearly Half a Century of Service to the Service Man*



**TESTS PICTURE TUBES, TOO!** With this BV Adapter, Model 3413-A tests every tube in a TV receiver, including the Picture Tube—without even removing tube from receiver or carton! Saves time!

FOR THE MAN WHO TAKES PRIDE IN HIS WORK

# Triplet

TRIPLETT ELECTRICAL INSTRUMENT CO., BLUFFTON, OHIO, U. S. A.

## Replacement Parts

(Continued from page 20)

with the standard value of say 0.002  $\mu\text{f}$  (which is within tolerance of the original) is contemplated, what must be its tolerance? If it conforms with standard industry practice, namely  $\pm 20$  percent, then it could have any value between 0.0016  $\mu\text{f}$  and 0.0024  $\mu\text{f}$ . Obviously it would be within tolerance on the high side but not on the low side.

Suppose that the contemplated replacement rated at 0.002  $\mu\text{f}$  was within a  $\pm$  tolerance of 10 percent, what then? On the low side it would have a value of 0.0018  $\mu\text{f}$  and on the high side it would be 0.0022  $\mu\text{f}$ . Again it is within tolerance on the high side but outside the tolerance on the low side.

Suppose we consider the next higher standard value, say 0.0025  $\mu\text{f}$  for the replacement. Would any normal tolerance satisfy? With a rating of  $\pm 10$  percent, the low limit would be 0.00225  $\mu\text{f}$  and the high limit would be 0.00275  $\mu\text{f}$ . Now the contemplated replacement is within tolerance on the low side but beyond tolerance on the high side . . . Is there any answer?

Of course there is! But before we describe it, we might present another practical question — how important is the capacitance tolerance? . . . A simple reply is to say that it all depends on the circuit where the capacitor is used. But this is a very indefinite answer. We know that bypassing capacitance values are not as important as capacitance values related to time constant circuits, or resonant circuits or coupling circuits. But does it make sense to set up a tolerance on the tolerance in each and every particular application of a capacitor? . . . To do this involves something else — namely complete knowledge concerning the conditions established by the design engineer in every section of a television receiver which he designed . . . This is very difficult to determine. It is much easier to recognize the requirements established in the design of the receiver as indicated by the constants of the capacitor, and to satisfy these requirements of capacitance and capacitance tolerance.

To do this is simple. It means nothing more than the procurement of a capacitor rated at the same nominal capacitance and capacitance tolerance as the original. This is no problem because design engineers are using standard values, and capacitor manufacturers, are making them. We admit that procurement practice of this kind for replacement purposes is somewhat of a departure from past tactics, but to adopt it makes most sense, because it enhances the possibility of making the proper repair and attaining best performance from the receiver.

The above suggestion to follow the capacitance tolerance stipulated for the original is subject to some qualifications, especially

in the case of paper dielectric and electrolytic capacitors. Some of the tolerance percentages are different for the + side than for the — side, as for example + 60 percent and — 20 percent. In that event a variety of selections is available. Assuming the same nominal value of capacitance, say 0.005  $\mu\text{f}$  for the original and the contemplated replacement component, a replacement rated at any value of + tolerance between 0 and 60 percent and — tolerance between 0 and 20 percent obviously is suitable.

But the leeway for selection is even greater than described. With a 60 percent tolerance on the + side, the upper limit is 0.008  $\mu\text{f}$ . On the — side, it is 0.004  $\mu\text{f}$ . Under the circumstances, any standard value of capacitance which, with its rated tolerance limits falls within these two extremes of capacitance, is suitable as a replacement as far as capacitance is concerned. Naturally, any capacitor whose measured values fall within these limits is satisfactory capacitance-wise.

The use of + 60 percent and — 20 percent as capacitance tolerances are purely illustrative. It could just as soon be + 100 percent and — 10 percent, as in some electrolytic capacitors. The same reasoning applies to any other set of capacitance values established by the tolerance limits for any type of capacitor. The more liberal the capacitance tolerance figures, the easier is it to find a suitable replacement in terms of capacitance. It is only when the capacitance is relatively small, say between 10  $\mu\mu\text{f}$  and 100  $\mu\mu\text{f}$  and the tolerance is severe, say 5 percent or even 10 percent in both directions — that it becomes difficult to find a replacement other than one which parallels the original in nominal capacitance and tolerance. Occasionally this happens with higher values of capacitance.

Two other items warrant comment, even if not complete at this time. One of these pertains to possible misinterpretation of these references to satisfying the capacitance requirement. This should not be construed as implying that as long as this constant and the tolerance constant requirements are met, free interchangeability exists between capacitor types. This is not so, for reasons which will become evident when the other constants are discussed.

The second item is a slight elaboration of a point already raised concerning capacitors rated at 10  $\mu\mu\text{f}$  and less. There isn't too much margin in these values for the selection of one standard value for another, based on the capacitance tolerance. One or two micromicrofarads do not seem like too much capacitance but when dealing with very small values to begin with, they represent high percentages. Moreover the selection of these small values is based on engineering requirement, and it is best servicing practice to comply with these needs, even if the reasons for their existence are not immediately apparent.

## TELL-A-FAULT

FILLS A MUCH NEEDED AID  
ON THE SERVICE BENCH.

Orville Hoffman  
Hoffman Radio Service  
521 Liberty Street  
Ripon, Wisconsin

"Should go a long way to assist servicemen in their work where they do not specialize in one make."

J. R. Kelley  
Riverdale, Maryland

"There isn't anyone more capable of furnishing us servicemen with this information than Rider."

William J. Stack  
R1, Box 38  
Sturtevant, Wisconsin

### NEED WE SAY MORE!

These comments are from servicemen just like yourself who are using TELL-A-FAULT in their everyday servicing work. They have found that TELL-A-FAULT does their troubleshooting for them. It can do the same for you!

This quadruple-threat service consists of:

- (1) time-saving pictorial, symptom and cure sheets
- (2) fault pinpointing circuit guides
- (3) servicing-techniques short cuts
- (4) how to use all sorts of test equipment

Save anywhere from 50 to 200 hours of troubleshooting time per year by using this practical service based on symptoms rather than circuitry. It completely removes the guesswork in locating receiver troubles by rapidly locating the faults and giving you the proper cures.

TELL-A-FAULT is only a few months old, but the idea has caught on with thousands of progressive service technicians throughout the country.

The entire service costs you less than twenty cents a week. You receive a full 12 month's TELL-A-FAULT for only \$10.00.

Start your subscription today! We'll send you your TELL-A-FAULT binder, subject separators and all the installments that have been released to date. For full information on the most unique SERVICE ever made available to TV and radio service technicians — write to Dept. TF 8.



JOHN F. RIDER  
PUBLISHER INC.  
480 Canal St., N. Y. 13, N. Y.

# Radio's Master Reports

(Continued from page 20)

**TRICRAFT PRODUCTS** — Added Model U-1, UHF antenna at \$7.50 dealer net.  
**TRIPLETT ELECTRICAL INSTR.** — Added No. 9989, signal tracing probe at \$9.50 dealer net, for use with Model 3441 TV-FM oscilloscope and BV adaptor for TV picture tube tests at \$7.90 dealer net.  
**TV WIRE PRODUCTS** — Added new series, formvar covered copperweld, at \$4.72 dealer net, per 100 feet and at \$47.21 dealer net, per 1000 feet.  
**VACO PRODUCTS** — Added No. RT-14, handy service kit, complete with 7 nut drivers, 2 Philips and 3 regular drivers plus extension piece at \$7.34 dealer net.  
**WEBSTER-ELECTRIC** — Added No. 90-25, separate teletalk amplifier for paging at \$120.00 list and 15 pair plastic interstation cable and junction box at \$.34 list (on reel).

## Discontinued Items

**ADVANCE ELECTRIC & RELAY** — Discontinued Model 400M, transmitter relay.  
**AMERICAN PHENOLIC** — Discontinued Model 14-358, twin lead transmission wire . . . Model 187-072 and Model 187-079, molded polyethylene rims and Model 509, rotator. Model 14-298, 100, 500, 1000 feet, remote control wire, temporarily discontinued.  
**CLAROSTAT** — Discontinued wire wound control 43-7000.  
**ELECTRONIC TECHNICAL INSTITUTE** — Discontinued Model 5207, Novice 80-M transmitter kit.  
**GENERAL ELECTRIC** — Discontinued Model RPX-046, broadcast type variable reluctance cartridge. Also discontinued G-10 series of transistors.  
**GON-SET** — Discontinued Model 3005, tri-band amateur converter and their Gonset radarray series.  
**KENWOOD ENGINEERING** — Discontinued Model 140, 7" wall bracket.  
**POTTER & BRUMFIELD** — Discontinued LC and LP series of plate circuit relays.  
**SHURE BROS.** — Discontinued Model 55 and Model 556, multi-impedance, super-cardioid microphones.  
**SIMPSON ELECTRIC** — Discontinued Model 340, signal generator.  
**STROMBERG-CARLSON** — Model RD-22, driver unit, discontinued.  
**SUPREME, INC.** — Discontinued Model 675, signal generator.  
**WEBSTER-ELECTRIC** — Discontinued Model 53D50, teletalk amplifier for paging and Model 5C45, speaker microphone.  
**WIRT PRODUCTS** — Discontinued auto radio ignition suppressors S-915 and S-918.

## Price Increases

**ASTATIC CORP.** — Increased price on "scanafar" booster, Model CT-1 to \$21.00 dealer net.  
**BLONDER-TONGUE** — Increased price on Model MT-1, matching transformer to \$3.90 dealer net.  
**CORNELL DUBILIER** — Increased price on Model 8BD, "hi-ball" auto aerial to \$3.03 dealer net.  
**DUMONT LABS.** — Increased price on two 12", one 16", four 17", four 20", and three 21" TV picture tubes.  
**FISHER RADIO CORP.** — Master audio control, Model 50-C, increased to \$97.50 dealer net.  
**GENERAL ELECTRIC** — Radio receiving tube 6BA7 increased to \$2.50 list. Also increased one 12", three 17", one 20" and one 21" TV picture tubes.  
**GON-SET** — Increased price on Model 1531, rhombic UHF antenna, with 9' mast to \$7.77 dealer net.  
**HICKOK ELECTRICAL INSTR.** — Increased price on Model 605, portable all-purpose tube and set tester to \$184.50 dealer net.

**R.C.A.** — Increased price on Model WO-88A, 5" oscilloscope to \$169.50 user price. Also increased power tube fittings 202F1 to \$23.85 user price . . . 211F1 to \$28.20 user price and 228F1 to \$67.60 user price.  
**STROMBERG-CARLSON** — Increased price on a number of items including No. MD-38S, dynamic microphone to \$70.00 list.  
**SYLVANIA** — Increased price on three 17", two 20" and one 27" TV picture tube.  
**V-M CORP.** — Increased price on record changers No. 150 to \$33.47 dealer net . . . No. 972 to \$40.17 dealer net and No. 985 to \$53.57 dealer net. (West Coast prices slightly higher)

## Price Decreases

**CREST LABS.** — Decreased price on cathode ray tube rejuvenators Model B to \$3.15 dealer net . . . Model C to \$2.20 dealer net and Model D to \$2.60 dealer net.  
**ELECTRONS, INC.** — Decreased price on grid control rectifier EL C6M to \$31.00 dealer net.  
**GENERAL ELECTRIC** — Decreased price on TV picture tubes 16KP4 and 16KP4A.  
**GON-SET** — Decreased price on Gonset line to \$6.24 dealer net/100 feet.  
**R.C.A.** — Decreased price on radio receiving tube 6L6G to \$3.00 list and electron tube 5654-t to \$4.90 list.  
**WIRT PRODUCTS** — Decreased price on slide switches SW 723 to SW 726.

## INDEX OF CHANGES

| Model No.  | Manual From | Page To | Tek-File Pack |
|--|-------------|---------|---------------|
| Andrea T.VL12<br>Ch. VL12  | 6-1         | 6-10    | 43            |
| Gamble-Skogmo<br>05TV1-43-9014A<br>15RA2-43-9105A<br>Ch. 15AY219 | 6-1         | 6-16    | 31            |
| Hoffman 612<br>Ch. 142   | 5-8         | 5-16    | 35            |
| Magnavox Ch. CT-270, 271, 272, 273, 274                          | 7-14        | 7-28    | 30            |
| Mitchell T16-2KB<br>T16-2KM, T16-B, T16-M                        | 6-1         | 6-4     | 45            |
| Sylvania 23M-1, 23B, 23M, 24M-1<br>Ch. 1-387-1                   | 8-118       | 8-139   | 13            |
| Sylvania 74M<br>Ch. 1-356 (C'05)                                 | 8-160       | 8-173   | 13            |

HAVE SUCCESSFUL SERVICING DELIVERED TO YOUR MAILING ADDRESS EVERY MONTH!

John F. Rider Publisher, Inc.,  
 Dept. C9  
 480 Canal Street  
 New York 13, N. Y.

Gentlemen:


Rather than take the chance of missing the alternate copy of SUCCESSFUL SERVICING at my jobber's, I am enclosing one dollar (\$1.00) to cover the cost of direct-to-my-home mailing every month.

Name .....

Address .....

City..... Zone .. State .....

Cash  Check  Money Order

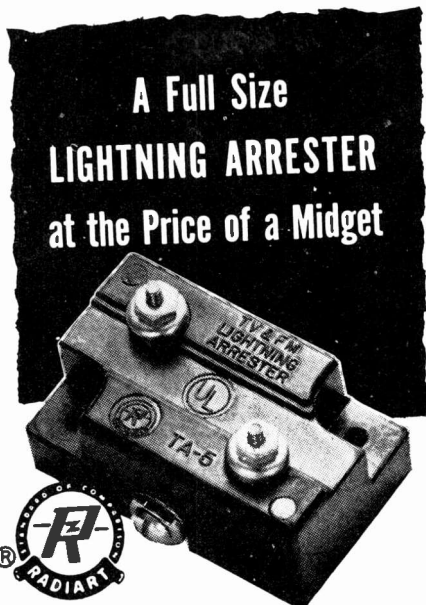

## LIGHTNING ARRESTER

**MODEL TA5** Real protection against lightning and static charges — the RADIART Lightning Arrester has all the features! Fits anywhere... inside or out... handles standard or jumbo leads... no wire stripping necessary... does not unbalance the line... low internal capacity... no loss of signal... internal resistance "leaks off" static discharges!  
 UNDERWRITERS LABORATORIES APPROVED.

THE RADIART CORPORATION

CLEVELAND 13, OHIO

Please mention Successful Servicing When answering advertising.

## GET YOUR COMMERCIAL TICKET EASIER WITH...

**RADIO OPERATOR'S LICENSE Q AND A MANUAL** (4th Edition) by Milton Kaufman Covers Elements 1 through 8. Complete discussion of answers to every technical question in the F.C.C. Study Guide! Used by over 50 leading schools. Only \$6.60 at jobbers, bookstores or direct from—



JOHN F. RIDER Publisher, Inc.

480 Canal Street, New York 13, N. Y.

REVISED JAN. 1953

COMING IN APRIL RIDER'S TV11

PERMIT NO. 9427  
 NEW YORK, N. Y.  
**PAID**  
 U. S. POSTAGE  
 Sec. 3466, P. L. & R.

J. L. HERRIN  
 HATTIESBURG, MISS.  
 1817 HARDY ST.  
 RADIO SERVICE CO.

Forwarding and Return Postage Guaranteed  
 480 CANAL ST., NEW YORK 13, N. Y.  
 JOHN F. RIDER PUBLISHER, Inc.  
 From