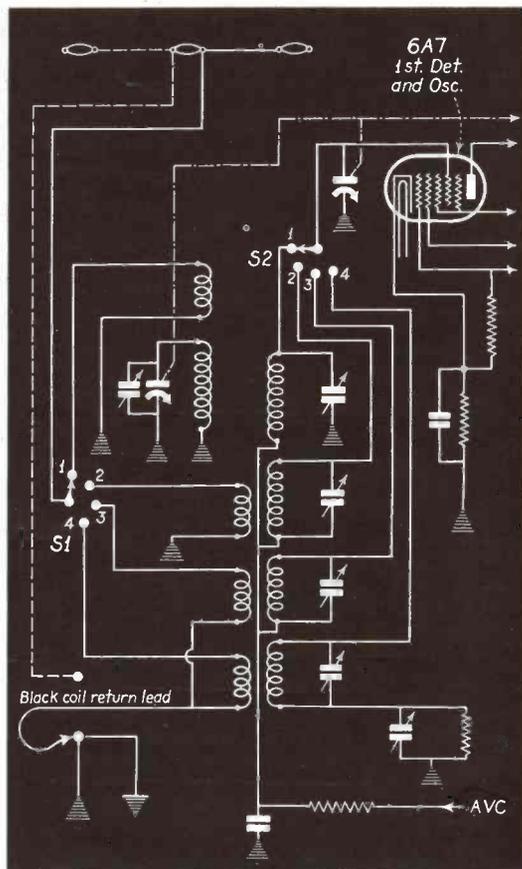




# SERVICE



## A MONTHLY DIGEST OF RADIO AND ALLIED MAINTENANCE



All-Wave Switching

(See Page 328)

PER COPY  
25 CENTS

SEPTEMBER  
1934



# WANTED: 900,000 replacement transformers for 1934

**A**ND that's a lot of anybody's transformers . . . certainly it's a lot of good business for the service men of the country even though the figures are estimated from the actual number of replacement transformers sold in 1933 and those sold to date this year.

Anyone with a mathematical mind and nothing else to do could go on from here and figure possible costs to the set owners and from there to the margin of profit to the service men.

All of which would be interesting but not nearly so important as a forecast of the kind of service those transformers were going to give. Because, these nearly-a-million transformers will be installed as **REPLACEMENTS** . . . to renew the original performance of the sets. Their performance is going to be a direct reflection for good or otherwise on the service men who install them.

Not all of these replacements can possibly be **STANCOR EXACT-DUPLICATE** Replacement Transformers . . . there are certain makes and models of receiving sets that never went into big enough production to warrant this organization or its authorized distributors making and carrying in stock **EXACT-DUPLICATES** for them. There are however

**STANCOR UNIVERSAL** Replacement Power Transformers, Audios and Chokes . . . most elastic and easy to install that are strongly recommended for these circumstances and, indeed, in emergencies may be used as full replacements with a high degree of satisfaction.

Of course there is nothing that is so positive in renewing original performance as **STANCOR EXACT-DUPLICATE** Replacement Transformers. They are identically like the original in every electrical and physical characteristic. There are no new holes to be drilled and no re-wiring jobs. In appearance, the customer is satisfied, because it looks like the original and . . . performs like the original.

All **STANCOR** Transformers for replacement carry either the **EXACT-DUPLICATE** Trade Mark or the **STANCOR** Trade Mark. They are packaged in a distinctive container carrying one or the other of the trade marks mentioned. Authorized **STANCOR** distributors all over the United States, Canada and our Island possessions can supply you with **STANCOR** catalogs and listings. To be sure your name is on the regular mailing list to receive all bulletins and information on **STANCOR** units, drop us a line here. It will be worth your time and important to your income.



Every Radio Service Man  
should be a member of the  
Institute of Radio Service Men

STANDARD TRANSFORMER CORPORATION, 862 Blackhawk Street, Chicago, Ill.

THE NEW  
WESTON MODEL 698  
SELECTIVE SET SERVICER  
**\$ 34.50**  
NET COMPLETE  
IN THE U. S. A.  
Including socket selector set,  
leads, carrying case, etc.

WESTON  
*built*

THE NEW  
WESTON MODEL 682  
TUBE CHECKER  
**\$ 29.25**  
NET  
IN THE U. S. A.  
With either counter or  
portable case.



2

*profit producers*  
FOR DEALERS AND SERVICE MEN

A Weston Selective Set Servicer, complete for \$34.50! A Weston combination portable and counter type Tube Checker for \$29.25! That's news... good news, for dealers and servicemen. No wonder these two profit-producing instruments are sweeping into favor.

Model 698 Set Servicer employs the improved Weston Method of Selective Analysis... making this a lifetime Servicer. Model 666 Type 1A Socket Selector Set is included at this low price, together with leads, instructions, carrying case, etc.

Model 682 Tube Checker is a combination servicer and merchandiser. Attractively finished and with a scale with a "good tube" area it makes a convincing merchandiser when mounted in the counter type case. A leatherette case is available for field work. Has a low obsolescence factor. Meets every requirement.

Every dealer and serviceman should get the facts about these two instruments. See them at your jobber's or send for descriptive bulletins. Weston Electrical Instrument Corp., 604 Frelinghuysen Ave., Newark, N. J.

WESTON  *Radio Instruments*

WESTON ELECTRICAL INSTRUMENT CORPORATION  
604 Frelinghuysen Avenue, Newark, N. J.

Send Bulletin on Weston Radio Instruments.

Name.....

Address.....

City and State.....

# SERVICE

A Monthly Digest of Radio and Allied Maintenance

Vol. 3, No. 9  
SEPTEMBER, 1934

EDITOR  
M. L. Muhleman

ASSOCIATE EDITOR  
Ray D. Rettenmeyer

## EDITORIAL CONTENTS

### FEATURES

- All-Wave Switching..... 328  
Impedance Bridge for Design and Testing Work  
By *Elmer Schulz*..... 338  
New All-Wave Antenna System  
By *G. S. Granger*..... 327

### ANTENNA (Standardized Servicing—II)..... 322

### ASSOCIATION NEWS ..... 348

### AUTO RADIO

- Arvin Model 16..... 336  
Crosley Syncrotube..... 336  
Majestic Twin Six..... 336  
Stewart-Warner R-117 Chassis..... 336  
1933 Oldsmobile Installations..... 336

### CIRCUITS

- A-K Model 511 Tune-O-Matic Data..... 329  
All-Wave Switching ..... Front Cover  
Atwater-Kent 217-D and 667-D..... 331  
Calculating Electrical Units, Part 3..... 344  
Emerson Models 39 and 59 All-Wave..... 333  
G.E. M-49 Phonograph Motor Data..... 338  
Impedance Bridge ..... 338  
New All-Wave Antenna System..... 327  
Phono. for RCA 60, 62 and 66..... 342  
RCA-Victor Model R-92 Recorder..... 340  
RCA-1C6 ..... 334  
Silvertone Model 1729..... 332  
Stewart-Warner R-117 Chassis..... 337  
Stromberg-Carlson No. 68..... 330  
Wurlitzer SU-5 ..... 334

### FORUM ..... 350

### GENERAL DATA

- Adjusting New Philco Dials..... 342

- A-K Model 511 Tune-O-Matic Data..... 329  
All-Wave Switching ..... 328  
Atwater-Kent 217-D and 667-D..... 331  
Emerson Models 39 and 59 All-Wave..... 333  
G.E. M-49 Phonograph Motor Data..... 338  
Philco Model 18 Change..... 332  
Philco Model 29..... 334  
Philco Model 34 Correction..... 335  
Philco Model 38 Changes..... 332  
Philco Radio-Phonograph Model 507..... 329  
Philco 58 and 84 Changes..... 342  
Phono. for RCA 60, 62 and 66..... 342  
RCA Victor Models 127, 327 Warning..... 334  
RCA-1C6 ..... 334  
Silvertone Model 1729..... 332  
Stromberg-Carlson, No. 68..... 330  
Westinghouse Models and I-F Peaks..... 334  
Wurlitzer SU-5 ..... 334

### HIGHLIGHTS ..... 346

### MANUFACTURERS ..... 353-354

### ON THE JOB

- Adjusting New Philco Dials..... 342  
Philco 58 and 84 Changes..... 342  
Phono. for RCA 60, 62 and 66  
By *E. M. Prentke*..... 342  
"Your Service Code"..... 342

### PUBLIC ADDRESS

- G.E. M-49 Phonograph Motor Data..... 338  
Impedance Bridge for Design and Testing  
Work—By *Elmer Schulz*..... 338  
RCA Victor Model R-92 Recorder..... 340

### SERVICE MAN'S NOTEBOOK (Calculating Electrical Units, Part 3)..... 344

BRYAN S. DAVIS  
*President*

JAS. A. WALKER  
*Secretary*

Chicago Office—608 S. Dearborn St.—C. O. Stimpson, Mgr.  
Telephone: Wabash 1903  
Cleveland Office—10515 Wilbur Ave.—J. C. Munn, Mgr.

Published Monthly by the

Bryan Davis Publishing Co., Inc.  
19 East 47th Street  
New York City

SANFORD R. COWAN  
*Advertising Manager*

A. B. CARLSEN  
*Circulation Manager*

St. Louis Office—505 Star Bldg.—F. J. Wright, Mgr.  
Wellington, New Zealand—Tearo Book Depot.  
Melbourne, Australia—McGill's Agency.

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price \$2.00 per year in the United States of America; 25 cents per copy. \$3.00 per year in Canada and foreign countries; 35 cents per copy.

OFFICIAL RADIO SERVICE MEN'S ASSOCIATION, INC.  
HARRY MARDAS, 406 Garlies Street, Winnipeg, Man.  
Phone: 51063  
Member Official Radio Service Men's Association

June 26, 1934

Clarostat Mfg. Co., Inc.  
287 N. 6th St., Brooklyn, N. Y.

Gentlemen:

Before I started using your products in the numerous repairs I have been doing, I was always called back to check the troubles in the radios which were continuously reoccurring.

It only took the first installation of the Clarostat volume control to prove its ability to handle the signals at their proper level and to step up the signal gradually as the volume was increased.

I have now increased my repair work to 30% and owe it to the Clarostat manufacturers for their turning out of the very fine products.


I would be very much obliged to receive your catalogue, covering the complete list of parts put out by Clarostat, and also your latest volume control guide. Thank you very much.

Very truly yours,  
(Signed) HARRY MARDAS  
The Radio Service Ma


An old story  
to us . . . and a  
good suggestion  
for you to follow.

Send for our new  
**Fall Replacement Guide and  
Catalog . . . it is FREE**

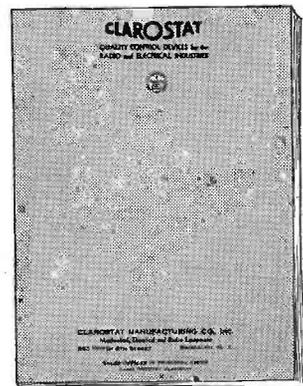Clarostat has made it easy for you to pick the right values for components used on all modern radio receivers. Full data for parts replacement is given on volume controls, tone controls, Clinch-Grip Flexible Resistors, Metal Cover Fixed Power Supply Resistors, Line Ballasts, L & T Pads, Series Mixers, Constant Impedance Devices and Standard Potentiometers.



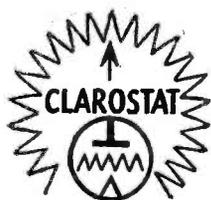Write today for your Free Catalog—it will help you give your customers better service, and will help make your replacement parts business profitable.



**CLAROSTAT**  
TRADE MARK REG. U.S. PAT. OFF.

**Clarostat Manufacturing Co., Inc.**  
287 North 6th Street, Brooklyn, N. Y.



# THE ANTENNA...

## STANDARDIZED SERVICING II

IN last month's editorial, we referred to the desirability of standardization in the servicing field. Other branches of the radio industry have standards and there is no good reason why the servicing field should not also have them.

It has already become apparent that if Service Men do not cooperate, the standards set for the servicing field may come from some other branch of the industry. Such standards may come from a branch either unacquainted with the problems of servicing, or impartial to the interests of the Service Man.

Standards and regulations are gained only by cooperation. It is impossible for five men to set standards and regulations for a group of twenty thousand unless the five men in some way represent the majority. Identical standards for all parts of the country are feasible, but regulations applicable to the city are not necessarily applicable to the small town. Moreover, regulations instituted to meet the necessities of eastern states may well work hardships on Service Men in western states.

Regulations should be left to local bodies, if regulations are even necessary. But standards should be set so that they apply nationally. This is logical since standards have to do with methods and equipment equal in applicability in all parts of the country and common to every Service Man. It would be foolish, for example, to have different tube-pin numbering systems for the south, the north, the east and the west. Yet the lack of standardization has created a condition similar to this example, in that there has been more than one system in use.

Before the Service Man can hope to straighten out the existing differences in the presentation of servicing data, in the methods of servicing, in the types of servicing equipment and in numbering and symbol arrangements, he will have to appoint men representative of the field to work out the problems for the whole group of Service Men throughout the country. Or institute nationwide interconnections between groups and associations so that the servicing field may work out its own problems and standards to the satisfaction of the majority, and at the same time gain the recognition and support of the other branches of the radio industry. In this manner the voice of the Service Man will reach the ears of the engineer and the manufacturer more effectively than it does now.

We believe that standardization can be gained most effectively through the cooperation of existing local and national service associations. Men should be selected by each group or association to represent the collective wishes of the Service Men. Such representatives would not necessarily have to meet in a body—though this would be the ideal way—but could carry on communication with a central bureau set up for the purpose of handling all proposals and votes. The central bureau should be operated by some man or men functioning as an intermediary between the Service Man and the engineering body of the radio industry. In this manner the central bureau would also keep the Service Man

advised of proposals for standards made by the radio engineers so that if objections to such proposals were in order, they could be submitted to the engineering group for study.

In considering standardization, it will be found that servicing procedure, servicing data and servicing equipment are items rather closely allied. For example, the introduction of point-to-point resistance measurement to the servicing field had a definite influence on the design of test equipment and the preparation of servicing data by the set manufacturers. The same sort of influence is evident in the alteration of some servicing data to conform with test-prod trouble shooting, but in this case the change was made so that Service Men would carry out their testing in this manner.

Many of these differences are understandable as there are cases where accurate measurements can be made with the plug-and-cable analyzer and other cases, more particularly in modern receivers, where accurate measurements are not possible at all points if plug and cable are used. Again, there are other cases where certain voltages cannot be read by any instrument owned by the average Service Man, in which case it is usually necessary to resort to resistance measurement as a check on the circuit in question.

Since radio receivers are not all the same in design, they cannot all be tested in the same manner. Alignment procedure for one receiver may be both inadequate and inaccurate for another receiver of practically the same design. These differences in circuit characteristics have to be accounted for in the servicing data.

Nevertheless, a study of present-day receiver servicing data leads one to believe that a partial standardization of procedure as well as presentation would not only simplify servicing but also keep down the number of testing units required in service work.

Standardization of testing equipment is quite a different matter. One might say that with standardization in other branches the testing equipment will automatically fall in line. The manufacturers of such equipment are sensitive to changes in the field and model their equipment accordingly. Moreover, these manufacturers are in a position to set the pace for the entire field without upsetting the applecart. When better and simpler means of testing are available, there will be testing equipment to fill the bill.

It may be that within the next year or so the Service Man will have to go in for sensitivity and selectivity tests on modern receivers. If this be the case, there is the opportunity of making these tests indicate not only the condition of a receiver, but also the nature of the fault, if there be one. If such equipment, together with a cathode-ray oscillograph, is used in all preliminary receiver examinations, the present-day test equipment will be used only for the actual tracing down of a bad resistor or condenser. Rather than complicate existing servicing methods, such equipment would tend to simplify the whole procedure.

# Consider all Points

## OHIOHM RESISTORS

- Trade mark and value stamped on each piece in addition to being R. M. A. Color Coded.
- "Protect-O-Packed" so as to prevent bent or "kinked" wire-leads and to assist in easy selection of proper values.
- A type of container or kit for every type of business.
- Metal Stock Cabinet for jobbers — Counter Server for dealers—First-Aid Kits for service men.
- Spark Suppressor Sets for eliminating ignition interference on auto radios.
- Sales helps and advertising to popularize resistors.
- *Get the OHIOHM story and get started with real net profits.*



Display card for popularizing resistor importance—includes actual OHIOHM Resistor on card

OHM DIAL—for determining resistance value of resistors in sets, according to R. M. A. color code. Furnished Free with First-Aid kit.



Service labels furnished free with First-Aid Resistor Kit.

Radio Resistor Guide also furnished free with initial order.

# OHIOHM

## PROTECT-O-PACKED RESISTORS

THE OHIO CARBON COMPANY • 12510 Berea Rd. • CLEVELAND, OHIO

RESISTORS are made in Canada by C. C. Meredith & Co., Ltd., Toronto

**COMPLETE**  
**AUTHORITATIVE**  
**FREE!**



**Mail**  
**this coupon**  
***NOW* for this**  
**profit making**  
**MANUAL**

MALLORY pioneered in the vibrator field—and set new standards of performance with the justly famous Mallory-Elkon Elkonode. Mallory pioneers *again*—this time by publishing a vibrator replacement and service manual that stands “head and shoulders” above any previous publication of its kind. The Mallory-Elkon Elkonode Service and Replacement Manual will enable any man to meet the ever-increasing service requirements of the automobile radio industry with greater ease, greater certainty—and greater *profit!*

Mail the coupon now for this book that will play a large part in building good business and good-will. Think of it—28 big pages of information that you can't afford to be without, *and it's absolutely free!*

**P. R. MALLORY & CO., Incorporated**  
 INDIANAPOLIS, INDIANA  
 Cable Address—Pelmallo




**P. R. MALLORY & CO., INCORPORATED**  
 Indianapolis, Indiana

Gentlemen:

Please send me a copy of the Mallory-Elkon Service and Replacement Manual—absolutely free.

Name \_\_\_\_\_

Address \_\_\_\_\_

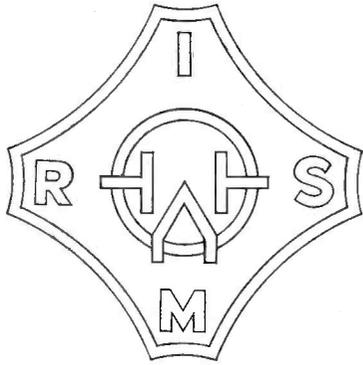

EVERY RADIO SERVICE MAN IN

---

---

# AMERICA

IS INVITED TO SEE THE

## "RADIO CYCLOPS"

and the latest in

RADIO PARTS AND TEST EQUIPMENT

at the

OFFICIAL CONVENTION

and

# EXHIBIT

of the

RADIO SERVICE INDUSTRY

at the

HOTEL PENNSYLVANIA

New York City

October 19-20-21 (Fri.-Sat.-Sun.) 1934




IT is expected that 3000 Radio Service Men will avail themselves of this opportunity to listen to one of the finest programs of Radio Service Subjects, handled by the ablest speakers in America.

THE very latest things in Radio Parts and Radio Test Equipment will be on display. The progressive manufacturers have scheduled the activities of their laboratories so that they can introduce new merchandise at this Exhibit.

---

The Institute of Radio Service Men Invites You to Attend  
ADMISSION FREE

# You Can't Do Without It . . .

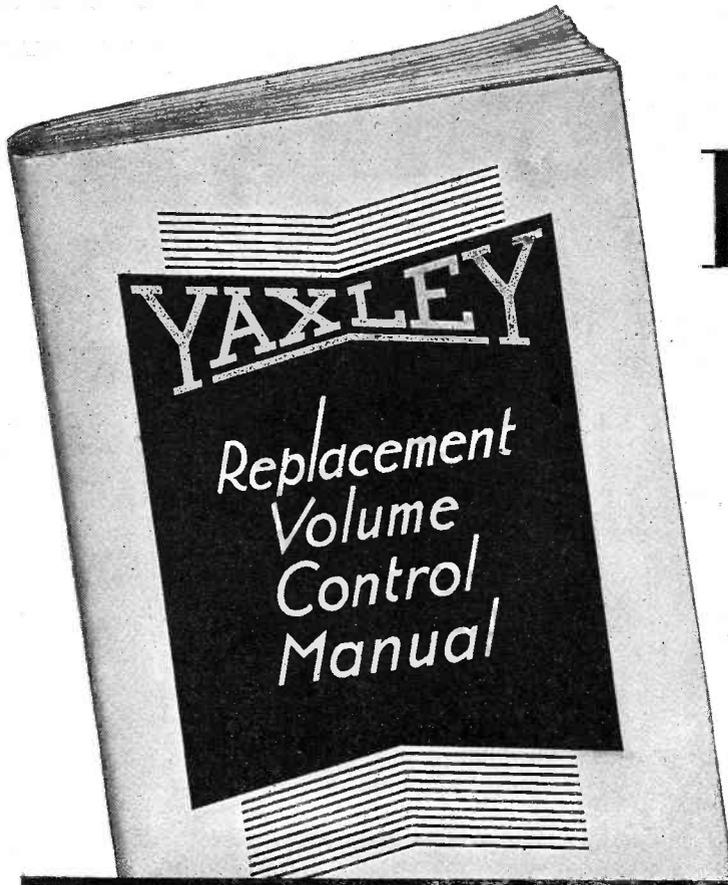

## And It's

# FREE!

*The most complete Manual for Service Men ever published . . . the first that is authoritatively accurate. There's nothing like it. You need it to simplify your work. You need it to make your work more profitable . . . and it's FREE! All you need do is send in this coupon.*

The publication of a complete manual of controls has been attempted often but never before accomplished. Now Yaxley meets the need with an illustrated book of more than 100 pages that is both complete and more definitely helpful than any authority. Along with other invaluable information it


lists the 30 new Yaxley Replacement Volume Controls that will service 98% of the 3200 set models now in existence. It shows, for example, how 4 Yaxley controls will cover 1398 models—how a single control will service 618 different models. Mail the coupon now for this indispensable book.

### YAXLEY MANUFACTURING CO., Incorporated

Division of P. R. Mallory & Company, Incorporated

Indianapolis : : : Indiana

Cable address: Pelmallo

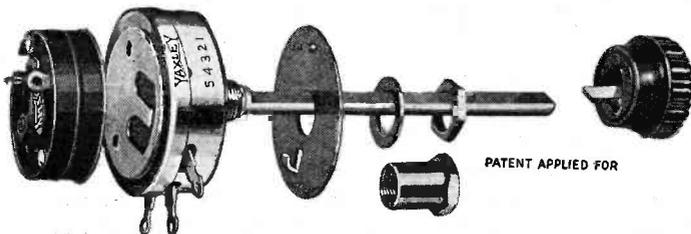

**You want to know about this new Yaxley Replacement Volume Control. It's the greatest advance ever made . . . the biggest boon to service men ever developed.**

*Detailed information is included in the complete Yaxley Replacement Volume Control Manual.*

YAXLEY MANUFACTURING CO., INCORPORATED  
Division of P. R. Mallory & Co., Incorporated  
Indianapolis, Indiana

Gentlemen: Please send me—absolutely free—a copy of the complete Yaxley Volume Control Manual.

Name \_\_\_\_\_

Address \_\_\_\_\_

My Jobber's name is \_\_\_\_\_

# SERVICE

A Monthly Digest of Radio and Allied Maintenance

FOR SEPTEMBER, 1934

## NEW ALL-WAVE ANTENNA SYSTEM

By G. S. GRANGER

**A**N all-wave antenna system that consists of either an inverted L-type or doublet antenna, a low-impedance transmission line, receiver transformer, and antenna coupling unit has recently been introduced. The unique feature of this system lies in its impedance-matching device which has been so designed that the signal *automatically* selects the most efficient circuit for its frequency.

### IMPEDANCE-MATCHING DEVICE

In Fig. 1 is shown the fundamental circuit of the antenna coupling unit, which in reality is nothing more than an impedance-matching device to be used with a doublet antenna, as shown in Fig. 2. It is common knowledge that fixed condensers have a lower impedance at high frequencies than they do at low frequencies. Therefore, when the receiver is tuned to the high frequencies, i. e., any short-wave band, the impedance of the two small condensers shown in Fig. 1 offer the path of least resistance to the incoming radio waves which pass directly through the condensers to the low-impedance transmission line. From this line the signal goes into the receiver impedance-matching transformer and then, by one of three distinct methods, directly to the receiver.

It is also well understood that a doublet antenna cut to a size which is most efficient on the short-wave bands will not function satisfactorily when used for the broadcast band, or vice

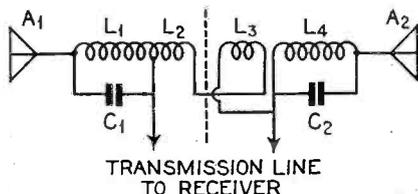


Fig. 1. The fundamental circuit of the all-wave, impedance-matching device, for use with the duplex antenna coupling system.

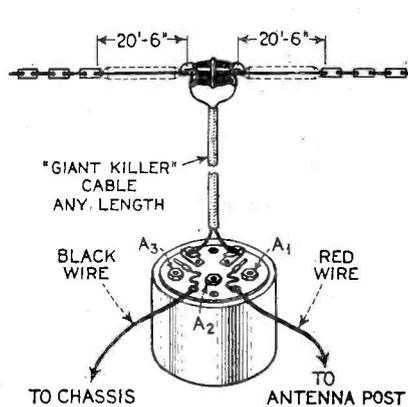


Fig. 2. Connections for the complete antenna system. The dotted lines indicate that cage aerials may be used.

versa. Hence, the transformers shown at either side of the dotted line in Fig. 1 are utilized to carry the broadcast signal into the transmission line at a gain over the signal which would be possible without these transformers. In this case, the impedance of the transformers is very much lower than the impedance of the fixed condensers and the incoming broadcast signal passes through the transformers in preference to the condensers.

It should be kept in mind that in each half of this antenna impedance-matching device we have a tuned circuit comprising the inductances L-1 and C-1 in one case, and L-4 and C-2 in the other. Both of these circuits have infinite impedance at the frequency to which they are tuned and, therefore, this point of resonant frequency must be located in some portion of the frequency spectrum which is not used for either the short-wave or the regular broadcast bands.

Fig. 3 shows the actual connections of the coupling unit and the two ends of the doublet.

### TRANSMISSION LINE

The transmission line is made up of two concentric wires covered by a good

heavy insulation as may be seen in both Fig. 2 and Fig. 4. Standoff insulators serve to hold the line from the wall while an insulator is provided where the line is brought in through the wall. The receiver end of the line connects with a receiver transformer, the impedance of the latter unit closely approximating the 70-ohm impedance value of the transmission line itself.

### RECEIVER TRANSFORMER

The wiring diagram of the receiver transformer is shown in Fig. 5. The output impedance of this transformer may be adjusted by means of simple telephone tip-jacks to match receivers with either high or low input impedance. A third connection is provided on this unit which enables the entire antenna plus the lead-in to be utilized as a regular T-type antenna, for areas where noise occurs in one band and not the others. In addition, this transformer provides a means of coupling a transmission line to the ordinary type of receiver without requiring changes in the receiver.

It is important that the leads from the receiver transformer be kept as short as possible. The red and black wire, supplied with the transformer, are of the correct length. This is particularly true of the black wire. Increasing the length of the black wire will tend to throw the entire system out of balance, resulting in a reduction in its noise reducing properties.

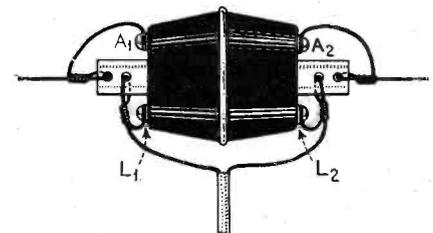


Fig. 3. Details of the antenna coupler, the circuit for which is shown in Fig. 1.

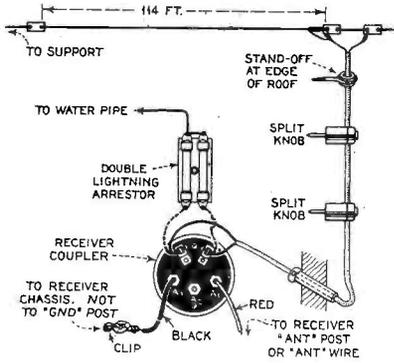


Fig. 4. The arrangement and connections for a simplex antenna system, using an "L" type aerial.

The red and black wires are provided with a telephone tip at one end, for inserting in the pin-jacks. The tipless end of the red wire is connected to the receiver antenna binding post. The spring clip on the black wire is connected directly to the receiver chassis itself.

On receivers which are made with an antenna wire and a ground wire, in place of the usual binding posts, connect to these wires. The best arrangement, in this case, is to connect the ground wire to a suitable ground connection (water pipes are to be preferred) and then connect the spring clip of the black cord directly to the most convenient part of the receiver chassis. The antenna wire coming from the receiver should be cut very short.

The best connections for the tipped ends of the red and black wires are determined by experiment. As a general rule, one determination of these connections is sufficient and the connec-

tion thus established need never be changed.

For receivers having high input impedance, the black tip goes into the jack marked "A3" and the tip on the red wire goes into the jack marked "A1." This connection is generally best for broadcast reception.

For receivers having low input impedance, the black tip remains in the same place, "A3," and the tip of the red wire goes to "A2." This is generally the best connection for the short-wave bands.

When the antenna and the lead-in cable are to be used as an ordinary aerial, the black wire is removed from "A3" and is left out of use, while the tip on the red wire is inserted in jack "A3." This arrangement is only suitable for use in areas where there is no local noise. In some locations it will be observed that local noise exists on some wavebands and not on others. In this event the "A3" connection may prove best.

On all bands, the best results will usually be obtained with the tip of the

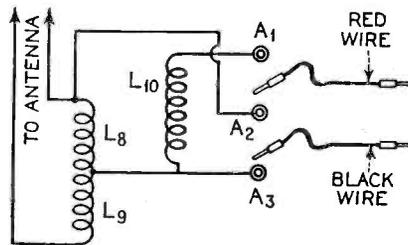


Fig. 5. By means of pin jacks, the impedance of the receiver transformer may be matched to that of the receiver input.

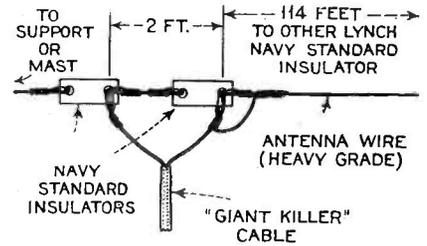


Fig. 6. Method of attaching the down-lead cable to an end-fed antenna, such as the one shown in Fig. 4.

black wire in "A3" and the tip of the red wire in either "A1" or "A2."

#### L-TYPE ANTENNA

Where space is available an L-type antenna is generally considered superior to the doublet type. Fig. 4 illustrates a system of this type. Such an antenna should be at least thirty feet above the ground. By reason of the size of the collector (antenna) the signal it picks up is rather large and compensates for small deficiencies between the antenna and the receiver which could not be tolerated in a collector of smaller size. Therefore, the impedance-matching transformer at the antenna is eliminated for both mechanical and financial reasons. The resulting antenna transmission line connection is shown in Fig. 6.

While best results are obtained with the flat top of the L-type aerial in a straight line, it is not necessary that it be so. However, no section of the horizontal portion should be nearer than 90° to any other section. The length of any individual leg is unimportant and may be any dimension which convenience permits.

## ALL-WAVE SWITCHING

(See Front Cover)

There is shown on the front cover the diagram of the input circuit for the Stewart-Warner Model R-127 All-Wave Receiver. This circuit is of interest for a number of reasons, one being that the switching arrangement automatically takes care of the type of antenna system used with the receiver and also governs the AVC action for each waveband.

#### THE ANTENNA CIRCUIT

We all know that for the best results from an all-wave receiver, it is highly desirable to employ some form of all-wave, noise-reducing antenna system. These antenna systems take different forms, but in most cases it is necessary to deal with a double rather than a single lead-in. For this reason set manufacturers are making provisions in their all-wave receivers for aeri-als of this sort, and at the same time making it possible to use the standard Marconi antenna for the broadcast band.

Referring to the cover diagram, a standard "L" type aerial is shown in solid lines. This, of course, may also be a "T" type. In either case there is a single lead-in wire.

If the ordinary "L" or "T" type antenna is to be used with the receiver for all wavebands, then the "black coil return lead" shown is connected directly to the chassis ground clip. It is so connected in the diagram. In this case we have the usual grounded antenna system, and the same aerial is used for all wavebands, it being connected to the desired coil through the arm of switch S-1.

If a doublet antenna is used—or an all-wave antenna system similar to the doublet, with two rather than one lead-in wire, the "black coil return lead" is disconnected from the chassis ground and connected instead to one lead of the doublet. This lead is shown in the diagram in dotted lines.

Under normal conditions, a "T" or "L" type antenna is desirable for use on the broadcast band and also the next lowest band, commonly referred to as the "police band." Below the police band a grounded antenna is not efficient unless separate antennas cut to proper length are used for each band. Moreover, it is necessary to provide for the elimination of man-made interference on the shorter wavelengths where such interference is prevalent. The ideal arrangement, therefore, is the use of an "L" or "T" type antenna for the broadcast and upper police bands, and a noise-reducing doublet for the shorter wavebands.

A single antenna may be used with the Stewart-Warner receiver. Tracing the connections of switch S-1 will show that on the two short-wave bands the leads from the doublet antenna are connected directly to the primary winding

(Continued on page 329)

# General Data . . .

## A-K Model 511 Tune-O-Matic Data

A simple diagram of the Tune-O-Matic is shown on this page.

The tuning motor is a shaded-pole induction type. The motor shaft rotates in only one direction, and the required forward and reverse drive for the variable condenser is secured by an ingenious and simple arrangement for tipping the motor, which is pivoted for this purpose. Tipping is accomplished by a solenoid and lever.

The motor drive shaft extends between two rubber-tired wheels, one large, and one small. When the solenoid is not energized, the motor drive shaft rests against the small wheel and the resulting motion drives the variable condenser in the direction from 540 to 1600 kc. When the solenoid is energized, the motor is tipped so that its drive shaft rests against the large wheel, and the variable condenser is then driven in the direction from 1600 to 540 kc.

The current that energizes the solenoid is controlled by a switch (mounted above the top rear of the variable condenser). This switch opens at 1600 kc and closes at 540 kc. The switch is operated by a cam on the shaft of the variable condenser.

### MECHANICAL DETAILS

Eight adjustable discs are mounted on the shaft of the variable condenser, which is extended out in back of the condenser. Each disc has a small insulated sector on the rim. Each disc is held by spring tension to the shaft. Normally, the discs do not move with respect to the shaft, but by holding the front gear of the variable condenser, and using a special wrench which is furnished with Model 511, each disc may be rotated on its shaft so that the insulated sector is in the desired position. Between adjacent discs there is a spacer which is keyed to the shaft. This prevents the movement of any disc other than the one moved with the wrench.

Eight contact fingers are mounted on one side of the discs, each finger contacting with the rim of its corresponding disc.

### ELECTRICAL ACTION

The electrical action is briefly as follows:

Assume that we have one lead of station "G" plugged in the 4:30 jack and the switch is set to automatic.

When the contact blade on the rear of the jack panel comes to the 4:30 jack, the electric circuit through the motor

and solenoid is completed and the solenoid tips the motor shaft against the large rubber-tired wheel. The motor turns the variable condenser from the automatic off position, near 1600 kc, across the dial to the frequency of station "G."

When the motor reaches this point, the insulated sector of disc "G" has come under its contact finger and the circuit, from the finger through the disc to ground, is broken. This cuts the high-impedance relay into the motor circuit and reduces the current through the motor and solenoid to such a low value that the motor stops turning and the solenoid lever comes up, throwing the motor drive shaft against the small rubber-tired wheel which acts as a mechanical brake, bringing the motor to a dead stop on station "G." Simultaneously, the relay has completed the 110-volt circuit to the set power transformer and the set, now tuned to station "G," begins to operate.

Now plug one of the "off" leads into the 4:45 jack. When the contact finger

moves off the 4:30 jack, the circuit through the relay is broken, the set is turned off, and the contact finger, now on the 4:45 jack, completes the circuit through the motor and solenoid, driving the condenser to 540 kc, where a cam on the shaft trips the switch, thus cutting out the solenoid, and the motor tips back against the small rubber-tired wheel, driving the condenser back in the opposite direction to 1600 kc.

Beyond the 1600 kc end of the dial, the cam on the variable condenser shaft again trips the switch, which opens, and the solenoid, being energized, tips the motor shaft against the large wheel, starting the condenser moving back. But at 1600 kc the insulated sector of the "off" disc comes under its contact finger, breaking the circuit and stopping the motor. *In the off position, no current is drawn by the set;* the only current is the small amount required by the electric clock.

Inspection of the diagram will show that the jack panel is shorted out by the switch when the condenser is moving from 540 to 1600 kc. For greatest accuracy all tuning is done while the condenser is moving from 1600 to 540 kc.

## ALL-WAVE SWITCHING

(Continued from page 328)

of the antenna transformer for switch positions 3 and 4. Note, however, that in switch positions 1 and 2 (broadcast and police bands) only one-half of the doublet is used—that part drawn in solid lines. The primary coils connected to positions 1 and 2 are both grounded, so that with switch S-1 in either of these positions, we have a grounded "L" type antenna.

It should also be noted that a band-pass circuit is used in the broadcast band, but in the broadcast band only. The variable condenser in the band-pass filter is a part of the main gang condenser, as indicated by the dotted lines.


### THE AVC CIRCUIT

The avc lead is shown at the bottom of the diagram. If you will trace through this lead, as well as the positions of switch S-2, it will become evident that automatic volume control is placed on the modulator tube for bands 1, 2 and 3 only. Band 4, the shortest waveband, does not have the avc connection, this circuit being grounded. This circuit tunes up to 20 mc and avc action on the modulator tube at these frequencies is not desirable.
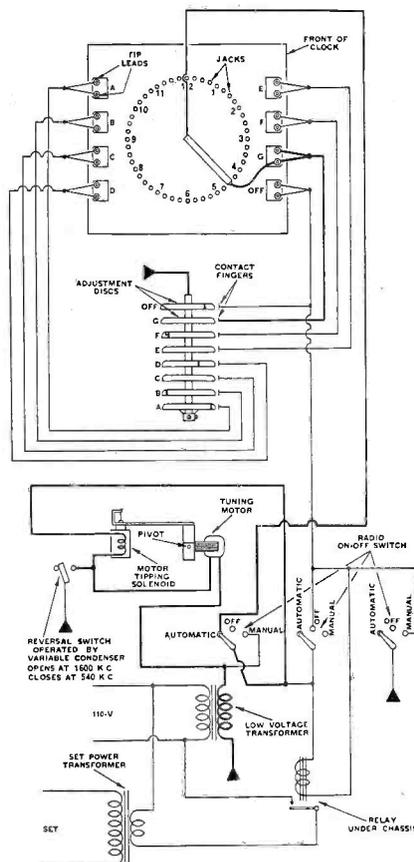
## Philco Radio-Phonograph Model 507

Model 507 uses the same chassis as the Model 118 receiver. It is intended for ac operation only.

The power consumption of the Model 507, with motor running, is 140 watts.



Circuit of the automatic tuning system used in the new A-K 511 Receiver.

**Stromberg-Carlson No. 68**

The r-f section of this receiver is very much the same as the one employed in the No. 69 All-Wave Selector, described on page 292, August, SERVICE.

The data on the arrangement and installation of the special antenna connections at the input of the receiver will be found on page 221 of the June issue of SERVICE. These data apply to both the No. 68 and No. 69 sets.

**CIRCUIT DESCRIPTION**

The No. 69 receiver has four tuning ranges. The switch contacts for each range are lettered in the accompanying diagram, and are as follows: A—520 to 1500 kc; B—1400 to 4200 kc; C—3.7 to 10.5 mc; D—8.9 to 25 mc.

A study of this switching arrangement will show that, no matter which band the switch is set to (with the exception of the broadcast band), the tuned coils in the adjacent band are shorted so that there can be no interaction between circuits.

A 6D6 tube is used in the r-f stage. Initial bias is supplied by the 300-ohm resistor, R-2. The r-f stage feeds a type 6A7 tube which is used only as the first detector or modulator, a separate type 76 tube being employed as the oscillator. The oscillator frequency is fed to grid No. 1 of the 6A7 tube through the blocking and coupling condenser C-19. Initial bias for the 6A7 tube is supplied by the 300-ohm resistor, R-5.

The 370-kc i-f output of the 6A7 tube is fed into a rather complicated circuit,

consisting of the tuned, iron-core inductor, L-19; the i-f filter L-20, C-23, which prevents the i-f signal from getting back into the r-f, modulator and oscillator circuits; and the iron-core i-f transformer L-29, L-30. It is seen that there are three tuned circuits between the modulator tube and the 6D6 i-f tube.

It should be noted that the plate circuit of the modulator tube also contains the volume-control potentiometer R-8. By means of this potentiometer the cathode voltage of the 6D6 i-f tube is varied over comparatively wide limits, thus varying the grid bias and controlling the gain of this stage.

The i-f tube feeds an air-core i-f transformer which is in turn coupled to one diode plate of the type 85 second detector and a-f tube. It should be noted that the detector diode plate is, practically, not biased, being connected directly to the cathode. Consequently, there is no delayed detector action. The control grid of the triode section of this tube, which is employed as an a-f voltage amplifier, is biased by the drop in voltage in the cathode resistor R-17. The triode is therefore self-biased.

**THE AVC CIRCUIT**

A 6B7 tube is used in the avc circuit. The control grid of the pentode section is coupled to the control grid of the 6D6 i-f tube through the coupling condenser C-58. The amplified i-f signal in the plate circuit of the pentode is fed to the diode plate through the avc i-f transformer L-41, L-42. The avc volt-

age is developed across resistors R-26 and R-27. Full avc voltage is placed on the r-f and modulator tubes through the filter network containing the resistors R-24 and R-25. The avc voltage for the 6D6 i-f tube is taken from the junction of resistors R-26 and R-27 and reaches the grid of the i-f tube through the filter resistor R-28.


The pentode control grid of the 6B7 tube is biased by the voltage drop across resistor R-30. The avc diode plate, which is grounded through the load resistors R-26 and R-27, is biased by the combined drop in voltage across resistors R-30 and R-31, which are connected in series. This bias on the diode plate provides delayed avc action.

**THE A-F AMPLIFIER**

Note that both the bass and treble controls are in the plate circuit of the 85 triode. The variable resistor R-9, just below the volume control in the diagram, is the treble control. This connects to the fixed condenser C-51 and functions the same as the usual type tone control. The bass control is composed of the resistor R-20, directly in the triode plate circuit, and the short-circuiting switch. Shorting the resistor attenuates the highs.

The triode of the 85 is transformer coupled to a type 42 tube employed as a driver. The driver is in turn transformer coupled to a pair of 42 tubes in push-pull. These tubes are connected as triodes and are operated Class A-B.

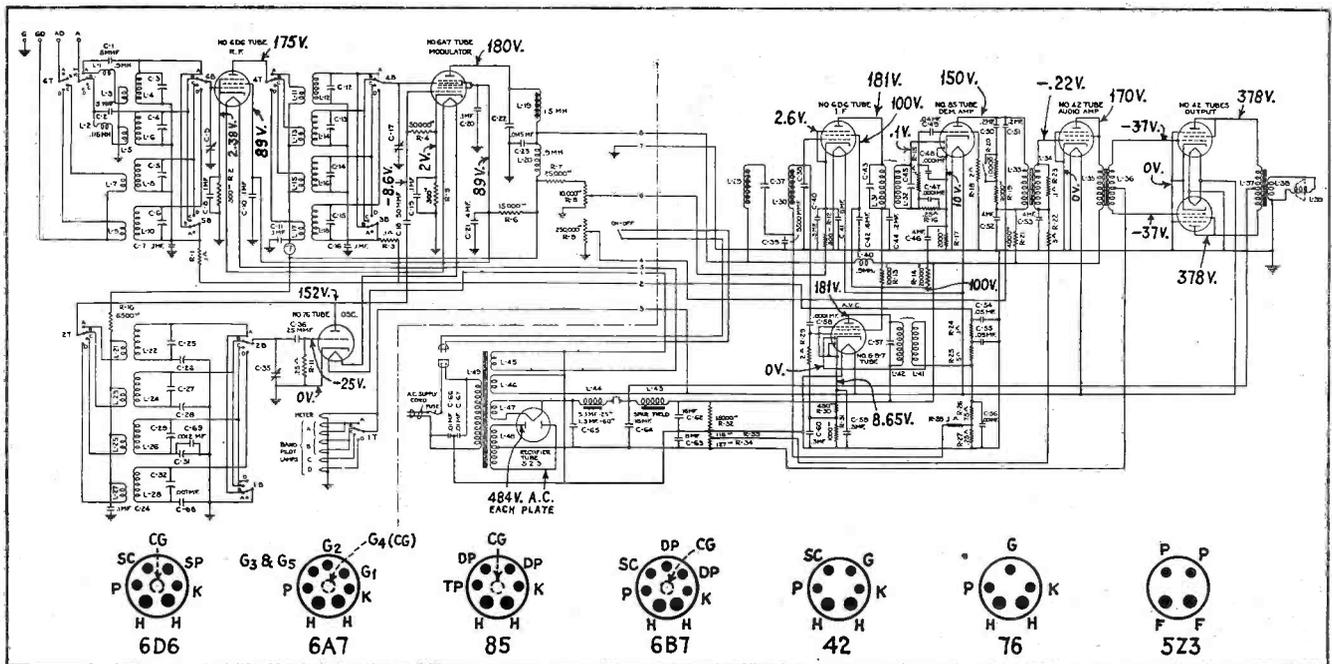It is of interest to note that both the driver tube and the push-pull tubes em-



Circuit of Stromberg-Carlson No. 68 All-Wave Receiver.

# GENERAL DATA—continued

ploy fixed bias, obtained from the voltage drop in resistors R-33 and R-34 in the negative leg of the power-supply circuit.

### VOLTAGE READINGS

Voltage values are given in the diagram. Readings should be taken with the set tuned to 1000 kc and volume control full on. The voltages given are based on a line voltage of 119 and allowances should be made for differences when the line voltage is higher or lower.

### Atwater-Kent 217-D, and 667-D


These are 110-volt dc receivers, using the same chassis. The heaters of all tubes are, of course, connected in series. (See Fig. 1.) Included in this circuit is the 6.3-volt dial lamp which shunts the 19-ohm resistor R-13. The voltage drop across this resistor is 6 volts, sufficient for the lamp.

### CIRCUIT DESCRIPTION

The receiver is a dual-wave job, covering the range from 540 to 3200 kc. The r-f stage, employing a type 78 tube, does not use an r-f transformer in the output circuit. Instead a high-gain tuned impedance is employed, the B voltage being fed to the plate of the r-f tube through an r-f choke. This is a typical parallel-feed circuit.

The type 37 oscillator tube is coupled to the first detector through a small coupling coil in the cathode circuit of the first detector. The 264-kc output

Fig. 2. Chassis layout for the A-K giving locations of trimmer condensers, etc.

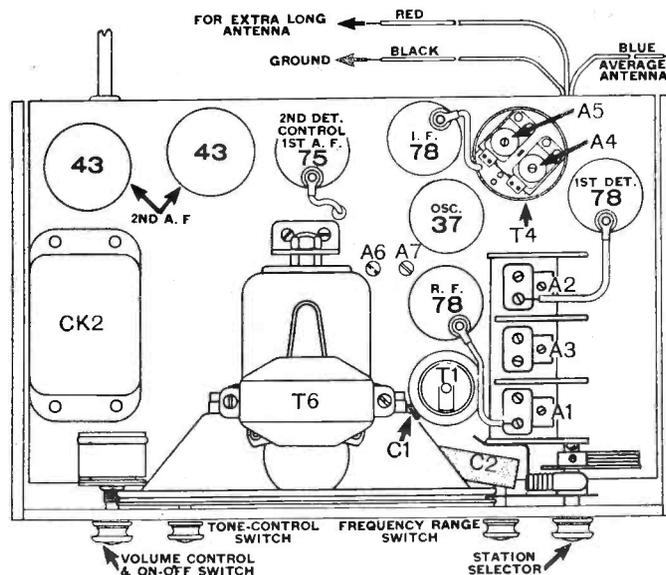

of the first detector is fed to the 78 i-f tube through a double-tuned i-f transformer. The i-f tube is transformer coupled to the second detector. The diode plates of this tube are used separately, the lower one for detection and the upper one for avc. The automatic bias control voltage is placed on the r-f, first detector and i-f tubes.

The triode of the 75 tube is resistance coupled to a pair of 43 pentodes connected in parallel to increase the power output at the low B voltage available.

### BIAS VOLTAGES

Note the manner in which the bias voltages are obtained. For example, the grids of the power pentodes are biased by the positive voltage placed on the cathodes. The common cathode connection is seen to terminate at one side of the dial lamp, this point being approximately 13 volts above the ground or return circuit. The cathode of the 75 tube is connected to the point between the resistors R-15 and R-16. This point is 1 volt above ground. The grid of the 75 triode is therefore at -1 volt in

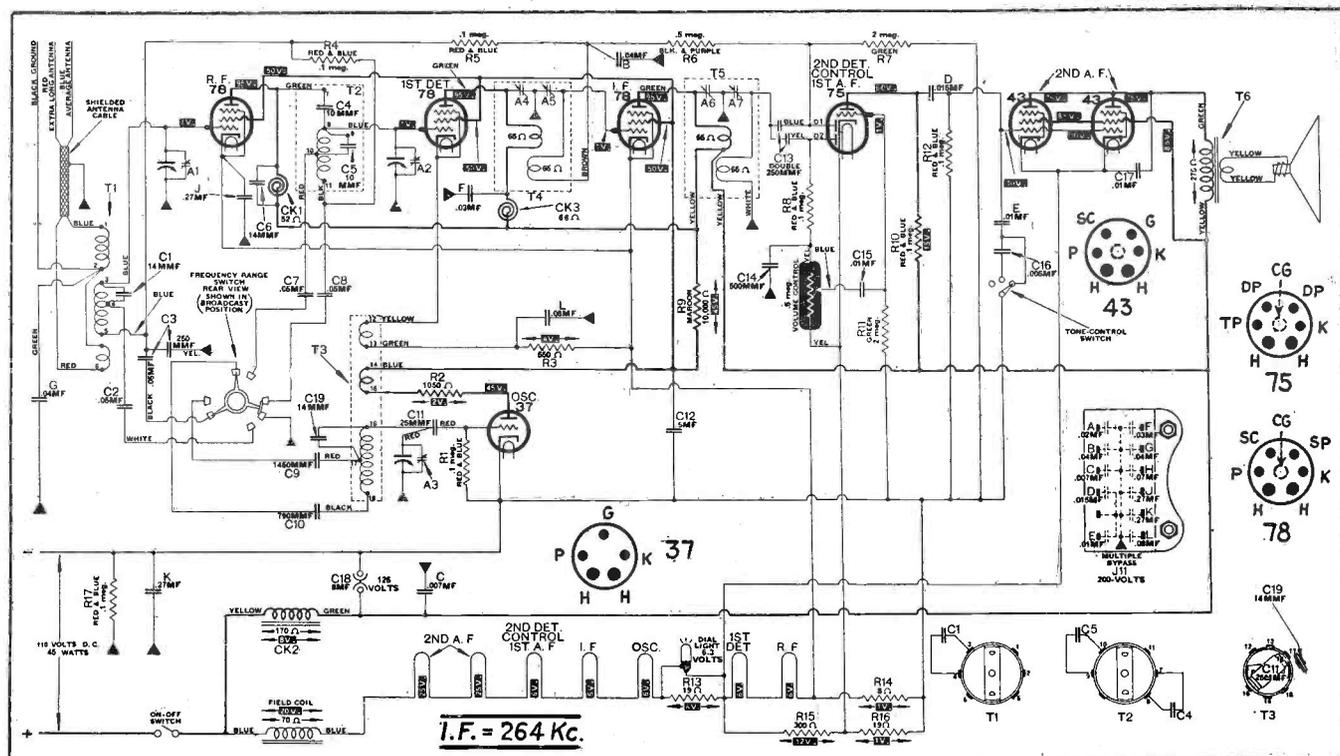


Fig. 1. Circuit of the A-K 217-D Receiver.

## GENERAL DATA—continued

respect to the cathode. The cathodes of the r-f, first detector and i-f tubes have a common connection which terminates at the left side of resistor R-14. This places an initial negative bias of 1 volt on the grids of these tubes.

The tone control is in the grid circuit of the power tubes. The speaker field is used as a filter choke and is in series with the tube heaters.

Fig. 2 shows the location of the tubes, trimmer condensers, etc., on the chassis. This is actually the chassis for the 217-D receiver. In Models 427-D and 667-D, the speaker is mounted in the cabinet, under the chassis. Otherwise there is no difference in the chassis.

### VOLTAGE READINGS

The voltages given in the diagram of Fig. 1 are read from the cathode of each tube, using the 250-volt scale of a 1000-ohms-per-volt meter. Readings should be made with the set in operation, no antenna, with the dial turned to a quiet point, and frequency range switch in the broadcast position.

### Silvertone Model 1729

In this 7-tube super a 78 r-f tube is used in the pre-selector stage which is coupled to the 6A7 oscillator-modulator. The 175-kc i-f signal created in the 6A7 plate circuit is amplified by the 78 i-f tube and then fed to the 37 avc-diode detector. The a-f output of this

tube is amplified by the 37 a-f tube and then fed to the 41 output pentode. A type 80 rectifier is used. The speaker field is connected in the negative leg of the power supply and serves as a filter choke. The voltage drop across resistor R-12 in series with the speaker field supplies the grid bias for the second a-f tube and the power tube.

### MODULATOR-OSCILLATOR CIRCUIT

Just in case you have forgotten these arrangements, coil L-2 feeds the broadcast signal to grid No. 4, the control grid of the 6A7. Coil L-3 (1-2) acts as the grid coil and coil L-3 (3-4) as the plate coil of a tickler feedback type of oscillator. Grids No. 2 and No. 3 of the 6A7 are the grid and plate, respectively. Since the electron stream is affected both by grid No. 4 and grids No. 2 and No. 3, a 175-kc signal is created in the plate circuit of the 6A7.

### AVC-DETECTOR

A 37 tube is used as a diode, with plate and cathode tied together. The grid then acts as the plate. The i-f signal is impressed between this plate and the cathode of the 37, in series with R-7 and the 725,000 ohms of the volume control. Diode current flows, creating a voltage drop across R-7 and the volume control with the grounded end of the control positive with respect to its other end. That portion of the voltage drop existing between the grounded end

of the control and the tap, is impressed on the control grids of the 78 and 6A7 tubes.

The audio component of the voltage across the volume control is picked off by the movable arm of the control and coupled to the grid of the 37 a-f tube.

### VOLTAGES AND ADJUSTMENTS

All voltages are given on the diagram. Read from elements to chassis. Take readings with antenna disconnected and no signal received.

When peaking the i-f transformers, use a low enough output from the test oscillator to render the avc action inoperative.

### Philco Model 38 Change

Starting July 1st, the ballast tube shunt resistor in the Model 38 (Code 122) has a value of 20 ohms, instead of 30 ohms as previously. This provides a slight increase in filament voltage which has been found desirable.

### Philco Model 18 Change

Starting with run No. 4, resistor (22) on diagram of Model 18 (Code 124) will be 1000 ohms instead of 2500 ohms.

There is a slight change in the antenna and oscillator transformers, the new ones being identified by a red paint mark on the bracket. No change in part number.

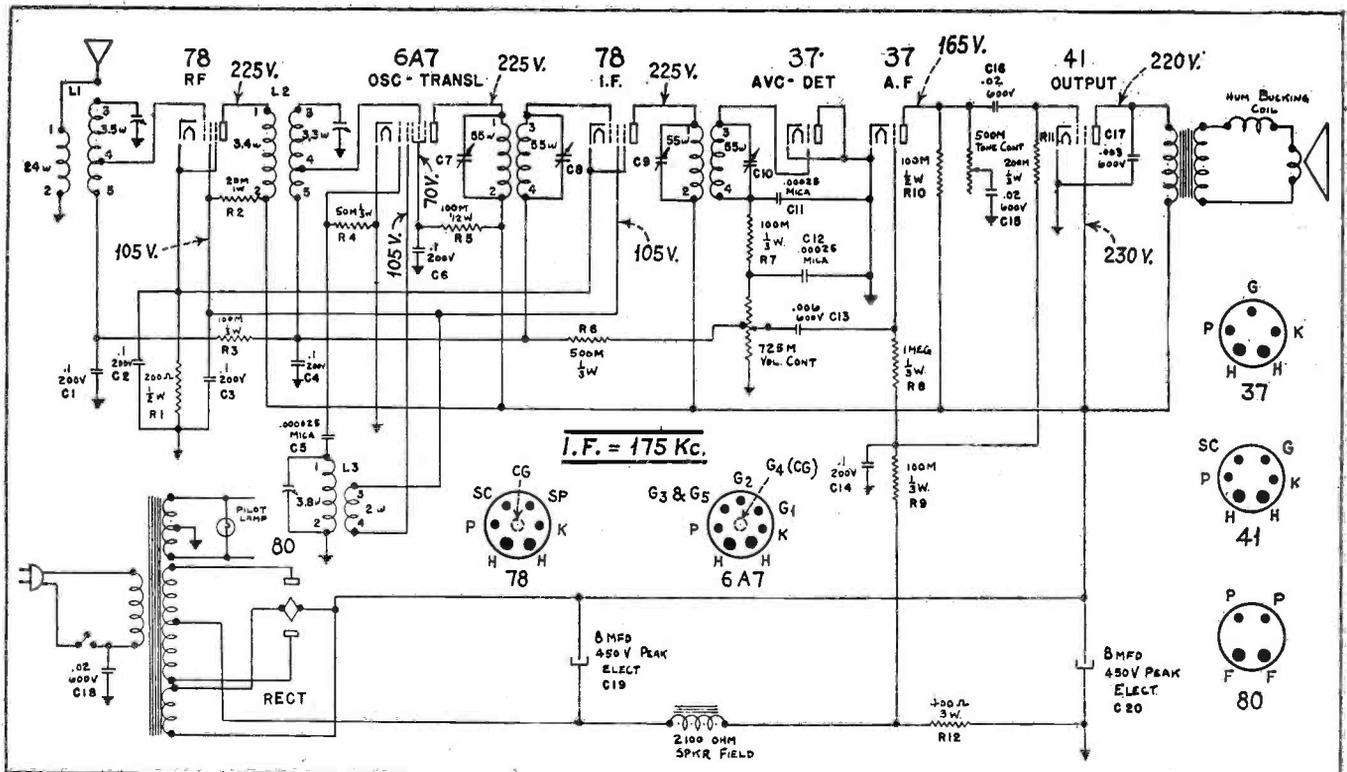


Diagram of Silvertone 1729.



Now adjust the short-wave antenna trimmer (the one on the free end of the antenna coil) until the signal again comes to maximum. When these conditions are fulfilled the receiver is aligned on the short-wave range. Therefore remove the 15,000-kc signal from the antenna.

**BROADCAST ALIGNMENT**

Now rotate the range switch to the right (broadcast position) and set the pointer of the dial to 1,425. Introduce a 1,425-kc signal from test oscillator into the antenna and adjust the oscillator trimmer (the trimmer on the oscillator coil, furthest from the edge of the chassis) for maximum response. Attenuate this signal.

Next adjust the broadcast antenna trimmer for maximum response (the trimmer on the end of the antenna coil closest to the chassis). Then remove the 1,425-kc signal from the antenna.

Now introduce a 600 kc signal into the antenna and rock the gang condenser back and forth around the 600-kc dial reading, and at the same time adjust the series padding condenser for maximum output. Leave the series padder set to the point of maximum sensitivity. (The series padder is on the side of the oscillator coil can.)

Broadcast alignment is now complete.

**ALIGNMENT NOTES**

When aligning it is best to put a strong signal into the circuit being aligned and as it is brought into alignment, gradually attenuate the signal until, when the final adjustment is made it is just strong enough to be read on the meter. Using a weak signal to make the final adjustment insures accurate settings of the trimmers.

The locations of the coils are as follows: Antenna coil; without shield, under chassis. Oscillator coil; in round can fastened to front of chassis, underneath. Last i-f coil; fastened to back of chassis, in small can, underneath. First i-f coil; on top of chassis with grid lead feeding into 58 tube. Second i-f coil; on top of chassis with grid lead feeding into 2B7 tube.

The voltages given in the diagram are based on a line voltage of 115 volts, and are measured between elements and ground.

**RCA Victor Models 127, 327 Warning**


These are 6-tube, 220-volt dc receivers. It is extremely important to use the utmost caution when operating the receiver outside the cabinet. Also

a knob must always be placed on the shaft of the main tuning condenser, as under certain conditions the full line voltage is obtained between this point and ground.

**RCA-1C6**

The 1C6 is a 2-volt filament type of tube designed to function as both mixer and oscillator in supers. This tube, which is similar in function to the 1A6, though not directly interchangeable with it, requires twice the filament current of the latter, but offers the feature of an extended operating range at the shorter wavelengths. It is therefore particularly suitable for use in battery-operated all-wave supers.

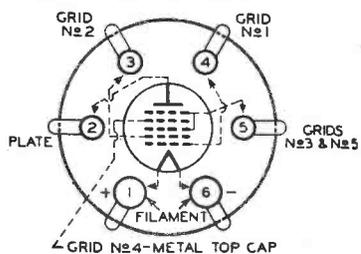**Tube Symbol and Bottom View of Socket Connections**



The following are the operating voltages of the 1C6 tube:

Filament voltage .....	2
Filament current (ma).....	120
Plate voltage .....	180
Grids 3 and 5 voltage.....	67.5
Anode-grid voltage* .....	180
Control-grid voltage .....	-3

\*Applied through 20,000-ohm dropping resistor.

**Philco Model 29**

Starting with Run No. 8, the cathode resistor (20 in wiring diagram) will be changed from 500 ohms to 400 ohms. This will prevent variation in performance of sets due to considerable variation in 6A7 tubes.

Condenser (54) in diagram is changed from .09 mfd to .05 mfd. This improves the fixed bass compensation used in this model.

**Westinghouse Models and I-F Peaks**

The i-f peaks of the new Westinghouse receivers are as follows:

Model	I-F Peak
WR-21 .....	456
WR-22 .....	456
WR-23 .....	456
WR-24 .....	456
WR-25 .....	172.5

The Model WR-25 is a 6-tube super designed for use as an auto or motor-boat receiver.

**Wurlitzer SU-5**

The Model SU-5 is a dual-wave super covering the broadcast band of 550 to 1500 kc and a short-wave band of from 1580 to 3700 kc. Changing the band in the antenna circuit is accomplished by throwing coils and capacities in parallel, and in the oscillator circuit by shorting one coil and placing an additional capacity in shunt with a second coil.

The 6A7 tube functions as modulator and oscillator. The 456-kc output is fed to the 78 i-f tube which is regenerated by the feedback coil in its cathode circuit. This increases the sensitivity and selectivity of the i-f stage. The output of the i-f stage is impressed on the diodes of the 75 tube. The diodes rectify the i-f signal and the dc voltage developed in the load circuit is used as a control bias for the first detector and i-f tubes. The a-f component of the signal is picked off the volume control potentiometer and fed to the control grid of the 75 triode. This triode is resistance coupled to the 43 pentode, the output circuit of which contains the variable tone control and a jack for external speaker. When the remote speaker is in use, the set speaker is inoperative.

All the tubes in the receiver are self-biased by resistors in the respective cathode circuits. In the case of the modulator and i-f tubes, the cathode resistors provide an initial bias only.

**CIRCUIT ADJUSTMENTS**

In aligning, connect the line cord lead marked with a red dot to the grounded side of the line. Connect the output meter from screen to plate of the 43 power pentode. Advance the tone and volume controls to their maximum positions (clockwise).

In all ganging operations use the weakest signal that will give a satisfactory indication on the output meter. Do this by reducing the input, not by retarding the volume control.

The i-f trimmer adjustments are carefully made and should not be disturbed unless the i-f amplifier is actually at fault. In that event, attach the antenna lead to a local oscillator tuned to 456 kc, keeping the signal input as low as possible. Then adjust the two i-f trimmers to give maximum indication in the output meter.

The first i-f trimmer is on the rear of the chassis directly under the first i-f transformer, between the 6A7 and 78 tubes. The slot adjustment is the primary trimmer. The hex nut adjustment is the secondary trimmer.

The second i-f trimmer is located on

# GENERAL DATA—continued

the top of the chassis pan, left end, near the volume control. The adjustments are the same as the first i-f trimmer.

*Under no circumstances shall the single trimmer at the extreme right rear of the chassis (usually marked with red) be adjusted.*

### TO CALIBRATE B. C. BAND

Turn the band switch to the broadcast position (clockwise). Set the dial pointer to the position where a station (or oscillator) of known frequency, about 1400 kc, should come in.

Then adjust the oscillator trimmer (screw adjustment, top of gang condenser, front-dial-end) until desired signal is heard. The calibration of the rest of the dial will then fall within reasonable limits with no further adjustment.

### ALIGNING B. C. BAND

Set dial to approximately 1400 kc, connect antenna lead to local oscillator

tuned to set, and check settings of volume and tone controls.

Then adjust r-f trimmer (screw adjustment, top of gang condenser, rear end) until output meter indicates maximum output. *Keep signal input low!* The alignment over the balance of the tuning range will then fall within reasonable limits without further adjustment.

### TO CALIBRATE S. W. BAND

Turn the band switch to the short-wave position (counter-clockwise). Set the dial pointer to a position where a station (or oscillator) of known frequency, about 3700 kc, should come in. Then adjust the short-wave oscillator trimmer (screw adjustment, under chassis pan, adjustable through hole in chassis pan top front, right corner near gang condenser) until the desired signal is heard. Calibration for rest of dial should then be okay.

### ALIGNING S. W. BAND

Set dial to approximately 3600 kc

(3.6 mc), connect antenna lead to local oscillator tuned to set and check settings of tone and volume controls.

Adjust short-wave r-f trimmer (screw adjustment, rear of antenna coil mounting bracket, between 6A7 and 78 tubes) until the output meter indicates maximum output. *Keep the signal input low!* The alignment over the balance of the tuning range will fall within reasonable limits without further adjustment.

### Philco Model 34 Correction

On page 290 of the August issue of SERVICE there is given a description of the second detector circuit of the Philco Model 34 battery-operated receiver.

It was stated in this article that the diode second detector also provided delayed avc for the r-f and i-f tubes. A close check of the circuit will indicate that no such action takes place, since the "alleged" control circuit does not exist.

We hasten to make apologies for a "vacation-time boner."

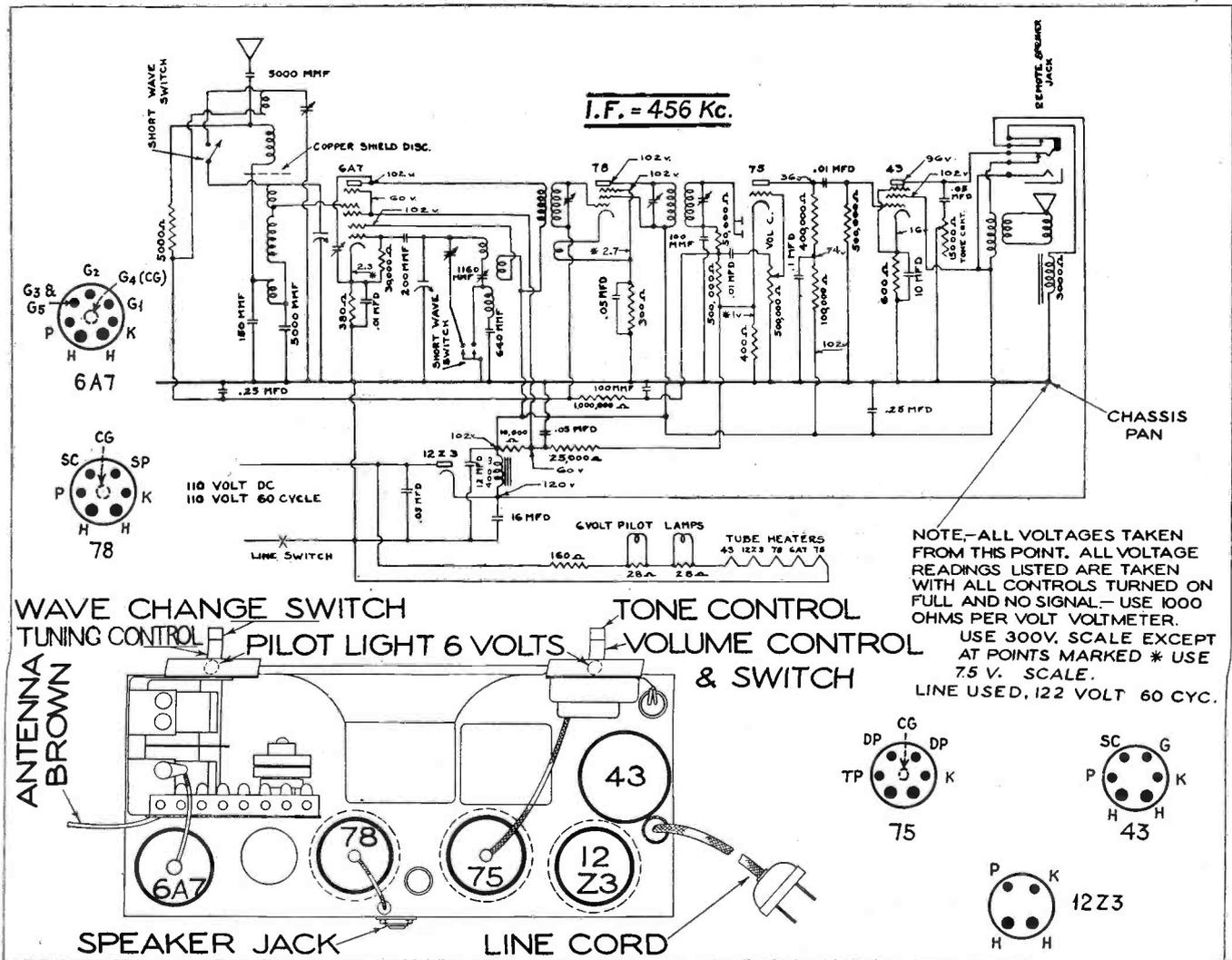


Diagram and data for Wurlitzer SU-5, with image-suppressor circuit.

# Auto-Radio . . .

## STEWART-WARNER R-117 CHASSIS

This chassis is used in the Model 1171 auto-radio receiver. See note regarding the reduction of dial illumination on page 297 of the August issue of SERVICE.

### CIRCUIT DESCRIPTION

The R-117 circuit is shown on the opposite page. There is a stage of r-f using a self-biased 78 tube. The bias may be decreased by shorting resistor 2 by closing switch 12. This is the sensitivity control switch.

The r-f tube feeds a 6A7 modulator-oscillator. The 177.5-kc output of the modulator feeds a 78 i-f tube, also self-biased. The i-f stage feeds the diodes of the type 75 second detector-avc and a-f tube. The avc voltage is developed in the diode load circuit containing the resistor 11, across which the avc voltage is developed. Full avc voltage is impressed on the r-f, modulator and i-f tubes through the resistor 5.

The control grid of the 75 triode is biased by the voltage drop in the cathode resistor 2. The triode is resistance coupled to the type 42 output tube. The grid bias for this tube is obtained from the voltage drop across the filter choke 33, in the negative leg of the power supply.

The tone control (condenser 14 and variable resistor 46) is in the plate circuit of the power tube. This is shown in the separate diagram of the dynamic speaker connections.

### PROTECTIVE RESISTOR

The filter system and the rectifier tube are protected against breakdown from the high peak voltages during the warming-up period by means of a special Globar resistor (No. 21 in the diagram) connected across the high-voltage secondary of the power transformer. This resistor has the unique property of dropping rapidly in resistance as the voltage across it rises, so that when the set is first turned on and secondary voltage is high, the resistor acts as a load on the power transformer and keeps the voltage below the danger point until the tubes warm up and take their normal current. When the B voltage drops to normal the protective resistor increases its resistance to about 500,000 ohms, so that it draws no appreciable current while the set is in use.

Because of its unique voltage characteristics, the Globar resistor cannot

be tested with an ordinary ohmmeter, since it will show a resistance of several megohms.

### I-F ALIGNMENT

The i-f trimmers are located on the top of the i-f transformers which may be reached by removing the front cover. The modulated oscillator should be set at exactly 177.5 kc and connected from the 6A7 control grid to ground. Adjust the oscillator output to give about half-scale reading of the output meter. Adjust all three i-f trimmers to give maximum reading.

The first i-f transformer has a double trimmer consisting of a slotted screw for one trimmer and a hex nut around it for the other. In adjusting the second i-f transformer single trimmer it is desirable to use an insulated screwdriver or one having only a small metal tip. After the i-f trimmers have been aligned once, go back and repeat the procedure, since any adjustment of one will affect the others to some extent.

### R-F ALIGNMENT

The gang condenser trimmers can be reached by removing the back cover. Connect a .00025-mfd mica condenser in series with the output of the test oscillator and the aerial lead of the receiver. Adjust the receiver to approximately 1400 kc and carefully tune the test oscillator to give maximum receiver output. Adjust the two trimmers nearest the shaft end of the gang condenser to give maximum output meter reading. The trimmer on the other condenser section (oscillator section) should not be touched unless the set does not calibrate properly.

The low-frequency oscillator padding trimmer located on the side of the chassis does not require adjustment in most cases.

### VOLTAGE READINGS

All dc voltages are read from socket terminal to the chassis, using a high-resistance voltmeter of 1000 ohms per volt. Readings will depend upon the voltage range of the meter. The values given in the diagram are based on a storage battery voltage of 6.0.

The oscillator grid voltage will vary from zero at 1400 kc to -5.0 volts at 600 kc. The oscillator anode voltage may vary from 118 volts at 1400 kc to 128 volts at 600 kc.

Actual bias voltage on the grid of the 42 tube is -15.5, which must be measured from ground to the filter choke terminal. Due to the high-resistance grid leak, the voltmeter will show only about -1 volt at the grid terminal.

### Arvin Model 16

The new Arvin Model 16 auto-radio receiver employs an intermediate frequency of 175 kc.

In connection with this receiver, it is suggested by the manufacturer that in districts where signal strength is abnormally low, a slight increase in sensitivity may be obtained by removing the inter-channel noise-suppression feature.

To those who have diagrams of this receiver, this may be accomplished by disconnecting resistor R-7 at point A and re-connecting it at point B. To those who do not have the diagram, it may be explained that resistor R-7 connects from the low end of the secondary of the detector i-f transformer, to ground. Thus, a slight bias is placed on the diode plates of the second detector. If this resistor is connected directly to the cathode of the second detector tube—the point B referred to—the diode plates will no longer be biased, and the sensitivity will therefore be slightly increased.

### 1933 Oldsmobile Installations

It is difficult to eliminate noise in these installations. If, after all suppressors and filters are put in and ignition noise still persists, run a shielded lead-in down the left front door post to the floor and then under mat to the receiver. Also be sure to shield the high-tension wire and battery supply wires. Keep control cables away from ignition coil on instrument panel—also shield coil with a shield can. A dome light filter may also be necessary.


### Majestic Twin Six

Some Majestic Model 66 receivers cut in and out, or stop altogether at times. In such cases replace the G-6A7-S tube, even though the old one may test okay.





The i-f peak of this receiver is 175 kc.
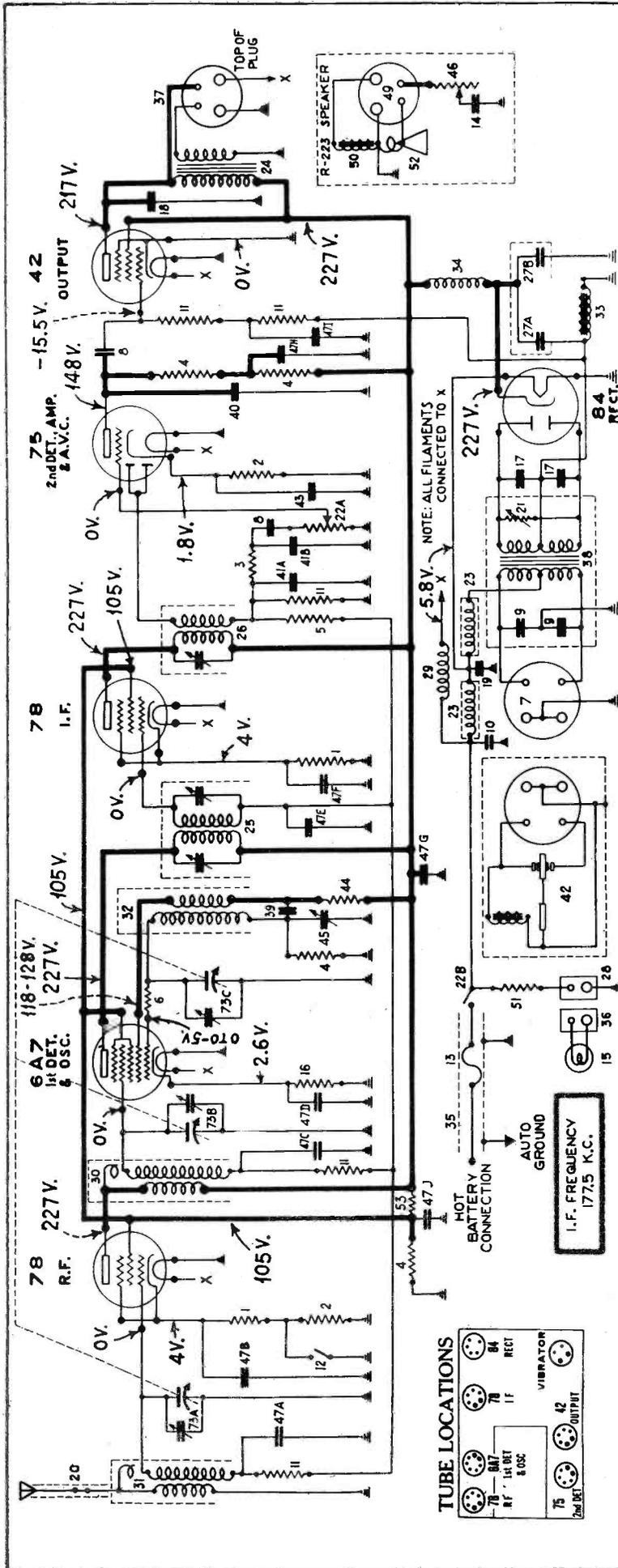
### Crosley Syncrotube

The new Crosley Roamio, Model 4A1 auto-radio receiver employs a new double-purpose tube, type 6SA4, which performs the functions of both rectifier and vibrator. It is called the Syncrotube.



DIAG. PART NO.	DESCRIPTION	DIAG. PART NO.	DESCRIPTION
1	500 Ohm 1/4 watt carbon resistor	49	Filament R.F. Choke
2	6000 ohm 1/4 watt carbon resistor	50	R.F. (B) coil and shield
3	10000 ohm 1/4 watt carbon resistor	51	Antenna (A) coil and shield
4	50000 ohm 1/4 watt carbon resistor	52	Miller (C) coil and shield
5	1.1 megohm 1/4 watt carbon resistor	53	Filament R.F. chokes
6	1000 ohm 1/4 watt carbon resistor	54	Supply lead and fuse housing
7	Vibrator socket (Standard type)	55	Pilot light cable and plug
8	.05 mfd 100 volt paper condenser	56	Speaker cable and plug
9	.05 mfd 100 volt paper condenser	57	Power transformer
10	.05 mfd 100 volt paper condenser	58	.00011 mfd. molded mica condenser
11	250,000 ohm 1/4 watt carbon resistor	59	.00011 mfd. molded mica condenser
12	15 square fuse	60	Dual .0005 mfd. molded mica condenser
13	6 volt pilot light bulb	61	Plug-in vibrator
14	83217	62	12 mfd 25 V. Dry Electrolytic Condenser
15	83217	63	40,000 ohm 1/4 watt carbon resistor
16	83293	64	Oscillator padding trimmer
17	83293	65	36000 ohm tone control variable resistor
18	83704	66	.05 mfd 100 volt paper condenser
19	83704	67	.05 mfd 100 volt paper condenser
20	83725	68	.05 mfd 100 volt paper condenser
21	83725	69	.05 mfd 100 volt paper condenser
22	83728	70	.05 mfd 100 volt paper condenser
23	83730	71	.05 mfd 100 volt paper condenser
24	83731	72	.1 mfd 400 volt paper condenser
25	83732	73	.1 mfd 400 volt paper condenser
26	83733	74	.25 mfd 100 volt paper condenser
27	83734	75	.25 mfd 100 volt paper condenser
28	83735	76	Three gang variable condenser with mtg. plate and shaft coupling.
		77	3 prong pilot light socket

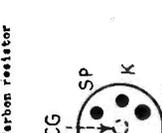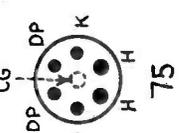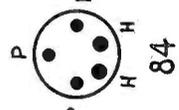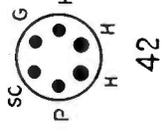


# Public Address . .

## IMPEDANCE BRIDGE FOR DESIGN AND TESTING WORK

The accompanying diagram shows an impedance bridge that has been found very convenient in radio service and power amplifier design. It may be used to measure input and output impedances of amplifiers, pickup units, microphones, etc., in order to insure correct matching of impedance. It is also very convenient for obtaining the correct impedance match between speaker and output tubes when replacing output transformers.
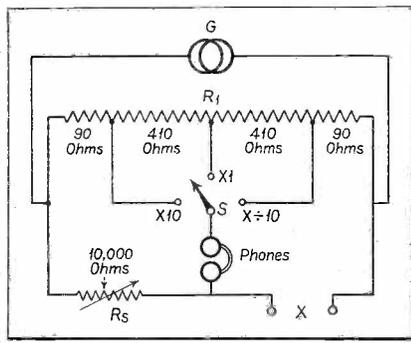
### CONSTRUCTION OF BRIDGE

The construction of the unit is fairly simple. The source of alternating cur-



Circuit for the impedance bridge described in the accompanying article.

rent,  $G$ , may be a buzzer or an audio oscillator. The resistor  $R_1$  should be wire wound. One of the wire-wound resistors with adjustable taps, as used for bleeder resistors, will be satisfactory. The taps may be set at the correct values by using a good ohmmeter or preferably by applying a known voltage across the resistor and measuring the current drawn by the resistor. Knowing the voltage and current, the resistance may be calculated from Ohm's law:  $R = E/I$ . The standard resistance  $R_s$  is a wire-wound variable resistance of 10,000 ohms. This resistance must be calibrated. This calibration may also be accomplished by means of Ohm's law. The switch,  $S$ , is a single-pole triple-throw switch of the rotary type.

### USING THE BRIDGE

In measuring an unknown impedance,  $X$ , the standard resistance and switch  $S$  should be adjusted for minimum sound in the phones. When minimum sound is obtained, the value of the unknown,

$X$ , is equal to the setting of  $R_s$  multiplied by the setting of the switch  $S$ . That is, when  $S$  is set at  $X10$ , the value of  $X$  is ten times the setting of  $R_s$ . When  $S$  is at  $X1$  the reading of  $R_s$  is equal to  $X$ . Similarly, when  $S$  is set at  $X \div 10$ ,  $X$  is equal to one-tenth of the setting of  $R_s$ .

The inductance of the resistors is not sufficient to cause any appreciable error. It will not be possible to completely balance the sound out of the phones because of the reactive components of  $X$ . However, in work of this sort the reactive component of the impedance is usually of little importance.

To measure the input or output impedance of amplifiers, microphones, etc., the input (or output) is connected across the terminals  $X$ . In the case of amplifiers it is desirable to have the operating voltages applied to the tubes during the measurement. However, in measuring the output impedance of an amplifier no signal should be applied to the amplifier.

### IMPEDANCE RATIOS

The impedance ratio of a transformer may be determined by connecting a known resistance across one winding of the transformer and measuring the impedance across the other winding with the bridge. The impedance ratio will be the ratio of the known resistance to the reading of the bridge. The voltage ratio is equal to the square root of the impedance ratio.

### DETERMINING LOAD RESISTANCE

The bridge has been found particularly advantageous in replacing output

transformers when using replacement transformers with tapped secondaries. It is necessary to have the plate load on the output tubes of an amplifier of the correct value in order to get the greatest output with the least amount of distortion. The value of the load resistance to be applied to the output tube may be determined from the tube manufacturer's specification for the given tube at the given operating voltages. In the case of push-pull, the impedance from plate to plate should be twice the value required for one tube. In rating tubes for Class B push-pull, the tube manufacturer gives the load resistance from plate to plate. After determining the load resistance (i. e., the impedance required across the primary of the output transformer), the primary of the transformer should be connected across the bridge terminals. The voice coil of the speaker is then connected across the various taps of the secondary until the required impedance is obtained across the primary as measured by the bridge.

ELMER SCHULZ,  
Lockhart, Texas.

### G. E. M-49 Phonograph Motor Data


The synchronous phonograph motor used in this receiver is shown in detail in the accompanying sketch. The two stator coils are connected in series and the motor is started by giving it a clockwise spin with the hand. If it is found to be difficult of starting, or if it runs at a subsynchronous speed such as at 70 rpm, such action may result from one of the following causes:

#### DIFFICULT TO START

This may be due to the stator failing to rotate on the outer bearing. This can be caused by the spaghetti sleeve being jammed in the slot, or sticking to the resilient bumper. The outer bearing not being properly lubricated may also cause this condition. It is important that the ball bearings be at the bottom of the main bearing assembly.
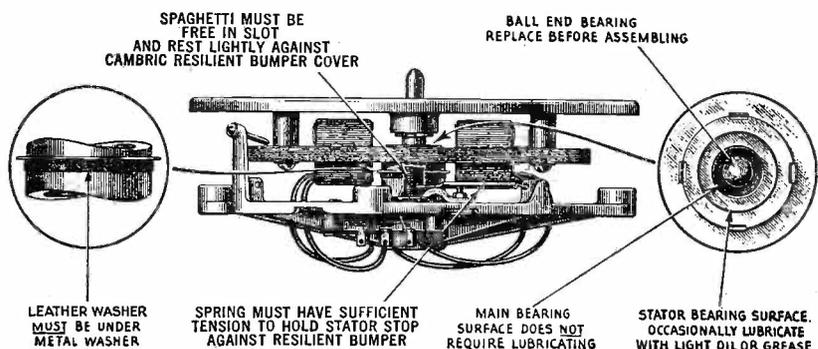
#### SLOW SPEED

If the turntable is jarred or slowed down, the motor may run at a sub-  
(Continued on page 340)



Details of the synchronous phonograph motor used in the General Electric M-49 Receiver.

# LATEST TECHNICAL INFORMATION

## YOURS FOR 10¢

The Hygrade Sylvania engineers have given you helpful books that cover general service data on both home and automobile radio receivers. Now available is a convenient 104-page technical manual containing the essential information every user of tubes must have to secure the optimum performance from any device employing vacuum tubes.

Complete data on over 90 types of receiving tubes is given along with base symbols, recommended operating conditions, circuit applications, amplifier classifications, receiver circuit diagrams, etc.—over 150 cuts and diagrams. Authoritative beyond question, because it was compiled after months of painstaking research by the famous Sylvania staff of tube and circuit engineers.

You need this new technical manual—it's as necessary as your voltmeter in service work. Just fill in the coupon below, attach 10 cents in stamps and mail today.

### YOURS for 10¢ in STAMPS



# Sylvania

REGISTERED U. S. PAT. OFF.

## THE SET-TESTED RADIO TUBE

Makers of  
Sylvania Tubes  
Hygrade Lamps  
Electronic Products



Factories  
Emporium, Pa.  
St. Mary's, Pa.  
Salem, Mass.  
Clifton, N. J. © 1934, H. S. C.

HYGRADE SYLVANIA CORPORATION  
Emporium, Pennsylvania (C-16)

Please send me the new Sylvania Technical Manual.  
I enclose 10¢ in stamps.

Name.....

Address.....

City..... State.....

synchronous speed, such as 70 rpm. This is remedied by merely lifting the tone arm from the turntable, thereby removing the load. The turntable speed will then immediately increase to normal.

VIBRATION AND HUM

A small amount of hum when starting, decreasing to a negligible amount while running, is normal. If excessive vibration occurs either at starting or running, it may be due to one of the following:

- (1) Insufficient lubrication in outer bearing or any other failure that will cause the stator to bind.
- (2) The metal washer should be above the leather washer at the bottom of the main bearing.
- (3) Motor not properly supported from motor board. Unless the motor is properly supported from the motor board, normal vibration will be excessive.

REMOVING ROTOR FROM STATOR

The rotor, which includes the turntable, may be removed by loosening the screw shown in the sketch until it clears the rotor, and then lifting the turntable. Be careful not to lose the ball end-bearing when this is removed. After replacing the rotor, tighten the restraining screw securely to eliminate the possibility of rattle in operation.

The motor consumes 4 watts. It should never be turned on when the rotor is removed, as in this condition excessive current will be drawn with consequent increase in temperature.

The above value of power consumption is average for a 60-cycle motor at 125 volts. At lower voltages the power consumption will be less.

RCA-VICTOR MODEL R-92 RECORDER

The Model R-92 is a special recording unit designed principally for making home recording records in dealers' stores. The unit consists of a special recording head and suspension arm assembly, a three-stage amplifier and a suitable power supply. Of special interest is the inclusion of two level-indicating lamps which permit the proper recording level to be maintained at all times. A Class B output stage provides sufficient power to operate the recorder at its optimum level.

CIRCUIT DESCRIPTION

Referring to the accompanying diagram, the sound to be recorded is picked up by the two-button carbon microphone M-2. The microphone is transformer coupled to the type 56 first a-f tube in the grid circuit of which is located the volume level control. Microphone current is obtained from across the 500-

ohm resistor R-12, which is a section of the bleeder system of the power supply.


The type 56 first audio tube is self-biased by the voltage drop in resistor R-2. The output of this tube is resistance coupled to a second type 56 tube employed as a driver. This tube is also self-biased, by resistor R-6.

The 56 driver is transformer coupled to the type 53 double tube which is operated Class B. The output of the 53 is in turn transformer coupled to the recording head. A feature of this output system is the two neon level-indicating lamps. They are both connected between the center tap and one side of the output transformer through a resistance network consisting of resistors R-8, R-9 and R-10. Full brilliancy in one lamp with occasional flashes of the second lamp indicates the proper amount of power for recording.

VOLTAGE READINGS

Voltage readings are given in the diagram. These are the voltages to be expected with the recorder in operation. No allowance has been made for current drawn by the test meter and if low-resistance meters are used, such allowances must be made.

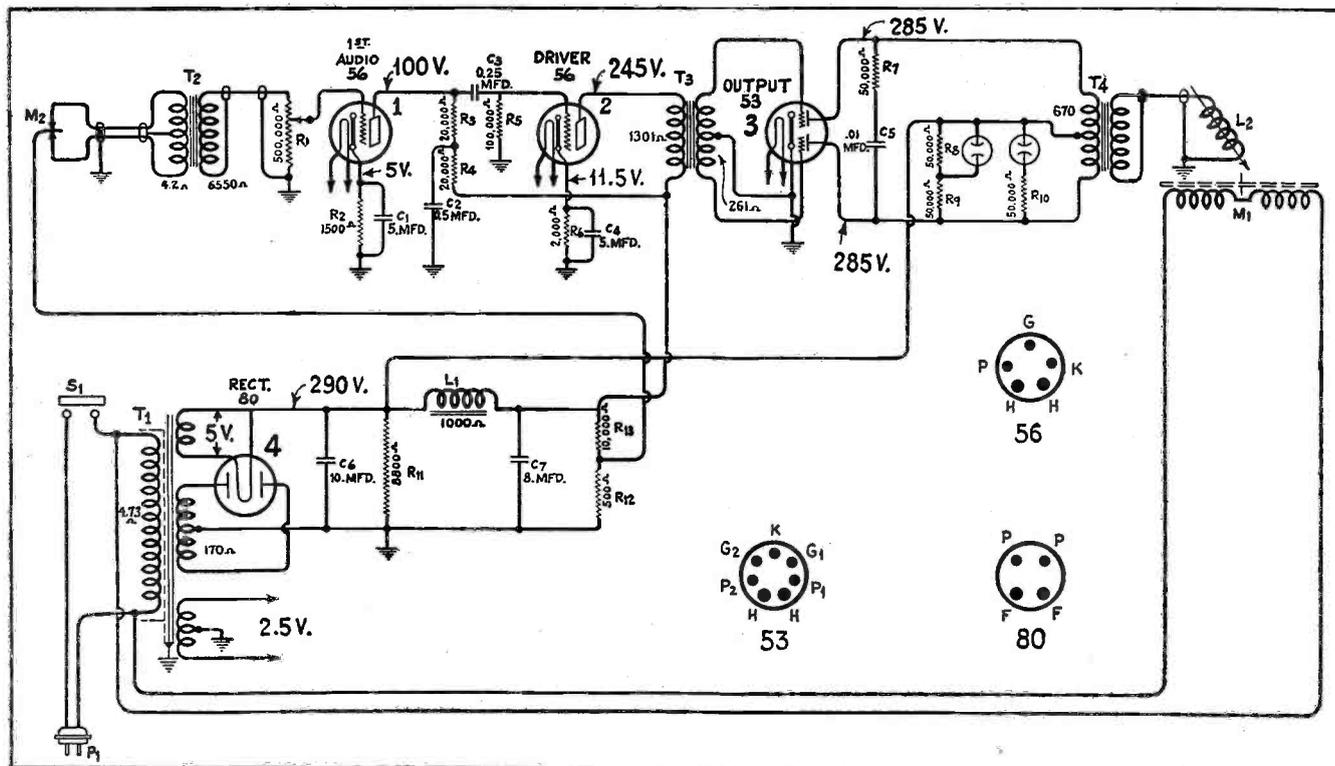The voltage given for the plate of the first 56 a-f tube is calculated. This is a high-resistance circuit and consequently the actual voltage cannot be determined with the usual type meter.



Circuit of RCA-Victor Model R-92 Recorder.

# Rider's Manuals

# HAD TO BE BETTER

to become the "Standard"

**I**NVESTIGATE before you buy any new manuals. Be positive that the manual you buy contains the greatest amount of information which will be the most valuable and helpful to you.

We say that you should have RIDER'S MANUALS. They are the Best manuals because they give you the greatest coverage of the radio industry and contain more service information of the kind you want and need—than all other manuals.

Take time off to read the comparative figures shown to the right. The superiority of Rider's Manual, Volume IV, also exists in Rider's Volumes I, II and III. . . . We guarantee you satisfaction with Rider's Manuals or your money back without any quibbling.

Buy On Merit. . . . Rider's Manuals cost more than other manuals—but—you GET MUCH MORE FOR YOUR MONEY!

Volume I . . . More than 1000 pages  
Price \$7.50

Volume II . . . More than 800 pages  
Price \$6.50

Volume III . . . More than 1150 pages  
Price \$7.50

Volume IV . . . More than 1060 pages  
Price \$7.50

Combination Volume I, II and III  
\$21.50 and \$25.00

Servicing Superheterodynes (New Ed.)  
288 Pages \$1.00

Servicing By Resistance Measurement  
203 Pages \$1.00

"Specialized" Auto Radio Manual (Vol. 1)  
Price \$3.50

See these manuals and books at your dealer. . . . Accept no substitutes.



John F. Rider, Publisher

1440 BROADWAY  
NEW YORK, N. Y.



## COMPARISON NO. 1

This comparison is made with the superheterodyne receiver as the basis because it is the major service problem confronting the service technician today.

### Total Number of Pages Including Index

Rider Manual, Volume IV . . . 1104  
Manual "A," Volume 4 . . . 402

### Total Number of Manufacturers in Volume

Rider Manual, Volume IV . . . 96  
Manual "A," Volume 4 . . . 33

### Number of Manufacturers of Superheterodynes

Rider Manual, Volume IV . . . 68  
Manual "A," Volume 4 . . . 26

### Number of Superheterodyne Schematics Presented

Rider Manual, Volume IV . . . 468  
Manual "A," Volume 4 . . . 212

### Number of Times I-F Peak Is Specified

Rider Manual, Volume IV . . . 396  
Manual "A," Volume 4 . . . 119

The above figures represent a comparison between Rider's Manual, Volume IV and another manual which is offered for similar use. . . .

Rider's Manuals include the Radiotron-Cunningham, National Union and Raytheon issues.

# ON THE JOB . . .

## "Your Service Code"

The Editor of *Sylvania News* has met quite a few Service Men, corresponded with hundreds of them, and from the things they have told him and things he has observed he has formed in his own mind a sort of composite picture of the ideal Service Man. Perhaps by putting this into words it will help all Service Men correct minor faults, and perhaps some of you will be able to supply details that have been missed.

1. He respects his profession. He didn't just go into servicing because he couldn't find anything else to do, but because he found it interesting and worth the time and energy he devotes to it.

2. He doesn't "know it all," and he never stops trying to learn. When he finds a problem that stumps him, he doesn't bluff, but gets the information he needs. He reads trade magazines, studies, goes to technical lectures and trade meetings, asks questions, experiments, keeps up with the times and the new developments in radio entertainment as well as in technical matters.

3. He isn't a "lone wolf." He realizes that in union there is strength, and is friendly and cooperative with other members of his profession. He doesn't "chisel," cut prices, or speak slightly about other Service Men to customers, thus decreasing confidence in the whole profession.

4. He uses high-grade materials and parts, and gives his best in the way of workmanship to each job. He never considers a job done until he is satisfied that it can't be improved.

5. He knows his costs, charges a price that will give him a fair profit, and his prices don't slide with every rumor that somebody else is charging less.

6. In his relations with his customers he maintains a professional attitude, neither too familiar nor apologetic. He is neat in his appearance and is careful of his customers' belongings. He is self-confident, without being "cocky" about his superior technical knowledge, and he is ready to explain if the customer wishes, or to keep quiet. If he chats he will not become personal, but will try to talk about something in which the customer shows an interest, preferably radio programs and entertainment. He is tactful. He does not belittle the set on which he is working, no matter how junky it may be. He is business-like in presenting his charges, and he itemizes so that the customer understands exactly

what he is paying for. He leaves his name and address—and a good impression—with the customer, and makes it a point to inquire within a few days whether the work has been satisfactory.


## Adjusting New Philco Dials

In the new model Philco receivers, which have scale readings up to 1720 on the broadcast-and-police band, a new method is used for setting the dial in the proper position on the shaft. This requires the use of a flat steel shim, of .006" thickness (Philco Part No. 45-2051). The adjustment is made as follows:


With the chassis connected to power supply and switch turned on, revolve the dial toward the 170 position (high-frequency end). Insert the shim under the "heel" of the oscillator section of the tuning condenser, and bring the "heel" down on the shim. Loosen the set screw in the front hub of the tuning shaft, and adjust the dial until the last line (full-length line, past 170 mark) coincides with the center of the glowing arrow indicator. Tighten the set screw. The dial is then correctly adjusted.
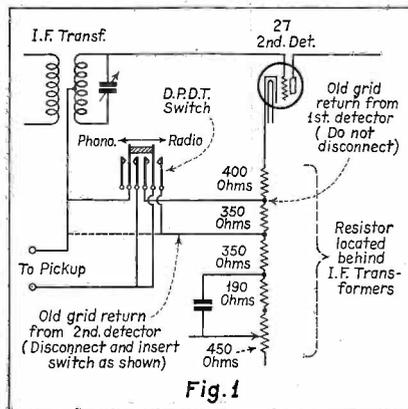
## Phono. for RCA 60, 62 and 66

The chassis used in the RCA Models 60, 62 and 66 is admirably adapted for record reproduction, providing the detector tube is operated on the straight portion of its curve, which can be accomplished if the circuit shown in Fig. 1 is used. This shows the necessary alterations in the cathode circuit, as well as the phonograph-radio switching arrangement. Any good double-pole, double-throw switch may be used for the change-over. Standard tip jacks are used for the phonograph pickup connections.



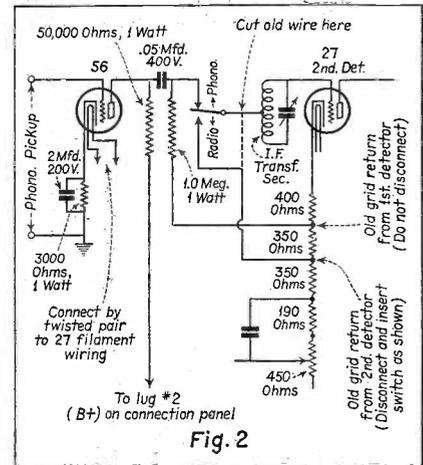Re-vamped second detector circuit of RCA 60, providing phonograph operation.



If more volume is required, an a-f stage should be added. The proper connections are given here.

If more volume is required than can be had with the pickup feeding the second detector tube directly, an additional stage may easily be incorporated, as shown in Fig. 2. In this case, a single-pole, double-throw switch is sufficient for phonograph-radio change-over. The extra parts required are: One type 56 tube; 5-prong tube socket; 3000-ohm, 1-watt resistor; 50,000-ohm, 1-watt resistor; 1-meg, 1-watt resistor; 2-mfd, 200-volt condenser; 0.05-mfd, 400-volt condenser; S. P. D. T. toggle switch.

E. M. PRENTKE,  
1950 East 105th St.,  
Cleveland, Ohio.

## Philco 58 and 84 Changes

On the second run of the Model 58 receivers, the center tap lead (black-yellow tracer) filament winding on the secondary of the power transformer is connected to one side of the pilot light. The other side of the pilot light is grounded. There is no change in the pilot light bulb.

### MODEL 84

The Model 84 may be changed to the Model 84A (25 cycles) by substituting power transformer No. 7422 for No. 32-7180 and replacing electrolytic condenser 30-2013 with 30-2028. The power transformer should be mounted before the electrolytic condenser to avoid difficulty in mounting.

On the second run of the Model 84 receivers, the center tap lead (black-yellow tracer) from filament winding of power transformer secondary is eliminated, and one side of the filament circuit and pilot lamp circuit is grounded

Group Subscriptions  
at SUBSTANTIAL SAVINGS!

- The Regular Subscription price for SERVICE is now \$2.00 per year.

You, no doubt, know many other Service Men who would like to receive SERVICE every month. Probably several other Service Men in your acquaintance are already subscribers.

Here are two plans whereby you can save money for yourself and your friends:

- 1—Subscriptions (new or renewals) can be purchased in groups of ten or more for \$1.00 per year each.
- 2—Subscriptions (new or renewals) can be purchased in groups of five to ten for \$1.50 per year each.

If your subscription is about to expire show SERVICE to five or ten of your friends. They, too, will want it. If they are already subscribers, they will want to renew or extend their subscriptions.

If you wish to *extend* your subscription at these savings, get five or ten others to subscribe at the same time.

Be sure to print clearly the name and address of all the subscribers, and send a check or money order covering the exact amount, noting in each case whether the subscription is a new one or a renewal.

*All Offers are Subject to Withdrawal Without Notice*

**Bryan Davis Publishing Co., Inc.**  
19 East 47th Street New York, N. Y.



SERVICE MEN SAY —


**YES! SIR!  
YOU CAN USE THESE  
BATTERIES 7 OR  
8 HOURS A DAY!**

**THEY CAN STAND THE GAFF!**

Owners of battery-operated sets can now listen to programs all day long and still get maximum service from their batteries! BURGESS Batteries—A, B and C—can stand the gaff! Repeated tests in our laboratories and in actual use have proved that they can be used for long periods at no increase in the "cost per hour." When an owner of a battery-operated set tells you he uses his set only three or four hours a day to "save" his batteries, you tell him to "change to BURGESS!" You don't have to "baby" BURGESS Batteries.\*

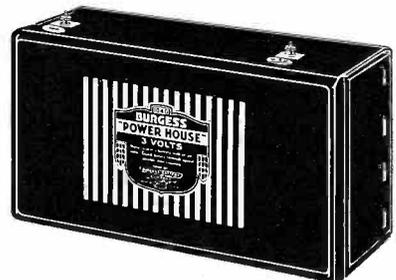**BURGESS POWER HOUSE**

The POWER HOUSE is a 3-volt DRY A battery designed specifically for use with modern 2-volt tube sets. Priced at \$3.20, it will give 400 Hours of dependable service at a cost of only 8/10¢ per hour!



The POWER HOUSE, distinctly a BURGESS development, consists of 40 size F cells arranged in two banks of 20 each, thus producing a long service life at a voltage within the proper range for radio service. It can be operated 7 or 8 hours a day because, like

**BURGESS "B" and "C" Batteries**

it has been built to stand the gaff! Recommend BURGESS Batteries to owners of battery-operated sets. As they enjoy more programs per day—and get the same number of hours of service from their black and white striped batteries—they will thank you.



\*Economical operation of 7 to 8 hours a day depends, of course, on the set being powered by batteries of the proper capacity.

**BURGESS BATTERY COMPANY, FREEPORT, ILLINOIS**

## CALCULATING ELECTRICAL UNITS

### PART 3

Last month we were considering the problem of a meter shunt. The shunt current,  $I_2$ , was found to be 60 amperes and the meter current,  $I_1$ , 30 amperes. Now the power lost in meter and shunt is

$$W = I^2 R = (90)^2 \times R$$

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{2} = \frac{2+1}{4} = \frac{3}{4}$$

$$R = \frac{4}{3}$$

$$W = \frac{90 \times 90 \times 4}{3} = 10,800 \text{ watts.}$$

In an actual case, the power lost would be a great deal smaller than this.

#### INTERNAL RESISTANCE

All batteries, or in fact all sources, have an internal resistance. This results in a loss within the battery itself, which in any precision work must be taken into account. In some cases, in fact, this internal resistance becomes a factor of major importance and always results in the terminal voltage, in operation, being less than the terminal voltage under open-circuit conditions . . . smaller by the amount of the internal-resistance drop. To illustrate, let us refer to Fig. 8, where  $r_1$  is the load resistance and  $r_2$  the internal resistance, the latter being shown outside and lumped for convenience. The relations now become

$$I = \frac{E}{R} = \frac{E}{r_1 + r_2} \quad (12)$$

$$V = E - Ir_2 \quad (13)$$


$$W = I^2 R = \left( \frac{E}{r_1 + r_2} \right)^2 r_1 \quad (14)$$

And if  $r_1 = r_2$

$$W = \frac{E^2 r_1}{4 r_1^2} = \frac{E^2}{4 r_1} \quad (15)$$
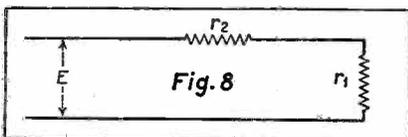
#### MAXIMUM POWER

Sometimes it is desirable to obtain maximum power from a battery. Let us see at what resistance maximum



Illustrating internal resistance.

power will be delivered to the load. Make, in Fig. 8,  $E = 10$  volts,  $r_2 = 500$  ohms, and  $r_1 = 250$  ohms. Then

$$W = \left( \frac{10}{500 + 250} \right)^2 250$$

$$= \frac{25,000}{562,500} = 0.044 \text{ watt.}$$


For  $r_1 = 500$ , use equation (15), thus,

$$W = \frac{100}{4 \times 500} = 0.05 \text{ watt.}$$

And for  $r_1 = 1,000$

$$W = \frac{100 \times 1,000}{1,500 \times 1,500} = 0.044 \text{ watt.}$$

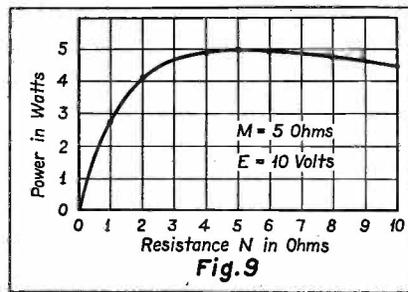From this it appears that maximum power is delivered to  $r_1$  when the latter is equal to the internal resistance  $r_2$ . The curve in Fig. 9 illustrates this graphically. For this condition the



Graph illustrating deliverance of maximum power.

power is equal to the generated voltage squared, divided by four times the termination resistance. Now, the reason for matching the resistance of any device is to draw maximum power from it. However, there are often very good reasons for matching certain apparatus at other resistances and sometimes these factors more than compensate for the advantage of maximum power.


#### SERIES-PARALLEL CIRCUIT

The diagram of Fig. 10 shows a series-parallel circuit. The two 8-ohm resistances in parallel are in series with two 4-ohm resistances, and the battery has an internal resistance of 2 ohms. The open-circuit battery voltage is 7 volts. We have

$$R = 2 + 4 + \frac{64}{16} + 4 = 14 \text{ ohms}$$

$$I = \frac{7}{14} = 0.5 \text{ ampere}$$
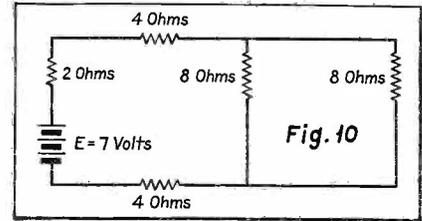
$$V = 7 - 0.5 \times 2 = 6 \text{ volts}$$



A typical series-parallel circuit.

$$W = \frac{6 \times 6}{12} = 3 \text{ watts delivered to the load.}$$

The total power  $W_t$  consumed in the circuit is

$W_t = E \times I = 7 \times 0.5 = 3.5$  watts, while the power consumed in the battery  $W_b$  is

$$W_b = I^2 R$$

$$= 0.5 \times 0.5 \times 2$$

$$= 0.5 \text{ watt.}$$

#### VOLTAGE RELATIONS

There still seems to be a great deal of confusion and differences of opinion in reference to negative voltages; yet Service Men are constantly being exposed to and working with them. In order to clear up this doubt and in order to better understand what is to follow, it is probably well to consider just exactly what is meant when we speak of potential.

All potentials, or voltages as they are generally called, are relative . . . relative to the potential of ground. Since it is necessary to have some definite starting point, ground potential has been assumed as being zero, and all other potentials are referred to this value. Now actually, the ground is not at zero potential but at some other value that is extremely difficult, if not impossible, to accurately determine. Confusion is quite apt to result unless this fact is kept in mind, for it is possible, since the ground is really at some potential higher than zero, to have a negative value with respect to ground.


A negative voltage simply means that the voltage, with respect to the absolute zero of potential, is actually lower than ground potential; and the negative sign is given it to indicate its value with respect to the assumed zero. For example, a minus five volts means that we have five volts less potential than we would at ground, although its actual value (which is unknown) might be 50 or 100 volts positive.

**They're  
HERE!**



# POWER WIRE WOUND RESISTORS


*in a NEW and Complete Line*

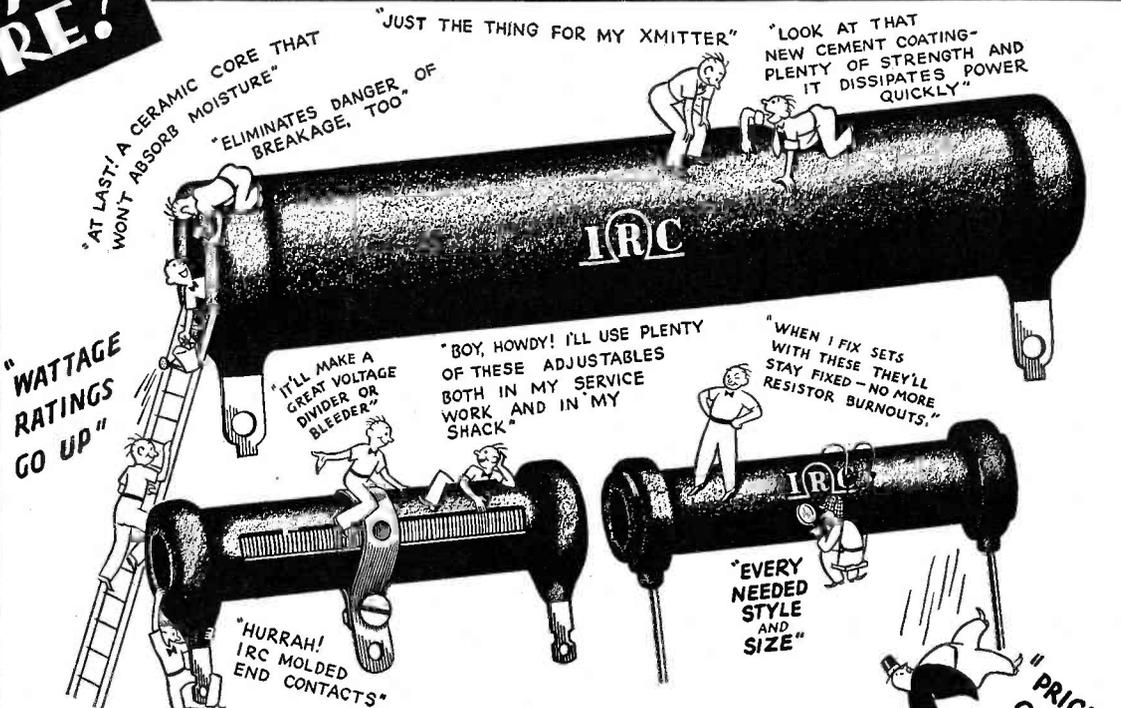

Write for  
Catalog S-100

INTERNATIONAL RESISTANCE CO.  
2100 Arch Street PHILADELPHIA, PA.  
In Canada: 187 Duchess Street, Toronto, Ont.

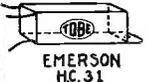**TOBE**  
EXACT DUPLICATE  
REPLACEMENT  
CONDENSERS



## CONDENSERS

—the **Standard** of the pioneer  
—the product of **Experience**.  
Designed for **Modern 1934 Service**:

- **Extreme Compactness**
- **Moisture Proof**
- **High Voltage Safety Factor**
- **Wide Capacity and Voltage Range**
- **Satisfactory Life**
- **Low Price**

and in addition to our regular standard condensers, through popular demand we are featuring

**TOBE** EXACT DUPLICATE  
Electrolytic  
Replacement Condensers

for latest models **AC-DC Midgets, All-Wave Supers, Auto Radios, and Standard Broadcast Receivers.**




Exact to originals as to physical dimensions, mounting holes, color and length of leads, etc. Peak voltage ratings are increased.



**Tobe Deutschmann Corporation**  
CANTON, MASS.

# Halldorson

## Replacement Transformers

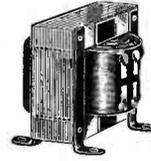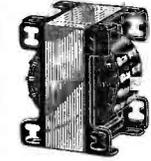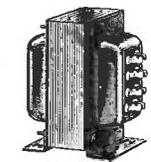

**INVISIBLE QUALITIES**—When you buy transformers you rely upon the manufacturer for the invisible qualities that give them merit. Outwardly one brand may look the same as another, but in operation one may fail while the other gives perfect results. Halldorson Transformers not only look their part, but in addition excel in such invisible qualities as insulation, regulation and reserve against overload.

**ADAPTABILITY**—Halldorson line of Replacement Transformers fits the requirements of the serviceman and jobber. One electrical design fits the maximum set models that convenience and economy permit. It neither multiplies beyond limit nor contracts beyond common sense the number of designs a jobber must keep in stock.

**REPUTATION**—The name "Halldorson" has long been associated with high quality products. It is the label of merit on the carton.

Ask your jobber. If he hasn't the line, send his name with your request for catalog.

**The Halldorson Company**  
4500 Ravenswood Ave., Chicago

# HIGHLIGHTS...

## BATHROOM RADIO

The editor of a contemporary publication has learned that there are 18 million bathrooms in the United States. Since people spend considerable time in this room of echoes, he feels that a special, waterproof radio is in order.

We cannot help but remark that radio broadcasting has already cut down the reading time of the average American. Newspapers and magazines have suffered alike. The American bathroom is practically their last stand.

If bathroom radios appear, newspapers and magazines might as well fold up and die.

## HIGH-FIDELITY BREAKS

On Wednesday evening, September 12, in the Grand Ballroom of the Hotel Waldorf-Astoria, New York City, Philco let loose with their new high-fidelity receiver—Sound Beam Diffuser and all.

We have made the following notation in our "little black book": The battle of the century is on! Philco challenges radio set manufacturers with new high-fidelity receiver. Set manufacturers challenge Philco with dittos. Philco and set manufacturers challenge broadcast stations to do them one better. Broadcast stations install new equipment and get over 500 cycles more than high-fidelity receivers will pass. Set manufacturers bring out high-high-fidelity (or high-ho-fidelity) receivers which will pick up sounds made by fish in water. Net result: The same old jokes regularly broadcast come through with better quality (?).

## WARE OPENS NEW BEDFORD BRANCH

Recently the Ware Radio Supply Company of 913 Centre Street, Brockton, Mass., a prominent New England parts distributor, opened a branch at 813 County Street, New Bedford, Mass., from which replacement parts and amateur equipment will be distributed.

Mr. Clifford Ware, heading this organization, attributes his success in the past business to a strict policy of handling only nationally advertised lines, carrying complete stocks, and hard work.

One of the features of the opening day of the New Bedford branch was an all-day demonstration by Engineers of the Tobe Deutschmann Corporation of the new Tobe Condenser Analyzer.

Note the attractive window display and the merchandising value of the shelf layout inside the store, shown on this page.

Mr. Ware reports that he received words of praise from many amateurs, dealers, and Service Men in the vicinity of New Bedford and Cape Cod, expressing appreciation for this local supply point from which they can draw their needs.

## KRUSE'S RADIOPHONE GUIDE (2nd Edition)

Robert S. Kruse has been a guiding light in the Ham field for many years. His writings have been concise, authoritative, and quite often decidedly original. The magazine *Modern Radio*, one of his ventures, and a highly successful one from the editorial standpoint, carried some of the best material on radio transmission and reception offered to the Ham, the experimenter and the Service Man.

*Kruse's Radiophone Guide* contains many of the fine articles originally published in *Modern Radio*. Back copies of this magazine are now scarcer than hens' teeth, which makes much of the data in the *Radiophone Guide* extremely valuable.

Mr. Kruse's book is intended particularly for the Radio Amateur whose activities are confined to the wavelengths below 200 meters. To this man the *Radiophone Guide* will prove a gold mine of information. However, the addition of "Batcher's Radiographs"—a group of 14 charts and graphs from which may be determined the answers to numerous radio problems—also makes the *Radiophone Guide* of considerable value to the Service Man. From these graphs it is possible to calculate without difficulty the values of coils and condensers to cover any combination of wavebands from 0.5 to 200 meters, the electrical values of a circuit ("Ohm's Law on Ice," they call it), the resultant values of equal or unequal resistors in parallel, resultant capacity of unequal condensers in series, etc. There is also a graph providing a painless dissection of the deci-

bel, which also permits the design of resistance pads.

The Service Man is also sure to be interested in the data covering the construction and use of an inexpensive oscilloscope, a short-wave converter, the chart giving microphone and amplifier levels, and the many short notes on receiving antennas and receiver design.

(*Kruse's Radiophone Guide*, second edition, 7 by 10, paper cover, 82 pages, well illustrated. For fifty cents, from Robert S. Kruse, Guilford, Conn.)

## IMPORTANT!

In the "Highlights" section, page 266, of the July issue of *SERVICE* the items headed "Sylvania Tube Stickers" and "New Sylvania Tube Manual" were misleading in that no mention was made concerning a charge for these articles. This was an oversight on our part. The Tube Stickers sell at \$1.00 per roll and the Manuals at 10 cents each.

## SPRAYBERRY MOVES

In line with the growing popularity of Sprayberry's Practical Mechanics of Radio Service, F. L. Sprayberry has announced his removal to new and larger quarters at 2548 University Place, N. W., Washington D. C. Here an entire floor is devoted to the Sprayberry laboratory and executive offices, thus insuring the utmost in service and cooperation with the hundreds of students in all parts of the world, it is stated.

Mr. Sprayberry has also announced a number of revisions and additions to his course to keep it strictly up to date at all times. Notable among these are complete coverage of short-wave radio and the all-important job of selling service. Throughout, the course is designed for those who are already actively engaged in the service business, being in the nature of a post-graduate course to enable them to handle all types of radio service work in the best and most practical way, it is said.


## SYLVANIA ANNOUNCES 12A7 TUBE

The Sylvania 12A7 type, a combination power pentode and rectifier tube designed especially for use in small ac-dc receivers where space is at a premium, is announced by the Hygrade Sylvania Corporation of Emporium, Pa. There is a 6.3-volt heater for each unit, the heaters being connected in series internally, thus making the rated heater 12.6 volts. Separate connections are brought out for the pentode-cathode, screen grid, and plate. The suppressor grid of the pentode section is connected internally to the pentode-cathode.

The rated power output from the pentode is 0.55 watt, and the maximum dc load current of the rectifier section is 30 milliamperes.
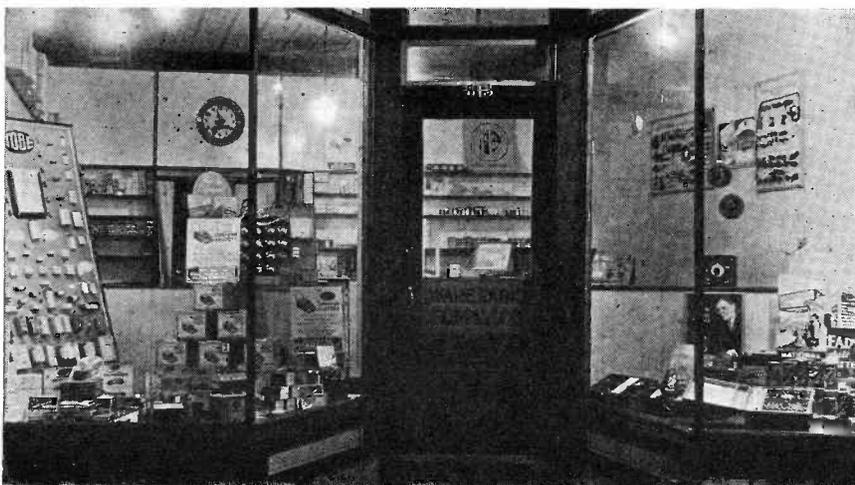
## HOWARD RADIO MOVES

The Howard Radio Company have a nice new factory building in Chicago. The entire plant is being moved from South Haven, Michigan, although a company in this same city will continue to make the cabinets for the Howard receivers.



Ware's new branch in New Bedford, Mass.

# THE **TOBE** CONDENSER ANALYZER

puts the Relaxation Oscillator to work. This Simple yet Scientific instrument will make money for you from the first time you use it.

The TOBE Condenser Analyzer tells instantly if condensers of any type or capacity, paper, mica, electrolytic, or oil are leaky—of low D.C. resistance, of high current leakage—if they are "open" or "shorted," if they are operating intermittently, or if they are in satisfactory condition.

## THE PROOF OF THE PUDDING—

"I congratulate you for the design of your TOBE Condenser Analyzer. I ordered one of Baltimore Radio Corporation and I am using it. It works wonderfully. The flashing sign and the interpretation of results are so uniform that after testing about four dozen of my spare condensers, I have reached the conclusion that it is the most practical instrument for servicing. Many old troubles that had no explanation to me have been cleared up. Intermittent performance and leaky condensers are responsible for many noises and distortions." Sincerely yours, R. del Valle Sarraga, P. O. Box 935, San Juan, Porto Rico, W. I.



## OBTAIN A **TOBE** CONDENSER ANALYZER TODAY—

From your distributor or direct from the factory. (Allow postage on six pounds.)

Net Price to Dealers of Servicemen, only \$11.40  
Price \$11.70 in Denver and the West Coast.  
Now available in 25 cycle, and 220 volt models.


**TOBE DEUTSCHMANN CORPORATION**  
CANTON, MASSACHUSETTS

# Leading Radio Engineers "OK" This Compact **TUBE TESTER**

... tests parts of tube that actually wear out in service.

A portable tester, selective type, very flexible for present and future type tubes. English reading dial, accurately calibrated, with laboratory standard, New Dayrad feature shows cathode leakage while tubes are hot. Also Dayrad Neon Shorts Tests showing leakages up to 100,000 ohms. Carrying case with removable lid.

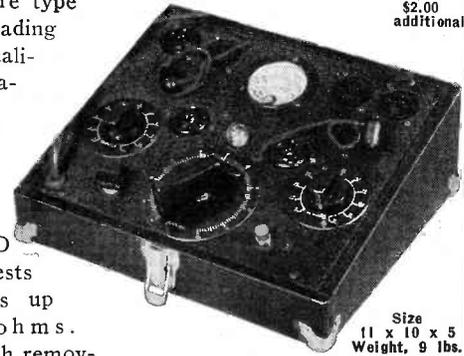Net Price to Dealer **\$29.75**  
25 cycle—  
\$2.00  
additional



Size  
11 x 10 x 5  
Weight, 9 lbs.

MADE BY

## "DAYRAD"

**THE RADIO PRODUCTS CO.**  
125 Sunrise Place, Dayton, Ohio



## National Union offers Supreme 35 Tube Tester

**\$10.00** DEPOSIT

October Only

Look! Act! . . . on this remarkable offer. A Supreme Model 35 Tube Tester . . . yours for only \$10.00 deposit and a National Union tube purchase agreement. You get the \$10.00 back as a merchandise credit as soon as you complete the agreement.

This Supreme tester is a brand new model . . . sturdy, efficient, great big easy reading dial. Imagine, this fine tester which would cost you \$29.95 is all yours FREE on this startling National Union offer for the month of October only.

Get full details at once from your jobber or write NATIONAL UNION. **OCTOBER ONLY!**

### Look At All N. U. Offers You!

**MORE PROFIT:** The 10 cent higher list price of National Union tubes gives you most profit margin. (Send for Profit Comparison Chart). **PRICE DECLINE PROTECTION:** Complete unlimited protection against list price declines on all shelf stock. **FREE SHOP EQUIPMENT:** Meters, manuals, tube testers, oscillators given with tube purchases. Get details! **FREE SALES AIDS, SERVICE AIDS, CHARTS AND DATA:** You can't afford not to tie up with National Union!

National Union Radio Corporation of N. Y.  
400 Madison Avenue,  
New York City.

S 9-34



Tell me more about . . .


Name . . . . .

Street . . . . .

City . . . . . State . . . . .

## "Multi-Tap" POWER TRANSFORMERS!

(Patent Applied for)

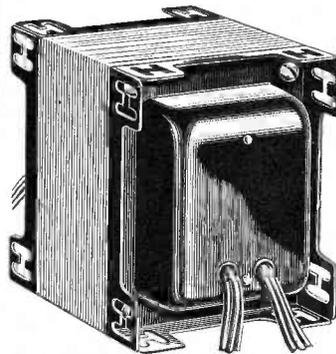

The wide range of adaptability of only five models "Multi-Tap" Universal Power Transformers is made possible thru various taps in these units which may be used singly or in combinations. The required current values can be delivered to each of the several leads in the set with any combination of tubes, as accurately as by the original power units. Easily installed.

### SERVICE MEN . . .

This is a real opportunity for you! "MULTI-TAP" Universal Replacement Transformers are

### NECESSITIES

to protect the enormous investments in radio sets now in use by your customers.

### Stock of Only Five (5) Power Transformers

provides immediate renewal of original performance in case of trouble in the transformer—the heart of the radio—in any more than 90% of all radios, whether "orphaned" or current models. Every radio dealer needs a kit of "MULTI-TAPS" to insure continued radio service to his patrons. AC 110-120 v., 50-60 Cy.; 220-240 v., 50-60 Cy.; 115 v., 25-40 Cy.; 150 v., 50-60 Cy.

### FREE FOR THE ASKING!

"MULTI-TAP" Bulletin No. 6, listing 1927 models of radios which you can immediately service with one of only 5 "MULTI-TAP" power; and input, output, and filament transformers.

## GENERAL TRANSFORMER CORP.

502 S. THROOP STREET CHICAGO, ILLINOIS

### GENERAL TRANSFORMER CORP.

502 S. Throop St., Chicago, Ill.

Send me a copy of your "Multi-Tap" Bulletin No. 6, listing 1927 models of radios which I can service with one of only 5 "Multi-Tap" transformers.

Name . . . . .

Address . . . . .

City . . . . . State . . . . .

# ASSOCIATION NEWS . . .

## R. T. G. NEWS

We have received a copy of the first issue of the *R. T. G. News*, the official organ of the Radio Technician's Guild of Massachusetts. The Guild was incorporated in 1933.

The magazine is edited by A. C. W. Saunders, 87 Marshall St., Medford, Mass. According to a statement in the first issue, the *R. T. G. News* is sent free to all Service Men, radio retail stores, radio wholesalers, and parts jobbers, and all those interested in bettering the Radio Service Industry. All communications should be addressed to the Editor.

The July number was a special "find the error" issue, with prizes offered. Since the contest has closed by this time, we venture to remark that vanadium is not a gas. Was that a part of the contest? It had better be!

## ELMIRA CHAPTER TO BROADCAST

The Elmira Chapter of the Institute of Radio Service Men is sponsoring a 15-minute broadcast each Saturday over radio station WESG, Elmira. This program should be of considerable interest to their regular listeners as well as to Service Men.

## R. T. A. EXAMINATIONS

In the April issue of *SERVICE*, "Association News", page 141, there appeared a short item concerning the general details of the plan for examinations which are to be given by the Radio Technicians' Association of San Francisco. A few of the problems to be given and answered as true or false are contained in the August issue of the *R. T. A. News* from which we quote:

"A neutrodyne circuit must be properly neutralized in order to be reasonably selective.

"If signals can be heard with a phone connected in parallel with the primary of the a-f transformer, but no signals with the phone in series with it, it would indicate that the primary is open.

"If the line voltage were low, you would step it up by inserting an auto transformer.

"A tube operated at high heater voltage lasts much longer than a tube operated at low heater voltage.

"Weak magnets in a reproducer are a source of poor tone.

"There are three distinct methods of attaching the voice coil to the cone.

"Due to the inefficient magnetic structure of the field housing of a dynamic speaker, and the large air gap necessary for the voice coil, the inductance of the field structure is much less than the first filter choke which precedes the field in the filter system.

"Five types of reproducers in use today are: magnetic horn, magnetic cone, dynamic, condenser and head phone.

"The dynamic speaker gives better reproduction when using a small baffle than when using a large baffle.

"A speaker is very seldom the cause of microphonics in a receiver even though indirectly through cabinet vibration.

"Major repairs on voice coil windings can only be taken care of by the use of

jigs and machines and should not be attempted unless the service shop is properly equipped.

"Every manufactured article has anywhere from a 30- to a 90-day guarantee and large repairs should be made on the device by the Service Man within the guaranteed period.

"On sets with parallel feed on the output tube, a shorted condenser will be evidenced by the same choked sound as an output tube with no grid bias.

"The Service Man should always present a lot of complicated looking tools and equipment for the customer to see.

"The technique of the Service Man should be based on not what to do, but how to do it.

"In receiving a service call on the telephone, the conversation should be extended as long as possible.

"Motor noise elimination may be secured by shielding low-tension ignition leads.

"A decibel is the standard equivalent of 7.8 watts of output power."

Well, how did you come out? Answer yes or no.

Do you approve of this method of examination, and do you believe the questions to be fair? We are not so sure about the question relative to the five types of reproducers. The answer could be yes and then again it could be no. On the whole, however, the questions appear concise and practical in nature.

## BUSINESS OPPORTUNITY

Intermediate-wave radio receivers at filling stations and other points along highways to obtain weather information for motorists have been suggested by the Bureau of Air Commerce. Every hour from the 68 airways broadcast stations scattered throughout the United States along the Federal Airways System weather reports are sent out on the air to assist flyers, and small receiving sets with a range of from 200 to 400 kc could make this information available to motorists.

### WEATHER BULLETINS

This service, if organized, could be made available to the transient motorist in the form of small bulletin boards to be placed in conspicuous places in service stations, bus stations, and local automobile clubs and associations on heavily traveled highways where an attendant could post the weather broadcasts as soon as they were sent out on the air. This would be of particular importance in the more rugged and mountainous sections of the country, where a fog may mean delay, heavy rain a washout, and a snow an impassible section of roadway. Using these proposed bulletins the motorist may take another route and avoid the possibility of these delays.

### DATA BEING USED

Automobile test tracks and automobile clubs have already found this means of determining the weather very valuable, but this service has not yet been placed at the convenience of the casual motorist and cross-country driver. Just as the airplane pilot depends on the weather reports to guide him through the skies, so will the automobilist depend on them in his selection of routes and the length of his day's travel.

It has been previously suggested by the Bureau of Air Commerce that the automobiles themselves carry these receivers for the reception of this weather information. The service that would be offered by filling stations and other points where the motorist is likely to stop would include cars not equipped with radios.

### ENTER THE SERVICE MAN

The Service Man should have no difficulty in building intermediate-wave receivers for the sole reception of these weather reports, as they need not be complicated affairs. As an alternative the Service Man could function as an intermediary between the manufacturer and filling-station operator, handling the sale and installation of the necessary equipment.

Considering the number of auto service stations, filling stations, bus stations, auto camps, etc., in most any locality, it appears that the Service Man has the opportunity of developing not only a new market, but a distinct service.

It is suggested that each Service Man start a bit of campaigning in his locality with a view to obtaining this added business. By all means, do not fail to contact the chain filling stations, as well as the independent fellows. The chain stations are always anxious to provide every possible service to motorists. Weather reports will draw added trade.

Here's a real opportunity. Why not hop to it?

## WHOLESALE OPENS ATLANTA BRANCH

On September 1st, Wholesale Radio Service Company opened a division in Atlanta, Georgia. This unit, although intended to serve the needs of Service Men, Experimenters and Amateurs in and around Atlanta, will also serve as a distinct mail order branch for the entire south.

An unusual service feature of this branch is in the form of a direct teletype communication system between Atlanta and New York. By this means any special orders can be taken in Atlanta and relayed to the New York Warehouse within two minutes. In this way shipments of special merchandise not available in Atlanta can be rushed from New York.

Mr. James Monroe will be General Manager, while Mr. A. Sidney Hardy, Jr., of Atlanta, will be in charge of local store sales.

## NEW TRANSCRIPTION COMPANY

W. O. Watson, the past decade engaged in technical work for the films, has been appointed chief recording engineer for Radio Release, Ltd., new Hollywood group of transcription producers. Perhaps best known for his recording of "Wings," Mr. Watson has done pioneer work since the early days of the flicker films.

Radio Release has taken over the former KMTR studios.

## SOLAR SERVICE LEAFLET

The Solar Manufacturing Corporation, 599-601 Broadway, New York, N. Y., have just issued their latest Service Leaflet, No. 5-S, which features a number of new Solar condenser developments. The fifteen pages in this leaflet give a great deal of technical data concerning Solar electrolytic, paper, and mica condensers. All requests should be addressed to the above company



Inverted Can Unit



Cardboard Box Unit



Auto Radio Vibrator Condenser



Sparion Types 5031, 5032 and 5033

## Exact Duplicate REPLACEMENTS

Is your trade fussy . . . wants identical replacements . . . will not accept makeshifts or general utility units?

OK. Just order Aerovox *Exact Duplicate* Replacements . . . finest replacement units obtainable . . . embodying Aerovox high-quality construction throughout . . . designed specifically for most standard sets.

Also stock the new Type PM5 general utility, universal voltage electrolytics . . . in two voltage ratings and five capacities . . . for all replacement purposes.

**Send for Data:** Latest Aerovox Catalog is yours for the asking. Also sample copy of the Aerovox Research Worker . . . a monthly collection of practical radio dope fresh from research laboratory and engineers—the cream of the crop of advanced radio information.



CORPORATION

80 Washington Street :: Brooklyn, N. Y.




## UNIVERSAL ALL-WAVE ANTENNA

**THE TRUE ALL-WAVE NOISELESS ANTENNA SYSTEM** that is **PRACTICAL** for dealer installation! Your choice of two antenna systems with one aerial kit. May be connected as a technically exact but expensive half-wave Hertz aerial (single or multiple doublet). This system may also be connected as the **Inexpensive** and **Effective** quarter-wave Marconi aerial. (Common inverted "L").

### SYSTEM TUNES TO LISTENING BAND

No matter which type of aerial is installed wave band change-over switches on the receiver Filterizer transformer **TUNE THE ANTENNA TO THE WAVE BAND BEING RECEIVED!** **DESIGNED BY SPECIALISTS IN RADIO NOISE ELIMINATION!** **AVAILABLE IN TWO MODELS**

**MODEL 34**  
All-Wave Aerial Filterizer Kit includes:  
1—Aerial Transformer.  
1—Receiver Transformer with wave band switches.  
50 ft. weather-proof twisted pair transmission line.  
1—**POWER LINE FILTER**, and all necessary aerial and ground wire, insulators, etc.  
Model 34.  
List Price .....\$6.95

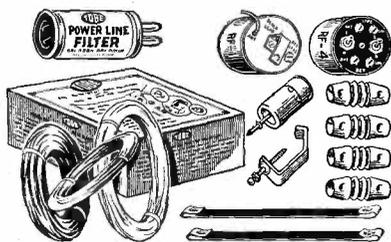

MODEL 34

**MODEL 35**  
Same as above except less Power Line Filter and aerial and ground equipment. List Price.....\$4.95

## A New TOBE LINE FILTER

priced to meet the purse of 17,000,000 RADIO OWNERS!



Can be plugged in at the radio to stop power line radiation. Can also be plugged in at the appliance to stop noise as it is created. Several can be sold in each home. Ideal for apartment houses, hotels, Y.M.C.A.'s, etc.

**TOBE DEUTSCHMANN CORP.**  
Canton, Mass.

# Slogan Contest AWARDS

The Rider's Manual slogan contest announced in the June issue of Service Magazine came to a close on August 15th, 1934. The following prizes were awarded by the Jury of Awards.

## 1st Prize (\$25.00)

Mr. W. A. Ivins  
230 Mill Street  
Mt. Holly, New Jersey

for

*"Use Rider's Manuals—Satisfy "All Customers"*

## 2nd Prize (\$10.00)

Mr. Allen Morse  
1012 7th Ave., No.  
Great Falls, Mont.

for

*"Rider's Manuals—The Serviceman's X-Ray"*

## 3rd Prize (\$5.00), Two Awards

Robert Walters  
Skykomish, Washington

for

*"As Necessary as an Analyzer"*

and

Charles F. Machin  
1020 Highland Ave.  
Windsor, Ontario  
Canada

for

*"As Necessary as Your Set Analyzer"*

## HONORARY MENTION

We have decided to award several copies of "Servicing Superheterodynes" to those men who deserve honorary mention for having submitted good slogans, which, while not of main prize calibre, were meritorious. Also to those men who submitted some excellent slogans which were not eligible for the main prizes because they exceeded the 10-word limitation. Honorary mention prizes are being awarded to:

Wm. Enderson, St. Cloud, Florida  
Alfred R. Gray, Northwood Ridge, N. H.  
A. G. Beyer, St. Louis, Mo.  
G. S. Johnson, Eastford, Conn.  
Andrew Schwab, Chehalis, Wash.  
H. H. Schock, Reading, Penn.

**John F. Rider**

1440 Broadway

New York City

# THE FORUM...

## HEAVEN AND OSCILLATORS

Editor, SERVICE:

While looking through past issues of SERVICE, in an unsuccessful attempt to find a diagram of the Clarion Jr., Model 320, I found, in the October, 1933 issue, page 364, a service note by Mr. C. King in which he identifies the ground wire by tying a knot in it.

For many years, I have been tying a knot in the aerial lead. We say marriages are made in heaven. When people are married, we also say they "tied the knot". Since the aerial is nearest to heaven, I tie the knot in the "sky wire" and not the ground.

Silly. But uniformity, even in this minor detail, may be a time saver.

Can you give us complete data on a real all-wave oscillator... one that holds its calibration? I suggest that you make up a model and give us the list of parts and calibration curves. While our job will doubtless have different curves, a general idea of where the various frequencies may be found on the dial will help in calibrating.

N. H. SILVERMAN,  
930 W. 17th St.,  
Lorain, Ohio.

*(We think your system is swell, providing you stick to the point as to where marriages ORIGINATE. Many of them END UP where one makes the ground connection.)*

*We had thought of designing an all-wave oscillator, but came to the conclusion that Service Men would rather buy the really excellent and rather low-priced jobs on the market, than to get all involved in the construction of such a unit. Moreover, the finished job would in many cases prove to be a disappointment. Accurate calibration is a prime necessity in an all-wave oscillator, and so is stability. However, if there is an active demand for the constructional details of such a unit, we will get to work. How many of you fellows are really interested in building your own all-wave oscillator? And what special features would you demand?*

—THE EDITOR).

## THE STATIC PAGE

Editor, SERVICE:

What have you done with the "Forum" in SERVICE? I have searched through and through the June and July issues and I can't find even the periods left. Something tells me that you don't mean "right by our Nell", but I don't want to believe that you have lost your "sensuama". I'll bet that not a single one of the thousands of "Forum" readers expected you to take the rap for "poor taste" in the last "Forum". We are all with you and for you, so be a good scout, Ed., and give us back the static page. If you will, maybe H. M. Bell (March, 1934) will kick in with some more helpful hints on how to be a "successful radio expert", or at least tell us the outcome of the percolator job. In any event the "electrician" should have another chance, though I suspect that he is too much of a gentleman to hit back.

Several months ago I listened to a very lively and enjoyable program from WJSV

(Washington, D. C., 1460 kc, 10 kw). Every few minutes during the program the tone would turn very sour. But I am willing to overlook some distortion if the program is interesting (we can't have everything), so I listened right through to the end. When they signed off for the night, I did not get up to turn the Scott off immediately, but sat thinking about waves and humps and fidelity curves in general. Then loud and clear as a bell came the announcer's voice, announcing the next number for KSTP (St. Paul, Minn., 1460 kc, 10 kw). So instead of getting out the oscillator and fibre wrenches, I turned out the lights and went to bed.

You can't expect US to write OUR letters to the Times, can you?

M. K. BARBER,  
Ft. Ethan Allen,  
Vermont.

*(Here is the old Static Page again. We missed it, too—but with half the fellows suffering from the heat and the other half off somewhere catching fish, our "letters-to-the-editor" became mere shadows-of-a-dream-of-things-long-passed. Now that there is an occasional bit of snap in the air, and a hitching of belts on the part of those who are all set to make a killing this Fall and Winter (as we are), things are picking up a bit. Again the good, old letters are coming in and we are pleased to note that the fellows are stirring about with questions, ideas, criticisms and compliments. The mail bag is fat and we are happy. BUT, will you guys kick through with MORE letters. What you doing? What's the news, and are you at the old number? Kick through—kick through*

—THE EDITOR).

## HIGH FIDELITY

Editor, SERVICE:

I cannot understand why you should use good space in SERVICE on high-fidelity receivers when there is "no such animal" on the market. Why don't you get down to earth and give us data we can use in our every-day work? We aren't even working on last year's receivers yet, so why all this high-fidelity stuff?

TED DEGROFF,  
Ghent, New York.

*(SERVICE has always had a very definite policy regarding new developments in the radio field. The basis of that policy has been education. Most of our readers have agreed that we can serve them better by keeping them informed of the additions and changes in engineering design. We attempt to interpret the advances as they are made, so that every reader can keep up-to-date. By the time this issue is printed high-fidelity receivers will be on the market. Most Service Men will be able to answer the questions hurled at them by their customers who will wish to know something about high-fidelity. The Service Man who can intelligently answer such questions will solidify his position with his customers. The important point, however, is understanding the essentials and being capable of acting in an emergency. High-fidelity receivers will be up for servicing before Christmas. You may get*

*one yourself. We hope you read the complete text published so that you will have some idea as to what it is all about.*

—THE EDITOR).

## TUBE PRONG NUMBERING

Editor, SERVICE:

I have been an interested reader of SERVICE since its first issue, and it is without a doubt of great value to Service Men. I sincerely feel, however, that you have failed miserably in protecting the service fraternity in connection with new tube base prong numbering systems.

When the old system was generally adopted a couple of years ago, it was a welcome relief from the situation as it then existed. Several thousand units of test equipment, both home and factory built, have been designed and built around this system. About nine months ago, the Vacuum Tube Committee of the RMA saw fit to adopt as standard a new system generally reversing the order of the old system.

I wrote this committee in protest of the change and others saw fit to do likewise. The courtesy of a reply or even acknowledgment was not, to my knowledge, made in any instance. Neither have I seen any published reasons for or defense of the new standard. I am totally at loss to hit upon any logical reason for making the change, while, on the other hand, the objections are numerous. Some one mentioned to me that it was instituted because most service work was performed with the chassis inverted. This is probably true as far as actual repairs are concerned, but what about preliminary testing in the customer's home and even on the bench? In other words, you are first supposed to use the cold-chisel, hammer and monkey-wrench, and then make your preliminary tests so that you can inform your customer why his radio does not sing anymore... and the probable extent his budget is going into the red.

Space does not permit me to go into detail as to the full extent of the damage. Suffice it to say that it will produce no end of confusion and knock into the proverbial "cocked hat" the present plug-and-adapter arrangement. For instance, under the old system the usual K prong of a seven-prong plug was connected to a certain point designated by the number 5. When you used a 7-5 adapter the K prong still came up as No. 5. If you attempt the same arrangement under the new system the usual K prong on the 7-5 adapter becomes No. 4 and comes up through circuit No. 5.

If the Service Man will sit down and study the situation over, he will realize what a beautiful trimming he and his test equipment have received.

It is indeed regrettable that no publication or organization has taken up the battle for the Service Man in this instance. The whole affair smacks of "cute politics" to satisfy the needs of some minority at the expense of the Service Man.

R. B. RITTER,  
4863 N. Woodburn St.,  
Milwaukee, Wis.

*(This is a matter which should not be taken lightly. May we have the viewpoints of others?—THE EDITOR.)*



Each Jefferson Transformer comes in individual labeled carton with instruction sheet prepared by Jefferson radio engineers.

# 4 Shielded Power Transformers Cover the Whole Field

Use SHIELDED transformers for replacement—the kind that best set builders use—that Underwriters' Laboratories require—that protect you.

4 Jefferson upright Shielded Power Transformers cover all replacement needs—from 4 to 5 tube midsets to the largest sets—including the increasingly popular 6.3 volt tubes. For use where space or other conditions make the use of shielded transformers impractical, there is a line of 3 unshielded, 3 semi-shielded Jefferson Power Transformers.

All Jefferson Transformers are conservatively rated. Thus you get, and can serve your customers with more transformer per dollar. They are safe and carry their rated load with very low heat rise, last longer, perform better. Load a Jefferson

and any other to their rated capacities and note the difference in heat rise.


Jefferson engineers have sat in the Councils of most of the country's best set builders. This experience dating back to the beginning of radio—is incorporated into all Jefferson products, makes them worthy of complete confidence.

Mail the coupon today for the new, free 59 Class B Amplifier diagram and complete information on Jefferson Radio Transformers.
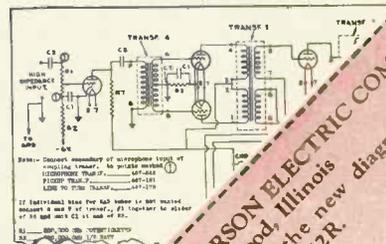
## Other Jefferson Radio Transformers

- Inputs
- Outputs
- Audios
- Microphone
- Filaments
- Line Chokes
- and Radio Fuses for every Receiver.

JEFFERSON ELECTRIC COMPANY  
Bellwood, (Suburb of Chicago), Illinois



JEFFERSON ELECTRIC COMPANY  
Bellwood, Illinois  
Please forward the new diagram and  copy of  
Catalog Sheet No. 342R.

Name \_\_\_\_\_ Address \_\_\_\_\_ City \_\_\_\_\_ State \_\_\_\_\_

**JEFFERSON**  
Radio Transformers

(B-135)

# SERVICEMEN:- *Your solution to* ALL WAVE PROBLEMS

The model No. 99 All-Wave Signal Generator is not a miracle instrument but a carefully designed and tested precision unit which has proven itself again and again with servicemen, service organizations, manufacturers, etc. This is true because of only for its appeal to the engineer but actual records have proven the following:



**MODEL NO. 99**  
Frequency range 100 to 22,000 KC.  
with 1,000 cycle modulation.

1. Saves hours of valuable time.
2. Analyzes the most difficult all-wave sets.
3. Gives you absolute confidence in any job.
4. Helps you build a satisfied clientele.
5. Leads to **BIGGER PROFITS** for you.
6. Gives the most value for the money. Net Dealer's Price .. **\$29.50**

Complete with Tubes, Batteries, Test Cords and Calibration Curves.

The model No. 99 has the following excellent characteristics: **DIRECT READING ON FUNDAMENTALS . . . NOT HARMONICS . . . FULL FREQUENCY COVERAGE . . . ABSOLUTE ATTENUATION AT HIGHEST FREQUENCIES . . . FREQUENCY STABILITY ASSURED . . . EXTREME ACCURACY . . . COMPACT . . . AN ABSOLUTE NECESSITY FOR MODERN ALL WAVE SET SERVICING!**

## MODEL NO. 77B SIGNAL GENERATOR

Frequency Range 100 to 3,000 KC.

The Model No. 77B broadcast and intermediate frequency oscillator is an inexpensive instrument of the same calibre as the Model No. 99.

The Model No. 77B is a compact, extremely handy instrument for general service work. The unit employs a type 30 and a type 1A6 tube. "A" and "B" batteries are self-contained within the Signal Generator. The instrument employs a unique circuit which generates both audio and radio frequencies independently. Through proper circuit arrangements, three separate and distinct types of signals may be obtained from the two sets of tip jacks on the front panel. They are: 1. Pure R.F. signals. 2. Pure audio signals. 3. Modulated R.F. signals. Modulation is fixed at 1,000 cycles.



**MODEL NO. 77B**  
Net Dealer's Price \$14.95  
F.O.B. New York

## SEND FOR COMPLETE TECHNICAL DATA ON THESE INSTRUMENTS

When ordering, please include cash deposit of 25%. If full amount is remitted with order, we will ship free of charge anywhere in the continental United States or Canada.

# WIRELESS EGERT ENGINEERING, INC.

179 VARICK STREET

NEW YORK, N. Y.

# THE MANUFACTURERS . . .

## NEW MULTITESTER

A new multitester, Model 403, which measures resistance values, voltages and currents on a 3/4-inch D'Arsonval moving coil type meter with a guaranteed accuracy of 2%, has just been announced by the Radio City Products Co., 48 West Broadway, New York, N. Y.



This instrument has three ohmmeter ranges, measuring all resistance values from 1/4 ohm up to 2,000,000 ohms. The three individual ranges are: 0-2,000-200,000-2,000,000 ohms. The instrument is entirely complete, compact and self contained; and it does not require additional batteries.

The voltmeter has a sensitivity of 2,000 ohms per volt for the four ranges. These ranges are: 0-5, 0-50, 0-250 and 0-750.


Two current scales are provided: First, 0-50 milliamperes for accurate measurement in radio circuits, and second, 0-500 microamperes for measuring very small currents.

An automatic selector switch turns to any desired range and circuit. Switch positions are etched directly on the panel. Tapered-compensator for battery voltage gives smooth zero adjustment on all ohmmeter ranges. Complete in compact case with all batteries ready to use. The unit weighs 6 pounds.
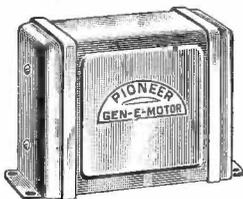
## COMPACT MODEL GEN-E-MOTOR

The Pioneer Gen-E-Motor Corp. of 644 W. Superior St., Chicago, Illinois, has just announced the new Model JW Gen-E-Motor.

This unit has been designed to replace the vibrator power supply in all popular auto-radio sets. It will fit within the housing of over twenty receivers, including the Majestic, General Electric, RCA, Motorola, Bosch, Audiola, and many others, it is stated.



Only three connections to the set are required. No other changes must be made, and the set operates in exactly the same manner as with the vibrator power supply.

The Model JW has a full ball-bearing mounted armature and is unconditionally guaranteed for one year. There are no adjustments to make. Enough lubricant for life is sealed in the bearings.

## NEW HAMMARLUND COIL FORMS

A new dielectric compound, known as XP-53, is used in the new low-priced, short-wave coil forms that have just been released by the Hammarlund Manufacturing Company, 424 West 33rd Street, New York City.

This insulating material is a light tan color, or natural, thus eliminating the usual color losses. Its other low-loss properties, plus the unique design of the forms, create an exceptionally effective unit. The forms are groove ribbed for air spacing of windings. There are also flange grips, and neat meter-index inserts, for wavelength indications. Another clever feature of the form is a threaded shelf molded inside, to permit mounting of a trimming or padding condenser, for tuning the coil to a fixed frequency, or for band-spread arrangement.

The coil forms come with 4, 5 or 6 prongs.

Complete kits of coils already wound to cover the entire range of frequency from 17 to 560 meters are also available, using the XP-53 material. One, known as the SWK-4, contains four, 4 prong, 2 winding coils, with a range of from 17 to 270 meters. Another, known as the SWK-6 kit, consists of four, 6 prong, 3 winding



coils, also with a range of from 17 to 270 meters. Then, there is the BCC-4, which is a 4 prong, 2 winding coil, for the broadcast band, or from 250 to 560 meters, and last, there is one more broadcast coil, known as BCC-6, which is a 6 prong, 3 winding affair, also covering the 250 to 560 meter band. The secondaries of the 17 to 41 and 33 to 75 meter coils are of heavy silver plated wire, affording minimum skin resistance losses. The secondaries of the other coils are of heavy gauge enameled copper wire. The broadcast coils are bank wound litz.

## REPLACEMENT CONDENSERS

A complete assortment of exact duplicate electrolytic replacement condensers for ac, dc midget radios, all-wave supers, and auto radios are available from the Tobe Deutschmann Corporation.

These replacement condensers, it is stated, are exact to the originals used by the set manufacturers in all respects, including physical dimensions, color and length of leads, and mounting arrangements, except, where space allows, the peak voltage rating of each section of the condenser has been raised.

A handy reference pocket card listing this complete assortment of condensers is available upon request to the Condenser Division of the Tobe Deutschmann Corporation, Canton, Mass.

## IDEAL TEST PRODS

The Ideal Test Prod, a new development of the Maywood Radio-Electric Manufacturing Co., 3533 East Slauson Ave., Maywood, Calif., permits the user to test in tube sockets or other small openings.

A phonograph needle for piercing insulation, paint, and the like, is sweated into the shank and may thus be replaced in a short time by application of heat. This procedure, in addition, does away with the usual cumbersome chuck.

Tinsel cord may be used with the prods without any soldering, and they state that there is no danger of its pulling out, though it is easily replaceable . . . the standard cord tips being held securely by the split-threaded section.


While tinsel cords are a part of the regular equipment, stranded wire cords will be furnished if desired.

These prods are furnished complete with 5-foot cords, with either spade or phone tips.

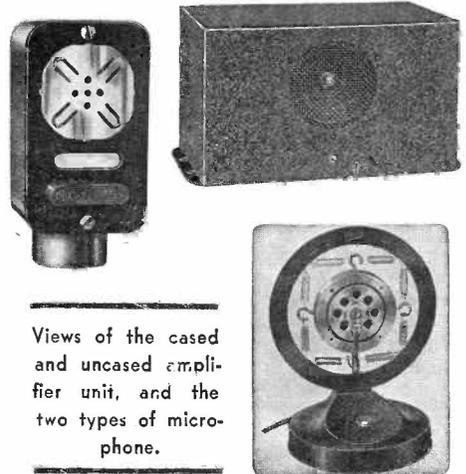
## ORD-O-PAM SPEECH SYSTEM

The S. H. Couch Company, Inc., North Quincy, Mass., have announced a one-way speech-amplifying system that may be heard a distance of 25 to 100 feet from the speaker, according to the noise level of the premises.

The system is comprised of a speaker-amplifier unit, microphone with flexible cable and terminal box, six-foot flexible cable and attachment plug for power supply, and signal-back pear-type push button attached to flexible cord.



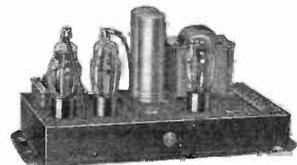Views of the cased and uncased amplifier unit, and the two types of microphone.




Three different type microphones are available, namely, counter or wall type, desk type, and handset type.

The speaker-amplifier unit may be obtained for ac, dc, or universal operation, and measures 13" x 6 7/8" x 8 1/16". The unit is mounted in an all-steel case with a black crystalline finish and comes equipped with tubes.


(Continued on page 354)

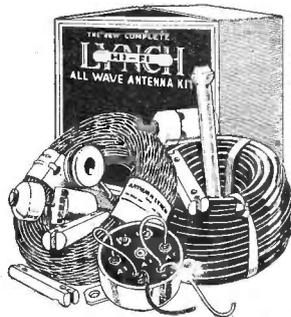**LYNCH ALL-WAVE ANTENNA KITS**

Arthur H. Lynch, Inc., 227 Fulton St., New York, N. Y., have placed on the market a new all-wave antenna coupling system, of the doublet type, and a complete all-wave antenna system. Both are available in kit form.



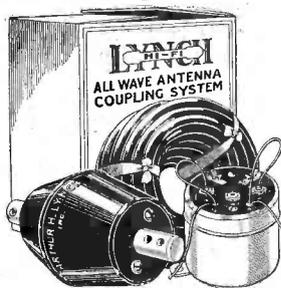The all-wave antenna system, known as the Lynch "HI-FI" (Hi-Fidelity) All-Wave Antenna System, is a complete kit, containing 125 feet of "HI-MHO" heavy wire, 35 feet of "Giant Killer" cable, a "HI-FI" Receiver Coupler, a porcelain lead-in tube, a 3-inch standoff insulator, 3 Navy-type antenna insulators and 2 split knobs.



The coupling system, known as the Lynch "HI-FI" All-Wave Antenna Coupling System, is for use with a doublet antenna where space is not large enough to use the All-Wave Antenna System. The impedance-matching device for the center of the doublet is said to make the antenna efficient on all waves. The kit contains a Duplex Antenna Coupler, a "HI-FI" Receiver Coupler, and fifty feet of "Giant Killer" cable.

**NEW AUTOGRAPHIC REGISTER**

Adapted particularly for radio distributors and dealers is a new style autographic register, announced by The Standard Register Company of Dayton, Ohio. No larger than an ordinary sales pad, this type register features portability and may be used for issuing sales records, estimates for repairs, delivery tickets, charge orders, and other records.

The newly designed register is known as the "Aristocrat". Made of duraluminum and sturdy constructed, it is designed for use where sales pads are now used and where the conventional type autographic register is too large.

Announcement has been made that the "Aristocrat" will be available in ten form sizes and two depths, the smaller one accommodating 150 forms while the master

model will handle 300 forms at one loading. The Master model is for use primarily where additional capacity is desired but where the conventional register is too large. A handy filing drawer is optional equipment on all models.

Additional information, descriptive literature and samples of forms adapted for use in this new register may be obtained without charge or obligation by writing to The Standard Register Company, Dayton, Ohio.

**ALDEN SHORT AND LEAKAGE TESTER**

The No. 9SC Tube Short and Leakage Tester, manufactured by the Alden Products Co., 715 Center St., Brockton, Mass., and shown in the accompanying illustration, accommodates all four, five, six, large seven and small seven prong tubes in two composite sockets. An insulated control-grid cap and lead are provided for con-



nection to all tube caps. A special neon tube indicates leakages up to 1,000,000 ohms as well as dead shorts. The tester, they state, is particularly useful in detecting cathode to heater shorts which cannot be tested in the average tube checker.

An additional feature is a pair of jacks which permit general continuity testing when used with a pair of test leads. The circuit is so designed that either test lead may be grounded without causing a short circuit. A single screw serves to mount the tester in any position, and five feet of cord is provided with a plug which may be plugged into either ac or dc.

**HICKOK MULTI-SELECTESTER**

The Hickok SG-4800-B Radio Tester was designed primarily to make available to the Service Man, in one convenient instrument, most of the fundamental test instruments used in locating electrical troubles in radio apparatus. It is a generalized instrument which is equally well adapted to the older method of trouble analysis by voltage and current and to the newer point-to-point analysis by resistance.

The meter used is a special D'Arsonval movement. The instrument is housed in a bakelite case with a flange diameter of 4¼ inches and a scale length of 27½ inches. The movement has a high torque and is well damped.

This one meter with its associated circuits gives the equivalent of 5 separate test instruments. The following is a brief description of these separate functions:

**DC Voltmeter:** This instrument has a sensitivity of 1,000 ohms per volt. The voltage ranges available are: 0-10, 0-50, 0-250, 0-500, and 0-1,000 volts.

**DC Milliammeter:** The dc milliammeter provides, in addition to a 0-1 milliamperere range, ranges of 0-10, 0-50 and 0-250 milliamperes. These ranges were chosen so

their scales would coincide with the dc voltage scales and make possible the reading of all dc quantities with one uniformly divided scale.

**AC Voltmeter:** The ac voltmeter in this tester has a sensitivity of 1,000 ohms per volt for all ranges. It uses a copper-oxide rectifier type circuit, the ranges available being the same as for the dc voltmeter, namely: 0-10, 0-50, 0-250, 0-500, and 0-1,000 volts.

**Output Meter:** The common terminal of the ac voltmeter is wired to a pinjack marked "Output" in series with which is a blocking condenser. When this "Output" pin-jack is used, together with any of the ac voltage jacks, a multi-range output meter is available for measuring audio-output voltages either across voice coils, magnetic speakers, or direct from plate of tube to ground.


**AC Compensator:** The ac compensator is a system incorporating a compensator resistance spool which adjusts the sensitivity of the meter movement to the efficiency of the rectifier. This resistance not only provides a convenient means of adjustment of the ac voltmeter to exactly 1,000 ohms per volt in production, but also provides a means of easily restoring the calibration should the efficiency of the rectifier be lowered by accidental overload in service.

**Ohmmeter:** The resistance meter circuit in the 4800-B is a standard direct-reading, battery-operated circuit. Four ranges are provided, giving overlapping coverage of all resistance values from 0.5 ohm to 10 megohms. The lowest scale covers resistance from 0.5 to 10,000 ohms. Other scales use the same calibration, multiplying by 10, 100, and 1,000. Batteries for ranges up to one megohm are contained in the tester. External 90 volts is necessary to use the 10-megohm range.

All of these various metering circuits are controlled by one rotary switch. This switch located at the lower left of the panel in the accompanying illustration has a clearly marked plate, indicating positions for the various circuits. The wiring is of such design that the meter will not be damaged should the switch be accidentally set on the wrong point.


**VAN METER DIALS**

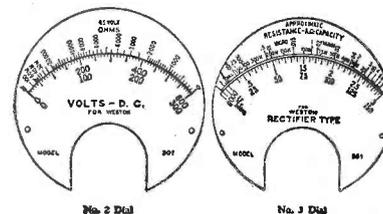D. L. Van Leuven, 410 E. 15th Street, New York, N. Y., has made available etched silver-metal meter dials for the Weston 301 and Jewell 88.



Dial No. 2, shown in the left part of the accompanying illustration, is for 1 mil. dc. This unit has two scale readings and an ohm scale of 0 to 100,000 using a 4.5-volt battery.

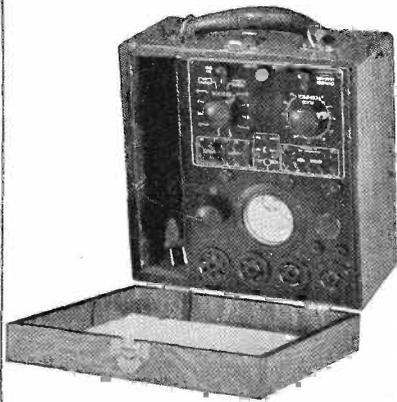Dial No. 3, shown in the right half of the illustration, is for 1 mil. ac rectified. This dial has two scales for ac volts, a 5,000 to 1-megohm ac ohms scale, and capacity range of .004 to 7 mfd.



**Serviceman's  
Portable  
Tube  
Checker**  
and VOLT-OHMMETER  
Model 427

Direct Reading—Checks Every Type of Tube—Also Has Neon Shorts Test and Cathode Leakage Test.

Has Meter Ranges for DC Volts—Milliamperes and Ohms. See Specifications.

Case of Solid Oak, Hand Finished. Dimensions Approx. 10" by 9" by 5".

**Specifications on Test Meter Ranges**

Ohms Range—Dial Calibrated Direct . . . No chart required. Reads 0-20,000 ohms / 0-200,000 ohms. Readings as low as 10 ohms easily made. Compensator provided to correct for battery voltage errors.

D.C. Volts Ranges . . . Scales of 0-10, 0-100, 0-300 volts D.C. (200 ohms per volt).

D.C. Milliamperes . . . Scales of 0-10, 0-100, 0-300 D.C. M.A.

Selection of Ranges . . . All scales selected by main switch—very simple and rapid to use.

**Net Price \$28.40**

**The Jackson Electrical Instrument Co.**  
DAYTON, OHIO


THE JACKSON ELECTRICAL INSTRUMENT CO.  
Dayton, Ohio.

Please send latest circular describing testing equipment.

Name .....  
Address .....

**JOBBER'S  
ATTENTION  
HAVE YOU STOCK  
FOR HOME RADIO  
SET INSTALLATIONS ?**

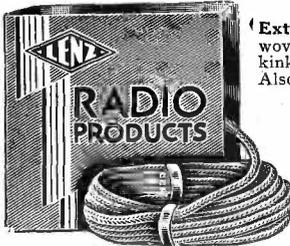Here are three essential items that insure better radio reception in the home (many others available—write for illustrated catalog No. 20 today!)



**INDOOR AERIAL**  
Extremely Flexible conductor, tightly woven brown cotton braid. Will not kink and can be easily concealed. Also suitable for loop aerials.

**BLACK POLISHED RUBBER COVERED LEAD-IN AND GROUND WIRE**

Conductor consists of stranded clean tinned copper wire. Insulation—high quality live rubber easily stripped. Put up in attractive CARTONS and on Spools.

**SHIELDED LEAD-IN AND GROUND WIRE**  
Consists of FLEXIBLE tinned copper conductors, heavy wall of FREE STRIP rubber and CLOSELY WOVEN tinned copper shield. Shield can be grounded, reducing interference, resulting in better reception.

**LENZ ELECTRIC MFG. CO.**

1751 No. Western Avenue Chicago, Ill.

Please send without obligation your new Lenz Radio Products Catalog No. 20.

NAME .....  
ADDRESS .....  
CITY ..... STATE .....


**NEW POLICY**

FOR

**Dealers and Distributors**

LIMITED TERRITORY AVAILABLE

WRITE FOR DISCOUNTS

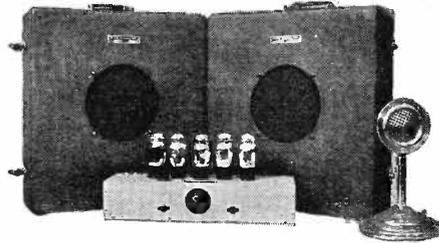

Portable address systems for inside and outside use - \$87.50 and up


Crystal Microphones. P.M. Dynamic Speakers, Amplifiers and Control Equipment for Rack and Panel Mounting. Precision Equipment for special uses. Special Systems for Dance Bands, Funeral Parlors. School and Hospital, Sound and Centralized Radio. Hotel Systems. Hearing Aids. Turntables. Transformers. Crystal Pick-ups. High Fidelity Units.

**Sound Systems, Inc.**

1311 TERMINAL TOWER

CLEVELAND, OHIO

**OHMITE**  
"DIVIDOHM"  
RESISTORS

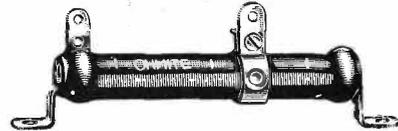

DIVIDOHM Resistors are ideal replacement units for service work; they are now made in five different sizes and in over a hundred resistance values. Protected by vitreous enamel, DIVIDOHMS insure your repair jobs and eliminate return calls. Patented percentage-of-resistance scale makes it possible to set as many adjustable lugs as needed at the proper points without troublesome meter manipulations. See Catalog No. 10 for complete listing of these handy units. Use the coupon below.

**OHMITE**

MANUFACTURING COMPANY

627 N. Albany Ave., Chicago, Ill.

Please send me a copy of your Catalog No. 10 and the name of my nearest OHMITE distributor.

NAME .....  
ADDRESS .....  
CITY ..... STATE .....

KENYON


PRODUCTS
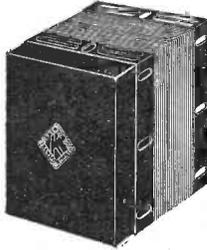
# So Handy!



Only five types. Yet KENYON replacement power transformers service over 95% of all standard sets. Only one type audio transformer and one type choke service all sets. Which all means minimum stock . . . maximum convenience . . . real profits.

Produced in real quantities, KENYON audio transformer and choke replacement units are exceptional value. Well built . . . and built to last. Service any set. Satisfactory performance assured. Universal mounting brackets facilitate installation. And only two types to carry in stock.



Nothing skimped in KENYON power transformer replacements. Sturdy. Generous proportions. Neat appearance. Novel mounting brackets permit mounting in any position and wide range of mounting hole spacings. Transformer voltage data stamped on lugs, eliminates errors. After soldering connections, insulating covers slip over ends. Live contacts covered.

And in addition to replacement units, don't forget that KENYON offers all types of transformers and chokes and other iron-core devices for new assemblies of all kinds.

## SERVICE DATA FREE

Get your copy of the handy transformer replacement chart indicating correct replacement for any type of standard set. Also latest KENYON catalog.



**KENYON  
TRANSFORMER CO., INC.**  
840 Barry Street New York City



*"E. H. Rietzke  
SPEAKING!"*



Mr. E. H. Rietzke, President of CREI and originator of the first thorough course in Practical Radio Engineering.

## Service Men! The PENCIL is as Important to You as Your PLIERS!

This is the same course in home-study form that many men have left their homes and businesses to study in our Residence School. If these men have enough faith in CREI to take a "year off" to study . . . then you surely can afford the few dollars and hours it takes to benefit by this thorough engineering course.

◆ **Be A Service ENGINEER . . . Not  
A Service "Mechanic"!** ◆

No matter how much business improves this Winter you can still handle only a limited number of jobs . . . there are only 24 hours in a day. If you are going to handle *more* and *better* jobs, it is up to you to increase your efficiency and knowledge! Then, you will not only be making more money, but will be sufficiently well trained to take advantage of the *big* opportunities that Radio offers the *technically trained* man!

Find Out Detail! Write today for full information about the CREI courses and how you can easily pay for them!

**Write Today for Free 40-Page Catalog!**



**Capitol Radio Engineering Institute**  
Dept. S-9  
14th & Park Rd., N.W., WASHINGTON, D.C.



**Radio Engineering**—Covering the design, production, engineering and test of Radio Receivers, Tubes, Parts, Amplifiers, Recording and Sound Projection Equipment.

Subscription, \$2.00 Yearly  
(Foreign \$3.00)

**BRYAN DAVIS PUBLISHING CO., Inc.**  
19 East 47th Street, New York City



**Communication and Broadcast Engineering**—Covering Radio Communication, Broadcasting, Police, Marine and Aeronautical Radio, Telephony and Telegraphy, Facsimile and Television.

Subscription, \$3.00 Yearly  
(Foreign \$4.00)

## How Do You Do It?

How do you solve the many servicing problems with which you have to contend . . . what special kinks have you worked out which help you in servicing receivers . . . have you developed shortcut schemes for testing, or built test devices that do the work better and faster?

No matter what the scheme or the device, there are many, many Service Men who would like to know the how's and why's—just as you would like to know about the schemes and devices employed by others.

## SERVICE WANTS TO KNOW!

If you have clever ideas and clever devices, we want to know about 'em as much as do our readers. Regular space rates are paid for all material accepted for publication.

All you have to do is give us the outstanding points, and a rough pencil sketch of the device if it happens to be such—and we will do the rest.

Come on, now, and kick in. Write up those ideas now and send them in to the . . .

## ON THE JOB DEPARTMENT

### BULLETIN NO. 106


Describes the Ward Leonard Remote Control Relays with their various contact combinations.

### BULLETIN NO. 507B

Is about Ward Leonard Underload and Overload Relays for tube protection.
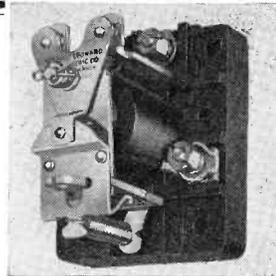
### BULLETIN NO. 507A

On the subject of Ward Leonard Vitrohm Resistors. You should know them.



## SERVICE MEN are interested in MIDGET RELAYS


Sound Systems, short wave sets and remote control all require dependable relays. Experienced Service Men place the same confidence in Ward Leonard Midget Relays as they do in Ward Leonard Resistors. If you do not know about these relays, their ratings and prices, fill in and mail the coupon below.

## WARD LEONARD RELAYS—RESISTORS—RHEOSTATS

WARD LEONARD ELECTRIC CO.  
MOUNT VERNON, N. Y.

Please send me FREE Bulletin Nos. . . . .  
Name . . . . .  
Street . . . . .  
City and State . . . . .  
Jobber's Name . . . . . S

# A "SHOT IN THE ARM"

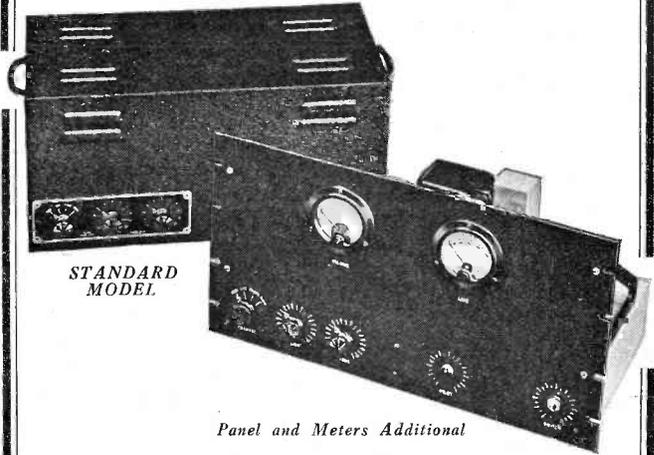

STANDARD  
MODEL

Panel and Meters Additional

### THE 60A AMPLIFIER

Uses 2-53s, 2-45s (Class "AB" Fixed Bias output, 18 Watts.)

Integral Power Supply 83 and 45 Rectifier.

Input for 500 ohm line—crystal mike—phono pickup and tuner, with built in selector switch, gain and tone controls.

Output—2, 4, 8, and 500 ohm lines.

Essentially flat curve—40 to 12,000 cycles.

The 60A is guaranteed (under normal usage) against electrical or mechanical defects for ONE YEAR.

ALAN keeps the wheels of industry turning during the "dog days" by forgetting profits.

A stock of parts acquired before present high prices became effective enables us to quote an extremely low price on this FINE amplifier. YOU COULD NOT BUY THE PARTS ALONE FOR THE SAME MONEY.

This unit lists at \$90.00, and has been sold by us for \$42.50. In order that our engineering and production staffs may be kept busy this month.

YOUR PRICE (less tubes).

**\$34.50**

A technical bulletin will be sent upon request. WRITE FOR IT.

**ALAN RADIO CORP.**  
83P CORTLANDT ST., NEW YORK, N. Y.  
Western Branch: 1028 So. Olive St., Los Angeles, Calif.

# Curtis Electrolytic CONDENSERS

Look good — are good.  
Made in any size, style and shape.



CURTIS CONDENSER CORPORATION  
3601 W. 140th Street, CLEVELAND, OHIO

## A Savings For Parts Distributors!

You can get immediate shipment of radio replacement parts, and short wave parts from *one* source, at prices

**AS LOW OR LOWER**  
than you can obtain elsewhere.


This is because we are now supplying 80% of the parts carried by several large chain stores, and therefore carry large stocks.

Send for latest price list and give us a trial.

## BOND RADIO CO.

11700 LIVERNOIS STREET DETROIT, MICH.

Don't Miss It . . . .

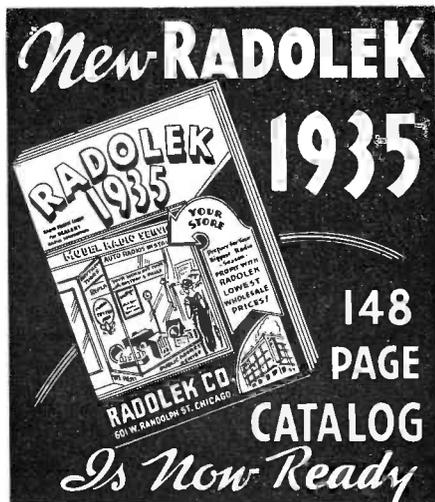


If you've changed your address since receiving our 1933 Catalog, or if you have not received a catalog from Radolek recently, send us your business card or letter-head immediately.

THE RADOLEK CO.

601-603 W. Randolph Street  
CHICAGO

## SERVICEMEN!

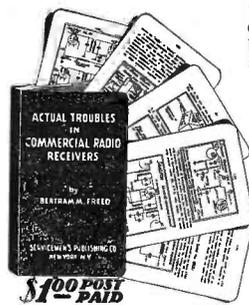

The book, "ACTUAL TROUBLES in COMMERCIAL RADIO RECEIVERS," by Bertram M. Freed, can be as valuable to you as your set analyzer.

Its 192 pages are chock full of information on faults that repeatedly turn up, as shown in an examination of many thousands of service-job reports. Over 500 Type Sets Treated with 47 Diagrams.

Includes Free Supplement

Look this book over! Your local supply house can fill your order (any mail-order house can supply this book even though it is not listed in their present catalog), or, send \$1.00 direct to:

SERVICEMEN'S PUB. CO., 136 SR Liberty St., N.Y.C.

## VISIT THE SERVICE BOOTH

AT THE  
OCTOBER

## I. R. S. M. CONVENTION

October 19 to 21  
HOTEL PENNSYLVANIA, NEW YORK

### INDEX TO ADVERTISERS

Aerovox Corp.....	349	International Resistance Co... 345	Radio City Products Co..... 359
Alan Radio Corp.....	357	Jackson Elec. Instrument Co.. 355	Radio Products Co., The..... 347
Allied Radio Corp.....	359	Jefferson Electric Co..... 351	Radolek Co., The..... 358
Bond Radio Co.....	358	Kenyon Transformer Co., Inc. 356	Rider, John F..... 341-349
Burgess Battery Co.....	343	Lenz Elec. Mfg. Co..... 355	Servicemen's Publishing Co.... 358
Capitol Radio Eng. Inst.....	356	Leotone Radio Co..... 359	Solar Mfg. Corp..... 359
Central Radio Labs.....	360	Mallory & Co., P. R..... 324-326	Sound Systems, Inc..... 355
Clarostat Mfg. Co., Inc.....	321	National Union Radio Corp. of N. Y..... 347	Standard Transformer Corp.
Cornell-Dubilier Corp.....	360	Ohio Carbon Co., The..... 323	Inside Front Cover
Couch Co., Inc., S. H.....	359	Ohmite Mfg. Co..... 355	Tobe Deutschmann Corp.
Curtis Condenser Corp.....	358	RCA Institutes, Inc..... 359	345-347-349
Freed's Radio Co.....	359	RCA Radiotron Co., Inc.	Ward Leonard, Elec. Co..... 357
General Transformer Corp.... 347		Fourth Cover	Weston Electrical Instrument Corp. .... 319
Halldorson Co., The..... 345		Radiart Corp., The..... 359	Wholesale Radio Service Co., Inc. .... Third Cover
Hygrade Sylvania Corp..... 339			Wireless Egert Eng. Inst..... 352
Institute of Radio Service Men 325			Yaxley Mfg. Co., Inc..... 326


Insist on this Trade Mark

**Radiart**  
TRADE MARK

Exact Duplicate Replacement  
**VIBRATORS FOR AUTO RADIOS**

Every electric auto radio in use means a vibrator replacement eventually. Only with Radiart can you cash in on this market completely. Only Radiart makes a COMPLETE EXACT DUPLICATE line. Only Radiart has the experience of furnishing initial equipment to more than 70% of the auto set manufacturers. Look for the orange and black label on the box and on the vibrator, if it isn't there it isn't a genuine Radiart vibrator. In making replacements choose the vibrator the set manufacturers themselves prefer—you will be sure of a satisfied customer. Available at all good jobbers. Write for catalog sheet.

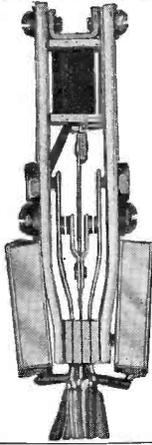**THE RADIART CORP.**  
13229 Shaw Ave. Cleveland, O.



**YOU—IN or OUT?**

Many good service men are actually out of business, but won't admit it! They're stale—inert to the modern method of selling radio service at professional prices. Guess-work-mechanics have treated set-owners so badly, that you also are mistrusted! BUT—today progressive radio men everywhere, Chuckkerize the customer to inspire confidence. They isolate radio faults quickly with a Chuckker compiled, cross-indexed trouble-chart. Then they explain, to the set-owner, the Chuckker repair-pricer feature which publishes the fee for that repair job. They must use a Chuckker because it is professional, looks official, and gets them that job at a price based upon a \$1.50 hourly labor rate, plus list-priced parts. Eliminate guesswork in What is Wrong and What to Charge! A Chuckker will keep you in business! We'll rush you a Chuckker postpaid for a \$1 bill.

**SEND  
DOLLAR  
BILL NOW!**

**FREED'S RADIO CO. Publishing Division S.**  
5053 Baltimore Avenue Philadelphia, Pa.

**SOUND PAM SYSTEMS**

Improved **Samson**

BASE TYPE AMPLIFIERS  
RACK AND PANEL EQUIPMENT  
ORD-O-PAM RESTAURANT ORDER SYSTEM  
PAM-O-GRAPH RECORDING SETS  
MICROPHONES (Carbon, Condenser, Crystal)

—Manufacturers—  
**S. H. COUCH COMPANY, INC.**

Established 1894  
NORTH QUINCY, MASS.  
Sales Offices in Principal Cities. WRITE FOR BULLETIN PI-10



**CHEER UP!!**

You can always find  
the part you need at

**LEOTONE**

Prompt — Quick — Accurate  
Service

Largest assortment of radio parts in town. Speaker manufacturers since 1921—P.A. specialist. Write us for literature on our S.W. receivers.

**LEOTONE RADIO CO.**  
63 DEY STREET NEW YORK, N. Y.

**SOLAR**

WET AND DRY ELECTROLYTIC  
PAPER AND MICA CONDENSERS

RECOGNIZED FOR  
SUPERIOR QUALITY  
IN ALL CLIMATES  
THE WORLD OVER

SOLD BY LEADING  
JOBBER'S EVERYWHERE

**SOLAR MFG. CORP.**  
599 BROADWAY  
NEW YORK

**BEST BY TEST!**  
ASK FOR  
CATALOG  
OF EXTREMELY  
COMPACT TYPES  
HANDY FOR SERVICE

**When Choosing  
a Radio School**

Consider the advantages  
afforded by the long-  
established RCA Institutes

The beginner or the experienced man who seeks instruction in any branch of radio will find courses designed for him . . . either at the resident schools in New York and Chicago or in the RCA Institutes Extension Courses for Home Study.

Following Units Especially Recommended to Readers of "Service":  
Elementary Radio Mathematics—Advanced Radio Mathematics—Advanced Radio Servicing—Sound Amplification

Resident schools are fully equipped, conveniently located, low weekly tuition rates. Home Study Courses are on the "no obligation" plan. Free post-graduate practical training period at a resident school.



Catalog on Request  
**RCA INSTITUTES, Inc.**  
Dept. SV-34

75 Varick Street, New York  
1154 Merchandise Mart, Chicago

**Better TEST EQUIPMENT!**

**KIT FORM Saves Money**



"304" KIT, \$15.65  
Complete, \$19.95

Write Dept. S-9 for FREE Data Sheets

**RADIO CITY PRODUCTS**  
48 West Broadway, New York City

**NEW TUBE  
TESTER "304"**  
Sensational success!  
Only tester with  
NEON-LIGHT leakage  
tests up to million  
ohms. "Good-  
Bad" meter. Years  
ahead in quality and  
usefulness.

**MULTITESTER "403"**  
Popular, compact model  
for auto and general test-  
ing. Equipped for all  
future needs. 3-range  
ohmmeter, 4-range volt-  
meter, microammeter.



"403" KIT, \$10.95  
Complete, \$14.95

**NEW**

**SERVICE GUIDE FREE**

A New ALLIED Catalog for 1935, packed with values for every Radio Serviceman, will be ready shortly. Reserve your copy at once and meet your autumn and winter business with confidence. You'll be able to give better service with equipment from ALLIED, and your margins of profit will be bigger than ever. Over 100 pages of highest quality standard radio equipment in the new 1935 ALLIED book! Thousands of exact duplicate parts—all leading makes of test instruments. Before you buy, consult your new 1935 ALLIED Catalog. It leads the field.

**ALLIED RADIO CORPORATION**


833 W. JACKSON BLVD., CHICAGO. Dept. N.

Gentlemen:  
Send me FREE your New 1935 Radio Catalog which is packed with thousands of highest quality radio parts selected especially for the Radio Serviceman.

Name .....

Address .....

# Gang-Way!

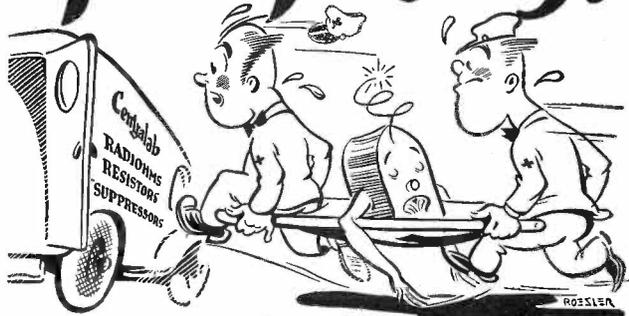

here's Real relief for run-down Radios!



The new patented RADIOHM



The sturdy fixed RESISTOR




The efficient MOTOR RADIO SUPPRESSOR

When the frantic parents of a once-healthy radio call on you to revive their loved one . . . see that your stock of life-giving CENTRAL-LAB replacement parts is in order.

For D. R.'s\* all over the country are doing heroic work with Centralab Radiohms, Resistors and Suppressors.

Experimenters too are using Centralab parts for better results.

\*D. R. Doctor of Radio.

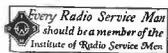

**Centralab**  
Central Radio Laboratories  
MILWAUKEE

**C-D**  
condensers

**IF**

24 Years of Experience  
24 Years of Specialization  
24 Years of Leadership  
24 Years of Fair Dealing

mean anything to you,  
they mean one thing—

## CORNELL-DUBILIER

Affords You the Most Value for Your Money and the Best Results in Your Work!

### Announcing

#### TYPE PE, PAPER CONDENSERS

##### SIMULATE ELECTROLYTICS IN APPEARANCE

Many service men actually prefer a paper dielectric bypass or filter condenser. This NEW line is brought out with the specific idea of supplying the wide demand for CORNELL-DUBILIER condensers in this particular style. Readily interchanged with electrolytic units.

450 V. D.C. Working—Cardboard Container Condensers—600 V. D.C. Peak, with wire leads—Duals, separate leads, no common

TYPE NO.	REPLACEMENT CAP. MFD.	LIST PRICE	YOUR COST
PE-C4002	2	\$0.75	\$0.45
PE-C4004	4	.90	.54
PE-C4008	8	1.15	.69
PE-C4404	4-4	1.50	.90
PE-C4408	4-8	1.70	1.02
PE-C4808	8-8	1.90	1.14

600 V. D.C. Working—Cardboard Container Condensers—800 V. D.C. Peak, with wire leads—Duals, separate leads, no common

PE-C6002	2	1.00	.60
PE-C6004	4	1.20	.72
PE-C6008	8	1.60	.96
PE-C6404	4-4	2.00	1.20
PE-C6408	4-8	2.35	1.41
PE-C6808	8-8	2.65	1.59

600 V. D.C. Working—Metal Container Condensers—800 V. D.C. Peak. Type PE-B, wire leads, inverted mounting; duals, separate leads, no common. Type PE-A, lug terminals, upright mounting, insulated common negative, with provision to ground common negative by means of attached lug.

PE-B6004	4	1.35	.81
PE-B6008	8	1.75	1.05
PE-B6404	4-4	2.25	1.35
PE-B6808	8-8	2.80	1.68
PE-A6515	5-15	4.50	2.70
PE-A6444	4-4-4	3.50	2.10
PE-A6888	8-8-8	4.90	2.94
PE-A6918	9-9-18	6.50	3.90



Cornell-Dubilier Corporation

Jobbers' Division  
4375 Bronx Blvd.  
New York City

# FREE

THE BIGGEST-LATEST-MOST COMPLETE  
1935 RADIO CATALOG

192 PAGES OF RADIO  
OF BARGAINS

OVER 50,000 ITEMS

BIG S.W. SECTION

GREAT P.A. DEPARTMENT

NEW REFRIGERATION  
DEPARTMENT

ALL NATIONALLY KNOWN  
LINES



## A Bargain Book of 192 Pages that will SAVE YOU MONEY

THIS amazing new 1935 Radio Catalog is the last word . . . the greatest Bargain Book of Radio ever published by us or any other company. There are more pages, more items listed, more nationally known lines, more Specialized Departments. Over 50,000 items have been assembled in this great 192 page book to make it the outstanding book of the Radio Industry.

There is a Special Department on the latest Broadcast and All Wave Receivers from 2 to 10 tubes. You'll find an entirely new Department on REFRIGERATION PARTS and accessories—a new money-making field for Servicemen. A whole section on PUBLIC ADDRESS is the most complete and all-inclusive thing of its kind.


Then there is our matchless SPECIALIZED SHORT WAVE DEPARTMENT which in itself is a complete catalog listing everything the Ham, Brasspounder and Experimenter will ever need. Sets, Kits, Transceivers, Pre-selectors, Converters, as well as other Short Wave parts and accessories. Practically every nationally known manufacturer is listed here. The complete list reads like a Who's Who of Radio . . . and everything is at LOWEST WHOLESALE PRICES!

For 13 years the "WHOLESALE" Catalog has been the Servicemen's "Bible." Today the greatest Radio Catalog ever printed—backed by the resources of the greatest organization of its kind in the world—is yours for the asking. *Get yours today!*



Build it yourself! This revolutionary sensation in the Short Wave Field was designed by 8 leading manufacturers. All of their experience in designing and manufacturing has gone to make this a Superhet that outperforms anything of its kind! Features that guarantee good foreign reception include: Continuous Band Spread, 10 to 500 Meter Tuning Range, 6 Tubes, Pre-adjusted Coils, etc.

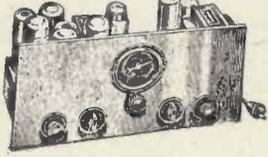Be sure to write for complete circuit diagrams, parts list and data sheet . . . FREE!



### Lafayette "19" TRANSCEIVER FOR 5 M. COMMUNICATION.

A new Transceiver that really gets out and lets you do things. One of the most powerful portable units ever offered in this class. Using a type 19 tube in a p.p. oscillator, it has a power output of approx. 2 watts (about 10 times the power of units in this class). More than enough output is obtained for speaker operation if desired.

The Lafayette "30" is similar to above except that it uses a type 30 tube as the oscillator for transmitting with type 33 pentode as modulator providing a strong signal that is clearly understood.

Both models were developed after research in both laboratory and field. Entirely self-contained. Weight but 26 lbs. complete with batteries. Write for complete information.



# WHOLESALE RADIO SERVICE CO.

Main Office and Warehouse  
100 SIXTH AVENUE • NEW YORK, N.Y.

Serving the South and Southwest  
430 W. PEACHTREE ST. N.W. - ATLANTA, GA.

Serving Northern New Jersey  
219 CENTRAL AVE. - NEWARK, N.J.

Wholesale Radio Service Co.  
100 Sixth Ave., Dept. 994  
New York, N. Y.

- Send me your new 1935 Catalog No. 56.
- Send me free data on the All Star Kit.
- Send me free details on the Lafayette Transceiver.

NAME .....

ADDRESS .....

CITY ..... STATE .....

