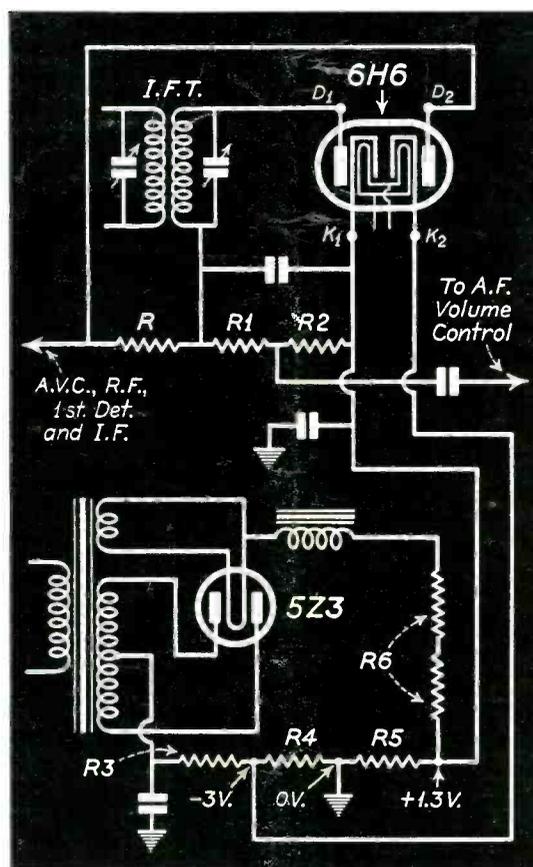


SERVICE

A MONTHLY DIGEST OF RADIO AND ALLIED MAINTENANCE




PER COPY
25 CENTS

Automatic Initial Bias Circuit
(See Page 439)

OCTOBER
1935


SERVICEMEN'S DOUBLE-HEADER

**POWER UNIT
EMERGENCY STOCK**

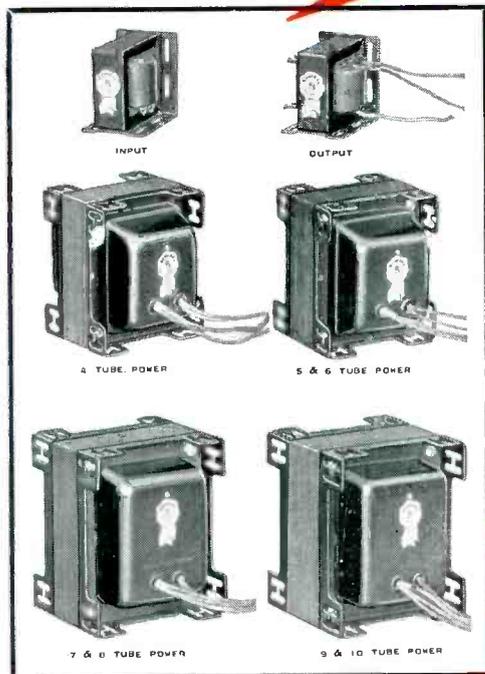

"Multi-Tap"
Reg. U. S. Pat. Off.
**POWER
TRANSFORMERS**
Patent
No. 1992415

**"STENTORIAN"
SOUND AMPLIFIER
NUCLEUS**

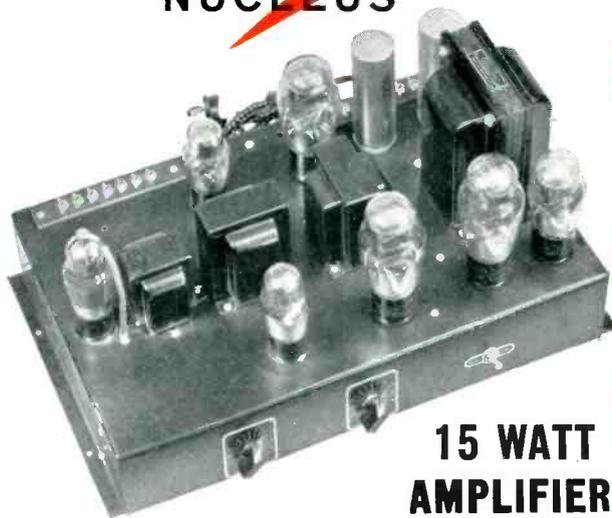

**15 WATT
AMPLIFIER**

Exact duplicates ELECTRICALLY Universally adaptable PHYSICALLY

REMEMBER! The Multi-tap Transformers are the modern service engineer's small-investment emergency stock!

Extra Windings are embodied on the coil, not always used, but very often needed—for instance, the extra 2.5 volt winding is essential for sets using 26 type tubes. The same applies to the extra 5.0 volt winding. **Low loss high permeability silicon steel core** of sufficient stack to leave a **factor of safety over the highest rating** specified for the unit. In certain instances, several tubes may be added to each rating with safety, or a cheaper grade of iron and fewer laminations could be used if there were no fluctuations in current supply.

Static Shields are in all "Multi-tap" coils! In many radios these overcome annoying line hum, interference from oil burners and the like. The "Multi-tap" is built with ample margin of safety for quality performance and dependability in more than 95% of the sets put out since 1927—either orphaned or current models.

Safety first on QUALITY!—this is the quickest way for service engineers and all of us to build up a profitable business!

REMEMBER Power Supply Units are the *nucleus*—the very heart—of good Sound Amplifiers. Build your amplifiers the "STENTORIAN" way for the finest results at the lowest cost.

GENERAL has designed and is now supplying its distributors with complete sets of Hi-Quality power supply units which are perfectly matched with the auxiliary equipment specified to insure brilliant clear sound reproduction over an exceptionally wide tonal range.

The **NUCLEUS** includes the proper power transformer, chokes, audios, and outputs, with a neatly designed black wrinkle-finished chassis equipped with lettered output and input terminal strips and marked tube sockets—for 6, 10, 15, and 30 watt Amplifiers. Some Class A and Class AB amplification. 2.5 and 6.3 volt tubes. Nuclei for two additional 6 and 15 watt Amplifiers—using the new All Metal tubes; for crystal or condenser mike Pre-amplifiers; and for small Class B Battery Amplifier.

The "STENTORIAN" way Sound Amplifiers provide clear, powerful sound coverage for convention halls, auditoriums, refectories, for athletic fields, ballrooms, night clubs, taverns, lodge halls, political rallies, banquet programs, office and factory call systems, race track announcements, concession barkers, truck and auto advertising, depot train call systems and the like. Their clarity of reproduction substantially increases the tonal area.

WRITE TODAY!—give us your jobber's name and address and we will send the bulletins mentioned below!

Free for the Asking!

- | | |
|--|---|
| <input type="checkbox"/> Multi-tap Guide listing 2114 radios which can be serviced with "Multi-tap." | <input type="checkbox"/> Auto-Radio "B" and Vibrator Guide for 220 auto-radio models. |
| <input type="checkbox"/> "STENTORIAN" Sound Amplifier Nucleus Bulletin. | <input type="checkbox"/> GENERAL 1935-b Catalog of Exact Duplicates and lower-priced alternates for over 400 models of radios, and full line of power supply units. |
| <input type="checkbox"/> "PROGRESSIVE" transmitter units for amateurs. | <input type="checkbox"/> Voltage changing (step-down and step-up) and voltage regulating transformers. |

GENERAL TRANSFORMER CORPORATION

502 SOUTH THROOP STREET, CHICAGO, ILL.

● MANUFACTURERS OF REPLACEMENT UNITS

GENERAL ELECTRIC

Announces

A SERIES OF FIELD SERVICE MEETINGS

**Sound Movies • Illustrated Lectures
Service Notes • Competent Speakers**

If you were one of the service men fortunate enough to attend the General Electric illustrated lecture on Metal Tubes last August, you have an idea of how instructive and chock full of up-to-the-minute information a G-E Field Service Meeting can really be.

You'll certainly want to attend a series of similar meetings, conducted by General Electric Radio experts, scheduled to be held in your locality at frequent intervals.

Attendance Free. Everybody is Invited

All radio service men and dealer salesmen, or others desirous of keeping up to date with the fast moving changes in radio, are cordially invited to attend General Electric's Field Service Meetings.

New developments in metal tubes and radio circuits make it necessary, now more than ever before, for radio service men and salesmen to keep pace with the many rapid changes in the radio art. These FREE lectures offer you this golden opportunity to keep abreast of the times.

**Practical Instruction in
Radio's Latest Developments**

General Electric's technical and practical experts will conduct this series of Field Service Meetings in the principal cities throughout the United States. These meetings will include Sound Movies . . . Illustrated Lectures . . . "Round-table" Discussions on Subjects Presented . . . Service Notes on General Electric Radio. Each meeting will fully present applicable facts relating to Metal Tubes and the servicing of General Electric Radio. It's an unusually practical course of instruction that will make your service business profitable . . . help you sell more G-E Radios . . . make more money now . . . and prepare for larger future success.



**GENERAL
ELECTRIC
RADIO**

MERCHANDISE DEPARTMENT
GENERAL ELECTRIC COMPANY
BRIDGEPORT, CONN.

General Electric Company, Bridgeport, Conn.
Attention: Section R-7810

Please send me the date and address of the next Field Service Meeting in my locality.

Name.....

Firm Name.....

Street Address.....

City..... State.....

*Mail the Coupon
for the Date of
Next Meeting in
Your Locality*

SERVICE

A Monthly Digest of Radio and Allied Maintenance
Reg. U. S. Patent Office. Member, Audit Bureau of Circulations

Vol. 4, No. 10
OCTOBER, 1935

EDITOR
M. L. Muhleman

ASSOCIATE EDITOR
Ray D. Rettenmeyer

EDITORIAL CONTENTS

FEATURES

- Automatic Initial Bias Circuit..... 439
A Versatile Tester for Vibrators
By A. R. Moseley..... 456
Profits in Old Set Conversion with Modern
Methods
By Tobe Deutschmann..... 437
RCA Victor Model C 15-3 Metal-Tube Re-
ceiver..... 440

ANTENNA

- New Business..... 434

ASSOCIATION NEWS..... 464

AUTO RADIO

- Atwater Kent Model 776..... 450
Installing Motorola GM Model Sets on Roof
Aerial..... 454
Locating Motorola Interference Feeders
By L. C. Dittmar..... 454
Motorola Magic Eliminode Notes..... 452

CIRCUITS

- Atwater Kent Model 776..... 450
Automatic Initial Bias Circuit..... Front Cover
Circuit Diagram of Browning-35..... 438
Converted Browning-35 Power-Supply Circuit 438
Fada Model 160..... 449

- RCA Victor Model C 15-3..... 441
Silvertone 1904 Series..... 445
Stewart-Warner R-130 Chassis..... 443
Typical Circuit for Remote Speaker Installa-
tion..... 458
Vibrator Tester Circuit..... 456

FORUM..... 467

GENERAL DATA

- Automatic Initial Bias Circuit..... 439
Fada Model 160..... 446
RCA Victor Model C 15-3..... 440
Silvertone Models 1904, 1904A, 1906, 1914,
1954, 1964, 1964A..... 444
Stewart-Warner R-130 Chassis..... 442

HIGHLIGHTS..... 468

MANUFACTURERS..... 470-472

ON THE JOB

- Auto-Radio Vibrators
By George F. Baptiste..... 458
A Versatile Tester for Vibrators
By A. R. Moseley..... 456
Remote Speakers
By F. C. Wolven..... 458

RECEIVER CASE HISTORIES..... 460-462

BRYAN S. DAVIS
President

JAS. A. WALKER
Secretary

New York Telephone: Plaza 3-0483

Chicago Office—608 S. Dearborn St.—C. O. Stimpson, Mgr.
Telephone: Wabash 1903
Cleveland Office—10515 Wilbur Ave.—J. C. Munn, Mgr.
Telephone: Republic 0905-J

Published Monthly by the

Bryan Davis Publishing Co., Inc.
19 East 47th Street
New York City

SANFORD R. COWAN
Advertising Manager

PAUL S. WEIL
Eastern Advertising
Manager

A. B. CARLSEN
Circulation Manager

St. Louis Office—505 Star Bldg.—F. J. Wright, Mgr.
Wellington, New Zealand—Tearo Book Depot.
Melbourne, Australia—McGill's Agency.

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price \$2.00 per year in the United States of America; 25 cents per copy. \$3.00 per year in Canada and foreign countries; 35 cents per copy.

HOWARD

Can Deliver!

METAL TUBE SETS

HOWARD foresaw the present shortage of materials and bought for the future with the largest commitments in HOWARD's long history.

As a result HOWARD *can deliver* the complete line including *metal tube sets!*

Nine receivers. 4- 5- 6- 7- and 9-tube models from \$17.95 to \$124.50. *Plus* the world's finest radio receiver—the 19-tube grand at \$295.00.

DISTRIBUTORS AND DEALERS WRITE OR WIRE FOR DETAILS! YOUR TERRITORY MAY STILL BE OPEN

HOWARD

HOWARD RADIO COMPANY

1737 BELMONT AVENUE, CHICAGO
AMERICA'S OLDEST RADIO MANUFACTURER

THE ANTENNA . . .

New Business

NEW P-A BUSINESS

THROUGH THE EFFORTS of the Radio Manufacturers Association, the Federal Housing Administration has finally agreed to make eligible for FHA financing under its Modernization Credit Plan any public-address systems of a permanent character. This includes installations for apartment buildings, hotels, office and other commercial buildings, hospitals, orphanages, colleges, factories and schools. It does not, however, include installations for private residences.

What this means is that anyone wishing a public-address system installation which is to be permanent, may apply through any of the many FHA credit outlets—local banks, etc.—for a loan to cover the complete cost of the job. The loan is repaid in equal installments over a period of from one to five years.

Here is a fine chance for the Service Man or Service Organization to whip up new business. Since the amount of interest one has to pay on the loan is decidedly moderate, and since the payments may be extended over a considerable period of time, it is actually possible to make the public-address installation pay its own way, with no initial outlay of cash on the part of the owner.

We offer the suggestion that you pick up your old public-address leads and also go after some new ones. Canvass your territory, but before doing so get some copies of the FHA Booklet which gives all the details on the loans and how they can be obtained. Your local bank should have copies of this Booklet available. Then show your prospects how easy it is to get a complete p-a installation.

Go to your local bank and get all the dope on how you should handle the jobs. You will find that all you have to do is submit the plans and installation costs to the credit agency. If everything looks okay, they will put up the entire amount required to cover both the cost of the public-address equipment and the installation charges.

Here is a big chance to increase your business. Don't let it slip by. Get all the dope on available public-address equipment right away so that you will be in a position to submit plans and costs on a moment's notice. Get organized on this . . . if you don't the other fellow is going to beat you to it.

BUILT-IN RADIOS

WORD HAS BEEN received that the FHA has also made eligible for financing under its Modernization Credit Plan any type of radio that is built into a home. This means that the owner of a private residence can borrow money to cover the cost of such an installation.

Here again there is offered to you a chance to increase your local business by undertaking the installation of built-in radio receivers for the home.

There are a number of manufacturers turning out "centralized" radio systems. These can be built into new homes in much the same manner as the electric wiring is installed. Or they can be worked into finished homes with very little extra effort.

Most of these centralized radio systems are rather

elaborate. If the home owner finds them too expensive, you can always turn to stock equipment and work out your own system. We will have some very interesting dope on this in the next issue.

The point is that the radio equipment must be a permanent installation, just as an oil burner or a complete cooking range are permanent installations, in that they can't be moved about. They are "integral parts" of the house, and the built-in radio must also be an integral part of the house if it is to be eligible for a government loan.

Thus, if you were to take a stock radio, disassemble it and install the chassis and speaker in the wall or in a built-in cabinet, the installation would be classed as permanent. So long as the radio remains in a separate cabinet which may be moved about from room to room or removed from the house like a piece of furniture, it is *not* a permanent installation and would therefore not be eligible for an FHA loan. We mention this because electrical refrigerators *are* eligible and are classed as permanent installations, yet they could be removed as readily as a stock radio.

Better start working on plans for canvassing your neighborhood, but first work out a few acceptable installations so that you will have something concrete to offer to prospects.

We will welcome data on installations made and the manner in which you went about closing the deals. Your experiences will assist other Service Men just as their experiences will assist you . . . so, don't keep it a dark secret.

SERVICING AND WAR

ACCORDING TO THE Radio Manufacturers Association, the public interest in short-wave radio is increasing by leaps and bounds. A part of this interest is undoubtedly due to the fact that "all-wave" or "dual-wave" features are practically "standard equipment" in the modern radio, so that the purchaser has these bands opened up to him as a matter of course. So—being inquisitive—he tries out these bands, and usually ends up an avid short-wave bug.

In any event, there are an enormous number of short-wave listeners today and the number is rapidly increasing. As cruel and as odious as war may be, it has an almost irresistible dramatic appeal, and radio listeners will find of absorbing interest the details of the conflict in Ethiopia. Anything may happen over there, and the broadcasting companies are all set to provide the details to the listening public. A good part of the drama will be presented on the broadcast band, but there is no telling what may come over some of the foreign short-wave stations. That's why the public wants a front-row seat in all broadcast wavebands.

The stage is set—are the radios? That's your job. Why not send out a teaser to your customers—suggesting that they let you "tune up" their all-wave receivers so that they won't miss any of the show, or suggesting that they purchase an all-wave receiver in the event that they do not own one.

Hats Off to the New King

Volume VI

Yessir, Fellas! *Hats off to KING VOLUME VI.* The volume you—with your suggestions helped develop as the most complete source of accurate service information. This is the biggest manual ever published—about 1,250 pages in a single volume!

Volume VI takes up where Volume V left off! Completes Rider's compilation of accurate service data, on all receivers up-to-date! A separate 90-page index.

Circuit diagrams on the 1935-1936 midgets, table and console models—mail order super-hets—standard manufacturer's receivers—stencil brand receivers—West Coast receivers—metal and glass envelope tube circuits—cathode ray tuning—voltage tables—I-F Peaks—socket data—visual alignment data using cathode-ray oscillograph—about 1250 pages of indispensable service data on about 1000 models—the greatest manual ever! More than 110 manufacturers in Volume VI.

Vol. VI—1,250 pages; separate complete 90-page index.....	\$7.50
Vol. V—1,204 pages; separate complete 64-page index.....	7.50
Vol. IV—1,060 pages; separate complete 40-page index.....	7.50
Vol. III—1,070 pages.....	7.50
Vol. II—800 pages.....	6.50
Vol. I—1,000 pages.....	7.50



**BOY!!
AM I GLAD
YOU GOT
HERE!**

Concise—complete—all the information you require to service intelligently, quickly and efficiently. All the info right at your fingertips! No filing! No memorizing! No guesswork!


With the help of the 6,350 pages in Rider Manuals you will be able to handle the most difficult and complicated, as well as the simplest jobs—quicker—do a better job—and make a bigger profit.

There are no other books or manuals available, anywhere in the world, that contain information so complete, concise, and up to the minute, information indexed for easy reference as contained in Rider's Manuals.

Can you afford to be without a complete set of Manuals? We should say Not!

SOLD WITH MONEY BACK GUARANTEE

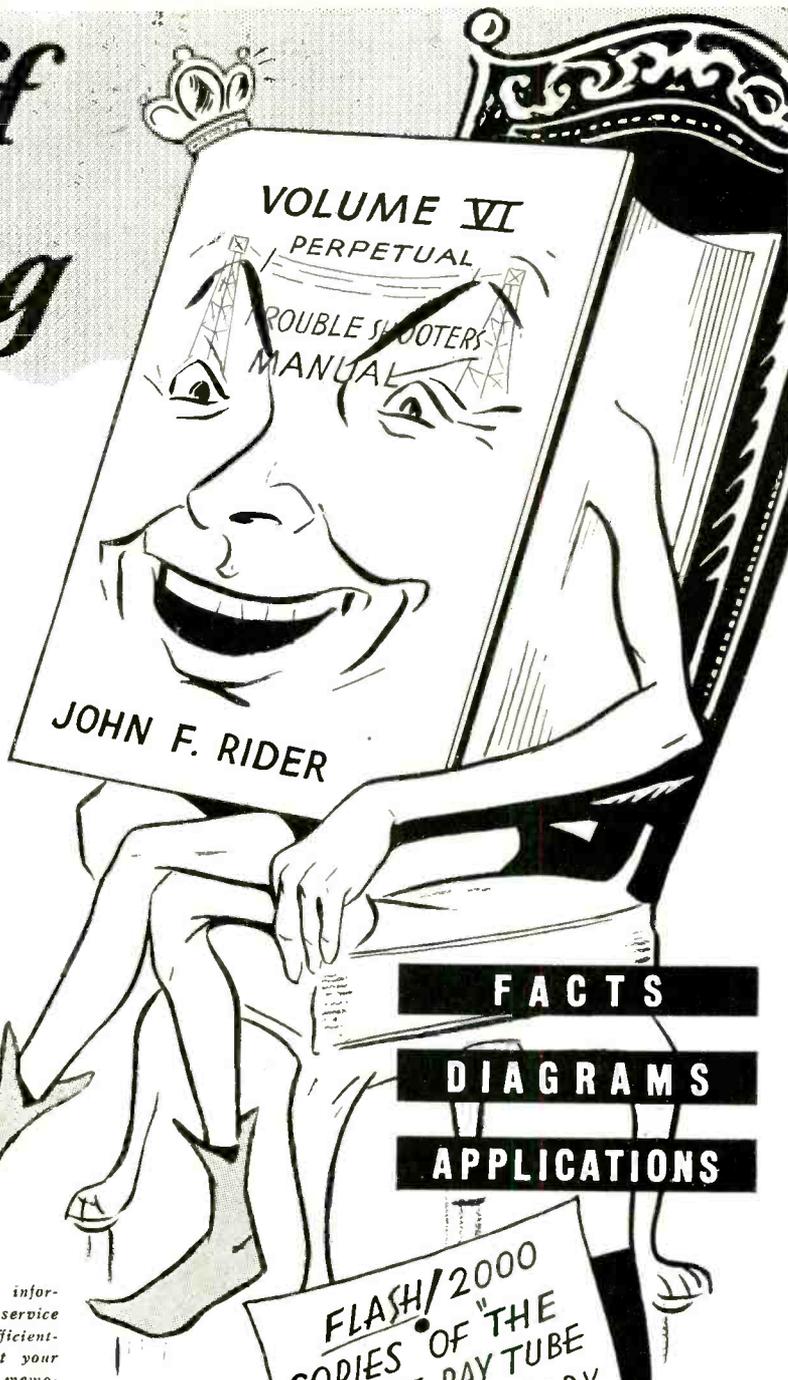RIDER JOHN F. RIDER PUBLISHER
Publications
1440 BROADWAY • NEW YORK



JOHN F. RIDER
1440 Broadway, New York City

SV105

Dear Rider:
Send me a copy of "Successful Servicing."

Name

Address

ELECTRAD

RESISTOR SPECIALISTS IN RADIO AND ELECTRICAL INDUSTRY SINCE 1923

How to Service:

R.C.A. RECEIVERS
R-14, R-15, RE-17, R-42, R-48

GENERAL ELECTRIC
RECEIVERS T-41, RC-3

GRAYBAR RECEIVER 678

WESTINGHOUSE
RECEIVER WR-4

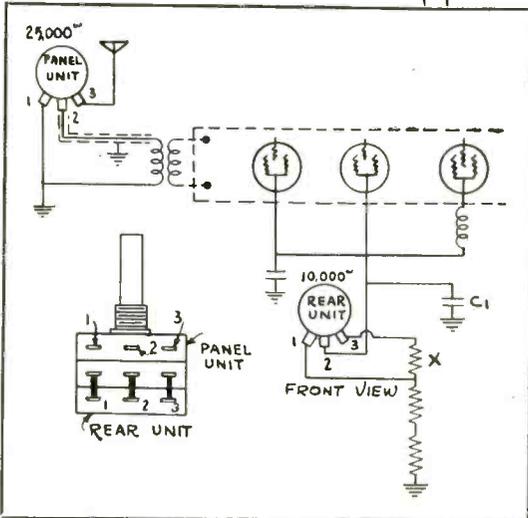



DIAGRAM SHOWS APPLICATION OF ELECTRAD CONTROL TO ABOVE NAMED RECEIVERS

THE above named receivers employ a tandem control, one section operating in the antenna control, another varying the screen voltage of the R.F. stages. The difficulty experienced with the screen grid section of this control has been hitherto caused by the relatively huge wattage dissipation required of it. Electrad has solved this problem by using a three-section unit and distributing the load of the screen grid section uniformly between two resistors instead of one. This assures long life and noiseless operation at but slightly increased cost.

The diagram shows the scheme of connections. The rear section (two units) is connected as a section of the bleeder resistance. In some models of the above named receivers this is already done. In other models, where the control is connected across a 12,000 ohm resistor (marked on the diagram), this resistor is disconnected and the two outside terminals of the control connected in its place. The connections for the front unit remain the same.

The addition of a 1 mfd. condenser (C.) 250 volt, from terminal 2 of the screen grid control to ground will improve the performance of the control.

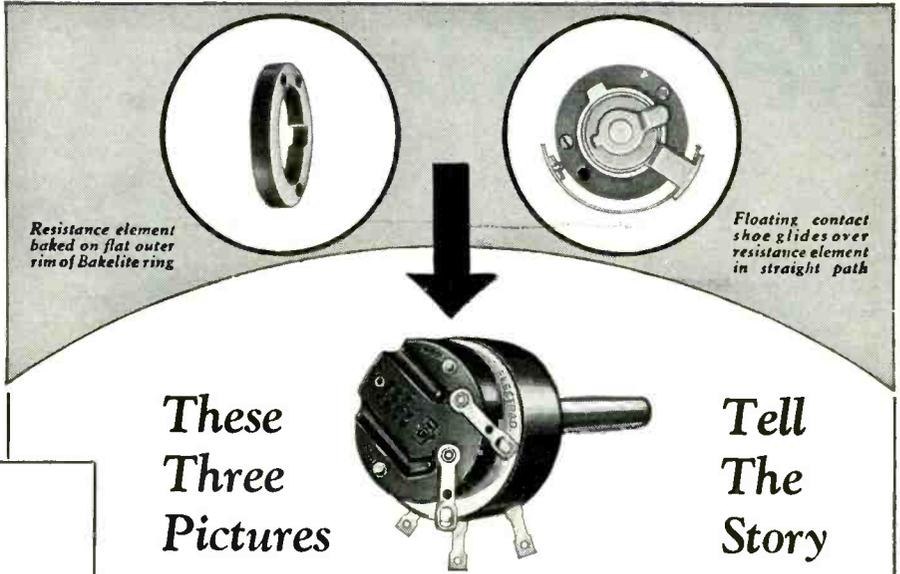The above is one of many special applications described in the **ELECTRAD VOLUME CONTROL GUIDE**. (See free offer alongside.)



These
Three
Pictures

Tell
The
Story

Of ELECTRAD'S New CARBON VOLUME CONTROL

WHEN you replace a volume control, you don't want kick-backs to waste your time and money. Install the new Electrad guaranteed quiet Carbon Volume Control and you will be safe and sure.

Above, at the left, you see the sturdy Bakelite ring, to the flat outer rim of which the Electrad resistance element is permanently fused. The current travels in a straight path.

No short cuts in current path, as in old-style controls, to cause overloading, uneven distribution and early breakdown.

To the right, you see the simple fool-proof mechanism. A special-alloy floating contact shoe glides over the resistance element, actually increasing in smoothness and quietness as the control is used.


In the center, you see the complete unit, with new-type power switch (approved by underwriters) attached — the smoothest, quietest, longest-lived volume control ever devised.

Write Dept. S-10 for Complete Details.

FREE New 100-Page VOLUME CONTROL GUIDE

To Bonafide Service Men

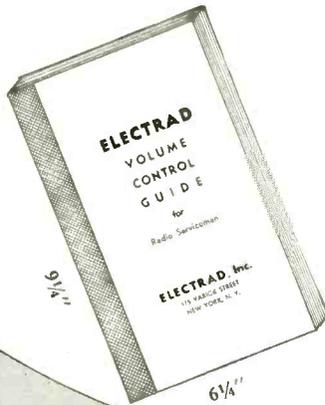The cost of this guide prohibits free distribution. But you may have a copy by return mail if you send us the carton flap (the part showing specification and resistance) torn from any new-type Electrad Carbon Volume Control carton, together with your business letterhead or business card. Address Dept. S-10.



RESISTOR SPECIALISTS

Featuring:

QUIET CARBON VOLUME CONTROLS

VITREOUS RESISTORS

TRUVOLT RESISTORS

POWER RHEOSTATS

Write Dept. S-10 for 1936 Catalog

175 Varick St., New York, N.Y.

ELECTRAD



SERVICE

A Monthly Digest of Radio and Allied Maintenance

FOR OCTOBER, 1935

PROFITS IN OLD SET CONVERSION WITH MODERN METHODS

By Tobe Deutschmann*

This is the first of a series of articles on the modernization of antiquated receivers, bringing them to a par with high grade 1936 models. This series will be entirely of a practical nature, and will describe conversions made on various popular and representative receivers of by-gone vintage, with the sole purpose of enabling the Service Man to duplicate these jobs. All of the "bugs" will be eliminated, and the way paved toward profits for the Service Man, with metal and glass tube modernizations.

ACCORDING to a recent report in the *New York Times*, 25% of all receivers now in use are obsolete. This number includes not merely receivers which were purchased a half decade ago, and which are obviously out-of-date, but even more recent models manufactured prior to the advent of all-wave popularity. There are, of course, other contributory factors toward obsolescence, such as automatic volume control, ease of operation, economy, high fidelity, low

*President, Tobe Deutschmann Corp.

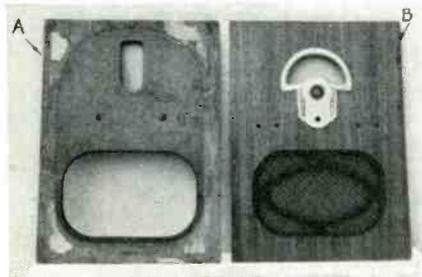


Fig. 1. Showing the original Majestic panel, A, and the new panel, B, prepared for the modernization job.

background noise, etc., and it is not an exaggeration to state that any set not incorporating every one of these features is not wholly modern.

MODERNIZATION ADVANTAGES

There is no doubt that a large number of these obsolete receivers will be replaced with new sets—which is as it should be. On the other hand, the fact that from five to eight million receivers are today antiquated offers opportunities of considerable potentiality to the Service Man in the modernization of such sets. Much has been written lately on this revived theme, and the arguments in favor of modernization are well known. Recapitulated they are: Economy—the securing of new set operation at one-third new set cost (for comparable results, providing the Service Man does a good job); the salvaging of a good portion of the original investment which in many instances ran into hun-

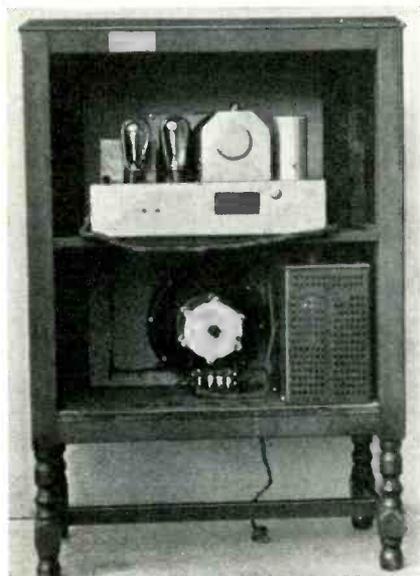


Fig. 3. Rear view of the Majestic 91 before modernization, and . . . (See Fig. 4).

dreds of dollars; retention of the old cabinet which the owner may be reluctant to relinquish through sentimental attachment or because it fits in with his individual scheme of interior decoration.

MECHANICS OF CONVERSION

The mechanics of such modernization are simple, and consist of substituting the essential part of an all-wave chassis for the existing tuner, retaining as much of the original installation as is practical—always the cabinet, and often the power supply, loudspeaker and audio amplifier. There are several all-wave chassis on the market available for this purpose. In this series, the writer will employ the Browning-35, because of his familiarity with the circuit and the inherent flexibility of the set which contributes greatly to its adaptability. Also,



Fig. 4. After modernization. The power pack, as will be observed, has been retained.

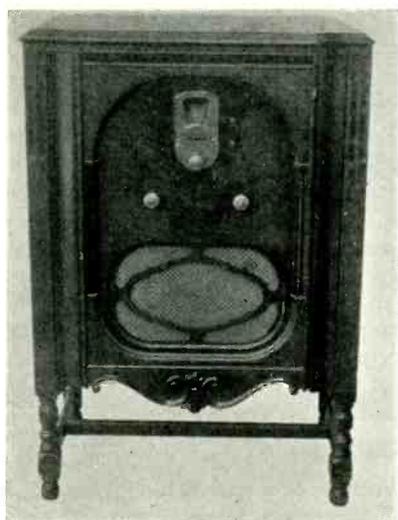


Fig. 7. The Majestic 91, vintage 1928-29.

Relatively simple electrical changes were required to effect the adaption. The circuit diagram of the simplified Browning as used in the conversion is shown in Fig. 5. The following parts have been eliminated from the standard kits and circuit: Power transformer, two 8-mfd filter condensers, the rectifying tube socket, the rectifying tube (providing that in the Majestic power pack is in good condition) and the loud-speaker. An output transformer, with an 8,000-ohm primary and a 4-ohm secondary has been added.

The power pack circuit is shown in Fig. 6, and is self-explanatory. Resistors R_1 and R_2 have been added, the first to supply the correct plate voltage to the chassis, and the second as a

bleeder resistance to provide excitation for the speaker field. The connections between the chassis unit and the power unit are indicated on the diagrams.

REASSEMBLING THE RECEIVER

The escutcheon is mounted with either five wood screws, or nuts and bolts, depending upon the exact method of re-assembling decided upon by the individual Service Man. Probably the most satisfactory method is to assemble the complete Browning-35 chassis (less the omitted parts, of course) utilizing the standard metal panel which holds the dial card. This greatly facilitates servicing, as the receiver can be removed from the cabinet and aligned with the dial card in position, on the service bench. In this instance, the escutcheon is fastened to the front, or wood panel, with good screws. Extension shafts (which are standard with this receiver for conversion purposes) are attached to the control shafts, and the chassis is pushed, on the cabinet shelf, into position. When the metal panel is flat against the wooden panel, the shafts will extend the correct distance and the knobs may then be mounted.

The second procedure eliminates the metal panel. The escutcheon is mounted with nuts and bolts, after being first used as a template to punch mounting holes in the dial card. The dial card is then mounted behind the escutcheon, spaced from the panel by the escutcheon bolts. This space provides room for the dial pointer. The dial card is secured by means of three additional nuts, the machine screws being sufficient length

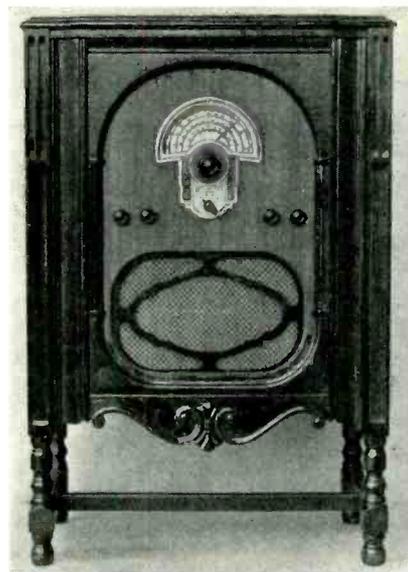


Fig. 8. The Majestic 91, vintage 1936

to accommodate this mounting. The chassis is then secured to the wood panel by the nuts holding the lower controls to the chassis.

It is not necessary to "float" or otherwise cushion the chassis. The construction of the Browning receiver mitigates against the effects of acoustic feedback to such an extent that this *tour de force* will rarely be necessary. The tuning unit itself is cushioned from the chassis.

CONTRAST

Figs. 7 and 8 demonstrate the pleasing contrast between the old and modernized receivers. The contrast in performances is comparable!

(To be continued)

AUTOMATIC INITIAL BIAS CIRCUIT

(See Front Cover)

RESIDUAL bias for tubes placed on automatic volume control is usually obtained through the use of separate cathode resistors, or by connecting the cathodes or grid-return leads to a point or points on a tapped resistor either positive or negative with respect to the chassis ground, depending upon the method used for obtaining the bias.

More recently, a few receivers have appeared wherein the residual bias—a negative voltage in this case—is impressed on the grids of the automatic bias-controlled tubes directly through the same lead that supplies the avc. However, the automatic residual bias system used in a number of the new RCA receivers is, to our knowledge, an entirely new way of obtaining this bias.

WHAT IT DOES

Referring to the circuit on the front cover, the modulated signal as obtained from the output of the i-f system is detected by one diode of the 6H6 tube. The a-f obtained by this process is

passed on to the a-f amplifier. The d-c voltage which results from detection of the signal is used in the usual manner for avc, and this voltage is impressed on the grids of the r-f, mixer and i-f tubes. The second diode of the 6H6 is used to supply the residual bias for these controlled tubes under conditions of little or no signal. This diode, under such conditions, draws current, which flows through resistors R, R-1 and R-2, thereby maintaining the desired minimum operating bias on the controlled tubes. On application of signal energy above a certain level, however, the auxiliary bias diode ceases to draw current and the avc diode takes over the biasing function. Thus it is seen that there is an electrical "see-saw" action between the two diodes, the signal, or lack of signal, being the determining factor.

OPERATION

The cathode K-1 and diode D-1 of

the signal-avc diode have positive potential in respect to chassis-ground as well as in respect to the cathodes of the controlled tubes when no signal is being received. This positive voltage is obtained by connecting the cathode K-1 to a point on the voltage divider plus 1.3 volts above ground. Since the residual bias diode connects to the cathode K-1 through resistors R, R-1 and R-2, it is also positive under no-signal conditions, and since its cathode K-2 is connected to a point between resistors R-3 and R-4 which is negative 3 volts with respect to ground, diode D-2 draws current. This produces a voltage drop across resistors R, R-1 and R-2 which overcomes the positive voltage and runs the circuit negative. With the application of a signal of sufficient voltage, the signal-diode circuit becomes negative and this also makes the residual-bias diode D-2 negative and it ceases to draw current. It is at this point that the signal diode takes over the bias control.

General Data . . .

RCA Victor Model C 15-3

This is a 15-tube (metal) five-band receiver and uses the 6E5 (Magic Eye) cathode-ray tuning indicator. This receiver covers the extraordinary wavelength range of 140 to 60,000 kc with a slight hole above 410 kc for the i-f peak frequency of the set.

A worthwhile description of the circuit and its features takes so much space that we shall hold over the alignment data until next month. This in itself is highly interesting since it provides a practical explanation of the manner in which to align a large receiver of this type with a cathode-ray oscillograph.

TUBE COMPLEMENT

Referring to the diagram of the Model C 15-3 on the opposite page, the tube line-up is as follows: An r-f stage using a 6K7; a 6L7 hexode first detector; a 6J7 oscillator; two i-f stages using 6K7's; an avc i-f stage using a 6K7 which feeds a 6H6 avc diode; a 6H6 diode second detector; a 6C5 in the first a-f stage; two 6C5's in push-pull in the a-f driver stage; two 6F6 tubes, pentode connected, in the push-pull output stage; a 5Z3 (glass) full-wave power rectifier and, last but not least, a 6E5 tuning indicator tube.

ELECTRICAL SPECIFICATIONS

The receiver is provided with a universal power transformer and may be used on lines having a wide range of voltages and frequencies. The power consumption of the receiver is 145 watts.

The set has an undistorted output of 10 watts and a maximum output of 15 watts.

The 12-inch speaker has a voice-coil impedance of 7.5 ohms at 400 cycles.

THE CIRCUIT

Six adjustable tuned circuits are used in the i-f system, each resonating at 460 kc. A three-section variable condenser tunes the secondary of the antenna transformer, the secondary of the detector input transformer and the oscillator coil on all bands with the exception of D, which has only its detector and oscillator tuned. Each tuning range has its own group of r-f and oscillator coils, they being selected as desired by operation of the band-change switch. Trimmer condensers are provided on all of the tuned circuits for use in obtaining precise alignment.

Band D Tuning

Special notice should be taken of the manner of tuning this ultra short-wave band (18 to 60 mc.). The r-f stage is unused when the range switch is turned to its Band D position and the signal is fed from the antenna directly to the first detector input circuit. The inductance of this circuit consists of a short length of bus wire to which the antenna lead is tapped at a definite predetermined point. The total length of this inductive wire from the stator of the tuning capacitor to ground represents the secondary of a high-frequency autotransformer, while the inductive section included between the antenna lead tap and ground forms the primary. Alteration of the dimensions and position of this wiring will change the tuning and alignment of the circuit, resulting in total lack of opera-

tion or seriously poor operation. It is therefore necessary when servicing to avoid changes in the wiring which includes Band D detector and oscillator r-f circuits unless the arrangement is restored to its exact original condition.

Similar caution should be observed when exchanging bypass condensers in these same circuits, since their values, physical positions, length of leads, quality of dielectric, etc., are critical and variations will definitely affect operation of the receiver. The small heater bypass condensers and ground terminals installed at the tube sockets are very important in this respect.

Oscillator Stage

The heterodyne oscillator circuit used in this receiver is an improved type, having exceptional frequency stability and uniformity of output over its various tuning ranges. It operates on fundamental frequencies which are fed to the 6L7 first detector hexode tube on an auxiliary mixing grid. The oscillator generates a signal which is at all times above the frequency of the incoming signal by 460 kc. As shown by the schematic diagram, the cathode of the oscillator tube is above ground potential for r-f, while the plate is effectively at ground potential. This particular arrangement, together with the plate and screen series resistors, makes the circuit independent of supply voltage variations in regard to stability and uniformity of output. Separate coils are used for each of the tuning ranges. The switching of the different bands is such as to short circuit certain unused coils which would absorb energy from the circuits used.

Intermediate Amplifier


Two stages of i-f amplification comprising three tuned transformers and two 6K7 tubes are arranged in cascade to operate at 460 kc. The transformers have their primaries as well as secondaries tuned by adjustable trimmer capacitors. These trimmers are designed to resist moisture, temperature and other detrimental factors which may affect their adjustments. Litz wire is used for the windings of the third transformer in order to provide the proper efficiency in driving the diode second detector.

Second Detector


Signal detection is brought about by the rectifying action of the 6H6 double diode tube. Audio signal obtained from the voltage drop across resistor R-19 in the diode circuit, is transmitted to the first audio stage by direct coupling. The direct signal component across resistor R-19 is used for bias for the 6C5 first audio tube.

Automatic Volume Control

The avc operates as a parallel sys-

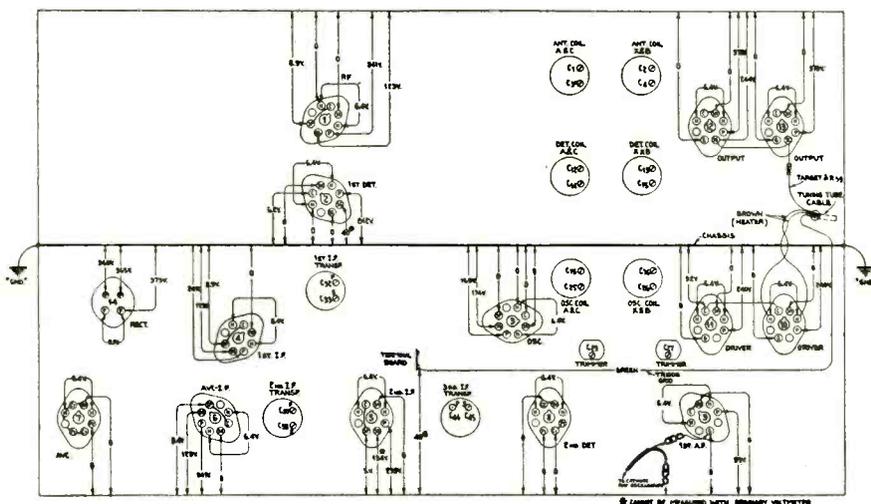

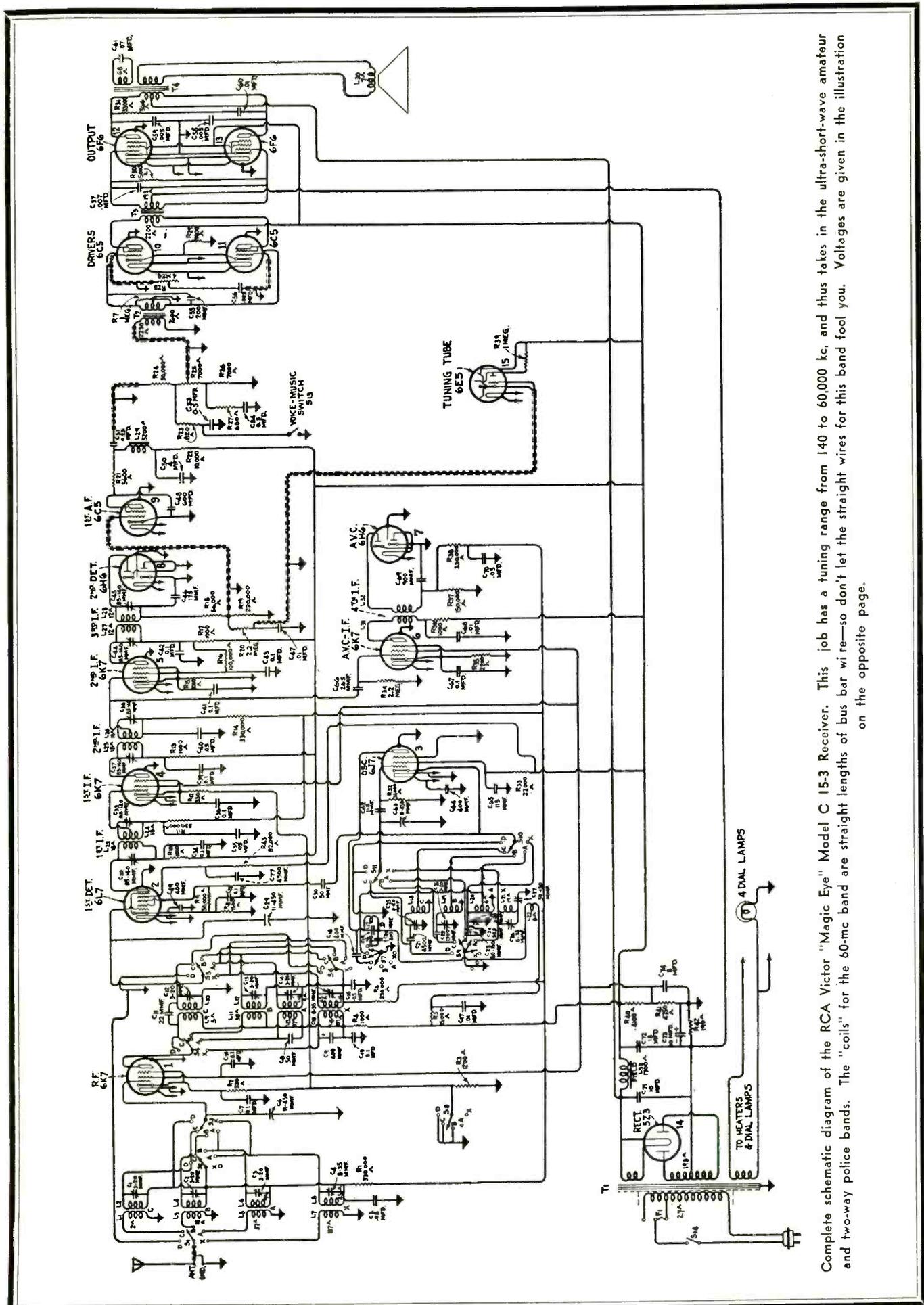Showing the location of coils, transformers, and sockets with voltage values for RCA Victor Model C 15-3.



Complete schematic diagram of the RCA Victor "Magic Eye" Model C I5-3 Receiver. This job has a tuning range from 140 to 60,000 kc, and thus takes in the ultra-short-wave amateur and two-way police bands. The "coils" for the 60-mc band are straight lengths of bus bar wire—so don't let the straight wires for this band fool you. Voltages are given in the illustration on the opposite page.

tem, being fed from the first i-f output through an auxiliary amplifier tube, a 6K7. This stage has an untuned input and broadly resonated output, as accomplished in the natural period fourth i-f transformer. A double diode 6H6 receives the signal at i-f frequency from the No. 6 stage and rectifies it in order to obtain the d-c component required for avc. This component, which develops across resistor R-37, is applied to the control grids of the r-f, first detector and i-f tubes through resistor-condenser filter systems. The value of the bias obtained by this process varies with the intensity of the received signal and in turn governs the amplification of the receiver, thereby automatically regulating the output to the same level when there are fading tendencies and similarly when tuning from station to station.

Audio System

Several stages of audio amplification provide excellent fidelity and wide range of volume both for short-wave as well as on the standard and long-wave bands. The high gain of the system has necessitated thorough shielding and careful manufacture. All wiring, transformers, etc., should always be placed as originally installed if it has been necessary to remove such for service purposes. Hum difficulties are likely to occur if this caution is not observed. Manual volume control is by means of an acoustically tapered potentiometer which conveys the audio output of the first a-f stage to the interstage coupling transformer. This control has tone compensation produced by filters connected to two points thereon. This gives the correct aural balance at different volume settings. A music-speech switch is provided in one of the volume control filter circuits for use in obtaining good speech intelligibility. On the speech position, the low-frequency tones are reduced. A push-pull driver stage is used between the first a-f and the Class AB output amplifier. A continuously variable high-frequency tone control is shunted across the grids of the driver tubes. A sharp, high audio-frequency cut-off is obtained by a tertiary winding on the audio output transformer and by the correct design of the driver and interstage transformers. This cut-off feature results in quieter operation by the reduction of high frequency noise, especially on weaker stations.

Rectifier and Filter

A 5Z3 full-wave rectifier tube is employed in the high-voltage supply system. The loudspeaker field coil serves as a filter reactor in conjunction with

high capacity, electrolytic condensers. Fixed bias voltages are made available at the filter output on a divider system, which is likewise well filtered with large capacitors.

Tuning Indicator

A 6E5 cathode-ray tube is used as a means of visually indicating when the receiver is accurately tuned to the incoming signal. This tube comprises an amplifier and cathode-ray section built in the same envelope. The cathode-ray section consists of a conically shaped luminescent screen upon which a pattern is formed by an effect of the detected signal after said effect has been amplified by the amplifier section which is fed from the second detector diode circuit. The size of the pattern is determined by the strength of the signal voltage, so that any change of tuning may be readily observed in order to facilitate tuning to exact resonance.

(To be continued)

Stewart-Warner R-130 Chassis

This chassis is used in receiver Models 1301 to 1309. The circuit is similar to that of the R-125 Chassis which it supersedes. An insert in the accompanying diagram shows the tone-control circuit of the Model R-130-AT in which the tone control is continuously variable.

THE CIRCUIT

There are two wavelength ranges, selected by the tandem switch sections 30-A and 30-B. The antenna circuit has band-pass characteristics when the receiver is set for broadcast reception. The band-pass tuner is composed of variable condensers 34-A and 34-B and the coils 32. Coil 37 is for the short-wave band.

The 6A7 mixer-oscillator feeds a single stage of i-f using a 6D6 tube. Detection takes place in the diode circuit of the type 75 tube. The voltage developed in the diode load circuit also provides avc to the mixer of the 6A7 and to the 6D6 i-f tube.

Initial bias for the 6A7 mixer is supplied by cathode resistor 19-A, and for the 6D6 i-f tube by resistor 19-B. Bias for the control grid of the 75 triode is obtained from the voltage drop in resistor 19-C in the negative leg of the power supply. Bias for the 42 pentode is provided by the total drop across resistors 19-C and 19-D.

ALIGNMENT

Preliminary to alignment, remove receiver chassis from cabinet, connect out-

put meter across primary of output transformer on dynamic speaker (yellow and red wires) and turn volume control to maximum. The test oscillator must cover frequencies of 456, 600, 1400 and 4000 kc.

ALIGNING I-F AMPLIFIER

Set test oscillator to 456 kc. Connect output leads to control grid of 6A7 and ground. Set receiver range switch to broadcast position and make certain no station is tuned in.

Then adjust the four i-f transformer trimmers for maximum, repeating each adjustment later, as there is a certain amount of interaction. Trimmer adjusters are reached through holes in the tops of the two i-f transformer shields (rear right of chassis).

BROADCAST-RANGE CALIBRATION

Check position of pointer on condenser shaft by turning the rotor plates to full mesh. The pointer should then coincide with the heavy horizontal line separating the broadcast and short-wave dial scales. If it does not, remove the dial glass and turn the pointer to the proper position, being careful not to break or bend the pointer.

Turn range switch to maximum clockwise position (broadcast setting). To calibrate at the high-frequency end, use a broadcast station signal between 1300 and 1420 kc, or a 1400-kc signal from the test oscillator. Turn receiver dial to exact frequency of station or oscillator and carefully adjust the broadcast oscillator trimmer for maximum. This trimmer can be reached through a hole to the right and slightly above the range switch.

BROADCAST-RANGE ALIGNMENT

Connect a .0001-mfd mica condenser in series with the test oscillator output and the receiver antenna lead (blue). *This condenser must remain connected for all broadcast and short-wave adjustments.* Do not connect any resistor in series with the condenser.

Proceed by grounding receiver chassis and connecting test oscillator ground lead to chassis. Set test oscillator to approximately 1400 kc and tune receiver to the signal. Then adjust the broadcast detector shunt trimmer and broadcast pre-selector shunt trimmer for maximum. The first mentioned trimmer is adjusted through a hole in the front of the chassis immediately to the right of the tuning dial scale. The latter trimmer is located on top of the middle gang condenser.

Retune receiver and check the adjustments of these two trimmers.

GENERAL DATA—continued

Follow by setting test oscillator to 600 kc, tune receiver to its signal, and adjust the broadcast oscillator padding trimmer. This is reached through a hole located at the extreme right of the chassis front. Retune receiver dial to a peak and readjust this trimmer. Continue this procedure until the reading of the output meter cannot be further increased.

Then repeat adjustments previously made at 1400 kc.

SHORT-WAVE RANGE CALIBRATION

Set receiver range switch to short-wave position and set test oscillator to exactly 16,000 kc. (If oscillator does not cover this frequency, use the second harmonic of 8000 kc or the fourth harmonic of 4000 kc).

Set receiver dial at 16 mc and adjust the short-wave oscillator calibration trimmer. This is located just to the right of the broadcast detector shunt trimmer on the chassis front. There will be two peaks in this adjustment. The correct one is that with the trimmer screw farthest out.

To make sure that you have not adjusted this trimmer to the image frequency, check this point by setting the receiver dial to the image frequency (approximately 15.1 mc) and determine if the image signal can be heard. (The image frequency is always the signal frequency minus twice the i-f frequency . . . in this case $16,000 - 912 = 15,088$ kc). If no signal can be heard at 15.1 mc receiver dial setting, even with greatly increased test oscillator output, but can be heard at 16.9 mc, the short-wave oscillator calibration trimmer is undoubtedly improperly adjusted to the image frequency and so must be reset to the proper peak with the screw farther out. After readjusting this trimmer, again check to determine if the image comes in at 15.1 mc and not at 16.9 mc.

SHORT-WAVE RANGE ALIGNMENT

Tune receiver very carefully to the 16-mc frequency of the test oscillator for maximum output reading. Then adjust the short-wave range detector shunt trimmer to a peak. This trimmer is located on the right side of the upright coil, near the front of the chassis. After this is done, try to increase the output meter reading by detuning the trimmer slightly and retuning the receiver dial. Continue detuning trimmer and retuning receiver dial until maximum output is obtained.

In some cases the receiver will oscillate when this short-wave detector shunt trimmer screw is set too far out. This

oscillation, which can be eliminated by correct adjustment, is normal when the detector circuit is tuned to the receiver oscillator frequency instead of to the correct signal frequency.

If the set seems to motorboat when making the short-wave adjustments, reduce the output of the oscillator. This motorboating will cease when an antenna is connected to the set.

Silvertone Models 1904, 1904A, 1906, 1914, 1954, 1964, 1964A

These Silvertone models are 6-tube, a-c operated superheterodynes, having two short-wave ranges in addition to the broadcast range. Models 1904A and 1964A use conventional glass tubes. The i-f, avc and output circuits of the other models use the "G" type tube, having a glass envelope, but the same kind of 8-prong base as metal tubes.

The tubes and their functions in Models 1904A and 1964 A are as follows:

- 6A7—oscillator—translator.
- 78—i-f.
- 75—detector, a-f.
- 76—avc.
- 42—output.
- 84—rectifier.

The tubes and their functions in Models 1904, 1906, 1914, 1954 and 1964 are as follows:

- 6A7—oscillator—translator.
- 6K7-G—i-f.
- 75—detector, a-f.
- 6C5-G—avc.
- 6F6-G—output.
- 84—rectifier.

Proceed by checking the adjustment of the short-wave detector shunt trimmer by tuning the receiver to about 15.1 mc and noting if the image frequency at this point is much weaker than the 16-mc signal. If the signal at the 15.1-mc dial setting is equal to or stronger than the 16-mc signal, the trimmer is not properly adjusted and must be re-adjusted, with the screw *further in*.

In some of the sets, the 40-ohm resistor, R-14 (see Fig. 1) is omitted and a grounded center tap on the transformer used instead.

In earlier production, R-3 was a 20,000-ohm, 1/2-watt resistor. In later production, this was changed to a 5000-ohm, 1/3 watt resistor. In sets using a 20,000-ohm resistor, if trouble is experienced due to the set not operating at the low-frequency end of the C band, which will be due to the oscillator "stalling," replace the 20,000-ohm resistor with a 5000-ohm one.

The coupling between primary and secondary of the i-f output transformer is variable and serves as the volume control.

R-7 is the resistor which supplies avc voltage. Residual bias is furnished by R-13.

"FLUTTERING" ON SHORT WAVES

A "flutter" in short-wave reception on Band C may appear under the following conditions.

1. Volume control on full.
2. Station delivering a strong signal.

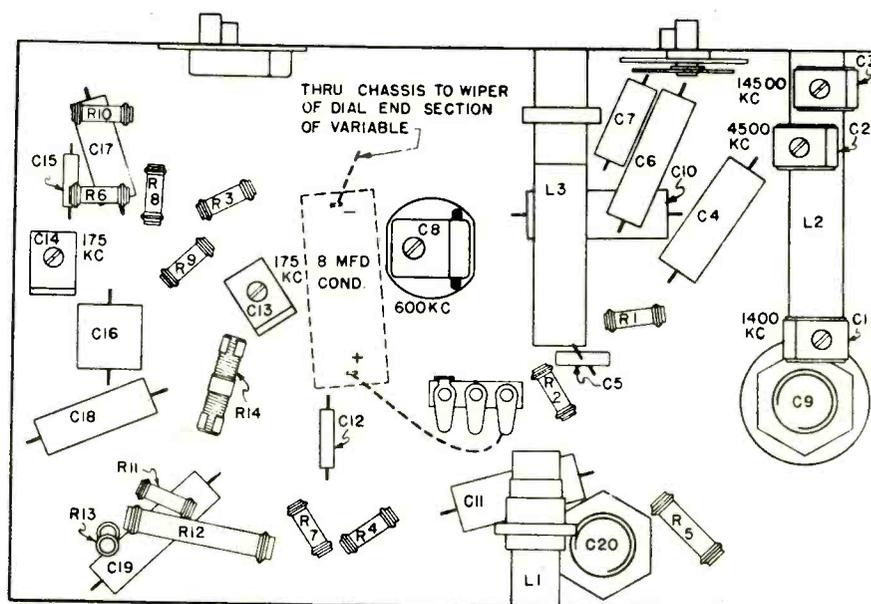


Fig. 2. Showing location of parts in Silvertone 1904 Series.

This flutter in no way indicates a defect in design or construction of the set. To completely eliminate it would require a more expensive circuit. It should not be a cause for complaint since it can be eliminated by reducing the volume control setting slightly. If an occasional customer is met who wants to pay the cost of making the necessary additions to the circuit, to prevent the flutter under any conditions, the following should be done:

Mount an 8-mfd. condenser as shown in dotted lines in Fig. 2. The lead from the positive terminal of the condenser should be connected to the terminal furthest removed from the condenser, on the triple terminal board. The negative lead from the condenser should be passed through the chassis and soldered to the wiper on the dial end section of the variable condenser. The leads should be made short and direct. Although this results in the 8-mfd. condenser being connected in parallel to C-10, it is important that the condenser be mounted as shown and the connections made as described (instead of directly across C-10).

ALIGNMENT

General:

During all of the alignment procedure, the volume control should be turned either all the way on, or else retarded slightly from the full "on" position, if retarding it is found to sharpen adjustments. The ground lead of the test oscillator should be connected to the chassis through a .1-mfd. condenser. The other lead of the test oscillator is to be connected in the manner described in the procedure. Where connection is made to a control-grid cap, it is important to leave the grid clip attached to the grid cap and to leave the tube shields in place. No attempt should be made to "kill" the oscillator section of the 6A7 during the alignment.

The output from the test oscillator always should be kept at the lowest possible value that will give a satisfactory output meter reading and the coupling between the test oscillator and the receiver should be made as loose as possible. In the case of r-f alignment on any of the bands, where the test oscillator is coupled to the antenna lead of the receiver with an antenna connected,

alignment will be most accurate if the coupling to the antenna lead is made very loose. (The antenna lead and the oscillator lead separated.) If the test oscillator has a variable control for its power output, it is better to turn this control to its high position and then decrease the signal input to the receiver by decreasing the amount of coupling between the test oscillator and the receiver's antenna lead. If an actual antenna is not used and is replaced by a condenser or resistor, as described in the procedure, the input to the receiver should be kept low by decreasing the power output from the test oscillator.

When peaking the antenna and translator trimmers, for all wavebands, the variable condenser should be "rocked" back and forth a degree or two while the trimmer is being adjusted. This should not be done when peaking the oscillator trimmers; in this case, the variable condenser is turned so that the plates are completely out of mesh and left in this position during the adjustment. When adjusting the oscillator trimmers, if it is found that two peaks can be obtained, use the one in which the trimmer is

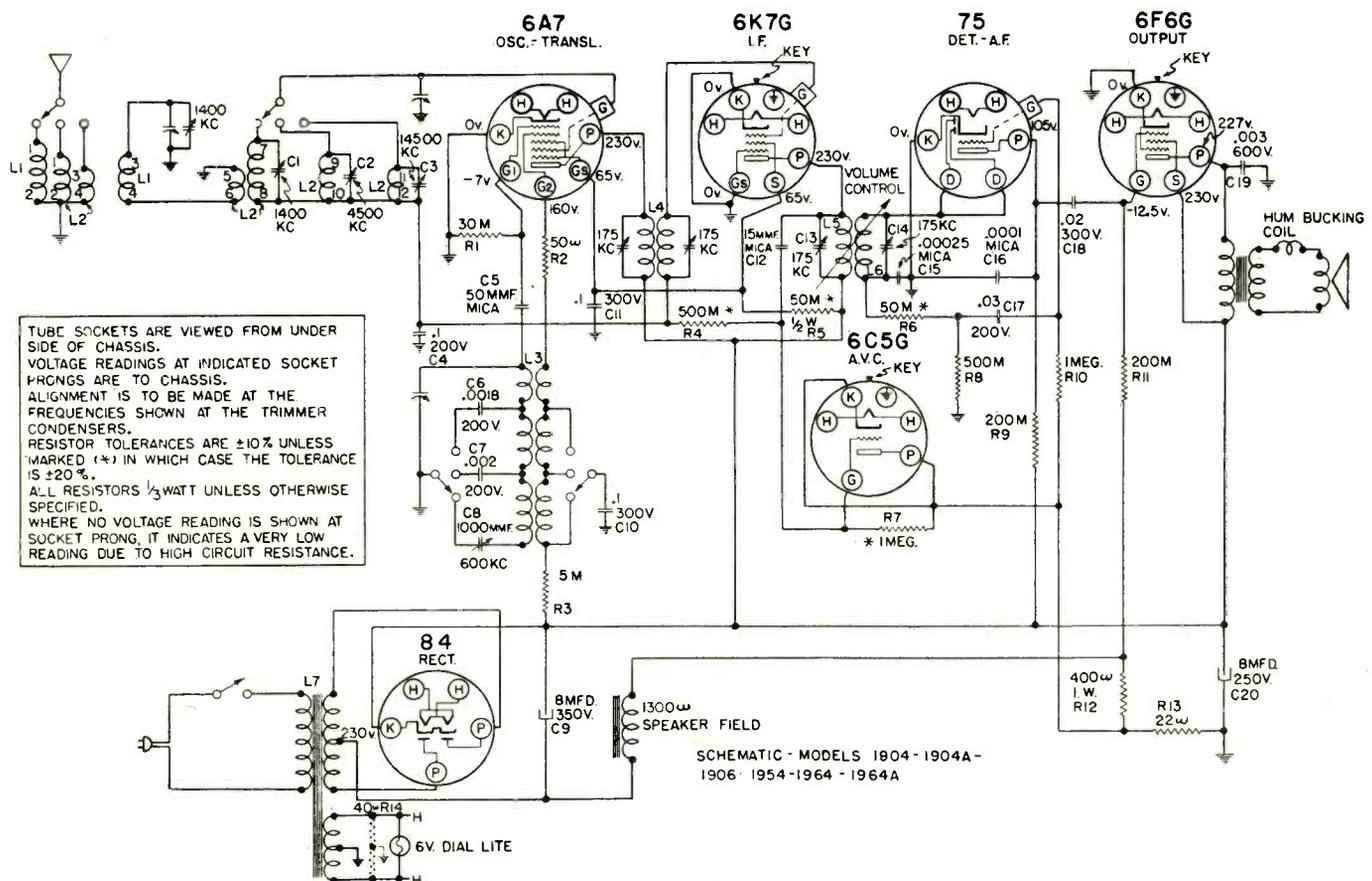


Fig. 1. Schematic diagram for Silvertone 1904 Series, giving voltages and parts values.

GENERAL DATA—continued

screwed further *out* (less capacity). When adjusting the antenna and transformer trimmers, if two peaks are found, use the adjustment in which the trimmer is screwed *in* furthest. Note that this is exactly *opposite* to the procedure for the oscillator trimmers.

Sequence of Alignment:

- Align i-f amplifier.
- Align short wave, Band C.
- Align short wave, Band B.
- Align broadcast, Band A.

I-F Alignment

Set the test oscillator to 175 kc and connect its output lead to the control-grid cap of the 6A7 tube.

Peak the i-f output transformer tuning condensers, C-13 and C-14. These are mounted under the chassis, as shown in Fig. 2.

Peak the i-f input transformer, mounted on top of the chassis.

Repeat the adjustments to secure greater accuracy.

R-F Alignment; Band C:

Loosely couple the output of the test oscillator to the antenna lead of the receiver, leaving the antenna connected. If it is impractical to use an actual antenna, the test oscillator can be connected directly to the antenna lead of the receiver, in series with a 400-ohm resistor and with no antenna connected to the receiver.

Set the test oscillator to 14,500 kc and tune in its signal. Then adjust C-3 for maximum output.

R-F Alignment; Band B:

Loosely couple the output of the test oscillator to the antenna lead of the receiver, leaving the antenna connected. If it is impractical to use an actual antenna, the test oscillator can be connected directly to the antenna lead of the receiver, in series with a 400-ohm resistor and with no antenna connected to the receiver.

Set the test oscillator to 4500 kc and tune in its signal. Then adjust C-2 for maximum output.

R-F Alignment; Broadcast, Band A:

Couple the test oscillator to the antenna lead of the receiver, with the antenna connected; or connect the oscillator directly to the receiver antenna lead, in series with a .00025-mfd. condenser and with no antenna connected.

Set the test oscillator to 1400 kc and tune in its signal. Then adjust C-1 and the trimmer on the middle section of the variable condenser for maximum output.

Set the test oscillator to 600 kc and

tune in its signal. Then adjust the padding condenser, C-8, for maximum output. The variable gang condenser should be "rocked" back and forth a degree or two while making this adjustment.

Repeat the 1400-kc adjustment and then the 600-kc adjustment.

VOLUME CONTROL

The volume control in these models consists of variable coupling between the primary and secondary of the i-f output transformer. It sometimes happens that the movable coil slips on its shaft with the result that the volume cannot be reduced to zero, or else that it passes through zero and then begins to increase again as the volume-control knob is turned counter-clockwise. This condition can be corrected as follows:

Tune in a strong local station.

Slightly loosen the set screw that holds the movable coil bracket to the volume-control shaft, so that the coil can be slipped around the shaft.

Turn the volume-control shaft all the way counter-clockwise.

Leaving the shaft in this full counter-clockwise position, slip the movable coil around the shaft to the point of minimum volume.

Securely tighten the set screw.

If, with the coil turned to the point of minimum volume the volume still is too high, it can be reduced by rearranging the flexible leads. If improperly arranged, the capacity coupling of these leads may prevent a low enough minimum volume. However, it is a simple matter to shift the leads and so reduce the volume.

Fada Model 160

The circuit of the Model 160 is shown in the diagram on page 449. A 6A8 is used as mixer and oscillator. This feeds a single stage of i-f using triple-tuned transformers in which is employed a 6K7 tube. The 456-kc output of this stage feeds the diode plates of a 6H6 tube. Diode P-1 is used for detection and diode P-2 for avc. Control bias is placed on both the mixer and i-f tubes.

The detector diode is not biased, as it is returned to its individual cathode through resistor (8). The avc diode is biased to provide delay action. This is accomplished by connecting the avc cathode K-2 to a point on the voltage divider which is positive 18 volts above ground. Initial bias for the 6A8 is supplied by cathode resistor (45), and initial bias for the 6K7 i-f tube by the cathode resistor (46).

The a-f component of the signal in the load circuit of the detector diode is impressed on the control grid of the 6F5 a-f tube through the volume-control potentiometer (44). The 6F5 tube is biased by cathode resistor (21). The output of this tube is resistance coupled to a type 6F6 power pentode. This tube is also cathode biased—by resistor (47).

All voltage and parts values are given in the diagram. The voltage readings are based on a line voltage of 118, and should be measured with no signal input and the waveband switch in the right-hand position. The reading on the anode of the 6A8 oscillator is 202 volts at 4.1 ma.

In order to adjust accurately the various trimmer condensers of the receiver in accordance with the following instructions, it is essential to use a shielded signal generator capable of giving a modulated carrier which can be attenuated at 456 kc, 600 kc, 1500 kc, 6 mc and 15 mc.

This receiver is equipped with an automatic volume control which necessitates setting the manual volume control of the receiver to its maximum position to insure accuracy in alignment. To control the signal output of the receiver it will be necessary to use the attenuator control of the signal generator.

ADJUSTMENT OF I-F CONDENSERS

The six intermediate-frequency condensers are located on the sides of the cans; with plate adjustment at bottom, link circuit in center and secondary at top, in each case.

1st—Disconnect the outside antenna system from the receiver.

2nd—Disconnect the control-grid lead from the 6A8 tube.

3rd—Connect the high-potential lead of the signal generator to the control grid of the 6A8 tube, and the low potential side to the receiver "ground" lead.

4th—Place an output meter (copper oxide type) across the speaker voice coil so that variations in signal output can be noted.


5th—Place the signal generator in operation and adjust the carrier frequency to 456 kc. Regulate the attenuator control of the signal generator so that the output signal is low enough to insure accuracy in adjusting the i-f condensers.

6th—With the aid of a bakelite type screw-driver, adjust the six i-f condensers to resonance; adjusting first the i-f condenser across the secondary wind-

(Continued on page 449)


Supreme Instruments Corp., Greenwood, Miss., U. S. A.

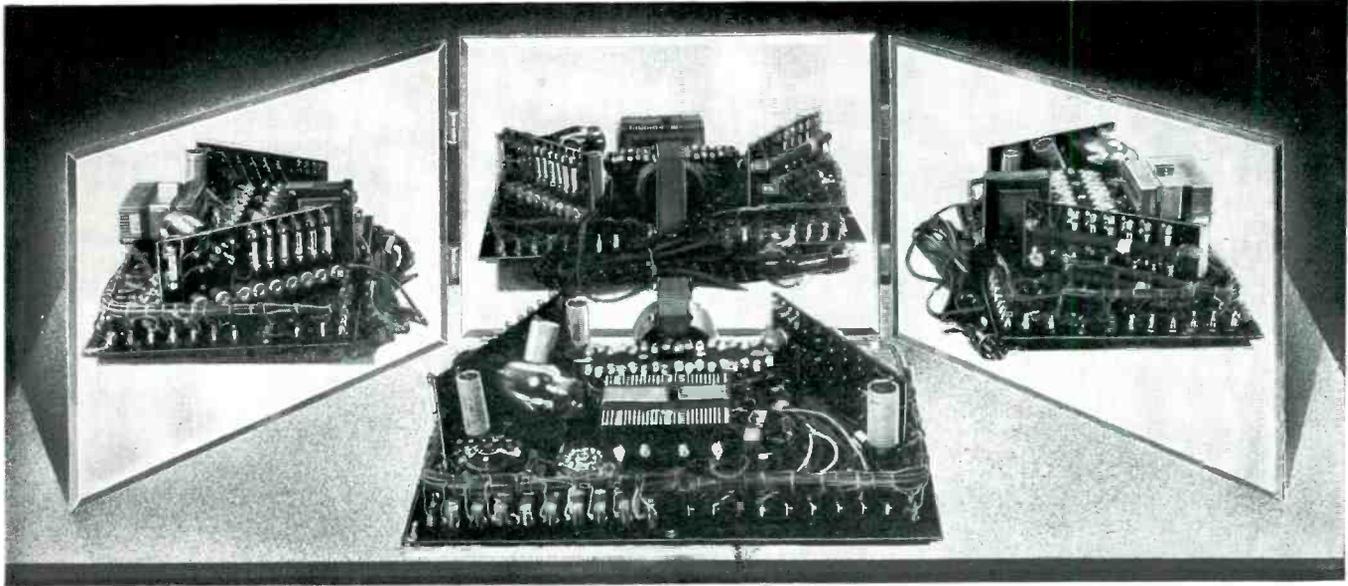● Export Dept., Associated Exporters Co., 145 West 45th St., New York City, N. Y. Cable Address, LOPREH, N. Y. ●



From All Angles . . . Inside or Out . . .

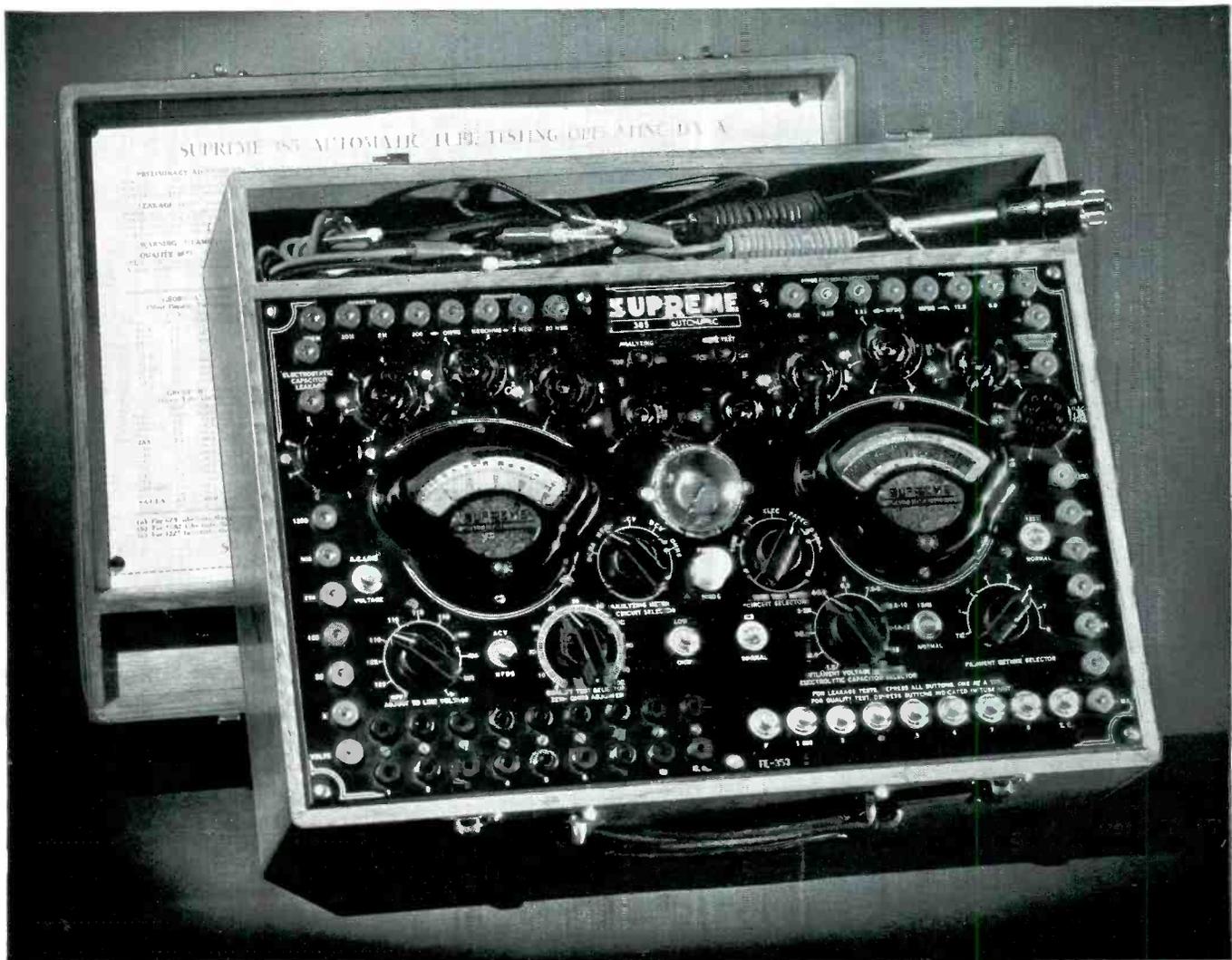● Superb Engineering ● Quality ● Appearance



Write For Catalog ● See Your Jobber

OCTOBER, 1935 •

SAY YOU SAW IT IN SERVICE

447

- - SUCCESS - -

FREE ADD-A-UNIT CABINETS MAKE BIG HIT WITH RADIO SERVICEMEN

TOBE offers the most sensational condenser value in years. Servicemen everywhere have simply deluged us with orders. There's a double reason for such unusual success. First, of course, because TOBE gives servicemen FREE—a steel ADD-A UNIT cabinet with every kit. Every serviceman needs a cabinet such as this and the TOBE Add-a-Unit way is the best method of getting it.

But more important—TOBE Condensers have been

used by servicemen for years. They are justly famous. TOBE Dry Electrolytic and Tubular condensers are first choice among engineers and servicemen where quality and performance are the first consideration. They cost *more* to make; they are painstakingly fabricated—but they deliver thousands of hours of uninterrupted and trouble-free performance. By using TOBE Condensers you will be doing yourself a service and gaining satisfied customers as well. Order one or more kits today!



TOBE Condenser Kit No. 1

TUBULAR Surgeproof and Openproof CONDENSERS. OIL PROCESSED!

Amt.	Cap. MFD	D. C. Volts Working	Type	Price List	Total
3	.001	600	M - 1@.18	.54	
2	.002	600	M - 2@.18	.36	
3	.005	600	M - 5@.18	.54	
5	.01	600	M - 10@.18	.90	
5	.02	600	M - 20@.20	1.00	
5	.05	400	M - 50@.22	1.10	
5	.10	400	410 T@.25	1.25	
3	.25	400	425 T@.35	1.05	
3	.50	400	450 T@.50	1.50	

Total List Price \$8.24
Less Serviceman's Discount of 40% 3.30

Net \$4.94
Plus fair cost of one TOBE Add-a-Unit Cabinet 2.00

TOTAL VALUE \$6.94
Servicemen's Net Cost of Condensers with FREE Cabinet. (TOBE Condenser Kit No. 1) only.... **\$4.94**

TOBE Condenser Kit No. 2

DRY ELECTROLYTIC CONDENSERS

In the Most Popular Sizes.

Amt.	Cap. MFD	Peak Volts D. C.	Type	List Price	Total
2	8	500	618	1.05	2.10
5	8	500	518	.95	4.75
2	4	500	514	.75	1.50

Total List Price \$8.35
Less Servicemen's discount of 40% 3.34

Net \$5.01
Plus fair cost of one TOBE Add-a-Unit Cabinet 2.00

TOTAL VALUE \$7.01
Servicemen's Net Cost of Condensers with FREE Cabinet. (TOBE Condenser Kit No. 2) only.... **\$5.01**

The illustration above shows both Kit No. 1 and Kit No. 2—already packed in an Add-a-Unit Cabinet which comes to you FREE! The illustration at the right shows a series of cabinets locked together to form a completed unit. Use TOBE Condensers and assemble your own cabinets. Order from your Wholesale Distributor today. If he cannot supply you, order direct from

TOBE DEUTSCHMANN CORP.
CANTON, MASSACHUSETTS

Export Dept.: 105 Hudson St., New York, N. Y.



SERVICEMEN !! MODERNIZING OBSOLETE RADIOS PAYS BIG MONEY

There are hundreds of radios in your own neighborhood which have become obsolete, yet which are difficult to replace because of long association with their owners. Now, an amazing *new* idea developed by Zeh Bouck has shown hundreds of Servicemen how they can make Big Money by converting obsolete radios in expensive cabinets, into modern *All-Wave, World-Wide* Radios of superlative performance. Leading Magazines have endorsed this plan and featured it editorially. Watch for their comments, or better still, send 25c for Mr. Bouck's new Book plus a complete Sales Promotion Kit which will get you into this lucrative phase of radio.

TOBE DEUTSCHMANN CORP.
Canton, Massachusetts

- Enclosed find \$..... for Condenser Kit No. together with FREE Add-a-Unit Cabinet.
- Enclosed find 25c for Zeh Bouck's new Book together with Complete Merchandising Kit.

Name

Address

City..... State.....

Auto-Radio . . .

Atwater Kent Model 776

The complete circuit of this auto-radio receiver is shown in Fig. 1. The 6D6 r-f tube and 6D6 i-f tube are cathode biased, with the voltage on the r-f cathode being equal to the combined drop in resistors R-1 and R-9. The 6A7 mixer is biased by cathode resistor R-5. The output of i-f transformer feeds directly the diode D-2 which is used for detection. The voltage across R-11 regulates the "squelch" or minimum signal level at which the detector diode begins to function. The combined voltage across R-11 and R-12 acts as the delay bias on the avc diode, D-1, which is fed through condenser C-9. This combined voltage also biases the control grid of the 85 triode.

CIRCUIT CHANGES

In early sets R-11 is 5000 ohms with

a drop of 4 volts, and R-12 is 15,000 ohms with a drop of 10 volts. In late sets these two resistors are each 10,000 ohms and there is approximately 6 volts drop across each. At the same time this change was made, the first a-f plate resistor, R-14, was changed from 0.1 meg. to 0.25 meg. With the 0.1-meg. resistor, the drop across it is 55 volts and the plate voltage is 125. With the 0.25-meg. resistor, the plate voltage is lower.

Early models do not have tone control, and the "A" filter circuit is slightly different from that shown.

The condenser C-17 in the lower right-hand corner of the diagram of Fig. 1 is 0.2 mfd, not 2 mfd.

ADJUSTMENTS

Equipment:

The oscillator should cover the i-f and r-f frequencies. It should be well

shielded and have a good attenuator. If the oscillator is not well shielded, it may be difficult to peak the pre-selector trimmers, owing to pickup by the first detector grid circuit. In general, it is advisable to connect a .00025-mfd fixed condenser in series with the pick-up lead at the antenna terminal of the set.

Use a sensitive output meter and keep the receiver volume control turned on full volume, and the tone control at high pitch. This is necessary to minimize the effect of the automatic volume control action of the set which would otherwise prevent sharp peaking of the trimmers.

A special i-f coupling unit should be used (A. K. No. 42590). This is placed on the grid cap of the i-f or first detector tube, as specified, and the lead that normally connects to the grid cap is attached to the coupling unit.

Use a non-metallic screwdriver for adjustment of the trimmers.

General:

Do not adjust trimmers unless the necessity is clearly apparent.

On the oscillator trimmer there are

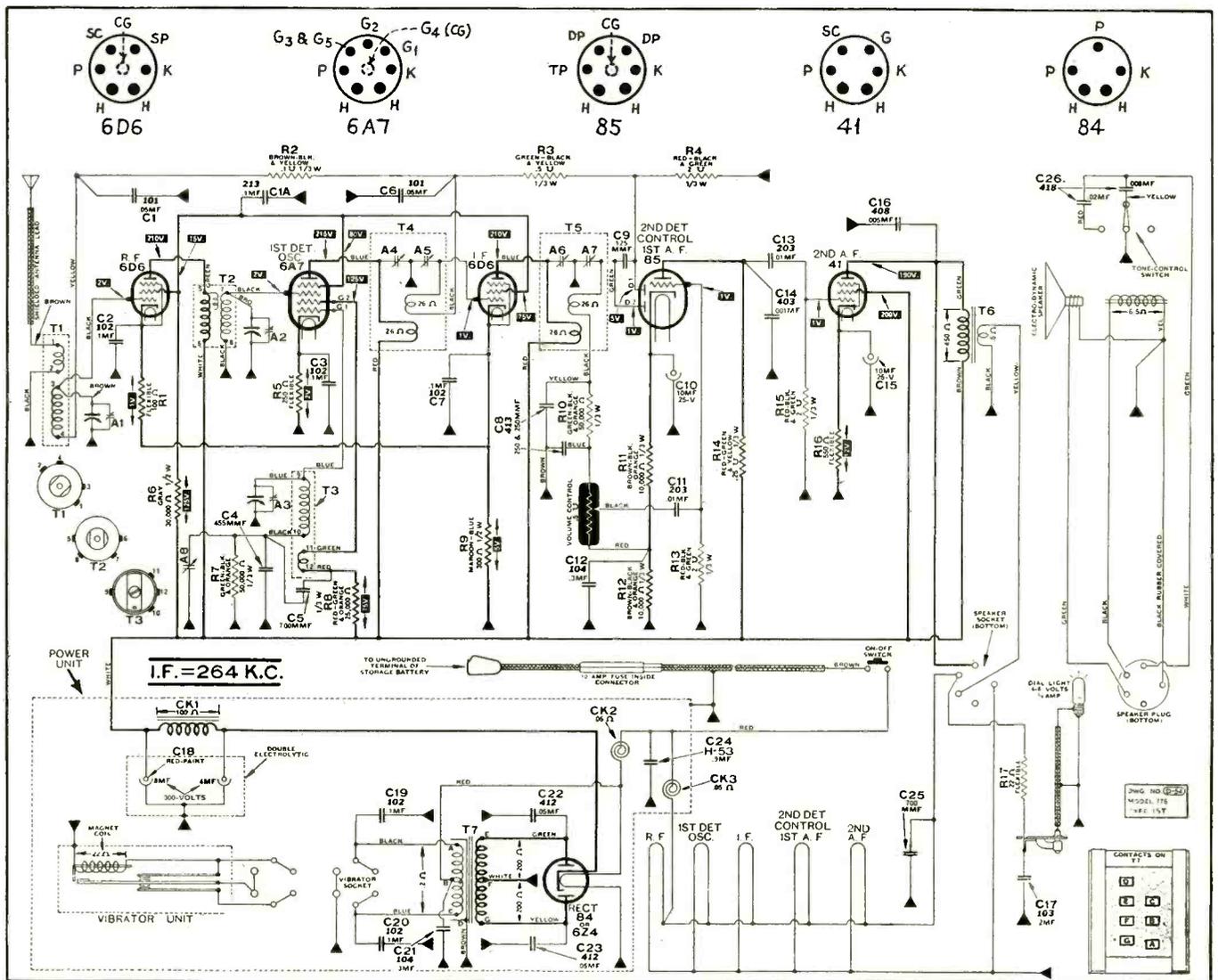


Fig. 1. Complete circuit diagram of the Atwater Kent Model 776 auto radio.

two different settings at which the signal will be received. Always use the first of these two positions as you screw the trimmer in from a loose or minimum-capacity position. *This is important.*

Check the i-f trimmers first.

In checking the set, do not disturb the position of the wiring any more than necessary.

Dial Calibration:

The dial calibration depends on the oscillator circuit of the set, providing that the i-f trimmers are correctly aligned to their specified frequency. The pre-selector (r-f and first detector) trimmers do not affect the dial calibration, but simply affect sensitivity.

The oscillator trimmer is used to adjust the high-frequency end of the scale.

The oscillator tracking condenser adjusts the low-frequency end of the scale.

If adjustment of the oscillator trimmer and the oscillator tracking trimmer does not correct the dial readings, it may be necessary to replace the fixed oscillator tracking condenser or the oscillator transformer.

Naturally the i-f trimmers should be checked and adjusted, if necessary, before any attempt is made to align the r-f oscillator trimmers.

ALIGNMENT

For location of trimmers, see Fig. 2. *I-F Trimmers:*

Connect i-f test oscillator (264 kc) to i-f tube by means of the i-f coupling unit. Peak A6, A7. Connect i-f test oscillator to first detector tube and peak A4, A5.

Dial-Pointer Adjustment:

Connect oscillator (560 kc) to antenna and ground and peak A8 while rocking the variable condenser for maximum sensitivity. Then adjust dial

pointer to 560-kc mark by turning the adjustment nut at rear of control unit. *R-F Trimmers:*

Connect r-f test oscillator to antenna and ground of set.

With oscillator and dial at 1500 kc, peak A3, A2, A1. Check frequency alignment at 560 kc.

Motorola Magic Eliminode Notes

The Magic Eliminode in the 1935 Motorola consists of a combination of an extremely efficient high-frequency filter and balancing system.

In practically every car the Magic Eliminode will completely eliminate ignition interference when the installation of the set is made according to instructions and the intensity of the motor noise is not so great so as to be beyond the range of the Magic Eliminode.

The Magic Eliminode should not be expected to work miracles or to do the impossible, but after analyzing its operation you will find it works on good, sound and fundamental principles.

ELIMINODE FILTER

The filter used in the Magic Eliminode operates most effectively at the lower broadcast frequencies; therefore, if when tuning the set from about 800 to 550 kc no motor noise is heard, it can be assumed that the noise level is within the range of the Magic Eliminode and the noise then heard when tuning toward 1500 kc may be easily balanced out with the movable eliminode coil and complete elimination of motor noise secured.

The Magic Eliminode will work in any car of welded steel body construction when the installation is made according to instructions and the accessories supplied with each set are properly used.

It is not guaranteed to work in extremely old cars in which the joints (not welded) between the various body sections have separated and rusted. It will not work when the interference level is so high as to be entirely beyond the range of the eliminode, but if by proper shielding and bonding the level is reduced sufficiently so that the filter will handle it at 600 kc, the balancer will take care of it over all other portions of the tuning range of the receiver.

In like manner there will be found many cars in which the filter is so effective that it alone completely eliminates all motor noise and balancing is not required. In that case *it is unnecessary to even connect the interference feeder to the Motorola.*

FORD V-8 INSTALLATION

To further acquaint yourself with the use and operation of the Magic Eliminode, let us follow a step-by-step procedure in the installation of a Motorola Model 100 in a 1934 V-8 Ford car.

The above combination is used because of the great sensitivity of the Model No. 100, and the fact that no distributor suppressor is used in the V-8 gives us a most extreme combination.

(1) Mount the set near the right center of the dash with the control head if preferred in the instrument panel.

(2) Mount the speaker near the steering column on the left side of the dash.

(3) Connect the "A" lead to a convenient point on the six-volt wiring as close to the starter switch as possible. Insert the speaker, dial light, tone control plugs in the receptacles at the right end of the receiver. Dress wires so that their position is remote to steering column and other wiring, control rods and pipes.

(4) Connect the two flexible control shafts to the radio by inserting them in their respective sockets and turning each approximately a quarter turn to the right.

(5) Take the small antenna lead-in junction box that has the short piece of shielded loom attached to it and fish the car antenna lead through this loom until the lead extends into the junction box. Now insert the set antenna lead-in through the ferrule in this box so that the two leads may be spliced together within the box and be totally shielded. *Spot the shield to the ferrule with solder to secure a good ground.* Next mount the junction box on left side of the cowl where paint has been removed and mount it up into the corner post. Bolt the box down firmly so as to secure a

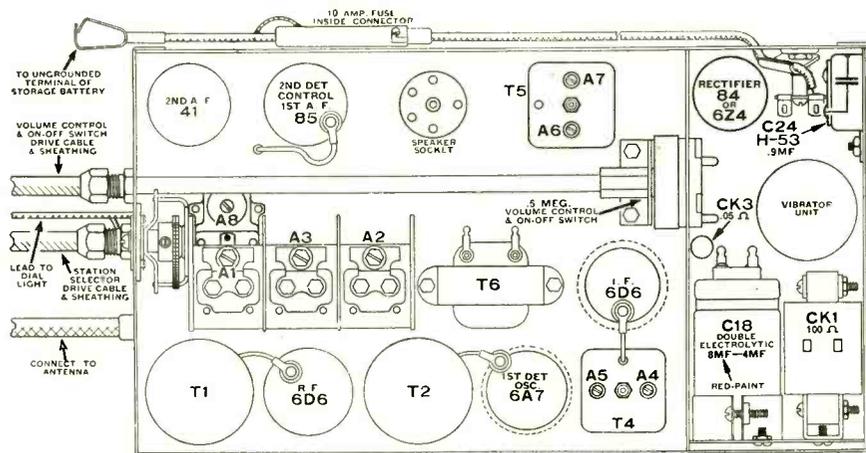


Fig. 2. Chassis of Atwater Kent Model 776.

Metal-Tube Merits PLUS Glass-Tube Efficiency "G" ARCTURUS "G" TUBES

(GLASS COUNTERPART OF ALL-METAL TUBES)

SELDOM has any development so quickly been accepted by critical engineers, dealers and servicemen who must be sure, in advance, of their every move.

Tested and efficient performance is assured in Arcturus "G" Tubes, built along experience-proved methods.


Arcturus "G" Tubes, identical in characteristics and pin connections to all-metal tubes, are interchangeable, and will do all that the metal tube does—and do it better!

No wonder, then, that several leading manufacturers use "G" Tubes in their sets and are able to ship in quantities . . . that the trade is using and preferring "G" Tubes where efficiency must be a certainty.

Some of their salient features are:

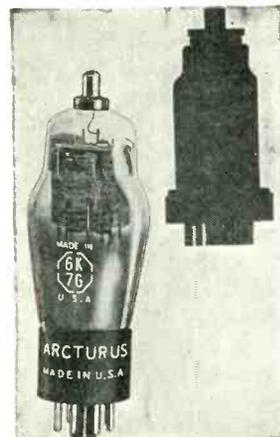1. Characteristics identical to all-metal tubes.
2. Pin connections and base same as all-metal tubes.
3. Type numbers correspond to all-metal tubes (except that our 5Y3 is a counterpart of the 5Z4).
4. Positively interchangeable with all-metal tubes.
5. Proved efficiency; built along conventional manufacturing practices; not an experiment.
6. Available now in quantities.
7. Currently used as initial equipment by several leading set manufacturers.

Characteristic Chart on Arcturus "G" Tubes will be sent on request. Arcturus Radio Tube Co., Newark, N. J.



Showing the general appearance of the "G" line tubes, with all-metal tube base-connections and guide pin.

ARCTURUS RADIO TUBES

Pioneer of 6 out of the 7 Fundamental Developments in a. c. tubes.

Build a NEW THORDARSON Public Address Amplifier

3 Sizes—6-Watt, 18-Watt, 30-Watt

New in design—new in performance—engineered to excel in every detail! You can net a nice profit by selling or renting these high-gain, high-fidelity THORDARSON amplifiers to auditoriums, ballrooms, carnivals, etc. By building your own, you save from \$20.00 to \$50.00 over the cost of a ready-made amplifier, yet have a unit incorporating the very latest developments, superior to any on the market. These amplifiers give high-fidelity amplification, exceptionally high gain, negligible hum, and realize their full rated output without

distortion. The 6-watt unit will supply two speakers; the 18-watt, four; and the 30-watt, six large speakers.

Get the Foundation Unit and Complete Instructions from Your THORDARSON Distributor

The Foundation Units are furnished complete with sockets and terminal strips, drilled and ready for assembly. The amplifiers use only standard parts—many of which you already have. Detailed assembly instructions furnished FREE.



Outstanding Features

- Rich full bass tone—natural high notes.
- Full power output without distortion.
- Hum is negligible.
- Gain from crystal mike: 6-watt, 106.2 Db.; 18-watt, 114.9 Db.; 30-watt, 118.4 Db.
- Any type of microphone may be used without changing the circuit.
- Provides current for carbon microphone.
- New input circuit—over-all gain compensated for any type of input circuit.
- Low and high impedance input terminals for radio, phonograph, or line input.
- Pre-amplifier an integral part of circuit.



Ask Your THORDARSON Distributor for Descriptive Catalogs, or Write
THORDARSON ELECTRIC MFG. COMPANY

500 W. HURON ST., DEPT. J, CHICAGO, ILL.

perfect ground. (*This is extremely important.*)

(6) Connect the dome-light filter in the dome-light circuit and ground its case thoroughly to the car body. Connect the generator condenser to the generator cutout. Connect the other condenser supplied, to the primary post of the ignition coil and ground it under a gear case cover stud or connect the ammeter condenser to the ignition switch, ground it to the instrument panel and connect noise feeder to the point where condenser is grounded. Place the screen under the floor mat on the right side of the toe boards and ground it to car body. Ground both sides of the hood thoroughly at their rear edges.

(7) Turn on the radio and the car motor and tune the dial across its tuning range to check for interference. *If no interference is encountered*, the installation is complete and no further work is necessary. *Do not connect the interference feeder as it is not needed.*

ELIMINATING INTERFERENCE

If, however, there is no interference at 600 kc, but it appears when tuning toward 1500 kc it will be necessary to use the balancer.

Proceed as follows:

With the set turned on and tuned to about 1200 kc, remove the volume control shaft bushing from its socket and insert it in the Magic Eliminode socket (located a little to the rear and above volume control socket), and turn volume knob all the way to the left. Next attach the clamp on the free end of the interference feeder to the choke rod, throttle rod or instrument panel. Now turn the volume control knob to the right until the noise is balanced out.

If the balancing coil travels its full length before balance is reached, it will be necessary to move the feeder clamp to another spot on the choke or throttle rod or some other point on the car, such as instrument panel, dash, etc., until a point of balance is secured.

If, when the set was first checked for motor noise, it was found that the noise could be heard at 600 kc, it indicates that its level is too high for the filter and it will be necessary to reduce its intensity by better grounding of all parts of the radio installation, *changing position of lead-in loom*, bonding instrument panel to dash, etc., or changing the mounting position of the antenna lead junction box to secure a better ground. *This is extremely important* and should be determined by trial. As soon as the interference level is brought down within the range of the filter at 600 kc,

the balancer may be employed to eliminate all interference over the rest of the tuning range of the receiver.

IMPORTANT POINTS

When making an installation with the Magic Eliminode be sure to remember the following:

(1) *That a good mechanical installation and perfect grounding of every part of the set is very important.* Do not expect a slipshod installation to give good results.

(2) The Magic Eliminode will eliminate interference within reasonable limits only, as encountered in any standard automobile. It cannot be expected to work in cases when, special high-voltage ignition coils, spark intensifier, ignition boosters, or ignition wiring changes have been made. *Remember it does not work miracles.*

(3) Use all accessories as supplied with each set and follow instructions carefully.

(4) When balancing out interference keep the hood down and grounded and have the car doors closed.

(5) Do not connect the interference feeder clamp to its point of interference pickup until after checking the filter only. If the filter is found to be sufficiently effective *do not use the interference feeder.*

In some cars there may exist a slight trace of interference when accelerating the engine. This may be overcome by connecting a Motorola dome light filter in series with the primary breaker point wire between the coil and distributor and ground it to the engine block.

Locating Motorola Interference Feeder

With regard to the installation of Motorola receivers, the guesswork can be taken out of properly locating the interference feeder during installation in the following manner:

(1) Complete the installation except the balancing.

(2) Screw the movable eliminode coil to the position of maximum coupling (clockwise direction).

(3) Closely study and remember the approximate amount of interference being picked up by the receiver.

(4) Disconnect the antenna lead at the junction box.

You can now apply the clamp on the interference feeder to any part of the motor, choke rod, throttle rod, oil pipe, ignition system, instrument panel, electric lock, cable, etc., that will produce a level of interference in the set slightly greater than the amount that you previously heard coming in over the aerial,

and this may be done with the hood of the car up if working in the motor compartment. After securing the proper point of hook-up, reconnect the antenna lead and turn the balancer in the counter-clockwise direction until balance is produced.

L. C. DITTMAR. *Courtesy Motorola*

Installing Motorola GM Model Sets on Roof Aerial

When installing GM model sets on roof aerial, always connect a .00015 mica condenser in series with the aerial lead. This condenser may be conveniently mounted in the antenna junction box. Its use is necessary because this set is designed to operate on the GM 47 under-car aerial, having a capacity of approximately 150 mmfd, and if used on a roof aerial without a series condenser you will be unable to properly track the antenna trimmer of the first tuning condenser.

GENERAL DATA

(Continued from page 449)

nal generator and insert a 250-mmfd mica condenser in its place.

2nd—Turn the wave-band selector switch to the right—broadcast position.

3rd—Adjust the carrier frequency to 1500 kc.

4th—Set the calibrated dial of the receiver to read 1500 kc.

5th—Adjust the BC. oscillator shunt compensator in the right coil can for maximum signal output.

6th—Adjust the BC. detector shunt compensator in the left coil can for maximum signal output.

BC. OSCILLATOR SERIES TRIMMER

1st—Adjust the carrier frequency output of the signal generator to 600 kc.

2nd—Turn the calibrated dial of the receiver to pick up this 600-kc signal.

3rd—With the aid of a bakelite type screwdriver, adjust the BC. oscillator series trimmer until a maximum signal is indicated on the output meter. To insure perfect alignment it is necessary to "rock" the ganged variable condenser in order to follow the maximum signal output. This trimmer is on the extreme left of the front base plate of the chassis.

4th—Having determined the maximum peak of the BC. oscillator series trimmer, re-adjust the carrier frequency of the signal generator to 1500 kc. Turn the calibrated dial to 1500 kc and re-adjust BC. oscillator shunt compensator and BC. detector shunt compensator for maximum signal output as outlined in the foregoing instructions.


Fear not



fair damsel
CENTRALAB
 will save you

"S#" that noisy control. This calls for heroic action, my good man. Get "CENTRALAB," the serviceman's friend, if you would save the goil.

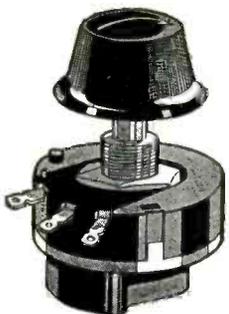Thousands of servicemen, everywhere, know the secret of smooth, noiseless controls . . . CENTRALAB.



For "better than ever before" results use CENTRALAB RADIOHMS for replacement . . . a small stock services practically all makes.

Every Radio Service Man should be a member of the Institute of Radio Service Men

Centralab

Milwaukee, Wis.

**RADIOHMS SUPPRESSORS
 FIXED RESISTORS**



*Actions Speak LOUDER
 Than Words!*



The manufacturer of the famous 4-Pillar Radio Tubes is making and delivering *all* types of the new Metal Tubes as initial equipment for 1936 receivers and for jobbers' and dealers' replacement stock.



SEEING IS BELIEVING . . .

but one can't see if METAL TUBES are even "lit", much less tell by simple examination if they are *perking* properly. This is where the good service men plus good test equipment come in. Each radio development makes good servicing more necessary. Raytheon's service deals give service men a wide range of instruments from which to choose. Write for full details. Also get the new Technical Tube Chart: 8th Edition (including all metal tubes). It's free!



RAYTHEON
TRADE-MARK
4-PILLAR RADIO TUBES

RAYTHEON PRODUCTION CORPORATION

30 East 42nd St., New York, N. Y. 445 Lake Shore Drive, Chicago, Ill.
 55 Chapel Street, Newton, Mass. 555 Howard St., San Francisco, Cal.

RAYTHEON PRODUCTION CORPORATION
 Dept. F10A, 30 East 42nd Street, New York, N. Y.

Please send 8th Edition Tube Chart

Name.....

Address.....

City.....

ON THE JOB . . .

A VERSATILE TESTER FOR VIBRATORS

By A. R. MOSELEY

THE unsung part of an automobile radio that comes in for much verbal abuse, because it refuses to operate after an uncomplaining life of service, is really a remarkable device and is responsible for the compact, efficient auto radios that are available today. This device is the vibrator and it is called on to run on low voltage from a run-down battery with the car lights on and the engine off, or on high voltage when the generator is feeding current to a well-charged battery and none of it being taken by the lights. Furthermore, the vibrator must operate on a high voltage under a "no load" condition until the tubes heat up.

The tester described in this article has proven its worth many times when adjusting points and in deciding whether the vibrator is or is not the cause of failure of the radio. It is not designed with the idea of making comparisons with the manufacturer's values, but to furnish the Service Man with a means of determining the worth of a vibrator. He can set his own standard for comparison.

VIBRATOR TYPES

In general, vibrators fall into two classes: Full-wave non-synchronous, sometimes called inverters; and full-wave synchronous, or self-rectifiers. As each Service Man is called on to service only a small group of the many vibrators now made, he can adapt this tester to his own business.

TESTER DETAILS

The fundamentals around which this tester is built are: A transformer, tube, meter and load, with suitable condensers and resistors to make the conditions under which the test is made as near as possible to actual operating conditions. In Fig. 1 the fundamental circuit is shown above the dotted line.

THE TRANSFORMER

Almost any auto-radio transformer can be used, but a Majestic transformer, if used, affords a place to mount Majestic vibrator units and makes possible the testing of a unit which otherwise could not be tested. The single-pole, double-throw switch S-3 makes the center tap of the transformer secondary

high or low depending on whether a full-wave non-synchronous vibrator with a rectifying tube, or a full-wave synchronous vibrator, is being tested. Of course, when the latter type is being tested no tube should be in the socket.

THE LOAD

The load is shown as a variable resistor, R-3, but it may be a tapped voltage divider; in fact, two resistances are enough, a low of 2000 or 2500 ohms and a high of 5000 or 6000 ohms. With these two values of load it is possible to set current and voltage standards which the vibrator on test must meet before it is OK'd. Two meters are shown, but the cost may be reduced by the use of either one, if fixed loads are used.

To further simulate actual operating conditions a resistance, R-1, and shorting switch, S-2, have been put in the battery circuit. The rating of this resistance will be determined by the transformer used and should be such as to reduce the voltage on the vibrator to about three volts. Three volts is the low limit used by manufacturers in designing their vibrators. The high limit of eight volts can be reached by using four cells of two six-volt batteries, or it can be approximated by using a battery with a high voltage and a charger.

THE SOCKETS

To this nucleus may be connected sockets for plug-in vibrators. In the lower part of the diagram are shown three sockets, two for inverters and one for full-wave self-rectifiers. These sockets are suitable for many of the most

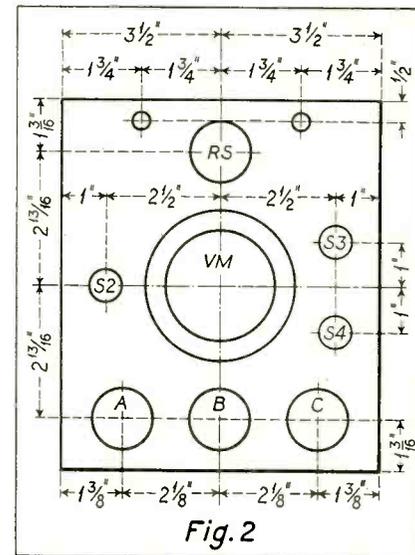


Fig. 2

A suggested layout for the vibrator tester.

popular makes of vibrators and other sockets may be added for almost any type plug-in vibrator, some of which take special sockets. Plugs with leads and clips can be made up for vibrators that do not plug in, but are connected by leads. When socket A or B is being used, the switch S-3 is in the lower position, while with socket C and no tube the switch is in the upper position.

A means for reversing the battery polarity adds to the versatility of this tester and a double-pole double-throw knife switch mounted on the test bench panel would not only be useful for this purpose, but for testing auto radios as well.

CONSTRUCTION

As there are no radio-frequency currents to be concerned with, this outfit may be built very compact. A suggested layout is shown in Fig. 2. The panel is 7" x 8" in size with holes for the four sockets, meter, three switches and bind-

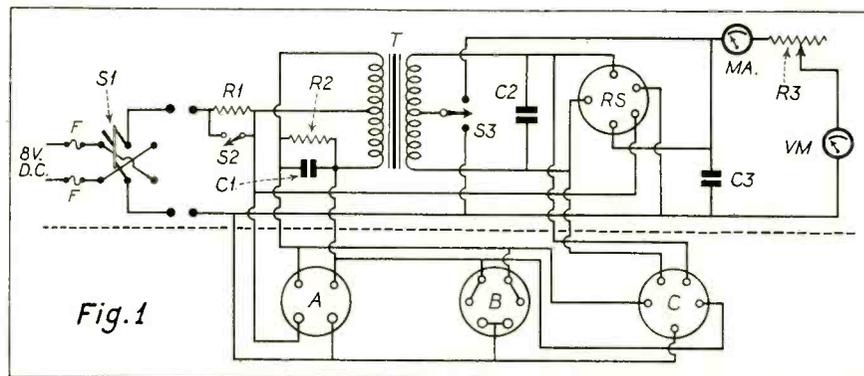


Fig. 1

Circuit diagram of the auto-radio vibrator tester described in the accompanying text.

Ready Now!



PROOF
that Serving
SERVICE MEN
is more than mere "lip service"
at FEDERATED

**Send for Your Copy—
It Protects Profits!**



WHEN dealing with Federated, your rights are respected, your profits protected! Our list price catalog is tangible evidence of what we mean by Cooperation! . . . With it, there's no need to lose out on sales . . .

Revealing no wholesale prices, Federated's LIST PRICE Set and Sound Equipment Catalog rescues many an order, creates many a profit! . . . Other Federated Services acclaimed by professional radio men include: Technical help from specialists, Pick-Up Service that avoids "splitting" orders, and a Low-Price Policy that guarantees . . . you never overpay at Federated!

Specify Catalog S105



8

BRANCHES

Speedier Service

NEW YORK CITY

25 Park Place
BArclay 7-7582

CHICAGO, ILL.

1331 So. Michigan Ave.
VicTory 4444

ATLANTA, GA.

546 Spring St. N. W.
Hemlock 4613

PITTSBURGH, PA.

343 Blvd. of the Allies
AtlantIc 9119

PHILADELPHIA, PA.

120 North 7th Street
Walnut 1663

NEWARK, N. J.

226 Central Avenue
MArket 2-5390

BRONX, N. Y.

534 E. Fordham Road
SEdgewIck 3-5904

JAMAICA, L. I.

92-26 Merrick Road
(168th St., off Jamaica Ave.)
REpublic 9-8187

ing posts. Underneath can be mounted the rest of the parts and all will fit into a box 7" x 8" x 6". Switch S-4 takes the place of rheostat R-3, for the load must be fixed as only one meter is used. S-4 is a single-pole double-throw toggle switch and changes the load from 2500 ohms to 5000 ohms.

The construction of this tester presents no difficulties in layout or wiring. However, it is advisable to use a good rubber-covered wire as the voltages in some of the circuits are quite high.

Auto-Radio Vibrators

In the manufacture of vibrators elaborate precautions are taken to prevent entrance of any minute particles of dirt, etc. Due to the small tolerances allowed in the construction of such units, small particles of foreign matter are liable to cause serious trouble by getting between the points on the vibrator reed. As a result, some manufacturers even wrap their vibrators in cellophane.

It might also be well to state that the largest percentage of the auto-radio trouble is due to improper sealing of repaired vibrators or to worn-out units. Probably it would be well to consider the useful life of a vibrator to be in the vicinity of 1000 hours.

Service Men will do well to handle vibrators with as much care as they do their own watches.

George F. Baptiste.

Remote Speakers

The difficulty of proper impedance matching in remote-speaker installations is greatly exaggerated. However, it is not a job for the "penny-pincher" and, if done at all, should be done well.

Magnetic speakers and blocking condensers are out. To satisfy the modern consumer, nothing less than a good dynamic will do. And, your modern customer isn't going to tolerate a drop in volume or tone quality when using the remote speaker. For these reasons tell the prospect that the job cannot be done with second-hand material or bargain parts that he may have on hand . . . this would constitute an actual waste in time and head-work. Make it clear that the installation must be a special one, custom-built to his individual requirements, if it is to be a credit to both of you.

THE SPEAKER

First of all let us consider the speaker. My first choice is a good permanent-magnet dynamic with an a-c operated


dynamic second. Find out what sort of set it is to be connected to and determine approximately the voice-coil impedance of its speaker and the amount of power it will handle. Then select a remote speaker which will approximate these characteristics.

CONDUCTOR TO SPEAKER

Do not try to feed any remote speaker direct from the plates of the tubes either with or without blocking condensers . . . it's rotten engineering and a sure way to get in wrong with the Underwriters. The line to the speaker should be of low impedance with one side grounded. Up to distances of 50 feet or so, feed direct to the voice coil; for distances over 50 feet, use a 200- or 500-ohm line with matching transformers. Durable, rubber-covered lamp cord makes a good conductor. High-priced jobs may use built-in wiring.

OUTPUT TRANSFORMER

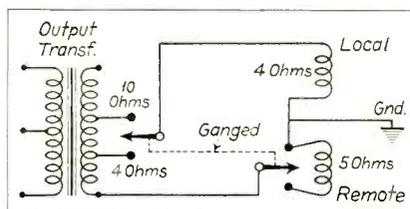Discard the output transformer used with the set and install a good universal



one. There are many of these units on the market that are designed to mount anywhere and to match anything into anything in two-ohm steps. For long-distance jobs, get a transformer to work into a 200- or 500-ohm line and a couple of transformers to match the speakers to the line.

THE SWITCHING SYSTEM

The switching system does not need to be complicated. For the majority of cases, a double-pole, double-throw switch will serve the purpose.

A TYPICAL INSTALLATION

The accompanying illustration shows a typical installation using two speakers, each speaker having approximately 4.5 ohms voice-coil impedance. The output transformer gave either 4 ohms or 10 ohms impedance when working out of push-pull 42's. When the remote speaker was not in use it was shorted out, while the other side of the switch changed to the 4-ohm tap; when the remote speaker was used the short was removed and the impedance raised to 10 ohms. This was desirable since it compensated for the resistance losses in the line.

In actual test, although the two

speakers were dissimilar and slightly different in sensitivity and tone quality, it was impossible to detect any change in tone of the local speaker when the remote speaker was cut in; and unless one listened very closely at the exact instant the change was made, it was impossible to detect any change in volume. Also, equal volume could be obtained from the speakers by means of a little adjusting.

Feeding the "high" speaker through a 100-ohm potentiometer arrangement will give surprisingly good results but should not be used for a volume control or for too great a degree of attenuation, as it will affect the tone and volume of the other speaker . . . and it wastes power. I prefer to shunt the voice coil of the "high" speaker. This automatically raises the output of the other speaker with little change in tone, and allows one to alter the tone quality of the "high" unit. If lower volume and less high notes are required, use a simple rheostat. If lower volume with retention of high notes is desired, use the rheostat with a choke wound with No. 20 wire on an old audio-transformer core. Slide the core in and out of the coil and adjust the rheostat until best results are obtained.

It is well to remember that when a rheostat is used to cut volume and high notes, the other speaker may sound too high-pitched. This may be remedied by using a fixed condenser of 0.02, 0.05, or 0.1 mfd. Proper choke-condenser combinations will permit the accentuation or elimination of any band of frequencies, but the need for these is seldom met in the realm of remote-speaker installations.

Several types of universal output transformers should be stocked. All will probably use different systems of tapping, and from these a tap system may be selected that will give the proper impedance change with the greatest possible convenience in switching. While mismatches of 10 to 20 percent may look bad on paper, it takes a good ear to detect them in the field.

CAUTION

Tell the customer not to operate the change-over switch with the set operating at moderate to high volume. This takes most of the load off the output tube or tubes and the voltage developed across the primary of the output transformer will go up to 1500 or 2000 volts . . . and more in many cases. Broken-down insulation and a burned-out transformer will result. Pentode sets are by far the worst offenders.

F. C. Wolven.



"QUIET" . . . is the insistent demand of millions who today own all-wave receiving sets. Give them what they want, by installing

NOISE-MASTER ALL-WAVE ANTENNA

This remarkable unit, A.A.K. patented and engineered with traditional CORWICO thoroughness, is building sales and good will for dealers and service organizations everywhere. It is actually AUTOMATIC electrically, requiring no adjustment or manual operation after it has been installed by a qualified Service Man.

FOR EVERY SET AND LOCATION

"NOISE-MASTER" picks up and clarifies feeble overseas signals, straining out the "man made" static that sometimes seems to make radio a curse instead of a blessing. Minimizing the noises caused by household appliances near the set, "NOISE-MASTER" improves broadcast as well as shortwave reception. It successfully operates more than one set from a single aerial. We guarantee that "NOISE-MASTER" will eliminate noise when properly installed, and urge you to recommend it at every opportunity.

Cat. No. 14 **\$6.75**
List Price


Send for latest complete literature describing this and other up-to-the-minute antenna units.



CORNISH WIRE CO., Inc.
30 Church Street
New York City

Use the New YAXLEY Manual

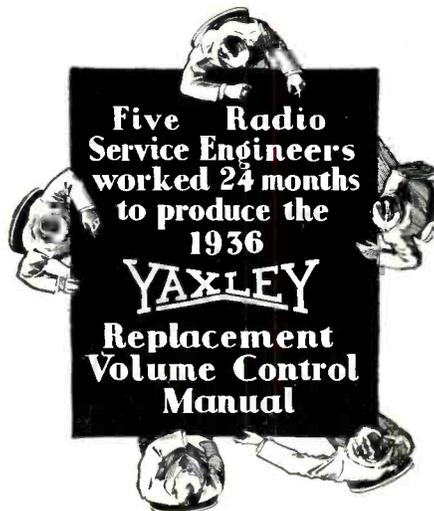and save yourself time
... trouble and money



Did the first issue of the Yaxley Replacement Volume Control Manual astonish you? The new edition will surprise you even more!

Five radio service engineers—specially trained for the Herculean task—spent two years in compiling it. Thousands of radio sets were examined—their schematic diagrams and volume controls thoroughly studied. All existing volume control circuits were carefully investigated.

Endless hours of research—compilation—testing—proving! Twenty-four months in the making, yet a free copy of this newest and greatest of replacement volume control manuals is yours for the asking.

The 1936 Yaxley Replacement Volume Control Manual lists over 5,000 models . . . provides a greater amount of important factual data . . . and contains a complete catalog of Yaxley approved radio products.

It's the most complete work of its kind that any service man ever saw. It's the most valuable work of its kind that any service man could possibly own.

YAXLEY MANUFACTURING DIVISION
of P. R. Mallory & Co., Inc.

INDIANAPOLIS, INDIANA

Cable Address: PELMALLO

Mail the
Coupon
NOW
for your
free copy

Yaxley Manufacturing Division
of P. R. Mallory & Co., Inc.
Indianapolis, Indiana

Gentlemen:

Please send me—absolutely free—a copy of the 1936 Yaxley Replacement Volume Control Manual.

Name _____

Address _____

My Jobber's Name is _____

RECEIVER CASE HISTORIES

Atwater Kent 708, 711

No signal; noisy operation on short waves: May be caused by defective tubes, silencing adjustment resistor, or wave-change switch. When checking wave-change switch resolder all connections to switch and realign set (resoldering will nearly always throw set out of adjustment).

George F. Baptiste.

Belmont 420

Whistle: Caused by oscillation in 38 power pentode amplifier. Replacing tube will correct oscillation, but trouble will again develop. Check control-grid and cathode-grid resistors for their proper value. Also check plate resistor of 76 r-f amplifier.

George F. Baptiste.

Crosley 137

Local reception, no distant reception: Caused by defective oscillator coil. Replacement necessary.

George F. Baptiste.

Emerson V4, LA, 415, 416

Lacking in pep; good local reception on higher frequencies, but low volume on lower frequencies: If voltage and tubes are okay, check antenna pickup coil. Move coil either up or down over secondary of first tuned r-f stage and realign antenna and interstage trimmer condensers. When output is satisfactory, cement antenna pickup coil in new position.

George F. Baptiste.

Ford Receivers

Noise: Ford cars equipped with the Ford and similar receivers may develop noise. This can usually be remedied by changing the ground of the shielded lead-in to the lower dashboard bolt.

Sometimes it is necessary to install a dome-light condenser. Ford patent No. 48-18823 is easy to use on all cars, and should be fastened to a convenient bolt at the dome-light center post.

L. Taeschner.

Grunow Chassis 7B, 11A

Dual-ratio drive will not stay in low-ratio position: Loosen two small screw-head bolts on drive sleeve assembly and push drive sleeve back slightly; retighten screws. If shaft will still not stay in low-ratio position repeat procedure until it will. Be sure the small bolts are screwed down tight.

Microphonic noises: Generally caused by chassis bolts being too tight. In replacing chassis after servicing do not let any of the shafts touch the wood of the cabinet.

Balancing all-wave receivers: These sets cannot be balanced with metal screwdriver. A small round piece of fibre rod filed down to a screwdriver point is the best.

Keith F. Martin.

Grunow 660, 662, 650

Bad tone: Change coupling condenser between 75 and 42 tube, using 0.01-mfd 600-volt unit. This condenser is located on left side of chassis, mounted behind short resistor strip (chassis turned upside-down, front towards repairer). These condensers should be changed in all of these models as soon as they come into the shop.

Keith F. Martin.

Kadette ES-19, ES-20

No operation: The 0.05-mfd bypass condenser in tone-control circuit may be shorted out. This will burn up the 50,000-ohm tone control. Replace both units.

This set also shorts out in the electrolytic condenser block. The red lead to this block is the plus of the 8-mfd and the 16-mfd units. The black lead is the negative of the 8-mfd condenser, while the yellow is the negative for the 16-mfd unit.

Keith F. Martin.

Karadio

Distant reception; no local reception: Condenser X in accompanying illustration partially shorted. This reduces

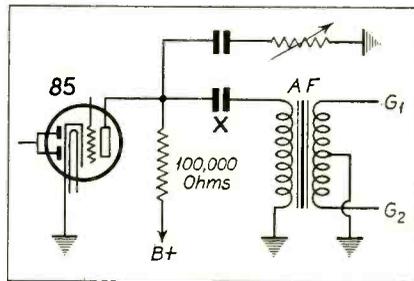


plate current. Also, for strong signal developed bias will be high enough to cause complete cut-off. This source of trouble is misleading, giving every indication of being a faulty oscillator circuit using a 36 tube.

A. A. Laramy.

Kolster K-60, K-62, K-100

High noise level and intermittent rasping noises which seem to be caused by a very critical r-f or first detector circuit: Voltage and current OK in these circuits and throughout set. No noisy or changed-value resistors.

Replace all noisy condensers. If trouble persists, remove r-f input coil. Take coil out of shield, and remove lead to

control grid, replacing it with waxed cotton-covered wire (rubber-covered wire is not satisfactory). Drill out hole in top of coil shield where control-grid lead comes through and insert rubber bushing or grommet as an insulator. Thoroughly clean bottom of coil shield and its bottom plate—also chassis—with sandpaper or carbon tetrachloride; then reassemble coil in shield and fasten solidly to chassis with screws. Discard old grid-cap clip and use "National Grid Grip" clip bent to solidly grip cap on tube. Next replace control-grid lead to first detector with one of same units used for the r-f tube. (The grid clip must be so solidly fastened to cap that tube can be moved around in socket by pulling and pushing on lead without clip rocking or slipping on cap.)

A. E. Lindner.

Kolster K-130, 132

Oscillator tube (56) stops functioning: If tube tests okay, check grid condenser and grid resistor for change in value. Also check oscillator plate resistor. Replacement of defective unit will put receiver back in operation. If the volume is now low it is probably caused by first audio-frequency transformer not supplying sufficient power for 47 power pentode tubes. This is a push-pull stage and the trouble is caused by the first audio (type 56) tube plate resistor increasing in value, thus resulting in a drop in plate voltage.

Tuning indicator failure: Caused by 10,000-ohm resistor connecting the neon tuning indicator to ground changing in value.

George F. Baptiste.

Lyric SA-120 Chassis

Failure to track on low frequencies: Caused by wearing of variable condenser gang bushing. This causes the rotary section to push backward, throwing the variable condenser gang out of proper position. Remedy by placing a thin washer between the bushing on the variable condenser gang (rotary section) and the frame of the condenser.

Defective resistor, condensers: The 20,000-ohm screen-grid resistor often opens. Replace with 10-watt, 20,000-ohm unit.

The 5-mfd tubular condenser in the screen of the second i-f tube is often the cause of bad tone. Also, 5-mfd tubular condenser in cathode of suppressor tube shorts out. Both of these condensers should be replaced as they do not have the proper peak voltages.

Keith F. Martin.



"E. H. Rietzke
SPEAKING!"



... America's Original
Radio Engineering School ...
OFFERS FOR THE FIRST TIME

A Newly Developed
Home Study Course in

SERVICE and PUBLIC ADDRESS ENGINEERING

... at a price you can afford!

This new CREI Service Course is the outgrowth of a study that disclosed a great need for more *Technically Trained* men in the Service field. It is NOT an ordinary service course ... for it BEGINS where other courses END. It is NOT for beginners. We are anxious to offer this course only to *professional* Servicemen who feel the need for Technical Training in Service Engineering. It is PRACTICAL right from the first lesson ... written in your own language, and it will start paying for itself right from the beginning.

Write Today for Complete Information

Every week new improvements, new equipment, new circuits, etc., are introduced. It is necessary that every Serviceman have a keener knowledge of fundamentals to be able to handle new problems. CREI needs no introduction. Right now, there are thousands of our students in all parts of the world ... and any of them can tell you what Technical Training can do for you!

GOOD Men Always Have GOOD Jobs

Radio is a young and growing industry. There is plenty of opportunity ahead for every man who is willing to put in the effort necessary for success. This is not an easy course. It takes time, study and effort ... but is the surest and shortest cut to SUCCESS!

Now Is the Time to Plan Your Future
in a Field Where TRAINING Pays


FREE!

Write for our new SERVICE COURSE SUPPLEMENT, which gives complete details of the course, and a lesson-by-lesson outline. Prices and easy terms are also included.

ILLUSTRATED
CATALOG ..

Mailed on Request

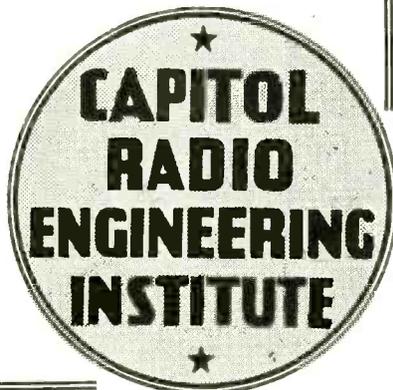14th and Park
Road, N. W.
Washington
D. C.
Dept. S-10



New! **MUTER**
Interference Filters



This "Traffic Cop" of Radio absolutely eliminates the man-made interference that comes in over the power line by merely attaching the Filter directly to the set itself.

Sell these filters with confidence and GUARANTEE their operation, because *they will do the job*. There's a real need for them.

Ask your jobber or take advantage of our trial offer. Write Dept. D-10.

MAIL THE COUPON!

THE MUTER COMPANY

1255 South Michigan Avenue
Chicago, Illinois



Please ship me one Muter Interference Filter at your trial offer of \$1.80 (\$3.00 list, less 40%).

- I am enclosing \$1.80
 Ship it C.O.D. for \$1.80

Name

Address

City State

RECEIVER CASE HISTORIES—continued

Philco 38-B

No operation on high frequencies: Remove oscillator coil and dip several times in cup of hot paraffin, being sure to leave a good coat of paraffin on the coil. Change 6000-ohm resistor in cathode of type 15 tube to a 4000-ohm unit.

Oscillation: If set oscillates all over dial, replace 0.5-meg resistor in screen circuit of second detector with 1-watt, 0.4- or 0.35-meg unit.

Keith F. Martin.

Philco 66

Set dead: Check for shorted bypass condenser (No. 27) in plate of 75 tube. This unit is tied between two 70,000-ohm, 0.5-watt resistors. Replace with 0.1-mfd, 600-volt condenser.

Keith F. Martin.

Philco 80

Set dead, no plate voltage on 36 second detector: Look for open 1-meg resistor.

Keith F. Martin.

Philco Shadow-Tuning Unit

Difficulty in aligning shadow-tuning unit: Bend shadow-lamp bracket to position giving proper shadow indication. If this causes shadow to be off center on screen, reverse leads from shadow-unit coil and readjust shadow-lamp bracket. Care should be taken when working on chassis or adjusting i-f trimmers not to short i-f plate circuit to ground. This forces shadow-tuning vane to revolve violently back and forth and is often cause of trouble.

W. B. Styles, Jr.

Pilot 31-81 Rainbow Super

Improperly rated resistor: Trouble with 10,000-ohm, half-watt resistor between first detector-oscillator screen and second detector screen. Replace with 1-watt unit.

Cut-off: Try a 6,000-ohm resistor as replacement for 10,000-ohm, half-watt unit in cathode circuit of detector-oscillator. This resistor is shown as 6,000 ohms in Rider's 4-6, but many sets of an earlier run used 10,000 ohms. Also circuit in Rider's shows a 2A5 in output, but earlier sets used a 47.

F. C. Wolven.

Radiola R-4

Ineffective volume control: Set blasts at full volume with volume control completely ineffective. Test r-f and i-f tubes for cathode-to-heater short or leakage. This effect may be intermittent. In case volume control replacement is necessary improvement may be made by using a 7,500- or 10,000-ohm unit (depending

upon signal strength in locality). The 8,000-ohm screen-to-cathode bleeder may then be changed to 12,500 ohms and returned to ground. The volume control should be set for a 500-ohm minimum. The chief advantage lies in smoother control due to excellent taper of replacement-type units.

F. C. Wolven.

Sparton 930-931 Models

Voltages O.K., bypass condensers O.K., tubes O.K.; still the set would only play from 1500 to 850 kc. . . . no stations above 850 kc. Thought at first might be condenser gang shorted at low-frequency end. Tested and found them O.K. Put my finger on stator of 4th section of variable condenser and I could receive low-frequency stations along with local stations, knowing thereby that oscillation was taking place and therefore no reception above 850 kc.

Took out the r-f section (not the bandpass section) and after prodding around and unsoldering several leads found the r-f plate choke of 1st 484 to be cold soldered and the plate of this 484 was getting plate voltage through the r-f coupling coil. (In these models there is an r-f coupling coil and a plate choke coil in parallel with the coupling coil.) Made a good soldered connection and the set played all over the dial.

Also watch out for the 15,000-ohm bleeder resistor in these models increasing in age. The writer took one out that read 15,000 ohms when cold and 67,000 ohms when warmed up.

E. Tuchlu

Wells-Gardner Peaks

I-F Peaks: The following is a complete list of the i-f peaks for the Wells-Gardner receivers produced in 1933, 1934 and first half of 1935:

Series	I-F Peak
00A	175
00B	175
0C	456
02A	175
02AA	175
05A	262
05AA	262
05BA	262
06A	175
07A	175
2B	456
5B	262
5D	456
5E	175
5Y (auto)	175
6B	175
6S (auto)	175
6U (auto)	262.5
7C	175

7D	456
9B	456
Z6Z1 (auto)	262

Series 7C are of the 6-volt "B Batteryless" type, while Series 6B are operated from 32 volts d-c.

Zenith I-F Peaks

In the following table are given the i-f peaks for the latest Zenith glass- and metal-tube receivers:

Chassis	I-F Peaks
5401	456.0
5405	456.0
5513	252.5
5513-A	252.5
5619	252.5
5621	456.0
5704	456.0
5903	456.0

And here is a list of the chassis models and the receiver models in which they are used:

Chassis	Receivers
5401	4-P-26; 4-T-26; 4-P-51; 4-T-51
5405	4-V-31; 4-V-59
5513*	5-S-29; 5-S-56
5513-A*	5-S-29; 5-S-56
5619*	6S-27; 6-S-52
5621	6-V-27; 6-V-62
5704*	7-S-28; 7-S-53
5903*	9-S-54; 9-S-55

The chassis models followed by asterisks are metal-tube receivers.

Zenith MH

Oscillator weak and cutting out, even after resoldering coil connections: If capacitors are good, put in new oscillator coil.

Earle J. Bancroft

Unstable AVC

In servicing any receiver in which the avc has become unstable, it is a good idea to look for slight leaks between the grid windings and the high-voltage circuits. I have found that a slight leakage will defeat the voltage supplied from the avc without showing up in any other voltage or resistance reading taken with ordinary meters. This trouble occurs in sets having a loop of wire for coupling on the r-f coils and moisture or a break in the wire covering. This permits a megohm or so of leakage under high-voltage, which is just enough so that the positive voltage working into the grid winding will cancel the negative voltage from the avc tube. Under this condition strong signals can not be handled. If the no-signal bias is also decreased the set will squeal and distortion will occur.

C. L. Fairchild



... A
Webster-
Chicago
Product

HG-417

NEW! 4-Stage Amplifier

for Crystal Microphone or Phonograph

FOR general public address work and party call systems—schools, churches, theatres, factories—this NEW 4-Stage Amplifier for crystal microphone or phonograph is ideal.

Many Desirable Features

Self contained. Completely enclosed. Field excitation for two dynamic speakers. Output 17 watts. Tapped output transformer. Fader control system. Speaker and microphone connections terminate in polarized plugs. Tubes, 1 6C6, 1 53, 3 2A5's, 1 5Z3.

Sound Men! Dealers!

HERE'S YOUR CHANCE. Earn More!

with this new Webster-Chicago unit. Get complete details—NOW! And remember—there's only ONE Webster-Chicago. It's IN Chicago.

Write for Bulletin—NOW!

THE WEBSTER CO., 3829 W. Lake Street,
CHICAGO, ILL.



SELL MORE SETS

• THE NEW BROWNIE All-Wave Antenna sells easily with every set—and keeps the set sold. For fine short wave reception is impossible without an all-wave antenna. The Brownie is one of the finest antennae on the market today. We challenge a comparison for distance, volume, clarity and freedom from interference.

The ANTENNA that Carries a Profit for the Dealer

Hook up a Brownie on a set in your showroom. Demonstrate its many superiorities. You will find it a quick money maker for there's a real profit on every Brownie you sell.

The Brownie is manufactured by a famous old line maker in the electrical field. It is constructed on the Balanced Doublet System with a new, super-efficient, matching transformer. Comes complete with necessary accessories for quick installation. Cash in on the national advertising campaign, starting soon in Colliers and the Saturday Evening Post. Write today for our quick—profit making deal.

PORCELAIN PRODUCTS, INC. Dept. B FINDLAY, OHIO

• JEFFERSON •

Universal Replacement Chart

{ Tells Transformer to Use }
{ on 2000 Different Sets }

Free Chart Simplifies Transformer Replacement

Radio men say "Best thing I ever saw," when they see the new Jefferson Universal Replacement Chart. Hangs on wall—tells at a glance what model Jefferson will duplicate or even improve on the performance of the original transformer in 2000 sets—over 95% of all A. C. sets.

Just as chart simplifies selection and eliminates mistakes, the Jefferson line of transformers solves servicing problems.

Universal filament windings equipped with taps to operate all popular tubes both 2½ or 6.3 volt heaters. Frequently required models made in 4 styles of mounting. Small stock permits immediate service—no waiting for a transformer that will fit. All leads clearly identified—another aid to speedy service without mistakes.

Make your work easier, speedier, hence more profitable by stocking this remarkably adaptable line.

Mail coupon today for new Chart and Catalog.

Jefferson Electric Co.
BELLWOOD, ILLINOIS
(Suburb of Chicago)
Canadian Factory:
535 COLLEGE ST., TORONTO



One of the popular styles of housings in which Jefferson Replacement Transformers are assembled.

JEFFERSON ELECTRIC CO.
Bellwood, Illinois

Please mail transformer selection Chart and Catalog.

Name

Address

City State

JEFFERSON ^{Radio} Transformers

ASSOCIATION NEWS . . .

THIRD ANNUAL NEW YORK IRSM CONVENTION

The Sales Managers' Club will fire the opening gun at the Third Annual New York Convention of the IRSM to be held at the Hotel Pennsylvania in New York City with a meeting at 3:00 P.M. on Friday, October 25. Charles Golenpaul, Chairman of the New York division, will officiate. Leading Chicago manufacturers will be in attendance.

The Convention proper will start at 8:00 P.M., with President Edgar C. Arnold presiding in collaboration with Fred L. Horman, Chairman of the Second Region. The evening session will be given over to technical discussions with the possibility of at least one man high up in the affairs of the radio industry appearing.

The Service Section of the Radio Manufacturers Association will meet at 10:00 A.M., Saturday, October 26, F. B. Ostman, Chairman, officiating.

The Saturday and Sunday afternoon sessions will be used for symposiums covering timely subjects of interest to the technical branches of the industry. Then on Saturday night the Committee reports the possibility of another radio personality together with two lecturers, one of which had been definitely decided upon—Walter Jones of Hygrade-Sylvania Corp.

The Parts Distributors have scheduled a meeting for 8:30 P.M. on Saturday, October 26. Maurice Despres will preside. All parts distributors are urged to be present.

On Sunday morning at 10:00 o'clock there will be an IRSM membership meeting to which only members of the Institute who are in good standing will be admitted. President Arnold will preside.

The Manufacturers' Representatives will go into a huddle at 2:30 P.M., Sunday. This meeting, while for manufacturers representatives solely, will be opened by one of the officers of the IRSM at the special request of the representatives themselves. However, the representatives will choose their own Chairman who will take charge of the meeting.

The Sunday night session will wind up the Convention. Arrangements have been made for Dr. O. H. Caldwell, a well-known figure in the radio industry, to deliver a brief talk, which will be followed by the technical lectures to close the meeting.

The following companies have reserved exhibit space at the Third Annual Convention and Trade Show of the Institute of Radio Service Men, October 25-27, 1935, Hotel Pennsylvania, New York City. See accompanying floor plan.

Aerovox Corporation.....	22
American Phenolic Corporation.....	6 R
Arcturus Radio Tube Company.....	43
Astatic Microphone Laboratory, Inc. 31 R	
Atlas Resistor Company.....	6 L
D. R. Bittan Sales Co.....	6R, 7, 8
The Brush Development Co.....	31 L
Bruce O. Burlingame.....	1
Caldwell-Clement, Inc.....	39
Carron Manufacturing Co.....	7 L
Central Radio Laboratories.....	26
The Clough-Brengle Co.....	20
Cornell-Dubilier Corp.....	9
Dale Parts, Inc.....	28 and 29
BRYAN DAVIS PUBLISHING CO.....	12
Tohe Deutschmann Corp.....	2
Electrad, Inc.....	35
Electronic Laboratories, Inc.....	44
Federated Purchaser, Inc.....	4
John M. Forshay.....	20, 21
Harry W. Gebhard.....	18, 19
General Transformer Corp.....	7 R
Hickok Electrical Instrument Co... 21	
Hygrade Sylvania Corp.....	27
International Resistance Co.....	19
Jefferson Electric Co.....	3
P. R. Mallory & Co.....	37
National Union Radio Corp.....	45
Ohmite Manufacturing Co.....	8
Operadio Manufacturing Co.....	16
Philco Radio and Television Corp. 33, 34	
The Radiart Corp.....	13
Radio City Products Co.....	42
Radio Instrument Co.....	46 R
RADIO RETAILING.....	38

RADIO TODAY.....	39
Raytheon Production Corp.....	36
RCA Manufacturing Co.....	23, 24, 25
John F. Rider, Publisher.....	11
Wesley W. S. Scharp.....	31
F. E. Schmitt.....	5
SERVICE.....	12
Shure Brothers Co.....	5 L
Paul Smalley.....	37
Solar Manufacturing Corp.....	17
Standard Transformer Corp.....	32
Supreme Instruments Corp.....	1
Technical Appliance Corp.....	5 R
Thordarson Electric Mig. Co.....	18
Triplett Electrical Instrument Co... 41	
Unified Transformer Co.....	40
Ward Leonard Electric Co.....	14
The Webster Company.....	30
Weston Electrical Instrument Corp. 15	
Wholesale Radio Service Co.....	10
Yaxley Manufacturing Co.....	37

CLEVELAND IRSM SHOW

On Saturday evening, Nov. 9th, there will be held a conference of radio Service Men from points within a radius of 300 miles of Cleveland; at the same time there will be a Soharsm meeting. This conference and the Trade Show following on Sunday and Monday will be held in the Grand Ballroom and in the Red Room of the Hotel Cleveland. An attendance of over 1000 is anticipated. A number of the exhibitors at the New York Show have arranged to move their complete exhibits to the Cleveland Show, which will be just two weeks later.

The program this year will follow along nearly the same lines as last year. In addition to the usual exhibits, there will be a large number of demonstrations of unusual radio and electronic phenomena. Several nationally prominent radio engineers will be in attendance and will present interesting papers during the lecture periods.

In order to be certain that all Service Men in this area are able to take advantage of the many educational features offered at this Exposition, a movement has been started to arrange for the radio service departments of all stores and for all independent service shops to be closed at 12 o'clock noon on Monday, November 11th.

NEAL BEAR, Trade Show Committee.


NEW YORK CHAPTER, IRSM

Under the auspices of the New York Chapter of the IRSM, RCA gave the first of a series of lectures which over a thousand enthusiastic members attended.

RCA presented a bang-up program of lectures which consisted of a lecture by M. M. Brisbin, who went thoroughly into the design of the 1935 RCA receivers and told us that he would be back again later in the season with two more lectures. About half-way through his lecture there was an intermission and time out for some entertainment and the presentation of the door prizes.

Mr. Morrissey of New York won first prize, which was an RCA oscillator; the five RCA manuals were won by Mr. R. Lasarouse of Brooklyn, and the RCA out-

(Continued on page 467)

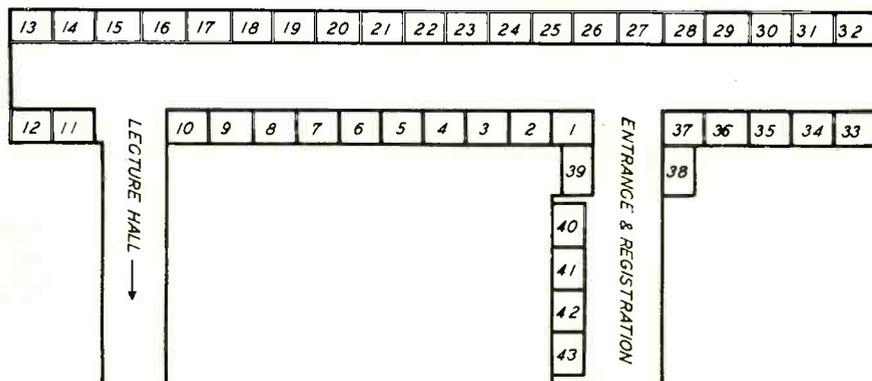

The booth layout of the IRSM convention exhibition space. See above listing for company names.

DAYRAD

Announces!

NEW INDEX SYSTEM

DAYRAD

TUBE TESTER

SIGNAL GENERATORS

With fundamental bands as low as 5 meters

SERIES 58 SET TESTERS

Complete flexibility for all metal tubes

*Remember, no special selector switches
are needed for testing metal tubes*

MEETS APPROVAL OF ALL TUBE MANUFACTURERS

WRITE FOR DETAILS

THE RADIO PRODUCTS CO.

125 Sunrise Place

Dayton, Ohio

SUBSIDIARY OF BENDIX AVIATION CORP.

Contractors to the United States Army Air Corps and Department of Air Commerce



CHROMSHIELD AMPLIFIER KITS


Another source of revenue for the enterprising service dealer. Schematic and point-to-point layouts furnished with each amplifier kit.



CK-7 METAL TUBE PREAMPLIFIER KIT

The CK-7 preamplified kit uses two metal 6C5 tubes in cascade amplification. A 6C5 is used as a rectifier. Careful placement of parts and shielded components is responsible for the extremely low hum and noise level in the CK-7 preamplifier. The overall gain is 55 DB.

	List	Net
CK-7 transformer kit mounted on chassis	\$16.00	\$9.60
AK-7 accessories includes all necessary resistors, condensers, sockets, AC cord and plug, hardware, wire	6.00	3.60

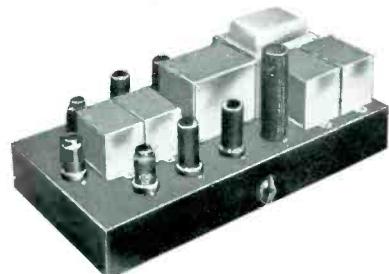

CK-8 METAL TUBE SUPER POWER AMPLIFIER

35 watts undistorted output; will handle up to 20 dynamic speakers. 8 tubes used: 3-6C5 triodes, 4-6F6's in Pentode A prime connection. 1-5Z4 rectifier. 95 DB gain. Input of amplifier will match crystal or ribbon mike outputs, also adapted for carbon or dynamic mikes through external transformer input.

	List	Net
CK-8 transformer kit mounted on chassis	\$34.00	\$20.10
AK-8 accessory kit for above—includes all necessary resistors, condensers, sockets, terminal strips, AC cord and plug, hardware, wire	11.00	6.60

UTC VARITAP UNIVERSAL DUPLICATE TRANSFORMERS

UTC is first to introduce a truly workable, non-complicated, highly desirable VARITAP arrangement on filament and plate windings of Universal Duplicate Transformers.

UTC VARITAP Universal Duplicate Transformers are adapted to fit more than 4000 types of sets with a minimum of chassis alterations. The SR types are provided with removable slotted brackets which permit a wide degree of flexibility in meeting mounting centers and overall chassis dimensions on any radio receiver. The VR types permit of vertical mounting with leads through bottom of chassis. However, the same degree of flexibility is permitted as to mounting centers. The mounting holes on the VR types are slotted to fit the majority of receiver mounting hole dimensions.

Thus the SR-2, VR-2, SR-3, VR-3 units will not only fit receivers requiring two separate 2½-volt windings, but also on all the new 6.3-volt receivers requiring two separate 6.3 windings.

The SR-6, VR-6 units will not only fit a great many receivers which cannot operate unless 3 separate 2½-volt windings are available—indeed these units are arranged so that they can be used in new receivers using three separate 6.3-volt windings.


The SR-5 is arranged so that it can be used on receivers using 210, 250 tubes or on Class B sets using 46 and 59 tubes at plate voltages of 425 or over.

The SR-1 is arranged so that it can be used either with 2A3 or 42A prime tubes in 10- to 15-tube sets. Either 2½- or 6.3-volt tubes can be accommodated.

The SR-4 may be used in sets using 1½- and 2½- and 5-volt tubes or 2½- and 5-volt tubes.

The VARITAP units fulfill all the requirements of universality in the radio service replacement field. These are just the units the serviceman will recommend for that replacement job.

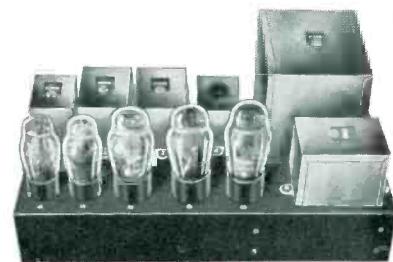
For further details on seven types of UTC CHROMSHIELD Power Amplifier Kits write for CS-1 Bulletin. Write for VR-1 Bulletin covering VARITAP and universal audio input and output transformers.



CK-1 AMPLIFIER KIT

The CK-1 amplifier has a power output of 10 watts normal—14 watts peak using 2A3 or 45 tubes in A prime operation. The overall gain is 48 DB. Two push pull stage using 56's into 45's or 2A3's makes possible a humfree high quality amplifier.

	List	Net
CK-1 transformer kit mounted on chassis	\$27.00	\$16.70
AK-1 accessory kit includes all necessary resistors, condensers, sockets, terminal strips, hardware, AC cord and plug, ready to wire	5.75	3.45

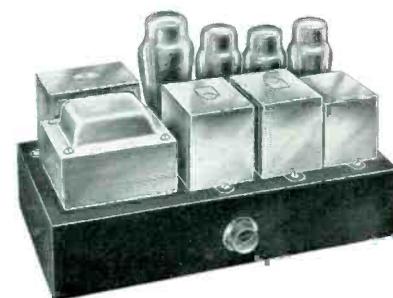

CK-2 AMPLIFIER KIT

The CK-2 amplifier kit is designed for use with crystal microphones. The gain is in excess of 100 DB and the power output is 10 watts. Only four tubes are used, including the rectifier. The plates of the first 6A6 tube are cascaded to permit very high amplification and stable voltage transfer to the second 6A6 driver tube. The final 6A6 is arranged in push pull class B operation.

	List	Net
CK-2 transformer kit with CS-35 output, including chassis	\$19.50	\$11.70
AK-2 accessory kit includes all necessary resistors, condensers, sockets, terminal strips, hardware, AC cord and plug, ready to wire	10.50	6.30



Left
SR type in horizontal mounting with removable slotted brackets.



Right
SR type for bottom chassis mounting, slotted brackets removed.



Left
SR type vertically mounted with removable slotted brackets.



Right
VR type with slotted holes for mounting with leads through chassis.

UNITED TRANSFORMER CORP.

72-78 Spring Street :: New York, N. Y.

EXPORT DIVISION: 15-19 LAIGHT ST., N. Y. C.

THE FORUM . . .

HOBBIES

Editor, SERVICE:

I think it would be interesting to learn about the hobbies of other radio Service Men. I do not believe that there are very many who are spending an appreciable amount of time building sets, experimenting with the short waves, etc., as a hobby. Personally, I like an occasional game of golf, fishing (any kind, salt or fresh water) and association meetings. Recently I started a stamp collection and find it quite interesting.

Also, I am fond of SERVICE. I read it thoroughly and receive plenty for my money.

A. S. MAGEE,
Bethesda, Md.

(Do any of you fellows go in for boondoggling?—EDITOR.)

LIKES SERVICE

Editor, SERVICE:

I have just purchased SERVICE (August) for the first time in five years of radio servicing. I am more than pleased to read such an "Engineering Knowledge Book." Talk about highlights! SERVICE is better than all the other radio magazines put together.

WALTER C. MATHIEWS,
Philadelphia, Pa.

(Thanks for the blushes.—EDITOR.)

SERVICE IN BOOK FORM

Editor, SERVICE:

After reading "The Forum" for several issues, I am prompted to write this letter.

SERVICE is all right. I have copies of all but a few early issues and my system is to get them bound in book form (every two years) at our local book bindery.

There are many things of value in SERVICE, and they overbalance the unused information for any Service Man no matter how well "he knows his stuff." For example, consider the write ups on new sets. These sets are usually not in our shops until after they appear in SERVICE, so that when my RCA dealer asks me what his latest set is all about I can tell him by just looking at the chassis. To know what systems are used in a receiver saves plenty of time when the customer is waiting for you to produce results.

Let any good Service Man tell the truth, and he will inform you that he is always studying, that he wants more mathematics, that he wants more everything . . . he knows that he needs it. So, lets have all the dope in SERVICE. It's been a good investment for me. I have been in the radio service business for 15 years and I still have a lot to learn.

C. L. FAIRCHILD,
Elgin, Illinois.

(The right dope. Why cut up magazines, only to find later that some valuable data was not kept.—EDITOR.)

ANSWERING MR. LOVELL

Editor, SERVICE:

I wrote a letter (published in May) in answer to the question concerning what the readers of SERVICE would like to have

published. What I intended to convey was not understood by some of the readers, and I would like to correct these misunderstandings.

Mr. W. A. Lovell believes that I am a newcomer, and that I don't know Ohm's law; he feels sorry for me and is willing to help me and other poor fellows who are trying to learn. Mr. Lovell's spirit is fine and deserves commendation, but I want to inform him that I have known Ohm's law for a good many years. While I have several little books explaining the theory, I only use Ohm's law in an emergency. I would rather have a schematic giving the values of the different parts and substitute for the defective ones exactly what the engineers put in the receiver in the beginning. Mr. Lovell, if you are the busy Service Man that you say you are, you should know that there is a great deal of difference between practice and theory. And, speaking of cigar-box receivers, you can set down with your pencil and figure out the line resistance, but if you will check against the manufacturer's specifications, you will find your calculations to be off by 20 to 50 ohms . . . and this same variation applies to any receiver or any circuit in a receiver using resistance. No doubt you can make the receiver perform, but when I service a receiver I try to bring back original performance.

In my letter I asked for fundamental theory. However, I really should have asked for fundamental theory pertaining to new developments. I don't care for a statement of Ohm's law, or "if the receiver is noisy, clean the condenser plates with a pipe cleaner, or file your ground connection with a piece of sandpaper." What I do want is information that will keep me abreast of the times and SERVICE is doing that very nicely. If I was a "smarty" I wouldn't need to read SERVICE or any other magazine, but I always have room for knowledge.

I also notice you took a slap at the fellows who use Rider's Bibles. I, for one, appreciate what Mr. Rider has done and is doing to help the Service Man. For your information, Mr. John F. Rider was the original editor of SERVICE, and I happened to be a subscriber at that time. I also would like to say that the Philco RMS is a wonderful help to the Service Man.

In closing I would like to suggest that Mr. Lovell get himself an RMA Resistor Color Code, an IRC Resistance Indicator and a few of Rider's Bibles. I think he will be able to do better service work in less time and he will not wear out so many pencils working with Ohm's law.

F. B. GUTHRIE,
Philadelphia, Pa.

ASSOCIATION NEWS

(Continued from page 464)

put meter was won by Mr. Steinhurst, also of Brooklyn.

Some of the well known entertainers present were: Dolly Dawn, usually heard with George Hall and Orchestra; Miss Durrell Alexander, often heard with Paul

Whiteman's Orchestra; Smiling Jimmy Ray, one of Fats Waller's proteges; Sonny Schuyler, often heard on the air with George Hall; and finally, to top off the program, Mr. Tony "Cabootch" Gruber, who gave a monologue that had the boys rolling in the aisles.

BROOKLYN NEWS

Brooklyn is still looking for a meeting place and hopes to start an extensive Fall program with a series of lectures, and is trying to get the members interested in giving their own lectures. Service Forums will definitely be held at every meeting.

Joseph Flaum.

SET ANALYZER MODERNIZING SERVICE

The Precision Apparatus Corporation, 821 East New York Avenue, Brooklyn, N. Y., are now featuring a modernizing service for obsolete set analyzers. This service is available at a standard price for the following models: Jewell Model Nos. 198, 199, 408, and 409; and Weston Model Nos. 537, 547, 565, and 566. For other models, modernization costs may be obtained upon application, it being necessary, however, to supply the following information: Manufacturer's name and model number of the complete instrument; also manufacturer and pattern number of the meters employed.

The modernized instrument allows for speedy voltage, resistance and current readings at all socket positions by the use of rotary switches. A master range selector makes possible the use of only two pin jacks, all ranges being available. Positive and negative selectors are used for obtaining socket analyses at various position pins. A current switch allows d-c current readings to be taken at any position, while an ohmmeter adjuster employs twin compensators, permitting the adjustment of all ohmmeter ranges.

The following voltage ranges are available: 0-4, 0-8, 0-16, 0-160, 0-800, a-c; 0-5, 0-10, 0-100, 0-500, 0-1000, d-c. The d-c current ranges provided are: 0-10, 0-100, and 0-500 mils; if desired, external shunts to 10 amps can be furnished for use in connection with auto-radio current tests. Resistance ranges and capacity ranges are also incorporated.

Literature may be obtained from the Modernization Division of the Precision Apparatus Corp.

NEW ARCTURUS WINDOW DISPLAY

A new and unique type of window display has just been issued by the Arcturus Radio Tube Company, Newark, N. J., for the use of its dealers and Service Men. Lithographed in 7 attractive colors, the display is a two-plane effect and carries three dynamic illustrations drawn by the country's leading artists, it is stated.

A special patented feature is employed whereby the dealer can change this new Arcturus display giving him a totally new display from day to day.

Display experts who have viewed this display in advance proclaim it as one of the outstanding pieces that has ever been produced, it is said. This display is available to Arcturus dealers and Service Men upon request to their Arcturus distributor.

HIGHLIGHTS . . .

GRAHAM RECEIVES APPOINTMENT

Hygrade Sylvania Corporation announces the appointment of Virgil M. Graham as head of the Sylvania Application Laboratory at Emporium, Pa. He will act as consultant to radio manufacturers and engineers, a position for which he is eminently fitted both through his radio engineering experience and his wide acquaintance in the industry. Mr. Graham will be assisted by Dr. Ben Kievit, Jr., who will continue in his present capacity as direct supervisor of the work conducted in the laboratory.

Since 1923, and until his acceptance of the Sylvania appointment, Mr. Graham has been Radio Engineer for Stromberg-Carlson, and assisted in the development of the first Stromberg-Carlson radio receiver to be put on the market.

He is also well known through his active leadership in technical committee work, having made important contributions to the improvement and advancement of radio standards. He edited the early NEMA handbooks of Radio Standards. Since 1931, he has been Chairman of the Standards Section of the RMA Engineering Division, was Chairman of the joint SEARMA Committee on Automotive Radio, 1932-34, and RMA Chairman of the Joint Coordination Committee of EEL, NEMA, and RMA on Radio Reception since 1933.

He is Fellow of the Institute of Radio Engineers, and a member of the IRE Board of Directors, and has been very active in IRE affairs in the Rochester Section.

Before leaving to take up his duties at the Sylvania plant, his associates at Stromberg-Carlson gave a farewell dinner in his honor, at which he was presented with a Ciné kodak and projector in appreciation of his long service and as a token of personal friendship.

WESSNER RECEIVES APPOINTMENT

S. W. Muldowny, Chairman of the Board of National Union Radio Corporation of New York, announced this week, the appointment of Mr. F. J. Wessner as General Sales Manager to succeed H. A. Hutchins, who has resigned to enter the advertising field.

Mr. Wessner has been engaged in sales promotional work with National Union since the formation of the company in 1929. As Assistant General Sales Manager, for the past five years, he has played a prominent part in the development of the National Union Service-Dealer Selling Program.

Prior to the time he became associated with National Union, he had gained a broad experience in sale direction and promotional work in his previous posts as Eastern Sales Manager of Ypsilanti Furniture Company and General Sales Manager of one of the country's outstanding textile houses.

OHMITE MOVES TO LARGER PLANT

D. T. Siegel, General Manager, Ohmite Manufacturing Company, Chicago, Illinois, announced that this company would be located in its new and larger plant at 4835 Flournoy Street after October first.

The need for additional factory space became increasingly necessary during the past year, and the new building was started the first of August. The new factory, which has more than twice the area of the old one, has been designed to furnish the utmost in shop convenience for the production of quality resistors and rheostats.

GROSS ADDS NEW DEPARTMENT

Gross Radio, Inc., 51 Vesey St., New York City, who carry a large stock of amateur equipment, have now put in a new department exclusively for the Service Man.

Their trained sales force will gladly explain the deferred payment plan on Supreme Test Equipment, it is stated.

ELECTRAD VOLUME CONTROL

Electrad, Inc., 175 Varick St., New York, N. Y., has published a 100-page Volume Control Guide just about as complete as it could be. It is a finely printed book measuring 6¼" by 9¼", and has a



looped cord—like a telephone directory—so that it may be hung by the side of the service bench, if desired, for instant use.

Replacement volume controls for practically every radio receiver built since the inception of broadcasting are clearly and accurately listed. Each model number is on a separate line, so that you can run through the listings of any one manufacturer and quickly find the set you want. For every set model number the listing includes the specification number of the proper Electrad control, its resistance in ohms, and its list price.

And here's the best part of all . . . these Volume Control Guides are free; a copy will be sent to any accredited Service Man for the asking.

SAYRE APPOINTED ASS'T. TO CUNNINGHAM

E. T. Cunningham, President of the RCA Manufacturing Company, announced the appointment of Judson S. Sayre as Assistant to the President.

Mr. Sayre, who brings many years of broad merchandising experience to his new duties, was formerly Manager of the electrical appliance and refrigeration division of the Montgomery Ward Company. Prior to that he was General Sales

Manager of the Kelvinator Corporation, with whom he had started nine years previously as Branch Manager, and held progressive positions as District Supervisor and New England Manager.

Mr. Sayre received his Bachelor of Arts degree from Ohio Wesleyan University, in 1919, and a year later his Master's degree from Columbia University. He then joined the Alexander Hamilton Institute as salesman for its famous business training courses, and remained with them for five years training new salesmen.

MODERN RADIO SERVICING, by Alfred A. Ghirardi, published by the Radio and Technical Publishing Co., 45 Astor Place, New York City, N. Y., 1300 pages, 706 illustrations, price \$4.00.

Modern Radio Servicing is really a second edition of *Radio Servicing Course*, but a rather large one, for the new edition contains 1300 pages in comparison to 182 pages for the preceding book. In planning this new volume the general style of the first issue was retained, and many additional chapters covering new topics were added.

This book has been divided into four parts. Part I has seventeen chapters devoted to the theory and construction of modern radio test equipment. The nine chapters of the second part are given over to the practical servicing of radio receivers. The third section of the book contains six chapters on specialized servicing problems, while the last part deals with vacuum-tube charts.

Part I begins with a four-page introduction and follows it with chapters on the theory of "Milliammeters, Ammeters, and Voltmeters" and "Methods and Instruments for Measuring Resistance." The remaining pages of this section are concerned with ohmmeters, condenser testers, capacity meters, output meters, vacuum-tube voltmeters, tube checkers, voltage-current set analyzers, point-to-point testing, and test oscillators. Data is included on commercial types as well as the types which may be built up by the Service Man.

Chapter titles of Part II are as follows: "Preliminary Tests for Trouble," "Peculiarities of AVC and QAVC Circuits," "Receiver Analysis by Voltage-Current Tests," "Receiver Analysis by Resistance Tests," "Testing Individual Radio Components," "Obscure Troubles Not Revealed by Analyzers," "Aligning and Neutralizing T-R-F Receivers," "Aligning and Neutralizing Superheterodyne Receivers," and "Repairing Individual Radio Components."

The third section covers the installation and servicing of auto-radio and marine receivers, and the servicing of all-wave receivers. The remaining chapters are entitled: "Reducing Electrical Interference," "High-Fidelity Receiver Problems," and "How to Sell Your Service."


Review questions are given at the end of nearly all the chapters, the total number being 723. Also, a complete, cross-referenced index has been included.

Modern Radio Servicing is a practical text on the theory, construction, and use of modern radio service equipment, and the rapid and systematic methods of radio servicing.

**For More Business
and Profits, Here's
An All-Wave Knockout!**



**TACO NOISELESS
ANTENNA**

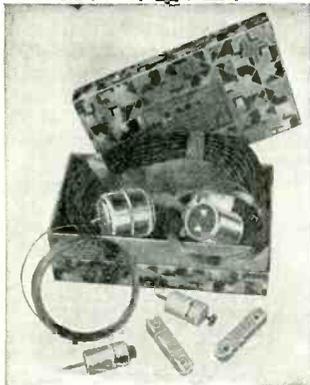

Improves broadcast, police, amateur and short-wave reception.

Permits aerial high above roof for maximum signal pickup.

Non-pickup downlead transmission line blocks all man-made static.

Kit form . . . factory assembled, wired, soldered . . . ready to string up.

Sells over counter and through service calls. Lists at \$6.75. Nice profit maker.

Best by test. Based on years of antenna specialization. We invite comparisons.



DATA Send for technical and sales facts. Order a kit from local jobber. And by all means try all systems before you decide which to handle.



**TECHNICAL APPLIANCE
CORPORATION**

17 East 16th Street
NEW YORK CITY

**"I'd Pay a Few Cents More for a
SPRAGUE ANY DAY!"**

"Remember," writes a successful serviceman, "if filter condensers fail to supply the proper voltage (as many 'bargain' condensers do) nothing about a radio can be wholly right. Other essential parts will work far below their standard of efficiency. The set might play, but never with its greatest volume or best tonal quality.

"I was surprised to find what a whale of a difference Sprague Condensers actually made in pepping up 'sick' sets. That's why I use 'em on every job.

They're cheaper in the long run—and they've helped me build a real reputation for getting *better than average results* from the average radio set."

Made in a complete line for every radio need. Sold by leading jobbers. Write for catalog.


SPRAGUE PRODUCTS CO.
North Adams, Mass.

**SPRAGUE
CONDENSERS**

Made Right Priced Right



**Cathode-Ray
Servicer**

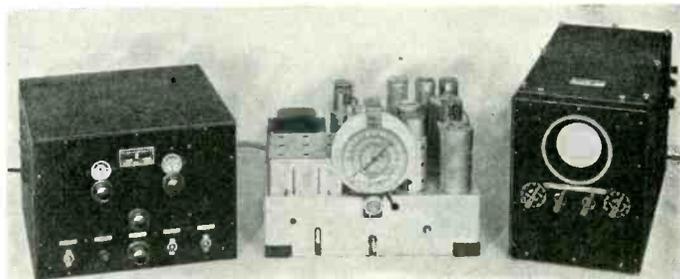

**—now used by every
leading set manufacturer!**

Grunow	Bosch	Stromberg-Carlson
Case	Stewart-Warner	Rodgers-Majestic
Mid-West	Crosley	Wells-Gardner
Zenith	Gilfillan	Horn

—and many other prominent radio set and part manufacturers use CLOUGH-BRENGLE Cathode-Ray Equipment in production, laboratory, and service departments.

No other group of instruments has so completely met the need for new and better methods with which to service modern radio receivers.

MODEL OM Frequency Modulated R. F. Signal Generator is used as an ordinary test oscillator for output meter work, but also has built-in fixed sweep frequency modulator for producing CALIBRATED receiver selectivity curves when used with any standard oscilloscope. Net \$57.75

MODEL 81 Frequency Modulator is used with any oscillator to produce the exclusive C-B CALIBRATED selectivity curve. Does not destroy oscillator calibration. Direct connection to oscillator output—no plug-in jacks to oscillator tuning circuit. Net \$34.25

MODEL CRA Cathode-Ray Oscilloscope provides every facility needed in modern analysis of receiver, amplifier, transmitter, and industrial voltage problems. Has horizontal and vertical amplifiers, linear sweep, and complete power supply. Net complete with Cathode-ray tube \$84.50

More "FIRSTS" for C-B

First to recognize the serviceman's needs in a day of ever-growing circuit and performance complications, CLOUGH-BRENGLE now brings a complete new line of instruments for 1936. Here are two that have won instant popularity:

MODEL 82 Direct-Reading All-Wave R. F. Signal Generator —90 k.c. to 20 m.c. continuously variable, all on fundamentals. Large 8½" scale. Battery operated. Complete with tubes less batteries. Net \$19.90	MODEL 79 Beat-Note Audio Oscillator —develops a uniform (within 2 Db.), pure sine wave voltage from 50 to 10,000 cycles. Operated from self-contained power supply. A necessary instrument for precision servicing of high-fidelity receivers. Complete with tubes. Net \$51.90
---	--

Write for New 1936 Catalog

The CLOUGH-BRENGLE Co.
1138 W. AUSTIN AVE. CHICAGO, ILL.

Send complete literature on the new C-B 1936 Line of Professional Service Instruments.

Name
Address

THE MANUFACTURERS . . .

NEW IRC INSULATED METALLIZED RESISTORS

Unique modern resistors specifically designed for exacting radio requirements of the present day and known as IRC Type "B" Metallized Resistors, have just been



announced by the International Resistance Company.

Retaining all advantages of the familiar Type "F" Metallized Resistors, these new units have complete high-voltage insulation protection and are constructed without metal ends. They can contact other parts without danger of shorting. Utilizing an improved metallized resistance element, they have an extremely low noise level and represent a distinct improvement in essential resistor characteristics such as accuracy, permanency of resistance value and durability under all operating conditions, it is said.

In the new Type "B" Insulated Resistors a sturdy casing of insulating compound is moulded completely around the Metallized resistance element, sealing it against moisture and protecting it from shorting on other parts. Like bakelite, this insulating material will not crack or deteriorate. Permanent contact between element and wire leads is obtained by a special bonding process which, after the insulation is moulded solidly around the assembly, cannot break or develop poor contact. Noise level is said to be unusually low, making these new resistors ideally suited for amplifier circuits and for critical television requirements.

IRC Insulated Resistors are both color coded and individually marked with resistance value and wattage rating. Identification is quick and easy. They are available in 1/2-watt and 1-watt ratings which will suffice for practically every installation however crowded it may be. Not only is the 1/2-watt (Type B-1/2) resistor as small as the usual 1/4-watt resistor, but it may be used universally for any rating up to and including 1/2-watt with greater efficiency and a higher factor of safety.

Flexible wire leads extend straight out from the ends giving a more effective lead length and avoiding danger of breakage when installing. They are tinned for easy soldering.

The 1-watt (Type B-1) IRC Insulated Resistor is made in all ranges from 300 ohms to 10 megohms. The 1/2-watt unit (Type B-1/2) is made in all ranges from 100 ohms to 5 megohms.

A new catalog containing full details will be sent on request to International Resistance Co., 2100 Arch St., Philadelphia, Pa.

TECH LABS PRODUCTS

Tech Laboratories, with a factory located at 703 Newark Avenue, Jersey City, N. J., is now engaged in manufacturing a line of standard and special precision resistance

instruments and allied products, for industrial and laboratory use.

The standard line includes—Attenuators, Potentiometers, L- Pads, T- Pads, H- Pads and other impedance-matching networks, Line Equalizers, Sound Level Indicators, Tap Switches, Precision Wire-Wound Resistors and Geophysical Instruments.

For attenuators and potentiometers impedance values range from one to a million ohms. Standard accuracies: two percent. Special accuracies: down to one-tenth of one percent. Steps: from one to sixty, any circuit, any loss per step.

These units are compact in mechanical design. They are entirely noiseless, and frequency characteristics are flat from zero to 50,000 cycles, it is said.

The first of a series of bulletins on this type of equipment and its application is now available.

"NOISE-MASTER" NOW AUTOMATIC

"Noise-Master" antenna, which was successfully introduced by Cornish Wire Co., several months ago, now features



automatic operation. Quoting from the latest literature of this manufacturer, "after 'Noise-Master' is properly installed . . . no adjustment is necessary and no manual operation is required, because this antenna is fully automatic electrically."

The literature referred to above is understood to contain schematic and construction details of the "Noise-Master" unit, also of other Corwico kits.

This manufacturer is also distributing a treatise on "All-wave Antenna," and folders in color for the set-owner may be had without charge by dealers for distribution to their prospects. Address the Cornish Wire Co., 30 Church Street, New York City.

NEW HYGRADE SYLVANIA TYPE 5Z4

A new type 5Z4 metal tube, directly interchangeable with the original "bird cage" 5Z4 metal rectifier, has been developed by Hygrade Sylvania tube engineers. The outstanding feature of the new Sylvania 5Z4 is the reduction in size, which was accomplished without loss in any of the electrical characteristics. Several constructional features have improved the physical structure of the tube.

The internal elements of the new Sylvania 5Z4 are similar to those used in the construction of the 83V glass rectifier. The complete assembly is enclosed in a metal shell of the same size as used

for the 6F6 power amplifier tube. This reduces the height to 3 1/4 inches and the diameter to 1 5/16 inches.

The newly constructed 5Z4 insures more perfect shielding, compactness, ruggedness, uniform characteristics and efficiency during life. The filament current drain is now 1.5 amperes as compared to the 2.0 amperes drain of the original 5Z4. The decreased filament wattage results in lower operating temperatures, comparable with the operating temperatures of other types of metal tubes.

The maximum d-c output current rating was maintained at 125 milliamperes for operation at 400 a-c volts (rms) per plate. This feature makes it possible to directly replace the original 5Z4 tubes now in use with the new Sylvania 5Z4. The new tube will also replace type 5Y3, the glass rectifier tube incorporating the octal-type base.

"NOISE-ELIDERS"

A. M. Flechtheim and Co., Inc., 136 Liberty Street, New York City, is introducing a new group of line-noise filters known as Noise-Eliders.

The Flechtheim Noise-Eliders are said to be effective in removing interference being conducted into the radio receiver through the power supply.

Full data on these units may be had by contacting A. M. Flechtheim and Co., Inc.

NEW HIGH-LEVEL VELOCITY MIKE

Amperite announces a new high-level velocity microphone with an unusual brilliancy on the higher frequencies. It is not boomy on close talking, it is said. Its output impedance of 2000 ohms permits operating directly into the grid—eliminating the input transformer. Requires 15 db less amplification than the lower impedance velocities, making it possible to build simple and compact amplifiers. Excellent for both studio and remote work.

The only limitation of the 2000-ohm impedance velocity is the limitation of cable



length. With 60' of ordinary 3/8" cable, the high-frequency response is still superior to the low-impedance velocity. For longer cable lengths, low capacity r-f cable can be used.

• SERVICE FOR

GEARED with CORNELL-DUBILIER CONDENSERS

● **FOR PROFIT**
The proven quality of C-D electrolytics, paper, mica and oil condensers assure you of a profit on every job. There is no need for profitless return calls or loss in valuable customer good will when you use C-D Condensers.

● **FOR SPEED**
Your most difficult requirements for exact duplicate replacements can be met by every authorized C-D distributor. There is no need to shop around for substitutes when you use C-D condensers.

● **FOR TODAY**
"Scientific"—"Modern"—these words are synonymous with C-D condensers. Largest plant in the world devoted exclusively to the manufacture of condensers.



Use C-D condensers on your next job and assure yourself of all around customer satisfaction and a guaranteed profit.

General catalog #128 and catalog #129 on exact replacements now available. Did you get your copy? If not write today!

CORNELL-DUBILIER
CORPORATION
4375 BRONX BOULEVARD
NEW YORK

FREE



RESISTOR CABINET

—with purchase of 35 CONTINENTAL insulated 1/2 or 1-watt resistors at your regular net price of \$4.20. Cabinet for resistor stock hangs on the wall; dial the rotary color code like an automatic telephone. A watt-ohm-volt chart appears below the colored dial.

● Condenser Engineering Bulletin 103 Free ●
Ask your Jobber for your copy

CONTINENTAL CARBON Inc.

13912 Lorain Ave., Cleveland, Ohio
Canadian Factory: Toronto, Ontario



No. 33 (Needle Ballast)
Listed at \$24.50

*"The standard by which others
are judged and valued"*

AUDAX

IN leading Radio Stations, Laboratories and Universities—wherever superlative pick-up performance is demanded—today you find AUDAX doing duty. Engineered to the nth power, immune to summer heat, humidity and other climatic conditions. Made to suit every demand from the humblest midget combinations to the HIGH FIDELITY requirements of fine transcriptions. What is *your* pick-up problem?

List prices \$9.50 to \$390.00
Special Recording Heads to Order

AUDAX COMPANY

500-S Fifth Avenue New York, N. Y.
"Creators of High Grade Electrical and Acoustical Apparatus Since 1915"

it's New!



WEBBER
No. 40
OSCILLATOR

BATTERY POWER SUPPLY
PORTABLE—USE ANYWHERE
ACCURATE WITHIN 1%
CATHODE RAY MODULATOR JACK

Jack supplied for using 25 division calibrated ATTENUATOR permits accuracy on repeating measurements and comparisons of receiver sensitivity. Has high output for neutralizing and adjusting sets badly out of alignment. Low output jack provides variable voltage which can be reduced below the level at which the AVC functions—accurate alignment of the most sensitive receivers assured. Portable—battery operated—does not require an AC line. Priced at \$24.95. Net.

SEE AT YOUR JOBBERS

Or use coupon below for full information about the Webber No. 40 Oscillator.

EARL WEBBER COMPANY

1217 W. Washington Blvd.
Chicago, Ill.

USE
THIS
COUPON

EARL WEBBER CO.
1217 W. Washington, Chicago, Ill.

Without obligation send me full information about the new No. 40 Oscillator.

Name
Address

NEW WESTON CAPACITY METER

A new multi-range capacity meter designed to meet requirements for a small, reasonably-priced unit, has recently been placed on the market by the Weston



Electrical Instrument Corporation, Newark, N. J. The new meter, known as Model 780, provides full-scale ranges of 10/1/0.1/0.01 microfarads, covering all capacity ranges in common use in radio receivers, since readings can be made down to as low as 100 micromicrofarads. It operates directly from any 115-volt, 60-cycle a-c outlet.

A convenient voltage adjuster compensates for small variations in line voltage, and an internal transformer insulates the device from the line. A pair of long test prod leads is provided with each instrument.

The meter has exterior dimensions of 5½ in x 3¾ in x 2½ in and weighs approximately 1¾ pounds.

SUPREME 189 SIGNAL GENERATOR

The Supreme Instruments Corporation, Greenwood, Mississippi, are offering a completely shielded all-wave signal generator, Model 189, using an electron-coupled circuit. This unit is said to provide un-



usual frequency stability over all ordinary variations in power-supply potentials or load conditions.

Carrier frequencies are calibrated directly on oversize airplane dial from 90 kilocycles to 30 megacycles. Calibration for each individual generator is effected by means of trimmer adjustments. The Model 189 is provided with self-contained audio oscillator for approximately 50 percent 400-cycle modulation note, and provisions are included for applying external modulation with microphone or phonograph pickup.

POLYIRON CORE I-F TRANSFORMERS

Polyiron, the interesting development of the Johnson Laboratories, is used in the Aladdin Radio Industries I-F Transformers now being manufactured in their new plant at 466 West Superior Street, Chicago.

Polyiron is a compound made of extremely small iron particles treated with an insulating material and molded into suitable forms which closely resemble solid metal.

The principal advantages of patented polyiron in the cores of the new high-frequency transformers are to concentrate the magnetic field, permitting much smaller size transformers, and to increase the "Q" ratio of inductance to resistance by



virtue of less copper being required for a given inductance, it is stated. The distributed capacity is also reduced by virtue of less wire being used.

This small size, 1½-inch square by 2½-inch high, including this dual mica insulated trimmer, makes these transformers suitable companions for the new iron tubes.

NEW TRIUMPH TUBE TESTER

The Triumph Manufacturing Co., 4017 West Lake St., Chicago, have introduced the Model 420 Triumph Tube Tester.

The Model 420 is mounted in a solid walnut cabinet styled for display on the counter and fitted with a dust-proof cover. A selective test of each element for open, short, leakage and load is provided. All elements in the tube are brought to separate switches which may be connected or disconnected in the circuit as is required for a complete test.

A line control is provided to permit setting the tester for the supply voltage.

The instrument is adjusted by the meter on the panel, as shown in the accompanying illustration.

Sufficient leakage sensitivity is provided so that true leakage conditions in a tube



are shown. The shells of metal tubes are not tied to the filament in this test. All elements are separate so that leakage tests in and between any two or more elements can be made.

The Model 420 will test all types of tubes—glass, metal, and metal-glass. The power-supply line is completely isolated from the test circuits.

It is stated that the Model 420 employs a circuit proposed by the Tube Standards Committee of the RMA. All tubes are classified on a rated load by class of service that the tube is intended for. This embraces general purpose tubes, diodes and battery types in metal or glass.

NEW 30-WATT P-A SYSTEM


Bell Sound Systems, Inc., of Columbus, Ohio, has announced the addition of a 30-watt p-a system, known as the Model P-A 5C, to their already extensive line of public-address systems. The new model is said to be a powerful, easily operated, complete system, arranged for transporting in three compact, Kerotal covered carrying cases. Though standard equipment includes two high-fidelity G-12 speakers, the unit has facilities for utilizing six speakers. By a series arrangement of transmission lines, it is possible to use as many as 12 to 15 speakers, it is stated.

The microphone is of the new crystal type, affording freedom from frequent re-packing and overhauling, and eliminating "hiss" and "background noise" when the instrument is jarred or moved, it is said. Two separate input channels permit the simultaneous use of two microphones or a microphone and phono pickup. Controls consist of two volume controls, tone control, selector switches and a-c on-off switch.

The Model P-A 5C is said to have frequency response uniform within plus or minus 2 db from 35 to 10,000 cycles. The circuit is the 5 stage, Class A type, resistance and impedance coupled, with all filter components built into the chassis.



NEWEST BUD TEST ADAPTER KIT

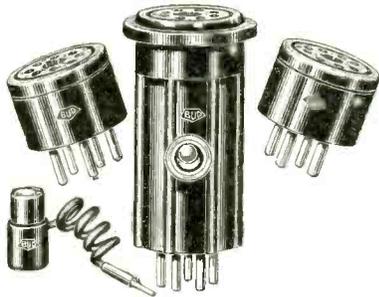

for testing
**ALL METAL
TUBES**
in your
**PRESENT
TUBE TESTER**

This Kit consists of three adapters as illustrated and a double grid clip suitable for All Metal Octal tubes and standard tubes.

No. 483 Kit—List \$4.00. Cost to Servicemen or Dealers \$2.40. Can be secured from your jobber or direct from us.

BUD RADIO, Inc.

1937 East 55th Street

Cleveland, Ohio

P.A. Systems



A Size and Type For Every Need

Radio men everywhere are making money with Bell Systems. Embodying the latest developments in radio science, and accurately built and tested by experts they offer you today's greatest value—efficient, convenient portable equipment that is practical for both portable and permanent installation. Foolproof in operation and low in cost, Bell Systems opens the door to a highly profitable market. Go after your share of this business—start now by writing for full details.



Model 3-C

Class A amplifier with 15 watt output. Two heavy duty 12" electro dynamic speakers. Two separate input channels with separate volume controls—also selector switches and A.C. on-off switch. High fidelity crystal microphone. Self contained in two black Keratol covered carrying cases. Total weight 74 pounds. The flexibility of this unit makes it a big seller.

Jobbers!

An exceptionally attractive proposition. Results other jobbers are getting is "proof of the pudding." Let's discuss the subject fully.

WRITE TODAY
for
COMPLETE DETAILS

BELL SOUND SYSTEMS Inc.

61-62 East Goodale St.
COLUMBUS, OHIO

Dependable



Suited to
SERVICE MEN'S NEEDS

**HIGHEST
QUALITY
SOUND
ENGINEERING**

Ken-Rad Radio Tubes

Glass or Metal
Radio Tubes
THE KEN-RAD CORPORATION, Inc., OWENSBORO, KY
Division of The Ken-Rad Tube and Lamp Corporation
Also Manufacturers of Ken-Rad Incandescent Electric Lamps


EVERYTHING IN RADIO UNDER ONE GREAT ROOF!



You can always get what you want from ALLIED—any brand . . . any size . . . any price . . . is yours right when you want it, because here, at ALLIED.

we have assembled under one roof, the most choice and complete radio stock in the country. ALLIED is able to serve you better—and does. We have bigger stocks than ever before—more people to serve you—more live high grade lines—more truly Personal Service for every individual Radio Serviceman—more Value than ever before.

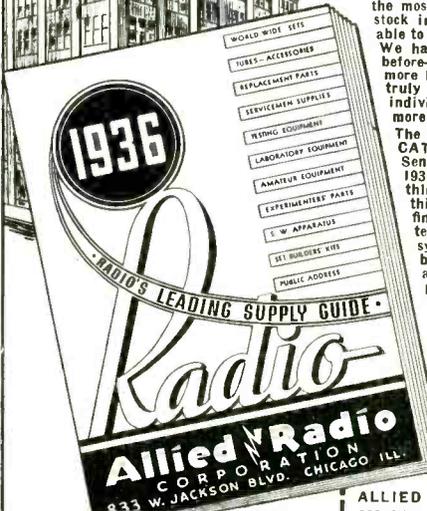The MOST COMPLETE RADIO CATALOG EVER PUBLISHED. Send for your copy of the new 1936 ALLIED Catalog. Everything you need in radio is in this book—thousands of the finest replacement parts—new test equipment, tools, P. A. systems, etc. Do your radio buying 100% from this catalog—page by page it will prove to you that we sell for less.



FREE

ALLIED RADIO CORP.
833 W. Jackson Blvd.
Chicago, Ill., Dept. N.

Send me your FREE 1936 Radio Catalog.

Name

Address

Allied Radio CORPORATION
833 W. JACKSON BLVD.
CHICAGO, ILLINOIS



You won't believe your eyes...

WHEN YOU SEE "little giants" by



ULTRA-COMPACT "Little Giant" ELECTROLYTIC CAPACITORS

The manufacturing, engineering and servicing arms of Radio are unanimous in praising the scientific efficiency of these fine little Capacitors

that do the work as well as the standard sized units, yet take much less space. "Little Giants" fit anywhere, because they are of minimum thickness. Only half the former size, yet they give full capacity and full voltage protection. They are typical of SOLAR engineering originality and skill.

IN TWO RATINGS
450 v.w. and 200 v.w.

Send for complete literature on these and other new SOLAR exclusive creations.



SOLAR MFG. CORP.

599-601 Broadway New York City
Manufacturing Affiliates in London, Paris, Berlin, Milan

STATEMENT OF THE OWNERSHIP, MANAGEMENT, CIRCULATION, ETC., REQUIRED BY THE ACT OF CONGRESS OF MARCH 3, 1933

Of SERVICE—A Monthly Digest of Radio and Allied maintenance published monthly at New York, N. Y., for Oct. 1, 1935.
State of New York, }
County of New York, } ss.:

Before me, a Notary Public, in and for the State and County aforesaid, personally appeared Bryan S. Davis, who, having been duly sworn according to law, deposes and says that he is the Business Manager of the SERVICE—A Monthly Digest of Radio and Allied Maintenance, and that the following is, to the best of his knowledge and belief, a true statement of the ownership, management, (and if a daily paper, the circulation), etc., of the aforesaid publication for the date shown in the above caption, required by the Act of March 3, 1933, embodied in section 537, Postal Laws and Regulations, printed on the reverse of this form, to wit:

1. That the names and addresses of the publisher, editor, managing editor, and business manager are: Publisher, Bryan Davis Publishing Co., Inc., 19 East 47th Street, New York, N. Y.; Editor, M. L. Muhleman, Mt. Vernon, N. Y.; Managing Editor, Ray D. Kettenmeyer, Madison, N. J.; Business Manager, Bryan S. Davis, Scarsdale, N. Y.

2. That the owners are: Bryan Davis Publishing Co., Inc., 19 E. 47th St., New York; B. S. Davis, Scarsdale, N. Y.; Roy T. Atwood, Albany, N. Y.; G. R. Bacon, Douglaston, N. Y.; J. C. Munn, Union City, Pa.; J. A. Walker, Richmond Hill, L. I., N. Y.; A. B. Goodenough, New Rochelle, N. Y.

3. That the known bondholders, mortgagees, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgages, or other securities are: None.

4. That the two paragraphs next above, giving the names of the owners, stockholders and security holders, if any, contain not only the list of stockholders and security holders as they appear upon the books of the company but also, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, is given; also that the said two paragraphs contain statements embracing affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock, and securities in a capacity other than that of a bona fide owner; and this affiant has no reason to believe that any other person, association, or corporation has any interest direct or indirect in the said stock, bonds, or other securities than as so stated by him.

5. That the average number of copies of each issue of this publication sold or distributed, through the mails or otherwise, to paid subscribers during the.....months preceding the date shown above is.....(This information is required from daily publications only.) BRYAN S. DAVIS, Business Manager.

Sworn to and subscribed before me, this 25th day of September, 1935. (SEAL) J. A. WALKER, Notary Public.

Queens Co. Clk's No. 3149, Reg. No. 7476. New York Co. Clk's No. 831, Reg. No. 7-W-514. My commission expires March 30, 1937.

What's SAFETY worth to you?

What if you DO save a few cents on low wattage resistors? Does that pay for your time and trouble if the resistor goes bad just after you've installed it? Does it make up for the fact that your customer probably thinks you don't know your business?

See the
OHMITE
Display at the
I. R. S. M.
Convention
Hotel
Pennsylvania
New York, N. Y.
Oct. 25-26-27

Play safe! "Brown Devils" are conservatively rated as to wattage and maintain constant resistance values. The exclusive OHMITE vitreous enamel coating locks each turn of wire in place (prevents shorts) and resists extreme weather conditions. "Brown Devils" are made in 10 and 20 watt sizes, and resistance values through 100,000 ohms. 1½ inch solidly anchored tinned lead wires make for easy installation. Ask your jobber or write for New Catalog 14.

OHMITE MANUFACTURING COMPANY


NEW ENLARGED QUARTERS AT
4827 Flournoy St, Chicago, Ill.

Send me your free 12-page Catalog 14 listing resistors, voltage dividers, rheostats, potentiometers, etc.



Mail
Today!

Tomorrow's MAGNETIC SPEAKER Today!

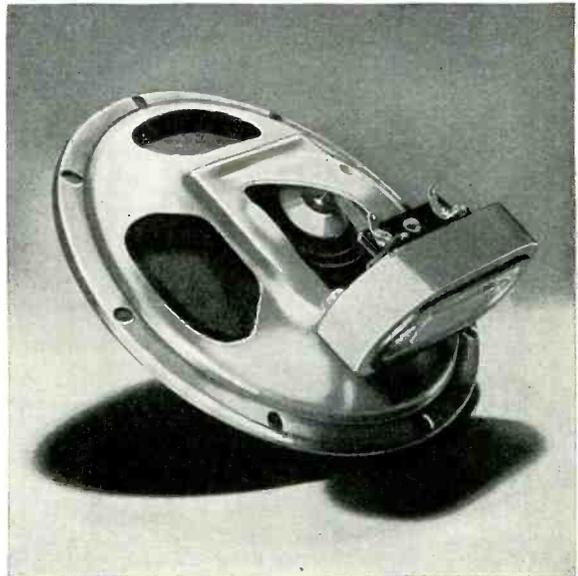

The Revolutionary "Hyflux" NEW WRIGHT-DECOSTER

- High Efficiency
- Permanent Dust Proofing
- Wide Frequency Range
- Rugged Construction

Write for Complete Details, Specifications, Prices.

WRIGHT-DECOSTER, Inc. 2253 University Ave.
St. Paul, Minn.

RELIABLE
AS THE NORTH STAR

NEW INSULATED Metallized
IRC RESISTORS



The first fully sealed and INSULATED Resistors—ideal and modern for every purpose. Use them anywhere without fear of shorts or opens. Quiet—vibration-proof—moisture-proof. The outstanding resistance development in years!

INTERNATIONAL RESISTANCE CO.
TORONTO, CANADA PHILADELPHIA, PA.

**Specially Designed for
Theater and School Auditorium
"Booster" Systems**

**Brush
Theater
Mike**

Brush T2S4P or theatre microphones permit actors a freedom of movement and naturalness, available with no other pickup. Vision of the audience is uninterrupted.

For small stages one, two or three mikes—in series—are hidden along the front of the stage like footlights. For larger stages left and right hand circuits are preferred. 100 ft. leads can be used and conventional high gain amplifiers.

Install T2S4P microphones on your next theatre or school auditorium booster system. Get the details now. Data Sheets Nos. 5 and 6 give complete information and installation diagrams. Free on request. Write for a copy today.



Brush T2S4P Microphone


The BRUSH DEVELOPMENT COMPANY
PIEZO ELECTRIC
1882 E. 40th St. CLEVELAND, O.
MICROPHONES • MIKE STANDS • TWEETERS • HEAD PHONES • LOUD SPEAKERS

Radiart
Vibrator and Auto Radio
ANALYZER
Costs You **\$7.50**
Only
Ask Your Jobber



THE RADIART CORPORATION
Shaw Ave. at 133rd St. Cleveland, O.

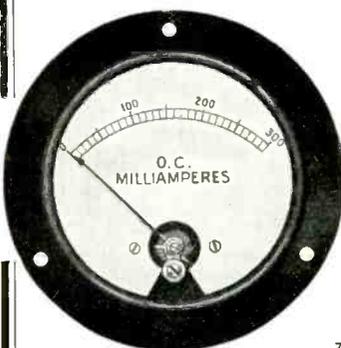HOYT
offers you
A COMPLETE LINE
of
RADIO METERS
at
Competitive Prices
write—
BURTON-ROGERS CO.
Sales Division of
Hoyt Electrical Instrument Works
755 Boylston St., Boston, Mass., U.S.A.
BUILDERS OF GOOD METERS FOR OVER THIRTY YEARS



"EASTERN" MIKE STANDS



The most complete line of "all-purpose" microphone stands on the market today. Handsome in appearance and scientifically practical in design. Eastern stands are supplied in 3 separate and distinct methods of changing height.

FREE—Illustrated catalog sheets describing the complete Eastern line. Write for them.

EASTERN MIKE-STAND COMPANY
56 CHRISTOPHER AVE. BROOKLYN, N. Y.
DICKENS 2-3538

Worth Climbing For!



The New Radolek 1935 Fall Edition of the Profit Guide is the most complete Radio Parts Catalog ever published—new, bigger and better. Everything in radio—at the right prices. Over 160 pages of valuable, money-saving "radio-buying" information. Over 10,000 separate Repair Parts—hundreds of new items—a complete, new selection of Radio Receivers and Amplifiers. Contains the most complete, exact duplicate, replacement parts listings, of volume controls, condensers, transformers, vibrators ever compiled. Nowhere, ever, has there been a Radio Parts Catalog comparable to this superb book. Every page brings you extra profits. This is your book—it's FREE. Send For It!

Radolek restricts distribution of the PROFIT GUIDE to those actively and commercially engaged in the Radio Business. Please enclose your Business Card or Letterhead.

THE RADOLEK CO.
644 West Randolph Street, Chicago


Send me FREE the Big New RADOLEK PROFIT GUIDE.

Name.....
Address.....
Are you a Serviceman? Dealer? Expm.

New POWER-LEVEL INDICATOR

Complete: \$28⁷⁵
KIT: \$21⁰⁰

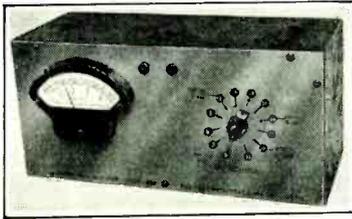Includes completely wired attenuator — less case and panel.



An important new instrument which accurately measures power levels from -12 to -43 decibels. Meter scale is calibrated from 12 to up 10 decibels.

Unique 10,000 Ohm constant impedance L type attenuator assures high accuracy and sensitivity. May be used as direct reading 4 range A.C. voltmeter for all frequencies.

Splendid instrument for gain measurements and as an output meter for all circuits from voice coil impedance up to input impedance of push-pull output transformers. Has 5" Fan Type Meter with knife edge pointer—500 microampere movement.

One of the many new items of R. C. P. economical test equipment you should know about. Visit our booth at I. S. R. M. Show in New York.

Write Dept. S-10 for New 1936 Bulletins.

RADIO CITY PRODUCTS CO.
88 PARK PLACE NEW YORK

New! POSITIVE-AND-SMOOTH-ACTION MIKE STANDS


Featuring positive, NON-SLIDING, ball-bearing clutch. Will never wear out . . . never require adjustment. WILL NOT "CREEP." Tightens with only 1/8 turn of clutch. Mike can be ROTATED WITHOUT LOOSENING CLUTCH. Smooth, PNEUMATIC-LIKE ACTION up and down. A model for every purpose.

WRITE FOR ILLUSTRATED BULLETIN S.

NEW! HIGH LEVEL VELOCITY MIKE

(High impedance—2000 ohms) Eliminates (1) separate pre-amp, (2) input transformer and its losses, (3) hum trouble and feedback.

WRITE FOR BULLETIN H.

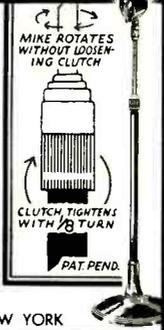

AMPERITE Company 561 BROADWAY NEW YORK

AMPERITE POINT Velocity **MICROPHONE**

HOW DO YOU DO IT?


How do you solve the many servicing problems with which you have to contend . . . what special kinks have you worked out which help you in servicing receivers . . . have you developed shortcut schemes for testing, or built test devices that do the work better and faster?

No matter what the scheme or the device, there are many Service Men who would like to know the how's and why's—just as you would like to know about the schemes and devices employed by others.

All you have to do is give us the outstanding points, and a rough pencil sketch of the device if it happens to be such—and we will do the rest.

Write up those ideas now and send them into the . . .

ON THE JOB DEPARTMENT

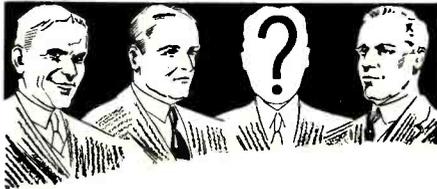

ONE OUT OF FOUR SERVICEMEN FAIL!

According to conservative estimates, one out of four servicemen fail or go out of business EVERY YEAR!

Will you be among them? Will you be one of the even larger group making only a bare living from the work. . . Or, will you join the select, ambitious few who, in every town and city, grasp existing opportunities and build an outstanding success?

Sprayberry Training is specifically designed for men who aim to be in the latter group. Through it, I want to help you forge ahead as I have already helped hundreds of others. I want to help you do all types of radio work easier and quicker—help you build a REAL future. And, as proof of what I might do for you, I can point to a record of success that is second to none.

**Let Me Help You Build
A REAL Future!**

Mine is not a "course" for beginners. It is **ADVANCED SERVICE AND BUSINESS TRAINING** for men who believe in looking ahead. No "stuff," fancy bindings or useless theory. From beginning to end, you get sound, **PRactical HELP**—at a fraction of the cost you might expect to pay. Investigate!



F. L. Sprayberry 2548 University Place, N. W.
Washington, D. C.

Without obligation, please send your free booklet "PUTTING PROFITS & EFFICIENCY INTO SERVICING."

Name
AddressS-10-35

RADIO AMATEUR CALL BOOK



is the only publication listing all radio amateurs throughout the entire world.

It also includes a complete list of High Frequency Commercial Stations, International Abbreviations and "Q" Signals, High Frequency Press and Weather Schedules, "Q", "R" and "T" Signals, U.S. Radio Inspection Districts, International Prefixes.

Every radio amateur should have a copy of this valuable book. Always up-to-date, published quarterly, single copies \$1.25, annual subscription \$4.

RADIO AMATEUR CALL BOOK, Inc.
612 So. Dearborn Street Chicago, Illinois

School Systems

**FHA Loans legalized for
Public Address Equipment**

A new low priced Educational Sound System for schools, including amplifier, all-wave tuner, automatic phonograph, four position input control panel, crystal microphone with floor stand and room control panel. Furnished in single or double channel, 10 to 70 room capacity. All single channel models completely wired for two channel conversion.

Ask for Bulletin "CS"

Sound Systems, Inc.
1311 Terminal Tower, Cleveland, Ohio



FOX SOUND EQUIPMENT CORPORATION



Recognized for years as the favorite of radio engineers.

FOX IMPROVED SOUND EQUIPMENT

—is the choice of service engineers.

A complete line that fills your every requirement perfectly. Each item is constructed on fundamental principles, pronounced by engineers to be most sound and modern. All "bugs" have been removed by prolonged tests. You need do no experimenting—Fox has done that for you. Built to a standard, Fox equipment is easy and quick to install and sure to render long, faithful, satisfactory service, all of which means greater profits for you and more pleasurable work.

Write today for free catalog, price list and technical data sheets.

FOX SOUND EQUIPMENT CORP.
3120 MONROE STREET, TOLEDO, OHIO, U. S. A.

NATIONAL HEARING WEEK

OCTOBER 20-26

Slogan: FORWARD, HARD of HEARING of AMERICA!

T R I M M

Help the Hard of Hearing go "Forward" to a new world of sound.

INSTALL GROUP HEARING AIDS in the churches and theatres.

USE TRIMM HEARING AID EQUIPMENT for quality of tone, efficient operation, and simplicity of installation.

Write for full details.

TRIMM

RADIO MANUFACTURING COMPANY
1528 ARMITAGE AVE. CHICAGO, U. S. A.

Majestic Cones and Field Coils

NOW READY—A new booklet illustrating and describing the entire Majestic line of field coils and cone assemblies. It will pay you to get a copy for ready reference on Majestic receivers. The most complete listing on this line of receivers. Mention your jobber's name and address when writing.

Territories open for live-wire sales representatives.
Get particulars—profits assured.

MULTIPLEX RADIO SERVICE, Inc.

88 FOURTH AVENUE - BROOKLYN, N. Y.
Phone: CUMberland 6-7153

ELECTRO-VOICE




NEW VELOCITY MICROPHONE

A new line of four models that is meeting with instant approval for high fidelity work. Correctly engineered and smartly styled, it brings together the combination of appearance and performance that is essential for present day sound pick-up. There are a host of exclusive features such as a built-in shock-absorber, instantly adjustable cradle, and a heavy screen housing that prevents resonance. All models available in either a 200 ohm or high impedance output. List prices are from \$25.00 to \$75.00. Sold by reputable jobbers, everywhere. Also a full line of Carbon Microphones priced from \$5.00 to \$25.00, list.

Electro-Voice Mfg. Company, Inc.
332 E. Colfax Ave. South Bend, Ind., U. S. A.

UTAH

VIBRATORS

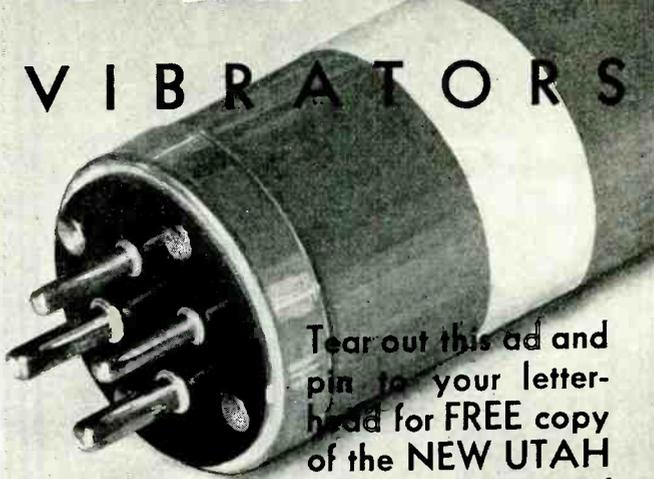

Tear out this ad and pin to your letter-head for FREE copy of the NEW UTAH General Catalog of vitalized radio parts

UTAH RADIO PRODUCTS CO.,
Orleans St., Chicago


Million—METAL TUBE TESTER



Tests all tubes, metal or glass, for omissions, shorts, leakages, using a new NEON METER principle. It also tests continuity and leakage of bypass and electrolytic condensers. Reads resistance directly up to 10,000 ohms. Leakage up to 6 megohms can be detected. Can be used as a NEON resonance indicator for set alignment. Tests both plates and diodes. Line voltage adjustment. Operates on 110 A.C. 60 cycles. The most complete and practical tester ever offered servicemen at anywhere near this price.

Dealers net cost Model CT
\$8.45

DeLuxe Vibrator Tester

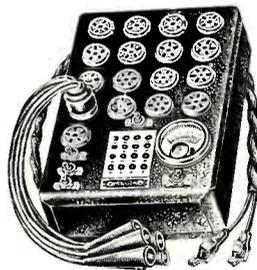

Tests all types of vibrators with sockets for more plug in types than most testers and spares for future use. Tests rectifier tubes of the new gaseous type as well as 84's. Octal socket provided for new metal auto set rectifier. Polarity reversing switch, tube or synchronous switch, on-off switch and a fused battery cable with clips. Buffer capacity is variable and meter reads exact condition of vibrator on POOR-GOOD scale. Separate scale is provided for reading primary current and for use as a 0-10 D.C. ammeter. A plug with handy insulated clips is provided for lead type vibrators.

Dealers net cost Model DV
\$16.95

If your local jobber cannot supply you order direct
20% deposit on C. O. D. shipments.

MILLION
RADIO AND TELEVISION LABORATORIES
361 WEST SUPERIOR ST. CHICAGO



RADIO ENGINEERING

Covering the design, production, engineering and test of Radio Receivers, Tubes, Parts, Amplifiers, Recording and Sound Projection Equipment. Published monthly.

Subscription, \$2.00 Yearly
(Foreign, \$3.00)



COMMUNICATION AND BROADCAST ENGINEERING

Covering Radio Communication, Broadcasting, Police, Marine and Aeronautical Radio, Telephony and Telegraphy, Facsimile and Television. Published monthly.

Subscription, \$3.00 Yearly
(Foreign \$4.00)

BRYAN DAVIS PUBLISHING CO., INC.
19 EAST 47th STREET, NEW YORK CITY

SERVICE? If you service, we can supply you with 'most anything in radio, from our large stock.

SUPREME INSTRUMENTS on Time Payments

This high grade line available from stock.

THE NEW WEBBER OSCILLATOR

FREQUENCY RANGE: Continuously variable from 90 kilocycles to 60 megacycles.

DIRECT READING FULL VISION DIAL: Effective scale length is approximately 37 inches.

CATHODE RAY OSCILLOGRAPH: Jack on front panel permits the use of a cathode ray modulator unit.


AUDIO SIGNAL: Is approximately 400 cycles, and audio voltage is available at panel jack.

Dealer's Net Price—\$24.45

RCA Oscillographs and Oscillators • Radio City • Burton • Triplett

GROSS RADIO, INC., 51 Vesey Street, New York, N. Y.

HOPE PARABOLIC DEFLECTOR BAFFLE

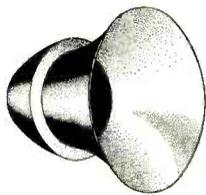

*All Aluminum
Weatherproof Housing*

Assures sound distribution of greater evenness and uniformity and cuts down feedback troubles effectively. The Hope Baffle is inconspicuous when installed. Constructed of heavy gauge spun aluminum, reinforced and free from metallic resonance. Hand-somely finished with special aluminum lacquer. Overall inside dimensions permit the Hope Baffle to be used with practically all standard cone speakers.

Inside of housing 12½" by 10" deep. Speaker opening 10". Length of horn alone 10". Bell 17" diameter. Overall outside 17" by 20". This model speaker baffle suitable for all 10, 11 and 12" speaker cones.

\$6.95 net

HOPE MFG. CO., 401 Broadway, New York, N. Y.

Write Dept. RS for illustrated literature on Hope horns and trumpets. A complete line at very low prices.



**NEW Phosphor Bronze
Dial Cable**

The Handiest Spool on the Market

SAMPLE SPOOL, 25 FT.

Special Price **50c**

ONLY ONE TO A SERVICE MAN - - ORDER ADDITIONAL SPOOLS FROM YOUR JOBBER

RIVARD MFG. CO... TOLEDO, OHIO

Jobbers: Write for Sample and Catalog



Radio Instruments

FOR PROFITABLE SERVICE AND TUBE SELLING

JACKSON INSTRUMENTS will not become Obsolete . . . Rugged in Construction . . . Economical to Own . . . Correctly Designed . . . Simple to Use. This Modern Equipment Makes Profit Possible. Saves Your Time and Gives Positive, Accurate Results.

Consult Your Jobber . . . Or Write to

Jackson Electrical Instrument Co.
430 Kiser Street, Dayton, Ohio

JACKSON

Curtis Electrolytic CONDENSERS




Greetings to I. R. S. M.

New York Convention

Patent No. 1950852

CURTIS CONDENSER CORPORATION

3088 WEST 106TH ST. CLEVELAND, OHIO

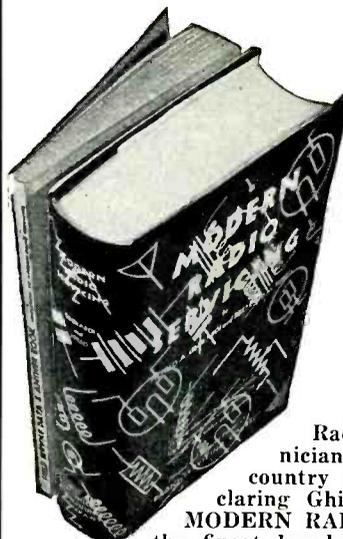

★
They say it's great!

Radio editors and technicians from all over the country are unanimous in declaring Ghirardi's newly-published **MODERN RADIO SERVICING** to be the finest bench-book ever written for practical, experienced service men. "The most valuable piece of equipment in my shop," writes one of them, and he is typical of many others whose enthusiasm has far exceeded our most optimistic expectations.

Ghirardi's book contains everything about radio servicing as it is practised today by the most successful service organizations in the U. S. Every modern test instrument and method (including the use of the Cathode-Ray Oscilloscope in servicing) clearly described and explained. Shows you how to do every kind of test and repair job in the newest and quickest way. All the latest 1935 dope presented in clear, easy-to-understand language. (1300 pages. 706 illustrations. 723 Review Questions. Price \$4.00)

It is supplemented by **RADIO FIELD SERVICE DATA**, a handy reference book to use on the job. (240 pages. 43 illustrations. Price \$1.50.)

**MODERN RADIO SERVICING
RADIO FIELD SERVICE DATA**

Combination Price—\$5.00

TEAR OUT AND MAIL TODAY

TO: RADIO & TECHNICAL PUBLISHING CO.
45 Astor Place, New York. Dept. S-10.

Please send free literature on books described.

Name

Address

Occupation

What kind of information do you need most? Test instruments?
 Newest test methods? Sales and advertising? Case histories?
 Repair methods?



New
ALL-WAVE
SIGNAL
GENERATOR

Dealer Net Price
\$14.40

With all improvements of present day engineering. All frequencies are fundamentals and stabilized, completely shielded and tube modulated. Plug-in coils for present 5 frequency bands, 100-21,000 kc. (Any new frequency range can be added by new coil.) Extra large scale permits accurate frequency settings. Large, accurate calibration curves supplied. In leatherette portable case complete with batteries and two No. 30 tubes. Dealer Net Price—\$14.40.

See Your Jobber

Write for
Complete Catalogue
READRITE METER
WORKS
Bluffton, Ohio

BUILT *Rugged*
TO STAND ABUSE

MODEL
554-A



ONLY
\$14.40


Readrite manufactures all types of testers used for servicing Radio Sets, including Set Testers, Tube Testers, Resistance, Continuity and Capacity Testers, Point-to-Point Testers and inexpensive Indicating Meters.

Readrite
TESTERS AND METERS




THE MARK OF
DEPENDABLE SERVICE
A NATIONAL PRODUCT

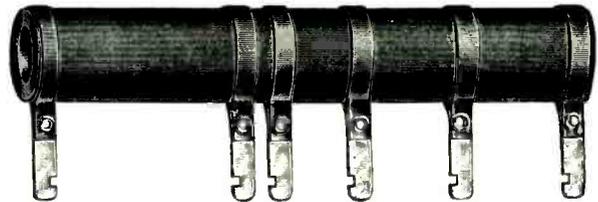ATLAS
CARRIES THE LOAD
TUBULAR WIRE WOUND RESISTANCES



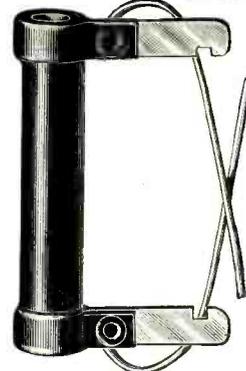ATLAS REPLACEMENT VOLTAGE DIVIDERS
in Both Fixed and Adjustable Types



PACK WIRE-WOUND
PIG TAILS

5 Ohms to 50,000 Ohms
Accuracy—2% Tolerance

ATLAS RESISTOR CO.
423 Broome Street
New York City

Export Dept.:
15 Laight Street, New York, N. Y.
Cable: ARLAB

WRITE FOR YOUR COPY OF 1936 CATALOG
Desirable Territories open for Sales Representatives

INDEX TO ADVERTISERS

A	H	Radio City Prod. Co..... 476
Aerovox Corp..... 482	Hope Mfg. Co..... 479	Radio Products Co., The..... 465
Allied Radio Corp..... 473	Howard Radio Co..... 433	Radolek Co., The..... 475
Amperite Corp..... 476	Hoyt Elec. Inst. Works..... 475	Raytheon Production Corp..... 455
Arcturus Radio Tube Co..... 453	Hygrade Sylvania Corp..... 451	Readrite Meter Works..... 480
Atlas Resistor Co..... 480	I	Rider, John F..... 435
Audak Company 471	International Resistance Co.... 475	Rivard Mfg. Co..... 479
B	J	S
Bell Sound Systems, Inc..... 473	Jackson Elec. Inst. Co..... 479	Solar Mfg. Co..... 474
Brush Development Co., The.. 475	Jefferson Electric Co..... 463	Sound Sytems, Inc..... 476
Bud Radio Co..... 473	K	Sprague Products Co..... 469
Burton Rogers Co..... 475	Ken-Rad Corp., The..... 473	Sprayberry, F. L..... 476
C	L	Standard Transformer Corp.... 423
Capitol Radio Eng. Inst..... 461	Lynch, Inc., Arthur H..... 482	Supreme Instruments Corp.... 447
Centralabs 455	M	T
Clough-Brengle Co., The..... 469	Mallory & Co., Inc., P. R..... 459	Technical Appliance Corp..... 469
Continental Carbon, Inc..... 471	Million Radio & Television Labs. 477	Thordarson Elec. Mfg. Co..... 453
Cornell-Dubilier Corp. 471	Mueller Elec. Co..... 482	Tobe Deutschmann Corp..... 448
Cornish Wire Co..... 459	Multiplex Radio Service, Inc.. 477	Trimm Radio Mfg. Co..... 477
Curtis Condenser Corp..... 479	Muter Co., The..... 461	U
E	O	United Transformer Corp..... 466
Eastern Mike-Stand Co..... 475	Ohmite Mfg. Co..... 474	Utah Radio Products Co..... 477
Electrad, Inc..... 436	Operadio Mfg. Co..... 482	W
Electro-Voice Mfg. Co., Inc., The 477	P	Webber Co., Earl..... 471
F	Porcelain Products, Inc..... 463	Webster Co., The..... 463
Federated Purchaser..... 457	R	Weston Elec. Inst. Corp.
Fox Sound Equip. Corp..... 477	RCA Mfg. Co., Inc.... Fourth Cover	Third Cover
G	Radio & Technical Pub. Co..... 479	Wholesale Radio Service..... 481
General Electric Co..... 431	Radiart Corp., The..... 475	Wright-DeCoster, Inc..... 474
General Transformer Corp.		Y
Second Cover		Yaxley Mfg. Division..... 459
Gross Radip Co..... 479		



This Catalog Can SAVE YOU MONEY - but It CAN Do Even MORE

THE "Largest Radio Catalog Ever Issued" can save you money, yes. You will find thousands of items—*nationally known and nationally advertised merchandise*—at money-saving prices! But you will also find other things equally important to you! For example, this catalog has been called a Guide Book for the radio service man, buyer and "ham." Whatever you need in the field of radio is listed—whether it be a new, year-ahead 24-tube radio receiver with metal tubes or a 5c binding post. Tubes, kits, replacement parts, P.A. and ham equipment, receivers, accessories, tools—*anything and everything*.

WHAT'S NEW IN RADIO!

Servicemen tell us this catalog helps them to keep posted on radio's newest developments. The latest improvements in every branch are accurately reflected in the illustrations and descriptions of new merchandise. Keeping ahead of the times is a routine affair here at Wholesale. Because of our huge purchasing power (Wholesale Radio is the largest institution of its kind in the world), leading manufacturers bring their newest

products to Wholesale Radio months ahead of their general release.

A RADIO SHOW IN ITSELF

It takes hours to actually read through this big new catalog—a radio show window more complete than any show could ever be. Spend some time with it—"shop" the Wholesale catalog! Keep it for handy reference—for comparison of prices and service. You will find it helpful *in many ways!*

Spend a moment, if you will, reading about the service that is our pride and joy—the fastest, most efficient service in the entire industry. Service made possible by three huge mail order centers in New York, Chicago and Atlanta maintaining *complete stocks* of brand new, guaranteed merchandise.

IF YOU HAVEN'T A COPY—

Send for it today! It's absolutely FREE, of course. Catalog number 59 — 196 pages — the latest, greatest radio catalog ever issued! The coupon below will bring you one by return mail. Mail it TODAY.

WHOLESALE RADIO SERVICE CO.
 NEW YORK, N.Y.
 100 SIXTH AVE.
 CHICAGO, ILL.
 901 W. JACKSON BLVD.
 ATLANTA, GA.
 430 W. PEACHTREE ST. N.W.

WHOLESALE RADIO SERVICE CO., Inc.
 100 Sixth Ave., Dept. S-105
 New York, N. Y.

Please rush FREE copy of your new 1936 Catalog No. 59.

Name

Address

Town State

Also at 542 E. Fordham Rd., Bronx, N. Y., and 219 Central Ave., Newark, N. J.

NOW--Complete Factory Assembled!
Saves 9-10ths of your Time . . .

NEW NOISE-REDUCING TWINS

**LYNCH HI-FI
Assembled Antenna**



All ready to hang. Saves 90% of installation time. Any serviceman can install it—quickly, easily, correctly. Makes every set perform **\$6.75** better List

The above kit with 50 feet of famous LYNCH Giant Killer Cable (instead of twisted pair) **\$8.50** List

**THE ONLY TWO COMPANION DEVICES
FOR REDUCING NOISE ON ALL WAVES**

LYNCH FILTERADIO

Cuts out objectionable noise from the light line, consumes no current. Makes interference from circuit breakers, motor generators, etc., practically negligible. Easy to install: simple to adjust. One type serves all purposes. **\$5.00** List



[If local jobber or dealer cannot supply you, order direct, or write for details.]

ARTHUR H. LYNCH, Inc., 227 Fulton St., N. Y.
PIONEER OF NOISE-REDUCING AERIALS



MIDGET ELECTROLYTICS

200 and 450 v. ratings. Standard capacities.

• Heavy cardboard case
• wax sealed
• mounting flanges
• prigtails.

• And new low prices!
Install them
they'll stay put!

That slide rule tells you this is the smallest non-skipped 8 mfd. 450 v. electrolytic available. For compact assemblies. Use individually or in groups. Tear off mounting flanges if not needed. • Stock small assortment and be ready for any condenser replacement need.

DATA Send for latest catalog covering complete condenser and resistor line. Also sample copy of Research Worker. Meanwhile, meet your local AEROVOX jobber.



AEROVOX

CORPORATION
80 Washington St. :: Brooklyn, N. Y.

**HERE'S AN
ALLIGATOR**

*You Can Keep for a Pet
Around Your Own Shop*



Dress him in a red or black rubber insulator and he's absolutely harmless! He's trained to crawl into any kind of a hole and bite hard—but only where you want him to bite.

THE MUELLER ALLIGATOR CLIP

Has long, slender jaws with teeth that really mesh all along the sides and on the front end.

Has both screw and barrel connection.

Is very small and handy to use.

AND—It can be had with red and black rubber insulators which cover everything but the nose.

STOCKED BY JOBBERS EVERYWHERE

Write Factory for Free Samples

No. 85 Clip (only)—List 6c—10 lots 4c each


No. 87 Insulator (only)—List 5c—10 lots 3c each

(Packed in boxes of 10—1/2 red—1/2 black)

MUELLER ELECTRIC CO.

1584 E. 31st ST., CLEVELAND, OHIO

NEW . . . Practical—Profitable

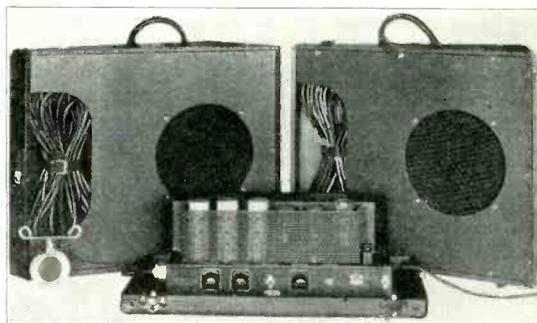

PORTABLE P. A. SYSTEM No. 99-F

A TWIN SPEAKER SYSTEM

You must investigate to appreciate its many advantages over ordinary public address systems. Ideal for halls, theatres, and outdoor public address use. Speakers can be set anywhere in the open and sound from both front and back of the speaker chassis is radiated in the direction desired.

**TECHNICAL
FACTS**

Designed to operate on 105-125 volt 50-60 cycle alternating current. Diaphragm crystal microphone has a 25 foot cable and a polarized plug. Hanging type fixture provided so that microphone can be hung from arch or ceiling if desired. Microphone and phone pickup volume control provide for mixing voice with musical background. Compact, light, easy to handle.

*Ask for details about P. A. System
No. 99-F*

**OPERADIO
MANUFACTURING COMPANY**

ST. CHARLES, ILLINOIS

Export Division, 347 Madison Ave., New York, N. Y.

INSTRUMENTS THAT

MARK


the dependable shop!

THE VACUUM TUBE VOLTMETER
THE SELECTIVE ANALYZER
THE ALL-WAVE OSCILLATOR

by **WESTON**



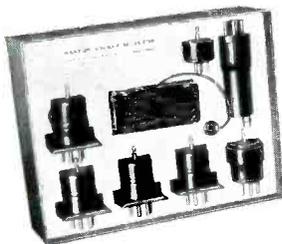THE WESTON
SOCKET SELECTOR SET
MODEL 666 TYPE 1B



Bring your analyzer out of the obsolete class with the inexpensive WESTON Socket Selector Set. Fits all Analyzers. Ask for full details.

Nothing can surpass this group of servicing instruments . . . from a standpoint of *efficient* servicing, or profitable servicing.

The Weston Selective Analyzer is a life-time instrument . . . ready for any and all receivers. It measures in fundamentals . . . current, voltage, resistance and output . . . fully protecting this analyzer against early obsolescence.

The All-Wave Oscillator is triple shielded and built with the same care as a laboratory instrument. It will do a precision aligning job on

all modern radio receivers.

The Vacuum Tube Voltmeter, used with the Oscillator, will measure gain per stage . . . r.f. amplitude in oscillator circuit of superheterodynes . . . check the pre-selector or i-f. stages in superheterodynes . . . check the impedance of chokes, condensers, etc., and other voltage measurements.

The coupon will bring you full data on these and all other Weston instruments for radio servicing . . . Weston Electrical Instrument Corporation, 604 Frelinghuysen Avenue, Newark, New Jersey.

WESTON

Radio Instruments

WESTON ELECTRICAL INSTRUMENT CORPORATION
604 Frelinghuysen Avenue, Newark, N. J.
Send bulletin on Weston Radio Instruments.

Name

Address

City and State

Buy with Confidence

where you see this sign



You will see this sign in the windows of leading distributors and on their counters. Its mere presence is evidence of leadership. Where you see it, buy with the confidence that here is an alive and alert firm whose business policy is to protect your interests by selling you only good merchandise. Genuine RCA Replacement Parts are an essential in service work, because they are built with the same precision as the original parts. When you repair any make of receiver with genuine RCA Parts your customer knows you have used the best. RCA Parts are, therefore, the best possible builders of good-will



for the distributors who sell them and the dealers and service men who use them in service work. Be sure to get the RCA Parts Catalogue, which not only lists thousands of parts, but also contains a guide to replacements in RCA Victor, G.E., Westinghouse and Graybar sets, a tube chart, diagrams of socket connections, and complete specifications of the various parts. RCA Service Equipment, such as the Oscillograph, Test Oscillator, Output Indicator, etc., is illustrated and described. The book contains 92 pages, is free, and can be had from any RCA Parts Distributor—wherever you see the RCA sign of confidence.

RCA PARTS DIVISION

RCA Manufacturing Co., Inc., Camden, N. J., a subsidiary of the
RADIO CORPORATION OF AMERICA