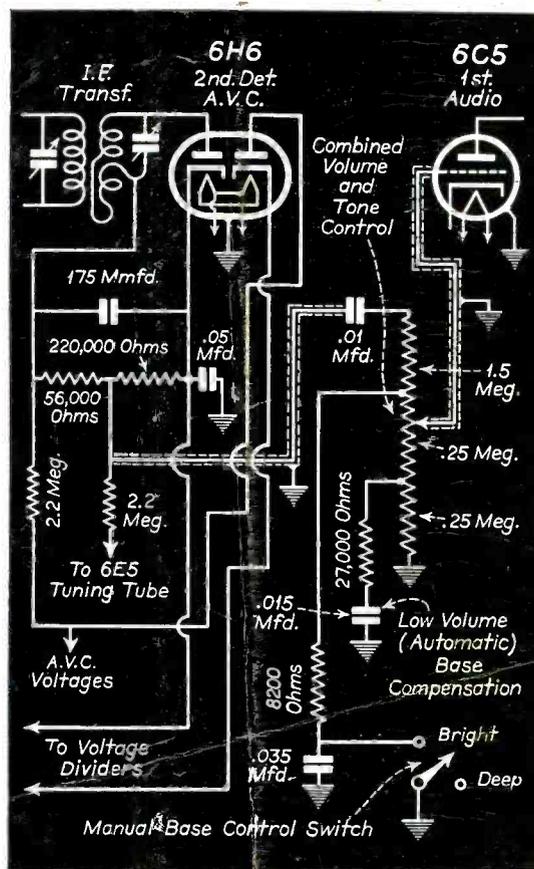


SERVICE

A MONTHLY DIGEST OF
RADIO
AND ALLIED MAINTENANCE



PER COPY
25 CENTS

Music-Speech Control Circuit
(See Page 252)

JUNE
1936



Leadership gives birth to Responsibility

In pioneering the dry electrolytic condenser, Mallory assumed a definite responsibility in the application and servicing of condensers in radio sets. And Mallory has not stopped with the production of a magnificent replacement condenser line, but has carried the principle of universal application to its logical climax by publishing the Mallory Condenser Service and Replacement Manual.

In developing the Mallory Vibrator, Mallory engineering in a few short years brought about really effective all-electric automobile radio reception. But Mallory engineering did not stop with the Mallory Replacement Vibrator line. Mallory has made effective servicing of auto radio sets a practical reality through the appearance of the Mallory Auto Radio Service and Replacement Manual.


In introducing constant improvements in Replacement Volume Controls, Yaxley engineering has brought about undreamed of precision in universal applications for set servicing. And leadership again asserted its sense of responsibility to servicing in compiling the Yaxley Replacement Manual and Service Guide to team with Yaxley Replacement Volume Controls and related parts.

In discharging its responsibility to servicing, Mallory demonstrates its leadership in a most practical way. The man who employs the Mallory-Yaxley Manuals in the universal application of Mallory-Yaxley Replacement Products procures for himself the most effective tools ever devised for an ever widening scope of profitable servicing.

MALLORY

P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA
Cable Address—Palmallo

YAXLEY

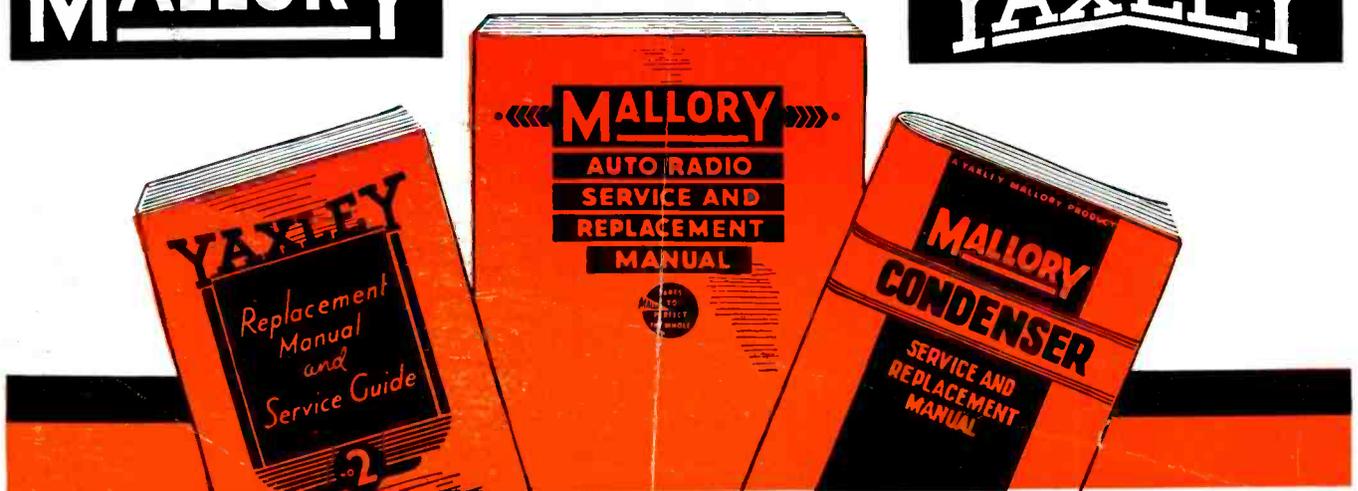

RESEARCH KEEPS GENERAL ELECTRIC YEARS AHEAD



Announces

Focused Tone

RADIO'S
NEWEST
MARVEL

Watch for Your Local
G-E Radio Distributor's
Announcement of His
Dealer Showing

- or better still, phone, wire or
write him for the date of this
important event.

Your customers will always be glad they bought
G-E Focused Tone Radio - and you will
ALWAYS be glad you sold it.

GENERAL  ELECTRIC
Focused Tone Radio

APPLIANCE AND MERCHANDISE DEPARTMENT, GENERAL ELECTRIC COMPANY, BRIDGEPORT, CONN.

SERVICE

A Monthly Digest of Radio and Allied Maintenance
 Reg. U. S. Patent Office. Member, Audit Bureau of Circulations

EDITOR

Robert G. Herzog

JUNE, 1936

VOL. 5, NO. 6

EDITORIAL CONTENTS

FEATURES

Hearing Aid Devices.....	263
Music-Speech Control Circuit.....	252
Practical Uses of The Decibel System By L. T. Chadbourne.....	251
Relayed Frequency Pickup By Mirko Paneyko.....	266
Supreme 89C Tube Checker.....	274
The Parts Jobber By Adolph Langer.....	253
The Signal Divider By Nathan I. Daniel.....	260

ANTENNA	248
---------------	-----

ASSOCIATION NEWS	280
------------------------	-----

AUTO RADIO

Bosch 636, 637.....	268
Zenith 7-M-91S, 7-M-91D.....	270

CIRCUITS

Atwater Kent 485Q, 515Q.....	257
Bosch 636, 637.....	268
Grunow 5G	254
High Gain Amplifier Using Signal Divider..	263
Multiple Use of Hearing Aid.....	264
Music-Speech Control Circuit..... Front Cover	
Supreme 89C Tube Checker.....	274
The Signal Divider Battery Biased.....	260
The Signal Divider Self Biased.....	260
Typical All Electric Hearing Aid.....	264
Wells Gardner 6F Service Changes.....	278
Wells Gardner 7K.....	258
Zenith 7-M-91S, 7-M-91D.....	270

GENERAL DATA

Atwater Kent 485Q, 515Q.....	256
Grunow Chassis 5G.....	254
Philco 70 Service Note By Al. Beers.....	259
Philco 87 Service Note By Al. Beers.....	259
Music-Speech Control Circuit.....	252
Technical Features of 1936 G.E. Radios....	255
Wells Gardner 7K.....	258

HIGHLIGHTS	282
------------------	-----

MANUFACTURERS	284
---------------------	-----

PUBLIC ADDRESS

Hearing Aid Devices.....	263
Practical Uses of The Decibel System By L. T. Chadbourne.....	251
Relayed Frequency Pickup By Mirko Paneyko.....	266
The Signal Divider By Nathan I. Daniel.....	260

RECEIVER CASE HISTORIES	276-278
-------------------------------	---------

TEST EQUIPMENT

Supreme 89C Tube Checker.....	274
-------------------------------	-----

BRYAN S. DAVIS
President

JAS. A. WALKER
Secretary

Chicago Office—608 S. Dearborn St.—C. O. Stimpson, Mgr.
 Telephone: Wabash 1903

Wellington, New Zealand—Tearo Book Depot.

Published Monthly by the

Bryan Davis Publishing Co., Inc.
 19 East 47th Street
 New York City

Telephone: Plaza 3-0483



SANFORD R. COWAN
Advertising Manager


PAUL S. WEIL
*Eastern Advertising
 Manager*

A. B. CARLSEN
Circulation Manager

Cleveland Office—10515 Wilbur Ave.—J. C. Munn, Mgr.
 Telephone: Republic 0905-J

Melbourne, Australia—McGill's Agency.

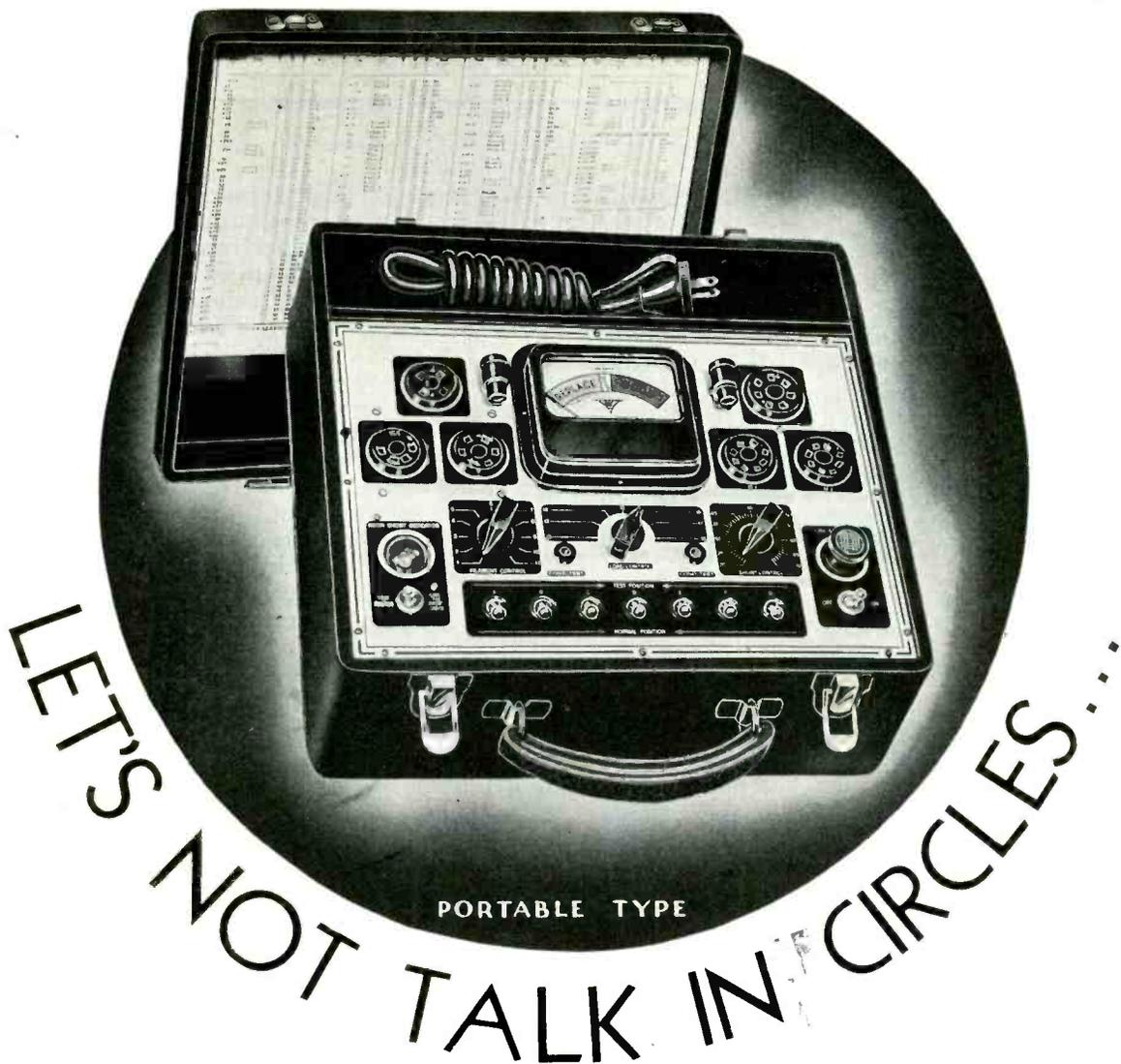Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.



FACTS are what you want... *and here they are!*

"PRECISION" ELECTRONOMETER Model No. 500. A Modern Tube Analyzer.

- IMPRESSIVE in appearance, SIMPLE in operation, will save time in quickly locating tube defects. Portable, counter and panel types available.
- EXTREME FLEXIBILITY is provided by means of a group of switches giving a complete FREE POINT TUBE ANALYSIS SYSTEM. This method amply affords a means of accommodating FUTURE releases without the necessity of wiring.
- ALL types of glass, metal, metal glass and octal base tubes can be accommodated. More than 300 tube numbers.
- LINE VOLTAGE is checked directly on the meter for accurate control.
- "HOT" INTER-ELECTRODE SHORT and "HOT" CATHODE LEAKAGE TESTS.
- NOISY and FADING tubes are detected through the use of a sensitive neon short check system and a hot cathode leakage test, in addition to the electron activity measurement.
- "TUBE MERIT" is indicated by readings of REPLACE—WEAK—GOOD, in three colors.
- All tests are obtained from any ONE of the individual required sockets (no shifting).
- Center tapped filament tubes Nos. 6Z5, 12A5 and 12Z5, that have internal cross connections, can be short checked without the use of extra switches.
- Each portion of multi-section tubes is given a SEPARATE test.
- Tubes are tested under PROPERLY RATED LOADS.
- SPECIAL DEALER PRICE.

PRECISION
 APPARATUS CORPORATION
 821 EAST NEW YORK AV., BROOKLYN, N. Y.

INTERESTED . . .

Send photographs, detailed specifications, circuit diagram and prices. Please include the name and address of my local distributor where I may see the ELECTRONOMETER Model 500 in operation.

Name

Address

City State

THE ANTENNA . . .

BATTERY RECEIVERS FOR UNWIRED HOMES

PRACTICALLY ALL THE larger receiver manufacturers, in their 1936 and 1937 lines, feature mantel and console type battery receivers in all price ranges for use wherever electric light lines are not available. Added to this, numerous wind and gasoline driven battery charging devices are being marketed. These items open the vast remote rural radio and service markets for exploitation. Although wind power is probably the oldest type of power harnessed by man, its practical application always has an intriguing and romantic aspect. The idea of "getting power to operate the radio for nothing" is an angle that may help sell both the receiver and the wind driven charger.

. . .

A NEW YEAR IN RADIO

THE RADIO MANUFACTURERS throughout the country have announced or are about to announce their 1937 line of radio receivers. Many features of these sets are worthy of note. The single band receiver is a rarity among the new announcements, and many cover the short-wave bands to as low as five meters. With the inclusion of automatic frequency control (as predicted in a recent issue of SERVICE) in the higher priced receivers, an attempt is made by some of the manufacturers to personalize the receiver by lettering the actual call letters of the stations on the dial. Tuning is remarkably simple in all these models.

Practically all the manufacturers have adopted the octal type tube socket giving the individual the choice between metal and metal-glass tubes.

Cabinets are similar to those presented last year except that the long, low, mantle type is featured to a greater extent. Speakers have also been improved and full high fidelity is available in many models. The famous 6L6 type tube has appeared in several models and over 30 watts of undistorted audio power can be delivered to the output circuits.

. . .

CONVENTIONS AND PUBLIC ADDRESS

THE PUBLIC ADDRESS HORIZON looks bright for the rest of the year what with the many conventions and exhibitions now in progress or about to begin. At such gatherings in the past public-address equipment played an important role when used for speech amplification, for announcements, for ballyhoo, for sound effects, for entertainment, for intercommunication, for recording of vocal events and numerous other purposes.

This year, decidedly a convention year, people are attending gatherings more than ever before. A much enlarged California-Pacific International Exposition, at San Diego, is running into a very successful second year. Visitors from every state in the Union will attend the Texas Centennial, to be celebrated throughout the state of Texas in cooperation with the main exposition at Dallas. The Great Lakes Exposition at Cleveland, the political conventions at Cleveland and Philadelphia, the nation-wide local political rallies and the countless centennials (such as those held at Bridgeport, Connecticut; Long Island, New York; Newark, New Jersey, and throughout the State of Arkansas); are now in progress or will open soon, many to continue for the rest of the year. In the light of past experience public-address equipment will play an important role, not only as expressed above, but for a host of other purposes still to be conceived.

With the recent improvements in microphones, phonograph pickups, speakers and tubes those prospects that already possess public-address equipment furnish a ready market for these improved accessories or even for rebuilding of their present amplifiers along high-fidelity lines.


. . .

HEARING AIDS

STATISTICS SHOW THAT there are over a million people throughout the United States that experience difficulty in hearing. This definitely shows that the market for hearing aid equipment is not limited.

In all hearing aid advertising it is best to take into consideration the sensitiveness of the deaf to their defect. They usually object to wearing the earpiece because they feel that their deafness becomes conspicuous by so doing. They do not realize that it becomes more conspicuous when they cannot hear.

To aid in making sales it is often advisable to loan an instrument to the prospect for a few days. The ears of the individual that experiences difficulty in hearing are not only deaf but they are also dull. That is to say the ears are unaccustomed to sound and require a little time to adjust themselves to their new found hearing. At first the user of the aid will hear the drone of conversation without being able to understand the individual syllables, unless they are facing the speaker and assisting the amplifier by lip reading. During this ear training period the Service Man can determine which type of earpiece (bone conductor or earphone) is better suited to the individual, and make such minor adjustments in the equipment that might be required. Because of the thrill these individuals experience on regaining their hearing they will carry their enthusiasm to every other deaf person in their acquaintance. Several satisfied customers is all the Service Man needs for a good start in this profitable field.

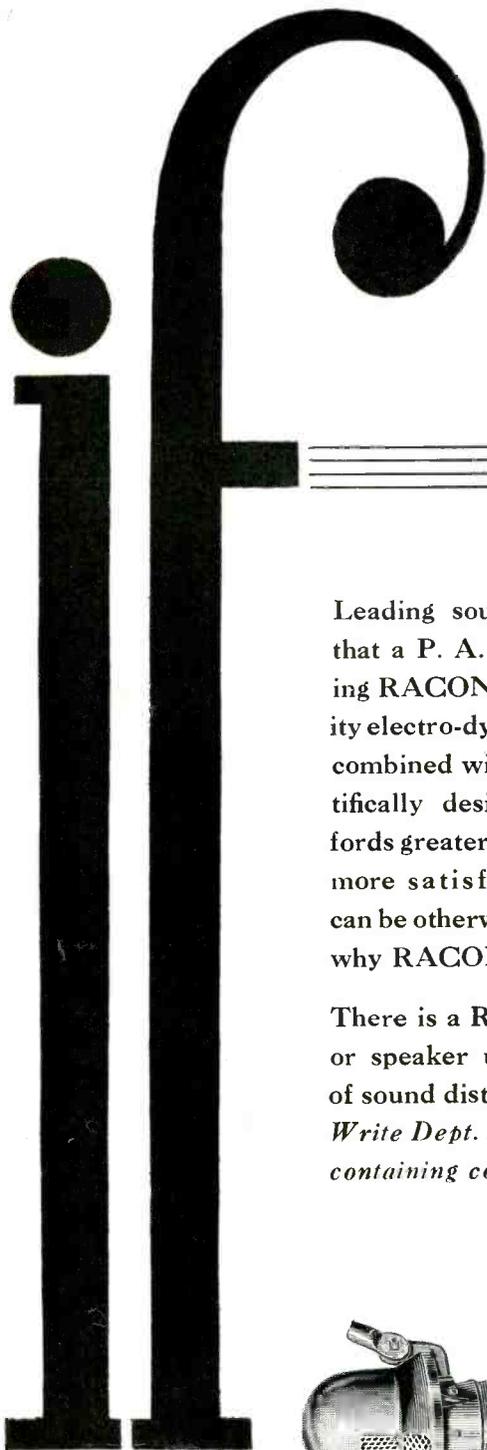

YOU WANT FINE SOUND REPRODUCTION

... call RACON!

Leading sound engineers agree that a P. A. installation employing RACON'S newest high fidelity electro-dynamic speaker units, combined with a RACON scientifically designed projector, affords greater sound efficiency and more satisfactory results than can be otherwise obtained. That's why RACONS are leaders!

There is a RACON horn, baffle, or speaker unit, for every type of sound distribution installation. Write Dept. S-6 today for catalog containing complete details.



4



1

2

3

1 RADIAL HORNS are accurately designed to project sound with even intensity throughout the complete 360 degree radius. Ideal for use on trucks, tower equipment, amusement parks, and auditoriums. There are no "dead spots" where Radial Horns are used.

2 UNBREAKABLE SIX FOOT TRUMPETS are demountable into three sections. Made of RACON Acoustic Storm Proof material, reinforced throughout, and guaranteed unbreakable. The ultimate in trumpet design, highly efficient and able to stand the roughest treatment.

3 A COMPACT SOUND PROJECTOR for yearly service. Consists of an all steel bullet, acoustically padded and having proper release for wide response. Can be mounted in any position; suitable for indoor or outdoor use.

4 The TURRET PROJECTOR consists of the new RACON high fidelity speaker, rigidly mounted on the "mechano-acoustic" impedance matching throat element and housed in all steel, acoustically damped bullet back. They may be mounted or hung in nearly any position.

RACON ELECTRIC CO. INC.

52 East 19th Street
LONDON, ENG.

New York, N. Y.
TORONTO, CANADA

RACON

You need this Book!

New 1937 Edition of
the Electrad Volume
Control Guide Now
Ready—*Get Your Copy
While Supply Lasts!*




Actual Size
6½x9½

This edition of the popular Electrad Volume Control Guide will be bigger and better than ever. The most complete listing of manufacturers, set models and control requirements you've ever had. Gives all latest specifications, resistances in ohms, list prices, etc., to enable you to make a quick, perfect replacement on any set you may be called in to service. Service men have found the previous Electrad Volume Control Guide a real trouble-saver and dollar-maker and this edition will be even better!

FREE if you send in 2 Complete Electrad Volume Control Cartons!

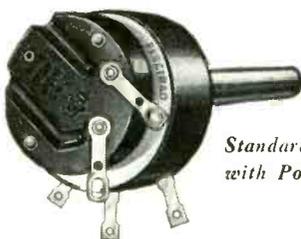Send in 2 complete Electrad Volume Control Cartons with your business card or letterhead and we'll send you the Guide free—and with it, we'll place you on the mailing list to receive all 1936 issues of the new Electrad Contact. The supply is limited. Send in your cartons at once!



Standard Replacement Unit
with Power-Switch attached.

What Service Men Say About the "Electrad Contact"

The first issue of the new Electrad Contact is now in the hands of service men who were on the 1936 Guide mailing list. Enthusiastic letters from readers are coming in every day. Read these excerpts—

"... by far the finest little dope sheet that has come to my attention." . . . H. J. Potthoff, N. Y. C.

"... enjoyed the first issue immensely. A valuable contribution to our cause." . . . Frank J. Lhotsky, Cicero, Ill.

"... takes up problems which service men are generally encountering. . . . A real addition to any service man's library and mighty helpful." . . . B. O. Burlingame, Greenwood, Miss.

"... contains much valuable information to the service man. Keep up the good Contact!" . . . John Kinsel, Pittsburgh, Pa.

YOU NEED THIS GUIDE—you'll certainly want the Contact—send in your 2 cartons and get both FREE! Do it now! Address Dept. S-6.

ELECTRAD, INC.
175 VARICK STREET, NEW YORK

SERVICE

A Monthly Digest of Radio and Allied Maintenance

FOR JUNE, 1936

PRACTICAL USES OF THE DECIBEL SYSTEM

By L. T. CHADBOURNE

THE decibel (db) provides a convenient method of measuring and rating amplifiers and other public-address equipment. Simple addition of db ratings indicates whether an amplifier possesses enough gain for a given microphone, or if preamplification is needed, how much gain the preamplifier must have. Or, if the same amplifier is to be used with both microphone and phonograph, for example, it may have enough gain for the first but too much for the second, resulting in overloading. The db ratings again will indicate how much attenuation (loss) must be introduced in the phono circuit. Modern amplifiers are often built with high-gain and low-gain input circuits, and references to db ratings will indicate which type of input device to connect to each.

The db is used in two ways, and these must be carefully distinguished. An amplifier may have, for example, a *gain* of 120 db, but a *power output* of 30 db. There is only one db, but it can be made to express two ideas, both very useful in practical operation provided that the distinction between them is clearly understood.

It will be helpful to consider first the use of the db to express gain, or amplification, and to ignore for the time being its use as a measure of power. In this connection one value lies in the fact that it expresses a large, complicated number by a small, simple number. Modern amplifiers may multiply the sound power applied to their input terminals in the order of a thousand billion times. In the decibel system, such an amplifier is said to have a gain of 120 db. If the amplification is one hundred billion, the gain will be 110 db. If the amplification lies somewhere between the two, the gain may be 115 db, or 118 db, and so on.

To determine the db equivalent of a whole number such as 1,000, simply count the zeros, and multiply by ten. There are 3 zeros in 1,000, and the db

equivalent is 3 times 10, or 30. Similarly, in one thousand billion (1,000,000,000,000) there are 12 zeros. Multiply 12 by 10, and the db equivalent of that amplification is 120. In one hundred billion there are only 11 zeros (100,000,000,000) and the db equivalent is 110. Unfortunately in actual practice power ratios do not come out in round numbers such as 10, 1,000, or 100,000 as used here; they are much more likely to be uneven figures like 12 or 976 or 96,354. The advantages of using the db are therefore much greater in simplifying calculations. The db equivalent of 96,354 is 49.8, a number which may not look simple but which is far more convenient to handle than 96,354 and for practical purposes may be considered 50. Simple tables are available for converting any power ratio to db.

A very important advantage of the db in connection with amplification problems is that large and clumsy numbers can always be *multiplied* by *adding* their db equivalents. Thus, a thousand times a thousand is a million. But 1,000 is equivalent to 30 db. Thirty plus thirty is 60. And 60 is the db equivalent of 1,000,000 (6 zeros multiplied by 10).

Suppose the output of a given microphone must be multiplied one thousand billion times before it can be heard by a public-address audience. Suppose the amplifier available is such that it will multiply the input given it by only 100 million. What pre-amplification is needed?

Using ordinary arithmetic, this question becomes: by what number must 100,000,000 be multiplied, to produce 1,000,000,000,000? Dividing the smaller number into the larger one gives 10,000 as the preamplification necessary.

But it is infinitely simpler to use the decibel equivalents of all these numbers, and say: 120 db gain is needed, the amplifier has only 80 db gain; 40 db must be added by the preamplifier.

Two advantages of the decibel sys-

tem have been outlined thus far: it expresses large, clumsy numbers by small, simple ones and it substitutes addition of small numbers for multiplication of large ones.

However, these advantages are not the chief reason for the existence of the decibel system. So far as arithmetic goes, that system is a convenience but not a necessity. The decibel system is necessary in considering the effect of sound upon the human ear. This will become clear after the second use of the db has been explored.

In addition to expressing amplification, the db is used to rate power level, as a valuable substitute for the watt. Obviously, since the db is capable of comparing the output power delivered by an amplifier with the input power supplied to that amplifier, it can also compare the same output power with any accepted standard, or "reference level." Thus, if the standard were chosen as 1 watt, a power of 100 watts would represent 20 decibels. Actually, 1 watt is not the standard chosen. There are several standards of power level. The most common is 0.006 watts or six milliwatts. Some engineers and manufacturers prefer 0.01 watt, or ten milliwatts. The older standard, however, is still preferred, and is the basis of most db ratings at the present time.

Taking 0.006 watt as the reference standard, assume an amplification of 10. There is 1 zero in ten; multiplying by 10 gives a level of 10 db above zero, or a power of 0.06. An amplification of 100 above zero gives 0.6, and (there are two zeros in 100) a level of 20 decibels. An amplification of 1,000 gives 6 watts, or 30 decibels; of 10,000, 60 watts, or 40 db.

Most microphones and other input sources have power levels far below zero. This is natural, since zero level (0.006 watt) was chosen as representing the minimum power that could be heard when operated through a stand-

ard telephone receiver. A modern microphone may have a level of *minus* seventy db, or lower.

Two practical precautions are necessary in using the db in ordinary work. One is to make sure that all db ratings are based on the same reference level; while the other is to make sure that they are based on actual working conditions, and not on an ideal setup that makes the microphone output or amplifier gain, as the case may be, look larger than they will actually prove in use.

While it is possible to calculate the db gain of an amplifier by consideration of its input and output impedances, the amplification factor of its tubes and the efficiency of the circuits in which they operate, the voltage gain of its transformers, and the losses introduced intentionally or otherwise, in practice it is customary to depend upon the manufacturer's rating. This may be optimistically expressed, and it may be necessary to obtain assurance that the rating given will apply with the input and output impedances actually to be used. Similarly, microphones may be rated under laboratory conditions, and the level that will be delivered to the input impedance of the amplifier used may have to be requested specifically.

Given the correct data, however, it is necessary only to add or subtract db ratings.

Many step-by-step volume controls used in sound work are arranged to change volume in the amount of three db per step. The value three is chosen because of the nature of the action of the human ear.

To understand this point, remember

Sound Apparatus	Power in Watts	Level in DB	Amplification	Gain in DB
Velocity Microphone	0.000,000,000,06	-80	10	10
	0.000,000,000,6	-70	100	20
Crystal Microphone	0.000,000,006	-60	1,000	30
	0.000,000,06	-50	10,000	40
Carbon Microphone	0.000,000,6	-40	100,000	50
	0.000,006	-30	1,000,000	60
Phono Pickup	0.000,06	-20	10,000,000	70
	0.000,6	-10	100,000,000	80
Telephone Receiver	0.006	0	1,000,000,000	90
	0.06	+10	10,000,000,000	100
	0.6	+20	100,000,000,000	110
Small P-A System	6.	+30	1,000,000,000,000	120
Large P-A System	60.	+40	10,000,000,000,000	130

that whenever volume in watts is *multiplied* by ten, the change is expressed in db by *adding* ten. Thus, 6 watts is a level of plus 30 db; 60 watts is a level of plus 40 db, and plus 50 db would be 600 watts.

Now the ear hears only changes in volume that are proportionate to the volume already present. If the sound level is one watt, an increase to 10 watts will decidedly be heard—but a change from 600 to 610 watts cannot be detected by any human being. Heavy traffic, trains or thunder create noise in that order of power, and will mask completely and render inaudible a ten-watt loudspeaker at equal distance from the ear.

The ear will detect an increase in volume only if the volume already existing *is doubled, or more than doubled*. Similarly, a decrease in volume will not be noticed unless the existing volume is reduced to one-half, or less.

If the existing volume is one watt, a change to two watts will be heard; but if the level is 6 watts an increase

to less than 12 watts will make little or no impression.

But in the decibel system, it is necessary to multiply volume by ten if 10 db are to be added to the db rating, and merely doubling the volume adds only 3 db.

That being the case, the smallest change in volume that can be heard is one of 3 db, and step-by-step volume controls are built accordingly.

If a loudspeaker system has an output power of plus 30 db, or 6 watts, the level must be increased to 33 db, or 12 watts, for the increase to be noticed. The next change that can be heard is to 24 watts, or 36 db; the next, to 48 watts, or 39 db, and the next (40 db being 60 watts) is to 42 db, or a wattage of 96.

All the figures hitherto used in this article are based upon the decibel system in which 0.006 watt is taken as the standard power level. If 0.01 watt is made the standard the method of calculation remains unchanged, but the resulting figures are altered.

MUSIC-SPEECH CONTROL CIRCUIT

(See Front Cover)

THE most common type of tone control, used on amplifiers and receivers, noticeably reduces the volume heard from the loudspeaker when the control is turned to the deep or base position. This makes it necessary for the listener to readjust the manual volume control. Along with the modern trend toward assuring the listener of the maximum in reception and convenience with a minimum of manual control, RCA and other manufacturers have automatically compensated for this reduction in volume. As far as the listener is concerned turning the tone control to the deep position has the effect of *adding* the base response.

THE TONE CONTROL CIRCUIT

The circuit which accomplishes this effect is shown on the front cover. The values given are those used in the RCA T10-3 receiver. A 2-megohm manual

volume control with taps at 250,000 ohms and 500,000 ohms from the low volume end is used as the grid load for the first audio tube (a type 6C5 in the particular circuit shown). Other values may be used depending upon the type of tube and the amount of compensation required.

BRIGHT POSITION

If the tone control is left in the normal or bright position the lower quarter of the volume control is shorted by the 8,200-ohm resistor. Characteristic curves for resistance-coupled amplifiers show that the efficiency of an audio stage is lowered (with no material effect on the frequency response) by reducing the resistance in the grid load circuit. The volume heard from the loudspeaker is consequently somewhat less than the receiver would deliver, for that setting of the volume

control, if the 8,200-ohm resistor were removed. This loss is suitably compensated in the original circuit design by sufficient increase in the gain obtained from this stage over what normally would be required.

DEEP POSITION

With the tone control in the deep position the 0.035-mfd condenser is connected in series with the 8200-ohm resistor. The higher frequency notes are still effectively shorted, since the resistance of the 0.035-mfd condenser to notes above 3000 cycles is less than 1600 ohms. On the other hand, the resistance of this condenser to the lower frequencies (in the neighborhood of 30 to 50 cycles) is of the order of 100,000 ohms. It is easily apparent that no reduction of volume should result, but

(Continued on page 266)

THE PARTS JOBBER

By ADOLPH LANGER*

THE Parts Jobber is called upon to offer every possible assistance to the Service Man in his territory. The successful Parts Jobber must maintain a policy of rendering the most competent service possible at all times. Constant maintenance of a complete, adequate stock of parts and supplies, coupled with an efficient system for rapid delivery, are fundamental factors in rendering proper assistance to the Service Man. But carrying an extensive stock is not the only factor. The Service Man should be assisted to take advantage of the ready source of necessary parts. Providing this advantage is definitely the Parts Jobber's responsibility to his dealers.

THE PARTS JOBBER'S SALESMAN

All salesmen should be thoroughly trained, not only as to the merits and applications of the many diversified items handled by the house, but also in what rightly is their personal obligations to the individual Service Man and dealers upon whom they call. Outstanding above all instructions to salesmen is the one that requires complete dealer satisfaction. Every piece of merchandise sold to a dealer must be exactly what the dealer requires to serve his purpose to the best advantage both as to quality and economy. Strict observance of this

*H. L. Dalis, Inc.

house rule by all salesmen will increase good will and avoid misunderstanding.

The Parts Jobber's salesman should also be prepared to help the Service Man build his own business. The salesman should furnish the Service Man with available consumer literature prepared by the various parts manufacturers and help him obtain the greatest advantage therefrom. Posting the Service Man on new saleable products is also part of the salesman's daily work.

Another service the Parts Jobber's salesman can render to his customer is that of advising him as to the variety and quantities of small parts his service department should stock to meet current requirements. The advice given in this respect should be the salesman's honest estimate of his customer's requirements judged from the salesman's experience with similar dealers. Overstocking any customer will hardly add to future goodwill.

THE INSIDE ORGANIZATION

Naturally a live, successful sales force requires the close cooperation of a trained, competent inside staff. From the moment an order reaches the house until the time it is placed into one of the delivery trucks the order should undergo the strict supervision of highly-trained department heads. Every effort

should be made to maintain speedy daily delivery service without sacrificing accuracy and dependability. Capable telephone order clerks especially trained to handle customers' emergency requirements are an integral part of every efficient Parts Jobber organization.

Technical problems, increased tremendously by the many changes and improvements in radio design and construction, make it imperative that the individual Service Man keep himself posted on all the latest service kinks and methods. The Parts Jobber should have a technical staff capable of rendering the Service Man practical assistance on such problems as the tolerance of resistors or condensers, etc. While the Service Man should not expect the Parts Jobber to render assistance in the actual servicing of a particular receiver, the Parts Jobber should cheerfully give aid in answering questions pertaining to manufacturers' ratings and similar problems coming under his proper sphere. To enable the technical staff to handle these inquiries efficiently and thoroughly, all available listings of receiver and accessory manufacturers should be collected and filed for ready reference.

Effective service rendered the dealer by any Parts Jobber, once again, goes beyond merely stocking merchandise and materials to fill the Service Man's requirements. Legitimate Parts Jobbers cooperate with the Service Man and dealer by confining themselves to catering entirely to those customers who maintain actual business establishments. Retail consumers and part-time Service Men should be referred to dealers in their locality.

Handling only dependable quality merchandise and selling at the lowest possible prices consistent with such quality further establishes dealer confidence.

Effective service demands that the Parts Jobber keep in step with modern conditions. Constant adjustment to meet the demands of changing conditions as they arise in the daily course of business is essential. The Parts Jobber should point the way to improvement for his customers.



Mr. Langer
at his desk.

General Data . . .

Grunow Chassis 5G

The Grunow 5G chassis is a 5-tube, 3-band receiver with avc, tone control, and a band-spread dial. The tubes used are: 6A7 first detector-oscillator, 6D6 i-f amplifier, 75 second detector-avc-audio amplifier, 42 power-output amplifier and 80 rectifier. The complete circuit diagram is shown in Fig. 1.

The frequency range is divided into three bands or divisions, one covering the band from 550 to 1750 kc (band A), one covering the band from 1700 to 5680 kc (band B) and the third covering the band from 5400 to 18000 kc (band C).

DIAL SETTING

Turn the knob until the condensers are fully meshed. The dial pointer (hour hand) should be on the horizontal line of the dial, pointing to 9 and 3 o'clock. The minute hand should be at 12 o'clock or in a vertical position.

I-F ALIGNMENT

Connect signal lead of test oscillator to grid of 6A7 through .25 mfd con-

denser. Connect the ground lead to the chassis.

(A) Set dial pointer to 1400 kc and range switch on position A.

(B) Place test oscillator in operation to 490 kc or 465 kc (see note below). Turn receiver volume control and tone control to maximum.

(C) Attenuate test oscillator output to lowest value, consistent with obtaining a readable indication on output meter.

(D) Adjust four i-f trimmers, A1, A2, A3, A4, located on the i-f transformers on top of chassis, see Fig. 2, until maximum output is obtained. During alignment, maintain as low a value of signal as will allow obtaining of accurate adjustment.

Note: Due to interference caused by commercial code stations in some locations, it has been necessary to use two intermediate frequencies on this receiver, one of 490 kc where code interference is in the neighborhood of 455 kc and the other where the interfering stations are operating in the 500 kc band, use an i-f of 465 kc.

The i-f of the receiver is stamped on

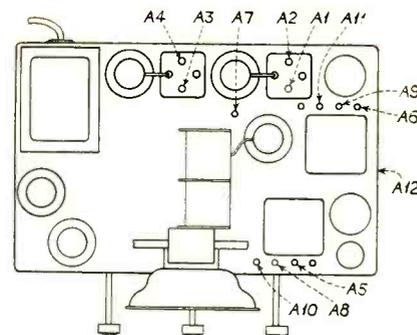


Fig. 2. Chassis view showing trimmer locations

the rear of the chassis, and if there is any doubt as to i-f peaking, it is only necessary to apply a variable i-f signal to the i-f amplifier and maximum output will indicate resonance or frequency at which the i-f's were peaked.

To further overcome this form of interference, sets peaked at 465 also incorporate a wave filter in the antenna circuit. This filter should be tuned to the same frequency as the i-f transformers. Tuning is accomplished after the set has been completely aligned by applying the i-f signal through to a .0002-mfd condenser to the antenna binding post of the receiver, and tuning the wave filter condenser (A12) (located on the right-hand side of the chassis)

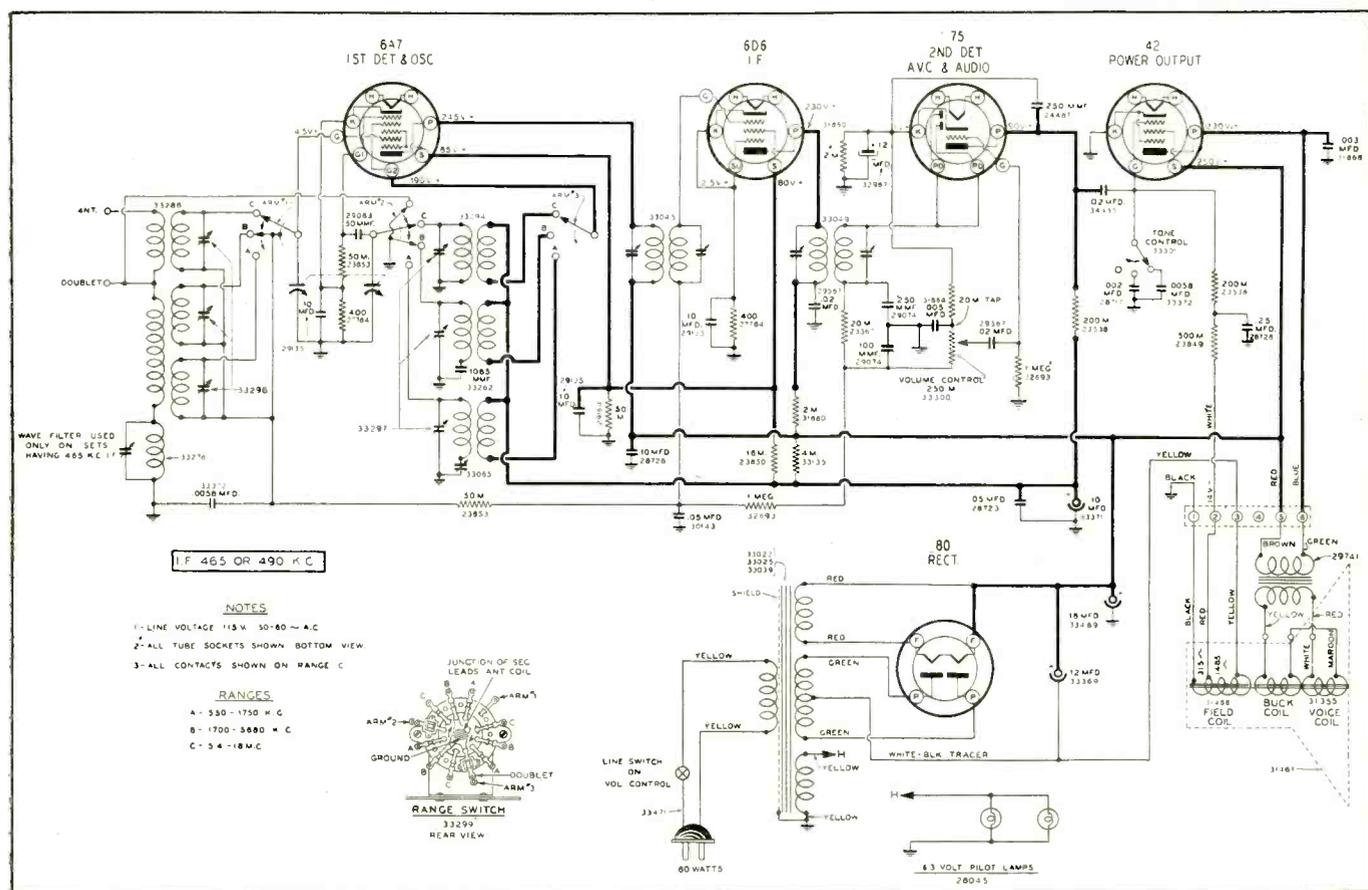


Fig. 1. Complete circuit diagram Grunow 5G.

Technical Features of 1936 General Electric Radio Receivers																							
Model No.	A51	A56	A52	A55	A53	A54	A63	A65	A64	A66	A67	A70	A75	A83†	A85†	A82	A86	A87	A88#	A125	A205†	A208#	N60
Cabinet	Compact	Console	Table	Console	Table	Compact	Table	Console	Table	Console	Console	Table	Console	Table	Console	Table	Console	Console	Console	Console	Console	Console	Auto.
Line * supply	105-130V 25-133~ A.C.-D.C.	A-C-V	A-C-V	A-C-V	A-C-V	105-130V 25-133~ A.C.-D.C.	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	A-C-V	6V. D.C.
Range	540-1720 Kc. 2.2-7.0 Mc.	540-1720 Kc. 2.3-7.0 Mc.	540-1720 Kc. 2.3-7.0 Mc.	540-1720 Kc. 2.3-7.0 Mc.	540-1600 Kc. 2.4-6.8 Mc.	540-1720 Kc. 2.3-7.0 Mc.	540-1800 Kc. 5.4-18.0 Mc	540-1750 Kc. 1.75-6.0 Mc. 6.0-19.5 Mc.	540-1740 Kc. 1.72-5.8 Mc. 5.8-18.0 Mc.	540-1740 Kc. 1.72-5.8 Mc. 5.8-18.0 Mc.	540-1740 Kc. 1.72-5.8 Mc. 5.8-18.0 Mc.	540-1750 Kc. 1.75-6.0 Mc. 6.0-19.5 Mc.	530-1650 Kc.										
Line watts **	52	70	65	60	75	60	85	100	100	85	100	100	100	100	100	100	105	150	125	125	325	7 Amp.	
Audio power	1.4	5.0	3.0	1.1	3.5	3.0	3.0	3.7	11	3.0	3.7	3.7	3.7	11	11	7.0	8.1	15	15	40	40	4	
I.F. Peak	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	465 Kc.	175 Kc.	
Dynamic sp'kr	6 1/2"	8"	9"	7"	6 1/2"	7"	8"	8"	8"	10 1/4"	10 1/4"	8"	10 1/4"	9"	11"	10 1/4"	10 1/4"	10 1/4"	10 1/4"	10 1/4"	(2) 10 1/4"	6"	
Tone control	2 Point	2 Point	2 Point	2 Point	2 Point	2 Point	2 Point	2 Point	Continuously variable														
Sensitivity control																							
Tuning meter																							
Dual speed tuning drive																							
"V"-Doublet terminal board																							
Variable condensers	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	3	
Number of tuned circuits	7	5	5	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	
Dial	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	Enlarged window	
R.F.																							
1st. Def. Oscillator	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6K7	
Intermediate frequency	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	
2nd. Def. A.V.C.	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	6Q7	
1st. Audio	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	25A6	6F6	
2nd. Audio	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	
3rd. Audio	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	
Rectifier	25Z6	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4	6X5	
Chassis No.	RB 15	RB 16	RB 10	RB 14	RB 9	RB 14	RB 8	RB 9	RB 8	RB 8	RB 8	RB 7	RB 7	RB 18	RB 18	RB 6	RB 6	RB 6	RB 5	RB 5	RB 2	N60	

* A 105-125V. 50-60~. V 105-120V, 200-230V. } 40-60~
 C 105-125V. 25-60~. 115-130V, 220-250V. }
 † Speech Clarifier ‡ Automatic phono. combination
 ** 105-125V. 50-60~

GENERAL DATA—continued

level without bringing the avc into action.

Short-wave Range

No trimmers on this range.

Broadcast Range

Connect signal generator to antenna and ground of set, using a 250-mmfd condenser in series with the antenna lead. With signal generator and dial at 1500 kc, peak the broadcast oscillator trimmer A2. Use the first peak as A2 is screwed in from a loose position. Tune generator to 560 kc and peak broadcast tracking trimmer A3 while rocking variable condenser one division around the 560 kc mark. Repeat adjustments at 1500 and at 560 kc if necessary.

Wells Gardner 7K

This model is a three-band receiver with the following tuning ranges: 148 to 380 kc, 535 to 1,730 kc and 5,750 to 18,300 kc. The maximum power output

is 3½ watts. A complete circuit diagram is shown in Fig. 1 with the tubes used, their functions and the voltages encountered throughout lettered on the diagram. The trimmer locations are given in Fig. 2. The voltages were measured with a 1,000-ohm-per-volt voltmeter with the antenna shorted to the chassis and the volume control on full.

DUAL VOLUME CONTROL

A dual manual volume control is employed. In one section the audio voltage applied to the first audio section of the 6B7 tube is varied (R10). In the other section, the r-f and i-f bias is varied (R2). The purpose of the latter section is to reduce the sensitivity of the receiver at the low volume settings in order to cut down noise pickup between stations. The variable section R2 is shorted out through contact No. 4 of the interstage section of the band

selector switch when in the short-wave position.

ALIGNMENT PROCEDURE

Correct alignment is extremely important in connection with all-wave high-fidelity receivers.

If a station is tuned in with the selectivity control in the broad position and this control is then turned to the sharp position, the station may disappear. This is not an indication that the receiver is out of alignment.

Use a non-metallic screwdriver for the adjustments. The complete procedure is as follows:

I-F ADJUSTMENT

Set the signal generator for a signal of 456 kc.

Connect the output of the signal generator through a 0.1-mfd condenser to the grid of the first detector.

Connect the ground lead of the receiver to the ground post of the signal generator.

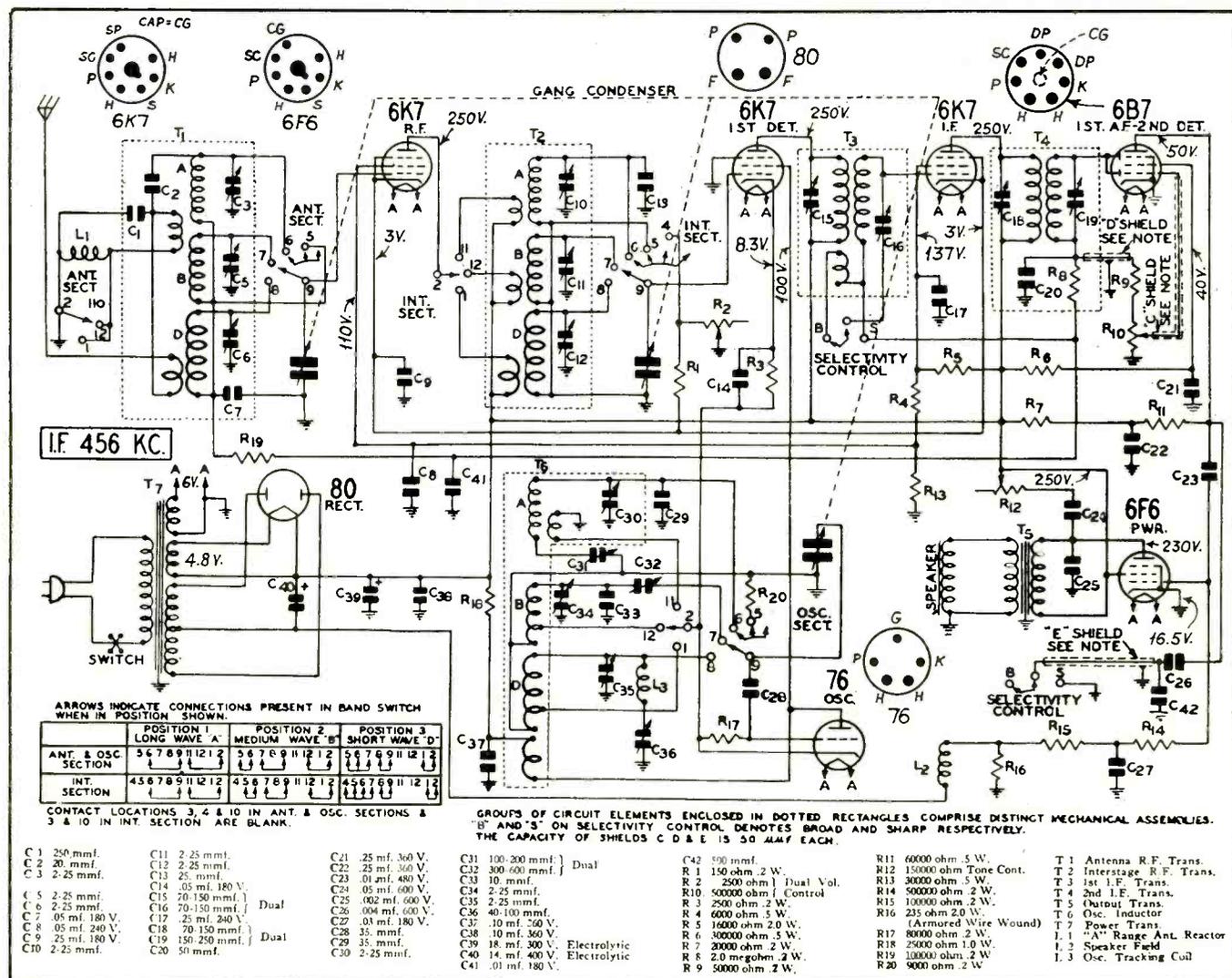


Fig. 1. Circuit diagram Wells Gardner 7K.

GENERAL DATA—continued

Turn the band selector to the range B position (medium-waveband—green dial color).

Turn the selectivity control to the sharp position and keep it in this position for all adjustments.

Turn the volume control to the maximum position.

Attenuate the signal from the signal generator to prevent the levelling-off action of the avc.

Then adjust the four i-f trimmers until maximum output is obtained. The adjusting screws for these condensers are reached from the top of the chassis.

RANGE A ALIGNMENT

380-kc Adjustment

Set the signal generator for 380-kc. Turn the rotor of the tuning condenser to the full open position.

Turn the band selector to the range A position (long-waveband—purple dial color).

Connect the antenna lead of the receiver through a 200-mmfd condenser to the output of the signal generator.

For this and all subsequent adjustments keep the volume control at the maximum position and attenuate the signal from the signal generator to prevent avc action.

Adjust the oscillator range A trimmer (C30) until maximum output is obtained. The location of this trimmer is shown in Fig. 2.

350-kc Adjustment

Set the signal generator for 350-kc.

Turn the rotor of the tuning condenser carefully until maximum output is obtained.

Adjust the interstage range A trimmer (C10) and antenna range A trimmer (C3) to maximum.

Do not change the setting of the oscillator range A trimmer.

165-kc Adjustment

Set the signal generator for 165-kc.

Turn the tuning condenser rotor until maximum output is obtained.

Turn the rotor slowly back and forth at the same time adjusting the 165-kc trimmer until the peak of greatest intensity is obtained. See Fig. 2 for location of this trimmer.

RANGE B ALIGNMENT

1,730-kc Adjustment

Set the signal generator for 1,730-kc.

Turn the rotor of the tuning condenser to the full open position.

Turn the band selector to the range B position (medium-waveband—green dial color).

Keep the antenna lead of the receiver

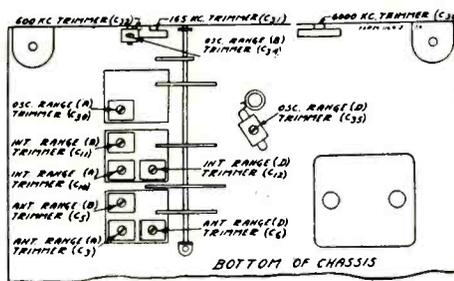


Fig. 2. Trimmer locations, W. G. 7K.

connected through the 200-mmfd condenser to the output of the signal generator.

Adjust the oscillator range B trimmer (C34) until maximum output is obtained. The location of this trimmer is shown in Fig. 2.

1,500-kc Adjustment

Set the signal generator for 1,500-kc. Turn the rotor of the tuning condenser carefully until maximum output is obtained.

Loosen the pointer set screw and set the large pointer at the 1,500-kc mark on the medium-waveband scale. Retighten the set screw.

Adjust the interstage range B trimmer (C11) and antenna range B trimmer (C5) to maximum.

Do not change the setting of the oscillator range B trimmer.

600-kc Adjustment

Set the signal generator for 600-kc.

Turn the tuning condenser rotor until maximum output is obtained.

Turn the rotor slowly back and forth at the same time adjusting the 600-kc trimmer until the peak of greatest intensity is obtained. See Fig. 2 for location of this trimmer.

RANGE D ALIGNMENT

18,300-kc Adjustment

Set the signal generator for 18,300-kc.

Connect the antenna lead of the receiver through a 400-ohm resistor to the output of the signal generator.

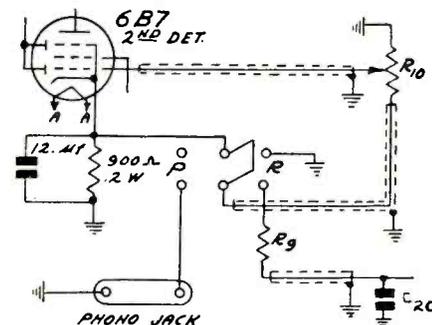


Fig. 3. Phono connections, W. G. 7K.

Turn the rotor of the tuning condenser to the full open position.

Turn the band selector to the range D position (short-wave band—red dial color).

Adjust the oscillator range D trimmer (C35) until maximum output is obtained. See Fig. 2 for location of this trimmer.

15,000-kc Adjustment

Set the signal generator for 15,000-kc.

Turn the rotor of the tuning condenser carefully until maximum output is obtained.

Adjust the interstage range D trimmer (C12) and antenna range D trimmer (C6) to maximum.

When adjusting the interstage range D trimmer, it will be necessary at the same time to turn the tuning condenser rotor slowly back and forth until the peak of greatest intensity is obtained.

Then go back and repeat the procedure as given for the 18,300-kc adjustment. If it is found necessary to make any appreciable change in the setting of the oscillator range D trimmer, the 15,000-kc adjustment must be repeated.

Do not make any further change in the setting of the oscillator range D trimmer.

6,000-kc adjustment

Set the signal generator for 6,000-kc.

Turn the tuning condenser rotor until maximum output is obtained.

Turn the rotor slowly back and forth at the same time adjusting the 6,000-kc trimmer until the peak of greatest intensity is obtained. See Fig. 2 for location of this trimmer.

PHONOGRAPH CONNECTIONS

Phonograph connections can be made as shown in Fig. 3. Knockouts are provided in the back panel of the chassis for mounting the phono jack and phono switch.

Philco 70

Intermittent noise: Plate and screen voltages on 47 varies from 38 to 220 v. Check 47 bias section on voltage divider, if defective replace; value 180-ohms.

Al. Beers

Philco 87

Hum: If the hum is not due to the filter condenser it may be caused by the two 0.5-mfd condensers (C19, C20) which by-pass the 26 filaments. If their d-c resistance is less than 25-megohms, noticeable hum will result.

Al. Beers

Public Address . . .

THE SIGNAL DIVIDER

By NATHAN I. DANIEL

THE advantages of push-pull operation of power tubes are well known. The greater power output and the decreased distortion, due to cancellation of even order harmonics, are highly desirable features of a push-pull circuit.

But in order to obtain push-pull action certain requirements must be met. The signal to be amplified must be supplied to both branches of the push-pull circuit with the same amplitude and in opposite phase. It has been general practice to resort to one of two methods or modifications of them, to satisfy the required conditions. Both, however, suffer drawbacks.

THE COMMON METHOD


The most common method of obtaining push-pull operation is to make use of an input transformer with a center-tapped secondary, which supplies each grid with a signal of equal magnitude and opposite phase. This would be ideal were it not for the fact that a really good transformer is rather expensive.

PHASE INVERSION

The other method of obtaining push-pull is phase inversion. This makes use of the fact that the signal at the plate of an amplifier tube is exactly out of phase with the signal at its grid. In operation one grid of the push-pull stage is fed directly from the preceding tube which also feeds an extra amplifier tube, which in turn feeds the other grid of the push-pull stage. The signal as applied to one grid of the output stage has passed through one more tube than the signal at the other grid and is consequently out of phase with it. In order to keep the signal voltages equal at both grids the extra or phase inverter tube receives only the correct fraction of the full output of the preceding tube. This is done as a rule by tapping the load resistance at the proper point.

Since one branch has one more tube than the other it is difficult to keep the overall amplification of both branches the same at all frequencies. Furthermore, the balance tends to be upset by changing the tubes or even by natural aging when they are not changed.

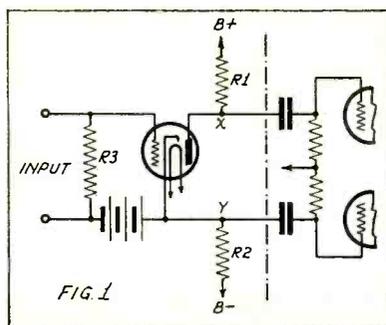Another type of push-pull amplifier has appeared which at first glance seems to use neither a transformer nor a phase



inverter. In this type, the grid of one of the output tubes is connected in the usual manner (resistance coupling generally) to the preceding amplifier tube. The other output tube obtains its signal from the plate circuit of the first output tube. Upon analysis it becomes apparent that this is also a phase inversion circuit, one tube performing the dual role of output tube and phase inverter.

In spite of its limitations, the phase inverter had enjoyed considerable success. This is due, of course, to the ease with which it lends itself to resistance coupling with the accompanying low cost and high-fidelity possibilities.

The preceding discussion has made it evident that it would be highly desirable if a push-pull circuit could be found that would permit of the use of resistance coupling, and also avoid the instability of the phase inverter.

Just such a circuit is presented in the following:

THE SIGNAL DIVIDER

Fig. 1 represents an ordinary triode with resistor R1 connected between plate and B plus, resistor R2 between cathode and B minus. Each resistor is approximately half the value of the plate resistor that would ordinarily be used with this tube in straight resistance coupling. R3 is the grid return resistor and is connected from grid to cathode through a grid biasing battery of the proper size. If a signal is now applied between grid and cathode, it will be amplified and appear across each of the load resistors R1 and R2 with equal amplitude but in exactly opposite phase. That this is so is evident from the following considerations. Since the current flowing through R1 and R2 is identical, and both resistances are equal in

value, whatever voltages are developed across them must also be equal (providing of course that incidental capacities due to tube structure or wiring are kept to a negligible value, or are equalized). Also note that as the plate current decreases the voltage drop across both load resistors decreases. Accordingly the potential at point X becomes more positive approaching B plus potential as a limit, while the potential at point Y becomes less positive and approaches B minus potential as a limit. When the plate current increases, the opposite relations hold true, points X and Y approaching each other in potential, with the theoretical limit that both can reach the voltage half way between B plus and B minus, or half the B supply voltage.

Perhaps a simpler way to look at the circuit is to regard the cathode-to-plate space as a variable resistance, Z, in series with R1 on one side and R2 on the other. As Z becomes large (due to the signal on the grid going further negative than the normal biasing voltage) point X is crowded toward B plus potential, while point Y is crowded toward B minus. As Z becomes smaller (as is the case when the grid goes less negative) points X and Y approach each other in potential. Evidently the potentials on points X and Y are always varying in the opposite directions and with equal magnitudes.


All that needs to be done now to obtain perfect push-pull operation is to connect points X and Y to the respective grids of the next stage through coupling condensers, as indicated to the right of the dotted line in Fig. 1.

For the sake of brevity and in order to avoid confusion, we shall hereafter refer to the above described circuit as a signal divider stage.

WITHOUT BIAS BATTERY

In Fig. 2 is shown a method of dispensing with the biasing battery. R4 is the self-biasing resistor of the usual value for the type of tube being used and C1 is a high capacity by-pass condenser of the low voltage electrolytic type.

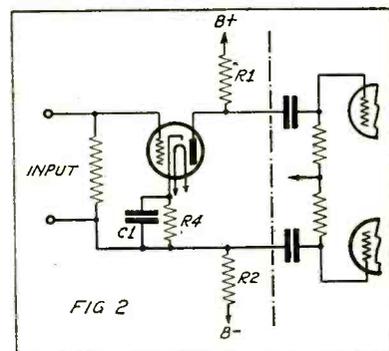Care must be taken that the tube chosen for the "signal divider" stage be capable of supplying an output volt-



2 out of 3 RADIO VIBRATORS are **MALLORY** made

MALLORY is recognized as **STANDARD**



Vibrators made by Mallory are *standard equipment* in America's most popular automobile radio receivers and in 6 volt and 32 volt household receivers.

The use of Mallory Replacement Vibrators is *standard practice* on the part of radio service men the country over.

A mere handful of Mallory Replacement Vibrators render universal service to over 3,000,000 automobile radio sets now in use.

Mallory Replacement Vibrators save time — save inventory — reduce stock investments. They are dependable in service. They provide more efficient performance and are easy to install. They build good will and good business!

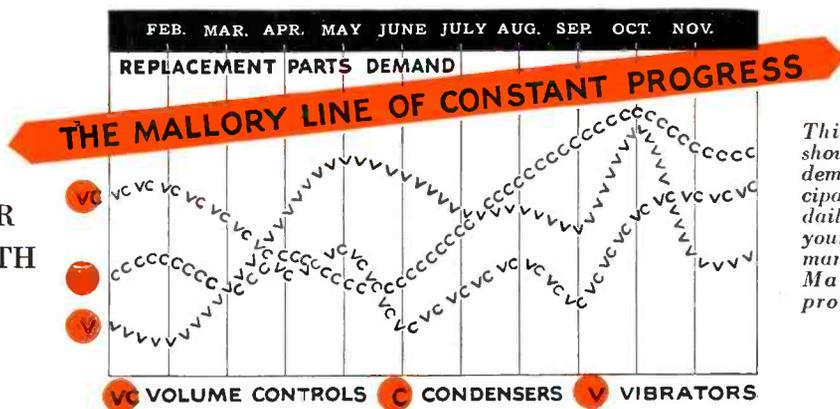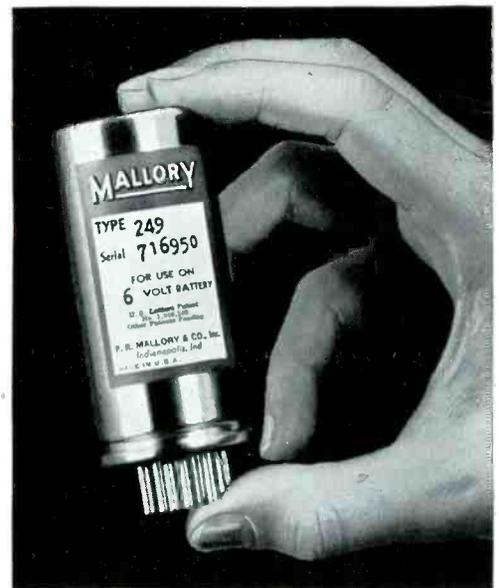Be sure your vibrator replacement work is done with Mallory. It pays — in profits, as well as in customer satisfaction — as thousands of service men can tell you.



This composite graph shows the trend of service demand for the three principal replacement items in daily service work. Check your needs with the demand — and depend on Mallory for constant progress.

BUILD YOUR
BUSINESS WITH
MALLORY

MALLORY

P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA
Cable Address—PELMALLO

YAXLEY

MORLEN BEAM TUBE AMPLIFIERS



A SUPERB ACHIEVEMENT IN PUBLIC ADDRESS AMPLIFIERS

THE new MORLEN MC60 and MC120 amplifiers, using the 6L6 Beam-Power Tubes in the output stages, make available to the rental operator and p.a. installer, two amplifiers, unexcelled in operating features and performance. The 6L6 beam-tube is a tetrode of high-power input sensitivity—the *utmost* in performance is obtained from tubes of this type by their use in the recently announced MORLEN "Power-Driver" circuit, as used in the latest MC models.

THE MC60 and MC120 amplifiers incorporate a universal, dual channel input, with full mixer control, a main gain control, and tone control. The output is a dual winding transformer having 500 ohms impedance across one winding and 15 ohms tapped at 8 and 4 ohms across the second winding. Practically any combination of speakers or other load devices can be operated from the MC output. Also included is a dual AC receptacle, a fuse under protective cover and a main AC ON and OFF switch. All MC amplifiers are complete on one chassis, from input to output and in power ranges from 19 to 120 watts.

Due to the elimination of interstage transformers (a feature of the "Power-Driver" circuit), the frequency response of the MC 6L6 amplifiers is essentially flat from 40 to 14,000 cycles, thruout a wider power range than with any other system.

Write Dept. S. 6 for detailed specifications.

MORLEN ELECTRIC COMPANY, INC.
60 W. 15TH ST. - NEW YORK, N. Y.

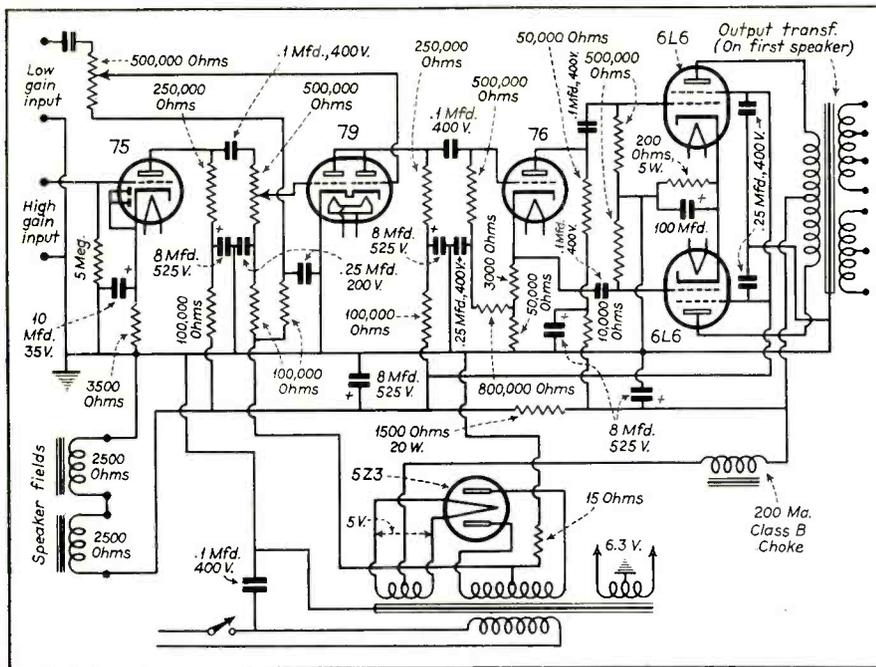


Fig. 3. High-gain amplifier using signal divider.

age sufficient to drive the power stage to full output. If the power tubes require an unusually high driving voltage (e. g. the 2A3 which requires 124 peak volts grid to grid) it becomes necessary to use a resistance coupled push-pull voltage amplifier stage ahead of the output stage. It is possible but not desirable, to boost the output voltage by using inductance instead of resistance in the "signal divider" load.

THE COMPLETE AMPLIFIER

The schematic of a complete amplifier is shown in Fig. 3. The problem of including amplification ahead of the signal divider was solved, and the results were well worth the effort.

The layout of parts aside from following general practice is not critical. The absence of transformers which might cause inductive hum pickup contributes to this flexibility.

Bias is provided for the 76 signal divider stage by the 3,000-ohm resistor in series with the 50,000-ohm cathode load resistor. The grid return is led to the proper potential by means of the 800,000-ohm resistor which also serves to isolate the grid circuit from the cathode circuit. This resistor, which is in parallel with the 50,000-ohm cathode load resistor as far as the signal currents are concerned, is of such value that the shunting effect offsets the series effect of the 3,000-ohm bias resistor. Thus the cathode load is kept at the

same value as the plate load.

The 15-ohm resistor in the transformer high-voltage return circuit need not be by-passed because of its low value. The 79 grid return network may be simplified by using a grid bias cell from each return to the ground. This not only eliminates the 15-ohm resistor but also eliminates both 100,000-ohm resistors and their 0.25-mfd condensers.

The signal delivered by the 79 appears across its load resistor, the B plus side of which is necessarily by-passed to ground. Therefore the signal when applied to the 76 appears between grid and cathode instead of between grid and cathode. As a result the signal divider stage loses most of its amplification properties, due to degeneration caused by the unby-passed load in the cathode circuit. The ratio of input signal to output signal appearing across cathode load is approximately one-to-one but as the signal across the plate load equals the signal across the cathode load, the total amplification of the signal divider is approximately 2. This holds true regardless of what type tube is used as signal divider as long as the signal is impressed between grid and ground instead of grid and cathode.

This partial loss of amplification is unimportant as it is easily made up for by the high gain of the 79. The important thing is that perfect push pull action with excellent fidelity is obtained at low cost.

Hearing Aid Devices

The following paragraphs taken from "The Volta Review," a monthly magazine for the hard-of-hearing, written by Florence Woolley under the title "Hearing With Deaf Ears," is a good argument to help put over the sale of the hearing aid amplifier.

"Do you know that to everyone, except those born totally deaf, hearing is just as necessary to physical well being as walking, seeing, eating, etc.? Of course a person can live without walking but he cannot live a normal, healthy life; the same applies to the other functions. I know that a great many of my friends will become indignant and say that the lack of hearing has no effect on their physical condition. I beg their most humble pardon and disagree. In the first place, every hard-of-hearing person suffers from some form of nervousness, which unconsciously he acquired with his loss of hearing. In the second place he lives under a constant strain that is anything but beneficial. And in the third place his mental attitude is not, and cannot be, that of a normally hearing person. All of this has a tendency to cut him off and leave him in a little world of his own, partly because he could not find any way to prevent it, but mostly because he was sensitive. The hardest thing for the hard-of-hearing person to say is, 'I cannot hear.' When I began to lose my hearing, I found out that strangers who did not realize I was deaf thought I was stupid. Now I would rather have people know that

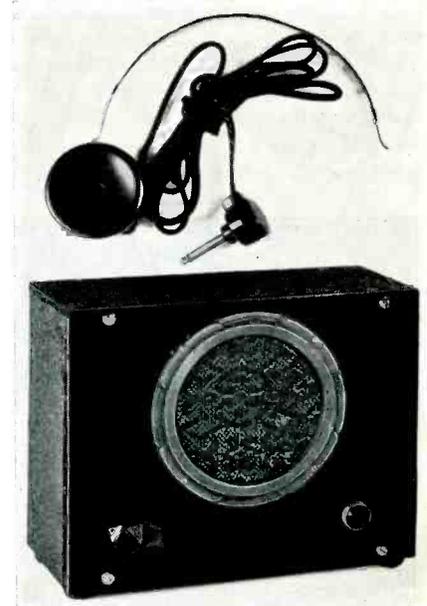


Fig. 1. Typical hearing aid.

I am deaf, and I find it a splendid alibi for any lack of brains.

"I was an entirely different person after I lost my hearing from what I had been when I had normal hearing. The only time I could be sure of not missing anything was when I was doing the talking, and I was actually getting tired of it. About this time, the hearing device manufacturers had a brain storm, or inspiration from heaven, or something, and began to make *real* instruments. It seems unbelievable that, after floundering along for so many years, they have made such rapid strides in the past three years. Hope furnished me with a real weapon and I made up my mind that I had been buried in silence long enough."

Hearing aid amplifiers are older than radio. In the early days of the vacuum-tube repeater they were used on telephones to assist the partially deaf in hearing telephone conversations. Carbon button microphones with button amplifiers were also used, and are still used, as portable lapel hearing aids. With the advances in tube and microphone design hearing aids were also improved. Portable battery amplifiers as well as all electric (a-c, d-c) aids are obtainable for every type of installation. In the home, at the office, on the street, in the theatre, church, or opera the partially deaf need no longer have difficulty in hearing—no more than a myopic individual need do without the convenience of glasses.

TYPICAL HEARING AID

The amplifier shown in Fig. 1 is a typical all-electric type for use at home, in the office, or wherever electric current (either a-c or d-c) is available. The cabinet in which the aid is housed can be chosen to best match the surrounding furniture. Soft rubber feet must be used to prevent shocks from reaching the microphone. The micro-

phone itself is mounted in its ring with flexible rubber bands. A sensitive carbon microphone is used in the amplifier pictured.

The complete circuit diagram is shown in Fig. 2. Metal tubes are used throughout. A 6F5 high-mu triode in the first stage, a 6C5 in the second stage and another 6C5 as the rectifier. The two stages are resistance coupled to each other. Microphone current is also supplied from the house mains through the rectifier-filter system.

PORTABLE AIDS

Portable types of hearing aid, making use of the '30 series of tubes, are also available. In this type the cabinet is usually designed for light weight and small size with due consideration to its long-life qualities under rough use. In the portable both the microphone and the chassis should be rubber mounted to completely prevent transmission of shock to the tubes or the microphone. Very small A and B batteries are available and suitable compartments must be provided. The entire aid, including batteries, need weigh no more than 7 pounds.

In some of the portable aids now available larger size batteries may be connected, through the use of suitable plugs, to provide economical use of the aid in the home or office.

In practically every hearing aid amplifier, using tubes for its amplification, a user with a 95 per cent loss of hearing could not only hear and understand normal conversation in a large office, but could also differentiate among speakers. The same user could take no part in the conversation when using the conventional label type of carbon button amplifier except through lip reading.

SALES SOURCES

The Service Man will find little difficulty in obtaining or building suitable

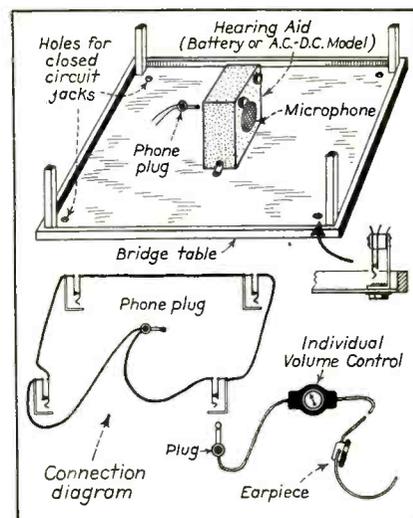


Fig. 3

equipment for a particular customer. His chief difficulty, rather, will be in locating and selling prospective customers. In small communities where each individual and his intricacies are known the partially deaf may be located by judicious questioning. Sales pressure must be tactful and is usually best in the form of printed matter, skillfully worded.

In larger communities hard-of-hearing individuals often form clubs or leagues. The names and addresses of the members of these leagues can be obtained from the secretary and used for direct-to-the-customer mail advertising.

Often the hard-of-hearing congregate in small groups and spend much of their time playing bridge or similar forms of group entertainment. A bridge table connected in the fashion shown in Fig. 3 will prove a convenient accessory to the complete enjoyment of the game. The loan of such equipment for an evening provides the entering wedge that may result in a sale of the complete unit.

A single desk or portable amplifier can be used in the circuit shown in Fig. 3 with a separate earphone for each player. The jack in each corner of the table is so connected that the dummy position (or any other position) can remove his earpiece without interrupting the functioning or disturbing the volume of the remaining players. Individual control of volumes at the earpiece is, of course, necessary in such installations. Similarly interconnected jackboxes can be constructed in the form of ash trays, chip-holders, etc., for multiple earphone connection to a single hearing aid amplifier.

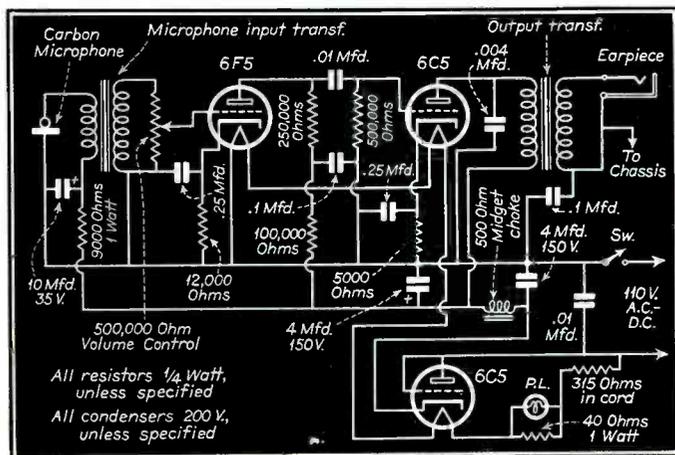


Fig. 2. Typical hearing aid circuit.



Most of the modern developments in quality audio transformers have been perfected by the UTC engineering staff. Among these developments are included the high permeability cast shield . . . the true hum balancing coil structure . . . the balanced variable impedance line which permits high fidelity response on every tap of a universal unit . . . the reversible mounting facilities . . . the separate ground terminal to assure positive connection to internal electrostatic shielding . . . etc. . . . Ask your local jobber for the U1100D bulletin containing detailed information and valuable circuit diagrams. This bulletin and the new UTC Circular Slide Rule . . . both for only 25c.

EXCLUSIVE UTC DISTRIBUTORS CARRYING A COMPLETE STOCK OF UTC PRODUCTS

Harvey's Radio.....105 W. 43rd St., New York, N. Y.
 Goldhamer's, Inc.....610 Huron Road, Cleveland, Ohio
 Wholesale Radio Service Co.....100 Sixth Ave., New York, N. Y.
 Wholesale Radio Service Co.....219 Central Ave., Newark, N. J.
 Wholesale Radio Service Co.....439 W. Peachtree St., N.W., Atlanta, Ga.
 Wholesale Radio Service Co.....911 Jackson Blvd., Chicago, Ill.
 Wholesale Radio Service Co.....542 E. Fordham Rd., Bronx, N. Y.
 Sun Radio.....227 Fulton St., New York, N. Y.
 Gross Radio, Inc.....51 Vesey St., New York, N. Y.
 Leeds.....15 Vesey St., New York, N. Y.
 Mohawk Electric Co.....1335 State St., Schenectady, N. Y.
 Walter Ashe.....1100 Pine St., St. Louis, Mo.
 Radio Shack.....46 Brattle St., Boston, Mass.
 Hatry and Young.....New Haven and Hartford, Conn.
 Film et Radio.....5 Rue Denis Poisson, Paris, France
 Hall's.....35 So. Cameron, Harrisburg, Pa.
 Herbach & Rademan.....438 Market St., Philadelphia, Pa.
 Radio Electric Service.....7th and Arch Sts., Philadelphia, Pa.
 Cameradio Company.....603 Grant St., Pittsburgh, Pa.
 W. H. Edwards & Co.....32 Broadway, Providence, B. I.
 Seattle Radio Supply, Inc.....2319 Second Ave., Seattle, Wash.
 Warren Radio.....1119 State Street, Erie, Pa.
 Radio Laboratories.....1515 Grand Avenue, Kansas City, Mo.
 Comet Radio.....65 Cortlandt Street, New York, N. Y.

Thor Radio.....167 Greenwich Street, New York, N. Y.
 San Francisco Radio Exchange.....1284 Market St., San Francisco, Cal.
 Straus Frank Co.....San Antonio, Texas
 Straus Frank Co.....Houston, Texas
 Rissi Brothers.....5027 Hamilton Ave., Detroit, Mich.
 Amateur Radio Equipment.....138 E. Butler Ave., Memphis, Tenn.
 Northeastern Radio.....281 Columbus Ave., Boston, Mass.
 Springfield Radio.....397 Dwight St., Springfield, Mass.
 Kraus & Co.....89 Broadway, Providence, R. I.
 Braid Electric Co.....107 Ninth Ave., Nashville, Tenn.
 Wisconsin Radio Supply.....134 W. State St., Milwaukee, Wis.
 Bruce Company.....206 E. Monroe, Springfield, Ill.
 Beaucaire Company.....228 Broadway, Rochester, N. Y.
 Dallas Electric Supply Co.....Dallas, Texas
 Peterson Lumber & Supply Co.....El Paso, Texas
 South West Radio Supply Co.....107 South St. Paul St., Dallas, Texas

SOUTHERN CALIFORNIA

Pacific Radio Exchange, Inc.....729 S. Main St., Los Angeles
 Radio Supply Co.....912 S. Broadway, Los Angeles
 Radio Television Supply Co.....1701 S. Grand Ave., Los Angeles
 Radio Specialties Co.....1816 W. 8th St., Los Angeles
 Zack Radio Co.....1000 S. Broadway, Los Angeles

UNITED TRANSFORMER CORP.
 72 SPRING STREET NEW YORK, N. Y.
 EXPORT DIVISION - 15 LAIGHT STREET, NEW YORK, N. Y.


A "RELAYED FREQUENCY PICKUP"

By Mirko Paneyko*

ELECTRICAL SOUND REPRODUCTION is based on the design and operation of a large number of components. It is generally assumed that the amplifier is the heart of a reproducing system and that the characteristics of the whole system are specified simply in terms of amplifier specifications. The design of the other two links of the system, the microphone or pickup and the loudspeaker, have lagged behind amplifier research.

We are here concerned with one particular link of a reproducing system, the phonograph pickup.

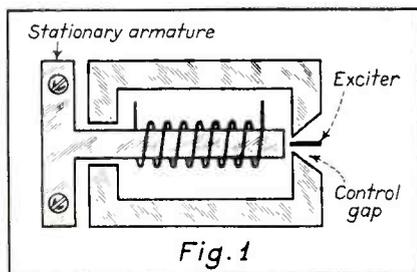As the first link of a reproducing system, the similarity of the pickup and the microphone is immediately apparent. Both constitute the first "electrical image-creating apparatus," the microphone being actuated by air vibrations and the pickup by record groove undulations. The difficult task of design of the phono pickup becomes apparent when one bears in mind that not only



must it be mechanically coupled to the record groove, but also in a high-impedance pickup sufficient displacement or stress must take place within the unit to generate approximately 2.0 volts—about two million times more than the output of a high-grade microphone. Despite commendable refinements in a few cases, the pickup of today is still a rather crude instrument—crude in comparison with the microphone—and it awaited definitely a new sort of idea, a new type of design.

The ideal pickup should have stability and dependability; a response characteristic which is flat from 50 to over 8,000 cycles, maintaining this response under large amplitude variations and changing weather conditions. It should also be able to withstand a temperature rise of from 40 to 60 degrees above 72 degrees F without ill effects and with normal response. The needle pressure on the

*Chief Engineer, M.P. Installations.

record should not exceed 2.75 to 3 ounces. The unit should be ruggedly built and adaptable to either low or high impedance. Further, it should be made as simple as possible to facilitate local servicing. The output could afford to be somewhat smaller than that of previously available models. Modern amplifier design scarcely calls for the necessity of large input voltages. The new unit to be described fulfills all the aforementioned conditions and great advance over present type units.

The reader is no doubt aware of the importance of the principle of relay, trigger or valve action. A small amount of motion, a small amount of energy is made to control large effects. If it were possible, in the described pickup unit, to keep the general dimensions of the magnetic circuit the same, and yet control the flux paths by the motion of a very small element rather than by that of the bulky armature, the problem of inertia and limited frequency response would be solved. This is exactly what has been accomplished in the new unit as may be seen from Fig. 1.

The armature is broken up into two parts: the major part, on which is wound the coil, is permanently clamped and stationary, while a very small portion, which the inventor refers to in his patent papers as the "exciter," reflects the motion of the needle and changes the magnetic reluctance of the armature path by changing the size of the "control air gap."

The moving system is reduced to the needle in its pivot and to the small exciter. The inertia of this system is considerably reduced, for not only is the mass of the exciter very small (see Fig. 2), but also the exciter is placed near the center of the axis of rotation so that the main part of the weight is that of the needle. A definite control of total effective inertia is obtained by using a longer or heavier needle for increased bass response, or a short and light

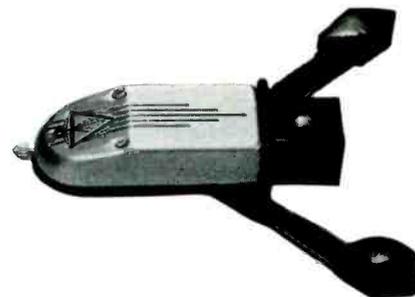
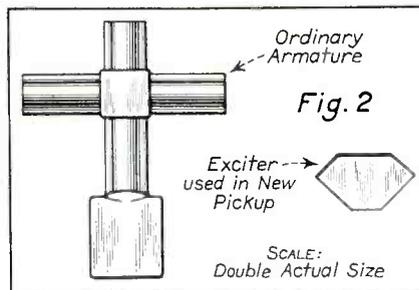


Fig. 3. The new pick-up.

needle for a flat overall response. The increased frequency range changes the surface scratch from standard records to a higher frequency hiss which is much less objectionable and easier to eliminate. The new unit when tested had a needle pressure of only 1.5 ounces on the needle point.

The construction of this pickup unit is very simple. The main part of the armature being stationary and solidly clamped, the oscillating part is easier to adjust and maintain in its proper position.

MUSIC-SPEECH CONTROL CIRCUIT

(Continued)

rather a slight increase since the grid load has been increased. Thus the net effect to the listener is an addition of the base notes.

LOW VOLUME COMPENSATION

Base compensation for the low volume settings of the manual volume control is a permanent part of the circuit. The circuit elements that provide this compensation consist of a 27,000-ohm resistor and a 0.015-mfd condenser which are connected to the 250,000-ohm tap of the manual volume control as shown in the cover diagram. When the volume control is at or below this tap the total resistance in the grid circuit to frequencies above 3,000 cycles is less than 30,000 ohms. For frequencies below 50 cycles the total impedance in the grid circuit is of the order of 150,000 ohms. This lower resistance to the high notes will effectively by-pass them to the ground circuits allowing the lower notes to feed the grid of the audio stage which in turn passes them on toward their final destination—the listener's ear.

• SERVICE FOR

**CONGRESSIONAL
LIBRARY
SELECTS**

**AUDAX
Pick-ups**

*The standard by which others
are judged and valued.*

Recently, the U. S. Library of Congress was in the market for FIVE THOUSAND Electric Pick-ups to be used on reading machines for the blind. . . . After drastic elimination tests on all makes and types,—AUDAX Pick-ups were selected.

AUDAX is prepared to supply your need, no matter what it may be.



The famous AUDAX "7-B" Cutter employs the identical principle as that of the magnetic cutter used in the new high fidelity recordings by the world's leading record manufacturers.

Cutters Listed from - - \$35.00 to \$125.00

Pick-ups Listed from - - \$9.50 to \$390.00

Watch subsequent issues for further details of the much talked of new-wide range development,—the AUDAX—

MICRODYNE

the "Relayed-Frequency" Pick-up


Write for information on all AUDAX Products

AUDAX COMPANY

500 Fifth Avenue

New York

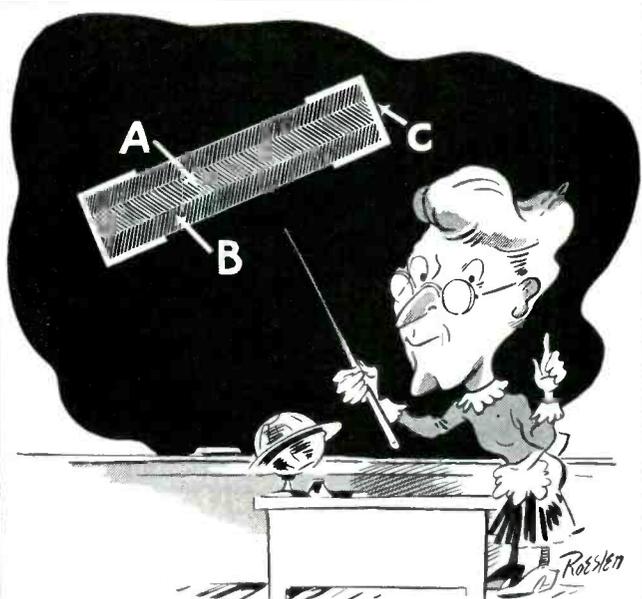"Creators of High Grade Electrical and Acoustical Apparatus Since 1915"




**The "A B C" of
Sturdy Resistors**

You'll go to the head of the class if you stick to CENTRALAB Fixed Resistors for your Replacement jobs.

You'll get A1 marks and earn special distinction as a fellow who "knows his stuff." Take teacher's advice and always use CENTRALAB Fixed Resistors (and Volume Controls.)

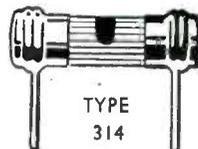- A. Center core of resistance material is surrounded by a dense shock-proof ceramic, providing strength and protection against humidity.
- B. Core and jacket are fired together at 2500 degrees F. into a single, solid unit, hard and durable as stone.
- C. Pure copper covers the resistor end for wire lead contact. Contact to the resistance material is at the extreme ends only, providing uniform resistance and Load distribution over *entire* length. End contacts do not short circuit part of resistance as in other types.



Every Radio Service Man
should be a member of the
Institute of Radio Service Men

Centralab

MILWAUKEE, WIS.

British Centralab, Ltd.
Canterbury Rd., Kilburn, London, N. W. 6, England

Centralab
68-70 Rue Amelot, Paris, France

VOLUME CONTROLS

FIXED RESISTORS

Auto-Radio . . .

Bosch 636, 637

The Bosch model 636 is a single-unit auto-radio chassis, power pack, and speaker with a separate remote control. The set is contained in a cylindrical housing. The model 637 differs only in that it uses a separate header type loudspeaker, installed on the header bar, above the windshield.

The complete circuit diagram is shown in Fig. 1, with complete information as to tube functions, socket connections, resistance and condenser ratings, voltages encountered, etc. The voltages given were measured with a 1000-ohm-per-volt voltmeter with the antenna connected to the chassis and the volume control on full. The voltage at the battery measured 6.3 volts.

ALIGNMENT PROCEDURE

1. Set test oscillator to 175 kc.
2. Set condenser gang to approximately 600 kc. This will be at a point where the condenser plates are nearly all in mesh. Turn the volume control on full.
3. Connect output meter across voice coil of speaker. This may be done by connecting one lead of the output meter to the blue lead of the speaker terminal

strip and the other lead to the frame of the chassis. The impedance of the voice coil is 3 ohms.

4. Apply test signal to grid of 78 i-f tube through a 0.5-mfd blocking condenser and adjust trimmer A to maximum output reducing output of test oscillator as required.

5. Apply test signal to grid of 77 first detector-oscillator and adjust trimmers B and C to maximum output (see Fig. 2).

6. Set test oscillator to 1500 kc and rotate condenser gang until the plates are wide open. Place a piece of paper (approximately 0.015" thick) between rotor and stator plates at the bottom of the gang and close the rotor down to this spacing. This is the exact setting of the condenser gang for the receiver oscillator at 1500 kc and should be carefully set as the resultant alignment of the receiver is directly dependent upon it.

7. Adjust trimmer D to maximum output, and then remove the paper gauge.

8. Set test oscillator and condenser gang to 1400 kc.

9. Apply test signal to grid of 77 r-i tube and adjust trimmer E to maxi-

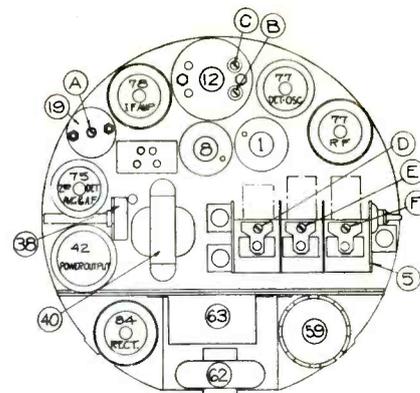


Fig. 2. Chassis view showing trimmer locations.

imum output.

10. Apply test signal to antenna lead through a 0.0002-mfd condenser and adjust trimmer F to maximum output.

11. Check sensitivity at several points.

Zenith 7-M-91S, 7-M-91D

These 7-tube auto-radio receivers are so designed that one or two separate speakers may be used.

The complete circuit diagram is shown in Fig. 1, together with the speaker connections, the functions of the various tubes, their base connections, a parts list, and the voltages encountered throughout the chassis. These voltages were measured with a 1000-ohm-per-


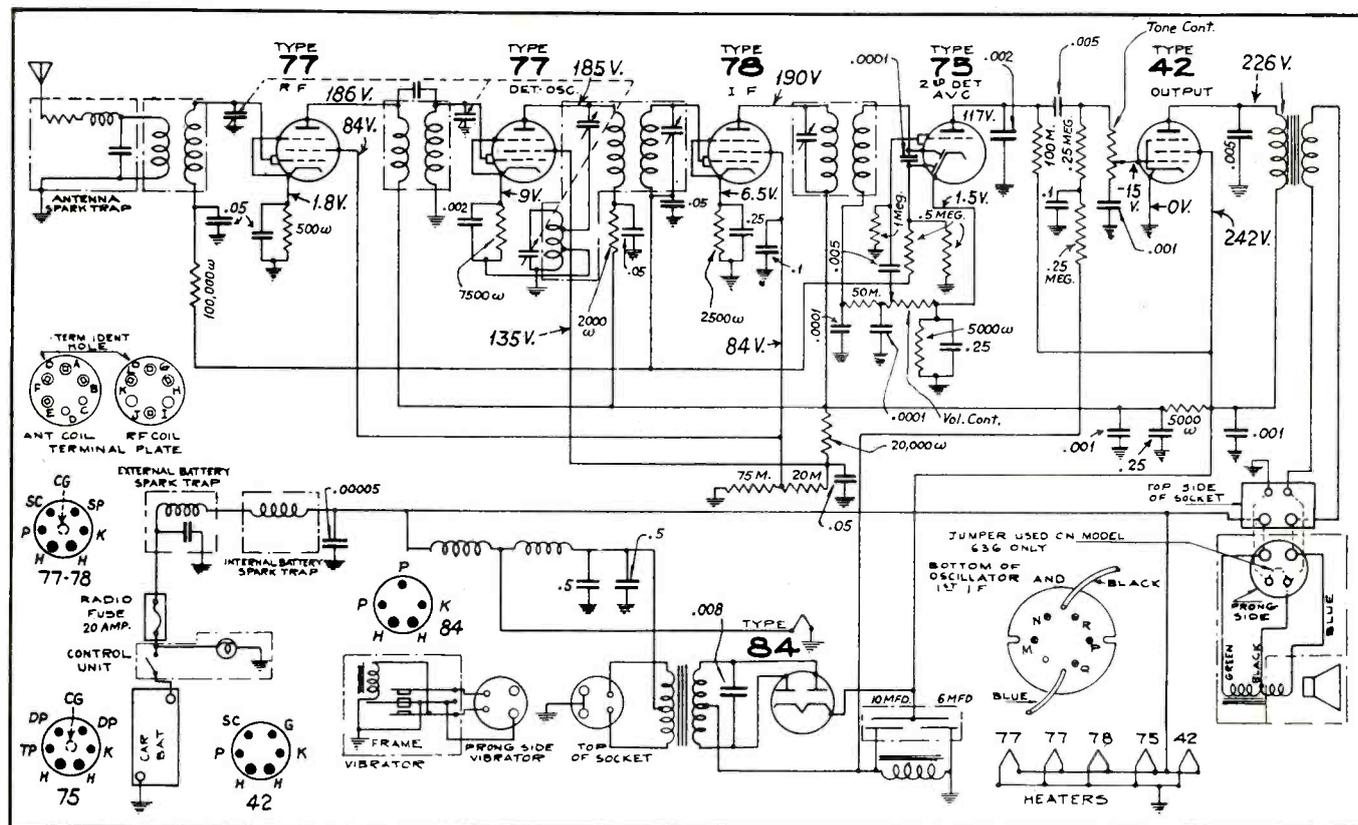



Fig. 1. Complete circuit diagram Bosch 636, 637.

WARD *AUTOMOBILE ANTENNAS*

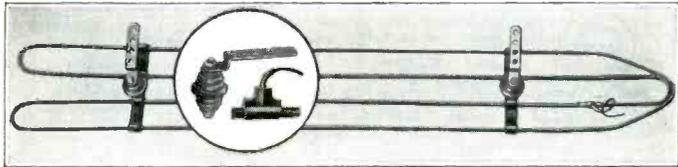
"An Auto Radio Is Only as Good as Its Aerial"
The WARD PRODUCTS Corp.
manufactures the
WORLD'S FINEST AUTO AERIALS



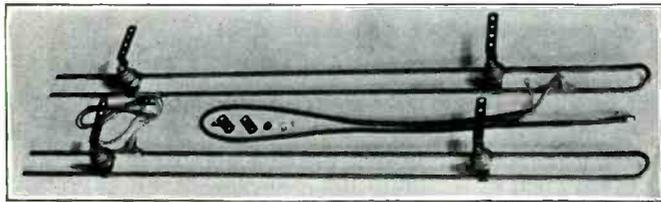
"Rubber Seal"
Model 4RC—Streamline List Price **\$2.95**



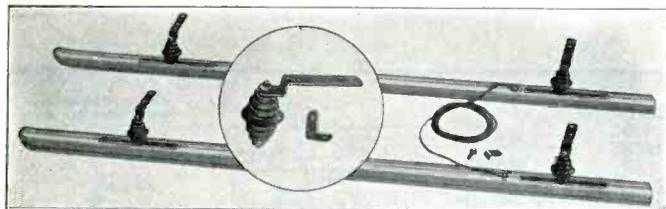"Rubber Seal"
Model HPR—Long-Range Twins List Price **\$4.00**



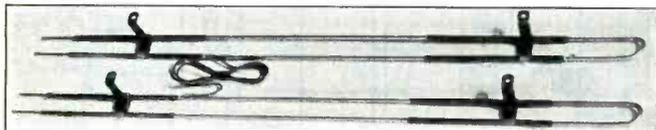Featuring the MAGIC-SKI Bracket
Model 2SK1—Duo Magic-Ski List Price **\$3.50**
Model 1SKI—Mono Magic-Ski List Price **\$2.00**



The Best Antenna Buy on the Market
Model 2MW—Dual Marvelwave List Price **\$2.75**
Model 1MW—Single Marvelwave List Price **\$1.50**



Model 1M—Magic-Super Aerial
 Over 68,000 already in use. Now improved in performance and construction.
 List Price **\$3.50**

ORDER TODAY FROM YOUR JOBBER!

Mail Coupon for More Information—and for free copy—
 "AERIAL NEWS"

To WARD PRODUCTS CORP.
 2129 Superior Ave.
 Cleveland, Ohio

Please send more information about WARD Aerials—and free copy "AERIAL NEWS."

Name

Address

THE SYLVANIA TECHNICAL MANUAL



IS GOING GREAT GUNS!

Every day from every corner of the world . . . more orders are coming in for the New Sylvania Technical Manual. And no wonder! Radio men have discovered that here is a real VALUE! Look at some of the subjects covered in this book:

1. 141 tube types listed with important circuit application information given on each type.
2. Characteristics on all types completely up-to-date. This includes all standard types of metal tubes.
3. Section on circuits has been increased to include 13 typical radio receiver and amplifier circuits which show proper use of the most popular types of tubes now being employed.
4. Curve data on ballast tubes for battery sets.
5. A 50% increase in contents.
6. The convenient pocket size has been retained in spite of the large increase in material.

Don't miss this value! Send 15c for the New Technical Manual NOW!

Hygrade Sylvania Corporation, makers of Sylvania Radio Tubes and Hygrade Lamps. Factories at Emporium, Pa.; Salem, Mass.; and St. Mary's, Pa.

THE SET-TESTED RADIO TUBE

SYLVANIA

HYGRADE SYLVANIA CORPORATION S-66
 Emporium, Pa.
 Please send me the new Sylvania Technical Manual. I enclose 15c in stamps.

NAME

ADDRESS

CITY..... STATE.....

AUTO-RADIO—continued

volt voltmeter with the antenna shorted to the chassis. Actual values may vary 15 per cent from those given. The volume control and the sensitivity switch should be on maximum during all measurements and adjustments.

A. Connect the service oscillator to the control grid of the 6A8 tube and the chassis.

Connect the output meter across the primary of the speaker transformer.

Set the service oscillator to 252.5 kc and adjust the trimmers on the i-f transformers for the greatest output reading. These adjustments should be repeated several times using as weak an input signal as possible so as to obtain greater accuracy.

B. Change the service oscillator lead from the grid of the 6A8 to the antenna connection. A male Delco Remy connector may be used in making a connection to the antenna lead.

Set the service oscillator at 1400 kc. Rotate the gang condenser one and one-fourth turns from the minimum setting. At the proper position eight teeth

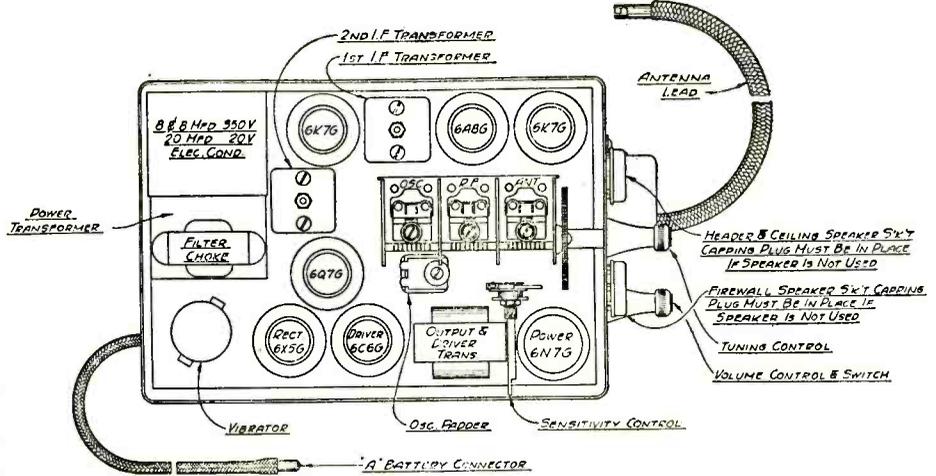


Fig. 2. Chassis view showing trimmer locations.

on the tuning gear will be visible past the gear bracket.

Adjust the oscillator, r-f, and antenna trimmers in that order to the point giving the greatest output.

C. Set the service oscillator at 600 kc and rotate the gang condenser to tune in

this signal. Move the gang condenser to and fro past the signal meanwhile adjusting the oscillator padder condenser until the combination of adjustments giving the greatest reading of the output meter is obtained.

D. Repeat operation B.

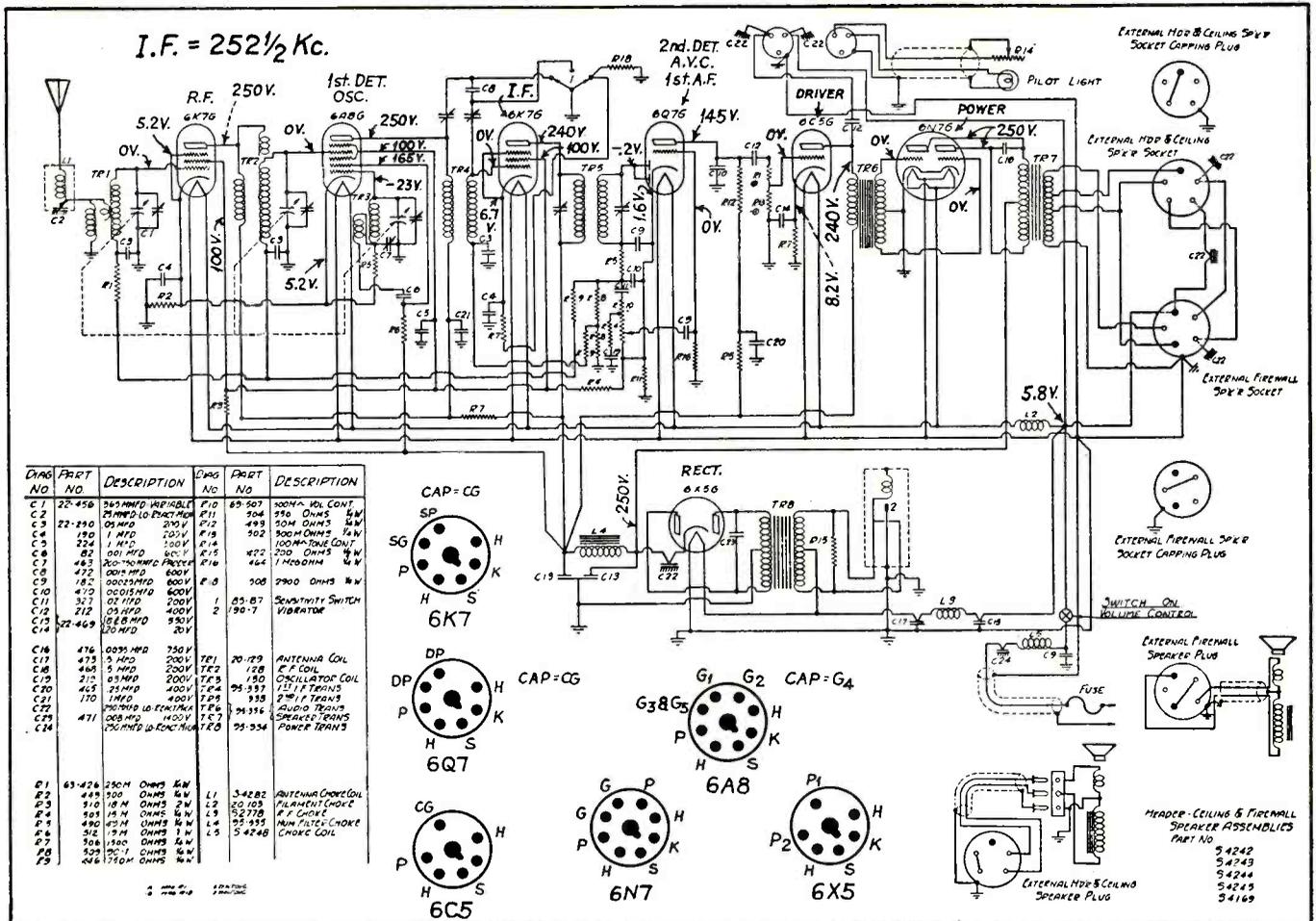


Fig. 1. Complete circuit diagram Zenith 7-M-91S, 7-M-91D.

WESTON

price reductions
save you up to
25%

DON'T DELAY...
ORDER THROUGH
YOUR JOBBER, OR
RETURN COUPON


Increasing demand for these standard,
precision test units makes these big
savings possible:

Model 692 ALL-WAVE OSCILLATOR
Was \$60⁰⁰ net **Now \$45⁰⁰ NET**

Model 669 VACUUM TUBE VOLTMETER
Was \$59⁶³ net **Now \$45⁰⁰ NET**

Model 780 CAPACITY METER
Was \$29²⁵ net **Now \$22⁵⁰ NET**

Model 687 OUTPUT METER
Was \$15⁰⁰ net **Now \$11²⁵ NET**

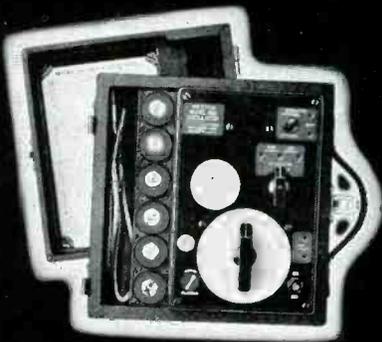

Model 692 - All-Wave Oscillator



Model 669 - Vacuum Tube Voltmeter

Weston Electrical Instrument Corporation
604 Frelinghuysen Avenue, Newark, New Jersey
Send full data on these and other WESTON test instruments.

NAME.....

ADDRESS.....

THE *Eyes* HAVE IT!

Your eyes
and the
Magic Tube

see all, know all . . .

QUICK As A Wink!

A refined and extended Wien Bridge, built into instantly useful form for the laboratory, shop and field.

TYPE CB-1-60

110 volts, 60 cycles

List price \$32.00
less tubes

Dealer's net **\$19.20**

TYPE CB-2-U

110-220 volts, 25-60 cycles

List price \$40.00
less tubes

Dealer's net **\$24.00**

For
Helpful New
Literature,
Mail the
Coupon



CAPACITOR ANALYZER and RESISTANCE-BRIDGE

MEASURES CAPACITY—range .00001 to 70.0 mfd.—MEASURES POWER FACTOR—direct in percentage—MEASURES RESISTANCE—range 50 ohms to 2 megohms—MEASURES INSULATION RESISTANCE—DETECTS ALL DEFECTIVE CONDENSERS—USEFUL CONTINUITY METER—LONG COLOR-CODED SCALES—DIRECT READING—CATHODE RAY TUBE—the magic 6E5 tube gives sensitive visual balance—SELF-CONTAINED COMPACT, PORTABLE.

SOLAR MFG. CORP.

599-601 BROADWAY

NEW YORK, U. S. A.

Manufacturing Affiliates in London, Paris, Berlin, Milan

Name

Position

Street

City




Christened By
AIRCRAFT RADIO
 OF
PITTSBURGH



"THE IRON HORSE"

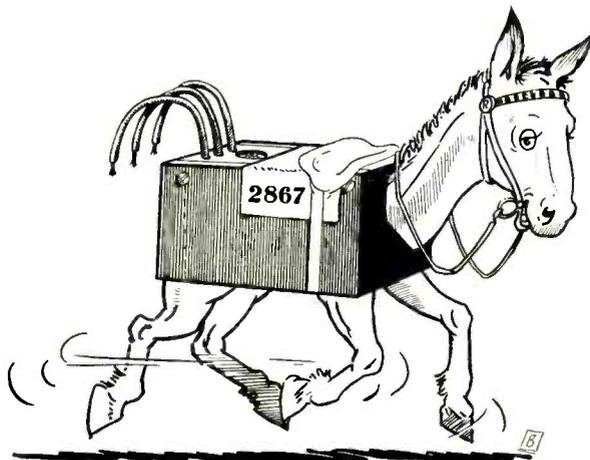18
 Manufacturers
 used this Vibrator
 as Standard
 Equipment.



*A Thoroughbred
 with a Proud History
 of Performance!*

● This vibrator was accepted by the manufacturers after the most rigid tests and now is twice as good as ever before (apologies to Jack Benny). It lasts longer—starts at lower voltages—shows less voltage drop during its life, etc. When you need vibrators insist upon Radiart. If you don't know the Radiart Jobber nearest you write us for this information.

Shaw Ave. at East 133rd St.

THE RADIART CORPORATION

Cleveland, Ohio

NEW Extension Auto Speaker



Model 930

**for Camping,
 Touring, etc.**

- 8" Nokoil Speaker gives electro dynamic performance yet draws no current from battery.
- Cabinet easily taken apart to make proper connections to the universal transformer which matches all tubes.
- Any service man can easily and inexpensively furnish proper length cord and plug-in connection for automatically disconnecting car speaker and connecting extension speaker.


Here is a big Summer Item

Our special low price enables you to make it a great leader. List **\$9.30**

Write for further particulars, complete catalog and name of your nearest distributor.

WRIGHT-DECOSTER, Inc. 2253 University Ave.,
 St. Paul, Minnesota
 Export Dept.: M. Simons & Son Co., New York
 Cable Address: "Simontrico"
 Canadian Office: Wright-DeCoster, Inc., Guelph, Ontario

VACUUM-SEALED

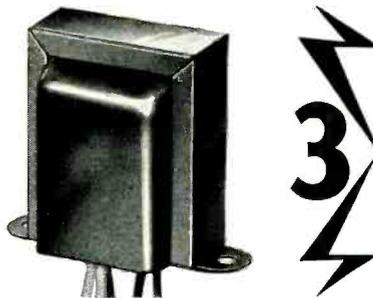

**MORE EXPENSIVE
 TO MANUFACTURE
 but
 LESS FAILURES
 and
 NO INCREASE IN
 PRICE**

HALLDORSON TRANSFORMERS

Halldorson Vacuum Sealed transformers meet the exacting requirements of the "aces" in the Radio Service profession. There is no skimping. . . . No cutting corners on production costs, and each transformer is impregnated under a vacuum seal (a special Halldorson process) rendering them practically impervious to atmospheric conditions. Try one of these transformers—give it "the works" and you too will join that select class of radio servicemen who are getting the maximum in transformer operation at

No increase in Cost



**See Your
 Jobber.
 Send for
 Catalogue.**

The
 Halldorson Company,
 4500 Ravenswood Ave.,
 Chicago, Ill.

Please send me your new
 catalogue.....

Name
 Address
 City..... State.....



AN HOUR A DAY *
SWEEPS THE COB-WEBS AWAY

... away from your technical attic.

SPEND

"AN HOUR A DAY WITH RIDER
ON
RESONANCE AND ALIGNMENT"

... and the second of this series is just
off the press.

"AN HOUR A DAY WITH RIDER
ON
**D. C. VOLTAGE DISTRIBUTION IN
RADIO RECEIVERS**"

will prove to be just as much of an aid, for it tells
you how D.C. voltages are fed to different parts of
a set and how the various resistances are calculated.
The price? Just half a dozen dimes.

... and another way to do some tech-
nical cobweb sweeping is to find out
from

**JOHN F. RIDER'S
THE CATHODE-RAY TUBE
AT WORK**

How the use of the oscillograph will enable you
to get more sets through your shop in a day.
The new edition has 332 pages and more illus-
trations than ever and costs but \$2.50.

... by the way, have you **ALL SIX
RIDER MANUALS?**

BUY THEM FROM YOUR JOBBER

* With RIDER

The Biggest Opportunity in Radio Today

\$\$ SOUND \$\$

FREE System
on
NATIONAL UNION
Deal



Webster-Chicago
Model C-10

3-Stage, 10 Watt Amplifier. Mixes microphone
and phonograph. 2-Button carbon microphone—
stretched duraluminum diaphragm—banquet stand
—25 feet cable. High grade 8" D.C. Dynamic
Speaker. (System handles one or two speakers.)

SOUND EQUIPMENT

**Sensational Expansion This Year . . . Volume Growing by
Leaps and Bounds . . . New Uses Found Every Day.**

National Union believes this field should gravitate to the radio service
dealer. Now is the time to get started. National Union makes it easy for
you to go into this business by furnishing equipment on National Union
deals, requiring minimum outlay of cash. Further, National Union will
help you learn the business; how to sell, how to rent, how to expand,
how to explore the possibilities, just the same way that they did in helping
service dealers build up service work. Don't delay—Get into sound now!

OTHER NATIONAL UNION OFFERS

In **SOUND EQUIPMENT** items available include 17 watt portable
system, 10-watt mobile system, phonograph pick-up and turntable, etc.
In **SERVICE EQUIPMENT** items available include tube testers,
analyzers, oscillographs, signal generators, modulators, meters, etc.
In **SHOP EQUIPMENT** items available include stock cabinets, coats,
display signs, etc. All items available free on attractive National Union
deals.

THE NATIONAL UNION WAY

Through National Union's help, radio service dealers everywhere have
been able to set up better equipped shops to do better work; also to obtain
merchandise helps that produce more customers. National Union has
constantly put the latest advances in scientific equipment as well as modern
selling aids within the reach of the service dealer. The National Union
deal calls for a dealer deposit which is rebated when the specified number
of tubes have been purchased. Over 50,000 completed deals. Every
service dealer should investigate.

National Union Radio Tubes Are Handled and Recommended By
More Service Dealers Than Any Other Make.

Act Now! Send Coupon! Let National Union Help You!

See Your National Union Jobber. Write for Complete Information.

NATIONAL UNION **THE ROAD TO BETTER BUSINESS**

1. Full guarantee on highest quality radio tubes.	4. N. U. jobber stocks are complete... No hunting for odd types.
2. Cut price business not solicited.	5. Timely business building aids.
3. Price Protection.	

NATIONAL UNION RADIO CORPORATION S636

570 Lexington Ave., New York City

Please send me more information on

..... Free offer for Webster-Chicago Sound System C-10.

..... Free offer for

Dealer Name

Address

City..... State.....

RECEIVER CASE HISTORIES

Aetna Midgets

When marked B. R. C. Chicago: These receivers are made by Belmont Radio Corp. and can be found in manuals under that name.

H. J. Hicks

A.K. 55

Poor high-frequency response: The high-frequency response of this model can be improved by removing the "quality condenser" connected across the plates of the 45's. The condenser is located in the audio transformer assembly. Remove the transformer from the chassis, take off the cover, and heat the assembly. The condenser will be found near the top of the can.

Allan Epstein

Apex 99

Low volume: When all voltages check low test the 4- and 8-mfd filter condensers for open or lowered capacity. A drop in plate voltage as great as 40 volts has been found with one of these condensers open.

Under such conditions very little hum is present which would otherwise throw suspicion upon one of these condensers at once.

Howard J. Surbey

Bosch 360

Oscillation on weaker stations, sometimes intermittent: This is usually caused by poorly grounded tube shields. The aluminum tube shield bases are attached to the chassis with rivets and as the bases tend to loosen and corrode in time so that the shields make a poor ground. The remedy is to bond the tube shield bases to the chassis with aluminum solder.

On the first model 360's the same rivets holding the tube shield bases on the top side of the chassis also hold soldering ground lugs on the under side. Naturally, these also tend to loosen and make a poor ground so it is also necessary to bond these ground lugs to the chassis with short pieces of wire.

Dead: Commonly caused by either filter condensers, C-39 and C-40, shorting or a section of R-3 resistor opening. The resistance of the sections of R-3 resistor, the values of which are not given on all diagrams, is in order from high side to ground as follows: 1,000, 12,000, 8,000, and 6,000 ohms.

Paul D. Shields

Bremmer Tully 82

Low volume: Low volume in this receiver is frequently caused by a break

in one of the two parallel wires of the ballast tube. This can be determined by inspection of the tube. A shorted r-f cathode by-pass can also cause low volume; replace with 0.5-mfd.

Harvey H. Schock

Brunswick 11

Poor high-frequency response: This receiver is exceptionally well designed, except for its high-frequency cut-off, which is due to too much by-passing after the second detector plate. Remove the small 0.001-mfd condenser connected to the second detector plate. Insert in its place a condenser of 0.00025-mfd.

W. Manola

Coronado 7700

Distortion: Earlier models experienced speaker troubles which were later eliminated by using speakers with bakelite voice coils. The input transformer also gave trouble on this model.

J. E. Steoger

Crosley 167

Inoperative: One 58 heater too bright, the other 58 heater does not light at all. Remove the lead from the dial lamp socket which runs through the chassis; insulate with spaghetti. The original lead often grounds to the chassis.

E. M. Prentke

Crosley 175

Inoperative: If the set drops out as the dial is tuned to the lower frequencies, replace the 7000-ohm cathode resistor in the oscillator circuit with one of 5000-ohm; realign.

Harvey H. Schock

Emerson A-C 7

Oscillation and weak reception: The 12,500-ohm, 2-watt resistor (G.R. 30 in the schematic) often drops in value to as low as 1600 ohms; replace with a 10-watt wire-wound unit. The screen by-pass condenser may also develop leakage. The condensers in this receiver should have a terminal resistance better than 100 megohms; replace any under this value.

Al. Beers

Grebe HS 4

Intermittent, noisy reception, oscillation: Replace both 8500-ohm resistors in screen feed circuit, using wire-wound ten watt units. Remove entire 6 section metal cased by-pass condenser. Replace the r-f and i-f cathode by-pass condensers with 0.1-mfd units; the second

detector cathode by-pass with 0.5-mfd; and the tone control condenser with a 0.02-mfd. The screen by-pass condensers are also 0.1 mfd.

E. M. Prentke

High-Gain Amplifiers

Hum: In many p-a amplifiers having a gain of over 100 db that are built on the same chassis with the power supply have a residual hum level that is more than desirable and is difficult to locate and persists in spite of the utmost effort spent to eliminate it.

Two simple remedies may be applied, and will always result in a marked reduction. The first is to ground every "ground" connection to a heavy copper bus-bar. This should be soldered securely to the chassis at several points. The second is the by-passing of the primary of the power transformer to the chassis by means of a 0.1-mfd or 0.25-mfd condenser. It is important to by-pass only one side of the line. By-passing both sides may result in more hum.

E. M. Prentke

Kolster K70, 72, 75, etc.

High pitched whistle: Some of these sets whistle because of interaction between 47 tubes and p.p. input transformer. This can be eliminated by soldering leads bonding the sections of the transformer case to the chassis in several places.

Allan Epstein

Midwest 16 Tube

Distortion at resonance: Realign the avc i-f transformer; if this stage is not peaked the avc voltage will be insufficient.

Poor quality, especially on phonograph: Replace the cathode by-pass condensers on all the audio tubes with 5-mfd, 25-volt units of some well-known manufacturer.

Allan Epstein

Philco 5 Auto Set

Inoperative: No plate or screen voltage, primary circuit draws 10 to 15 amperes, filter condensers and buffer check O.K. The cause of this condition is breakdown of power transformer windings. A new transformer is indicated.

E. M. Prentke

RCA R-75

Low volume: In many cases this receiver can be pepped up by changing the three 0.1-mfd by-pass condensers in the avc circuit.

Allan Epstein

Rx

LENZ ELECTRIC MFG. CO.
1751 North Western Avenue
Chicago, Illinois
ESTABLISHED 1904

PRESCRIPTION

*On Auto Radio Service -
Use Lenz Quality Wire and Cables to insure a permanent repair job + complete customer satisfaction*



TRY SPRAGUES...
and note the difference



WE INVITE YOU!

... If you have had condenser trouble, either with Spragues or any other make, all we ask is that you try the Sprague 1936 line. Practically short-proof. Extra safety factor. No need to check surges. One standard voltage for all jobs, the highest you'll ever need. Designed throughout to meet modern service requirements - Improved in practically EVERY characteristic fully guaranteed. Now made in a complete 450 Volt Line as well as famous Sprague "600's." Try them - test them. Judge for yourself!

Write for our new free catalog

SPRAGUE PRODUCTS CO.
North Adams, Mass

SPRAGUE 600 LINE CONDENSERS
AMERICA'S FINEST LINE OF QUALITY UNITS

**17 WATT . . .
PORTABLE . . .
SPARKLING
BRILLIANCE**



Incorporating every known improvement . . . for best and enduring performance, and for simplified, damage-proof operation.

SYSTEM INCLUDES:

- Dual Diaphragm Crystal Microphone
- 4 Stage Amplifier Using 6 Tubes (Furnished)
- Dual Input Mixing System
- One or Two 12" D.C. Dynamic Speakers

Model PA-417A



WEBSTER-CHICAGO offers you today's finest in P.A. systems at thoroughly competitive prices. WEBSTER-CHICAGO has earned its reputation for building outstanding trouble-proof sound equipment—the kind every service dealer likes to sell and recommend.

See your Jobber. See for yourself that WEBSTER-CHICAGO merchandise does not cost more. Write for catalogue.

STRICT DEALER POLICY

FULLY LICENSED

TIME PAYMENT PLAN

FREE — "A Short Course in Sound Engineering"

Webster-Chicago is now preparing a limited edition on the above. Every sound man; jobber, dealer, service man will want one of these up-to-date pamphlets covering engineering and sales details. If you wish one, send in your name. Printing will be limited to those desiring this information.

THE WEBSTER CO.
3825 W. LAKE STREET, CHICAGO, ILL.

WEBSTER-CHICAGO manufacture a complete line of synchronized public address systems, sound equipment, amplifiers and accessories of all kinds.

THE WEBSTER COMPANY, Section JN-5, 3825 W. Lake St., Chicago, Ill.
Without obligation please send me

..... More information on Model PA-417A. Send complete catalogue.

Name

Address

City State

RECEIVER CASE HISTORIES—continued

Wells-Gardner 6F

Excessive hum: Excessive hum may be encountered in the early models of this receiver. These models can be identified by the letter A stamped on the under side of the chassis. Should hum exist follow the steps outlined below:

Check the 6B7 and 6F7 tubes. Several new tubes should be tried and the effect noted.

A cardboard shim about 3/32 in. thick should be placed under the choke (L4, see service manual).

The 4-mfd, 150-volt electrolytic (C35) should be replaced by a 12-mfd, 300-volt condenser.

If the hum level is still objectionable after the above changes have been made, the following procedure should be followed:

1. Remove the heater connections from the 6B7 and 6F7 sockets, leaving the ground connection on the 6F7 socket. Remove the ground from the terminal strip to the A power cable plug terminal, and from this terminal connect a wire (white) to a ground lug near the 6K7 second i-f as shown in the accompanying diagram.



Remove the wire connecting the heater of the 76 avc diode tube to the insulated terminal strip. The other heater connection of this tube should be removed from the terminal of the A power cable plug and connected, as shown, to the lug on the insulated terminal strip, to which one terminal of candohm resistor R20 is also connected. This last heater connection and the heater wire for the 6K7 second i-f tube and the ground wire (white) from the A power cable plug, referred to above, should be twisted together and kept away from the 6B7 and 6F7 tube sockets as shown.

Connect the other terminal of candohm resistor R20 to the opposite terminal of the A power cable plug with reference to its former position, as shown in the accompanying illustration.

2. Connect the 6F7 and 6B7 heaters in series between ground and the terminal of A power cable plug to which the candohm resistor R20 was formerly connected.



3. A new resistance of 130 ohms, 2.5 watts (candohm R39) is placed near the volume control in the position shown in the illustration. As shown in the diagrams the ungrounded lug on R39 is connected to the heater terminal of the 6B7 which also connects to the A power cable plug.

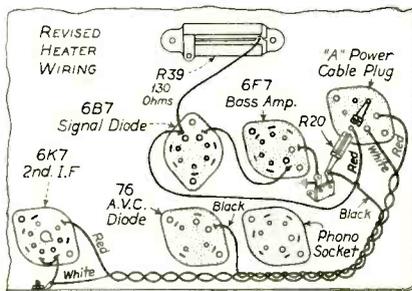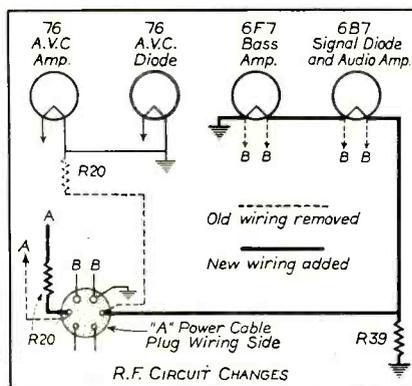4. The pilot light lead, which formerly connected to the 6B7 heater, is now connected to the 76 oscillator tube



heater. This is best accomplished by drilling a 1/4 inch hole in the chassis near the oscillator tube socket and bringing the lead down from the left-hand side of the dial assembly.

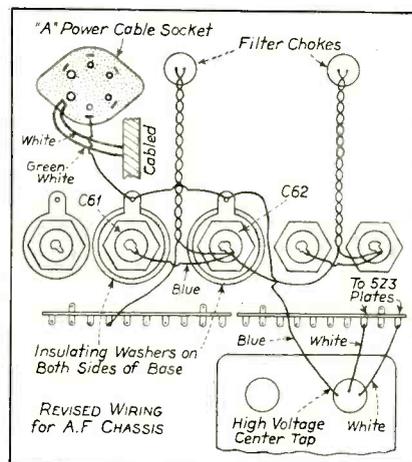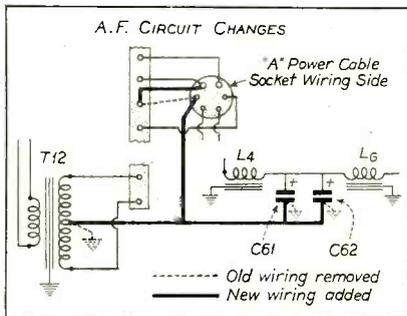5. Remove the filter condensers (C61 and C62) from the chassis. Enlarge the holes to 29/32 in diameter. Place an offset washer on each electrolytic and



mount on the chassis so that the offset part of the washer fits into the hole. Put on a plain fibre washer, contact lug, lockwasher and nut, respectively.

6. Then disconnect the high voltage center tap of B power transformer T12 at the ground lug and connect it to the negative contact lug on one of the electrolytics. Next connect the negative contact lugs together, as is shown in the accompanying illustration.

7. Replace the choke wires on the positive side of the electrolytics, C61 and C62, and also the blue wire connecting the two positive terminals together.

8. At the A power socket, disconnect the green and white tracer wire at the cathode terminal and connect to the cathode heater terminal. Connect the cathode terminal to the contact lugs on the electrolytics, as illustrated.

Westinghouse W 24

Noisy reception: If the receiver develops noise at the slightest vibration suspect the tube sockets. These may be tightened in the usual manner with a long-nose pliers.

Harvey H. Schock

Westinghouse WR 5, WR 6

Noisy reception: Noisy reception in this model is often caused by a poor connection of the electrostatic shield in the power transformer to the chassis. The lead to this shield (which usually consists of an extra layer of winding between the primary and the secondaries) should be scraped free from the tar surrounding the transformer and grounded to the frame and the receiver chassis.

Harvey H. Schock

Zenith A-B-C-D

Poor operation: Check the plate, screen, and bleeder resistances in these models. Generally some of the resistors will have increased to a much higher resistance than their correct value. The bias resistor of 900 ohms for the 45's should be replaced with a 10-watt resistance.

Paul D. Shields

Zenith 91, 92

Inoperative: If this receiver is inoperative until the 24A tube used as the avc rectifier is removed from its socket, check the avc voltage divider connected between the cathode and screen. This section if open will stop reception. Replace with a one watt 15000-ohm resistor.

RCA Radio Service Tip File



UNIT-MATCHED P.A. EQUIPMENT *The Bunk?*

Sounded like a selling idea when I first heard it . . . but after checking with other service men who do lots of Public Address work

I'm not so sure NOW

. . . in fact I *know* it isn't the bunk. If other manufacturers have the same thing, it may be just "follow the leader," but boys, if you're not buying Portable P. A. Units, amplifiers, microphones and speakers from OPERADIO then you don't know what smooth, swell working, profitable P. A. installations are.

Give that Operadio outfit a try like I did. You won't regret sending for their Catalog No. 10 . . . be sure and address Dept. S.

Ask about our convenient time payment plan.



OPERADIO

MANUFACTURING COMPANY
Unit-Matched P. A. Equipment at its Finest
ST. CHARLES, ILLINOIS

TOBE SURGPROOF
TUBULAR CONDENSERS



THIS IS
NOT AN AD!

RATHER it is a simple truth gleaned from the notes of many servicemen—to the effect that ordinary condensers cannot be used successfully in bypassing high radio-frequency circuits in short and all-wave receivers. A NON-INDUCTIVE capacitor of the *highest quality*—preferably with short-path soldered leads—must be employed if satisfactory results are to be obtained. The TOBE SURGPROOF tubular is such a condenser.



TOBE DEUTSCHMANN CORP.
CANTON, MASS.



General

manufactures
the most complete line of
ALL-ALUMINUM TRUMPETS..
DEFLECTOR BAFFLES..HORN
FITTINGS . . and the NEWLY
DEVELOPED CONE SPEAKER
TRUMPET



#22—3½' trumpet,
22" bell.
List Price... **\$26.25**



#32—6' trumpet,
32" bell.
List Price... **\$46.25**



#20—3' cone trumpet, for 5-6" cone unit, 21" bell.
List Price... **\$20.00**



#30—3½' cone trumpet, for 5-6" cone unit, 32" bell.
List price..... **\$25.00**

#8 JR light gauge baffle horn, speaker opening 8".
List Price... **\$7.50**

#8 heavy gauge baffle horn, speaker opening 8".
List Price..... **\$9.50**



#10 JR light gauge baffle horn, speaker opening 10".
List Price..... **\$9.50**

#10 heavy gauge baffle horn, speaker opening 10".
List Price..... **\$11.25**

#300—Heavy Duty baffle stand with tilting bracket for regular parabolic deflector baffle.
List Price..... **\$20.00**
(Stand only)



#23-T triple connector.
List Price.. **\$13.75**



#22-Y dual connector.
List Price **\$11.25**



A complete new catalog is yours for the asking. Write for it.

GENERAL ILLUMINATING CORP.
16 CALENDER ST. PROVIDENCE, R. I.

ASSOCIATION NEWS . . .

INSTITUTE OF RADIO SERVICE MEN REPORTS

The IRSM Qualification Plan

We need not reiterate concerning the unsavory conditions that existed, and to a large extent still exist, in the radio service field in the larger cities. Unscrupulous and incompetent Service Men without proper equipment are recognized, and reap rewards in many cases larger than those obtained by honest, competent, well-equipped technicians. The harm created through the continued activity of such Service Men to both the victimized public and the service profession in general cannot be estimated. Numerous guilds, trade unions and associations (among them the IRSM) were formed to fight such vicious practices. These organizations, while successful in so far as individual Service Men are concerned, have affected the conditions only slightly in some of the larger cities. Unscrupulous service agencies still reap large profits and incompetent Service Men still drag along.

With a view to overcoming these conditions, the IRSM is attempting to establish a qualification project. This project has as its object the "development of a means to ascertain the technical ability of persons engaged in radio servicing and to establish and maintain ethical business standards in the radio service industry." To advance this end the IRSM has already created a "profitless" corporation called the National Radio Service Qualification Project, Inc. This corporation in turn is to be the parent of two additional "profitless" corporations which will be incorporated in the near future.

The first of these, The National Board of Radio Standards, Inc., is to have representation from the manufacturers, the broadcasters, the service employers, the service employees, and the public. Its purpose is to "prescribe an examination to determine the technical qualifications of persons engaged in radio servicing; to employ examiners . . . a staff to grade papers; and certify qualifications. . . ."

The other corporation, Radio Service Registry, Inc., is to be composed of the group passed upon in accordance with the qualifications of the first corporation. Continued membership in this group is dependent upon the Service Man's conduct as a member.

Examinations will be conducted in cities that the Service Men can reach with a minimum of expense. The IRSM will prepare a question-and-answer book which prospective applicants may borrow in order to properly prepare for the examination.

Persons franchised under the Qualification Project shall be required to show that they are keeping abreast of development in the radio arts in order to hold their franchise. The Board of Directors in organizing the program has stipulated that there shall be a re-examination every two years; and that such re-examination shall be based on developments during a two-year period ending six months prior to the date of the re-examination.

The Board of Directors has established an initial fee of \$10.00, payable with application. The aforementioned fee shall

cover the cost of the examination, and, in the event that the applicant fulfills the requirements, the issuance of credentials. What remains will be used for the purpose of promoting the project to the radio public and protecting the rights of those who are entitled to the benefits of the project. The aforementioned fee of \$10.00 shall also cover the registration for one year thereafter.

For a limited time, a reduction in the initial fee shall be effective in accordance with the approval given by the Board of Directors. (The exact amount will be announced later.)

The annual fee after the first year shall be \$5.00.

In the event that an applicant fails to pass the examination prescribed by the National Board of Radio Service Standards, he shall be permitted to take the examination again on the next succeeding examination date, or at any time when an examination is conducted in a city conveniently located to him. The applicant shall be required to pay an additional fee of \$1.00 for each such additional examination necessary for him to qualify.

Cleveland Chapter IRSM

All members of the Cleveland Chapter having survived the recent trade show held in the "Windy City," have settled down to business again.

Mr. Quinn, chairman of our technical papers committee has worked out a V.T.V.M. Construction data and diagrams are available.

Along with our service forum we conduct a publications review; several members are assigned to cover the highlights of news and new developments as they are introduced.

On May 25 the executive officers of the Cleveland Chapter drove down to Akron and set up an Akron Chapter of IRSM. Twenty-four members constitute the chapter group and from all indications they are going to town in a big way.

Plans are well under way for a co-operative Service Men's picnic, to be held the latter part of August, including a parade of sound trucks and service cars to the picnic grounds.

At one meeting each month the Cleveland chapter of the IRSM gives over a part of the time to a review of radio publications of interest to Service Men. Several are appointed to prepare and deliver the reviews, changing the reviewers from time to time. Chark Quinn, an officer of the section, started the idea and it has proved to be of value in stimulating the men to later look up and read valuable articles which might have been overlooked, thus increasing their knowledge and efficiency. This idea is submitted with the hope that other service groups will try it out and find it helpful and interesting.

L. Vanquinten.

Brooklyn, N. Y., Chapter

The Brooklyn Chapter has really gotten under way, and is growing by leaps and bounds. They have acquired a meeting

place of their own in the Oddfellow's Hall in Brooklyn, and meet on the third Monday of every month.

Over 150 members and guests put up their tools for the evening and turned out for the first meeting in the new quarters. Atwater Kent and its distributor for the New York area provided the speakers of the evening. Mr. Kelley, of the Factory Service Department, who was introduced by Mr. C. Craig of the Sales Force, described the circuits of the new Atwater Kent receivers. Refreshments in the form of beer and pretzels were served after the meeting and a good time was had by all.

New York Chapter

The New York Chapter has been having some very fine meetings, the latest of which was given by Stromberg-Carlson, at which time Mr. O. Wells, who is Service Manager for their New York distributor, gave the boys some service hints on repairing Stromberg-Carlsons. Mr. P. J. Collison of the same firm gave a short talk on the methods of selling and installing p-a systems with special reference to quality and right type of equipment for the job. A Service Forum was held before the meeting, Charles Seidman presiding. Joseph Flaum, Secretary.

NRI ALUMNI NEWS

New York Metropolitan Area Chapter

The first issue of our little magazine, "The Metropolitan Area Chapter Tattler," is just off the press and is already asserting itself as a worthy contender for Chapter bulletin honors. The Editor, Mr. R. Pettit, assures the boys he is going to do everything within his power to make it interesting, informative, and give the rest of the Chapter bulletins a run for their money.

Social meetings will be the first Thursday of every month—where we will have a get-together and have fun. For more details on the social meetings attend the business meetings. The business meetings will be held on the third Thursday of each month. The address is 12 St. Marks Place, New York City (near 3rd Avenue).

You can get full information about joining our ranks by writing Mr. L. J. Kunert, 66-11 74th St., Middle Village, L. I., N. Y.

Philadelphia Camden Chapter

A great deal of the credit goes to Mr. J. P. Hornbrook and Mr. William Trimble for the continued success of our Radio bulletin, *The Philcam Key*. These live wires are getting the news and material we need to put our bulletin over in a big way.

Four meetings are held every month—one business meeting and three service meetings. Every member is urged to attend as many meetings as possible. We cannot fail to note that the fellows we see here the most are the same boys who make the most money. Apparently these fellows are the ones who realize that it takes plenty of good hard study and an ever increasing desire to know more to go to the top.

(Continued on page 282)



So MUCH for So LITTLE!

Years of antenna specialization and the largest plant devoted exclusively to antenna kits makes this new quick-selling system possible. Just compare these features—and the price.

- ★ All-wave, self-selecting, noise-reducing system; factory assembled, wired, soldered.
- ★ Armored (steel-strand) copper antenna wire for maximum strength. Non-corroding wire and joints.
- ★ Special twisted-pair downlead cable. Automatic-switching set coupler.
- ★ Complete. Attractively packaged. Ready to string up. Only \$4.50 list! A big value for small price.


Write for technical and sales data on this new kit. Also on Type 200 DeLuxe Kit for those extra fussy customers of yours who insist on superlative results.

• **TECHNICAL APPLIANCE CORP.**
Pioneers in Noiseless Antenna Systems
17 EAST 16th STREET :: NEW YORK CITY



Dramatize Your Resistor Stock!

Insulated
CONTINENTAL
Carbon Resistors

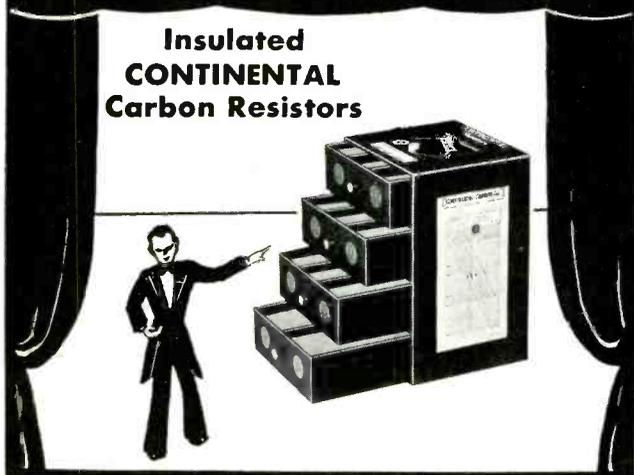

This attractive cabinet FREE with the purchase of 70 CONTINENTAL Carbon insulated resistors consisting of two each of 35 selected standard values. The cabinet is 7' x 10' x 6' deep, with ample room for 500 resistors in the four drawers. Two handy, self-calculating resistor charts are provided for convenient reference. Ask your CONTINENTAL Carbon distributor for full details.

Send for Resistor Engineering Bulletin 104, free!

CONTINENTAL CARBON Inc.



13912 Lorain Ave., Cleveland, Ohio Toronto, Ontario



Famous makers of P. A. equipment offer another **WINNER**

BELfone

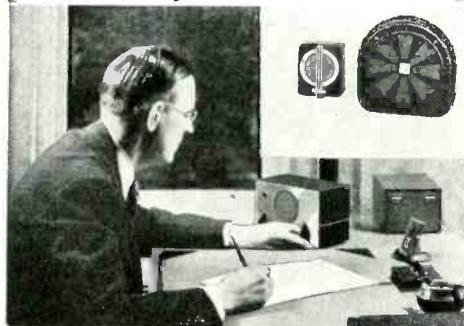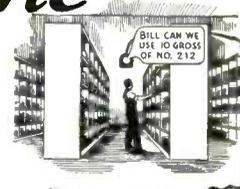A complete Intra-Department Communicating System for **\$39.50**



Mr. Radio Man! Here's a red hot seller. Just what restaurants, offices, factories and stores want. Permits two way conversation. A demonstration closes the order—puts profit in your pocket.

Interesting proposition for jobbers.

WRITE TODAY FOR DETAILS

BELL Sound Systems, Inc.
61-62 East Goodale St.
Columbus, Ohio



HAIL... THE NEW RANGER EXAMINER

- ★ Accurate to 2%
- ★ Molded Case
- ★ Selector Switch
- ★ With Test Leads and Two Alligator Clips

Pocket D.C. VOLT-OHM-MILLIAM-METER—Model 735



DEALER PRICE... **\$10.80**

A Sensational Development at a Sensational Price

Here is the handy, general purpose instrument you have always wanted... Precision built, D'Arsonval movement... Accurate... At the unbelievable price of \$10.80.

Slips in the coat pocket, provides all the D.C. measurements required by the radio serviceman. The selector switch makes operation as simple as the larger multimeters.

Reads D.C. 15-150-750 volts at 1000 ohms per volt; 1.5-15-150 Milliamperes; 5-1000 low ohms; 0-100,000 high ohms at 1.5 volts.

MAIL COUPON NOW



READRITE METER WORKS
617 College St., Bluffton, Ohio
Please send me more information on the Ranger-Examiner.....
Name
Address
City State

HIGHLIGHTS . . .

THE ELECTRAD CONTACT

Electrad, Inc., 175 Varick St., New York City, publishes a magazine called "Contact." Service Men may obtain issues of this publication by returning two complete Electrad volume control cartons to the manufacturer.

PURCHASE PREMIUM PLAN

The Tilton Electric Corp., 15 E. 26th St., New York City, makers of the Ex-Stat line of volume controls and resistors, offer premiums to the Service Men who continue to use their products. Complete details of the plan as well as premium catalogues may be obtained at the above address.

WESTON REDUCES INSTRUMENT COSTS

Prices as much as 25 per cent less than previous levels on standard test equipment are made possible by a new policy in merchandising recently applied by the Weston Electrical Instrument Corp., Newark, N. J. No departure from previous standards will be made.

ISOLANTITE GRID INSULATION

The Raytheon Engineering Department reports the perfection of a method for spinning Isolantite grid cap insulation wafers into metal tubes designed for conversion and r-f amplification. The use of Isolantite in place of bakelite reduces r-f losses in the grid circuit of tubes like the 6A8, 6L7, and 6K7 to values equivalent to the lowest glass bulb losses.

It is recalled that Raytheon, working in cooperation with a phenolic insulation manufacturer, developed a phenolic material with losses midway between the original phenolic wafer and Isolantite. This improvement, announced in November of last year, is retained in the metal tubes used chiefly for audio work.

MILLER CATALOG

The J. W. Miller Co., 5917 S. Main St., Los Angeles, Cal., publish a catalog (No. 36) describing their line of coils, coil shields, r-f chokes, etc. Copies may be obtained directly from the Miller Co.

GHIRARDI ADVISES TELEVISION STUDY

A. Ghirardi, author of "Modern Radio Servicing," believes that the Service Man who has thoroughly mastered the principles of both electricity and radio and brought himself up to date in all his methods will have an overwhelming advantage when television is finally introduced to the public.

G. E. RADIO TOUR


Following the initial presentation of the G. E. Focused Tone Radio Line to the eastern G. E. distributors at Bridgeport, Conn., June 4, the G. E. Radio Division is conducting a nation-wide series of meetings to present the sets to dealers and their salesmen in each sales district.

CORNELL-DUBILIER APPOINTMENTS

The Cornell-Dubilier Corp., 4377 Bronx Blvd., New York City, announces the following appointments: Mr. R. W. Mitscher as sales representative for the state of New York with offices at 487 Ellicott Square Bldg., Buffalo; Mr. Stanley Walters, graduate engineer from M.I.T., has been appointed to the Engineering Department.

UTC BULLETIN

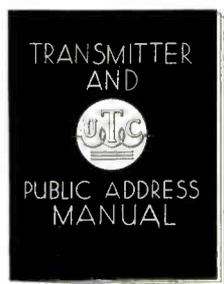The research department of the United Transformer Corp., 72 Spring St., New York City, has completed a study of transmitter and p-a circuits and applica-



tions. This information has been compiled into an attractive 44-page illustrated bulletin. A limited number of copies will be available at local distributors for the nominal sum of 25c.

FERRANTI IN LARGER QUARTERS

Ferranti Electric, Inc., manufacturers of transformers, instruments, surge absorbers, etc., have just announced the removal of their executive and sales offices to larger quarters at 30 Rockefeller Plaza, New York City. Mr. W. R. Spittal, manager, stated that this move was necessary due to increased sales of Ferranti products.

OHIOHM INFORMATION SHEETS

Two information sheets giving interesting test data, dimensions and hookups for the Ohiohm series of auto-radio interference suppressors by the Ohio Carbon Co., 12508 Berea Rd., Lakewood, Ohio, are now available upon request.

VOLUME CONTROL CHECK TEST

To acquaint Service Men with recent refinements, Clarostat Mfg. Co., 285 N. 6th St., Brooklyn, N. Y., is asking interested parties to check the latest Clarostat units and report their findings. Standard Clarostat volume controls are being sent free to authorized Service Men requesting same together with a check test form to be filled out and returned to the manufacturer.

Any Service Man interested in making the check test may write to Clarostat for a volume control of either the wire-wound or the composition-element type, any resistance value and any standard taper.

GENERAL ILLUMINATING CATALOG

The General Illuminating Corp., 16 Calender St., Providence, R. I., have released a loose-leaf catalogue describing the complete line of General Exponential Equipment.

This interesting book illustrates all-aluminum trumpets, horn adapters, deflector baffles, stands, and cone speaker trumpets.

A copy will be mailed upon application.

ARCTURUS G ADDITIONS

Since introducing G tubes a year ago last April, the Arcturus Radio Tube Co., Newark, N. J., experiencing a demand for this line, has had to round out that series.

LENZ WIRE CATALOG

The Lenz Electric Mfg. Co., 1751 N. Western Ave., Chicago, publish a catalogue obtainable upon request. A novel feature of this catalogue is a chart showing the various uses to which each type of Lenz wire can be put in wiring a radio receiver.

EASTERN MIKE-STAND CATALOG

Eastern Mike-Stand Co., 56 Christopher Ave., Brooklyn, N. Y., manufacturers of "Eastern" microphone stands, announce a new catalogue describing their complete line of microphone stands.

Among the new items are listed a short circuiting switch-swivel unit and a shock absorber coupling.

A copy of this catalogue may be had by writing to the above address.

ASSOCIATIONS—Continued

Chicago Chapter

Mr. P. W. Kidd, of the Supreme Radio Service Company, will continue his series of informative talks on the popular subject of radio servicing. We can't give you his subjects, but we can promise you that they will be something you cannot afford to miss. Come on down and learn how another expert does it!

Baltimore Chapter

The *Baltimore Bulletin* continues to be a highly informative and interesting publication. Under the editorship of Mr. Wilmer B. Giese, whose prolific pen has captured the attention of large radio manufacturers, a great deal of the credit goes to him. The last issue came out with a bright green cover.

Detroit Chapter


The regular round table discussion of radio receiver troubles is being continued with great success. It is surprising how much a fellow can learn by attending these meetings and taking part in these discussions. So any of you members who have some technical problem, or a particular receiver giving you difficulty, let us know what it is. We will all take a hand in trying to "iron" it out.

P. J. Murray—NRI News.

HETRO AUTO RADIO

The 20 feature
NOMAD

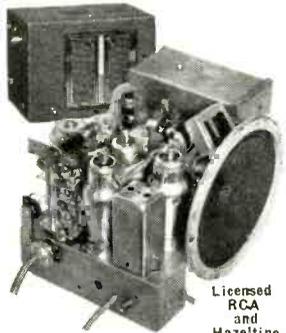- One minute servicing.
- Remove Vibrator tubes chassis without dismounting.
- No suppressors.
- One bolt installation.
- Modern, fits all cars.
- **RIGHT PRICE, BIG PROFITS.**



Licensed
RCA
and
Hazeltine

Write Today for Description and Prices.

HETRO ELECTRICAL INDUSTRIES, Inc.

4611 Ravenswood Ave. Chicago, Ill., U. S. A.

Here Next Month:

Tru-Fidelity

by

THORDARSON

Most Sensational
Audio Development
in Radio History

BRUSH *Spherical* MICROPHONE



• A specially designed, general purpose microphone for remote pickup, "P. A." and commercial interstation transmission work. Low in price... but built to Brush's traditionally high mechanical and electrical standards. Wide frequency response. Non-directional. No diaphragms. No distortion from close speaking. Trouble-free operation. No burton current and no input transformer to cause hum. Beautifully finished in dull chromium. Size only 2½ inches in diameter. Weight 5 oz. Output level minus 66 D. B. Locking type plug and socket connector for either suspension or stand mounting furnished at no extra cost. Full details, Data Sheet No. 13. Free. Send for one.

BRUSH *Lapel* MICROPHONE



• For after dinner and convention speakers, lecturers, etc. Gives great mobility—the smallest, lightest microphone on the market. Size 1½ x 1¼ x ¾. Weight with coat attachment less than 1 oz. Special internal construction and rubber jacketed outer case insures quiet operation. No interference from breathing noises, etc. Typical Brush sound cell response and trouble-free operation. Details on request.

The **BRUSH** DEVELOPMENT COMPANY
PIEZO ELECTRIC
1882 E. 40th St. CLEVELAND, O.
MICROPHONES • MIKE STANDS • TWEETERS • HEAD PHONES • LOUD SPEAKERS

"HERE'S A SOUND PLATFORM"



Here's a platform that means more customers—quicker sales—bigger profits for every Serviceman and Sound man—Knight Political Sound Equipment! Portable, permanent and mobile types, for 110 Volt AC, 6 Volt, and combination 110 Volt AC—6 Volt operation. Every system is compact, easy to install, low in cost—designed especially for Political Sound needs! Extra-strong volume to reach hold large crowds—built-in sturdiness to withstand hard usage—prices that offer you the greatest profit making possibilities in years!

Political P. A. Sales Bulletin and 136 Page

Radio Catalog

Send for both—a punchy, value-packed sales promoter; and the most complete catalog in Radio, containing a special Public Address section. The catalog reveals new money-making opportunities that you never thought of before—the Bulletin sells complete Knight Sound Systems for you. Get set for the coming campaign—write for both today!

ALLIED RADIO CORP.

833 W. JACKSON BLVD. Dept. N CHICAGO, ILL.



Ken-Rad Radio Tubes

Ken-Rad Radio Tubes are made to give clear, dependable reception. They satisfy customers and build good will for dealers. Write for full information.



Genuine Glass or All-Metal Radio Tubes

THE KEN-RAD CORPORATION, Inc., Owensboro, Ky.
Division of The Ken-Rad Tube and Lamp Corporation
Also Mfrs. of Ken-Rad Incandescent Electric Lamp.

NEW AND UP-TO-DATE REPLACEMENT VIBRATOR
GUIDE NOW READY FOR DISTRIBUTION STOP WHERE
SHALL WE SEND YOUR COPY ADVISE

UTAH RADIO PRODUCTS CO.
CARRINGTON

URPC 820-S-6 CHICAGO, ILL.

TEAR OUT THIS AD—PIN TO YOUR LETTERHEAD AND MAIL TO DEPT. 5.
FOR COMPLETE DETAILS AND FREE CATALOG

UTAH RADIO
PRODUCTS CO.

Utah Radio

DALENS ST.
CHICAGO, ILL.

THE MANUFACTURERS . . .

OPERADIO TURRET PROJECTOR

There are many instances where directional sound projection calls for a horn. Operadio model 42 was designed and built to adapt a dynamic cone speaker to this type of horn service.

Specifications and further details may be had by writing to Operadio Mfg. Co., St. Charles, Ill., for catalog 10-E.

SMALL CANNED ELECTROLYTICS

The lasting quality of the metal-can electrolytic, together with a marked reduc-



tion in bulk for a given capacity, is achieved in a new line of dwarf units just announced by Aerovox Corp., 70 Washington St., Brooklyn, N. Y.

WEBBER SERVICE LABORATORY

The Engineering Department of Earl Webber Company, 1217 Washington Blvd., Chicago, has announced a complete radio service department on wheels, known as the Webber Official Radio Service Laboratory.

For complete details write for bulletin R9.

TRIMM HEARING AID EQUIPMENT

The Trimm Radio Mfg. Co., 1770 W. Berteau Ave., Chicago, manufacture a complete line of hearing aid amplifiers for individual and for group use. They also feature a complete line of hearing aid equipment such as earphones, microphones, remote control boxes, etc.

Complete information on these items can be obtained from the manufacturer.

TACO ANTENNA KITS

The Technical Appliance Corp., 17 E. 16th St., New York City, announce two all-wave antenna kits. The standard type 500 and a deluxe type 200. Both are completely assembled at the factory. Armored



copper wire is used for the aerial sections. An automatic switching set coupler is used.

Complete information is available from the factory.

INTER-COMMUNICATING SYSTEM

The Bell Sound Systems, 61 E. Goodale St., Columbus, Ohio, introduces a new line of intra-department communicating systems under the trade name of Belfone.

With a combination of three standard units and very simple wiring a number of variations of multiple hookups can be provided.

Complete details can be obtained from the manufacturer.


PORTABLE SERVICE LABORATORY

Model 1206 Triplett Master Unit Test Set is a complete radio service laboratory in portable form. Included in the master set are Models 1200 volt-ohm-milliammeter; 1210-A tube tester; 1220-A three point tester; and 1231 direct-reading all-wave signal generator.

Complete information may be obtained from the Triplett Electrical Instrument Co., Bluffton, Ohio.

STENTORIAN AMPLIFIER

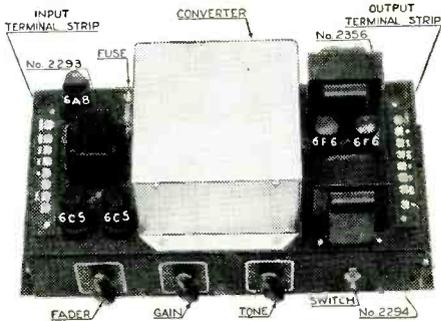The General Transformer Corp., 500 S. Throop St., Chicago, has added a 15-watt



high-gain amplifier nucleus to their line. A bulletin describing the kit may be obtained upon request.

CONTINENTAL BATTERY CHARGER

Continental announces a new self-starting gasoline-driven six- and twelve-volt battery charger and auxiliary lighting plant unit designed principally to be used as a battery charger for battery operated radio sets.

Complete information can be obtained from the manufacturer, Continental Motors, Detroit, Mich.

BRUSH CRYSTAL HEADPHONES

The Brush Development Co., East 40th St. at Perkins Ave., Cleveland, Ohio, has just announced the introduction of two new models of Brush crystal headphones to supplement the Brush Type A 2-phone model.

Additional information may be obtained from the manufacturer.

MUSIC MASTER SOUND SYSTEMS

The Turner Co., Cedar Rapids, Iowa, features three complete sound systems each designed for portable use. Power ratings are from 12 watts on the smallest to 20 watts on the largest. Complete description of these "Music Master" systems can be had from the manufacturer.

WARD RUNNING BOARD ANTENNA

The Ward Products Corp., 2135 Superior Ave., Cleveland, Ohio, feature a streamlined running-board antenna. The entire antenna is rubber covered and has a moulded rubber lead wire connection. A special type of mounting bracket eliminates the necessity of drilling the running board.

WRIGHT-DE COSTER EXTENSION SPEAKER

The Wright-DeCoster eight-inch Nokoil Reproducer has been housed in the cabinet illustrated for use as an extension speaker in connection with any auto-radio receiver. The speaker is equipped with a



universal output transformer which matches all output tubes.

Complete information can be had from the manufacturer.


TOBE BRIDGE

A bridge designed about the 6E5 cathode-ray tube offers visual null indication in the measurement of inductance, capacitance and impedance. The bridge, manufactured by the Tobe Deutschmann Corp., Canton, Mass., is completely self-contained, comprising the usual standards, ratio arms, 60- and 1200-cycle oscillators, power supply, amplifier and indicator tube. In addition to the 6E5, a 6J7 is employed as the dual frequency oscillator, while an 84 is used in the rectifying circuit.

The sensitivity of the electric eye is adjustable, facilitating a rough balance, and providing the sensitivity desirable for a precise null. The range of the bridge is from 2 mmfd to 100 mfd in capacity; from a fraction of one ohm to one megohm in resistance; and from 10 microhenrys to 100 henrys of inductance.

AMPERITE CABLE TYPE TRANSFORMER

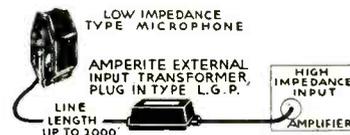The Amperite Corp., 561 Broadway, New York City, offer a cable type of external input transformer designed to operate low-impedance microphones directly into amplifiers having high-impedance input. It permits the cable of the low



impedance microphone to be any length up to 2,000 feet.

Additional information can be obtained from the manufacturer.

• SERVICE FOR



Handy Handful




Just that! Compact cardboard case PBS series electrolytics for general use. Reliable. Inexpensive. • Single, dual, triple section units. 200 and 450 v. working. Popular capacities. • Ideal for AC-DC midget set replacements. Also for experimental hookups. • Ask your dealer for the PBS line.

AEROVOX

CORPORATION

80 Washington Street Brooklyn, N. Y.

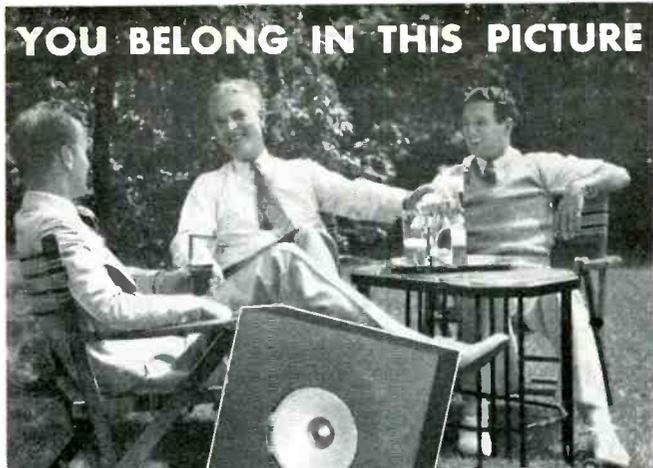Send for general catalog. Also sample copy of monthly Research Worker.



YOU BELONG IN THIS PICTURE

OUTDOOR SUMMER CALLS FOR Magic Magnet Extension Speakers

THE tremendous extension speaker market, practically untapped and highly profitable, is opened to the servicing field for the first time on a practical basis by the Cinaudagraph Magic Magnet Speakers.

Every owner of a radio receiver (and there are some 22,000,000 in America!) is a prospect. For porch, garden, bedroom, for every spot not reached by the set. They're a cinch to sell—these Magic Magnet Speakers with their high fidelity characteristics, sturdy construction, and simple installation features—only two wires being required for hook-up.

Extension speakers have proven a boon in England. Why not here? Just try selling your customers on the idea. You will be surprised at the response. *Details sent on request.*

CINAUDAGRAPH CORP. • STAMFORD, CONN.
Speaker Div. Dept. "A"

CINAUDAGRAPH

JUST OFF THE PRESS!



SIX PAGE CATALOGUE
DESCRIBING MOST
COMPLETE LINE
OF QUALITY

Mike Stands

Write for Your Copy to:

EASTERN MIKE-STAND CO.
56 CHRISTOPHER AVENUE BROOKLYN, N. Y.

Here Next Month:
Tru-Fidelity

by

THORDARSON
Most Sensational
Audio Development
in Radio History



"NOISE-MASTER"

Makes every
receiving set
a BETTER set

**Electrically
AUTOMATIC
in operation**

LIST PRICE \$6.75

Also available with special transformers for European broadcast bands . . . list \$7.00

Eliminates static on both broadcast and shortwave bands.



QUIET is what the set-owner craves, and here's the way to give 'em what they want. This A.A.K. licensed product, designed and engineered with typical CORWICO thoroughness, needs no manual operation after a qualified service-man has adjusted it. It eliminates noise and improves reception EVERYWHERE. Use it on your next installation!

Write for descriptive literature on this and other CORWICO units.

Cornish Wire Co., Inc.

30 Church Street New York City

GET ON THE LIST FOR THESE BIG FREE CATALOGS



• The four mastheads, illustrated show the four big catalogs sent to every Burstein-Applebee customer this year. Each catalog is brim full of latest information and lowest wholesale prices on Radio, Electrical and Refrigeration Equipment. Write today—get your name on the list to receive every Burstein-Applebee catalog issued.

BURSTEIN-APPLEBEE CO.

1012-14 McGee Street Kansas City, Missouri

CORNELL-DUBILIER



**Type
JR
CONDENSERS**

ONE of the outstanding developments in the condenser industry... The type JR... C-D ELECTROLYTIC, is absolutely revolutionary in size and construction.

COMPACT • CONVENIENT • EFFICIENT
These condensers offer positive money-making possibilities to the Serviceman. Service thousands of models with this versatile series.

Reduce your money tied up in stock and still keep yourself well prepared for any emergency.

Supplied with sturdy mounting feet and color coded wire terminal leads, the JR series will make any job a "cinch." Bulletin 131-A available free of charge gives full technical details.

CORNELL-DUBILIER

C O R P O R A T I O N

4375 BRONX BOULEVARD
NEW YORK

Get a Political Job It's Easy Money

STENTORIAN SOUND AMPLIFIER NUCLEUS



The hottest political campaign in years is directly ahead! Political organizations of all parties will need public address systems with a "Stentorian" tone. Dealers and Sound engineers can make good quick profit in selling or renting sound amplifiers built the "Stentorian" way.

G.T.C. Nuclei furnished for stationary and mobile outfits. Easy to understand directions for wiring supplied with each Nucleus. Power supply units are the HEART—the very nucleus of Sound Amplifiers. Each "Stentorian" NUCLEUS includes matched power transformer, chokes, audios, outputs with neat black wrinkle finished chassis, lettered terminal strips, marked tube sockets. "Stentorian" Sound Amplifiers provide wide tone range and good clear sound coverage for convention halls, auditoriums, stadiums, refectories, athletic fields, ballrooms, night clubs, taverns, lodge halls, banquet programs, political rallies, office and factory call systems, truck or auto advertising for concession barkers, race track announcements, depot train call systems, and the like.

The "Stentorian" way is the most economical way for Quality Sound Amplifiers.

GENERAL TRANSFORMER CORPORATION
(Manufacturer of Replacement Units)

502 S. Throop Street
Chicago, Ill.

15 Watt
Amplifier
Nucleus

High Gain for Crystal
or Velocity or Carbon
Microphones



Free for the Asking!

interesting illustrated bulletin on "STENTORIAN" Sound Amplifier Nuclei and name of distributor nearest you.

TWIN GROUP HEARING AIDS

ARE THE

FINAL CHOICE OF CHURCHES

- Superior Quality
- Excellent Performance
- Dependable Service
- Reasonable First Cost
- Low Maintenance Cost

SERVICEMEN

This is your field

Go after those extra profits.

TRIMM RADIO MFG. CO. Dept. S-6
1770 W. Berneau Ave., Chicago, Ill.

LEADING the field— the advantage of EXPERIENCE

FOX LOW LEVEL

(Tone Bell) REPRODUCER



Capable of reproducing a wide range of frequencies, it is designed to augment and strengthen all kinds of sound with complete distribution and without annoying projectional features. Especially valuable for inside installations or in small areas.

Technically correct as to curve, it is constructed of special alloy, finished in Fox standard aluminum and can be moved through 180° in a longitudinal direction. The unique mounting bracket is attached at the center of gravity, making directional adjustment perfectly stable. It can be secured by three wood screws for permanent installation on vertical or horizontal structures. The cradle is free to turn through a radius of 360°.

The sound chamber is equipped with the proper air by-pass for bass reproduction without distortion. Write for further details and prices.

FOX SOUND EQUIPMENT CORPORATION
3120 Monroe Street Toledo, Ohio

INDEX TO ADVERTISERS

Aerovox Corp.	285	General Illuminating Corp.	279	Radolek Co.	287
Allied Radio Corp.	283	General Transformer Corp.	286	Readrite Meter Works.	281
Arcturus Radio Tube Co.	287	Halldorson Co., The.	273	Rider, John F.	275
Audak Company	267	Hetro Elec. Industries, Inc.	283	Solar Mfg. Corp.	272
Bell Sound Systems, Inc.	281	Hygrade Sylvania Corp.	269	Sound Systems, Inc.	287
Bond Radio Co.	288	Ken-Rad Corp., The.	283	Sprague Products Co.	277
Brush Development Co., The.	283	Lenz Elec. Mfg. Co.	277	Supreme Instruments Corp.	
Burstein-Applebee Co.	285	Mallory & Co., Inc., P. R.		Third Cover	
Centralab	267	Second Cover-261		Technical Appliance Corp.	281
Cinaudagraph Corp.	285	Morlen Electric Co., Inc.	262	Thordarson Mfg. Co.	283-285-287-288
Continental Carbon, Inc.	281	Muter Co., The.	288	Tobe Deutschmann Corp.	279
Cornell-Dubilier Corp.	286	National Union Radio Corp.	275	Trimm Radio Mfg. Co.	286
Cornish Wire Co.	285	Ohmite Mfg. Co.	287	United Transformer Corp.	265
Curtis Condenser Corp.	288	Operadio Mfg. Co.	279	Utah Radio Products Co.	283
Eastern Mike-Stand Co.	285	Oxford-Tartak Radio Corp.	288	Ward Products Co.	269
Electrad, Inc.	250	Precision Apparatus Corp.	247	Webster Co., The.	277
Electro-Voice Mfg. Co., Inc., The	287	RCA Mfg. Co., Inc.	Fourth Cover	Weston Elec. Instrument Corp.	271
Fox Sound Equip. Corp.	286	Racon Electric Co., Inc.	249	Wholesale Radio Service Co.	288
General Electric Co.	245	Radiart Corp., The.	273	Wright-DeCoster, Inc.	273

ELECTRO-VOICE



For high-fidelity P.A. work, the ELECTRO-VOICE V-2 meets every requirement. Its wide, flat response gives a naturalness of reproduction, rarely found in other types. Feed-back is greatly reduced and hum pick-up eliminated through ingenious design. Incorporates many other desirable features such as the locking cradle, internal shock-proof assembly and 20' well shielded cable. Performance, appearance, simplicity of operation and value merge in the ELECTRO-VOICE Model V-2. Try one on your next installation. List price: \$35.00.


See your distributor or write for literature.

ELECTRO-VOICE MFG. CO., INC.
332 E. Colfax Ave., South Bend, Ind.
Export Office: 15 Laight St., New York, N. Y.

Here Next Month: *Tru-Fidelity*

by
THORDARSON
Most Sensational
Audio Development
in Radio History

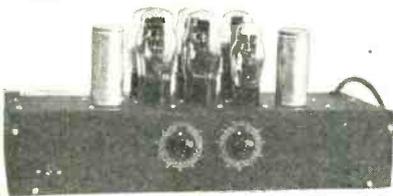Electronic Mixers for Crystal Microphones, Phono Units or other high impedance input.



Each position consists of a 2-stage push-pull amplifier with a balanced 2-unit volume control between stages.

Two-position Mixer. Also supplied for 3 or 4 positions.

Write for
Bulletin 14

SOUND SYSTEMS, INC.

6545 CARNEGIE AVENUE CLEVELAND, OHIO

ONLY ARCTURUS gives you ALL 4

The most complete tube line in the industry—ARCTURUS gives you 4 separate avenues to sales and profits. Unless you stock Arcturus Tubes, you're missing those additional profits that should be yours.

For full details of the 4-Way Arcturus line and the new 'Coronet' Metal Tubes write:


**ARCTURUS RADIO
TUBE CO.**
NEWARK, N. J.

Check any other line against Arcturus

TYPE OF TUBE	ARCTURUS	OTHERS
GLASS	✓	
"G"	✓	
METAL	✓	
METAL (TO REPLACE OLD GLASS TUBES)	✓	



ARCTURUS
"Coronet"
METAL TUBES

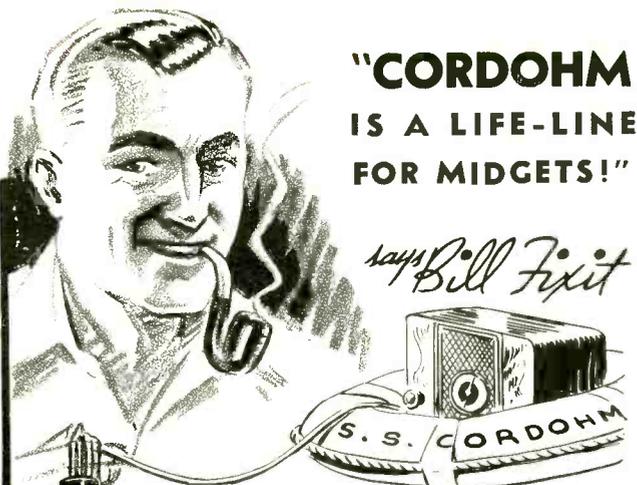

**"CORDOHM
IS A LIFE-LINE
FOR MIDGETS!"**

says Bill Fixit

"Line cord resistors have to take a lot of abuse. I've been looking for one that won't short out after the wire has been bent a few times, or wedged up against the wall . . . and I've found what I wanted! It's the OHMITE Cordohm."

Send for your
Copy of OHMITE
Catalog 14 FREE

Copper conductors in the CORDOHM are equivalent to No. 18 wire (16 strands of No. 30), insulated with 1/64 inch rubber wall served with cotton braid for extra protection. The resistance element is wound on an asbestos core, with a heavy serving of asbestos. A special non-breakable plug prevents the braid from unravelling, and insures a positive contact. Made in eight resistance values covering practically all tube combinations used in universal sets. Ask your jobber!

OHMITE
MANUFACTURING COMPANY

4827 Flournoy Street, Chicago, Ill.

Manufacturers of Resistors of All Types

PUBLIC ADDRESS *Sales-Promoter* with List Prices



Just Off The Press!

Another Radolek "Profit-builder" for you! A complete "Public Address Salesman." All prices are shown at your list selling prices. Show this book to your customers—it clinches the sale and protects your profits. Beautiful illustrations—complete descriptions—5 to 60 watts Everything in P. A.



Repair Parts Profit Guide

The new Radolek 1937 Radio Guide is completely revised—right up to the minute—everything in radio—at the right price. Over 10,000 Repair Parts—a complete selection of Receivers, Amplifiers, Tubes, Tools, Books, Instruments—always in stock—ready for speedy shipment to you. You need this big Radio Parts Catalog. It's free! Send for it.



**FREE
Send
This
Coupon**

RADOLEK

603 W. RANDOLPH STREET, CHICAGO

Send the Radolek Profit Guide Free
Send the P. A. Sales Promoter Free

NAME _____
ADDRESS _____
Serviceman? Dealer? Experimenter?

Curtis

Electrolytic
CONDENSERS

USED FOR MANY YEARS
BY THE SAME
SERVICEMEN!

Ample Proof of Their
Dependability and
High Quality

"STANDARD"
6 volt to 550 volt

"BLUE RIBBON"
630 volt

*Tested in Millions of Installations.
Satisfaction Guaranteed.*



Patent
No. 1950352

CURTIS CONDENSER CORPORATION

3088 WEST 106TH ST. CLEVELAND, OHIO


POLITICS PAYS



PROFITS

Sound trucks . . . portable P.A. systems . . . permanent P.A. installations . . . are all in greater demand this year because it is a presidential campaign year.

Political organizations of all parties are going to rent, or purchase outright, various types of public address equipment. We are exclusive world-wide distributors for Lafayette who have prepared a special LIST PRICE catalog to help YOU sell P.A. equipment. Most important of all Lafayette engineers have spent months in the development of new, finer P.A. equipment. Send for your FREE copy of Lafayette's complete P.A. list price catalog No. 64. Get on the political band wagon with Lafayette for profits in P.A. Simply address Dept. F5.

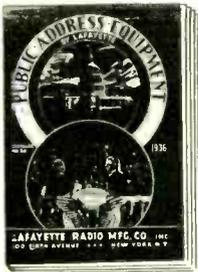

WHOLESALE RADIO SERVICE CO.
NEW YORK, N.Y.
100 SIXTH AVE.

CHICAGO, ILL. 901 W. JACKSON BLVD.
ATLANTA, GA. 430 W. PEACHTREE ST. NW.
BRONX, N.Y. 542 E. FORDHAM RD.
NEWARK, N.J. 219 CENTRAL AVE.

Here Next Month:
Tru-Fidelity

by
THORDARSON
Most Sensational
Audio Development
in Radio History

J O B B E R S

NEW LOW PRICES



Write for FREE 1936 CATALOG showing complete line of—

- Replacement Parts
- Short Wave Parts
- P A Equipment
- Ham Parts

Buy 80% of your fast moving radio parts from ONE source and SAVE MONEY. Reduce your inventory—increase your turnover, by means of our

RUSH shipment plan. All orders shipped day of receipt.

BOND RADIO COMPANY

Dep't 236
11702 LIVERNOIS, DETROIT, MICH.
Several profitable territories are still open for sales representatives. Write stating particulars.



SOUND . . . As You WANT It!



Specially Designed
EXPONENTIAL HORN by OXFORD

Marvelous reproduction and projective power! Patented fabricated acoustic material. Waterproof and Weatherproof! Scientifically designed for use with electro-dynamic cone unit. Heavy cast supporting lugs. 23" bell diameter. 27 1/2" long. Weight 12 lbs. Silver finish. List Price, only \$25.

Ask Your
Jobber or
Write Now
for Bulletin 362A

OXFORD-TARTAK
RADIO CORPORATION

915 W. VAN BUREN ST. • CHICAGO, U. S. A.



Candohms

ARMoured WIRE WOUND RESISTORS

OVER TWELVE MILLION IN USE
WRITE TODAY FOR COMPLETE CATALOG

THE MUTER COMPANY
1235 SO. MICHIGAN AVENUE, CHICAGO



399 De Luxe Analyzer

89 De Luxe Tube Tester

I WILL GIVE YOU BOTH THESE SUPREME INSTRUMENTS FOR ONLY \$9⁵⁰ DOWN + \$8⁴⁹ PER MONTH

Your Parts Jobber

189 SIGNAL GENERATOR

Supreme 189 Signal Generator — both modulated and unmodulated — self-contained 400 cycle audio oscillator — unusual frequency stability through special electron-coupled circuit — carrier frequencies directly calibrated. Only \$4.00 DOWN and \$3.66 PER MONTH.



It is no longer necessary to save money to buy a SUPREME. Get the instrument now and pay for it on the easiest possible terms while you use it. Ask your Parts Jobber or write the factory about the S. I. C. Easy Payment Plan. Everybody's doing it!

SUPREME INSTRUMENTS CORP. GREENWOOD MISS., U. S. A.
 EXPORT DEPT., ASSOCIATED EXPORTERS CO., 145 W. 45th STREET, NEW YORK, N. Y., CABLE ADDRESS: LOPREN, N. Y.

Here's a new

RCA AUDIO OSCILLATOR

...essential in service work

AND AVAILABLE ON EASY TERMS*

Every shop needs an audio oscillator. For instance, when trying to locate a speaker rattle without one, you have to tune in a program and wait until the rattle frequency happens along. With the oscillator you just run up and down the scale until you hear the rattle. You do the job in a few minutes, impress the customer, earn your fee in quick time. Other uses: checking P. A. systems, demonstrating fidelity, testing transformers and amplifiers, determining frequencies observed on screen of RCA Oscillograph. Also used in conjunction with RCA Test Oscillator. Case is same size as the latter instrument . . . This new RCA Audio Oscillator is an outgrowth of the famous \$215 laboratory model RCA Audio Oscillator, designed and made by same engineering and factory staff. Price made possible by quantity production. Now ready for delivery. Ask your distributor for complete information.



New RCA Beat Frequency Oscillator has many features not obtainable elsewhere. Wider frequency range, 30 to 15,000 cycles. Tapped output transformer permits matching impedances of 5,000, 500 and 250 ohms, all balanced to ground. Easily and quickly calibrated at 30, 60, 120, 180, 240 cycles, with neon indicator. Entirely AC operated. Output 60 milliwatts. Weight only 10¼ pounds. Contains 4 new-type RCA acorn tubes, plus rectifier. Tubes alone cost \$20.35. Complete with tubes ready to operate, \$64.50 f.o.b. Camden, New Jersey.



*For your customers
who want to*
TUNE BY EYE

RCA offers a genuine RCA Cathode Ray Tuning Indicator Kit. Can be installed in almost any receiver that has automatic volume control. The kit is complete, everything you need, including tube, socket, cable, clamp and bracket, escutcheon. Easily and quickly installed. Price \$3.00. Stock No. 9688.



See your RCA Parts Distributor for RCA Test Equipment now available on an attractive time payment plan. Parts Division, RCA Manufacturing Co., Inc., Camden, N. J.

RCA Parts



**1935 VOLUME of
RCA Victor Service Notes
NOW READY!**

*Includes not only all the RCA
Victor Service Notes, but a wealth
of technical charts and data. Sub-
stantially bound in durable cloth.
Price \$1.00 f.o.b. Camden.*