



**Here's the Big News
for 1937!!**

ALL


Schematics—Circuits	Condensers
Volume Controls	Tubes
I. F. Peak Frequencies	Vibrators
Transformer Circuits	

in ONE book

For the first time — under ONE Cover — all the information you need in servicing sets. Not only in *One* book but on *one* page, on *one* line, you find the answer for any servicing problem for any radio set. You bet! Over 12,000 different models are covered in this one compact, complete, authentic, up-to-the-minute compendium. The new

MALLORY-YAXLEY

Radio Service Encyclopedia

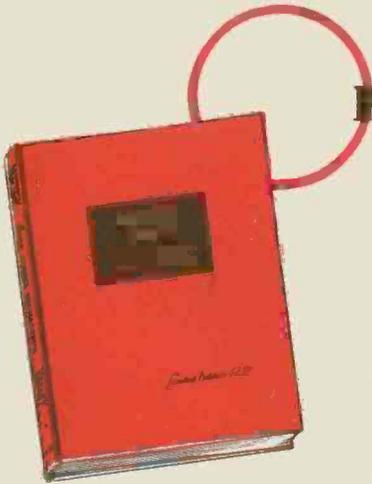

They said it couldn't be done — that any one would be crazy to try it. But Mallory-Yaxley invested \$75,000 in hard cash and years of painstaking investigation; corralled the experience of thousands of practical servicemen. And we have achieved the impossible.

For the first time, accurate, detailed instructions are given on the thousands of receivers that ordinarily are headaches to the most experienced Service engineers. No need now to worry about the dope on the tough ones. This book gives the correct answer always. What's that worth to you? Boy, the sky is the limit.

We have prepared this Encyclopedia for you. Your Mallory-Yaxley distributor has your copy ready for you to examine. Your share of the cost is a trifle. Buy the book — if in a week it does not pay its way, if you would part with it for twice what you paid for it — return the book and get your money back. But act today; the edition is limited.

Over 200 pages of exact information. Bound in waterproof, washable cloth and printed on paper that stands the gaff... it is a permanent working reference.

Use
YAXLEY
REPLACEMENT
VOLUME CONTROLS

P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA
Cable Address — PELMALLO

Use
MALLORY
REPLACEMENT
CONDENSERS... VIBRATORS

**MEASURE G-E METAL TUBES
UNDER ANY BUYING INDEX YOU CHOOSE**

**.... and you'll
find them your
first choice for**

QUALITY

LONG LIFE

DEPENDABILITY

PRECISION

PERFORMANCE



**For Customer Satisfaction
USE G-E METAL TUBES**

GENERAL  ELECTRIC

THE ORIGINAL METAL TUBE

APPLIANCE AND MERCHANDISE DEPARTMENT, GENERAL ELECTRIC COMPANY, BRIDGEPORT, CONNECTICUT

SERVICE

A Monthly Digest of Radio and Allied Maintenance

Reg. U. S. Patent Office. Member, Audit Bureau of Circulations

EDITOR

Robert G. Herzog

JANUARY, 1937

VOL. 6, NO. 1

EDITORIAL CONTENTS

FEATURES

A Cathode-Ray Oscillograph for the Service Man	12
A-C Bridge Measurements in Service Procedure By Glenn H. Browning.....	37
A Direct-Coupled Beam-Power Amplifier By A. C. Shaney.....	44
Crosley WLW Audio Amplifier.....	48
Double Superheterodyne (Westinghouse) ..	11
Individual Batteries for Philco Sets.....	32
Master Antenna Systems.....	9
Reducing Code and Image Interference....	34

ANTENNA	6
---------------	---

ASSOCIATION NEWS	50
------------------------	----

AUTO RADIO	
Atwater Kent 556.....	28
Crosley A-366	28

CIRCUITS	
Atwater Kent 556 Auto Radio.....	28
Condenser Analyzer Part of Bridge Circuit	52
Crosley A-366 Auto Radio.....	30
Crosley WLW Audio Amplifier.....	48
Direct-Coupled Beam-Power Amplifier....	47
Direct-Coupled Signal Divider.....	44
Double Superheterodyne (Westinghouse)	
Front Cover	
G. E. E-129.....	17
Philco 37-116 (Codes 121-122).....	22
RCA Model 150 Test Oscillator.....	13
RCA Model 151 Cathode-Ray Oscillograph	12
Resistance Measurement With the Bridge..	52
Sentinel-Erla 65B	15
Series Wave Trap.....	34
Shunt Wave Trap.....	34

Stabilized Bridge Type Rectifier System...	44
Stromberg-Carlson 160-L Circuit Change...	42
Tobe A-C Bridge-Analyzer.....	38

GENERAL DATA

Crosley WLW Audio Amplifier.....	48
Double Superheterodyne (Westinghouse) ..	11
G. E. E-129.....	16
Individual Batteries for Philco Sets.....	32
Philco 37-116 (Codes 121-122).....	20
Reducing Code and Image Interference....	34
Sentinel-Erla 65B	15
Service Notes	26-43
Technical Features of 1937 G.E. Radio Receivers	19
Type 25L6 Beam-Power Amplifier.....	43

HIGHLIGHTS	54-58
ED-ER	

MANUFACTURERS	56-58
---------------------	-------

ON THE JOB

Individual Batteries for Philco Sets.....	32
Reducing Code and Image Interference....	34

PUBLIC ADDRESS

A Direct-Coupled Beam-Power Amplifier By A. C. Shaney.....	44
Crosley WLW Audio Amplifier.....	48

RECEIVER CASE HISTORIES	40-42
-------------------------------	-------

TEST EQUIPMENT

A Cathode-Ray Oscillograph for the Service Man	12
A-C Bridge Measurements in Service Pro- cedure By Glenn H. Browning.....	37

BRYAN S. DAVIS
President

JAS. A. WALKER
Secretary

Chicago Office—608 S. Dearborn St.—C. O. Stimpson, Mgr.
Telephone: Wabash 1903
Wellington, New Zealand—Tearo Book Depot.

Published Monthly by the


Bryan Davis Publishing Co., Inc.
19 East 47th Street
New York City
Telephone: Plaza 3-0483



SANFORD R. COWAN
Advertising Manager
PAUL S. WEIL
Eastern Advertising
Manager
A. B. CARLSEN
Circulation Manager

Cleveland Office—10515 Wilbur Ave.—J. C. Munn, Mgr.
Telephone: Republic 0905-J
Melbourne, Australia—McGill's Agency.

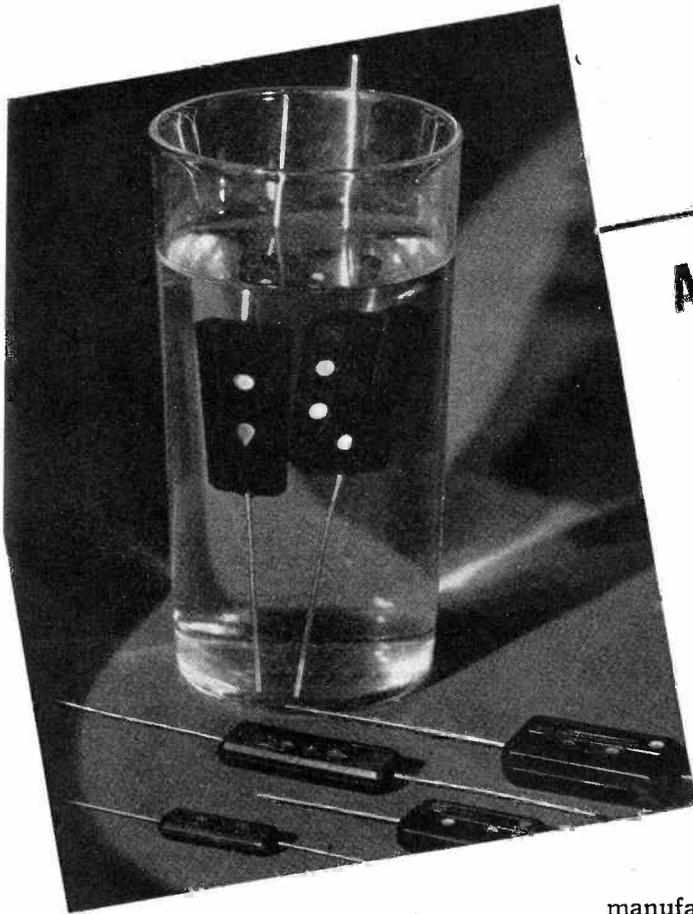Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.




ABSOLUTELY PROTECTED AGAINST MOISTURE AND HEAT

The one piece bakelite covering of Micamold Molded Paper Condensers and Molded Wire Wound Resistors is a protection against moisture and heat far beyond the requirements of use. You can even boil them in water for an hour and then use them with perfect results. This is positive proof of the effectiveness of the bakelite covering on these condensers and resistors, originated and perfected by Micamold. Micamold products have

long been the choice of leading set manufacturers because of conservative ratings, uniform excellence and long life. Now they are offered to the serviceman for replacement purposes. You owe it to yourself to know more about these revolutionary items. Of further interest is the fact that Micamold replacement parts are inexpensive.

Condensers up to 1000 volts in standard capacities

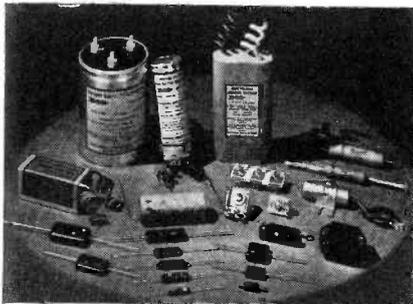Resistors up to 2 watt in popular resistance values



Micamold manufactures a full line of Electrolytic, Paper, Mica and Trimmer Condensers and Wire Wound and Carbon Resistors. Many items are exclusive with Micamold. If your jobber does not have our catalog with list prices, write us for a copy.

MICAMOLD PRODUCTS CORPORATION

Flushing and Porter Avenues

Brooklyn, N. Y.



Send for FREE Samples.

In order that you can see and test these items yourself, we will send, postage prepaid, free samples with a list value of over 40 cents. Don't miss this generous offer.



CONDENSERS - RESISTORS

MICAMOLD PRODUCTS CORPORATION, Flushing and Porter Avenues, Brooklyn, N. Y.

Please send me free samples as advertised.

Name

Address

City State

Jobber's Name S

THE ANTENNA . . .

NEW SET SALES

THAT THE SERVICE MAN has the opportunity to exert considerable influence on the purchaser of a new receiver, especially when that receiver is used to replace an old set, can not be denied. In many cases the set owner decides to buy because he has just been given a large estimate for repairs to the old set. "Why spend \$12.50 to repair that piece of junk when for a few dollars more I can get a new all-wave job?" is a theme we hear continuously. As we have said before, the wideawake Service Man will not lose by this procedure. Estimates should *not* be lowered but rather increased to encourage the purchase of the new set.

Those Service Men who sell receivers will readily agree with us, since their profit on the new set sale will more than offset that lost in service work during the course of the year—and here is a profitable customer for service for the next year (if he is treated O.K. during the guarantee period).

We believe that the other Service Men can readily afford to encourage the purchase of a new set and earn ten or fifteen dollars in commission through a suitable setup with a friendly local dealer. This neat commission should prove easier to earn than the hoped for profits on one or more troublesome jobs servicing an obsolete and fast dying receiver.

• • •

PUBLIC ADDRESS

WE HAVE, IN THESE columns, from time to time stressed the importance of the public-address field and the Service Man's place in that field. We have pointed out that the use of sound amplification is no longer classed as a novelty—it is taking its place among the necessities of life like the automobile and the radio.

Estimates of the p-a business for the coming year show an expected increase of 100 percent over last year. You should get your share of that business. Make it known that you are able to handle p-a installations. Look up prospects.

Many doors were closed for p-a sales because prospects have heard only the poor efforts of earlier outfits. Some even have these relics gathering dust on their shelves. It is up to you to keep your equipment up-to-date—give

demonstrations—open these doors once again for added p-a profits. With the increasing improvements in micro-phones, phonograph pickups, speakers, tubes and other sound equipment few can complain of unsatisfactory reproduction.

Public-address equipment can be used for purposes too numerous to mention. Almost in any type of business it can increase efficiency as a call system. Amplifiers are gradually taking an outstanding place in funeral parlors for playing records during services. On trucks, in stadiums, in lecture halls, in churches and in the theater the p-a system is indispensable. To the Service Man all this spells profits.

• • •

TELEVISION

NOW AND AGAIN IN the daily and Sunday newspapers and in the newsstand magazines, the coming of television is heralded. More conservative magazines have not only refused to announce television's approach but have used considerable space in denying that approach. Up to now SERVICE has merely reported on events in this most interesting field. Until the time that television becomes a Service Man's problem we will do little more.

• • •

RISING PRICES AND THE SERVICE MAN


WE HEAR FROM THE tube manufacturers that tube prices have been increased some 11 percent more or less. This is along the line of predictions in the forecast published in the December issue of SERVICE. If the predictions hold these increases are only the forerunners of general price rises on all parts and accessories.

Although the general rise in tube prices was only 11 percent the average increase among the ten types (80, 24A, 27, 45, 35, 47, 71A, 26, 01A and 112A) which enjoy the most volume in replacement sales is over 20 percent. This means an actual increase of over \$3,500,000 in gross profit to dealers and Service Men in the sale of replacement tubes during 1937.

Service Men, for this reason, should welcome these justified price increases in tubes and other replacement components.

QUIET PERMANENT RUGGED

"THE NAME TELLS YOU
IT'S A MASTERPIECE"

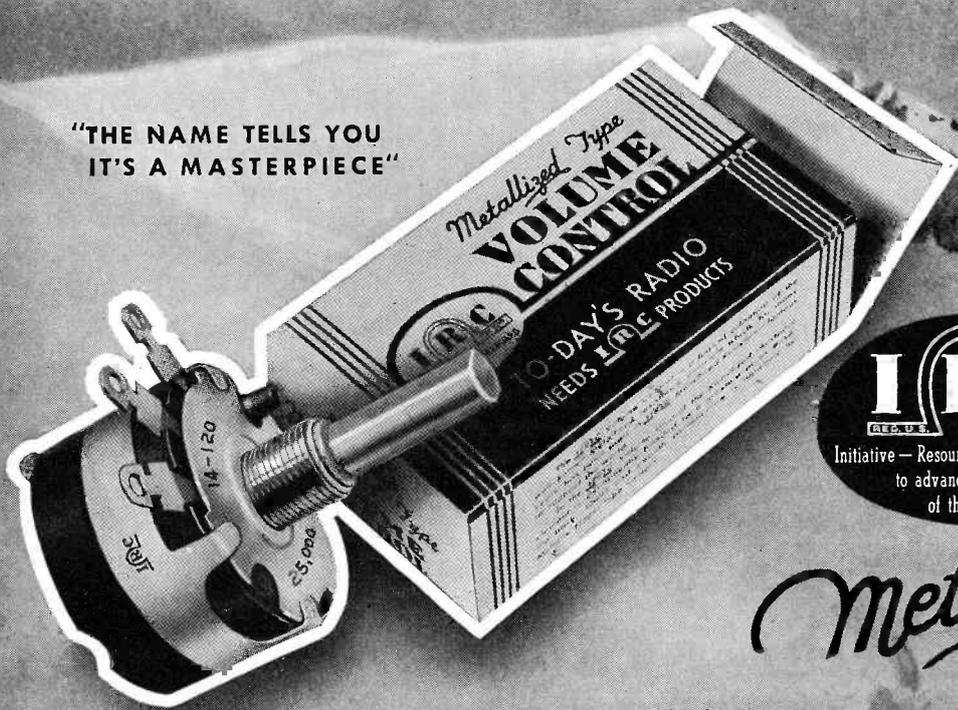

Metallized

VOLUME CONTROL

INTERNATIONAL RESISTANCE COMPANY

401 NORTH BROAD STREET, PHILADELPHIA, PA.

Factories or Licensees in Canada, England, France, Germany, Italy, Denmark and Australia

[MAKERS OF RESISTANCE UNITS OF MORE TYPES, IN MORE SHAPES, FOR
MORE APPLICATIONS THAN ANY OTHER MANUFACTURER IN THE WORLD]

Now!
A.V.C. Testing
Simplified



with
MODEL 1200-C
VOLT-OHM-
MILLIAMMETER

Dealer Price **\$24.³³**

- ★ 5000 OHMS PER VOLT D.C.
- ★ RESISTANCE READINGS TO 7.5 MEGOHMS.

- ★ FOR ALL RADIO MEASUREMENTS NOT REQUIRING A NO CURRENT DRAW VACUUM TUBE VOLTMETER

● A.V.C. (Automatic Volume Control) places automatic bias voltage on the grids of the I.F. tubes. Voltage varies with signal strength. Test is made by measuring comparative diode voltage or value of resistance.

All this can be done simply and quickly with the new Triplet Volt-Ohm-Milliammeter Model 1200-C.

● Model 1200-C has separate A.C. and D.C. instruments in Twin Case with tilting feature for accurate reading. Ohms Scales separately adjusted. Low loss switch. (Contact error less than 1/2%) Low Ohms scale requires but 6 2/3 milliamperes. Accuracy both A.C. and D.C. guaranteed within 2%. All Metal Case.

Scale Reads: D.C. 10-50-250-500-1000 Volts at 5000 Ohms per volt; 250 Microamperes; 1-10-50-250 Milliamperes; 1/2 to 500 low ohms, backup circuit; 15-1500 Ohms; 1.5 and 7.5 Megohms; A.C. 10-50-250-500-1000 Volts.

A TRIPLETT MASTER UNIT

SEE YOUR JOBBER

WRITE FOR CATALOG



TRIPLETT ELEC. INSTRUMENT CO.
 171 Harmon Ave., Bluffton, Ohio

Without obligation please send me more information on
Model 1200-C;Complete Triplet Master
 Unit Line.

Name

Address

City..... State.....

SERVICE

A Monthly Digest of Radio and Allied Maintenance

FOR JANUARY, 1937

MASTER ANTENNA SYSTEMS*

DIRECTLY and indirectly, the enterprising Service Man must be interested in the master antenna system. Directly, it means a new and profitable source of income and the contact with many potential customers. Indirectly, it provides the necessary signal pickup and noise suppression for the satisfactory operation of sets which he installs and services.

It's a logical development. Just as more electric outlets are called for these days to take care of more lamps and appliances, so more antenna facilities and radio outlets are required today to operate the several sets in a better type household, let alone the requirements of the apartment house building. Also, there are hospitals, hotels, club buildings and other institutions as prospects. And no saturation point is ever likely to be in sight.

EASY TO SELL

Any large or small apartment house or public building in which a plurality of radio sets are to be operated without their owners coming to blows, is ripe for a master antenna system. In the case of the apartment house owner, the main sales argument is reduced maintenance costs. The roof happens to be a real sore spot. Available figures indicate that 9 per cent of total maintenance costs goes for roof repairs and upkeep. Take away that jungle of poles and wires and insulators and roof maintenance costs take a nose dive. There is no longer reason for tenants trooping over the roof, straining standpipes, fumbling with flashings and otherwise causing damage. But tenants will insist on good radio reception. And that is where a master antenna system comes in, with its trim, neat, permanent steel masts, its simple aerials and its inconspicuous downleads connecting with outlets throughout the building.

Local ordinances are also coming to

the rescue in making sales. Some municipalities have already passed and are enforcing stringent laws regarding those radio jungles. Fire authorities are frowning on wire mazes that may cause loss of life and limb to firemen working on the roofs. Insurance companies are none too fond of the general mess. All these factors help create a market for master antenna systems.

In a nutshell, the apartment house owner or management is sold first on the idea of saving money by reduced maintenance costs, second on the idea of coaxing in new tenants and keeping old ones satisfied. The investment is trivial especially when compared with the advantages. Also, the many installations already in use will help sell more. It's the old game of "follow the leader." One radio-wired house in a locality sets the pace for others.

The home-builder can be sold on the idea of convenience at an insignificant increase in total building costs. Even

the standing house can be radio-wired for very little, greatly adding to its comfort and resale value.

THE PRELIMINARY SURVEY

The prospect naturally wants to know "how much?". That information must be based on a preliminary survey.

In the case of an apartment house the building is checked for floor plans; locations of radio outlets; available super-structures that can serve as supports; required masts; stringing the aerial wires; running of transmission lines along walls or through walls, and other essential details.


For estimating purposes and layout of an installation the starting point is the determination of the number and the location of the radio outlets. In the usual apartment house the living-room is the customary place for the outlet. With the help of a floor plan, it is easy to locate the most convenient placement of the transmission line or downlead. This line in turn determines the direction and arrangement of the aerials. Full advantage is taken of super-structures such as water tanks, elevator-shaft houses, pent-houses, and so on, that can be pressed into service as supports for the aerial wires swung high above these bases, as clear of the building as possible. Elsewhere, masts must be employed for supports.

Fortunately, there is a cold mathematical basis for arriving at an estimate. Guesswork is reduced to a minimum. Standardized components and materials are available at set list prices and trade discounts. Labor costs are readily figured because of the comparative simplicity of the installation work.

THE SYSTEM AT A GLANCE

The master antenna system consists of the aerial proper with its necessary supports; the transmission line or downlead, and the required number of outlets. That's all there is to it.

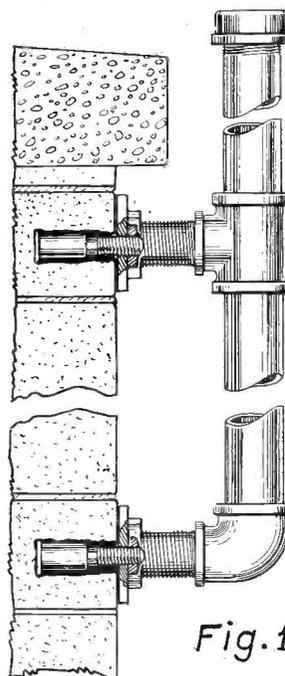More detailed, the aerial foundation kit consists of two lengths of aerial wire



* The material for this article was supplied by the engineering department of the Technical Appliance Corp.

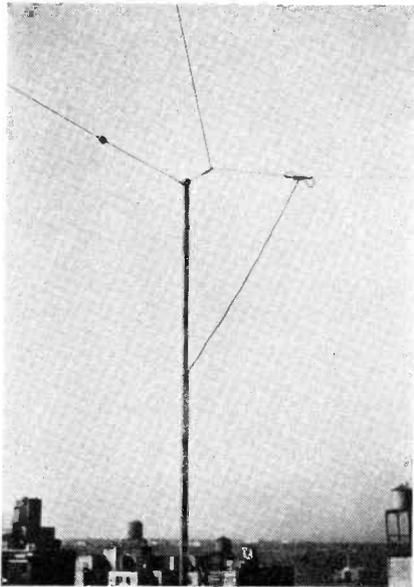


Fig. 2. Typical iron-pipe mast for master antenna system.

for a di-pole or doublet antenna; a transfer unit and any length of twisted-pair cable for the transmission line; the necessary heavy-duty insulators and the strain insulators.

The recommended masts are 1½-inch galvanized iron pipe, capped at top for protection against weather. The mast is supported by an elbow at the bottom, and by a tee reamed out to receive the pipe. The suggested arrangement is shown in Fig. 1. The necessary pipe and fittings may be obtained from a local plumbers' supply house, eliminating most of the guesswork of arriving at a cost. A couple of hours should suffice to erect and anchor a mast.

With the aerial strung up and supported, the twisted-pair transmission line is led to the lightning arrestor con-

Fig. 5. The wire is being laid in a groove cut out of the tiled roofing. It should be covered up with pitch, effectively sealing it in place.



veniently located on a parapet or side wall. The ground connection is made to the roof flashing or to a standpipe known to be properly grounded.

The transmission line then continues over the parapet or cornice and down the side wall in the case of exposed wiring, which is generally followed particularly in existing buildings.

PERMANENCY THE KEYNOTE

Every precaution must be taken to make the job permanent and maintenance free. The sloppy workmanship that distinguishes many ordinary aerial installations simply won't do when it comes to the master antenna system. Any Service Man who is not a good mechanic may as well forget this master antenna proposition here and now unless he intends to reform his ways.

Thus iron pipe masts, as already explained, take the place of flimsy and bent wooden poles, the use of which is discouraged on most city buildings if not actually prohibited by building code. The twisted-pair transmission line is carefully protected from wear and tear

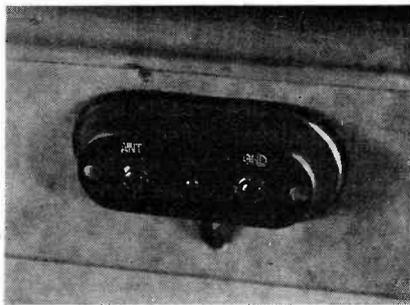


Fig. 4. Exposed type outlet unit mounted on window sill.

where it touches the roofing or masonry. In crossing over the parapet wall, for instance, the transmission line is covered with copper tubing for protection. Better still, it is passed through a slot or cleared out joint which can be filled with pitch or caulking compound. In passing over a penthouse terrace the cable (with additional protection covering), is buried in an expansion joint and sealed with pitch.

The transmission line along side walls is firmly anchored by knobs or other means. Available in black or neutral to blend into the wall color scheme, the transmission line is quite inconspicuous.

At the point closest to a coupler or outlet, the transmission cable is bared. The coupler leads are passed through a hole in the window frame and soldered to their respective transmission line conductors, outside the wall of the building. The joints are taped and varnished to prevent corrosion. The coupler or outlet of the exposed-wiring type is mounted on the inside window frame or

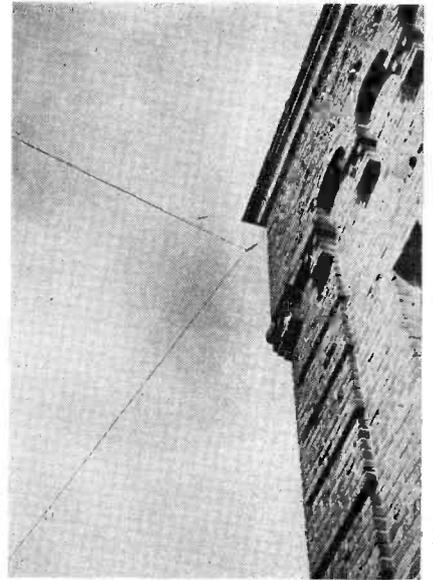


Fig. 3. Best aerial is in the clear.

on a baseboard. It provides two binding posts marked "Ant" and "Gnd" for set connections.


TEST AS YOU GO

By means of an ordinary midget receiver of average sensitivity and selectivity, each coupler or outlet is tested for reception as connections are completed. If each coupler tests O.K. as installed, the entire installation will test O.K. when completed: Thus there is no time lost trying to run down bugs which would be troublesome in the completed job.

THE CONCEALED WIRING JOB

So far we have dealt with the exposed-wiring job, which isn't much more than any all-wave noiseless antenna system installation. With a con-

Fig. 6. Single radio outlet box, showing coupler unit. This is the knob and tube kind of wiring for private dwellings shown on incomplete wall.

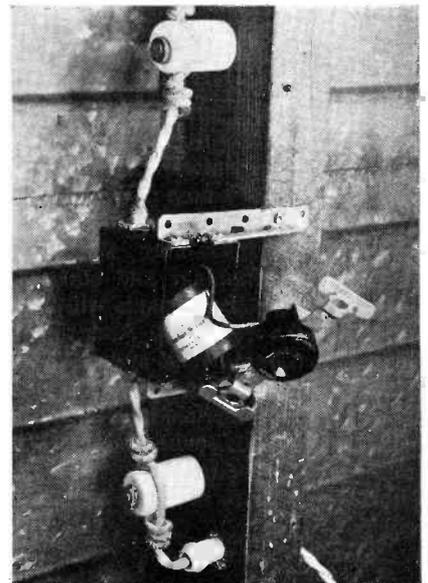

cealed wiring job the roof end remains exactly the same as for the exposed-wiring job. The transmission cable passes from the aerial and lightning arrester to a conduit tube leading into the building. The transmission cable may be passed through conduit or BX, or even strung on knobs and passed through tubes between walls. After all, there isn't any current or voltage involved, so that the wiring is not hazardous in the slightest degree. But then the underwriters and local inspectors may be leary of such free and easy wiring and may insist on the usual conduit or BX variety.

In place of the exposed type outlet, the concealed job makes use of standard outlet boxes to take the outlet coupler. In some jobs the outlet is for radio alone. A regular gem box serves to hold the small coupler coil whose red and

black leads go to the transmission line, while other leads connect with "Ant" and "Gnd" of the receptacle binding posts or pinjacks. In other jobs where the power outlet is to be combined with radio, the coupler coil fits on one side and is separated from the power receptacle by a simple metal shield. A 4-inch (square) box does nicely for a combined outlet.

FOR THE PRIVATE RESIDENCE

When it comes to private homes, the story is much the same, except simpler and easier to sell and do. The aerial is either of the outdoor kind, swung between roof and a tree or other building in the shape of a double V to obtain sufficient length in limited space. The transmission line is run down between partition walls and suitably held by knobs and tubes. In the new building

this wiring may be done when the studing is still exposed. But even in the existing building, the wiring may be readily snaked about.

Outlets, either of the exposed or outlet box type, can be installed wherever a radio program may entertain or enlighten the household.

PROFIT FOR SERVICE MAN

Once again the Service Man steps in as the logical salesman. The master antenna system can be recommended and talked up in many quarters. A nice profit awaits him on the completed installation.

There's money in that master antenna system idea. And it takes less effort to get some of that money than is the case with sets and repairs and other phases of the servicing game. So the Service Man may as well climb on the bandwagon now.

DOUBLE SUPERHETERODYNE

(See Front Cover)

THE circuit diagram shown on the front cover gives the essential circuit of a typical double superheterodyne. The parts values given are those in the Westinghouse model WR-315 12-tube receiver.

THE CIRCUIT

In the all-wave, double superheterodyne, with an r-f stage, the incoming signal is fed to an r-f coil and tuning condenser through a suitable band-switching arrangement. Here the signal is pre-tuned and fed to the grid of an r-f amplifier, a 6K7 in the circuit shown on the cover. The amplified signal from the plate of the r-f tube is fed (through the band switch) to a second r-f coil and tuning condenser which tunes it further and passes it on to the grid of an oscillator-detector stage which mixes it with a locally-generated signal 465 kc above it in frequency. The tuned, local signal is generated in the oscillator section of this tube (a 6A8 in the circuit shown) and its frequency difference is maintained through tuning the respective oscillator coils with one section of the main tuning condenser and its associated network of padders and trimmers. The resulting signal on the plate of the oscillator-detector (if the receiver is properly aligned and tuned) is always 465 kc regardless of the frequency of the station to which the receiver is tuned.

In the double superheterodyne, as in

the conventional superheterodyne, this 465-kc signal is fed to a tuned i-f transformer the secondary of which is coupled to the grid of the succeeding stage. The 8-mh choke between the first modulator and the primary of the first i-f transformer is for the purpose of attenuating the variable oscillator frequencies. If these are passed to the grid of the second modulator, a series of tweets will be heard; these tweets are produced whenever the variable oscillator frequency differs by about 100 kc (the second i-f) from a harmonic of the fixed oscillator. At the grid of this succeeding stage the double superheterodyne differs materially from the conventional superheterodyne. In the conventional super the grid in question is that of the usual i-f amplifier—in the double superheterodyne this tube is an oscillator-modulator which mixes the 465-kc i-f signal with a locally generated "fixed" frequency signal of 365 kc to produce on the plate of this tube (another 6A8 in the circuit shown) the second intermediate frequency of 100 kc. The local 365-kc signal is generated in the oscillator section of this oscillator-modulator tube. The 100-kc signal obtained from the oscillator-modulator plate is further amplified by one or two tuned i-f stages.

CAREFUL SHIELDING ESSENTIAL

The "fixed" oscillator stage, with its coils, condensers, resistors and asso-

ciated wiring, must be carefully shielded and isolated to prevent its signal, or the harmonics of its signal, from straying to the r-f circuits of the receiver. Pick-up of these signals would cause tweets at the respective points on the dial (365 kc, 730 kc, 1095 kc, etc.).

The automatic frequency control tube (not shown in the diagram) is connected across the "fixed" frequency oscillator stage. The afc circuits are similar to those described in previous issues of SERVICE.

ADVANTAGE OF DOUBLE SUPERHETERODYNE

The chief advantage of the double superheterodyne lies in that it provides a "fixed" frequency oscillator upon which the automatic frequency control may be applied. Since the afc can be applied apart from the tuning circuits of the receiver its use can be obtained without affecting the frequency coverage of any tuning range of the receiver. Uniform control action can be more easily obtained on every frequency range of the receiver.

It is thus possible to tune from a strong local signal to a weak distant signal on the adjacent channel with the afc switch in its on position. If two strong signals are 20-kc apart, a blank interval will appear between them when tuning from one to the other, in the absence of a signal on the channel be-

(Continued on page 43)

A CATHODE-RAY OSCILLOGRAPH

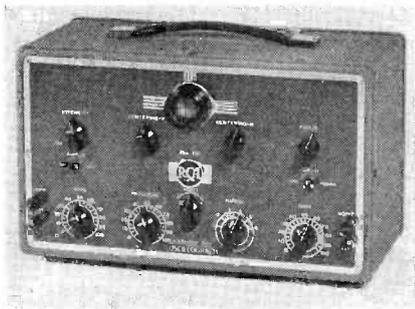


Fig. 1. The RCA model 151 cathode-ray oscilloscope in its portable carrying case. Front view showing calibrated screen and controls.

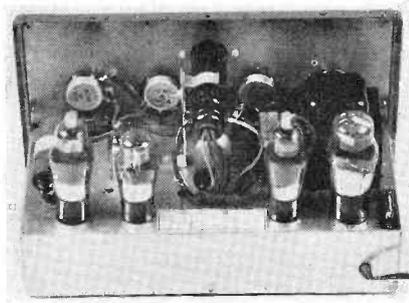


Fig. 2. The rear of the RCA model 151 cathode-ray oscilloscope with the case removed, showing positions of parts and tubes.

ALTHOUGH some 18 to 20 percent of the full-time Service Men have already purchased cathode-ray equipment, the devices have, in the past, been essentially laboratory equipment. However, with the advent of the type 913 cathode-ray tube the oscilloscope become a typical service tool.

THE 913 TUBE

The heart of the new oscilloscope, shown in Figs. 1 and 2, is the 913 high-vacuum cathode-ray tube which utilizes the all-metal construction and has a viewing screen approximately one inch in diameter.

The electron source of the 913 is a substantial cathode indirectly heated. The cathode, control electrode (grid) and focusing electrode which functions also as an accelerating electrode, constitute an electron gun for projecting a beam of electrons upon the fluorescent screen. The resulting luminous spot, easily visible in a well-lighted room, can be regulated as to size and intensity

by suitable choice of electrode voltages.

The two interconnected sets of electrostatic plates in the 913 produce fields at right angles to each other, and consequently deflections at right angles. One set serves to reproduce the phenomena under observation; the other is used for the time sweep.

Because of its small size and its ability to produce a bright image at low voltages, the 913 is suited for compact, portable oscillographic equipment. These features, in addition to the relatively low cost of the 913 and its associated apparatus, make this tube practicable for use in many types of test equipment where a larger cathode-ray tube would not ordinarily be employed.

The base pins of the 913 fit the universal eight-contact octal socket, which may be installed to hold the tube in any position. The metal shell is connected to anode No. 2 within the tube.

The heater is designed to operate at 6.3 volts. The cathode is connected within the tube to one side of the heater.

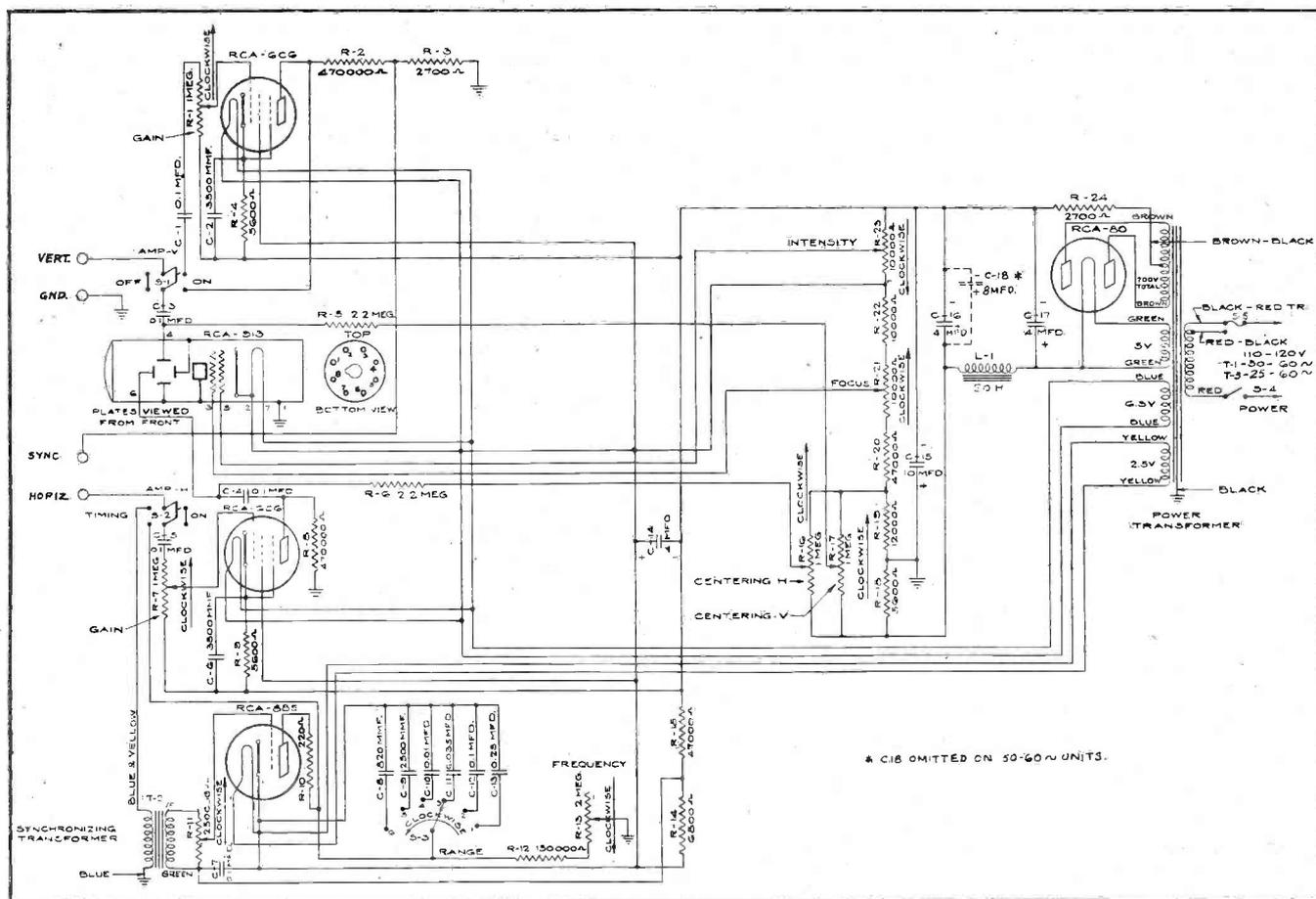


Fig. 3. The RCA model 151 cathode-ray oscilloscope circuit diagram.

FOR THE SERVICE MAN

The terminal for this common connection is base pin No. 2 to which the grid and anode returns are made.

The fluorescent screen employed in the 913 is of the phosphor No. 1 (medium persistence) type. It has good visual properties as well as high luminous efficiency.

The d-c supply voltages are conveniently obtained from a vacuum-tube rectifier. Since the cathode-ray tube requires very little current the filter requirements are simple. A 4- or 8-mfd condenser provides sufficient filtering.

Two sets of electrostatic plates, producing fields at right angles, provide for deflection of the electron beam. One deflecting plate of one set is connected within the tube to one plate of the other set, to anode No. 2 and to the shell.

THE CATHODE-RAY OSCILLOGRAPH

The cathode-ray oscillograph is an instrument adaptable to a wide variety of applications. A few of the more important are: the study of wave shapes;

measurement of modulation and peak voltages; adjustment of and location of faults in radio receivers and a-f amplifiers; comparison of frequencies; the indication of balance in bridge circuits, and visual alignment. Due to the relatively low cost of the 913 and its associated apparatus, to the low voltages at which it can be operated and to the small size and portability of equipment in which it is employed, this tube should find very general use by Service Men.

A circuit diagram of the RCA cathode-ray oscilloscope, designed around the 913 tube, is shown in Fig. 3. The electrode voltages are obtained from the rectifier with its associated filter and bleeder circuit. A small value of bleeder current is essential and makes the simple filter adequate. A variable voltage for the control electrode and for anode No. 1 is obtained from potentiometers in the bleeder circuit.

THE DEFLECTING PLATES

One set of deflecting plates is used



Fig. 4. The RCA model 150 test oscillator in its portable carrying case. Front view showing dial and panel arrangement.

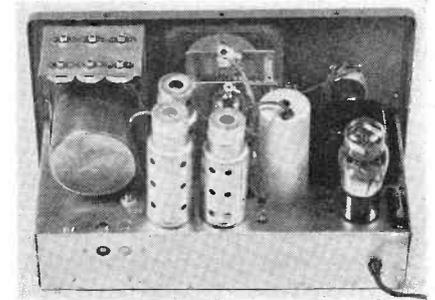


Fig. 5. The rear of the RCA model 150 test oscillator, showing positions of parts and tubes.

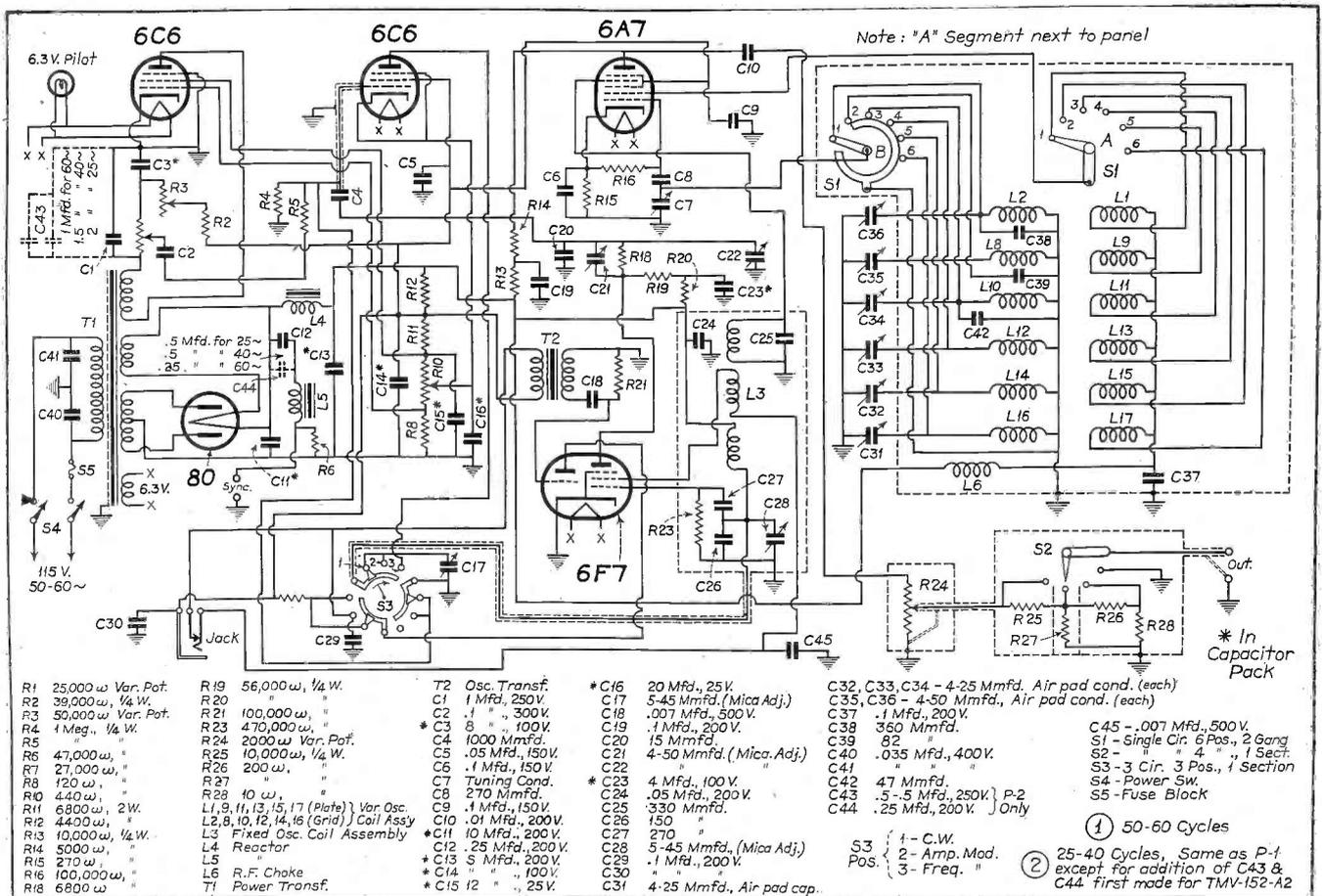


Fig. 6. The RCA model 150 test oscillator circuit diagram.

for the phenomena under observation; the other set, for the time sweep which serves to spread the tracing across the fluorescent screen. In order to maintain the free plate of each set at essentially the d-c potential of anode No. 2, each of these plates is connected through a (high-ohmage) resistor to the anode No. 2 socket terminal. The value of this resistor is such that the electron beam is not distorted by d-c potentials built up on the deflecting plates. In cases where the fluorescent spot is off center, a variable d-c bias is provided in series with each of the deflecting plate resistors. The polarity of each control voltage is such that the spot can be shifted in both directions so as to provide a pattern centering adjustment.

SPOT REGULATION

Focusing of the fluorescent spot produced by the beam is controlled by adjustment of the ratio of anode No. 2 voltage to anode No. 1 voltage. The ratio is varied by adjustment of anode No. 1 voltage as shown in the circuit diagram.

Regulation of spot size and intensity can be accomplished by varying anode No. 2 current and voltage. The current to anode No. 2 is increased by decreasing the bias voltage applied to the control electrode (grid). An increase in anode No. 2 current increases the size and intensity of the spot. An increase in the voltage applied to anode No. 2 increases the speed of electrons which increases spot intensity and decreases spot size.

In applications involving voltage measurements, the anode No. 2 current should be reduced to the minimum value consistent with the desired brilliance of pattern. Where high brightness is an important consideration, the voltage applied to anode No. 2 may be increased to the maximum rated value. This procedure, however, it not always desirable because the greater speed of the electrons in the beam causes reduced deflection sensitivity.

The 913 is designed to provide as high a current in the electron beam as is consistent with good focusing qualities. This high-current capability is a distinct advantage for obtaining bright patterns covering a relatively large area, but must be used with caution when the spot traverses slowly any portion of a large pattern or when the pattern size is small. Where recurrent phenomena are involved, a pattern, or some portion of it, having too high a power input per unit area may cause the rating of the fluorescent screen to be exceeded. A "slowly-moving spot" is tentatively defined as a fluorescent spot which is traveling slowly enough to be seen as a spot, rather

than as a trace or line. With patterns of this type, the power input to the screen should be limited as in the case of a stationary spot.

Photographs of recurrent phenomena (producing stationary patterns) appearing on the viewing screen of the 913 can be made with an ordinary camera. Due to the low anode voltage and moderate screen-input power at which the 913 is operated, the photographing should be done in subdued light in order to obtain as much contrast as possible between the fluorescent pattern and the background. The time of exposure will depend upon the speed of the camera lens, the kind of film or plate emulsion used, the magnification of the pattern, and the brightness of the image on the viewing screen. Verichrome film gives excellent results.

AMPLIFIERS AND SWEEP CIRCUIT

As can be seen from the circuit diagram, Fig. 3, the RCA oscillograph (model 150) is complete in its portable case with amplifiers, sweep circuit and power supply.

A single stage is provided, for each set of deflecting plates, using a 6C6 tube in each stage. The amplifiers have a voltage gain capable of giving full-scale deflection on the 913 screen with only 1 $\frac{1}{4}$ volts on the input to the amplifier. The frequency characteristic of the amplifiers is flat from 30 to 10,000 cycles. Gain controls are provided for varying the sensitivity. Switches are also provided so that the input to either plates can be connected directly to these plates.

The linear timing axis provided has a range from 30 to 10,000 cycles and has two controls (one fine and one coarse). These controls, together with the synchronizing control, are used to make the pattern stationary on the 913 screen. An 885 tube is used as the sweep oscillator.

THE FREQUENCY-MODULATED OSCILLATOR

As a companion to the cathode-ray oscillograph, RCA has produced an all-wave, frequency-modulated test oscillator. The oscillator, like the oscillograph is housed in a gray, crinkle-finished, portable carrying case.

Continuous frequency range from 90 kc to 32 mc is available in six bands. Separate coils are used for each band with individual air-dielectric trimmers for each coil. The entire coil assembly is separately shielded from the oscillator chassis.

A 4-in. diameter dial with 340 degrees of rotation provides over twelve inches of frequency calibrated scale. Two knobs are provided giving both fine and coarse tuning ratios. Indirect lighting and a projected zero line eliminate the

possibility of parallax on reading the scale.

Both frequency and amplitude modulation are available. No amplitude modulation is present with the frequency modulated signal.

Internal 400-cycle amplitude modulation is provided and remains constant at 30 percent at all frequencies. The frequency and waveform of the modulation also remains constant throughout the range of the oscillator.

A three-step output attenuator in addition to a continuously-variable attenuator provide minute control of the output signal; variable from 0 to $\frac{1}{4}$ volt.

Two 6C6 tubes are used, one as the sweep tube and the other as the generator of the sweep voltage. A type 6A7 tube is used as the r-f oscillator and mixer and a type 6F7 is used as an audio and fixed frequency (r-f) oscillator. An 80 tube rectifier provides d-c for the plate, screen and cathode voltages required in the instrument which is completely self-powered from the 60-cycle a-c (or 25-cycle) line.

THE CIRCUIT

Frequency modulation, in the RCA model 150 oscillator, begins in the plate coil of the 6C6 sweep tube. This coil is wound on the a-c power transformer (T_1). Frequency modulation is thus introduced into this circuit by the variation in the inductance of this winding because of the amplitude variation of the a-c supply. The winding is tuned by the condenser (C_1) across it.

By suitable rectification and amplification in another 6C6 sweep tube, this modulation, together with a fixed r-f signal generated in the pentode section of the 6F7 tube, is fed to the r-f transformer L_2 . A secondary winding on this transformer feeds these signals (when the modulation switch is in the proper position) to the pentode section of the 6A7 mixer tube.

The oscillator section of the 6A7 mixer is used to generate the tunable r-f for the range from 90 kc to 32 mc. The resulting signal on the plate of the 6A7 tube is frequency modulated at a rate of 120-cycles per second over an adjustable band width of from 1 to 40 kc.

When the modulation switch is in the amplitude modulation position a 400-cycle audio frequency note, generated in the triode section of the 6F7 tube, is picked up in the pentode section of the 6A7 mixer and serves to modulate the (amplitude of the) tuned r-f signal.

In the other position of the modulation switch an unmodulated r-f signal, generated in the oscillator section of the 6A7, is obtainable from the output posts of the test oscillator.

Material for this article was supplied by the RCA Mfg. Co., Inc.

General Data . . .

Sentinel-Erla 65B

The Sentinel-Erla 65B is a five-tube battery-operated superheterodyne receiver employing glass tubes of the two-volt series. Two bands are covered with a range of 535 to 1720 kc and 2.3 to 6.3 mc, respectively. A type 19 output tube provides push-pull class B operation with a 30-tube as driver. A 6-inch permanent-magnet dynamic speaker is used in the table models and an 8-inch one is used in the console models.

ALIGNMENT PROCEDURE

The procedure outlined below should be followed carefully, otherwise the receiver will be insensitive and the dial calibration will be incorrect. The trimmer and padder condensers are referred to by their function as indicated in Figs. 2 and 3.

I-F ALIGNMENT

(a) Connect the ground lead of the test oscillator to the set ground. Connect the other lead to the grid cap of the 1C6 tube through a 0.02-mfd series condenser. Do not remove grid clip.

(b) Set test oscillator to exactly 465 kc and turn receiver volume control on full.

(c) Peak each of the second i-f transformer trimmers.

(d) Peak each of the first i-f transformer trimmers. To assure more accurate trimmer setting repeat above adjustment several times, always using lowest possible test oscillator output consistent with readable output meter scale deflection.

WAVE-TRAP ALIGNMENT

(a) Connect the high output side of the test oscillator through a 0.00025-mfd condenser to the receiver antenna lead and the low side to the set ground.

(b) Set test oscillator frequency to exactly 465 kc and adjust the 465-kc wave-trap trimmer condenser for *minimum* 465-kc signal response.

BROADCAST BAND ALIGNMENT

(a) Adjust band selector switch for operation on 535 to 1720 kc band. Leave test oscillator lead connected to receiver antenna lead through a 0.00025-mfd series condenser.

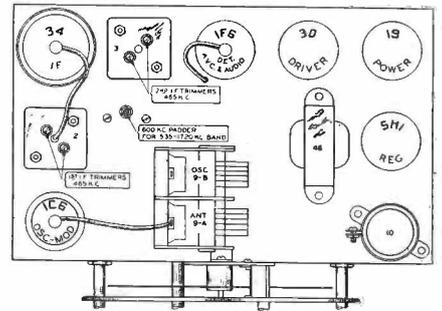


Fig. 2. Tube and trimmer locations.

(b) Check tuning dial adjustment by turning gang condenser until plates touch maximum capacity stop (completely in mesh), at which point the dial needle must be exactly even with the last line at the low frequency end of the dial calibration. If the dial needle does not point exactly to the last line, move needle to correct position.


(c) Set test oscillator frequency and receiver dial to exactly 1720 kc.

(d) Adjust 1720 kc oscillator trimmer to bring in 1720 kilocycles test oscillator signal to maximum output.

(e) Tune receiver dial and set test oscillator frequency to exactly 1400 kc.

(f) Adjust 1400 kc antenna trimmer for maximum sensitivity.

(g) Set receiver dial and test oscilla-

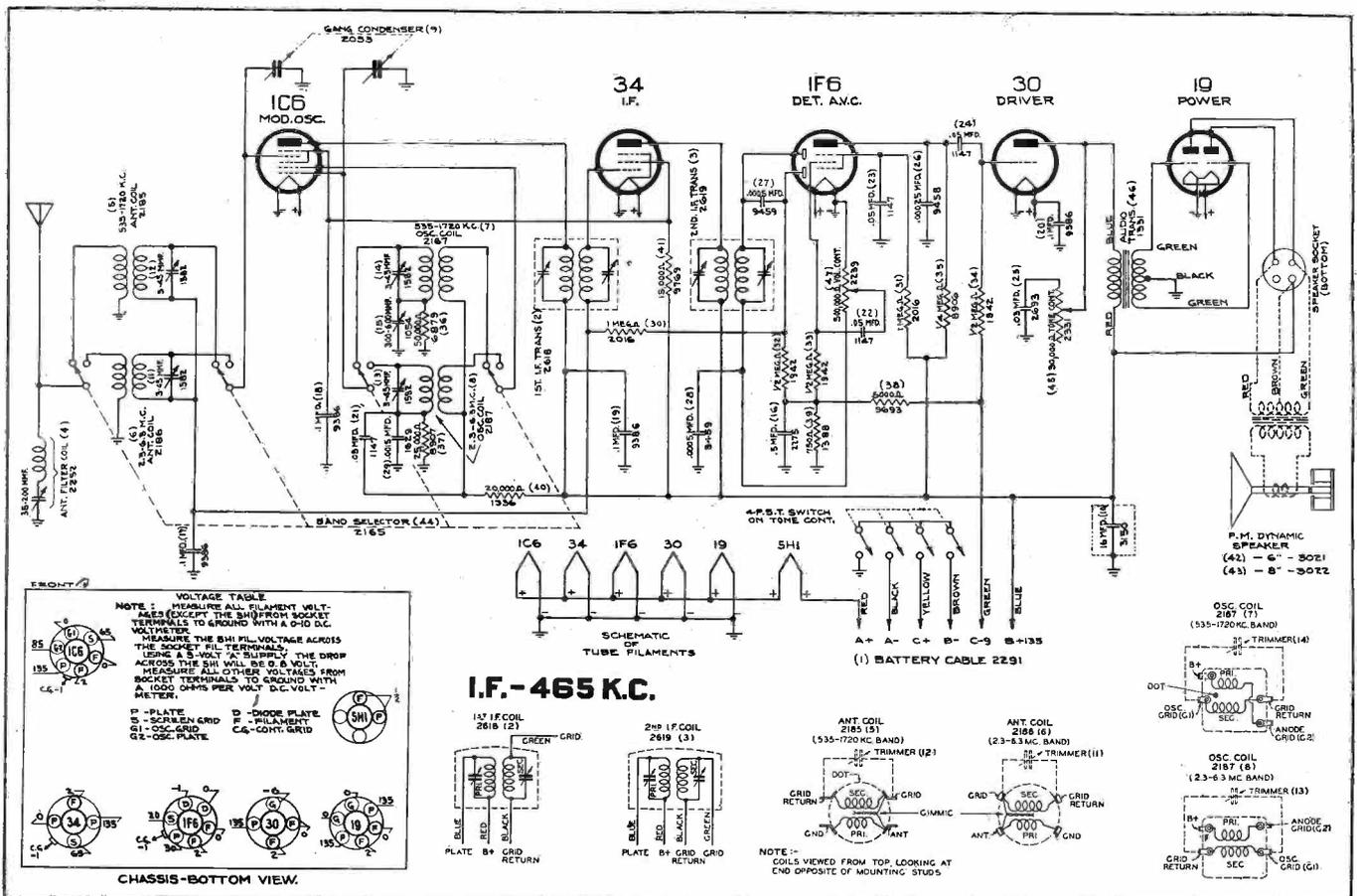

Sentinel-Erla 65B circuit diagram.

in order to provide the differential afc voltage.

DETECTOR AND AVC

The plates of the 6H6 twin diode are fed in push-pull by the secondary of the third i-f transformer. Two balanced diode loads consisting of R-24 and the series resistance of R-21, R-22, and R-23 are provided. The afc voltage is developed across the sum of all these resistors, while the audio voltage appears across the sum of R-21 and R-22 and R-23. The audio frequency thus provided is transferred to the a-f system for amplification and reproduction. The direct-current component of the rectified signal produces a voltage drop across the above three resistors. That existing across R-21 and R-22 is employed for operating the 6K7 "Colorama" tuning tube. Switch S-10 permits the application of either full or partial voltage to the tube, thereby permitting control of the color indication in accordance with prevailing receiving conditions. The d-c voltage developed across R-21 is utilized for automatic volume control action by employing the same to bias the r-f amplifier, converter, and first i-f amplifier tubes. Initial bias for these tubes is obtained by returning resistor, R-21, to the minus 3 volt tap of the voltage divider. The second i-f tube receives no avc and is self-biased. This minimizes the possibility of non-linear distortion on strong signals.

AUDIO SYSTEM

The audio voltage developed across the diode load is applied to the volume control, R-32, through the isolating capacitor, TC-49. This control is compensated by means of dual resistance-capacitance networks to provide the proper balance of high and low frequencies at different volume control settings. The movable arm on the volume control selects the amount of audio signal applied to the control grid of the 6C5 audio amplifier tube and thus regulates the output of the receiver. The output of the 6C5 audio tube is transformer coupled to the control grids of the two 6F6 output tubes which operate in a push-pull connection.

The music-speech control consists of a switch actuated at one extreme of the tone control rotation corresponding to that providing maximum high note response. This provides better speech clarity by decreasing the bass compensation which is accomplished by shunting capacitor TC-53 with TC-52. The bass compensation is removed entirely on the short-wave bands by the switch S-2; hence the music-speech control is

only effective in the broadcast "B" band. Continuously variable tone control is provided by capacitor TC-59 and variable resistor R-34 shunting the grids of the push-pull output tubes.

SILENT TUNING

Silent tuning is provided by the switch S-9 which is actuated by the tuning knob of the receiver. Pulling the tuning knob out slightly closes switch S-9 and kills the audio output by grounding the 6C5 grid. The afc is also removed by this operation which permits a sharp indication of resonance by noting the "Colorama" lights. When a station has been satisfactorily located in this manner, the tuning knob is pushed in to its original position and the switch opened.

POWER SUPPLY

The d-c power for the operation of the receiver is supplied by a power supply system employing a 5Z4 full-wave rectifier tube which, together with a suitable network of resistors and capacitors, supplies the required voltages and filtering action.

COLORAMA TUNING

These receivers are equipped with color tuning, a novel method which indicates approach to resonance by means of a change in color of the light illuminating the tuning scale. The technical features of this method of tuning were fully described in the December, 1936, issue of SERVICE.

AUTOMATIC FREQUENCY CONTROL

These receivers also employ automatic frequency control (afc) which is a device for automatically controlling the oscillator frequency in such a way that, although the receiver is not exactly tuned to the signal being received, an intermediate frequency of 465 kc will still be produced. The operation of the automatic frequency control as applied to the General Electric receivers was completely described in the October and November (1936) issues of SERVICE.

ALIGNMENT PROCEDURE

The receiver should first be allowed to run for fifteen minutes in order to reach its approximate normal operating temperature. Before making any adjustments, it is wise to determine the correctness of the existing alignment. This may be done by supplying a signal from the test oscillator to the receiver and inserting a "Tuning Wand" into the coil involved.

To realize the full advantage of the performance built into these receivers at the factory, circuit alignment using cathode-ray oscilloscope equipment is much to be preferred. The oscilloscopic method is particularly advantageous in aligning the i-f tuned circuits.

See Fig. 2 for the location of all trimmer capacitors.

I-F ALIGNMENT

Although the use of the cathode-ray oscilloscope for alignment purposes is to be preferred, it is possible to make the i-f trimmer adjustments with reasonable accuracy using a 465-kc signal generator and output meter.

Place a modulated signal of 465 kc on the grid of the last i-f (6K7) tube with the volume control set at maximum and the afc switch *turned off*. Place a low-range a-c voltmeter or other output indicator across the voice coil of the loudspeaker. Adjust the output of the signal generator so that an indication of not more than two or three volts is obtained on the output meter.

Adjust and readjust the primary trimmer for maximum output and *the secondary for minimum output*. This latter adjustment will be very broad. Apply the signal input to the grid of the first i-f (6K7) tube and adjust both primary and secondary trimmers for maximum output, reducing the input as necessary to obtain approximately the same output indication as before. Apply the signal input to the grid of the converter (6L7) tube and adjust both primary and secondary trimmers for maximum output indication in the same manner.

It is now necessary to make a fine adjustment of the secondary trimmer of the last i-f (afc) transformer which is as follows: without changing the frequency of the signal generator, place the input lead on the rubber insulation of the converter (6L7) grid lead. This will provide a small signal input through the capacity between the leads. Increase the attenuator setting if necessary to make the output audible. If the signal generator is provided with a means of removing the modulation, this should be done. However, the adjustment may be carried out satisfactorily even with a modulated generator signal.

Now tune in any broadcast signal in the usual manner and tune the receiver carefully for zero beat between this carrier and the 465-kc signal generator. It may be necessary to use a short antenna or to remove it entirely if the station is a strong local. Throw the afc on and adjust the last i-f secondary (afc) trimmer to give zero beat.

..Technical Features of 1937 G.E. Radio Receivers..

Model No.	E-51	E-61	E-62	E-68	E-71	E-72	E-76	E-79	E-81	E-86	E-91	E-95	E-101	E-105	E-106	E-126	E-129	E-155	U-50	U-51	U-55	U-70	U-75
Cabinet *	T	T	A.C.	Ce	T	T	Ce	Ce†	T	Ce	T	Ce	T	Ce	Ce	Ce	Ce†	Ce	T	T	Ce	T	Ce
Power Supply	A _C /D.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	2 V. B. B. Batt.	6 V. Batt.	6 V. Batt.	6 V. Batt.
No. of Bands	2	2	2	3	3	3	3	3	3	3	3	3	3	3	3	4	4	5	1	2	2	3	3
* Range (Kc.)	540-7000	540-7000	540-7000	540-18,000	540-18,000	540-18,000	540-18,000	540-18,000	540-18,000	540-18,000	540-18,000	540-18,000	540-18,000	540-18,000	540-18,000	540-70,000	540-70,000	140-540-70,000	540-1700	540-1750	540-1750	540-18,000	540-18,000
Power Consumption	-	70 W.	80 W.	80 W.	80 W.	80 W.	105 W.	105 W.	100 W.	100 W.	105 W.	105 W.	110 W.	110 W.	155 W.	165 W.	165 W.	-	-	-	-	-	-
Audio Power	5 W.	5 W.	5 W.	5 W.	5 W.	5 W.	5 W.	5 W.	10 W.	10 W.	10 W.	10 W.	14 W.	14 W.	15 W.	15 W.	15 W.	35 W.	-	-	-	-	-
I.F. Peak (Kc.)	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465
Dynamic Speaker	6 1/2"	8"	6 1/2"	12"	8"	8"	12"	12"	12"	8"	8"	12"	12"	12"	12"	12"	12"	15"	-	-	-	-	-
Tone Control	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes
Music-Speech Control																							
Silent Tuning																							
Personalizer																							
Sentry Box																							
High-Low Speed Tuning																							
Bass Compensation																							
Wave Trap or Presetor																							
Variable Condensers	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2
Number of Tuned Circuits	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6	6
Colorama Tube																							
R. F.																							
1st. Det. Osc.	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8
Intermediate Freq.	6K7	6K7	6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7	(2) 6K7
2nd. Det. A V C																							
1st. Audio	6Q7	6H6	6F5	6H6	6H6	6H6	6H6	6H6	6H6														
2nd. Audio																							
Output	25A6	6F6	6F6	6F6	6F6	6F6	6F6	6F6	6L6	6L6	6L6	6L6	6L6	6L6									
Rectifier	25Z6	5W4	5W4	5W4	5W4	5W4	5W4	5W4	5Z4	5Z4	5Z4	5Z4	5Z4	5Z4									
A F C																							

* T = Table
Ce = Console
† Phono Combination

Sound Engineers Acclaim **AUDAX**

Microdyne

THE "RELAYED-FREQUENCY" PICK-UP

The advent of MICRODYNE has once again proven conclusively that sound engineers KNOW what they want. In all parts of the country, North—East—South—West, and in foreign lands; MICRODYNE has been subjected to the most severe tests under all climatic conditions. The overwhelming opinion: MICRODYNE is

"The Standard by Which Others Are Judged and Valued"

AUDAX *Magneto-Inductive*

Pick-ups—Built on the time-tested, un failing, unvarying Magneto-Induction principle . . . the identical method used in the actual making of the remarkable new high-fidelity records. Preferred by leading Universities, Radio Stations, Theatres and Sound Engineers . . . wherever SOUND must be of the very best!

NEW . . . *MICROMATIC*



AUDAX
AA-76

For use with records up to 18". High frequency range. Ball-bearing compound movement. Low gravity center. Remarkably fine tracking. Featherweight. Low or high impedance.

AUDAX AA-74—MAGNETO-CHROMATIC—Technically identical with AA-76, for use with records up to 12". Featherweight on record. Low or high impedance.



AUDAX HR-62

Listed at \$15.00

MAGNETO-CHROMATIC—Low priced model for records up to 12". Excellent frequency response. Featherweight on record. Low or high impedance.

There are several other AUDAX models to fill every need from the humblest portable to the most exacting transcription requirements. If your jobber cannot supply you, write direct. AUDAX pickups list from \$9.50 to \$390.

An interesting new brochure—"Pick-up Facts"—is now available to the trade. Write for your copy.



A sound engineer's pick-up! The more technical and exacting the listener, the better this superfine instrument squares with his ideals. For the first time since the advent of pick-ups in 1926—here is absolute recording-microphone fidelity—uncompromising in *facsimile* performance and scientific uniformity. Yes—it's MAGNETO INDUCTIVE.


AUDAX Recording Heads

AUDAX cutters are built on the Magneto-Induction principle as used in the making of Hi-Fidelity records by foremost manufacturers. AUDAX cutters are used in leading radio stations, recording studios; wherever quality transcriptions are demanded.

Listed from \$35.00 up

AUDAX COMPANY, 500 Fifth Avenue, New York

"Creators of High Grade Electrical and Acoustical Apparatus Since 1915"

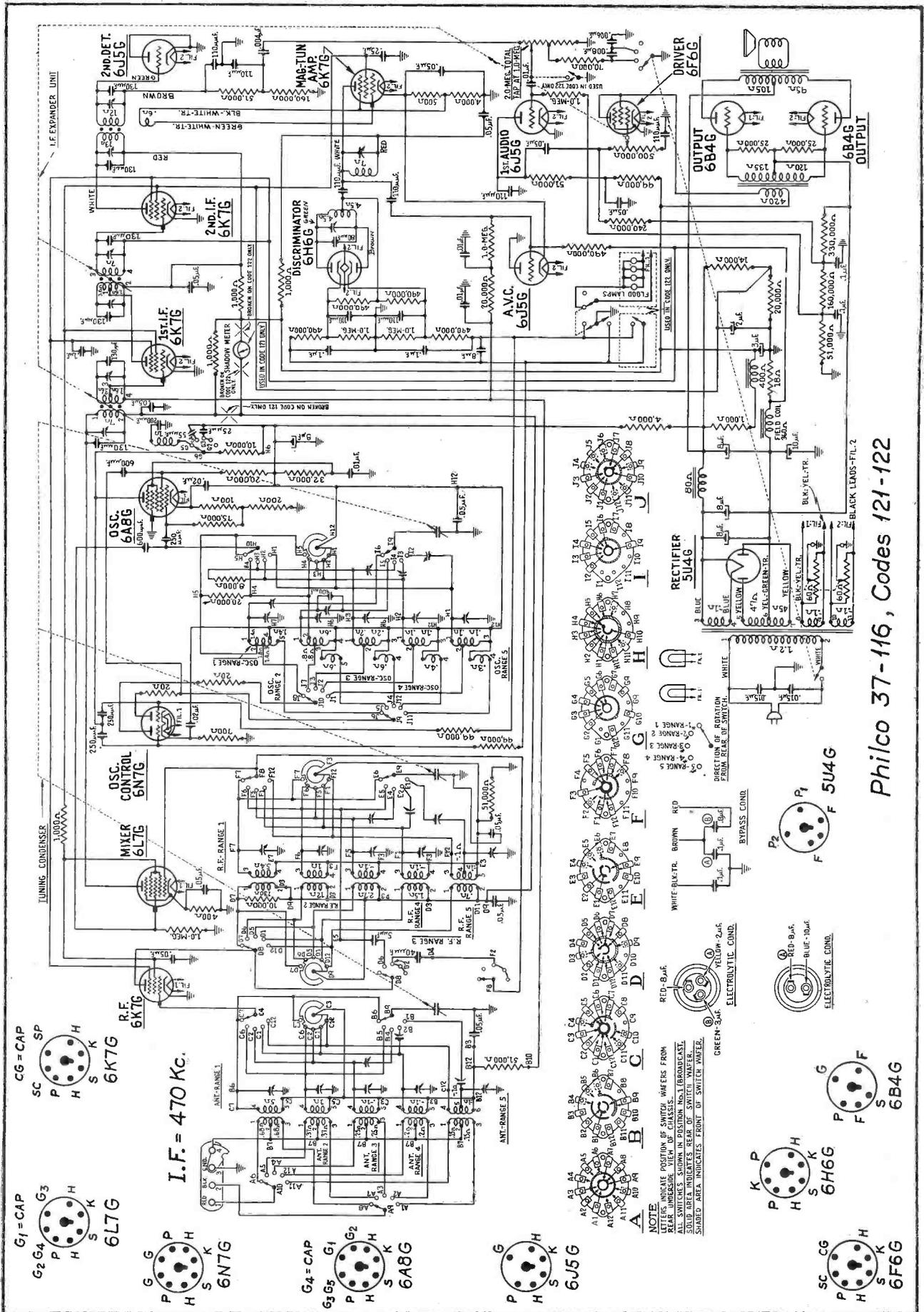

Philco 37-116, Codes 121-122


RIDER

MANUALS

NOW IN SEVEN VOLUMES

Remember:

YOU PAY FOR THEM

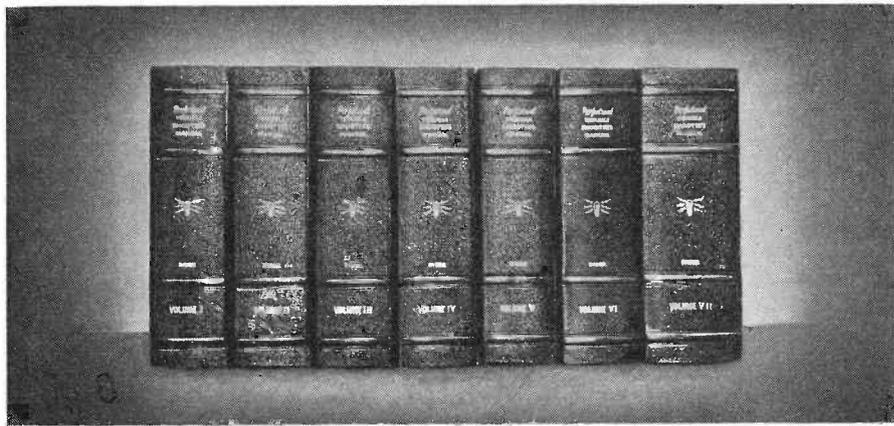

Even if You Don't Have Them!

If you're trying to service today's complicated radios without complete service information—if you're wasting time running to your jobber to use his manuals—if you're taking chances with late deliveries of repair work which might not "stay repaired"—you are paying a high price in time and money for "getting along" without a complete set of Rider Manuals. *It's actually costing you money NOT to have them!*

Be sure you have *all* necessary circuit information **WHEN YOU NEED IT.** Be sure your set of Rider Manuals is *complete*, by ordering any missing volumes from your jobber today.

VOLUME VII JUST OUT

1600 PAGES — \$10.00 — Covering 1936-1937

Volume VI	\$7.50	covering	1935-1936
Volume V	7.50	"	1934-1935
Volume IV	7.50	"	1933-1934
Volume III	7.50	"	1932-1933
Volume II	6.50	"	1931-1932
Volume I	7.50	"	1920-1931

Sold by all good radio jobbers

Changes — changes! That's the history of the superheterodyne circuit. Rider shows you how to analyze the parts of the circuit quickly, to make repairs at a profitable speed.
SERVICING SUPERHETERODYNES
288 pages—
profusely illustrated..... **\$1.00**

THE CATHODE-RAY TUBE AT WORK

Complete, practical and accurate information on cathode-ray tubes, oscillographs, etc.! Now, with the introduction of the new and cheaper Cathode-Ray Tube this development looms even more important than ever before. This is the only book on the subject written especially for the service man.

336 pages — over 450 illustrations **\$2.50**

An Hour a Day with Rider on **AUTOMATIC VOLUME CONTROL.** Vital technical information on all types of AVC. Speeds up your AVC work—makes it more profitable. 96 pages —65 easy to understand illustrations; hard cover **60c**

An Hour a Day with Rider on RESONANCE & ALIGNMENT

A clear explanation of what happens when a circuit is tuned to resonance. The book about which the Service Editor of Radio News said, "Should you experience the least difficulty in assimilating its contents don't blame the book—it's . . . evidence you need it."

96 pages — hard cover — 48 explanatory figures.... **60c**

SERVICING RECEIVERS BY MEANS OF RESISTANCE MEASUREMENTS

Take the guesswork out of servicing by using an ohmmeter in your diagnosis. This book tells you how. This method represents the logical solution to the radio servicing problem and is right in line with the continuity data being furnished by the set manufacturers.

203 pages— 93 illustrations ... **\$1.00**

An Hour a Day with Rider on **D-C VOLTAGE DISTRIBUTION** in Radio Receivers. Explains how it is led through various types of networks to tube elements. 96 pages, hard cover, 69 illustrations **60c**

JOHN F. RIDER, Publisher 1440 Broadway, New York, N. Y., U. S. A.

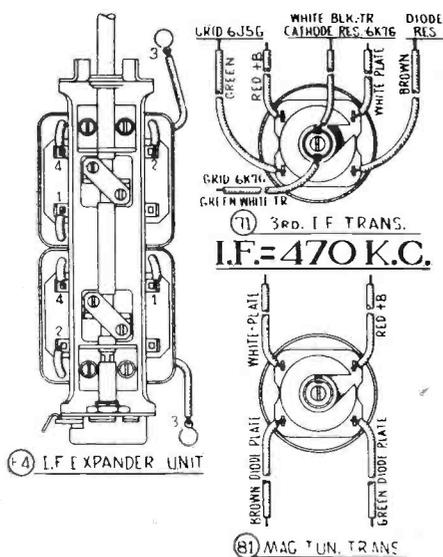


Fig. 3. Philco 37-116 i-f transformer.

a tuning-wand or similar device before making changes.

DIAL CALIBRATION

In order to adjust this receiver correctly the dial must be aligned to track properly with the tuning condenser. To do this proceed as follows:

(1) Loosen the set screws on the shaft coupling of the tuning condenser. Then turn the tuning condenser until the plates are in the maximum capacity position. Now set the glowing beam indicator on the index line at the low-frequency end of the broadcast band. With dial and tuning condenser in this position tighten set screws.

(2) Turn the tuning condenser control until the indicator is on the first division from the index line.

(3) With the dial in this position, loosen the shaft coupling set screws. Then turn the dial until the indicator is again on the index line. Tighten the set screws in this position.

Note: Be careful when turning the dial that the position of the tuning condenser is not disturbed.

I-F ALIGNMENT

(1) Connect the signal generator output lead in series with a 0.1 mfd condenser to the grid of the 6L7G tube, and the ground connection of the output lead to the chassis.

(2) Set the receiver volume control in the maximum position. Turn the fidelity-selectivity control clockwise; magnetic tuning control in the "off" position (counter-clockwise); range switch in position No. 1 (broadcast); tuning condenser to approximately 580 kc, and adjust the signal generator for 470 kc.

(3) Adjust compensators (64B)

first i-f secondary; (64A) first i-f primary; (64D) second i-f secondary; (64C) second i-f primary; (71S) third i-f secondary and (71P) third i-f primary for maximum output.

(4) Turn the fidelity-selectivity control to the expanded position (counter-clockwise). The intermediate-frequency curve is now checked for symmetry as follows: slowly shift the signal generator dial between 460 kc and 480 kc. As the dial is turned two peaks will be indicated on the output meter—one about 465 kc and the other about 475 kc. These peaks should give the same deflection or reading on the output meter. If they are unequal, compensator (71S) must be readjusted slightly to the right or left—depending on which peak gives the lowest reading—until they are equalized.

Each time the compensator is set in another position, rotate the signal generator dial through 460 to 480 kc and note the reading of each peak on the output meter. If the peaks become more equal when compensator (71S) is turned to the left, continue in this direction until they are equal. If they become more unequal turn the compensator to the right. Continue this adjustment in either direction until the peaks equalize.

(5) After adjusting the third i-f transformer, turn the fidelity-selectivity control clockwise (selective position) and adjust the attenuator of the signal generator for maximum output. Now tune the primary compensator (81P) of the magnetic tuning transformer for minimum output.

R-F ALIGNMENT

Tuning range 11.5-18.2 mc

(1) The signal generator output lead with the 0.1-mfd condenser is connected to terminal No. 1 on the aerial input panel (rear of chassis) and the generator ground lead to terminal No. 3. Terminals 2 and 3 must be connected with the shorting link provided on the panel.

(2) Set the magnetic tuning control in the off position, and the fidelity-selectivity control in the extreme clockwise position. Set the range switch in position No. 5 (11.5 to 18.2 mc). Turn the receiver and signal generator dials to 18 mc and adjust the generator attenuator for a readable indication on the output meter. Now adjust compensator (43D) by turning the screw (clockwise) to the maximum capacity position, then slowly turn it counter-clockwise until a second maximum peak is reached on the output meter. The first peak from maximum capacity is the

image signal and the receiver *must not* be adjusted to this signal. On some receivers, however, only one peak will be found, therefore, adjust compensator (43D) to this peak. If the above procedure is correctly performed, the image signal will be found at 17.060 mc by advancing the signal generator input, and turning the receiver dial to this frequency mark on the scale.

(3) Leaving the signal generator and receiver dials at 18 mc the antenna and r-f compensators (7D) and (25D) are now adjusted by connecting a variable condenser, Philco part No. 45-2325 (approximately 0.00041 mfd), across the oscillator compensator (43D) contact (first contact from the left side of the receiver facing rear underside view of the chassis) and ground. Now tune the added condenser until the second harmonic of the receiver oscillator beats against the signal from the generator, resulting in a maximum indication on the output meter. Note: It may be necessary to increase the signal generator output to obtain a signal of sufficient strength for reading on the output meter. Compensators (7D) and (25D) are now adjusted for maximum output. After these adjustments, remove the external condenser and readjust compensator (43D) as given in paragraph 2 above.

(4) Turn the signal generator and receiver dials to 12 mc and adjust compensators (43E), (25E) and (7E) for maximum output.

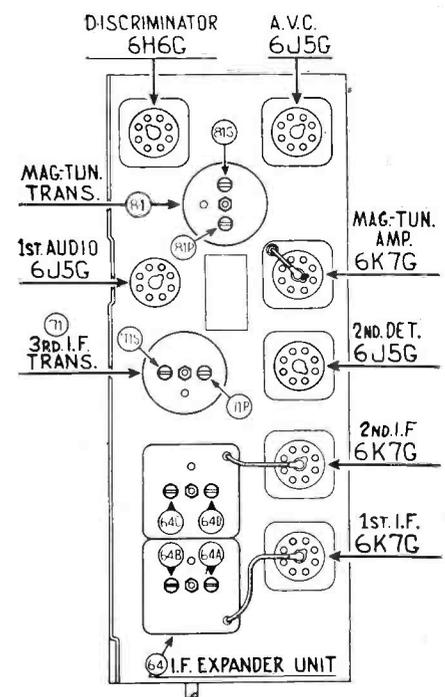


Fig. 4. Philco 37-116 i-f stages.



Model 430

Only
\$18.00

for Model 430
 DIRECT READING
TUBE TESTER

★ Positively checks all type tubes according to data contained in latest recommendation of tube engineers.

RELIABILITY AT LOW COST

- TESTS ALL TYPE TUBES
- HAS LINE VOLTAGE ADJUSTMENT
- HAS LEAKAGE AND SHORT TEST
- USES TRIPLETT DIRECT READING INSTRUMENT
(Good-Bad Scale)

MODEL 430 is an up-to-the-minute 1936-37 Tube Tester. Five flash type sockets provide for all type tubes. The tester operation is very simple and indicates condition of the tube for dealer and customer on Direct Reading GOOD-BAD colored scale of Triplett instrument. Will also test for inter-element shorts and leakages. Complete in attractive, sturdy quartered oak case. Sloping panel of silver and black. Suitable for portable and counter use.

Dealer Price \$18.00

MODEL 431, same as 430 except has Readrite GOOD-BAD meter.

Dealer Price \$14.40

SEE YOUR JOBBER—WRITE FOR CATALOGUE



READRITE METER WORKS
 117 College Dr., Buffalo, Ohio

Without obligation please send me:
 —More information on Readrite Model 430.
 —Literature if interested in

Name
 Address
 City State

(5) Readjust compensator (43D) as given in paragraph 2 above, for maximum output.

(6) Readjust compensators (7D), (25D) and (43D) as given in paragraph 3 above. This readjustment is to correct any variation that the low-frequency compensator may have caused in the high end of this range.

Tuning range (7.35-11.6 mc)

(1) Turn selector switch to range 4. Set the signal generator and receiver dials to 11.0 mc. Now adjust compensator (43B) for maximum output. Check for image at 10.06 mc.

(2) Leaving signal generator and receiver dial turned to 11.0 mc, connect the external variable condenser across the oscillator compensator (43B) contact (third contact from left side of the receiver facing rear underside view of chassis) and ground. Tune the added condenser for maximum output, then adjust compensators (7B) and (25B) for maximum output. Remove the added condenser and adjust (43B) for maximum output.

(3) Turn the signal generator and receiver dials to 7.5 mc and adjust compensators (43C), (25C) and (7C) for maximum output.

(4) Readjust compensator (43B) as given in paragraph 1 above.

(5) Readjust compensators (7B), (25B) and (43B) as given in paragraph 2 above.

Tuning range (4.7 to 7.4 mc)

(1) Turn selector switch to range 3. Set the signal generator and receiver dials for 7.0 mc and adjust compensators (43), (25), and (7) for maximum output.

(2) Rotate the signal generators and receiver dials to 5.0 mc, then adjust compensators (43A), (25A), and (7A) for maximum output.

(3) Readjust compensators (43), (25) and (7) on the 7.0 mc signal.

Tuning Range (1.58 to 4.75 mc)

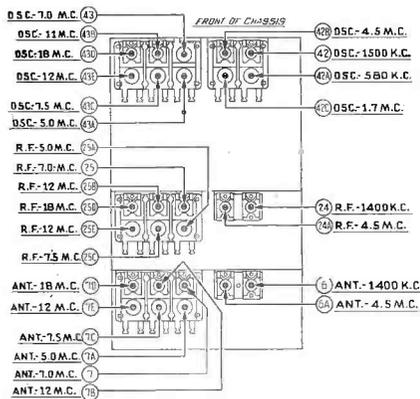


Fig. 5. Philco 37-116 r-f trimmer locations.

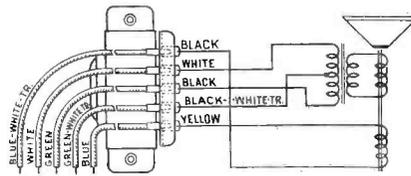


Fig. 6. Philco 37-116 speaker connections.

(1) Turn the selector switch to range 2. Set the signal generator and receiver dials to 4.5 mc. Now adjust compensators (42B), (24A) and (6A) for maximum output.

(2) Rotate the signal generator and receiver dials to 1.7 mc. Compensator (42C) oscillator series is now adjusted for maximum output as follows:

First tune compensator (42C) for maximum output, then vary the tuning condenser of the receiver for maximum output about the 1.7 mc dial mark. Now turn compensator (42C) slightly to the right or left and vary the receiver tuning condenser for maximum output. If the output reading increases, turn compensator (42C) in the same direction a trifle more, and again vary the tuning condenser for maximum output. If the output reading increases, turn compensator (42C) in the same direction a trifle more, and again vary the tuning condenser for maximum output. If the output decreases, set the compensator in the opposite direction. This procedure of first setting the compensator and then varying the tuning condenser is continued until there is no further gain in output reading.

(3) Readjust compensators (42B), (24A) and (6A) for maximum output as given in paragraph 1 above.

Tuning range (530 to 1600 kc)

(1) Set selector switch in range 1. Rotate the signal generator and receiver dial to 1500 kc. Adjust compensators (42), (24) and (6) for maximum output.

(2) Turn the signal generator and receiver dials to 580 kc. Compensator (42A) oscillator series is now adjusted, using the same procedure as given in paragraph 2 under tuning range (1.58 to 4.75 mc). The only difference in the two adjustments is the frequency and compensator used.

(3) Readjust compensator (42) on 1500 kc and compensators (24) and (6) on a 1400 kc signal.

MAGNETIC TUNING ADJUSTMENTS

(1) Leave the selector switch in position 1. Set the fidelity-selectivity control in the selective position (clockwise). Magnetic tuning in the out position. Turn the signal generator and dial to 1000 kc, then adjust the re-

ceiver tuning condenser for maximum output.

Note: It is very important to accurately adjust the receiver tuning condenser, also, adjust the signal generator attenuator to maximum output.

(2) Turn the magnetic tuning control to the on position (clockwise). Compensator (81S) secondary of magnetic tuning transformer is now adjusted for maximum output. If the indicator of the output meter goes off scale, turn the volume control of the receiver toward the minimum position until a readable indication is obtained.

(3) The above adjustment is now checked for accuracy, by turning the magnetic tuning control off. When this is done there should be no change in the tone of the receiver signal. If a change of tone or a hiss develops, it indicates a shift in frequency and the adjustment must be made again.

Majestic 21, 22, 23

Inoperative when tone control is in modified position: Caused by shorted 0.022-mfd condenser in this circuit. This defect is plainly indicated when diagram is inspected. However, it is stated on the diagram that six leads must be unsoldered to remove bottom plate, which work is not necessary to replace this condenser, as it may be replaced by unscrewing the right-hand side chassis plate only.

Howard J. Surbey

Sparton 57, 57-A, 57-B

Hum and oscillation at resonance: The ground connection to the shielding that covers the 75 grid lead often breaks away from its contact at the volume control. Resoldering the connection will eliminate the condition.

William Sollis

Stewart-Warner R-123

Inoperative: Check the 0.1-mfd condenser (No. 24) connected from the 6A7 screen to the chassis for short. Replace with one of higher voltage rating.


Howard J. Surbey

Truetone 80A

Inoperative: Test the 0.1-mfd condenser used to by-pass the plate return of the three type 24 tubes to the ground. This condenser is designated as C-12 on the circuit diagram furnished with the receiver. These receivers are manufactured for the Western Auto Supply.

Howard J. Surbey

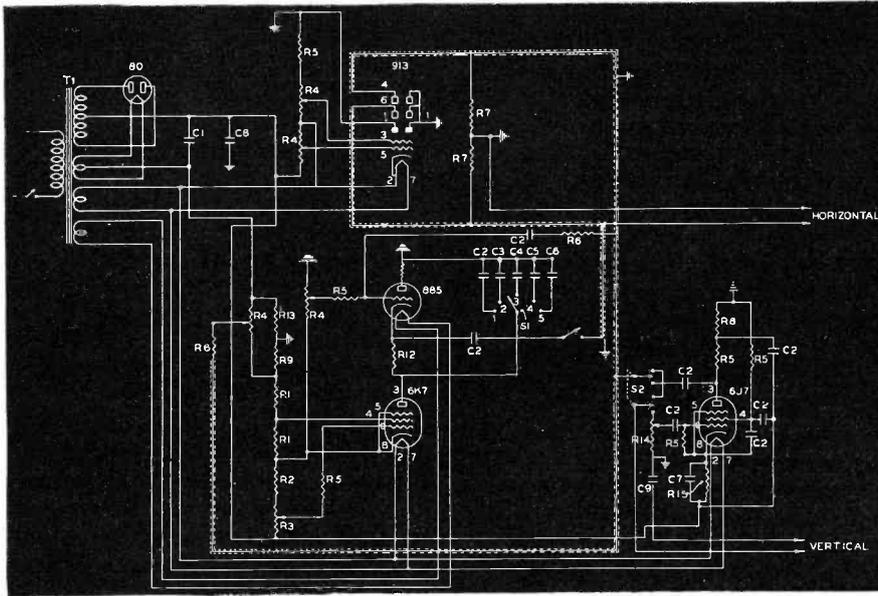The UTC PA913 transformer is the key unit in a *really stable* 913 oscilloscope



Here is an oscilloscope circuit that incorporates all the desirable features of its big brothers in addition to being **UNUSUALLY STABLE**. A typical layout is shown (see picture) . . . of a very compact and serviceable instrument.



FEATURES: Vertical beam centering control; Vertical sweep amplifier with provision for cutting amplifier in or out; Linear sweep with five (5) position switch for selection of sweep frequencies; Linear sweep amplitude control; Fine frequency control; Positive self-locking synchronization circuit which keeps the image locked at any frequency.

PA-913—Pri. 115 A.C. 60 cy. Secondaries up to 450 A.C. 6.3 V 1.2 amp.—2½ V 1.5 amp. —5 V 3 amp. Net price..... \$2.40

PARTS FOR 913 OSCILLOSCOPE

- | | | | |
|-------------------|--------------------------------------|------------------|-------------------------------|
| C-1 8 mfd. filter | C-9 .25 | with switch | R-13 10,000 ohms |
| C-2 .1 400 volt | R-1 30,000 ohms | R-5 ½ meg. | 10 watt |
| C-3 .2 | R-2 750 ohms | R-6 1 meg. | R-14 1 meg. pot. |
| C-4 .005 | R-3 10,000 potentiometer with switch | R-7 2 meg. | R-15 5,000 ohms |
| C-5 .001 | R-4 ½ meg. potentiometer | R-8 ¼ meg. | S-1 Single pole five position |
| C-6 .0005 | | R-9 25,000 ohms | S-2 DPDT |
| C-7 10 mfd. | | R-10 50,000 ohms | T-1 PA 913 |
| C-8 2 mfd. | | R-12 1,000 ohms | |

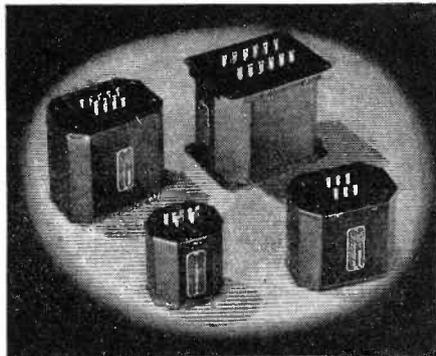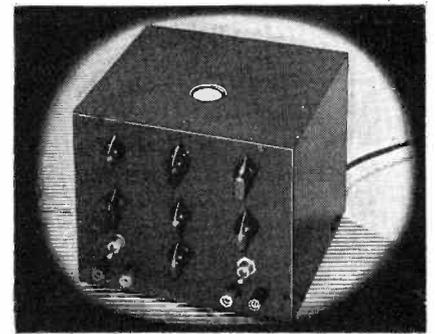Each PA 913 transformer comes with a complete data sheet covering oscilloscopes for service and amateur applications.



... Name your tubes ...

the new UTC PA VARIMATCH transformers will match all of them to a broadcast line or to any voice coil. These transformers never become OBSOLETE. They are sure to match new tubes yet to be announced.

The UTC PVM items are companion units to the UTC VARIMATCH amateur transformers which match any modulator tubes to any RF load.

PVM-1

For all audio tubes up to 10 watts audio. Output 500, 200, 15, 8, 5, 3, 1½ ohms. Some typical tubes single or push pull: 19, 31, 33, 41, 42, 43, 45, 47, 48, 49, 53, 59, 71A, 79, 89, 2A3, 2A5, 6A6, 6F6, 6V6, 25A6, 25L6.

Net Price **\$3.00**

PVM-2

For all audio tubes up to 20 watts audio. Output 500, 200, 16, 8, 5, 3, 1½ ohms. Some typical tubes for single, push pull, or push pull parallel: 19,

PVM-3

31, 33, 41, 42, 43, 45, 46, 47, 48, 49, 50, 52A, 300A, 53, 59, 71A, 79, 89, 841, 843, 1602, 2A3, 2A5, 6A6, 6F6, 6L6, 6V6, 25A6, 25L6.

Net Price **\$4.80**

PVM-4

For all audio tubes up to 50 watts audio. Output 500, 200, 16, 8, 5, 3, 1½ ohms. Some typical tubes in push pull parallel: 42's, 45's, 46's, 50's, 52's, 300A's, 59's, 2A3's, 2A5's, 6F6's. In push pull self or fixed bias: 6L6's, 10's, 807's, 801's.

Net Price **\$7.50**

PVM-5

For all audio tubes up to 100 watts audio. Output 500, 200, 16, 8, 5, 3, 1½ ohms. Some typical tubes push pull parallel: 6L6's, 10's, 807's, 801's, push pull 845's, 800's, etc.

Net Price **\$12.00**

PVM-5

For all audio tubes up to 250 watts audio. Output 500, 200, 16, 8, 5, 3, 1½ ohms. Typical tubes: 211, 242A, 203A, 830B, 852, 838, 4-800's, 4-845's, ZB 120, etc.

Net Price **\$19.50**

UNITED TRANSFORMER CORP.

72 SPRING STREET

NEW YORK, N. Y.

EXPORT DIVISION: 100 VARICK STREET NEW YORK, N. Y. CABLES: "ARLAB"

Auto-Radio . . .

Atwater Kent 556

The model 556 is a single unit auto-radio receiver using 6 metal or metal-glass tubes. One additional speaker may be used. The set consumes approximately 6.8 amperes with one speaker. If an extra speaker is added the additional drain is approximately 1 ampere. This model is arranged for use *without change* with either positive or negative terminal of the car storage battery grounded.

ALIGNMENT PROCEDURE

When adjusting trimmers, keep the volume control and tone control turned full clockwise.

Use an Atwater Kent (No. 42590) i-f coupling unit to couple the signal generator while aligning i-f trimmers.

In order to keep below the avc level, it is necessary to use the weakest possible output from signal generator that will give a reading on a sensitive-output meter.

I-F ALIGNMENT

Turn variable condenser until plates are completely out of mesh.

Connect signal generator (264 kc) to cap of i-f tube by means of the coupling unit. Peak two trimmers on top of T5.

Connect signal generator to cap of first detector tube and peak two trimmers on top of T4.

Repeat adjustments for greater accuracy.

DIAL ADJUSTMENT

With variable condenser fully meshed, the arrow indicator should be adjusted (by means of screw in center of dial lamp opening at rear of tuning unit) to the mark beyond the 550-kc end of dial.

R-F ALIGNMENT

Connect signal generator (1500 kc) to antenna and chassis, using a 200 mmfd fixed condenser in series with the antenna lead. With dial at 1500 kc, peak A3 (oscillator), A2 (first detec-

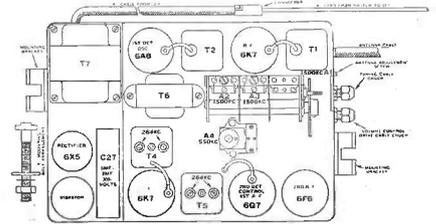


Fig. 2. Tube and trimmer locations.

tor) and A1 (antenna). Use first peak as A3 is screwed in from a loose position.

With signal generator at 550 kc, peak tracking condenser A4 while rocking tuning control slightly around the 550-kc mark.

Repeat adjustments at 1500 and 550 kc if necessary.

Crosley A-366

The Crosley model A-366 is a six-tube superheterodyne receiver designed for operation with a header speaker, an under cowl speaker or both. The power supply unit is an integral part of the chassis and is completely shielded from the remainder of the receiver.

ALIGNMENT PROCEDURE

All the circuits in this receiver are very accurately adjusted at the factory


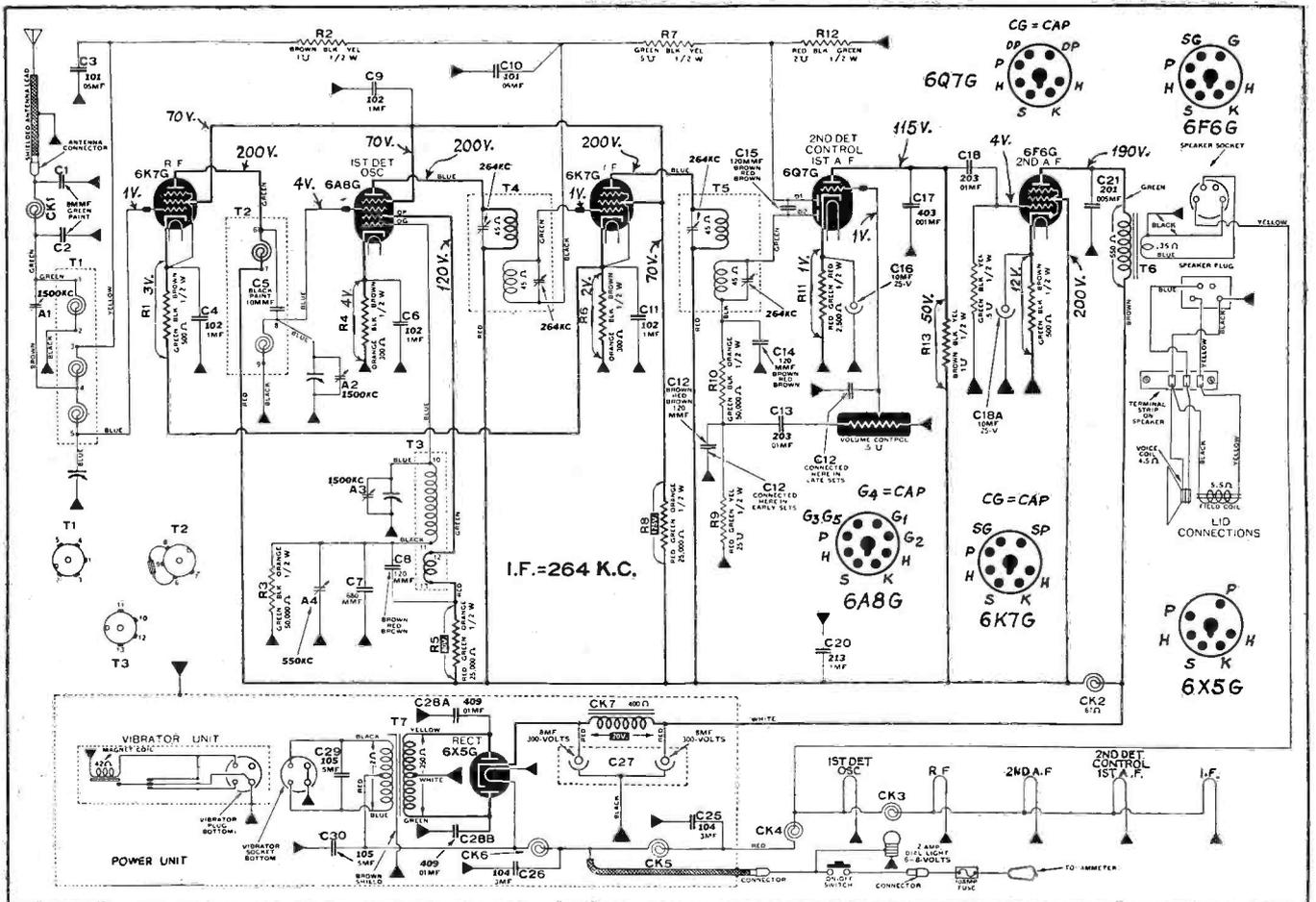


Fig. 1. Atwater Kent 556 circuit diagram.

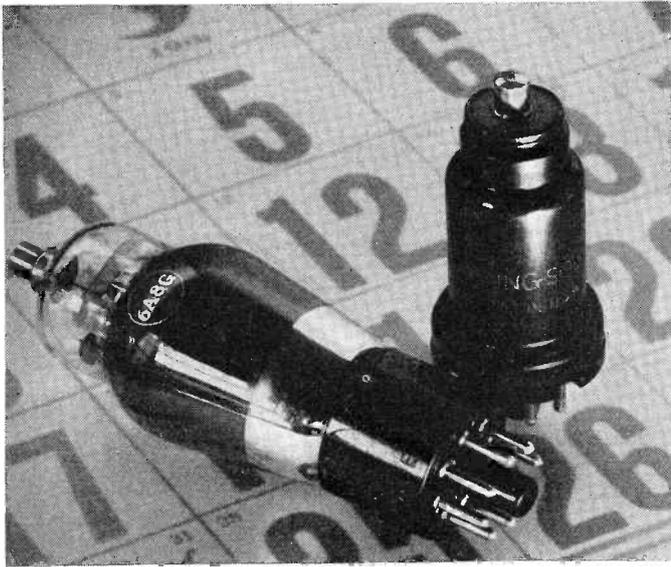

for 1937

SELL TUBES ON
"Velvet"

In the Tung-Sol consignment plan there's no such thing as tied-up capital. A stock of Tung-Sol radio tubes on your shelves means "velvet" sales. You pay only for tubes sold. Orders — not cash investment — keep your stock replenished.


Desirable locations are still open for independent service organizations which can qualify. Write for the name of your nearest Tung-Sol tube wholesaler today.

TUNG-SOL
Tone-flow radio Tubes

TUNG-SOL LAMP WORKS, INC.
Radio Tube Division

Sales Offices: Atlanta, Boston, Charlotte, Chicago, Dallas, Detroit, Kansas City, Los Angeles, New York. General Office: Newark, N.J.

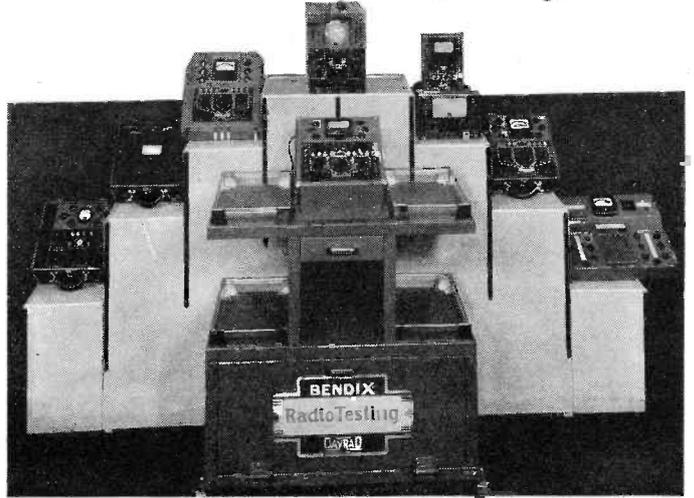*The less you guess
the more you profit!*



The BENDIX-DAYRAD Complete Line embraces EVERY needed type of Radio Test Equipment

PICTURED here are the biggest little profit-builders in existence for any radio service organization. Bendix-DayRad builds and guarantees them. Reading "from left to right," in the rear row, they are:

The Bendix-DayRad Portable Tube Tester, the Series 58 Radio Set Tester, the Series 22C Counter-type Tube Tester, the new Series 65 Cathode Ray Oscillograph for circuit-balancing and general set alignment, the Series 57 Portable Mult-O-Meter for test and analysis of auto and household radio sets, the Series 36-A All Wave Signal Generator (underneath Mult-O-Meter), the Series 20-C Portable Tube Tester which will test many transmitting tubes as well as receiver tubes, and at the extreme right, the Series 115 Auto Radio Vibrator Tester. On the testing stand in front is the new Series 200 Combination Testing Unit.

To list here all the precision tests this complete line of equipment will make would be impossible. Why not send the coupon below and get the new Bendix-DayRad descriptive catalog? Then choose the particular Bendix-DayRad units that best fit your needs.

Remember, on the basis of time saved and good will gained, "The less you guess the more you profit."

BENDIX
DAYRAD

LOW PRICES . . . SMALL DOWN PAYMENT

— SEND COUPON TODAY! —

BENDIX PRODUCTS CORPORATION

(Subsidiary of Bendix Aviation Corporation)
401 Bendix Drive, Dept. 32, South Bend, Ind.

Send me your new catalog of Bendix DayRad Radio Service Instruments.

Name

Street

City State

My Jobber's Name

WAIT A MINUTE . . .

LET'S GET THIS
STRAIGHT!



This is a No. 771—4½-volt Radio "C" Battery. It contains cells compounded especially for "C" battery work. This makes its capacity bear the correct relation to "B" battery capacity. This means that on modern battery receivers, practically all of which bleed the "C" Battery during periods of operation, the "C" voltage goes down in step with the "B" voltage. This preserves the ideal relationship between grid and plate voltage for best receiver performance throughout the entire life of the batteries. The No. 771 Battery *should never be used for other than "C" battery purposes.*



This is a No. 761—4½-volt *General Purpose* Battery. The size and composition of the cells in this battery make it suitable for such purposes as filament current supply for two 2-volt tubes in series, microphone battery, relay battery, and other uses where the No. 771—4½-volt Radio "C" Battery is not recommended.

NATIONAL CARBON COMPANY, INC.

General Offices: New York City
Branches: San Francisco, Chicago

Unit of Union Carbide  and Carbon Corporation

The word "EVEREADY" is the trade-mark of National Carbon Co., Inc.

THE ANSWER
TO A SERVICEMAN'S
PRAYERS...AND PROBLEMS



● Sylvania's famous Technical Manual is right up to the minute with the newest developments in radio . . . answers questions, solves problems, *saves* time and money! And it costs only 15¢!

This gives you an idea what it contains:

184 pages bound in a neat, handy size that slips right into your pocket.

Lists 193 tube types with important circuit application information on each.

Tells all about glass, metal and "G" type tubes, including those for Majestic receivers. Also full information on SYLVANIA "Ballast Tubes."

You'll need this Manual on your very next job! So *clip the coupon* and mail it today.

Hygrade Sylvania Corporation, makers of Sylvania Radio Tubes and Hygrade Lamps. Factories at Emporium, Pa.; Salem, Mass.; and St. Mary's, Pa.

SYLVANIA

THE SET-TESTED RADIO TUBE

HYGRADE SYLVANIA CORPORATION
Emporium, Pa.

S-17

Please send me the Sylvania Technical Manual. I enclose 15¢ in stamps or coin.

Name

Address

City State

ON THE JOB . . .

Individual Batteries for Philco Sets

Many owners of Philco battery receivers have desired to use individual A, B, and C batteries but have had no information to guide them in making the changeover.

THE "AIR CELL"

The earlier models were equipped with either ballast tube for use with a 3-volt dry A battery, or with a circuit-closing plug in the ballast tube socket for use with a 2-volt storage battery. Later models have neither ballast tube nor ballast tube socket. In either case no provision is made so that the owner can use an "Air Cell" A battery. While some owners have used this battery with the ballast tube, this is not recommended. In the first place, the ballast tube is designed to regulate the voltage of a 3-volt dry A battery to suit 2-volt tube filaments, whereas the "Air Cell"

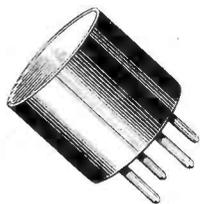


Fig. 1. Conversion resistor plug.

is a 2.5-volt battery. Furthermore, its voltage is so nearly constant as to require no regulation, so that a fixed resistance in the filament circuit is all that is required.

CONVERSION RESISTORS

These fixed resistors are available in the form of a plug and are known as conversion resistor plugs. They are made by most of the resistor manufacturers. There are seven types, four of which are used with Philco sets. A data sheet, covering the use of conversion resistor plugs, is available.

Some of the later models of Philco battery receivers have no provision for a ballast tube. In these sets the battery voltage may be reduced by the attachment of a fixed resistor of the proper value in series with the connection to either of the terminals of the battery. These resistors can be purchased already made up. Five ranges of filament current drain are covered, three of which are used on Philco receivers.

THE B AND C BATTERY ADAPTER

Philco battery receivers are equipped with a B and C battery cable which terminates in a single seven- or eight-prong plug. This plug is designed to fit into the socket of a combination B

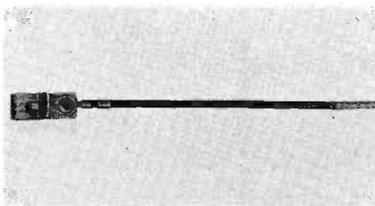


Fig. 2. Eveready "Air Cell" resistor.

and C battery usually called the "BC" pack. Where the set owner prefers the economy of individual plug-in B and C batteries the changeover may be accomplished through the use of a B and C battery adapter. This adapter consists of a cable having either a seven- or an eight-prong socket on one end and suitable battery plugs on the other. The plug on the receiver cable is connected to the adapter socket, and the individual battery plugs connect into the sockets of standard types of B and C batteries.

For use with table models, where the B and C batteries would ordinarily be exposed, a battery container can be obtained. This container in external appearance is much the same as the "BC" pack, but enables the use and replacement of the B or C batteries in individual sections.

CONVERTING PARTICULAR MODELS

For the conversion of each model of Philco battery receiver proceed as follows:

Philco 34 and 34-A: Use type 7 conversion resistor plug in the ballast tube socket. Use a No. SA-850 "Air Cell" A battery. Attach a B and C battery adapter No. 5394-8 to the battery cable. Use three 45-volt B batteries and three 4½-volt C batteries. A battery container may be used to house the batteries for the table models.

Philco 38 and 38-A with type 15 converter tube: An SA-850 may also be used with this model through the use of a type 7 conversion plug in the ballast tube socket. However, a type A-

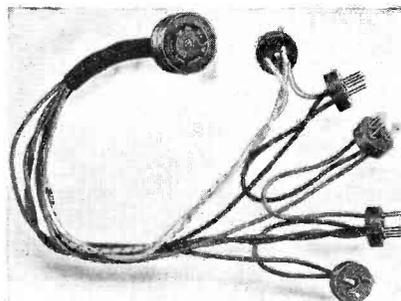


Fig. 3. B and C battery adapter.

600 "Air Cell" may be used if the dial lamp is removed and a type 4 conversion resistor plug is inserted in the ballast socket. Adapter No. 5394-7 is necessary in order to convert to the use of three 45-volt B batteries and two 4½-volt C batteries. A battery container may also be used with table models if desired.

Philco 38 and 38-A with type 1A6 converter tube: Use a type 5 conversion resistor plug in the ballast tube socket with a type A-600. Attach adapter No. 5394-7 to the battery cable. Use three 45-volt B and two 4½-volt C batteries.

Philco 38 and 38-A with type 1C6



Fig. 4. Eveready B-C battery container.

converter tube: Use a type 6 conversion resistor plug in the ballast tube socket with a type A-600. Attach adapter 5394-7 to the battery cable. Use three 45-volt B and two 4½-volt C batteries.

Philco 39 and 39-A: Use a type 7 conversion resistor plug in the ballast tube socket with a SA-850, or remove the dial lamp and use a type 4 plug and an A-600. Adapter No. 5394-8 should be used to accommodate three 45-volt B and three 4½-volt C batteries.

Philco 623 and 623-A: Use a type 7 conversion plug with No. SA-850, or remove the dial light and use a type 6 plug and a No. A-600. Attach adapter 5394-7 to the cable for use with three 45-volt B and two 4½-volt C batteries.

Philco 37-33: Use an "Air Cell" resistor No. 540-560 connected to either terminal of a No. A-600. Adapter 5394-7 accommodates three individual 45-volt batteries and two 4½-volt C batteries.

Philco 37-38: Use resistor 740 connected to either terminal of a No. SA-850, or use resistor 660-680 and battery A-600 and replace the 120-ma dial lamp with a 60-ma light. Adapter

*The material for this article was supplied by the National Carbon Co., Inc.




New OHMITE POWER LINE CHOKES

*"Just the thing
to cure R. F.
Interference"*

says Bill Fixit

"Many's the time I've wished for a unit like this to keep interference from a near-by transmitter out of a customer's receiver."

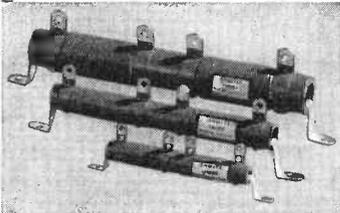Z-20, 5 ampere chokes may be installed at the receiver with the usual by-pass condensers to serve as a filter for high frequency currents. Z-21 and Z-22, 10 and 20 ampere chokes are suitable for installation at transmitters or other high frequency apparatus to prevent R. F. Currents from going out over the power line. For further information ask your jobber, or write for Bulletin 105—FREE.




OHMITE

Manufacturing Co.

4827 Flournoy St
Chicago, Ill.

Manufacturers of Resistors,
Rheostats and Tapswitches

Cashing in on HOME RADIO WIRING

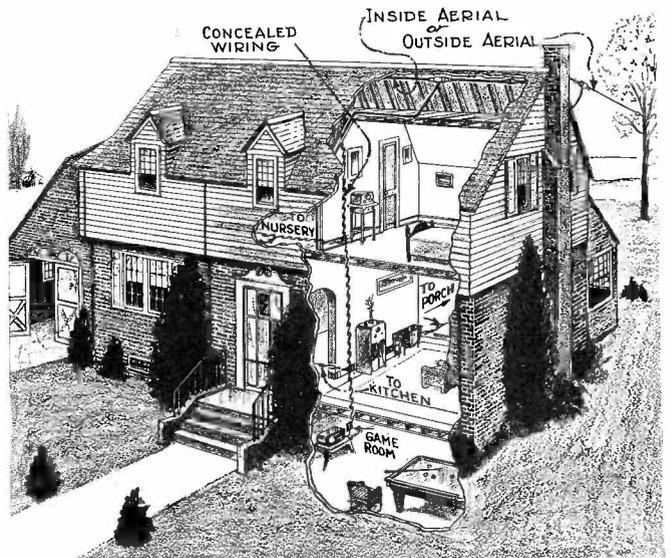

THE one-set home is passing. Two or more sets are the order of the day in the average household. And that's why the TACO Master Antenna System—one aerial serving as many as 25 sets through convenient outlets—is so popular in modern private homes as well as largest apartment houses. Just consider these features:

★



A purely aerial system — no master amplifiers, central radio set, tubes or other troublesome and costly equipment.

★


Positively foolproof—once properly installed, it functions for years without attention.

★

Exposed wiring coupler mounted on inside window sill or baseboard.

Available in simple kit form—Master Foundation Unit for complete aerial, and as many couplers as required outlets.

★

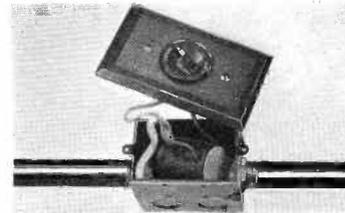

Simple exposed wiring for existing apartment houses; concealed BX or conduit for new apartment houses; or knob-and-tube for private residences.

★

Concealed wiring coupler for conduit wiring.

Clears roofs and walls. Provides ideal reception. Sells more and better sets. Builds your business and profits.

★

FREE MANUAL! Describes system in detail for apartment houses and private residences. Tells how to estimate jobs, how to install, how to test, etc. Write for your *free copy* TODAY!

TACO

TECHNICAL APPLIANCE CORPORATION

Pioneers in Noiseless Antenna Systems

17 EAST 16TH STREET

NEW YORK CITY

SANDY THE SERVICEMAN

Says:

NOW is the time to buy **WHOLESALE!** I'm orderin' enough parrrts and tubes from my **WHOLESALE CATALOG** to take care of my purchasin' for the next three months! I know that prices are advancin' in every line. So I'll save many dollars in 1937 by usin' my **BIG 156-PAGE CATALOG.**

And I get everything I need . . . from a screen grid clip to a 24-tube superhet phono-combination, from **WHOLESALE.** They handle all the national brands y'know. Another thing I like is the **QUICK and EFFICIENT** way they take care of my orders! Within **TWENTY-FOUR HOURS!** Aye, lads . . . that's "**WHOLESALE**" SERVICE.

Fall in line behind Sandy . . . and **BUY "WHOLESALE!"** NOW! Hoot Mon! 'Tis smarrt r'be thrirrity!

Big 156-page Catalog No. 65-5A7 FREE. Over 10,000 Real Bargains! Send for your copy today.

**SAVE MONEY BY
BUYING THE
"WHOLESALE"
WAY**

**BIG
156 PAGE
CATALOG
FREE**

SEND FOR YOUR
COPY TODAY

OVER 10,000 REAL BARGAINS!

WHOLESALE RADIO SERVICE CO. INC.

NEW YORK, N. Y. • CHICAGO, ILL. • ATLANTA, GA.
100 SIXTH AVENUE 901 W. JACKSON BLVD. 430 W. PEACHTREE ST., N. W.

5394-7 connected to the battery cable will accommodate three 45-volt B and two 4½-volt C batteries in individual sections.

Philco 37-623: Same procedure as for the model 37-38.

Philco 37-643: Use resistor No. 660-680 connected to either terminal of a No. A-600. Attach an adapter No. 5394-7 to the cable and use three 45-volt B and two 4½-volt C batteries.

Reducing Code and Image Interference

The "image" of a station appears at a point on the dial of twice the i-f peak subtracted from the fundamental frequency of the station causing the "image" to appear. For example, twice 465 kc is 930 kc, and this subtracted from 9,530 kc (the fundamental frequency of W2XAF) gives a reading of 8600 kc on the dial, if the receiver is accurately calibrated and aligned.

The amount of "image response" in a superheterodyne receiver depends upon a number of factors. The inherent design, the number of radio-frequency stages used ahead of the first detector, the amount of shielding used around the oscillator and intermediate amplifier tubes and circuits, and the power (indirectly) of the transmitting station, are among the few of these factors.

Several complaints have been recently received from listeners to International Broadcast Station W2XAF regarding the subject of code or telephone radio stations operating on or near the assigned frequency of W2XAF or 9530 kilocycles.

Upon investigation, however, it was found that the stations mentioned as the cause of the interference were not operating within this channel assigned internationally for international broadcast stations, namely, from 9500 to 9600 kilocycles, but were operating in full accordance with and abiding by the international agreements on frequencies between 10,440 to 10,460 kilocycles which lie within the 9600 to 11,000 kilocycle band assigned for commercial fixed services.

Interference on W2XAF from such stations in a superheterodyne receiver is generally due to the "image response" of the receiver itself when tuned to a desired signal. If the desired station is operating on 9530 kilocycles (W2XAF), the oscillator, in many modern receivers, operates at a higher frequency, namely, 9530 kc plus the intermediate frequency (usually about 460 kc or 9990

kc.) If the r-f selectivity for frequency conversion is inadequate, an incoming signal above the oscillator frequency at 9990 kc plus 460 kc, or 10,450 kc, may produce an audible beat note with the desired signal.

The image response ratio for a receiver without a radio-frequency amplifier preceding the converter averages about 4 at 10,000 kc. This means that the image signal would have to be 4 times as strong as the normal desired signal to produce the same audio output from the receiver. With a r-f amplifier preceding the converter, the image response ratio increases to about 140 at the same frequency in typical all-wave receivers. An additional r-f amplifier would increase the image response ratio to about 5000. Therefore, one or more r-f stages before the converter adds radio-frequency selectivity to discriminate against a signal at the image frequency. In addition, increased sensitivity also results and this may be desirable for improving the signal-to-noise ratio in a receiver not having an r-f amplifier.

A tuned preselector, added for the high-frequency band used, should reduce the interfering signal by a factor of 35. Adding such a device requires an additional tuning control.

Shifting the intermediate frequency about 10 kilocycles either way will eliminate interference only from a particular signal, and requires careful re-alignment of all circuits of the receiver to hold substantially the same scale calibration. This change may be made by competent Service Men who have the necessary instruments and equipment.

When the intermediate frequency is shifted 10 kilocycles, the image frequency is shifted 20 kilocycles. This should be sufficient except for very high speed keying of the interfering signal. It is important that the intermediate frequency is not shifted too much, as this may seriously affect the tracking of the r-f and oscillator tuned circuits.

Probably the simplest method for reducing image frequency interference is

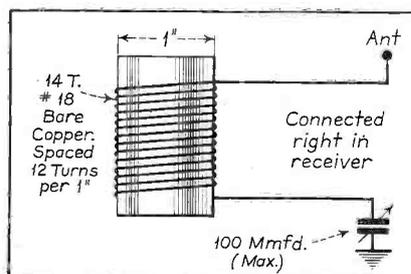


Fig. 1. Series wave trap.

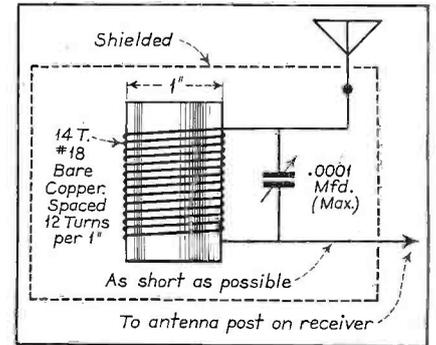


Fig. 2. Shunt wave trap.

to add a wave trap in the antenna circuit. This will be fairly effective if the intermediate frequency is above 450 kilocycles. The trap may consist of a good quality midget variable air condenser having a maximum capacitance of 100 micromicrofarads, and an inductance of about 4.5 microhenries. The inductance should be of the "low-loss" type. It has been found that a 1-inch diameter thin bakelite threaded form (12 turns-per-inch) wound with 14 turns of No. 18 B & S bare copper wire to be about right for tuning out interfering signals from 7000 to 18,000 kc. Depending upon the antenna used and receiver coil constants, the trap may be connected with the coil and condenser in series from the antenna post to the chassis, or the coil and condenser may be connected in parallel. This shunt circuit is then connected in series with the antenna load.


In either case, it is desirable to shield the coil and condenser, and if a midget air condenser is used, the entire trap may easily be mounted in a can such as used to shield the intermediate-frequency coils. For best results the trap should be mounted very close to the antenna terminal using short leads, in order to prevent undesired signal pickup in the lead extending from the trap to the antenna post.

The trap may be adjusted by tuning in the desired signal on the receiver and adjusting the midget trap condenser for minimum interference from a station on the image frequency. Or, the interfering station may be tuned in at two times the intermediate frequency above the desired signal and then adjust the trap tuning for minimum response. A slight decrease in the strength of the desired signal may be found when the trap is tuned to the image, depending upon the losses in the wave trap coil.

FACTORY CAPACITY

Increased
35%

RAYTHEON
TRADE MARK

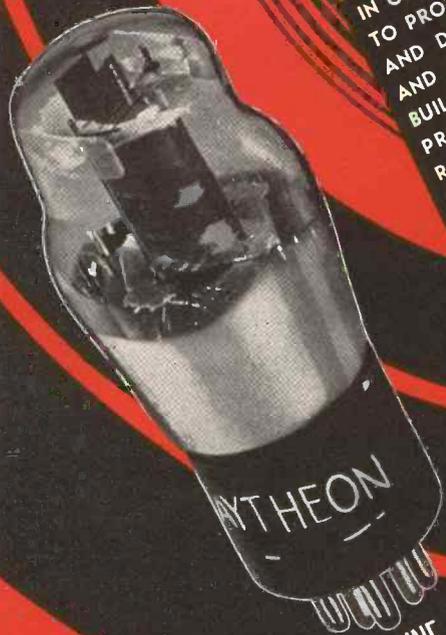

IN ORDER TO TAKE CARE OF THE CONSTANTLY INCREASING DEMAND AND TO PROTECT THE TREMENDOUSLY GROWING MANUFACTURERS', JOBBERS' AND DEALERS' REQUIREMENTS FOR RAYTHEON TUBES, NEW EQUIPMENT AND NEW PRODUCTION MACHINERY HAVE BEEN INSTALLED IN A NEW BUILDING, GIVING AN ADDITIONAL UNIT WHICH INCREASES RAYTHEON'S PRODUCTION CAPACITY BY 35%! WITH THESE INCREASED FACILITIES, EVEN DURING THE SEASON OF PEAK DEMAND! RAYTHEON GUARANTEES CONTINUED PROMPTNESS TO ALL ITS CUSTOMERS MEETING THE EXACTING REQUIREMENTS OF LEADING SET ENGINEERS WHO SPECIFY RAYTHEON TUBES, INCREASINGLY PROTECT JOBBERS AND DEALERS WHO HANDLE THE RAYTHEON LINE AND GUARANTEE THE QUALITY AND SALABILITY OF RAYTHEON'S PRODUCTS. LICENSED SET MANUFACTURERS EQUIP THEIR SETS WITH RAYTHEON TUBES BECAUSE THE NAME RAYTHEON INSURES TRADE AND CONSUMER QUALITY APPEAL, AND HIGHER COMPARATIVE SET UNIT PRICES WITH LESS SALES RESISTANCE. NO WONDER RAYTHEON TUBES ARE USED AND DEMANDED BY ALL LEADING RADIO PARTS DEALERS AND SERVICEMEN FOR GREATER TUBE PROFITS.

THE MOST COMPLETE LINE—ALL TYPES OF GLASS, OCTAL BASE, METAL AND AMATEUR TRANSMITTER TUBES
RAYTHEON PRODUCTION CORPORATION
420 Lexington Ave., New York, N.Y.
445 Lake Shore Drive, Chicago, Ill.
555 Howard St., San Francisco, Cal.
415 Peachtree St., N. E., Atlanta, Ga.
55 Chapel Street, Newton, Mass.

TEST EQUIPMENT...

A-C BRIDGE MEASUREMENTS IN SERVICE PROCEDURE

By GLENN H. BROWNING*

WITH the increasing complexity of radio servicing, the tools of the Service Man have become more and more those of the laboratory technician and engineer. In 1934 and '35, the popularization of the oscilloscope was definitely indicative of this tendency. Today the Service Man is beginning to appreciate the utility of the a-c bridge—particularly in capacity measurements.

The superiority of the bridge over the conventional forms of capacity meters are the wide range (10 micromicrofarads to 100 farads in the bridge to be described), and the highly significant advantage of power-factor determination. In the case of capacity meters the determination of capacity is made by means of the equivalent impedance of a condenser without considering its power factor with the result that if the power factor is very high the capacity as indicated on the meter is incorrect. In the past, power factor has been pretty much the concern of the design engi-

neer, despite the fact that considerations involving power factor have been responsible for baffling service problems (such as apparently incurable loss of sensitivity), impermanent and otherwise unsatisfactory repairs. This has been partially due to the fact that the importance of power factor has not been appreciated. Its treatment has been largely neglected in service literature, and in engineering texts it has been usually considered in terms of phase angle—terms that have little meaning to the Service Man.

POWER FACTOR


The power factor of a capacitor (which may be a conventional condenser, or represented by the capacity between twisted leads, or between the shield and the wire in a shielded cable) is pretty much just what the term implies. In charging, a certain amount of electrical power is stored in a condenser. In a perfect condenser all of this power would be returned on discharge. Unfortunately there are no per-

fect condensers, and the power factor is an index of the amount of loss. In the perfect condenser the power factor would be zero—i.e., there would be no loss.

The power factor of a condenser is really a measurement of the power loss in condensers of fixed size; more precisely, it is the energy loss at a given voltage per unit capacity. Naturally if the condenser has a large value—for instance, 2 mfd—there is more energy loss than there would be in the same type of condenser whose capacity was only 0.2 mfd. However, the power factor of these two condensers would be the same since power factor takes into account the size of the condensers as well as the energy loss (watts loss). In paper or mica condensers the power factor of a good condenser is extremely low, ranging from about one one-hundredth of one percent power factor in the case of a mica condenser to one-half of one percent power factor in the case of paper condensers. The increase in power factor of a condenser of the paper type with age indicates, in all probability, deterioration due to the presence of moisture, consequently rising power factors in this type of condenser indicate that failure is imminent. From a Service Man's standpoint this indication of failure in a condenser before it actually takes place is extremely valuable, for it forestalls a repeat repair job for which the Service Man may have difficulty in collecting.

The power factor of electrolytic condensers is, of course, very much higher than paper, mica, or similar materials, for two reasons: first, the aluminum oxide film which makes up the dielectric in the electrolytic condenser has a higher power factor than either mica or paper; second, the electrolyte which is in contact with the negative terminal of the condenser may have considerable resistivity. Any current flowing in and out of the condenser must pass through this electrolyte and as a consequence the energy dissipated per unit capacity is high. As has been said, increasing power factor in a paper condenser foretells that the condenser is deteriorating. This is not in general true with electrolytic condensers whose normal power-factor range is from 4 to 20 percent. If the Service Man finds a filter condenser whose power factor is less than 20 percent measured at 60 cycles (the 60-cycle and 120-cycle measurements are very nearly the same) he will find that the filtering efficiency is not a great deal impaired. However, condensers which have power factors over 20 percent will show a marked deficiency in filter circuits.

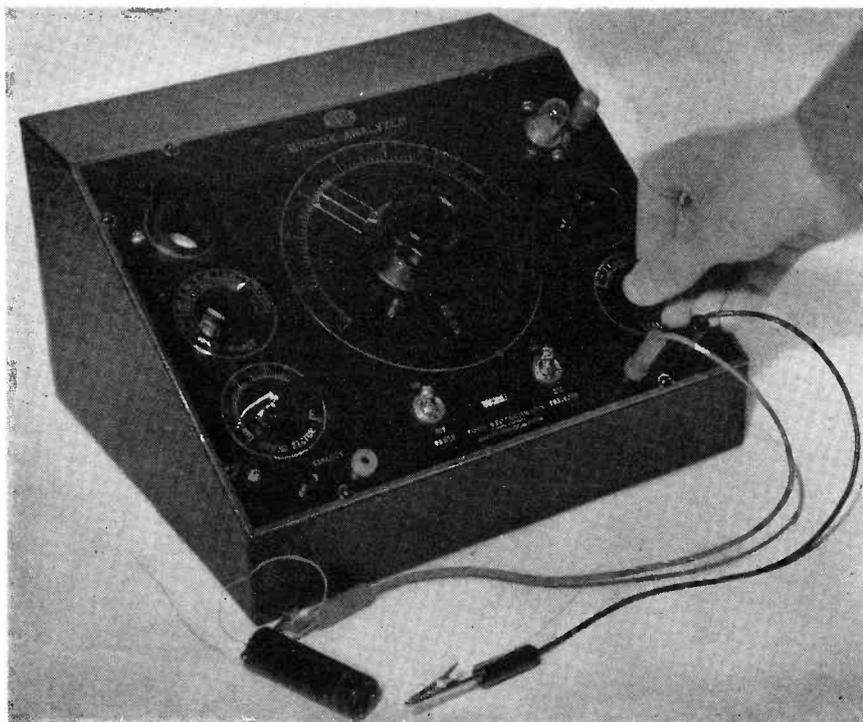Probably the simplest electrical circuit for understanding power factor is



Tobe a-c bridge-analyzer.

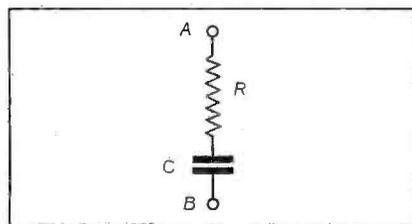


Fig. 1.

that shown in Fig. 1, where R is a resistance inherent in the condenser C. A and B are considered as the condenser terminals. Obviously not all of the energy impressed across the terminals of this condenser upon charge will be returned on discharge as there will be a loss in the resistor proportional to the square of the charging current. Referring to Fig. 1, the power factor of the condenser will be equal to

$$\text{p.f.} = \frac{R}{\sqrt{R^2 + \frac{1}{C^2\omega^2}}}$$

where R is the equivalent series resistance of the condenser whose capacity is C and where ω is 2π times the frequency. The above equation, however, reduces to $RC\omega$ for practical purposes in cases where the power factor is less than 10 percent. Of course, for mathematical purposes the circuit shown in Fig. 1 may be reduced to a condenser which is practically perfect (i.e., has no loss) in parallel with a resistance R_p in which case the power factor of the condenser may be expressed as

$$\frac{1}{\sqrt{1 + R_p^2 C^2 \omega^2}}$$

where C is the capacity of the condenser as before, R is the equivalent parallel resistance, and ω is 2π times the frequency.

An inspection of Fig. 2 would indicate that a d-c measurement made on R_p would be sufficient to determine the power factor of the condenser. However, such is not the case, for in a condenser made up of a thick dielectric as shown in Fig. 3 where pockets of moisture were present, the d-c resistance of the condenser might be practically infinite while the power factor of the condenser might be very appreciable. The reason for this is that every time the condenser is charged up by an alternating voltage there is energy dissipated due to the resistance present in the moisture pockets. As a consequence, Fig. 1 actually gives a very much clearer picture of what is meant by power factor.

It might be said in passing that if the d-c leakage of a condenser is high (i.e., the equivalent parallel resistance of the condenser is low) that the power factor is always higher than normal. However, the reverse is not true—i.e., just because the power factor of a condenser is high does not necessarily mean that the d-c leakage is high.

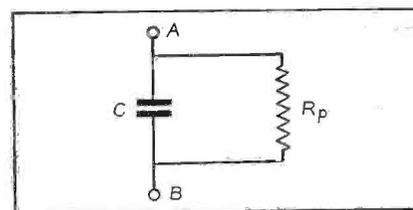


Fig. 2.

THE A-C BRIDGE

The a-c bridge gives the Service Man a tool which enables him to not only measure the capacity of a condenser but also determine its power factor. Combined with the capacity bridge a d-c analyzer for determining leakage values up to more than 1400 megohms

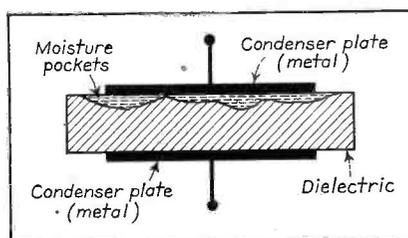


Fig. 3.

is included in the analyzer shown in Fig. 4. It will be noted that the bridge is of a conventional type with the 6G5 tube as the null indicator. The 6G5 is a variable-mu electron-ray tube which, when no voltage is impressed on the grid, has a dark shadow angle of approximately 90 degrees. It makes an excellent null indicator, for when an a-c voltage is impressed on the grid the shadow angle is reduced.

An amplifier consisting of a 6C6 tube

is employed ahead of the 6G5 which insures obtaining adequate sensitivity over the entire range of capacity and resistance measurements. A considerable amount of sensitivity is required when the power factor of a condenser is to be determined with accuracy. The capacity range of the bridge is from 10 mmfd to 100 farads while the power-factor range is from 0 to 50 percent. A switch is incorporated so that the standard condenser used as one arm of the bridge may be switched to a standard resistance in which case the bridge measures the values of resistors from 0.1 ohm to 1 megohm. Both the resistance and the capacity measurements are made at 60 cycles. A decade range switch which is used as a multiplier is incorporated so that a linear scale calibrated from 0.1 to 1.0 is used for the balance determination. This is an important feature contributing to the accuracy and ease of operation of the instrument, for there is no bunching of the capacity or resistance readings at one end of the dial. Further improvement in accuracy results from the use of the decade switch which provides a

(Continued on page 52)


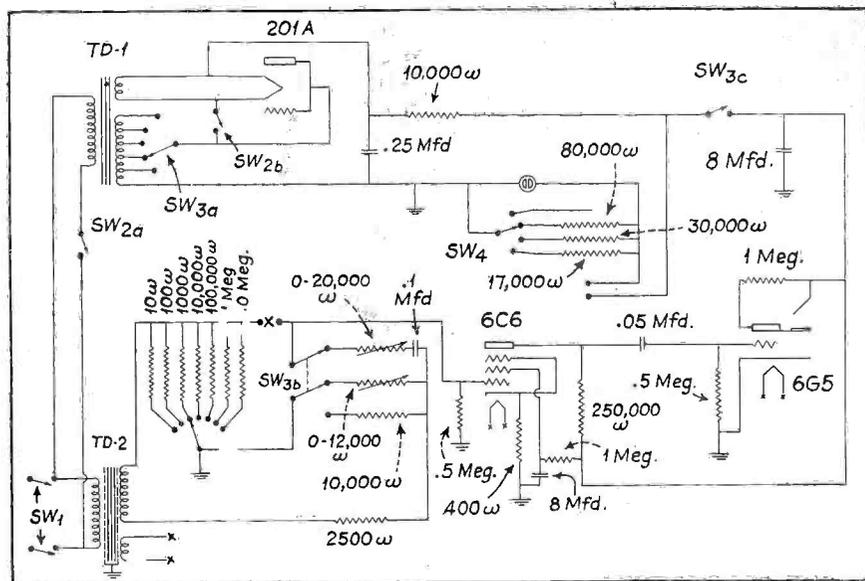


Fig. 4. Tobe a-c bridge-analyzer circuit.

Ol' Man Centralab broadcasts-

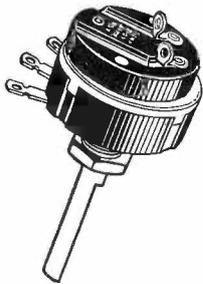

That genial chap . . . the friend of servicemen and experimentors takes time out to remind you that every control problem can be met (better and easier) with CENTRALAB CONTROLS. Smoother—because of the long, no-rubbing contact, they give “profitable” service for a long time. Change to CENTRALAB.



A mere handful will service practically any set—old or new

Centralab

Division of Globe-Union Mfg. Co., Inc.
Milwaukee, Wisc.
British Centralab, Ltd.
Canterbury Rd., Kilburn, London, N. W. 6, England
French Centralab Co.
118 Ave. Ledru-Rollin, Paris XI, France

VOLUME CONTROLS
FIXED RESISTORS
WAVE CHANGE SWITCHES

To Help You Sell More Sound Equipment



Probably you have felt like lots of other Sound Dealers that you could do a bigger job in Sound Equipment if you could get a little bit of help and cooperation from the manufacturer. Webster-Chicago now offers you a well-balanced program that will definitely work for you to get more business.

Shown above are:

1. Sound Engineering Book. 16 pages packed with Engineering and Sales Data. Copy available to you free of charge.
2. School Bulletin—A sales mailing piece for school principals, superintendents and architects—Also series of letters.
3. Inter-Office Communicating System Folder. Gotten up definitely to open doors . . . well worth a trial in any locality.
4. Factory Call System Mailing Piece. There is a big market for Call Systems. This mailing piece is unusual and will get attention.
5. Personal Dealer Signs. Here are signs with your name. Inquiry getters and business pullers for you, to put in your window, to place with all jobs you rent, to put in prominent places like hotel lobbies, or other spots available to aggressive dealers. Get more information.


Other helps are in process. In addition, Webster-Chicago maintains a steady advertising campaign to actual consumers resulting in hundreds of direct inquiries each month. Inquiries are forwarded to nearest Webster-Chicago dealer.

Remember also that with Webster-Chicago you will be handling a complete line of Sound Equipment and Accessories of All Kinds.

WEBSTER-CHICAGO

- Fully Licensed
- Strict Dealer Policy
- Time Payment Plan

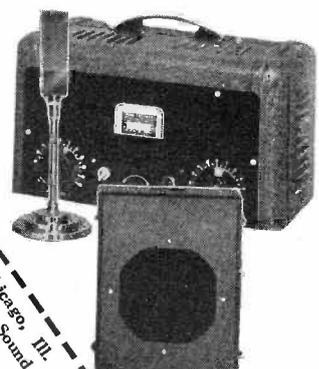WEBSTER-CHICAGO, Section J-5, 3625 W. Lake St., Chicago, Ill.
Please send me without obligation—
 Information on Following Sales Help
 Free Manual on Sound Engineering on Following Information on Sound Equipment
Name _____
Address _____
City _____
State _____



RECEIVER CASE HISTORIES

A-C, D-C Receivers

Intermittent fading: Intermittent fading and erratic operation of small a-c, d-c sets is often nothing more than a defect in the resistor feeding the screen grid of the detector. Many sets feed the detector screen directly from B positive through a 2-5 meg resistor by-passed with 0.05-0.25 mfd. The least defect in either resistor or condenser will be shown if a high resistance voltmeter is connected between B positive and screen as this will give a great increase in volume.

Francis C. Wolven

Grunow 501, 520, 530, 550 (Chassis 5B)

Speaker rattle: This is often caused by the leads from the output transformer which may touch the cone. Moving the leads further back and fastening them to prevent them from returning to the cone should clear the difficulty.

Howard J. Surbey.

Philco III, IIIA

Intermittent operation: After checking the set thoroughly and making change after change the stubborn brute would continue to fade after several hours of playing.

The real cause of the fading was poor contacts on the tube sockets. The set uses eleven tubes and a speaker plug with four contacts. These contacts are of the single spring type and loosen easily. The remedy is to bend each spring until the contacts grip tightly. None of the springs should be neglected because they are under condensers and difficult to reach.

Jim Kirk

Philco 805, 806, 807, 808, 809

Weak signals: After checking the coupling condensers check the i-f trimmers for low resistance wax. It is advisable to remove all wax or replace the trimmers. Realignment is necessary, of course.

Allan Siepman

Silvertone 1840, 1842

Inoperative: The 2A5 grids glow a bright red. This is caused by an open primary on the output transformer.

To assure against the recurrence of this defect the plate current of the 2A5 can be reduced (without materially affecting the response of the receiver) by connecting a low value resistor (about 100 or 200 ohms) in series with the cathode of the 2A5.

Richard C. Clapp

Stewart-Warner R-147

Hum: Several simple circuit changes have been developed which are effective in reducing hum where it is excessive and is not caused by defective tubes or parts.

For residual hum: (Between station hum) Remove the 0.5-mfd condenser connected from the chassis to the mounting nut of the input electrolytic condenser (the one nearest the power transformer). Replace the 0.5-mfd condenser with a 10-mfd 25-volt electrolytic condenser. The positive terminal of this condenser must be connected to the chassis. This change should always be made in combination with the following one, since either change may increase the hum if made alone.

Locate the 210,000-ohm resistor connected from the plate of the 6C5 tube to one of the 5Z4 socket terminals.

(a) Disconnect the end of this resistor going to the 5Z4 socket.

(b) Connect a 51,000-ohm resistor in series with the disconnected end of the resistor and the lug on the 5Z4 socket from which it was unsoldered.

(c) Connect a 0.25-mfd condenser from chassis to the junction of the above two resistors.

Remove the twisted green and brown wires connecting to the tone control and replace them with a shielded twisted pair. Ground the shield at both ends. Route the shielded wire so that the shielding does not ground the mounting nut on the electrolytic condenser nearest the power transformer.

Separate the single green volume control wire from the transformer and a-c leads.

In all cases of either residual or modulation hum, tighten down the power transformer mounting screws after the set is hot.

Early production sets did not have the resistance-capacity filter consisting of a 260,000-ohm resistor and a 0.1-mfd condenser in the grid circuit of the 6F5. In these early sets a 1.1 meg resistor was connected from the 6F5 grid to the bias resistor network. The later sets used a 760,000-ohm resistor connected from the grid to the filter resistor and condenser. On any of the early sets which do not have the filter, a 260,000-ohm, $\frac{1}{4}$ watt resistor should be added in series with the end of the 1.1-meg grid resistor which connects to the bias network. A 0.1-mfd, 150-volt condenser should be connected from chassis to the junction of the 260,000-ohm and 1.1-meg resistors.

For modulation hum: (On stations

only) Make this change even though no modulation hum is heard in the shop. Replace the 0.1-mfd screen-grid by-pass condenser (diagram No. 28) connected to the 6A8 socket with the 0.5-mfd, 150-volt by-pass condenser which was disconnected from the mounting nut of the input electrolytic condenser.

Important: If there is still too much hum after making the above changes be sure to check for defective tubes.

Stewart-Warner R-148

For modulation hum: (On stations only) Make this change even though no modulation hum is heard in the shop.

Remove the 0.1-mfd, 150-volt condenser connected to the screen-grid circuit of the 6K7 r-f tube. Replace it with a 0.5-mfd 150-volt paper condenser.

For residual hum: (Between station hum) Locate the red-blue wire running from the 5V4G socket heater terminal to the speaker socket. Disconnect one end of the wire and re-route the wire along the back of the chassis so that it is at least two inches above the 6H6 and 6C5 sockets when the chassis is upside down. Reconnect the wire.

A twisted pair should be placed along the front of the chassis so it can be used to connect the heater terminals of the 6K7 r-f and the 6L6 sockets. First connect a black wire to the grounded heater terminal of the 6K7 r-f socket (the heater terminal near the front of the chassis) and a blue wire to the hot heater terminal of the same socket. The other end of the black wire must be connected to the grounded heater terminal of the 6L6 nearest the front of the chassis and the other end of the blue wire must be connected to the hot heater terminal of the other 6L6 socket (the one nearest the 6C5).

Remove the input audio transformer mounting screw nearest the front of the set. Rotate the transformer around its other mounting screw until the free end is toward the rear of the chassis. There is a hole in the chassis at the proper point to mount the transformer by means of the small machine screw, lock-washer and nut. Pull the transformer leads away from the tube sockets. Sometimes an intermediate position of the transformer will result in less hum but this necessitates drilling either one or two new mounting holes.

Tighten down the power transformer mounting bolts preferably when the set is hot.

THE Group Subscription Plan for *Service* enables a group of service men, dealers or jobbers to subscribe at one-half the usual yearly rate.

The regular individual rate is \$2.00 a year. In groups of 4 or more, the subscription rate is \$1.00 a year. (In foreign countries, \$2.00.)

The service departments of thousands of dealers, independent service men, etc., have used this Group Plan for years, in renewing their subscriptions to *Service*.

Each subscriber should print his name and address clearly and state his occupation—whether a dealer, jobber, independent service man, service organization, etc.

Remember this Group Plan when Your Subscription Expires

(Service)

Bryan Davis Publishing Co., Inc.

19 East 47th Street

New York, N. Y.



**Sealed
Against
Moisture**

Plastic-Sealed Audio and Output Transformers and Chokes

● Here is what an east coast Virginia radio parts dealer says:—"On close inspection of the Hermetically Sealed transformer, we find that there could be no better transformer built for this location. We are located on the Virginia Peninsula which is almost surrounded by salt water. This salt atmosphere penetrates the best of transformers not coated. The Jefferson in our estimation tops them all."

● Many have found the Jefferson Plastic-Sealed Transformers have answered their requirements . . . Sealed in their tough elastic non-brittle jacket, the windings are completely protected.

Listings below allow you to make your selection—your radio parts jobber can supply you . . . JEFFERSON ELECTRIC COMPANY, Bellwood (Suburb of Chicago), Illinois. Canadian Factory: 535 College St., Toronto, Ontario.

**SELECT
FROM LIST
BELOW**

ASK YOUR RADIO PARTS JOBBER

JEFFERSON ^{Radio} Transformers

AUDIO TRANSFORMERS			
CAT. NO.		SIZE	PRICE
467-501	1 to 2 Audio	2-7/8 x 1-5/8 x 1-7/8"	\$1.25
467-502	1 to 2 P. P. Input	2-7/8 x 1-5/8 x 1-7/8"	1.30
467-503	1 to 3 Audio	3-1/4 x 1-7/8 x 2-1/8"	1.50
467-504	1 to 3 P. P. Input	3-1/4 x 1-7/8 x 2-1/8"	1.60

OUTPUT TRANSFORMERS			
for Single or P. P. Output Tubes—71A, 45, 33, 42, 47, etc.			
467-509	2 Watt-7000-4/6 Ohms	2-7/8 x 1-5/8 x 1-7/8"	\$1.20
467-510	3-1/2 Watt-7000-6/8 Ohms	3-1/4 x 1-7/8 x 2-1/8"	1.35

CHOKES			
Small filter and plate chokes			
466-(590)	20 Hen.-50MA.-425 Ohms	3-1/4 x 1-7/8 x 2-1/8"	\$1.50
466-(540)	250 Hen.-10MA.-5000 Ohms	2-7/8 x 2 x 2-1/2"	1.30

RECEIVER CASE HISTORIES—continued

Stromberg-Carlson 68

Alignment: In aligning this model the avc amplifier trimmer (C57) should be tuned for *minimum* between the two peaks on the output meter.

Additional service data: With the selector unit on its right side, the top row of trimmers are for the A band; the second row for the B band; the third row for the D band and the fourth row for the C band. The A band low-frequency padder is on the front-left side, the lower condenser. The B band low-frequency padder is the left upper; the C band padder is on the lower right side—the D band has no padder. A tuning wand is practically the only way to check the bottom trimmers since even an all fibre rod will detune them slightly.

The fuse clips in these models should be checked for corrosion and noise.

H. M. Bell

Stromberg-Carlson 125

Replacing dial lamps: Facing the rear of the chassis, remove the 6K7, 6A8, 43 and 25Z5 tubes. With the right hand passed to the right of the nearest i-f transformer, remove the nearest pilot lamp from the bracket. Pull the lamp to the right side of the i-f transformer where the bulb can be removed.

Insert left hand to the left of the other i-f transformer and lift lamp socket from bracket. The bulb can now be removed from the socket by supporting socket with right hand inserted over gang condenser. To remove bulb from socket, *do not* place thumb or finger directly under the bulb. Support ends of black insulator wings between the first and second fingers of the right hand. Push in on the bulb and turn slightly to left and release pressure—grasp bulb and pull out.

After replacing the pilot lamps by methods similar, but opposite to the above, the tubes should be replaced in their respective sockets.

Stromberg-Carlson 130


Replacing dial lamps: Turn the pointer to about 0.9 on the broadcast band. The lamp for illumination of the pointer will be found just above the gang condenser. The other lamp is found on a fixed bracket above the gang condenser.

Stromberg-Carlson 140

Replacing dial lamps: Turn the pointer to about 1.1 on the broadcast band. The lamp for the illumination of the pointer will be found between the gang condenser and the nearest i-f transformer. The other two lamps are on fixed brackets just above the gang condenser.

Stromberg-Carlson 160-L

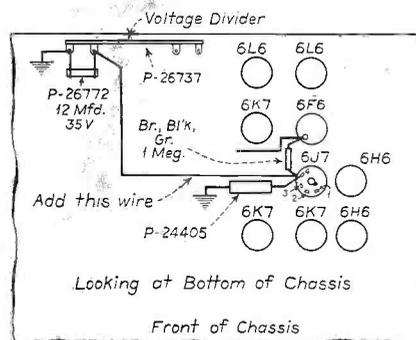Service note: Variations in new 6J7 tubes have occasionally caused distortion in the automatic tone control circuit of the 160-L receiver, as first released. These tubes function correctly after aging a few hours. Also it has been found possible to eliminate this possibility of distortion with new or aged tubes by adding a wire, as shown below, to stabilize the screen voltage.



This modification was put in effect at the factory in all 160-P and 180-L receivers, and in all 160-L produced after October 23, 1936.

Stromberg-Carlson 160-L, 160-P

Rushing noise: Background hiss or rushing noise, when encountered in a 160-L or 160-P receiver, can usually be cleared by replacing the 6A8 modulator tube.

Incidentally, the 6A8 tube removed from a 160 can frequently be employed with full satisfaction in a Stromberg-Carlson 125, 130, 140, 145, 150 or 180 receiver. Thus, clearing noise in a 160 becomes simply a matter of swapping 6A8 tubes with another Stromberg-Carlson.

The trouble is thought to be due to a slight defect in the weld in the second grid, occurring in a small percentage of 6A8 tubes. It does not show up on tube checkers, and causes no noise where the tube is used with potential on this grid as in the latter models.

Stromberg-Carlson High-Fidelity Models

Tuning: (Broadcast band) Set owners often complain that the high-fidelity control detunes the receiver, or that tuning can be sharpened appreciably after adjusting for high fidelity. This indicates lack of attention to the instruction books accompanying each of the receivers, which specifically state that "On the broadcast band, a high-fidelity Stromberg-Carlson radio should *always* be tuned with the fidelity control set for standard fidelity. *Never* retune the set

after advancing to the high-fidelity position."

The change in tuning meter swing or in the shadow on the tri-focal eye tube, noticed when adjusting from standard to high fidelity, indicates a broadening of the sidebands to give a wider frequency response. If the operator retunes the radio after adjusting to high fidelity—or if he then tunes in another station without returning to standard fidelity—the receiver will invariably be tuned to one or another of slightly off-resonance peaks, resulting in distortion.

Standard fidelity position on Stromberg-Carlson models employing the big bronze dial is indicated by half-red and half-white showing in the fidelity-tone control aperture and a small white dot appearing on the red side. At standard position the tone control is fully operative.

Tuning: (Short-wave bands) For short wave reception, the above instructions do not apply. Turn the high-fidelity control so that the red part of the indicator covers approximately three-quarters of the aperture. This provides maximum sensitivity on the short-wave ranges and at the same time spreads the tuning a little for easier location of short-wave stations. At the present time, there is practically no high-fidelity broadcasting on short waves, but this partial use of the fidelity control will help to find and hold the short-wave stations.

Stromberg-Carlson Telephone Mfg. Co.

Wells-Gardner 2DL

Hum: If a-c hum is encountered in this model check the following:

Be sure that the volume control lugs are not grounding on the flat portion of the metal chassis wall which supports the rubber mounting foot.

The bottom plate under the chassis must be under the r-f end of the chassis and away from the filter choke. If it is in the center or left side (from the back of the chassis) move it to the right side about a half inch from the mounting bolt holes.


Wells-Gardner All Models

Shipping bolts: (All models except 5K and 4C) If these bolts are not removed, the chassis will not float freely on the rubber cushions and microphonic noises will result, especially on the short waves. Not only must the bolts be removed when the set is installed, but also in the stores if a good demonstration is to be made.

Service Department
WELLS-GARDNER & Co.

Type 25L6 Beam-Power Amplifier

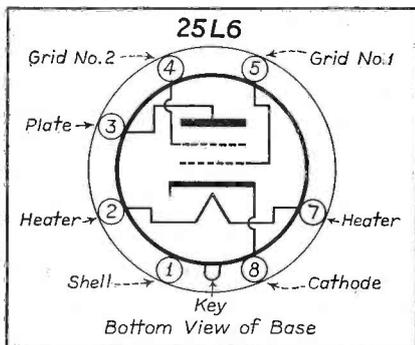
The RCA-25L6 is a power-amplifier tube of the all-metal type for use in the output stage of transformerless (a-c, d-c) radio receivers, especially those designed to have ample reserve of power-delivering ability. This new tube provides high power output at the relatively low plate and screen voltages available for transformerless receivers.



Type 25L6 base connections.

The high power output is obtained with high power sensitivity and high efficiency.

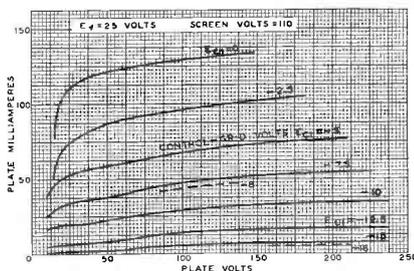These distinctive features have been made possible by the application of directed-electron-beam principles in the



Average plate characteristics.

design of the 25L6. The design is similar to that of the RCA-6L6 with the difference that the 25L6 is intended especially for operation in a-c, d-c receivers.

Courtesy RCA Mfg. Co., Inc.

Wells-Gardner 7L, OEL, 2DL

Rectifier tube: A 5Z4MG (metal glass) rectifier tube is used in these models. It is not advisable to replace this type with the metal equivalent the 5Z4. The latter tube will not operate satisfactorily at the voltages used in these models.

DOUBLE SUPERHETERODYNE


(Continued from page 11)

tween. If a weak, fading signal is between two strong signals on the adjacent channels, it can normally be held under control even during severe fading, as the control is not subject to capture by the strong adjacent signals unless the detuning is near the extreme limit of control. All the above statements apply equally to the entire range of an all-wave receiver.

CHOICE OF I-F

The choice of the two intermediate frequencies was influenced by a number of considerations. The first i-f, as in the conventional superheterodyne, should be as high as possible from the standpoint of image ratios; it should be on a channel which will be relatively free from feed-through interference. The second i-f should be low in order that the percentage frequency differences handled in the afc discriminator be as large as possible; however, if it is too low, difficulty may be encountered in providing adequate bandwidth for high-fidelity reception. The relative frequencies of the two i-fs must be such that high-order beats do not arise when the receiver is tuned over a signal channel. As compromise values from these considerations the first i-f of the WR-315 was chosen as 465 kc, while 100 kc was adopted for the second i-f, giving a normal fixed-oscillator frequency of 365 kc.

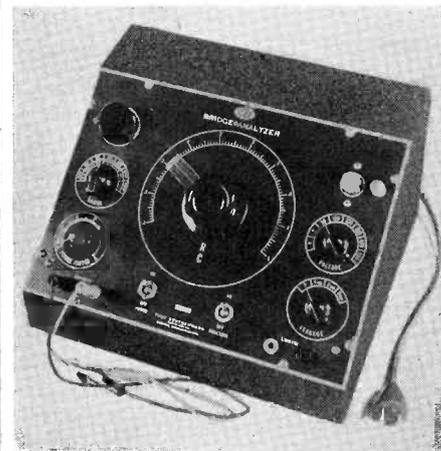exact TEST of CONDENSERS and resistors . .



Bridge Analyzer

Good servicemen have long wanted a single low-priced instrument for making every necessary test of condensers and resistances. The TOBE Bridge Analyzer is IT! Elusive types of receiver trouble, like high resistance contacts, poor power factor, and intermittent open circuits, can generally be traced to condensers or resistors, even though the latter may not be definitely shorted or permanently open. This instrument will show definitely and accurately the condition of every condenser and resistor. If you own a TOBE Bridge Analyzer, you'll need no other equipment for testing condensers. All dials are direct reading, eliminating other involved types of calculation. Briefly, by means of this analyzer, you may determine the resistance values between 1 ohm and 1,000,000 ohms, as well as values of capacitance between 10 mmf. and 100 mfd. and the resistance, power factor, leakage, and general condition of any electrolytic, mica or paper condenser.

MONEY BACK GUARANTEE

Complete with built-in power supply for any 110 volt 60 cycle circuit, electric eye with pre-amplifier, neon tube for conventional analyzer service, and detailed operating instructions. If this instrument does not prove to be all we claim, if for any reason you're dissatisfied with its performance under actual working conditions, SIMPLY RETURN IT AND YOUR MONEY WILL BE INSTANTLY REFUNDED.

TOBE BRIDGE ANALYZER, complete with 1-6G6, 1-6C6, 1-01A, and 1 neon tube. Net price..... **\$28.50**

TOBE DEUTSCHMANN CORP.
Dept. A-10, Canton, Massachusetts

Please ship one complete TOBE BRIDGE ANALYZER at \$28.50, all shipping charges prepaid, under your ABSOLUTE SATISFACTION OR MONEY BACK GUARANTEE. I enclose Payment in full, Deposit of \$5.00, balance C.O.D.

Name

Address

Town..... State.....

TENTATIVE CHARACTERISTICS

Heater voltage	25.0 volts
Heater current	0.3 ampere
Maximum overall length	3 3/4"
Maximum diameter	1 5/16"
Base	Small Octal 7-Pin

Single Tube Class A₁ Amplifier Operating Conditions and Characteristics

Subscript 1 indicates that grid current does not flow during any part of input cycle.

Heater voltage	25.0	volts			
Plate voltage	110 max.	110 max.	110 max.	110 max.	volts
Screen voltage	110 max.	110 max.	110 max.	110 max.	volts
Grid voltage	-7.5	-7.5	-8	-8	volts
Zero-signal plate cur.	49	49	45	45	milliamperes
Max.-signal plate cur.	55	51	52	48	milliamperes
Zero-signal screen cur.	4	4	3.5	3.5	milliamperes
Max.-signal screen cur.	8	10.3	8	10.5	milliamperes
Signal input voltage.	5.3	5.3	5.65	5.65	volts (RMS)
Plate Resist. (approx)	10,000	10,000	10,000	10,000	ohms
Transconductance	8,200	8,200	8,000	8,000	Microohms
Load resistance	1,500	2,000	1,500	2,000	ohms
Distortion:					
Total harmonic	11	10	13	11.5	percent
Second harmonic	10	3.5	12	4.5	percent
Third harmonic	4	8.5	4.5	9.5	percent
Power output	2.1	2.2	2.2	2.2	watts

Public Address . . .

A DIRECT-COUPLED BEAM-POWER AMPLIFIER

By A. C. SHANEY*

AN amplifier using the direct-coupled circuit is capable of producing equal potential amplification at all frequencies, within the limits set by the interelectrode capacity of the tubes, and equal frequency amplification at all potentials within the audible band.

Although the idea of direct-coupled amplifiers is not new (it was first introduced by Messrs. Loften and White about the time the first type 24 screen-grid tube made its appearance) it has from time to time been revived and built in quantity, only to fall by the wayside whenever the announcement of a new supertriode or pentode served to hold the technicians' interest.

The circuit as originally introduced had two major drawbacks. The ampli-

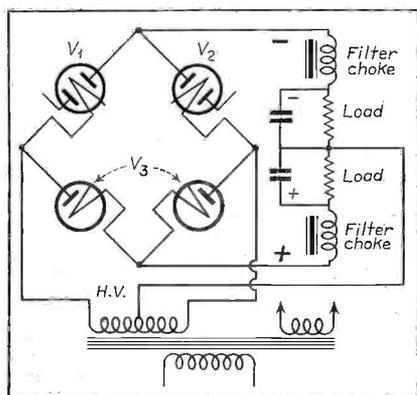


Fig. 1. Stabilized bridge type rectifier system.

fiers were subject to trigger action and in spite of considerable research no adequate push-pull circuit was available.

TRIGGER ACTION

Trigger action is a term applied to the phenomenon occurring when an amplifier is blocked or becomes inoperative due to a strong and maintained signal fed to its input. This effect is caused by a surge in the plate current which in turn lowers the grid bias voltage sufficiently to shift the stage off its normal E_g-I_p curve and maintain itself in this blocked state. Naturally, the amplifier was inoperative during these periods and often had to be shut off in order to release the trigger action. This effect is avoided, in the amplifier de-

*Amplifier Co. of America.

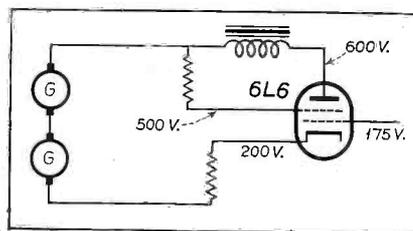


Fig. 2.

scribed herewith, through the use of a bridge type stabilized rectifier and filter system. For simplicity the rectifier circuit is segregated in Fig. 1.

PUSH-PULL ATTEMPTS POOR

After the circuit had gained in popularity many attempts were made to convert the single-ended direct-coupled amplifier to one of the push-pull variety and with varying degrees of success. Few lived up to their anticipated performance. As all of these inverter systems used a coupling condenser true inversion did not take place at all frequencies and amplitudes.

Critical adjustments were particularly annoying to the many experimenters who first attempted to build the amplifier. Little attention was paid to the regulation of the power supply or compensation for variations in plate current of different output tubes. These factors all contributed to the unjust condemnation of this truly revolutionary high-fidelity circuit.

A NEW VERSION

With the advances made in amplifier design it becomes a relatively simple matter to design a stabilized bridge type rectifier capable of supplying a fixed voltage to a three-stage direct-coupled amplifier utilizing a signal divider (this

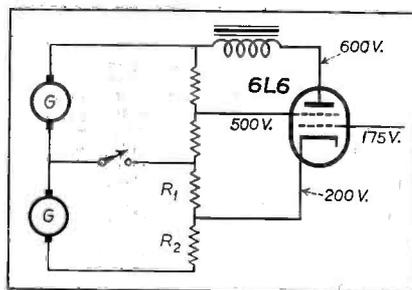


Fig. 3.

is not to be confused with a phase inverter) which is capable of driving two 6L6 tubes in true push-pull fashion.

In order to simplify the discussion of the circuit each portion will be treated individually.

THE RECTIFIER SYSTEM

A uniform load resistance connected across a conventional bridge type rectifier will have no potential difference between its center tap and the center tap of the a-c voltage winding supplying the system. If these two points are connected as shown in Fig. 1 no current (other than the normal load currents) will flow.

The use of a choke in each leg of the rectifier output with appropriate filter condensers produces the stabilized bridge rectifier as shown in Fig. 1.

The advantages of this rectifier system are manifold. The pivot of the circuit (the voltage at the mid-point of the load) is always kept at a constant potential and detrimental trigger action is avoided. Over 600 volts (d-c) is available from a 650-volt center-

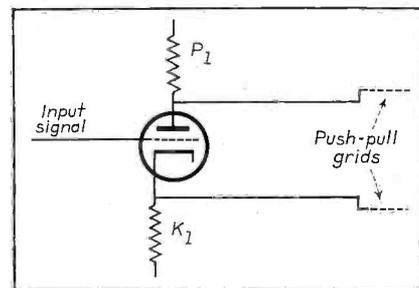


Fig. 4. Direct-coupled signal divider circuit.

tapped transformer. Hum potentials are cancelled because of identical choke coils and by-pass condensers in each output leg of the rectifier. The hum potentials picked off each leg are equal but opposite in phase and cancel when fed to the zero potential mid-point of the bridge rectifier.

Since mercury vapor tubes (83 type) are not available with isolated filaments for each half of the tube, two tubes must be used for rectifying one of the voltage phases while the third rectifier is used in the conventional manner. In order to keep the regulation of each side perfectly balanced, only one plate of V_1 and V_2 should be used.

STABILIZED CIRCUITS

The analysis of the stabilizing action of the entire system can best be illustrated by redrawing the rectifier diagram and one of the output tube circuits as indicated in Fig. 2. For purposes of simplicity, the rectifier has been drawn as two d-c generators connected in tandem.

One of the 6L6 tubes is shown con-

(Continued on page 47)

A NEW SUPREME ACHIEVEMENT!

The 555 DIAGNOMSCOPE
Combines 4 instruments in ONE



Now you can have all the equipment necessary for modern up-to-date cathode ray service work—complete in one impressive unit! The Diagnoscope is actually four instruments in one . . . a complete testing laboratory in itself! [1] Cathode Ray Oscilloscope [2] Frequency Modulator [3] Audio Oscillator [4] All-Wave Signal Generator which may be used [a] Unmodulated [b] Frequency Modulated Internally [c] Amplitude Modulated Externally [d] Amplitude Modulated Internally by 400 Cycle Fixed Frequency.

Before you buy any instruments, see the 555 Diagnoscope at your parts jobber. Its many new outstanding features . . . its simplicity of operation . . . its conveniently arranged controls . . . and its beautifully designed streamlined case will astound you! Contains 10 tubes. Completely A. C. operated.

Your parts jobber offers you convenient time payment terms on any SUPREME instrument, making it easy for you to purchase them *now!* You don't have to wait until you are ready to pay all cash.

See your parts jobber today. Ask him to show you the Diagnoscope. He will give you full details on how you can purchase it on the S.I.C. easy payment plan.

500 AUTOMATIC

Combines 12 essential servicing instruments:
A. C. Tube Quality Checker. Tube Hot Leakage, Short and Open Tester. Electrolytic Filter Capacitor Leakage Tester. Paper and Mica Capacitor Leakage Tester. Complete Point-to-Point Radio Analyzer. Multi-Range D. C. Voltmeter. Multi-range Ohmmeter. Multi-range Megohmmeter. Multi-range A. C. Voltmeter. Multi-range Decibel Meter. Multi-range Milliammeter. Multi-range Output Meter. \$7.50 Down—\$6.61 per Month for 10 Months. Cash price . . . \$66.95



550 RADIO TESTER

Performs the operations of 13 essential servicing instruments with 43 functions and ranges: Radio and P. A. Analyzer. Electrolytic filter and electrostatic capacitor leakage, also Electrolytic and Electrostatic capacitor tester. Multi-range ohmmeter. Multi-range D. C. Voltmeter. Multi-range A. C. Voltmeter. Multi-range milliammeter. Multi-range decibel meter. Multi-range output meter. D. C. ammeter. \$6.00 Down—\$5.55 monthly for 10 months. Cash Price . . . \$55.95



\$15.00 Down
\$12.05 per month
for 12 months
Cash Price \$147.95



WHERE SHOULD THE RADIO SERVICE MAN LOCATE HIS PLACE OF BUSINESS?

"This interesting booklet is the result of a nationwide survey made for your benefit. Write me today and I will mail you a copy free of charge."

Your parts jobber
Remember—YOUR CREDIT IS GOOD WITH SUPREME!

SUPREME INSTRUMENTS CORP.
GREENWOOD, MISSISSIPPI, U. S. A.

An Outstanding Announcement!

Dykanol impregnated and filled paper filter capacitors, conceived and developed in the laboratories of.....



TYPE TL

The type TL series of high voltage filter condensers were designed for power supplies, high power amplifiers, television circuits, transceivers, etc. Hermetically sealed in round aluminum containers, similar to those employed in the construction of electrolytic capacitors. One terminal is insulated, the other grounded. Can be conveniently mounted in either upright or inverted position.

CAP. MFD.
2
3
4

1
2

.5
1

WORKING VOLTAGE 600 V., D. C.
SIZE
2½ x 1½
4½ x 1½
4½ x 1½

WORKING VOLTAGE 1000 V., D. C.
2½ x 1½
4½ x 1½

WORKING VOLTAGE 1500 V., D. C.
2½ x 1½
4½ x 1½

CAT. NO.
TL-6020
TL-6030
TL-6040

TL-10010
TL-10020

TL-15005
TL-15010

LIST
\$2.25
2.75
3.00

2.25
2.75

3.00
3.50

Full rated capacity—full rated voltage at these attractively low prices. For complete technical information and listing see your local jobber or write direct for catalog 135A.

WET AND DRY ELECTROLYTICS . . . PAPER . . . MICA . . . DYKANOL
WORLD'S LARGEST EXCLUSIVE MANUFACTURERS OF CAPACITORS



CORNELL-DUBILIER

nected through $\frac{1}{2}$ of the output transformer to the high voltage terminal.

It will be noted that although 200 volts is applied to the cathode, the grid is 25 volts less negative (175 volts is applied to the grid) while the plate is 400 volts above cathode (600 volts above ground) and the screen 300 volts (500 volts above ground). Under these conditions the no-signal current is 50 ma for the plate and 5 ma for the screen. Approximately a 2700-ohm bias resistor will be required.

At full-signal conditions an increase of 19 ma (combined increase of plate and screen current) flows through R_2 so that the cathode voltage would be raised 51.3 volts. This degenerative effect not only lowers the available power output but discriminates against the low frequencies so that these would be practically lost. If the circuit of Fig. 2 is altered slightly as in Fig. 3 (a form of stabilized power supply) the cathode voltage remains constant at all values of plate and screen current.

The reason for this is that an external bridge circuit is formed and the cathode current divides equally, half flowing through resistor R_1 while the other half flows through R_2 . Voltage equalization takes place with the division of current, so that a constant cathode potential is maintained above ground. All plate and screen circuits of the amplifier are of the bridge circuit

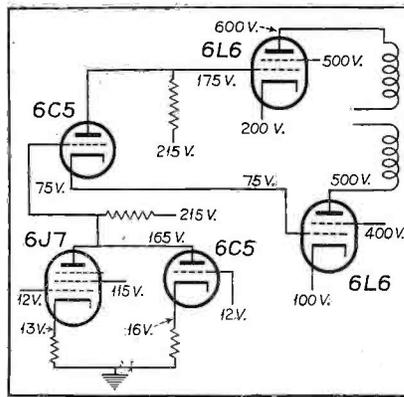


Fig. 5. Voltage distribution in the amplifier.

self-neutralizing type. Some of them are more complex and utilize the current flowing through two or more tubes to effect voltage stabilization.

THE SIGNAL DIVIDER

The ideal phase inverter will equally divide the amplitude of a signal and separate their phases by 180° . Naturally, this action must take place equally for all frequencies and amplitudes within limitations set by the tube itself. Any circuit utilizing a coupling condenser cannot accomplish this because of the varying capacitive reactance presented by the condenser to the varying audio frequencies. Transformers are similarly limited in their phase inversion action

because of the varying inductive reactance of both of the primary and secondary windings. In the face of these handicaps, circuits utilizing conventional phase inverters may be adjusted for inversion at one frequency and amplitude. As the frequency decreases, inversion is retarded and conversely as the frequency increases, phase inversion is accelerated. Thus, only within very narrow frequency limits will the inverted signal be 180° out of phase with the original signal. Amplitude distortion is, of course, predominant in transformer inverters unless unusual care is exercised in the design and construction of the transformer.

The phase-inverter circuit shown in Fig. 4 typifies the simplest voltage divider and inverter available. It is entirely devoid of all capacitive and inductive reactance (excepting for the interelectrode capacitance of the tube element) and is capable of dividing a signal into two equal amplitudes and at the same time inverting one of the signals (180° out of phase) with the other.

The plate load of the tube is divided into two equal non-reactive parts and one section (pure resistance) is inserted in the cathode circuit forming the cathode load resistor. During the positive cycle of the input signal, the plate current increases with a subsequent drop in plate voltage because of


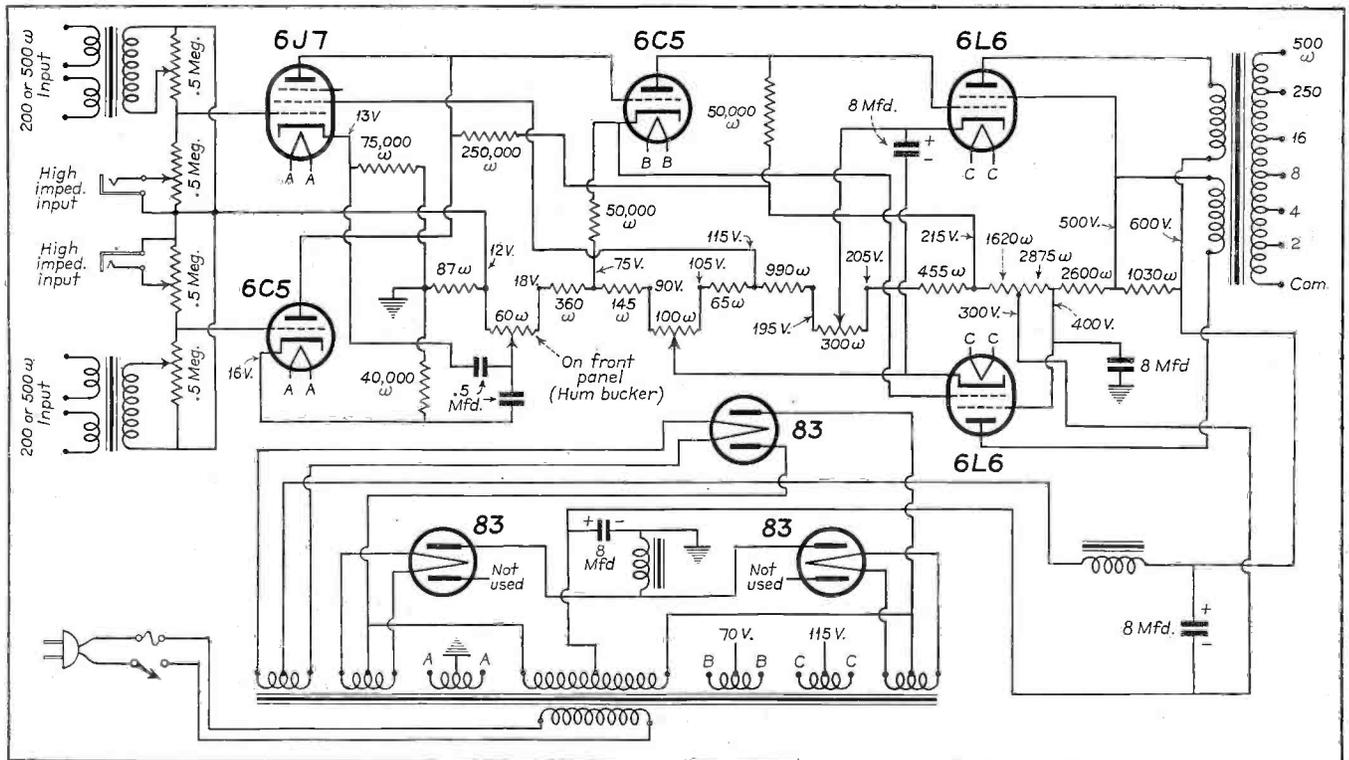


Fig. 6. The complete beam-power amplifier.

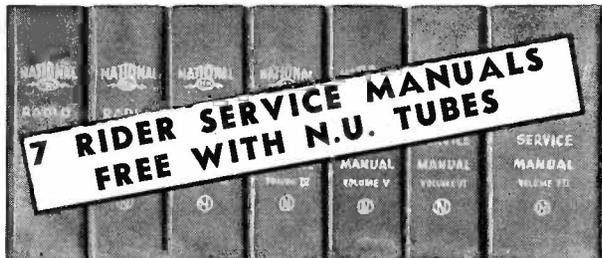NATIONAL UNION AUTHORIZED BY J. F. RIDER TO OFFER HIS MANUALS FREE



**MR. JOHN F. RIDER, NOTED
AUTHOR OF SERVICE BOOKS**

● A necessity of modern service work is complete technical data on all makes of radio receivers. Mr. John F. Rider recognized this need years ago and compiled a great library of radio set circuits and information. National Union also knew how important service manuals would be. National Union decided that every service specialist in the country must have the chance to own the manuals compiled by Mr. Rider. National Union therefore makes it possible to get this library FREE. All seven volumes are given with the purchase of

N. U. tubes. N. U. is officially authorized by Mr. Rider to offer his great service library FREE. If you want any one or all of the Rider Service Manuals write now, ask how to get them or consult with your National Union distributor!

FREE SHOP EQUIPMENT, TOO!

No need for the alert and aggressive service expert to read about all the fine scientific instruments which service equipment manufacturers are making and wish that he might own them. Why? He can own them! How? By getting them Free with the purchase of National Union radio tubes.

National Union has given servicemen throughout the United States more than 50,000 pieces of fine equipment. If you're not taking advantage of National Union's service dealer plan, you're missing the greatest opportunity in the radio industry today.

All you do is contract to purchase a few tubes per week, place a small deposit, which is refunded to you after the tube purchase is completed and the instrument you have selected is yours "for keeps," without any strings attached. Meanwhile, remember that you have the use of the instrument all during the time tube purchases are being made.

ABOUT N. U. RADIO TUBES

National Union manufactures a complete line of radio tubes in glass, metal and G-types. National Union's high quality has made them the outstanding favorite in the radio service profession. All sales policies have been formulated with the idea of making National Union radio tubes the ideal replacement tube for the radio dealer. This has been backed up with a selling program that means real support and help to the wide-awake dealer. Dealers and jobbers handling National Union radio tubes are the leaders in repair parts and service.



NATIONAL UNION RADIO CORP., S-1-37
570 Lexington Ave., New York City

Tell me how to get Rider Service Manuals and other free equipment.

Name

Street


City State

ANOTHER MAJOR VIBRATOR IMPROVEMENT BY THE LEADER— No More Broken Leads

Utah has always been the leader in the design and manufacture of vibrators for radio purposes. This organization has pioneered in vibrator design, and is the recognized and leading source of the radio industry for this part.

Every Utah Vibrator embodies the same high qualities of workmanship and design found in other Utah products.

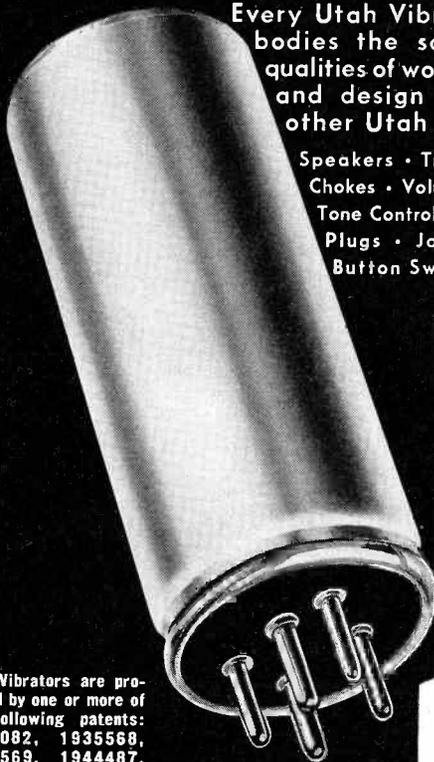- Speakers • Transformers
- Chokes • Volume Controls
- Tone Controls • Resistors
- Plugs • Jacks • Push Button Switches



Utah Vibrators are protected by one or more of the following patents:
1924082, 1935568,
1935569, 1944487,
1946563, 1951614,
1961053, 2009425.
Other patents pending.



VIBRATORS

UTAH RADIO PRODUCTS CO.
CHICAGO, U. S. A.

TORONTO ONTARIO CANADA BUENOS AIRES (UCOA RADIO PRODUCTS CO.)

"15 YEARS OF LEADERSHIP"

ASSOCIATION NEWS . . .

RADIO ASSN. OF CALIFORNIA

Three cheers for Mr. John Powers of Techna, who spoke at the last meeting in 1936 and gave an informative, interesting and understandable talk on acoustics, speakers, impedance matching, etc. Mr. Downy of the Techna sales department displayed some fine equipment. President Digby's plea for pictures brought forth only one snapshot. We sure ought to be able to do better than that. Carl won the turkey, and another meeting and another year goes into the records.

Mr. L. C. Rayment spoke on "Vacuum-Tube Applications in Medical Diagnosis" at the meeting held January 4 at 921 Harrison Street, in Oakland. Mr. Rayment is doing some outstanding work in this field and his talk brought forward many interesting items. He brought along some equipment and gave actual demonstrations.

The question box wanted to know something about the infinite impedance detector. Carl Penner had the dope handy and gave a brief explanation.

At the January 18 meeting, Mr. Frank Kesser, marine editor of the Tribune, will speak on "Mysteries of the Sea."

As in the past, radio and service dealers may be admitted directly to regular membership. Service Men are admitted after examination and may obtain information and dates for examination from Gordon Braun who has been appointed as agent for the examining committee. Applications for examination should be with Mr. Braun not later than any Monday, meeting night.

The treasurer has become plumb militant. Dust off your membership card and bring it along—or else!

H. R. Anderson, Secretary

PRISMA

On Tuesday, January 5, on the twenty-fourth floor of the Architects' Building at 17th and Sansom Street, in Philadelphia the new officers of the PRISMA were installed. With plans pretty well shaped up, the motor warmed up, just waiting to spin the propeller and zoom away!

The new officers are as follows: Charles Wrigley, president; Jesse Ehly, vice-president; Stanley W. Myers, treasurer; F. B. Guthrie, recording secretary and John Breichner, corresponding secretary. The new members of the advisory board are as follows: E. F. Benson, Joseph W. Bishop, E. S. Walker, E. M. Oldach and Frederick A. Meyers.

The newly elected officers are making a plea for the full cooperation of every member of the PRISMA.

Brother Scroggs' new address is now in care of Schuck Electric Co., Germantown. Treat him well, Fred—He's a nize boy.

There are a lot of fellows who are now out of the woods and are looking forward to a new year that will see the profits going toward a bulwark for the future instead of being used for mending fences and paying debts.

All except Bob Andrassy. He went in

hock again for a new car. P. S.: So did Hen Dornheim.

We extend our sympathy to Mr. T. J. Tucci for the loss of his mother on November 21, 1936.

New Year's resolutions: To stay away from revolving doors, Dave Krantz; To stay home on foggy nights, Elmer Benson; To stay off committees, Ben Doan; To never drink any more beer, Paul Keller; To never give a sucker an even break, De Long; To talk back to his wife, Mike Rogers; To wear a fedora the year 'round, Jesse Ehly; To get my "stuff" to the Editor on time, Willie De W.; To pay my dues on January 5—and attend every meeting on time, Every Member.

Roy Lowe is walking around on air sporting his new title. Good luck and a lot of big business, Roy!

Repair and trouble men are cordially invited to our open meetings—first Tuesday of each month at 17th and Sansom Streets. Also anyone else who is interested in our technical talks.

To say that the recent election was a hotly contested one would be putting it too mildly—but we hope that everyone is satisfied. To the winnah! . . . Lots of luck and success!

J. T. Gallagher

RADIO TECHNICIANS GUILD

Big doings are again expected at RTG headquarters as the newly elected officers buckle down to work. The new regime is as follows: S. S. Malo, president; G. L. Chapman, vice-president; Frank L. Kennes, treasurer and George W. Feldman, secretary. The new board members are: A. C. Saunders, Mr. H. Lahey and Mr. B. Roessel.

A campaign for membership has already been outlined and surpasses everything attempted so far. It is the Guild's aim to help the Service Man out of the doldrums and to aid him in obtaining a living wage.

All interested Service Men are invited to attend the open meetings held the fourth Monday of each month, at the Hotel Lenox in Boston.

We have been bragging to one of the other magazines about the fine job SERVICE did with the recent articles on automatic frequency control. Keep up the good work.

George W. Feldman

ASSOCIATED RADIO TECHNICIANS

Vancouver, B. C. Chapter

A meeting of the ART was held on November 4, at the D. V. A. Hall. Thirty members were present.

The door prize was won by Mr. Wheatcroft.

A financial statement for the dance was submitted by Mr. A. Johns.

The secretary's correspondence included a very interesting letter from the R. M. A. service division in which they extend their full cooperation to this organization, and the newly formed branch in Victoria.

Mr. T. Brown then gave a detailed re-

port on the committee's activity in Victoria, stating that the branch is now fully formed, and has a membership of 25 Service Men.

Mr. Paine, owing to pressure of work, resigned from the publicity committee. Mr. D. Clark was appointed to take his place.

An examination for admission to membership in the ART will be conducted in the D.V.A. Hall on January 17, 1937. All associated are expected to write at this sitting.

Wilf Munton, the librarian, gave an interesting review of the recent magazines and books added to the library at the last meeting.

On Friday, December 4, the Sparton Co. and their B. C. Distributors, Canadian Fairbanks-Morse, tendered a dinner to the Associated Radio Technicians of B. C. There were 75 present and no chicken was left when Mr. Geo. Foster of London, Ont., rose to speak, on "Why the Factory Does Not Build Sets as the Service Men Think They Should." His story of production methods and of triumph over the problems that beset the building of a modern radio held his audience attentively. And at the conclusion he was invited to speak on refrigeration at the regular meeting of the ART on December 8.

A word of thanks is due Messrs. Smith and Salter of the sales staff for arrangements they made; also, Mr. Doug Flower, who is an old member of the ART, and was introduced as new local service manager for Sparton.

The fine attendance at the December 8 meeting surprised everyone as nobody realized the interest that existed in refrigeration, and if all who heard it are not now qualified refrigerator mechanics, they at least know the why and how of it. Thanks, Fairbanks-Morse and Sparton—may the benefits of this fine gesture be mutual.

A special meeting of the Vancouver Chapter was held in the D. V. A. Hall on December 29. After two postponements Mr. A. T. Johns of Marshall-Wells delivered his talk on automatic volume control. An interesting and profitable evening was enjoyed by all present.

At the meeting on January 12, Mr. A. Birnie, instructor at Spratt-Shaw, is to lecture on Automatic Frequency Control.

It has been decided to have one or more special talks at every meeting for the next three months. Service Men really interested in advancing themselves cannot afford to miss these lectures.

Victoria, B. C. Chapter

On November 16, in the Eagles Hall, a meeting of the Victoria Chapter was held, with Jack Allison in the chair.

The meeting was turned over to Mr. Monte Lennox of Vancouver, who outlined details which would have to be arranged for incorporation, etc.

The date of incorporation was set as January 2, 1937.

Mr. Lennox then gave a brief report on the annual meeting of the ART in Vancouver. Following this he explained the use of the "microvolter" and also gave a condensed talk on avc.

AC CURRENT ANYWHERE!

In CARS . . . On FARMS . . . In DC DISTRICTS

With **ATR** ^{DC}/_{AC} **INVERTERS**

For Operating . . .

Standard 110-Volt or 220-Volt A.C. Radios, Public Address Systems, Electrical Testing Equipment, etc.



LIST PRICE **\$1850***

*Without Radio Filter
\$22.50 with Built-in Filter
(Standard Discounts Apply)

PROVEN—DEPENDABLE—GUARANTEED

OUTSTANDING FEATURES • Interference-Free All Wave Radio Operation
• Improved Long Life ATR Vibrators • Four-Point Voltage Regulators
• 16 Different Types for DC Input Voltages ranging from 6 to 220 volts, and having AC output voltages of both 110 and 220 volts.

OTHER ATR PROFIT MAKERS

ATR AUTO RADIO "A" BATTERY ELIMINATOR



Specially Designed for Demonstrating and Testing Auto Radio Sets on Regular AC Lines, 105-125 Volts, 50-60 Cycles. Has many other uses. Comes completely equipped with On-Off Switch, Pilot Light Indicator, 10 ampere Fuse, Rubber Mounting Feet, 6 ft. Rubber Cord, Heavy Gauge Metal Cabinet.

DEALERS' NET PRICE
\$12.95

ATR Automatic Tapering BATTERY CHARGER

Keeps Auto Battery fully charged right in the car! Operates from any 110 volt AC 50-60 cycle line. Equipped with a full wave dry disc type rectifier unit. Current tapers off as battery becomes charged. Comes completely equipped with Polarized Dash Receptacle and Plug, Fuses, 9 feet DC Cord, 12 feet AC Cord, On-Off Toggle Switch, and Complete Instructions.



LIST PRICES (Standard Discounts Apply)
Model 450. Max. charging rate 1 1/2 amp. \$9.67.
Model 600. Max. charging rate, 6 amp. \$11.45.
Model 1000. Max. charging rate, 10 amp. \$14.25.

• Write or Wire for Additional Information
• Sold by Leading Jobbers Everywhere

AMERICAN TELEVISION & RADIO CO.

St. Paul, Minnesota, U. S. A. Cable Address: "Likex" New York

YOU CAN'T KEEP PACE



with
"Model T" Training!

A car ten years old is not more out-of-date today than are many radio service men. Radio service is becoming not only more technical, but also more highly competitive. The man who hopes to get ahead must have adequate MODERN training NOW!

Advanced Home Study Training in
RADIO SERVICE AND PUBLIC ADDRESS WORK

FOR PROFESSIONAL SERVICEMEN
Terms As Low As \$5 Monthly!

This course has been prepared from years of actual work and contact in the service field. We know what you men need and how to teach it. Insure your radio future by training now . . . in your own home. Start any time . . . take up to three years to complete.

FREE BOOKLET

Write today for this helpful, illustrated booklet, "The Key to Successful Servicing." Get all the facts now!



RADIO SERVICE INSTITUTE


SUBSIDIARY OF CREI

Dept. S-1, 3308—14th St., N.W., WASH., D. C.

New Thordarson Servicing Guide

Big, profusely illustrated handbook that every service man needs.

Only
15c

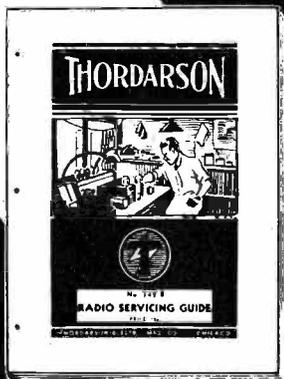

NOW!

Send for your copy TODAY. Delay may cost you time and money.

Ask your jobber or write.

THORDARSON Electric Mfg. Co.
500 W. Huron St.
Chicago, Illinois

Thordarson Electric Mfg. Co. Dept. "Z"
500 W. Huron St., Chicago, Ill.
Enclosed find 15c for the new Thordarson Servicing Guide. (Postpaid.)


Name

Address

City..... State.....

"I FIXED HER RADIO

What'll I do now?"

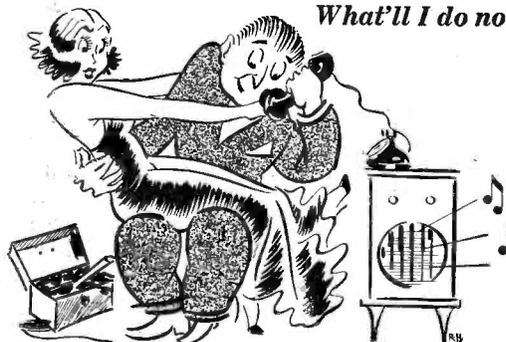

Naturally you first restock your service kit so that you will have Ward Leonard Resistors for your next job. Ward Leonard Resistors have always been dependable and their ratings conservative. The service man finds they pay because the work he does with them is satisfactory. Send for bulletin and price list.



WARD LEONARD ELECTRIC CO.

South Street, Mount Vernon N. Y.

Please send me Service Men's Bulletin 507A.

Name

Street

City..... State.....

Jobber

AMPERITE presents..



Featuring.. Distinguished in Quality, Design, and Construction

1. Output increased 6 DB.
2. Triple shielded—against all RF or magnetic fields, entirely eliminating hum pickup.
3. Eliminates feedback troubles.
4. Excellent for close talking and distant pickup.
5. Acoustically designed to eliminate any possibility of cavity resonance.

Models RBHn (High Impedance); RBMn (200 ohms) \$42.00 List

NEW! Models RBSn, RSHn—Excellent All-around Microphones for Speech and Music. Slightly lower output and frequency range than above. Appearance same as above. \$32.00 List

NOW! A specially designed microphone built to Ampelite standards; can be used for both speech and music. No peaks. Flat response. Triple shielded. Shock absorber. Swivel bracket.

Models RAL (200 ohms); RAH (2000 ohms) \$22.00 List

FREE! TO DEALERS AND SERVICE MEN: A striking window decal, advertising your **SOUND SERVICE**, and displaying the new Ampelite Velocity. Write for it now!

AMPERITE Co. 561 BROADWAY, N. Y. Cable Address: Alkem. New York

AMPERITE Velocity MICROPHONE

RACON

pioneers again!



Permanent Magnet Horn Units

These efficient P.M. units require no outside excitation. Available in two types; both the 36% Cobalt steel and the newest high flux Alnico type magnets are used to supply maximum flux density in the air gap.

Cast bronze case, completely enclosed, makes unit water tight. Continuous operating capacity 10 watts. Peak load capacity 30 watts. 15 ohm impedance at 1000 cycles.

Electro dynamic type units also available in all sizes.

RACON'S catalog J.1 describes the complete line of Horns, Electro-dynamic Units and Acoustical Sound Projectors.

RACON ELECTRIC CO., INC.
52 E. 19th St. New York City

TEST EQUIPMENT—continued

linear sweep for each of the ranges. This decade switch is so marked that the value indicated by its pointer multiplied by the value indicated on the main dial at balance gives the capacity of the condenser under test or the value of the resistor under test as the case may be.

THE ANALYZER SECTION

The analyzer part of the bridge places a d-c voltage on the condenser under

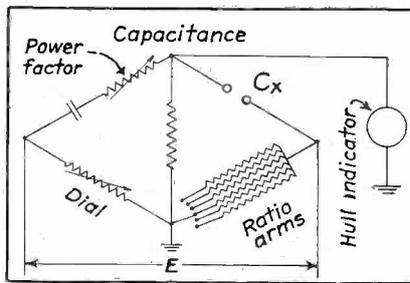


Fig. 5. Condenser analyzer part of bridge circuit.

test. This voltage may be varied from about 35 volts to 550 volts. The d-c leakage of the condenser is then determined under actual operating conditions. For by-pass condensers, etc, a d-c test of this nature is extremely valuable, for high leakages in a coupling condenser in a resistance-coupled amplifier will cause the quality of the set to be greatly impaired, and many times this d-c leakage cannot be determined at low voltage. The writer has known of cases where a condenser is practically a complete short circuit at operating voltages and has a high resistance (resistance approaching a good condenser) on a low-voltage test. This was due to the fact that a hole was burned in the paper as the result of the initial breakdown. However, insufficient power was developed by the breakdown voltage which was fed through a resistor to carbonize the paper. Lower than working voltage was not sufficient to jump the minute gap between the condenser foils with the result that the condenser tested good at 45 volts. In passing it might be stated that this same condenser had about a 3 percent power factor, which was not considered sufficiently high to cause it to be removed from the circuit. As a consequence of this and similar investigations, it is felt that from a service standpoint it is advisable to test certain by-pass condensers at or near operating voltage.

The condenser analyzer part of the bridge (circuit diagram in Fig. 5) uses a neon tube for indication of all leakages so that the Service Man can deter-

mine the serviceability of any condenser used in the radio receiver.

Intermittent open condensers which are one of the worst bugaboos in servicing may be determined by obtaining a balance on the bridge and then manipulating the leads to the condenser. If the eye tends to close or "wink" when the leads are manipulated, it indicates an intermittent condenser. Naturally open-circuit condensers are detected by obtaining a bridge balance which is near the minimum capacity of the bridge.

GRID LEAK MEASUREMENT

The writer has had some experience with grid resistors which checked perfectly on an ohmmeter, yet when placed in a radio receiver caused a considerable amount of distortion after the set had been on for fifteen or twenty minutes. This distortion was finally found to be due to an increase in the resistance of the resistor for some undetermined reason, probably due to the heat radiated from the power transformer. It has been found that the analyzer part of the bridge gives an excellent method for checking such resistances for their constancy with an appreciable voltage across them, for the Service Man may place the resistor across the analyzer terminals of the bridge and adjust the voltage and leakage switches so that the neon tube just lights. Any increased

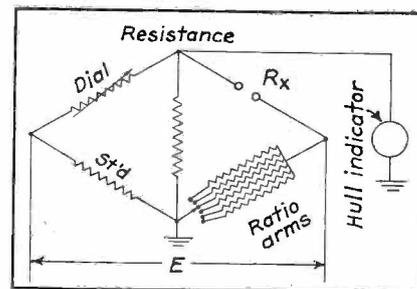


Fig. 6. Resistance measurement with the bridge.

resistance with heating will cause the neon tube to be extinguished.

All in all, the combination instrument provides facilities for complete condenser analysis—with advantages possessed by neither bridge nor analyzer alone—plus provision for resistance measurements over a range and with a permanency of calibration heretofore not incorporated in service apparatus.

In conclusion, it might be well to state for the benefit of the Service Men who have considered the operation of a bridge complicated, that, with the aid of the electronic eye, adjustments can be made with greater facility than tube tests on the average equipment.

As a CALL SYSTEM



PERMITS TWO-WAY CONVERSATION


Belfone is sweeping the country. And it isn't any wonder. Every business can profit from its convenience. It's more than a remarkably efficient, low-cost, easily installed inter-office communicating system that permits any number of stations to converse by a flip of a key. As a call system it's ideal. By using loudspeakers you can not only locate parties but they can answer from anywhere. Ask for details on this money-maker.

Mr. Jobber and Mr. Dealer, Belfone opens a profitable market. Built in various capacities it is suited for any type of business. Investigate.

ALL-PURPOSE SOUND SYSTEMS

Remember that Bell also manufactures a full line of P. A. equipment for portable or permanent use—a capacity for every need. Low in cost. Unexcelled in tone fidelity. Foolproof, dependable construction. Bell gives you better values and makes money for you.

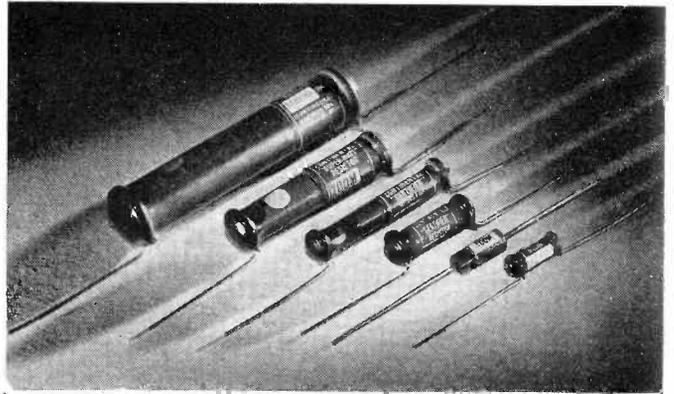BELL SOUND SYSTEMS, Inc.
61-62 E. Goodale St. Columbus, Ohio
308 West Washington St. Chicago, Ill.



CONTINENTAL Insulated Resistors

insure circuit stability. These accurate and conservatively rated units are the choice of leading radio and instrument makers. Reading from left to right: M5, 5-watt, list, \$.50; E2, 3-watt, list, \$.30; D2, 1-watt, list, \$.20; G4, 1/2-watt, list, \$.17; M5, 1/2-watt, list, \$.17; K7, 1/4-watt, list, \$.17. Ceramic insulation used on all except M5, which is insulated with molded bakelite. Specify CONTINENTAL Carbon insulated resistors on your next order.

JUST OUT—Handy Pocket Data on Radio Interference—an informative up-to-date booklet which helps you sell radio interference elimination service. Price 10 cents, postpaid.



13912 Lorain Avenue, Cleveland, Ohio Toronto, Canada

TO DEALERS AND SERVICEMEN

TRIAD RADIO TUBE FREE!

UP TO \$1.25 LIST

A DARING NEW PLAN

To convince you of the superior quality of Triad Radio Tubes—we are offering absolutely free any Triad Tube up to \$1.25 list with your purchase of Triad Radio Tubes; also free Engineering Data Chart. Mail coupon below—back will come your Free Tube Certificate. Present it to your jobber when you purchase Triad Tubes and get your Free Tube—save \$1.25.

MAIL TODAY!


TRIAD MANUFACTURING CO., Inc. THIS COUPON WORTH \$1.25
Dept. A-12 Pawtucket, R. I.

Sure I'll try Triads. Send me Free Tube Certificate... good for \$1.25. Also FREE Engineering Data Chart.

Name _____
Address _____
Town _____ State _____
Jobber's Name _____

"THE QUALITY NAME IN RADIO TUBES"

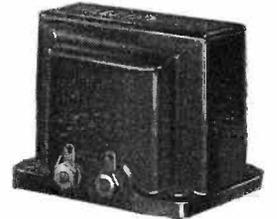Impervious to moisture . . it's vacuum sealed



Type B Mounting

All Halldorson transformers are vacuum-sealed. The vacuum sealing is positive in action and insures uniform impregnation of all windings. The process was developed by Halldorson engineers both as to manufacturing procedure and selection of impregnating material. The result is an effective skin tight covering that does not crack, flake off or open up, even in tropical climates. It is one transformer that is really impervious to moisture.

For better transformer satisfaction buy

Halldorson Vacuum Sealed Transformers

The Halldorson Co., 4500 Ravenswood Ave., Chicago, Ill. S-137
Please send me your new catalogue of Vacuum Sealed Transformers.

Name _____
Address _____
City _____ State _____

HIGHLIGHTS . . .

RAYTHEON INCREASES TUBE PRICES

As a result of changes in type costs due to increased material and labor costs, variations in the proportional demands for the different types and need for additional revenue in every branch of the tube business, the Raytheon Production Corp. has announced an increase in tube prices effective immediately.

Raytheon has believed for a long time that tube prices have been too low to provide a proper profit for the distributor, dealer or Service Man. It is expected that the distributors, dealers and Service Men will welcome the new list prices. They should result in greater profits to all concerned in the sale of receiving tubes during 1937.

WEBSTER SALES REPRESENTATIVE

The Webster Electric Co., Racine, Wis., announces the appointment of the Kay Sales Co., Tulsa, Oklahoma, as district sales representative for the states of Oklahoma, Arkansas and the extreme western section of Tennessee, to include Memphis.

J. P. Kay, manager of the Kay Sales Co., has had many years' experience in the radio and sound equipment field and is well known to the trade. He will personally supervise the merchandising of Webster Electric sound equipment, phonograph pickups, and the "Teletalk" intercommunicating system.


SUPREME EQUIPMENT MANUAL

The Supreme Instruments Corp., Greenwood, Miss., has prepared a 60-page manual on tube tester and radio tester design. The manual contains complete descriptive material on the 1937 Supreme line, their circuits, their functions and their ranges.

Copies of this manual may be had directly from the manufacturer. The price is 15c.

ATLAS RESISTOR DISPLAY

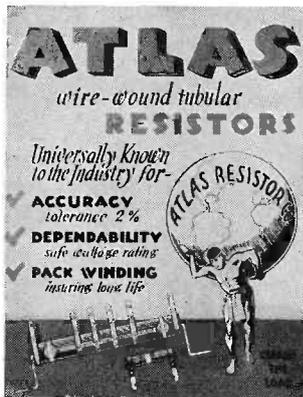The Atlas Resistor Co., 423 Broome St., New York City, are distributing to dealers



and jobbers a colored display board designed to help sell Atlas Resistor products. These cards may be obtained directly from the manufacturer.

SPEEDEX SALES AGENT

D. R. Bittan Sales Co., Inc., 27 Park Place, New York City, has been appointed sales agent for the Speedex Manufacturing Co., of San Francisco, manufacturers of amateur and professional keys and buzzers.

CLOUGH-BREngle 1937 CATALOG

A new and complete description of over twenty C-B instruments, including r-f signal generators, oscillographs, audio oscillators, analyzers, and vacuum-tube voltmeters is now available. Shows down payment and monthly payments for each instrument on the new C-B "Pay-As-You-Earn" Plan. Address your request for a copy to The Clough-Brengle Company, 2815 W. 19th St. Chicago.

SOLAR REPRESENTATIVES

Mr. James Schoonmaker, 4133 Shenandoah Ave., Dallas, has been made district sales manager for the Solar Manufacturing Corp., for the Texas territory.

Mr. E. P. Demarest, 1127 Venice Blvd., Los Angeles, has been made district sales manager for California.

Both executives are favorably known to merchants and Service Men in their territories.

The Solar Manufacturing Corp., 599 Broadway, New York City, manufacturers of radio and electrical parts has just announced a 5 per cent wage increase to its 750 employees.

RCA RADIO TUBE PRICES UP

After years of steadily declining prices, the RCA Radiotron Division of the RCA Manufacturing Co. has announced an increase in the prices of practically all types of receiving tubes, effective January 2, 1937.

Eugene N. Deacon, general sales manager of the RCA Radiotron Division, pointed out that the large number of different types of tubes, for many of which there is now only a limited demand because of the obsolescence of the radio sets in which they are used, and mounting material and labor costs have made a complete review of costs necessary. Mr. Deacon believes that the newly announced prices, which represent an overall increase of 11 per cent over former tube prices, will be welcomed by dealers and Service Men as a step in the right direction of increasing dollar unit sales on radio tubes from the all-time low to which they had fallen. In its announcement, RCA has suggested that its wholesale distributors quote dealers on a net unit price basis, rather than on a discount basis, a procedure which simplifies quoting, billing and record keeping, and gives the dealer his cost and profit margin at a glance.

ARLAB MOVES

The Arlab Manufacturing Co., manufacturers of magnetic and dynamic speakers have rented the plant at 430 S. Green St., Chicago.

The Arlab Manufacturing Co. has recently acquired the Baritone Radio Co.

NATIONAL TRADE SHOWS

The Radio Parts Manufacturers National Trade Show, Inc., meeting in Chicago on December 16, named the dates of two industry shows to be held during 1937. They



S. N. SHURE

will be sponsored by the Radio Manufacturers Association and the Sales Managers Club through the vehicle of the above-mentioned show organizations.

Managing director of both shows will be Kenneth A. Hathaway of Chicago.

The spring shows will be held in Chicago over a four-day period, June 10-13, inclusive, at the Stevens Hotel. The fall show will be held in New York City, October 1-3, inclusive. The hotel for this show has not yet been selected.

It is anticipated that the annual Radio Manufacturers Association convention will be held in Chicago immediately preceding the National Trade Show. Three other meetings are definitely set for the period of the show—those of the Sales Managers Club, the Institute of Radio Service Men, and "The Representatives."

Industry leaders have been struggling with the formation of a show organization, which would be all inclusive, for more than six months. Appointed representatives of RMA and the Sales Managers Club, meeting at various times in Chicago and New York, finally concluded that greatest good would result by the creation of a non-profit corporation for the special purpose of conducting the shows, with both groups having representation on the board.

S. N. Shure, of Shure Brothers Co., Chicago, was elected president of Radio Parts Manufacturers National Trade Show, Inc., by the Board of Directors on December 16.

Other officers of the show corporation are: A. A. Berard, Ward Leonard Electric Co., Mt. Vernon, N. Y.; Arthur Moss, Electrad, Inc., New York City. Directors are Fred D. Williams, International Resistance Co., Philadelphia, and Messrs. Berard and Shure.

(Continued on page 58)

NOKOIL

The recognized Standard
of comparison for
Permanent Magnet Speakers

Model
980



8"
Nokoil

**RADIO
PUBLIC ADDRESS
INTERCOMMUNICATION SYSTEMS**

"A NOKOIL Speaker for every purpose"

Send for prices and catalog describing the
10 different Nokoil models.

Ask for the name of our nearest distributor.
Wright-DeCoster distributors are always
anxious to cooperate.

WRIGHT-DeCOSTER, Inc.

2253 UNIVERSITY AVENUE, ST. PAUL, MINN.
Export Dept.: M. Simons & Son Co., N. Y. Cable Address: "Simonrice"
Canadian Office: Associated Sales Co., Guelph, Ont.

DUMONT

ELECTROLYTIC CONDENSERS
**GUARANTEED
UNCONDITIONALLY**

Now at reduced prices.



4 mfd.—PV 600 your cost 24c.
6 mfd.—PV 600 your cost 27c.
8 mfd.—PV 600 your cost 30c.
8-8 mfd.—PV 600 your cost 58c.

*Exact duplicates for every
radio.*

Licensed under U. S. A.
Patent reissue No. 19604.

*For free catalog and your nearest
Dumont jobber, write to us.*

Manufactured by


Dumont Electric Co., Inc.

514-516 BROADWAY
NEW YORK, N. Y.

Paper — Mica — Electrolytics



Announcing....
4 NEW AERIALS BY WARD

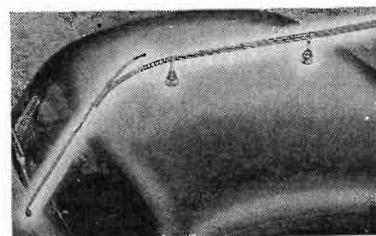

MODEL S.T.R.—The "Stratosphere"—List Price \$5.00 — Maximum efficiency. Enhances beauty of any car. Also **MODEL T.A.** "Tur-rette" for windshields that open.

MODEL A.L.T.—The "All-Range"—List Price \$4.25 — For cars with windshields that open — Also **MODEL A.L.** for windshields that do not open. No drilling in top necessary. Fits all cars.

MODEL F.L.—The "Flex-Rod"—List Price \$3.50 — Sensational Hinge Aerial — Fits all cars — Flexible — Efficient — No drilling.

IMPROVED MODEL H.P.R.— "Long-Range Twins"—List Price \$4.00—America's Finest Running Board Aerial—simple installation.

**1937 CATALOG READY
SEND COUPON TODAY**

The **WARD PRODUCTS Corp.**
WARD BUILDING CLEVELAND, OHIO
IN CANADA: ALPS RADIO CORP., TORONTO, ONTARIO

USE THIS COUPON

WARD PRODUCTS CORP.
Ward Bldg. - Cleveland, O.

Send Ward's 1937 Aerial Catalog.

Name.....

Address.....

Check Dealer Jobber Service Man



Composition-element controls for higher ohmages.

★

Wire-wound controls for greater current-handling capacity.

★

Choice of resistance values and tapers.

★

Ad-A-Switch snaps on back of case.

★

Flexible resistor supplied for grid biasing.

★

No better controls made. Just try them!

for a Good Job

Correct data regarding volume control replacement for any set, plus the precisely matched unit for the job. ● That's what CLAROSTAT means to you when it comes to profitable servicing. ● You can't afford anything less.

Free MANUAL: Big 80-page book covers control and resistor requirements of all standard sets. Ask your jobber or write us for copy.

CLAROSTAT

MANUFACTURING CO.
Incorporated

285 North Sixth St.
Brooklyn, N. Y.



THE MANUFACTURERS . . .

UNIVERSAL RECORDING AMPLIFIER

The Universal Microphone Co., Inglewood, Cal., is producing a medium-priced recording amplifier which incorporates a phase-inverter system; a low- and high-pass filter arrangement operated by a single control knob and a neon volume indicator.


The 120-db gain makes the amplifier suitable for use with any type of microphone or pickup and the combination high- and low-pass filter allows the adjustment of the frequency characteristic.

All metal tubes are used in the circuit; the output is 8 watts. A switch is provided for changing the output from the loudspeaker to the recording head.

RANGER-EXAMINER ACCESSOR

The Readrite Meter Works, Bluffton, Ohio, has introduced a portable model 740 volt-ohm-milliammeter, one of the Ranger-Examiner single testers.

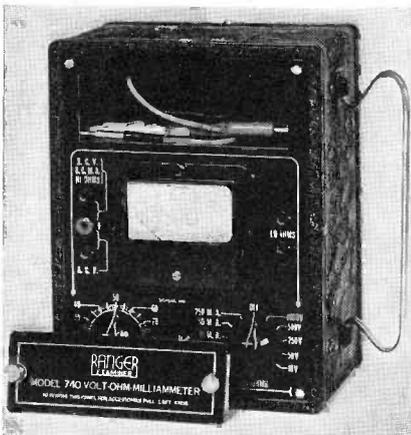The unit has a Triplet precision instrument with scales reading: 10-50-250-500-1,000 a-c and d-c volts at 1,000 ohms per



volt; (d-c accuracy 2 per cent, a-c, 5 per cent) 1-10-50-250 d-c milliamperes; 0-300 low ohms; high ohms to 250,000 at 1½ volts. Provision for higher resistance readings by addition of external batteries.

Sturdy metal case with black electro-enamel finish is 5⅞ in. x 7⅞ in. x 4⅛ in. Built-in compartment with snap-on cover holds all accessories. Panel is silver and black. Carrying handle folds against the side of the case when not in use. Model 740 volt-ohm milliammeter.

CENTRALLAB "SWITCHKIT"

Centralab has made switches available to the trade in knocked-down form. Switch requirements vary greatly, and it is obvious that a relatively few types of switch sections and mechanical parts can be assembled in a great many different combinations.


The Centralab Switchkit is a 75-drawer steel cabinet containing sufficient parts to assemble 35 switches. The assortment of parts included, however, is sufficient to assemble 161,700 different types of switches.

A descriptive bulletin, describing the "switchkit" in detail, is available upon re-

quest to Centralab, 900 E. Keefe Ave., Milwaukee, Wis.

ELAMCO SERIES B AMPLIFIERS

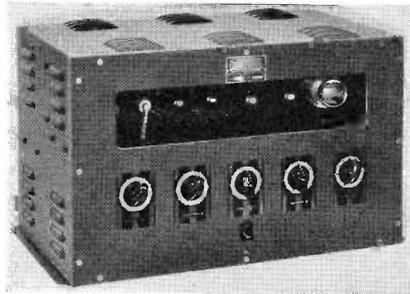A series of moderately priced amplifiers ranging from 10 to 28 watts output has



been introduced by the Electric Amplifier Corp., 135 W. 25th St., New York City.

The Elamco series B, as these amplifiers are called, are obtainable in three forms, standard, portable and rack-panel models. Six high impedance channels are provided on each amplifier as well as multiple line connections. Field supply is also provided for one or two speakers.

TRIAD 6AB6G


Triad Manufacturing Co., Inc., has added the 6AB6G to the "Triadyne" series. The new tube has the universal octal type base and a small ST-12 bulb. Its filament current is 0.5 ampere at 6.3 volts. Its characteristics are similar to the 6B5, the 6N6G and the 6N6-MG.

ARCTURUS ADDS NEW TYPES

The Arcturus Radio Tube Co., Newark, N. J., has added the following types to their line: 1A4, 1B4, 6E5, 6G5, and the following "G" tubes (glass tubes with octal bases): 1C7G, 1F5G, 1H4G, 1H6G, 1J6G, 5U4G, BV4G, 5X4G, 5Y4G and the 6B8G.

CLARION SOUND SYSTEM

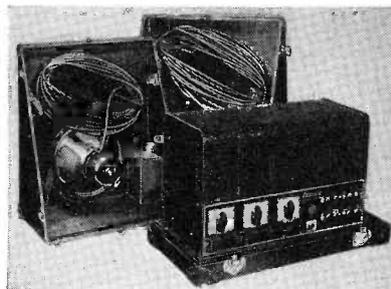The Transformer Corp. of America has made available to Service Men a brochure



describing their Clarion model C55 portable sound system. The C55 has a rated output of 25 watts and 35 watts peak. Output terminals are provided for various voice coil impedances as well as for 50, 250 and 500 ohm lines.

For this brochure and other technical data, address the Transformer Corp. of America, 69 Wooster St., New York City.


CLOUGH-BREngle OSCILLOGRAPH

The new type 913 cathode-ray tube has made possible a new form of cathode-ray oscillograph, the model 105, which has just been announced by the Clough-Brengle Co. of 2815 West 19 St., Chicago.

Except for physical size and screen area, this instrument is identical to the larger oscillograph, the model CRA. Performance features such as the built-in linear sweep, separate high sensitivity amplifier for both horizontal and vertical inputs and beam centering controls on the front panel have been retained in the model 105.

The entire unit is contained in a carrying case, 8⅞ inches high, 8¼ inches wide and 9⅜ inches deep. The finish is baked black crystalac with an etched silver and green front panel. An adjustable hood surrounds the cathode-ray tube and may be extended several inches out from the front panel to keep all direct light off the tube screen.

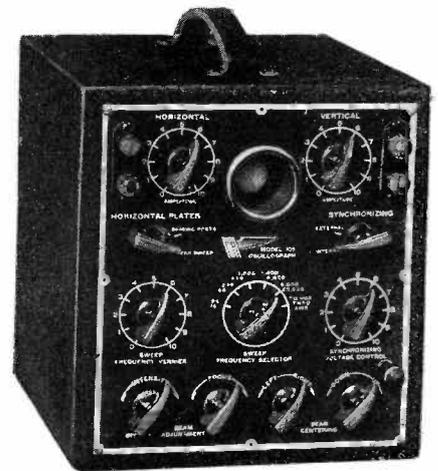The model 105 is supplied complete with tubes for direct operation from 110-volts,




60-cycle power supply. Special models for other voltages and currents are available.

The instrument is complete for all servicing, transmitting, and general laboratory applications. For visual alignment, the model OM-A frequency modulated signal generator or model 81-A separate frequency modulator may be connected directly to the oscillograph by means of a plug-in cable.

Complete descriptive bulletin and price may be secured by writing the manufacturer.

SYLVANIA MAKES TUBE PARTS

Sylvania's radio tube parts building, measuring 200 feet by 60 feet, employs a group of workers whose effort is concentrated on the manufacture and inspection of over 175,000,000 parts during the year. These parts include cathodes, collars, plates, hooks, grid leads, anchors, cages, diode shields, etc. Mica is procured from British India and is carefully inspected for gas content, iron and thickness. It is then fabricated.

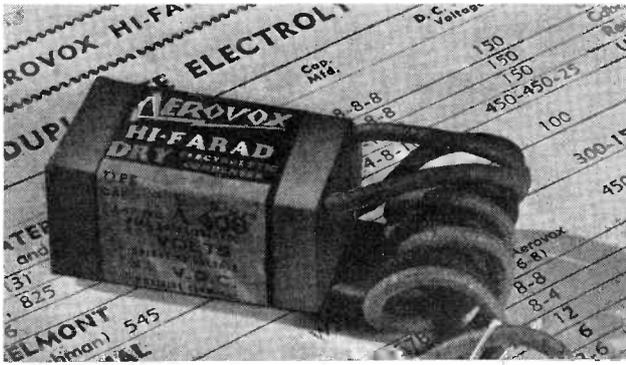

Exact-Duplicate REPLACEMENTS



Exact replacements for all standard sets.

★

Most extensive listing available.

★

Units matched mechanically, electrically, visually.

★

Electrolytic and paper types.

★

Cheapest in the long run.

There's only one way to do a real job on condenser repairs. That's an exact-duplicate replacement for that wornout original equipment. ● AEROVOX offers the widest choice of exact duplicates. ● And you save money, time and trouble by using exact duplicates.

New CATALOG: Contains several pages of exact-duplicate condenser listings. Also other condensers and resistors of AEROVOX line. Copy on request.



BRUSH

Sound Cell
MICROPHONES

BR2S



BR2S Spherical Microphone

This Brush sound cell microphone has blazed a new trail in the fields of "P. A.," remote pick-up and amateur applications.

The BR2S is one of 12 types of sound cell microphones manufactured by Brush. Hundreds of Brush Microphones go into service each month. Supreme performance plus mechanical perfection and dependability in the BR2S are now AVAILABLE AT . . .

A NEW LOW PRICE

\$37.50 This new price has been made possible by the constantly increasing popularity and demand for this type of Brush sound cell microphone. Join the Brush enthusiasts and realize sound quality.

Write for complete Technical Data.



THE MUTTER COMPANY 1255 S. MICHIGAN AVE., CHICAGO, ILL.

NEW MUTTER CATALOG NOW READY STOP ZIPPHM
REPLACEMENT RESISTORS NEWEST AND BEST
STOP FULL DETAILS ON REQUEST.

THE MUTTER COMPANY

TWS - 10 - Chicago Ill 217 PM

CANDORMS
ZIPPHMS
SWITCHES
SPRASHIELDS
BRIDGES
DECADE BOXES


JACK SPANLAN
PETE DAILEY

LES MUTTER

FLOYD CHURCHILL
FRED STEVENS

DEPENDABLE
QUALITY
AND
RELIABLE
SERVICE
ALWAYS

MUTTER FLASH

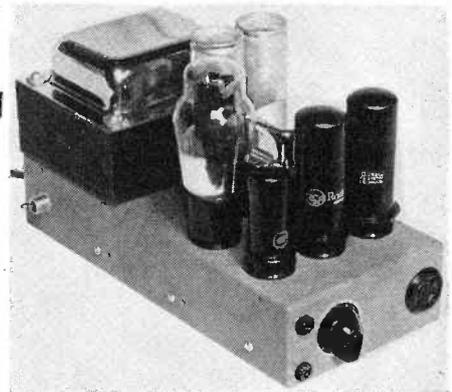

NEW! Sensational AUDITION EQUIPMENT

The 3-A is a 32 Watt amplifier which with its 18 inch Super Giant Speaker has an acoustic sound output equal to a 214 Watt System. It will drive one to four Super Giant Speakers to completely cover the largest indoor enclosure, and will comfortably and easily cover 50,000 to 100,000 people. An unequalled booster amplifier to raise the power of existing P A equipment, the 3 A provides flexibility never before available.

Send in the coupon today for complete details on this sensational new audition equipment.

McMURDO SILVER MASTERPIECE AMPLIFIERS
FULL DETAILS FREE MAIL THIS COUPON

McMURDO SILVER CORP.
2900 So. Michigan Blvd.
Chicago, Ill., U. S. A.

Please rush me full details on new 3 A Masterpiece Audition Equipment.

Name _____
Address _____

MANUFACTURERS—continued

OPERADIO P-A SYSTEM


The model 115 portable p-a system is a 12-watt Class A system. It is suitable for orchestra and voice reinforcement, for soloists and public speakers; it permits mixing one or two low-level inputs such as a crystal and phonograph input; has two variable tone controls, one for high frequencies and one for low frequencies. The 115 furnishes complete power supply for the model 681 preamplifier which makes the 115 usable with high-impedance crystal microphones or for frequency attenuation.

The 115 comes complete with a 10-inch speaker with rubber cable and a polarized plug. Provision is made for the use of an additional speaker. A dual diaphragm crystal microphone is also supplied with the system.

Additional information may be obtained from the Operadio Manufacturing Co., St. Charles, Ill.

DUCO PAPER CONDENSER

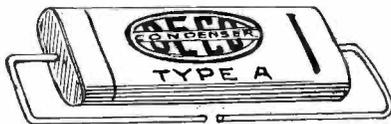A new type of paper condenser, impregnated with a compound which insures against the absorption of moisture, is made by the Dumont Electric Co., Inc., 514 Broadway, New York City, in accordance with RMA specifications. Its shape reduces r-f pickup, a cause of noise in sensitive circuits. The condenser is protected



from moisture by a layer of aluminum varnish and its shape enables its use in small spaces.

G-E "CHARGING SHOP"

A new G-E Tungal "Charging Shop," which will charge as many as twelve 6-volt batteries or six 12-volt batteries at 6 amperes and is intended primarily for use in service stations and garages, has been announced by the General Electric Company's Appliance and Merchandise Dept., Bridgeport, Conn. It is of heavy steel, one-unit chassis construction, with all parts panel-assembled.

The 12-battery charging shop is housed in a steel cabinet finished in red with an ivory panel. Compartments on each side provide space for battery tools and jumpers, carrying straps, etc. Shelves of the cabinet hold 12 batteries, which are accessible for testing without removing. The unit is equipped with four-acid-proof molded rubber trays, battery clips and jumpers for 12 batteries, and an all-rubber cord and plug for connection to 110-volt, 60-cycle a-c circuits. The complete unit is protected by an acid-resistant finish.

BIRCO "SWITCH-O-MATIC" ANTENNA

To guard against the possibility of incorrect or poor connections the Birco "switch-o-matic" antenna, introduced by the Birnbach Radio Co., Inc., is completely connected and soldered at the factory. No

switching is required on either the short-wave or broadcast band.

Complete information on this new type of antenna may be obtained from the manufacturer, Birnbach Radio Co., Inc., 145 Hudson St., New York City.

ASTATIC PICKUP

After much research the Astatic Micro-



phone Laboratory, Inc., Youngstown, Ohio, has released a crystal pickup known as the Tru-Tan model B constructed with an off-set head which holds the needle, throughout the entire playing of a 12-inch record, practically true to the tangent of the circle at all points (maximum error never exceeds 1.5 degrees from the true tangency).

In addition to its performance features the model B pickup has a full double row ball-bearing base swivel with hardened steel pivot trunnion.

Another feature is the provision for needle loading—which consists of a reversible head permitting the needle to be dropped in from the top.

TURNER MICROPHONE

The Turner Co., Cedar Rapids, Iowa, has announced the model VT-73 microphone. An adjustable swivel head permits the microphone to be used either on the desk or as a hand microphone. An output level of -55 db is available from the VT-73.



It is designed chiefly for voice transmission.

The VT-73 is complete with stand, cable and shielded plug.

HIGHLIGHTS—continued

HYTRON GIVES BONUS

In keeping with the times the Hytron Corp., Salem, Mass., has granted a bonus in the form of an additional week's salary to all of its employees. At the same time it was announced that the New York office of the company, under the management of David Cohen, has been moved to 315 Fourth Ave.

SPRAYBERRY FOUR-COLOR DIAGRAM

To facilitate study of the action of a tuned-radio-frequency receiver, the Sprayberry Academy of Radio, 2548 University Place, N.W., Washington, D. C., has announced a lesson in which a circuit diagram in four full colors plays a prominent part. This and other lessons with color diagrams now in the course of preparation will be supplied with Sprayberry training at no additional cost to students.

By illustrating various circuit components in color, study is greatly simplified. It becomes easy for the student to trace a signal through the circuit or to understand the action of various units. Refinements, frequently found in modern radio, have purposely been omitted to further simplify the subject. These refinements, however, are dealt with individually in later lessons so that the student has a thorough grounding in fundamentals before tackling them.

WARD PRODUCTS MOVE

The Ward Products Corp., manufacturers of automobile aeriels and sound systems, have recently moved into their own new building on East 45th St., Cleveland, Ohio. They have doubled their manufacturing space and enlarged their sales of-



fices. In addition to their Cleveland plant, the Ward Products Corp. have a branch in Canada and an export office in New York City.

TOBE "FILTERETTE" CATALOG

Specific recommendations for quelling man-made static are given in the current issue of the Tobe Deutschmann Corp. "Filterette" catalog in which are presented the results of ten years' laboratory and field research by this organization in the radio interference eliminating field.

Forty-two stock models from which may be chosen a suitable unit for any application are fully described and their installation illustrated in this handbook for the Service Man.

The catalog also tells how Service Men may have placed at their disposal the services of an engineering staff devoted exclusively to the study of radio interference problems.

TRIUMPH APPOINTMENT

J. P. Kennedy, formerly an account executive for The Fensholt Co., was named sales and advertising manager of the Triumph Manufacturing Co., Chicago. In his new position, Mr. Kennedy expects to develop the direct-to-dealer sales policy of the Triumph Manufacturing Co. and to seek new markets for radio and electrical instruments.



"SPRAGUE SC'S
ARE THE BEST
I'VE FOUND
FOR
P. A. WORK!"

SPRAGUE
The Standard of Condenser Quality

Of all the thousands of Sprague Inverted Aluminum Can Type Dry Electrolytics (Type SC's) sold last year, I'm convinced that MORE THAN HALF were used in Power Amplifier equipment where exceptionally good filtering and the ability to stand sudden surges are absolutely essential. Servicemen themselves will tell you they build up to 650 to 670 volts—and with extremely low leakages. We have done our best to give you the finest replacement condensers. **We challenge competitors to equal their quality and electrical characteristics.** Let me send the new Sprague Catalog today to help you on your next condenser order.

SPRAGUE PRODUCTS CO.
North Adams, Mass.

FACTS

on

SERVICE CIRCULATION

70% own their own business.

81% carry a stock of tubes.

89% carry a stock of parts.

78% carry a stocks of sets.

Over 22,500 full-time, professional servicemen read the magazine each month.

Over 800 legitimate distributors of parts and accessories subscribe to SERVICE.

AUTO-RADIO—continued

ADJUSTING ANTENNA COMPENSATOR

(a) Set the signal generator to 600 kc.

(b) Tune in the 600-kc signal with the station selector for maximum output.

(c) Adjust the antenna compensating condenser for maximum output.

(d) Repeat operations (b) and (c) alternately until no further improvement can be obtained.

(e) Set the signal generator at 1400 kc again."

(f) Tune in the 1400-kc signal with the station selector for maximum output.

(g) Readjust the trimmer on the antenna section of the tuning condenser for maximum output.

It will be necessary to adjust the antenna compensating condenser to the car antenna after the receiver has been installed in the car.

(a) After the installation is complete, tune in a weak station between 55 and 65 on the dial.

(b) Adjust the antenna compensating condenser for maximum volume in the speaker.

PUBLIC ADDRESS—continued

denser-resistor combination ahead of the 6N6 output tubes.

The high-frequency channel has a frequency range of from 2500 cycles to 12,000 cycles. It was found possible during tests to obtain frequencies as high as 25,000 cycles but that present-day broadcast facilities do not lend themselves to the reception and reproduction of these higher audio frequencies, and therefore, 12,000 cycles was set as the upper limit of audio frequencies. Power output of this channel is about 12 watts.

SPEAKERS

One 18-inch auditorium type of speaker is used for the low-frequency output, two 12-inch speakers are used for the mid-frequency output, three high-frequency diaphragm type speakers or tweeters are used for the output of the high-frequency channel. In the cabinet the 18-inch speaker is mounted as low as possible and in the center of the cabinet with the two 12-inch speakers on each side set at an angle of approximately 30 degrees with the front plane of the cabinet. One tweeter is mounted directly above the large speaker with two on each side at the same angle with the front as the 12-in speakers.

A. P. Richards, Crosley Radio Corp.

"Right you are, Buddy
and Sprague
small PTM's can't be
beat as

**INEXPENSIVE
SERVICE
REPLACEMENTS."**




CONDENSERS
USE SPRAGUES... and Note the Difference

Fellows, you'll find these small Cardboard Dry Electrolytic ETCHED FOIL Condensers (Sprague Type PTM) are built to take everything the rectifier will give them. They mean more pep for the set plus better tonal quality. Both you and your customers will quickly note the improvement. Conservatively rated at 525 volts, yet servicemen themselves say they'll take surges as high as 560 and even 580 volts! Won't break down because you can't reach the sparking point. **FAMOUS SPRAGUE HUMIDITY-PROOF SEALING** Truthfully and sincerely, and other features at no additional cost.

Henry Kalman
Sales Manager

SPRAGUE PRODUCTS CO.
North Adams, Mass.

"BULLET" DYNAMIC MICROPHONES

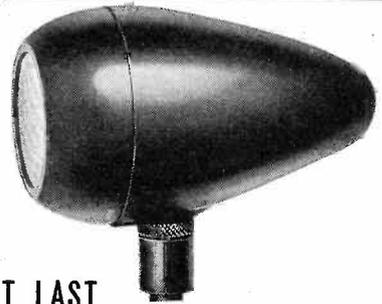

AT LAST
an ALL-PURPOSE Microphone . . .

T. R. 2—Standard model "Bullet" . . . the ultimate in dynamic microphone design . . . List price \$39.50.

T. R. 3—New model "Bullet" . . . smaller than T. R. 2 but with relatively the same characteristics . . . List price \$24.50.

Consider these outstanding "BULLET" features combined in one microphone . . .


- Maximum sensitivity
- Effective at long distance from amplifier
- Wide choice of impedances
- Remarkable tone quality
- Attractive, modern appearance
- Unequaled for severe outdoor work

Send for circular and technical data

TRANSDUCER CORPORATION

30 Rockefeller Plaza
New York, New York

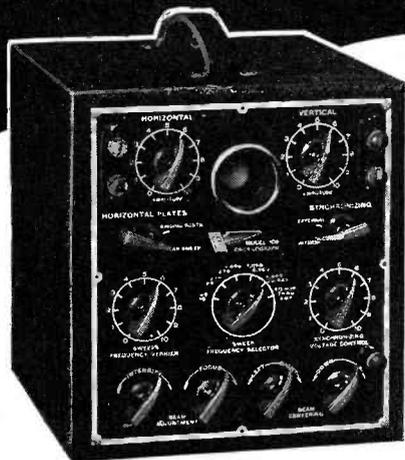NEW — a low cost C-B Oscillograph MODEL 105 with Linear Sweep, Dual Amplifiers, etc.



You Need Every One of These Exclusive Features

Uses the new Type 913 one-inch Cathode-ray tube and provides every feature of the most expensive oscillographs, such as: Linear Sweep with synchronizing circuit using the Type 885 Thyatron; separate High Gain Amplifiers for horizontal and vertical plates; Beam Centering Controls; and adjustable light shield for Cathode-ray tube screen.

Compact, easily portable — yet the most complete instrument ever offered using the Type 913 tube. Not one of these features can be omitted without so limiting the utility of the oscillograph that any saving is wasted by limited performance. Write for bulletin describing this instrument in detail.

Complete with five tubes, net cash \$48⁹⁰
Pay-As-You-Earn. \$5.50 down

Oscillators for Use with MODEL 105

This instrument now makes it possible for you to secure complete Cathode-ray Receiver Servicing equipment for only \$9.50 down (MODELS 81-A and 105). Designed for use with either the MODEL OM-A Frequency Modulated Oscillator or the MODEL 81-A Frequency Modulator, to produce calibrated selectivity curve images by single or double trace method.

The CLOUGH-BRENGLE CO.

2817 W. 19th St., Chicago, U.S.A.

Send at once full description of the new MODEL 105 Cathode-ray oscillograph and time payment order blank.

Name.....
Address.....

See Your Jobber Today — Or Use This Coupon

Farewell to "man-made" static



• "Man-made" static and other extraneous noises are effectually "strained out" . . . FILTERED is the word . . . by the scientific "NOISE-MASTER" Antenna, which improves reception on both shortwave and broadcast bands. Do your customers a favor; recommend this great A. A. & K. licensed aerial system for PURER radio reception.

Cornish Wire Co., 30 Church Street, New York, N. Y.

"NOISE-MASTER" No. 14. List \$6.75

Brings in overseas signals stronger, and eliminates "man-made" static on broadcast as well as shortwave band. For better reception on EVERY location.

"NOISE-MASTER" No. 18. List \$3.40

First time at this popular price: simple doublet type, SELF-SELECTING, recommended for clarifying shortwave reception.


"NOISE-MASTER" No. 19. List \$4.80

SELF-SELECTING doublet type, with junction-box in the antenna line. Assures excellent all-wave reception.

INDEX TO ADVERTISERS

A		H	
Aerovox Corp.	57	Halldorson Co., The	53
American Television & Radio Co.	51	Hygrade Sylvania Corp.	31
Amperite Co.	52		
Amplifier Co. of America	62	I	
Audak Company	25	International Resistance Co.	7
B		J	
Bell Sound Systems, Inc.	53	Jefferson Electric Co.	41
Bendix Products Corp.	29		
Birnback Radio Co.	62	K	
Brush Development Co., The	57	Ken-Rad Tube & Lamp Corp., Inc.	62
C		Mc	
Centralab	39	McMurdo Silver Corp.	57
Clarostat Mfg. Co., Inc.	55		
Clough-Brengle Co., The	60	M	
Continental Carbon, Inc.	53	Mallory & Co., Inc., P. R.	Second Cover
Cornell-Dubilier Corp.	46	Micamold Products Corp.	5
Cornish Wire Co., Inc.	60	Muter Co., The	57
Curtis Condenser Corp.	62		
		N	
D		National Carbon Co., Inc.	31
Dumont Electric Co., Inc.	55	National Union Radio Corp.	49
E		O	
Electric Amplifier Corp.	61	Ohmite Mfg. Co.	33
Electro-Voice Mfg. Co.	62	Operadio Mfg. Co.	61
F		R	
Fox Sound Equip. Corp.	62	RCA Mfg. Co., Inc.	Fourth Cover
		Racon Elec. Co.	52
G		S	
General Electric Co.	3	Radio & Tech. Publ. Co.	61
General Transformer Corp.	61	Radio Service Institute	51
		Raytheon Production Corp.	36
		Readrite Meter Works	25
		Rider, John F., Publisher	23
		Royal Typewriter Co., Inc.	62
		S	
		Solar Mfg. Corp.	Third Cover
		Sprague Products Co.	59
		Supreme Instruments Corp.	45
		T	
		Technical Appliance Corp.	33
		Thordarson Elec. Mfg. Co.	51
		Tobe Deutschmann Corp.	43
		Transducer Corp.	59
		Triad Mfg. Co., Inc.	53
		Triplett Elec. Inst. Co.	8
		Tung-Sol Lamp Works, Inc.	29
		U	
		United Transformer Corp.	27
		Universal Microphone Co., Ltd.	62
		Utah Radio Products Co.	49
		W	
		Ward Leonard Elec. Co.	51
		Ward Products Corp.	55
		Webster-Chicago	39
		Weston Elec. Inst. Corp.	35
		Wholesale Radio Service Co., Inc.	33
		Wright-DeCoster, Inc.	55
		Y	
		Yaxley Manufacturing Division	Second Cover

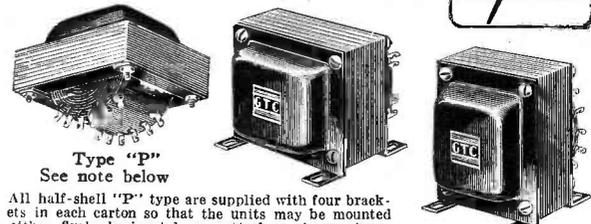PULL & PUSH
MOISTURE PROOFED TRANSFORMERS



Type "P"
See note below

All half-shell "P" type are supplied with four brackets in each carton so that the units may be mounted either flush, horizontal or vertical as shown above.

FREE Form 31—bulletin listing transformers and chokes to meet service engineers' every need.

GENERAL TRANSFORMER CORPORATION
 502 S. Throop St., Chicago, Ill.


The OPERADIO Line
is the Profit Line—
your one dependable source of supply

Ask About Our New Time Payment Plan for **UNIT-MATCHED** PUBLIC ADDRESS EQUIPMENT and RADIO SET REPLACEMENT SPEAKERS

SEND FOR CATALOGS 10 and 10D Address Dept. S

OPERADIO MANUFACTURING COMPANY
 ST. CHARLES ILLINOIS

RADIO AMATEUR CALL BOOK

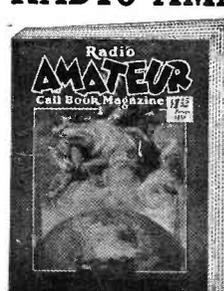

is the only publication listing all radio amateurs throughout the entire world. It also includes a complete list of High Frequency Commercial Stations, International Abbreviations and "Q" Signals, High Frequency Press and Weather Schedules, "Q", "R" and "T" Signals, U.S. Radio Inspection Districts, International Prefixes.

Every radio amateur should have a copy of this valuable book. Always up-to-date, published quarterly, single copies \$1.25, annual subscription \$4.


RADIO AMATEUR CALL BOOK, Inc.
 612 So. Dearborn Street Chicago, Illinois

I.F.'s
RMA COLOR CODES
Ignition Interference Data
Wire Tables
Case Histories
Trouble Shooting
WIRING DIAGRAMS
AUTOMOBILE
TUBE DATA

Get all this invaluable job data in the new enlarged edition of
RADIO FIELD SERVICE DATA

Every radio service man needs Ghirardi's new loose-leaf data book for quick and handy reference. As a time- and money-saver it has no equal anywhere! The "Case Histories" section alone (with trouble symptoms and remedies for over 1,500 receivers) is worth many times the cost of the book, to say nothing of the 5,424 "I.F." listings, etc., etc.

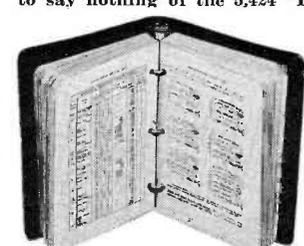With the **SUPPLEMENT SHEETS** issued twice a year you can always have the latest authentic data right at your finger tips. **SEND THE COUPON TODAY! MONEY-BACK GUARANTEE.**



2,199
 Pre-tested IDEAS on how to get more business. You'll get them all in another brand-new book—
"RADIO BUSINESS Promotion and Management"
 Explains everything about the business side of radio work. How to start and run a radio business. How to sell radio sets and service. How to advertise. Practical, proved methods and ideas. The first and only book of its kind! Ready this month. Send now for **FREE CIRCULAR BB.**

436 Pages
81 DIAGRAMS
26 CHARTS & TABLES
\$2.50
 with Jan. & June '37 SUPPLEMENTS

Combination Offer: Ghirardi's 1300-page **MODERN RADIO SERVICING** together with **RADIO FIELD SERVICE DATA— \$6**

45 Astor Place, New York, Dept. S-17
 Radio & Technical Publishing Co.

Enclosed find \$6 for Combination Offer on both servicing books, including Jan. & June '37 Supplements to DATA book. Postpaid. (Foreign \$6.50.)

Enclosed find \$2.50 for **RADIO FIELD SERVICE DATA** alone, with Jan. & June '37 Supplements. Postpaid. (For. \$3.)

Please send free circulars on both servicing books.

Please send free circular (BB) on new Radio Business book.

Name

Address

HOW DO YOU DO IT?

How do you solve the many servicing problems with which you have to contend . . . what special kinks have you worked out which help you in servicing receivers . . . have you developed shortcut schemes for testing, or built test devices that do the work better and faster? No matter what the scheme or the device, there are many Service Men who would like to know the how's and why's—just as you would like to know about the schemes and devices employed by others.


All you have to do is give us the outstanding points, and a rough pencil sketch of the device if it happens to be such—and we will do the rest. Write up those ideas now and send them into the . . .

ON THE JOB DEPARTMENT

ELAMCO **AMPLIFIERS** fulfill every public address need!

NEW—radically different—unique in design—embodying exclusive features heretofore found only in the most expensive custom-built equipment. Yet ELAMCO Amplifiers are most reasonable in cost. In the best interests of your business, write for new Series B and C bulletins—NOW. They will show you how to increase your P. A. profits. Strict Dealer Policy.

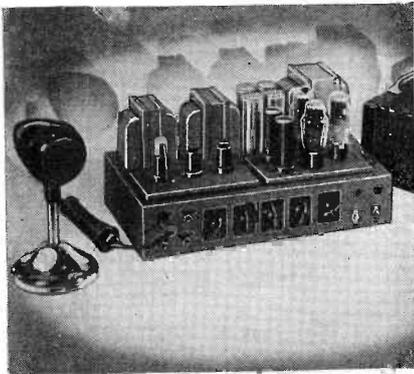ELECTRIC AMPLIFIER CORP., 133 WEST 25th STREET, NEW YORK CITY



NEW

Non-Reactive Dynamic Beam-Power Amplifier and Streamlined Bullet Electro-Dynamic Microphone.

Available at an almost unbelievable Low Price!

Provides unrestricted frequency response, two-phase bridge rectification, variable polar characteristics, etc., etc.

Write for Circular No. 3714 for complete details.

development by A. C. Shaney.
AMPLIFIER CO. of AMERICA
 39 West 20th Street New York, N. Y.



Switch-O-matic All Wave Antenna

Here is an all-wave antenna kit that really will improve your reception because it has been factory connected and soldered to eliminate incorrect and poor connections.

FEATURES include: Easy to install. Antenna Transformer matches impedance to transmission. No signal loss in transmission to receiver coupler. No switching for s.w. or broadcast.

No. 375—All Wave Antenna. \$4.25 ea. list
 No. 376—All Wave Antenna for sets with built-in aerial selector. \$3.50 ea. list

See your jobber. If he cannot supply you, write direct to Dept. S-1.

BIRNBACH RADIO CO.
 145 HUDSON ST. BIRCO NEW YORK, N. Y.

Curtis Electrolytic CONDENSERS



Our exact duplicates enable you to make satisfactory repairs on all makes of radios.

Patent No. 1,950,352

CURTIS CONDENSER CORPORATION

3088 WEST 106TH ST. CLEVELAND, OHIO

Export Office: 135 Liberty Street, New York City—Cable: "Tapei"

ELECTRO-VOICE




Public Address men, everywhere, are standardizing on ELECTRO-VOICE microphones. Constant improvement resulting from unceasing research keeps this line ahead of the field. When you buy an ELECTRO-VOICE product, you buy the latest in engineering design.

Six Velocity models priced from \$19.50 to \$75.00 list. Carried in stock by leading distributors.

ELECTRO-VOICE MFG. CO., INC.

332 E. Colfax Ave., South Bend, Ind.

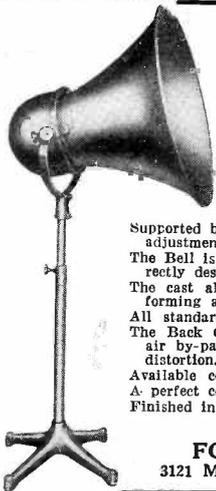Export Office: 100 Varick St., New York, N. Y.



OUTSTANDING! The New Fox B-5 Universal Baffle Type Horn

Quality construction. Completely universal in directional characteristics.

Supported by a sturdy adjustable cradle complete with lock screw adjustment.

The Bell is made of FOX special alloy horn material and is correctly designed for utmost output.

The cast aluminum throat collar reinforces the entire assembly, forming a perfect foundation for speaker mounting and cradle. All standard 12-inch speakers can be used.

The Back Cover is of heavy horn material and has the proper air by-pass so that the speaker can breathe, thus eliminating distortion.


Available complete with adjustable stand.

A perfect combination for indoor or outdoor work.

Finished in standard aluminum gloss or Fox special wrinkle.

Write for catalog sheets and prices.

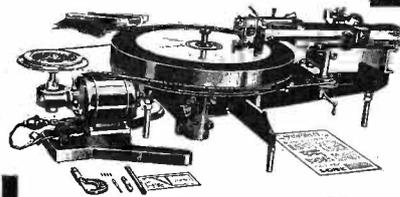FOX SOUND EQUIPMENT CORP.
 3121 Monroe Street Toledo, Ohio



Record Piano Music at 33 1/3 R.P.M. with UNIVERSAL Professional Recording Machine

New, improved design—Scientifically correct—Superlative performance—Solid, heavy, dependable—Precision machined for long and continued use—16-in. distortion proof turntable disc—Constant speed rim drive—110 volt A.C. 100% synchronous reversible motor—Individually calibrated timing bar provides for both 33 1/3 and 78 R.P.M. at 90, 110, and 130 lines per in.—Solid steel bar slide—The climax of four years of research and experiment—Positively the last word in instantaneous recording equipment.

Write for latest folder giving detailed description.

UNIVERSAL MICROPHONE CO., Ltd.

424 Warren Lane, Inglewood, Calif., U. S. A.

★ ALWAYS CARRY **Ken-Rad** Radio Tubes

Ken-Rad genuine all-metal radio tubes are dependable. They give outstanding performance. Write for information.
KEN-RAD TUBE & LAMP CORP., INC.
 Owensboro, Ky.

Also manufacturers of Ken-Rad Incandescent Electric Lamps

BUSINESS VOTES ROYAL FIRST




First in Speed, First in Ease, First in Capacity, First in Economy, First in Durability. 17 exclusive improvements—more than 100 refinements. Phone for a demonstration of the New Royal. . . . Compare the Work!

ROYAL TYPEWRITER COMPANY, INC.

2 PARK AVENUE, NEW YORK CITY
 Branches and Agencies the World over.

EASY-WRITING ROYAL

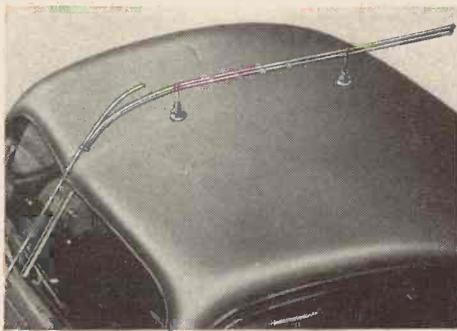RCA Auto Antennas offer wealth of fine features for High Efficiency!



RCA AUTO-TOPTENNA

Stock Number 9792—List price \$5.00

CHECK THESE FEATURES:

- ✓ ELIMINATES WHEEL STATIC AND MOTOR NOISE.
- ✓ Fits all cars—all models.
- ✓ Provides simple installation. Drilling in steel top unnecessary.
- ✓ Streamline design enhances beauty of any automobile.
- ✓ Removable without mutilating car. A chromium button is furnished to restore cowl if antenna is removed.
- ✓ Triple-chromium plated, has molded bakelite insulators.
- ✓ Special cement furnished for suction cups.
- ✓ Operation not affected by climatic conditions.
- ✓ A special shielded fitting to cover inside terminal of this antenna is also included. Insures perfect shielding—prevents possibility of noise pickup in antenna terminal.

For 1937 RCA offers you the finest line of auto antennas, complete "from top to bottom"—both as to location and price. Scientifically designed antennas, ranging from \$1.50 to \$6.00 list. They're universal—designed for use with all makes of radios and autos. They're streamlined for the new 1937 cars. See the many features of RCA auto antennas.




RCA AUTO-WHIPTENNA

Stock Number 9793—List price \$3.50

CHECK THESE FEATURES:

- ✓ ELIMINATES WHEEL STATIC AND MOTOR NOISE.
- ✓ Quickly installed—usually less than five minutes—no drilling required.
- ✓ Attaches to hinge pin of any car.
- ✓ Extremely efficient for maximum signal pickup.
- ✓ Extremely flexible—guaranteed unbreakable.
- ✓ Triple-chromium plated with molded all-weather rubber insulation; attractive appearance.
- ✓ Same model fits all cars.
- ✓ Easily installed... you merely remove hinge bolt on either side of car, attach antenna, and return the bolt. That's all there is to it—no drilling, no holes or cementing to top necessary.

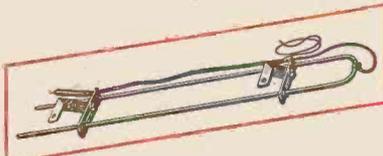

RCA DI-POLE AUTO ANTENNA

Stock Number 9605

List price \$2.60

An under-car antenna that provides efficient station pickup and also eliminates ignition noise pickup. This antenna can be simply, quickly and easily installed.

For weak signals RCA Inl-antenna gives high signal pickup. Stock No. 12322—list price \$5.00... for quick installation RCA Roof Antenna. Stock No. 7622—list price \$1.50.

RCA presents the Metropolitan Opera every Saturday afternoon. And "Magic Key of RCA" every Sunday 2 to 3 P. M., E. S. T. Both on NBC Blue Network.



Parts for PROFIT

RCA Manufacturing Co., Inc., Camden, N. J. • A service of the Radio Corporation of America