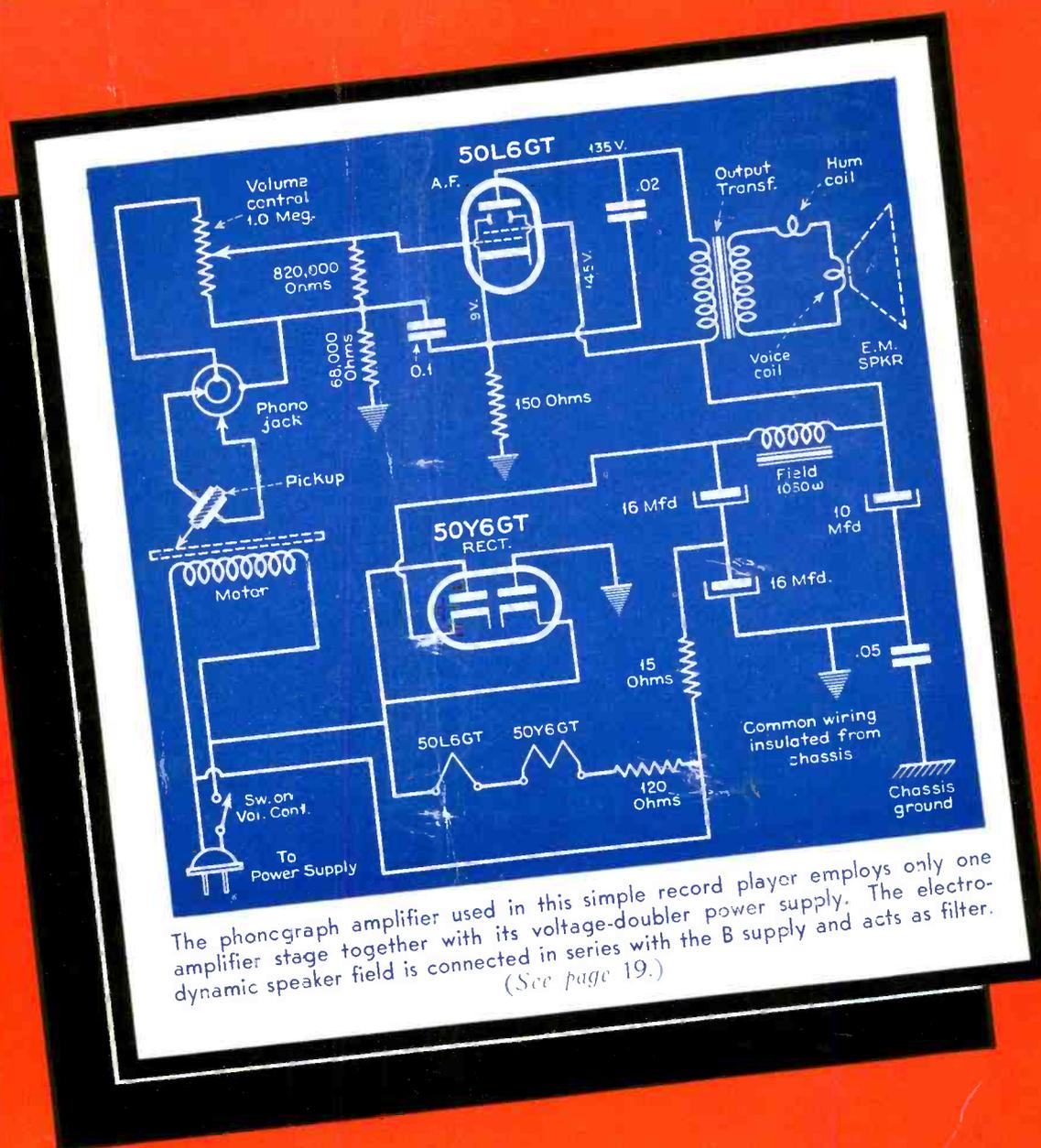


SERVICE



APRIL
1942



This, Too, Is In The Line Of Duty

The radio service engineer has a home front job. It is not spectacular. It involves more irritations than cheers. But it is all-important, this task of maintaining radio sets in good working order. It calls for knowledge, ingenuity and time-proven, standardized replacement parts.

Mallory appreciates the obstacles of material shortages and production restrictions that confront radio servicemen in wartime. Mallory is playing its role in war production, but Mallory likewise is doing its level best to keep you properly supplied with adequate parts—quality standardized parts—Mallory Approved Precision Products.

And if you're not using Mallory friendly technical help that is yours, free for the asking—you're missing the biggest contribution Mallory has ever made to the radio service fraternity.

Mallory engineers have made mighty strides in adapting parts production to available materials without sacrificing quality. Mallory research is working incessantly to develop new helps, anticipating the future and maintaining the leadership that for years has caused the radio service fraternity to say, "We always can rely on Mallory and Mallory Distributors."

P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA

Cable "Pelmallo"



Pledge

**TRIPLETT MEN AND WOMEN
HAVE SIGNED THIS PLEDGE
TO AMERICA'S VICTORY**

The Nation needs us strong—

I WILL KEEP FIT!

Lost hours help our enemies.
My working time is America's time—

I WILL TAKE NO "TIME-OFF"!

Carelessness causes accidents.
Accidents annually cost enough man-hours to build 15,000 bombers—

I WILL BE CAREFUL!


Some American soldier may die if indifference to
the importance of small jobs results in poor work—

I WILL KEEP MY INTEREST!

The future welfare of America will rest upon the increased
knowledge which will emerge from present necessity—

I WILL ADVANCE!

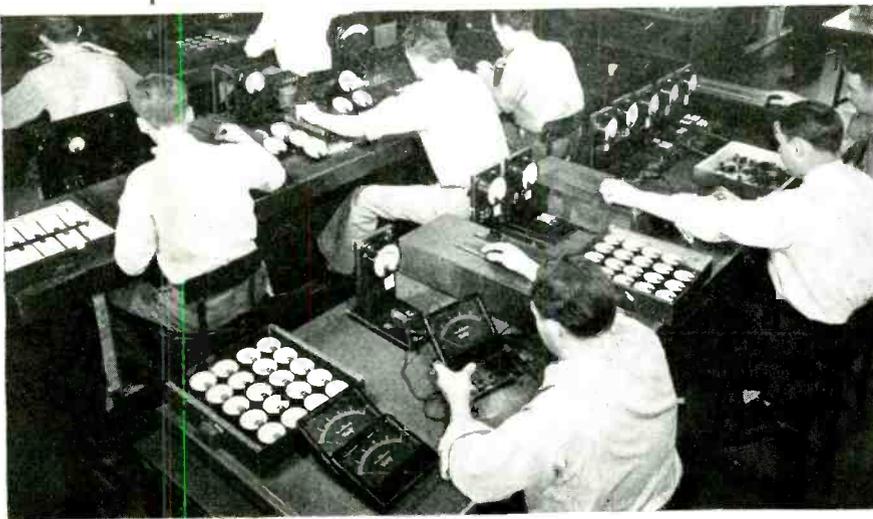These things I PLEDGE that our future
may be secure for Life, Work and Service.



Accuracy—as Ever

Despite the rush of present production there is no relaxation from rigid requirements of accuracy in calibration and inspection of fine Triplett instruments. No compromise is permitted to affect in the slightest those exacting standards which have become the international Hallmark for precision and quality.

TRIPLETT ELECTRICAL INSTRUMENT CO.

BLUFFTON, OHIO

SERVICE, APRIL, 1942 • 1

OUR EXPERIENCES in the field of late seem to indicate that manufacturers, jobbers and Service Men have not taken the trouble to study the priorities and allocations system in connection with their orders and purchases. Some manufacturers and jobbers, for example, have been accepting orders for equipment, which to obtain, requires a priority of the highest type. Somehow they hope that there still is a possibility of obtaining it. On the other hand, Service Men have been peeved at other jobbers who have refused to take such orders. In general, there are complaints all around over very slow deliveries on items that can be obtained.

With the country at war, we have been told again and again by our leaders that business as usual is no longer possible. We must put up with all types of inconveniences, delays and sacrifices to enable full use of the country's facilities for war production. And, too, we should study the situation to determine just what types of things we can't get for non-military use, what we can get for essential civilian use, and what items we can possibly substitute for those we can't get.

AIRCRAFT engineering departments are sorely in need of electrical meters for design and test work. With meter manufacturers overloaded with orders, however, even the aircraft industries' A-1-A priority rating can't get deliveries quick enough to permit this vital part of our war effort to go full-speed ahead.

The aircraft producers are willing to pay good prices for any such meters that they can purchase, and have enlisted the aid of SERVICE in an effort to obtain them from our readers. D. E. Gaskill, of the purchasing department of Lockheed Aircraft, suggests that all owners of meters of any type submit lists of such equipment to SERVICE Magazine. The lists should contain all details such as make, model, range and case style, and should also indicate the condition of the instrument.

After the war, when amateur and private activity can be resumed an ample supply of new instruments, undoubtedly of highly improved design, will be available. It therefore seems advantageous to all concerned for you to turn in every spare item immediately.


	Page
Census of Radio Receiver Ownership (Chart)	24
Keep Them Listening	24
Railroad Sound. <i>By A. B. Armistead</i>	5
Record Player	19
Ser-Cuits. <i>By Henry Howard</i>	7
Solving Shortage Problems in A-F Circuits. <i>By Robert G. Herzog</i>	13
Wien Bridge Audio Oscillator. <i>By Robert Stang</i>	16
Book Reviews	31
Case Histories	18, 22
Circuits	
Airline 14BR683 Antenna Input	18
Airline 14BR736B	12
Belmont 12A52	11
Emerson FV426, FV433	8
Output Tube Circuits	13, 14
Phase Inverter Circuits	14, 15
Railroad Sound Switching and Interconnections	5, 6
RCA 26BP	7
RCA QU56C, QU56M Service Note	22
RCA R56, RS119 Record Player	Front Cover
Silvertone 7056	11
Silvertone 7069 Production Change	22
Silvertone 7071 First Detector-Oscillator	12
Silvertone 7083, 7087, 7089	7
Silvertone 7112	8
Wilcox Gay A105 Recorder Combination	30
Cover Diagram	
Record Player (RCA R56, RS119)	19
Index to Advertisers	32
Manufacturers	
Catalogs, Bulletins, Etc.	26
Displays	21
Expansion	26
New Products	25, 26
News	27
Personnel	28
Trade Jottings	27
Short Item	
Iron to Glass Seal	21
Sound	
Railroad Sound. <i>By A. B. Armistead</i>	5
Record Player (RCA R56, RS119)	19
Solving Shortage Problems in A-F Circuits. <i>By Robert G. Herzog</i>	13
Test Equipment	
RCA 158, 160B Cathode-Ray Oscilloscope Service Note	22
RCA 160 Cathode-Ray Oscilloscope Service Note	22
Wien Bridge Audio Oscillator. <i>By Robert Stang</i>	16

Copyright, 1942, Bryan Davis Publishing Co., Inc.

BRYAN S. DAVIS
PresidentF. WALEN
SecretaryChicago Office:
608 S. Dearborn Street
C. O. Stimpson, Mgr.
Telephone: Wabash 1903Published Monthly by the
**Bryan Davis
Publishing Co.**
Inc.19 East 47th Street
New York City
Telephone: PLaza 3-0483PAUL S. WEIL
General ManagerF. WALEN
Advertising ManagerA. GOEBEL
Circulation Manager
Wellington, New Zealand
Tearo Book Depot
Melbourne, Australia
McGill's Agency

OUT IN *Front*


with

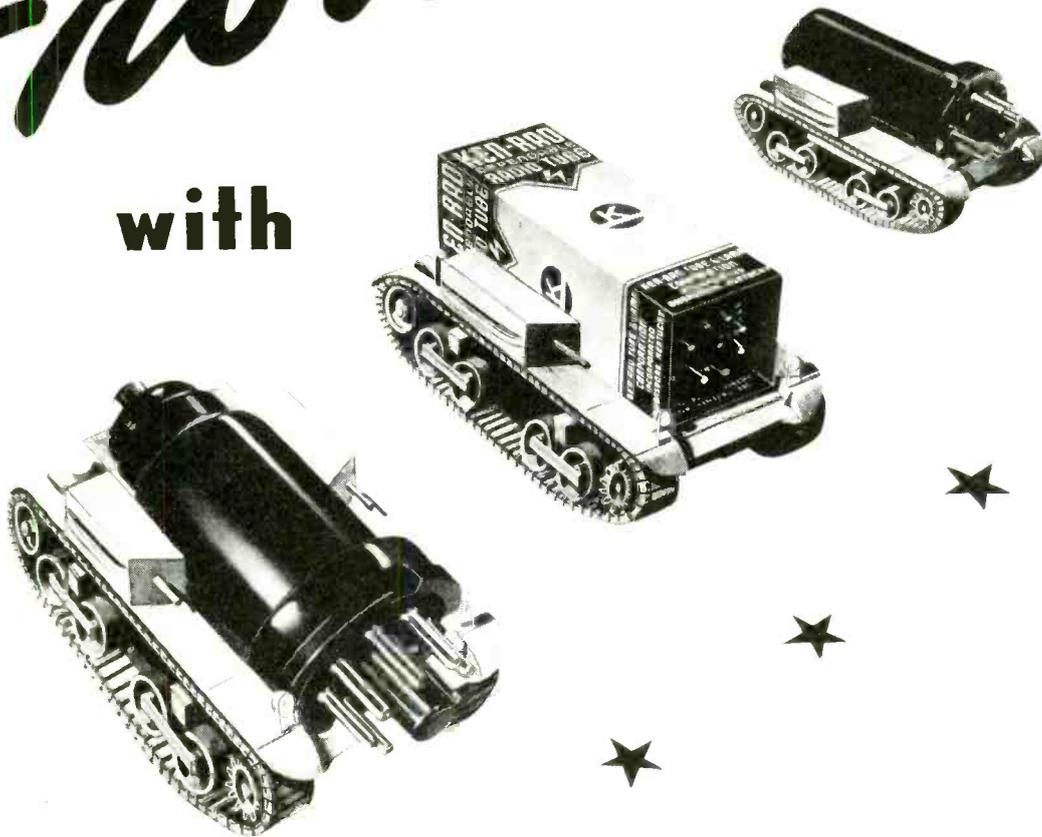

★ METAL TUBES

Yes, radios with metal tubes are out in front in performance. That's why we make and recommend them. That's why 80,000,000 are now in use.

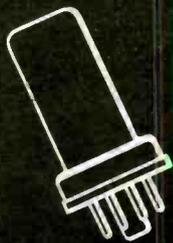Handle Ken-Rad Metal Tubes and Be Sure of Satisfied Customers.




KEN-RAD

Metal Radio Tubes



KEN-RAD TUBE & LAMP CORPORATION, Owensboro, Kentucky

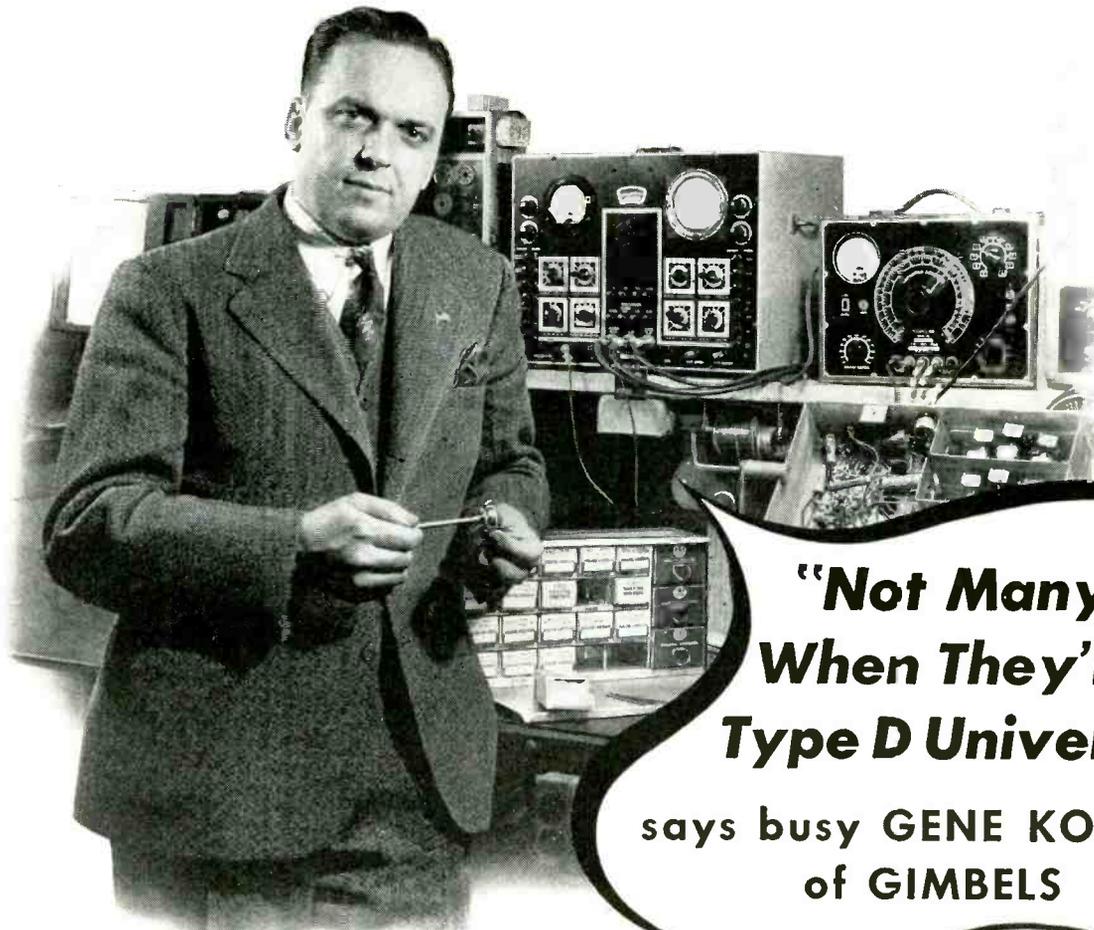HOW MANY VOLUME CONTROLS MAKE A SERVICE STOCK?



**"Not Many!...
When They're IRC
Type D Universals,"**
says busy **GENE KOEHLER**
of **GIMBELS**

Probably one of the busiest radio service departments in the East, is that of Gimbel's department store in Philadelphia, managed by Gene Koehler—and there you'll find the IRC Volume Control Cabinets with their 18 Type D Universal Tap-in Shaft Controls on the job in a big way.

"I've never checked your claim that the 18 controls in this cabinet will handle up to 87% of all control replacements," says Mr. Koehler, "but it sounds just about right. In handling hundreds of jobs a month, we seldom have to buy a control type that isn't included in the cabinet. This means a big saving in our time and a worthwhile increase in our efficiency—especially today when it is often difficult to get certain special controls.

"Often, when we think we're 'stuck' for a replacement that might take time to get from the factory, we're pleasantly surprised to

find a control of the proper electrical specification in the IRC Cabinet. Then, all we have to do is select the proper Tap-in Shaft. Seldom do we get a job where one of the four available IRC Shafts will not fill the bill.

"The IRC Control Kit also makes it easy to check our control stock. Actually, in a shop the size of ours, we have three Cabinets, each containing the full 18-control assortment so that we won't run short of any item on busy days. A glance at the empty compartments then tells us in an instant just what controls should be re-ordered.

"Type D Controls with Tap-in Shafts are a great idea—and so are the Kits. We certainly wouldn't want to be without either!"

Take a tip from Mr. Koehler! Put your servicing in tune with the times. See the IRC Master Control Kit at your IRC jobber's today.



Type D UNIVERSAL CONTROLS ... WITH TAP-IN SHAFTS



Four shaft types make it easy to select the right one for almost any job. Will not pull or vibrate loose once tapped securely into the control socket.

HANDLES 4 OUT OF 5 JOBS!...The 18 Type D Controls, 6 switches and 5 extra shafts in this IRC Master Control Kit handle from 70% to 87% of all control replacements. You pay only the regular net of \$14.97 (\$24.95 list) for the controls, switches and shafts. The All-Metal Cabinet is included at no extra cost!



INTERNATIONAL RESISTANCE COMPANY, 401 NORTH BROAD STREET, PHILADELPHIA, PA.

SERVICE

A Monthly Digest of Radio and Allied Maintenance

ROBERT G. HERZOG, EDITOR

RAILROAD SOUND

By A. B. ARMISTEAD

INSPECTOR OF TELEPHONES, TELEGRAPHS AND SIGNALS
NORFOLK AND WESTERN RAILWAY COMPANY

IT GOES without saying that the railroads have been sorely pressed in these serious times to keep up with the demand for their services. Many have expanded their facilities and others have reopened lines that have been unused for over a decade. In all these cases intercommunications facilities perform in a major role. Loudspeakers, intercommunicators, carrier-call systems, telephones and the like are doing their share to help the railroads do their best job for our war effort.

In connection with the construction of a new classification yard by the Norfolk and Western Railway at Roanoke, Va., recently, several types of communications systems were installed. These included PBX telephones

at all important locations, teletype printers in the yard office and retarder towers, a two-way carrier telephone between the hump conductor and the engineer of the hump locomotive, and a two-way loudspeaker system serving the yard offices, retarder towers, hump conductor, switchmen and brakemen.


The utilization of an extensive loudspeaker system for the purpose of maintaining communication between the various members of the operating personnel of a classification yard, while not new, involves some interesting considerations. From the technical stand-


point the requirements in this case are fairly simple: First, the system must be highly reliable. Second, there must be enough power output from the yard speakers to give adequate coverage and at the same time overcome such background noises as hissing steam, exhaust noises from the locomotives, clanking of coupling cars, etc. And, too, the system must be flexible in regard to selecting called stations, switching, etc.

Flexibility

In order to meet the requirements of flexibility, the RCA 50-watt amplifiers purchased, were co-related with pre-amplifiers and appropriate starting, switching and selecting circuits. The latter devices and connections were all

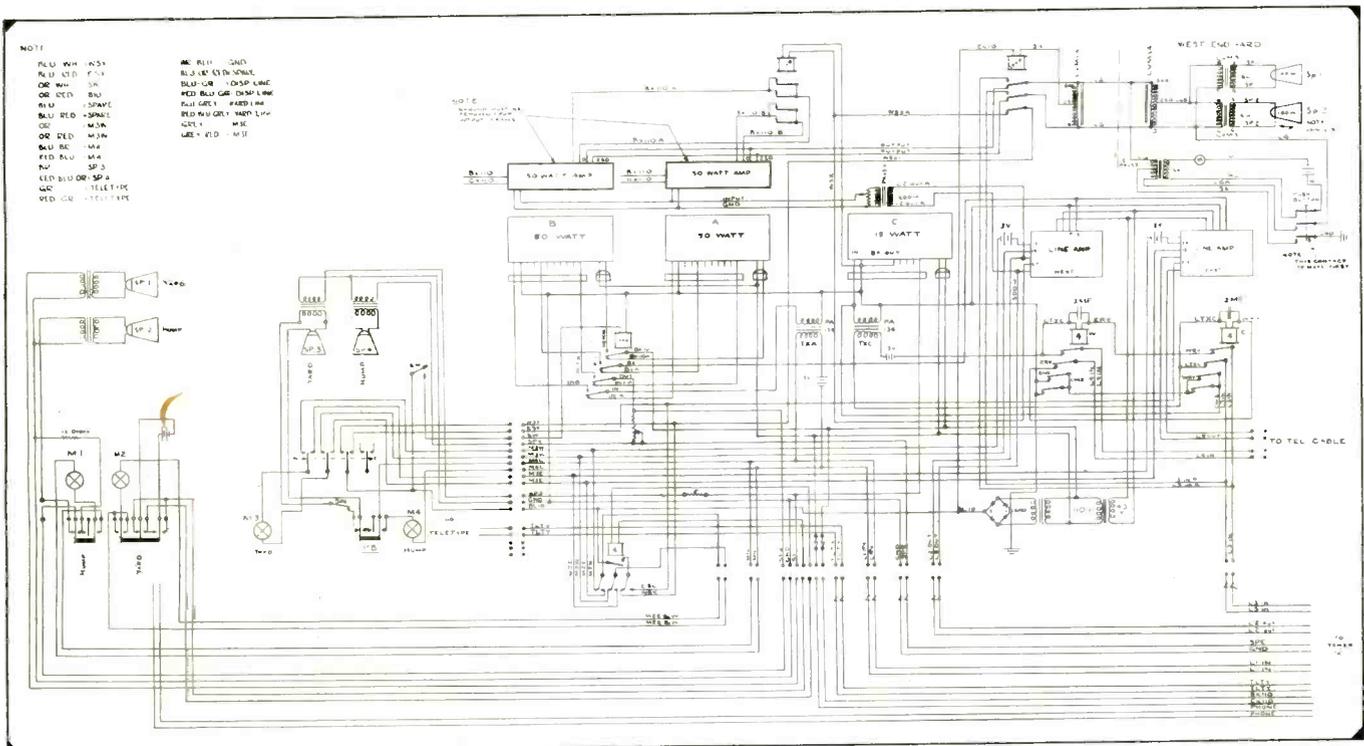A complete intercommunication system has recently been installed in the classification yards at the Norfolk and Western Railway Company in Roanoke, Va.



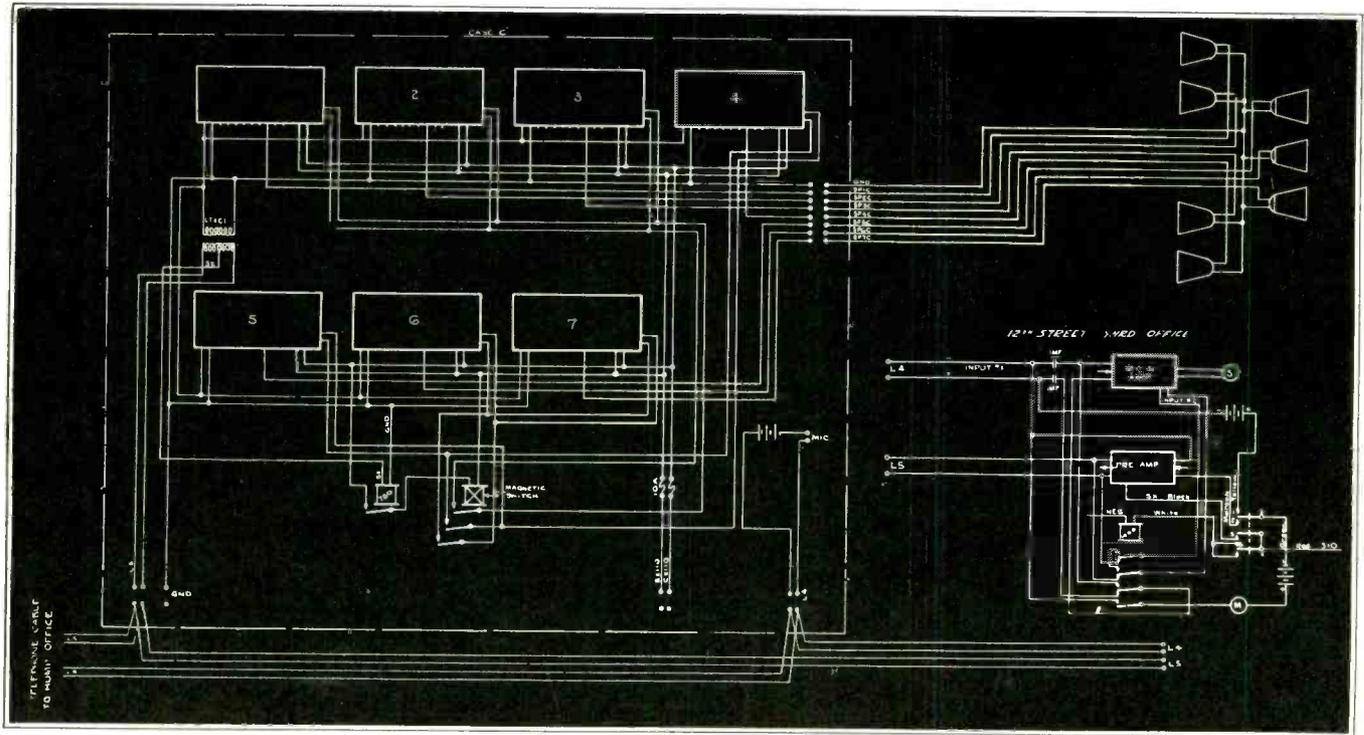

The loudspeaker system in the classification yards is completely interconnected by means of an efficient switching system.

designed, constructed and installed by the railroad company's engineers.

In this installation intelligibility is considered to be the paramount requisite and high-fidelity is not necessary. The tower speakers, especially, being mounted close to the operators, must be clear and crisp but not too loud. For this reason, in constructing the preamplifiers, special design features were included to cut-off all frequencies below approximately 300 cycles. The results achieved well warrant the effort spent in design. Speaker cone travel is reduced and all booming noise is absent from the output. Thus cone life is increased and a high degree of intelligibility is obtained.

The accompanying illustrations show the general layout involved in this in-

stallation, together with a diagram of connections and a circuit of the switching system. Upon the layout is indicated the locations of the various buildings, instrument cases, and towers utilized in this communication system installation.

The diagram of connections shows the relationship between the microphones and loudspeakers of the several groups; all related parts are indicated as tied to the same line. The physical location of each microphone-loudspeaker group is shown by the broken line extending to the associated track layout. The typical circuit diagram is illustrative of the electrical connections between the several elements of each microphone-loudspeaker group.


Standard equipment has been adapted and used throughout the loudspeaker system in the classification yards in this Southern railway.

As shown by the diagram of connections, microphones at both the hump and the yard office simultaneously control the clustered loudspeakers on Towers Nos. 1 and 2. The same two microphones may be switched to simultaneously control the clustered loudspeakers on Tower No. 3, and the loudspeaker in the Twelfth Street yard office. Microphones located at the East-bound switchman's shanty, and scattered across the distribution yard, control the loudspeakers at the hump and in the yard office.

Equipment

All the equipment mentioned, other than the microphones and loudspeakers, is contained in steel cases and is connected to the various control points and loudspeakers through underground cable. Care is being taken to prevent

(Continued on page 20)

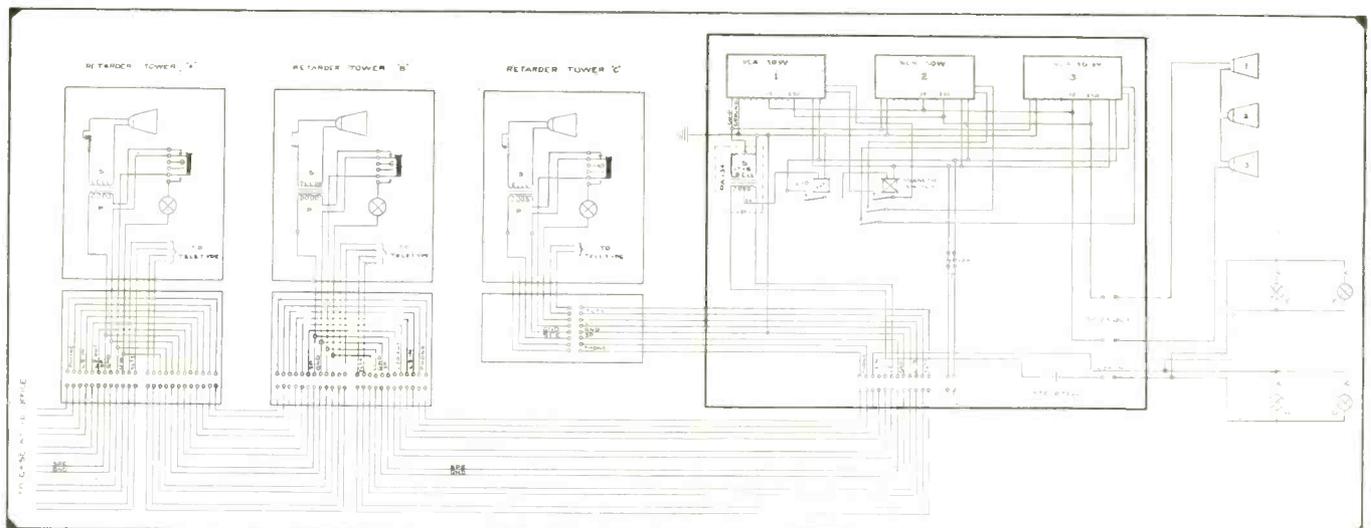

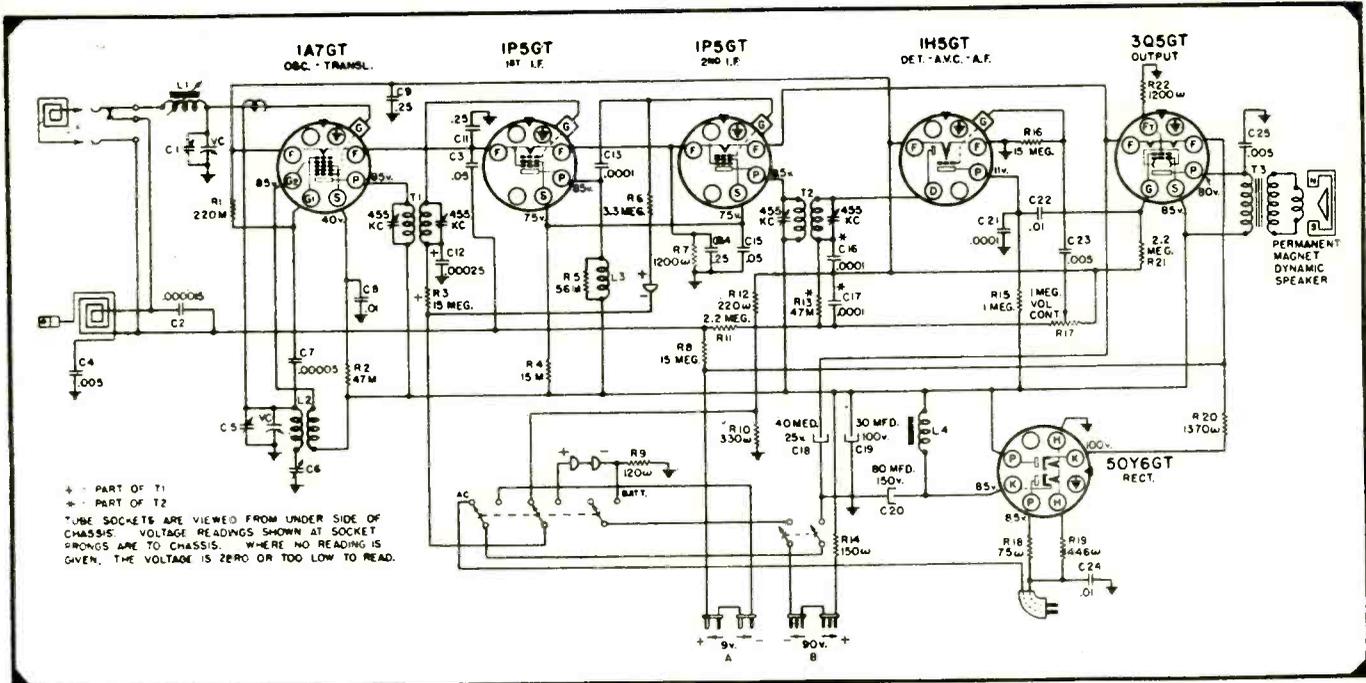


Fig. 2. Silvertone 7083, 7087, 7089.


SER-CUITS!

By HENRY HOWARD

WITH THE ARRIVAL of spring, battery portables again take precedence—not that they have been up in the attic during the winter—for,

Fig. 1. RCA 26BP combination line and battery portable. A 117-volt rectifier supplies power for both plate and filament supply during line operation.

since the introduction of combined battery-line operation a few years back, these have been versatile all-year sets. Fig. 1 shows a typical 5-tube and rectifier well-designed, sensitive, portable RCA Model 26BP. This receiver uses a genuine 3-gang tuning with a complete r-f stage. Only the 1A7GT converter is served by avc, the r-f stage having a 2.2-meg grid leak supplying bias while the 1T4 i-f stage uses a 5.6 meg leak.

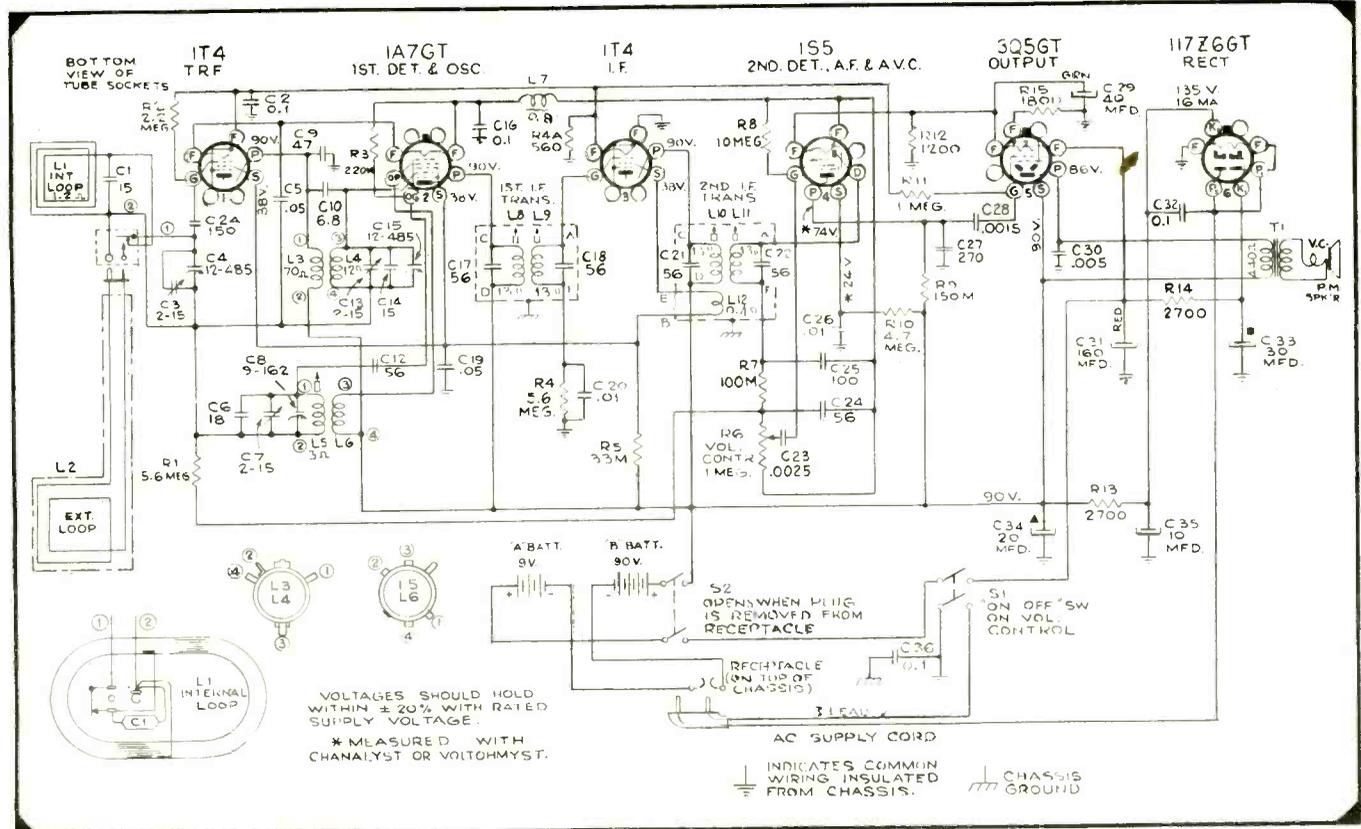

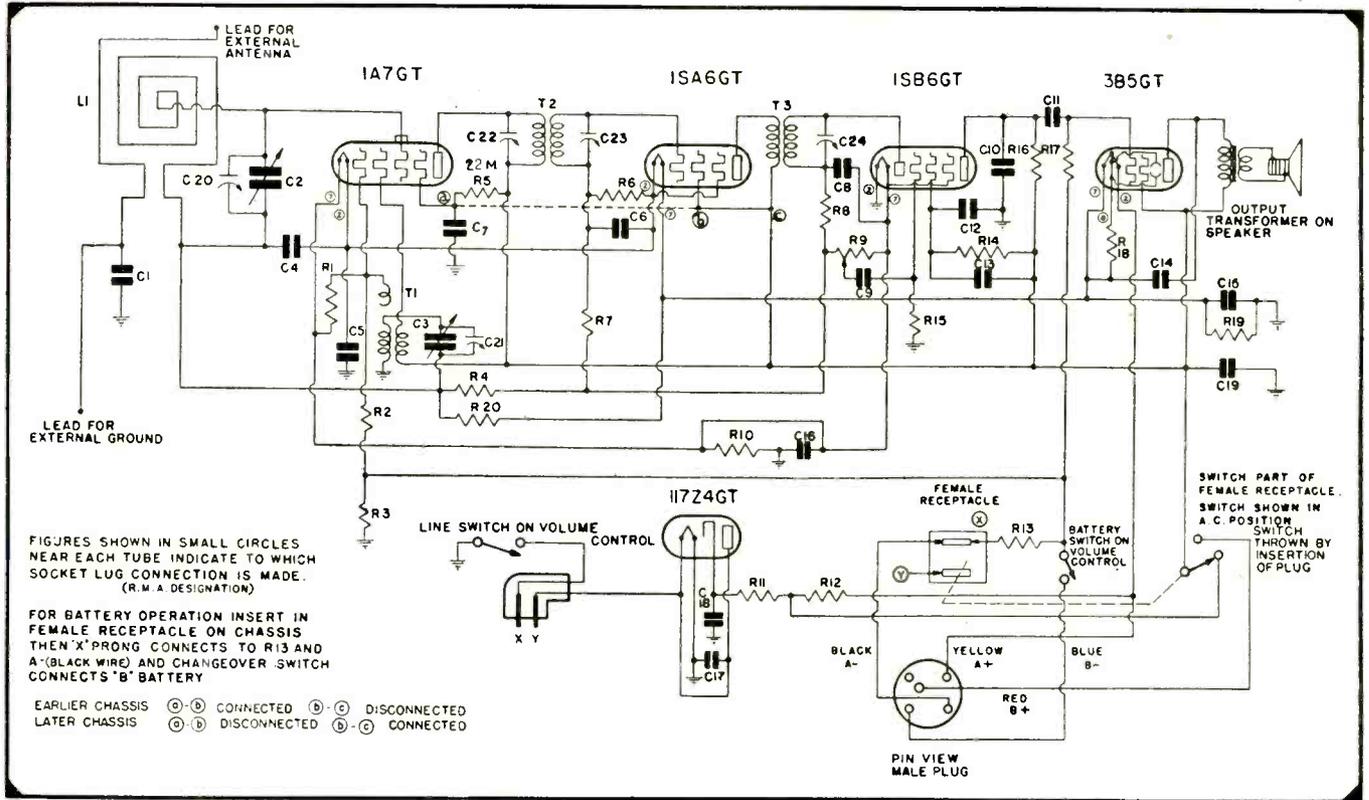


Fig. 3. Emerson FV426, FV433.

Note the arrangement in this stage with the 0.01-mfd by-pass. The i-f gain is increased by the use of a tickler coil in the screen-grid lead which we have mentioned in previous articles.

The filters in this receiver are rather complete. The filament supply comes from one section of the 117Z6GT rectifier through a filter consisting of 30-mfd, 2,700 ohms and 160-mfd. Another 40-mfd condenser is used after the first tube, the 3Q5GT. Note the 1,800-ohm equalizer resistor from the filament tap to ground. Between the i-f and converter filament an r-f filter is used. This consists of an r-f choke and 0.1-mfd by-pass condenser. A 560-ohm equalizing resistance is also used at this

point. The B-supply filter is conventional. The detector-avc filter uses 100 mmfd, 100,000 ohms, and 56 mmfd. An external loop may be bought as optional equipment when it is desired to operate the set in difficult locations.


Silvertone 7083, 7087, 7089

Silvertone Models 7083, 7087 and 7089 of Sears, Roebuck are 6-tube jobs with two i-f stages. Instead of the popular resistance coupling between the i-f tubes, this group of receivers use a

form of impedance coupling in which the first i-f plate load consists of a choke and a resistor in parallel. (See Fig. 2.) The second i-f grid return is through a 3.3-meg grid leak and a bias cell with *positive* towards the grid. This is part of the sensitively compensating circuit for low battery operation in which both i-f tubes are forced to draw plate current by keeping the grids from going too negative. Note two more bias cells in series which are applied to both i-f stages.

The rectifier circuit is quite unusual. One diode of the 50Y6GT is used as a half-wave rectifier while the other is used as a filament resistor. An 80-mfd condenser, filter choke, and 30-mfd, sec-

Fig. 4. Silvertone 7112.

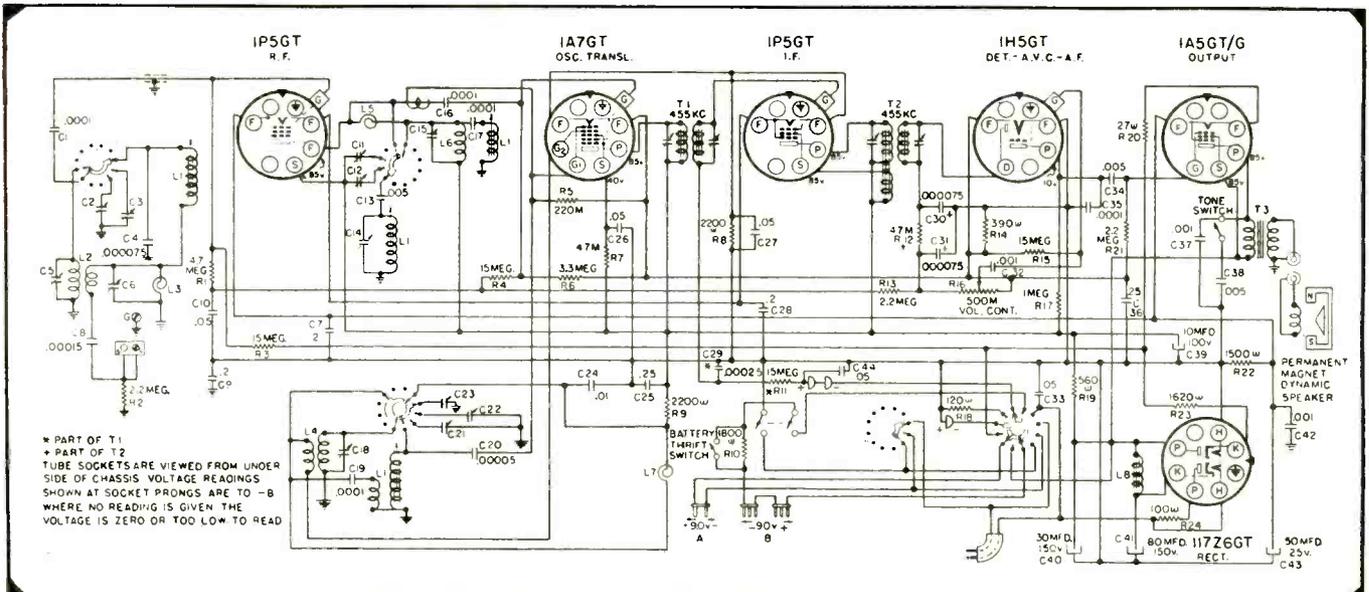

NATIONAL UNION *De Luxe* AMPLIFIER

15 Watts Output . . . Less than 3% Distortion . . .
at rated output . . .

Patented Circuit . . . Permits Extreme Compactness

W15A-
Amplifier includes set of 5 N U
Loktal Tubes.

W15A-C-
Portable Case Only — Imitation
Leather (space for Amplifier
W15A, Two 8" P.M. Speakers,
Microphone and Cable).

W15A-CS-
Portable Case with
2—8" P.M. Speakers.



The Patented Circuit Provides . . .

SMOOTH AND FLEXIBLE CONTROL OF BOTH VOLUME LEVEL AND TONE GRADATIONS OVER A WIDE RANGE . . . TWO MIKE INPUTS AND ONE PHONOGRAPH INPUT MAY BE SEPARATELY CONTROLLED OR MIXED FOR SIMULTANEOUS OPERATION . . . CONTINUOUSLY VARIABLE SEPARATE BASS AND TREBLE TONE CONTROLS . . . EASILY ACCESSIBLE FUSE . . . HOUSED IN COMPACT ATTRACTIVE GREEN CRACKLE FINISHED CABINET WITH PLASTIC IVORY KNOBS AND CARRYING HANDLE.

SPECIFICATIONS

Rated Output: 15 Watts.

Peak Power Output: 25 Watts.

Distortion: Less than 3% at Rated Output.

Tone Controls: 1—Bass Boost Control.
1—Treble Tone Control.

Frequency Range: ± 1 Db from 50 to 10,000 cycles

Input Circuits: Two high impedance microphones.
One high impedance phonograph.

Output Circuits: Variable Impedance Output. Two
Speaker Sockets. Each Socket
has Combination Voice Coil and
110 V A.C. Terminals

Output Impedances: 4-8-16-500 Ohms.

Power Considerations: 110-117 Volts 60 Cycle
A.C.

Power Consumption: 50 Watts.

Circuit: Special Patented Output and Bass Control
Circuits.

Tubes: National Union Loktal 2-7N7—2-7C5—1-7Z4.


Size: Extremely Compact 8⁵/₈ x 5⁵/₈ x 5⁵/₈.

Weight: 12 Pounds.

Ask Your N.U. Distributor or Write

NATIONAL UNION RADIO CORP.

57 STATE STREET, NEWARK, NEW JERSEY

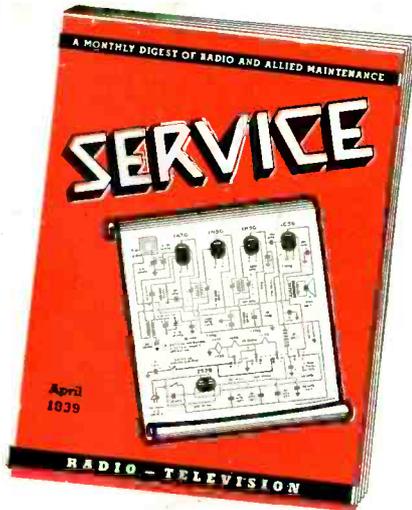

Geared to the Wartime Needs of Radio Service

SERVICE—19 E. 47th St., N. Y. C.

Please enter annual subscription (12 issues) for each of the undersigned for which payment is enclosed at the rate of \$1.00 each; foreign \$2.00. (This rate applies only on 4 or more subscriptions when occupations are given.)

Name

Address

City-State

Occupation

Title (Service Mgr., etc.)

Employed by

State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer

Name

Address

City-State

Occupation

Title (Service Mgr., etc.)

Employed by

State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer

Name

Address

City-State

Occupation

Title (Service Mgr., etc.)

Employed by

State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer

Name

Address

City-State

Occupation

Title (Service Mgr., etc.)

Employed by

State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer

—When Exact Duplicates are Unavailable

Data prepared by a group of leading receiver design engineers discussing various circuits and procedure necessary for making component substitutions.

—When even Substitutes are Unavailable

Articles by Editor Herzog and engineers from parts companies and laboratories dealing with repairs of components and accessories.

—When Industrial Electronic Service is Required

Technical discussions by Alfred A. Ghirardi and other engineers who specialize in electronic development—for industry, for control, for protective use.

—When the Latest Data on Circuits is Needed

Henry Howard's circuit analyses each month with diagrams and parts values.

—Sound—Case Histories—Shop Notes





Remember that until further notice the Group Rate **(\$1.00 Yearly instead of the regular \$2.00 Yearly)** is still in effect.

ond condenser form a 60-cycle filter for both A and B supplies. Another 40-mfd condenser is used after the 3Q5GT filament as a further filament filter. The equalizing resistor in this output tube is 1,200 ohms.

In addition to the electron coupling from oscillator to converter which is inherent in the use of the Type 1A7GT first detector tube, additional capacity coupling is provided to the control grid. These sets also use iron-core loop-load-



At the right is shown the RCA AVR100 aircraft receiver. Directly below is shown (Fig. 5) the circuit of the Belmont 12A52. At the bottom of the page (Fig. 6) Silvertone 7056.

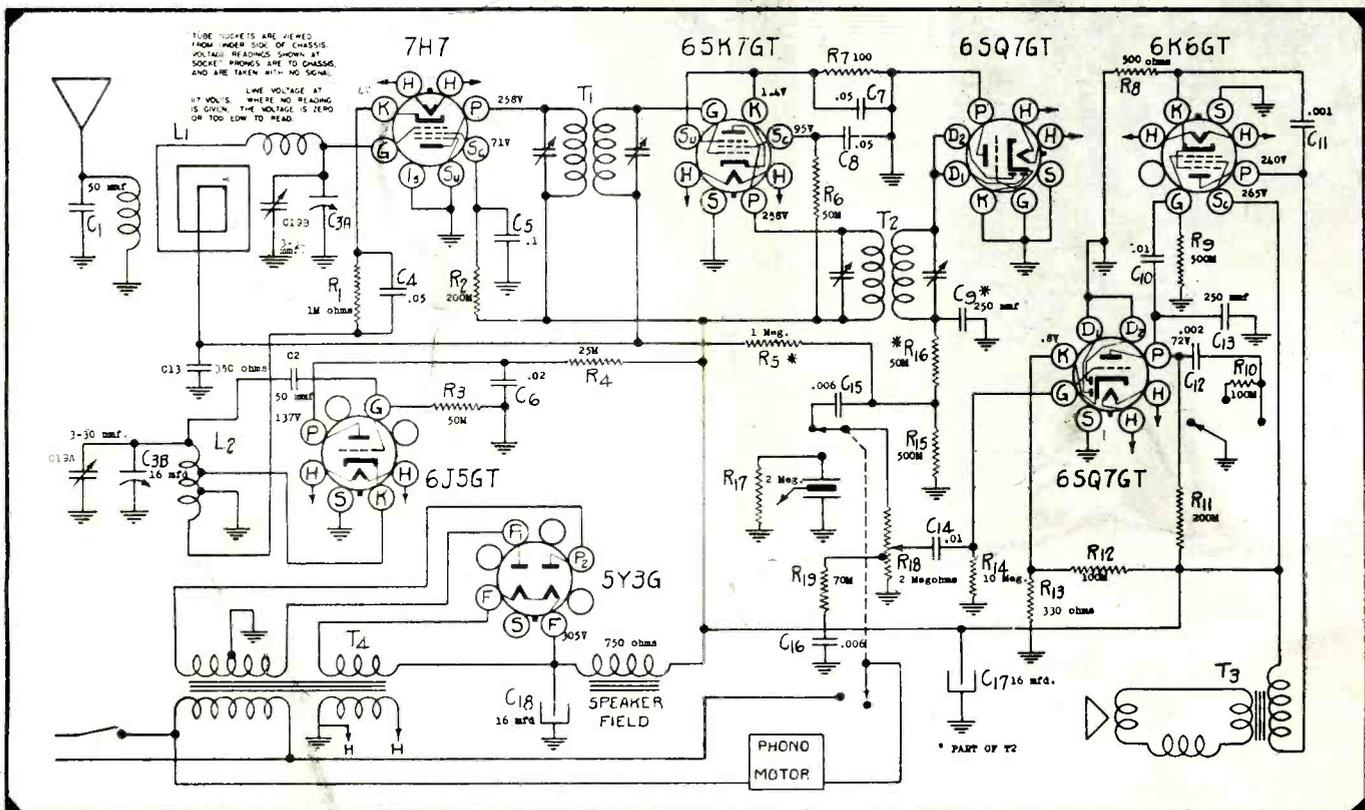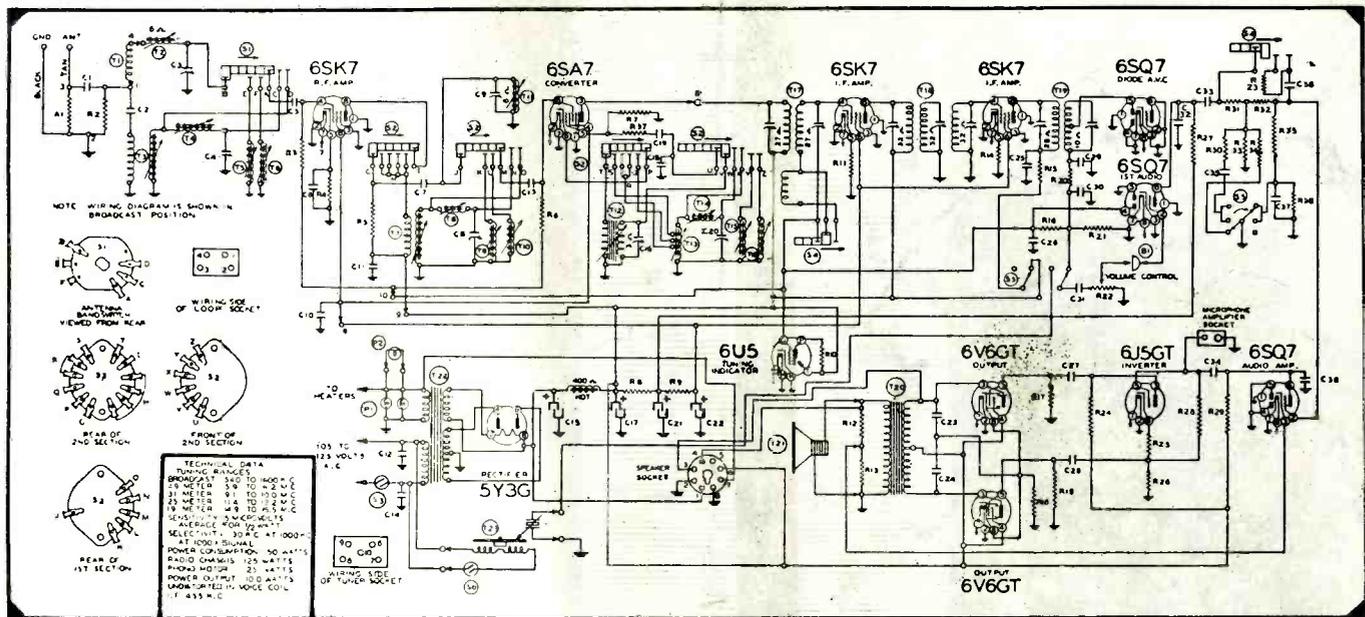

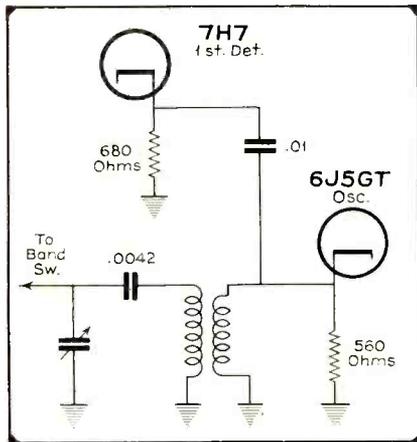


Fig. 7. Silvertone 7071.

ing coils and external loops may be plugged in when desired.

Emerson FV426, FV433

Emerson Models FV426 and FV433 are standard 5-tube battery and line portables which use a 117Z4GT rectifier. The 3B5GT beam-power tube derives its bias from oscillator r-f voltage taken from the grid circuit as shown in Fig. 3. Paralleling the 220,000-ohm grid leak is a network consisting of a 1-meg and 0.47-meg resistors in series, with the power tube grid return connected to the junction. The bias voltage is the half-wave rectified r-f of the oscillator frequency. Filtering action is obtained from the series resistors mentioned plus the 3.3-meg grid leak of the power tube combined with the r-f by-pass condenser (60 mmfd) from the first audio plate to ground. The audio coupling con-

denser is so large compared to the by-pass that it offers negligible impedance to the r-f.

The volume control has a dual on-off switch which opens both battery and line circuits. For battery-to-line switching a female receptacle is arranged to take the line plug, the insertion of which causes the change-over.

Silvertone 7112

Permeability tuning and 3-bandspread ranges are featured in Silvertone Model 7112, 6-tube battery and line receiver. Fig. 4 illustrates the r-f end showing the tuned r-f stage and the method of tuning to the 4 wave bands. Paralleled coils are used in addition to shunting condensers. Iron-cored i-f transformers are also featured and the second transformer has a tickler coil.

A 117Z6GT is employed as rectifier for line operation with a filter choke in the A and B filter. For economical operation from battery power a thrift switch is provided which cuts in an 1,800-ohm resistor in the minus B lead.

RCA AVR100, AVR101

A bit off the beaten path but of unquestionable interest, we believe, are two midget aircraft receivers for light planes—the RCA AVR100 and AVR101. These are extremely compact battery sets using five common portable series tubes: 1R5 mixer, two 1T4 i-f amplifiers, 1S5 second detector a-f and 1S4 output. Filament drain is 300 ma; B drain is 11-15 ma at 67½ volts, depending upon the volume control set-

ting. The normal frequency range of the AVR100 is 550-1500 kc, 195-405 kc. 278 kc (aircraft traffic control frequency) is claimed without disturbing the dial setting by throwing the waveband switch to a third position. Model 101 is only a beacon receiver covering 195-405 kc. The i-f of both sets is set at 490 kc.


The sensitivity of these midgets is equivalent to average commercial airline performance and the sets are designed to use both loop and standard antenna and one or two pairs of phones. When a beacon antenna is used, ignition shielding is not required in many installations. However, for loop reception, shielding is almost a necessity. The signal voltage, especially when operating on the null for direction finding, is much lower on the loop. Internal shock mountings permit operation under severe conditions. Weights are 3 lb, 7 oz with a battery of 4 lbs and cable of 6 oz. Where a transmitter is carried, the receiver battery may be eliminated.

Belmont 12A52

Belmont Model 12A52, a 12-tube, 5-band combination a-c receiver-phono job, has permeability tuning with a t-r-f stage, two tuned i-f stages with a triple-tuned transformer between them, and a 3-stage audio system with feedback and separate bass and treble tone controls. The i-f system has a wide-band response for high-frequency repro-

(Continued on page 29)

Fig. 8. Airline 14BR736B.

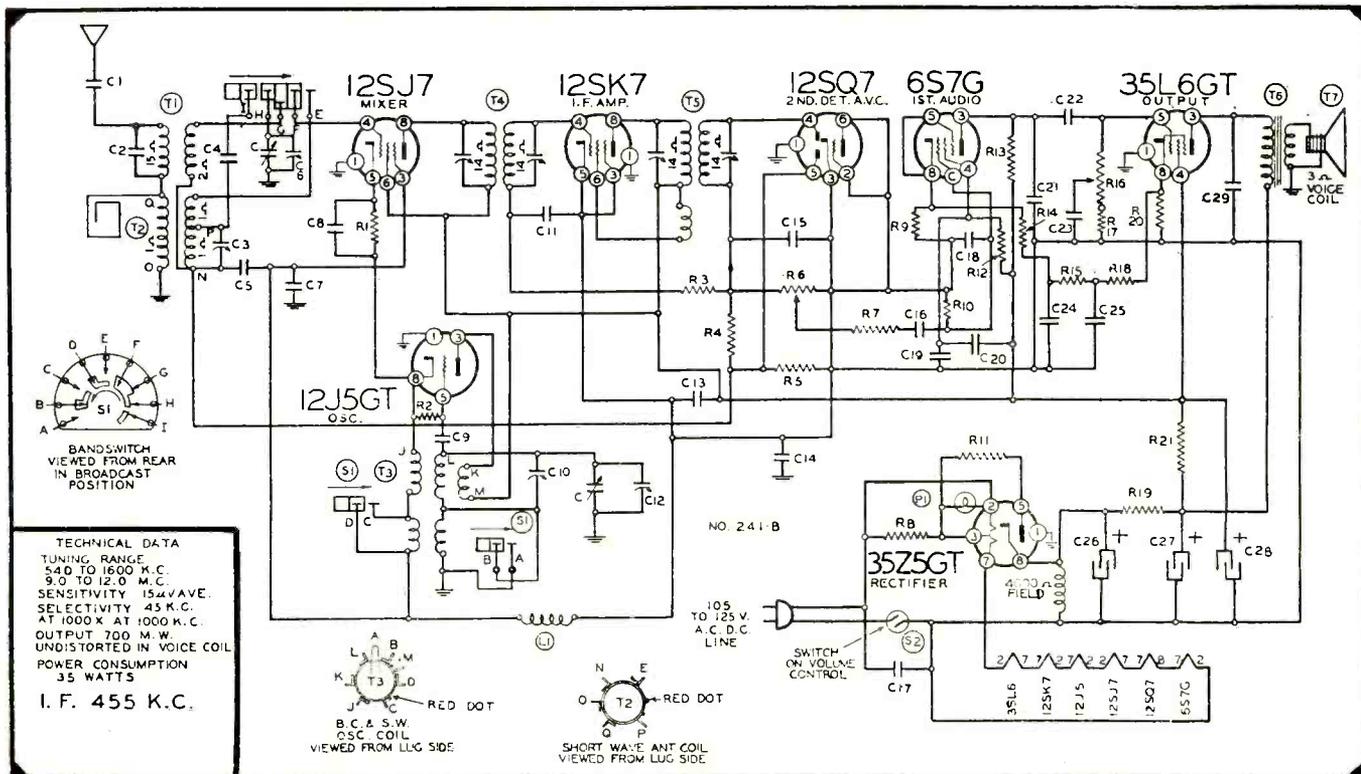

SOLVING SHORTAGE PROBLEMS In A-F Circuits

By Robert G. Herzog

EDITOR

IN THE PAST few months we have been presenting, in these columns, information covering the basic fundamentals of superheterodyne circuits. Typical circuits have been shown and their variations explained. It has been the purpose of this series to give the reader an understanding of underlying theory, in order to enable him to make slight alterations in the circuit constants and in design without impairing receiver performance, in the event of shortages of particular parts. Every attempt has been made to give complete information in simple form so as to cover as wide a scope as possible.

Various receiver circuits from the antenna input through the second detector and avc circuits have been covered in previous articles. This month's article deals with the audio-frequency portion of the receiver.

Resistance Coupling

In the early days of radio, audio stages were coupled by means of transformers. More recently resistance coupling has become practically the only method of interstage audio signal transfer. Almost without exception modern receivers use transformers only to couple the loudspeaker to the output tube.

Even in push-pull stages, resistance coupling is used universally in present-day receivers. To obtain proper condi-

tions for push-pull operation phase inverters are used. These devices were discussed at some length in the September, 1941, issue of SERVICE.¹

Audio Circuits

Audio amplifiers are generally well understood, although the reasons for the choice of certain values of resistance or capacity in coupling the audio stages are not always clear. In Fig. 1 the plate resistance for the triode amplifier tube, which is generally combined with the second-detector tube, is designated as R_p . The coupling condenser C and the grid resistor R_g are drawn in a rather unusual arrangement, primarily to show that these two components in series form a parallel circuit across the plate load resistance R_p . The a-c resistance of C and R_g together are almost always greater than R_p . Values for C range between 0.006 and 0.02 mfd in different makes of receivers; R_g from 100,000-ohms to 3 megohms in different models. The condenser C and the resistor R_g are paired and the choice of the value of one more or less designates the value of the other.

It cannot be stressed too greatly that the coupling condenser (C) must be of the highest quality obtainable. Any leakage in this unit will put a positive bias on the output tube. Such a bias will cause the tube to draw extremely excessive current and can lead to injury of the tube, and often, to the rectifier and power transformer as well.

The control grid of the output tube is connected between the condenser C

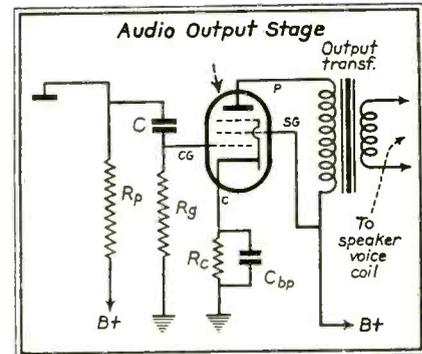


Fig. 1. A popular method of obtaining bias for the output stage is by means of a self-bias resistor connected in series with the cathode.

and the resistor R_g . These two elements can be compared to a potentiometer with the control grid of the output tube connected to the potentiometer arm. It will be recognized with this type of illustration that if condenser C is of small capacity, having a high impedance to low frequencies, the low-frequency signal fed to the grid of the output tube will be much smaller than the proportion of high-frequency signal which is passed along from the detector. Consequently, for good quality R_g should have high resistance and condenser C should be reasonably large.

Individual Variations

Figs. 1 to 4 inclusive show typical output stages. In Fig. 1, bias for the

Fig. 3. Part of the voltage drop across the speaker field is often utilized to give bias for the output stage by means of a voltage divider.


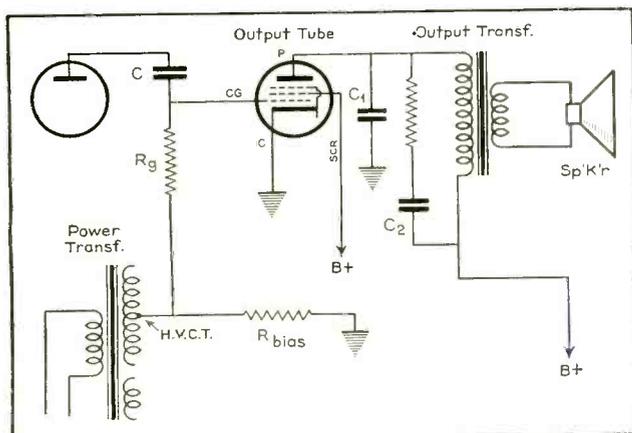


Fig. 2. Bias for the output tube is taken, in some receivers, from the drop across a resistor connected in the negative B supply return.

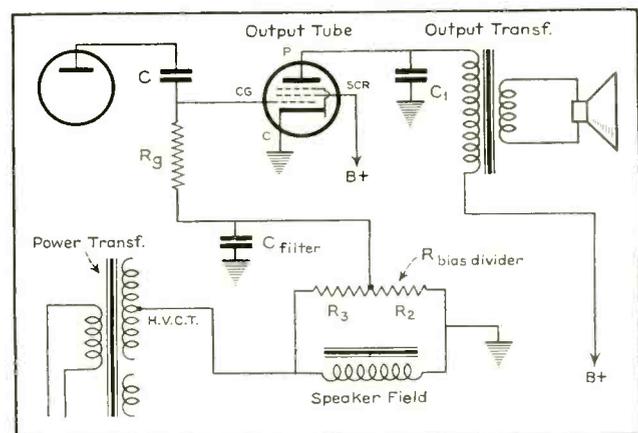

to provide the necessary signal input ratio, values of resistors and condensers in the phase inverter circuit are no more critical than those of other audio stages.

Fig. 6 shows a type of phase inversion that has enjoyed some popularity in the past few years. In this type of circuit the phase inverter tube acts as a sort of signal divider. The audio signal for the first push-pull stage is taken from the plate of this divider, while that for the second push-pull stage is taken from the cathode of the divider. The resistors R_1 and R_2 in this circuit are equal and are approximately half the value of the normal load resistor.

A single tube provides both amplification and phase inversion in the circuit of Fig. 7. A resistor of low value is connected in series with the screen of the first pull-pull output tube. The signal voltage developed across this resistance is fed to the second push-pull output tube. The value of this resistance determines the portion of the signal which will be fed to the second tube and depends upon the tube types employed.

A more recent innovation in phase inverter circuits is shown in Fig. 8. This circuit is commonly known as the self-balancing phase inverter and permits a somewhat wider range of tolerance in the choice of circuit components. This tolerance is permitted because a certain amount of degeneration is provided. Fig. 9 shows the same circuit adapted to a fixed bias arrangement.

In these circuits a resistor (R_3) is connected between ground and point (a) and is common to the plate circuit of tube A and to the plate and grid circuits of tube B. Because of this common connection the magnitude of the signal voltage across R_3 , which is applied to the grid of tube B, depends on the difference between the values of output-signal currents of tubes A and B. Hence, the effects of variations in the value of R_3 or the effects of possible variations between different tubes of the same type used in position B are very small. The circuit is degenerative, because a portion of the output of tube B is fed back to the input of tube B. Hence, the stability that is characteristic of degenerative amplifiers is obtained. It should be noted that the gain measured from the input (E_i) to tube

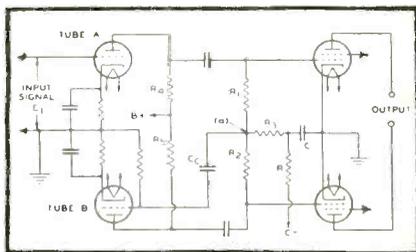


Fig. 9. The self-balancing phase inverter can be adapted to a fixed-bias arrangement.

A to the output (E_o) from the transformer's primary is only a few percent less than that obtained from the circuit of Fig. 5.

The ratio E_a/E_b cannot be made equal to unity with this self-balancing circuit by any adjustment of the value of R_3 , because of the degenerative action. However, with the values of resistors ordinarily employed in this circuit, E_a/E_b is approximately 1.1. A 10 percent unbalance in the push-pull output stage of a receiver can easily be tolerated. An analysis of the circuit shows that, as the gain of tube B is increased, the ratio of E_a/E_b approaches unity.

Values and tolerance of resistors R_1 , R_2 , R_4 and R_5 that are usually employed in the circuit of Fig. 5 may be used in the self-balancing circuit.

Possible Substitution

The various resistors and condensers used in the circuits shown in the illus-

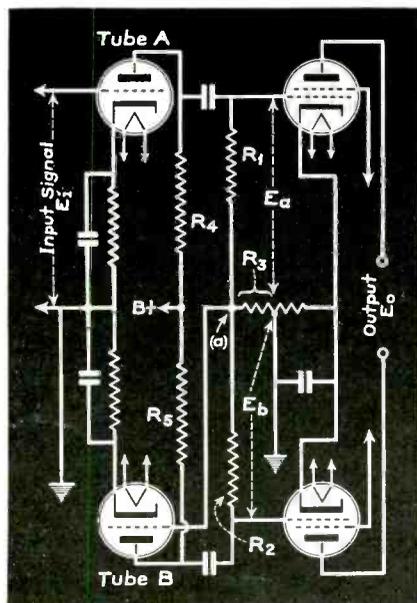


Fig. 8. Self-balancing phase inverter provides the conditions for push-pull operation.

trations this month do not always permit the large percentage of variation possible in other parts of receiver. For example, in the simple output stage shown in Fig. 1 any change larger than 20%, in the value of the coupling condenser (C) will cause a corresponding change in the frequency response of the receiver, unless a similar change is made in the accompanying grid resistor (R_g) in the opposite direction. Any great change in both of these components will alter the plate load of the previous stage, since they are connected in parallel across it. For this reason changes should be restricted to within 20 per cent of the value specified.

The by-pass condenser across the cathode-bias resistor (R_c) is not criti-

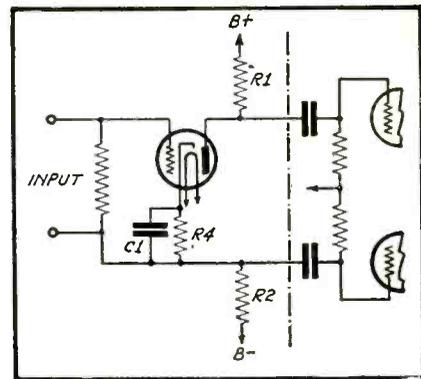


Fig. 6. This circuit divides the normal plate load between the plate and cathode circuits.

cal and any value larger than that specified may be used. In some receivers manufacturers omit this condenser to provide a degree of degeneration. This procedure may be followed where the gain in the output stage is sufficient to permit it.

The plate by-pass condenser (C_{b1}) is not too critical and a change of 25 percent will not affect the performance noticeably.

In Fig. 2, a 20 percent alteration is permissible in the values of any of the components shown, except R_{bias} . Similar changes are also permissible in Figs. 3 and 4, except for the bias resistor R_{bias} in Fig. 4, where duplicate values with close tolerance should be employed.

In degenerative circuits a variation of plus or minus 25 percent in parts values is generally allowable, since any ill effects will be cancelled by the feedback.

Where self-bias is employed, and doubt exists as to the value of the bias resistor, it is suggested that the reader consult one of the tube manuals mentioned above. By following the specifications given in these books good results can be obtained in all but very special cases.

With the exception of the bias resistors in the various phase inverter circuits shown and the screen resistor of Fig. 7 and the resistors R_1 and R_3 in Fig. 5 a variation of 20 per cent + or - is permissible in any of the other components. It is advisable to keep the values of the bias resistors, as well as the others mentioned, to within 10 percent of those specified by the receiver manufacturers.

Summary

The fundamentals of audio amplifiers are simple and are easily mastered. The choice of values for component parts is dependent upon the types of tubes chosen, and is usually specified by the tube manufacturer. Listings showing these values are found in easily available tube manuals.

Resistance coupling in single output
(Continued on page 29)

CASE HISTORIES



AIRLINE 62-196

Intermittent noise: If the 0.25-mfd condenser connected between the blue and red resistors on plate of 6B7 tube is leaking the red resistor will become noisy. Replace both. *T. Henshaw*

AIRLINE 62-236

Noisy: A defective 0.0075-mfd, 1,600-volt condenser connected on plates of 84 tube can cause excessive noise. *T. Henshaw*

AIRLINE 62-305

Intermittent: Intermittent reception can be caused if the 0.1-mfd condenser connected between terminals 4 and terminals 5, 7 and 8 of ID5G tube opens. *T. Henshaw*

AIRLINE 62-325

Distortion at medium or low-volume levels: Change 1/2-meg second-detector screen resistor to 0.7 meg to improve reproduction at low-volume levels. *T. Henshaw*

AIRLINE 62-475

Whistles around 600 kc: Install 0.25-mfd condenser in parallel with 8-mfd filter, which will not always by-pass r-f currents, as it becomes older. Replacing the 8-mfd unit will also cure trouble. *T. Henshaw*

AIRLINE 14WG683

Production change: In the issue B chassis, a loading coil with an adjustable iron core is connected across the secondary winding of the short-wave loop aerial as shown in the accompanying partial schematic. The interstage range D and interstage range B trimmers have been relocated.

CROSLEY 154

Burns out volume control: The volume control in this model is of the antenna shunt-cathode bias type. Since many people use a ground on the antenna post an a-c voltage is put across the control. At low volume this burns out the control. If a condenser of 0.01-mfd capacity is connected from the antenna post to the low end of volume control, and the old lead is removed, the control will be protected. *A. Knickiner*

EMERSON CU CHASSIS

No Volume: This receiver came in with the tubes interchanged. As a result of this the a-c filament current passed through the 6J5GT cathode resistor. The overload burned the resistor down to about 600 ohms. When the resistor was replaced with a proper 1/2-watt 1,000-ohm unit I noticed that there was no cathode by-pass condenser, which led to considerable degeneration. Probably this condenser was omitted from the original design to avoid overload on strong locals, but in a rural district all the pep obtainable on these t-r-f jobs is needed. A by-pass improved the gain considerably.

As in all jobs involving design alterations considerable judgment must be exercised in applying the changes. After all, we knew this omission wasn't an oversight, but in weak locations the added condenser was definitely an improvement. *R. G. Chrouh*

PHILCO TH7

Set distorts after about twenty minutes of playing: A new 35A5 will generally make the set operate properly. *A. Knickiner*

PHILCO 42-122, CODE 121

Microphonics: To prevent audio micro-

phonics 10,000-ohm resistor (26) was changed to 4,700 ohms. Chassis with this change are marked run 2.

PHILCO 42-126, CODE 121

Improving power output: To improve the audio power output, the 800-ohm resistor (52) ohms was changed to 680 ohms.

PHILCO 42-350, CODE 121

Fluttering: To improve filtering in the rectifier circuit and prevent flutter on the f-m band, electrolytic condenser (40)-(40A), 4-4 mfd, 400 volts was changed to 4-12 mfd. The 4-mfd section is connected to position (40A) and the 12-mfd section in position (40), across the rectifier output.

To prevent parasitic oscillation the ground lead of condenser (30) is removed from contact 4 of the 7V7 first i-f tube socket and connected to contact (8) of the same tube socket.

PHILCO 42-360, CODE 121

Production change: In some later production chassis of Model 42-360 a 7Y4 rectifier tube is used in place of an 84 tube.

PHILCO 42-1001, 1002, 1003, 1004, 1005

Converting the phonograph motor for use on 50 cycle a-c lines: The motor in this model is designed for operation on 60-cycle a-c lines. The motor will operate satisfactorily on 50-cycle lines. All that is necessary is to change the drive ratio between the motor pulley and the turntable drive pulley. This is accomplished by putting a coil spring (Philco Part No. 28-8999) over the motor drive pulley. Screw it on the drive pulley counterclockwise with the long pigtail at the top. The pigtail can be cut off after the spring has been placed on the pulley.


PHILCO 42-1003, CODE 121-122

Production changes: The light beam pickup arm (9) of later production Code 122 chassis was changed from metal to plastic. The counterweight, when using the plastic tone arm (Philco Part No. 318-2863) is 3 oz. A new rubber bumper is also required (Part No. 54-4167).

PHILCO 42-1012, 42-1013, CODE 121

Loop repairs: If the loop aerial (broadcast and short-wave) is removed from the cabinet for replacement or repairs, it should be remounted with the side of the loop having the red or red and white lead toward the rear of the cabinet. This is necessary to increase the stability at the low-frequency end of the broadcast band and to reduce whistles.


(Continued on page 22)

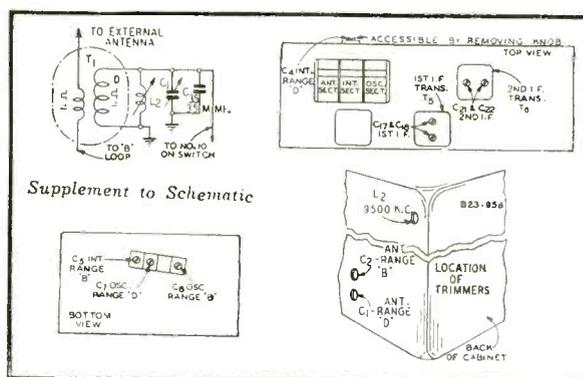

RECORD PLAYER

(See Front Cover)

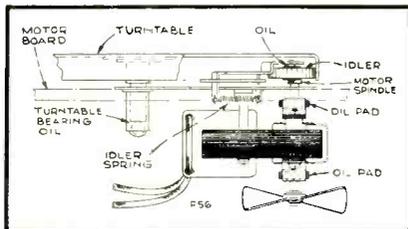
THIS TWO-TUBE model is a complete electric phonograph using a single beam-power tube in an amplifier having an undistorted power output of 2.25 watts and a maximum output of 4.5 watts for jitterbugs (who are unconscious of quality). The high level crystal pickup has sufficient output voltage to drive the 50L6GT to full power output with standard commercial records. Some difficulty might be experi-



A fan-cooled induction motor mounted directly to the top of the 11½ by 8¾-inch fabricoid covered cabinet drives the small turntable by means of a rubber tired idler wheel.

enced in playing home recordings which are usually of somewhat lower level than commercial pressings.

Note the amplifier input circuit. Instead of the a-f cathode being by-passed in the usual manner, with a large electrolytic or, as is being done more and more lately, or left completely unby-passed to provide degenerative feedback, an R/C decoupling system is used. The low side of the 1-meg volume control is run to cathode through a 0.1-mfd condenser and to ground through 68,000 ohms. The cathode resistor of 150 ohms does

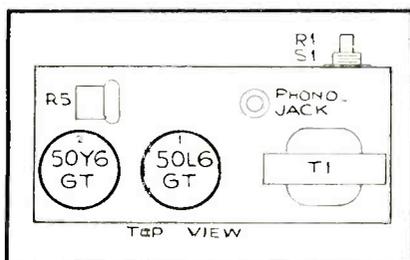

The simple amplifier together with the 5-inch electrodynamic speaker is contained in the small open-top cabinet. The entire unit (motor plus amplifier) draws only 50-watts from the power lines.

not require by-passing to prevent degeneration because most of the input voltage is routed through the 0.1-mfd condenser direct to the cathode—so it does not get to the ground and cannot get through the cathode bias resistor. There will be a slight output audio voltage drop in this resistor, however, but



NOT A SUBSTITUTE!

...It's a Super-Rugged Sprague "Dry" Specially Built to Do a Wet Electrolytic Job

WARTIME restrictions make it difficult to supply wet electrolytic condensers because of their aluminum thread-neck cans—but, thanks to Sprague engineers, you can keep right on making wet electrolytic replacements, and do it with the same assurance as though you were using the finest wet electrolytic condensers ever built.

The answer is the new Sprague Type WR Replacement Capacitor—a tubular cardboard dry electrolytic of very high voltage formation. Not only will WR's stand the peak voltages often impressed on wet electrolytics, but they'll handle

the AC ripples that might cause standard 450-volt dry electrolytics to overheat to the point where they break down. The diameter of WR's is the same as that of standard wets so that they will fit the screw-type can mounting holes. Their metal feet can then be soldered to the chassis for firm mounting.

Sprague Type WR's are now available in three sizes—WR-8 which replaces wets from 4 to 8 mfd.; WR-16 to replace capacities from 12 to 18 mfd., and WR-25 to replace capacities from 20 to 40 mfd. Ask your Sprague jobber today!



WARNING! Don't be fooled! Although standard dry electrolytic condensers can sometimes be used as wet replacements, your safety margin is apt to be mighty thin. High surge voltages and AC ripples may cause trouble. That's why it pays to play safe by using the new Sprague WR Types. They're not substitutes. They're actually built to do a wet electrolytic job. They're the real thing as far as performance and durability are concerned.

SPRAGUE WET REPLACEMENTS

(SPECIAL WR TUBULAR DRYS)

SPRAGUE PRODUCTS COMPANY, North Adams, Mass.


this is negligible when compared to the tube plate resistance drop.

The high power output is made possible through the use of a 220-volt power supply which is obtained from a voltage-doubler, rectifier-filter circuit. Voltage multiplier circuits have inherently poor regulation. Hence, they are best used in circuits demanding constant current and, preferably, not too much. Stated another way, the best operating conditions demand a high-impedance load. We consider the voltage doubler well adapted to this single stage phono-

graph amplifier, which does not demand excessive current.

The voltage doubler charges two condensers individually, then takes an output voltage from both in series. The condensers here are 16 mfd, so the filter circuit consists of 8 mfd, the speaker field and 10-mfd output condenser. Note the 15-ohm surge suppressor in series with the line connection to the voltage doubling condensers.

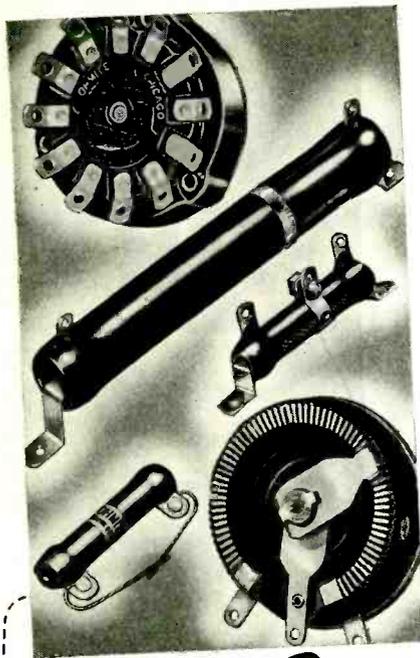BUY UNITED STATES
WAR SAVINGS BONDS AND STAMPS
EVERY PAY DAY



LONGER LIFE!

For Essential Equipment when

you use **OHMITE** Resistance Units

Life-savers—that's what you need in vital replacements today—and that's what you get in Ohmite Resistors, Rheostats, Chokes and Tap Switches. Their service-record on land, sea and in the air proves it. The wide range of types and sizes makes it easier for you to obtain what you need. Let Ohmite Jobbers help you.

Send for Handy Ohm's Law Calculator



Solves any Ohm's Law problem with one setting of the slide. Requires no slide rule knowledge. Size 4 1/8" x 9". Yours for only 10c to cover handling cost.

At Your Jobber or Send Coupon

OHMITE MANUFACTURING CO.
4877 Flournoy St., Chicago, U. S. A.

Send Free Catalog 18.
10c enclosed Send Ohm's Law Calculator.

Name _____
Address _____
City _____ State _____ Service 4-42

Be Right with OHMITE
RHEOSTATS • RESISTORS • TAP SWITCHES

RAILROAD SOUND

(Continued from page 6)

crosstalk by proper selection of the pairs carrying input and output circuits.

The power amplifiers used in A, B, and C (see illustrations) are 50-watt, RCA Type No. MI-4288 and feature pushpull 6L6s in the output stage. These are driven from a pair of 6C5s in push pull. The amplifiers are arranged to supply plate and heater voltages for the preamplifier circuits.

The microphones are Western Electric Type F1, carbon-button units. Microphone current is utilized in some of the circuits to operate starting relays. This type of microphone has been selected because the signal output level is high, eliminating the necessity for high-gain preamplifiers. As a precaution against induction noises on long lines, signal levels are maintained as high as practicable without adding complications to the circuit and connections.

Reliability

In order to meet the requirement that the system must be highly reliable, every consideration was given to such problems as proper power levels and proper tube loads. Each amplifier is operated conservatively. The two amplifiers which drive the tower loudspeakers, for example, have resistors in series with the 110-volt input power lines which feed the plate power transformers, in order to control the voltage fed to the amplifiers. Only one of the tower amplifiers is used at a time. The second unit is always available through a changeover relay, should trouble develop in the amplifier in use. The changeover relay is controlled by a switch on the yard office control panel. This arrangement is used because both heater and plate voltage is applied to these amplifiers continuously. All other amplifiers in the system have heater voltage only applied continuously. The plate voltage in each case is switched on as required, by means of the relays in the microphone circuits as mentioned above.

From the standpoint of servicing, any amplifier can be removed without taking the system out of service. Routine servicing includes regular checkup on tubes, batteries and connections. All the main power amplifiers are standard and may be interchanged or replaced by spares if trouble develops.

Power Output

In order to meet the second requirement, that of sufficient power output,

each 100-watt RCA loudspeaker is driven by an individual 50-watt amplifier. Enough of these amplifier-loudspeaker combinations are provided to more than fulfill the power requirement. No amplifier or loudspeaker need be operated at its maximum level.

In attempting to cover a large area of this sort with adequate sound level, two methods are possible. A number of small speakers can be placed at intervals, or a number of large speakers can be placed in clusters, arranged so as to cover the required territory. In the former method the problem of voice distortion arises due to the fact that sound from the several speakers reaches the listener at different times and often in such phase relationships that words are partially cancelled or distorted.

To offset this phase distortion the latter method, namely, placing larger speakers in clusters was selected. The resulting two-way communication system covers the new yard and in actual operation has fulfilled all the requirements.

Since instant communication is provided throughout the yard much time is saved in switching and classifying the large freight traffic handled through this terminal. This enables expanding the amount of business that can be handled with the available facilities.



Big in VALUE

Readrite RANGER MODEL 432-A

The Outstanding Tube Tester Value
Checks all type tubes including Loctals, Bantam Jr., 1.4 volt Miniatures, Gaseous Rectifier, Ballast, High Voltage Series, etc. Filament Voltages from 1.1 to 110 volts. Direct Reading GOOD-BAD Meter Scale. Professional-appearing case with accessory compartment large enough for carrying Model 739 AC-DC Pocket Volt-Ohm-Milliammeter, thereby giving the serviceman complete testing facilities for calls in the field.
Model 432-A with compartment, Dealer Net Price \$20.73. Model 432-A in case less compartment \$19.65. Model 739, Dealer Net Price \$10.89.

WRITE OR CATALOG — Section 417, College Drive

READRITE METER WORKS, Bluffton, Ohio

DISPLAYS

• • • • A program to enable radio dealers to take a forceful part in promoting the Victory theme was launched in Mid-March by Zenith Radio Corp., Chicago. The program, according to J. J. Nance, vice-president and director of sales, has a three-fold



purpose: First, to give dealers colorful display material for windows and store floors that will enable them to take an active part in promoting the Victory theme. Second, to explain why radio sets will not be available, after present distributors' and dealers' stocks have been exhausted, by dramatizing how Zenith production has been commandeered by the nation's armed forces. Third, to continue the close association in the public mind of Zenith dealer and manufacturer.


IRON TO GLASS SEAL

TIGHT SEALS between iron and glass, eliminating the need for nickel and cobalt, critical war metals, are now being made with a new development of General Electric scientists, it is said.

From the early days of the electric lamp, a problem of construction has been to make a tight seal between metal and glass. It is also involved in making radio tubes. Even with tubes in which the glass is replaced by one of metal, the lead-in wires pass through glass insulating bushings. The difficulty is that most kinds of glass expand with heat at a different rate from that of the metal. Glass and metal may be tight at one temperature, but when they are heated the glass will either crack or pull away from the metal, because the change in their dimensions is not the same.

Platinum was used in the first electric lamp, since it has nearly the same rate of expansion as the glass then employed. Various substitutes for platinum

RADIART VIBRATORS

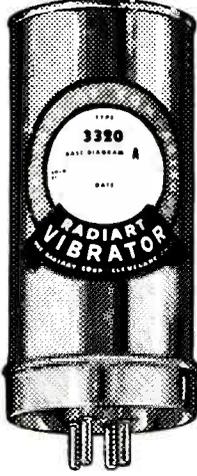



for performance!

DEPEND UPON RADIART VIBRATORS to keep irreplaceable auto and farm radios in service, and to power reliably the mobile radio equipment so vitally necessary to military operations and civilian defense.

Write for latest catalog

THE RADIART CORP., CLEVELAND, O.

were devised, which were satisfactory for lamp seals, though they were not adapted to the large seals used for powerful vacuum tubes, for example. However, special nickel-iron-cobalt alloys were developed for this last application.

Since nickel and cobalt are used in many ways for war equipment, and their supply is extremely limited, the new invention is an important one. For certain applications it permits tight seals to glass without the use of critical war materials.

General Electric engineers, Drs. Albert Hull and Louis Navias, have devised a series of glass compositions

which can be used with iron and certain iron alloys. The rate of expansion of these glasses is very close to that of iron. In seals using these glasses a further development of Dr. Navias also proves useful. When a glass containing lead is sealed in contact with iron, some of the lead atoms migrate from the glass into the metal. This weakens the joint, and may let air leak into the tube. Dr. Navias proposed placing a thin layer of lead-free glass directly over the metal, then sealing the lead-containing glass to that. The thin glass layer prevents the lead from reaching the iron, yet it is not thick enough to crack and let air in.

you spend less
but get more

**WHEN YOU BUY RCP
TEST EQUIPMENT**

Every RCP high-precision test instrument does the work of several ordinary instruments, in some cases as many as 43! That's one reason RCP test equipment is in service in so many shops today. Add this to RCP's higher quality and lower cost, and you'll see how much you can save—in actual dollars and cents—when you use RCP dependable test equipment.



**AC-DC
COMBINATION
TUBE AND
SET TESTER
RCP
Model 802**

Tests all new and old tubes and ballast tubes. Hot interelement short and leakage tests on individual elements. Line voltage regulation 103 to 135 volts, indicated on meter. Meter is fused against burn out. AC and DC voltmeters, each 0/10/50/500/1000. DC milliammeter 0/1/10/100/1000. DC amps 0/10. Also, D.B. and output meter. Where else could you buy these two top-quality instruments individually, at this low price? Complete with tube, battery and test leads. Dealer Net Price.....

\$33.95

**AC-DC
MULTI-RANGE
SUPERTESTER**



**RCP
Model 411**

Provides accurate measurements in ranges never before available in small instruments. Five AC and five DC voltage ranges, 0/10/100/250/1000/5000 volts. AC current range 0-2.5-5-25 amps. DC current ranges 0-1-10-25 amps. Three ohmmeter ranges to four megohms. DC millamps 0/10/100. DC microamps 0/200. In hardwood case. Dealer Net Price.....

\$19.45

Send at once for new catalog describing complete RCP money-making line.



**RADIO CITY
PRODUCTS CO., INC.**

88 PARK PLACE • NEW YORK, N.Y.

CASE HISTORIES

(Continued from page 18)

RIM DRIVE PHONO MOTORS

60 to 50-cycle conversion: A spring sleeve is used to increase the diameter of the motor-drive spindle, to compensate for the slower speed of the motor when used on a 50-cycle line. To apply the spring sleeve to the motor spindle, lock the rotor manually and press spring gently over the end of spindle, twisting the free end of spring counter-clockwise (to unwind coil) until the end of spring is flush with end of spindle.

The ends of spring should not pro-

trude, and all coils should be close together, allowing a flat, even surface on the motor spindle to contact the rubber drive.

RCA Service Note

RCA 16X4


R-f plate load resistor change: In some production, the load resistor in the plate circuit of the r-f tube is changed from 3,900 to 2,200 ohms.

RCA 28X5

Insufficient push-button range: In Model 28X5 if the push-buttons have insufficient range, realign the r-f at exactly 455 kc. If this does not correct the trouble, replace the main oscillator coil (RCA Stock No. 38685) and realign the set. The correct coil has no number stamping; do not use the coil stamped 95106-501.

RCA 6U56C, 6U56M

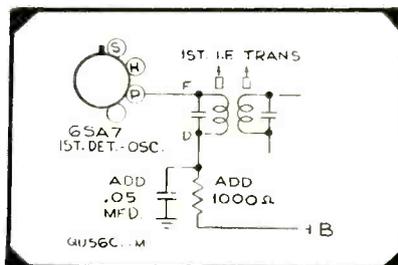Instability: Development of appreciable r-f impedance in the electrolytic filter capacitor, as the condenser ages, creates common coupling and may cause oscillation. To eliminate this possibility,



an R/C filter is connected in the +B lead of the first detector plate circuit, as shown in accompanying sketch.

RCA T80

Push buttons hard to operate: Loosen the dial pointer cable and the bind will disappear. Also put a little lubricant on the dial pointer tracks.

A. Knickiner

**RCA 158 AND 160B CATHODE-RAY
OSCILLOSCOPE**

Filter circuit change: In some first production of Model 158 and 160B cathode-ray oscillographs, numbered in the 2,000 series, the 0.1-mfd first-filter capacitor may short due to a starting-voltage surge. To prevent recurrence, replace the 27,000-ohm input filter resistor (R38 in 158, R33 in 160) with a 120,000-ohm, 1-watt resistor. This change should be made when the shorted 0.1-mfd capacitor is replaced.

RCA 160 CATHODE-RAY OSCILLOSCOPE

Vertical "Bounce": The 160 oscillograph has extremely good low-frequency response, passing a 4-cycle square wave with good fidelity. It is


possible to encounter instances in which a line-voltage meter, due to its inertia will indicate little or no variation of voltage, whereas the oscillograph will exhibit noticeable vertical "bounce" due to line-voltage fluctuations.

If you desire to retain the normal low-frequency response of the 160 yet have a power line which varies in voltage appreciably, it is necessary to provide voltage regulation, such as TMV173 voltage regulator. However, if the extreme response of the 160 is superfluous for the particular application in mind it can readily be reduced, affording a reduction of the "bounce" to an unobjectionable value. This is accomplished by removing the present coupling condenser, C20, and substituting a 0.05-mfd, 400-volt unit. The response is then down a few percent with a 15-cycle sine-wave input. (The 160B incorporates filtering circuits to eliminate vertical "bounce.")

For applications in which it is desired to connect directly to the cathode-ray tube deflecting plates, such as the observation of a modulated r-f envelope from a transmitter, it is possible to completely eliminate the vertical "bounce" by merely disconnecting either side of the coupling capacitor, C23.

SILVERTONE 7069


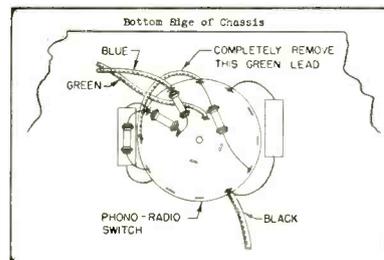
Improving phonograph operation: Chassis of this model, identified by the number 101.658, can be improved with respect to the operation of phonograph records by cutting the green wire on the phone switch as shown in the ac-



companying diagram. Chassis which have had this change made in production are identified by the suffix number -1, or a subsequent number.

SILVERTONE 7079

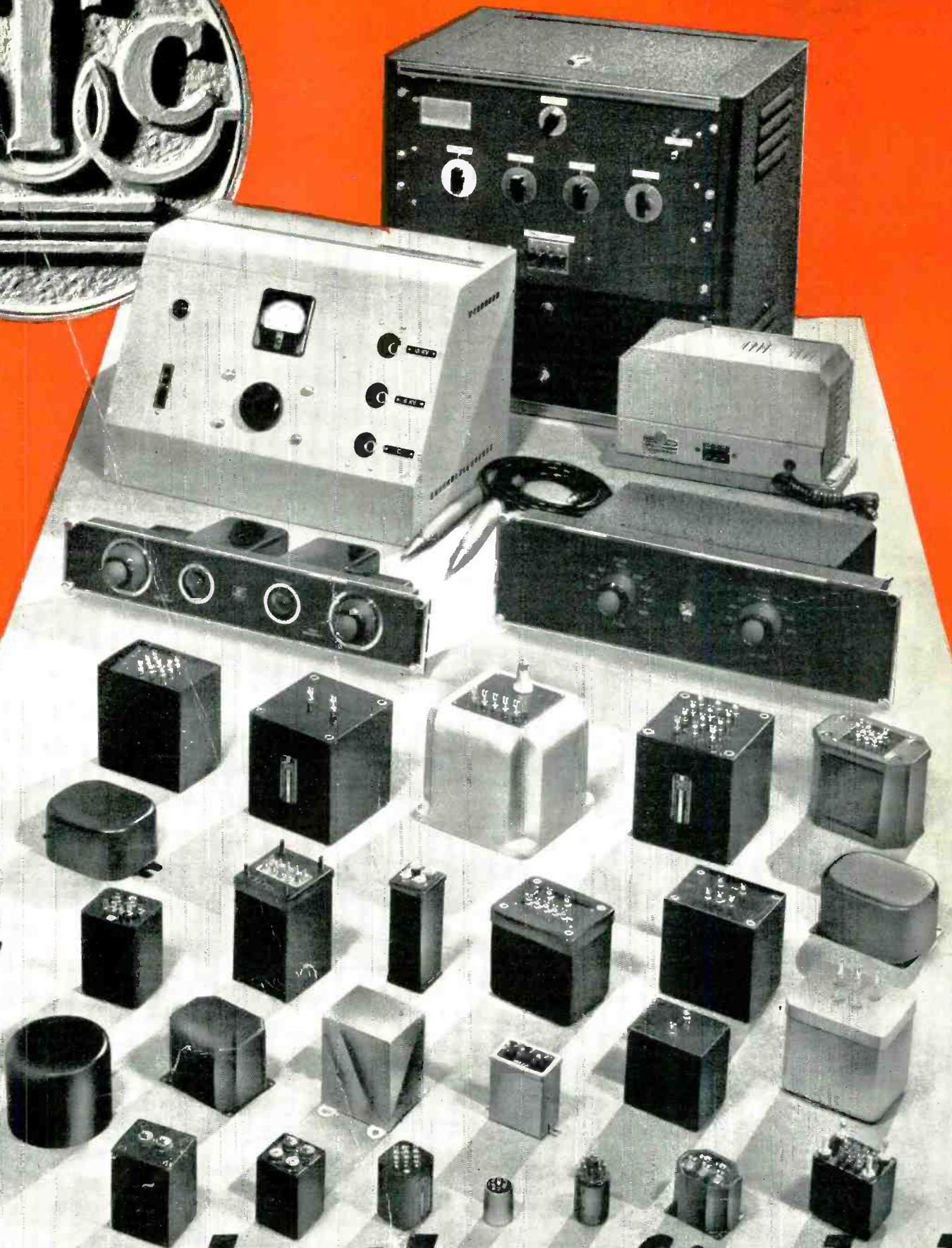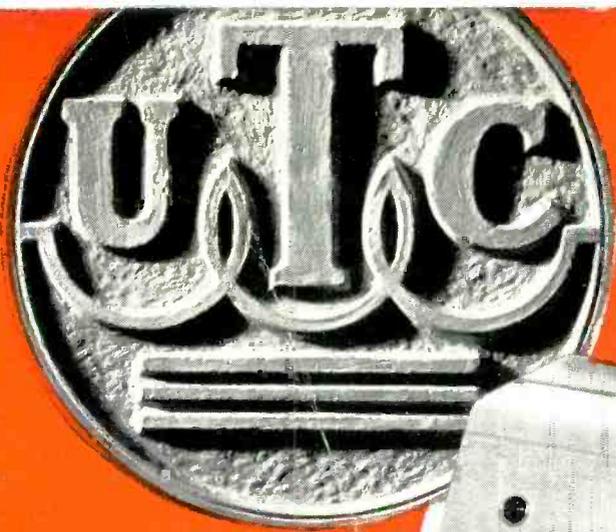Chassis Nos: Chassis identified as 101.620-3 are the same as 101.620-2, except that the loop is wound directly on the cabinet frame and covered by the cabinet covering. The loop is of low impedance requiring the addition of an antenna loading coil. Slight filament circuit revisions are also incorporated.



Leads the field

UNITED TRANSFORMER CO.

150 VARICK STREET



NEW YORK, N. Y.

EXPORT DIVISION: 100 VARICK STREET NEW YORK, N. Y. CABLES: 'ARLAB'

KEEP THEM LISTENING

The data listed below, covering the percentage of homes in 30 states owning radio receivers, should prove useful to the Service Man in reviewing his market. The average radio receiver requires attention every 192 days according to a survey made by the publishers of SERVICE. With the average charge per call about \$3.50, Service Men in the states mentioned can figure the total probable revenue in their own neighborhood.

THE ACCOMPANYING table from the Second Series Housing Bulletins presents data on radios in homes for 30 selected states and the District of Columbia, for which the tabulations have now been completed. Similar statistics for states, counties, metropolitan districts, and urban places will be presented in the Second Series Housing Bulletins, by states. Data for additional states will be presented in further releases in this series as the figures become available.

Nearly three-fourths of the homes had radio sets in the states listed, ac-

ording to data from the Census of Housing of 1940 released by Director J. C. Capt of the Bureau of the Census, Department of Commerce. Radio ownership was highest in Connecticut and Rhode Island where sets were reported in 95.7 percent of the occupied dwelling units. Less than two-fifths of the homes in Mississippi reported receivers. The proportion of homes with radio sets was highest in the urban areas of the selected states, in which 85.1 percent of the occupied dwelling units had receivers as compared with 71.5 percent in the rural-nonfarm areas and 52.4 percent in the rural-farm areas.

Between 1930 and 1940 tremendous increases have occurred in the number of home radio sets in all of the selected

states. In the total of these states the proportion increased from 26.9 percent in 1930 to 71.1 percent in 1940. It should be noted that few of the larger States are included in the present list and that the percentages based on the resulting totals are not representative of the United States as a whole. This is indicated by the fact that the United States total for 1930 showed 40.3 percent of the homes with radio receivers, as compared with 26.9 percent in these 30 selected states and the District of Columbia.

Radio Men: Your country needs you! Get in touch with the Army or Navy recruiting station nearest your home for full details.

The listings below cover only 30 states and the District of Columbia. Additional data will be presented as soon as it is available.


STATE	TOTAL				URBAN				RURAL-NONFARM				RURAL-FARM				PERCENT WITH RADIO, 1930
	Number reporting	With radio		Number not reporting	Number reporting	With radio		Number reporting	With radio		Number reporting	With radio					
		Number	Per cent			Number	Per cent		Number	Per cent		Number	Per cent				
Total.....	10,100,900	7,184,895	71.1	297,369	4,229,077	3,599,945	85.1	2,653,365	1,905,262	71.5	3,208,458	1,679,688	52.4	26.9			
New England:																	
Maine.....	213,204	184,348	86.5	5,764	86,108	80,245	93.2	87,905	73,856	84.0	39,191	30,247	77.2	39.2			
New Hampshire.....	129,768	116,809	90.0	3,178	73,584	68,636	93.3	40,570	35,236	86.9	15,604	12,937	82.9	44.4			
Vermont.....	90,569	80,253	88.5	1,866	31,820	30,404	95.5	34,486	30,213	87.6	24,263	19,636	80.9	44.6			
Rhode Island.....	184,661	176,739	95.7	3,045	168,506	161,891	96.1	13,610	12,604	92.6	2,545	2,244	88.2	57.1			
Connecticut.....	436,164	417,258	95.7	12,518	295,820	285,068	96.4	116,898	111,444	95.3	23,446	20,746	88.5	54.7			
West North Central:																	
Iowa.....	683,963	617,005	90.2	17,861	303,448	284,354	93.7	157,602	138,015	87.6	222,913	194,636	87.3	48.5			
North Dakota.....	148,179	131,000	88.4	3,864	33,149	31,374	94.6	45,981	39,395	85.7	69,049	60,230	87.2	40.9			
South Dakota.....	160,894	136,049	84.6	4,534	42,361	39,191	92.5	48,203	39,408	81.8	70,330	57,450	81.7	44.2			
Nebraska.....	352,662	298,790	84.7	8,082	142,823	132,428	92.7	87,432	72,448	82.9	122,407	93,916	76.7	47.9			
Kansas.....	496,101	411,984	83.0	15,008	217,344	196,458	90.4	124,789	102,849	82.4	153,968	112,677	73.2	38.9			
South Atlantic:																	
Delaware.....	68,870	59,921	87.0	1,671	36,109	33,331	92.3	21,398	18,513	86.5	11,363	8,077	71.1	45.9			
District of Columbia	169,102	158,377	93.7	4,343	169,102	158,377	93.7	-	-	-	-	-	-	53.9			
Virginia.....	610,878	409,978	67.1	16,654	237,564	199,670	84.0	169,708	114,756	67.6	203,606	95,552	46.9	18.2			
West Virginia.....	434,386	326,347	75.1	10,429	136,771	122,709	89.7	188,680	142,190	75.4	108,935	61,448	56.4	23.3			
North Carolina.....	764,144	471,863	61.8	25,515	232,226	180,456	77.7	210,757	142,468	67.6	321,151	148,939	46.4	11.2			
South Carolina.....	422,263	209,542	49.6	12,705	120,074	80,519	67.1	122,576	73,498	60.0	179,613	55,525	30.9	7.6			
Florida.....	504,011	326,447	64.8	15,876	285,228	217,044	76.1	147,816	81,444	55.1	70,967	27,959	39.4	15.4			
East South Central:																	
Alabama.....	650,709	321,671	49.4	23,106	219,023	152,650	69.7	152,082	82,906	54.5	179,604	86,115	30.8	9.5			
Mississippi.....	515,369	205,613	39.9	19,587	115,976	71,289	61.5	92,692	47,177	50.9	306,701	87,147	28.4	5.4			
West South Central:																	
Arkansas.....	480,955	244,586	50.9	14,870	119,571	86,598	72.4	108,082	58,001	53.7	253,302	99,987	39.5	9.1			
Louisiana.....	577,965	307,883	53.3	14,563	257,531	186,913	72.6	132,687	69,626	52.5	187,747	51,344	27.3	11.2			
Oklahoma.....	589,919	405,754	68.8	20,562	244,949	204,412	83.5	135,162	87,273	64.6	209,808	114,069	54.4	21.6			
Mountain:																	
Montana.....	156,024	134,503	86.2	3,939	62,031	57,114	91.3	48,480	40,924	84.4	44,963	36,465	81.1	31.9			
Idaho.....	137,521	118,824	86.4	4,206	49,062	44,795	91.3	40,059	33,697	84.1	48,400	40,332	83.3	30.3			
Wyoming.....	67,687	57,126	84.4	1,687	26,767	24,489	91.5	22,370	18,603	83.2	18,550	14,034	75.7	34.1			
Colorado.....	305,824	258,573	84.5	10,176	168,476	154,155	91.5	75,854	59,231	78.1	61,494	45,187	73.5	37.8			
New Mexico.....	125,134	66,609	53.2	4,341	45,060	32,680	72.5	41,659	19,824	47.6	38,415	14,105	36.7	11.5			
Arizona.....	127,250	87,781	69.0	3,883	47,602	39,234	82.4	54,162	37,508	69.3	25,486	11,039	43.3	18.1			
Utah.....	136,747	126,418	92.4	2,740	80,248	76,243	95.0	36,342	32,771	90.2	20,157	17,404	86.3	41.1			
Nevada.....	32,178	26,200	81.4	1,113	12,780	11,405	89.2	15,360	11,889	77.4	4,038	2,906	72.0	30.6			
Pacific:																	
Oregon.....	327,809	290,644	88.7	9,683	167,414	155,813	93.1	89,963	77,496	86.1	70,432	57,335	81.4	43.5			

NEW PRODUCTS

Additional information and prices of the products described below may be obtained, without obligation, from the respective manufacturers.

SILVER-MICA CAPACITORS

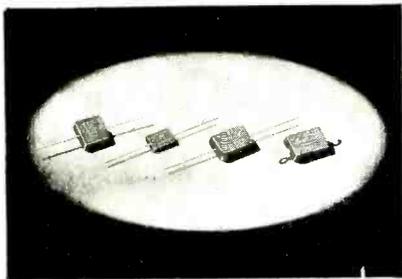Solar Manufacturing Corp., Bayonne, N. J., announce their Types MWS, MOS, MKS and MLS standard silver-mica capacitors, supplied in low-loss Bakelite. They are commonly employed




in frequency-modulation circuits, and automatic tuning arrangements where an unusually high degree of stability is essential, it is said. A unique Solar silvering process assures the permanent adherence of silver to mica, vital for long-term stability characteristics, according to Solar's engineers.

To differentiate these units from ordinary mica capacitors, these capacitors are marked with a silver dot in the center of the body identifying "silver-mica" construction.

INDICATOR LIGHT


A new indicator that lights only when the circuit is broken is announced by Littelfuse, Inc., 4757 Ravenswood Ave., Chicago. It is listed as No. 1414, and is applicable to any circuits, circuit breakers, line switches, etc.

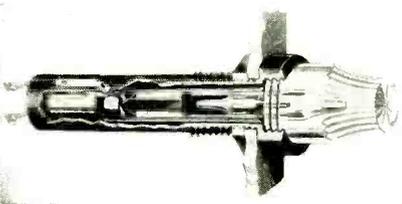When installed in connection with remote motor control it gives a visible signal to show "on" or "off." When the circuit breaker opens the light goes on. It is obtainable for 24- or 48-volt filament lamps, with which no resistor is



used. Otherwise, a built-in 200,000-ohm protective resistor is employed in series with a neon lamp. The resistor prevents the lamp from burning out on unexpected high voltages. The neon lamp

Why Waste Time!

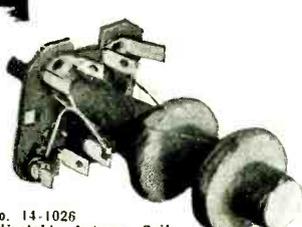

No. 14-1026
Adjustable Antenna Coil



No. 14-1027
Adjustable R.F. Coil



No. 14-1028
Adjustable Oscillator Coil

No need to waste your valuable time waiting to obtain an exact duplicate of Antenna, R.F. or Oscillator Coils when you can replace with the Meissner Universal adjustable coils. They will replace the broadcast band coils in practically any receiver in use today.

Adjustable Ferrocarril iron core used in these coils add gain and selectivity to the receiver. Continuously variable in inductance over a wide range, these coils will "track" with other coils in the receiver after a simple screw driver adjustment.

In stock at all Meissner jobbers . . . Net Price 83 cents each. Try them on your next coil replacement job.

GET YOUR COPY TODAY!

The best quarter investment you ever made. Meissner's I.F. Transformer Replacement Manual. Lists replacement I.F. Transformers for practically all models of radios since the advent of super-hets . . . only 25 cents at your Meissner jobbers.

Write for Complete New Catalog—Address Dept. SE-4



MT. CARMEL, ILLINOIS
"PRECISION-BUILT PRODUCTS"

glows on currents as low as 100 microamperes.

RECORDING DEVICE

Back talk is the specialty of the Mirrophone, new recording and reproducing device manufactured by the Western Electric Co., 195 Broadway, New York City. This is the way it works: The performer speaks into microphone. The performer's voice is recorded magnetically on a strip of metal tape. A flip of a switch and his voice comes back at him.

The Mirrophone already has a number of diverse applications to its credit. One midwestern radio station, for in-

stance, has a Mirrophone set up in its announcers' room. As each announcer comes on duty, he reads his commercial copy to the Mirrophone, then listens to the playback. Station's executives say that the announcers, able to hear and criticize their own speech without the delay attendant on processing wax recording, have greatly improved their work.

Many universities and schools have put the Mirrophone to work in their speech departments. The device has also been found helpful to stutterers and other speech defectives. It is currently at work in the nation's crowded Capi-

(Continued on following page)

KEEP A BALANCED TUBE STOCK ALWAYS ON HAND



Win Customer Goodwill
With Quick Service



KEEP 'EM PLAYING



WITH *Electronic*

RADIO TUBES

FAMOUS FOR
LONG LIFE AND
FINE RECEPTION

GENERAL ELECTRIC



Old Man Centralab
reminds you to always "specify
Centralab" when ordering parts.

-  **FIXED RESISTORS**
-  **CERAMIC CAPACITORS**
-  **VOLUME CONTROLS**
-  **WAVE CHANGE SWITCHES**
-  **TOGGLE SWITCHES**


Centralab
DIVISION OF GLOBE UNION INC.
MILWAUKEE, WIS.

tol, helping to improve the "telephone voices" of Uncle Sam's thousands of new secretaries and telephone operators.

The Mirrophone permits continuous operation. As each recording is made, the previous one is erased.

L-F TIME BASE GENERATOR

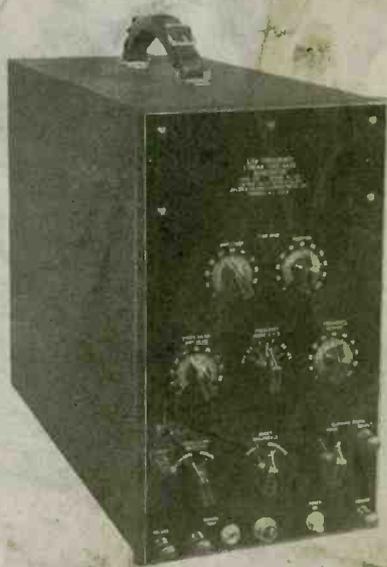For oscillograph studies requiring sweep frequencies as low as one cycle



every few seconds, a low-frequency linear-time-base generator, Type 215, is

announced by Allen B. Du Mont Laboratories, Inc., Passaic, N. J. In conjunction with an oscillograph with a long persistence tube, or with photographic methods, this accessory opens up new fields of investigation. This accessory opens up new fields of investigation in low-frequency transient and phenomena. Vibration studies and strain measurements, low-frequency electrical observation, electrocardiography and electroencephalography, are facilitated by this new unit. The frequency range of the instrument, from 0.2 to 125 cps, corresponds to rotating speeds of 12 to 7500 rpm, thus permitting the use of an oscillograph for the visual study of certain characteristics of rotating machinery at low and medium speeds. Transient observation is provided for a single-stroke sweep circuit. The maximum undistorted output signal is approximately 450 volts peak-to-peak, balanced to ground. The single sweep is initiated either manually or by observed signal.

EXPANSION

• • • • Paul Tartak, president of Cinaudagraph Speakers, Inc., has released the information that his company completed the task of moving to their new factory building at 3911-3929 So. Michigan Ave., Chicago. According to Jerome S. Gartner, secretary of Cinaudagraph, this move was made in anticipation of the need for additional floor space for production of radio and electrical equipment for the United States Signal Corps and other branches of governmental service.

Mr. Gartner advises that Cinaudagraph's present line of speakers will be available to distributors as long as materials are available. Cinaudagraph Speakers, Inc., were formerly located at 921 W. Van Buren St., Chicago.

CATALOGS, BULLETINS ETC.



Copies of the catalogs and bulletins discussed below may be obtained directly from the respective manufacturers mentioned. Write for them today!

• • • • A bulletin describing the Du Mont Type 215 low-frequency linear-time-base generator and its applications, is available.

(Continued on page 28)

SOLVING SHORTAGE PROBLEMS

(Continued from page 13)


stages as well as in push-pull stages is universal in present-day receivers. Phase inversion is used to obtain the necessary conditions for push-pull operation. Various common-phase inverter circuits are shown in Figs. 5, 6, 7, 8 and 9.

Some of the components used in resistance coupled stages are somewhat more critical than those employed in other parts of the receiver, and should be kept to within 10 percent of the manufacturer's specified value. Several of the components, however, permit a greater variation.

SER-CUITS

(Continued from page 10)

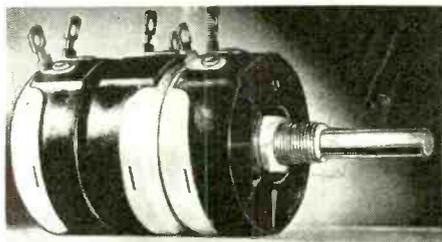duction which is controllable by the treble tone switch. Note the first i-f transformer in Fig. 5 which is designed to broaden the pass band in the treble position. Note also that the diode detector is tapped down on the third i-f transformer which looks like a sacrifice in voltage, but which reduces the loading and actually improves the gain at high signal levels where the diode



★ Of course the real money today is in sound systems—anything from P-A and theatre installations, yes and even local broadcasters, down to high-fidelity amplifiers required for proper FM reception.

★ In this regard, don't overlook Clarostat sound-system controls. The wire-wound T-pad constant-impedance Series CIT-58 control, shown above, is typical. Also L-pads, mixers, constant-impedance output attenuators, etc. All part of the Clarostat complete line of controls and resistors.

★ Interested? Then ask our local jobber for literature on sound-system controls. Or write direct to Dept. S-4, Clarostat Mfg. Co., Inc., 285-7 N. 6th St., Brooklyn, N. Y.



current runs high. Another application of impedance matching.

Three 6SQ7s are used; one for a diode, one for first audio and one for second audio. The second audio cathode is connected to the voice coil winding such that it receives about one-eighth of the output voltage, providing considerable feedback. This flattens the electrical response of the amplifier, greatly aiding the attainment of high fidelity. The 6J5 inverter is a degenerative type with a split cathode resistance. Note the elaborate tone control system in the output circuit of the first audio; also the bias cell as first audio bias.

Silvertone 7056

Sears Roebuck has a unique oscillator injection means in the converter stage of Silvertone Model 7056, a 7-tube phono combination. Shown in Fig. 6, the 7H7 converter is connected to a tap on the oscillator coil. A bias resistor of 1,000 ohms is also in the cathode lead and this resistor is shunted with a by-pass condenser to pass both signal and oscillator frequencies.

By providing a tap on the bleeder, the cathode resistance of the first audio is reduced to 330 ohms and is left un-bypassed. Further degeneration is provided in the 6K6GT output stage with a 500-ohm cathode resistor. This set has an automatic phono-radio switch which connects the phonograph when the pickup arm is raised.

Silvertone 7071

Fig. 7 shows another method of cathode injection in the mixer circuit as used in another Silvertone set, Model 7071. The first detector cathode is tied to the oscillator cathode through a 0.01 by-pass. The oscillator cathode is above ground potential by the drop in the cathode tickler coil. Both cathode resistors are necessarily un-bypassed. The plate is shunt fed to the oscillator transformer and a stabilizing resistor is used in the plate circuit.

Airline 14BR736B

Cathode coupling is applied in an entirely different vein in Ward's Airline Model 14BR736B, 7-tube, a-c/d-c set. As shown in Fig. 8, the first a-f tube has a 1,000-ohm cathode resistor; the output tube a 150-ohm resistor, both un-bypassed. Between these cathodes a low-pass filter provides feedback. The first-audio screen-drop resistor is by-passed with a 0.04-mfd condenser. The screen is also by-passed to B—by a 0.1 mfd. A 4,000-ohm field is connected across the rectifier output. This receiver uses an open loop as a self-contained

(Continued on following page)

More Help from

SYLVANIA SERVICEMAN SERVICE

by
FRANK FAX



A SHORT time ago Uncle Sam told the radio-buying public, "That's all there is, there isn't any more." That puts it up to you servicemen to keep the nation's radio sets—57 million of them—in trim for the duration.

Yes sir, there's plenty of work ahead, but to get your share, you've still got to scratch for it. And that's why we've prepared a couple of new sales helps to add to the long list now available to you.

One is a set of "Radio Alert" post-cards. These emphasize the importance of good radio reception in air raids and black-outs, pointing out that radio may be the only open means of communication during alerts. The price of the cards to you is just a penny apiece for postage.

The other new item is a booklet of radio caretaking hints for housewives—a timely reminder to the ladies that their annual spring scouring should include a look-in at the radio, too.

Every one of the thirty helps listed below—including the two new ones—is obtainable at your local jobber. Or, if you prefer, write direct to me, Frank Fax, Dept. S4, Hygrade Sylvania Corporation, Emporium, Pa.

- | | |
|--|--|
| 1. Window displays, dummy tube cartons, timely window streamers, etc. (From your Sylvania jobber only) | 16. Technical manual |
| 2. Counter displays | 17. Tube base charts |
| 3. Electric clock signs | 18. Price cards |
| 4. Electric window signs | 19. Sylvania News |
| 5. Outdoor metal signs | 20. Characteristics sheets |
| 6. Window cards | 21. Interchangeable tube charts |
| 7. Personalized postal cards | 22. Tube complement books |
| 8. Imprinted match books | 23. Floor model cabinet |
| 9. Imprinted tube stickers | 24. Large and small service carrying kits |
| 10. Business cards | 25. Customer card index files |
| 11. Doorknob hangers | 26. Service garments |
| 12. Newspaper mats | 27. 3-in-1 business forms |
| 13. Store stationery | 28. Job record cards (with customer receipt) |
| 14. Billheads | 29. "Radio Alert" Post-cards |
| 15. Service hints booklet* | 30. Radio Caretaking Hints to the Housewife |

SYLVANIA

RADIO TUBE DIVISION
HYGRADE SYLVANIA CORPORATION

SERVICE, APRIL, 1942 • 29



"Absolutely tops! First day it helped me repair 4 sets within 3 hours—4 sets I hadn't been able to fix in 2 days." . . . writes M. Penezak, a serviceman in Lawrence, Mass.

710 PAGES
new
revised
enlarged

The Biggest Help in Service Work Today!

why don't you too do every one of your servicing jobs faster? Get this help from this new 2nd edition of Ghirardi's

RADIO Troubleshooter's HANDBOOK

ARE YOU UP TO YOUR NECK IN SERVICE WORK NOW?

More and more alert servicemen all over the country are learning that they can't afford to be without Ghirardi's new, up-to-the-minute second edition of RADIO TROUBLESHOOTER'S HANDBOOK. It speeds Troubleshooting . . . saves time hunting for Servicing Data . . . saves Repair Time . . . because it contains all the factory-checked, time-saving working data every serviceman needs, indexed for quick split-second reference.

"The information I received from Ghirardi's RADIO TROUBLESHOOTER'S HANDBOOK paid for the book at least THREE times over within four hours of the time the postman delivered it," writes C. Paul Luzon, a serviceman in Burlington, Vt. If you too are up to your neck in radio service work—this new Handbook will save you precious hours every working day.

"Saves loads of time, even if a shop has a complete set of service manuals" . . . writes W. Pooser, Jr., a serviceman in Augusta, Ga.

Yes, no matter how many service manuals you may have, this new, complete 710-page

New "REPLACEMENT BATTERY" Wall Chart


For a limited time only! Gives "Type" numbers of all the "COMPARABLE" and "REPLACEMENT" A, B, and A-B Batteries (of 23 battery manufacturers) for 1250 models of 100 makes of Portable battery-operated radio receivers. Worth many dollars, this big 17" x 22" wall chart is yours for only 10c. Send for one today.

SEE GHIRARDI'S BOOKS AT YOUR LOCAL DEALER TODAY

RADIO & TECHNICAL PUBLISHING CO.

Dep't. S 42 • 45 ASTOR PLACE, NEW YORK, N. Y.

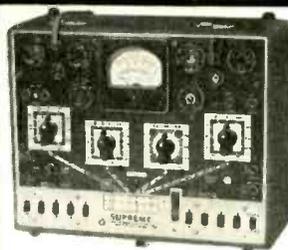SERVICE MEN HAVE BOUGHT OVER 100,000 SUPREME TESTERS



Be sure you see the complete SUPREME line before you purchase new test equipment. See your Jobber or write for new catalog.

WRITE FOR NEW CATALOG AND PRICES

SUPREME

TESTING INSTRUMENTS

GREENWOOD, MISSISSIPPI U. S. A.

WHEN YOU CHANGE YOUR ADDRESS

Be sure to notify the Subscription Department of SERVICE at 19 E. Forty-seventh St., New York City, giving the old as well as the new address, and do this at least four weeks in advance. The Post Office Department does not forward magazines unless you pay additional postage, and we cannot duplicate copies mailed to the old address. We ask your cooperation.

antenna for both short wave and broadcast.


Wilcox Gay A105

The audio filters used in Wilcox-Gay's Model A105 make an additional stage of amplification necessary for phono operation. Fig. 9 shows the


crystal pickup equalizer including the $\frac{1}{4}$ -meg load connected to the 6J5 grid. Coupling the 6J5 plate to the 6SQ7 is a 2-section pi-type low-pass filter designed to cut off the high audio fre-

quencies sharply, acting as a scratch filter. The loss in highs that results is probably not obvious but the reduction in noise certainly is. Plenty of the new higher priced piano and concert recordings seem disappointingly noisy, and require such precautions.

Fig. 9. Wilcox Gay A105 recorder combination.

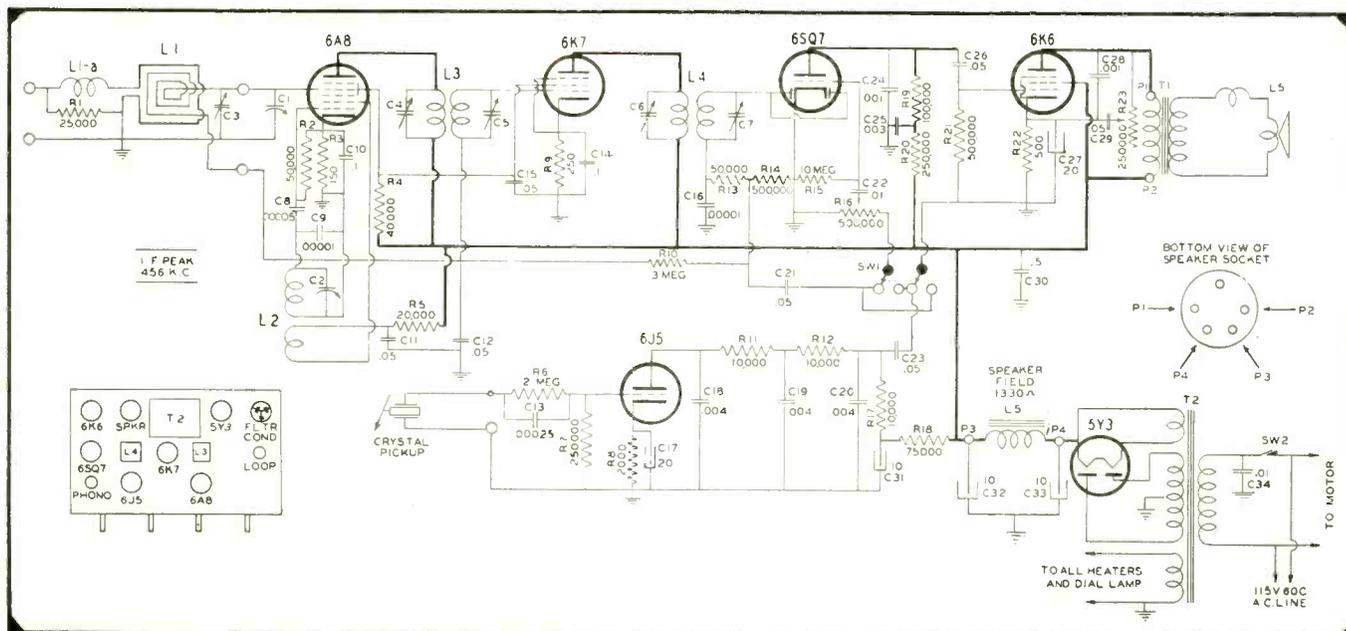

Radio's MASTER ENCYCLOPEDIA

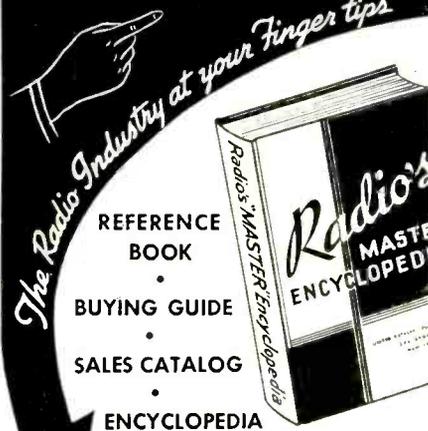

The Radio Industry at your Finger tips

REFERENCE BOOK
BUYING GUIDE
SALES CATALOG
ENCYCLOPEDIA

**9th EDITION
OVER 800 PAGES**

THE ONLY OFFICIAL RADIO PARTS AND EQUIPMENT MANUAL

It took six years and thousands of dollars to develop this "MASTER CATALOG" of the radio industry to its present size—yet it costs you only \$2.50.

Compiled in co-operation with and approved by the Radio Manufacturers Group as the industry's official source book.

GIVES THIS IMPORTANT DATA

Contained within the hard covers of this 800 page MASTER BOOK are the listings of the products of 90% of all Radio Parts and Equipment Manufacturers in the industry. In it you will find many thousands of items, such as electronic devices, transmitting and receiving sets, tubes, antennas, transformers, condensers, replacement parts, meters, laboratory test equipment, relays, plugs, coils, wire, and numerous other radio components. Thousands of clear illustrations with descriptions and specifications. —Yes, this is your "MUST HAVE BOOK".

•• WHO USES IT? ••

As the official source book of the radio industry it is constantly used by many American and Foreign governmental agencies, also industrial organizations, engineers, purchasing agents, laboratories, radio amateurs and service men, radio distributors, broadcast stations, schools, colleges, libraries, and by many others interested in Radio and allied fields.

SAVES TIME—SAVES MONEY

WHERE, WHAT AND HOW MUCH: Such information is instantly at your fingertips. This Valuable RADIO MASTER eliminates the maintenance of bulky files. It is completely indexed for speedy reference.

If you buy, sell or specify you will find the RADIO MASTER an indispensable and handy book to have around at all times.

MONEY BACK GUARANTEE!

Order your copy today—look it over. You will find it to be an excellent investment; if not, return it to us in five days for full refund.

The price is only \$2.50 shipped anywhere in U.S.A.—\$3.00 elsewhere. We prepay transportation charges if remittance accompanies order.

UNITED CATALOG PUBLISHERS, Inc.
106A Lafayette St. New York, N. Y.

Index of Advertisers

	Page
A	
Aerovox Corp.	31
C	
Centralab	26
Clarostat Mfg. Co., Inc.	29
G	
General Electric	26
H	
Hygrade Sylvania Corp.	29
I	
International Resistance Co.	4
K	
Ken-Rad Tube & Lamp Corp.	3
M	
Mallory & Co., Inc., P. R.	Inside Front Cover
Meissner Mfg. Co.	25
N	
National Union Radio Corp.	9
O	
Ohmite Mfg. Co.	20
P	
Polymet Condenser Co.	28
R	
Radiart Corp., The	21
Radio & Technical Publishing Co.	30
Radio City Products Co., Inc.	22
RCA Mfg. Co., Inc.	Back-Cover
Readrite Meter Works	20
Rider Publisher, Inc., John F.	27
S	
Simpson Electric Co.	28
Solar Mfg. Corp.	Inside Back Cover
Sprague Products Co.	19
Supreme Instruments Corp.	30
T	
Triplett Elec. Inst. Co., The	1
U	
United Catalog Publishers, Inc.	32
United Transformer Co.	23
Y	
Yaxley Mfg. Division	Inside Front Cover



hurry!

Make your advertising space reservation within the next few days for the important MAY number of

SERVICE

A Monthly Digest of Radio and Allied Maintenance
Member A. B. C.

Guaranteed paid coverage of the buying power of the radio replacement parts field. Not a bit of waste circulation.


**FINAL FORMS CLOSE
MAY 11th**

●

Buy War Bonds and Stamps Regularly

●

TO "KEEP 'EM FLYING"
UP HERE...

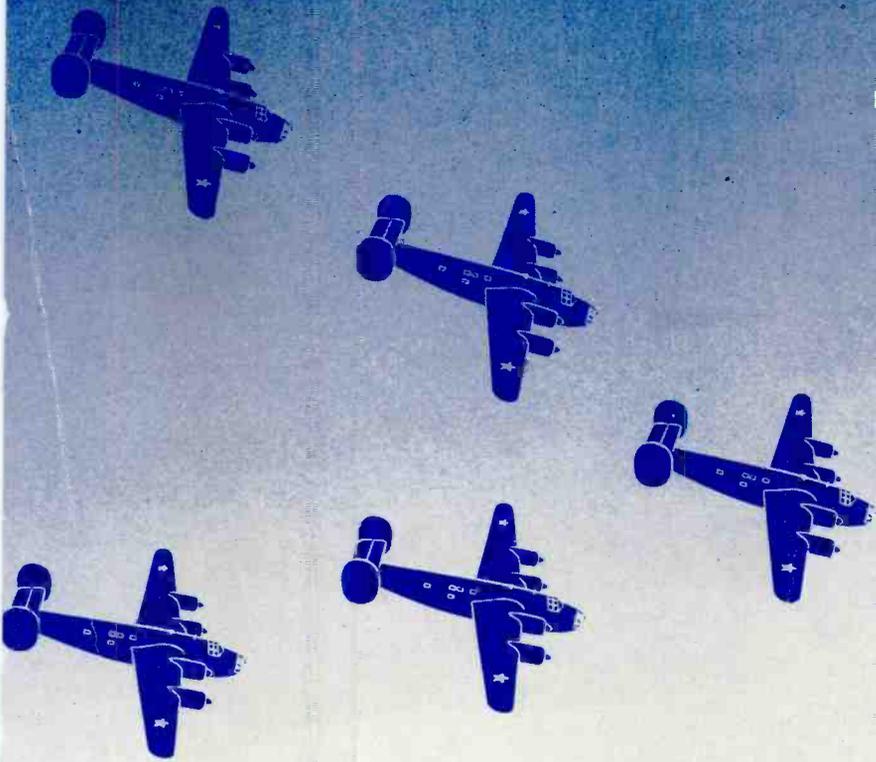

USE LESS ALUMINUM DOWN HERE!



Select SOLAR Electrolytics
which are "Aluminum-Savers"


ALUMINUM-SAVER TYPE DY

Zinc containers; excellent moisture protection. Convenient "twist-prong" mounting. Hermetically sealed and properly vented. Available in a wide range of single and multiple capacity units at all voltages.

ALUMINUM-SAVER TYPE DH


Processed cardboard containers. Provided with both mounting strap and mounting feet, for horizontal or upright mounting. Available in a wide range of single and multiple capacity units at all voltages.

SOLAR MFG. CORP., Bayonne, N. J.

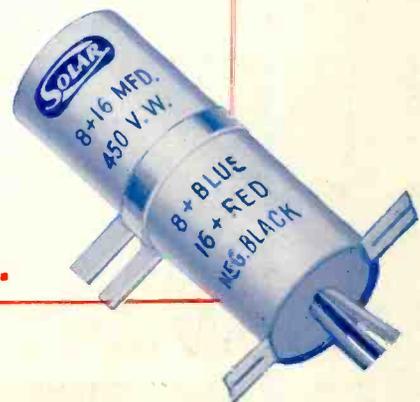

Ask for leaflet ALS-1

RCA AUDIO CHANALYST

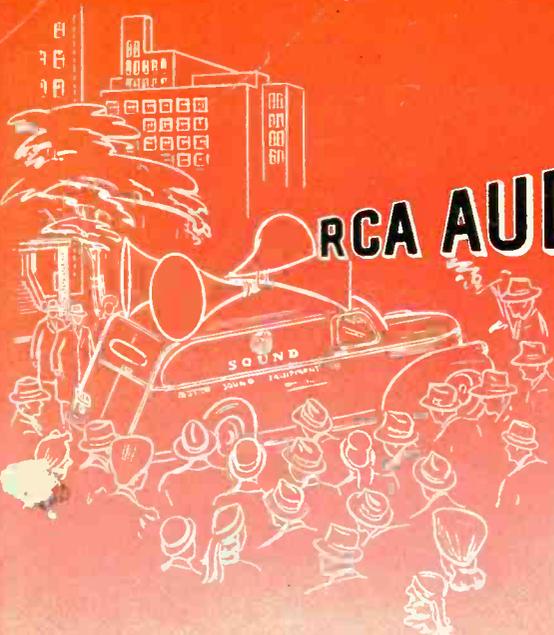

STOCK No. 170


\$225⁰⁰ net

Complete with cover and leads (Height, 12¹⁵/₁₆" ; Depth, 9³/₈" ; Width, 18⁷/₈" . Weight, unpacked, 35 lbs.)



"The Signal's the Thing!"

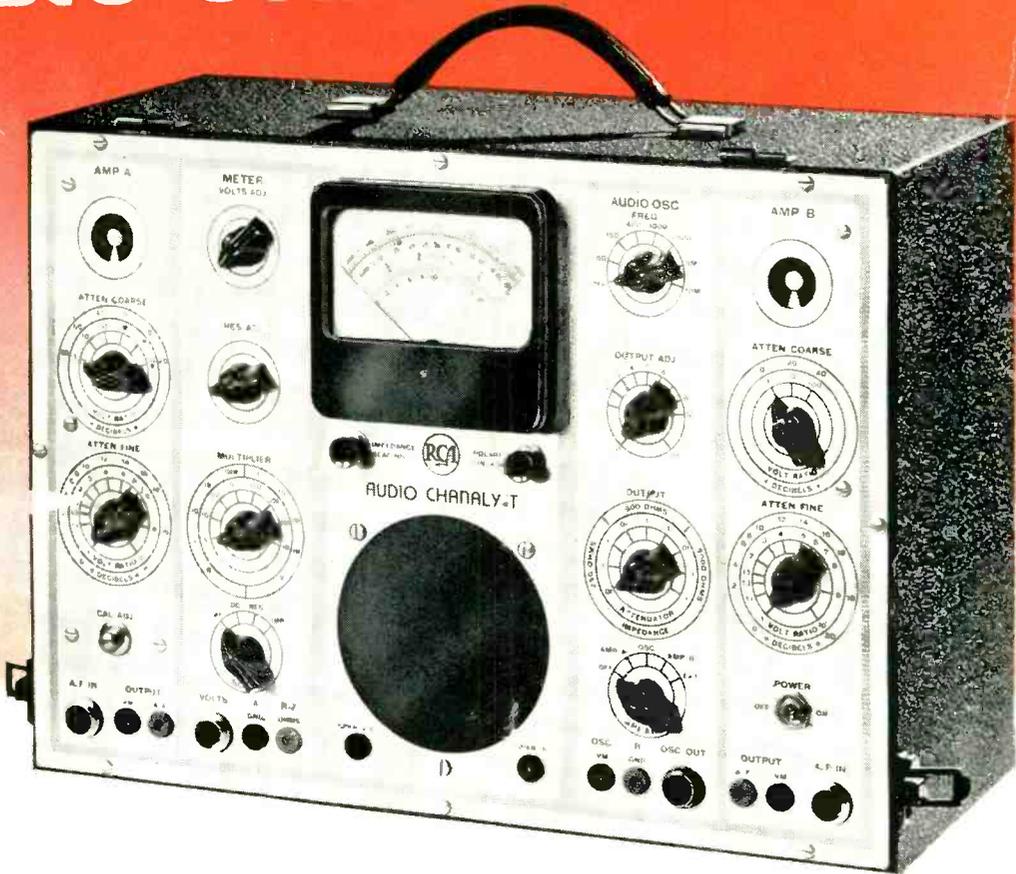With RCA Test Equipment being produced in ever-increasing quantities for war purposes, it has been impossible to supply many items for ordinary commercial and civilian uses. The signal tracing instruments illustrated here, however—and various other RCA units as well—are being produced steadily and are being supplied on priority orders.



A NEW TIME-SAVING MONEY-MAKER FOR THE SOUND EQUIPMENT SPECIALIST

All that the RCA Rider Chanalyst has meant to the radio industry in terms of better, faster and more accurate work, the new RCA Audio Chanalyst now means to the installation and checking of audio equipment.

Compact and portable, the Audio Chanalyst contains all necessary equipment for matching up a new sound installation or locating trouble in an old one. It will hold a continuous check on four different audio circuit conditions simultaneously without appreciably interfering with the operation of the system. It is equipped for all types of audio testing, such as checking gain and operating levels; noise and hum levels; a-f (a-c) and d-c voltages; resistance and impedance; supplying spot frequencies throughout the audio spectrum, and many more. A loudspeaker is provided for listening tests.

The RCA Audio Chanalyst permits a complete, rapid analysis of any audio system, and affords a positive means of isolating any troubles that may exist. To the busy technician, it comes as an instrument that will quickly pay for itself in the time it saves as well as in the greater efficiency its use makes possible. Sold by RCA Tube and Equipment Distributors. Folder free. Get the facts!



RCA Chanalyst Converter

Stock No. 164—Net \$55.00 (including Chanalyst coupling lead and special test cable and probe)

RCA Junior VoltOhmyst

Stock No. 165—Net \$37.50

RCA Rider Chanalyst

Stock No. 162—Net \$107.50



TEST EQUIPMENT

RCA MANUFACTURING CO., INC., Camden, N. J. • A Service of the Radio Corporation of America