


Service Business... and lots of it

That's what you want, isn't it? And brother, it's what you'll get when C-D's new, pre-tested promotional program goes to work for you.

Eye-catching post cards—punchy mailing pieces—attention-getting newspaper ads—hard-selling book matches—all these and lots more are included in this big promotional program which has actually *proved* its ability to help bring in service customers.

With the field getting crowded you no longer can depend on the sign in your window to keep you in business. Now is the time to step out from competition and build *your* name as *the* radio service shop in your community.

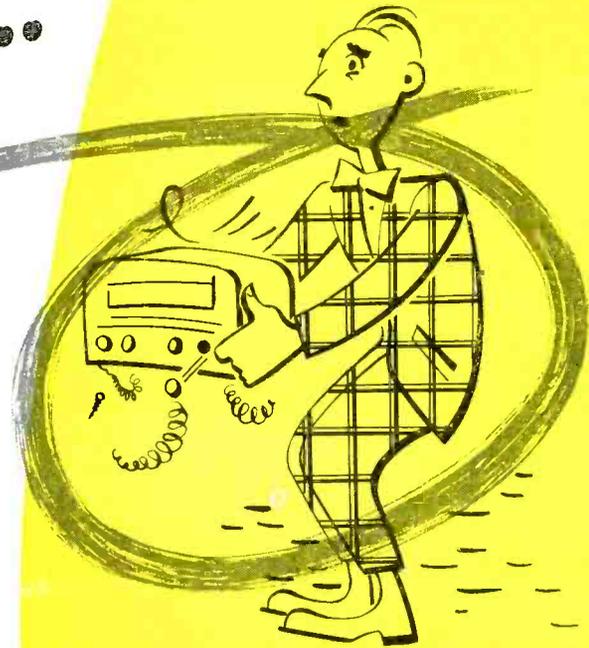
Don't wait until some competitor beats you to the draw. Find out from your jobber **TODAY** how C-D's new, tested promotional material will help you to build up the service business you want.



C-D HELPS THAT WILL BRING CUSTOMERS TO YOUR SHOP
You can get them all through your jobber



NEWSPAPER MATS

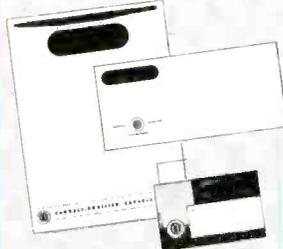


STATIONERY



DECALS

COUNTER CARDS

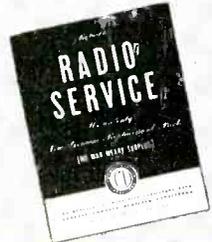

POSTCARDS



MATCH BOOKS

Your reputation depends
on the parts you use




Don't take chances—use C-D's Dwarf Tigers. They're top quality, long-lasting—fine where heat and humidity make the going tough.

FREE

your subscription to the "CAPACITOR"—the service man's bible. All the radio data of the month—every month—condensed for you. Mail coupon TODAY.

CORNELL-DUBILIER ELECTRIC CORP.
South Plainfield, New Jersey

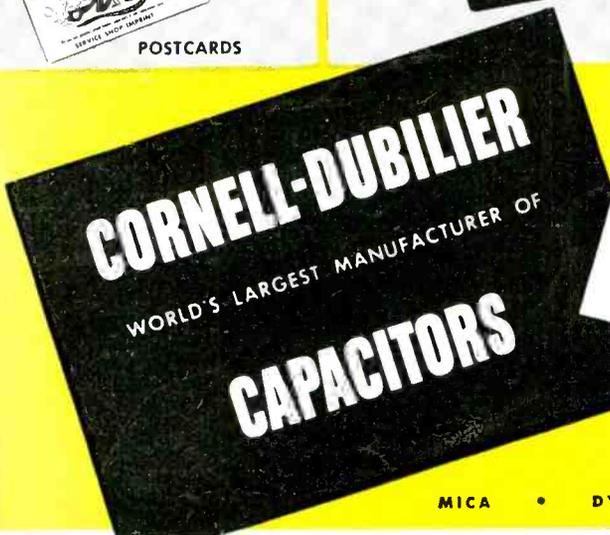
NAME.....
ADDRESS.....
CITY.....
STATE..... ZONE.....



MICA • DYKANOL • PAPER • ELECTROLYTIC

KEN-RAD

RADIO TUBES

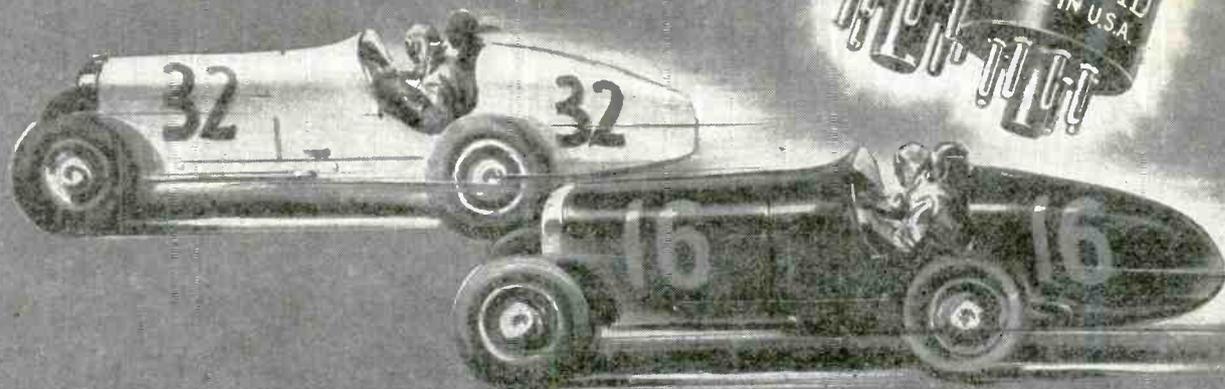

WITH KEN-RAD TUBES
You'll Set the Pace
 in SALES-SERVICE VOLUME...and PROFITS!

AHEAD of the field *always*—that's the position Ken-Rad tubes offer you as dealer or service man! New sets, with new circuits, are pouring into the market. Ken-Rad's up-to-the-minute research—*General Electric backed*—brings new-design tubes to you as needed, enabling you to work with confidence in the field of FM and other postwar radios.

Clients properly served are your backlog of future business. *You'll serve all radio*

owners better with Ken-Rad tubes . . . because in addition to their modern design, tone-rich performance is a feature . . . because each precision-made Ken-Rad tube is uniformly, dependably like others of its type . . . because 100-percent manufacturer responsibility is cartoned with every tube that you sell!

So team up with Ken-Rad for more sales to more customers, new and repeat—now and tomorrow.

Behind Ken-Rad radio tubes stands Electronics' first and greatest name—GENERAL ELECTRIC.



Write for Booklet ETR-16, "Essential Characteristics," the most complete digest of tube information available.

176-E1-6350

KEN-RAD

DIVISION OF GENERAL ELECTRIC COMPANY
 OWENSBORO, KENTUCKY

EDITORIAL

PLANNING, not only work of the day, but work of the future, has always been a profitable program to follow. During the next few years, the planning program will be more important than ever to the Service Man.

With the prospects of new highs in the sales of f-m and television receivers, and a-m receivers with their new types of circuits and components, Service Men will, with a carefully-planned installation, repair and maintenance program, be in a bright position to capitalize on the innumerable possibilities that will present themselves.

Such a program will demand the widest assortment of tools and test equipment that financial conditions will permit, and a working familiarity with new types of circuits and components used. To acquire this familiarity will require a careful study of all manufacturer's bulletins, latest technical data such as appear in SERVICE, new books, technical bulletin service, data and modern business practice books and bulletins now being published.

Familiarity with new housing developments also will be found to be an invaluable planning-program feature, for it will provide many leads for new business. And many set dealers will be found to be a useful source of new business leads, for they're always anxious to cooperate with local Service groups in both installation and maintenance work.

In including f-m as an important factor in the planning program, Government authorities have been used as a basis for this recommendation. In a recent talk before broadcasters in Chicago, FCC chairman Charles R. Denny said: "F-m is not coming. It's here. And it's growing fast. Already there are 66 stations in operation and 564 more authorized. In addition, there are 307 applications pending. Our long range plans for f-m look forward to the day when every square inch of every state from the Atlantic Ocean, west to the middle of the Dakotas, Nebraska, Oklahoma and Texas will be covered night and day with city f-m signals. Similarly f-m signals will blanket the Pacific Coast states." That's quite a statement. The FCC also has expressed the same enthusiasm in television. It won't be long before telecasts will be made in dozens of other cities besides those presently operating. The telephone company is rushing their coaxial cable program from coast to coast for television broadcasts.

The Service Man who will take full cognizance of these prospects and plan for the future will be a mighty busy man during the next few years.



Reg. U. S. Patent Office

Vol. 15, No. 12

December, 1946

LEWIS WINNER

Editor

ALFRED A. GHIRARDI
Advisory Editor

F. WALEN
Managing Editor

	Page
Annual Index, SERVICE, 1946	20
Midget Components for British Portables. By H. B. Barnard ..	9
New Models	27
Postwar V-T-V-M with Ohm-Db-Ma Measurement Features. By M. E. Lewis	10
R-C Amplifier Design Features. By Martin B. Roggers	12
Ser-Cuits. By Henry Howard	18
Servicing Helps. By Frank C. Keene	30
Tools and Accessories for the New Service Ship. By Alfred A. Ghirardi	16
CIRCUITS	
Capitol U-24 (Cover)	41
E-L Vario Tuner	42
Sylvania Polymeter	18
Vomax V-T-V-M	10
COVER	
Phono Portable for A-C/D-C/Battery (Capitol U-24)	41
SERVICING HELPS	
A-C/D-C Sensitivity Improvements	30
R-F Oscillator Remedies	30
Index to Advertisers	44
Manufacturers	
News	32
New Products	38
Jots and Flashes	44

Copyright, 1946, Bryan Davis Publishing Co., Inc.

Published monthly by Bryan Davis Publishing Co., Inc.
52 Vanderbilt Avenue, New York 17, N. Y. Telephone MURray Hill 4-0170



Bryan S. Davis, President
Paul S. Weil, Vice Pres.-Gen. Mgr.



A. Goebel, Circulation Manager
F. Walen, Secretary

Chicago Representative: Lawrence Wehrheim, 5510 W. Lemoyne Ave., Chicago 51, Ill.; Telephone MERRimae 7919
Cleveland Representative: James C. Munn, 2656 E. 126th St., Cleveland 20, Ohio; Telephone CEDar 7783
Pacific Coast Representative: Brand & Brand, 1052 W. Sixth St., Los Angeles 14, Calif.; Telephone MICHigan 1732
Brand & Brand, 1085 Mounadnock Bldg., San Francisco 5, Calif.; Telephone DOUGlas 4475

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

Radio Parts are EASY to identify

when you use
PHOTOFACT* FOLDERS

PARTS LIST AND DESCRIPTIONS

TUBES

ITEM No.	TYPE	REMARKS	REPLACEMENT DATA	INSTALLATION NOTES
1	6X4	Rectifier	6X4	
2	6AR5	Detector	6AR5	
3	6AV6	AF	6AV6	
4	6BE6	AF	6BE6	
5	6BD6	AF	6BD6	
6	6BE6	AF	6BE6	
7	6BE6	AF	6BE6	
8	6BE6	AF	6BE6	
9	6BE6	AF	6BE6	
10	6BE6	AF	6BE6	
11	6BE6	AF	6BE6	

CAPACITORS

Capacity values given in the rating column are in mfd. for Electrolytic and Paper Capacitors, and in mmfd. for Mica and Ceramic Capacitors.

ITEM No.	RATING	TRUETONE PART No.	MALLORY PART No.	SOLAR PART No.	SPRAGUE PART No.	AEROVOX PART No.	CORNELL-DUBIER PART No.	IDENTIFICATION CODES AND INSTALLATION NOTES
7(A)	40	500256	FP306*	DY-40+20-150	EL-24	AF88D	UP3515	Filter*
(B)	20	502158	TP429	S-4-2	TC-2	484-.2	DT4P2	Line Isolating
8	.2	502157	TP426	S-4-05	TC-15	484-.05	DT4S5	Line Filter
9	.05	502151	TP423	S-4-01	TC-11	484-.01	DT4S1	Prv. Amp. Plate
10	.01	502156	TP407	S-6-004	TC-24	484-.004	DT5D4	Audio Coupling
11	.004							

CONTROLS

ITEM No.	RATING	TRUETONE PART No.	MALLORY PART No.	SOLAR PART No.	SPRAGUE PART No.	AEROVOX PART No.	CORNELL-DUBIER PART No.	IDENTIFICATION CODES AND INSTALLATION NOTES
1	100							
2	100							
3	100							
4	100							
5	100							
6	100							
7	100							
8	100							
9	100							
10	100							
11	100							

RESISTORS

ITEM No.	RATING	TRUETONE PART No.	MALLORY PART No.	SOLAR PART No.	SPRAGUE PART No.	AEROVOX PART No.	CORNELL-DUBIER PART No.	IDENTIFICATION CODES AND INSTALLATION NOTES
1	100							
2	100							
3	100							
4	100							
5	100							
6	100							
7	100							
8	100							
9	100							
10	100							
11	100							



SIMPLE!

ACCURATE!

FAST!

CAPACITORS

Capacity values given in the rating column are in mfd. for Electrolytic and Paper Capacitors, and in mmfd. for Mica and Ceramic Capacitors.

ITEM No.	RATING		REPLACEMENT DATA								IDENTIFICATION CODES AND INSTALLATION NOTES
	CAP.	VOLT	TRUETONE PART No.	MALLORY PART No.	SOLAR PART No.	SPRAGUE PART No.	AEROVOX PART No.	CORNELL-DUBIER PART No.	INSTALLATION NOTES		
7(A)	40	150	500256	FP306*	DY-40+20-150	EL-24	AF88D	UP3515	Filter*		
(B)	20	150	502158	TP429	S-4-2	TC-2	484-.2	DT4P2	Line Isolating		
8	.2	400	502157	TP426	S-4-05	TC-15	484-.05	DT4S5	Line Filter		
9	.05	400	502151	TP423	S-4-01	TC-11	484-.01	DT4S1	Prv. Amp. Plate		
10	.01	400	502156	TP407	S-6-004	TC-24	484-.004	DT5D4	Audio Coupling		
11	.004	400									

What's your biggest headache when servicing radios? Identifying parts? With PHOTOFACT FOLDERS it's easy to locate and identify any item you want to find. Just look at the Complete Parts List . . . a list that's keyed to clear chassis photographs and a full page, easy-to-read schematic diagram. For instance, the capacitor listing alone gives complete data on capacity, voltage rating, function, replacement types . . . even includes installation notes.

No service problem can stump you when you use PHOTOFACT FOLDERS. They result from the actual examination of the receiver involved, and are not copied from the manufacturer's service data or from looking at his schematics. They tell you everything you need to know about any set manu-
*Trade Mark Reg.

factured since January 1, 1946—even to the restringing of dial cords. They do this by means of pictures, full-page schematics, original technical notes that help you work faster, more accurately...easily increase the number of jobs you can do in a week by fifty percent.

PHOTOFACT FOLDERS are sold in sets of 40, each set covering new radios, phonographs, record changers, intercommunication systems, recorders and power amplifiers within a short time after they reach the market. Their cost is only \$1.50 a set, including membership in the Howard W. Sams Institute. No other radio service compares with PHOTOFACT FOLDERS in completeness, accuracy or timeliness. Use the coupon. Mail it to your nearest radio parts supply house.

PUBLICATION DATES:
Set No. 9 December 19
Set No. 10 December 29

Cut this out and MAIL IT TO YOUR DISTRIBUTOR. If you do not know his name and address, send it directly to Howard W. Sams & Co., Inc., 2924 East Washington Street, Indianapolis 6, Indiana, and we will see that your nearest distributor gets it. In Canada—write to A. C. SIMMONDS & SONS, 301 King Street East, Toronto, Ontario. Canadian Price \$1.75.

PLEASE PRINT

Send Set No. 10 Send Set No. 9
(Circle one or more of following) Send Set No. 8, 7, 6, 5, 4, 3, 2, 1 (at \$1.50 a set)
 Send me a DeLux Binder (at \$3.39)
My (check) (money order) (cash) for _____ is enclosed. (If you send cash, be sure to use registered mail)

Name _____

Address _____

City _____ Zone _____ State _____

Company Name _____

My Distributor's Name _____

City _____

In Each PHOTOFACT FOLDER You Get—



1. A cabinet view of the receiver to help you establish identity and control functions.
2. A top view of chassis and speaker to identify component parts and alignment points.
3. A bottom view of chassis and/or accessories.
4. A complete list giving keyed reference to all parts, alignment and schematic diagram.
5. A complete, full-page schematic diagram.
6. Stage gain measurements listed on the schematic diagram.
7. A complete voltage and resistance analysis chart for rapid check of operational values.
8. Complete alignment instructions on the receiver consistent with the keyed alignment points indicated on photographs.
9. Dial cord diagram and restringing instructions.
10. Complete disassembly instructions where required.

HOWARD W. Sams & CO., INC. RADIO PHOTOFACT SERVICE

In Canada—write to A. C. SIMMONDS & SONS, 301 King Street East, Toronto, Ontario


OUR GREATEST ACHIEVEMENT

IN 16 YEARS OF
**"SERVICE for the
 SERVICEMAN"**

Greatest...
 IN
SERVICE
 "clarified schematics"
 and a separate
 "HOW IT WORKS" book

Greatest...
 IN
COVERAGE
 OVER 120
 SET MANUFACTURERS

Greatest...
 IN
SIZE
 2100 PAGES

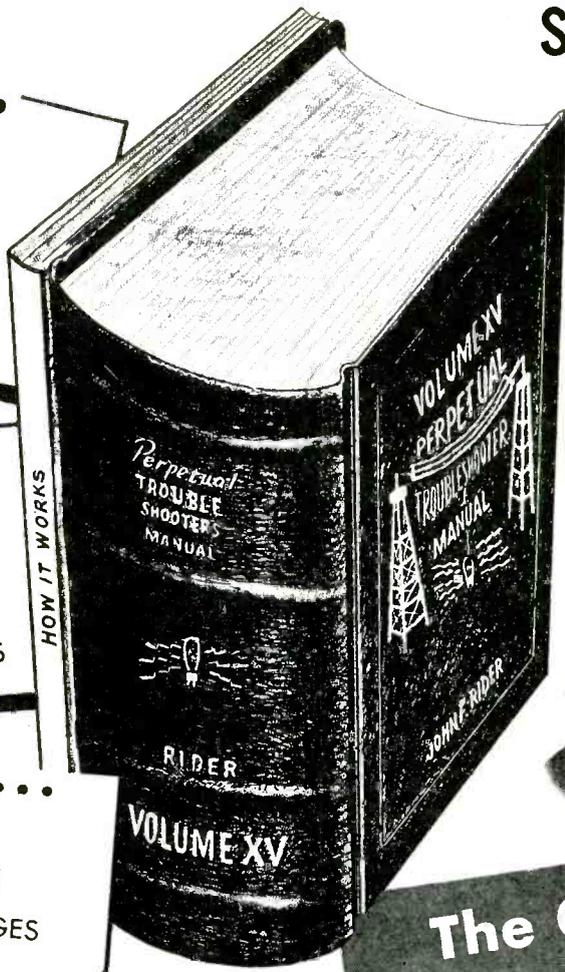

Proud as we are of the time-saving qualities of every Rider Manual, we consider Volume XV our crowning achievement in this respect. Thousands of man hours have gone into its preparation in order to save thousands of servicemen millions of hours.

"Clarified schematics," and separate "How It Works" book are but two of the exclusive features that characterize the thoroughness of presentation on the products of over 120 receiver and associated equipment manufacturers; but two of the reasons why Rider Manual Volume XV is the biggest single volume yet issued.

Nowhere will you find anything to equal it in completeness and helpfulness. Nowhere will you find the wealth of original material which means a saving of your valuable time—cash in your pocket.

Volume XV is the latest contribution to our continuing promise that you will always find in Rider Manuals all the servicing information you need to operate with the utmost efficiency and profit.

John F. Rider



**The GREATEST
 RIDER MANUAL
 Volume XV
 OUT IN JANUARY**

OTHER RIDER MANUALS

Volumes XIV to VII, each volume.....	\$15.00
Volume VI.....	11.00
Abridged Manuals I to V (1 vol.).....	17.50
Record Changers and Recorders.....	9.00

JOHN F. RIDER PUBLISHER, INC.
 404 FOURTH AVENUE, NEW YORK 16, N. Y.
 Export Div.: Rocke-International Corp., 13 E. 40 St., N. Y. C. Cable: ARLAB

RIDER RADIO BOOKS KEEP YOU IN TOUCH WITH SUCCESS

Inside the Vacuum Tube Solid concept of theory and operation	\$4.50
Understanding Microwaves Provides foundation for understanding	6.00
Radar Entertaining, revealing, in lay language	1.00
The Cathode Ray Tube at Work Accepted authority on subject	4.00
Frequency Modulation Gives principles of FM radio	2.00
Servicing by Signal Tracing Basic Method of radio servicing	4.00

The Meter at Work An elementary text on meters	\$2.00
The Oscillator at Work How to use, test and repair	2.50
Vacuum Tube Voltmeters Both theory and practice	2.50
Automatic Frequency Control Systems —also automatic tuning systems	1.75
A-C Calculation Charts Two to five times as fast as slide rule	7.50

Hour-A-Day-with-Rider Series—

On "Alternating Currents in Radio Receivers"	
On "Resonance & Alignment"	
On "Automatic Volume Control"	
On "D-C Voltage Distribution"	\$1.25 each



This new Rider Book, soon to be announced, will be of lasting usefulness to everyone interested in any phase of radio.

yesterday
proved
its quality

today
proves
its VALUE



IN THE FIELD



IN THE SHOP



Combination "DYNOPTIMUM" tube and set tester Model 802N

Accurate — dependable — compact — with a degree of flexibility that places it in a class all its own.

There you have it in a nutshell—a *partial* description of RCP's new, improved Model 802N. But *only* a partial description—because you can't describe this remarkable servicing instrument *fully* to anyone who has never used it.

Only by using it yourself can you learn all the features


that make Model 802N the unquestioned favorite of radio service men everywhere.

Examine Model 802N next time you see your jobber. Use it. Find out how it can speed up your work — add dollars to your income.

In handsome hardwood carrying case, complete with self-contained battery and test leads—Price \$59.50.

Check these features

- Exclusive method of A-C voltage measurements which eliminates temperature and frequency errors.
- Famous Dynoptimum test circuit employs 6H6 tube and has zero temperature characteristic while providing an extremely wide frequency range of 30 cps to 50 kc.
- 100,000 — ohm range is battery operated permitting resistance checks when regular A-C supply is not available.
- Capacity meter for testing electrostatic and electrolytic capacitors for leakage.
- Special adaptations are included for checking individual sections of multi-purpose tubes.
- Convenient jack for head-phone noise test to check swinging, noisy, or high-resistance connections.
- Large, rugged 4½" square-face meter with Alnico high-torque movement for quick, accurate readings.
- Housed in handsome, hand-rubbed, hardwood carrying case with compartment and self-latching cover. Furnished with high-voltage test leads.

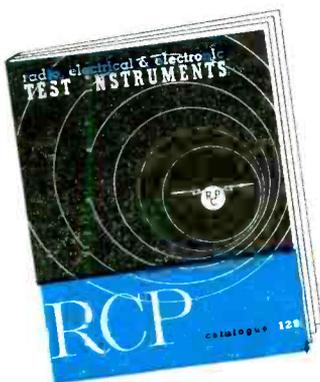

RANGES

D-C VOLTMETER: 0/10/50/500/1000 volts.
(1000 ohms per volt)

A-C VOLTMETER: 0/10/50/500/1000 volts.

D-C MILLIAMETER: 0/1/10/100/1000 milli-amperes.

D-C AMMETER: 0/10 amperes.

OHMMETER: 0/500/5000 ohms, 0/0.1/1/10 megohms.

DECIBEL METER: -8 to +15, +15 to +29, +29 to +49, +32 to +55 DB.

OUTPUT METER: 0/10/50/500/1000 volts.

If you'd like to have a complete display of America's finest line of testing equipment, write for a free copy of Catalog No. 129.

RCP INSTRUMENTS—BEST FOR EVERY TEST

RADIO CITY PRODUCTS COMPANY, INC.


127 WEST 26th STREET



NEW YORK 1, N. Y.

Listen!

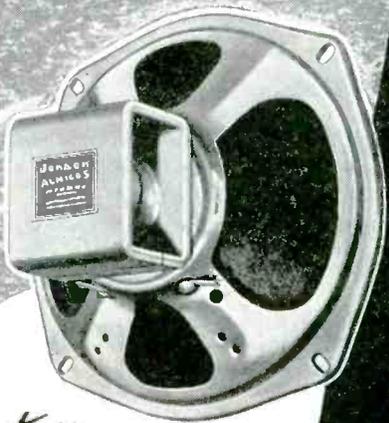2 NEW Jensen Extended Range High-Fidelity PM SPEAKERS



These two Jensen speakers, with *ALNICO 5* PM design, provide excellent high-fidelity performance. Excellent as replacement and modernizing units for FM and television receivers, radio-phonograph combinations, for studio monitoring, wired music, and for similar applications. Installed in Jensen Bass Reflex* cabinets, they provide exceptionally high-quality reproduction with added octaves of bass response.

*Trade Mark Registered

Listen ... it's a Jensen SPEAKER

Model P12-SH (Superseding PM12-CT). A new 12-inch high-fidelity *ALNICO 5* PM speaker. Designed for use with Jensen Model A-121 or Model D-121 Bass Reflex cabinets. Maximum power handling capacity in speech and music systems, 3 watts. Voice coil impedance, 6-8 ohms.

Standard Fidelity Model P12-S. Voice coil impedance, 6-8 ohms. Power handling capacity in speech and music systems, 3 watts.

Listen ... it's a Jensen SPEAKER


Model P8-SH (Superseding PM8-CT). A high-fidelity 8-inch *ALNICO 5* PM speaker. Recommended for use with Jensen Model A-81 Bass Reflex cabinet. Maximum power handling capacity in speech and music systems, 6 watts. . . . Voice coil impedance, 6-8 ohms,

Standard Fidelity Model P8-S. Voice coil impedance, 3-4 ohms. Maximum power handling capacity in speech and music systems, 8 watts.

BASE REFLEX CABINETS



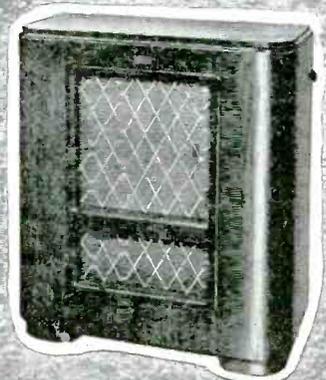Model A-81 —
for Model P8-SH speaker
Model A-121 —
for Model P12-SH speaker



Model D-121 —
for Model P12-SH speaker



Jensen

SPEAKERS
WITH
ALNICO 5

Designers and Manufacturers of Fine Acoustic Equipment ©1946

JENSEN MANUFACTURING CO., 6621 S. LARAMIE AVE., CHICAGO 38, U. S. A.

In Canada: Copper Wire Products, Ltd., 11 King St. W., Toronto, Ont.

SPRAGUE TRADING POST

is coming Back!

Your Own Swap, Buy or Sell Advertisement Run FREE—Send it in today!

Have you any parts or equipment you'd like to trade or sell to some other radio man who could put them to good use?

Are there any hard-to-get items you'd like to buy?

Want to get a radio job — or to hire a helper?

If so, write up your advertisement in brief form, rush it to Sprague. We'll run it **ABSOLUTELY FREE OF CHARGE** in the famous Sprague Trading Post that will start again next month in seven leading radio publications: **RADIO NEWS, RADIO CRAFT, QST, SERVICE, RADIO SERVICE DEALER, RADIO MAINTENANCE** and **RADIO & TELEVISION RETAILING.**

This famous Sprague service needs no introduction. During the war over 12,000 individual free classified advertisements were run for our friends. Everything, from parts and equipment to complete radio shops, was bought, sold and exchanged as a result.

In discontinuing The Sprague Trading Post at the close of the war, we thought there was no longer any need for it. But we were wrong! Hundreds of letters flooding in from all parts of the country tell us so. "*We need this sort of thing now as much as we ever did!*" is the gist of what our service and amateur friends say, "*Start it going again!*"

And so we're doing it! Send in your swap, buy or sell advertisement today!

Sincerely yours,

Harry Kalker
Sales Manager

**THIS IS THE WAY YOUR
FREE AD WILL LOOK**

FOR SALE — Standard model all-wave signal generator, \$25; modern tube tester with adapters, \$27.50; popular phono motor, \$15; power transformers and other parts. Write for list. **YOUR NAME and ADDRESS HERE.**

WANTED — Input i-f transformer and oscillator coil assembly for Model 15 Majestic. Will pay cash or trade. What do you need? **YOUR NAME and ADDRESS HERE.**

HELP WANTED — Need radio service man for busy dealer store in small Midwestern city. Well equipped shop. Write giving full details of experience. **YOUR NAME and ADDRESS HERE.**

INSTRUCTIONS: Print or type your advertisement CLEARLY. Hold it to 40 words or less including name and address. Confine it to radio subjects only. **MAKE IT EASILY UNDERSTANDABLE!** No commercial advertisements are acceptable. Sprague reserves the right to reject any copy that, in our opinion, does not fit in with the spirit of this free service. Your advertisement will be run in the first possible issue of at least one of the seven magazines on our list.

**Write it now. Mail it to
Dept.
SPRAGUE PRODUCTS COMPANY
North Adams, Mass.**



CAPACITORS AND *KOOLOHM RESISTORS FOR EVERY RADIO SERVICE AND AMATEUR NEED

*Trademark Reg. U. S. Pat. Off.

SYLVANIA NEWS

RADIO SERVICE EDITION

DEC.


Prepared by SYLVANIA ELECTRIC PRODUCTS INC., Emporium, Pa.

1946

ONE DEVICE NOW USED BY RADIO SERVICEMEN FOR GREAT VARIETY OF TESTS

Electrical Measurements Made Easy With New Sylvania Unit!

The SYLVANIA Poly (MULTI- PURPOSE) Meter

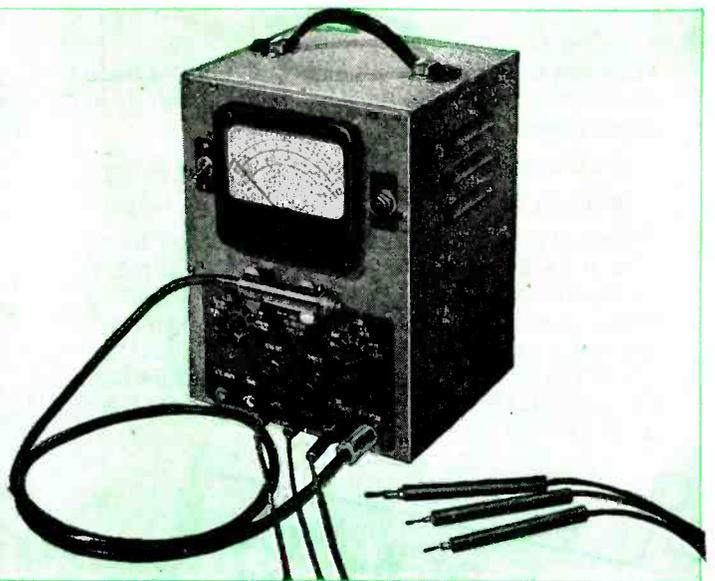

Radio servicemen now can use the new Sylvania Poly (MULTI-PURPOSE) Meter type 134 to facilitate a multitude of electronic measurements and tests to radio equipment.

This product of Sylvania Research is stabilized against errors due to voltage variations or gas current in tubes. All accessories included. See your Sylvania Distributor.

CHARACTERISTICS AND SPECIAL FEATURES

Tests audio, A.C. and R.F. voltages from 20 cps to 300 mc through use of proximity fuze-type tube built into handy probe. Full scale range of 3, 10, 30, 100, 300.

Measures D.C. from .1 to 1,000

volts in full scale ranges of 3, 10, 30, 100, 300, 1,000.

Measures D.C. current from .1 milliampere to 10 amperes in full scale ranges of 3, 10, 30, 100, 300, 1,000 milliamperes and 10 amperes.

Measures resistance from $\frac{1}{2}$ ohm to 1,000 megohms in full scale ranges of 1,000, 10,000, 100,000 ohms and 1, 10, 1,000 megohms.

ACCURACY

D.C. ranges $\pm 3\%$ of full scale.

A.C. ranges $\pm 5\%$ of full scale up to 30 volts and $\pm 7\%$ above 30 volts.

R.F. ranges $\pm 5\%$ of full scale up to 10 volts; $\pm 7\%$ from 10-100 volts; $\pm 10\%$ on 300 volt range.

Ohms $\pm 6\%$ to the left of $\frac{1}{2}$ scale; $\pm 13\%$ to the left of $\frac{3}{4}$ scale.

Current $\pm 3\%$ of full scale on all but 10 ampere scale which provides $\pm 5\%$ of full scale.

INPUT IMPEDANCES

R.E. ranges—2.7 megohms resistance shunted by approximately 3 mmf. capacity.

A.C. ranges—2.7 megohms resistance shunted by approximately 40 mmf. capacity.

D.C. ranges—16 megohms resistance. Remember the Sylvania Poly (MULTI-PURPOSE) Meter type 134. It's beautifully styled, compactly designed, has easily read meter and dials.

SYLVANIA ELECTRIC

Emporium, Pa.

MAKERS OF RADIO TUBES; CATHODE RAY TUBES; ELECTRONIC DEVICES; FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES; ELECTRIC LIGHT BULBS

SERVICE

MIDGET COMPONENTS For British Portables

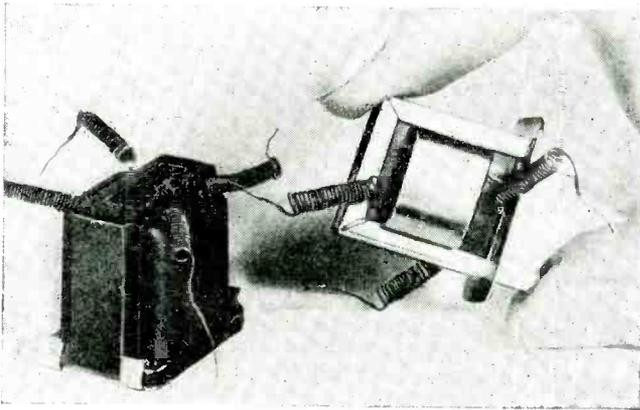


Fig. 1. Midget audio-frequency transformers which are available in skeleton form or with a bakelite case.

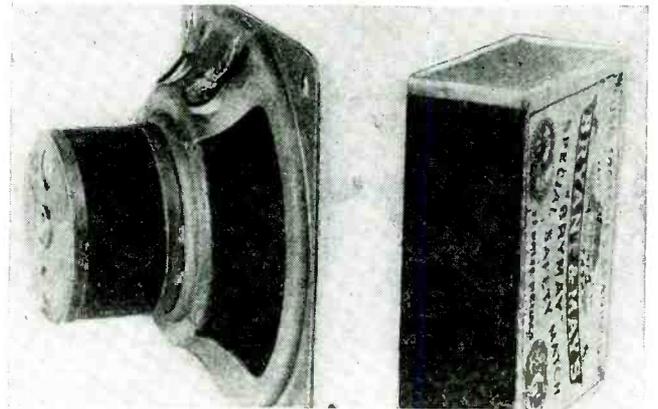


Fig. 2. Miniature permanent-magnet moving-coil loudspeaker which handles an input of 1/2 watt.

ONE OF THE BIGGEST MANUFACTURING problems with which Britain's radio industry was faced during World War II was that of reducing the size of components to a fraction of their standard dimensions.

There had been little or no demand in Britain for *personal* portables and manufacturers had not, therefore, gone into the question of miniaturization. When, however, the Supply Ministries requested industry to produce miniature components for lightweight equip-

by **H. W. BARNARD**

London, England

ment to be used by forward troops and for such apparatus as combined transmitter-receivers small enough to be worn on the belt by agents and members of resistance groups in enemy-occupied territory, research workers in Britain's radio industry set about

getting the proverbial quart into a pint bottle.

An excellent example of miniature design was the miniature capacitor developed for the proximity fuse, a tubular paper capacitor, rated for a d-c working voltage of 500. The overall length for capacitances of from 0.0005 to 0.01 mfd was 3/4", excluding connecting wires, while the diameter varied from 1/8" to 1/2". The units, wound and connected to provide mini-

(Continued on page 28)

Fig. 3. Parts of a small moving coil headphone, compared with a safety razor blade. The moving coil is only 1/2" in diameter.



Fig. 4. Prototype of Britain's first miniature 4-tube 2-band superhet portable, with its layer-built high-voltage battery photographed against a telephone for comparison. Plastic case for set is 8 3/4" x 3 3/4" x 3 3/4".



(Courtesy Vidor)

POSTWAR V-T-V-M



An analysis of the Vomax, with practical operation and maintenance data based on twelve months of field experience.

Fig. 1. Control panel of the vacuum-tube voltmeter which measures resistance, d-c, db, d-c and a-c volts from 20 cycles to over 100 mc.

by M. E. LEWIS

IN LOCATING AND CORRECTING troubles in receivers, accurate measurements must be used. It is impossible, for instance, to check operating potentials of the many vacuum tube circuits in the modern receiver without measurement equipment. Measurements are the basic, fundamental yardstick by which proper or faulty operation must be diagnosed.

Before the war voltage measurements, due to limitations of then available meters, were pretty much restricted to measurement of voltages present in power circuits of receivers—circuits in which voltages to be measured would not be disastrously dropped by application of low-resistance, power-consuming meters. Then usual voltmeters could not be used to measure actual operating voltages upon a-c-controlled grids, series-resistance-isolated plates and screens, high-resistance a-c lines, or at resistance-coupled amplifier grids and plates. The

possibility of really time-saving measurement of a-f, i-f and r-f signal voltages lay in the distant future. This was because the usual 1000 ohm-per-volt d-c meter required significant power to function, power not available in such circuits. In a-c circuits the situation was even worse. Copper-oxide rectifiers, used to convert a-c voltages into current required to actuate the d-c meters, not only showed very low input resistance, but exhibited errors seriously increasing with frequency even in the low a-f range.

The need to measure voltages, present in circuits of such high resistance that they could not possibly supply the current required to actuate simple volt-ohm-milliammeters resulted in the development of vacuum-tube voltmeters. In their prewar forms v-t-v-m units were afflicted with errors due to variations in operating potentials of their own vacuum tubes, errors due to changes in characteristics of ageing tubes, and false readings due to small but real residual gas and ion cur-

rent in these tubes. Nevertheless the v-t-v-m was a great step forward. Their general usage only awaited further development of the art. That development has been achieved, prewar deficiencies have been overcome and the v-t-v-m has become a *must tool* of every Service Man.

In developing a postwar v-t-v-m, one designer¹ has produced a combination unit, a vacuum-tube-volt-ohm-db-ma meter. This instrument, the Vomax, shown in Fig. 1, features a removable r-f probe for direct contact to r-f and i-f circuits.

V-T-V-M Operation

In placing the unit in operation, the r-f probe must be fully inserted into its panel receptacle, with black (negative) and red (positive) test prod tips *not* inserted in panel jacks. The a-c plug is then inserted in line. *Adj.Ω* knob is turned so that *on-off* switch clicks on and pilot bezel illuminates. While allowing 30 to 60 seconds for tube warm-up, *Function* knob is set to *D.C.+* and *Range* knob to 3 V. Then meter pointer is set to zero on meter scale by adjusting *Set V. Zero* knob.


As tubes warm up meter pointer may move up or down scale, possibly even off scale. Incidentally, the meter cannot be injured by over-scale deflection. It can be injured only by overload in direct-current measurement, but is protected against burnout in all voltage, resistance and db operations. If this meter deflection isn't desired during tube warm-up, *Function* knob may be set to *ma* position for initial 30 to 60 second warm-up period.

With these initial adjustments completed, several interesting instrument-characteristic tests may be conducted. It is possible, for instance, to see to what extent errors due to grid and gas current have been eliminated by moving the *Range* knob from 3 V progressively through all six positions to 1200 V.

Meter zero will not shift more than 1% to at most 2% of full scale as *Range* switch is rotated. In rotating this switch the value of grid resistance (meter's d-c input resistance) of the upper section of the center 6SN7GT is changed from 50

¹McMurdo Silver.

Fig. 2. Interior view of v-t-v-m.

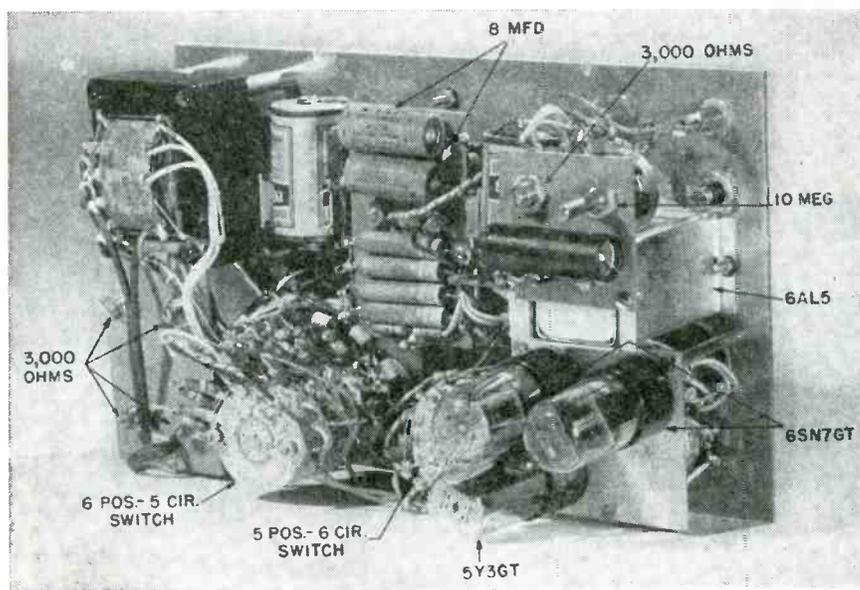

R-C AMPLIFIER

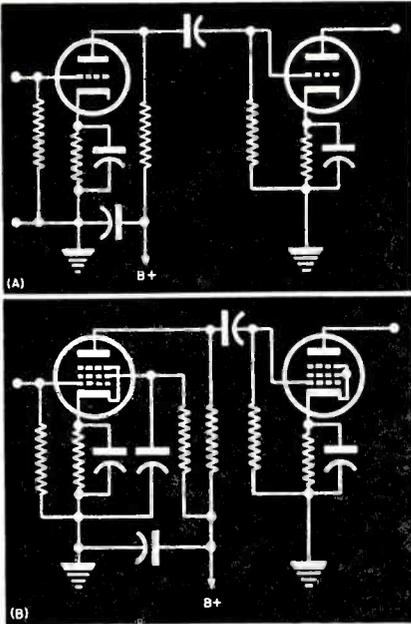



Fig. 1. Two typical resistance-capacitance coupled audio amplifiers. In *a* we have a triode type. In *b* a pentode has been substituted. The essential difference between the two circuits is the use of the screen-grid circuit. Component values are a function of the frequency response and the gain.

THE TWO IMPORTANT characteristics of an audio amplifier are the stage gain and the frequency response. In audio stages using resistance and capacitance in the coupling network, both frequency response and amplification are, in part, a function of component values, and are also closely related to each other.

Fig. 1 shows two typical resistance-coupled amplifiers, one employing a triode, the other a pentode. In essence, both employ the same system.

In Fig. 2 we have the *r-c* network of the triode, isolated from the associated tubes for simplicity. In *a* R_1 represents the plate load resistor. This is shown as returning directly to ground, since for audio voltages the *B* supply filter capacitor acts as an effective short, due to its very low reactance or a-c resistance to audio frequencies. R_2 is the grid return resistor of the following stage while C_1 is the coupling

Fig. 2. Here the *r-c* component of the audio amplifier of Fig. 1 has been isolated. In *a* the components have been arranged to show that the coupling capacitor and grid resistor form a voltage divided network. In *b* the resistor, R_{c1} , is used to represent the equivalent resistance of the coupling capacitor.

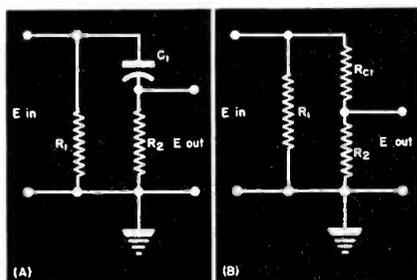

capacitor. In *b* the coupling capacitor has been replaced by its equivalent a-c resistance. It will be noted that the capacitive resistance, in conjunction with the grid-return resistor, form a virtual voltage divider for any voltages developed across the plate load resistor.

Since the a-c resistance of the coupling capacitor will vary depending on the frequency of the impressed voltage, the voltage across the grid resistor will also vary. In explanation, the formula for computing the reactance of a capacitor for any frequency is

$$X_c = \frac{10^9}{2\pi f C}$$

Where: X_c = capacitive a-c resistance in ohms

f = frequency of voltage in cycles

C = capacitance in microfarads

Once the reactance of a capacitor has been established, the action of voltage and current is the same as in d-c circuits. Thus, a .016-mfd capacitor has a reactance of 100,000 ohms at 100 cycles, 10,000 ohms at 1,000 cycles, and 1,000 ohms at 10,000 cycles.

Since the value of the grid resistor remains constant at all frequencies, a proportionately greater percentage of the imposed audio voltage will appear across the grid resistor, as the frequency increases.

Now let us assume that in the network of Fig. 2a the capacitor, C_1 , has a value of .016 mfd, R_1 is a .25-megohm resistor and R_2 is a .5-megohm unit. For an input voltage of 10, the drop across R_2 will be:

$$\begin{aligned} \text{At 100 cps.} & \dots \frac{R_2}{R_{C1} + R_2} \times E \\ & \dots \frac{.5}{.5 + 100,000} \times 10 \text{ or } 8.85 \text{ volts} \\ \text{At 1,000 cps.} & \dots \frac{.5}{.5 + 10,000} \times 10 \text{ or } 9.8 \text{ volts} \\ \text{At 10,000 cps.} & \dots \frac{.5}{.5 + 1,000} \times 10 \text{ or } 9.99 \text{ volts} \end{aligned}$$

If the value of C_1 were increased to .16 mfd, its reactance or a-c resistance would be 10,000 ohms at 100 cps, 1,000 ohms at 1,000 cps, and 100 ohms at 10,000 cps. Solving for the grid voltages at these frequencies, we would

have 9.8, 9.99 and 9.999 volts, respectively. Thus, increasing the value of the coupling capacitance would tend to give a more uniform output over the audio range.

A similar expedient would be to increase the value of grid resistor. Thus, if the grid resistor were increased to 1 megohm, with a coupling capacitance of .016 mfd, the grid voltage for a 10-volt input would be 9.1 volts at 100 cps, 9.9 volts at 1,000 cps, and 9.99 volts at 10,000 cps. Therefore, increasing either C_1 or R_2 will achieve a more uniform response over a band of frequencies, as well as increase the voltage at all frequencies. In another sense, it may be said that the low frequency response has been improved, since both expedients afford a greater effect at the low frequencies than at the high frequencies.

The actual resistance values are slightly lower, due to the presence of the tubes. This will be discussed later in this article.

The next influence on the operation of the *r-c* amplifier is the cathode network, consisting of the cathode resistor and associated bypass capacitor.

The cathode bypass capacitor is, as the term implies, a bypass for any audio voltages developed across the cathode resistor; Fig. 3. In *a*, a typical resistance-coupled audio amplifier stage is shown. Fig. 3b shows the equivalent resistive load on the *B* supply. R_p designates the resistance of the plate-to-cathode path within the tube. Any a-c voltage developed across this circuit would cause voltage drops to appear across all three resistors. However, for a-c voltages, the tube's plate resistance and cathode resistor are actually in parallel with the load resistance; Fig. 3c. In the presence of the reactance introduced by the bypass capacitor, the a-c voltage drop across the cathode resistor would be reduced, since the capacitor is in parallel with it. This has two important aspects.

First, since the a-c voltage drop across the cathode resistor would serve no useful purpose in the amplification functions of the tube, the drop across the plate-load resistor would be increased, slightly. However, this is not the chief purpose of the bypass capacitor.

The effective input circuit is directly between grid and cathode. Therefore

DESIGN FACTORS

by MARTIN B. ROGERS

any voltage, either a-c or d-c, would affect the sum voltage impressed on the grid. Since the a-c voltage developed across the cathode resistor is in opposite phase to the input voltage impressed on the grid, it would buck the input voltage. Thus, the input voltage would be decreased, and, in turn, the resultant plate voltage. This principle is the basis of inverse feedback, and tends to reduce the stage gain. And thus we have the second purpose of the capacitor; where gain is desired, the value of bypass capacitor determines the stage gain. In this respect, since the reactance of the capacitor increases as the frequency decreases, the stage gain will be reduced at low frequencies and increased as the frequency increases. Thus, a high farad bypass capacitor would increase the gain at low frequencies in much the same manner as it does when used for circuit coupling.

In receiver design, where component cost is a factor, the lowest capacitance consistent with adequate design is used, since the cost is less. In service work the same cost factor does not obtain. For this reason, it is permissible to use a 25-mfd bypass to replace a 5-mfd. In some respects this procedure is advised providing a reduction in hum, since many tubes introduce hum in their cathode circuit, due to the proximity of the tube cathode sleeve to the a-c heated filament. Leakage between the cathode sleeve and the filament will create a slight 60-cycle voltage across the cathode resistor, which, in turn, will be amplified by the tube. On the other hand, some receivers purposely use low-farad capacitors which permits a slight hum in the first audio stage. By using a low-farad capacitor, a low-frequency bucking voltage is created in the cathode circuit which cancels out the hum, along with other low frequencies.

The value of cathode resistor is determined by the operating voltages and plate-load resistance. In general, the higher the value of plate-load resistance the higher will be the value of cathode resistance. Again, the higher the applied *B* voltage, the lower will be the cathode resistor.

The cathode voltage also influences the stage gain and fidelity. Thus, too

high a cathode voltage may cause the tube to approach its cutoff voltage, in which case not only will the stage gain be reduced, but since the plate current will approach the zero point, amplitude distortion will be introduced. This is equivalent to the detector action of the tube, in which only half of the a-c envelope is amplified. The action is demonstrated in Fig. 4.

The cathode voltage also determines the maximum permissible input driving voltage. If the input voltage at the grid were to exceed the cathode, the net grid voltage would then be positive and the grid would then draw current. This would cause distortion, since the load on the input source would vary from practically no load when the grid is biased, to a comparatively heavy load when the grid is positive. It should be noted that most a-c and v-t meters measure rms voltages, which are 70% of the peak value. Therefore, for each volt of cathode bias, only .7 volt of input voltage, as measured on a v-t voltmeter is permissible.

The maximum value of grid resistor, which should always be used, is usually found by consulting the tube manual. In general, higher values of grid resistance are used with cathode bias than with fixed bias. The value of grid resistance is determined by the tube characteristics and its construction. Some gas always remains in the tube when it is evacuated. This gas has a tendency to create some current flow in the grid circuit. This current flow will create a positive grid voltage which will, to some extent, cancel the bias voltage. In some tubes this action may continue until the excessive plate current destroys the tube. In those tubes employing cathode bias, the self-regulating action of the bias resistor prevents this action, since any increase in plate current increases the bias, which in turn, decreases the plate current. Thus, the cathode resistor acts as a safety factor.

The screen voltage, like the cathode voltage, determines the plate current. And, like the cathode circuit, introduces an impedance into the plate circuit. Thus, in pentode circuits, the screen voltage should be adjusted to give the desired plate current. The

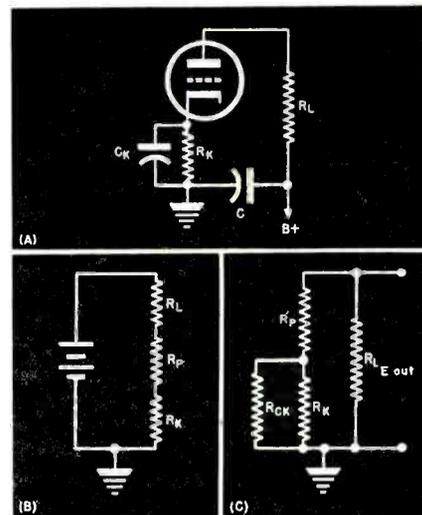


Fig. 3. In *a* an individual triode r-c amplifier is shown. In *b* appears a plate network across the *B* supply. In *c* we have the equivalent plate impedance. It will be noted that the reactance of the cathode bypass is in shunt with the cathode resistor for audio voltages.

plate current, in turn, determines the ratio of actual plate voltage to the voltage drop in the plate-load resistor. The proper size screen-dropping resistor may best be determined by consulting tube manual tables for resistance-coupled amplifiers. Since the screen grid introduces impedance in the plate circuit, the value of bypass capacitor will affect the low-frequency response in much the same manner as the cathode bypass. Generally, a .5-mfd capacitor is sufficient, although higher values will increase the low frequency response.

The gain of an audio stage is a function of the amplification factor of the tube and the load resistance in the plate circuit. An important aspect of component values comes to light when the circuit is analyzed in terms of effective load impedance. Fig. 5 shows the total load impedance of an r-c amplifier stage for both high and low frequencies. For the low frequencies the plate resistance of the tube is in parallel with the plate-load resistance. These, in turn, are in parallel with the reactance of the coupling capacitance which, in turn, is in series with the grid resistor of the following stage.

At high frequencies, the coupling capacitor loses its importance, but two additional factors are introduced. These are the input and output capacitances of the tubes involved. For example, the input capacitance of a 6C5 is 4.4 mmfd and the output capacitance is 12 mmfd. Since these capacitances are in parallel, they may be represented by their equivalent reactance, or resistance. At 10,000 cps this is equivalent to a load impedance of less than 1 meg-

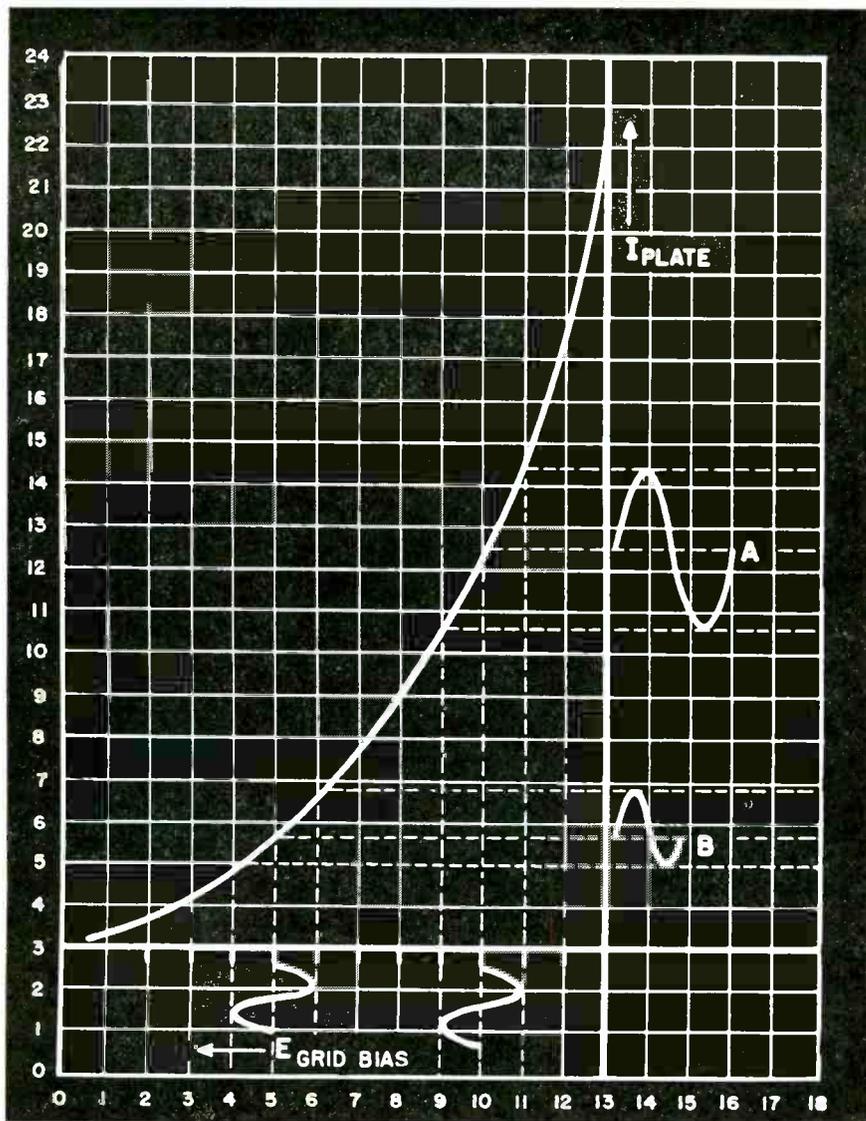


Fig. 4. Here is shown the effect of incorrect bias on an audio tube. Curve A is the response at normal bias, while B shows the distortion resulting from too high a bias. The action is equivalent to that of a biased detector.

ohm. Its effect on the high-frequency response will therefore be considerable, if higher resistance plate and grid resistors are used. On the other hand, the 6SF5 has input and output capaci-

ties of 4 and 3.6 mmfd, permitting higher values of load resistance.

Where Fig. 5 shows the equivalent plate-load impedance, it also shows the equivalent grid-load impedance. The same logic applies to this circuit. Therefore the size of grid resistance is also limited by the input and output capacitances of the tubes employed.

The foregoing has been explained to show that increasing the value of plate and grid resistors will not necessarily increase the stage gain or the frequency response beyond certain limits. Therefore, when designing *r-c* amplifiers, all factors must be taken into consideration.

Practical design factors influence the choice of components. For exam-

ple, cathode bypass and coupling capacitances are limited in value, when used for low frequency improvement, by the filter systems used. Using large values may sometimes cause regeneration and feedback, or oscillation. To prevent this, *r-c* filter networks may have to be used in the plate and grid circuits of *r-c* amplifiers. The control grid filter network is only used when fixed bias is employed. Again, the design of the stage will be influenced by the purpose of the stage. That is, whether the stage is to be used for low-level or high-level operation. If low-level operation is intended, higher values of plate-load resistance may be used. On the other hand, if high output voltage is needed, components must be so selected that the voltage at the plate of the tube represents at least 50% of the supply voltage. For high gain at low levels, the actual plate voltage may be reduced to 20% of the supply voltage.

Where low-frequency response is desired, fixed bias is sometimes preferable to self bias. By obtaining the bias voltage from a bleeder resistor, a lower impedance path is thus possible, permitting the return of the cathode directly to ground. Since the bleeder network utilizes higher currents than are obtainable from the individual tubes, bias-resistance paths of 25 to 50 ohms are possible. However, *r-c* filter networks may be necessary in the grid circuits for decoupling purposes. This is particularly desirable where pentode tubes are used, since the same reasoning applies to the screen-grid supply.

In some receivers, it will be noted that the 6SQ7, when used as a detector and first audio tube, does not use any bias voltage. Where this condition obtains, it will be noted that the grid resistor is of the order of 5 to 10 megohms. The same is true of many battery-type tubes. There are several factors which influence this type of design. The first, of course, is the cost factor. The elimination of a cathode resistor and bypass is a saving. Electrically, this method is feasible, since it is only used where low *B* voltage supplies are used. Since the gain of the tube is quite high, and since they are usually used in conjunction with beam-power type output tubes which require very low driving voltages for maximum output, the applied grid-input voltage is always a very small portion of one volt. The high resistance in the grid circuit prevents any appreciable current drain on the input system, since even a one-microampere grid current would create a bias voltage of 5 to 10. Again, since the input

(Continued on page 43)


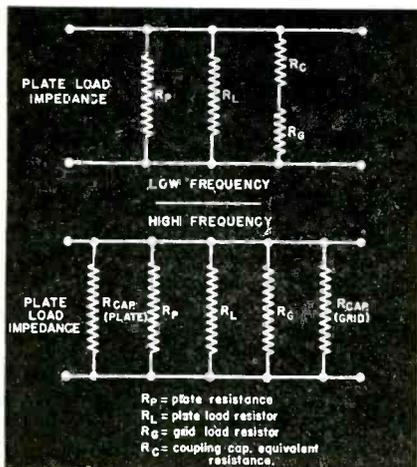


Fig. 5. The true plate load impedances at low and high frequencies. At low frequencies, the reactance of the coupling capacitor is a factor, while at high frequencies the input and output tube capacitances affect the plate load impedance.

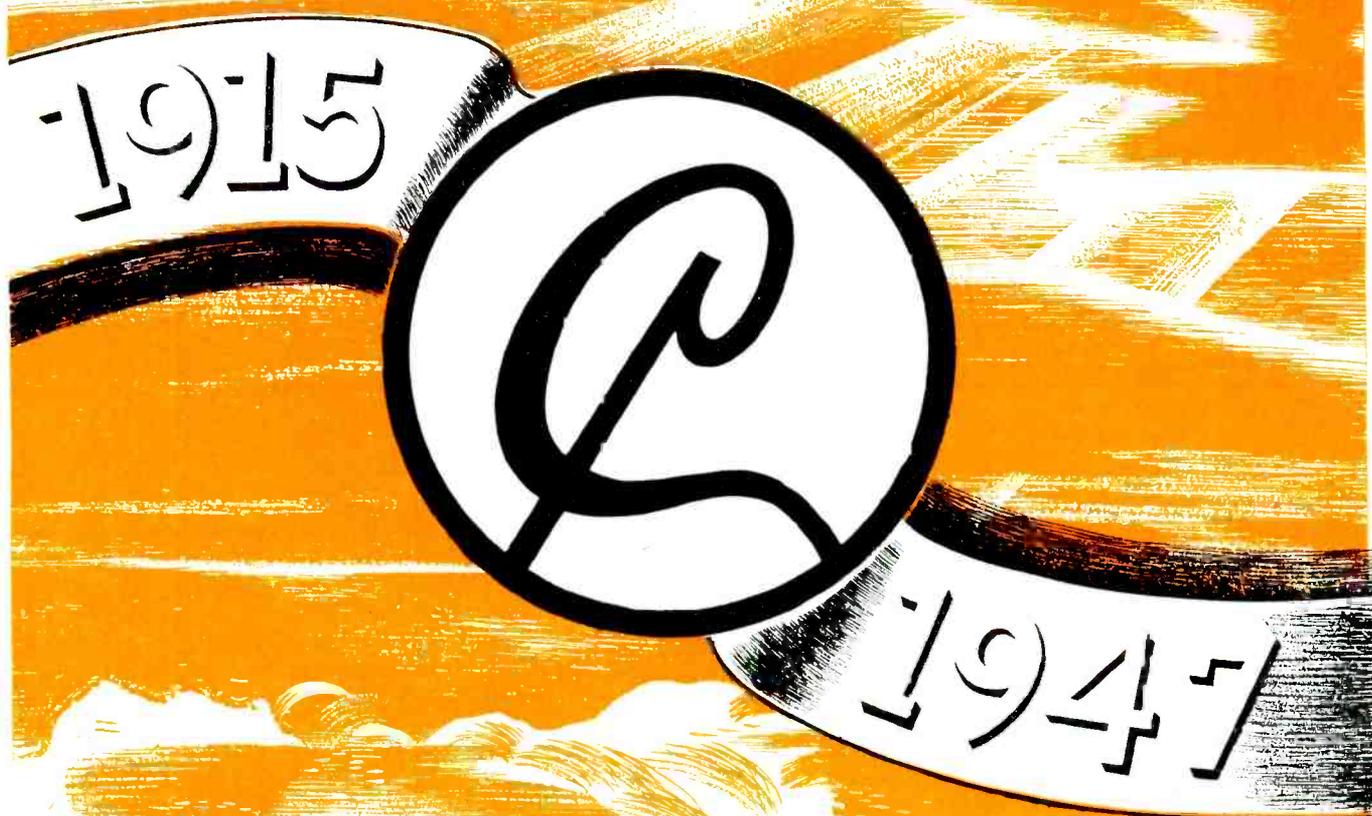The Symbol of High Quality and Performance for Over 30 Years



An Old Timer extends the Season's Greetings

Cunningham wishes you all a merry Christmas and a prosperous New Year.

Cunningham is going to do everything possible to help *make* 1947 a prosperous New Year for you. Not just by helping you sell more tubes—but by helping in the other departments of your business, so that your over-all profits will be greater in the coming year. That means the best in sales and service promotion material, the best and most up-to-date technical

literature, plus the benefits of the expert merchandising counsel of a corps of field representatives who survey the markets and report their findings regularly to Cunningham distributors.

Remember, too, that Cunningham is backed by the engineering leadership of the Radio Corporation of America, and has been a favored tube for more than 30 years. It all adds up to the fact that you'll be ahead with big "C" in 1947.



**A QUALITY PRODUCT FOR RADIO SERVICEMEN
AND DEALERS BY THE RADIO CORPORATION OF AMERICA**

TOOLS And ACCESSORIES

For the NEW SERVICE SHOP

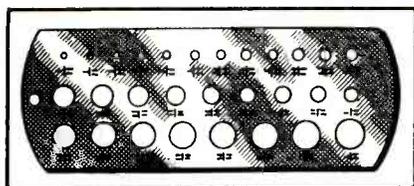


Fig. 1. A twist drill gauge.

OTHER TOOLS OF IMPORTANCE to the Service Shop include drill gauges, rules and scales, dividers, trimming knives, woodworking tools, and trouble-shooting lights.

Twist Drill Gauge

The various uses for a drill gauge were explained in the first article (*Basic Tools*) of this series,³ so they will not be repeated here. A simple gauge of the type shown in Fig. 1 will suffice.

Rules and Scales

Only a few simple measuring tools are required for making all necessary measurements of size, distances, etc. Some form of long measuring rule is

assumed to be necessary for some jobs—for example, measuring the length of wire needed for outdoor antenna installations, extension wiring, etc. A 6' flexible steel push rule of the type illustrated at (a) of Fig. 2 will come in handy for such work. A 2' folding rule of the type shown at (b), which contains a metallic sliding caliper for measuring the diameter of such round objects as bolts, tuning capacitor shafts, tube sockets, etc., is also recommended.

An extremely useful multi-use rule and gauge that costs only a dollar, and is supplied in a leather case, is illustrated at (c). In laying out the holes that are to be cut in a chassis or panel for objects such as tube sockets, control shifts, meters, etc., just to cite one

example, the rule and gauge may be used as a center-finding tool (because the center of a hole which may have been spotted by drawing the circular outline of the object to be mounted can be found with it). It may also be used as a square, as a level protractor for measuring or laying out angles, or as a circle divider. These uses are illustrated by the inset drawings at the right of (c) of Fig. 2. When twist drills are being resharpened, the proper fixed angle to which the drill point should be ground may be checked with it, as illustrated in the main drawing at (c). Of course the 5" ruled scale also has many uses.

Dividers

Dividers are extremely useful in chassis or panel layout work. Wing dividers of the kind illustrated at (a) of Fig. 3 are recommended. Distances between mounting and other holes can be laid out accurately with them.

(Continued on page 34)

Fig. 3. At (a), a pair of wing dividers. At (b), a trimming knife with three interchangeable blades of different sizes. (Trimming knife views, courtesy Somar Specialty Corp.)


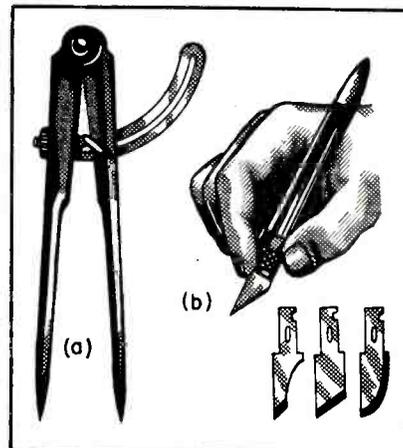


Fig. 2. A few simple types of rules or scales that enable all ordinary measurements to be made. (Courtesy General Hardware Mfg. Co.)

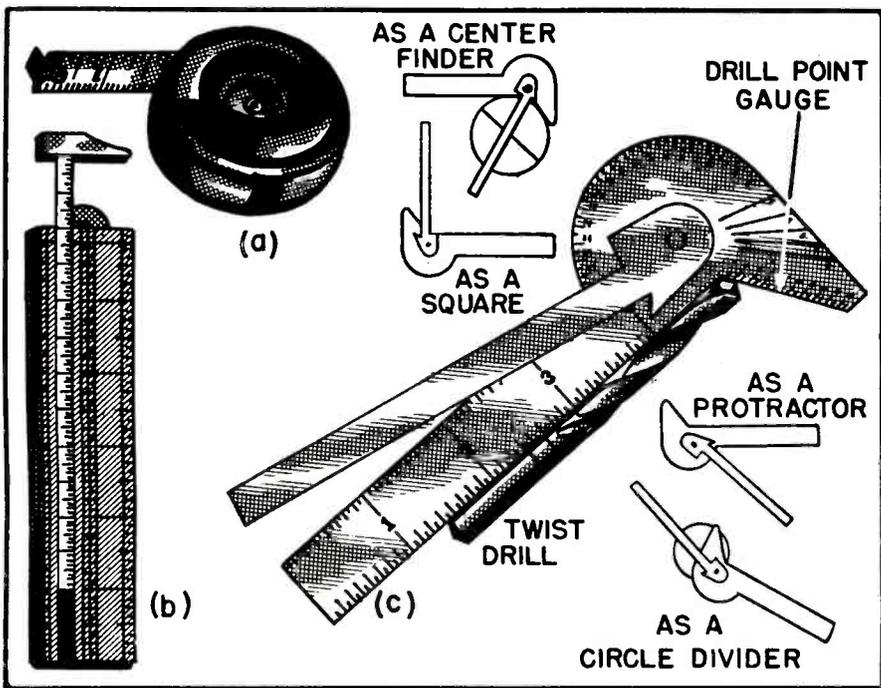

The new **PLANT** *the recognized* **PRODUCTS**




OUR NEW HOME
Addison · Elston and Kedzie Avenues
Chicago, Illinois

the Standard of **PERFORMANCE** *that assures you of Satisfied Customers*

To serve you better in 1947, we add new streamlined plant facilities. Now, more than ever, you can look to Stancor for the complete selection of Replacement and General Purpose Transformers proven in performance to give your customers lasting satisfaction.

Stancor's highest standard of product performance, advanced designs and universal application will continue to make Stancor your favorite . . . will continue to help you build your reputation for dependable, satisfactory service.

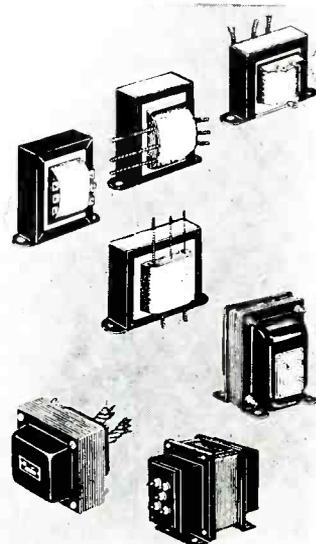Yes, Stancor has the **PLANT** . . . the **PRODUCTS** . . . and the **PERFORMANCE** . . . to help make your service business bigger and more profitable in 1947.



STANCOR

STANDARD TRANSFORMER CORPORATION


1500 NORTH HALSTED STREET · CHICAGO, ILLINOIS

A VERY


Merry Christmas



RUSSELL MAGUIRE
President

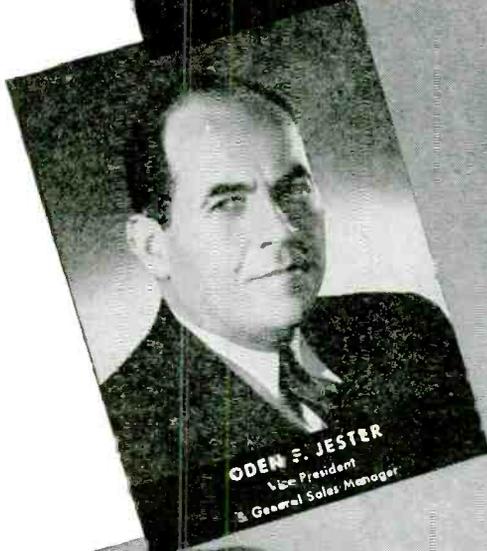

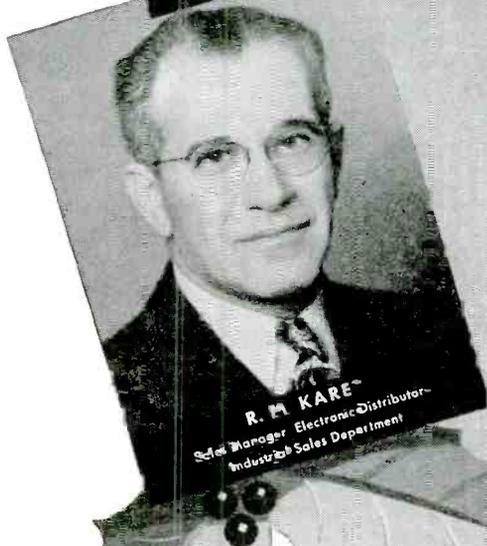ODEN F. JESTER
Vice President
General Sales Manager



R. M. KARE
Sales Manager Electronic Distributor
Industrial Sales Department

We pause at this age-old season of good will to greet our many friends in the radio and electronic industries and to extend to all of them our best wishes for a Merry Christmas and a Happy New Year. A year has passed since the formation of the Electronic Distributor and Industrial Sales Department . . . a year during which we have developed into a smoothly functioning organization, known from coast to coast for the quality of our three great lines, Thordarson, Meissner and Radiart. We are proud of this success and we are grateful to those in the industry who have helped to make it possible.

Now as we stand at the beginning of a new year we are firmly resolved that the products and services of these member companies will continue to reflect the wealth of engineering skill and production know-how which has distinguished them in the past.

Russell Maguire
O. F. Jester
R. M. Kare



ELECTRONIC
DISTRIBUTOR

AND INDUSTRIAL SALES DEPARTMENT

336 N. MICHIGAN AVENUE • CHICAGO II, ILLINOIS

MEISSNER • THORDARSON • RADIART

JANUARY, 1946 — DECEMBER, 1946

ANTENNAS

- Antennas of Television. *By Paul W. Schwehn*.....Feb.
 Antenna Equalizers (Truetone D2615).....Mar.
 Antenna Plates (Truetone D2610-1).....Mar.
 Antenna Series Resistors (Ward 54BR-1505A).....Mar.
 Hanks of Wire for Antennas (Arvin 444).....June
 Loops for S-W (Wells Gardner 37D14-600).....May
 Loop Inputs (Stewart Warner Models).....Jan.
 Installing Television Receiver Antennas. *By R. B. Carwood*.....Mar.
 Reducing Resonant Peaks with Antenna Resistor (Belmont 4B17).....Sept.
 Reducing Resonance with Antenna Resistor-Capacitor Circuit (DeWald).....Oct.
 S-W/B-C Antenna Inputs (RCA56X5).....Feb.
 Three-Position Waveband Switching (RCA 56X5).....Feb.

CAPACITORS

- Capacitor Service Instruments. *By William M. Robinson*.....May
 Capacitors (Types, Uses, Construction). *By Alexander M. Georgiev*.....Apr.

CHARTS

- Charts for Determining Resistors Needed for Filament and Heater Shunt Circuits. *Nov.*
 Quick Reference Charts. *By E. B. Menzies*. *Nov.*
 Charts for Determining Watt Dissipation. *Nov.*

CIRCUIT ANALYSES

- Analyzing Intermittents. *By Willard Moody*. *Jan.*
 AVC Systems in Communications Receivers. *By Frank G. Strong*.....Jan.
 Communications Receivers (Design and Use of R-F Gain Controls, S and R Meters, Band Spreading, Variable Selectivity I-F Stages). *By Thomas T. Donald*.....Feb.
 Communications Receivers as Service Instruments. *By Thomas T. Donald*.....June
 Communications Receivers Today. *By Thomas T. Donald*.....Sept.
 Current Receivers (See Listing under Receivers and Cover Diagrams)
 Fixed Attenuators for Public-Address Systems. *By Willard Moody*.....May
 Oscillator Circuits in Television Receivers. *By R. B. Carwood*.....June
 Ohm's Law (A Simplified Analysis). *By L. A. Mohr*.....Jan.
 Ohm's Law (A Simplified Analysis). *By L. A. Mohr*.....Feb.
 Ohm's Law (Problems and Solutions). *By L. A. Mohr*.....Apr.
 Resistance-Coupled A-F Systems.....Dec.
 Silver Vomag V-T-V-M.....Dec.
 Television/F-M Receiver Features. *By R. B. Carwood*.....July
 Triode-Pentode Circuits.....Dec.
 Tunable Rejector Circuits.....Mar.
 Vario-Tuner (E-L Type).....Dec.
 V-H-F Test Unit (Sylvania Polymer).....Dec.
 Voltage Distribution. *By L. A. Mohr*.....Mar.

CONVERTERS

- A 88 to 108-MC Converter for the New F-M Band. *By Samuel Sabaroff*.....Aug.

COVER DIAGRAMS

- 2-Band 5-Tube Receiver (Pilot B-3).....July
 4-Tube Clock Control Receiver (G.E. 50).....Aug.
 5-Tube Battery-Electric Receiver (Emerson 505).....May
 5-Tube Beam Power Receiver (Ward 64WG-1804A).....Apr.

- 5-Tube A-C/D-C Receiver (Templeton E-510, 519).....Jan.
 5-Tube Rechargeable 2-Volt Portable (G.E. 250/260).....June
 8-Tube Auto Receiver (Motorola 705).....Sept.
 Balanced Loop Receiver (Stewart-Warner 9014-E).....Oct.
 Phono Portable for A-C/D-C/Battery (Capitol Phono U-24).....Dec.
 Postwar Model with Iron Core I-F's (G.E. 100 Series).....Feb.
 Postwar Personal Receiver (RCA 54R 1-2-3).....Mar.
 Two-Band Phono Receiver with Variable Reluctance Pickup (G.E. 326-327).....Nov.

EDITORIALS

- Color in the Service Shop.....Sept.
 Evil of Overcharging.....Oct.
 F-M Receiver Production.....July
 Importance of Installations in F-M and Television.....Apr.
 Instruments Required for F-M Servicing.....July
 Manufacturers' Opinions on Television Servicing.....May
 Miniature Component Design.....Aug.
 New Television Channels.....Feb.
 OPA Price Approvals.....May
 Oscilloscope-Oscillograph Term Debate.....Sept.
 Planning Installations.....Apr.
 Planning for 1947.....Dec.
 Postwar Circuit Advancements.....June
 Radio Parts Show.....May
 School Sound Systems.....Mar.
 Servicing F-M Receivers.....July
 Surveying your Community to Establish a Service Shop.....Jan.
 Television Antennas.....Mar.
 Television Receiver Designs.....Feb.
 Television Receiver Production.....Feb.
 Television Servicing as Viewed by the Manufacturer and Service Man at the TBA Conference.....Oct.
 Television Training in Great Britain.....Aug.
 Television Week.....Sept.

FEATURES

- 1946 Radio Parts and Electronics Equipment Conference and Show.....Apr.
 A 88 to 108-mc Converter for the New F-M Band. *By S. J. Sabaroff*.....Aug.
 A-C Power Transformer and A-C/D-C Grounding Problems.....July
 AVC Systems in Communications Receivers. *By Thomas T. Donald*.....Jan.
 Analyzing Intermittents. *By Willard Moody*. *Jan.*
 Annual Index, SERVICE, 1945.....Jan.
 Annual Index, SERVICE, 1946.....Dec.
 Antennas for Television (Installation Problems and Their Solutions). *By Paul W. Schwehn*.....Feb.
 At the 1946 Radio Parts Show in Chicago.....June
 Communications Receivers (Design and Use of R-F Gain Controls, S and R Meters, Band Spreading and Variable Selectivity in I-F Stages). *By Thomas T. Donald*.....Feb.
 Capacitor Service Instruments. *By William M. Robinson*.....May
 Capacitors (Types, Uses, Construction). *By Alexander M. Georgiev*.....Apr.
 Checking Dead Receivers (Trouble Shooting Filament Circuits in A-C/D-C Models). *By S. Heller*.....June
 Color Dynamics for Your Service Shop. *By Alfred A. Ghirardi*.....Mar.
 Communication-Receiver Single-Channel Remote Control. *By E. B. Menzies*.....May
 Communications Receivers as Service Instruments. *By Thomas T. Donald*.....June
 Communications Receivers as Service Instruments. *By Thomas T. Donald*.....Aug.
 Communications Receivers Today. *By Thomas T. Donald*.....Sept.

- Connecting Speakers and Headphones in Parallel. *By Frank C. Keene*.....June
 Deflection Circuits in Television Receivers. *By Frank G. Strong*.....Jan.
 Determining Ratings and Current-Carrying Capacities of Transformer Windings. *By Frank C. Keene*.....June
 Electromagnetic Deflection Systems in Television Receivers. *By Edward M. Noll*.....Sept.
 Electromagnetic Deflection Systems in Television Receivers. *By Edward M. Noll*.....Oct.
 Eliminating Noise at the Receiver. *By William M. Robinson*.....Sept.
 Fixed Attenuators for Public-Address Systems. *By Willard Moody*.....May
 Fluorescent Lamp Interference Filters. *By Leonard Milton*.....Nov.
 If I Ran a Service Shop. *By Charles Golenpaul*.....Apr.
 Industrial Intercommunications. *By Maurice F. Keir*.....Oct.
 Installing Selenium Disc Rectifiers.....Sept.
 Installing Television Receiver Antennas. *By R. B. Carwood*.....Mar.
 Midget Components for British Portables. *By H. W. Barnard*.....Dec.
 New Models.....Jan.
 New Models.....Feb.
 New Models.....Mar.
 New Models.....Apr.
 New Models.....June
 New Models.....July
 New Models.....Aug.
 New Models.....Sept.
 New Models.....Oct.
 Ohm's Law. *By L. A. Mohr*.....Jan.
 Ohm's Law Problems and Solutions. *By L. A. Mohr*.....Apr.
 Old Timer's Corner.....Jan.
 Old Timer's Corner.....Feb.
 Old Timer's Corner.....Mar.
 Old Timer's Corner.....May
 Old Timer's Corner.....June
 Old Timer's Corner.....Aug.
 Old Timer's Corner.....Sept.
 Old Timer's Corner.....Oct.
 Oscillator Circuits in Television Receivers. *By R. B. Carwood*.....June
 Portable Oscillographs with 2" C-R Tubes. *By M. W. Beacay*.....Oct.
 Postwar Receiver Dial Drives. *By John T. Martin*.....Mar.
 Postwar V-T-V-M. *By M. E. Lewis*.....Dec.
 Quick-Reference Charts. *By E. B. Menzies*. *Nov.*
 Replacing 35Z5 with a 100-ma Selenium Rectifier.....Nov.
 Sales Helps and the Service Man. *By Kenneth C. Burcaw*.....Oct.
 Ser-Cuits. *By Henry Howard*.....Jan.
 Ser-Cuits. *By Henry Howard*.....Feb.
 Ser-Cuits. *By Henry Howard*.....Mar.
 Ser-Cuits. *By Henry Howard*.....Apr.
 Ser-Cuits. *By Henry Howard*.....May
 Ser-Cuits. *By Henry Howard*.....June
 Ser-Cuits. *By Henry Howard*.....July
 Ser-Cuits. *By Henry Howard*.....Aug.
 Ser-Cuits. *By Henry Howard*.....Sept.
 Ser-Cuits. *By Henry Howard*.....Oct.
 Ser-Cuits. *By Henry Howard*.....Nov.
 Ser-Cuits. *By Henry Howard*.....Dec.
 Service Aids.....Jan.
 Servicing Helps.....Jan.
 Servicing Helps. *By Frank C. Keene*.....Feb.
 Servicing Helps.....Mar.
 Servicing Helps. *By Frank C. Keene*.....Apr.
 Servicing Helps. *By Frank C. Keene*.....June
 Servicing Helps. *By Frank C. Keene*.....July
 Servicing Helps. *By Frank C. Keene*.....Aug.
 Servicing Helps. *By Frank C. Keene*.....Sept.
 Servicing Helps. *By Frank C. Keene*.....Oct.
 Servicing Helps. *By Frank C. Keene*.....Dec.
 Simplified Analysis of Ohm's Law (Part II). *By L. A. Mohr*.....Feb.

For Efficient Radio Electronic Arteries...

Choose Amphenol Components!

Amphenol is known, and relied upon, by amateurs and professionals in every branch of radio and electronics. The encyclopedic array of more than 8,000 different Amphenol components completely serves the entire range of frequencies in use today.

Amphenol engineers steadily are helping to pierce the veil of the unknown in the higher television and FM frequencies. They have been among the pace-setters in achieving the higher standards of mechanical efficiency and electrical correctness upon which progress in these fields depends.

Teamed with top-flight production facilities, Amphenol research has continuously developed new products to keep the Amphenol line of cables, plugs, connectors, fittings, sockets, antennas and plastic components the most complete available from any one source in the world today.

Wherever you find electrons at work, you'll find Amphenol components recognized as the standard of performance.

AMERICAN PHENOLIC CORPORATION, CHICAGO 50, ILLINOIS

In Canada - Amphenol Limited - Toronto

AMPHENOL

COAXIAL CABLES AND CONNECTORS - INDUSTRIAL CONNECTORS, FITTINGS AND CONDUIT - ANTENNAS - RF COMPONENTS - PLASTICS FOR ELECTRONICS

JANUARY, 1946 – DECEMBER, 1946

Television and the Service Man. *By R. B. Carwood*Jan.

Television/F-M Receiver Features. *By R. B. Carwood*July

Television Receiver R-F and Mixer Stages. *By R. B. Carwood*May

Television Servicing as Viewed by the Manufacturer, Engineer, Service Man and Instructor at the TBA Conference in New York City (Highlights of Talks Presented Before TBA Television Receiver Panel by John F. Rider, Ernest A. Marx, Madison Cawein, George Duvall, W. L. Jones, W. L. Parkinson, Richard A. Burtner, W. J. Jones and Albert Preisman)Nov.

R-C Amplifier Design Factors. *By Martin B. Rogers*Dec.

The Television Signal (An Analysis of Its Composition). *By R. B. Carwood*Feb.

Testing with the C-R Oscillograph. *By S. J. Murcek*Mar.

Testing with the C-R Oscillograph. *By S. J. Murcek*Apr.

Tools and Accessories for the New Service Shop. *By Alfred A. Ghirardi*Apr.

Tools and Accessories for the New Service Shop. *By Alfred A. Ghirardi*May

Tools and Accessories for the New Service Shop. *By Alfred A. Ghirardi*June

Tools and Accessories for the New Service Shop. *By Alfred A. Ghirardi*Aug.

Tools and Accessories for the New Service Shop. *By Alfred A. Ghirardi*Sept.

Tools and Accessories for the New Service Shop. *By Alfred A. Ghirardi*Oct.

Tools and Accessories for the New Service Shop. *By Alfred A. Ghirardi*Dec.

Trends in Sound: Highlights of New EquipmentJuly

Trends in Sound: Loudspeakers. *By S. J. Arthur*July

Trends in Sound: Loudspeakers. *By S. J. Arthur*Aug.

Trends in Sound: Microphones. *By Richard L. Stewart*July

Trends in Sound: P-A Amplifiers. *By Kelvin R. Martin*July

Trends in Sound: Phono Pickups. *By B. K. Martinson*Aug.

Tunable Rejector CircuitsMar.

Two-Band Phono Receiver with Variable Reluctance Pickup (G.E. 326-327)Nov.

Use of TrimmersJuly

Voltage Distribution (Part II). *By L. A. Mohr*Mar.

Volume and Tone Control Resistors (Repairing, Reconditioning and Circuit Substitutions. Part XI). *By Alfred A. Ghirardi*Jan.

Volume and Tone Control Resistors (Repairing, Reconditioning and Circuit Substitutions. Part XII). *By Alfred A. Ghirardi*Feb.

Volume and Tone ControlsMar.

FREQUENCY MODULATION

A 88 to 108-MC Converter for the New F-M Band. *By Samuel Sabaroff*Aug.

Television/F-M Receiver Features. *By R. B. Carwood*July

INTERCOMMUNICATIONS

Industrial Intercommunications. *By Maurice F. Kerr*Nov.

LIMITERS, DISCRIMINATORS, AVC, AFC AND DETECTORS

AVC Biasing (Wells Gardner 37014-600)May

AVC Biasing from 12SA7 Converter (Electromatic 512)May

AVC Biasing in Miniature Tube Receivers (Garod 5D)Sept.

AVC Detector Loading Circuit (Crosley 56FA)Oct.

AVC Systems in Communications Receivers. *By Thomas T. Donald*Jan.

Hallicrafters SX-28 (AVC)Jan.

Hammarlund SP-200X (AVC)Jan.

National NC-200 (AVC)Jan.

MINIATURE TUBES

Garod 5DSept.

Motorola 5A1Sept.

Pentode Miniatures in Phono Portable (Capitol U-24)Dec.

NOISE

Analyzing Intermittents. *By Willard Moody*Jan.

Eliminating Noise at the Receiver. *By William M. Robinson*Sept.

Eliminating Vibrator HashFeb.

Interference Filters, Fluorescent LampsNov.

Occasional Crackling Noise Elimination (Philco 29)Mar.

Rushing Noise Elimination (G.E. JFM90)Mar.

OSCILLATORS

DuMont 180X (Tel. Osc. Circuit)June

G.E. HM225 (Tel. Osc. Circuit)June

Oscillator Circuits in Television Receivers. *By R. B. Carwood*June

RCA TRK-90 (Tel. Osc. Circuit)June

Television Receiver R-F and Mixer Stages. *By R. B. Carwood*May

PARTS

Capacitors *By Alexander M. Georgiev*Apr.

Fixed Attenuators for Public Address Systems. *By Willard Moody*May

Midget Components for British Portables. *By H. W. Barnard*Dec.

Volume and Tone Control Resistors (Repairing, Reconditioning and Circuit Substitutions). *By Alfred A. Ghirardi*Jan.

Volume and Tone Control Resistors (Repairing, Reconditioning and Circuit Substitutions). *By Alfred A. Ghirardi*Feb.

PERMEABILITY TUNING

Admiral 4A1Oct.

Belmont 4B17Sept.

Emerson 508June

Motorola 5A1Sept.

Radiola 61-1, 2 and 3Aug.

RCA 55U/55AUAug.

Truetone D2610-1Mar.

Truetone D2615Mar.

Vario-Tuner (E-L Type)Dec.

PHONOGRAPHS, PICKUPS, RECORD PLAYERS, ETC.

Electromatic 512 (4-tube rectifier phono)May

Phono Portable for A-C/D-C/Battery (Capitol U-24)Dec.

RCA 55U, 55AUAug.

Trends in Sound: Phono Pickups. *By B. K. Martinson*Aug.

Ward 54WG-2007AMay

Ward 54WG-2700AMay

Westinghouse M-130, H-122 (Phono Model)May

Wind-up-A-C Motor in Phono Portable (Capitol U-24)Dec.

PORTABLES

Admiral 4A1 (4-tube)Oct.

Airline 64BR-1051ASept.

Emerson 508June

Garod 5D (4-tube a-c/d-c/battery)Sept.

G. E. 250June

Midget Components for British Portables. *By H. W. Barnard*Dec.

Motorola 5A1 (4-tube)Sept.

Motorola 4B12 (4-tube)Sept.

RCA 56X, 56X2, 56X3 (5-tube a-c/d-c)Feb.

POWER SUPPLIES

Battery Economizer Circuits (Motorola Series)Sept.

ECA AE (With B Power Conservation Circuit)July

Hum Neutralizing (RCA 56X Series)Feb.

Line-Powered Farm Receiver SupplyAug.

Miniature Tube Power Supply (Used in Garod 5D and Motorola 5A1 Models)Sept.

Motorola 4B12 (4-tube Model with Battery Economizer)Sept.

RECEIVERS

A 88 to 108-MC Converter for the New F-M Band. *By Samuel Sabaroff*Aug.

Andrea 1F5 (Electrostatic Deflection Circuit)Jan.

Admiral 6A1 (3-Gang Tuner Model)Apr.

Admiral 4A1 (4-Tube Portable)Oct.

Admiral 5B1 (4-Tube) A-C/DC 150-Mil Model)Apr.

Airline 64BR-1051A (A-C/D-C/ Battery Portable)Sept.

Arvin 444, 444A (3-Tube)June

Belmont 4B17 (4-Tube Battery)Sept.

Circuits in Television Receivers, Oscillator. *By R. B. Carwood*June

Communications-Receiver Single-Channel Remote Control. *By E. B. Menzies*May

Communications Receivers as Service Instruments. *By Thomas T. Donald*June

Communications Receivers as Service Instruments. *By Thomas T. Donald*Aug.

Crosley 56FA, 56FB (5-Tube, 2-Band Farm Type)Oct.

DeWald A500, A503 (4-Tube)Oct.

DuMont 14" Television Model (Deflection Circuit)Jan.

DuMont 180X (Television Oscillator)June

ECA 101 (4-Tube A-C/D-C)Nov.

ECA AE 250 (5-Tube 250-Mil A-C/D-C Model)July

Electromatic 512 (4-Tube Phono)May

Eliminating Noise at the Receiver. *By William M. Robinson*Sept.

Emerson 502 (4-Tube A-C/D-C)June

Emerson 505 (5-tube A-C/D-C/Battery)May

Emerson 508 (Battery Pocket Receiver)June

Fada P22, P28A (Detector and First A-F Circuit)Feb.

Garod 5D (A-C/D-C/Battery, 5-Tube with Miniatures)Sept.

G. E. HM 225B/226B (Magnetic Deflection Circuit)Jan.

G.E. 100 Series (Postwar Models with Iron Core I-F's)Feb.

GE 225B (Television Oscillator Circuit)June

GE 250/260 (5-tube Rechargeable 2-volt Portable)June

G.E. 50 (4-Tube Clock-Control Receiver)Aug.

G.E. 326-327 (Two-Band Phono with Variable Reluctance Pickup)Nov.

Globe Electronic 6U (5-Tube with Lock-In-Tubes)May

Hallicrafters SX-28 (AVC Circuit)Jan.

Hallicrafters SX18 (Gain-Control Circuit)Feb.

Hallicrafters SX18 (Image Rejector Circuit)Mar.

Hallicrafters SX 18 (Image Rejector Circuit)Mar.

Hallicrafters S-40 (9-Tube, 4-Band)Sept.

Hammarlund SP200-X (AVC Circuit)Jan.

Motorola 45B12 (4-Tube Portable)Sept.

Motorola 5A1 (4-Tube Portable with Miniature Tubes)Sept.

Motorola 705 (8-Tube Auto Receiver)Sept.

National NHU (S Meter Circuit)Feb.

National NHU (R-F Gain Control)Feb.

Packard Bell 5FP (4-Tube A-C)Nov.

Pilot B-3 (Two-Band 5-Tube Receiver)July

Radiola 61-1, 2 and 3 (5-Tube)Aug.

RCA 54B 1-2-3 (Postwar Personal Receiver)Mar.

NOW AVAILABLE FOR IMMEDIATE SHIPMENT!

Please place your order with your regular radio parts jobber. If your local jobber cannot supply you, kindly write for a list of jobbers in your state who do distribute our instruments or send your order directly to us.



The New Model CA-11 SIGNAL TRACER

Simple to operate . . . because signal intensity readings are indicated directly on the meter!

Essentially "Signal Tracing" means following the signal in a radio receiver and using the signal itself as a basis of measurement and as a means of locating the cause of trouble. In the CA-11 the Detector Probe is used to follow the signal from the antenna to the speaker — with relative signal intensity readings available on the scale of the meter which is calibrated to permit constant comparison of signal intensity as the probe is moved to follow the signal through the various stages.

Features:

- ★ SIMPLE TO OPERATE — only 1 connecting cable — NO TUNING CONTROLS.
- ★ HIGHLY SENSITIVE — uses an improved Vacuum Tube Voltmeter circuit.
- ★ Tube and resistor-capacity network are built into the Detector Probe.
- ★ COMPLETELY PORTABLE — weighs 5 lbs. and measures 5" x 6" x 7".
- ★ Comparative Signal Intensity readings are indicated directly on the meter as the Detector Probe is moved to follow the Signal from Antenna to Speaker.
- ★ Provision is made for insertion of phones.

The Model CA-11 comes housed in a beautiful hand-rubbed wooden cabinet. Complete with Probe, test leads and instructions.....Net price

\$18⁷⁵

The New Model 450 TUBE TESTER

Specifications:




- Tests all tubes up to 117 Volts including 4, 5, 6, 7, 7L, Octals, Loctals, Bantam Junior, Peanut, Television, Magic Eye, Hearing Aid, Thyratrons, Single Ended, Floating Filament, Mercury Vapor Rectifiers, etc. Also Pilot Lights.
- Tests by the well-established emission method for tube quality, directly read on the scale of the meter.
- Tests shorts and leakages up to 3 Megohms in all tubes.
- Tests individual sections such as diodes, triodes, pentodes, etc., in multi-purpose tubes.
- New type line voltage adjuster.
- NOISE TEST: Tip jacks on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.
- Works on 90 to 125 Volts 60 Cycles A.C.

SPEEDY OPERATION assured by newly designed rotary selector switch which replaces the usual snap, toggle, or lever action switches.

The model 450 comes complete with all operating instructions. Size 13"x12"x6". Net weight 8 lbs. **\$39⁵⁰** Our Net Price.....

The New Model 670P SUPER-METER

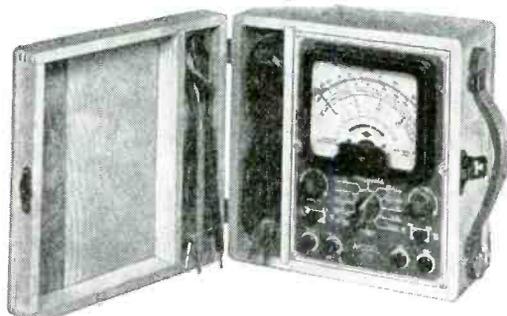A Combination Volt-Ohm Milliammeter plus Capacity Reactance Inductance and Decibel Measurements



Specifications:

D.C. Volts: 0 to 7.5/15/75/150/750/-1,500/7,500 Volts.
A.C. Volts: 0 to 15/30/150/300/1,500/-3,000 Volts.
Output Volts: 0 to 15/30/150/300/1,500/-3,000 Volts.
D.C. Current: 0 to 1.5/15/150 Ma. 0 to 1.5 Amperes.
Reactance: 0 to 500/100,000 ohms. 0 to 10 Megohms.
Capacity: .001 to .2 Mfd. .1 to 4 Mfd. (Quality test for electrolytics).
Reactance: 700 to 27,000 Ohms. 13,000 Ohms to 3 Megohms.
Inductance: 1.75 to 70 Henries. 35 to 8,000 Henries.
Decibels: -10 to +18. +10 to +38. +30 to +58.

Added Feature:

The Model 670P includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 volts.

The Model 670P is housed in a hand-rubbed, portable oak cabinet complete with cover, test leads and all operating instructions.

\$35⁷⁵

NET

SUPERIOR INSTRUMENTS CO.

DEPT. B - 227 FULTON STREET, NEW YORK 7, N. Y.

JANUARY, 1946 - DECEMBER, 1946

RCA TRK5 (Electrostatic Deflection Circuit)Jan.
 RCA TRK 90 (Television Oscillator Circuit)June
 RCA 55F (Battery Farm Receiver).....Aug.
 RCA 55U-55AU (4-Tube Phono Model).....Aug.
 RCA 56X, 56X2, 56X3 (5-Tube A-C/D-C).....Feb.
 RCA 56X5 (Two-Band)Feb.
 RCA 56X11 (Two-Band)Feb.
 RME 41-43 (Gain Meter Circuit)Feb.
 Stewart-Warner 9002-A, B, P and R (5-Tube A-C/D-C)Jan.
 Stewart-Warner 9014-E (Balanced Loop Receiver)Oct.
 Templeton E-510 (5-Tube Postwar A-C/D-C)Jan.
 Truetone D2610-1 (A-C/D-C, 4-Tube).....Mar.
 Truetone D2615 (A-C/D-C 5-Tube).....Mar.
 Ultradyne L-46 (5-Tube A-C/D-C with Lock-In Tubes)May
 Ward 54BR-1503A (4-Tube A-C/D-C).....Mar.
 Ward 54BR-1505A (A-C/D-C 4-Tube).....Mar.
 Ward 54WG-2007A (4-Tube A-C/D-C).....May
 Ward 54WG-2700A (2-Band 6-Tube A-C Phono)May
 Ward 64WG-1804A (5-Tube Beam-Power Receiver)Apr.
 Wells-Gardner 37D14-600 (2-Band A-C/D-C)May
 Westinghouse H130/H122 (AC/DC 5-Tube with 300-Mil Tubes)May
 Zenith 4KO16-4KO35 (4-Tube Battery).....Oct.
 Zenith 6G001 (3-Gang, 5-Tube Battery, A-C/D-C)Oct.

SERVICING HELPS

A-C Power Transformer and A-C/D-C Grounding ProblemsJuly
 A-C/D-C Sensitivity Improvements.....Dec.
 Battery-Saving Circuits (Motorola 45B12).....Sept.
 Checking Dead ReceiversJune
 Color Dynamics for Your Service Shop. By *Alfred A. Ghirardi*.....Mar.
 Connecting Speakers and Headphones in ParallelJune
 Converting 110 v to 6 v for Auto-Set TestingSept.
 Dead or Intermittent, Not Due to Tube (RCA 5T)Jan.
 Determining Ratings and Current-Carrying Capacities of Transformer Windings.....June
 Dial Drive with Idler Pulleys (RCA 56X11)Mar.
 Dial Drive with Series Spring (Truetone D2610)Mar.
 Distortion on Strong Signals (Zenith 8S586)Mar.
 Drum and Three-Idler Drive System (Ward 54BR-1503A)Mar.
 Drum Drives (G.E. 100 Series)Mar.
 Eliminating Hum in P-M Speaker Models (Packard-Bell 5FP)Nov.
 Eliminating Hum in E-M Speaker Models.....Nov.
 Feedback Circuit (ECA 101)Nov.
 Flexible Light Control for Repair Work.....Oct.
 Helical Spring Drive (Belmont 6D111).....Mar.
 How to Check Power Supplies; Locate Distortion in Battery Portables; Eliminating Vibrator Hash; Avoid Tube Burnouts; Use Resistors and Capacitors Properly in A-C/D-C Ground Circuits. By *Frank C. Keene*Feb.
 Howl (Philco C 1908)Mar.
 Hum-Reducing System (Emerson 502).....June
 If I Ran a Service Shop. By *Charles Golenspaal*Apr.
 Installing Selenium Disc RectifiersSept.
 Intermittent Fluttering Reception (Philco 1808)Mar.
 Loop in Cover of Tester as Antenna.....Oct.
 Loss of Volume (Pilot T-71).....Mar.
 Motorboating (Philco 70)Mar.
 Multiple Headphone Circuits.....Oct.
 Occasional Crackling Noise (Philco 29).....Mar.

OscillatorsOct.
 Periodic Oscillation, Low-End of Dial (Motorola 250)Mar.
 No Reception (Stromberg-Carlson 486).....Mar.
 Postwar Receiver Dial Drives. By *John T. Martin*Mar.
 Postwar V-T-V-M (Silver Vomax).....Dec.
 Record Amplifier Using 117N7 Instead of a 70L7. By *Frank C. Keene*.....Apr.
 Removing Meter Face Static Charges.....Oct.
 Replacing a 37 with a 76Aug.
 Replacing 35Z5 with a 100-ma Selenium RectifierNov.
 R-F Oscillation RemediesDec.
 Rushing Noise (G.E. JFM 90)Mar.
 Set Inoperative, 5T4 Rectifier and Power Transformer Get Very Hot (RCA 813K)Mar.
 6-Speaker Phono LinkDec.
 Tunable Receptor CircuitsMar.
 Use of TrimmersJuly
 Wells-Gardner 37D14-600 Dial System.....Mar.
 Ward 54BR-1501A Dial DriveMar.
 Ward 54BR-1505A Drum DriveMar.
 Ward 54WG-1801A Dial Drive System.....Mar.
 Ward 64WG-1804A Dial Drive with Dial-Light DiffuserMar.
 Ward 54WG-2500A Dial Drive System.....Mar.

SPEAKERS

Loudspeakers. Trends in Sound. By *S. J. Arthur*July
 Loudspeakers. Trends in Sound. (Part II). By *S. J. Arthur*Aug.

SOUND

4-Tube Phono Model (Electromatic 512).....May
 Automatic Record Changer Model (RCA 55U/55AU)Aug.
 Diode-Super-Control Pentode Amplifier (Stewart Warner Models)Jan.
 Fixed Attenuators for Public-Address Systems. By *Willard Moody*May
 Miniature Tube Power Amplifier Circuit (Motorola 5A1)Sept.
 Multiple Headphone CircuitsOct.
 Phono Portable for A-C/D-C/Battery (Capitol Phono U-24)Dec.
 Preamplifier for Variable Reluctance Pickup (G.E. 326-327)Nov.
 6-Speaker Phono SystemDec.
 The R-C Amplifier. By *Martin B. Rogers*Dec.
 Trends in Sound: Loudspeakers. By *S. J. Arthur*July
 Trends in Sound: Loudspeakers. (Part II). By *S. J. Arthur*Aug.
 Trends in Sound: Microphones. By *Richard L. Stewart*July
 Trends in Sound: P-A Amplifiers. By *Kelvin R. Martin*July
 Trends in Sound: Phono Pickups. By *B. K. Martinson*Aug.
 Push-Pull Phono Model (Westinghouse H130/122)May
 Variable Reluctance Pickup (G.E. 326-327)Nov.

TELEVISION

Antennas for Television (Installation Problems and Their Solutions). By *Paul W. Schuehn*Feb.
 Deflection Circuits (DuMont, G.E. and RCA Models)Mar.
 Deflection Circuits in Television Receivers. By *Frank G. Strong*Jan.
 Electromagnetic Deflection Systems in Television Receivers. By *Edward M. Noll*Sept.
 Electrostatic Deflection Circuit (Andrea IF5)Jan.
 Electrostatic Deflection Circuit (DuMont 180X)Jan.
 Electrostatic Deflection Circuit (RCA TRK15)Jan.

Intra-Store TelevisionFeb.
 Oscillator Circuit (RCA TRK90).....June
 Oscillator Circuits in Television Receivers. By *R. B. Carwood*June
 Oscillator and Mixer Circuit (G. E. HM 225B)June
 Oscillator and Mixer Circuit (DuMont 180X)June
 Magnetic Deflection System (G.E. HM 225B).....Jan.
 Multiple Television Antenna Systems.....Nov.
 Problem of Television Servicing.....Nov.
 Remote Control Television Antennas.....Nov.
 Service Man's Approach to Television ServicingNov.
 Television and the Service Man. By *R. B. Carwood*Jan.
 Television/FM Receiver Features. By *R. B. Carwood*July
 Television Receiver Antennas, Installing. By *R. B. Carwood*Mar.
 Television Receiver R-F and Mixer Stages. By *R. B. Carwood*May
 Television Servicing Plan of G.E.Nov.
 Television Servicing Program of RCA.....Nov.
 Television Servicing Program of DuMont.....Nov.
 Television TrainingNov.
 The Service Man and Television.....Nov.
 The Television Signal (An Analysis of Its Composition). By *R. B. Carwood*Feb.

TEST EQUIPMENT

Capacitor Service Instruments. By *William M. Robinson*May
 C-R Oscillograph, Testing with The. By *S. J. Murcek*Mar.
 Communications Receivers as Service Instruments. By *Thomas T. Donald*June
 Communication Receivers as Service Instruments. By *Thomas T. Donald*Aug.
 Instruments Required for F-M Servicing.....July
 Postwar V-T-V-M. By *M. E. Lewis*Dec.
 Portable Oscillographs with 2" C-R Tubes. By *M. W. Bracey*Oct.
 Sylvania PolymeterDec.
 Testing with the C-R Oscillograph. By *S. J. Murcek*Mar.
 Testing with the C-R Oscillograph. By *S. J. Murcek*Apr.
 V-T Proximity-Tube Type Probe (Sylvania Polymeter)Dec.

TONE COMPENSATION

A-F Tone Control System (Wells Gardner 37D 14-600)May
 Shunt Tone Control (Electromatic 512).....May
 Tone Switching Circuit (RCA 55U).....Aug.

TOOLS

Tools and Accessories for the New Service Shop. By *Alfred A. Ghirardi*Apr.
 Tools and Accessories for the New Service Shop. By *Alfred A. Ghirardi*May
 Tools and Accessories for the New Service Shop. By *Alfred A. Ghirardi*June
 Tools and Accessories for the New Service Shop. By *Alfred A. Ghirardi*Aug.
 Tools and Accessories for the New Service Shop. By *Alfred A. Ghirardi*Sept.
 Tools and Accessories for the New Service Shop. By *Alfred A. Ghirardi*Oct.
 Tools and Accessories for the New Service Shop. By *Alfred A. Ghirardi*Dec.

VOLUME CONTROLS

Degeneration and V-C Circuit (ECA AE).....July
 Detector Load Resistance Circuit (Admiral 6A1)April
 Volume and Tone Control Resistors (Repairing, Reconditioning and Circuit Substitutions) Part XI. By *Alfred A. Ghirardi*.....Jan.
 Volume and Tone Control Resistors (Repairing, Reconditioning and Circuit Substitutions) Part XII. By *Alfred A. Ghirardi*.....Feb.
 Volume and Tone ControlsMar.

POSTWAR V-T-V-M

(Continued from page 11)

by Set *V*. Zero knob with *Function* knob set to *D.C.+* and *Range* knob set to 3 *V*, *Function* knob is shifted to *a-c* position. Meter zero will not change more than 1% to 2%. If zero does shift an old, unsheathed, or poorly grounded *a-c* power line will usually be the cause. The remedy is simple. If reversing the *a-c* plug in the *a-c* power outlet does not make *a-c* meter zero coincident with *D.C.+* zero, a lead from a good ground should be clipped onto one of the four panel screws of the instrument.

The unit also permits the measurement of the actual magnitude of *a-c* voltage radiated by the local power line, electrical appliances and all similar sources of such undesired radiation. For this measurement the red test lead tip is inserted in the *+V-Ω-MA* jack, allowing it to act as an antenna. The meter reading may be anything from a fraction of one volt up to 30 volts or more. This is actually *a-c* energy being picked up by the unterminated red test lead acting as an antenna. This can be proved by handling this lead, moving it about, touching its metal tip, and noting the increase in voltage registered, which our body adds, when a finger touches the red prod tip. The long time-constant of the diode input circuit can also be checked during these tests by touching the red prod tip to a panel thumb-screw. Meter reading will take several seconds to fall to zero, due to desirably slow leaking off of charge built up on .03-mfd capacitor by local *a-c* fields discharging through a 20-megohm resistor and 37.5 megohm through 125,000-ohm resistors in series.

If the black test lead tip is inserted into the *Com. Gnd.* jack and both red and black prod tips are contacted to a source of *a-c* voltage, the false but quite real voltage registered by the meter due to the antenna effect of the lead when unterminated and exposed to locally radiated *a-c* fields will disappear, and the correct voltage of the source being measured will be indicated.

By providing an unshielded red test lead input capacity of the instrument has been kept low and the instrument can be used to measure *a-c* voltages beyond 100 kc. Where the user is more concerned with *a-c* voltage measurements at *a-c* power-line frequency, the antenna effect of the intentionally unshielded red test lead may be eliminated by using a shielded test lead consisting of an ordinary test prod terminating the inner conductor of a length of one-wire shielded microphone cable. The far end of this test lead would plug into the *+V-Ω-MA* jack, the shield braid of which would terminate at meter end either at the *Com. Gnd.* jack or through a spring clip to a panel thumb-nut.

The R-F Probe

To study operation of the probe, it should be withdrawn from its shell from the panel receptacle. No change in meter zero will be observed. If a finger is now applied to the live tip of the *r-f* probe, the meter will register locally present *a-c* voltage fields, since the body is now acting as an antenna to pick them up. Touching the probe tip to a panel thumb-

(Continued on page 26)



MAKES 90 OUT OF 100 RADIO TROUBLES Easy to Repair!

Complete, Easy Instructions for Repairing Common Troubles in Practically Every Model and Make of Radio in Use Today

Eliminates Needless Testing — Enables You to Repair Two Radios in the Time Ordinarily Required for One

PAYS FOR ITSELF ON THE FIRST JOB!

TELLS WHAT TO DO • EXACTLY HOW TO DO IT
As valuable to a radio repair man as a recipe book is to a cook!
\$5

What's wrong with the radio you want to repair? A defective transformer? Wiring insulation trouble? A faulty capacitor or resistor? Don't guess! Don't waste time in needless, tedious testing! Just look up that particular make and model in Ghirardi's famous **RADIO TROUBLESHOOTER'S HANDBOOK**. Nine times out of ten, this big book will tell you exactly what is wrong—and exactly how to repair it. You don't have to be an expert to use the **HANDBOOK**—and there's no better way of getting invaluable, practical service training. Over 400 pages are chock-full of this factual Case History repair data on over 4,800 receivers, auto radios and record changers of 202 different manufacturers—practically every radio set in use today! Over 300 additional pages contain hundreds of repair charts, tube charts, data on tuning alignment, transformer troubles, tube and parts substitution data, color codes—all designed to help you repair any radio ever made **EASIER, BETTER and FASTER**. Ideal for either busy service shops or for beginners. Only \$5 complete — on our 5-Day Money-back Guarantee basis.

Ghirardi's **RADIO TROUBLESHOOTER'S HANDBOOK** (above) is the ideal book to have on hand for training new helpers, repairing either cheap or expensive sets quickly and profitably, eliminating needless test time and equipment—and **MAKING MORE MONEY**.



ALL THE SCIENCE OF RADIO-ELECTRONIC SERVICING IN ONE GIANT BOOK

MAKES COMPLICATED JOBS EASY TO DO!

Alfred A. Ghirardi's **MODERN RADIO SERVICING** gives you a **COMPLETE, MODERN EDUCATION** in truly professional radio-electronic service methods of the kind that will be your "Open, sesame!" to the big-money opportunities that only well-trained servicemen are in a position to grasp. It is a complete, scientific servicing course from A to Z. You'll be surprised how easily understandable it makes every phase of the work even if you have had no previous service training. And, if you are already in the business, you'll be pleased to learn how this big 1300-page book will serve as a "refresher" course. Not only will it help you handle repair jobs quicker, better and more profitably, but it also will give you the necessary basic training to equip you for profitable industrial electronic work. Specifically written and designed for home study. 1300 pages; 706 clear illustrations. 720 Self-Test Review Questions make it easy for you to check your progress every step of the way. Fully indexed. Only \$5 on our famous 5-Day Money-back Guarantee.

ENDORSED BY EXPERTS EVERYWHERE

From beginning to end, **MODERN RADIO SERVICING** brings you the kind of modern professional "Know How" that will pay big dividends for years to come. Gives complete data on test instruments and their use, preliminary trouble checks, scientific circuit analysis and trouble-shooting, parts repair and substitution, how to start and operate a successful service business and many other subjects.

MONEY-BACK GUARANTEE

MURRAY HILL BOOKS, Inc., Dept. S-126, 232 Madison Ave., New York 16, N. Y.

- Enclosed find \$..... for books checked; or send C.O.D. (U.S.A. only) for this amount plus postage. I may return the books for refund within 5 days if not fully satisfied.
- RADIO TROUBLESHOOTER'S HANDBOOK \$5** (\$5.50 foreign)
- MODERN RADIO SERVICING \$5** (\$5.50 foreign)
- MONEY-SAVING COMBINATION OFFER:** Both of the above big books, only \$9.50 (\$10.50 foreign)

Name

Address

City & Dist. No. State

SPECIAL OFFER!

Let **RADIO TROUBLESHOOTER'S HANDBOOK** save you time on common radio service jobs! Let **MODERN RADIO SERVICING** train you for complete professional, electronic work. Get **BOTH BIG BOOKS** at the special price of only \$9.50 for the two. Send coupon today!

POSTWAR V-T-V-M

(Continued from page 25)

nut will cause the meter reading to fall to zero, since the meter input is short-circuited, and cannot pick up voltage radiated from the power line, etc.

We can now check a-c meter accuracy together with r-f probe operation. The *Range* knob is set to 120 volts, *Function* knob to A.C., and the probe is inserted in its panel receptacle. Red and black test prods are connected to the a-c line. Meter should read the voltage of same accurately to within $\pm 5\%$. Now the r-f probe should be withdrawn and its tip contacted to one side of the a-c line, the shell (or tip of the black prod) being connected to the other side of the line. The meter will read only about 80-odd volts. This is quite proper. When we measure voltages using the r-f probe directly, we have substituted a .0005-mfd capacitor for .03-mfd capacitor in the diode rectifier input circuit. The .0005-mfd unit is suitable for a-c voltage measurement in the 15,000 cycle up to over 100 megacycles range. Its reactance is too high for accurate low-frequency measurement. That's why the instrument automatically replaces the .0005 with a .03 when the r-f probe is plugged into panel, to make low-frequency (down to 20 cycles) measurements possible through the panel jacks which include the .03-mfd capacitor in their circuit.

[To be continued]

WIRE RECORDER PREVIEW



Webster-Chicago wire-recorder preview test at plant at 5610 Bloomingdale Avenue, Chicago.


TRAILER P-A



A p-a system recently installed in a trailer by Broadcast Recorders, Inc., 1538 N. Cahuenga Blvd., Hollywood, Calif. Unit included a 5-channel mixer, recording amplifiers and two recorders.

ACKNOWLEDGMENT

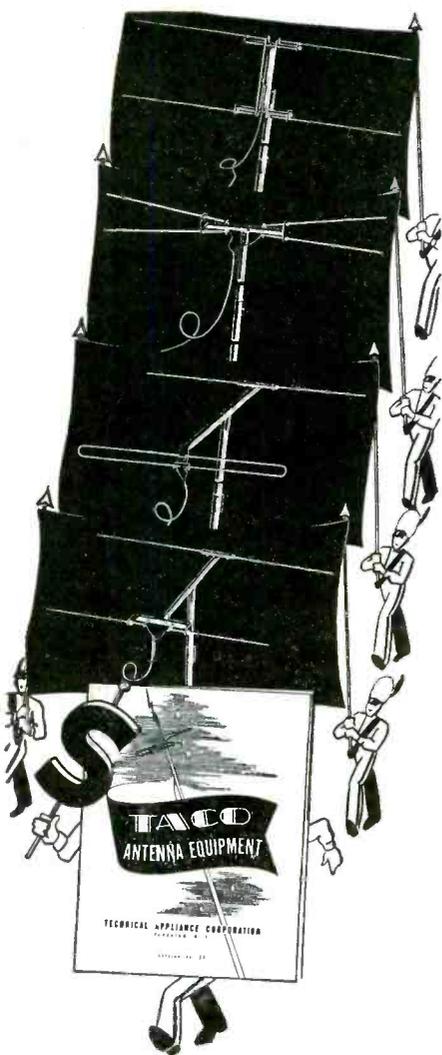The November issue carried schematic diagrams on Learadio models 561-562-563 and also the Philco model 43-200 series. These were reproduced without required permission from Howard W. Sams Photofact Folios. We are deeply regretful that this occurred.



More Installations . . .

More Sales Dollars . . .

More Profits . . .

★ Those new sets—AM, FM, TELEVISION . . . are no better than the antenna equipment used. Former make-shift jobs simply won't do. Set owners expect, demand and will pay for superlative performance.

And that's where TACO antenna equipment comes in. There's a type for every kind of receiver. Also the TACO Master Antenna System for apartment houses, hotels, hospitals, etc.

★ Ask Your Jobber . . .

If you want to make more money, ask your jobber for the latest TACO catalog. Or write us direct. Start handling and installing TACO antenna equipment today—for the best in reception—for better business.



Check These CONCORD VALUES!

Concord has them! Radio and Electronic Parts, Supplies and Equipment of every kind, for every need . . . long awaited, hard-to-get items . . . new merchandise, just received . . . Hundreds of bargains to check NOW for IMMEDIATE SHIPMENT from CHICAGO or ATLANTA.

Write for catalog of Radio Parts and Electronic Equipment. Packed with Radio Needs—new and scarce items—Bargains. Write Dept. S-126.

CRESCENT AUTOMATIC RECORD CHANGER

Simple, single control, plays ten 12" or twelve 10" records automatically. Rejects any record desired, or permits optional playing of records manually. Only three moving parts while changing. Fast . . . changes records in 5 seconds. Has self-starting, 78 R.P.M., 110 volt 60 cycle A.C. heavy duty motor. Finished in two-tone brown with attractive plastic trim. Requires only 5 1/4" head room and fits any cabinet with 12 1/2" x 16 1/4" changer area. **\$19.95**
C22503. SPECIAL

ALNICO V 5" P.M. SPEAKER

New Alnico V magnet provides maximum performance with minimum weight. Normal wattage 3, peak wattage 4 1/2. V.C. impedance 3.2 ohms. depth 2 7/16". **\$1.98**
5B7009



9003 VHF Midget Super Control RF 95 Pentode Tube

HEAVY DUTY LINE FILTER Solar Elim-O-Stat. Completely shielded. Type EN106. **\$1.79**
5B3218 Each

WIRE STRIPPER

Strips wire instantly! Fastens to bench or other support. Wire stripped to any length. Strips wire up to 12 MM diam. Each **98¢**
C15268

D.C. MILLIAMMETERS

2 1/2" flange mounting type. Black dull finish bakelite case. Mfg. Hinge included. Large, clearly legible dial calibrations. Either **5B4122—0-20 M.A.D.C.** or **5B4116—0-300 M.A.D.C.** Special **\$3.23**



Supreme Model 543B 1000 O. P. V.

A Sensitive Meter

Has pin jack terminals, and includes the following ranges: — 0/6/60/600 D. C. M. A., 0/15/150/600/3000 V. A. C. and D. C., 0/2000/200,000 ohms. This meter is convenient to carry. Weighs 28 ozs. Uses full size 3" meter with a rugged, accurate I.M.A. movement. All resistance ranges are operated by batteries furnished with the unit. Bakelite case. Size: 5 7/8" x 2 1/16" x 2 1/8". Shpg. wt. 2 lbs. **\$18.57**
C21745

TUNER UNIT TU-10-B

Continuous frequency range from 10 MC. to 12.5 MC. VFO oscillator tuning section, buffer, coupling, capacitors and choke & buffer output matching tapped coil & condenser. Size 1 5/8" h. x 7 3/8" h. **\$2.95**
A54132

3 Mfd. 4000 Volt Hi-Voltage CONDENSER

Large 3 mfd., 4000 v. D.C. condenser, hermetically sealed in an aluminum can. Size 4 1/2" x 3 11/16" x 7 3/4" high. **\$4.95**
5B3168

T-17-B 200 Ohm Carbon Mike.

Lightweight, with press-to-talk button. Built-in filter to suppress carbon hiss. 5' rubber covered cable and **\$2.49**
PL-68 3-circuit plug supplied. 5B7062


Midget Volume Control — 1 Meg. ohm Standard 3/4" Bushing, 1/2" dia. Shaft, 3/4" long, with split 90° spline for push-on knob. **\$1.35**

STANCOR Universal Output Transformer Type A 3856. Primary for all single or push-pull plates. Secondary adjustable from 1 to 30 ohms. Two-inch mounting centers. 4 watts at 35 mils. **\$1.32**
C1675. SPECIAL


CONCORD RADIO CORPORATION

LAFAYETTE RADIO CORPORATION
CHICAGO 7 ATLANTA 3
901 W. Jackson Blvd. 265 Peachtree Street


NEW MODELS

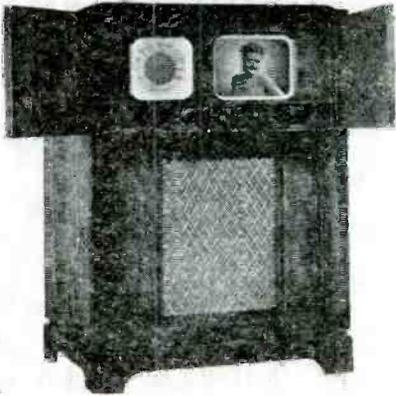


G.E. 801 direct-view television receiver producing a 10" picture. Receiver covers a-m broadcast channels.

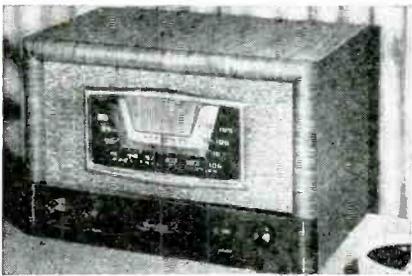

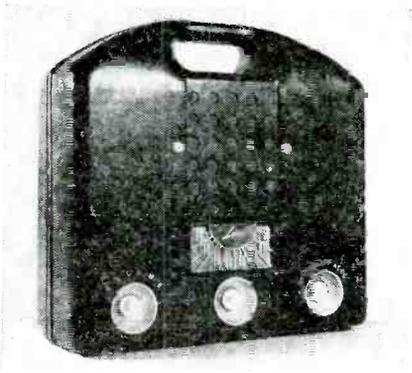Bendix 747-A f-m/a-m receiver using ratio detector.



Lewyt a-c/d-e/battery portable.

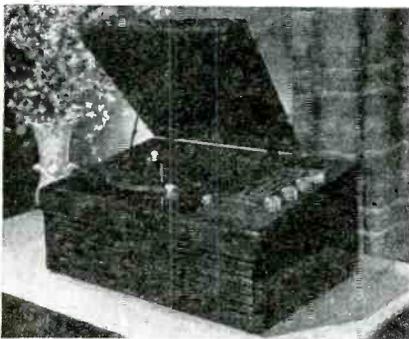

Air King combination 6-tube superhet featuring automatic record changer for 14" or 12" records. Has beam-power output.

A TIGHT SPOT where Cherry Blind Rivets were invaluable. Operator is riveting perforated aluminum insulation retainer sheets to structure back of electric cables. Because Cherry Rivets were available it didn't matter that electric cables had already been run.



Here's How... A CONTROLLED PULL

... irons out fastening kinks



High Strength, self-plugging type Cherry Blind Rivet



Tight clinching pull-through hollow type Cherry Blind Rivet

A CONTROLLED PULL instead of a pound. There's no hammering or bucking because Cherry Blind Rivets are installed with a controlled pull from one side of the work only.

A SIMPLE ONE-HAND OPERATION vs. a tough two-man job. Installing a Cherry Blind Rivet is a fast, one-hand operation requiring only three simple steps: (1) inserting rivet in hole; (2) engaging the rivet; (3) actuating the gun.

SPECIAL CHARACTERISTICS establish Cherry superiority over all other blind fasteners: (a) Greater shank expansion; (b) Greater allowable variance in material thickness for a given rivet-length. These factors mean uniformly tight, strong joints under actual production conditions where hole sizes and sheet thicknesses cannot always be controlled closely.

FAMILIARITY BREEDS RESPECT wherever Cherry Blind Riveting is used. This simplified, speed-up fastening technique is finding more and more friends in more and more industries by providing secure, permanent fastening... while cutting production costs.

CHERRY RIVETS. THEIR MANUFACTURE & APPLICATION ARE COVERED BY U. S. PATENTS ISSUED & PENDING

Cherry Rivet

Company


LOS ANGELES 13, CALIFORNIA



Get this Cherry D-45 Manual. Write to Dept. L-268, Cherry Rivet Co., 231 Winston Street, Los Angeles 13, California

THE MASTERS CHOICE!

SUPREME MODEL 504B TUBE AND SET TESTER

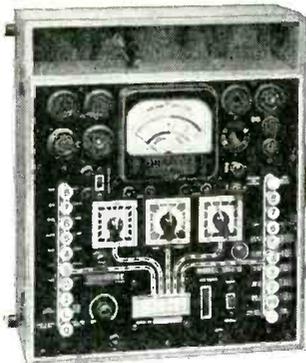

Any craftsman distinguishes himself by the appearance of his tools and equipment. For 19 years SUPREME equipment has identified thousands of successful radio service engineers. SUPREME equipped repair shops distinguish themselves for their professional appearance, dependability, and profitable operation.

One among the complete group of SUPREME radio testers is the Model 504B Tube and Set Tester.

- **METER**— large 4-inch square-face meter, 500 microampere.
- **SPEED**— push-button operated.
- **FLEXIBLE**— simple, yet Universal Floating Filaments feature insures against obsolescence.
- **SIMPLICITY**— roll chart carries full data for tube setting. No roaming test leads when using multi-meter—only push a button.

SPECIFICATIONS

DC VOLTS — 1000 Ohms per volt: 0.5-25-100-250-500-1000-2500.
AC VOLTS — 0.5-10-50-250-1000.
OUTPUT VOLTS. 0.5-10-50-250-1000.
OHMMETER. 0-200-2000-20,000 Ohms
0-2-20 Megohms

Condenser Check:

Electrolytics checked on English reading Scale at rated voltages of 25-50-100-200-250-300-450 volts.

Battery Test:

Check dry portable "A" and "B" batteries under load.

SUPREME

SUPREME INSTRUMENTS CORP.
GREENWOOD, MISS.
U. S. A.



"SUPREME BY COMPARISON"

See the complete SUPREME line.
Write for new SUPREME catalogue
No. 446.

BRITISH PORTABLES

(Continued from page 9)

imum inductance, were dried and impregnated under vacuum in petroleum jelly and then immersed in high-melting-point wax.

This design technique prompted the recent development of a plain-foil electrolytic capacitor, 1 $\frac{1}{8}$ " x $\frac{1}{2}$ ". This has been made possible by mounting the small negative electrode within a thin metal case and then closing the ends of the case on to synthetic rubber end-plugs, through which the connecting tags pass. They are said to have exceptionally good temperature characteristics. At -50° C, the capacitance is still approximately 50% of its value at 15° C; maximum working temperature is 71° C. There are six values available, the smallest being 1 mfd and the largest 20 mfd, their maximum peak working voltages being 350 and 12 respectively. Other miniature capacitor designs have included paper capacitors in aluminum tubes with synthetic rubber end-plugs, varying in diameter from 1/5" to 3/8" and in capacity from 0.001 to 0.1 mfd, with overall lengths from 1" to 1 $\frac{1}{2}$ ".

Using wartime miniature design techniques, a manufacturer recently produced thumbnail type a-f chokes and transformers. Despite their small size these transformers and chokes, which measure 1 3/64" long, 1 $\frac{1}{8}$ " deep and 1 $\frac{1}{8}$ " high, have a very uniform response throughout the audio range.

A series of i-f transformers, designed for maximum gain and selectivity, yet occupying a minimum of space, manufactured during the war for inclusion in walkie-talkie sets and miniature receivers for beach landing parties, are now available for general use. The coils are contained in enclosed pot-type iron-dust cores with adjustable iron-dust center cores. Trimming capacitors are mounted inside the screening can which measures 1 $\frac{1}{8}$ " deep by 1 $\frac{1}{8}$ " square. Tested between a 6K7 and a standard voltmeter, these transformers had a gain of 60 at a frequency of 1 mc; at 2.1 mc the gain was 28 and at 4.86 mc it was 15.

The most outstanding reduction in size is probably that of the midget p-m moving-coil loudspeaker. One type has an overall diameter of 2 $\frac{1}{2}$ " and occupies a depth of 1 $\frac{1}{8}$ ". This miniature speaker, the voice coil of which is half an inch in diameter, is capable of handling inputs of up to 1/2 watt.

A recently produced moving-coil earphone uses a miniature moving coil and cone diaphragm; the permanent



WIRES




made by engineers
for engineers.....

CORNISH WIRE CO., INC.
15 Park Row • New York City, 7



BARGAIN SPECIAL

18
VOLUME-
CONTROLS
only \$2.95

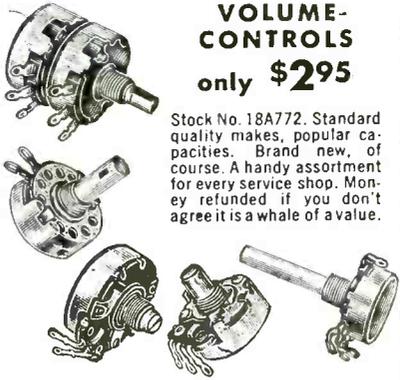

Stock No. 18A772. Standard quality makes, popular capacities. Brand new, of course. A handy assortment for every service shop. Money refunded if you don't agree it is a whale of a value.

RESISTOR ASSORTMENT

Quality makes, insulated, RMA color coded assortment of 100 (50 one watt and 50 one-half watt) all popular capacities. Handy color code chart included.
No. 18A74. Per assortment . . . \$1.95

IN OUR BIG CATALOG

Many more outstanding values in big BA Catalog. Write if you do not receive it. And order now from this ad while these big values are still available. Add for postage.

BURSTEIN-APPLEBEE CO.
1012 McGee, Kansas City 6, Mo.

magnet is less than an inch in diameter and the moving coil, $\frac{1}{2}$ " in diameter, consists of four layers of 46 s-w-g in a 0.032" gap.


Multi-Contact Switch

In response to a request from Britain's Ministry of Supply for a miniature multi-contact switch, capable of withstanding conditions in the Far Eastern war zone, one company produced a rotary wave-change switch with all moving parts and contacts hermetically enclosed in a $\frac{3}{4}$ " diameter and $\frac{1}{8}$ " deep container. In producing this switch it was necessary to silver-plate the very small contacts with a very fine finish to provide a relatively small contact area that had a contact resistance of $\frac{1}{100}$ th of an ohm and a current-carrying capacity of 50 ma. The problem was solved by making the contact springs from phosphor bronze strip on which pure silver, a thousandth of an inch thick, was rolled. The switch is now available with 12 contacts, in single-, two-, three-, and four-pole.

Miniature two-gang and three-gang tuning capacitors, with an overall depth behind the panel of 1.87" and 2.67", respectively, also produced for the Forces, will be available for general use very shortly.

Other components and accessories which have been greatly reduced in size during the past year or two are composition fixed resistors, now little thicker than a pencil lead, selenium rectifiers and B batteries.

AT BENDIX SERVICE SCHOOL

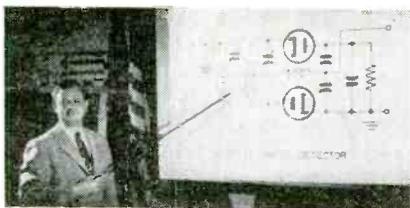

D. H. Kresge, service manager for radio and television, Bendix Radio Division, Bendix Aviation Corporation, discussing operation of the ratio-detector system, used in Bendix f-m receivers, before members of a service school recently conducted by Bendix.

SYLVANIA TEST EQUIPMENT STUDY



Sylvania test equipment under study at the Emporium plant by . . . (left to right) R. W. Andrews, G. C. Isham, J. T. Mallen, S. J. McDonald, H. G. Kronenwetter, John Hauser, R. F. Henderson, H. C. L. Johnson, H. H. Rainier, G. R. Wannan and R. P. Almy.



Cherrio! Merry Christmas

Astatic is happy to extend sincere holiday greetings and best wishes . . . and at the same time to express its deep appreciation of your kindness, courtesy and patronage during the year now ending. May Astatic continue to warrant your confidence and friendship not only this Christmas but through many Christmases to come.



SERVICING HELPS

by FRANK C. KEENE


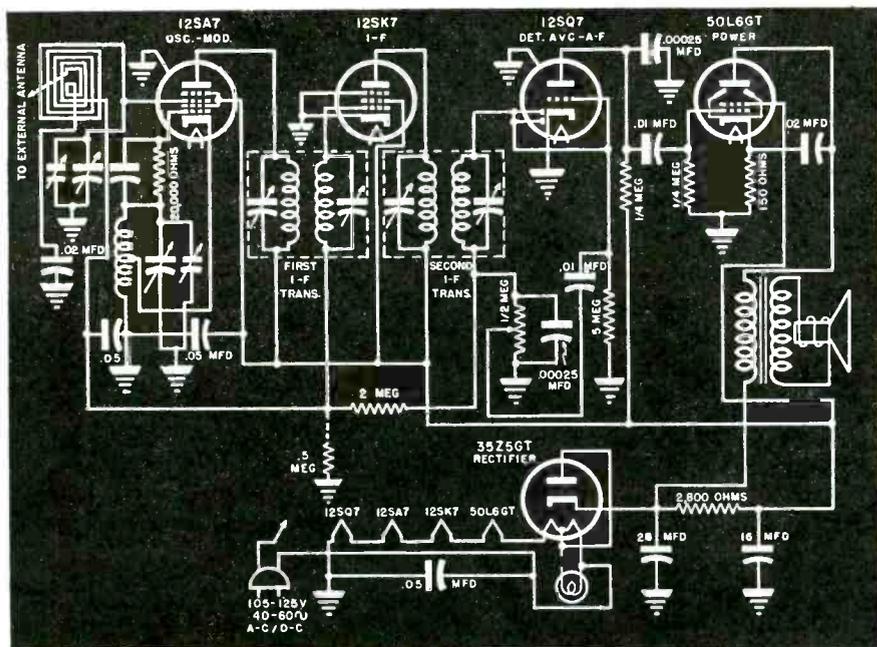


Fig. 1. (Van Houten Query). G.E. LCP 508 used to study lack of sensitivity problem.

I HAVE FOUND THAT a-c/d-c receivers several years old seem to lack sensitivity, even though a stage-by-stage check reveals normal gain. Are there any cures for this deficiency?—James Van Houten.

Fig. 2. (Pett Query). The r-f portion of Sparton 74 analyzed in the oscillation problem of Mr. Pett.

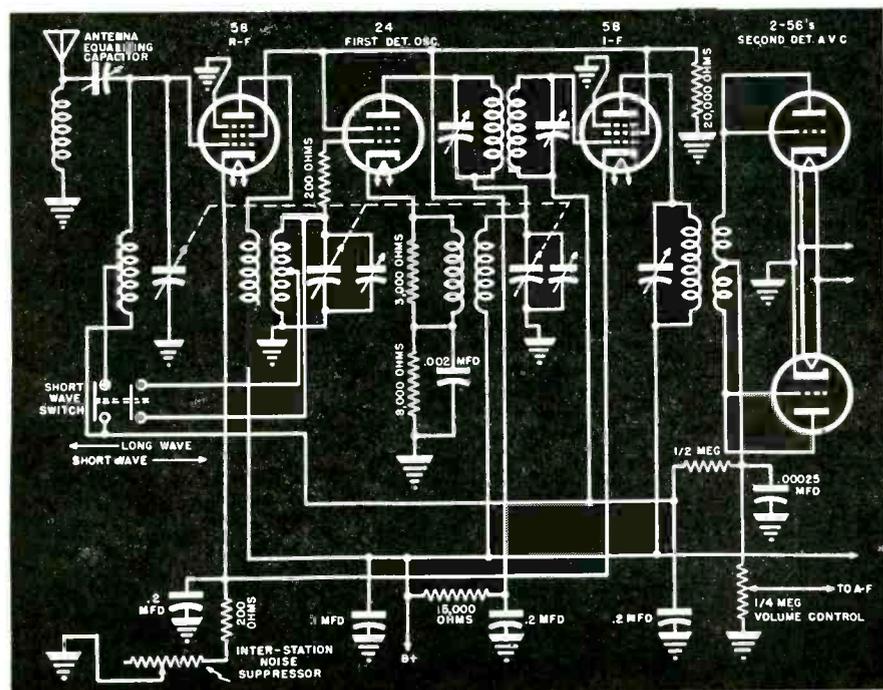To analyze this problem, let us study a typical midget receiver; Fig. 1 (G. E. LCP 508). If realignment and new



tubes do not have the desired effect, the filter network should be checked. A voltage check may show that the filters need replacing. The use of high farad capacitors is recommended.

Three other kinks may help when other methods fail. The first is to insert a .5-megohm resistor from the avc bus to ground at the r-i end of the avc filter resistor. This would have the effect of reducing the avc action, decreasing the bias on the r-f tubes, and increasing the apparent gain of the receiver. This should only be used where there are no exceptionally strong local signals.

The second kink is to move the loop antenna further away from the chassis. This, in effect, improves the loop's Q. If this is not feasible, a thin copper sheet might be inserted between the loop antenna and the chassis proper. The sheet should be attached to the chassis. This is equivalent to an electrostatic shield between the chassis and the loop, and reduces the signal absorption of the chassis.

IN SERVICING A 1934 Sparton 74, I found what appeared to be an oscillating first i-f. That is the set played weakly with the grid cap off, but with the cap on, hum, oscillation and instability appeared. The trouble was particularly acute on the high-frequency end of the dial. Neither changes of components nor the usual circuit changes cured the trouble. Have you any suggestions?—Murray A. Pett.

It seems that the trouble does not lie in the i-f stage proper, but in the r-f portion of the receiver; Fig. 2. It is unlikely that the i-f would oscillate only at the high frequency end of the dial. Oscillation is due to feedback, which means that some portion of the signal is getting back from the output to the input of a tube. If the wiring of the receiver has not been changed, this type of trouble can be traced to a defective r-f bypass capacitor.

There are three points where this trouble may arise. These are the control grid, the screen grid and the cathode circuits. In this particular receiver the most logical point to test first is the avc system. It will be noted

(Continued on page 43)



FOR

**THE BROADCAST STATION
THE HIGH FIDELITY AMPLIFIER
THE LABORATORY**

**LINEAR
STANDARD**



Linear Standard audio units are the closest approach to the ideal component from the standpoint of frequency response, wave form distortion, efficiency, shielding, and dependability. Guaranteed response ± 1.3 DB, 20—20,000 cycles. The standard of the broadcast industry . . . units available for every audio and power application.

**ULTRA
COMPACT**



For compact, high fidelity equipment, UTC Ultra Compact units are unequalled. Light in weight, yet providing frequency response ± 2 DB from 30 to 20,000 cycles. All units except those carrying DC in primary employ true hum balancing coil structure which, combined with high conductivity outer case, insures good inductive shielding. Units available for all audio applications up to + 10 DB in operating level.

**INTERSTAGE
FILTERS**



UTC Interstage Filters (10,000 ohms impedance) are available in low pass (LPI), high pass (HPI), and band pass (BPI) types for all frequencies from 200 to 10,000 cycles. Designed to effect 6 DB loss at cutoff frequency . . . 35 DB at .75 and 1.5 times cutoff frequency . . . 40 DB at .5 and twice cutoff frequency. Dual alloy magnetic shielding reduces pickup to 150 Mv. per gauss.

VARITRAN



Varitran units provide an ideal means of voltage control for AC equipment. Performance features include high efficiency . . . excellent regulation . . . universal mounting features . . . self-contained fuse protection. Available in 115 volt and 230 volt models with from 1 to 11 Amp. output rating. These units afford stepless adjustment of voltage from 0 to 113% of line voltage.

United Transformer Corp.

150 VARICK STREET NEW YORK 13, N. Y.
EXPORT DIVISION: 13 EAST 40th STREET, NEW YORK 16, N. Y., CABLES: "ARLAB"

BETTER VALUES from **ARROW!**

Army Aircraft Receiver

Model BC-946-B

Broadcast Band from 520 to 1500 KC, tube complement, 3-12SK7, 1-12SR7, 1-12A6, 1-12K8; can be used with 24V dynamotor supplying A & B power; can be converted to AC or DC or 32-volt sets; 3 stages of IF used, uses 3-gang condenser, complete with tubes and schematic.

Each **\$12.95**
Dynamotor DM32A, **4.95**
each

Supreme Foundation Meter

40 Micro Amps., 20,000 ohms per volt. 4 1/2" square. Manufactured by Supreme Instruments Corp. Each..... **\$8.95**

HEADPHONES

Signal Corps, 8000 ohms and 200 ohms, ea. **\$ 2.49**
Lots of 10 **19.50**
2000 ohms Headphones, Trimm, ea. **1.79**
Lots of 10 **16.00**

SPEAKERS

PM Alnico, 4"	Each	\$1.60
5"	1.65
6"	2.25
4x6	2.15
6" extra heavy	2.85
8"	3.85
Dynamic, 12"	6.95
1000 ohm field		

Hickok 2 1/2" AC Volt Meter

Each **\$3.49**
Lots of 10 **\$29.50**

3 1/2" G. E. Automatic Time Meter

60 cycle 110 volts. This time meter consists of a cyclometer driven by a telechron synchronous motor. Connect to an electric circuit; it will measure and indicate the number of hours, tenths of hours or minutes that the circuit is in use. Shipping wt., 6 lbs. List \$17.00. Your cost **\$4.95**

SIGNAL CORPS RECEIVERS

6 tubes: 3-12SK7, 1-12SR7, 1-12A6, 1-12K8; 100-550 Kc. (specify freq. desired) 3-6 mc power 28 VDC, mfd. by Western Elec, etc. Ship. wt. 19 lbs. Original cost \$99.23. Complete with tubes, whole receiver at cost of tubes only, slightly used—your **\$6.95**

Wholesalers, dealers, institutions and other quantity purchasers . . . write, wire, phone for quantity prices.

Dept. E

ARROW SALES Inc.

59 West Hubbard Street, Chicago 10, Ill.
Telephone: Superior 5575



BEN FRENCH JOINS SAMS' PHOTOFACTS

B. V. K. French has been named director of field relations of Howard W. Sams & Co., Inc., Indianapolis, Indiana.

Mr. French will act as liaison between the manufacturer and the servicing profession.

Mr. French was formerly supervisor of the Mallory Research Laboratory.



* * *

R. B. UNGER NOW WARD PRODUCTS ASSISTANT SALES MANAGER

Roy Brown Unger has been appointed assistant sales manager of the jobber division of the Ward Products Corporation, Cleveland.



* * *

COLLINS BECOMES AEROVOX CHIEF ENGINEER

Joseph L. Collins has been named chief engineer of the Aerovox Corporation, New Bedford, Mass. He has been head of the electrolytic engineering division since 1938, and before that in charge of electrolytic engineering of Sprague Electric Company.

* * *

SCENIC RADIO CATALOG

A 16-page catalog has been issued by Scenic Radio & Electronics Co., 53 Park Place, New York City 7, N. Y.

Items featured in the catalog include volt-ohm-milliammeters, signal generators, tube testers, oscilloscopes, vacuum-tube voltmeters, signal tracers, audio amplifiers, phonograph players, automatic record changers, loudspeakers, tubes, microphones, antenna kits, radio text books, etc.

Harry Adelman is president of Scenic Radio.

* * *

S. LUBIN JOINS SPRAGUE ELECTRIC

Samuel Lubin has joined the staff of the field engineering department of the Sprague Electric Company, North Adams, Mass. Mr. Lubin will locate in

For Soldering in
Tight Places . . .

DRAKE

No. 400 Soldering Iron

Smallest Industrial Iron
Ever Designed

60 Watts — 1/4 in. Tip
Only 9 in. long. Wt. only 8 oz.

This mighty mite is backed by DRAKE's 25 years of soldering iron manufacturing experience. The high quality and long-service of DRAKE Soldering Irons have made them outstanding favorites with all types of radio men everywhere. The DRAKE No. 400 is an outstanding value at



Only **\$4.50**
List

Drake Has an Iron
for Every Purpose.
Ask Your Radio
Parts Jobber

DRAKE ELECTRIC WORKS, INC.

3636 LINCOLN AVE., CHICAGO 13, ILL.

NEWCOMB JOBBERS LEAD
THE FIELD IN PROFITS
SELLING THE FINEST
EQUIPMENT MADE TODAY

**AMERICA'S
TOP QUALITY
AMPLIFIER
WILL GIVE
YOU
MORE PROFIT
PER SALE**

A sound rule for increasing jobber profits will be sent to you upon request. Write for free booklet.

Newcomb
AUDIO PRODUCTS CO.

2815 So. Hill Street, Dept E
Los Angeles 7, California

Washington, D. C., in charge of contacts with all government agencies.

Mr. Lubin was formerly with the new development section of the Technical Standards Division of R. E. A.



STROMBERG-CARLSON F-M ADAPTER

To convert prewar f-m receivers to the new 88-108 mc bands, a simplified adapter has been invented by George Driscoll, manager of Stromberg-Carlson Company f-m station WHFM, Rochester, N. Y.

The adapter is being marketed by Stromberg-Carlson.

KOETKE JOINS NEDA

Norman A. Koetke has joined the executive staff of the national office of NEDA.

OPERADIO APPOINTS FRED D. WILSON GENERAL SALES MANAGER

Fred D. Wilson has become general sales manager of Operadio Manufacturing Co., St. Charles, Ill. Mr. Wilson has been in charge of jobber sales of the company's commercial line and trademarked equipment.



RADIOLAB CATALOG

A catalog, No. 6E-2, listing multi-testers, signal generators, oscilloscopes, sound amplifier systems and student construction kits for schools and laboratories, has been issued by the Radiolab Publishing & Supply Co., 652 Montgomery St., Brooklyn 25, N. Y.

WNBT AND WPTZ TO EXCHANGE TELEVISION PROGRAMS

An agreement providing for the exchange of commercial and sustaining television programs between WNBT in New York and WPTZ in Philadelphia has been signed by the National Broadcasting Company and Philco Corporation.

BENDIX RADIO APPOINTS MASTER SERVICE DEALERS

Seven servicing organizations have been named to service Bendix aviation radio equipment by George Myrick, manager of personal aviation sales for Bendix Radio. The service organizations are

(Continued on page 37)

CAPITOL RADIO ENGINEERING INSTITUTE — Where Professional Radiomen Study



—“Service” Mag. Photo

Good-Paying Jobs . . . Security . . . A Bright Future Can Be Yours! Meet the Challenge With the Aid of CREI Home Study Training and Keep Pace With Radio

Foresighted radio servicemen are looking ahead to the future. A future that has unlimited opportunities and real profits for those who have the “Know-How” to SERVICE television, FM, industrial electronic equipment, and the many other new radio developments.

Join the many professional servicemen who are studying at home the new developments, the new techniques with CREI . . . protecting their future jobs, their businesses by acquiring the new “Know-How”, NOW!

CREI's reputation for home study training has been proved over 19 years. Important new developments have been included in our present course. Trained instructors give you personalized attention and guidance *all the way*.

Find out for yourself how CREI can help you to greater security and prosperity. Send in the coupon now! Actually *see* what CREI has to offer.

VETERANS! CREI IS APPROVED FOR “G.I.” TRAINING!

RESISTANCE

—To New Ideas Has Cost Many a Man a Great Future. We all know the classic stories of the people who scoffed at Edison, Ford, DeForest. It was the scoffers who lost out when the rewards poured in. Now with radio-electronics entering a great, new era, when it may well emerge in greatly magnified form, you fellows who are in on the ground floor and don't prepare now for the future fall in the same class as those early scoffers.

E. H. Rietzke
President of CREI

Capitol Radio Engineering Institute

An Accredited Technical Institute

E. H. RIETZKE, President

Dept. S-12, 16th and Park Road, N.W., Washington 10, D. C.

Branch Offices:

New York (7): 170 Broadway

San Francisco (2): 760 Market Street



If you have had professional or amateur radio experience and want to make more money, let us prove to you we have the training you need to qualify for a better radio job. To help us intelligently answer your inquiry—PLEASE STATE BRIEFLY YOUR BACKGROUND OF EXPERIENCE, EDUCATION AND PRESENT POSITION.

S-12

Capitol Radio Engineering Institute
16th and Park Road, N. W., Dept. S-12, Washington 10, D. C.

GENTLEMEN: Please send me your free booklet, “Your Opportunity in the New World of Electronics”, together with full details of your home study training. I am attaching a brief résumé of my experience, education and present position.

Name

Street

City..... Zone..... State.....

I am entitled to training under the G. I. Bill.



The
UNIVERSAL
Electrolytic

● Heretofore offered only in cardboard-case container, this type is now available in an aluminum can—the postwar Aerovox Type PRVC.

This truly universal replacement electrolytic readily doubles for twist-prong, spade-lug and screw-base types. To install, center screw is removed, metal cleat slipped off, wire leads passed through mounting hole, and metal cleat and screw now replaced from underside of chassis and tightly drawn up. Insulated positive and negative wire leads. Multiple sections have concentrically-wound sections with common negative. In all popular voltages and capacitances.

● Ask Our Jobber . . .

Order your Aerovox Type PRVC metal-can cleat-mounting electrolytics from him. Have a stock on hand for those rush jobs. Ask for postwar catalog—or write us.



FOR RADIO-ELECTRONIC AND INDUSTRIAL APPLICATIONS

AEROVOX CORP., NEW BEDFORD, MASS., U.S.A.
Export: 13 E. 40th St., New York 16, N.Y. • Cable: 'ARLAB'
In Canada: AEROVOX CANADA LTD., Hamilton, Ont.

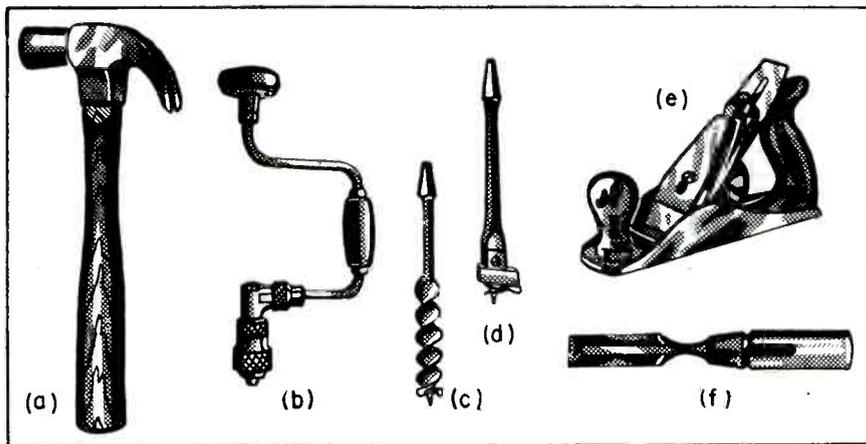


Fig. 4. Some of the essential woodworking tools that are often used around the shop.

TOOLS

(Continued from page 16)

can be used for transferring distances directly from a rule, or for scribing circles or parts of circles. They often are needed merely for measuring distance of separation between parts already mounted, or for dividing spaces into equal parts, or determining the dimensions of irregularly shaped work. Their points should be kept sharp. A pair of wing dividers about 6" long will be satisfactory.

Trimming Knives

One of the handy little craftsman's knives, made to take several interchangeable surgical steel blades of various sizes and shapes, is handy for all trimming operations on dial cords, speaker cones, speaker grille cloth, and a variety of other uses. The three blade shapes illustrated with the knife at (b) of Fig. 3 are practical for Service Shop use.

Woodworking Tools

A few of the more essential woodworking tools should be included in the tool equipment of the Service Shop, for they are needed when counters, shelves, cupboards, etc., are to be installed, for alteration work on wooden radio cabinets, and for a variety of other construction and alteration jobs around the shop. If a test bench is to be built, or altered, they are absolutely necessary!

Tools required include a medium size crosscut saw for cutting across the grain of wood, and a medium size rip saw for cutting along the grain.

A carpenter's claw hammer is needed for driving nails. The claw is useful

for removing nails from wood, etc. One is illustrated at (a) of Fig. 4.

A carpenter's hand brace of the type illustrated at (b) is required for turning wood-boring tools. Needed too are some of the other types of hole-cutting tools already described. The carpenter's brace has a 2-jaw chuck

(Continued on page 36)

The
HOUSE OF A MILLION RADIO PARTS

SERVICE MEN—
SOUND MEN—
AMATEURS—

Write for the latest Lifetime BARGAIN BULLETIN just off the press! Thousands of money-savers in parts, supplies, equipment.


Lifetime
SOUND EQUIP. CO., Dept. 85
911-913 JEFFERSON AVE., TOLEDO 2, OHIO

PROTECT YOUR FUTURE
BUY YOUR EXTRA SAVINGS BONDS NOW



High Efficiency Auto Antennas


PUT more mileage on your cash register with this distinctive line of auto antennas. They're a hit with the car owner every time he hits the road. Built to pull in programs clearly, they keep noise reception at a low level. Designed to fit every car, these five models are bound to pull in profits for you. It's a self-starter program with plenty of powerful sales follow through. For more information, write: *General Electric Company, Electronics Department S-6811, Syracuse 1, New York.*

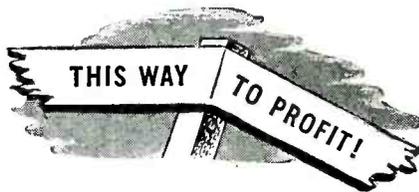

Check and double check this list of

FEATURES:

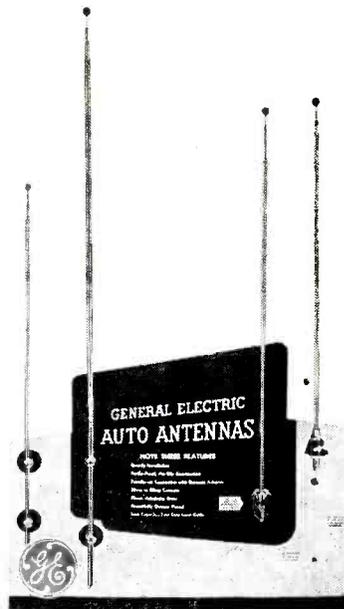- Completely equipped with a newly developed low capacity, low loss lead cable.
- Speedy installation, positive interference-proof, lead coupling.
- Ferrule-set connection with bayonet adapter.
- Rattle-proof, no-slip, fluid type construction.
- High efficiency, low resistant silver to silver contacts.
- Finest Admiralty brass, beautifully chrome plated.



Free display board with every order for 24 antennas.

GENERAL ELECTRIC

168-E3


Model 2450 ELECTRONIC TESTER

★
There's never been a tester like this!

Here's a tester with dual voltage regulation of the power supply DC output (positive and negative), with line variation from 90 to 130 Volts. That means calibration that stays "on the nose"! That means *broader service* from a tester that looks as good as the vastly improved service it provides. This model includes our Hi-Precision Resistor which outmodes older types.

HIGHLIGHTS — 12 ranges: DC and AC. Volts 0-2.5-10-50-250-500-1000 • DC MILLIAMPS: 0-0.1-1.0-10-50-250-1000 • OHMS: 0-1000-10,000-100,000 • MEGOHMS: 0-1-10-100-1000 • CAPACITY IN MFD: 0-.005-.05-.5-5-50 • LOAD IMPEDANCE: 5 megohms on DC Volts • CIRCUIT LOADING: Low frequencies. Circuit loading equal to 8 megohms shunted by 35 mmfd. High frequency circuit loading equal to 8 megohms shunted by 5 mmfd.

Detailed catalog sheets on request.

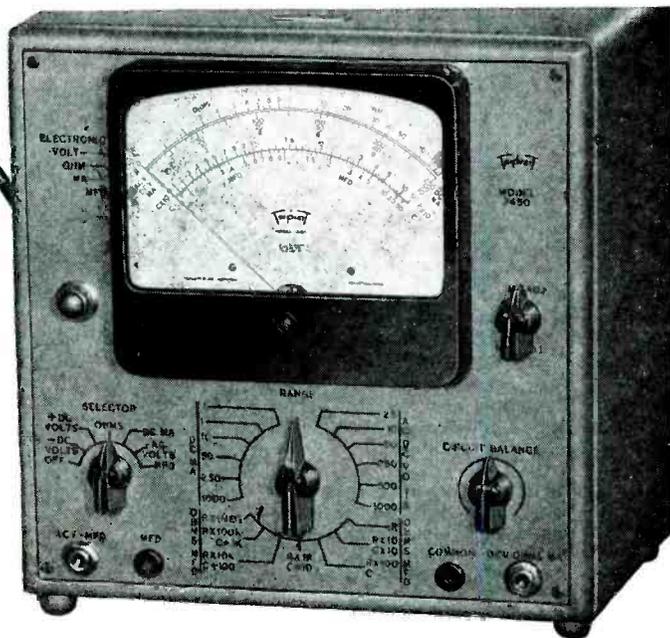

*Precision first
...to last*


Triplet

ELECTRICAL INSTRUMENT CO. BLUFFTON, OHIO



Give your Service Job the EXTRA PROTECTION

of WARD LEONARD Vitrohm Resistors

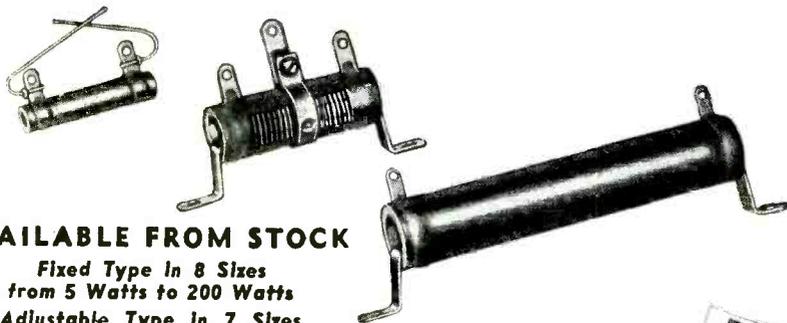

AVAILABLE FROM STOCK

Fixed Type in 8 Sizes
from 5 Watts to 200 Watts
Adjustable Type in 7 Sizes
from 10 Watts to 200 Watts

The installation of VITROHM wire-wound resistors insures that *extra* performance you want in critical circuits. With exclusive features developed in the WARD LEONARD laboratories . . . these resistors meet the most rigid specifications. They provide long, trouble-free service, avoid call-backs, build satisfied customers and greater profits. Available in wide range of resistance values.

**AUTHORIZED DISTRIBUTORS
EVERYWHERE**

Ward Leonard Electric Co., Radio and Electronic Distributor Division, 53E W. Jackson, Chicago 4

**SEND FOR
FREE CATALOG**

Gives complete data and information on Ward Leonard Vitrohm Resistors carried in stock. Write for Catalog No. D-2.



WARD LEONARD RELAYS • RESISTORS • RHEOSTATS

Electric control devices since 1892

Automatic Combinations—NOW!

The New Arnold Shure Automatic Wired Record Player ready for immediate delivery.

The Shure automatic record player connects easily to any radio. Its featherweight crystal pickup and quiet, smooth changer action assure high quality playing of ten 12" records or twelve 10" records. Every one of your customers can now own a fine automatic combination at a remarkably low cost.

Shure players are shipped complete with A.C. cord and shielded cable—only 2 wires to connect and it's ready to play.


Your price only \$21.92 net

F.O.B. Chicago, Illinois

OPA Retail Price — \$31.30 — Zone 1

OPA Retail Price — 33.87 — Zone 2

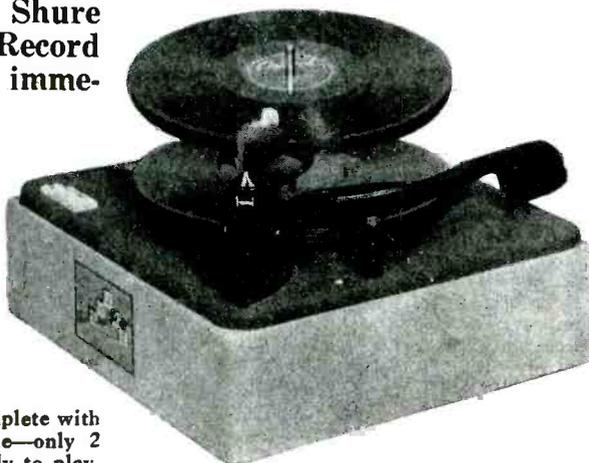Orders are now being accepted for immediate delivery—no waiting. Terms: 2% check with order. Or 25% deposit, balance express C.O.D.



PHONO AMPLIFIERS

1-Tube Phono. Amplifier.....\$2.35 ea.
3-Tube Phono. Amplifier..... 4.50 ea.

PM SPEAKERS

4" Alnico (5) PM Speaker.....\$1.89 ea.
5" Alnico (5) PM Speaker..... 1.49 ea.
6" Alnico (5) PM Speaker..... 1.89 ea.

TUBULAR ELECTROLYTICS

100-MFD-25 V....\$.22 ea.	10-MFD-450 V....\$.29 ea.
10-MFD-50 V.... .22 ea.	16-MFD-450 V.... .39 ea.
20-MFD-150 V.... .22 ea.	10-10-MFD-450 V.... .59 ea.
30-MFD-150 V.... .29 ea.	20-20-MFD-150 V.... .29 ea.
40-MFD-150 V.... .39 ea.	30-20-MFD-150 V.... .39 ea.
50-MFD-150 V.... .45 ea.	40-30-MFD-150 V.... .45 ea.
8-MFD-450 V.... .25 ea.	50-30-MFD-150 V.... .59 ea.

HOLLANDER RADIO SUPPLY CO.
549 West Randolph Street Chicago 6, Illinois

TOOLS

(Continued from page 34)

which clamps the square bit shank diagonally across opposite edges. It will be well to purchase a brace that is equipped with a ratchet for working in close quarters.

Along with the brace should go several wood auger bits, shown at (c). Sizes sufficient for all ordinary purposes are: 1/4", 3/8", 7/16" and 1/2".

For boring larger holes in wood, an expansion bit of the type illustrated at (d) is useful. This has a cutter whose position may be adjusted for drilling holes of various sizes. These bits are made in several sizes; the one illustrated will bore holes from 1/2" to 1" diameter. When larger holes are to be bored, the fly-cutter illustrated at (e) of Fig. 4 may be used.

Whether or not a plane, shown at (d), is to be purchased depends upon the scope of the carpentry work to be done, and finances.

A small 1/2" or 3/4" wood chisel, of the type shown at (f), will certainly be needed. One having an unbreakable type handle and a high grade steel blade that will retain its cutting edge should be chosen.

A small combination oil stone (medium-fine) will enable you to keep the cutting edges of all the fine cutting tools around the shop in good workable condition.


Adequate Tool Equipment

A Shop that contains most, or all of, the tools listed and described thus far in this series may consider itself well equipped from the standpoint of mechanical tools.

Articles to follow will describe additional special-purpose time-saving devices, and accessories, that also are desirable.

(To be Continued)

Fig. 5. A handy Service Man's vest pocket kit containing 6 hex key wrenches. (Courtesy The Allen Manufacturing Co.)

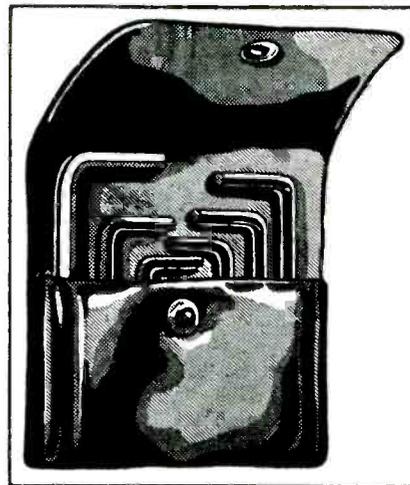

NEWS

(Continued from page 33)

Palo Alto Airport, Inc., Palo Alto Municipal Airport, Palo Alto, California; Aircraft Sales and Service, Inc., Boeing Field, Seattle, Washington; Aero Enterprises, Inc., Sky Ranch Airport, Denver, Colorado; Northwestern Aeronautical Corporation, Holman Field, St. Paul, Minnesota; U. S. Flying Services, Inc., Albert-Whitted Airport, St. Petersburg, Florida; Page Airways, Inc., Municipal Airport, Rochester, New York; and D. L. Grubb, John Rodgers Airport, Honolulu, Hawaii.

* * *

SUPERIOR ELECTRIC CATALOG

A 12-page catalog describing variable-voltage transformers, automatic voltage regulators and test units has been prepared by the Superior Electric Company, 713 Laurel Street, Bristol, Conn.

* * *

DE MAMBRO OPENS NEW HAMPSHIRE BRANCH

The De Mambro Radio Supply Co., Inc., have opened a branch at 1308 Elm Street, Manchester, N. H. Ted Von Hagen is manager of the new branch.

* * *

ELECTRO-VOICE CARDYNE CARDIROID DYNAMIC MICROPHONE BULLETIN

A 2-page bulletin (No. 131) describing the Cardyne cardioid dynamic microphone has been issued by Electro-Voice, Inc., Buchanan, Michigan.

Bulletin shows unidirectional polar patterns of the microphone providing wide-angle pickup at front.

* * *

METROPOLITAN ELECTRONIC CATALOG

A 16-page catalog describing signal generators, volt-ohm-milliammeters, signal tracers, multimeters, tube testers, capacitance-resistance bridges, decade boxes, oscillographs, and record changers, has been issued by Metropolitan Electronic and Instrument Co., 6 Murray Street, N. Y. 7, N. Y.

* * *

SUPREME PUBLICATIONS DIAGRAM INDEX

An index to six volumes of the "Most-Often-Needed Radio Diagrams" manuals has been published by Supreme Publications, 9 South Kedzie Avenue, Chicago 12, Illinois.

* * *

SOLAR MOLDED PAPER CAPACITORS NOW SIGNAL CORPS-AAF COLOR CODED

The Signal Corps-AAF color code has been adopted for the molded paper capacitors of the Solar Manufacturing Corp., 285 Madison Avenue, N. Y. 17, N. Y.

* * *

OLSON CATALOG

A 32-page catalog listing microphones, amplifiers, fluorescent fixtures, and as-



IS THE HERITAGE OF OXFORD SPEAKERS

1 OXFORD SPEAKERS, with their remarkable stamina assure that when used as replacements that they will not break down in normal or extended usage. The over a million units now in use as original installations are the very best guarantee of that statement.

2 OXFORD SPEAKERS have the new pressure-thread device, which holds the pole-piece against the magnet, increases sensitivity and prevents pole-piece decentering. This new development is but one of many improvements which assure the jobber of long and trouble-free installations meeting the most exacting type specification.

3 OXFORD SPEAKERS are designed for handling the maximum power input in relationship to their size, and further embody response curves which permit the speaker to be used in radio receivers of quality.

Until the war, the loudspeaker was comparatively undeveloped from the first ineffectual unit which made its appearance in the middle 1920's. By consistent research in this highly complicated field, OXFORD engineers have improved almost every part until there is little resemblance, except in exterior appearance, between the OXFORD SPEAKER of today and the pre-1942 unit.

It will be found that the OXFORD SPEAKER can withstand greater overloads for longer periods, and provide cleaner, better reproduction than was believed possible just a short five years ago.



OXFORD RADIO CORPORATION
3911 SOUTH MICHIGAN AVE., CHICAGO

sorted parts has been published by Olson Radio Warehouse, 73 East Mill Street, Akron, Ohio.

* * *

ERNEST L. WARD ELECTED SPRAGUE ELECTRIC VICE PRESIDENT

Ernest L. Ward has been elected vice president of the Sprague Electric Company, North Adams, Mass.

* * *

MALLORY MYE ENCYCLOPEDIA

The 5th edition of the MYE servicing encyclopedia containing over 4,000 replacement listings has been published by

P. R. Mallory, Inc., Indianapolis, Ind. Replacement data covers controls, capacitors and vibrators.

* * *

BUNTING NOW GARRARD S-M

Lee Bunting has been appointed sales manager of Garrard Sales Corporation, New York, American agents for the Garrard automatic record changer.

Mr. Bunting was formerly sales manager of the record changer division of Maguire Industries, Inc.

* * *

DON E. CORSON JOINS SOLAR


Don E. Corson has been appointed manager of the special products division of Solar Manufacturing Corporation.

NEW PRODUCTS

STAR TESTER

A volt-ohm-milliammeter, model M 11 Star Tester, has been announced by Star Measurements Company, 442 East 166th St., New York 56, N. Y. Voltage ranges are provided up to 1,000 volts on both a-c and d-c. Current ranges up to one ampere and resistance ranges up to five megohms are also incorporated. Calibrated db scales are provided for measurements as high as 54 db; zero power level is based on a 6 mw level in a 500-ohm line.

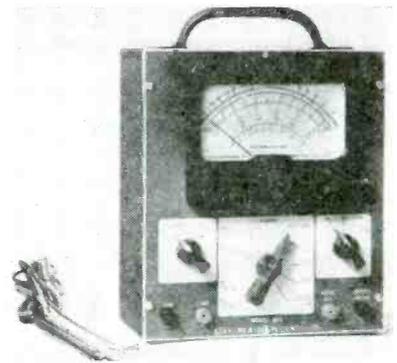Instrument features a 4½", 400 micro-ampere Marion meter. Entire instrument weighs 4 pounds.




* * *

SPECO P-A MIXER

Max-Mixer, providing the use of additional microphone inputs to amplifiers, has been released by Special Products Company, Silver Spring, Maryland.

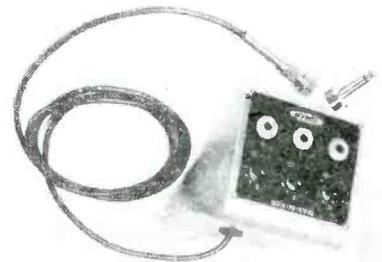Mixer permits plugging in of one, two or three microphones.



* * *

ALTEC LANSING AMPLIFIERS

A-c/d-c 4-watt amplifiers, A-319A and A-319B, have been announced by Altec Lansing Corporation, 1161 North Vine St., Hollywood, Calif.


A-319A amplifier has a balanced bridging-input transformer with a 5000-ohm input designed for bridging across 250-500-600 ohm lines without requiring isolating transformers.

The A-319B amplifier has a high impedance input for crystal pickup use.

Both amplifiers have an adjustable low-frequency bass boost. The A-319A has an adjustable high-frequency treble boost to compensate for line losses. A-319B has an adjustable high-frequency control to eliminate needle scratch. Amplifiers have inverse feedback taken from a tertiary winding on the output transformer thus leaving the output ungrounded.

Nominal output load impedance, 8 Ω

AMERICAN CAPACITORS

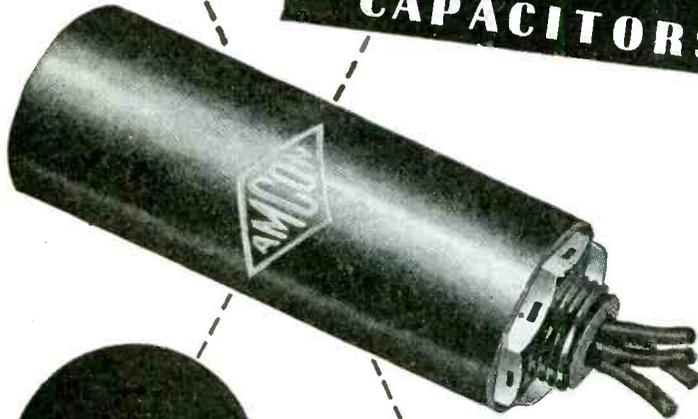

All standard types,
Write for the new
Amcon catalog.

Amcon precision engineering
means dependable, unfailing
Capacitor performance.



AMERICAN CONDENSER CO.

4410 N. Ravenswood Ave., Chicago 40, Illinois



RAYTHEON

MANUFACTURING COMPANY

Excellence in Electronics

RADIO RECEIVING TUBE DIVISION

NEWTON, MASSACHUSETTS CHICAGO

"...and put Raytheon tubes in my set please." That's the customer specifying "Raytheon"—a name he knows to be synonymous with quality and dependability. Stock Raytheon tubes to keep your customers happy; to keep your business growing.

15 ohms. Tubes include 6SJ7, 6J5, (2) 25L6, (2) 25Z6.



NATIONAL UNION VIBRATORS

Universal type auto vibrators, Univibes, standardized to a minimum of 8 types, that are said to serve the replacement demands of over 2500 different models of auto receivers, have been announced by National Union Radio Corporation, Newark, New Jersey.



JFD CEMENTS AND SOLVENTS

JFD Manufacturing Co., 4117 Fort Hamilton Parkway, Brooklyn 19, N. Y., has reorganized its line of radio cements, solvents and carbon tetrachloride. Each of these items will come packaged in the four most popular sizes. These are the 4 ounce, 8 ounce, 16 ounce, and the 1-gallon sizes. Line of cements will come with the brush affixed to the metal cap.



G. E. A-M/F-M TUNING TUBE

An electron-ray indicator, 6AL7-GT, that is said to be particularly useful in f-m sets, has been announced by the tube division of G. E.

In this tube patterns appear on a fluorescent screen located near the end of the glass bulb. The 6AL7-GT employs a translucent screen, or target, consisting of a transparent disc on which the fluorescent material is deposited. The fluorescent pattern can be viewed through the screen.

The translucent-type screen enables all other tube electrodes such as heater,



WEBSTER Model 55
PLAYS THROUGH YOUR RADIO

It's a natural for teenagers—and for grown-ups as well. An Automatic Record Changer on a harmonizing base. Just the thing for Play Room or Living Room or to play favorite recordings thru "the other radio."

EASY TO CONNECT

Model 55 can be quickly connected to most radios—simply plug it in. Comes complete with cords and plugs.



The Choice of Music Lovers

WEBSTER CHICAGO
5610 Bloomingdale Avenue, CHICAGO 39, ILLINOIS
32 years of Continuous Successful Manufacturing

cathode, deflecting plates, etc., to be behind the target and out of sight. In previous tubes with reflecting-type targets it has been necessary to locate cathode and deflecting plates in front of the screen, thereby making it necessary to mask out the center of the screen.

By controlling the bias of the space-charge grid the target current and pattern brightness can be affected. Six volts negative grid bias is sufficient to black-out completely the pattern if the target voltage is less than 315 volts d-c.

On tune is indicated when two halves of a pattern which appear on the screen at the end of the tubes are aligned. Deviation from the proper tuning condition

on one side of resonance will raise one edge of the pattern and deviation on the other side of the resonance will lower the pattern edge.

In receivers where squelch voltage is available the pattern can be made to disappear completely between stations thus providing a difference between on tune and between-station presentation.

RCA TUBES

Four new tubes have been announced by the tube department of RCA.

Two of these new tubes—1P42 and 3C33—are for industrial control applications; the other two—12AU7 and 35B5

(Continued on page 40)



UNIMETER

This unit fulfills an extremely important need for general utility portable service equipment. It has wide range coverage for both a-c and d-c measurements of voltage, current measurements on d-c and the popular ranges on resistance.

The UM-3 is designed to clearly indicate all the functions which aid in the prevention of application of high voltages when preparing for current or resistance measurements. Other G-E units for better servicing include: CRO-5A Oscilloscope, PM-17 Electronic Voltmeter, YYW-1 High Voltage Multiplier.

For details write:

General Electric Company,
Electronics Department,
S-6411, Syracuse 1, New York.

Electronic Measuring Instruments



GENERAL ELECTRIC

177-E3

UM-3

NEW PRODUCTS

(Continued from page 39)

—are additions to the miniature tube family.

The 1P42 is a very small *head-on* type of high-vacuum phototube. Diameter $\frac{1}{4}$ ".

Semi-transparent cathode surface is sensitive to light sources predominating in blue radiation.

The 3C33 power amplifier contains two, high-perveance triode units in an envelope. Has a 12.6-volt heater.

The 12AU7 is a small, twin-triode amplifier having characteristics which are very similar to those of the larger types 6SN7-GT and 12SN7-GT.

Mid-tapped heater permits operation from either a 6.3- or a 12.6-volt supply.

The 35B5 is a beam power amplifier and is for use in the output stage of a-c/d-c receivers. It is capable of providing 1.5 watts output.

TRIPLETT TRANSCONDUCTANCE READING TUBE TESTER

A tube tester, 2425, providing microhm (dynamic mutual conductance) readings has been announced by Triplett Electrical Instrument Co., Bluffton, Ohio. Transconductance readings are made possible through measurements directly proportional to gm.

Short and open tests of every tube element.


Metal case, 10" x 10" x 5 $\frac{3}{4}$ ". For counter or portable use.



* * *

AMCON PLASTIC CAPACITORS

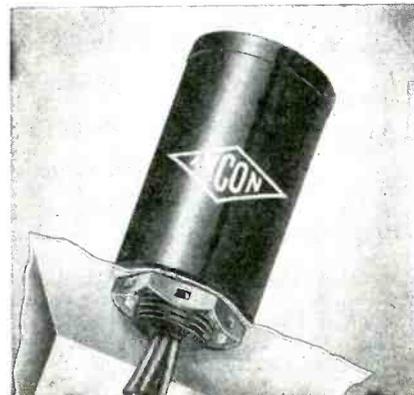Plastic case capacitors, Amcon Little PL, $\frac{2}{8}$ " high and $\frac{1}{8}$ " diameter, have been announced by the American Condenser Company, 4410 N. Ravenswood Ave., Chicago 40, Illinois.



Presenting The New Improved
JFD REMOTE-O-CABLE REPLACER

Length 10 $\frac{1}{2}$ in.,
Width 4 $\frac{1}{2}$ in.,
Height 13 in.,
Shipping Weight
29 $\frac{3}{4}$ Pounds.

The Most Efficient Auto Radio Tuning Cable-Servicing Machine in Use Today!

1. SWEDGES SHAFTING TO PREVENT UNRAVELLING.
2. CUTS SHAFTING TO EXACT LENGTH.
3. REPLACES OLD FITTINGS ON NEW SHAFTING.
4. CASING GROOVE MAKES CUTTING EASY.

Service Men's Net Cost \$67.52

J. F. D. MANUFACTURING CO., 4111 FT. HAMILTON PKY. W. BIRKIN, N. Y.

PHONO PORTABLE For A-C / D-C / Battery

(See Front Cover)

THE ADVENT OF MINIATURE tubes has permitted the development of many unique receivers and amplifiers. Recently, for instance, Capitol Phonographs of Hollywood produced an a-c/d-c/battery portable phono, model U-24, using a 1S5 diode-pentode as a triode first-stage voltage amplifier feeding a 3Q4 battery-power pentode and a 50B5 line-powered beam-power tube in parallel.

This 3-way portable, with a battery life of approximately 250 hours when operated intermittently, features a double-spring wind-up motor for battery and d-c line operation in addition a standard type a-c motor. The mechanical motor is capable of playing three ten-inch records with one winding.


A crystal pickup feeds a 1/2-megohm volume control through a 0.1-mfd isolating capacitor and bass attenuating equalizer. The equalizer consists of 10 megohms in parallel with a .00047-mfd capacitor, making the reactance equal the resistance at 33.6 cycles and causing this frequency to be attenuated about 91%. The 1S5 is operated without grid bias except for a small drop through the volume con-

trol. Plate load consists of 330,000 ohms in parallel with a 680,000-ohm power-stage grid leak and a series tone-control circuit with a 3-megohm resistor and .005-mfd capacitor.

The 3Q4 is used for battery operation only, obtaining its bias from 390 ohms in series with the B battery. Its filaments are operated in parallel for convenient 1 1/2-volt A supply. Audio power output is about 150 milliwatts. The 50B5 serves as the power output tube on line operation, delivering about 1 watt into the tapped output transformer. Full primary is used to match the higher impedance 3Q4, only part of the winding to match the 50B5. Filament power for the 1S5 is obtained by running the cathode current of 50 ma through the 1S5 and 120 ohms, the audio frequencies being effectively shunted by a 100-mfd capacitor.

A battery-line switch, with three circuits, opens B battery at negative terminal; opens B battery at positive terminal, connecting the plates and screen grids to the rectifier output; and opens A+ lead, disconnects the 3Q4 filament and connects the 1S5 filament to 120-ohm cathode bias resistor.

SPEED UP REPAIRS WITH THESE G-C AIDS!

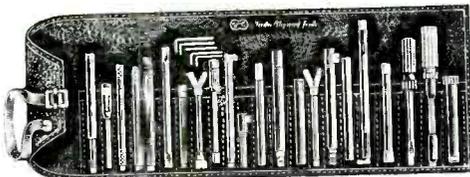


G-C PROFESSIONAL ALIGNMENT KIT

Here's a complete Alignment and Neutralization Kit in handy roll-type leatherette case that contains all the tools necessary to service any set—thirty finely machined tools that will save many man hours and do the job the professional way. The right tool is always at hand.

No. 5024..... List Price \$19.95

Send for Latest
G-C Catalog
No. 147

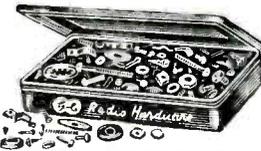

G-C HELL BOX

Thousands of assorted small parts such as screws, nuts, bolts, washers, clamps, lugs, radio and electric parts packed in neat metal box. A real treasure chest of these little parts the service man is always looking for.

No. 6500..... List Price \$4.00

G-C DeLUXE HARDWARE LABORATORY

Convenient steel rack, designed to hang on wall or stand on bench, contains over 2100 essential Electronic Hardware items, packed in 40 clear glass jars with screw caps. Ideal for laboratories, radio service shops, factories, experimental labs, home work shops, etc.

No. 6604..... List Price \$24.00



GENERAL CEMENT MFG. CO.
ROCKFORD, ILLINOIS

**Attention
GI JOE!**

Here's Your Opportunity to be First to

Start Your Own RADIO SERVICE SHOP

Complete Starting-in-Business
Package Stocks of


**TEST EQUIPMENT
TUBES, PARTS, TOOLS**

\$350 up

Act quickly! Meet the pent up demand for radio service. Turn your special service training into a profitable business of your own. No fuss. No worry. Here's everything you need—\$350 up. Details upon request! Write, wire or phone

TRIPLETT 666

"POCKET"
VOM **\$15.25**
A.C.-D.C. Volts
0-10-50-250-1000
0-10-100-500 D.C.Mills
0-300-250000 Ohms
Size 3x6x2

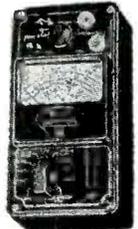

TRIPLETT 666H

\$20.00

Same as above plus
5000 V. ranges

Triplet 6305C Output Meter
Regular **\$24.50** Special .. **\$16.50**

0-1.5-6-15-60-150 Volts. 4000 OHM Impedance.
3" Meter 100 Microamp movement

Triplet 6065 .. Regular **\$16.67**
Voltage & Polarity Tester, Special **\$11.95**

Ideal for plant maintenance work! Checks 115-220-440 line at a glance! Indicates AC or DC visually! Indicates DC Polarity visually!

HALLICRAFTERS S-38



\$39.50

S-40 (replaces
S20R)

\$79.50

HAMMARLUND-HQ129X \$168

Speaker for HQ129X \$10.50

THE DEFIANT! \$83.95 Complete
25 Watt Sound System, wired, ready to use!



A reliable amplifier with 2 mike and 1 phono inputs, two 12" 20 oz. 13 watt PM speakers with 25' cables, two 12" walnut 7 ply wall baffles; one crystal microphone with table stand and 15' shielded cable.

THE CHALLENGER! \$69.95 Complete
25 Watt Sound System

Same as above except includes one speaker and baffle.

PHILCO BEAM OF LIGHT

Selenium Cell only, no holder **1.00**

20% deposit required on all C.O.D. orders. 2% transportation allowance on orders of \$25.00 or more accompanied by payment in full.

Write for
FREE CATALOG

RADIO
**RADIO SUPPLY &
ENGINEERING CO., Inc.**
126 SELDEN AVE. DETROIT 1, MICH.


SER-CUITS

(Continued from page 18)

adjustments permitting correct zero setting for all ranges through one front panel adjustment, range switch for multiplier values and five jacks for plug-in test-lead readings of a-c and d-c volts, ohms, amperes and milliamperes.

Measurement Ranges

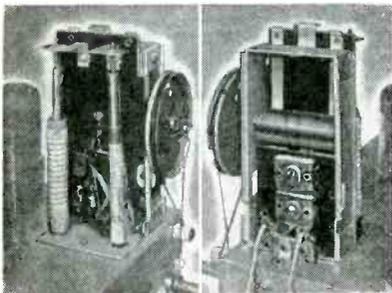Measurement ranges include: d-c volts . . . 0-3, 0-10, 0-30, 0-100, 0-300, 0-1000; a-c volts (a-f, 20-15,000 cps) 0-3, 0-10, 0-30, 0-100, 0-300; r-f volts (10 kc-300 mc) 0-3, 0-10,



The E-L Vario-Tuner. Left, coil side; right, trimmer side.

0-30, 0-100, 0-300; d-c current, 0-3 ma, 0-10 ma, 0-30 ma, 0-100 ma, 0-300 ma, 0-1000 ma, 0-10 amperes; resistance, 0-1000 ohms, 0-10,000 ohms, 0-100,000 ohms, 0-1 megohms, 0-10 megohms and 0-1000 megohms.

E-L Vario-Tuner

Many have requested additional information on the permeability-tuning type units that were mentioned in the editorial of the November issue of SERVICE. In Fig. 2 appears a recently-announced type Electronic Lab Vario-Tuner, that offers many of the features pointed out in the editorial. It consists of an r-f tuned unit and an oscillator section.

Tuner Features

Designed to cover the 540 to 1,620-kc range, with an i-f of 455, the r-f coil has an inductance of 220 microhenries $\pm 2\%$, tapped at 53 microhenries $\pm 2\%$. The r-f trimmer capacity is 30 mmfd. Approximately 12 mmfd is added to this trimmer by the input capacity of the r-f amplifier tube.

To tune, a ribbon drive mechanism is used.

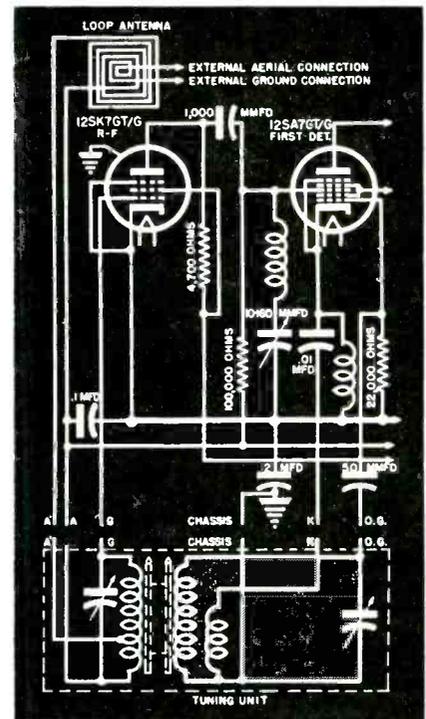


Fig. 2. Electronic Laboratories permeability tuning unit connected to input of an a-c/d-c receiver. Loop shown in circuit is also an E-L unit with an inductance of 147 microhenries.

SERVICE MEN! For Immediate Delivery

National brand 20x20 150-volt condensers, 70¢ each, 10 for \$5.95.

Power Transformer, Universal Mounting, 325-0-325--40/50 ma; 6.3V-2a; 5V-2a. \$3.25.

Fluorescent Light Filters, 70¢ each, 10 for \$5.95.

4 x 6 oval speakers—Alnico magnet, \$3.75 each.

Tinned aerial wire—100 feet, 40¢ each.

Write for our latest bulletin, Dept. S-1

Distributors of RADIO EQUIPMENT

CHIEF ELECTRONICS

104 MAIN STREET, POUGHKEEPSIE, N. Y.

In PHILADELPHIA — — — it's ALMO

TRY US FIRST!

ALMO RADIO COMPANY

509 ARCH STREET - PHILADELPHIA 6, PENNA.

Lo - 3 - 0513

Lo - 3 - 0513

TUBES—PARTS

RADIO DEALERS—SERVICEMEN

Send for our list of available tubes and repair parts. Sylvania, Tung-Sol, Ken-Rad.

M. V. MANSFIELD CO.

937 LIBERTY AVE.

PITTSBURGH 22, PA.

—YOU GET PERSONAL SERVICE AT SCENIC—

● MAIL ORDERS OUR SPECIALTY ●

SUPREME 565 v.t.v.m.	\$63.50	SIMPSON 215 v.o.m.	\$32.50
SUPREME 562 audolyzer	127.00	SIMPSON 260 v.o.m.	38.95
TRIPLETT 2405 v.o.m.	56.75	RCP 802-N tube & set tester...	59.50
TRIPLETT 2432 sig. gen.	88.50	DUMONT 274-5" scope.....	99.50
McMURDO-SILVER "Vomax" ..	59.85	DUMONT 208-B 5" scope.....	235.00
McMURDO-SILVER "Spart" ..	39.90	ELECTRONIC Design Voltohmmyst	52.00

● NEW CATALOG AVAILABLE ON REQUEST ●

25% deposit should accompany C.O.D. orders.

SCENIC RADIO & ELECTRONICS CO.

53 PARK PLACE

NEW YORK 7, N. Y.

J. V. Duncombe Co.

WHOLESALE DISTRIBUTOR

ELECTRONIC EQUIPMENT, TUBES and PARTS

1011 West 8th Street

Phone: 23-546

Erie, Pa.

ALL NATIONALLY KNOWN RADIO PARTS—AMATEUR SUPPLIES, NATIONAL UNION, SYLVANIA AND RCA TUBES

GET TEST EQUIPMENT AT:

SUN RADIO
& ELECTRONICS CO., Inc.

122-124 QUANE ST. - NEW YORK 7, N. Y. - BRclay 7-1640

WHEN YOU CHANGE YOUR ADDRESS

Be sure to notify the Subscription Department of SERVICE at 52 Vanderbilt Ave., New York 17, N. Y., giving the old as well as the new address, and do this at least four weeks in advance. The Post Office Department does not forward magazines unless you pay additional postage, and we cannot duplicate copies mailed to the old address. We ask your cooperation.

OUR NEW CATALOG IS READY

PLUGS

PILOT LIGHT SOCKETS

JACKS


BARRIER TERMINAL STRIPS

HARDWARE, etc.

The Herman Smith Catalog is a volume that belongs in the "stock" of every dealer and serviceman. You'll find hundreds of items . . . many of the hard-to-find variety. All first quality . . . all fully guaranteed. Send for your FREE copy today.

HERMAN H. SMITH, Inc.

405 44th Street, Brooklyn 20, N. Y.

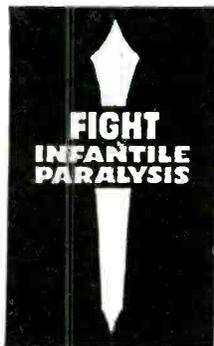

MARCH OF DIMES
JANUARY 15-30

SERVICING HELPS

(Continued from page 30)

that the avc feeder is common to both the r-f and i-f circuits. Therefore, the first point to check is the .2-mfd bypass capacitor. It is suggested that the capacitor in the receiver be removed from the circuit when checking.

The next point to check is the value of resistance in this circuit. An appreciable increase in resistor value, more than 15%, may affect the receiver operation adversely.

The .2-mfd screen grid bypass capacitor should be checked next. The use of a high value of screen grid bypass, say 5 mfd or more, will sometimes improve the response. You should use a capacitor with a voltage rating equal to the plate voltage, since surges may blow out a smaller voltage rated capacitor.

Since the cathodes of the r-f and i-f amplifiers are tied together, a defective bypass at this point would also induce oscillation. In addition, an open interstage noise suppressor would cause weak signals, or no signals at all.


In these days of tube shortages, it is interesting to note that the three 56 tubes (one not shown is the first audio stage) could be replaced with a single duo-diode-triode, such as the 6R7.

R-C AMPLIFIER


(Continued from page 14)

source is a diode, which itself draws current, the fractional current drain of the tube will not cause distortion. The high plate-load resistance coupled with the low-plate voltage supply would prevent any appreciable current drain with resultant damage to the tube. This particular type of tube is designed for a high value grid resistance.

6-SPEAKER PHONO

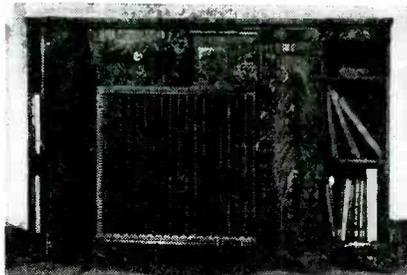

British phono model, the London Reproducer, recently introduced in this country. Features a 4-stage push-pull amplifier with three sets of 6J5 triodes and a pair of PX25 outputs. In the first three stages, negative feedback is used. Volume control between the second and third stages is provided by twin resistance-capacitance circuits shunted across the output of the second stage, plate to plate, the capacitive portions of the network providing bass compensation at low-volume levels. Speaker system consists of six 12" p-m units connected in parallel.

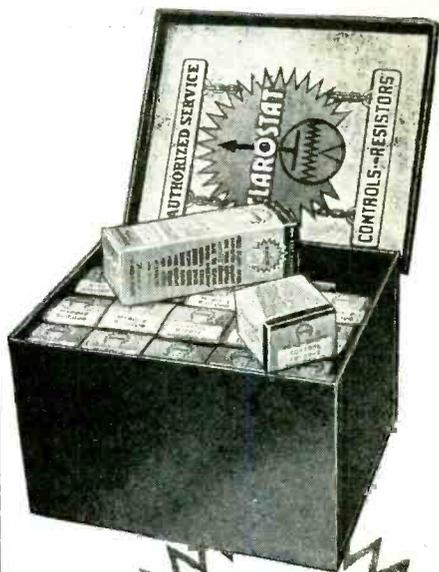

You asked for it!

SERVICEMAN'S

KIT No. 4

★ With this kit you're ready to service upwards of 95% of the standard radios. And you can keep the kit complete by re-ordering individual items.

CONTROLS and SWITCHES

Kit contains 17 selected volume and tone controls. Most popular ohmages and taps. Also 8 Ad-A-Switches—both s.p. and d.p. types. Plus 4 Glasohms (glass-insulated flexible resistors).

PLUS—DATA and PLAQUE

Packed in a neat, sturdy, green-lacquered steel cabinet (no advertising or outside label). Kit includes Clarostat Volume Control Selector and Authorized Service plaque. A big \$32.15 value; "special" to you at only \$17.79!

★ Ask Our Jobber . . .

Ask for this "special"—get yours before the supply runs out. If you're not acquainted with the nearest Clarostat jobber, write us and we'll bring you together.



CLAROSTAT MFG. CO., Inc. · 285-7 N. 6th St., Brooklyn, N. Y.

Order from LAKE!
You'll Make No Mistake!

RADIO CABINETS & PARTS

NOW AVAILABLE!



Postwar
2 Post
RECORD-
CHANGER

With luxuri-
ous brown
leather-
ette portable
case. 15" L. x


35" W. x 10" D. Latest electronic develop-
ments make this modern record-changer the
finest on the market today!

Changer \$18.50
Cabinet for same \$8.95

DE LUXE RECORD-CHANGER and AMPLIFIER CASE

De luxe changer case with ample room for am-
plifier. Overall dimensions: 20" L. x 16" W. x
10" H. Sturdily built of 3/4" plywood, de luxe
brass hardware throughout. Inside dimensions:
15 1/2" L. x 14 1/2" W. x 9 1/2" H

Net \$12.95

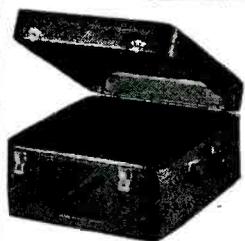

DELUXE
PHONO
CABINET

Covered in lux-
urious, genuine
brown leather-
ette, has de-
luxe brass

hardware throughout, made completely of ply-
wood with brown plastic handle, has padded
top and bottom. Motor board 14" x 14 1/2".
Overall dimensions 16" L x 15" W x 8" H.

Your net price \$8.95



Portable Phono-
graph Case of sturdy
durable plywood, in
handsome brown
leatherette finish.
Inside dimension
16 1/2" long, 14" wide,
9 1/2" high. Has blank
motor board. As il-
lustrated. Specially
priced at

\$6.95

Also blank table cabinets of walnut veneer in
the following sizes, with speaker opening on
left front side: (*Note: * has center speaker
grill.)

4 1/2" - 8 1/2" L x 6 1/2" H x 4" D	\$1.95
4 1/2" - 10 1/2" L x 8 1/2" H x 6" D	\$2.75
4 1/2" - 12 1/2" L x 10 1/2" H x 8" D	\$3.25
4 1/2" - 14 1/2" L x 12 1/2" H x 10" D	\$4.50

*Speaker Opening in center of front side.

All types of radio cabinets and parts are
available at Lake's Lower prices. A large
stock is listed in our catalog.

SERVICEMEN—RETAILERS

Write today for our new, illustrated
16-page catalog NR-116. It's free. Get
on our mailing list. Dept. D.

Write for our SPECIAL CATALOG on micro-
phones, amplifiers and sound equipment.

Lake Radio Sales Co.
615 W. Randolph Street
Chicago 6, Ill.

JOTS AND FLASHES

SERVICE SCHOOLS are now being run by many manufacturers to train distributor organization service manager and key service personnel the latest techniques in both business management and repair of modern equipment. Several distributors are, in turn, presenting similar sessions for local Service Men. Training certainly appears to be a key item in servicing today! . . . The need for special provisions for television antennas in new apartment houses was stressed by Dan D. Halpin, RCA television receiver sales manager at a recent meeting of the Building Owners and Managers Association in Philadelphia. Mr. Halpin described the recent installations of the RCA Antennaplex System in the Hotel Pennsylvania and Hotel New Yorker to solve a multiple-dwelling antenna problem. . . . Half-wave and doubler power supply systems are analyzed in a 16-page Mallory technical manual reprint now being distributed by the Federal Telephone and Radio Corporation. . . . Milo Radio and Electronic Corp. have been appointed exclusive distributors for the St. George Recording Corporation wire recorder. Unit, which can be hooked up to any amplifier, also plays standard records. . . . Del Wake-man has resigned as advertising manager of the Magnavox Company, Ft. Wayne, Indiana and joined Ekco Products Company, Chicago, as advertising manager. . . . A special television demonstration room has been installed by the Fair Store in Chicago. Up to eleven receivers can be demonstrated in this room. . . . William Carduner, president of the British Industries Corporation, recently sailed to England on the Queen Elizabeth. . . . A 3-color window display promoting tubes has been prepared by Sylvania Electric Products Co., Inc. . . . Frank Folsom, executive vice president of RCA, in charge of RCA Victor Division, has received a certificate of appreciation from the War Department. . . . Newark Electric Company has acquired additional office and warehouse facilities at 242-50 W. 55th Street, New York City. . . . Edward Miller is now field representative for Snyder Manufacturing Company, Philadelphia. . . . Walter F. Marsh, sales manager of Allied Radio Corporation, has been delivering talks on wire recorders before various associations and clubs. . . . Folders describing intra-video antenna systems and television receivers have been released by the Telicon Corporation, 857 Madison Avenue, New York 21, N. Y. . . . Myron J. Morris is now manager of the service division of ECA. . . . A listing of exact duplicate controls appears in the November issue of the "Centralab Jobber Outlook". . . . Paul K. Povlsen has been named assistant to the president of the Galvin Mfg. Company. Mr. Povlsen was formerly vice president in charge of production and engineering for the J. I. Case Company, Racine, Wisconsin. . . . Charles Friedman has been named sales manager of the communications division, Radio Receptor Company, Inc., 257 W. 19th Street, New York. . . . Employees of Meck Industries received a "cost-of-living" increase recently. . . . Robert E. Sargent, Paul Nichols and Walter C. Hustis, formerly with Jefferson-Travis, have formed a sales representative company, Land-C-Air Sales, Inc., 14-16 Pearl Street, New York.

ADVERTISERS IN THIS ISSUE

SERVICE INDEX—DECEMBER, 1946

AEROVOX CORPORATION	34
Agency: Austin C. Lescarboursa & Staff	
ALMO RADIO CO.	42
AMERICAN CONDENSER CO.	38
Agency: Carobell & Royola	
AMERICAN PHENOLIC CORP.	21
Agency: Burton Browne, Advertising	
ARROW SALES, INC.	32
THE ASTATIC CORPORATION	29
Agency: Wearstler Advertising, Inc.	
BURSTEIN-APPLEBEE CO.	28
Agency: Frank E. Whalen Advertising Co.	
CAPITOL RADIO ENGINEERING INSTITUTE	33
Agency: Henry J. Kaufman & Associates	
CHERRY RIVET CO.	27
Agency: Dana Jones Co.	
CHIEF ELECTRONICS	42
Agency: The Graphic Co.	
CLAROSTAT MFG. CO., INC.	43
Agency: Austin C. Lescarboursa & Staff	
CONCORD RADIO CORP.	26
Agency: E. H. Brown Adv. Agency	
CORNELL-DUBILIER ELECTRIC CORP.	Inside Front Cover
Agency: Reiss Advertising, Inc.	
CORNISH WIRE CO., INC.	28
Agency: Hart Lehman, Advertising	
DRAKE ELECTRIC WORKS, INC.	32
Agency: William Hoffman & Associates	
J. V. DUNCOMBE CO.	42
GENERAL CEMENT MFG. CO.	41
Agency: Turner Adv. Agency	
GENERAL ELECTRIC CO.	35, 40
Agency: Maxon, Inc.	
HOLLANDER RADIO SUPPLY CO.	36
Agency: Turner Adv. Agency	
JENSEN MANUFACTURING CO.	6
Agency: Burton Browne, Advertising	
J.F.D. MFG. CO.	40
Agency: Bergman-Jarrett Co.	
KEN-RAD DIVISION GENERAL ELECTRIC	1
Agency: Maxon, Inc.	
LAKE RADIO SALES CO.	44
Agency: Sander Rodkin Adv. Agency	
LIFETIME SOUND EQUIPMENT CO.	34
Agency: The Miller Agency Co.	
MAGUIRE INDUSTRIES, INC.	19
Agency: City Adv. Agency	
M. V. MANSFIELD CO.	42
MURRAY HILL BOOKS, INC.	25
Agency: The Harry P. Bridge Co.	
NATIONAL UNION RADIO CORP.	Back Cover
Agency: Hutchins Advertising Co., Inc.	
NEWCOMB AUDIO PRODUCTS CO.	32
Agency: Stevens-Hall, Advertising	
OXFORD RADIO CORP.	37
Agency: Signal Corp.	
RADIO CITY PRODUCTS CO., INC.	5
Agency: Reiss Advertising, Inc.	
RADIO CORPORATION OF AMERICA	15
Agency: J. Walter Thompson Co.	
RADIO SUPPLY & ENGINEERING CO.	41
Agency: Karl G. Behr Adv. Agency	
RAYTHEON MFG. COMPANY	38
Agency: Burton Browne, Advertising	
JOHN F. RIDER PUBLISHER, INC.	4
Agency: Lansford F. King, Advertising	
SCENIC RADIO & ELECTRONICS CO.	42
SIMPSON ELECTRIC CO.	Inside Back Cover
Agency: Kretzker & Melton, Inc.	
HOWARD W. SAMS CO., INC.	3
Agency: The Altkin-Kynett Co.	
HERMAN H. SMITH, INC.	43
Agency: Shappe-Wilkes Inc.	
SPRAGUE PRODUCTS CO.	7
Agency: The Harry P. Bridge Co.	
STANDARD TRANSFORMER CORP.	17
Agency: Burnet-Kuhn Adv. Co.	
SUN RADIO & ELECTRONICS CO.	42
Agency: Bass & Weber Co., Inc.	
SUPERIOR INSTRUMENTS CO.	23
Agency: Bass & Weber Co., Inc.	
SUPREME INSTRUMENTS CORP.	28
Agency: O'Callahan Adv. Agency, Inc.	
SYLVANIA ELECTRIC PRODUCTS INC.	8
Agency: Newell-Emmett Co.	
TECHNICAL APPLIANCE CORP.	26
Agency: Austin C. Lescarboursa & Staff	
TRIPLETT ELECTRICAL INSTRUMENT CO.	35
Agency: Western Advertising Agency, Inc.	
UNITED TRANSFORMER CORP.	31
Agency: Shappe-Wilkes Inc.	
WARD-LEONARD ELECTRIC CO.	36
Agency: Henry H. Teplitz, Advertising	
WEBSTER-CHICAGO CORP.	39
Agency: William Hoffman & Associates	



**This Is
Good
News!**

... our greatly increased production on Simpson Model 260 makes it available to you NOW at your jobber's

The Simpson 260 is easily the world's most popular set tester for television and radio servicing. You cannot touch its precision, its useful ranges, or its sensitivity in any other instrument selling for the same price or even substantially more.

It has been a long time since we have been able to produce enough 260's to meet the demand, because the 260 has consistently out-sold every other remotely similar test instrument. The reason is simple: it out-performs and out-values them all. Simpson advanced engineering and unyielding standards of quality and precision manufacture enable it to *stay* accurate under conditions ordinary instruments cannot survive.

Incidentally—production on other Simpson instruments is clearing, too. We feel confident that it will not be long before you can buy those Simpson instruments you have waited for.

Ask your jobber for the Simpson 260—he has it now!

SIMPSON ELECTRIC COMPANY
5200-5218 W. Kinzie St., Chicago 44, Ill.

Simpson

INSTRUMENTS THAT STAY ACCURATE

**SIMPSON 260, HIGH SENSITIVITY SET TESTER
FOR TELEVISION AND RADIO SERVICING**

Ranges to 5000 Volts—Both A.C. and D.C.
20,000 Ohms per Volt D.C.
1000 Ohms per Volt A.C.

At 20,000 ohms per volt, this instrument is far more sensitive than any other instrument even approaching its price and quality. The practically negligible current consumption assures remarkably accurate full scale voltage readings. Current readings as low as 1 microampere and up to 500 milliamperes are available.

Resistance readings are equally dependable. Tests up to 10 megohms and as low as 1/2 ohm can be made. With this super sensitive instrument you can measure automatic frequency control diode balancing circuits, grid currents of oscillator tubes and power tube, bias of power detectors, automatic volume control diode currents, rectified radio frequency current, high- μ triode plate voltage and a wide range of unusual conditions which cannot be checked by ordinary servicing instruments. Ranges of Model 260 are shown below.

Price, complete with test leads \$38.95
Carrying case 5.55

Volts D.C. (At 20,000 ohms per volt)	Volts A.C. (At 1,000 ohms per volt)	Output
2.5	2.5	2.5 V.
10	10	10 V.
50	50	50 V.
250	250	250 V.
1000	1000	1000 V.
5000	5000	5000 V.

Milli-amperes	Micro-amperes	Ohms
D.C.		
10	100	0-1000 (12 ohms center)
100		0-100,000 (1200 ohms center)
500		0-10 Megohms (120,000 ohms center)

(5 Decibel ranges: -10 to +52 DB)

ASK YOUR JOBBER


UNIVIBE... *The Universal Vibrator!*

8 TYPES
SERVICE
OVER 2500
AUTO
RADIO
RADIO



N. U. AUTO RADIO VIBRATORS ARE BUILT FOR ENDURANCE!

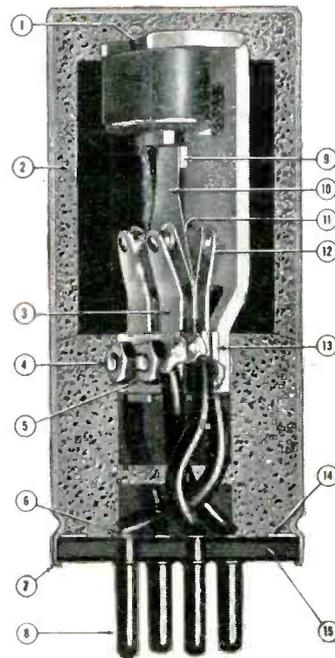1. Welded pole pieces for life-time adjustment accuracy.
2. Snug fitting synthetic sponge insulation for quiet operation.
3. Spot-welding of fingers, in contact against each other and the center reed, reduces voltage drop in center reed assembly.
4. Vibration proof adjustment by means of double-screw stack.
5. Pressure plate on top of stack keeps stack tight under tension over wide ranges of temperature.
6. Extra flexible roped wire leads eliminate strain and weakening.
7. Metal can, spun at bottom, seals vibrator against dust and dirt.
8. Plated pins assure minimum contact resistance.
9. Face of center reed weight is surface-ground to improve magnetic coupling.
10. Center reed uniformly stressed to prevent breakage.
11. Specially tempered reed and side contact arms.
12. Corrosion resistant silver-plated side contact arms.
13. Precision ground bakelite spacers for structural and dimensional stability.
14. Steel ring, molded into shock mount, centers and holds vibrator upright when can is sealed.
15. Neoprene wafer in hermetically sealed vibrators effectively seals vibrator against atmospheric pressure changes and moisture.



Typical Synchronous Vibrator Construction

NEW LINE COVERS 97% OF ALL VIBRATOR REPLACEMENTS

UNIVIBE—the complete 8-model vibrator line—covers the replacement needs of over 2500 auto radio models! Provides quick, easy replacement of worn out vibrators in 182 makes of auto radios, as old as 1936!

Think of it—97% service coverage with only 8 fast-moving numbers—every one a repeat profit producer!

Yes, Univibe is right at the top in quality. Well known “balanced resonance” design, of extra heavy duty construction, means 33% longer vibrator life by actual test.

Here is another money-making radio parts line for National Union dealers.

For immediate delivery order Univibes today from your N. U. Distributor.

NATIONAL UNION RADIO CORPORATION, NEWARK 2, N.J.

NATIONAL UNION RADIOS, TUBES AND PARTS

Receiving Tubes • Transmitting Tubes • Special Purpose Tubes • Cathode Ray Tubes • Radio Sets • Phototubes
Panel Lamps • Flashlight Bulbs • Ballasts • Volume Control • Condensers • Batteries • Auto Vibrators