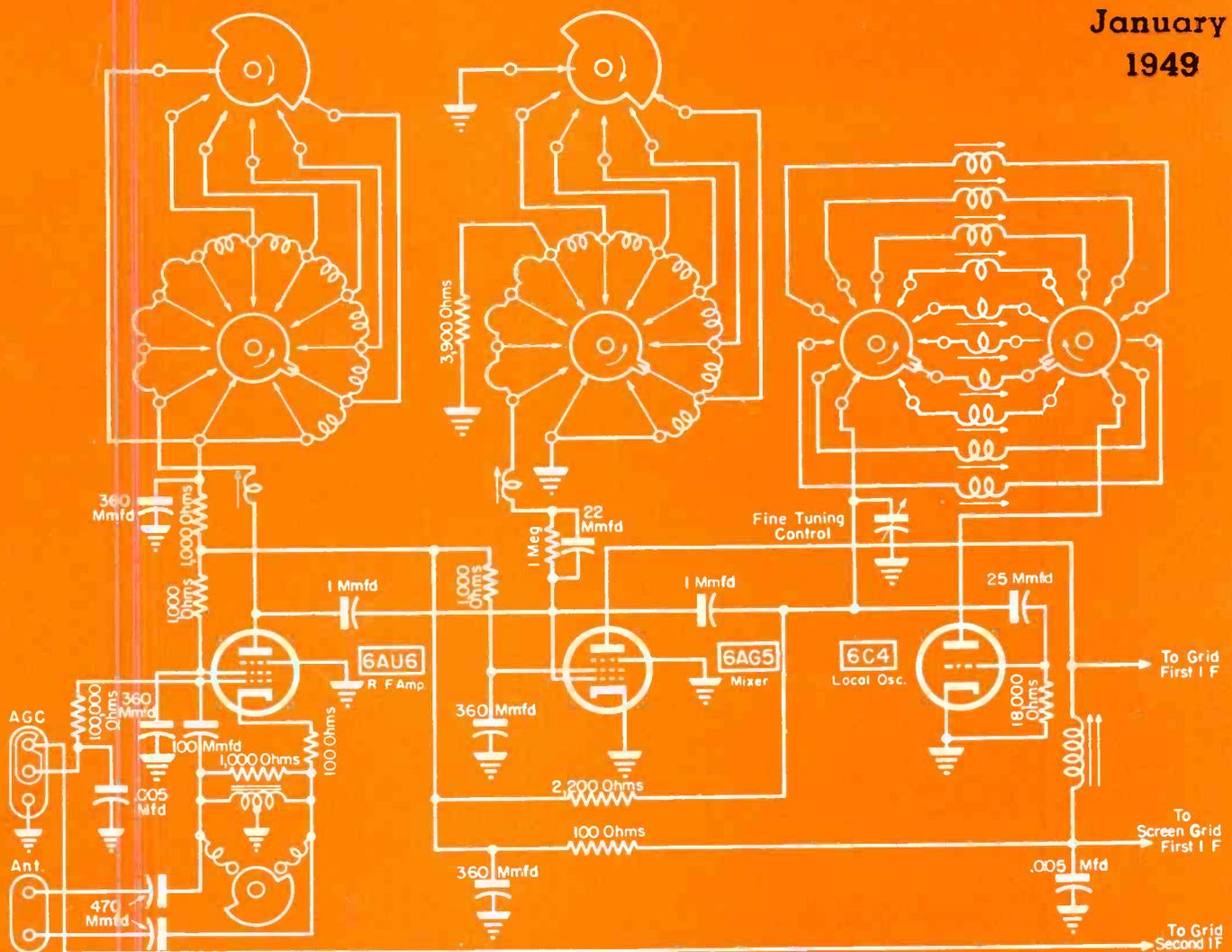


SERVICE

January
1949





Front end of a 7" direct-view twin-speaker TV receiver featuring the intercarrier-sound system.

[See page 2]

save 1,000 service hours
with this complete, up-to-date

c-d capacitor manual

For Radio Servicing

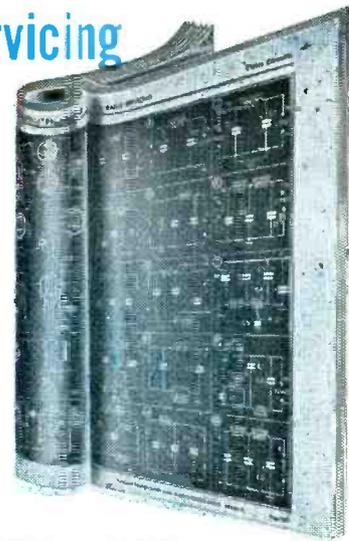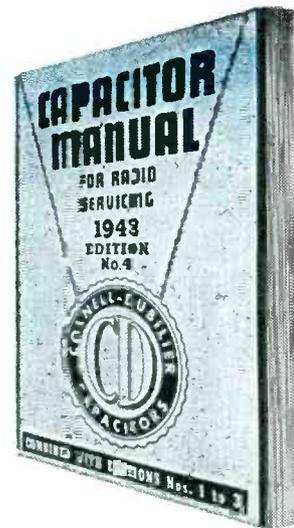

4th Edition by popular request!
OVER 400 PAGES!

Pocket Size—Accurate Parts Tables—Easy Circuit Diagrams

Why hunt and peck for the right capacitor replacement? This complete manual shows you the correct unit at a glance. Simplified tables and diagrams help you service any new or old radio set *faster, easier, more profitably*. You can save 1,000 hours or more in service time. Call your Cornell-Dubilier jobber now or mail coupon for your copy. List price \$.50. Cornell-Dubilier Electric Corporation, Dept S19, South Plainfield, N. J. Other Plants in New Bedford, Worcester, and Brookline, Mass., and Providence, R. I.

Manufacturer and Model No.	C-2K Type	CAPACITY	MTC					Rct's	Pct's	A-200 200K
			20	25	30	35	40			
ALLIED RADIO CORP. C-2K 10000	10	10000	100	100	100	100	100	100	100	
10104C	10	10000	100	100	100	100	100	100	100	
10104D	10	10000	100	100	100	100	100	100	100	
10104E	10	10000	100	100	100	100	100	100	100	
10104F	10	10000	100	100	100	100	100	100	100	
10104G	10	10000	100	100	100	100	100	100	100	
10104H	10	10000	100	100	100	100	100	100	100	
10104I	10	10000	100	100	100	100	100	100	100	
10104J	10	10000	100	100	100	100	100	100	100	
10104K	10	10000	100	100	100	100	100	100	100	
10104L	10	10000	100	100	100	100	100	100	100	
10104M	10	10000	100	100	100	100	100	100	100	
10104N	10	10000	100	100	100	100	100	100	100	
10104O	10	10000	100	100	100	100	100	100	100	
10104P	10	10000	100	100	100	100	100	100	100	
10104Q	10	10000	100	100	100	100	100	100	100	
10104R	10	10000	100	100	100	100	100	100	100	
10104S	10	10000	100	100	100	100	100	100	100	
10104T	10	10000	100	100	100	100	100	100	100	
10104U	10	10000	100	100	100	100	100	100	100	
10104V	10	10000	100	100	100	100	100	100	100	
10104W	10	10000	100	100	100	100	100	100	100	
10104X	10	10000	100	100	100	100	100	100	100	
10104Y	10	10000	100	100	100	100	100	100	100	
10104Z	10	10000	100	100	100	100	100	100	100	

CORNELL-DUBILIER · WORLD'S LARGEST MANUFACTURER OF CAPACITORS

FILL IN — MAIL COUPON TODAY!

Cornell-Dubilier Electric Corp., Dept. S19
South Plainfield, New Jersey

Please rush my copy of the new C-D Capacitor
Manual for Radio Servicing. I am enclosing \$.50
money order () check () stamps ()

my jobber is

Name

Shop

Address

City Zone State




1910



1949

mica
dykanol
paper
electrolytic

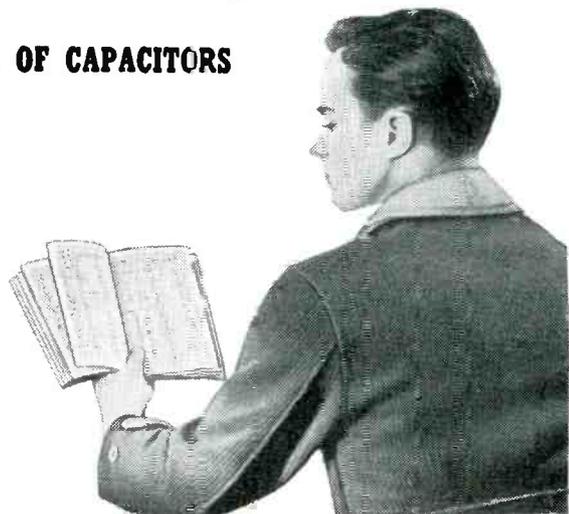

MAKES FRIENDS...AND KEEPS THEM!



GENERAL  ELECTRIC

181-MA2-8850

FIRST AND GREATEST NAME IN ELECTRONICS

RADIO · TELEVISION · ELECTRONIC
SERVICE

LEWIS WINNER
Editorial Director

F. WALEN
Assistant Editor

ALFRED A. GHIRARDI
Advisory Editor

	Page
Association News	34
FM Tuner Design. By John B. Ledbetter	10
Rotary Switch 7" TV Model. (Cover)	18
Ser-Cuits (Olympic, Hallicrafters and Farnsworth Models)	30
Servicing Helps. By P. M. Randolph	26
Ten Years Ago In Associations	34
TV Receiver Visual Alignment Techniques. By Lester L. Libby	14
TV Receiver Production Changes. By Donald Phillips	22
The Business Aspects of TV Installations. By Ira Kamen	12
Views and News. By Lewis Winner	9
 CIRCUITS	
Bendix 235 TV Chassis	15
Browning RV-10 FM Tuner	10
G. E. SPX-001 Variable Reluctance Preamp	26
Hallicrafters T-61/T-67 TV Chassis	32
Mallory Inductuner Converter Circuit	11
Meissner 8C FM Tuner	11
National NC-TV-7/NC-TV-7M (Cover)	20
Olympic RTU-3 TV Duplicator	30
Pilotuner (FM Tuner)	10
 COVER	
National NC-TV-7/NC-TV-7M	18
 SERVICING HELPS	
Preamp Equalizing Methods	26
 TV RECEIVER PRODUCTION CHANGES	
Adding AFC To Motorola VT71	24
Eliminating Howl in the G. E. 810 and 814	24
Eliminating Pulling at Top of the Picture in Admiral 30A1	24
Improving Audio IF Selectivity in G. E. 810	22
Substituting 6AU6 for 6AG5 in Admiral 30A1	24
Tuning Drive Revision in G. E. 810	22
Vertical Size Modification in G. E. 810	22
 Index to Advertisers	 48
 Manufacturers	
New Instruments . . . Accessories	47
New TV Parts . . . Accessories	45
News	43
Jots and Flashes	48

Entire contents Copyright 1949, Bryan Davis Publishing Co., Inc.



Published monthly by Bryan Davis Publishing Co., Inc.
52 Vanderbilt Avenue, New York 17, N. Y. Telephone MURray Hill 4-0170



Bryan S. Davis, President Paul S. Weil, Vice-Pres., Gen. Mgr. F. Walen, Secretary A. Goebel, Circulation Manager


Cleveland Representative: James C. Munn, 2253 Delaware Dr., Cleveland 6, Ohio. Telephone: ERlevew 1726

Pacific Coast Representative: Brand & Brand, 1052 W. Sixth St., Los Angeles 14, Calif. Telephone: MICHigan 1732
Suite 1204, Russ Building, San Francisco 4, Calif. Telephone: SUTter 1-2251

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

NOW! The Famous \$500 Photofact TELEVISION COURSE in Book Form!

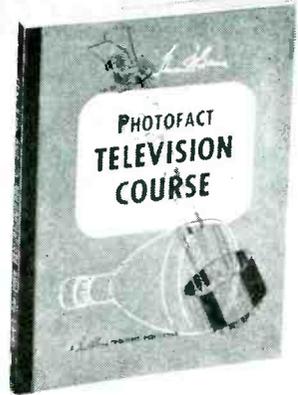Previously available only to Photofact subscribers—now published to answer the insistent demand of the entire Radio Industry




Now you can own the book that gives you a *complete, clear* understanding of modern TV principles, operation and practice. Previously available only in PHOTOFACT Folder Sets, this superb course has been bound in unified book form to meet an overwhelming demand from radio men in every branch of the industry. Written in clear, easy-to-follow language, profusely illustrated, packed with valuable up-to-the-minute data. Covers every phase of television—gives you the groundwork you *must* have to become a successful TV service technician. Bring your television knowledge up-to-date this easy, economical way. The PHOTOFACT Television Course is available at your jobber—order your copy today! Over 200 pages; fully illustrated; **\$300** sturdy binding, 8½ x 11". Only..

A "Must" for Everyone in Radio!

NEW! 1948 Automatic Record Changer Manual

New Volume 2 covers 45 models made in 1948, including new LP and dual-speed changers, plus leading Wire and Tape recorders. It's easy to service record changers when you have the PHOTOFACT Record Changer Manual handy. Complete, accurate data—based on analysis of actual equipment. Gives full change cycle data, information on adjustments, hints and kinks, complete parts lists, exclusive "exploded" diagrams. Have this time-saving, money-making book in your shop. Over 400 pages; de luxe **\$675** bound, 8½ x 11". Only.....

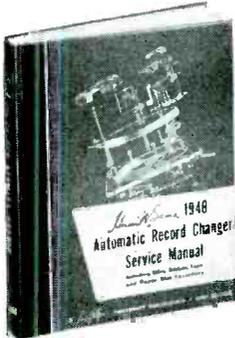

1947 EDITION. Volume 1, Automatic Record Changer Manual. Covers more than 40 different post-war changer models manufactured up to 1948. Includes full hard-to-get data on leading Wire, Ribbon, Tape and Paper Disc Recorders. 400 pages; fully illustrated; 8½ x 11", hard cover. Only.....**\$4.95**

NEW! Specialized Photofact Volumes



POST-WAR AUDIO AMPLIFIERS and Associated Equipment

This is the book that's wanted by custom-builders, audio men and sound engineers. Covers a wide variety of well-known audio amplifiers and FM and AM tuners, *plus* data on important wire and tape recorders. Presents a complete analysis of each unit. A "must" for custom-installers and for sound service specialists. 352 pages; fully illustrated; in sturdy binding, 8½ x 11". Only..... **\$3.95**



POST-WAR COMMUNICATIONS RECEIVER MANUAL

New! Invaluable to Amateurs and Short Wave Listeners. Complete technical analysis of more than 50 of the most popular communications sets on the market. An invaluable service aid, a perfect buying guide for purchasers of communications receivers. All data based on actual examination and study of each unit. 264 pages; profusely illustrated; durably bound, 8½ x 11". Only..... **\$3.00**



NEW! Photofact Volume 5

Latest addition to the famous PHOTOFACT Volume series—brings your file of post-war receiver service data right up to December 1948! Most accurate and complete radio data ever published—preferred and used daily by thousands of Radio Service Technicians. Everything you need for faster, more profitable servicing. Order Volume 5 today—keep ahead with PHOTOFACT—the *only* Radio Service data **\$18.39** that meets *all* your needs! In deluxe Binder...

- Vol. 5. Models from July 1, 1948 to Dec. 1, 1948
- Vol. 4. Models from Jan. 1, 1948 to July 1, 1948
- Vol. 3. Models from July 1, 1947 to Jan. 1, 1948
- Vol. 2. Models from Jan. 1, 1947 to July 1, 1947
- Vol. 1. All post-war models up to Jan. 1, 1947

FREE Photofact Cumulative Index

The easiest way to own the world's finest Radio Service Data is to subscribe regularly to PHOTOFACT Folder Sets. Send for the FREE Cumulative Index to PHOTOFACT Folders covering *all* post-war receivers up to the present. Helps you find the Folders you want in a jiffy. Get this FREE Index at your Jobber or write for it now.



ORDER THESE BOOKS FROM YOUR JOBBER

HOWARD W. SAMS & CO., INC.
INDIANAPOLIS 7, INDIANA

Radio Industry Red Book



The RED BOOK tells you in *one volume* what you need to know about replacement parts for approximately 17,000 sets made from 1938 to 1948. Includes complete, accurate listings of all 9 major replacement components—not just one. Lists correct replacement parts made by 17 leading manufacturers—not just one. Covers original parts numbers, proper replacement numbers and valuable installation notes on: Capacitors, Transformers, Controls, IF's, Speakers, Vibrators, Phono-Cartridges. *Plus*—Tube and Dial Light data, and Battery replacement data. 448 pages, 8½ x 11". **\$3.95** sewed binding. ONLY.....

TUBE PLACEMENT GUIDE. Shows you exactly where to replace each tube in 5500 radio models, covering 1938 to 1947 receivers. Each tube layout is illustrated by a clear, accurate diagram. Saves time—eliminates risky hit-and-miss methods. 152 pages; handy index. ONLY..... **\$1.25**

DIAL CORD STRINGING GUIDE. The book that shows you the *one right* way to string a dial cord. Here, in one handy pocket-sized book, are all available dial cord diagrams covering over 2300 receivers, 1938 through 1946. Makes dial cord restringing jobs quick and simple. ONLY..... **\$1.00**

GREATEST ADVANCE IN V.O.M. HISTORY

Beautiful Streamlined Instrument.

Large 5 1/2 Inch Meter in special molded case under panel.

Resistance Scale Markings From .2 Ohm To 100 Megohms... Zero Ohms Control Flush With Panel.

Only one switch... Has Extra Large Knob 2 1/2" Long... Easy To Turn... Flush With Panel Surface.

New Molded Selector Switch... Contacts Are Fully Enclosed... will retain lubrication without dust contamination.

Batteries Easily Replaced... New Double Suspended Contacts.

All Resistors Are Precision Film Or Wire Wound Types... Sealed For Permanent Accuracy.


Unit Construction... Resistors, Shunts, Rectifier, Batteries All Are Housed In A Molded Base Built Right Over The Switch... Provides Direct Connections Without Cabling... No Chance For Shorts.



Inside view cover removed...inverted

TECH DATA

D.C. VOLTS: 0-3-12-60-300-1200-6000, at 20,000 Ohms/Volt
 A.C. VOLTS: 0-3-12-60-300-1200-6000, at 5,000 Ohms/Volts
 D.C. MICROAMPERES: 0-60, at 250 Millivolts
 D.C. MILLIAMPERES: 0-1.2-12-120, at 250 Millivolts
 D.C. AMPERES: 0-12, at 250 Millivolts
 OHMS: 0-1000-10,000; 4.4 Ohms at center scale on 1000 scale;
 44 Ohms center scale on 10,000 range.
 MEGOHMS: 0-1-100
 DECIBELS: -30 to +4, +16, +30, +44, +56, +70
 OUTPUT: Condenser in series with A.C. Volt ranges

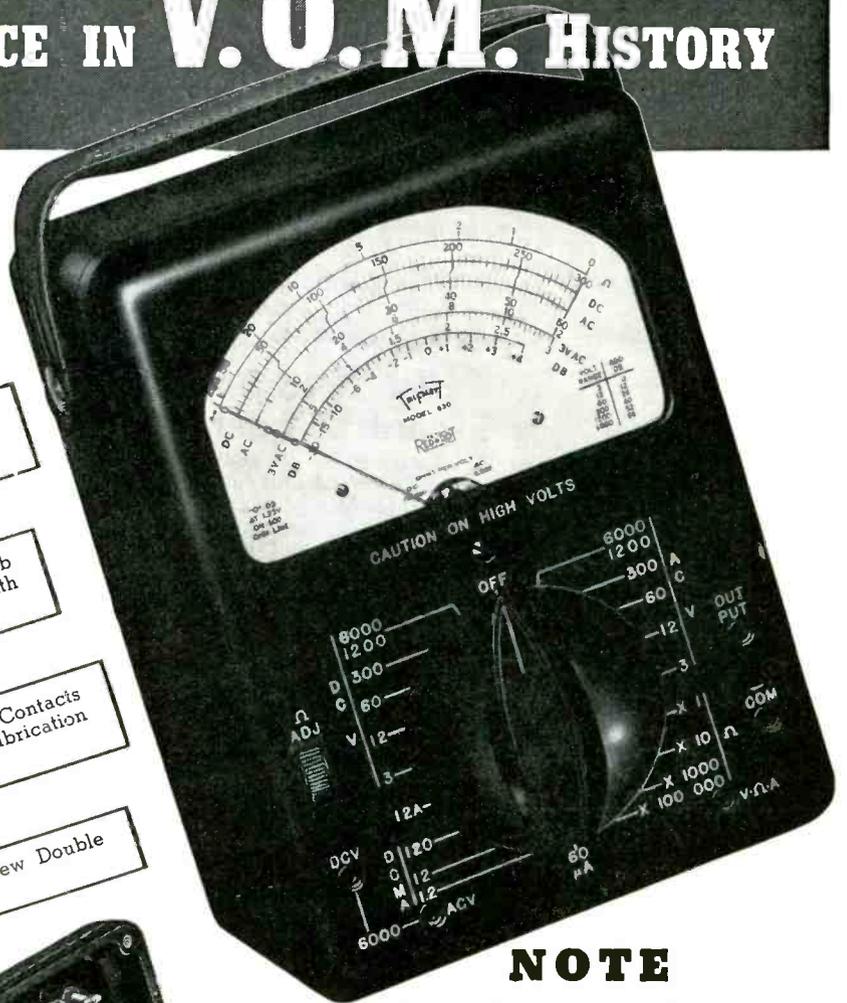

NOTE
the Sensational
Improvements
Model 630

\$3750 U.S.A.
 Dealer Net

Leather Carrying Case \$5.75
 ADAPTER PROBE FOR TV
 HIGH VOLTAGE TESTS EXTRA

A completely new Volt-Ohm-Mil-Ammeter that does more... has proved components... and will give a lifetime of satisfaction.

Precision first... to Last.




TRIPLETT ELECTRICAL INSTRUMENT CO. • BLUFFTON, OHIO

In Canada: Triplett Instruments of Canada, Georgetown, Ontario

MINIATURE TUBE MERCHANDISER TM-30

It's NEW!
IT'S CLEAR PLASTIC

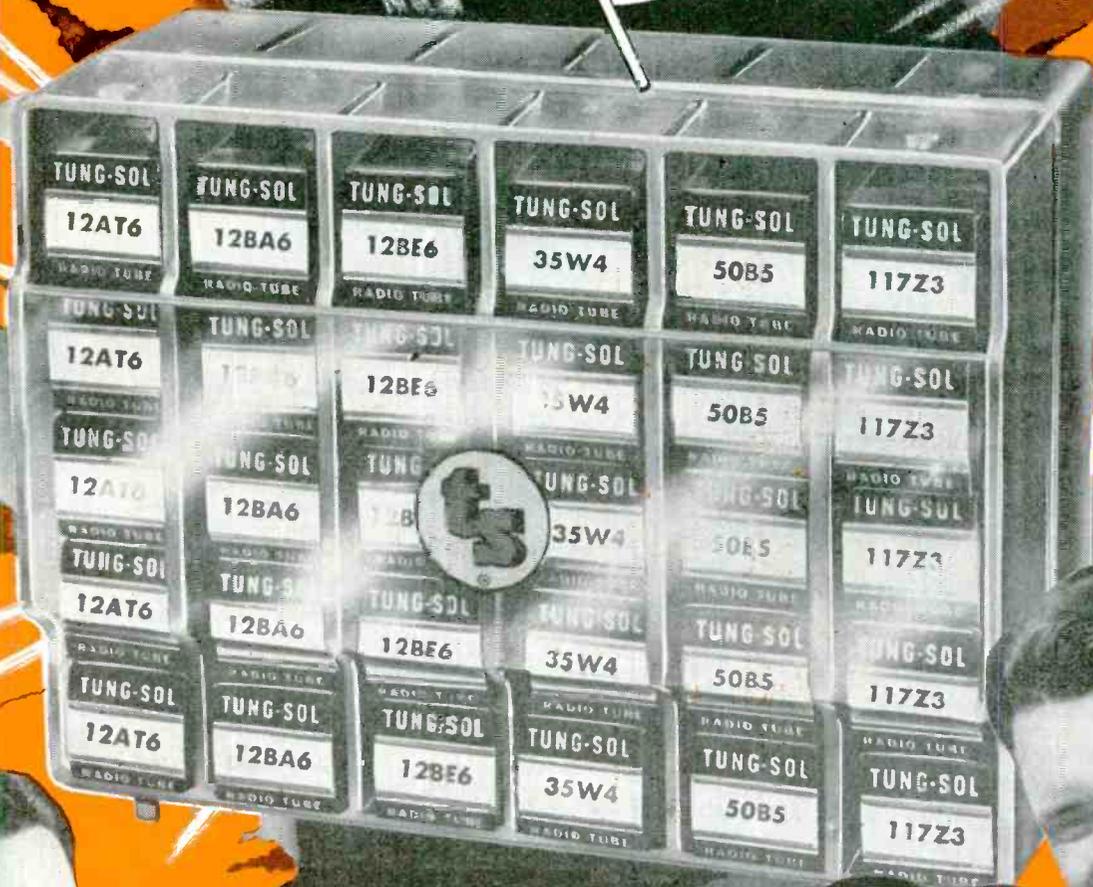


**SOLVES STACKING
PROBLEM!
KEEPS SHELVES
TIDY!**

**INVENTORY AT
A GLANCE!
INSTANT SELECTION!
REDUCES SPACE
REQUIREMENTS!**

TUNG-SOL LAMP WORKS INC., NEWARK 4, NEW JERSEY
Manufacturers of Electron Tubes and Radio Dial Lamps
SALES OFFICES: ATLANTA • CHICAGO • DALLAS • DENVER • DETROIT • LOS ANGELES • NEWARK

Build YOUR OWN TEST EQUIPMENT

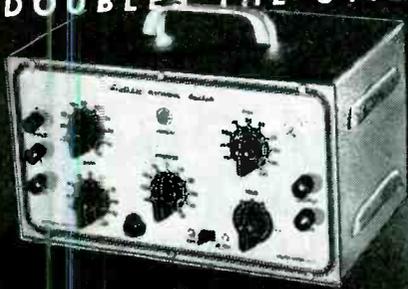Heathkit ELECTRONIC SWITCH KIT DOUBLES THE UTILITY OF ANY SCOPE




\$34.50

Gives two separately controllable traces with individual inputs on any scope.
See both the input and output traces, locate distortion, phase shift, etc., immediately.
Individual gain controls and positioning control. Coarse and fine sweeping rate controls. Complete Heathkit matches others, with 5 tubes. All metal parts are punched, formed and cadmium plated. Complete with tubes, all parts, detailed blueprints and instructions. Shipping Wt. 13 lbs.
Nothing ELSE TO BUY

HEATHKIT CONDENSER CHECKER KIT

\$19.50

Nothing ELSE TO BUY

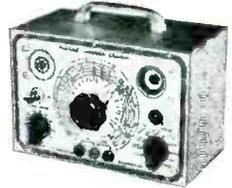

A condenser checker anyone can afford to own. Measures capacity and leakage from .00001 to 1000 MFD on calibrated scales with test voltage up to 500 volts. No need for tables or multipliers. Reads resistance 500 ohms to 2 megohms. 110V 60 cycle transformer operated complete with rectifier and magic eye indicator tubes. Easy quick assembly with clear detailed blueprints and instructions. Small convenient size 9" x 6" x 4 3/4". Wt. 4 lbs.

HEATHKIT SIGNAL GENERATOR KIT



\$19.50

NOTHING ELSE TO BUY

Every shop needs a good signal generator. The Heathkit fulfills every servicing need, fundamentals from 150 Kc. to 30 megacycles with strong harmonics over 100 megacycles covering the new television and FM bands. 110V 60 cycle transformer operated power supply.
400 cycle audio available for 30% modulation or audio testing. Uses 6SN7 as RF oscillator and audio amplifier. Complete kit has every part necessary and detailed blueprints and instructions enable the builder to assemble it in a few hours. Large easy to read calibration. Convenient size 9" x 6" x 4 3/4". Wt. 4 1/2 lbs.

HEATHKIT SIGNAL TRACER KIT




\$19.50

Nothing ELSE TO BUY

Reduces service time and greatly increases profits of any service shop. Uses crystal diode to follow signal from antenna to speaker. Locates faults immediately. Internal amplifier available for speaker testing and internal speaker available for amplifier testing. Connection for VTVM on panel allows visual tracing and gain measurements. Also tests phonograph pickups, microphones, PA systems, etc. Frequency range to 200 Mc. Complete ready to assemble. 110V 60 cycle transformer operated. Supplied with 3 tubes, diode probe, 2 color panel, all other parts. Easy to assemble, detailed blueprints and instructions.
Small portable 9" x 6" x 4 3/4". Wt. 6 pounds. Ideal for taking on service calls. Complete your service shop with this instrument.

HEATHKIT SINE AND SQUARE WAVE AUDIO GENERATOR KIT

The ideal instrument for checking audio amplifiers, television response, distortion, etc. Supplies excellent sine wave 20 cycles to 20,000 cycles and in addition supplies square wave over same range. Extremely low distortion, less than 1%, large calibrated dial, beautiful 2 color panel, 1% precision calibrating resistors, 110 V 60 cycle power transformer, 5 tubes, detailed blueprints and instructions. R.C. type circuit with excellent stability. Shipping weight 15 pounds.

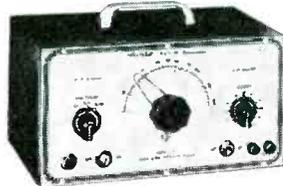

\$34.50

Nothing ELSE TO BUY

THE NEW HEATHKIT VACUUM TUBE VOLTMETER KIT


The most essential tool a radio man can have, now within the reach of his pocketbook. The Heathkit VTVM is equal in quality to instruments selling for \$75.00 or more. Features 500 microamp meter, transformer power supply, 1% glass enclosed divider resistors, ceramic selector switches, 11 megohms input resistance, linear AC and DC scale, electronic AC reading RMS. Circuit uses 6SN7 in balanced bridge circuit, a 6H6 as AC rectifier and 6 x 5 as transformer power supply rectifier. Included is means of calibrating without standards. Average assembly time less than four pleasant hours and you have the most useful test instrument you will ever own. Ranges 0-3, 30, 100, 300, 1000 volts AC and DC. Ohmmeter has ranges of scale times 1, 100, 1000, 10M and 1 megohm, giving range .1 ohm to 1000 megohms. Complete with detailed instructions. Add postage for 8 lbs.



\$24.50

Nothing ELSE TO BUY

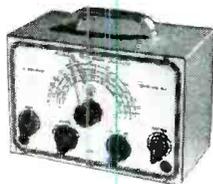HEATHKIT FM AND TELEVISION SWEEP GENERATOR KIT



\$24.50


NOTHING ELSE TO BUY

THE BASIC FM AND TELEVISION SERVICE INSTRUMENT

At the lowest cost possible, anyone can now service FM and television receivers. The Heathkit sweep generator kit operates with oscilloscope and covers all necessary frequencies. A few pleasant hours assembling this kit puts any organization in position to share the profits of the FM and TV boom.

Every part supplied — grey crackle cabinet, two color calibrated panel, all metal parts punched, formed and plated. 5 tubes, complete detailed instructions for assembly and use. Shipping weight 6 lbs.

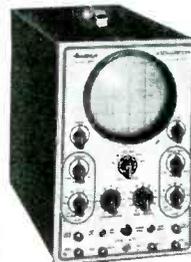The NEW 1948 HEATHKIT 5 INCH OSCILLOSCOPE KIT



\$39.50

NOTHING ELSE TO BUY

New improved model of the famous Heathkit Oscilloscope. Building an oscilloscope is the finest training for television and newer servicing technique and you save two-thirds the cost. All the features and quality of instruments selling for \$100.00 or more. Supplied complete with cabinet, two color panel, 5B1 tube, 2 5Y3 tubes, 2 6S17 tubes and 884 sweep generator tube. Power transformer supplies 1000V negative and 350 volt positive. Sweep generator 15 cycles to 30 M. cycles. Has vertical and horizontal amplifiers. Oil filled filter condensers for long life. Complete blueprints and instructions included.



The **HEATH COMPANY**

... BENTON HARBOR 11, MICHIGAN

SYLVANIA ADVERTISING HELPS SERVICE DEALERS INCREASE THEIR SERVICE BUSINESS!

Read what these 3 dealers say about Sylvania's Dealer Campaign for Summer and Fall

ELECTRONICS Service Company

F. M. Radio Recording Equipment
Public Address
Phone 1-2342
Tulsa, Oklahoma
October 23, 1948

Advertising Department
Sylvania Electric Products Inc.
Emporium, Pa.

Gentlemen:
We would like to express our appreciation to Sylvania for its co-ordinated advertising campaign. It has, so far, resulted in a steady increase in our service business. During September our business increased 30 per cent and to date in October it has shown a 28 per cent increase. We feel that this increase is due to this campaign since we have used it exclusively during this time.

We have used the radio spot announcements over our local station and mailed the direct mail postal cards to our customers. We have also used the newspaper ad mats in our local paper upon occasion.

It is a great help to the radio service business to have this service provided so inexpensively. Thanks to you of Sylvania.

Very truly yours,
Vernor P. Rodgers, Jr.
Vernor P. Rodgers, Jr.
Manager and Prop.

VPR:ML

"September business increased 30%"

DAMON'S RADIO SERVICE
1006 E. 14th ST. SAN LEANDRO

RADIO Radio Service

Dial TR 4353
1006 East 14th Street
SAN LEANDRO, CALIF.

R. H. DAMON

Advertising Department
Sylvania Electric Products
Emporium, Pa.

Gentlemen:

Enclosed is my order for the second kit in the Sylvania co-ordinated advertising program.

I took over this business on July 1 and have been using the advertising material from your first kit. I have found that it really pays to advertise. The previous business was bankrupt and had no volume of service business.

With help from Mr. J. A. Hall, the local Sylvania salesman, and the advertising material furnished by him, my business now shows great promise. Mr. Hall works for C. C. Brown Co. of San Francisco, one of your distributors. Mr. Hall filled my rush order for a Sylvania Tube Tester which has already increased my sale of tubes.

I am enclosing a few copies of my ad using Sylvania ad mats which appear in the local paper, the San Leandro News Observer, and the San Leandro Shopping News. These papers have a circulation of 18,000. This type of advertising brought in over 100 radio sets for repair during the month of July. I hope business grows like this every month from now on.

Sincerely yours,

R. H. (Bob) Damon
Damon's Radio Service
1006 E. 14th Street
San Leandro, Calif.

"Newspaper ads brought in over 100 radio sets for repair during July!"

216 FOURTH AVE., WEST
PHONE 1564
ASHLAND, WISC.

MYERS RADIO SERVICE CO.

Advertising Department
Sylvania Electric Products
Emporium, Pa.

Dear Sir:

I am writing to tell you how much your co-ordinated advertising has helped my business.

I have used the postal cards, the window displays and the radio spot announcements to promote my business. The spot announcements are used seven times a week over our local radio station. They are used at various hours so I have contacted a large range of people.

I make my living entirely through service and the sale of used records, so anything which helps to increase my business is very valuable to me. Since I have been using your campaign my business has increased from an average of \$90.00 per week to about \$135.00 per week gross. My use of the campaign has cost me about \$12.00. Before I used the campaign I was spending an average of \$7.00 per week. For the extra expense I have certainly received a fair return.

I am very much pleased with the radio spots in your booklet.

Robert Myers
Myers Radio Service Co.

"Gross business increased from \$90.00 to \$135.00 per week"

SYLVANIA'S FEBRUARY, MARCH AND APRIL CAMPAIGN IS NOW READY. Here's what it contains:

- 3 Postal Card Mailings—one for each month.
- 3 Window Displays—one for each month.
- 3 Window Streamers—one for each month.
- 6 Newspaper Ad Mats—two sizes for each month.
- Radio Spot Announcements—several for each month.

SEND FOR FULL INFORMATION NOW!

Remember, this campaign designed for your use ties up directly with Sylvania's ad campaigns on a national scale. You pay only the postage on the government postal cards you mail. Sylvania supplies everything else free! Mail coupon today!

SYLVANIA ELECTRIC

RADIO TUBES; CATHODE RAY TUBES; ELECTRONIC DEVICES; FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES; LIGHT BULBS; PHOTOLAMPS

Sylvania Electric Products Inc.
Advertising Department
Room R-1901
Emporium, Pa.

Gentlemen: Please send me full details on your February, March and April Service Dealer Campaigns.

Name _____

Company _____

Address _____

City _____ Zone _____

State _____

RADIO · TELEVISION · ELECTRONIC SERVICE

TV, FM and Sound

THE TWO EXTREMELY IMPORTANT factors in the radio art, *FM and Sound*, have unfortunately received a vacillating type of attention from too many Service Men. The FM receiver has been dismissed as an attachment and a gadget by scores of Service Men and the sound system, particularly in the FM set, has been overlooked completely. It seems to have taken the television receiver to project the importance of the frequency-modulation system of reception and the audio end, too. For in the television set, there is quite an elaborate FM set feeding into an audio system, which is not always too elaborate or even acceptable. In capitalizing on the full capabilities of the audio end of the TV set, a thorough acquaintance with the FM and audio section are *must* factors. The circuit of the FM portion of the TV set, which is similar to that used in most standard FM and AM/FM receivers, must be studied as carefully as the video receiver itself. Every design feature should become familiar ground to facilitate servicing and, most important, provide a quality signal to the audio end.

Because of the importance of the FM phase of the TV set as well as the virtues of the system for receiving purposes only, complete coverage of the field will continue to be emphasized in every issue of *SERVICE*. Incidentally, there's a book which has just come off the press, directed entirely to *Frequency Modulation* which will undoubtedly become a bible with every Service Man. Written by Nathan Marchand, who has authored a score of articles for us, and published by Murray Hill Books, it contains over 400 pages of well-illustrated copy detailing every phase of FM in receiving and transmitting, fixed and mobile, and particularly the servicing of modern sets. This book is a *must* for reading and study.

As indicated, the sound portion of the TV set also merits careful consideration from the Service Man. In most sets, the full capabilities of the system are far from achieved, because of a limited output amplifier and particularly small speaker, two items dictated by production and, often, eco-

nomics. Many Service Men have found on many occasions that the use of a special speaker cabinet can provide concert-grand-type reception, much to the customers surprise. To demonstrate, portable cabinets with small and large type speakers have been constructed, and connected to a switching system operating into an impedance matching transformer as well as an additional high fidelity amplifier to further demonstrate how improved quality can be provided. Some Service Men have found these demonstrations so successful that they have set up special departments to promote, sell and install these *TV Sound Systems*, as they are called by the Service Men. It's become quite a profitable business and seems to be booming daily.

Just how some of the boys have set up these *TV Sound Systems* will be described in an early issue of *SERVICE*. Watch for this extremely interesting discussion.

Taxicab Radio

LAST MONTH Samuel Freedman offered an informative analysis of the features of 2-way taxicab radios and just where troubles occur in them.

We have received some additional information from Mr. Freedman covering another very important phase of servicing of taxicab radios, the type of servicing practiced today. There appear to be three types: (1) Servicing only when required, where the Service Man charges only the actual labor and parts on occasion; (2) preventive maintenance and routing service, where a Service Man or service organization handles a fleet on a contract basis involving a certain charge per vehicle per month plus the cost of parts. The amount of this charge determines whether the parts shall be at list, net or halfway between these two extremes; and (3) fleet owner operation of his own servicing depot with full-time maintenance employees.

On a contract basis the usual charge per car is \$5.00 per month, with extra for parts. However, there are servicing contracts in force in various parts of the country ranging from a minimum of \$2.50 to a maximum of \$10.00 per car per month, exclusive of

parts. Installation of equipment brings charges from \$15.00 to \$25.00 per car, the charge varying with the number of vehicles, types of vehicles and their availability.

Anyone making an adjustment to the transmitter in a taxicab radio set-up which may result in improper or off-frequency operation on the air must be licensed by the FCC. The easiest license examination possible to obtain for such work is a *radiotelephone second class*, which requires no knowledge of telegraphy.

Production Changes

IN STUDYING the variety of television receiver circuit diagrams which come across our desk, we found that revisions in these circuits were being made very often. In fact, many of the new models were found to have undergone up to nearly one hundred revisions in circuitry.

To keep Service Men posted on these revisions, *SERVICE*, beginning with this issue, presents a special TV receiver production change section (*page 22*).

Every effort will be made to present complete coverage on the changes being made each month.

Hope you like this new feature.

Long-Playing Records

THE RECENT INTRODUCTION of the 45-rpm record system has prompted a new, intriguing installation and servicing problem for the Service Man.

This system, developed by RCA, differs from the Columbia method not only in the increase in speed from 33 $\frac{1}{3}$, but in the size of the record, the RCA being a 6 $\frac{7}{8}$ -inch disc and providing up to slightly more than five minutes of playing time. The record is also a bit thicker through the center portion from a 1 $\frac{1}{2}$ " center spindle hole to midway down the record. In addition, the pickup has a pressure of 5 grams and the needle is slightly thinner than the Columbia *lp* type.

A special eight-record automatic record-changer has been developed for the 45-rpm discs. An analysis of this record changer and other components and accessories for the new 45-rpm system will appear soon in *SERVICE*.
—L. W.

Features of Seven Types of Front-End Systems: Permeability, Inductance, and Variable Capacitor Tuning; Continuously Variable Inductance Control; Modified Straight and Circular Long-Line Inductance Tuning, and the HF Variometer Method.

in many receivers. Generally speaking, variable-inductance systems have several advantages over capacity-tuned systems. There are other factors, however which must be taken into consideration in each tuner design.

In *uhf* receivers and converters employing the usual variable-capacitor method of tuning, several disadvantages are encountered which prevent optimum performance over any considerable range of frequencies. Since the signal-to-noise ratio, gain, image rejection and stability are affected by lumped capacities in the tuning capacitor, a practical limit must be placed on the total frequency range to be covered in any one band. This necessitates, for practical purposes, either a different system of tuning which is capable of tuning a wide range of frequencies in one continuous band, or a system of capacity-tuning wherein the tuned circuits are designed to operate efficiently over a narrow band of frequencies with bandswitching employed to change from one band to another. The only trouble with this system is the introduction of distributed capacity in the band switch and in the leads running to it, along with mutual coupling between turret coils and the possibility of trouble in the switch contacts.

Other disadvantages are excessive stray capacity in the gang unit, common coupling between gang sections, rotor contact resistance, bulky size, and a tendency to being microphonic in operation. In addition, the gain in a capacity-tuned circuit tends to decrease as the frequency increases. These problems have been solved by a number of FM receiver manufacturers through careful design and improved circuitry. However, capacity-tuned systems have five substantial advantages: (1) simplicity in design and operation, (2) low cost, (3) long operating life, (4) relatively trouble-free service, and (5) adaptability to mass-production.

The unit shown in Fig. 1 is an example of a reliable, low-cost *capacity-tuned* unit. Stability is accomplished in the front-end portion through the use of heavy brass capacitor plates. Rigidity in plate construction reduces drift caused by thermal contraction and expansion. Figs. 3, 4 and 5 illus-

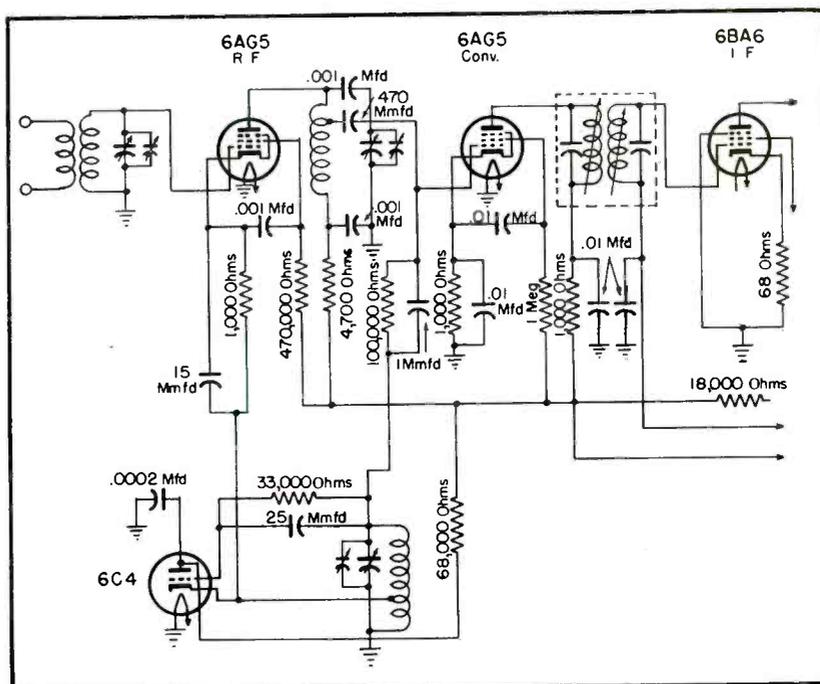



Fig. 5. Meissner 8C FM tuner circuit, which features capacity tuning.

trate other type tuners employing capacity tuning. Many FM/AM receivers also use capacity-tuned front ends.


In *inductance-tuned* systems, some of the main advantages are improved

circuit Q , minimum of distributed capacity effects, increased tuning range, less likelihood of common coupling, less tendency toward microphonics, (Continued on page 35)

Fig. 6. Converter circuits using the inductance tuning method developed by Mallory.

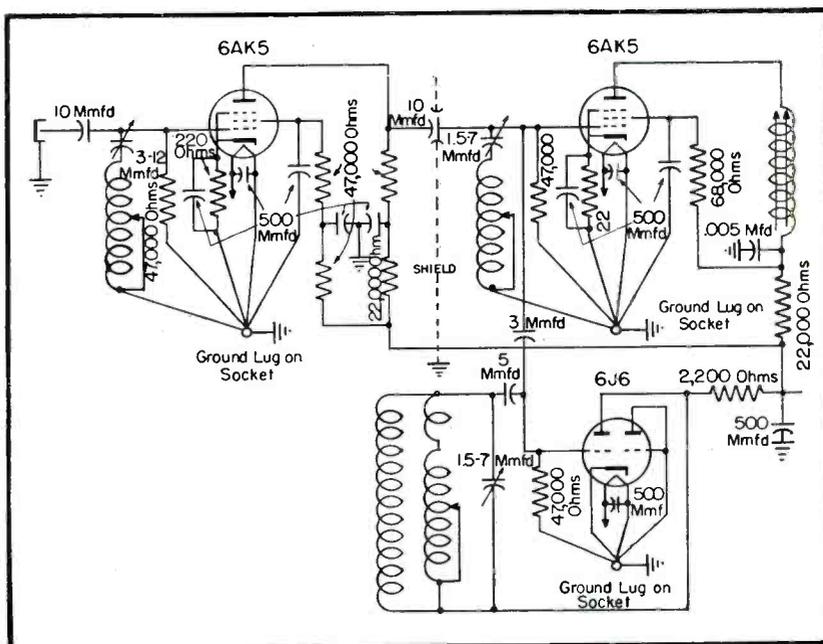

The Business Aspects of

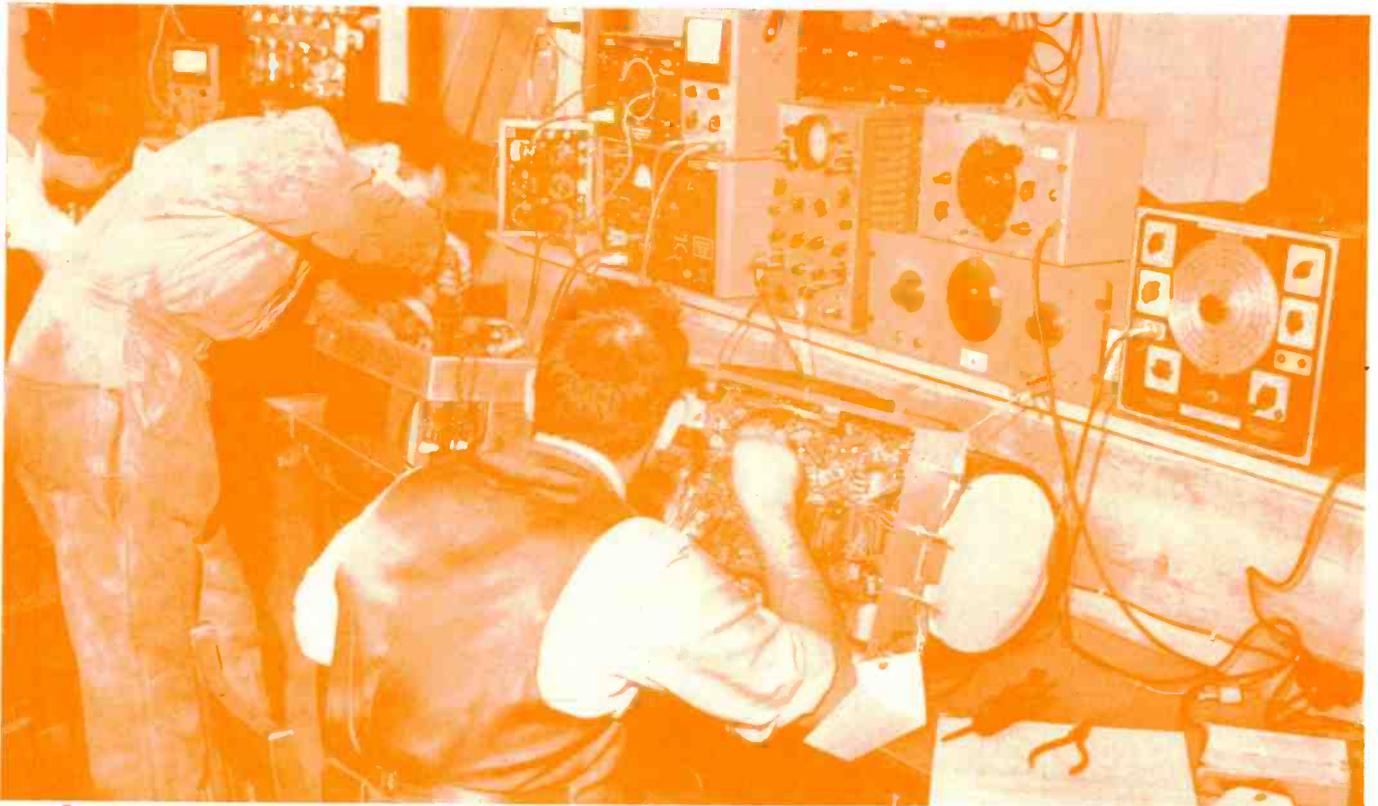

Careful Application of Management Programs Extremely Essential to the Successful Conduct of TV Installation and Service Work Today, Particularly in the Use of Correct Types of Installation and Servicing Agreements and Warranties.

THE BUSINESS aspects of TV antenna installations are as important as the technical factors, for unless TV installation men can realize a satisfactory income from their efforts, it is quite impossible to render any form of the efficient service essential to the promotion of a wide public acceptance for TV receivers.

TV receivers are being sold today on a *guaranteed basis* with the majority of customers receiving a one-year warranty on installations.

There are three groups who are participating in TV installation work today:

- (1) Servicing dealers.
- (2) Independent TV installation and service companies selected by TV distributors, dealers, or TV manufacturers.
- (3) Service companies or divisions

of TV manufacturing organizations.

By far, the greatest number of TV antenna installations are being performed by those in groups 2 and 3.

Most dealers prefer not to do their own installations since the removal of the installation and service responsibility from overhead enables the dealer to determine his overhead liability more accurately and therefore eliminate those *hidden costs* which are the cause of so many business failures.

The non-servicing dealers usually sell the TV installation warranty to the customer with the statement that he supports the warranty and in some

cases he states further "that this warranty is supported by the manufacturer of the TV receiver."

Basis of Warranty Plan Success

The basis for the full success of all of the customer warranty plans is mutual good faith between the television manufacturers and their dealers. The manufacturers are dependent upon their own or approved independent service organizations to perform TV installations on a level which will develop the best possible reputation for their equipment. The TV receiver dealer is dependent upon the manufacturer for maintenance of product integrity. Under those agreements where the manufacturer establishes the installation and service warranty, the manufacturer is dependent upon his

Above: A well-planned TV service bench which provides rapid checks in trouble shooting to accelerate receiver return, always a good business practice. (Photo taken at Associated Television Service Corp. by Louis Rosenberg)

TV Installations

by **IRA KAMEN**

Manager, Television Antenna Dept.
Commercial Radio Sound Corp.
New York City

dealers for full cooperation under his warranty plans.

There are three types of mutual agreements currently used:

- (1) Between the manufacturer and independent installation and service companies.
- (2) Between the distributor or dealer and independent TV installation and service companies.
- (3) Between TV manufacturers, distributing companies and TV receiver purchasers, which are often in the form of warranties.

While there are no standard forms for agreements between TV receiver manufacturers and independent TV receiver installation and service companies, it is important that an *epidemic failure clause* be included in all types of agreements as a protection for the TV installation and service company. Most of the reliable, experienced manufacturers provide this protection clause in their agreements.

There are two types of epidemic failures:

- (1) Ten per cent or more of the installations made by the installation and service company over some fixed period develop identical failures.
- (2) Repetitious failures of components of any kind credited as manufacturers' design defects. (*Note:* All field modifications correcting design defects are always considered as the manufacturer's responsibility.)

Manufacturers pay the Service Men group a fixed fee for all service calls resulting from epidemic failures.

Incidentally manufacturers always include a statement noting that . . . "Epidemic failures shall not include failure of the antenna installation."

There are six major points which may be used as a guide in preparing an agreement between a manufacturer and independent Service Men:

- (1) Fee for warranty period.
- (2) Definition of standard installation.
- (3) Procedure for handling non-standard installations.

- (4) Parts guarantee.
- (5) Protective clause against damages caused by *Acts of God*, and customer negligence.
- (6) Cancellation clause.

An *assist clause* is also a very desirable point to have included in a contract between the installation and service company. Such a clause is evidence of the manufacturer's good faith.

An *assist clause* usually provides that the manufacturer shall . . . "supply the installation and service company with sufficient TV chassis to enable them were necessary to replace the models requiring shop repairs. The customers chassis shall be repaired and subsequently returned to the customer's TV receiver cabinet. Title to these replacement chassis shall be retained by the manufacturer. The installation and service company agrees to insure these replacement chassis while on their premises or in transit."

The second type of agreement, which is between the distributor or dealer and independent installation and service companies passes on the manufacturers' guarantees to the installation and service company and thus is actually similar to the direct agreement between manufacturers and independent installation and service companies. The main differences usually occur when the dealers make direct arrangements with those installation and service companies who have limited financial responsibilities. These agreements usually include the following types of clauses:

- (1) The installation and service company shall be paid by the dealer only for work done, with the balance of the money paid by the customer for his one-year warranty to be paid on a pro rata basis periodically as the guarantee time is consumed.
- (2) All installation and Service Men are to be bonded and covered by insurance so that the dealer is protected against law suits arising from the negligence of personnel employed

(Continued on page 37)

Customer's TV Maintenance Policy

In consideration of the amount of \$_____, which you paid to your Stewart-Warner Dealer, the Authorized Service Station whose name appears in the registration section of this policy, has contracted to provide the following service **FOR A PERIOD OF THREE MONTHS** on the Stewart-Warner receiver herein identified by model and serial number:

Furnish all labor, materials, replacement parts, and tubes (including the picture tube) that may be required to repair or maintain the specified receiver and antenna in proper working order for best possible reception of television signals within the limitations of the customer location for a period of three months from date of installation as shown in this policy, provided that such service and replacement components are necessitated by normal usage of the receiver.

The service provided by this policy shall normally be available and rendered during the regular working hours of the customary work-week. Every effort will be made to give prompt attention to service requests of an urgent nature.

EXCEPTIONS

1. **MISUSE: SERVICING BY UNAUTHORIZED PERSONS:** This policy shall be voided immediately if the said television receiver has been subjected to misuse thru negligence or otherwise, if the serial number has been altered, effaced or removed, or if the receiver and antenna have been adjusted or serviced by any person other than a representative of the Authorized Service Station or the Stewart-Warner Distributor.
2. **DAMAGE:** This Policy does not cover replacement or repair due to loss or damage incurred in transportation of the television receiver, or due to fire, lightning, theft or other causes beyond the control of the Service Station.
3. **ELECTRICAL INTERFERENCE:** The television receiver specified herein and its antenna have been designed and installed to minimize the effects of external interference that may be created by passing automobiles, appliances, diathermy machines, aircraft, short wave and FM receivers and other electrical equipment such as motors and converters; however, liability on the part of the Service Station for the elimination of such interference in either the picture or sound is limited to minimizing the effects of such interference by utilization and correct placement of the proper antenna and transmission line.
4. **SUBSEQUENT INSTALLATION:** This Policy does not cover subsequent installations resulting from structural alteration of the premises, redecorating or movement of the instrument to a new location. If the receiver is moved from the point of original installation during the term of the Policy the Service Station shall be entitled to charge their regular fee for making an installation at the new address.
5. **AUXILIARY POWER SUPPLY:** The Service Station assumes no liability with respect to the installation, service or maintenance of motor-generators, converters or other devices that may be used under certain circumstances to supply power to the specified receiver, nor to the effects produced by such equipment on the performance of the receiver.
6. **FCC STANDARDS:** This Policy does not cover any changes in the specified receiver that might be required as a result of revisions in present television standards by the Federal Communications Commission.
7. **LIABILITY OF RECEIVER MANUFACTURER:** Stewart-Warner Corporation shall not be liable for any loss or damage to the customer or any other person resulting from or in connection with the installation, use, or servicing of the said television receiver.

VALIDATION OF POLICY

This policy shall be valid only upon payment of the prescribed fee and after the Registration Record Form has been properly filled out and signed by an accredited representative of the Authorized Service Station who installs the receiver. Factory and distributor copies of Registration Record Slips must be mailed as directed on bottom line of each.

A typical manufacturer's maintenance policy.
(Courtesy Stewart-Warner)

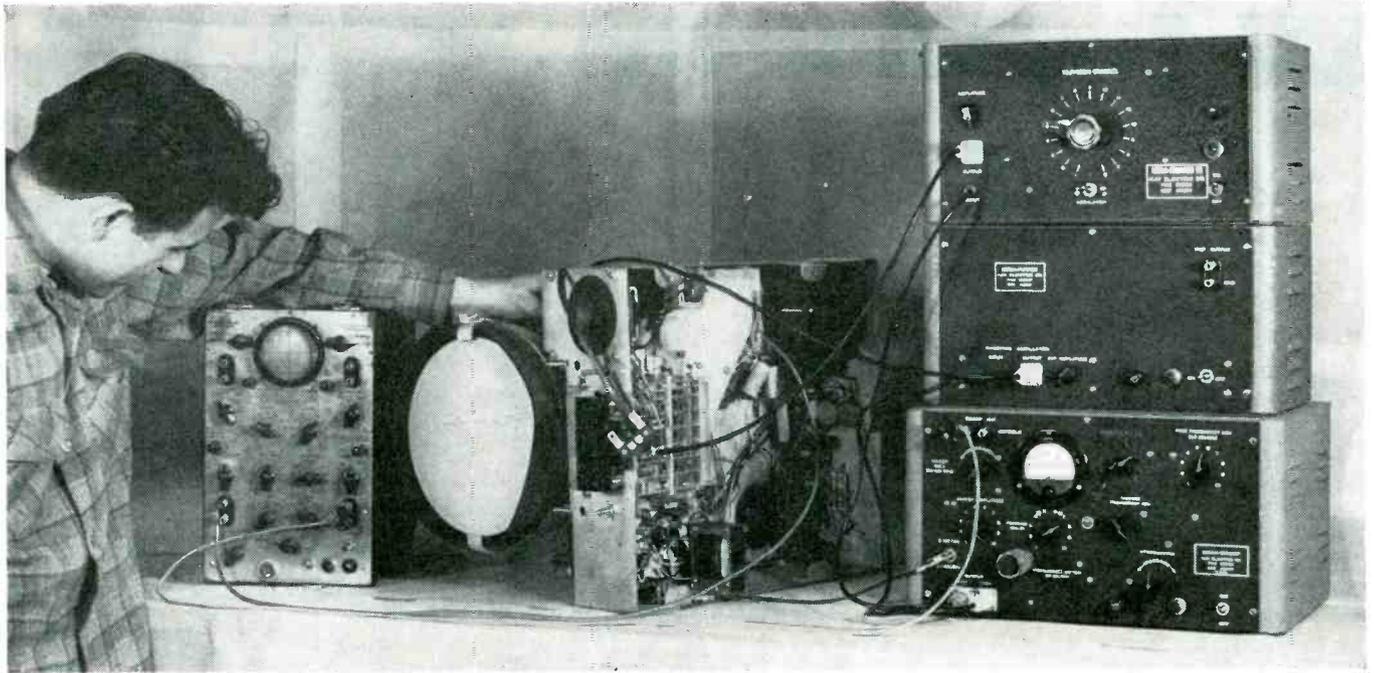


Fig. 1. Aligning the Bendix 235 TV receiver. Equipment used includes a 'scope, wide-range sweeping oscillator,¹ crystal-controlled *if* quadruple marker pip generator² and a twelve-channel crystal-controlled *if* sound carrier marker generator.³ Not shown in this view, but required during certain phases of *if* alignment procedure, is a 29 to 39-mc tuneable *if* marker generator⁴ employed in the alignment procedure applied to the Tele-Tone TV-149 receiver⁵. Although the setup above shows the picture tube mounted in place on the TV receiver chassis, it is generally necessary to remove this tube before proceeding with any *if* alignment work in order to attain access to some of the *if* transformer adjustments. For a preliminary overall alignment check where the sweeping oscillator is fed into the antenna output terminals, the picture tube need not be removed.

TV Receiver Visual Alignment Techniques

Part III . . . Circuit and Test Analysis of the Bendix 235 TV Chassis.

CONTINUING WITH OUR discussion* of alignment techniques for particular models of TV receivers, we shall now consider the recently introduced Bendix 235M1 and 235B1 models. Both use the same chassis.

Circuit Analysis

Last month appeared a discussion of the *rf* tuner or *front end* portion of this unit, a December issue front cover feature. This month, the entire circuit is presented, Fig. 2. The heavy lines on the schematic show the paths for all signals of varying amplitude. It will be noted that a superhet circuit is used, with the first three *if* stages serving as a common amplifier chain for both the sound and picture signals.

The sound *if* carrier is selected from the plate circuit of the third 6AG5 *if* (V_{10}) and fed through a 6AG5 stage of sound *if* amplification (V_4) and a 6AU6 limiter stage (V_5) before it is

by **LESTER L. LIBBY**

Chief Engineer

Ohmega Laboratories and Kay
Electric Co.

demodulated in a conventional 6T8 FM discriminator circuit (V_6). The 6T8 is a multi-purpose type, combining within one envelope three diodes and a triode. The triode section is employed as a first audio amplifier and is fed by capacitive coupling directly from the output of the discriminator. The volume control is located between this first audio amplifier stage and a

6Y6 power output tube (V_7). One of the diode sections of the 6T8 (pin 6) is used to delay the *agc* bias voltage applied back to the *rf* amplifier. The 6Y6 audio output stage is a conventional beam power amplifier.

Returning to the *if* channel, it will be noted that the 6AG5 fourth *if* (V_{11}) serves only as a picture or video *if* amplifier, feeding directly into the picture detector which is a 1N34 crystal diode. The output from the picture detector is fed into a 6AC7 stage of video amplification (V_{12}) whose output is connected directly into the 10" 10BP4 picture tube, V_{13} . The signal output of the 6AC7 video amplifier consists of all the sync pulses as well as the actual picture signal and is, of course, a fluctuating *dc* voltage. Although the cathode of the picture tube is at all times at a negative potential with respect to chassis ground, the picture signal is positive in phase, i.e., the dark portions of the picture and the sync

*SERVICE, October and November, 1948.

¹Mega-Sweep.

²Mega-Pipper.

³Mega-Marker, Sr.

⁴Mega-Marker.

⁵SERVICE, October, 1948.

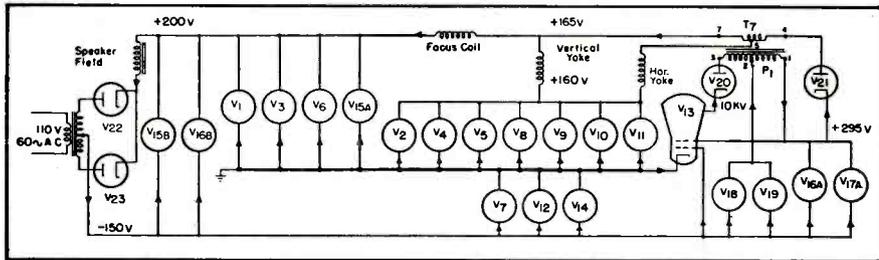


Fig. 3. Power supply distribution and division of potentials in the Bendix receiver; arrows indicate direction of electron flow rather than the conventional positive current flow.

to the following horizontal oscillator (V_{17B}). In other words, the frequency of the horizontal oscillator is synchronized by the horizontal sync pulse train after the phase of this pulse train has been properly adjusted by the 6SN7GT (V_{17A}). It should be kept in mind that the horizontal oscillator, which is of the blocking-oscillator type of circuit, operates in such a manner that its free-running frequency is always slightly lower than the standard television

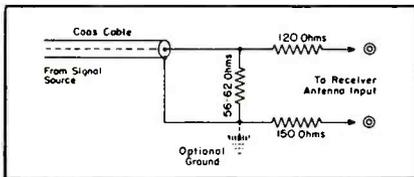


Fig. 4. Resistance matching pad, coax-to-balanced.

horizontal sync pulse frequency of 15,750 cps. This means that the incoming sync pulses or signals always exert a controlling force on the horizontal oscillator so as to increase its resultant frequency up from its normal free-running point.

The discharge network upon which the output of the horizontal oscillator acts is connected in the plate circuit of

the 6SN7GT (V_{17B}). From this network the resultant saw-tooth wave is fed to a pair of 7A5 horizontal output tubes, V_{18} - V_{19} , and then through a special horizontal sweep transformer and control circuit to the horizontal magnetic deflection coils in the yoke on the picture tube.

During the very short period of time in which the horizontal sweep is returning the electron beam to the left side, or starting position, of the picture tube, the rate-of-change of current in the horizontal sweep transformer is very high. This rapid change in current is utilized in the primary autotransformer circuit to generate the high voltage required for the second anode of the picture tube. This high voltage is rectified by a 1B3GT (V_{20}) and applied to the picture tube anode at approximately 10,000 volts.

To prevent regeneration or oscillation occurring in the horizontal sweep output circuit, a 6W4GT diode damping tube (V_{21}) is connected in the circuit so as to prevent any appreciable oscillation from occurring.

The low-voltage power supply using a pair of 6W4GTs (V_{22} and V_{23}), provides plate voltage to all of the tubes in the television receiver except the pic-

ture tube. The various tubes in the receiver are connected between the +200 volt and -150 volt busses and ground so as to constitute a voltage divider system. This eliminates the need for a high-wattage bleeder system, reduces the total power consumption of the receiver and allows the use of a lighter-weight power transformer. The manner in which the power supply distribution and division of potentials takes place is illustrated in the voltage block diagram, Fig. 3. The arrows in this block diagram indicate the direction of electron flow rather than the conventional positive current flow. It will be remembered that electron flow is from negative to positive, e.g., from cathode to plate within a vacuum tube, and is hence the reverse of the conventional positive current flow.

Production Changes

Returning for a moment to the circuit diagram, Fig. 2, the diagram shown applies to the A type chassis. There are six other types, B, C, D, E, F and G, indicated by a large block letter within a square, rubber stamped on the chassis.

The code D chassis carries the following revisions:

- (1) Resistors R_{42} , R_{45} and R_{50} were changed from 27 to 68 ohms, $\frac{1}{2}$ watt 10%.
- (2) Resistor R_{41} was deleted and replaced with an rf choke L_{53} .
- (3) Capacitor C_{35} was changed from .25 to 10-mfd, 200-volt electrolytic.
- (4) Resistor R_{138} , 3.3 megohms, was deleted.
- (5) Resistor R_{124} was changed from 1800 to 8200 ohms.
- (6) Junction of C_{131} and R_{131} has been returned to chassis ground instead of to the -150 volt lead.
- (7) Resistor R_{70} was connected directly to pin 2 of V_{16A} (plate) instead of to the junction of R_{65} and R_{74} .
- (8) Alignment frequency of L_{14} was changed from 35.9 to 32.9 mc.
- (9) Alignment frequency of L_{20} was changed from 33.1 to 35.7 mc.
- (10) Alignment frequency of L_{23} was changed from 35.9 to 35.7 mc.
- (11) Alignment frequency of L_{24} was changed from 33.1 to 32.9 mc.

In the E chassis, a $\frac{1}{2}$ -watt 27-ohm resistor has been connected to terminals 1 and 2 of the horizontal centering potentiometer and to the junction of terminal 1 of the vertical centering potentiometer, C_{80B} and L_{42} .

In the F chassis, thirteen revisions have been included:

A 6BG6G has been inserted in place of two 7A5s (V_{18} and V_{19}) and is now V_{10} .

A 4-ampere fuse has been added
(Continued on page 40)


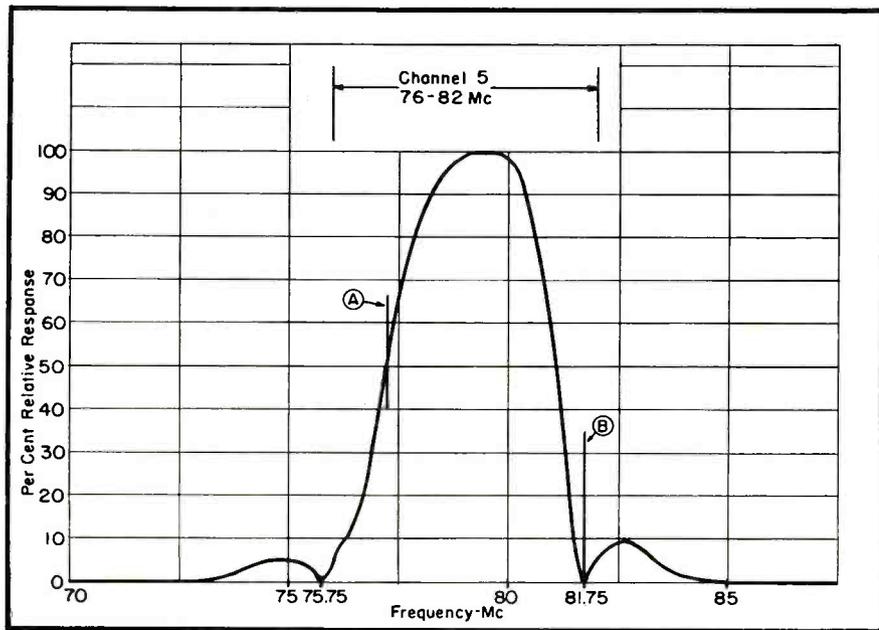
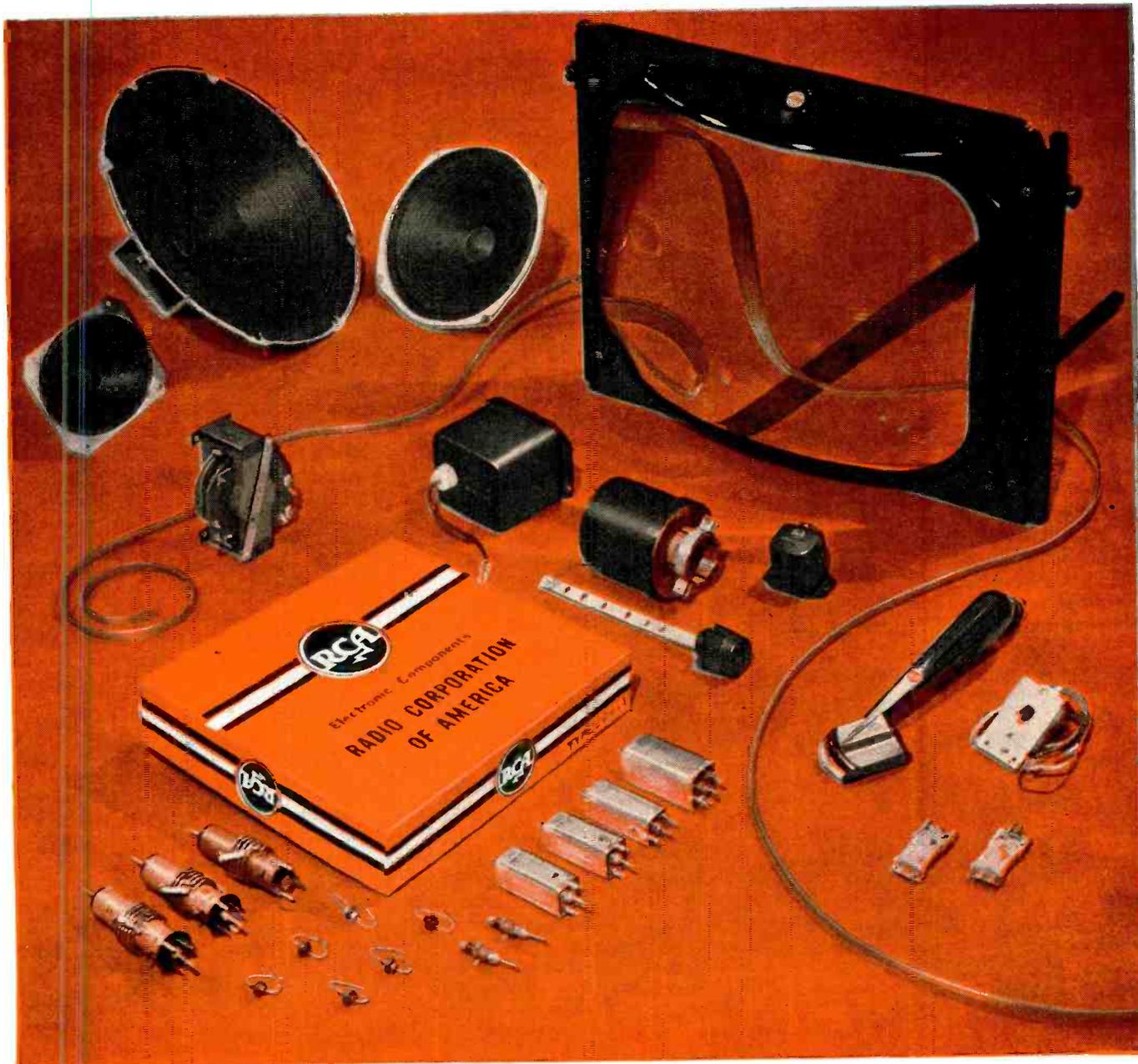


Fig. 5. Overall response at video detector. At (A) appears the picture rf carrier point, 77.25 mc, and at (B) appears the sound rf carrier point, 81.75 mc.

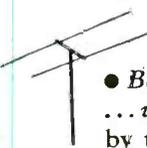

... RCA's quality line of standard parts and accessories ... for TV, FM and AM


 • Better because they're RCA-engineered ... widely accepted because they're backed by the greatest name in radio and television ... these standard parts and accessories mean greater sales and service volume for you throughout the year.

Now you can obtain *all* the major components

required for television receiver repair or construction ... a quality line of PM and field-coil speakers that meet practically all replacement needs ... plus a profitable line of accessories for FM, television, and phonograph modernization. And you can get them all from *one* dependable source of supply ... your local RCA Distributor.

ALWAYS KEEP IN TOUCH WITH YOUR RCA DISTRIBUTOR



RADIO CORPORATION of AMERICA
ELECTRONIC COMPONENTS
HARRISON, N. J.

SERVICE, JANUARY, 1949 • 17

Rotary Switch 7" TV Model

THE FRONT END of a 22-tube 7" TV receiver featuring intercarrier sound, switching via separate inductors controlled by movable iron cores and a dual 6" speaker system appears on the cover this month; National NC-TV7. To facilitate study of the front end, the complete circuit of the receiver is shown in Fig. 1.

The *rf* unit selects the desired signal, amplifies and converts the signal to provide an output at the plate of the mixer, consisting of heterodyned picture and sound carrier frequencies for the twelve channels: For channels 2 to 6, the picture carrier is 37.3 mc and the sound carrier is 32.8 mc; for channels 7 to 13 the picture carrier is 34 mc, and the sound carrier 38.5 mc.

The input circuit of the 6AU6 *rf* amplifier tube is designed for a 300-ohm balanced line. The input signal is fed to the grid and cathode of the tube. A center-tapped coil with an iron core is connected to the antenna terminals for coupling purposes on channels two through six. On the higher frequency channels, two small air-wound coils are switched across the center-tapped iron-core coil to maintain the desired coupling. The plate circuit of the *rf* tube is resonated by an adjustable, brass core coil, in series with a multi-tapped coil.

It is possible to apply *agc* to the grid of the *rf* tube through a terminal panel which is fitted with a link switch to remove *agc* from the tube in fringe areas etc., where an increase in sensitivity is desired. Coupling to the

[See Front Cover]

mixer grid is accomplished through a capacitor, on channels 7 through 13; the coupling is inductive on the lower channels.

The mixer circuit employs a 6AG5 pentode with grid leak bias. The grid of the mixer is resonated in the same manner as the plate circuit of the *rf* amplifier tube.

The local oscillator employs a 6C4 triode in a modified ultra-audio circuit. B+ is fed to the plate of the tube through a 2200-ohm resistor, R₇. Each channel has a separate inductor made adjustable by a movable iron core. A variable capacitor connected in the grid of the oscillator serves as the fine tuning adjustment. The oscillator operates on the high side of the picture carrier on channels 2 through 6 and on the low side of the picture carrier on the higher frequency channels.

IF Amplifier and Video Detector

The intercarrier sound system used in this model differs mainly from the conventional system in that the heterodyning frequency which determines the sound *if* frequency is the picture carrier and the *FM* sound carrier is not separated from the picture carrier until just before the video signal is applied to the picture tube. The intercarrier sound is relatively independent of local oscillator tuning, because the sound *if* is determined at the transmitter and not in the receiver. The system consists of three stages of symmetrical *if* amplifiers and four stagger-tuned circuits with two alignment frequencies. Traps are not required in this system, thereby greatly simplifying the alignment procedure.

The three *if* stages are similar for the most part. Tuning is accomplished by means of adjustable iron-core coils; the alignment frequency of L₁₀ and L₂₀ is 34.8 mc, of L₂₀ and L₂₄, 36.9 mc. By use of a symmetrical curve in the *if* band pass, the local oscillator is operated on the low side on the high-frequency channels to maintain oscillator stability. The plate supply to *if* tubes, V₆ and V₆, is shunt fed through *rf* chokes. This is done in the case of

V₆ to keep the resistance in series with the *if* plate and diode detector small, and in the case of V₆ to keep the impedance in the grid of V₆ small to prevent bias from developing on this grid by noise pulses which are of sufficient amplitude to draw grid current. If bias were produced, the gain would be reduced for a time following each noise pulse. Each noise pulse, which modulates the carrier towards the black level, is followed by a white tail which would produce objectionable on the picture. The *agc* voltage is applied to the grids of the first and second *if* tubes.

The video detector is a conventional diode. The input to the detector is tapped down on L₂₄ to obtain the proper operating Q. The output of the detector is fed through a series peaking choke, L₂₅, and a shunt peaking choke, L₂₆, to the input of the video amplifier. In this manner a video response is obtained relatively flat to 3.5 mc.

Automatic Gain Control



The automatic gain control circuit utilizes one-half of a 6AL5. The *agc* action in TV receivers is comparable to that of *avc* in conventional receivers. In this model *agc* is applied to the first two *if* tubes and the first *rf* to keep the contrast of the picture fairly constant with different signal input levels. This permits the op-

(Continued on page 41)

CAPACITORS		CAPACITORS	
C-1	Ceramic, 300 mfd., 500 vdc	C-17	Ceramic, 0.005 mfd., 500 vdc
C-2	Ceramic, 0.005 mfd., 500 vdc	C-18	Ceramic, 0.005 mfd., 500 vdc
C-3	Mica, 470 mfd., 500 vdc	C-19	Ceramic, 0.005 mfd., 500 vdc
C-4	Mica, 470 mfd., 500 vdc	C-20	Ceramic, 0.005 mfd., 500 vdc
C-5	Ceramic, 1 mfd., 500 vdc	C-21	Ceramic, 0.005 mfd., 500 vdc
C-6	Ceramic, 300 mfd., 500 vdc	C-22	Ceramic, 0.005 mfd., 500 vdc
C-7	Ceramic, 300 mfd., 500 vdc	C-23	Ceramic, 0.005 mfd., 500 vdc
C-8	Ceramic, 22 mfd., 500 vdc	C-24	Paper, 0.25 mfd., 400 vdc
C-9	Ceramic, 1 mfd., 500 vdc	C-25	Mica, 300 mfd., 500 vdc
C-10	Ceramic, 300 mfd., 500 vdc	C-26	Mica, 2200 mfd., 500 vdc
C-11	Ceramic, 300 mfd., 500 vdc	C-27	Mica, 330 mfd., 500 vdc
C-12	Not used	C-28	Ceramic, 3 mfd., 47 mfd., 500 vdc
C-13	Ceramic, 25 mfd., 500 vdc	C-29	Ceramic, 10 mfd., 500 vdc
C-14	Variable (Special)	C-30	Paper, 0.1 mfd., 400 vdc
C-15	Ceramic, 0.005 mfd., 500 vdc	C-31	Ceramic, 5 mfd., 25 mfd., 500 vdc
C-16	Ceramic, 300 mfd., 500 vdc	C-32	Ceramic, 1 mfd., 500 vdc
C-17	Ceramic, 1500 mfd., 500 vdc	C-33	Paper, 1 mfd., 400 vdc
C-18	Ceramic, 0.005 mfd., 500 vdc	C-34	Elect., 10 mfd., 400 vdc
C-19	Ceramic, 300 mfd., 500 vdc	C-35	Paper, .05 mfd., 400 vdc
C-20	Ceramic, 1500 mfd., 500 vdc	C-36	Paper, 0.005 mfd., 500 vdc
C-21	Ceramic, 0.005 mfd., 500 vdc	C-37	Paper, 0.1 mfd., 400 vdc
C-22	Ceramic, 0.005 mfd., 500 vdc	C-38	Elect., 10 mfd., 25 vdc
C-23	Ceramic, 0.005 mfd., 500 vdc	C-39	Mica, 330 mfd., 500 vdc
C-24	Paper, 0.25 mfd., 400 vdc	C-40	Paper, .05 mfd., 400 vdc
C-25	Mica, 300 mfd., 500 vdc	C-41	Paper, .02 mfd., 600 vdc
C-26	Mica, 2200 mfd., 500 vdc	C-42	Paper, .005 mfd., 500 vdc
C-27	Mica, 330 mfd., 500 vdc	C-43	Mica, 100 mfd., 500 vdc
C-28	Ceramic, 3 mfd., 47 mfd., 500 vdc	C-44	Paper, .01 mfd., 400 vdc
C-29	Ceramic, 10 mfd., 500 vdc	C-45	Mica, 100 mfd., 500 vdc
C-30	Paper, 0.1 mfd., 400 vdc	C-46	Paper, .01 mfd., 400 vdc
C-31	Ceramic, 5 mfd., 25 mfd., 500 vdc	C-47	Variable Mica, 2.5-35 mfd.
C-32	Ceramic, 1 mfd., 500 vdc	C-48	Ceramic, 500 mfd., 10,000 vdc
C-33	Paper, 1 mfd., 400 vdc	C-49	Ceramic, 500 mfd., 10,000 vdc
C-34	Elect., 10 mfd., 400 vdc		
C-35	Paper, .05 mfd., 400 vdc		
C-36	Paper, 0.005 mfd., 500 vdc		
C-37	Paper, 0.1 mfd., 400 vdc		
C-38	Elect., 10 mfd., 25 vdc		
C-39	Mica, 330 mfd., 500 vdc		
C-40	Paper, .05 mfd., 400 vdc		
C-41	Paper, .02 mfd., 600 vdc		
C-42	Paper, .005 mfd., 500 vdc		
C-43	Mica, 100 mfd., 500 vdc		
C-44	Paper, .01 mfd., 400 vdc		
C-45	Mica, 100 mfd., 500 vdc		
C-46	Paper, .01 mfd., 400 vdc		
C-47	Variable Mica, 2.5-35 mfd.		
C-48	Ceramic, 500 mfd., 10,000 vdc		
C-49	Ceramic, 500 mfd., 10,000 vdc		

Fig. 1 (a) (left) and (b) (right), list of parts for the National TV receiver circuit which appears on page 20.

RESISTORS		RESISTORS	
R-1	1,000 ohms, 1/2 watt	R-50	40 ohms, 5 watts
R-2	100,000 ohms, 1/2 watt	R-51	100 ohms, 1/2 watt
R-3	100 ohms, 1/2 watt	R-52	400 ohms, 2 watts
R-4	5000 ohms, 1/2 watt	R-53	70 ohms, 4 watts
R-5	1000 ohms, 1/2 watt	R-54	1000 ohms, 1 watt
R-6	1,000,000 ohms, 1/2 watt	R-55	2,000,000 ohms, 1 watt
R-7	2000 ohms, 1/2 watt	R-56	10,000 ohms, 1 watt
R-8	18,000 ohms, 1/2 watt	R-57	3,000,000 ohms, 1 watt
R-9	10,000 ohms, 1/2 watt	R-58	5,000,000 ohms, 1 watt
R-10	82 ohms, 1/2 watt	R-59	Variable, 5,000,000 ohms
R-11	100 ohms, 1/2 watt	R-60	100,000 ohms, 1 watt
R-12	100 ohms, 1/2 watt	R-61	100,000 ohms, 1 watt
R-13	10,000 ohms, 1/2 watt	R-62	100,000 ohms, 1 watt
R-14	82 ohms, 1/2 watt	R-63	100,000 ohms, 1 watt
R-15	100 ohms, 1/2 watt	R-64	100,000 ohms, 1 watt
R-16	100 ohms, 1/2 watt	R-65	1,000,000 ohms, 1 watt
R-17	10,000 ohms, 1/2 watt	R-66	1,000,000 ohms, 1 watt
R-18	82 ohms, 1/2 watt	R-67	1,000,000 ohms, 1 watt
R-19	100 ohms, 1/2 watt	R-68	1,000,000 ohms, 1 watt
R-20	340,000 ohms, 1/2 watt	R-69	Variable, 5,000,000 ohms
R-21	22,000 ohms, 1/2 watt	R-70	100 ohms, 1/2 watt
R-22	2,700 ohms, 1/2 watt	R-71	100,000 ohms, 1 watt
R-23	100,000 ohms, 1/2 watt	R-72	1,000,000 ohms, 1 watt
R-24	30,000 ohms, 1 watt	R-73	Variable, 5,000,000 ohms
R-25	8,700 ohms, 1 watt	R-74	100 ohms, 1/2 watt
R-26	8,200 ohms, 1/2 watt	R-75	100,000 ohms, 1 watt
R-27	1,000,000 ohms, 1/2 watt	R-76	Variable, 10,000,000 ohms
R-28	1,000,000 ohms, 1/2 watt	R-77	100,000 ohms, 1/2 watt
R-29	100,000 ohms, 1/2 watt	R-78	100,000 ohms, 1 watt
R-30	Variable, 1,000 ohms, 500	R-79	100,000 ohms, 1 watt
R-31	8,200 ohms, 1/2 watt	R-80	100,000 ohms, 1/2 watt
R-32	1,000,000 ohms, 1/2 watt	R-81	2,000,000 ohms, 1/2 watt
R-33	22,000 ohms, 1/2 watt	R-82	2,000,000 ohms, 1/2 watt
R-34	270 ohms, 1/2 watt	R-83	800,000 ohms, 1/2 watt
R-35	22,000 ohms, 1/2 watt	R-84	100,000 ohms, 1/2 watt
R-36	340 ohms, 1/2 watt	R-85	1,000,000 ohms, 1 watt
R-37	340 ohms, 1/2 watt	R-86	2,700,000 ohms, 1 watt
R-38	180,000 ohms, 1/2 watt	R-87	4,700 ohms, 1/2 watt
R-39	15,000 ohms, 1/2 watt	R-88	Variable, 1,000,000 ohms
R-40	Variable, 35,000 ohms, 1/2 watt	R-89	Variable, 1,000,000 ohms
R-41	150,000 ohms, 1/2 watt	R-90	220,000 ohms, 1/2 watt
R-42	33,000 ohms, 1 watt	R-91	1,200,000 ohms, 1/2 watt
R-43	82 ohms, 1/2 watt	R-92	Variable, 5,000,000 ohms
R-44	470 ohms, 1/2 watt	R-93	10,000 ohms, 1 watt
R-45	26,000 ohms, 2 watts	R-94	10,000 ohms, 1 watt
R-46	33,000 ohms, 1/2 watt	R-95	1,000,000 ohms, 1/2 watt
R-47	33,000 ohms, 1/2 watt	R-96	1,000,000 ohms, 1/2 watt
R-48	Variable and switch, 1,000,000 ohms	R-97	1,000,000 ohms, 2 watts
R-49	8,200,000 ohms, 1/2 watt	R-98	1,000,000 ohms, 1 watt
R-50	390,000 ohms, 1/2 watt	R-99	2,700,000 ohms, 1 watt
R-51	270,000 ohms, 1/2 watt	R-100	100,000 ohms, 1 watt
R-52	47,000 ohms, 1/2 watt	R-101	1,000,000 ohms, 1/2 watt
R-53	100 ohms, 1/2 watt	R-102	1,000,000 ohms, 1/2 watt
R-54	20 ohms, 10 watts	R-103	100,000 ohms, 1 watt
R-55	82 ohms, 1/2 watt	R-104	1,000,000 ohms, 1 watt

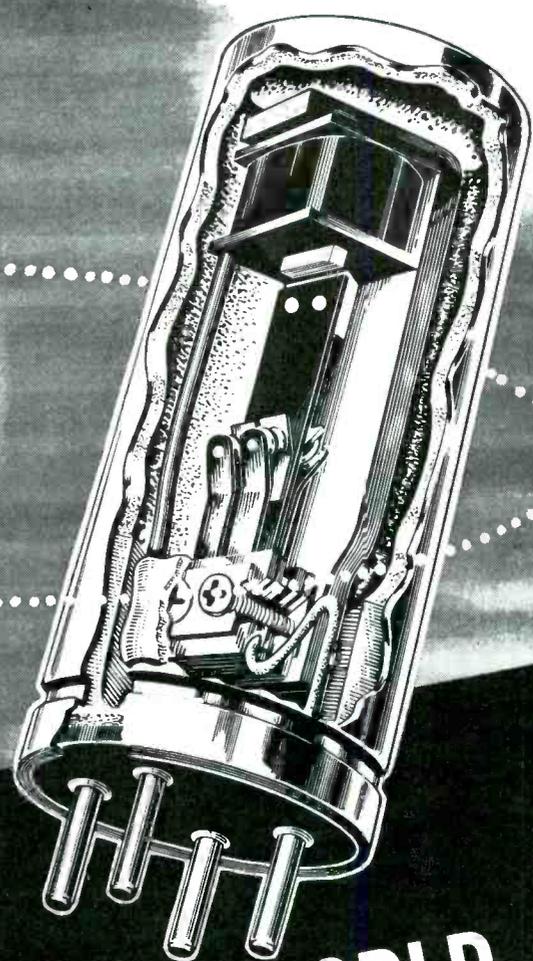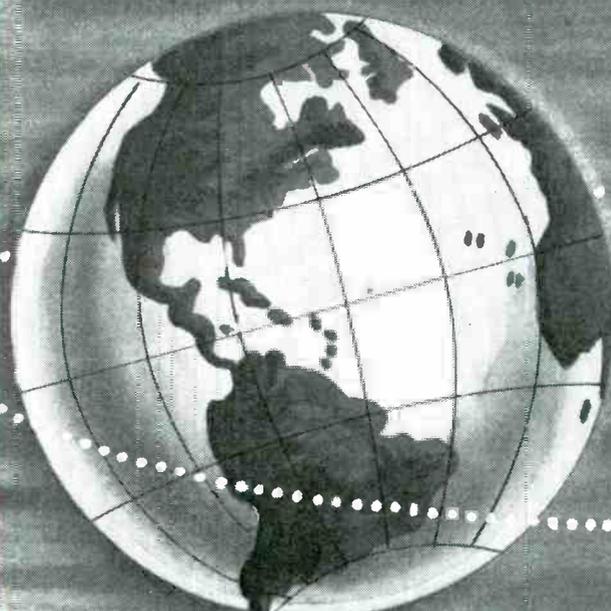

The Most Complete REPLACEMENT VIBRATOR LINE IN THE WORLD

Reputation is not built overnight! Radiart's reputation has grown over the years because of its many points of superiority! Beyond the fact that the quality and design of every one of the 82 types of Radiart Vibrators . . . is beyond compare . . . the solid completeness of the line makes them the favorite wherever good vibrators are sold FOR MOST EVERY NEED TO ORIGINAL SPECIFICATIONS . . . there is a CORRECT Radiart replacement vibrator! NO OTHER VIBRATOR MANUFACTURER CAN MAKE THAT STATEMENT! Guess work is eliminated . . . all good jobbers carry most all numbers in stock . . . if your jobber does not have the number you want . . . he can get it, FAST . . . as special orders are given speedy attention . . . with immediate shipment of his order! Insist on Radiart for the EXACT REPLACEMENT Vibrator . . .

IT'S RIGHT WHEN IT'S RADIART



LEADING THE FIELD SINCE 1935

THE RADIART CORPORATION
CLEVELAND 2, OHIO
EXPORT . . . SCHEEL INTERNATIONAL . . . CHICAGO 18, ILLINOIS


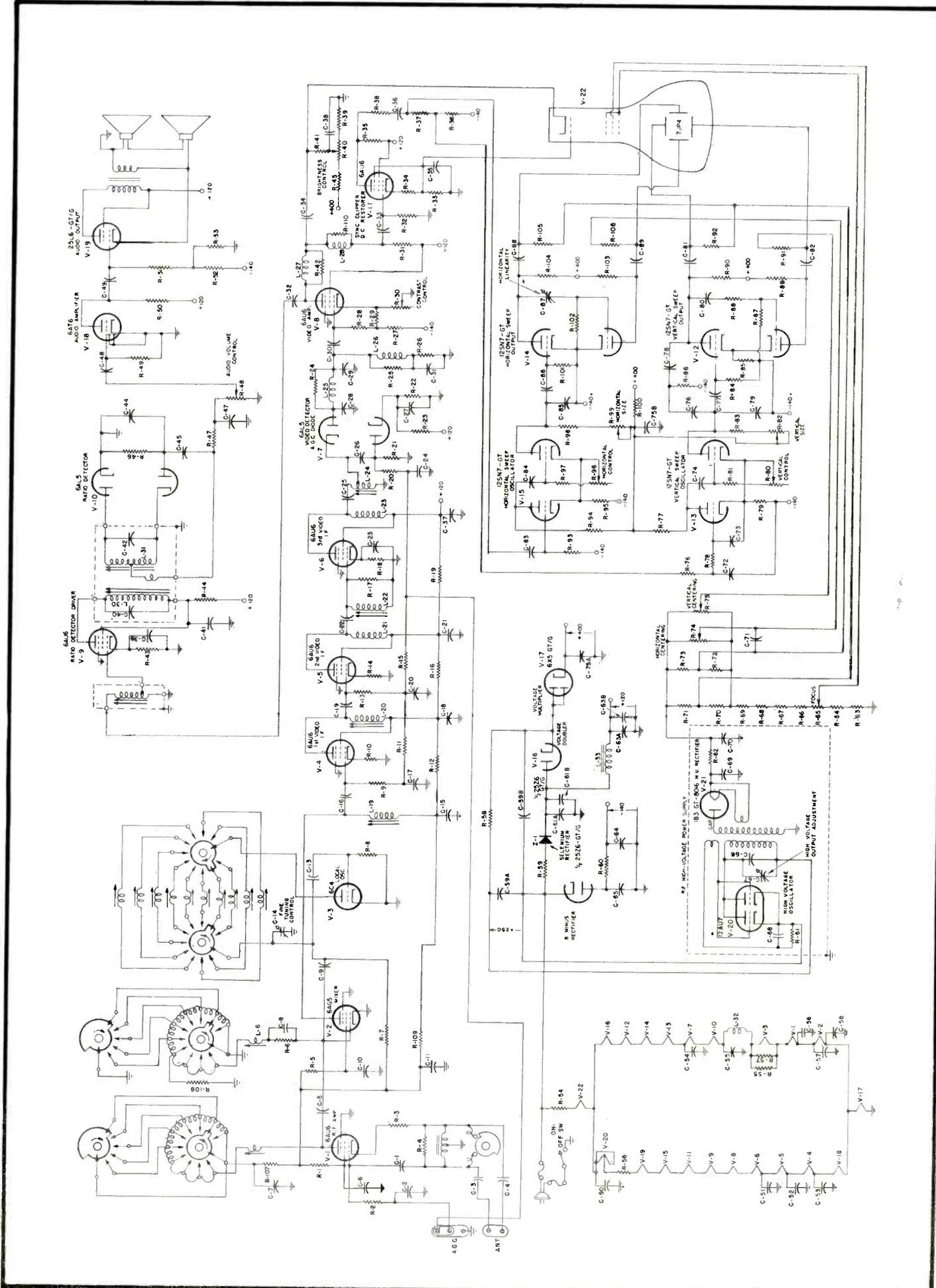
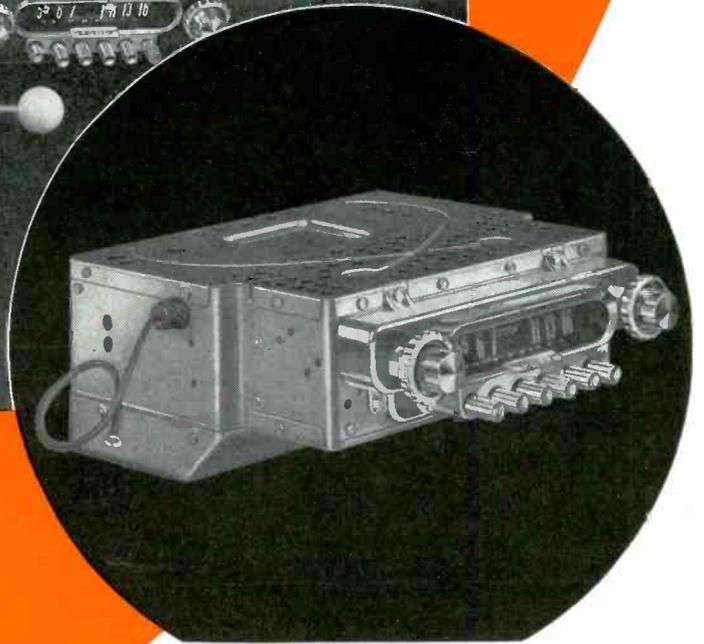


Fig. 1. Complete circuit diagram of the NC-TV-7/NC-TV-7M. (See parts lists on page 18.)

AUTO RADIO and HYTRON go together

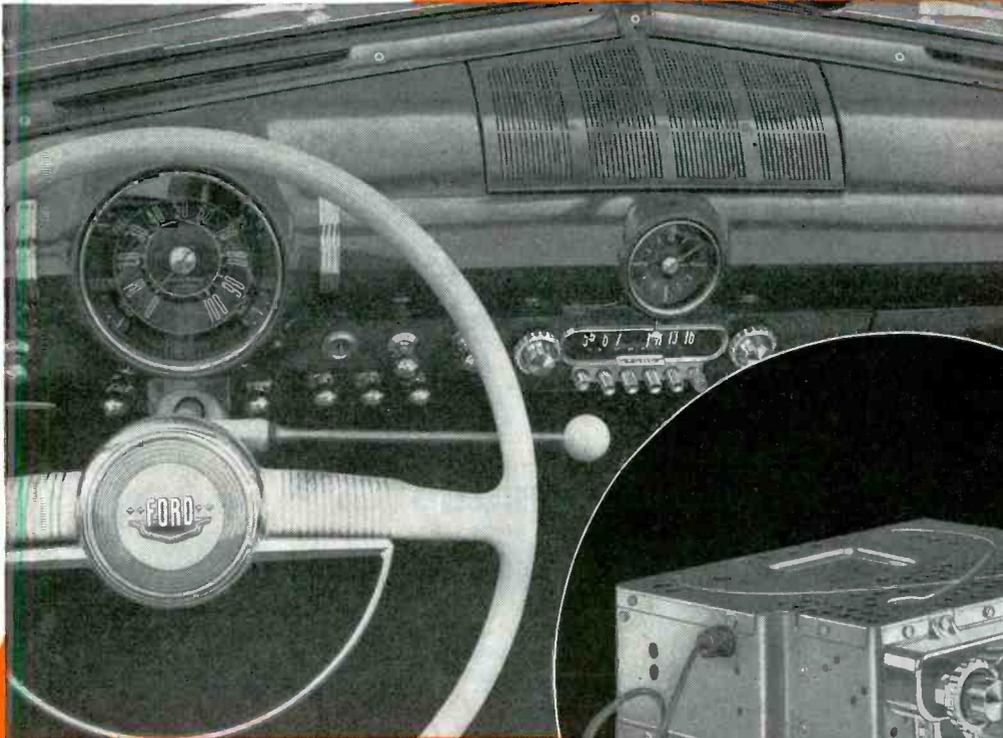

"A Ford in your future?" There will probably be a fine new Ford radio receiver on the dash. Chances are good this receiver will be equipped with tubes by Hytron. For Hytron is a major supplier of Ford auto radio tubes. That is only natural. Hytron *specializes* in auto radio tubes — both GT and miniature. Close engineering co-operation with leaders like Ford help make Hytron auto radio tubes leaders, too. 'Nuff said. Hytron and auto radio go together.

SPECIALISTS IN RADIO RECEIVING TUBES SINCE 1921.

HYTRON

RADIO AND ELECTRONICS CORP.

MAIN OFFICE: SALEM, MASSACHUSETTS



SERVICE, JANUARY, 1949 • 21

TV Receiver Production Changes

First of a Series of Monthly Analyses of Production Changes in TV Receiver Circuit and Mechanical Designs Based on Data Supplied By TV Set Manufacturers. In this Installment Appear Notes on a New String Tuning Drive for the G. E. 810, Improving Audio 1F Selectivity and Brightness Control and Removing Howl in 810; Adding AFC to the Motorola VT71; And Substituting 6AU6s for 6AG5s in the Admiral 30A1.

G. E. 810 Revisions

THE TUNING CONTROL on the G.E. 810¹ TV model has been changed from a rubber pulley friction drive to string drive, to eliminate a small amount of backlash which resulted in critical tuning adjustment on the high frequencies.

When making this change, it is necessary to remove and discard the rubber tuning control pulley, tuning drum and knurled tuning control concentric shaft; Fig. 1.

Vertical Size Change

On late production models, the vertical size potentiometer and R_{106} were interposed to protect the rectifier circuit against damage due to shorts in the vertical size control. The red wire from the vertical size control to the junction of C_{62} and L_{20} should be connected from the same side of the vertical size control to C_{33} . The end of R_{106} connected to C_{33} should be removed and connected to the junction C_{62} and L_{20} .

Audio 1F Selectivity Improvement

To improve the selectivity of the audio if channel on the G.E. 810 and 814 and, increase the attenuation to the video if signal and to vertical pulses which might cause hum or noise, a transformer T_{21} has been substituted for L_6 . The addition of this transformer reduces the audio if band width to approximately 300 kc. (The catalog number for this transformer is RTL-090.) To replace L_6 with T_{21} , it is necessary to remove coupling capacitor C_{38} and coil L_6 . The primary of T_{21} should be connected between pin 5 of V_{22} and the load resistor R_{102} . Terminal 1 of T_{21} should be connected to R_{102} . A

by DONALD PHILLIPS

bypass capacitor C_{300} must be connected from the junction of R_{102} and terminal 1 of T_{21} to ground. Terminal 2 of T_{21} should be connected to pin 5 of V_{22} . Terminal 3 of T_{21} must be connected to ground. Terminal 4 is connected to pin 1 of V_{17} .

This transformer mounts in the same manner as L_6 and is double tuned. Therefore, when tuning this stage, it is necessary to adjust two iron cores of T_{21} for maximum amplitude and symmetry about the 21.8 marker.

Howl in G.E. 810/814

It has been found in the 810 and 814 receivers that howl may be caused by one or more of the three following reasons:

- (1) A microphonic converter-oscillator 12AT7.
- (2) The capacitor, C_3 , located on the head-end unit under the tuning capacitor, may start vibrating.
- (3) The metal guide ring on the rear side of the oscillator wafer rotor

section or the textolite rotor in the oscillator wafer of the channel switch may be loose.

A lead weight (RHX-014) is available to mount over the 12AT7 to dampen out mechanical vibration of the tube envelope and the internal components of the tube.

To prevent the capacitor C_3 from vibrating, a rubber block (RMM-081) may be wedged between the edge of C_3 and the front apron of the head-end unit. To facilitate the installation of this piece, it is suggested that it be cut into a V or wedge shape so that the edge of C_3 will be held in the channel of the rubber cushion.


Item 3 can be corrected by cementing the textolite rotor to the shaft and the rotor guide ring on the rear side of the oscillator wafer rotor to the textolite rotor with *Dekadhes Cement*. Extreme caution should be observed when applying this cement. The cement should only be applied to the guide ring and the textolite rotor. The cement *should not* touch the fingers of electrical contact ring which extends through the textolite rotor.

In these models, R_{21} has been changed from a 3300-ohm 1-watt unit to 3300-ohm 2-watts. It was found that this resistor increased in value slightly, therefore limiting the brightness obtainable on the picture tube.

Adding AFC to Motorola VT71²

IN ADDING AFC to the VT71, it is necessary to change the functions of several tubes and to change one tube: V_{11} , a 12SN7, contains the horizontal sweep oscillator as before and a diode replaces the second clipper; V_{10} , a 12SN7, now contains both clippers; V_7 , formerly a


Fig. 1. How to make a tuning drive change in the G. E. 810 TV receiver. The length of string required for this conversion is 19 1/4".

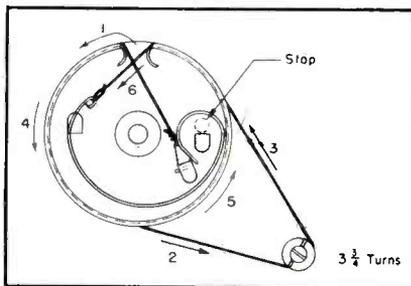

¹SERVICE; December, 1948.
²SERVICE; March, 1948.

**"It's KNOW-HOW
that counts!"**

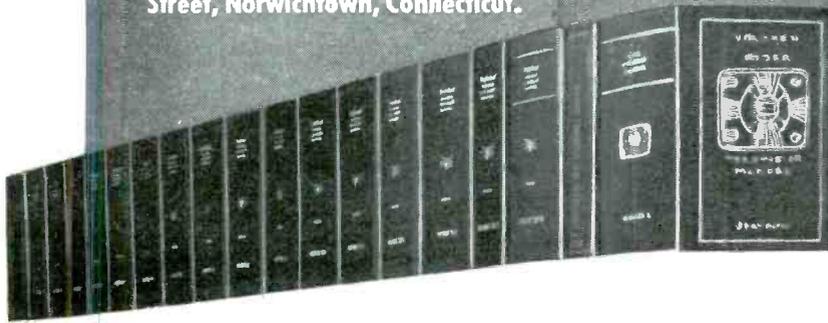— says Bud Ward, Owner of
Ward's Radio Service, 24 Town
Street, Norwichtown, Connecticut.



Bud Ward is an invalid paralyzed from the neck down. He mastered radio and repairs with his "voice"... by directing the hands of an ex-Marine apprenticed to him under the G-I Bill. Though handicapped, Bud Ward is known as a radio wizard around Norwichtown and has built up a mighty successful servicing business. "My Rider Manuals are my bible of radio servicing," says Bud. "Having to use someone else's hands to do my work, the clear and concise service data is a 'must' with me."

**Leading Servicemen from Coast-to-Coast
Build Better Business with**

RIDER MANUALS

A ready-reference for all sets from 1930 to 1948 — Volumes 1 to 18 are at your Jobber's now. He also has Volume 1 of the Rider Television Manual.


"I've got the ONE, now I'm
waiting for the TWO" — Bud Ward

VOLUME

2

**RIDER
TELEVISION MANUAL
PLUS 2 Separate Books, "HOW IT
WORKS" and INDEX**

If you operate in a TV area, a John Rider TV Manual is as important to you as a pair of pliers. Rider Television Manuals contain the OFFICIAL, AUTHENTIC, RELIABLE DATA as supplied by the set manufacturers themselves. You don't have to guess... you know immediately what's wrong and what's to be done. Each Manual includes GIANT SIZE Schematics to guide you and your men to a quick solution of any TV servicing problem.

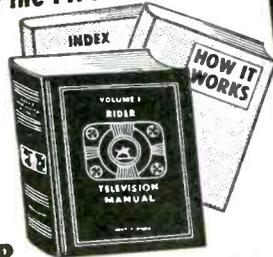

Your Jobber Has It!

RIDER PA MANUAL

The first industry-wide public address equipment Manual incorporating the amplifier production of 147 manufacturers from 1938 to 1948.

2024 Pages PLUS "How It Works" Book which explains theory of various PA circuits and method of rapidly locating faults. **\$18.00**
Including index.


RIDER MANUALS

Television Manual, Volume 1 (plus How It Works and Index)	\$18.00
Volume XVIII	19.80
Volume XVII	16.50
Volume XVI	8.40
Volume XV	19.80
Volume XIV to VII (each volume)	16.50
Volume VI	12.50
Abridged Manuals I to V (one volume)	19.80
Record Changers and Recorders	9.00
Master Index, Covering Manuals, Vols. I to XV	1.50

Order Now!

VOLUME

18

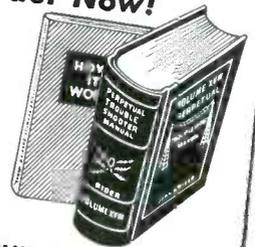

2036 Pages PLUS Separate "How It Works" Book and Cumulative Volumes XVI, XVII, and XVIII INDEX. Both Books, Complete... **\$19.80**

Rider Manuals Give You

- GREATEST COVERAGE... 27,000 models and 14,000 chassis in 25,830 pages... AM and FM.
- AUTHORIZED FACTORY-FACTS... servicing techniques direct from the set manufacturers themselves.
- CIRCUIT THEORIES EXPLAINED... "How It Works" Books explain electronic and mechanical innovations in sets covered by Manuals.
- LOWER COST... Rider Manuals deliver data at less than a penny per receiver model.

RIDER MANUALS mean SUCCESSFUL SERVICING

JOHN F. RIDER, PUBLISHER, Inc.
480 Canal Street, New York 13, N. Y.
Export Agent: Rocke International Corp., 13 E. 40th St., N.Y.C.
Cable, ARLAB.

NOTE: The Mallory Radio Service Encyclopedia, 6th edition, makes reference to only one source of radio receiver schematics—Rider Manuals.
ANOTHER NOTE: The C-D Capacitor Manual for Radio Servicing, 1948 edition No. 4, makes reference to only one source of receiver schematics—Rider Manuals.

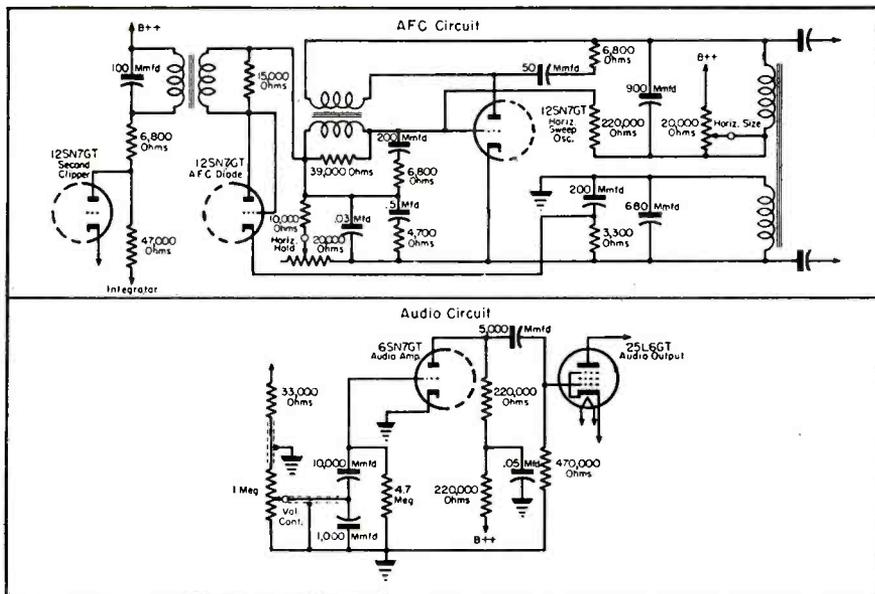


Fig. 2. Circuits developed to provide *afc* for the Motorola VT71 TV receiver. The audio circuit changes required are also shown in this figure.

6SQ7, has been changed in production to a 12SN7 and contains the first audio amplifier and the vertical sweep oscillator. In adding *afc* to existing receivers, however, a 6SN7 is used in place of the 6SQ7 in the V_7 socket. This simplifies the filament circuit change considerably.

Physical Layout Changes

Except for the filament circuit, the addition is identical electrically with current production. However, there is a considerable difference in the physical layout of the components made to simplify the change.

Procedure

- (1) Clip out lead grounding pin 1, V_7 ; remove couplate (printed circuit) entirely.
- (2) Move C_{131} , .005 from pin 2 to pin 1, V_7 ; add another .005 in parallel or use a .01 in place of C_{131} .
- (3) Move one end of R_{54} , 4.7 meg from pin 2 to pin 1, V_7 .
- (4) Clip out jumper between pins 3, 4 and 5, V_7 , and put jumper between pins 3 and 6, V_7 .
- (5) Remove C_{138} , 1000, from terminal strip west³ of V_7 and connect it between pin 3, V_7 , and the same terminal on the strip east of V_7 to which C_{131} , .01, and the shielded green lead are attached.
- (6) Add 220,000-ohm unit between pin 2, V_7 , and junction of R_{30} , 220,000 ohms and C_{41} , .05.
- (7) Add 220,000-ohms between pin 5, V_{12} , and B— on strip east of V_7 .
- (8) Add .005 between pin 2, V_7 and pin 5, V_{12} .
- (9) Clip out white lead from pin 6 of the ballast tube to the selenium rectifier (B—); this is the only filament change required.
- (10) Unsolder all leads going to pins 2, 3, 4, 5 and 6, V_{10} . Remove entirely blue lead going to pin 2.
- (11) Clip red lead (B+) from pin 6, V_{11} , and solder it to pin 6, V_{10} .
- (12) Unsolder all leads going to pins 4, 5 and 6, V_{11} . Remove completely from circuit, .05 from pin 4, 1 meg from pin 6, 10,000 ohms from pins 4 and 6, 50 mmfd from pins 5 and 1, 6800 from pin 5 and 3900 ohms from pin 2.

- (13) Add 10,000 ohms from pin 4 to pin 6, V_{10} .
- (14) Add 1 meg from pin 2 to pin 6, V_{10} .
- (15) Add .05 mfd. from pin 2 to pin 4 (lay it next to chassis southwest of V_{10} , use spaghetti on leads).
- (16) Move two white leads (B—) which were on pin 6 to pin 3, V_{10} .
- (17) Add terminal strip (one grounded, two insulated terminals), bolting or riveting through hole southeast of V_{10} .
- (18) Run lead from pin 5, V_7 , across chassis to terminal 1 (southernmost) on strip just put in.
- (19) Add blue lead from R_{54} , 3.3 meg, on strip south of V_8 to same point (terminal 1).
- (20) Run lead from pin 4, V_7 , across chassis to terminal 2 (northernmost) of strip just installed.
- (21) Tie C_{54} , .1 mfd, from vertical hold control to terminal 1 of same strip.
- (22) Tie C_{141} , C_{110} and R_{114} (.001, 250, and 3.3 megohms respectively) to terminal 2 of same strip.
- (23) Replace C_{51} , .01, with .03 (runs from horizontal hold control).
- (24) Construct and install sub-assembly: (100 mmfd, pins 1 to 3, 15,000-ohm pins 2 to 4, transformer red lead to pin 4, other lead from same end to pin 3, green lead to pin 1, other lead to pin 2. Mount with bolt or rivet on north side of strip through easternmost of the two holes north of V_{11} . Terminal 1 goes on the west terminal 4 on the east.
- (25) Connect lead from pin 4, sub-assembly, to pins 4 and 5, V_{11} .
- (26) Connect lead from pin 3, sub-assembly, B++ on horizontal size pot.
- (27) Connect lead from pin 2, sub-assembly, to junction of R_{111} , R_{110} and C_{51} .
- (28) Connect loose ends of C_{17} , .01, and C_{48} , .01, to pin 3, V_{10} .
- (29) Connect R_{44} , 47,000 ohms, to pin 5, V_{10} .
- (30) Put R_{48} , 6,800 ohms, between pin 5, V_{10} , and pin 1 sub-assembly.
- (31) Add 3,300 ohms from pin 3 to pin 6, V_{11} .
- (32) Add 200 mmfd from pin 6, V_{11} , to any convenient B— point (e.g. pin 3, V_8).
- (33) Add .5 (200 μ) from pin 2, sub-assembly, to open lug (terminal 2) on terminal strip south of V_{11} . Put capacitor close to chassis in open area east of V_{11} .
- (34) Add 4,700 ohms from pin 3, V_{11} , to terminal 2 of strip mentioned in step 33.
- (35) Add 6,800 ohms and 200 mmfd in series

³Locations are specified by points of the compass using this convention; with the chassis upside down, the front panel controls are north, the hold controls, etc., are south, the selenium rectifiers are west, etc.

⁴SERVICE; October, 1948.

- across R_{110} , 39,000 ohms (from pin 1, V_{11}).
- (36) Add 6,800 ohms and 50 mmfd (use C_{10} which was removed) in series from pin 2, V_{11} , to terminal 1 on terminal strip south of V_{11} . This terminal 1 already has one of the blocking oscillator leads attached to it.
- (37) Add 220,000 ohms, 2 watts, from horizontal size arm to pin 1, V_{11} .
- (38) Replace C_{66} , .05, in the high voltage oscillator stage with a 10 mfd, 350 v.
- (39) Replace C_{138} , 900 mmfd, with 680 mmfd.
- (40) Replace V_7 , 6SQ7, with a 6SN7.

Admiral 30A1⁴ Revisions

Tube substitution: The 6AG5s have been used for V_{302} and V_{303} in the 30A1 models. Future production will use 6AU6s as a substitute. Due to differences in interelectrode capacities, video *if* transformers T_{301} and T_{302} must be changed when the 6AU6s are used. (When 6AU6s are used for V_{302} and V_{303} , T_{301} will be part number 72A81 and T_{302} will be part number 72A82. Connections to the substitute transformers are identical to those used with transformers 72B40 and 72B41, used with 6AG5s).

Chassis Code Changes

When 6AU6s are used for V_{302} and V_{303} in place of 6AG5s, the chassis will be identified by E after the chassis type number. For example, such a chassis would be marked 30A1S-E.

Pulling at Top of Picture

In the Admiral 30A1 receivers, pulling at the top of the picture may show up in some models across the top of the picture extending approximately 1" down from the top of the picture. It can be noticed when there are vertical lines running to the top of the picture or pattern. These lines will pull to the right or left for a distance of 1" from the top of the picture.



Trouble in Vertical Sync

This trouble is caused by a portion of the vertical synchronization pulses riding through the horizontal sync discriminator circuit and upsetting the horizontal oscillator momentarily. As the vertical sync pulses occur 60 times per second this out of phase condition would exist immediately after the vertical blanking pulses and therefore show up in the top portion of the picture only. The low-frequency response of the horizontal sync discriminator can be reduced to overcome this problem. It is recommended that resistors R_{413} and R_{414} be changed from 470,000 ohms each to 180,000 ohms each. It will then be necessary to readjust the horizontal oscillator.

This change is being made in production at present.

Your Raytheon Tube Distributor Hands Prestige to You on a Platter

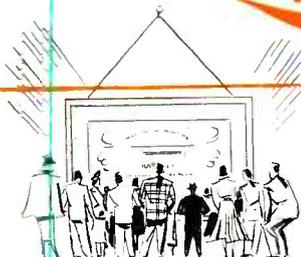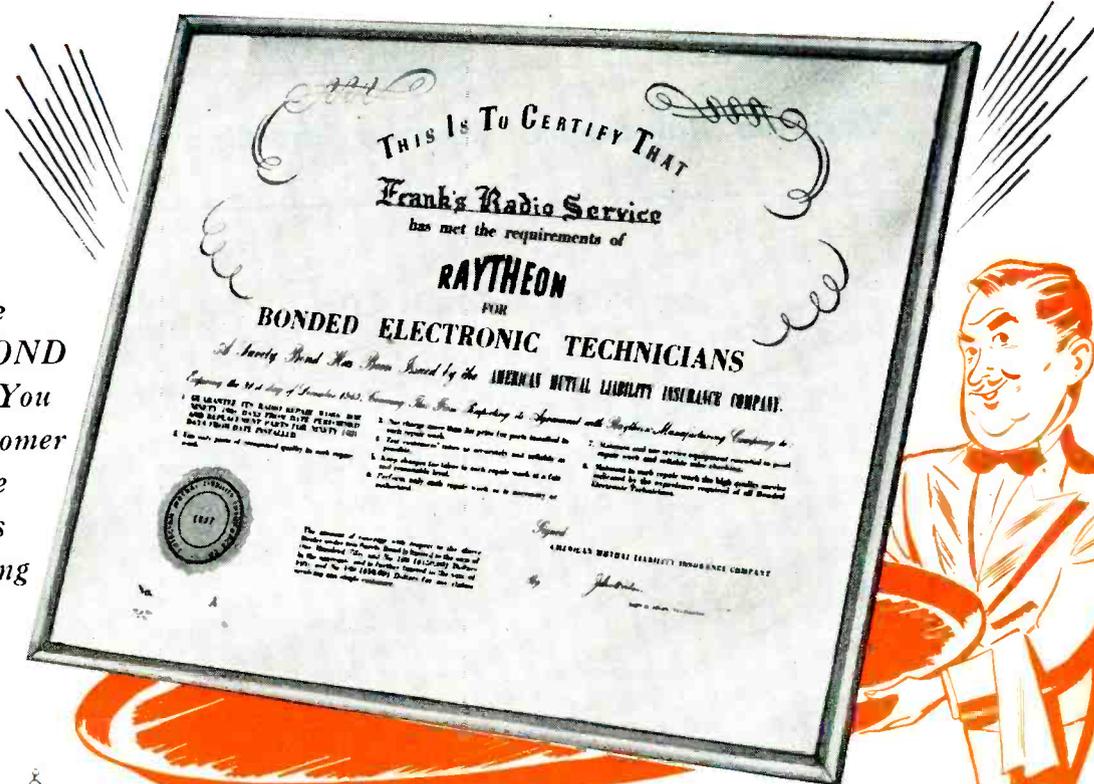— A Service Guarantee BOND That Offers You Genuine Customer Insurance — Yet Costs You Nothing



This RAYTHEON SURETY BOND is the best evidence you can give your customers that you stand out from the crowd when it comes to the quality and reliability of radio service. It's an iron-clad 90-day BONDED guarantee on your labor and parts backed by a nationally known insurance company with assets of close to a hundred million dollars!

Raytheon pays for this Bond

The Raytheon Tube Distributor in your area has it ready for you—if you can qualify. Get in touch with him at once and start getting the cream of the business in your locality.

Why RAYTHEON Tubes

- 1. Good tubes** — produced by one of the oldest and soundest manufacturers in the industry—with an unsurpassed reputation for engineering achievement in electronics, and with the most advanced methods and equipment for quality control.
- 2. Best Distributors** — Raytheon Tube distributors are carefully chosen. You'll recognize the one nearest you as one of the best parts distributors in town. He has to be, as sponsor of the Raytheon Bonded Dealer Program.
- 3. Consistently advertised** — Raytheon national advertising and point-of-sale display material constantly reminds your customers and prospects of the value of the Raytheon name on every tube.
- 4. Universally accepted** — From the biggest Magnetrons to the tiniest hearing aid tubes Raytheon stands for quality. Raytheon tubes are instantly accepted as the finest that can be had.

Why RAYTHEON Bantal Tubes



The new Raytheon Bantal Tube simplifies your tube stock while it gives you a better tube to sell—rugged eight pillar construction, completely shielded internally means superiority in performance. Eight fast-moving Bantals replace sixteen equivalent GT and metal types.

Always ask for Raytheon Bantals

RAYTHEON

Excellence in Electronics

RAYTHEON MANUFACTURING COMPANY

RADIO RECEIVING TUBE DIVISION

NEWTON, MASSACHUSETTS • CHICAGO, ILLINOIS • LOS ANGELES, CALIFORNIA

RADIO RECEIVING TUBES • SUBMINIATURE TUBES • SPECIAL PURPOSE TUBES • MICROWAVE TUBES

Servicing Helps

Variable Reluctance Preamp Equalization

Preamp—Equalization*

To PERMIT the use of the variable reluctance type pickup¹ with the phono systems of normal receivers and audio amplifiers, it is necessary to employ a pream-equalizer.² Equalization provided in the dual-purpose unit affords the best compromise between record noise and high-frequency response and low-frequency response and rumble due to off-center recordings or turntables.

Magnetic reproducers operate on a velocity basis; that is, the output voltage is proportional to the velocity of the stylus movement when tracing a record groove. Present day recordings are made with a characteristic as shown in Fig. 1. This is an average curve and varies from manufacturer to manufacturer, no standards having been set for the industry. The frequency at which the low end of the curve starts to drop varies from 300 to 500 cycles depending upon the manufacturer, and the point at which the high-frequency end of the curve starts to rise ranges in the region of 1000 to 2000 cycles, although here too the ex-

by P. M. RANDOLPH

act frequency and the amount of rise vary with the manufacturer. Some of the available recordings do not have the high-frequency increase at all. Generally these are the older recordings which have been re-released.

Fig. 1 also represents the output voltage of an ideal magnetic device reproducing the average present day recordings. The output below the low-frequency cross-over point falls off 6 db/octave, the output above the high-frequency cross over point rises 0-6 db/octave. Thus it can be seen that equalization of the cartridge output is necessary to provide satisfactory reproduction.

It has been found that full equalization of the low-frequency portion of the curve is not desirable, since there are heavy low-frequency elements present in the reproduction due to imperfections in the turntable and motor

*From notes prepared by N. S. Cromwell, G. E.
¹G. E. RPX-010.
²G. E. SPX-001.

bearings, and to eccentricities and rough spots in the recording. These low-frequency elements are composed of extremely high-signal levels and will overload the amplifier and loudspeaker unless care is taken to provide low-frequency attenuation. To provide a means of reducing these objectionable low-frequency elements, the low-frequency compensation in the variable-reluctance preamp-equalizer has been designed to have a 3 db/octave rise rather than the full 6 db. This provides satisfactory bass response for all but very few applications and effectively reduces the low-frequency rumbles. The 50-cycle response with the equalization provided is down about 8 db from the theoretically perfect response which would be achieved by the use of 6 db/octave equalization. This is not serious, since bass equalization must be provided in the main amplifier to compensate for the low-frequency characteristic of the human ear. The degree of compensation required depends upon the volume at which the sound is being reproduced, and is of the order of 25 to 30 db at normal room listening level. It can be seen that the 8 db is of minor importance as compared to the 25 to 30 db loss in the ear. The shape of the curve of the preamplifier response characteristic, however, is such that the extreme low frequencies, below the useful limit, are considerably attenuated and the rumble frequencies reduced. (L_f compensation is provided by R₁₀₅, R₁₀₄ and C₁₀₃.)

If required, the low-frequency response can be maintained ±2db from
 (Continued on page 47)

Fig. 2. Schematic of preamp equalizer; G.E. SPX-001.



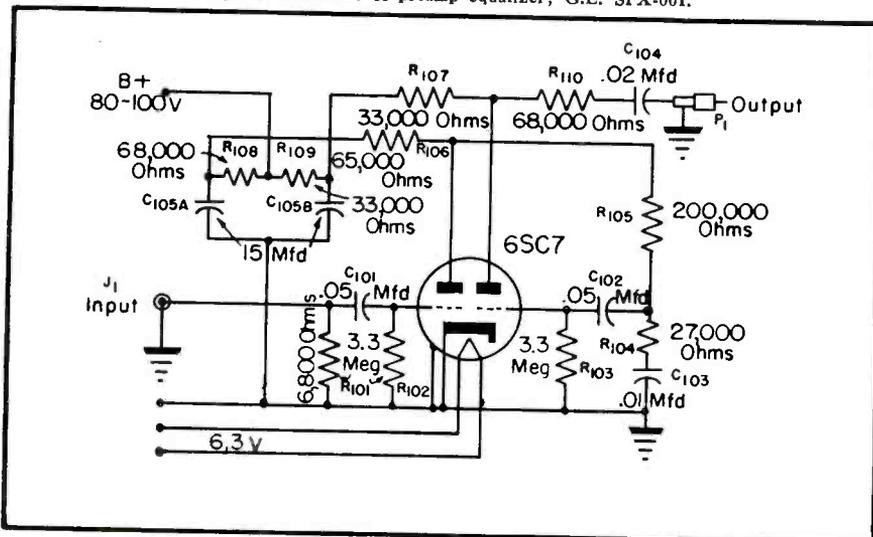


Fig. 1. Velocity characteristic of average present day recordings.

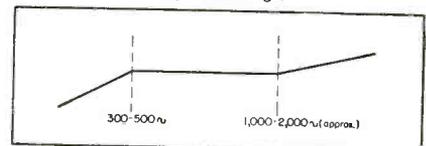

NEW!

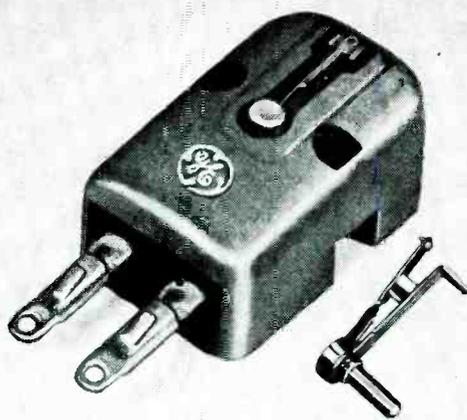

G-E VARIABLE RELUCTANCE CARTRIDGE

*with the replaceable stylus for
Conventional and Long Playing Records*

NOW—in one small unit—all the sales and performance advantages of the G-E Variable Reluctance Cartridge plus this additional consumer economy feature—the Replaceable Stylus.

Negligible needle scratch and needle talk, minimum record wear, wide frequency response, freedom from resonance peaks, realistic reproduction—these are maintained at all times, simply, easily, economically with the Replaceable Stylus.

No more changing of the entire cartridge means more frequent replacement of stylus by the consumer because he can do it himself so easily.

Four simple steps—and presto! The worn stylus is replaced and maximum high quality performance is restored for the critical listener.


Note, too, these additional features:

- New notched design . . . one-third smaller . . . improved shape . . . more generally adaptable to various tone arms.
- More clearance for record changers.
- Higher lateral compliance for more faithful tracking.
- More economical for the customer—more sales for the dealer.
- Cartridges available for LP records with 1 mil stylus; for conventional records with 3 mil stylus.

For complete information on the new Variable Reluctance Cartridge write: *General Electric Company, Electronics Park, Syracuse, New York.*



1 Simply remove cartridge from tone arm.

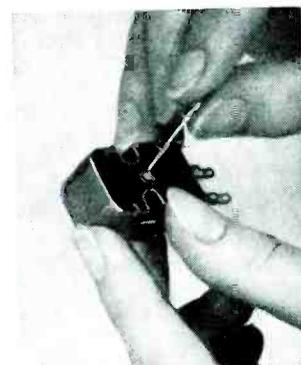

2 Use paper clip or wire to force stylus out of the cartridge.



3 Insert new stylus into cartridge with fingers.




4 Press firmly into position with thumb nail.

You can put your confidence in—

GENERAL ELECTRIC

178-H1

SERVICE, JANUARY, 1949 • 27

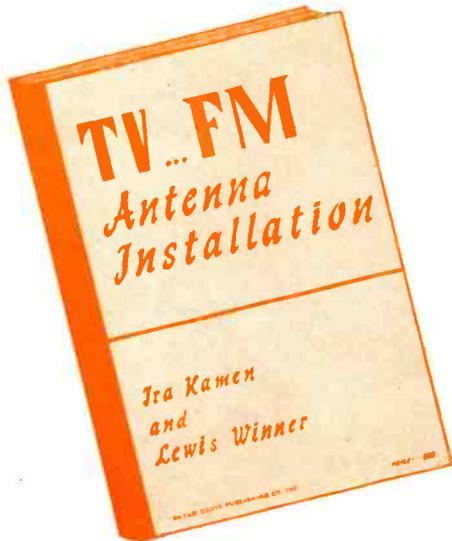

HERE IT IS—

THE FIRST PRACTICAL BOOK

ON THE INSTALLING OF TV and FM RECEIVER ANTENNAS

TV...FM ANTENNA INSTALLATION

OVER 100 PAGES OF PROFUSELY
DIAGRAMMED, PRACTICAL,
UP-TO-THE-MINUTE
INFORMATION COVERING—

by IRA KAMEN
and LEWIS WINNER

Antenna Tools

(Basic Tools Required . . . Application of the Correct Tools for Specific Types of Installations, Involving Flat-top Roofs, Slate Roofs, Tile Roofs, Chimneys, Etc.)

The TV Antenna Installation Problem

(Fundamentals of All TV Installations . . . Judging Specific Application Features of the Various Types of Antennas Which Can Be Used for TV Work . . . Solving Reflection Problems . . . Improving Signal-to-Noise Ratio.)

Solving the Problems of 12-Channel Reception

(Factors With Which Service Men Must Be Familiar to Accurately Install Antennas For Full-Band Coverage . . . Typical Problems Analyzed.)

High Frequency TV Antenna Installations

(Antennas and Installation Procedures Which Afford Best Results. Solving Major Installation Problems Involving Tuned Indoor and Outdoor Antennas. Application of Stub Filters.)

TV Interference

(Analysis of Nine Sources of Interference and Solutions Which Have Proved Effective.)

Fringe Reception

(Selecting and Installing Antennas for Maximum Reception in Areas Over 45 Miles From Stations.)

TV Master Antenna Systems

(Typical Multiple Dwelling Antenna Systems for Simultaneous Operation of Many Receivers From a Single Antenna Array and Amplifier Setup.)

FM Antennas

(Analysis of Practical FM Antennas . . . Selecting Proper Antenna for Rural and Urban Jobs.)

The Business of TV Antenna Installations

(How to Conduct Successfully TV Installation and Service Work Today . . . Proper Use of Correct Types of Installation and Servicing Agreements and Warranties.)

TV Antenna Tricks of the Trade

(Indexed for Quick Reference)

BRYAN DAVIS PUBLISHING CO., INC., Book Dept.
52 Vanderbilt Avenue, New York 17, N. Y.

Send me a copy of TV . . . FM Antenna Installation, post-paid, for which I am enclosing \$2.00.

NAME

ADDRESS

CITY AND STATE


28 • SERVICE, JANUARY, 1949

● The first edition, now going to press, is limited in quantity. Order Your Copy NOW!

Price \$2 Post Paid

MAKES THE BEST TELEVISION RECEPTION BETTER

THE
Quality
ANTENNA
LINE

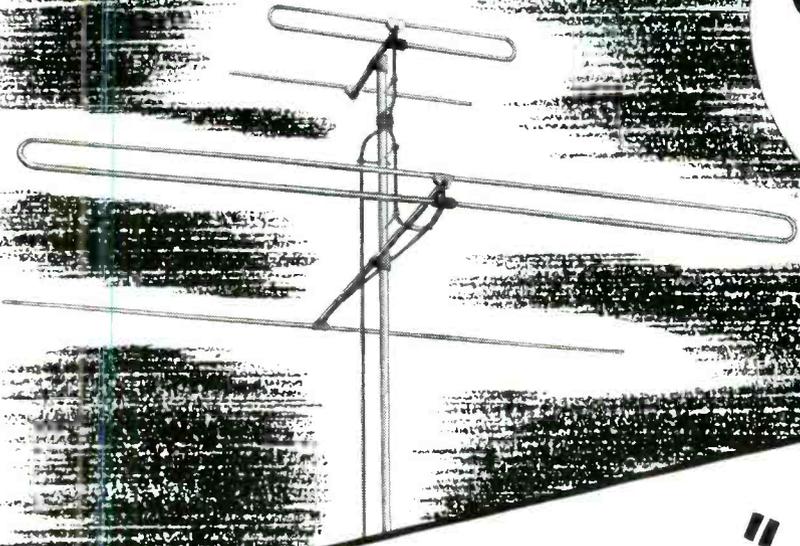

"Simpli-Flex" TELEVISION and FM ANTENNAS

SIMPLI-FLEX means just what it says! SIMple to install . . . FLEXible for any requirement! Its design allows it to be built up from the basic dipole to multiple stacked all-channel arrays by the addition of reflector kits and additional arrays as required when more stations get on the air.

● Here is the most successful . . . the best engineered antenna line in the field! The Radiart line of antennas is GUARANTEED to produce the ultimate in television and FM reception . . . covering all 12 channels! Radiart Simpli-Flex antennas get the picture — where others fail . . . so install RADIART . . . for TROUBLE FREE . . . SPEEDY . . . AND LESS COSTLY INSTALLATION!



No "assembly puzzles" with Radiart's "SIMPLI-FLEX" design. No degree in engineering or truck-load of tools needed — absolutely no loose hardware. One minute assembly, one man installation!



High strength, well engineered design of more than ample safety factor, with simple, sturdy all aluminum castings, elements, and heat-treated support masts for PERMANENT installations.



"WEATHER-SHIELD" polystyrene terminal block encloses lead-in connections and protects from all weather conditions! Keeps electrical performance at maximum.




IT'S RIGHT WHEN IT'S RADIART

THE RADIART CORPORATION

CLEVELAND 2, OHIO

MANUFACTURERS OF THE FAMOUS RED SEAL VIBRATORS

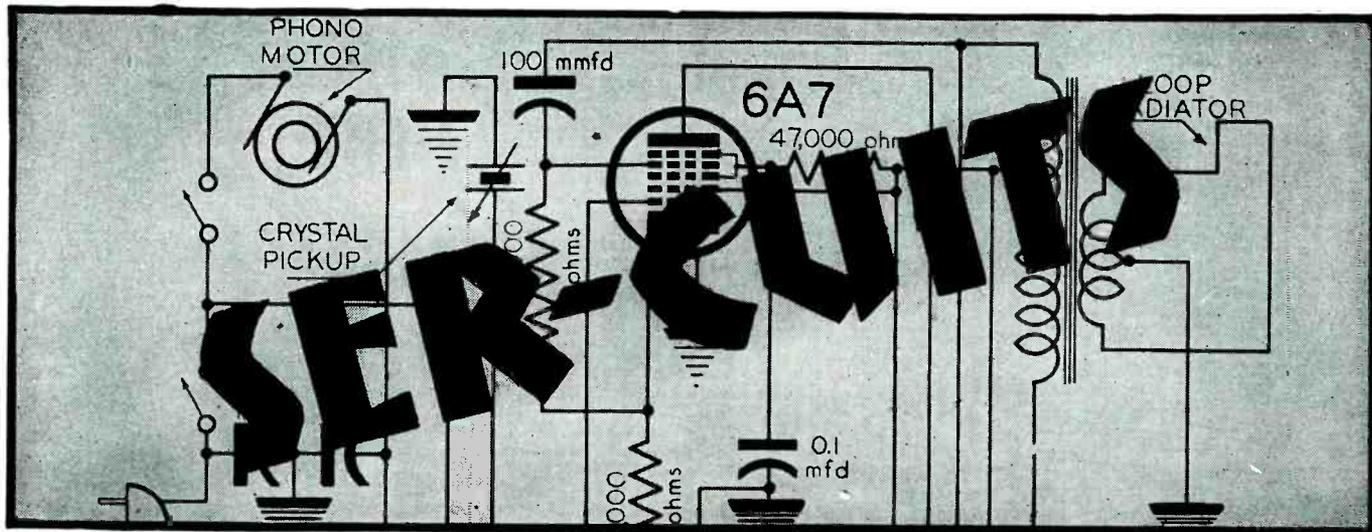EXPORT . . . SCHEEL INTERNATIONAL . . . CHICAGO 18, ILLINOIS



Olympic TV Duplicator Circuit . . . The Hallicrafters T-61/T-67 Push-Button TV Model . . . Farnsworth GV 260 Differentiation and Horizontal Control System.


TV DUPLICATORS, which are becoming increasingly popular in the home as well as hotel, contain many interesting circuit innovations. In one type, the Olympic RTU-3, shown in Fig. 1, there are 10 tubes including the rec-

tifiers and picture tube: Video amplifier which is flat to 4 mc, *dc* restorer, vertical and horizontal blocking oscillators, vertical and horizontal output, synchronization amplifiers and clippers,

power supplies for high and low voltage supply, and audio amplifier.

The signal to acutate the duplicator unit is obtained from the video and audio output stages of the television receiver. These signals are fed from

Fig. 1. The Olympic RTU-3 duplicator.

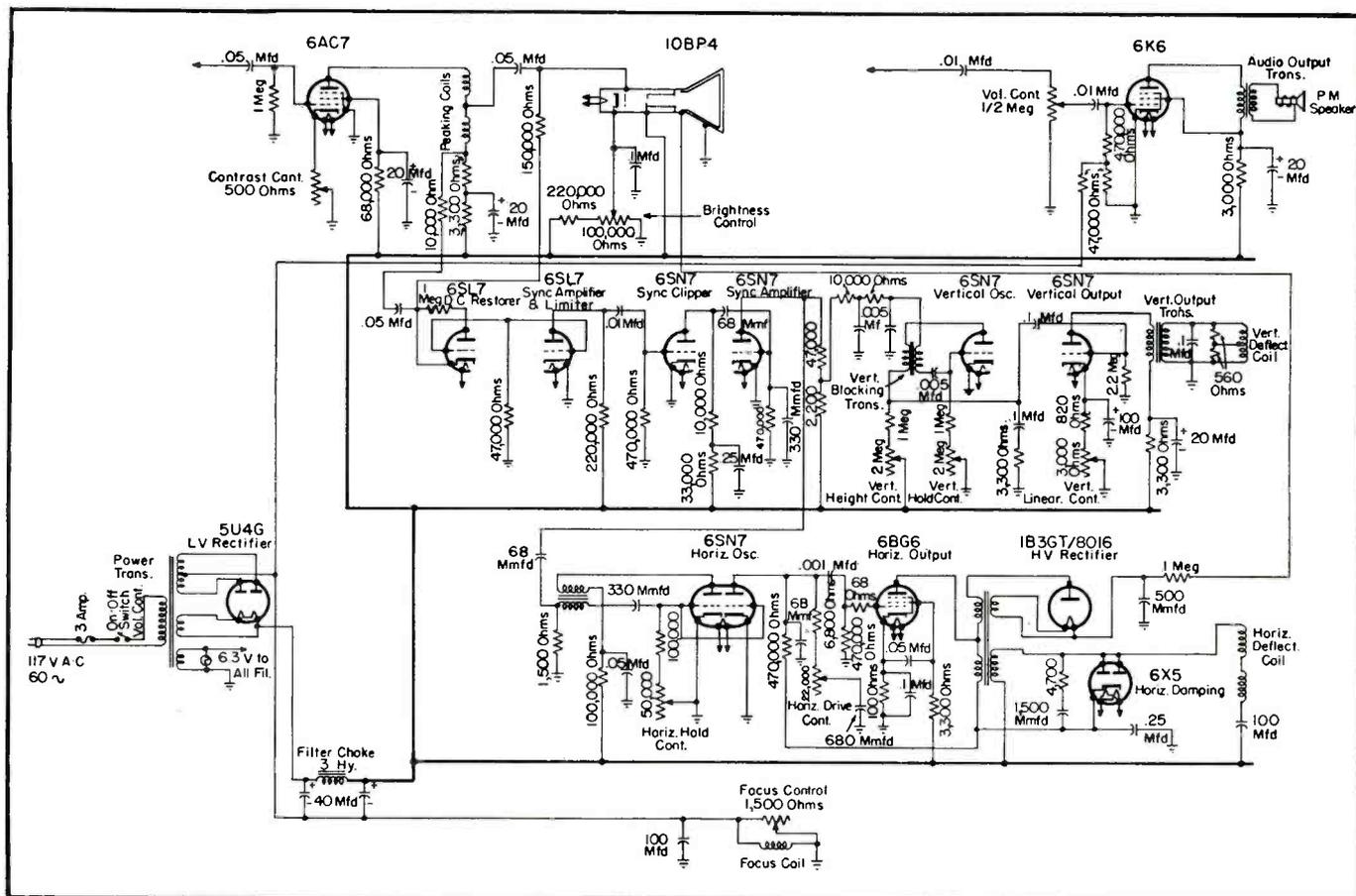

the receiver to the duplicator unit by a special coax cable consisting of RG62/U and a single insulated conductor. The video connection to the television receiver is made at the video output tube. This is the last tube in the video amplifier circuit, feeding the grid of the picture tube. Most manufacturers return the cathode of this tube either directly to ground, or to ground through a resistor, or a resistor-capacitor combination. This connection to the cathode of the tube must be opened and a coax cable inserted, the cathode return being completed through a 92-ohm resistor contained at the duplicator unit.

This return serves a dual purpose: It is the cathode bias return for the video tube and it is the terminating resistor for the coaxial cable. It is for this reason that the resistor used must be 92 ohms to match the surge impedance of the RG62/U coaxial cable used. *Any different value will be a serious mismatch* and will impair the quality of the picture. The 92-ohm resistor is supplied with the duplicator and is contained in a removable 4-prong plug.

When more than one duplicator is used, the plug containing the terminating resistor must be removed and an extension cable inserted in its place. Care must be taken, however, that the last unit in the chain must retain the plug with the 92-ohm resistor in its place.

In making the audio connection, a series combination of a 10,000-ohm resistor and a 1,500-ohm resistor is shunted across the primary of the output transformer. From the junction point of these two resistors a coupling capacitor of not less than .01 mfd/600 *wv* is connected, with a single insulated wire from the adapter cable connected to this capacitor.

Where the TV set does not have the cathode of the video output tube returned to ground or chassis but to a point *negative* with respect to chassis, the shield of the RG62/U coax must be connected to this point and *not to ground*. Care must be taken not to permit the shield to touch the chassis anywhere in the set. Otherwise the negative bias, which may be used throughout the set will be shorted out. The center conductor must be connected to the cathode and any resistor shunting the center conductor and shield must of course be eliminated.

The duplicator can be used with many types of TV sets, such as the Admiral 30A15, 30A16; Andrea C-VJ12, T-VJ12; Belmont 22AZ21,

(Continued on page 32)

Here's your **PORTABLE** oscillograph for **RADIO and TELEVISION SERVICING...**



DU MONT
Type 164-E
RUGGED!
LOW COST!

Weights only 20 lbs!
Does a complete servicing job!

TYPICAL USES

- Signal tracing.
- Correcting power-supply ripple.
- Detecting microphonic tubes.
- Replacing output transformers.
- Aligning video amplifiers.
- Trouble-shooting sync and sweep circuits of television receivers.

OTHER FEATURES

- Vertical amplifier response at full gain within 20%, from 5 cps to 100 kc.
- Identical amplifiers for vertical and horizontal deflection.
- Recurrent sweep from 15 to 30,000 cps.
- Return trace blanking.
- Sine wave test-signal output.

\$127.20

CAT. NO.
1064-A

• The Type 164-E is a rugged, low-cost, light-weight cathode-ray oscillograph capable of doing a complete radio and television job. Even though its price is low, nothing has been sacrificed in the way of quality in building this instrument for you.

In the design of the Type 164-E, emphasis has been placed on combining simplicity and portability with utility. Those are the things that are important to you.

And please remember too, the Type 164-E is a time-tested, proven oscillograph. This popular oscillograph, now in such general use among servicemen, has stood the test of many years' usage.

So when you buy your oscillograph for better servicing, if it's a Type 164-E you can be sure it's of the best.

DU MONT *for Oscillography*
ALLEN B. DU MONT LABORATORIES, INC., PASSAIC, N. J.
CABLE ADDRESS: ALBEEDU, NEW YORK, N. Y., U. S. A.

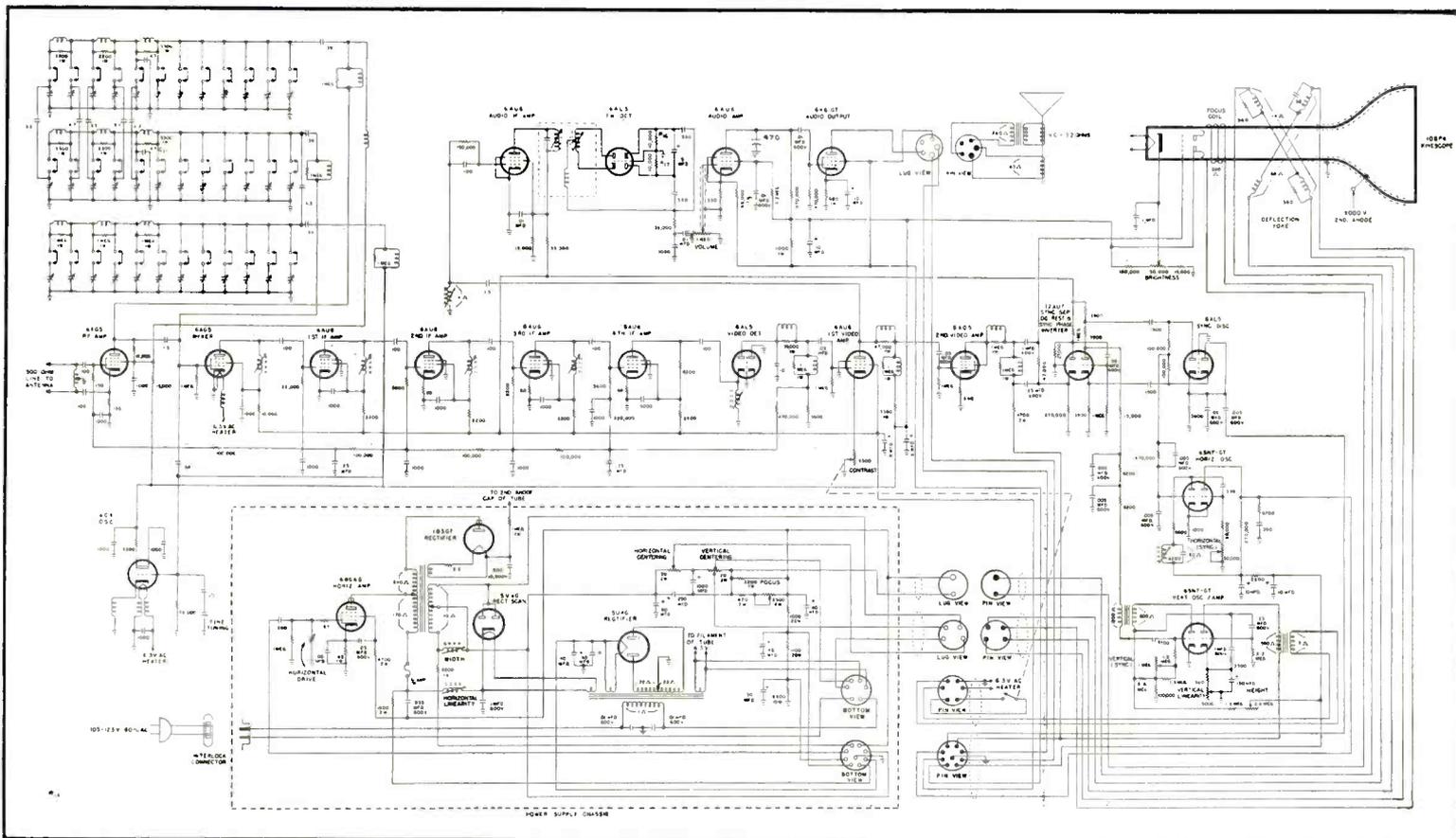


Fig. 2. Circuit of the Hallicrafters T-61 and T-67 TV chassis.

22AX22; Emerson 545; Fada 799; RCA 630TS, 648TPK, 641TV, 830TS; Garod, 3912TVFMP; DeWald BT100, etc.

Hallicrafters T-61/T-67

IN FIG. 2 appears the latest version of the Hallicrafters' push-button 10" model, T-61/T-67, using twenty-one tubes.

This model has an intercarrier sound *if* of 4.5 mc, picture carrier of 26.25 and sound carrier of 21.75 mc.

The second anode potential is approx. 9,000 v. Improper operation of the horizontal sweep circuit or circuit faults in the high voltage filter generally accounts for an abnormal anode potential. If the anode potential is low, the horizontal drive adjustment must be checked. This can be done in two steps:

(1) Connect a 50-megohm resistor string in series with a 200 microampere meter. Connect the free meter terminal to the chassis and the high side of the resistor string to the anode cap of the picture tube. The connection to the anode cap may be made with a fine wire slipped under the connector. Make up the resistor string with 10-megohm one or two watt resistors to

provide a safety factor for voltage breakdown. If the 10-megohm resistors are used, a total of five will be required to obtain the 50 megohms. The setup should be self-supporting and adequate clearance being achieved between the resistor string and chassis parts to prevent high voltage breakdown.

(2) Turn on the receiver and set the *brightness* and *contrast* controls at minimum. The microammeter will read approx. 180 microamperes of 9,000 v at the anode. The anode potential is measured in this manner (*contrast* and *brightness* controls at minimum, meter current approx. 200 microamperes) to simulate the picture-tube load on the high voltage power supply.

Due to a broad frequency response of the *if* amplifier, it is necessary to use a 24.5-mc signal generator or oscillator (unmodulated) as a beat frequency oscillator to locate the center frequency of the *if* amplifier response for the correct local oscillator adjustment. This *bfo* generator should be loosely coupled by means of a wire from the generator output placed in close proximity to the 6AL5 video detector.

The high frequency signal genera-

tor output should be connected to the receiver's antenna transmission line through two 150-ohm carbon resistors, one connected in each conductor of the transmission line. Then an electronic voltmeter should be connected across a 5600-ohm resistor in the plate circuit of the 6AL5.

Farnsworth GV-260

TRACING THE differentiation and horizontal control circuit of the Farnsworth GV-260, last month, we found that the reactance of the cathode-coupling capacitor was considerably higher than the 10-ohm cathode resistor through which the oscillator currents flow. Therefore, the current leads the voltage by almost 90°. Potential and current associated with a resistor being always in phase, the potential injected into the cathode is essentially 90° ahead of the potential at the grid of the oscillator. This injected potential appears at the plate of the reactance tube in like phase—leading—and is injected into the oscillator. This is the same phase difference that would be expected from an inductance—the potential leading the current. Therefore, the reactance tube and associated circuit appears to the oscillator be an inductance, and frequency shift is had

even as though an inductance were attached across the oscillator coil.


Direct potential upon the grid of the reactance tube determines the amount of amplification within the tube. Highly negative amplification is reduced—and the amount of out-of-phase potential is reduced. Thus it appears to the oscillator that the size of our hypothetical inductance varies.

This direct-control potential must be a function of the oscillator frequency, so that as the frequency tends to deviate from its correct value a change in control potential will restore correct frequency through the action of the reactance tube.

In this model magnetically coupled to the oscillator winding of the transformer is a discriminator circuit quite similar to the detection circuit of an FM receiver. The sync pulses, along with the local oscillator pulses from the 6K6, are injected into the discriminator. Therein, comparison is made between the two frequencies and a direct control potential is derived. Frequency is maintained constant, despite sudden temporary bursts of interference, because of the long time constant in the control-voltage circuit.

Differentiation of the pulses from the local oscillator is obtained by a 390-mmfd capacitor and 6,800-ohm resistor, injection being to a clipper tube, one-half section of a 6SN7. Plate current flows only during the positive portions of the incoming pulses because the grid is quite highly negative. Some negative potential is from the cathode resistor; more due to grid current flowing through the 6,800-ohm resistor. This assures that, should the pulse amplitude change over a period of time, still only the positive of the sync pulse will pass.

REPLACEMENT STYLUS

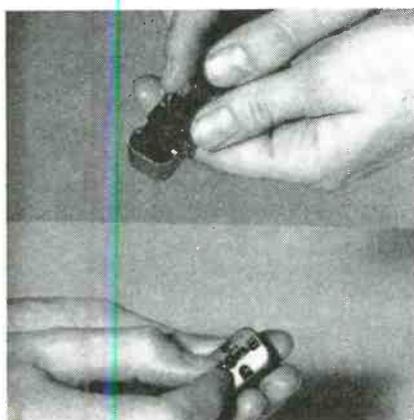

Two steps followed in exchanging the stylus of a variable reluctance phono cartridge. Top view shows how the stylus can be pushed out with a paper clip; bottom view shows how a new one can be inserted. (Courtesy G.E.)

The Capacitors that Lick

MOISTURE
VIBRATION
HEAT

... yet cost you not one cent extra!

SPRAGUE PHENOLIC MOLDED TUBULAR CAPACITORS

Types **TM** and **MB**

(600 Volts)

(1600 Volts)

Take a look at Sprague Type TM and MB Phenolic Molded Tubular Capacitors! See how their sturdy phenolic jackets offer *complete* protection against moisture, vibration and heat—the three factors that cause 9 out of 10 failures in ordinary wax tubulars. Then try Sprague TM's and MB's on your toughest jobs—and you'll quickly understand why these little units represent the greatest capacitor development in modern radio servicing history! Sprague TM's and MB's are a "must" for auto radio, aircraft radio and television applications. And because they cost exactly the same as ordinary wax cardboard tubulars, wise servicemen use them exclusively for all service replacements. There are no service complaints, no dissatisfied customers when you use Sprague TM's and MB's.

Get the genuine article! Be sure and ask for Sprague TM's and MB's by name!



SPRAGUE PRODUCTS COMPANY
North Adams • Massachusetts

JOBGING DISTRIBUTING ORGANIZATION FOR PRODUCTS OF THE SPRAGUE ELECTRIC COMPANY

ASSOCIATIONS



ARTA-ARSD

OFFICERS of the Akron Radio Technicians Association and the Associated Radio Service Dealers of Columbus, Ohio, met recently at a dinner in the Columbus Athletic Club to discuss the formation of a State Federation.

Members of the Akron group who attended the meeting were: D. C. Bruner, secretary; George Phillips, president; C. Kehree, treasurer; Jake Mintz and Cecil King. ARSD of Columbus was represented by Al Ray, president; William Hetrick, treasurer; Charles Hildreth, secretary; John Graham, editor of ARSD News and Fred Colton, chairman of the technical committee. Paul H. Wendel of Howard W. Sams & Co., and A. C. W. Saunders, Sams' television lecturer, were also at the meeting.

After the dinner the entire group attended a television lecture by Saunders in the main auditorium of the Central High School, Columbus. This was the twenty-seventh Saunders lecture in the Fall series arranged by Howard W. Sams and was sponsored by Hughes-Peters, Inc.; Thompson Radio Supplies; Whitehead Radio Co., and ARSD.

THE ARSD News reports that Bert Charles of WVKO was a recent guest. He outlined the activity of their new FM station, and offered ARSD free time, which was accepted. As a result, 15-minute ARSD programs were scheduled over WVKO.

At a recent association TV lecture by Al Saunders in the Sterling Hotel, Wilkes-Barre, Pa.: Joseph Czapracki, treasurer, Radio Service Association of Luzerne County, Pa.; Saunders; Milan Krupa, president, and Marino Ruggere, secretary of the Luzerne County association. (Courtesy Paul Wendell, Howard W. Sams)



TEN YEARS AGO

From the Association News Page of SERVICE, January, 1939

RUSS LUND, of Clough Brengle, delivered a talk on *Dynamic Testing of Receivers* before the Alton, Ill. Chapter of RSA. . . . Glenn Browning was guest speaker at the Boston, Mass. Chapter and discussed servicing with the 'scope and the vacuum-tube voltmeter. He explained alignment, *ave*, *afc*, checking of circuits and finding distortion, and alignment of remote circuits. . . . Walter Kensworth of RCA Institutes, Chicago, spoke on TV before the Chicago Chapter. At the annual election Ray Manson was reelected president, and Robert L. Storey was renamed secretary. Harold Cunningham was elected vice president and O. S. Dawson, treasurer. . . . TV was described as a forthcoming major industry at several chapter meetings. The Danville group declared that they . . . "should be constantly on the alert for TV developments in spite of the fact that it was believed that television would not reach their community for some time." And the Houston Chapter indicated its TV interest by setting up several sources. . . . A. G. Mohaupt of the Radio Training Association covered *Alignment Procedure Under Dynamic Testing* before the Detroit Chapter. . . . The 1939 Lansing Chapter elected four to the board of directors for a two-year term: Ed Bloom, L. W. Aubil, J. H. Howe and Max Huntoon. E. J. Budd, C. Kachelski, H. Carlisle and R. Bell were elected to one-year terms. . . . Over 900 Service Men attended a meeting of the Metropolitan New York Chapter to listen to John F. Rider explain and demonstrate the Rider Chanalyst. . . . Charles W. Fox was elected president of the St. Paul chapter. . . . Dick Harris was named president of the Steubenville, Ohio, Chapter. Paul Wright became vice president; Walter Stephanovich, treasurer, and Leonard Roberts, Jr., secretary. . . . George Connors of Sylvania addressed the New Hampshire Chapter on the servicing of ten-dollar midgets at a profit.

ducing surface noise on records; Jack Gray of C.G.E. who spoke on the FM system of the Ontario Provincial Police, and how they control their 250 mobile units and 30 stations; and Nick Foster, Superintendent of Seattle Technical school, who explained TV servicing.

FM Tuners

(Continued from page 11)

and increased efficiency and circuit stability. A high Q is made possible by the high L/C ratio and the absence of distributed capacitance. Absence of lumped capacities is also responsible for a high order of efficiency and overall circuit stability. Since a variable inductance exhibits much less minimum capacity than a variable capacitor, a much wider range of frequencies may be covered without the use of switching.

Systems employing continuously-variable inductance have several advantages. All losses due to resistance and distributed capacity in switch contacts and leads are eliminated, and microphonics and mechanical operation are reduced to a minimum. Since mechanical operation is minimized, longer, more trouble-free operating life can be expected.

In one tuner³ using the continuous variable method the entire range of FM and TV frequencies is covered in one complete operation. The tuner consists of three separate variable inductance units ganged on a rotatable ceramic and brass shaft. As the unit is tuned, a sliding shorting bar (or trolley) varies the effective inductance and progressively shorts out the unused turns. This permits the inductance and distributed capacity effects to be minimized and allows a much higher operating frequency than would otherwise be possible. A converter developed by Mallory and employing the Inductuner is shown in Fig. 6.

Inductance tuning can be accomplished in several other ways. One is through use of modified long-lines,³ with straight transmission lines $5\frac{1}{2}$ " long, spaced $\frac{1}{2}$ " apart. Two sets of lines are employed, one for rf tuning and the other to tune the oscillator. Tuning is accomplished by moving shorting strips along the lines.


Circular long-line tuning is used in another type⁴ where six long-lines (a set of two for each stage) are bent into a semi-circle and tuned by shorting bars. Since the shorting bars travel in a rotary motion, they are attached directly to the tuning shaft.

In another type of inductance tuner,⁵ tuning is accomplished by varying the

(Continued on page 36)

³Du Mont Inductuner, made under Paul Ware Mallory patents; see December, 1948, SERVICE.

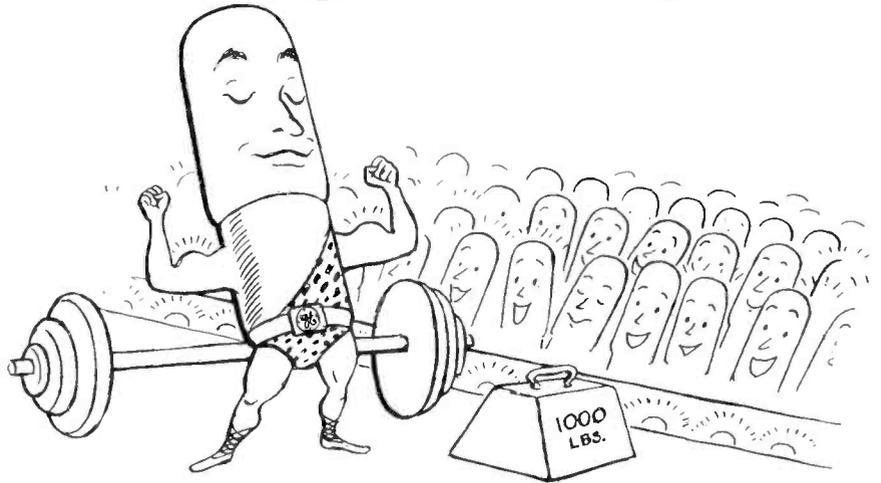
The little lamp that became the strong, silent type



LIGHTING radio dials is no job for a "weaking" lamp. Testing many old style lamps, General Electric engineers found that certain frequencies caused severe vibration that often tore the filament apart. Poor contact between the filament legs and lead-in wires also resulted in tiny arcs or changes in resistance that caused radio interference.

That's why G-E dial lamps have been made "the strong, silent type." Improved design minimizes vibration, provides positive connection between the filament and lead-in wires.

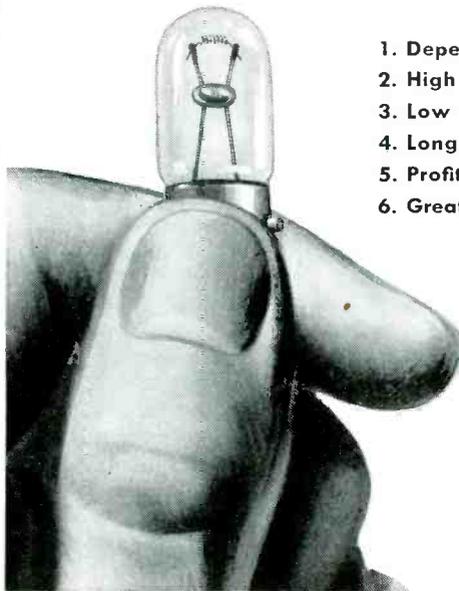For information on prices and types of G-E miniature lamps, call your nearby G-E Lamp office. Or write to General Electric Co., Division 166-S 1-49, Nela Park, Cleveland 12, Ohio.



1. Dependable, trouble-free performance.
2. High level of maintained light output.
3. Low current consumption.
4. Long life.
5. Profitable to handle.
6. Greater dealer acceptance.



G-E LAMPS


GENERAL ELECTRIC

FM Tuners

(Continued from page 35)

For **HIGH** Performance
In **LOW** Signal
Areas . . .

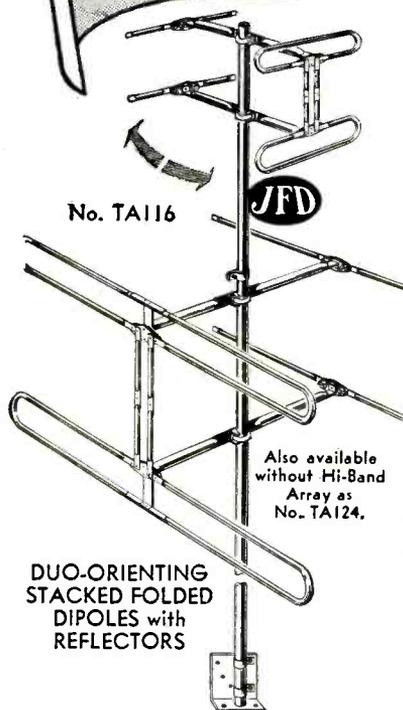The
ALL NEW
JFD **Super-Beam**
HI-LO TV Array



DUO-ORIENTING
STACKED FOLDED
DIPOLES with
REFLECTORS

LOOK AT THESE LONG-RANGE PERFORMANCE FIGURES FROM ACTUAL REPORTS!

CITIES	DISTANCE IN MILES
Albany - New York	125
Cleveland - Pittsburgh	120
New Haven - New York	110
San Diego - Los Angeles	100
South Bend - Chicago	90

OUTSTANDING FEATURES!

- ✓ Gives full 12 channel TV reception plus FM.
- ✓ Supplied complete with 10' Mast, All-Angle Mounting Bracket and Stand-Off Insulators.
- ✓ U-Bolt Clamp construction provides 1/8, 1/4 or 1/2 wavelength spacing of 2, 4, 6, or more bays on mast for tremendous stacking flexibility — also permits independent orientation of each bay.
- ✓ Lightning-fast assembly time.
- ✓ Impedance of 150-260 ohms and +8.6 DB gain.
- ✓ All-weather Roto-lock insulator made from loss polystyrene for perfect high frequency insulation.

Write for Literature



4111 Ft. Hamilton Parkway
Brooklyn 19, N. Y.

"Manufacturers of the World's Largest Line of
TV/FM Antenna Equipment"

inductance of a two-turn coil by means of a movable plate inserted between turns. A fixed value of capacitor is also used in the tuned circuits.

Permeability-tuned systems are still another form of inductance-tuning. The main disadvantage of permeability tuning arises from the problem of adapting it to mass-production. Since the coils have few turns, and because a large wire size must be used to maintain high Q , difficulty is often experienced in winding coils with sufficient uniform pitch to insure satisfactory tracking and calibration. One manufacturer has developed a permeability-tuned coil which uses a special braided tinsel for the winding. Although this results in greater ease in winding, improved Q and increased tuning range, very close control of the winding pitch must still be maintained. Other difficulties are mounting and wiring arrangements, the necessity for very thin-walled coil forms, winding terminations, etc. These disadvantages, however, have been overcome by several FM receiver manufacturers. Belmont, for example, employs a continuous-tuning, mechanically-ganged permeability tuner in their 21A21 television receiver. In one tuner⁶ there is a patented head featuring brass plungers to attain a Q of approximately 200.

A permeability-tuned head is used in the Zenith 7E01. In this model the top capacitor gang tunes the AM band, the permeability-tuned FM section appearing at the bottom. Coils employed in the rf and detector stages have four paralleled windings to increase the amount of frequency coverage per degree of slug insertion. Since the oscillator covers a smaller frequency range, a single wire-wound coil is satisfactory. A similar system of tuning is also used in a tuner made by Transvision; FMF-2.

Permeability-tuned transmission lines are also used by Motorola. By employing highly-efficient coax-line tuning in a double-superhet circuit, extremely high gain, sensitivity, and selectivity, along with very low stage noise, is accomplished. In fact, the high Q of the converter circuit eliminates the need for an rf stage and allows use of a 4.3-mc if frequency. This

⁶Edwards Fidelotuner.


⁴Approved Electronics.

⁵G. E. Guillotine tuner.

⁸Brooks, FMT-10.

⁷Bendix egg beater; SERVICE, July, 1948.

It's For You . . .

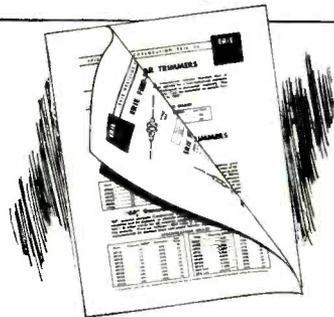

ERIE RESISTOR'S New Catalog

You can rely on the performance of Erie Resistor components when repairs call for replacement. If your distributor cannot supply you, write us for information, and ask for the new catalog.

Electronics Division
ERIE RESISTOR CORP., ERIE, PA.
LONDON, ENGLAND TORONTO, CANADA.

frequency permits greater stability and gain, as well as easier tuning adjustments, than the standard 10.7-mc frequency.

In still another type of variable-inductance tuning system the tuning unit encompasses a high-frequency variometer method.⁷ Basically, the rotor and stator inductances are wires shaped in variometer style. Angular rotation of the rotor wire varies the inductance in the circuit. Three of these units are ganged on a non-metallic shaft to reduce interstage coupling effects. Advantages of such a system are freedom from microphonics and vibration, lightweight, sturdy construction, and easy to produce.

Many variations of the foregoing tuning systems are to be found in commercial FM tuners and FM/AM receivers. The tuners described are those more commonly known.

Many methods are used to provide gain, stability, etc., in the oscillator and other sections of the receiver. Generally, a ceramic trimmer having a negative coefficient is connected in the oscillator tank circuit to compensate for warm-up drift. Input circuits generally are designed for 300-ohm antenna leads, often with provisions for con-

necting to a 72-ohm coaxial leadin. Double-conversion is used in several models such as the Meissner 9-1091 and the Motorola coaxial tuner, etc. Double-conversion allows greater selectivity, increased antenna gain, increased oscillator stability, greater freedom from regeneration, and very high image ratio.

Credits

The author is indebted to C. R. Miner, Myron F. Melvin, Gus Wallin, V. R. Beck, William J. Harrison, G. H. Browning, G. M. Brooks, and Norman Skier for material assistance in the preparation of this article.

TV Business

(Continued from page 13)

by the installation and service company.

In the case of the small installation and service company devoting its full efforts to one or two dealers, the service company should try to be protected with a cancellation clause which states that . . . "In the event of cancellation, for reasons other than expiration of agreement, the dealer will be charged for all material and labor purchased or supplied prior to work stoppage, plus all reasonable costs arising from cancelling all material orders not yet received."

This clause is extremely important when the installation company must procure specialized material for TV receiver lines which are of the *custom installation* type.

Probably the most important agreement is the customer warranty. Failure by the independent installation and service company to clearly define the work they intend to do, and the parts they will guarantee, in their customer warranty agreement, may result in losses in labor and material that wipe out anticipated profits.

Typical Warranties

A general customer warranty outlines the responsibilities of an installation and service company and the contingencies against which the company must be protected, and usually states that the agreement is between the television installation and service company and the purchaser of the TV receiver. There are usually two sections covering installation and service.

In the installation portion of the contract five points are normally covered:

(1) The service group will fur-

(Continued on page 38)

TRANSVISION

**PRESENTS
THE NEW**

MODEL 12CL TV KIT

Brings the biggest and best in television within the reach of everyone.

GIGANTIC VALUE!

OVER

200

**SQ. IN. PICTURE
VISIBLE FROM ALL ANGLES**

(Picture much bigger than a tabloid newspaper page.)
IMAGE IS EQUAL to that of a 20" tube—even sharper and clearer—and it is visible from all angles.

\$399⁰⁰

NET

Includes Kit, Cabinet, Lens, Table, Antenna and 60 Ft. of Lead-In Wire

EQUIVALENT OF \$1000.00 SETS!

Price of the new 12CL electromagnetic kit includes these outstanding features:

- 12½" picture tube with special fitted All-Angle Lens and color kit.
 - Beautiful select-grain cabinet and roto-table.
 - New all-channel continuous tuner Model CT-1.
 - New all-channel hi-gain antenna and 60 feet of lead-in wire.
- Nothing else to buy.


TRANSVISION REMOTE CONTROL UNIT KIT

Will operate any TV receiver from a distance. Turns set on, tunes in stations, controls contrast and brightness, turns set off. Ideal for installations where the television receiver is inaccessible. Tuner unit is a high gain, all-channel unit with about 50 micro-volt sensitivity. Easy to assemble in about an hour.

Model TRCU, with 25 feet of cable. . . . Net \$69.00
Without cabinet Net \$65.00

ASSEMBLE Your Own CABINETS

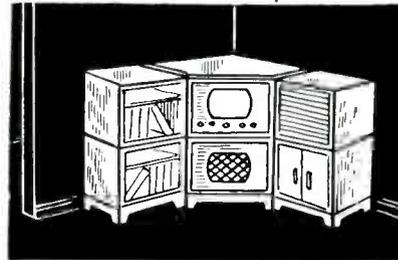Transvision's "MODULAR" Cabinets come in knock-down, unpainted units, offering an unlimited range of combinations, including even a bar. Finish them off to suit your taste.



Corner piece, shown above, has room for TV, Phono, Record Storage, and open Book Case. COMPLETE. Net \$84.00

For other units and prices, write for "Modular" Catalog.



MODEL 12CL TV KIT

- Features 12½" tube with fitted All-Angle Lens, giving over 200 sq. inch picture which is visible from **anyplace** in a room.
- Gives ideal long-range reception with **CONTINUOUS TUNING ON ALL CHANNELS**.
- **COMPLETE** with Cabinet, Lens, Roto-Table, Antenna, Lead-in Wire.
- **A BIG PROFIT-MAKER** for service dealers. This kit is TOPS—ideal for homes, clubs, taverns, and other commercial installations.

**EASY TO ASSEMBLE . . .
NO TECHNICAL KNOWLEDGE REQUIRED**

Transvision's simple step-by-step Instruction Sheet makes assembling a TV Kit a pleasure. Each kit comes complete with all-channel double-folded dipole antenna and 60 ft. of lead-in wire. *Nothing else to buy!*

TRANSVISION ALL-CHANNEL TELEVISION BOOSTER

To assure television reception in weak signal areas, or areas which are out of range of certain broadcast stations, Transvision engineers have designed this new booster. It increases signal strength on all television channels. **Tunes all television channels continuously.** Can be used with any type of television receiver. Unusually high gain in upper television channels. Model B-1. LIST \$44.95

TRANSVISION COMPLETE LINE OF TELEVISION COMPONENTS

Essential units for building a quality television set . . . Transvision makes available a complete line of high quality parts competitively priced. Included in this line are Filter Chokes, all types of Transformers, Focus Coils, Deflection Yokes, Coils—and, of course, major units such as Picture Tubes, Antennas, Lenses, etc., etc.

WRITE FOR COMPONENTS FOLDER P-1

RADIOMEN . . . You Can GET INTO the TELEVISION BUSINESS IN A BIG WAY WITH THE TRANSVISION DEALER PLAN

Write for Dealer Folder D-1

TRANSVISION, Inc. Dept. S New Rochelle, N. Y.

In Calif.: Transvision of California, 8572 Santa Monica Blvd., Hollywood 46

All prices 5% higher west of Mississippi; all prices fair traded. All Prices Subject to Change Without Notice



**CAN YOU
USE THIS
SPECIAL CONDENSED
CATALOG?**

★ **THE RJC-2 SPECIAL CANNON ELECTRIC** Condensed Catalog covers the electrical connectors sold through our 300-odd regular radio parts distributors for radio and sound applications such as microphones, amplifiers, transmitters, receivers, etc. They include type series "P", "X", "XK", "XL", "TQ". Also shown in the same catalog are Sectional Cable Terminals, Laboratory & Switchboard Connectors and Bayonet Type Lamp Sockets. List prices are given on all items. Address Dept. A-268 for your free copy.

SINCE 1915

**CANNON
ELECTRIC**

Development Company

3209 HUMBOLDT ST., LOS ANGELES 31, CALIF.
IN CANADA & BRITISH EMPIRE:
CANNON ELECTRIC CO., LTD., TORONTO 13, ONT.
WORLD EXPORT (Excepting British Empire):
FRAZAR & HANSEN, 301 CLAY ST., SAN FRANCISCO

TV Business

(Continued from page 37)

nish all labor and material necessary to effect a *normal* installation.

(a) A normal installation is one which can be made with: (1), A single antenna assembly of a type approved by the manufacturer; (2), 100 feet of transmission line, and (3), utilization of existing power outlet facilities and line cord furnished with the receiver.

(2) All installations are guaranteed by the service company for a period of _____ subject to proper handling by the purchaser or other persons in the purchaser's premises.

(3) The service company will not guarantee the installation under the following conditions:

(a) Acts of God, public enemy, fire, air raid, hostilities or any other cause beyond its reasonable control.

(b) Relocation or modification of the installation by personnel other than those assigned by the service company.

(c) Interferences caused by neighboring TV receivers, amateur transmitters, and electromedical apparatus.


(4) The service company installations made during the absence of the purchaser will be installed in accordance with the instructions received from the purchaser's family, employees or others on the purchaser's premises.

(5) The service company will adjust the TV antenna only for those TV stations transmitting at time of installation. Further adjustments for new stations placed in operation during the life of this agreement will be made for a fixed fee, to be established by the service company for each installation area.

In the *Service* section two points are usually covered:

(1) The service policy is void if the TV receiver is serviced or tampered with by persons not assigned by the _____ service company.

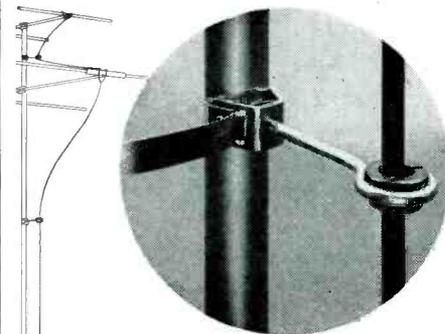(2) All normal repairs will be made without additional charge to the purchaser for a period of _____ except for those repairs due to misuse by the purchaser, members of the pur-



Phoenix ANTENNA MAST STAND-OFF INSULATORS

- Attaches to any size mast in 10 seconds.
- Just pull strap through, then turn screw eye.
- No more swinging lead-ins with broken wires.
- A MUST for every good installation.

List Price **25¢** each

A complete line of Television Antenna Mounts. Send for literature.

**At Leading Jobbers and
Dealers - or Write to
Phoenix Electronics Inc.
Lawrence, Mass.**

chaser's family, Acts of God, etc.

All repairs which are not covered by the contract are usually billed to the customer on a time and material basis.

There is no limit to the number of service calls in a purchaser's warranty, except where the calls are unjustified. Many purchasers expect motion picture quality from their TV Receiver and request service everytime their picture *wiggles* from line voltage surges, airplanes, ignition, etc. These types of complaints are usually referred to the manufacturer, whose local representative serves as an arbiter on such matters.

The successful installation and service company models their personnel after the public utility Service Man, all being taught four important fundamentals: (1) To be businesslike during a call, without being rude; (2) spend as little time as possible in the customer's home; (3) neatness of dress, and cleanliness habits for protecting the customers property, and (4) proper technique to instruct the customer in the operation of the receiver.

The television installation and service company must realize that while the salesman sells the TV receiver, it is up to the service company to keep the receiver sold.

WARRANTY

Receiver

"Bendix Aviation Corporation warrants to the purchaser of each new Bendix Radio television receiver that any part thereof (except tubes and lamps) which proves to the company's satisfaction to be defective in material or workmanship within 90 days from the date of original purchase for use will, at the company's option, be repaired or replaced.

"Any defect in said receiver should be brought to the attention of the dealer from whom it was purchased, who will be authorized to furnish or arrange for repairs or replacement within the terms of this warranty."

Picture Tube

"Picture tubes used in new Bendix Radio television receivers are, under this warranty, proportionately adjusted on the basis of one year's initial service. Full adjustment will be allowed for the first 90 days after original purchase at retail and decreasing allowances will be made for the ensuing 9 months at the rate of 10% a month. e.g., the fourth month after such purchase the allowance is 90%, during the fifth month 80%, and so on until the twelfth month realizes only a 10% adjustment. Claims for adjustment under this policy are acceptable only for a period of one year's service by the user, and must be substantiated by sales records."

"The foregoing is in lieu of all other warranties express or implied and Bendix Aviation Corporation neither assumes nor authorizes any person to assume for it, any other obligation or liability in connection with said receiver."

Owner's Policy

The purchaser of a new Bendix Radio television receiver may avail himself of more comprehensive service and broaden the scope of the foregoing warranty through arrangement with the Bendix Radio Dealer at the time of the original purchase of the receiver at retail.

Cautions

Each Bendix television receiver has been carefully shielded to prevent personal injury from inadvertent contact with high voltages employed to all television receivers. It is advisable, however, to refer to trained television technicians for any adjustments required within the cabinet.

Each television receiver operates only on 105-125 volt, 60 cycle alternating current. If power supply is questioned, consult local power company for information.

Ample ventilation is provided in cabinet design, and in order to prevent excess parts failures, this ventilation should not be impaired in the placement of the receiver.

If any evidence of improper operation occurs for which no correction is known, turn receiver off and consult qualified television service personnel before again placing instrument into operation.

A typical manufacturer's warranty form and a caution note supplied with every receiver. (Courtesy Bendix)

RCA HF TV ANTENNA

A hf TV (type 203A1) antenna has been announced by the RCA Tube Department.

Antenna (folded dipole and folded dipole reflector) is designed for mounting on the same mast as the RCA 225A1 or similar television antennas.

Both the hf and lf antennas may be oriented independently for best reception. A harness is used to couple the two antennas into the signal transmission line running to the receiver. Besides permitting the single transmission line to serve for both antennas, the harness is said to act like an automatic switch so that when the receiver is tuned to stations in the high channels, only the hf antenna appears to be connected to the transmission line. When low channel stations are tuned, only the low frequency antenna is in effect, connected to the transmission line.

NEW TORQUE DRIVE KIT

Makes Sales and Service Easy!

3 TYPES
REPLACE OVER
150 STANDARD
MODELS

Lightest, Most Efficient,
Crystal Pickup Cartridge
Ever Produced!



SELL MORE CARTRIDGES

It's a colorful display . . . creates interest . . . and action . . . helps you sell more replacements to old and new customers.

SATISFY MORE CUSTOMERS

You give faster replacement service. Your customers get more pleasure and more good plays . . . even from old, worn records!

SIMPLIFY YOUR SERVICE JOB

It's a complete service Kit, too. Contains everything for time-saving, labor-saving replacement. Gives you 3 basic models that replace over 150 standard types.

MAKE MORE MONEY

Saves ordering time and service time. Cuts overhead. You make a good profit on every cartridge sale . . . and every service job. Builds needle sales, too! Put the Kit on display . . . take one with you on your service calls. Available in Kit "A" (Osmium) and Kit "B" (Sapphire). Each Kit contains 6 cartridges, 4 extra needles, mounting plates, replacement chart.

Order from your E-V Distributor or write for Bulletin No. 142

ELECTRO-VOICE, INC., BUCHANAN, MICH.

Export: 13 East 40th St., New York 16, N. Y., U. S. A. Cables: Arlab

E-V Pat. Pend. Licensed under Brush Patents.

NEW MODEL L14 MICROGROOVE
CRYSTAL CARTRIDGE AND NEW
MODELS 20 AND 22 MAGNETIC
CARTRIDGE FOR REGULAR AND
MICROGROOVE ALSO AVAILABLE

IT PAYS TO REPLACE WITH

Electro-Voice

Everybody agrees
ATR VIBRATORS
are **TOPS!**

ATR

AUTO RADIO VIBRATORS
have Ceramic Stack Spacers



A COMPLETE LINE OF VIBRATORS...

Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction, featuring Ceramic Stack Spacers for Longer Lasting Life.

Backed by more than 17 years of experience in Vibrator Design, Development, and Manufacturing.

ATR PIONEERED IN THE VIBRATOR FIELD.

NEW VIBRATOR GUIDE FREE



ATR
"A" BATTERY ELIMINATORS

for DEMONSTRATING AND TESTING AUTO RADIOS

New Models... Designed for testing D. C. Electrical Apparatus on Regular A. C. Lines. Equipped with Full-Wave Dry Disc Type Rectifier, Assuring Noiseless, Interference-Free Operation and Extreme Long Life and Reliability.

NEW MODELS NEW DESIGNS
NEW LITERATURE
ATR "A" Battery Eliminator, DC-AC Inverters, Auto Radio Vibrators

See your jobber or write factory

AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA-U. S. A.

TV Alignment

(Continued from page 16)

between L_{46} and the junction of pin 3 of V_{21} , R_{80} and C_{113} .

Resistor R_{109} was changed to 5600 ohms.

Resistor R_{111} is now 100 ohms.

Resistor R_{140} , a 5-watt 7500-ohm wire-wound unit is now between ground connection at C_{46B} and electrolytic can B- terminal.

Resistor R_{141} , a wirewound 10-watt 7500-ohm unit, has been added between ground connection at C_{46B} and B+ (160 V) connection at C_{90A} .

Resistor R_{135} has been changed to 1500 ohms, 2-watts.

Resistor R_{106} has been changed to 3300 ohms, 1-watt.

Resistor R_{111} has been changed to 68 ohms, 2-watts.

Resistors R_{142} and R_{143} were added and connected in series between terminals 5 and 7 of the horizontal output transformer.

Capacitor C_{112} is now a .05 mfd 600 v. Resistor R_{104} now has a value of 150,000 ohms, 2-watts.

Resistor R_{144} (1000 ohms $\frac{1}{2}$ w) has replaced the decoupling choke L_{25} .

Two changes were made in the G chassis:

Horizontal centering potentiometer, R_{87} , is now a 200 ohm unit.

Vertical centering potentiometer, R_{80} , now has a value of 100 ohms.


Alignment Procedure

Preliminary Overall Check: Before attempting any alignment adjustments on the receiver it is prudent to verify whether or not such action is necessary by making a preliminary overall check of the receiver response curves, both picture and sound. If this check reveals that the response curve shapes or frequencies have departed appreciably from their normal values then you can proceed with the complete alignment adjustment procedure. To make such a preliminary check, the output of the sweeping oscillator is combined with the output of the twelve channel crystal-controlled rf sound carrier marker generator and fed

to the receiver antenna input terminals through a coaxial-to-balanced matching pad. This matching pad arrangement is shown diagrammatically in Fig. 4. (It is important that the setup be constructed of good grade one-half watt carbon resistors, using the shortest possible pigtail lead lengths to keep them as non-inductive as practicable). The vertical input terminals of the alignment 'scope are connected by means of a length of shielded cable to *video test* terminal G and chassis ground, after first making sure that the 'scope has a blocking capacitor in series with its *high side* vertical terminal, as is usually the case. The horizontal input terminals of the 'scope are connected to the sawtooth sweep output terminals of the sweeping oscillator, as was described previously.*

The following procedure should then be followed:

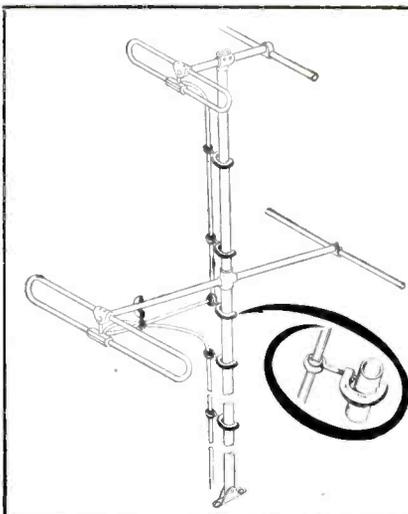- (1) Disable the *agc* circuit of the receiver by placing a jumper from the *agc* amplifier grid (pin 4 of V_{150}) to the junction of R_{28P} (contrast control) and R_{122} .
- (2) Set the contrast control to produce -3.5 volts of *if* bias as measured from terminal Q to chassis with a *vtvm*.
- (3) Push channel 5 button on the receiver, and set up the sweeping oscillator for a sweep excursion of approximately 15 mc and a center frequency of approximately 79 mc, the center of the 76 to 82-mc channel 5 band. Use the *high* output connector of the sweeping oscillator and turn its attenuator knob completely clockwise to obtain a full 26 db of attenuation which it provides.
- (4) Switch the crystal-controlled rf sound carrier marker generator to channel 5 (81.75 mc output frequency) and adjust its



The New **Mueller**

"TENNA-CLAMPIPE"

(Clampipe T. M. Reg. U. S. & Can. Pat. Off.)

A Stand-off Insulator that Clamps on Quickly-Easily-Almost Anywhere

Supporting TV and FM Antenna Lead-ins on Masts, Cross-arms, Basement Pipes or any other Handy Place.

SIMPLY TURN THE SCREW-EYE BY HAND FOR A SOLID, PERMANENT GRIP.

An assembly of the famous Mueller Clampipe Ground Clamp and a Screw-eye with plastic, insulating grommet. Offered for flat or round cable. **ASK YOUR JOBBER.**

Send for Free Sample & Catalog 810.

MUELLER ELECTRIC CO.

1565 E. 31st St.

Cleveland 14, Ohio

output level to new maximum, turning its modulation switch on.

With the 'scope vertical gain adjusted to a sensitivity of approximately one inch of deflection per volt of input a pattern resembling that shown in Fig. 5 should appear on the 'scope screen.

[To Be Continued]

7" TV Model

(Continued from page 18)

erator to switch from station to station without having to reset the contrast control each time.

Cathode bias is used to delay the application of *agc* voltage until the video output is sufficient for full contrast.

Two time constants are used: C_{20} and R_{21} is the first with a time constant approximately one picture line long; C_{23} and R_{20} is the other and is considerably longer. Because of the short time constant C_{20} stores only a small amount of energy and at the end of each line the voltage across it has dropped to about the black level at which time C_{20} is again charged. Due to the small amount of energy stored in C_{20} it discharges quickly, even though it may charge to the peak of an interfering noise pulse, thereby minimizing the effect of relatively long noise pulses on receiver performance. The longer time constant, C_{23} and R_{20} , filters out the *ac* component and the 60-cycle component caused by the vertical sync pulses.

Video Amplifier, DC Restorer and Sync Clipper

This system employs two 6AU6s. A sync-negative signal from the video detector is applied to grid of the video amplifier, V_8 , so that noise pulses, with an amplitude greater than that of the signal, will have negative polarity. The video amplifier stage is so designed that with a full contrast picture on the picture tube, the top of the sync signal will be at about cutoff and noise signals above this level will drive the stage beyond cutoff and be clipped. The contrast control is placed in the cathode of the video amplifier tube and controls the contrast by controlling the gain of the video stage. The range of the gain adjustment is about 8:1. The gain is not allowed to go to zero since this would attenuate the inter-carrier sound signal below a usable level. The bias for the video amplifier remains constant at approximately 1.5 volts and is independent of the setting of the contrast control. A pair of



MODEL DM—Compact low cost 2 pole, shaded pole motor designed for portables, table models and other instruments in which space is an important factor. Simple speed change mechanism incorporates a special long-lasting molded neoprene belt.

Only **GI** offers you
TWO rim drive
DUAL SPEED PHONOMOTORS



MODEL DR—Deluxe model.

4 pole, shaded pole motor for use in all high-grade instruments in which the ultimate in performance is desired. Novel speed change mechanism is both simple and positive in operation.

Here they are . . . not one, but TWO dual speed phonomotors by General Industries . . . for both 33½ and 78 R.P.M. operation.

Representing years of research and development, either of these motors will accommodate both the new long-playing and conventional type records. Both motors have been proved in extensive laboratory tests—and already are being widely used in many leading phonograph instruments.

Like all GI Smooth Power products, both new dual speed phonomotors are built to the highest quality and performance standards attainable. Their cost, however, is surprisingly low.

For additional information, specifications and quotations, write *today* to:



The GENERAL INDUSTRIES Co.

DEPARTMENT O • ELYRIA, OHIO

peaking coils, L_{27} and L_{28} , are placed in the plate of the tube to maintain an output relatively flat to 3.5 mc. The output is coupled through a capacitor, C_{34} , and resistor R_{41} to the cathode of the picture tube.

The other 6AU6 tube restores the *dc* component, clips the sync from the composite signal and then clips the sync on the other side. A *dc* voltage is developed across cathode resistor, R_{33} , which is proportional to the average value of the input signal. This voltage is applied to the grid of the picture tube to reinsert the *dc* component. The value of the cathode bias

is such that all picture information is beyond the tube cutoff and only sync pulses appear in the plate. These pulses are clipped on both sides since their peak amplitude rises beyond the tube's cutoff. The pulses are then fed through a voltage divider network to obtain the desired voltage for application to the horizontal and vertical sweep oscillators.

Horizontal Sweep Circuits

The horizontal sweep oscillator employs a 12SN7GT in a *Potter-type*
(Continued on page 42)

**MORE CAPACITANCE
... LESS BULK...**

AEROVOX

**TWIST-PRONG
BASE**

ELECTROLYTICS



• It's the "new look!" See it right on the labels. Higher voltages and capacitances—without increase in sizes — in some numbers!

That makes these handy twist-prong base electrolytics handier than ever. Prongs extend through mounting surface and are twisted or bent to hold unit rigidly in place. May be mounted on fibre (insulated) or metal (grounded) socket-shaped washer riveted or eyeletted on chassis. Ideal for initial equipment. Indispensable for replacements.



• Our jobber stocks Aerovox twist-prong base Type AF electrolytics. See listings in latest catalog for your precise needs. Ask our jobber for your copy — or write us.



**FOR RADIO-ELECTRONIC AND
INDUSTRIAL APPLICATIONS**

AEROVOX CORP., NEW BEDFORD, MASS., U.S.A.
Export: 13 E. 40th St., New York 16, N.Y. • Cable: 'ARLAB'
In Canada: AEROVOX CANADA LTD., Hamilton, Ont.

(Continued from page 41)

cathode-coupled multivibrator circuit. The input sync signal is of negative polarity with a potential of about $\frac{1}{4}$ to $\frac{1}{2}$ volt. The method used in the initial adjustment of the controls in this circuit is quite interesting. The horizontal size control, R_{90} , is set for the largest possible size picture consistent with good linearity. The anode voltage on the picture tube is then adjusted by means of capacitor, C_{87} , to obtain the proper size picture. In this manner correct size is obtained along with the brightest possible picture. Thereafter, the horizontal size control is used for slight adjustment of the size of the picture. The sawtooth output of the sweep oscillator is applied to one grid of the 12SN7GT push-pull horizontal sweep output dual tube. Phase reversal is obtained by capacity coupling between the plate of the first triode to the grid of the other. A horizontal linearity adjustment is provided by a capacitor, C_{87} .

Vertical Sweep Circuits

The vertical sweep oscillator circuit is the same as that employed for the horizontal circuit. The output of the sweep oscillator is applied to one grid of the 12SN7GT push-pull vertical sweep output dual tube. Phase reversal is obtained by driving the same grid from a resistive voltage divider circuit from the plate of the first triode to ground.

Intercarrier Sound System

Coupling from the video amplifier to the sound system is accomplished through a 1-mmf capacitor, C_{23} , whose small value minimizes any possible effect on the gain of the video amplifier below 4.5 mc. A trap inductance, L_{29} , with an adjustable iron-core, is made resonant at 4.5 mc for maximum transfer of the audio signal. The impedance in the grid circuit of the 6AU6 ratio detector driver is kept low by tapping down on inductor, L_{29} , to prevent self-oscillation of the tube. An audio output of 2 volts rms for 25-kc deviation at the detector necessitates the use of an audio amplifier ahead of the audio output. Degeneration is used in the audio output stage to improve the audio fidelity.

Low Voltage Power Supply

A low-voltage power supply furnishes voltages to the receiver circuits with potentials of +120, 250, 400 and -140 volts. The +120-volt supply is obtained across 50 + 50-mfd capaci-

tors (C_{63A} and C_{63B}) from a selenium rectifier after filtering by choke L_{38} . The rectified output of one-half of the 25Z6GTG adds to the output of selenium rectifier to produce the 250 volts for the rf high-voltage oscillator tube. The output of the 6X5GTG adds to the 250 volts to produce 400 volts across the 40 + 40 mfd capacitor, C_{75A} . The other half of V_{16} is used as the B-rectifier to furnish 140 volts negative. This negative supply is used as bias for the video amplifier and audio output stage and in addition is added to the 400-volt supply for a total of 540 volts for the deflection circuits. The drain is approximately 160 ma at 120 volts, 25 ma at 250 volts, 15 ma at 400 volts and 15 ma at 140 volts negative.

High Voltage Power Supply

The high-voltage power supply is completely enclosed in a shield compartment to prevent emission of rf energy into the receiver circuits and as a safety measure. A 12AU7 is used as the rf oscillator and it is operated well within its maximum rating. The oscillator voltage is applied to the primary of a transformer, T_8 . The high-voltage is developed across the secondary of the transformer rectified by the 1B3GT/8016 and is then filtered before being applied to the bleeder resistor network.


Heater Supply

The picture tube and the 6X5GTG rectifier are rated at 6.3 volts and .6 ampere. The balance of the tubes are arranged in two .3 ampere strings connected in parallel. The total voltage of one of the strings is 6.3 less than the other and a resistor, R_{59} , is added to make up the difference. Since the 6C4 heaters require .15 ampere, they are shunted by a pair of resistors, R_{65} , R_{77} , and thus draw .3 ampere at 6.3 volts. All the tubes in this series-parallel combination draw approximately 103 volts. A resistor, R_{84} , is placed in series with the entire combination.

RIDER PUBLIC ADDRESS EQUIPMENT MANUAL

A 2024-page *Rider Public Address Equipment Manual* has been published by John F. Rider Publisher, Inc., 480 Canal Street, New York 13, N. Y. Manual contains servicing data of 147 pa equipment manufacturers. It embraces a ten year span—1938 to date. An added extra is the *How It Works* book, which describes the special circuitry found in various p-a systems. Priced at \$18.00.

FOR TELEVISION TESTING AND SERVICING

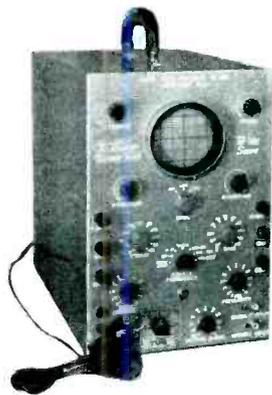

TEE VEE SCOPE
Model TV-90

Net Price \$127.50

Combines the two essential instruments needed in television testing—alignment—service. A complete oscilloscope and a complete sweep generator that can be used independently. Tee Vee 90 combines two units for compactness and portability—meticulously engineered in advanced design and construction. Oscilloscope also has its own variable linear sweep. Sinusoidal sweep with phasing control for use with internal R.F. sweep generator when testing band pass characteristics. Synchronization provision for either internal positive, external or line frequency.

Z axis terminal permits intensity modulation of electron beam. Input jack provided for marker signal. Independent sweep has range of 4.5 to 40 m.c. in 3 bands giving choice of any I.F. frequency desired. Band width can be varied continuously from 50 K.C. to 50 M.C. Attenuation of R.F. output is continuously variable and is applied through low loss coaxial cable. Traveling detector probe included for observing signal at any point of R.F. circuit under test.

105-130 volts 50-60 cycles. Weight 25 lbs. Size 14 x 8 x 12 1/2 inches. Finished in attractive hammertone grey. Supplied complete with tubes, probe, coaxial output cable and operating instructions ready to operate.

WRITE FOR CATALOGUE 1 S

RADIO CITY PRODUCTS CO., INC.

152 West 25th St.  New York 1, N. Y.

G. E. APPOINTMENTS

Edward A. Malling has been appointed sales manager of quartz and germanium crystals for the specialty division of G. E.

George F. Devine has been appointed assistant to the manager of sales of the specialty division of G. E. Prior to his new appointment he was commercial engineer for the specialty division, previously having worked on radio receiver design for the electronics department's receiver division.

NATIONAL UNION RADIO LICENSES RCA

National Union Radio Corporation, Orange, N. J., has entered into a six-year license agreement with RCA granting the latter company and its subsidiaries the use of National Union's patents and research development work.



AKERROYD AND BACKER NOW CHICAGO TRANSFORMER REPS

Arthur E. Akeroyd, with offices in Boston, Mass., and James J. Backer of Seattle, Wash., have been named reps for the replacement line of transformers of the Chicago Transformer Division, Essex Wire Corporation.



Art Akeroyd



Jim Backer

BURROWS JOINS MEISSNER AS SALES-AD MANAGER

Robert E. Burrows has been appointed sales and advertising manager of the Meissner Division of Maguire Industries, Inc., Mt. Carmel, Ill.

Burrows was formerly with Westinghouse Electric International Company, New York City, where he was manager of the home radio department.



TRANSVISION TELEVISION COMPONENTS FOLDER

A 4-page folder, No. P-1, describing and illustrating 19 television parts has been published by Transvision, Inc., 460 North Ave., New Rochelle, N. Y.


Components described include filter chokes, low-voltage transformers, high-voltage transformers, video *if* transformers, audio *if* transformers, power transformers, vertical output transformers, vertical blocking oscillator transformers, horizontal blocking oscillator transformers, horizontal output transformers (fly-back), focus coil, deflection yoke, ratio detector transformers and horizontal linearity coils.

SUPREME TEST EQUIPMENT CATALOG

A 24-page catalog, No. 848, illustrating and describing tube and set testers, tube and battery testers, dynamic tube testers, multi-meters, portable set testers, electronic set testers, push-button set testers, fixed-frequency signal generators, *af* and *rf* oscillators, audio generators, audolyzers, 3" and 5" scopes and panel meters, has been announced by Supreme, Inc., Greenwood, Miss.

RADIO TROUBLESHOOTER'S HANDBOOK

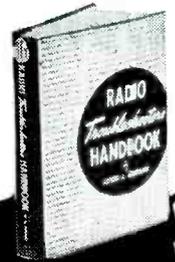ELIMINATES USELESS TESTING . . . on 4 jobs out of 5



...YOUR COMPLETE PRACTICAL RADIO SERVICE LIBRARY

...in two giant books



MODERN RADIO SERVICING

A complete guide to troubleshooting, instruments, circuit analysis, repair.

LEARN TO WORK BY MODERN PROFESSIONAL METHODS

Train for the big pay jobs!

1 Ghirardi's MODERN RADIO SERVICING is a complete 1 vol. course in all phases of professional radio-electronic repair. Tells how to make preliminary trouble checks on difficult jobs; how to analyze any circuit and its components; how, when and where to use all types of test instruments and interpret their readings to track down the trouble—even how to start a service business of your own. Everything is explained simply and thoroughly. 706 clear illustrations and 723 self-test review questions make study easy. Read it for 10 days AT OUR RISK! Complete 1300-page book only \$5—or see special combination price offer below.

CUT TIME IN HALF ON COMMON SERVICE JOBS

2 Work faster—make more money

Almost 4 out of 5 radio repair jobs can be handled as easily as falling off a log! Just look up the model of the set to be fixed. Chances are Ghirardi's RADIO TROUBLESHOOTER'S HANDBOOK tells exactly what the trouble is, exactly how to fix it. Gives common troubles, their symptoms and remedies for over 4800 radios by 202 manufacturers. Hundreds of additional pages contain tube data; transformer trouble listings, alignment charts and dozens of diagrams, etc., for faster, better service on any radio ever made. NOT A "STUDY" BOOK... Just look up the information you want, when you want it! Only \$5—or see special combination offer.

MONEY-SAVING OFFER!

Let Ghirardi's RADIO TROUBLESHOOTER'S HANDBOOK save time, help you make more money on common service jobs. Let MODERN RADIO SERVICING train you in truly scientific servicing that can pave your way to the big money jobs. Get BOTH big books at the special price of only \$9.50 for the two (\$10.50 foreign). Read these helpful books for 10 days at our risk.



Dent, S-19, Murray Hill Books, Inc., 232 Madison Ave., New York 16, N. Y.

Send me the Ghirardi Books checked below for 10-days examination on approval. In 10 days I will pay for the books, plus a few cents postage, or return them postpaid (Postage paid on cash orders; same return privilege. Books sent on approval in U. S. only)

MODERN RADIO SERVICING \$5 (\$5.50 outside U.S.A.)

RADIO TROUBLESHOOTER'S HANDBOOK \$5 (\$5.50 outside U.S.A.)

SPECIAL MONEY-SAVING OFFER Both of above big books only \$9.50 (\$10.50 outside U.S.A.)

Name

Address

City & Zone..... State.....

Servicemen:

HERE IS YOUR SOLUTION TO TELEVISION CAPACITOR TROUBLES...

THE NEW **AMOIL**

PROCESSED TELEVISION BY-PASS CAPACITOR



6000 VOLTS D.C.
CAP. .0005 to .05

NEW SHIELDED CAPACITOR

Completely eliminating any capacity between outer foil and chassis, the new Amcon Shielded Capacitor is highly effective in stopping hum or other extraneous signal noise.



Here is a new capacitor that really "stands up" under the voltages and temperatures encountered in Television circuits. Amoil processed, these new capacitors approach closely the electrical properties of fine mineral oil impregnated units. Simple tubular construction with high melting point wax seal results in an attractive price range.

Ask your Jobber about these two new Amcon Capacitors.

AMERICAN CONDENSER CO.

4410 N. RAVENSWOOD AVENUE, CHICAGO 40, ILL.



Astatic FL SERIES Pickups

Play BOTH 33 $\frac{1}{3}$ and 78 RPM Records WITHOUT changing Needle Pressure or similar adjustments

NOT HAVING to change needle pressure or make similar adjustments—in switching from 33-1/3 to 78 RPM Records with Astatic FL Series Pickups—has done much to put these revolutionary phonograph playing arms in a leading position in the new long-playing equipment field. All that the user need do is change cartridges. Takes only a second, because they are designed to fix themselves in playing position on the same slip-in principle which firmly joins barrel and cap of many modern fountain pens. New engineering, mechanically and electrically, assures perfect tracking, unparalleled reproduction, at the featherlight needle pressure of five grams. Comparable reproduction quality at lower cost is available in other Astatic units, which round out the complete Astatic Long-Playing Line. Write for new brochure, giving full details, illustrations.



FL-33 CRYSTAL PICKUP



FLC-33 CRYSTAL PICKUP



FLT-33 CRYSTAL TRANSCRIPTION PICKUP



400-OT-33 CRYSTAL TRANSCRIPTION PICKUP



Astatic Crystal Devices manufactured under Brush Development Co. patents

HYTRON OCTOBER CONTEST WINNER

First prize in the October Hytron Service Men's contest was won by Charles A. Hurray, Jr., 529 Taylor Avenue, Avalon, Pittsburgh 2, Pennsylvania. Hurray received a Weston model 769 high frequency electronic analyzer.



Left to right: Jack Ludgate, Hytron rep.; center, Al Bauer, manager of the John Marshall Company where presentation was made; and Charles A. Hurray, Jr.

ELECTRO-VOICE TORQUE DRIVE REPLACEMENT SELECTOR GUIDE

A torque drive crystal pickup cartridge replacement selector guide, No. 146, has been published by Electro-Voice, Inc., Buchanan, Michigan.

Chart lists 3 basic types of torque drive cartridges that are said to replace over 150 standard model crystal pickup cartridges in common use.

WELLER SOLDERING TIPS HANDBOOK

A 20-page handbook, *Soldering Tips*, offering a step-by-step discussion of soldering, do's and don'ts etc., has been published by Weller Manufacturing Co., Packer Street, Easton, Pa.

Can be obtained at 10c per copy from any Weller distributor, or by sending 10c in coin direct to Weller.

RIDER MANUAL VOLUME XVIII

Volume XVIII of the Rider manuals will be available at all Rider jobbers in late January, 1949. The latest addition will contain more than 2,000 pages. AM, FM and auto receivers, as well as a special record changers section will be included. *How It Works* books explaining modern theory will be included with a cumulative index covering volumes XVI, XVII and XVIII. Price, \$19.80.

MEISSNER CATALOG

A 12-page catalog, 48B, covering TV kits, TV rf tuners, if strips, audio if strips, AM/FM tuners, analysts, portable radio-phonorecorders, superhet kits, chokes, replacement if windings, rf coils, oscillator coils, plastic if transformers, iron-core ifs and AM/FM radio-phonorecorders, has been prepared by the Meissner Manufacturing Div. of Maguire Industries, Inc., Mt. Carmel, Ill.


TAC PROJECTION MANUAL

A 93-page manual, covering assembly details on a projection assembly TV receiver, has been published by Television Assembly Co. Manual prepared by John F. Rider Labs in collaboration with Gerard R. Francoeur, TAC's chief engineer, covers TAC Model P-520. Available at \$2.50 per copy.

Camco


TV and FM ANTENNAS
(Swift-Rig)

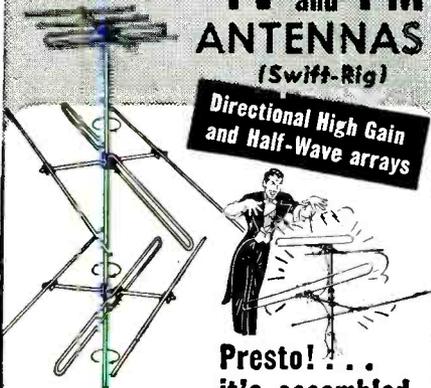Directional High Gain and Half-Wave arrays



Presto! . . . it's assembled

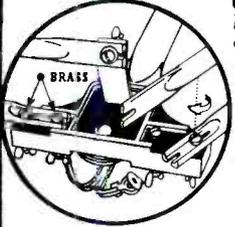"Swift-Rig" antennas are completely assembled — Just Unfold and Lock in Place . . . A matter of minutes.



One of the leading lines of TV and FM Antennas and Accessories Made.

Outstanding Features

- PERMANENT LOW RESISTANCE . . . nickel plated brass screws and "SWIFT RIG" LUGS at electrical contacts
- SEPARATE STACKED ARRAYS . . . Directional High Gain antennas for each band of frequencies

Send for catalog showing complete Camco line of antennas and accessories including Roto-Matic Window and Hy-Gain Indoor Antennas, Combination Screw Eyes for 300 ohm line and coaxial cable, Mast-Mounting brackets (chimney, vent pipe, wall-mount), "Swift-Rig" Lugs, etc.

CAMBURN • INC.

32-40 57th St., Woodside, L. I., N. Y.

FOR T-V SERVICING

Investigate the Mega-line of instruments:

- MEGA SWEEP
- MEGA PIPPER
- MEGA-MARKER
- MEGA-MARKER SR.

Request Catalog


Kay Electric Company

19 Maple Ave., Pine Brook, N. J.

New TV Parts . . . Accessories

ARTISAN TV WORKSHOP TRAILER


A workshop trailer designed for transporting ladders, tools, materials and equipment for use by television installers has been announced by Artisan Products, Inc., 3540 W. 140 St., Cleveland 11, Ohio. Has side compartments on each side equipped with shelves and a material tray, together with key locking handles. Trailer body is available for installing on a 1/2-ton and 3/4-ton truck chassis. Bulletin B contains further data.

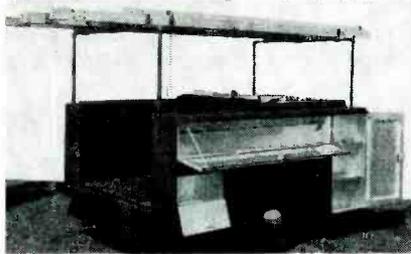

TELREX CONICAL ANTENNAS

A stacked conical V beam, 4X-TV for channels 2 to 13, has been announced by Telrex, Inc., 26 Neptune Highway, Asbury Park, N. J.

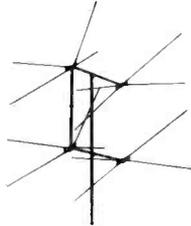Has low inception angle, 4:1 front-to-back ratio on all frequencies, 150-ohm non-varying center impedance. Can be used with 72, 150 or 300-ohm transmission lines.



TACO STACKED HF TV ANTENNA ADAPTER

A hf TV antenna adapter, type 444, has been announced by Technical Appliance Corporation, Sherburne, N. Y.

By means of a coupling clamp included in the kit, the antenna can be mounted directly above the lf antenna. A connecting stub, cut to the correct electrical length and allowing enough mechanical length to orient the hf antenna independently from the low-frequency antenna, is also furnished.

JFD TV ANTENNA KITS

Four low-band and high-band TV antenna kits, the Sky-King series, have been announced by the JFD Manufacturing Co., Inc., 4117 Ft. Hamilton Parkway, Brooklyn 19, N. Y.

The Sky-King series is made up of 4 separate antenna kits: No. LD1 (low-band), consisting of one lf straight dipole, crossarm, lf reflector and 1/2 wavelength of 300-ohm twin-lead; No. HD1 (high-band), consisting of one hf straight dipole, crossarm, hf straight reflector and 1/2 wavelength of 300-ohm twin-lead. Two other kits are folded dipole lf and hf versions.

MAN! . . . This new OHMITE RESISTOR CABINET sure saves me time!

Get YOUR All-Plastic Cabinet by Purchasing the Resistor Assortment

of 1/2-watt "Little Devils" . . . \$12⁵⁰
or 1-watt "Little Devils" . . . \$18⁷⁵

It's easy to find the right resistor . . . fast . . . in this handy, handsome, all-plastic OHMITE cabinet. Compact — only 9" x 5 1/4" x 4 3/4" — its 40 compartments are packed with a selected serviceman's assortment of 125 individually marked "Little Devil" resistors in 40 values from 10 ohms to 10 megohms. And, you pay only the regular price of the resistors . . . nothing extra for cabinet.



See Your Distributor

BROWN DEVIL

Vitreous Enamel Resistors



A favorite with servicemen. Easily mounted by its tinned wire leads. In sizes 5, 10, and 20 watts. Tol. ±10%.

DIVIDOHM

Adjustable Resistors



Vitreous enameled. 10 to 200 Watts. Ideal for securing odd resistance values.

OHMITE MANUFACTURING CO.
4877 Flournoy Street • Chicago 44, Ill.

Be Right with
OHMITE


RHEOSTATS • RESISTORS • TAP SWITCHES

MOBILE WORKSHOP TRAILER

for TELEVISION INSTALLATION SERVICE

E
C
O
N
O
M
I
C
A
L

E
F
F
I
C
I
E
N
T

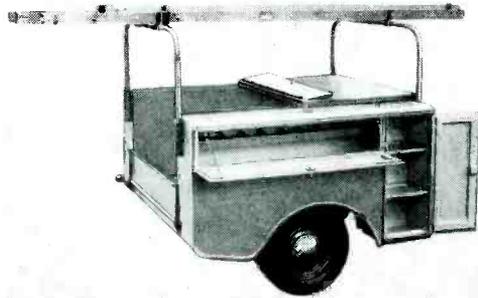

The All Purpose Workshop Trailer of All Steel Construction Can Be Readily Towed by a Car or Truck



Two lengths 75" and 90"
—Equipped with 2,000# capacity axle, Adjustable landing gear and safety coupler. Trailer body has shelves, material tray, and key locking door handles.



Write for "Bulletin B" Describing Trailer, or "Bulletin A" Covering Light Service Bodies for Installation on 1/2 and 3/4 Ton Trucks

ARTISAN PRODUCTS, INC.

3540 WEST 140th STREET

CLEVELAND 11, OHIO


ANDREW TV/FM DI-FAN ANTENNA

A broadband antenna, type 710 Di-Fan, that is broadly tuned to all television and FM channels, has been announced by the Andrew Corp., 421 Seventh Ave., New York 1, N. Y.

The horizontal directivity pattern of the Di-Fan in TV channels 2 through 6 and in the FM band is a figure eight, broadside to the major axis of the antenna. In the high-frequency TV channels 7 through 13, the forward gain is decreased somewhat while the angle of acceptance is enlarged.

Maintains 300 ohm standard impedance over the TV bands. Elements constructed of aluminum alloy. Supporting parts of plated steel.

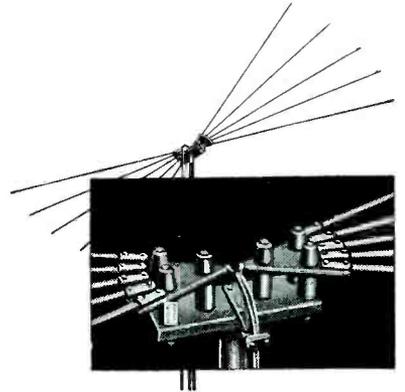For further information write to J. F. White.



* * *

PHOENIX ELECTRONICS STANDOFF INSULATOR

An antenna standoff insulator which clamps on masts up to 1 1/2" in diameter, has been announced by Phoenix Electronics, Lawrence, Mass.

Lead-in cable is held in place by a plastic insert.

* * *


RCP TV 'SCOPE AND SWEEP GENERATOR

A combination 'scope and sweep generator, Tee Vee 90, has been announced by Radio City Products Co., Inc., 152 West 25 Street, New York City.

'Scope can be used independently with its own sinusoidal sweep generator. Sync is provided for internal positive or line frequency.

Independent sweep generator has continuously variable bandwidth from 50 kc to 6 mc with range of 4.5 to 30 mc.

* * *

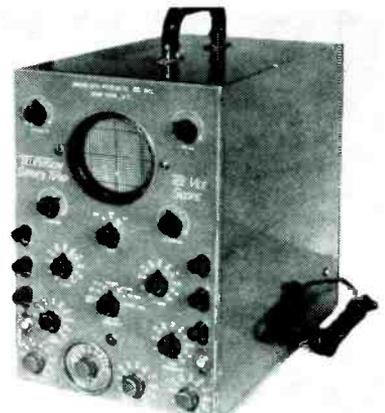

FM-AM SIGNAL GENERATOR

HICKOK Crystal Controlled

High FM output.

- FM frequencies to 160 MC.
- Two sweep frequencies —30KC and 50MC.
- Self-contained decibel meter.
- Audio frequencies 0 to 15,000 cycles. Plus many other features.

Mail this ad for literature and free copy of our regular 50c Service Instruction Manual.

THE HICKOK ELECTRICAL INSTRUMENT CO.
10921 Dupont Avenue • Cleveland 8, Ohio




Ask For Model 288X

telrex INC.
CONICAL ANTENNAS
RUTHERFORD AVENUE ON ROUTE 35
ASBURY PARK, N. J. PHONE ASBURY PARK 1 0119

BOX 879A, ASBURY PARK, N. J.

- Hi-Gain Stacked Conical "V" Beam
- Channels 2 to 13 Plus FM
- Low Inception Angle
- Extremely High Signal to Noise Ratio
- 150 Ohm Non-varying Impedance
- Use 72, 150 or 300 Ohm Transmission Lines
- Universal Mounting Clamps

SEE YOUR DISTRIBUTOR

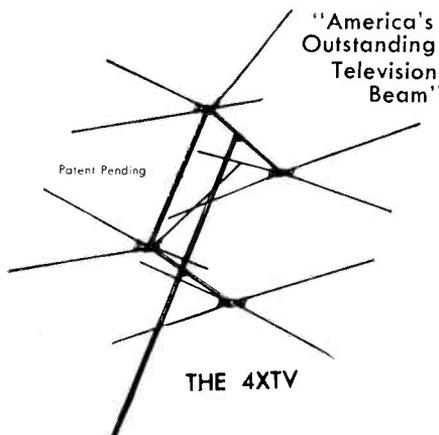

"America's Outstanding Television Beam"

Patent Pending

THE 4XTV



REMEMBER It's Exclusive!

Only Quam manufactures the Adjust-A-Cone Speaker! It is designed with a voice coil, which, instead of being permanently glued to the basket as in ordinary construction, can be adjusted laterally and accurately centered before leaving the factory.

This means that rubbing voice coils, generally so common when they are glued, are practically eliminated in Quam Adjust-A-Cone Speakers.

It is developments like this, ensuring perfect performance and customer satisfaction, that make Quam Speakers the logical choice of the serviceman!

Write for Catalog of
Quam Adjust-A-Cone Speaker

QUAM-NICHOLS CO.
526 East 33rd Place
Chicago 16, Illinois

QUAM SPEAKERS ARE LISTED IN
THE RADIO INDUSTRY RED BOOK

Servicing Helps

(Continued from page 26)

1000 cycles to 50 cycles by changing the value of the 2700-ohm resistor, R_{104} , to 12,000 ohms and the value of the .01-mfd capacitor, C_{103} , to .03 mfd. This type of equalization provides a rise of 2 to 2.5 db at 300 cycles and a drop of 1 to 2 db at 50 cycles. Alternately, two compensation stages can be incorporated.

This effectively provides the full 6 db/octave and will produce an output curve which is flat within ± 1 db from 1,000 to 50 cycles.

[To Be Continued]

Instruments . . . Accessories

SYLVANIA DC VOLTAGE MULTIPLIER FOR POLYMER

A *dc* voltage multiplier for the Sylvania polymer, which extends *dc* voltage measurements to 10,000 volts, has been announced by the Radio Tube Division of Sylvania Electric Products, Inc., 500 Fifth Avenue, New York 18, N. Y.

When used in place of the standard Polymer low-voltage probe, it multiplies each of the present *dc* voltage ranges by a factor of 10.

* * *

JENSEN CONSOLES

A radio-phono cabinet, the customode Imperial Console, has been announced by the Jensen Manufacturing Company, 6601 S. Laramie, Chicago, Illinois. Incorporates a correctly proportioned bass reflex enclosure for 15" speakers.

Console is 36" high, 37 $\frac{1}{4}$ " wide and 18" deep. Record changer compartment is of the integral drawer type and accommodates drop, micro-groove, or intermix-type changers. Two drop-front door compartments are provided for tuners, amplifiers or similar equipment.

Satin-finish brass door pulls. Available in muted blonde or Cordovan mahogany.



* * *

AMCON TV CAPACITORS

TV capacitors, *Amoil* type, rated at 6,000 volts *dc*, in capacities from .0005 to .05 mfd. have been announced by The American Condenser Company, 4410 N. Ravenswood Avenue, Chicago 40, Illinois. Uses Amcon's newly developed petroleum product, which is said to approach electrical properties of capacitors impregnated with mineral oil.

* * *

TUNG-SOL TUBE LABEL

A decalcomania type tube label designed to withstand the extreme operating temperatures of some of the hot miniature tubes, has been announced by Tung-Sol.

It is said that the label will not scorch, smoke, have offensive odor, or discolor.

•

Noll TV Article

THE EDWARD NOLL article on TV sync will appear in February SERVICE.

CHECK!

TOUGHER POWER RHEOSTATS!



MAXIMUM HEAT DISSIPATION

Because wire winding is on insulated metal core and imbedded in cold-setting inorganic cement. Excellent heat conduction takes thermal strain off wire.

POSITIVE CONTACT

Graphite-copper contact shoe provides short-path conduction between third rail and wire winding. Uniform contact pressure. Shaft and bushing insulated from current-carrying arm, for safety.

LASTS AND LASTS!

Exceptionally rugged mechanically and electrically. Trouble-free design. No smoking, burning, charring. 25- and 50-watt ratings. Favorites in those "stay-put" assemblies.

CLAROSTAT



Ask your
Clarostat
jobber for
latest cat-
alog. Or
write us.

Controls and Resistors

CLAROSTAT MFG. CO., Inc., Dover, N. H.

In Canada: CANADIAN MARCONI CO., LTD.
Montreal, P.Q., and branches

MUSIC AND PAGING

NOW ALL IN ONE PACKAGE

FOR RESTAURANTS, SMALL FACTORIES, RETAIL STORES AND DISPLAY ROOMS



A flip of the switch stops music, adjusts response and opens paging for entire area or only a portion as desired.

List Price with Tubes and Cover **\$7950**

The Newcomb Model P-10 delivers a full clear 10 watts. Includes bass boost and treble boost or attenuation controls. Selective paging switch saves hours of installation time. With Micro-Groove changer provides lowest cost good music for commercial use PLUS desirable paging feature.

Look to the complete Newcomb line of amplifiers for more easy-selling features, more models to choose from, wider price range, greater quality at any price... all combined to help you make more repeat sales, more profit.

See your Newcomb distributor or write for specifications of the PM-10. It's another example of Newcomb leadership in the sound equipment field.

NEWCOMB AUDIO PRODUCTS CO.

6824 LEXINGTON AVE. • HOLLYWOOD 38, CALIF.

JOTS AND FLASHES

"TV IN 1949 will pass many other industries on its way up to one of the top ten industries of this country," predicted Ross D. Siragusa, president of Admiral Corp., in his annual message to the industry. He said that production for the industry will be more than doubled in '49 with an estimated 2,000,000 receivers being produced against 800,000 in '48. . . . TV tube production may soon be stepped up substantially as a result of new manufacturing techniques developed by the Pittsburgh Plate Glass Company. Older methods of molding glass blanks to obtain spherical perfection have been replaced by a method whereby the meticulous grinding and polishing operations are reduced to a standardized process which is completed while the glass is still flat. A newly developed bending process permits perfect sphericity. The new type face plates may be applied to glass and the alloy cones of the metal-type picture tubes soon to appear in TV models. . . . Operadio won first choice for a booth at the '49 Radio Parts Show, to be held in May in Chicago, at the recent booth drawing in New York City, and selected booth 87. James Millen was second and selected booth 140; V-M Corp., was third, selecting booth 42; Kwikheat Co. was fourth and selected booth 80, and Win-charger, was fifth, selecting booth 176. . . . Airdesign, Inc., Upper Darby, Pa., and Electronic Controls, Inc., East Orange, N. J., have been acquired by Tele-Video Corp., 241 Fairfield Avenue, Upper Darby, Pa. Paul Weathers is president of Tele-Video. . . . Zenith Radio has purchased the Rauland Corp. . . . Shuler Supply Co., 415 Dryades Street, New Orleans, La., has been appointed Sylvania distributor. . . . Bernie Brown, treasurer of D. R. Bittan Co., 53 Park Place, N. Y. 7, N. Y., was married recently. . . . The National Radio Parts Co., 611 New York Ave., Brooklyn, N. Y., are now Sylvania distributors. . . . Leroy W. Beier, 600 South Michigan Avenue, Chicago 5, Ill., is now a rep for Cannon Electric. . . . Les A. Morrow has been named a rep for Newcomb Audio Products, Hollywood, and will represent them in Ohio, Kentucky, West Virginia and western Pa. . . . Rocke, Inc., 13 E. 40th St., New York 16, N. Y., will represent the Clippard Instrument Lab. in metropolitan New York, northern New Jersey and Conn. . . . Louis G. Pacent Jr., has been appointed vice president in charge of manufacturing at Radio Speakers, Inc., 221 E. Cullerton St., Chicago, Ill. . . . Burrows Sales Co. is now located at 1152 South Olive St., Los Angeles 15, Calif. . . . Edward P. Atcherley has been named northwest division manager of renewal tube sales for Sylvania. . . . Paul Hetenyi, formerly president of Solar, has become a consulting engineer for Aerovox. . . . Robert Brotherson, 325 N. Hubbard St., Jackson, Mich., has become a sales rep for Aerovox in the Michigan area. . . . C. Philip Galloway is now sales manager of the L. S. Brach Manufacturing Co., Newark, N. J. . . . Charles Golpenpaul of Aerovox and R. C. Sprague of Sprague Electric are on the program and speakers committee for the RMA silver anniversary celebration which will be held during the week of May 16 in Chicago, coincident with the annual parts show.

ADVERTISERS IN THIS ISSUE


SERVICE INDEX—JANUARY, 1949

AEROVOX CORP.	42
Agency: Austin C. Lescarboursa & Staff	
AMERICAN CONDENSER CO.	44
Agency: Campbell, Reynolds & Evans	
AMERICAN TELEVISION & RADIO CO.	40
Agency: Firestone-Goodman Adv. Agency	
ARTISAN PRODUCTS, INC.	46
THE ASTATIC CORPORATION	44
Agency: Wearstler Advertising, Inc.	
CAMBURN, INC.	45
Agency: Bass & Co.	
CANNON ELECTRIC DEVELOPMENT CO.	38
Agency: Dana Jones Co.	
CHICAGO TRANSFORMER DIV., ESSEX RADIO CORP.	6
Agency: Burton Browne, Advertising	
CLAROSTAT MFG. CO., INC.	47
Agency: Austin C. Lescarboursa & Staff	
CORNELL-DUBILIER ELECTRIC CORP.	Inside Front Cover
Agency: Reiss Advertising	
ALLEN B. DUMONT LABORATORIES, INC.	31
Agency: Austin C. Lescarboursa & Staff	
ELECTRO-VOICE, INC.	39
Agency: Henry H. Teplitz, Advertising	
ERIE RESISTOR CORP.	36
Agency: W. S. Hill Co.	
GENERAL ELECTRIC CO.	1, 27
Agency: Maxon, Inc.	
GENERAL ELECTRIC LAMP DIV.	35
Agency: Batten, Barton, Durstine & Osborn, Inc.	
THE GENERAL INDUSTRIES CO.	41
Agency: Meldrum & Fewsmith, Inc.	
THE HEATH COMPANY	7
Agency: G. Dean Arend, Advertising	
HICKOK ELECTRICAL INSTRUMENT CO.	46
Agency: White Adv. Co.	
HYTRON RADIO & ELECTRONICS CORP.	21
Agency: Henry A. Loudon—Advertising	
J. F. D. MFG. CO., INC.	36
Agency: Bergman-Jarrett Co.	
KAY ELECTRIC CO.	45
Agency: George G. Felt	
P. R. MALLORY & CO., INC.	Inside Back Cover
Agency: Altkin Kynett Co.	
MUELLER ELECTRIC CO.	40
MURRAY HILL BOOKS, INC.	43
Agency: The Harry P. Bridge Co.	
NEWCOMB AUDIO PRODUCTS CO.	48
Agency: Gail Hall Advertising	
OHMITE MFG. CO.	45
Agency: The Fensholt Co.	
PHOENIX ELECTRONICS, INC.	38
Agency: Milton Richards	
QUAM-NICHOLS CO.	47
Agency: Triangle Adv. Agency, Inc.	
THE RADIART CORP.	19, 29
Agency: Ohio Adv. Agency	
RADIO CITY PRODUCTS CO.	43
Agency: Jaman Advertising, Inc.	
RADIO CORPORATION OF AMERICA	17, Back Cover
Agency: J. Walter Thompson Co.	
RAYTHEON MFG. CO.	25
Agency: Walter B. Snow & Staff	
JOHN F. RIDER PUBLISHER, INC.	23
Agency: Shappe-Wilkes Inc.	
HOWARD W. SAMS & CO., INC.	3
Agency: George Brodsky, Advertising	
SPRAGUE PRODUCTS CO.	33
Agency: The Harry P. Bridge Co.	
SYLVANIA ELECTRIC PRODUCTS INC.	8
Agency: Newell-Emmett Co.	
TELREX, INC.	46
Agency: Consuelo Evans, Inc.	
TRIPPLETT ELECTRICAL INSTRUMENT CO.	4
Agency: Western Adv. Agency, Inc.	
TRANSVISION, INC.	37
Agency: H. J. Gold Co.	
TUNG-SOL LAMP WORKS, INC.	5
Agency: G. M. Freystadt Associates, Inc.	

The Little Fellow
Gets BIG Results!



The Mallory Midgetrol

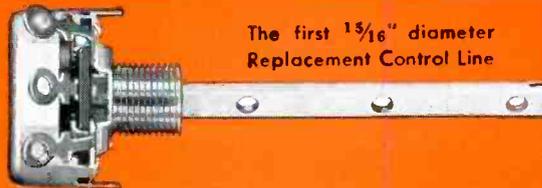

"Phenomenal!"—that's the only word to describe the lightning-like acceptance of Mallory's revolutionary new standard in volume controls. But its success was a foregone conclusion when you realize what the Mallory Midgetrol offers:

WIDER APPLICATION—The small size lets you service portables, auto radios and small AC-DC receivers requiring $\frac{15}{16}$ " controls.

SIMPLER INSTALLATION—The new and unique flat shaft design of the Mallory Midgetrol saves installation time with *all* types of knobs.

LESS INVENTORY—Electrical characteristics allow you to use the Mallory Midgetrol to replace $1\frac{1}{8}$ " as well as $\frac{15}{16}$ " controls. Since no special shafts are required, you carry fewer controls in stock.

Quietest and Smoothest by Actual Tests

And Mallory Midgetrol stays quiet, too. Creative research that has made Mallory the standard in carbon controls has seen to that. In addition, the Mallory Midgetrol offers nine big features all NEW:

NEW SIZE NEW SHAFT NEW SWITCH NEW CONTACT
NEW DESIGN NEW EXTENSION NEW ELEMENT NEW TERMINAL
NEW TWO-POINT SUSPENSION

See your Mallory Distributor for this new standard in carbon controls

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS
*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Engineering leadership is behind every

Cunningham tube



RCA Laboratories, Princeton, N. J.
RADIO CORPORATION of AMERICA

CUNNINGHAM TUBES are far more than the end product of a factory. Behind every Cunningham tube are the vast engineering resources of the famed RCA Laboratories. It is here that continuing research in the fields of chemistry, metallurgy, and electron behavior helps to make *good tubes better*.

Engineering leadership is one of the reasons why you can be confident that every Cunningham tube

you install in a receiver meets the highest standards of quality and dependability.

Cunningham tubes have enjoyed customer acceptance for over 32 years. Whether it's metal, miniature, or glass, there's a Cunningham type to meet practically every service requirement. Your Cunningham Distributor keeps complete stocks on hand to meet your immediate needs.

SEE YOUR CUNNINGHAM DISTRIBUTOR TODAY



A QUALITY PRODUCT OF THE
RADIO CORPORATION OF AMERICA