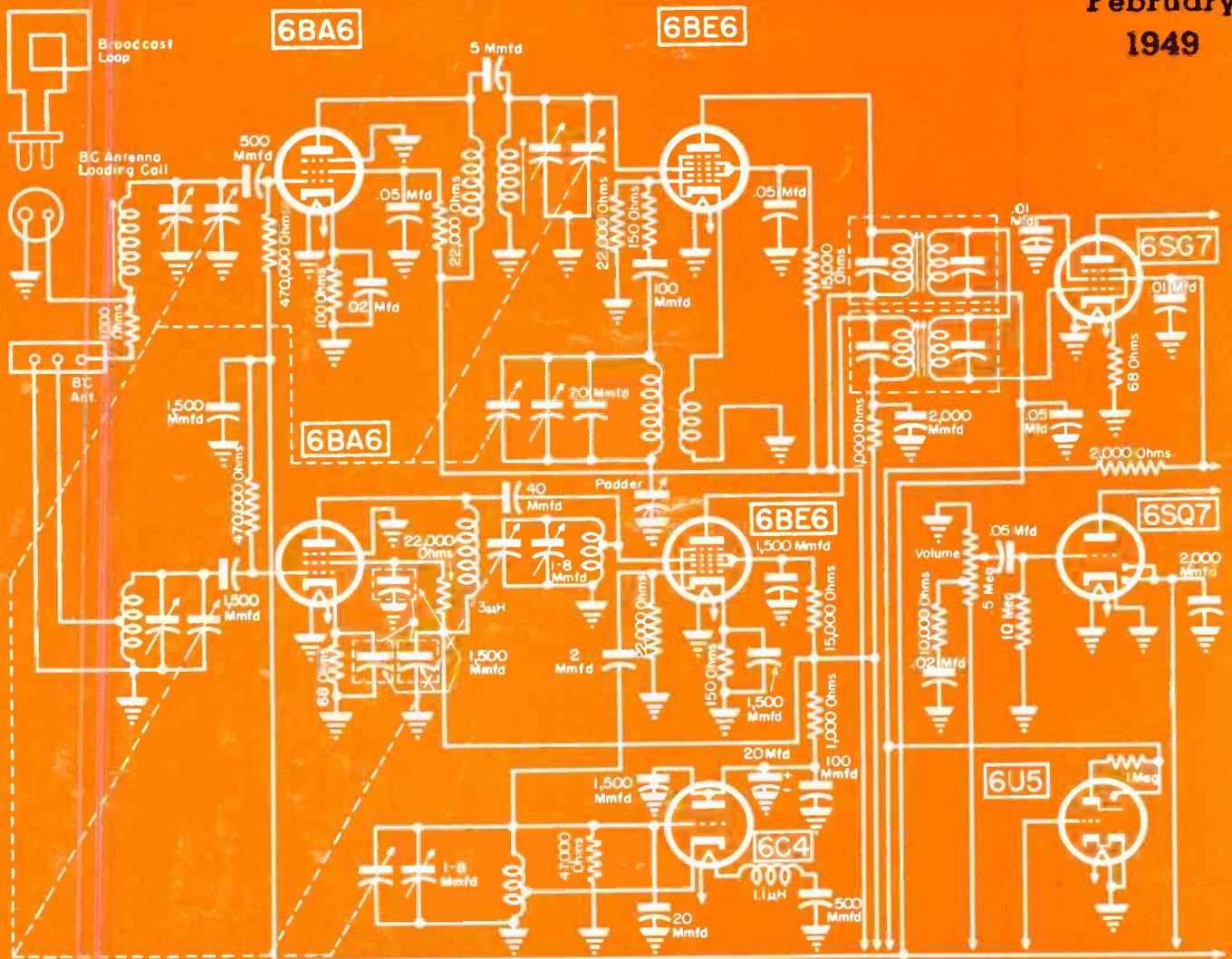


SERVICE

February
1949



The *r_f* converter, mixer, oscillator, *1_f*, first of and tuning indicator stages of a 10-tube AM-FM tuner.
[See page 2]

C-D'S NEW VIBRATOR



- years ahead in simplicity of construction
- embodies latest developments plus C-D's famous built-in standard of quality
- designed by the nation's foremost vibrator engineers
- a complete line of replacements available

For your local C-D distributor, consult your Classified Telephone Directory . . . or write direct for further details. Cornell-Dubilier Electric Corporation, South Plainfield, New Jersey. Other plants in New Bedford, Brookline, and Worcester, Mass.; Providence, R. I. and Indianapolis, Indiana.

1910



1949

CORNELL-DUBILIER

world's leading manufacturer of

**VIBRATORS
CAPACITORS • CONVERTERS**

"KEN-RAD TUBES BRING REPEAT BUSINESS!"



Says C. F. PATTERSON, J & M Radio Service Shop, 838 North Rampart, New Orleans, La. Like thousands of reliable service men, Mr. Patterson insists on Ken-Rad tubes because he knows quality pays off.

"I started in business in 1933 and I've been using Ken-Rad tubes ever since!


"In all that time I've never had a complaint. Ken-Rad tubes perform. They last. No other tube I know does a better job for you or your customers.

"This is important, because you've got to satisfy customers if you're going to build repeat business.

"Ken-Rad tubes always satisfied my customers. And that satisfies me."



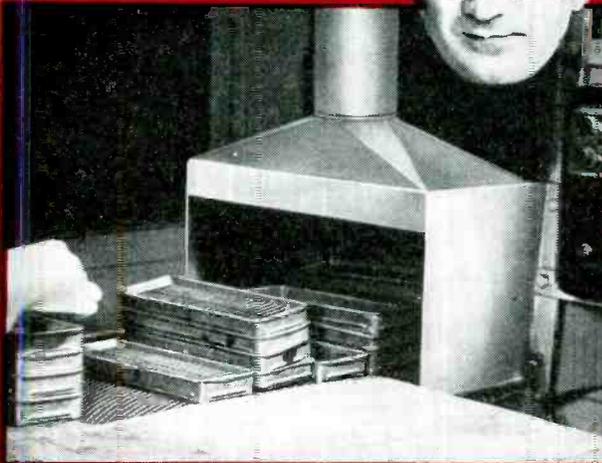HUGH WATSON, Foreman, Grid Section, where grids are shown below going into 700-degree (centigrade) GE furnace to be de-gassed and de-oxidized. Every precaution is taken in making Ken-Rad tubes to assure top performance, long life.



"KEN-RAD TUBES ARE TESTED TUBES!"

"Ken-Rad tubes satisfy customers and build repeat business because they're tested tubes. Tops in quality, stamina, endurance.

"I know—because I've been supervising the making of Ken-Rad tubes for years.

"We make Ken-Rad tubes with the greatest of care. They're thoroughly tested for noise, microphonics, static, life, shorts, appearance, gas, air and hum.

"You can sell them with confidence. And you can rely on them to increase business, too!"



The Serviceman's Tube

KEN-RAD *Radio Tubes*

PRODUCT OF GENERAL ELECTRIC COMPANY

Schenectady 5, New York

102-MA2-8850



LEWIS WINNER
Editorial Director

F. WALEN
Assistant Editor

ALFRED A. GHIRARDI
Advisory Editor

	Page
AM/FM Tuner and AF Amplifier (Cover)	18
Association News	26
Custom-Built Cabinets. By Martin W. Elliott	24
Horizontal AFC System in Magnavox TV Receivers. By J. F. Bigelow	14
Ser-Cuits (Sparton Indirect View TV Sets)	20
Servicing Helps. By P. M. Randolph	34
Ten Years Ago in Associations	26
TV Antenna Installation Tricks of the Trade. By Ira Kamen	12
Viewing Areas of TV Receivers. By Robert P. Wakeman	10
Views and News. By Lewis Winner	9

CIRCUITS

A <i>dprt</i> Switch Circuit for HF or LF Antennas and Coax Lines	13
A Two-Gang Double-Pole Three-Position Switch Circuit for Insertion of Pads in 300-ohm Line	13
Basic Circuit of Magnavox AFC TV System	14
Coax Switching Circuit	13
Divider and Decoupler Network Circuits	30
Dual-Purpose Antenna Array for 72 and 300-ohm Lines	29
Espey 513 AM/FM Tuner (Cover)	18
Espey 514 AF Amplifier	18
Flexible Pad Circuit for Adjustment of Signal Level Between 300-ohm Line and Input	13
Parallel Coax-Line Setup	13
Pad Circuit for 72-ohm Line Adjustment	13
Sparton 4939TV/4940TV/4941TV Receivers	20

COVER

AM/FM Tuner (Espey 513)	18
-------------------------------	----

SERVICING HELPS

HF Peaking Circuit	36
LF and HF Peaking Circuits	36
Preamp Equalization	34
Service Notes on Philco 48-1270, Crosley 66TA, Philco CR4-6, G. E. 250/260 and Silvertone 101.802	38
Table of Coax Cable Characteristics	34

Index to Advertisers	48
----------------------------	----

Manufacturers

New Instruments . . . Components . . . Accessories	46
New TV Parts . . . Accessories	43
News	47
Jots and Flashes	48

Entire contents Copyright 1949, Bryan Davis Publishing Co., Inc.



Published monthly by Bryan Davis Publishing Co., Inc.
52 Vanderbilt Avenue, New York 17, N. Y. Telephone MURRAY Hill 4-0170



Bryan S. Davis, President Paul S. Weil, Vice-Pres., Gen. Mgr. F. Walen, Secretary A. Goebel, Circulation Manager


Cleveland Representative: James C. Munn, 2253 Delaware Dr., Cleveland 6, Ohio. Telephone: ERLEVIEW 1726

Pacific Coast Representative: Brand & Brand, 1052 W. Sixth St., Los Angeles 14, Calif. Telephone: MICHIGAN 1732
Suite 1204, Russ Building, San Francisco 4, Calif. Telephone: SUTTER 1-2251

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

NOW! The Famous \$500 Photofact TELEVISION COURSE in Book Form!

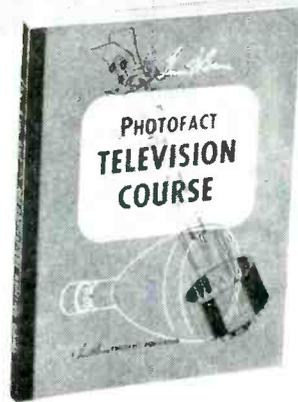Previously available only to Photofact subscribers—now published to answer the insistent demand of the entire Radio Industry



Now you can own the book that gives you a *complete, clear* understanding of modern TV principles, operation and practice. Previously available only in PHOTOFAC T Folder Sets, this superb course has been bound in unified book form to meet an overwhelming demand from radio men in every branch of the industry. Written in clear, easy-to-follow language, profusely illustrated, packed with valuable up-to-the-minute data. Covers every phase of television—gives you the groundwork you *must* have to become a successful TV service technician. Bring your television knowledge up-to-date this easy, economical way. The PHOTOFAC Television Course is available at your jobber—order your copy today! Over 200 pages; fully illustrated; \$300 sturdy binding, 8½ x 11". Only.. **\$300**

A "Must" for Everyone in Radio!

NEW! 1948 Automatic Record Changer Manual

New Volume 2 covers 45 models made in 1948, including new LP and dual-speed changers, plus leading Wire and Tape recorders. It's easy to service record changers when you have the PHOTOFAC Record Changer Manual handy. Complete, accurate data—based on analysis of actual equipment. Gives full change cycle data, information on adjustments, hints and kinks, complete parts lists, exclusive "exploded" diagrams. Have this time-saving, money-making book in your shop. Over 400 pages; de luxe **\$675** bound, 8½ x 11". Only.....



1947 EDITION. Volume 1, Automatic Record Changer Manual. Covers more than 40 different post-war changer models manufactured up to 1948. Includes full hard-to-get data on leading Wire, Ribbon, Tape and Paper Disc Recorders. 400 pages; fully illustrated; 8½ x 11", hard cover. Only..... **\$4.95**

NEW! Specialized Photofact Volumes




POST-WAR AUDIO AMPLIFIERS and Associated Equipment

This is the book that's wanted by custom-builders, audio men and sound engineers. Covers a wide variety of well-known audio amplifiers and FM and AM tuners, plus data on important wire and tape recorders. Presents a complete analysis of each unit. A "must" for custom-installers and for sound service specialists. 352 pages; fully illustrated; in sturdy binding, 8½ x 11". Only..... **\$3.95**



POST-WAR COMMUNICATIONS RECEIVER MANUAL

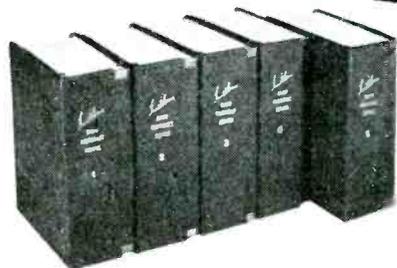New! Invaluable to Amateurs and Short Wave Listeners. Complete technical analysis of more than 50 of the most popular communications sets on the market. An invaluable service aid, a perfect buying guide for purchasers of communications receivers. All data based on actual examination and study of each unit. 264 pages; profusely illustrated; durably bound, 8½ x 11". Only..... **\$3.00**




NEW! Photofact Volume 5

Latest addition to the famous PHOTOFAC Volume series—brings your file of post-war receiver service data right up to December 1948! Most accurate and complete radio data ever published—preferred and used daily by thousands of Radio Service Technicians. Everything you need for faster, more profitable servicing. Order Volume 5 today—keep ahead with PHOTOFAC—the *only* Radio Service data **\$18.39** that meets *all* your needs! In deluxe Binder...

- Vol. 5. Models from July 1, 1948 to Dec. 1, 1948
- Vol. 4. Models from Jan. 1, 1948 to July 1, 1948
- Vol. 3. Models from July 1, 1947 to Jan. 1, 1948
- Vol. 2. Models from Jan. 1, 1947 to July 1, 1947
- Vol. 1. All post-war models up to Jan. 1, 1947

Radio Industry Red Book

The RED BOOK tells you in *one volume* what you need to know about replacement parts for approximately 17,000 sets made from 1938 to 1948. Includes complete, accurate listings of all 9 major replacement components—not just one. Lists correct replacement parts made by 17 leading manufacturers—not just one. Covers original parts numbers, proper replacement numbers and valuable installation notes on: Capacitors, Transformers, Controls, IF's, Speakers, Vibrators, Phono-Cartridges. Plus—Tube and Dial Light data, and Battery replacement data. 448 pages, 8½ x 11". **\$3.95** sewed binding. ONLY.....

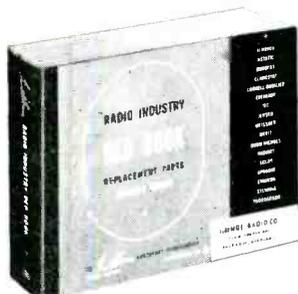

TUBE PLACEMENT GUIDE. Shows you exactly where to replace each tube in 5500 radio models, covering 1938 to 1947 receivers. Each tube layout is illustrated by a clear, accurate diagram. Saves time—eliminates risky hit-and-miss methods. 192 pages; handy index. ONLY..... **\$1.25**

DIAL CORD STRINGING GUIDE. The book that shows you the *one right* way to string a dial cord. Here, in one handy pocket-sized book, are all available dial cord diagrams covering over 2300 receivers, 1938 through 1946. Makes dial cord restringing jobs quick and simple. ONLY..... **\$1.00**

FREE Photofact Cumulative Index

The easiest way to own the world's finest Radio Service Data is to subscribe regularly to PHOTOFAC Folder Sets. Send for the FREE Cumulative Index to PHOTOFAC Folders covering *all* post-war receivers up to the present. Helps you find the Folders you want in a jiffy. Get this FREE Index at your Jobber or write for it now.



ORDER THESE BOOKS FROM YOUR JOBBER


HOWARD W. SAMS & CO., INC.
INDIANAPOLIS 7, INDIANA

Have ALL THE FUN
SAVE 2/3 THE COST

Build YOUR OWN TEST EQUIPMENT

1 Heathkit VACUUM TUBE VOLTMETER KIT

Everything you want in a VTVM. Shatterproof solid plastic meter face, automatic meter protection in burn-out proof circuit, push pull electronic voltmeter circuit assuring maximum stability. Linear DC and AC scales. AC and DC full scale ranges of 3V-10V-30V-100V-300V-1000V. A total of 24 ranges. Isolated DC test prod for signal tracing and measurements of voltage while instrument is in operation. An ohmmeter section accurately measuring resistance of 1/10 ohm to one billion ohms with internal battery. Extremely high input resistance 11 megohms on all ranges DC and 6.5 megohms on AC. All these features and many more are the reasons hundreds of radio and television schools are using Heathkit VTVM's and recommending them to all students. Like all Heathkits, the VTVM kit is complete, 110V. 60 cycle power transformer, 200 microamp meter, tubes, grey crackle cabinet, panel, test leads, 1% ceramic precision divider resistors and all other parts. Complete instruction manual. Better start your laboratory now.
Shipping weight 8 lbs..... **\$24.50**

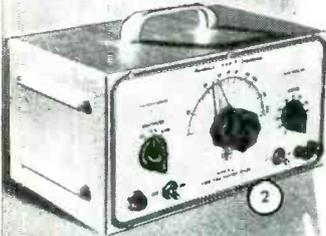


2 Heathkit SINE AND SQUARE WAVE AUDIO GENERATOR KIT

The ideal instrument for checking audio amplifiers, television response, distortion, etc. Supplies excellent sine wave 20 cycles to 20,000 cycles and in addition supplies square wave over same range. Extremely low distortion, less than 1%, large calibrated dial, beautiful 2 color panel, 1% precision calibrating resistors, 110V. 60 cycle power transformer, 5 tubes, detailed blueprints and instructions. R.C. type circuit with excellent stability.
Shipping weight 15 lbs..... **\$34.50**




3 Heathkit CONDENSER CHECKER KIT

Checks all types of condensers, paper mica — electrolytic — ceramic over a range of .00001 MFD. to 1000 MFD. All on readable scales that are read direct from the panel. NO CHARTS OR MULTIPLIERS NECESSARY. A condenser checker anyone can read without a college education. A leakage test and polarizing voltage of 20 to 500 volts provided. Measures power factor of electrolytics between 0% and 50%. 110V. 60 cycle transformer operated complete with rectifier and magic eye tubes, cabinet, calibrated panel, test leads and all other parts. Clear detailed instructions for assembly and use. Why guess at the quality and capacity of a condenser when you can know for less than a twenty dollar bill.
Shipping weight 7 lbs..... **\$19.50**

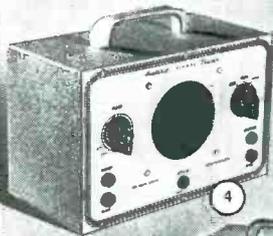

4 Heathkit SIGNAL TRACER KIT

Reduces service time and greatly increases profits of any service shop. Uses crystal diode to follow signal from antenna to speaker. Locates faults immediately. Internal amplifier available for speaker testing and internal speaker available for amplifier testing. Connection for VTVM on panel allows visual tracing and gain measurements. Also tests phonograph pickups, microphones, PA systems, etc. Frequency range to 200 Mc. Complete ready to assemble. 110V. 60 cycle transformer operated. Supplied with 3 tubes, diode probe, 2 color panel, all other parts. Easy to assemble, detailed blueprints and instructions. Small portable 9" x 6" x 4 3/4".
Shipping Wt. 10 lbs..... **\$19.50**

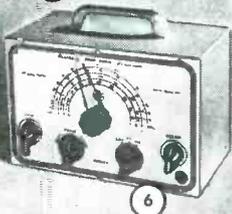

5 The NEW 1949 HEATHKIT 5-INCH OSCILLOSCOPE KIT

New improved model of the famous Heathkit Oscilloscope. Building an oscilloscope is the finest training for television and newer servicing technique and you save two-thirds the cost. All the features and quality of instruments selling for \$100.00 or more. Supplied complete with cabinet, two color panel, 5BP1 tube, 2 5Y3 tubes, 2 6SJ7 tubes and 884 generator tube. Power transformer supplies 1000 volt negative and 350 volt positive. Sweep generator 15 cycles to 30 M. cycles. Has vertical and horizontal amplifiers. Oil filled filter condensers for long life. Complete blueprints and instructions included.
Shipping weight 25 pounds. **\$39.50**
Express only.....



6 Heathkit FM AND TELEVISION SWEEP GENERATOR KIT

A necessity for television and FM. This Heathkit completely covers the entire FM and TV bands 2 megacycles or 230 megacycles. The unit is 110V. 60 cycle transformer operated. Uses two 6J6 tubes, two 6C4 tubes and a 6X5 rectifier. An electronic sweep circuit is incorporated allowing a range of 0 to 10 MC. A sawtooth horizontal sweeping voltage and phase control are provided for the oscilloscope.

The coils are ready assembled and precision adjusted to exact frequency. As in all Heathkits, the best of parts are supplied, Mallory filter condenser, zero coef. ceramic condensers, all punched and formed parts, grey crackle cabinet, 5 tubes, test leads, etc. Better get it built now and be ready for the FM and TV business. Shipping Wt. 6 lbs... **\$24.50**

7 Heathkit SIGNAL GENERATOR KIT

Every shop needs a good signal generator. The Heathkit fulfills every servicing need, fundamentals from 150 Kc. to 30 megacycles with strong harmonics over 100 megacycles covering the new television and FM bands. 110V. 60 cycle transformer operated power supply.

400 cycle audio available for 30% modulation or audio testing. Uses 6SN7 as RF oscillator and audio amplifier. Complete kit has every part necessary and detailed blueprints and instructions enable the builder to assemble it in a few hours. Large easy to read calibration. Convenient size 9" x 6" x 4 3/4". Ship. Wt. 7 lbs..... **\$19.50**

ORDER DIRECT FROM THIS AD.
WE WILL SHIP C. O. D.
Add Postage for Weight Shown


HEATH COMPANY
BENTON HARBOR 11,
MICHIGAN

GT and HYTRON go together

HERE'S WHY

- 1 Hytron originated the Bantam GT—the most popular receiving tube.
- 2 Hytron has introduced more than fifty GT types.
- 3 Hytron has the longest—the most extensive experience with GT's.

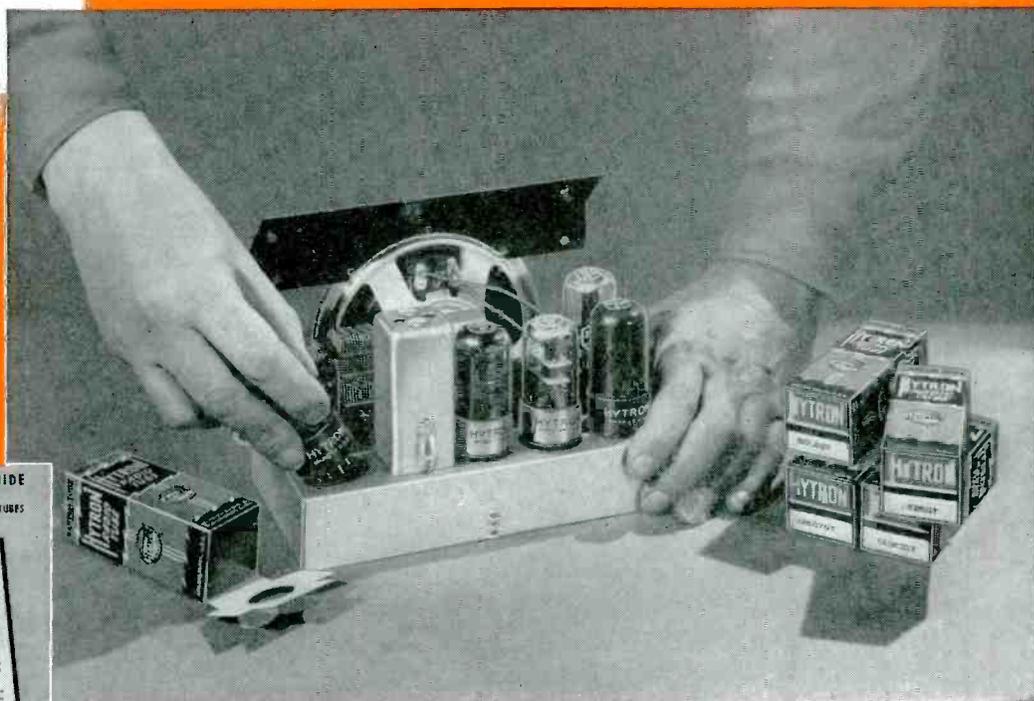Your conclusion: Think of Hytron when you think of GT. Ask for the original and best. Simplify your inventory problems, too. Stock the popular Hytron GT to replace G, metal, or GT.



← New 3rd Edition HYTRON REFERENCE GUIDE for MINIATURE ELECTRON TUBES

Six pages—91 miniature tubes, 19 of them new. Unique, contains pertinent data and basing diagrams for all miniatures announced to date, regardless of make. Lists similar larger prototypes.

NOW AVAILABLE AT YOUR HYTRON JOBBERS.

SPECIALISTS IN RADIO RECEIVING TUBES SINCE 1921.

HYTRON

RADIO AND ELECTRONICS CORP.

MAIN OFFICE: SALEM, MASSACHUSETTS





OVER 100 PAGES OF PROFUSELY
DIAGRAMMED, PRACTICAL,
UP-TO-THE-MINUTE
INFORMATION COVERING—

NOW ON THE PRESS

THE FIRST PRACTICAL BOOK

ON THE INSTALLING OF TV and FM RECEIVER ANTENNAS

TV... FM ANTENNA INSTALLATION

by IRA KAMEN
and LEWIS WINNER

Antenna Tools

(Basic Tools Required . . . Application of the Correct Tools for Specific Types of Installations, Involving Flat-top Roofs, Slate Roofs, Tile Roofs, Chimneys, Etc.)

The TV Antenna Installation Problem

(Fundamentals of All TV Installations . . . Judging Specific Application Features of the Various Types of Antennas Which Can Be Used for TV Work . . . Solving Reflection Problems . . . Improving Signal-to-Noise Ratio.)

Solving the Problems of 12-Channel Reception

(Factors With Which Service Men Must Be Familiar to Accurately Install Antennas For Full-Band Coverage . . . Typical Problems Analyzed.)

High Frequency TV Antenna Installations

(Antennas and Installation Procedures Which Afford Best Results. Solving Major Installation Problems Involving Tuned Indoor and Outdoor Antennas. Application of Stub Filters.)

TV Interference

(Analysis of Nine Sources of Interference and Solutions Which Have Proved Effective.)

Fringe Reception

(Selecting and Installing Antennas for Maximum Reception in Areas Over 45 Miles From Stations . . . Tower Installations . . . Estimating Tower Costs.)

TV Master Antenna Systems

(Typical Multiple Dwelling Antenna Systems for Simultaneous Operation of Many Receivers From a Single Antenna Array and Amplifier Setup.)

FM Antennas

(Analysis of Practical FM Antennas . . . Selecting Proper Antenna for Rural and Urban Jobs.)

The Business of TV Antenna Installations

(How to Conduct Successfully TV Installation and Service Work Today . . . Proper Use of Correct Types of Installation and Servicing Agreements and Warranties.)

TV Antenna Tricks of the Trade

(Antenna Installation Devices Which Will Improve Picture Fidelity.)

(Indexed for Quick Reference)

BRYAN DAVIS PUBLISHING CO., INC., Book Dept.
52 Vanderbilt Avenue, New York 17, N. Y.

Send me a copy of TV . . . FM Antenna Installation, post-paid, for which I am enclosing \$2.00.

NAME

ADDRESS

CITY AND STATE

6 • SERVICE, FEBRUARY, 1949

● The first edition, now on the press, is limited in quantity. Order Your Copy NOW!

Price \$2 Post Paid


Tube Testers for Today and Tomorrow...

SPECIFY
TRIPLETT

UP and DOWN


Lever Switching Connects Each Tube Pin to Proper Circuit

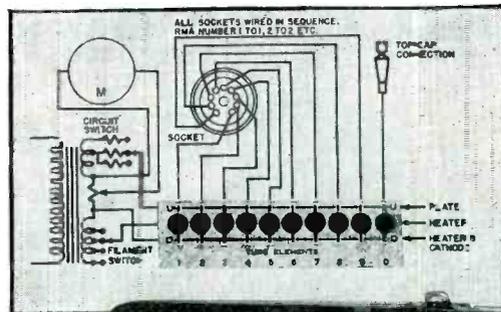- 1. ALL ELEMENT CHECK** — Thorough conclusive test of tube elements, shields and taps. The only commercial tester to get at each tube pin and make an open and short check.
- 2. NO HUNTING FOR SOCKETS** — No plugging into wrong socket. Circuit flexibility requires only one socket for each type of tube base.
- 3. CIRCUIT CLARITY** — Lever switch numbering corresponds to RMA tube pin numbers, connected to bring out each active tube element. A simple up or down motion of the lever instantly makes the connection.
- 4. OPERATION SIMPLICITY** — Minimum of control settings plus straightforward arrangement of this outstanding emission circuit. Generally not more than five of the 10 lever switches need be set.
- 5. "PICTURE" YOUR CIRCUIT** — Assures confidence in tests and enables special tube checks for balanced circuits, special loads, etc. "Trick" switching circuits make it more difficult for the serviceman to "picture" his test circuit.
- 6. SET UP YOUR OWN TEST FOR NEW TUBES** — The "pictured" circuit and straightforward test procedures enable the user to set up data for new tubes. A feature rarely found in commercial type tube testers.
- 7. INDIVIDUAL CONTROL FOR EACH TUBE ELEMENT** — Takes care of roaming elements, dual cathode structures, multi-purpose tubes, etc., in addition to standard value tests.



TUBE TESTER MODEL 3413
Triplet lever switching circuit arrangement has 7 distinct advantages contributing to maximum flexibility, simplicity of operation and anti-obsolence.

NET DEALER PRICE \$66.75

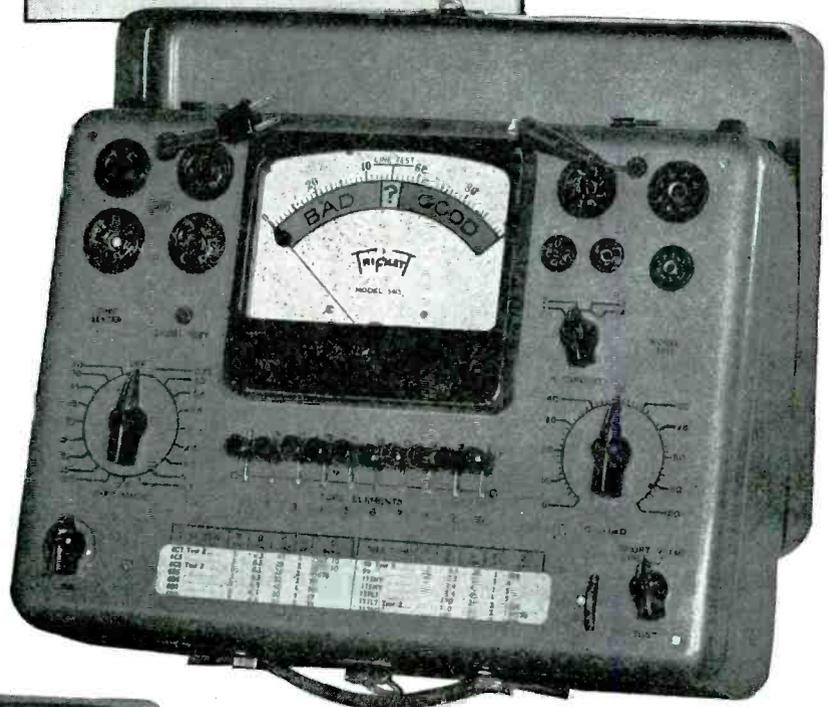

... Combination Volt-Ohm-Mil-Ammeter Model 3480

This tester combines the Tube Tester Model 3413 with complete facilities for voltage current and resistance analyses... a real economy for those shops requiring a combination tube tester and volt-ohm-mil-ammeter... Attractive two tone metal case with detachable hinged cover...

TECH DATA

D. C. Volts: 0-3-12-60-300-1200, at 10,000 Ohms/Volt.
A. C. Volts: 0-3-12-60-300-1200, at 2,000 Ohms/Volt.
D. C. Amps: 0-12, at 250 Millivolts.
D. C. Millamps: 0-1-2-12-120, at 250 Millivolts.
Ohms: 0-1000-10,000 (10-100 at center scale).
Megohms: 0-1-50 (10,000-500,000 Ohms center scale).
Output: Output Jacks, Condenser in series with A. C. Volt ranges.
Scale: 5.6" long on top scale arc. 0-1000 Ohms and 0-50 Megohms on top arc.
0-12-60-300 A. C. and D. C. Volt figures are on four separate arcs. Scale markings are black on white except A. C. are red on white; 0-1K Ohms scale is green on white.



MODEL 3480 \$98.75 ... U.S.A. Dealer Net

SEE AT YOUR RADIO PARTS DISTRIBUTOR OR FOR MORE INFORMATION ... WRITE

TRIPLET ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO, U.S.A.


In Canada: Triplet Instruments of Canada, Georgetown, Ontario

Precision first... to Last



NOW..

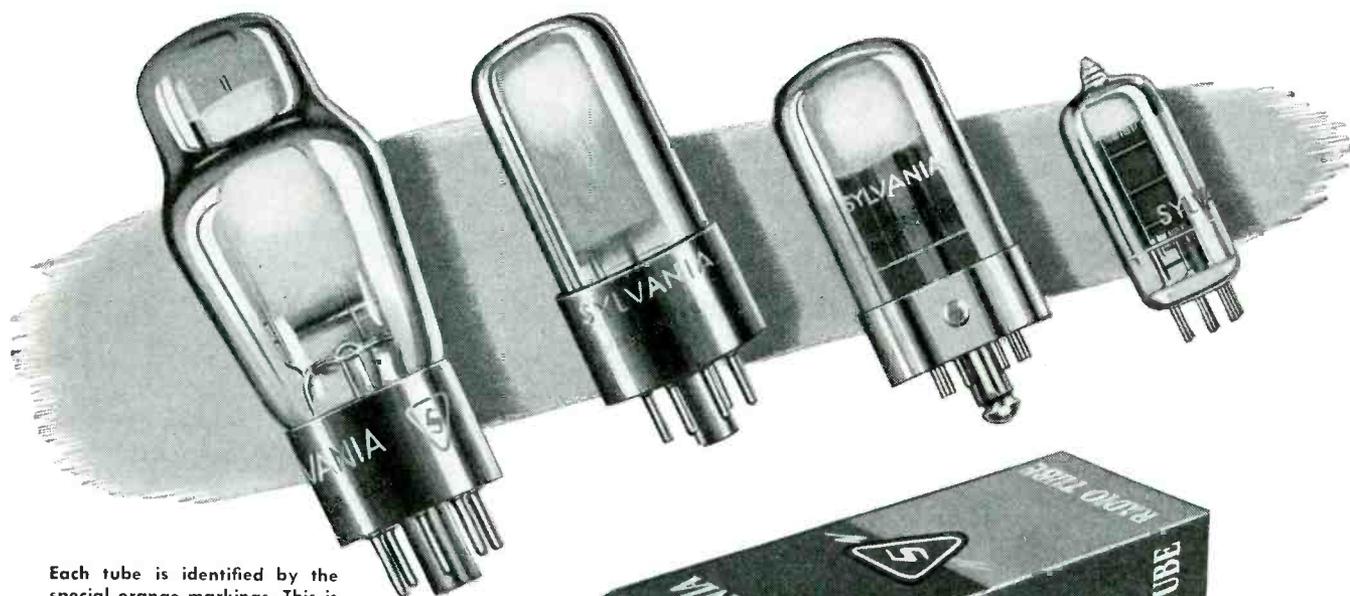SYLVANIA RECEIVING TUBES SPECIALLY PROCESSED FOR FINER TELEVISION PERFORMANCE!




Each tube is identified by the special orange markings. This is your assurance of the higher quality demanded by television.

Now, when you replace worn-out receiving tubes in your customers' television sets, give them the finest in television reception with these new receiving tubes *specially processed* by Sylvania for the extra-tough requirements of television service.

These new Sylvania television tubes, in the new bright orange and green television cartons, actually undergo *three times more exacting tests* to insure they are unsurpassed! Their higher quality and superior performance more than justify their small additional cost.

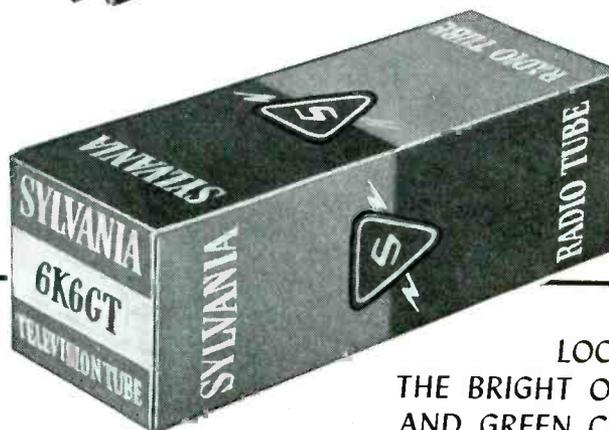They are not just good tubes, they are *superior* tubes . . . results of Sylvania's years of experience in the electronics field. Be sure you have a ready supply for increased television tube replacement business. See your Sylvania Distributor today! Sylvania Electric Products Inc., Radio Tube Division, Emporium, Pa.



LOOK FOR
THE BRIGHT ORANGE
AND GREEN CARTON

Replace worn tubes with these specially processed Sylvania tubes made to pass television's rigid requirements.

AVAILABLE NOW IN THE FOLLOWING TYPES

1B3GT	6J6	7F7
6AG5	6K6GT	7H7
6AL5	7B4	7N7
6BG6G	7B5	7Z4
	7C5	

SYLVANIA ELECTRIC

RADIO TUBES; CATHODE RAY TUBES; ELECTRONIC DEVICES; FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES; PHOTOLAMPS; ELECTRIC LIGHT BULBS

RADIO · TELEVISION · ELECTRONIC
SERVICE

Compensation for Your Knowledge

TV AND FM with its varied installation and servicing problems, have once again demonstrated the value of *know-how* and particularly its use. How often a Service Man, who because of a lack of familiarity with a receiver, or the required test unit, or the necessary installation equipment, will begin to set up a stream of excuses and apologies for his failure to get that income and also the respect of his customers which he feels he so richly deserves.

At a recent service meeting, when a speaker, representing a service company, pointed out that his group were able to ask for and receive quite a sum for a certain type of installation which would guarantee interference-free reception in a certain type of area, a Service Man arose and, quite disturbed, claimed that a large company could demand a substantial fee for such services, but a small independent could not begin to make such claims, since the customer would not only feel he is being overcharged, but in doubt over the maintenance of a guarantee offer. And in addition, this Service Man also felt that the customer would go next door and get a better price. In reply, the company representative pointed out that if the Service Man knew his business, thoroughly understood the problems, and believed in himself and his knowledge, these fears could be dismissed. For, continued our speaker, whether you are an independent operator or associated with a service company, that *know-how* is still the answer to getting what you deserve.

Continuing, we were told that there is no need to worry about the fellow next door if you have the ability based on experience and study, since the fellow next door, armed with the same ability, will feel as you do and make the same charges or perhaps more, for he may feel his time is even more valuable to him. And then, we were told, if competition insists on price cutting, you can be sure that these competitors don't know the answers and you'll be called in to remedy the errors introduced by this price-cutting competitor.

An independent Service Man, who has been eminently successful as a

TV installer and Service Man supplemented our speaker's remarks, saying that many Service Men are quickly realizing that those *sure-we'll-do-it-for-less* fellows are no competition and actually, these operators are rapidly disappearing from the problem scene. We were then told about two other extremely important factors in servicing and installation which must not be overlooked in this return-for-your-effort picture, and these were appearance and conduct. Unfortunately, too many Service Men seem to forget that they are visiting homes and not factories, and have to dress and act accordingly. Whether the call involves outdoor or indoor work, it is essential that the Service Man should not present himself in factory or mechanic's garb. With this uninviting appearance he will be received accordingly, and receive, probably, a mechanic's fee. His dress can be simple but neat, we were told, similar to that worn by the telephone repair man. If heavy indoor or outdoor work is required, a lab jacket or overalls can be slipped on. In addition, conversation should be on a level which will gain the respect of the customer.

This Service Man then stated that the latter two points are too often assumed to be mere trivialities and completely discounted. The results of this indifference are well-known, he said, adding up to a lack of work, loss of income, the eventual loss of confidence and very lean of acceptance. We were then told that many service companies conduct weekly sessions in which these factors are stressed. Service Men who attend these meetings are told that conduct and apparel rules *must* be followed.

At many other service meetings, the subject of professional conduct and apparel has been a featured topic. During a talk at a recent meeting of the Federation of Radio Servicemen of Pennsylvania in Harrisburg, during which James M. Skinner, vice president in charge of service and parts at Philco, received an award for "outstanding contribution to progress of radio service in '48", Skinner strongly emphasized the importance of personal appearance, conduct and the application of *know-how* in the home.

Here is cash register advice, which

demands attention, and when followed will cause a merry jingle and a healthy black set of figures in the books.

Those TV Antennas

THE VARIETY OF UNUSUAL POSSIBILITIES which exist in the TV antenna installation business were effectively highlighted by Charley Golenpaul, jobber sales manager of Aerovox, during a recent service meeting talk.

"Television antenna work is quite a business," Golenpaul said, "since there is not only the sale of the antenna which is involved, but the labor.

"The variety of antenna installations ranging from the simplest single dipole to the elaborate stacked arrays and reflectors, and again from a direct mounting on the roof peak, to a lofty mast supported by a chimney mount, means that Service Men can meet just about every purse and purpose.

"Even after the installation has been made, service organizations are in for still more business. When additional TV stations come on the air in their territory, wide-awake Service Men go after their previous installations and suggest improvements to bring in the new programs, such as supplementary antennas, realignment of existing antennas, the use of boosters, etc. Amazing as it may seem, there seems to be no limit to what the TV enthusiast will spend to enjoy the best in television."

TV in '49

FROM BURTON BROWNE of Chicago has come an excellent slogan for '49 which, expressed in an effective symbol declares that "1949 is TV Year."

We agree with you Burt, for '49 is certainly a TV year.—L. W.



VIEWING AREAS OF TV

Lucid Analysis Reveals Why the Rectangular Viewing Area Shape Was Selected Initially for Picture Tubes, Advantages of Its Application and How It Compares With Other Types of Viewing Area Shapes In Use Today.

EARLY WORKERS in television spent considerable time studying the possible shapes and aspect ratios for the most desirable presentation of the picture. The examples set by many of the world's great paintings, by motion pictures and by the simple fact that most of man's activities occur in a horizontal area, all influenced the final choice of a rectangular picture having a width-to-height ratio (aspect ratio) greater than unity. Many ratios were suggested based on scientific, pseudo-scientific, and even practical reasons. Most of these lie between the limits of 1.2 and 1.8 and, *golden ratios* and *dynamic symmetry* notwithstanding, it is probable that the public would enjoy television equally well with most of the suggested aspect ratios. It was, however, necessary to standardize so that a given receiver would be able to reproduce pictures from all transmitters with equal efficiency. The aspect ratio finally chosen was 4:3 with the long side horizontal.

This standardization still left considerable leeway for the receiver manufacturer. To date, at least, most TV receivers have employed picture tubes having circular screens and there appears to be considerable difference of opinion as to the most satisfactory manner for presenting a rectangular picture on such a screen.

Typical Viewing Areas

Fig. 1 illustrates the viewing areas most commonly seen. Type *a* is usually employed on monitoring equipment in the studio where size is immaterial, but it is necessary to examine all parts of the picture. Types *b*, *c* and *d* are representative of viewing areas on commercial receivers. In this drawing the white area is that actually devoted to the picture. The black area

by
ROBERT P. WAKEMAN

Research Division

Allen B. DuMont Laboratories

is that portion of the tube not used and the shaded area is that portion of the picture which is transmitted but not seen at the receiver because the beam is off the screen when it is being reproduced. The sketches *a'*, *b'*, *c'* and *d'* show the effect on the picture in each of the four cases.

The Rectangular Picture

A study of Fig. 1 indicates that it is desirable to sacrifice part of the picture in the interest of enlarging the remainder and using a greater percentage of the tube area. The extent to which this procedure should be carried has rightly been left to the manufacturer by the standards committees. However, it is felt that the consequences of enlarging the picture on a given tube should be quantitatively appreciated by the industry and the public.

The condition shown in Fig. 1a occurs when the height of the picture is 0.6 that of the *useable* diameter of the picture tube. Fig. 1d shows the condition when the picture height is equal to the usable tube diameter. Within these limits the actual area occupied by the picture is given by the expressions:

$$A = \frac{D^2}{4} \left\{ \begin{array}{l} \pi - 2(\cos^{-1} a) \\ + \cos^{-1} 4/3a \\ - a\sqrt{1-a^2} \\ - 4/9a \\ \sqrt{9-16a^2} \end{array} \right\} \text{ for } 0.6 \leq a \leq 0.75$$

$$A = \frac{D^2}{4} \left\{ \begin{array}{l} \pi - 2(\cos^{-1} a) \\ - a\sqrt{1-a^2} \end{array} \right\} \text{ for } 0.75 \leq a \leq 1.00$$

$$\text{where: } a = \frac{h}{D}$$

h = Picture height

D = Useable diameter of tube

The percentage of the transmitted picture, which is actually seen, is:

$$\% \text{ pix} = \frac{A}{\frac{\pi}{4} D^2} \times 100$$

and the percentage of the useable area of the tube which is employed is:

$$\% \text{ tube} = \frac{A}{\frac{\pi}{4} D^2} \times 100$$

Fig. 1 indicates that as *a* ($\frac{\text{Height of Picture}}{\text{Useable diameter of tube}}$) is increased, the percentage of the picture actually seen is decreased, whereas the percentage of the useable tube area is increased.

Viewing Area Conditions

Fig. 2 illustrates the relation between these three quantities with *a* taken as the independent variable. Thus, when *a* = 0.6, the entire picture is viewed, but only 61% of the tube is used and when *a* = 1.0, the entire tube is used but we see only 59% of the picture. Since the percentage of picture seen decreases very slowly at first, while the percentage of tube used increases quite rapidly, it would appear to be good economics to make *a* somewhat greater than 0.6. It should be noted that the small percentage of the transmitted intelligence which is lost by this procedure is of relatively little importance, since the center of interest in a picture is usual-

Receivers

ly concentrated near the center of the screen and we are merely clipping the corners. If overdone, however, it may be very annoying, especially when trying to read titles.

Compromise Conditions

The third curve on Fig. 2 is the product of the two percentages, and the maximum may be a possible criterion for a good compromise. This maximum indicates that we should use about 83% of the tube and see about 92% of the picture. This corresponds to an a of 0.73. In b' and c' of Fig. 1 can be seen the effect of having a equal to 0.70 and 0.75, respectively. It might be noted here that the use of a mask having rounded corners with radii equal to one-fourth the picture height (RMA standard) will not eclipse any more of the picture in these three cases. This is not true, of course, in the case of Fig. 1a'.

The Square Picture

One other possible compromise should be mentioned at this point. At the receiver, the vertical sweep amplitude may be made equal to that of the horizontal sweep. This converts the 4:3 aspect ratio to a square picture which may be made to employ the entire area of the picture tube and reproduce 78% of the transmitted picture. Obviously, in addition to losing a sizeable portion of the transmitted information, this procedure results in nullifying the standard 4:3 aspect ratio as set forth by the

Table 1

Nominal diameter ..	7	10	12	15	20
Useable diameter ..	6¼	9¼	11	14	18¾
Pix area when 100% of pix is viewed ..	19	41	58	94	168
Pix area when 95% of pix is viewed ..	24	53	75	121	218
Pix area when 90% of pix is viewed ..	26	56	80	129	232

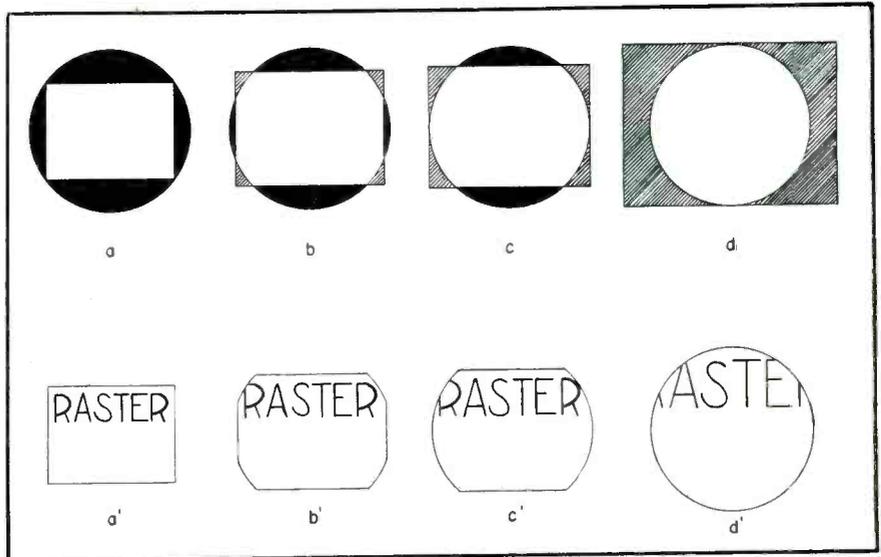


Fig. 1. Viewing areas most commonly seen on picture tubes. The illustration in a is that of the viewing screen on monitor equipment, while in b , c , and d appear the viewing areas on typical commercial TV receivers. In a' , b' , c' and d' appear the effects on the picture in each of the four types of areas illustrated in a , b , c and d .

RMA and adopted by the FCC, as well as producing a vertical elongation of all objects in the scene.

able diameters were obtained from manufacturer's specifications and laboratory measurements.


Useable Diameter/Area

Throughout this discussion the terms *useable diameter* and *useable area* have been employed. Table 1 shows the *useable diameters* of five standard tubes together with the area in square inches which may be obtained when various percentages of the transmitted picture are actually viewed; the use-

Best Picture Areas

The majority of television receivers now on the market employ picture areas close to that indicated as optimum by the curves in Fig. 2. It is believed that a continuance of this policy will promote the greatest public acceptance of television.

Fig. 2. The relation between percentage of picture viewed, percentage of tube employed and the product of the two percentages is illustrated here.

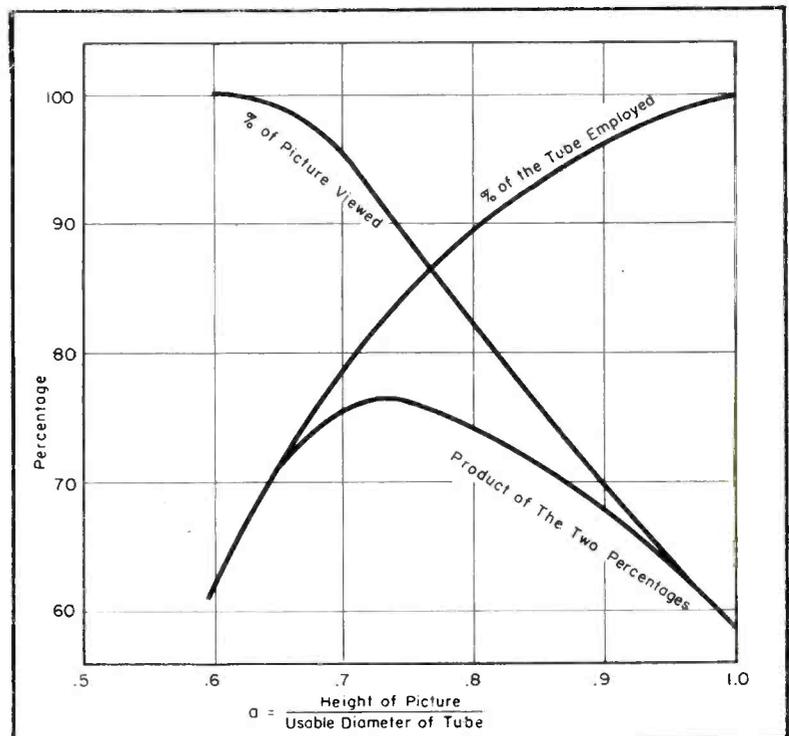

TV Antenna Installation Tricks of the Trade

IN MANY TV installations it is necessary to incorporate *antenna installation devices* to improve picture fidelity. These devices, which feature unique circuitry, perform specific functions in the antenna system.

One type device, an *attenuation pad* (Fig. 1), is used to reduce the signal level at the input of the TV receiver and thus:

(1) Prevent a strong TV signal from overloading the receiver input and producing crossmodulation. Crossmodulation, which manifests itself by one TV pattern appearing behind another, is most common between adjacent channels, i.e., 2 and 4, 4 and 5, 7 and 9, 8 and 10, 9 and 11, 10 and 12, and 11 and 13.

(2) Reduce the TV signal level input so that the contrast control on the TV receiver has a practical range of adjustment. Strong TV signals (more than 20 millivolts) may make the contrast control so sensitive, that in 10° to 45° of manual adjustment the picture can be overcontrasted (turned black) by the person operating the contrast control. In this instance, the attenuation of the pad has to be increased until a contrast control adjustment of 100° (approximately $\frac{1}{3}$ rotation of the control) can be realized before the picture is overcontrasted.

(3) Minimize effect of a reflection which cannot be eliminated by other means. Often when the TV signal is of reasonable strength, it is possible to attenuate the direct signal to a point where the reflected signal is below the noise level and the direct signal is still of usable strength.

The attenuation pad shown in Fig. 1 may introduce an impedance mis-

by **IRA KAMEN**

**Manager, Television Antenna Dept.
Commercial Radio Sound Corp.
New York City**

match of 1.25:1 as the resistor marked x is set at its minimum and maximum values. However, this mismatch is of no consequence in power loss and standing-wave-ratio. In fact, this pad provides a better match over the entire TV band (54-216mc) than the average TV receiver and will often compensate for the deficiencies of a TV receiver whose input impedance may vary considerably with frequency.

Three design factors were considered in the evolution of this circuit:

(1) Only one resistor needs adjustment for a large range of attenuation settings.

(2) A simple assembly can be made on a bakelite plate which enables quick change of the single resistor (x) which is varied in steps to obtain the desired attenuation level.

(3) Resistors of low value and which are subject to a minimum variation with frequency are employed. Higher resistor values have been known to vary in resistance as much as 25% when required to pass 200 mc currents.

This flexible pad, with its slight mismatch, can be used in even the most critical attenuation adjustments. To assemble theoretical attenuation pads which provide a perfect match at various attenuation steps is impractical as the calculated values are usually not as manufactured and would therefore have to be calibrated. The Service

Man would require an expensive set of low tolerance resistors, as in optimum design all values of the H pad would require change as the attenuation steps increase. The casualty value of resistors which are assembled and dissembled is also very high. In a series of carefully scrutinized antenna tests no practical differences were noted for all attenuation values between the perfectly matched attenuation pad and the pad shown in Fig. 1.

Fig. 2 shows another type of attenuation pad which can be used to adjust the TV signal level between a 72-ohm coaxial line and a 72-ohm receiver. By keeping the series resistor, x , to a minimum of 100 ohms it is *not possible* for the TV receiver load in parallel with the 85-ohm resistor to effect a serious mismatch on the coaxial cable termination.

This unit can also be neatly assembled on a bakelite plate for adjustment of TV signal levels.

Since the input impedance of the pads shown in Figs. 1 and 2 approximates the impedance of the transmission lines, at the termination end, all the signal from the antenna is absorbed and little energy is reflected back up the antenna lines.

In many installations in primary signal areas, only one or two stations of a total of four or six in the area may require attenuation. Therefore it may be necessary to provide a selector switch which will enable the user to insert attenuation on the channels where the signal strength is excessive and remove the attenuation on those channels where the TV signals are of a satisfactory level.

A two-gang, double-pole, three-position switch can be used to connect

How to Construct Attenuation Pads for 72 and 300-Ohm Lines, Connect Two TV Receivers to Single and Dual Arrays, Use Jumper Link Assemblies to Permit Use of Folded Dipoles or Broadband Straight Dipoles With 300 or 72-Ohm Lines, Apply Divider and Decoupling Networks Which Permit Use of Single Line With HF And LF Antennas, etc.

attenuation pads to the receiver; Fig. 3. Such an arrangement provides, in switch position 1, connection of the 300-ohm transmission line directly to the 300-ohm input of the receiver; in position 2, insertion of an attenuation pad (type shown in Fig. 1) between the 300-ohm transmission line and the receiver; and in position 3, the insertion of another pad with a different level of attenuation between the transmission line and the receiver.

Before assembling the transmission line and the pads on this type of switch a careful check should be made of the quality of the pictures without the switch in the circuit. The addition of the switch between the transmission line and the TV receiver should not affect the picture quality on any channel.

Fig. 4 shows another type of switch application using a coaxial switch for connecting the pads described in Fig. 2 between a coaxial line and a 72-ohm receiver. The circuit shown functions in the same 1, 2, 3 sequence described for the two-gang 300-ohm transmission line selector switch.

In some of the larger private dwellings it is common for two TV receivers to be permanently installed in the different sections of the home. It is really not necessary to install a separate antenna for the second receiver when the coaxial cable or transmission line from each TV receiver can be paralleled across the antenna terminals as shown in Fig. 5. The fact that both transmission lines are properly terminated by the receiver minimum loss input pad (Fig. 2) assures complete absorption of the incoming signals and therefore reflections cannot pass up one transmission line and down the other.

This parallel arrangement shown in Fig. 5 may not be satisfactory under the following conditions:

(1) In fringe areas where the slight loss due to paralleling lines or use of

Fig. 5. How to parallel coax lines to secure simultaneous operation of two receivers from a single antenna.

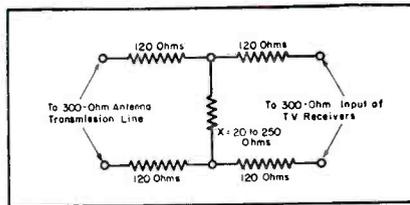
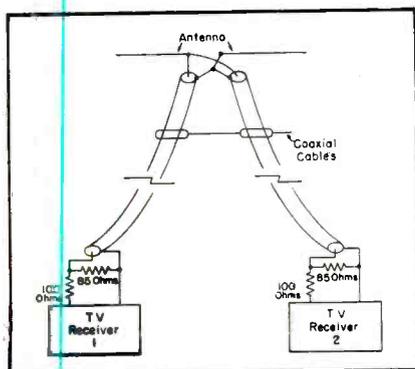


Fig. 1. Flexible pad for adjusting signal level between 300-ohm transmission line and 300-ohm receiver input.

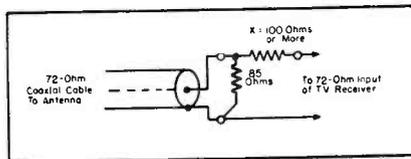


Fig. 2. Simple pad for adjustment of signal level between 72-ohm coaxial line and a receiver with a 72-ohm unbalanced input.

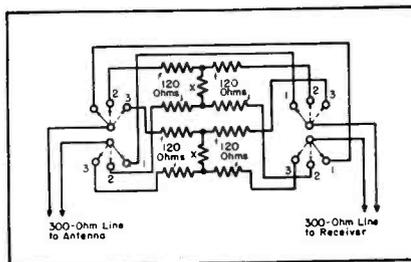


Fig. 3. A two-gang double-pole three-position selector-switch arrangement which permits insertion of pads in 300-ohm lines in those channels where the TV signals are too strong.


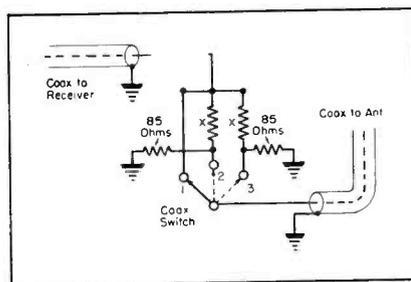


Fig. 4. Coaxial switch circuits which adds circuit attenuation on those TV channels where the TV signals are too strong.

Fig. 6. Paralleling coax line for simultaneous operation of two receivers from two antennas for all-channel interference-free reception.

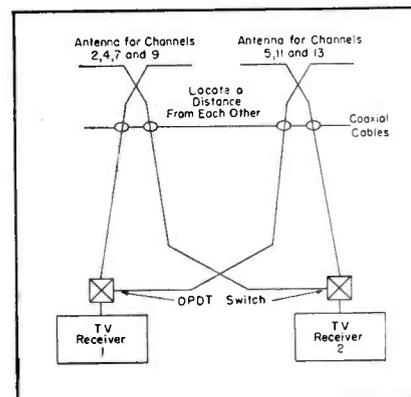

pads will drop the picture into the snow.


(2) When both receivers are going to be operated simultaneously on different TV channels, in which the re-radiation from one receiver tuned to channel 2, 3, 7, 8 or 9 may interfere with reception on another TV receiver tuned to channel 5, 6, 11, 12 or 13, respectively.¹ In a majority of instances a home owner would prefer to tolerate this interference on one channel during the periods in which both receivers are going to be operated simultaneously, rather than have two antenna arrays on his rooftop. It is also possible that separate antennas may not solve this interference problem for when two antennas are installed adjacent to each other on a chimney stack the cross channel interference radiation may be as prevalent as when the transmission lines are coupled directly together on a single antenna. Two antennas will only solve the interference problem when they can be located far enough from each other and adjusted so that energy radiated from the antenna connected to receiver 1 will not mar the pictures on receiver 2 to an objectionable degree.

In many complex areas, on multiple dwelling roofs, it is necessary to install two antennas to provide all channel reception. If the two antennas are judiciously located so that each antenna covers the specific channels, as indicated in Fig. 6, it is possible to parallel two receivers on the two arrays (to be located as far apart as possible) for interference-free reception. To keep both transmission lines terminated properly as the antenna selector switches are thrown from one

(Continued on page 29)

¹Ira Kamen, SERVICE; October, 1948. This article offers a complete analysis of this type of interference and shows a couple of patterns which indicate the manifestations of this interference.

Fig. 7. Circuit of double-pole double-throw switch arrangement, used in the Fig. 7 setup in the selection of either antenna, which maintains the load on the unused coax line.

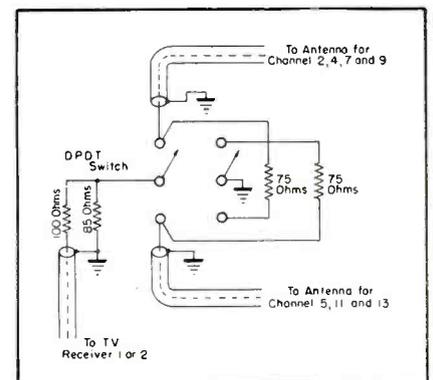

Horizontal AFC System in

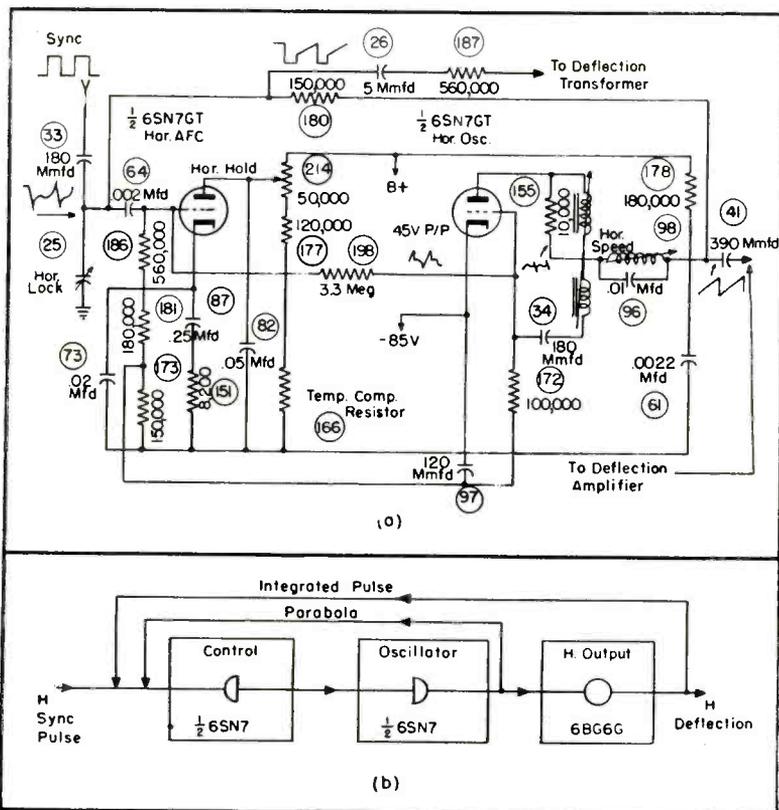


Fig. 1. Basic circuit of the Magnavox horizontal afc system.


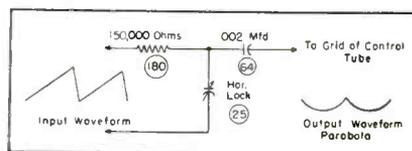


Fig. 2. The parabola circuit.

Fig. 3. Integrated deflection pulse circuit.

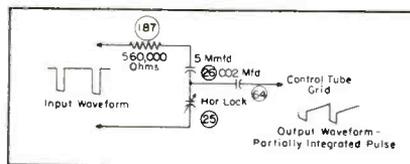

MOST TELEVISION RECEIVERS, presently manufactured, employ some means of frequency stabilization in the horizontal deflection oscillator, as a means of improving immunity to received noise (interference) impulses which tend to momentarily disrupt horizontal synchronization.

In the Magnavox receiver the stabilization method (Fig. 1) employs a control tube, $\frac{1}{2}$ 6SN7, which serves to control the frequency of the oscillator; a horizontal oscillator of the blocking type, $\frac{1}{2}$ 6SN7; and a 6BG6G horizontal deflection amplifier, not specifically pertinent to the present discussion, except that its output pulse is fed back to the control tube.

Basic Considerations

Fundamental (non-synchronized) frequency of a blocking oscillator may be controlled over a limited range, by varying its *dc* grid bias. Such a variable is applied to the oscillator tube, as frequency control, the control potential being derived from the control circuit, which is in part a function of frequency difference between the incoming sync pulses and the oscillator.

The width of the sync pulses changes with this frequency difference, as they appear at the control grid of

the control tube. Under such a change in pulse duration, the average plate current is also changed. Plate current passing through the cathode resistor provides a *dc* potential which is an automatic variable under frequency-shift of the oscillator, and which serves to re-establish correct frequency.

The Control Tube Circuit

Applied to the control tube grid is a complex waveform consisting of a parabola, a partially integrated pulse from the horizontal deflection yoke, and the sync pulse from the sync amplifiers. These are derived in the following manner:

(a) **Parabola**—Across a .0022 mfd capacitor (61) appears a sawtooth of potential, produced by pulse-output of the blocking oscillator across the capacitor. This is taken off by a 150,000-ohm resistor (180) to appear across the variable horizontal lock (25). These two components form an integrating circuit, making a parabola from the sawtooth.

(b) **Integrated Deflection Pulse**—At the output of the horizontal deflection transformer appears a pulse of negative polarity, which is the normal deflection pulse applied to the deflection

yoke. This is applied to the same control grid of the control tube, through resistor 187 (560,000 ohms) and a 5-mmfd capacitor (26) which form an integrating network. Such a series *rc* network is recognized as a so-called *peaking* circuit employed in some deflection systems to form a combined sawtooth-plus-pulse waveform from a simple pulse. It partially integrates the deflection pulse.

(c) **Sync Pulse**—Also applied to the control tube grid is the positive sync pulse.

(d) The Combined Waveform

These three components are applied to the grid, across the horizontal lock capacitor, a variable. They add to form the composite (combined) waveform; Fig. 4. This is a simple addition, a function of their respective instantaneous amplitudes and their phase relationships. Phase between the parabola and the integrated deflection pulse is always a constant, since they both are derived directly from the horizontal oscillator. Between these and the sync pulse, however, the phase varies as there is tendency for frequency difference between the oscillator and the incoming sync pulses. Therefore, the composite waveform

Magnavox TV Receivers

Basic Considerations ... Control Tube Circuits Used ... Sync Pulse Action ... How the Horizontal Hold Control Works ... Cathode Circuit Design ... Oscillator Circuit Performance ... Coil Design ... Sawtooth Formation.

changes as such frequency-shift occurs, as illustrated in Fig. 4.

This complex waveform appears across the *horizontal lock* capacitor, and the potential developed is a variable; given increase in capacity, potential is reduced and decrease of capacity leads to increased control grid potential.

Effect of the Signal

The control tube operates at low plate potential (between 100 and 130 volts), its *dc* grid bias being around minus 10 volts. Initial bias is supplied by the negative oscillator grid, through a 3.3-megohm resistor. With such low plate potential, plate current cutoff is reached by a modestly negative grid, and the applied *ac* grid signal produced plate-current flow only over its most-positive portion, thereby selecting the sync pulse which is now a variable in width; Fig. 5.

Furthermore, if plate current flows over only a portion of the cycle, its average value is a function of the relative time duration; the average value over the complete cycle is less when the pulse is of short duration than

by **J. F. BIGELOW**

Director of Service Training
The Magnavox Company

when it is long. The illustration shown is exaggerated, but illustrates the principle. Then, as pulse width varies with frequency-drift of the horizontal oscillator, a change in potential appearing across the cathode resistor results. Through a voltage-divider network consisting of resistors 181 (180,000 ohms) and 173 (100,000 ohms), this change is applied to the grid circuit of the oscillator by connection of the oscillator's grid resistor to the network.

Horizontal Hold Control

The *horizontal hold* control varies the plate-cathode potential between 100 and 130 volts. Thus, it changes the tube's plate current-grid voltage characteristics so that, with given grid bias, slightly more or less of the peak signal input amplitude appears in the plate circuit. Thus, the average plate current undergoes change, which is

reflected into the oscillator grid circuit; this control over narrow limits, oscillator frequency.

As correction to thermal drift in the overall circuit, plate voltage at this tube section is also changed by a resistor, 166 (30,000 to 38,000 ohms) having a high negative temperature coefficient. This resistor is physically located about one-half inch above a power resistor so that as the instrument warms, thermal drift of the oscillator is compensated. In practice, thermal drift is evidenced by change in horizontal positioning of the picture, necessitating re-adjustment of the *hold* control; if serious, it may be impossible to re-establish the picture by means of this control.

Cathode Circuit

To obtain an average from the pulses of plate current, it is necessary to use a rather large capacity, serving as a filter across the cathode resistor. More positive sync of the oscillator will be had, however, if there is a

(Continued on page 31)

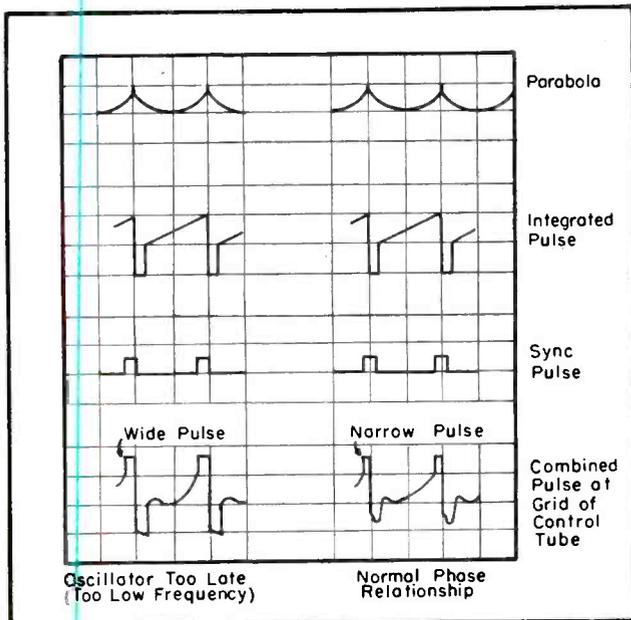


Fig. 4. Composite wave form which results when the three components (parabola, partially integrated pulse, and sync pulse) are applied to the grid across the variable horizontal lock capacitor.


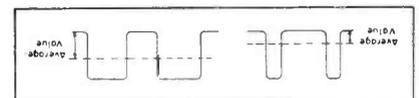


Fig. 5. Effect of the signal; low plate potential prompts a plate current cutoff, caused by a modestly negative grid. The applied *ac* grid signal produces plate current flow only over its most positive portion, thereby selecting sync pulse which is now variable in width.

Fig. 6. Pulse component, integrated to be nearly a sawtooth.

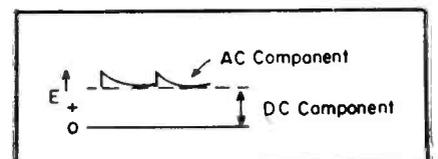

DEMONSTRATION ACROSS GENERAL ELECTRIC



In city after city dealers and servicemen have witnessed amazing demonstrations proving the outstanding quality and superiority of G-E speakers. Many distributors have purchased these demonstration units to show dealers just what we mean when we say—General Electric Speakers are *quality* speakers.

If you have not seen these demonstrations—if you have not seen General Electric speakers operate under difficult conditions, be sure to contact your local distributor. There is a marvelous exhibition of speaker performance waiting for you.

ASK FOR THESE EYE-OPENING, EAR-CONVINCING PROOFS:

- A G-E speaker playing under water.
- A standard replacement 4" speaker taking the output of a 25-watt amplifier.
- Comparison of the frequency response of various sized speakers.
- Comparison of the sensitivity according to magnet weight.
- Hear large speaker performance in small speakers.
- See a man standing on a speaker without damaging the all-weld frame.
- Also insist upon hearing the Variable Reluctance Cartridge playing a cracked record without reproducing the click, or a worn record without excessive needle scratch.
- Ask for the high fidelity performance demonstration of the Variable Reluctance Cartridge.

For complete information on General Electric speakers, write:
General Electric Company, Electronics Park, Syracuse, New York.

You can put your confidence in—

GENERAL  **ELECTRIC**

THE NATION PROVED SPEAKER QUALITY!


THERE IS EVERY GOOD REASON TO STOCK G-E SPEAKERS

Every G-E speaker is performance-engineered at Electronics Park.


Every G-E speaker is equipped with the Aluminum Foil Base Voice Coil.

Every G-E speaker can handle plenty of power.

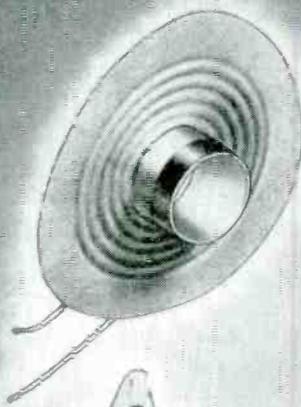Every G-E speaker is designed to have the proper frequency response required for the job.



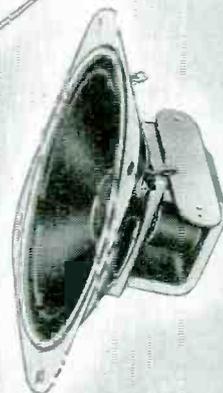The inside story of G-E speaker superiority—the Aluminum Foil Base Voice Coil.



4" and 5½". For small set replacements, drive-in theaters, car radios, etc.



6" and 8". For larger set replacements, public address systems, car radios.



10" and 12". For public address systems, console radio replacement.

AM/FM Tuner and AF Amplifier

THE FRONT END of an AM/FM tuner (Espey 513) diagrammed on the cover this month features an *rf* tuning unit designed around miniature tubes, miniature *rf* chokes, and special ceramic capacitors. The AM and FM tuning circuits are completely independent of each other since separate tubes and separate tuning gang sections are employed. For instance, the variable capacitor consists of a multiple six-gang unit with three sets of AM and three sets of FM rotor and stator plates.

For AM, a low-impedance type loop antenna is used. It was selected since its placement in the cabinet is not critical.

A 6BA6 is used in a tuned *rf* amplifier. This tube feeds a 6BE6 converter through tuned interstage *rf* transformers for increased gain and selectivity. Iron-core miniature 455-kc *if* transformers are used, a 6SG7 serving as an *if* amplifier. The detector is a 6J5 connected as a diode. The detected audio is fed through a printed circuit diode filter network into the audio section of the bandswitch.

The FM antenna input is designed for 300-ohm transmission line. A

[See Front Cover]

folded dipole antenna, suitable for attaching to the rear of the cabinet is supplied. This antenna may be replaced with a standard 300-ohm FM dipole.

A 6BA6 serves as a tuned *rf* amplifier stage. A 6BE6 is the mixer tube, and the grid circuit of this tube is tuned. A signal from a separate 6C4 local oscillator is injected into grid 1 of the 6BE6 *mixer* through a small ceramic capacitor. The local oscillator is drift compensated by means of ceramic temperature compensating capacitors.

The 6SG7 *if* tube is also used as the FM *if* amplifier with a separate miniature 10.7-mc iron-core transformer feeding a 6SH7 ratio detector driver tube. The ratio detector transformer is a slug tuned unit wound on special ceramic forms. A 6AL5 double diode is used as the detector. Disc type ceramic capacitors are used for bypassing the FM *if* circuits.

The FM audio line has a standard de-emphasis network to equalize the

audio frequency response. Both the AM and FM have individual *avc* systems, which operate a 6U5 tuning indicator tube on both bands.

A 6SQ7 is used as the first audio amplifier; this is the only audio tube on the 513 chassis. The bass and treble controls are in the grid and plate circuits of this tube. The bass control circuit is a high pass filter with variable cut-off frequency, while the treble control is a variable high-frequency audio attenuator network.

A phono input socket is wired in for use with a record player.

Voltages for powering a phono pickup preamp are present at a *Utility Socket* on the top of the chassis.

A power supply for this model uses two 5Y3GT rectifiers.

Audio Section

The audio section has a 6J5 feeding another 6J5 used as a self-balancing phase inverter.

Four 6V6GTs are used in a push-pull parallel output circuit to drive a multi-tap output transformer. Inverse feedback voltage is taken from the secondary of this transformer and applied to the cathode circuit of a 6J5.

Output impedances of 4, 8, 15, 250 and 500 ohms are available at the output transformer secondary.



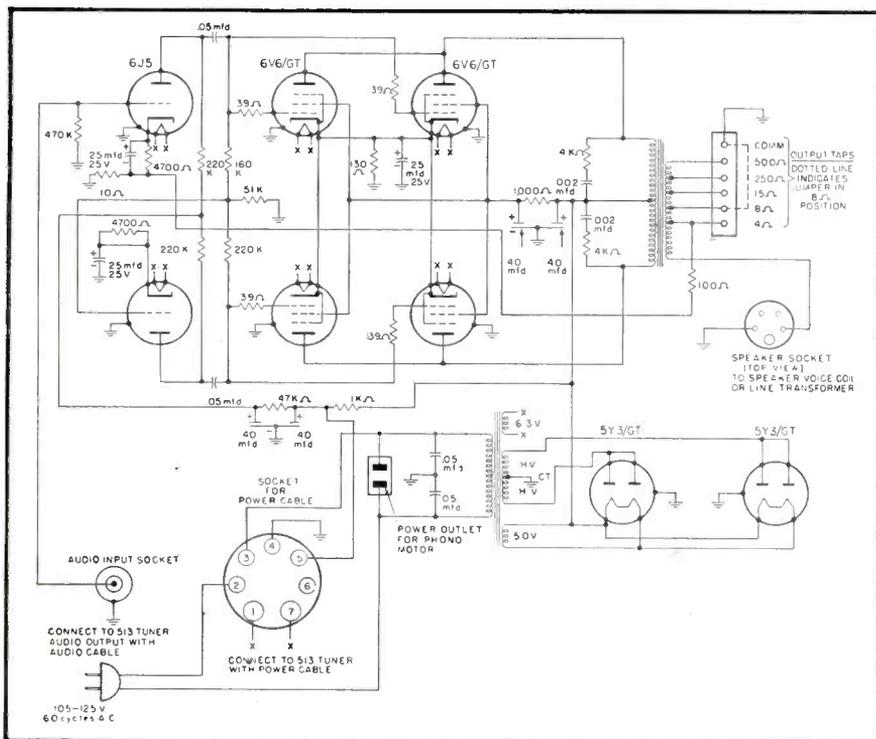


Fig. 1. Circuit of the audio amplifier designed for the tuner.

Fig. 2. View of the amplifier and tuner.

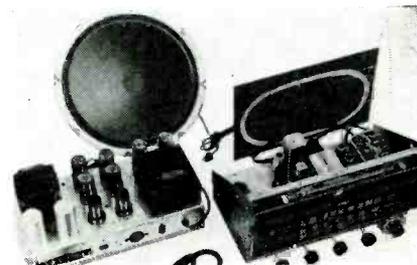

82 TYPES

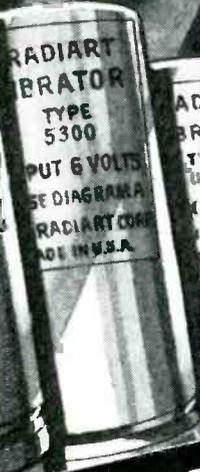

ONLY ONE OF THE REASONS THAT MAKE
RADIART
THE GREATEST
REPLACEMENT
VIBRATOR LINE

• Another reason for Radiart's nation-wide preference is the complete selection of vibrator types manufactured! There is a CORRECT Radiart replacement vibrator for most every need . . . to ORIGINAL SPECIFICATIONS! This completely eliminates guess work . . . and assures peak performance because no "next best" type is installed! Good jobbers everywhere carry almost all types in stock . . . or can get quickly any number you want! In addition . . . each of these 82 types is precision engineered . . . and manufactured under the most careful inspection that assures peak performance from every Radiart vibrator . . . always!


IT'S RIGHT WHEN IT'S RADIART



THE RADIART CORPORATION

CLEVELAND 2, OHIO

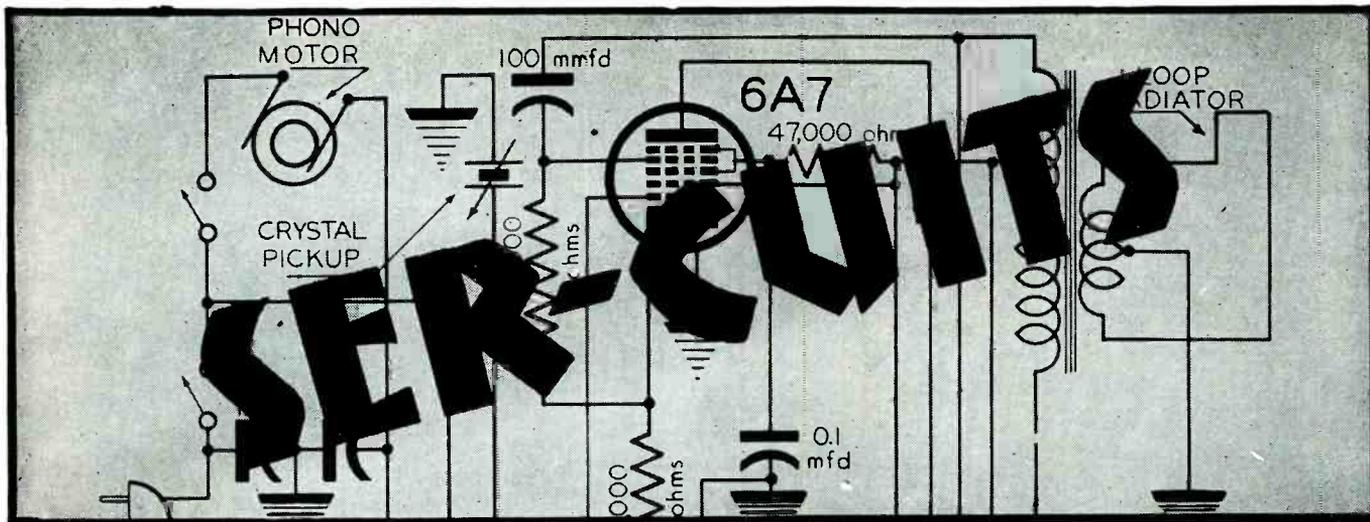MANUFACTURERS OF THE FAMOUS RED SEAL VIBRATORS



Circuit Features of the Sparton Indirect Viewing TV Models

INDIRECT viewing with a special type of mirror in the lid of the cabinet is being featured in several types of TV receivers. In one model, the Sparton series 4939TV/4940TV/4941TV, twenty-eight tubes are used, and the picture tube is a 10" 10BP4.

The mirror used is of special design. Unlike other mirrors, this type is silvered on the top side instead of the back and does not have the glass for protection, but a plastic safety shield is provided.

In this model, Fig. 1, the *rf* tuner is a separate sub-assembly of the receiver. It contains the *rf* amplifier, converter, local oscillator, fine tuning control, station selector switch, input transformers, *rf* amplifier coils, oscillator coils and the individual tuning adjustments for the transformers and coils. It amplifies the selected *rf* signal and provides at the converter plate a picture *if* carrier of 26.25 mc and a sound *if* carrier of 21.75 mc.

In the *rf* amplifier, T_1 to T_6 together with incremental inductances L_2 , L_3 and L_4 are input transformers tuned to channels 2 to 13. The secondary of each of these transformers forms a parallel resonant circuit with the input capacity of the 6BH6 *rf* amplifier. The inductances of the secondaries of transformers T_1 through T_6 , tuned to channels 2 to 6 are adjusted by means of individual slugs placed within these coils. Incremental inductances L_2 , L_3 and L_4 are added in series with the slug-tuned secondaries of transformers T_6 , T_7 and T_8 , tuned to channels 8, 10 and 12 to form tuned circuits for channels 7, 9 and 11. Thus the secondary

of T_6 tuned to channel 8 with an added series inductance L_2 forms the tuned circuit for channel 7 and so on with channels 9-10 and 11-12. The secondary of transformer T_8 is slug tuned for channel 13. On channels 7 through 13 15-mmfd capacitors (C_1 , C_2 , C_3 , C_4) are placed in series with the secondaries of transformers T_6 through T_8 . In this way, the effective shunt capacity with which these coils resonate is decreased and the use of larger inductance values is permitted.

Converter

Each of the inductances, L_5 through L_{10} , forms a tuned pi-network with the input capacity of the 6AG5 converter and the output capacity of the 6BH6. These resonant circuits are tuned to channels 2 to 13 and couple *rf* energy to the grid of the 6AG5. Since the oscillator output and the *rf* signal are both fed to the grid of the 6AG5 the heterodyne products (*if* frequencies) appear at the converter plate.

The inductance of coils L_5 through L_6 , tuned to channels 2 through 6, is adjustable by means of individual slugs placed within these coils. Incremental inductances are added to the slug tuned coils for channels 8, 10 and 12 to form tuned circuits for channels 7, 9 and 11. L_{10} is slug tuned to channel 13.

In the plate of the converter there are three tuned circuits:

- (1) L_{34} with C_{12} forms a parallel resonant circuit tuned to 27.75 mc which acts as a series trap presenting a high impedance to

the *if* frequency of the adjacent channel sound carrier.

- (2) L_{25} with C_{18} forms a parallel resonant circuit tuned to 94 mc, which acts as a series trap preventing the oscillator injection voltage from developing bias on the grid of the 6BH6 (V_1), the first video *if* stage.
- (3) L_{26} in conjunction with the output capacity of the 6AG5 converter and the input capacity of V_1 forms a parallel resonant circuit tuned to 22.4 mc, which is the first stage of a stagger tuned video *if* system.

RF Oscillator


The local oscillator is a conventional Colpitts system. The inductances, L_{17} through L_{28} , together with the incremental inductances L_{23} , L_{25} and L_{27} , form the oscillator tank circuits and are tuned to channels 2 to 13. Fine tuning is accomplished by means of a .5 to 1.5-mmfd variable (C_{121}), which has a capacity range sufficient to produce a ± 300 kc variation in oscillator output frequency on channel 2 and a variation of approximately ± 2 mc on channel 13. The output of the oscillator is coupled to the grid of the converter by means of a 1.5-mmfd capacitor, C_{10} . The oscillator operates at a frequency above that of the received signal.

Sound IF and Ratio Detector

The sound and picture *if* signals are common to the first and second pix *if*

MINIATURE TUBE MERCHANDISER TM-30

It's NEW!
IT'S CLEAR PLASTIC

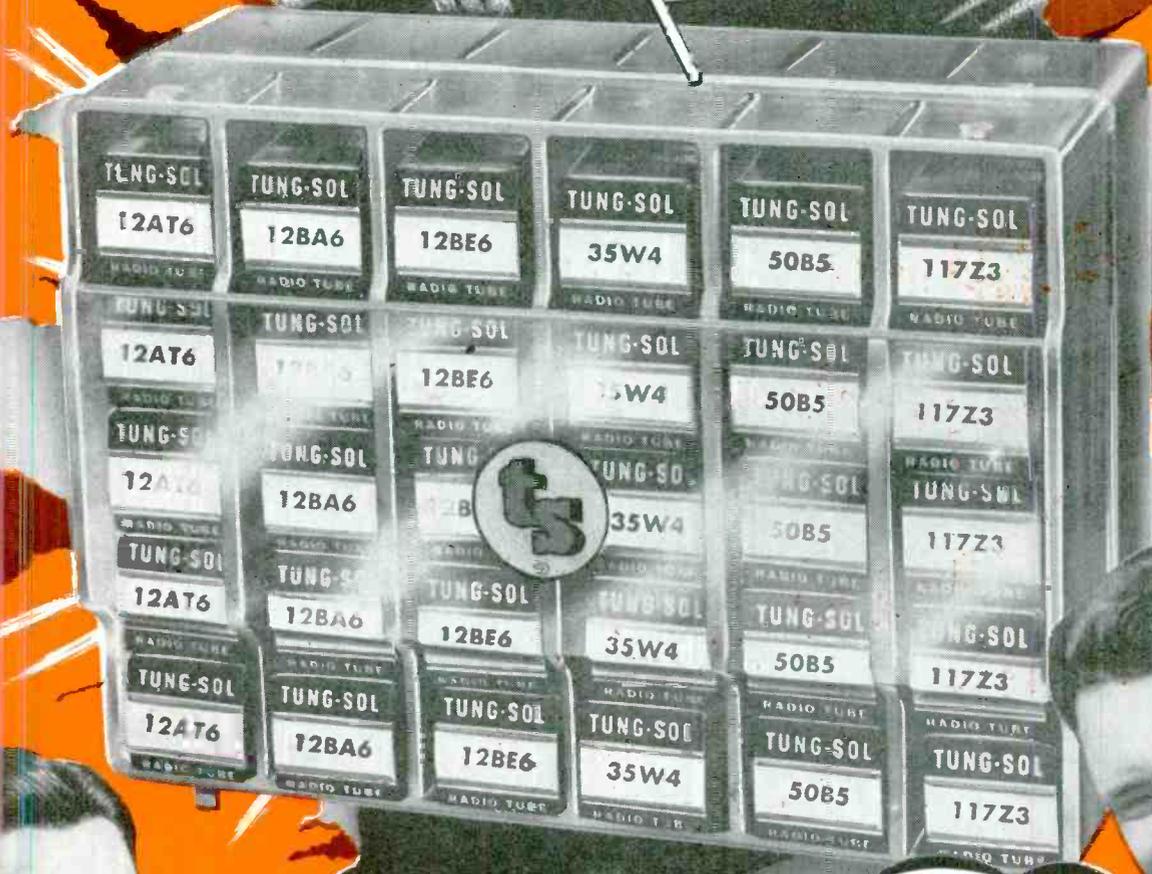

**SOLVES STACKING
PROBLEM!
KEEPS SHELVES
TIDY!**

**INVENTORY AT
A GLANCE!
INSTANT SELECTION!
REDUCES SPACE
REQUIREMENTS!**

TUNG-SOL LAMP WORKS INC., NEWARK 4, NEW JERSEY
Manufacturers of Electron Tubes and Radio Dial Lamps
SALES OFFICES: ATLANTA • CHICAGO • DALLAS • DENVER • DETROIT • LOS ANGELES • NEWARK


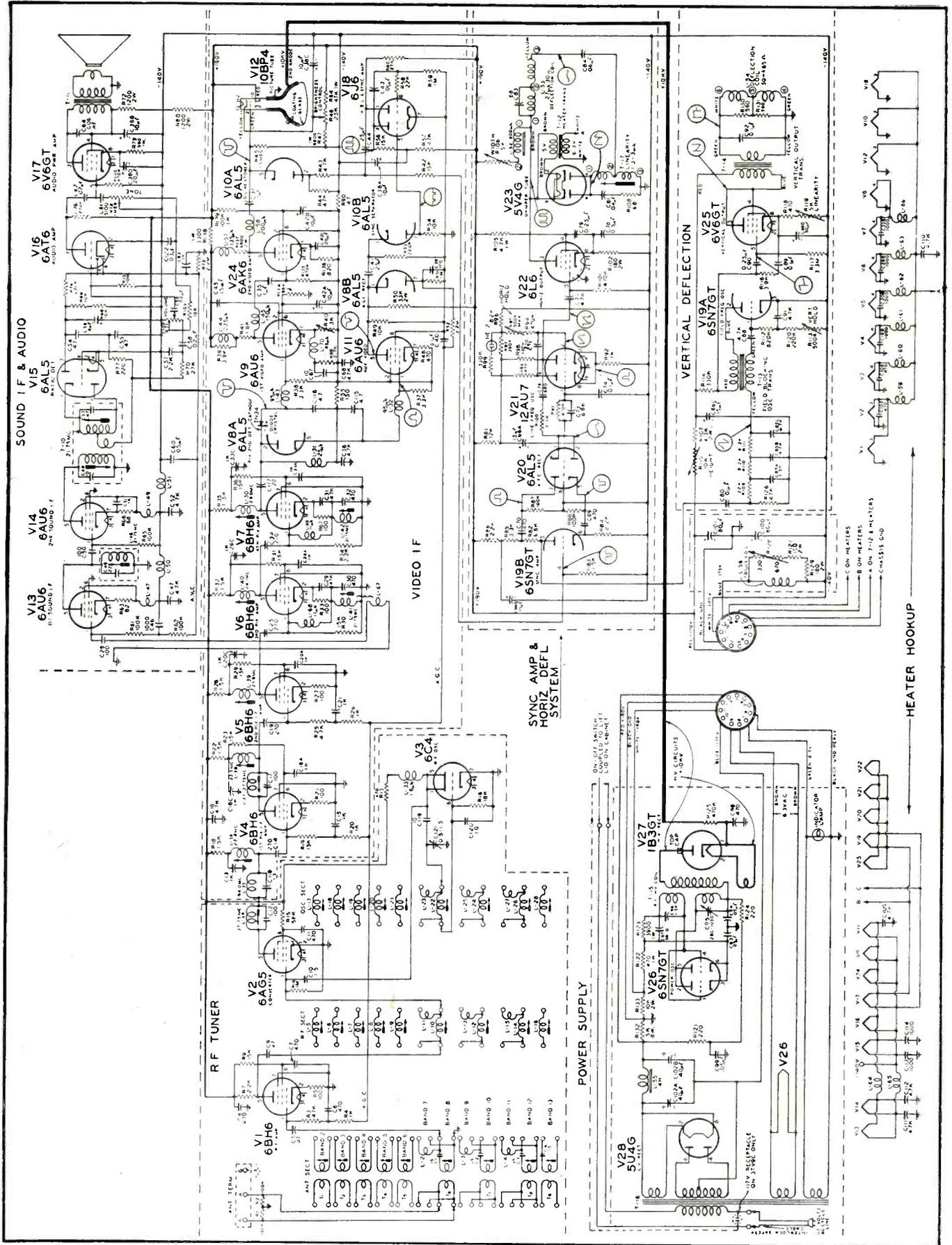


Fig. 1. Schematic of the Sparton TV chassis.

stages using 6BH6s. At the output of the third 6BH6 pix stage, sound energy is taken off by means of L_{m1} , the

sound take off loop, which is inductively coupled to L_{m2} , a 21.75-mc cath-

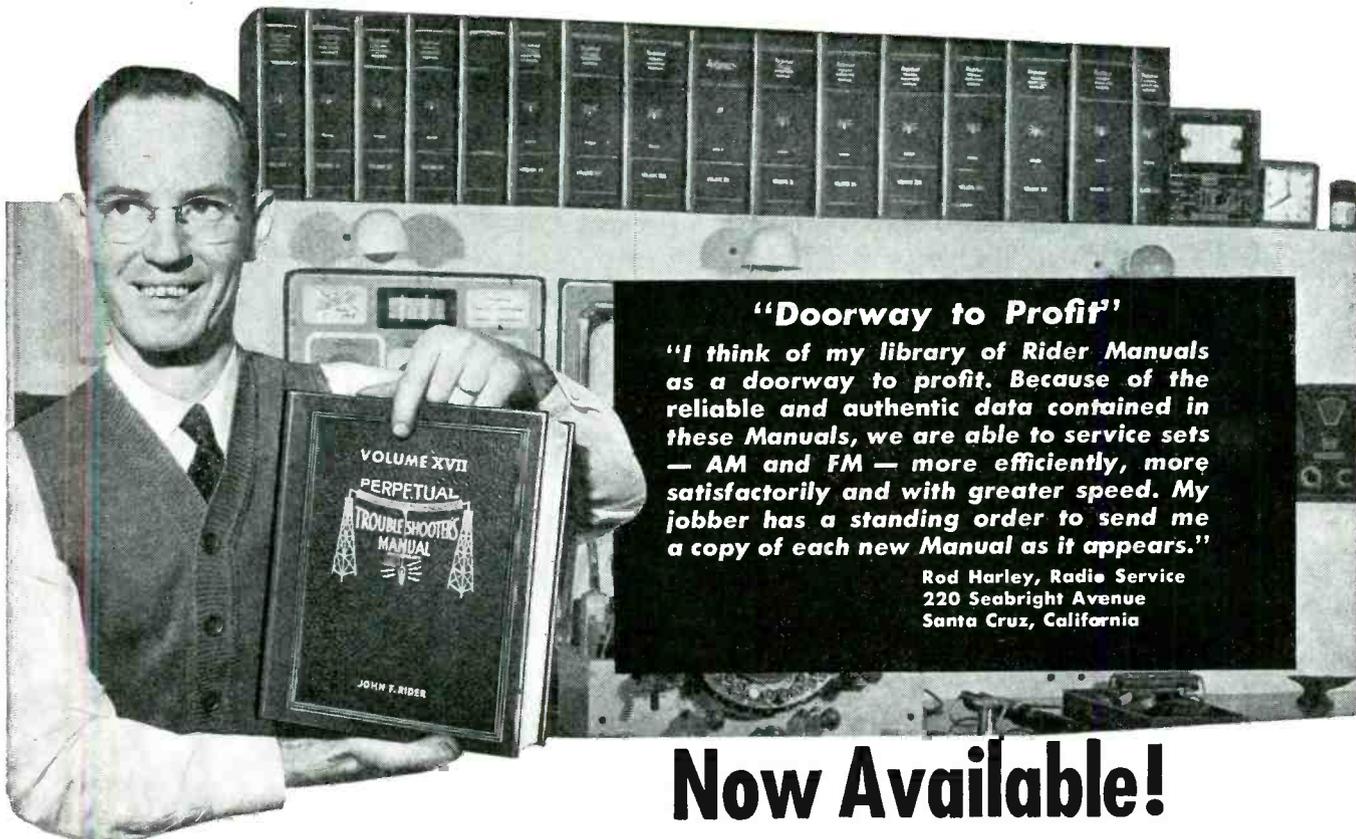ode trap. This energy is fed to the first sound *if* stage. Two stages of
(Continued on page 40)



"Doorway to Profit"

"I think of my library of Rider Manuals as a doorway to profit. Because of the reliable and authentic data contained in these Manuals, we are able to service sets — AM and FM — more efficiently, more satisfactorily and with greater speed. My jobber has a standing order to send me a copy of each new Manual as it appears."

Rod Harley, Radio Service
220 Seabright Avenue
Santa Cruz, California

Now Available!

Volume XVIII in the profit-building library of RIDER MANUALS *The World's Greatest Compilation of Radio Servicing Data — Including AM, FM and TELEVISION — and allied equipment*

2036 Pages PLUS Separate "How It Works" Book and Cumulative Volumes XVI, XVII and XVIII Index. Both Books . . . **\$19⁸⁰** complete

This is the biggest RIDER MANUAL of them all. 2036 FACTORY-AUTHORIZED, fact-crammed pages . . . comprising the greatest number of models and chassis of AM and FM receivers and record changers of more than 100 manufacturers . . . up to date to January, 1949. Here are the exclusive RIDER "Clari-Skematrix" to help you do a better, faster, more profitable job. Here is the famous "HOW IT WORKS" Book which fully explains electrical and mechanical innovations in VOLUME XVIII. Here is the authentic, reliable data direct from the manufacturers themselves . . . data which make RIDER MANUALS the easiest to understand, the simplest to use, and the best to help you make more money.

To Be Shipped To Your Jobber Late February!

VOLUME 2

RIDER TELEVISION MANUAL

Plus Separate "How It Works" Book

Volume I was an instantaneous "hit" . . . volume II is sure to be even more in demand—BECAUSE no serviceman in a TV area can afford to be without RIDER TV MANUALS. They contain the OFFICIAL Manufacturer's authorized data from the set makers themselves, and include Double spread, Triple spread, and GIANT SCHEMATICS to put you on the right track toward solving any TV problem.

Equivalent of 2300 pages—"How It Works" Book; cumulative Vol. I and Vol. II, and Index. . . **\$18⁰⁰**

RIDER PA MANUAL

The first industry-wide Public Address Equipment Manual, incorporating the amplifier production of 147 manufacturers from 1938 to 1948. 2024 Pages PLUS "How It Works" book which explains theory of various PA circuits and method of rapidly locating faults.

\$18⁰⁰ including Index.

JOHN F. RIDER, PUBLISHER, Inc., 480 Canal Street, New York 13, N. Y.
Export Agent: Rocke International Corp., 13 E. 40th St., N.Y.C., Cable, ARLAB.

RIDER MANUALS

- Television Manual, Volume I (plus "How It Works" and Index) \$18.00
- Television Manual, Volume II (plus "How It Works" and Index) 18.00
- Volume XVIII 19.80
- Volume XVII 16.50
- Volume XVI 8.40
- Volume XV 19.80
- Volume XIV to VII (each volume) 16.50
- Volume VI 12.50
- Abridged Manuals I to V (one volume) 19.80
- Record Changers and Recorders 9.00
- Master Index, Covering Manuals, Vols. I to XV. 1.50

RIDER MANUALS mean SUCCESSFUL SERVICING

NOTE: The Mallory Radio Service Encyclopedia, 6th edition, makes reference to only one source of radio receiver schematics—Rider Manuals.
ANOTHER NOTE: The C-D Capacitor Manual for Radio Servicing, 1948 edition No. 4, makes reference to only one source of receiver schematics—Rider Manuals.



Fig. 1*

Custom-Built Cabinets

CUSTOM-BUILT CABINETRY is rapidly becoming a major factor in the TV shop, affording the Service Man an unusual opportunity to develop a new and extremely profitable department.


The cabinets, in the main, include basic designs which are adaptable to many types of rooms with a variety of interior decorations. To facilitate the sale of such cabinets, one manufacturer¹ has prepared a brochure which not only illustrates the types which are available, but the actual woods in which the cabinets can be supplied.

Cabinet Flexibility

The custom-built cabinet, which is particularly applicable to kit-made receivers, is quite flexible in its application since it can be made to accommodate all of the equipment or parts of the setup. In one case, as shown in Fig. 1, provisions were made for not only mounting the television and radio

¹Transvision, Inc.

Fig. 2*

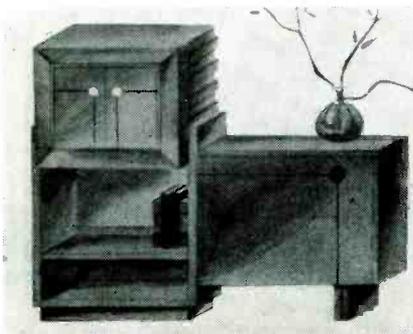

by **MARTIN W. ELLIOTT**

receivers, but phonograph albums and a bar, too. This design can readily be applied to accommodate books or a desk, as well as the radio and TV equipment, or the side sections can be omitted and a TV and radio housing used only for the television and radio receiver.

Combination Setup

In Fig. 2 appears another approach to the custom-built cabinet idea with provision in this case for a television and radio receiver in the left-hand column and phonograph in the right.

Provisions for Shelves

In Fig. 3 appears still another type of custom-made cabinet in which numerous shelves are a featured item. Often there is a need for extra shelf space for dishes, books, record albums or even a portable phono unit and the flexible shelf arrangement is an extremely handy and useful provision in such instances.

Speakers and Amplifiers

The custom-made cabinets have their advantages, too, in serving as housings


for separate speakers and amplifiers which is an extremely effective high-fidelity accessory in any installation.

Sectional Cabinets

Sectional type cabinets have been found very effective in custom-built installations, serving to set up a moderate priced package where cost is a factor. In many designs the sectional theme has been planned so that each unit has its own integral purpose and yet when matched with other sections provides an interesting ensemble of cabinetry.

With the advent of remote controlled TV, the increased use of separate speaker systems and the desire to employ cabinetry which harmonizes with the design of the room, the custom-built idea has become an item which merits the attention of every Service Man.

Fig. 3*

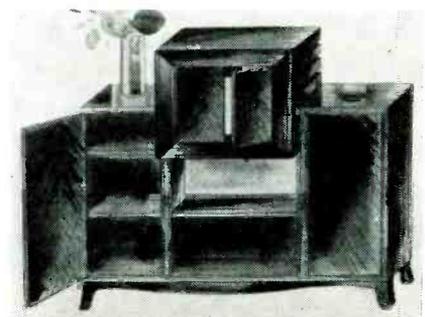

*Courtesy Transvision, Inc.

SERVES AND PLEASES MILLIONS!



GENERAL  **ELECTRIC**

176-GA7-8820

FIRST AND GREATEST NAME IN ELECTRONICS

ASSOCIATIONS



John F. Rider congratulating Max Leibowitz upon his reelection as president of the Associated Radio-Television Servicemen of New York. Looking on (left to right) are Harry Weigand, who was re-elected vice president, Noel Payne who was named corresponding secretary and Arthur Silverberg who was rechosen for the post of recording secretary.

PRSMA

AT A RECENT MEETING of the Philadelphia Radio Servicemen's Association, Dave Krantz was elected president. Dick Devaney was elected vice president; Stanley Myers, treasurer; John Zagury, corresponding secretary, and Frank Gerhard, Sr., recording secretary.

An extensive membership drive has been planned by PRSMA under the direction of Paul Lau. As a part of this program and also to continue to familiarize the public with its activities, PRSMA has renewed its mutual

cooperative broadcasting contract with KYW.

An educational, advertising and entertainment program is also being planned. To assist in this expanded program, nine new members have been added to the advisory board.

FRSAP

AT AN ELECTION of officers for the Federation of Radio Servicemen's Associations of Pennsylvania, at the William Penn Hotel in Harrisburg, Pa., Dave Krantz was elected chairman. Robert Reidy of the Lehigh Valley

Officers of PRSMA and of the Federation of Radio Servicemen's Associations of Pennsylvania who attended a recent TV lecture by Al Saunders in Philadelphia, left to right: Dave Krantz, Dick Devaney, Saunders, Larry Oebbecke and Stanley W. Myers.

(Photo courtesy Paul H. Wendel of Howard Sams)



TEN YEARS AGO

From the Association News Page of SERVICE, February, 1939

THE FT. WAYNE, Indiana, and St. Joseph, Missouri, associations joined RSA. . . . Officers of the Ft. Wayne Chapter were Henry A. Schryver, president, and E. Moening, secretary and treasurer. The St. Joseph Chapter was under the direction of Cleo Blodgett. E. R. Sullwold was secretary and Russell Goerhe, treasurer. . . . At a meeting of 200 members of the Toledo, Ohio, group, it was decided to become affiliated with RSA. . . . The service group in Pekin, Illinois, began taking the necessary steps to join the RSA. . . . The inter-chapter renewal dues contest, with a copy of Rider's Volume IX as the prize, was drawing to a close. . . . A 100% renewal in membership was achieved by 12 chapters: Houston, Texas; Alton, Illinois; Binghamton, New York; Danville, Ill.; Duluth, Minn.; Freeport, Ill.; Holyoke, Mass.; Jamestown, N. Y.; Nashville, Tenn.; Oklahoma City, Okla.; Peoria, Ill., and Steubenville, Ohio.

Radio Servicemen's Association was elected vice chairman, and John Rader of the Reading Radio Servicemen's Association was named secretary and treasurer.


During the election meeting, officers of the Mid-State Radio Servicemen's Association of Harrisburg presented a complete analysis of the results of their recent preventive maintenance program which, it was learned, was extremely successful.

AR-TSNY

THE RESULTS OF THE ANNUAL ELECTION of the Associated Radio-Television (Continued on page 28)



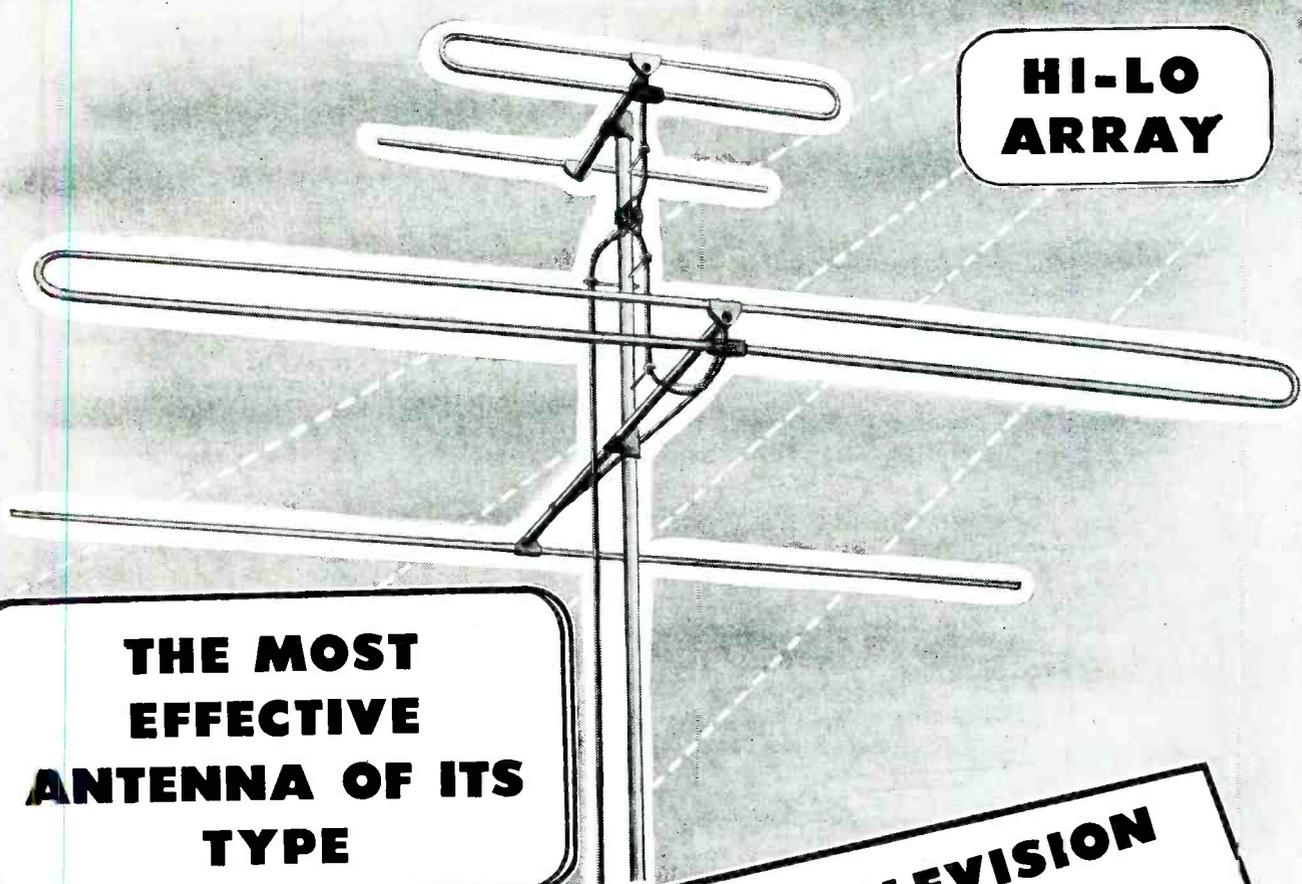Dr. Victor Wouk, chief engineer of Beta Electronics Company, who spoke on TV power supplies at a recent meeting of AR-TSNY.



**HI-LO
ARRAY**

**THE MOST
EFFECTIVE
ANTENNA OF ITS
TYPE**

**"Simpli-Flex" TELEVISION
and
FM ANTENNAS**
THE QUALITY ANTENNA LINE

Radiart's superiority asserts itself once again! This Television and FM Antenna line has been enthusiastically received everywhere! One of the reasons for this remarkable preference is the 85 ATV HI-LO array. By means of its exclusive matching network . . . it assures minimum interaction between arrays thus offering results equal to two separate independent and costly installations! It features independent orientation with minimum interference from other arrays! RADIART SIMPLI-FLEX ANTENNAS GET THE PICTURE ALWAYS . . . even where others fail . . . for trouble free . . . speedy and less costly installations . . . order RADIART!



No "assembly puzzles" with Radiart's "SIMPLI-FLEX" design. No degree in engineering or truck-load of tools needed — absolutely no loose hardware. One minute assembly, one man installation!



High strength, well engineered design of more than ample safety factor, with simple, sturdy all aluminum castings, elements, and heat-treated support masts for PERMANENT installations.



"WEATHER-SHIELD" polystyrene terminal block encloses lead-in connections and protects from all weather conditions! Keeps electrical performance at maximum.



IT'S RIGHT WHEN IT'S RADIART

THE RADIART CORPORATION

CLEVELAND 2, OHIO

MANUFACTURERS OF THE FAMOUS RED SEAL VIBRATORS

TV Tricks of Trade

(Continued from page 13)

position to the other, it is necessary to employ 72-ohm dummy loads, as shown in Fig. 8, to absorb the antenna signals on the transmission lines which are not terminated with the TV receiver inputs.

One of the simplest devices for making an antenna flexible in application for the installer is the antenna assembly shown in Fig. 8. By means of the adjustment of jumper links, a folded dipole array (a) can be converted to a broadband straight dipole (b) as required for connection to 300-ohm transmission line or 72-ohm coaxial cable.


The dipole shown in (b) has a broadband characteristic since each straight dipole is a half section of the folded dipole (a) and therefore the straight dipole effectively has a larger cross-sectional area than a simple straight tubular rod. It is a theoretical fact that the resistance of an antenna element increases more rapidly than its inductance as its cross-sectional area increases; and since antenna $Q = \text{inductance/resistance}$, it is apparent that the antenna in (b) has a relatively low Q characteristic and thus a broadband response. This broadband response with one pair of antenna elements is usually effective for channels 2 to 6 or 7 to 13 but not for both TV bands.

In Figs. 9 (a)² and (b)³ are diagrammed two antenna networks which can be used with composite high and low-frequency arrays to avoid the use of a separate transmission line for each array. These networks minimize interaction between the high and low-frequency arrays. The high and low-frequency arrays are usually independently rotated for best TV signals regardless of direction as the networks are so designed that they do not affect the pick-up pattern of either array. These networks function with antennas of either the folded or straight dipole type.

The divider network shown in (a) traps any high-frequency signals, in-

(Continued on page 30)


Fig. 8. A dual-purpose antenna array which permits the installation of 300 or 72-ohm transmission lines by the adjustment of jumper links. The arrangement shown in (a) is for a 300-ohm impedance at the terminals C and D. In (b) we have a jumper link setup for a 72-ohm impedance at terminals C and D.
(Courtesy Vertrud)

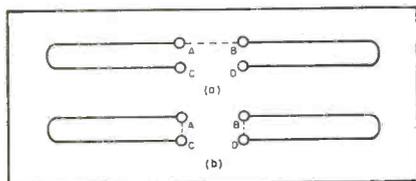

when **ALIGNMENT is BUILT-IN**
trouble is built out!

Philmore
TELEVISION
Pre-Aligned **KITS**

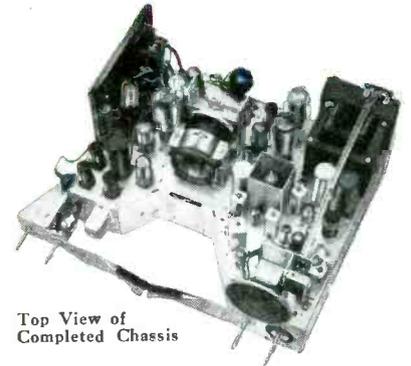Designed for 16" Kinescope
as well as 10"-12"-15" tubes



Top View of Completed Chassis

PRE-ALIGNED FOR ASSURED RESULTS

Experience with TV receivers built from kits proves there is only one way to insure good pictures. That is by supplying a kit with the 12-channel tuner, picture I.F. and sound I.F. stages pre-assembled and pre-aligned on instruments essential for these precision operations.

The circuit used is the famous 630 TS which gives long range performance and the highest quality picture of any television set yet produced.

EASY TO ASSEMBLE

Among the exclusive Philmore features are the big, step-by-step lithographed schematic blueprints, and easy-to-follow, detailed assembly directions and photographs which come with every Philmore TV receiver kit. Every part is numbered and clearly identified. Anyone handy with simple tools can readily assemble the pre-aligned Philmore Television Kit.

Another major advantage derived in purchasing a Philmore Television Kit is that a 10", 12", 15" or 16" Kinescope Tube can be used without any change in the circuit. The 15" or 16" Kinescope Tube can be used by merely changing the bracket.

PROFITS BEGIN WITH THE SALE OF THE KIT

For twenty-seven years the name of Philmore has been symbolic of the best in radio. Philmore pre-aligned TV kits can be sold with complete confidence that, once assembled according to the detailed instructions furnished with it, the finished set will produce high-fidelity pictures and sound with no further adjustments necessary.

Remember too, that with the sale of Philmore pre-aligned TV receiver kits, a market is created for picture tubes up to 16", antennas, cabinets and lead-in wire, etc.

Jobber Inquiries Invited. For descriptive literature, write to

Philmore MANUFACTURING COMPANY, INC.
DEPT. S-2, 113 UNIVERSITY PLACE, NEW YORK 3, N. Y.

A Partial List of Distributors

EAST

Fort Orange Radio Dist.
642 Broadway
Albany, New York

Wholesale Radio Parts Co., Inc.
311 West Baltimore St.
Baltimore, Md.

Radio Electric Service Co.
5 No. Howard St.
Baltimore 1, Md.

Radio Shack Corp.
167 Washington St.
Boston 8, Mass.

The Louis M. Herman Company
885 Boylston St.
Boston 16, Mass.

The Eastern Company
630 Memorial Drive
Cambridge, Mass.

D. & H. Distributing Co.
311 S. Cameron St.
Harrisburg, Pa.

Hatry & Young
203 Ann St.
Hartford 3, Conn.

Davis Electronics Corp.
204 Main St.
Hempstead, L. I., New York

Chanrose Distributing Co.
170-16 Jamaica Ave.
Jamaica, L. I., New York

Krich-Radisco, Inc.
422 Elizabeth Ave.
Newark 8, N. J.

Metropolitan Radio Electronics Corp.
17 Union Square
New York 3, N. Y.

Bruno-New York, Inc.
460 W. 34th St.
New York, N. Y.

Harrison Radio Corp.
10 West Broadway
New York 7, N. Y.

Newark Electric Co., Inc.
242 West 55th St.
New York 19, N. Y.

Radio Electric Service Co.
N. W. Corner 7th & Arch Sts.
Philadelphia, Pa.

Raymond Rosen & Company
32nd and Walnut Sts.
Philadelphia, Pa.

SOUTH

The Yancey Company
340 West Peachtree St., N.W.
Atlanta 3, Ga.

Sterling Radio Supply
1602 McKinney
Houston, Texas

P. I. Burks Company
911 W. Broadway
Louisville, Kentucky

MID-WEST

Olson Radio Warehouse
73 E. Mill St.
Akron, Ohio

Wedemeyer Electronic Supply Co.
213 North 4th Ave.
Ann Arbor, Michigan

Newark Electric
323 West Madison St.
Chicago 6, Ill.

Lukko Sales Corp.
5024 Irving Park Rd.
Chicago, Ill.

Radio & Electronic Parts Co.
519 Huron Road
Cleveland 15, Ohio

Winteradio, Inc.
1468 West 25th St.
Cleveland, Ohio

Radio Electronic Supply Company
1112 W. Warren Ave.
Detroit, Mich.

Ferguson Radio Supplies
622 W. Baltimore Ave.
Detroit 2, Michigan

Cosmopolitan Radio Company
524 Washington St.
Gary, Indiana

Van Sickle Radio Company
34 West Ohio St.
Indianapolis 6, Ind.

Ame Radio Supply Corp.
510 W. State St.
Milwaukee 3, Wis.

Van Sickle Radio Company
1113 Pine St.
St. Louis 1, Mo.

WEST

Universal Radio Supply Co.
1404 Venice Blvd.
Los Angeles, Calif.

Shelley Radio Company
2008 Westward Blvd.
Los Angeles, Calif.


Leo J. Meyberg Co.
2027 So. Figueroa St.
Los Angeles, Calif.

Radio Products Sales Company
1214 First Ave.
Seattle, Wash.

AMPHENOL

ORIENT

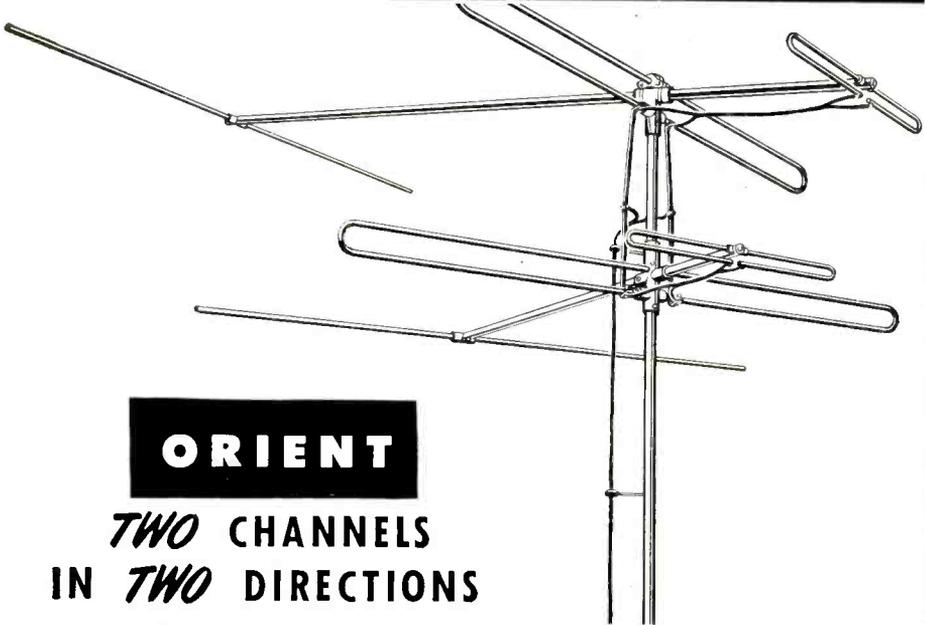adapt STACKING to the conditions of the area...



ORIENT


TWO CHANNELS IN TWO DIRECTIONS

The usual objective of Antenna Stacking is for the purpose of acquiring db gain—with Amphenol's 114-302 Stacked Array there is a plus value, another adaptation, one which is very important in congested TV areas. Both the upper and lower bays provide all-channel reception and each bay may be individually oriented. Overlapping signals or station interference on same channels within receiving areas may now be separated—if and when the bays are stacked for orientation. In the smaller illustration lower right, observe the same array stacked for db gain on all channels. Amphenol Antennas offer many plus values in being perfected electrically and mechanically in every detail.

To keep posted on all that's new in TV and FM Antennas, be sure your name is on the Amphenol list to receive the monthly issue of ENGINEERING NEWS. Current issue contains timely information on these subjects—yours for the asking.

AMPHENOL

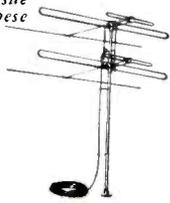
AMERICAN PHENOLIC CORPORATION
1830 SO. 54TH AVENUE • CHICAGO 50, ILLINOIS



channels for which it is not adjusted. The high-frequency channel signals picked up by the low-frequency elements may have out-of-phase reflections with respect to the TV signals on the high-frequency elements, and unless the networks filter out the high-frequency signals on the low frequency rods, the high-frequency channel pictures may be marred unnecessarily by reflections.⁴

⁴Ira Kamen, SERVICE; August, 1948. This article describes the tests which must be made to determine the feasibility of combining high- and low-frequency arrays without special networks.

Fig. 9. Divider (a) and decoupling network (b) arrangements used to isolate a high and low-frequency antenna array for connection to a common transmission line. In the arrangement shown in (b) the 37" of 300-ohm line must be run on an angle so that the vertical distance between the high and low-frequency array is not more than 33". Open stub in (b) should be 12½" long.

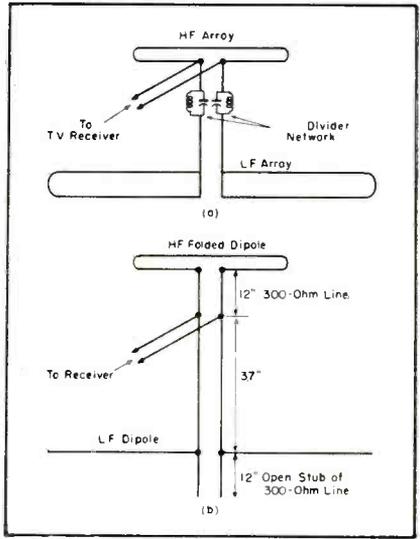

DAVE TURNER LENDS A HAND



David Turner, chairman of the board of the Turner Company, Cedar Rapids, Iowa, at one of the "Keep the Pot Boiling" Salvation Army stands erected during the recent drive to aid the needy, prior to the holiday season. Mr. Turner was one of the originators of the plan.

TV Tricks of The Trade

(Continued from page 29)

tercepted by the low-frequency array, and prevents such signals from entering the common transmission line circuit to the receiver.

The decoupling network shown in (b) has a 12½" stub filter on the low-frequency array which acts to attenuate the high-frequency signals induced into the low-frequency array. The splice connection 12" down from the high-frequency array provides for the most efficient transfer of TV signals,

intercepted by both arrays, to the common receiver transmission line.

The networks shown in Figs. 9 (a) and (b) filter the low-frequency array of high-channel signals because the low-frequency quarter-wave elements are efficient at their three-quarter wavelength which is in the upper TV band (174-216 mc) and therefore will pick up considerable signal on those

²AAK.
³RCA.

Horizontal AFC

(Continued from page 15)

small component of the sync pulse applied to the oscillator grid, superimposed upon the dc control potential.

There are two considerations *working against* each other: A large capacitor averages the pulses and removes from the developed potential incoming signal components, which are in addition to the true sync pulse; it is possible that a little more than strictly the peaks of control tube signal, the variable-width sync pulses will be passed. These are undesirables in the cathode circuit. It also removes the sync-pulse component, desired for more positive sync.

As a solution, the cathode circuit consists of two parts, one having long time constant, and one of short time constant. Resistors 181 (180,000 ohms) and 173 (100,000 ohms) are large with respect to 151 (8,200 ohms). The latter, then, may be disregarded as far as low-frequency components of signal (plate current) are concerned, and the .25 mfd capacitor plus 280,000 ohms of resistance affords a long time constant.

Fast response is achieved by a combination of .02 mfd and 8,200 ohms (the .25-mfd unit is electrically a short-circuit to high-frequency signals). An integrating network (same as the *peaking circuits*) resistor 151 and capacitor 81 provides the desired pulse component, integrated to be nearly a sawtooth; Fig. 6.

The Oscillator Circuit

Basic Operation: Using the second section of the 6SN7 tube, the oscillator of the blocking type operates as follows: Oscillation is caused by coupling between plate and grid circuits, through an iron-slug transformer. When oscillation occurs, a magnetic flux is built up in the transformer and the grid is driven toward the positive. Plate current is increasing. As the grid goes positive, grid-current flows and power is taken from the circuit, being absorbed in the grid-coupling capacitor. The rate of rise of magnetic flux falls off.

With decreasing flux, the polarity of potential across the coil reverses, becoming less positive at the grid. Plate current is thus falling to add further to the rate of magnetic field decay; the action is cumulative and the grid is driven highly negative, to complete plate current cutoff. Then, the tube is idle until the high negative potential placed upon the grid coupling

(Continued on page 32)

MAKE MORE

PROFIT

Replace Phono Pickup Cartridges

WITH

**TORQUE
E-V
DRIVE**

- Makes Cartridges Easier to Sell and Install
- Saves Ordering-Time and Servicing-Time
- Improves Record Playing
- Turns Prospects into Satisfied Customers
- Builds Cartridge and Needle Business



Greatest Merchandising Opportunity in Cartridge History!

YOU CAN MAKE the replacement of phono pickup cartridges a *profitable side* of your servicing. No longer is it necessary to order one cartridge for each repair job. With the 3 basic models in the **TORQUE DRIVE KIT**, you can immediately replace any one of over 150 types in common use. Furthermore, the revolutionary **TORQUE DRIVE Crystal Cartridge** modernizes your customer's player, greatly improves reproduction, prolongs record life. Has replaceable Osmium-Tip or Sapphire-Tip needle.

HANDY SALES AND SERVICE KIT

Enables you to make most replacements immediately. Has 6 quick-selling cartridges, 4 extra needles, mounting plates, and replacement guide. Available in Kit "A" (Osmium) and Kit "B" (Sapphire).

Write for Bulletins 141-142, and name of nearest E-V Distributor

ELECTRO-VOICE, INC., BUCHANAN, MICHIGAN

Export: 13 East 40th St., New York 16, U. S. A., Cables: Arlab

E-V Pat. Pend. Licensed under Brush Patents


New Model L14 Microgroove Crystal Cartridge and new Models 20 and 22 Magnetic Cartridge for Regular and Microgroove also available.

IT PAYS TO REPLACE WITH

Electro-Voice

Television Is "Tops"

WITH TENNA·ROTOR

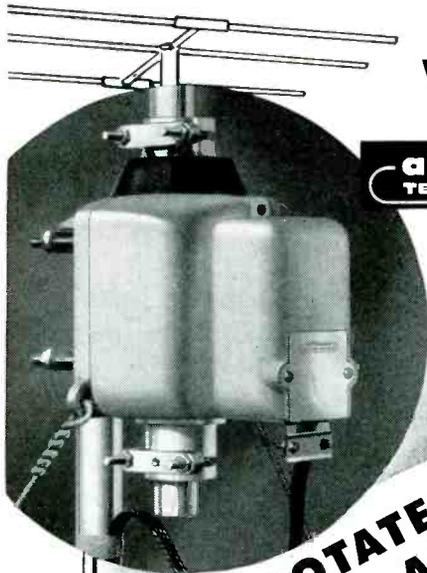

alliance
TENNA·ROTOR

GETS **STRONGER SIGNALS**

ROTATES TV AND FM ANTENNA

LIST PRICE **\$39.95**



CONTROL BOX
Size of box 5" x 5"

Operates in any weather.
Fits most types of antenna.

Model
ATR
Size of
rotor
unit
7 3/4"
x 5 1/4" x
8"

Shipping
Weight
12 Lbs.

Takes
Max.
Antenna
O.D.
of 1 3/8"

Alliance Tenna-Rotor is an electric antenna rotator. It assures correct antenna "beaming"—gives positive control of antenna rotation to select the exact position for "peaked" reception! Tenna-Rotor is quick and easy to install—the electric powered rotor unit resists corrosion—is enclosed in a split zinc, die-cast housing, and is operated from a plastic control box which plugs into any 110 volt, 60-cycle house circuit. A 3-position switch rotates antenna clockwise or counter clockwise and stops it at the right point. Four-conductor inter-connecting cable from rotor to control box is made available at 5 1/2¢ per foot.

TV and FM service dealers, and users, will find that the Alliance Tenna-Rotor simplifies and improves new and existing installations!

Write for catalog sheet and illustrated folder.

alliance motors

ALLIANCE MANUFACTURING COMPANY • ALLIANCE, OHIO
Export Department; 401 Broadway, New York, N. Y., U. S. A.

Horizontal AFC

(Continued from page 31)

capacitor leaks off through the grid resistor. When the tube again becomes conductive, plate current rises and the action is repeated. There are, therefore, pulses of plate current, during the time when the grid is not highly negative. At the grid, we see a sawtooth of potential, superimposed upon which is a positive pulse; Fig. 7.

In this illustration, at (a), the high negative grid potential is leaking off the grid resistor; (b), the tube begins to conduct and the grid is driven posi-

tive; (c), the grid is driven sharply, highly negative.

Therefore, the time constant of the grid-coupling capacitor and grid resistor determines how long will be required for the charge to leak off, and the fundamental frequency of the oscillator. Changing either affords frequency-control. Thus, the 100,000-ohm grid resistor is a special unit having zero temperature coefficient, for stability over thermal change.

Synchronization

As the grid becomes less negative, we may inject a positive pulse which

causes the tube to become conductive slightly ahead of the time that it would otherwise conduct. The pulse would therefore trip the oscillator prematurely and so control frequency. This would be a sync pulse. On the other hand, we may vary, by means external to the oscillator, the dc grid bias which, together with the negative grid potential developed across the grid resistor, determines how far negative the grid will go. For example, assume that the grid resistor is connected to a positive potential with respect to the cathode, rather than directly to the cathode. The grid will not be driven as far negative with respect to its cathode and it will require less time for the tube to become conductive after the plate current cutoff. The frequency is therefore subject to any potential applied, externally, as bias. This, plus a sync-pulse component, is the principle of the afc circuit.

The Oscillator Coil

It is the purpose of the oscillator coil to afford regeneration. The circuit tends to oscillate at a frequency determined by the coil's resonant frequency, but is stopped by a high negative potential at the grid. There is, however, one-half circle of oscillation. It is necessary that the grid be driven negative very rapidly, for this half-cycle corresponds to the retrace time in scanning. Should the antiresonant frequency of the tuned circuit be low, the one-half cycle of oscillation would be long and beam-retrace in scanning would be excessively long. The circuit is therefore tuned to approximately 70 kc, so that one-half cycle corresponds to the retrace time¹ in


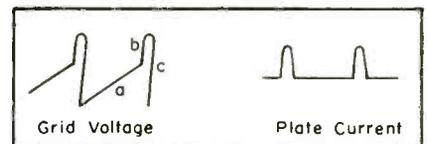


Fig. 7. Sawtooth of potential at grid superimposed upon which is a positive pulse: a, high negative grid potential is leaking off grid resistor; b, tube begins to conduct and grid is driven positive; c, grid is driven sharply, highly negative.

Fig. 8. Output wave form of series of damped oscillations which result when 10,000-ohm damping resistor is removed.

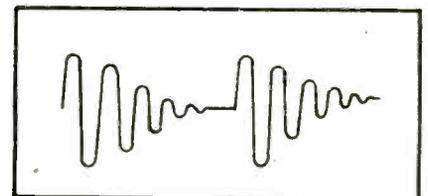

scanning. This is controlled by slug-adjustment.

There are in the plate circuit, pulses of current which tend to shock-excite the resonant circuit. A 10,000-ohm resistor across one section of the coil damps out such oscillation. If the resistor be removed, the output waveform is that of a series of damped oscillations and the scanning of the tube will follow a like pattern across the screen (the scanning spot will oscillate back and forth, instead of travelling with a linear motion); Fig. 8.

Manual Frequency Control

Between the coil and the output circuit is an antiresonant circuit. This, too, is shock-excited and oscillates at its resonant frequency. Since it is in series with the plate supply ($B+$), its oscillation waveform is superimposed upon the supply potential. By varying its resonant frequency, control of the blocking oscillator frequency operates in the following manner:

Suppose that the oscillator grid is negative, the negative charge is leaking off and the tube will soon become conductive. If, at that time, a higher positive potential is placed upon the plate, the tube will no longer be at a condition of current cutoff, and it will be tripped into oscillation. Approximately a sine wave of potential is superimposed upon the dc supply potential, the result of shocked-oscillation of the manual frequency-control antiresonant circuit. It does not *alone* trip the synchronized oscillator; it is not *the* element which precisely determines oscillation time, but it does influence the circuit to the extent that it prepares the plate circuit to be tripped by the sync-component applied to the grid. The nearly sine wave is rather broad and not suitable to be a fine, deciding element in frequency control. The manual frequency control elements form a circuit which is predominantly capacitive, of low Q and therefore quite stable.

Forming the Sawtooth

Thus far, we have assumed constant potential from one plate supply, and

(Continued on page 39)

²Time between horizontal scans is $1/15,750$ or about 63 microseconds. Retrace time is approximately 7% of this, or 4.4 microseconds. Since $f = 1/T$, $f = 1/4.4 \times 10^{-6} = .15 \times 10^6 = 150$ kc. Thus, one full cycle occurs in 4.4 microseconds at 150 kc. Since we wish to accomplish $1/2$ cycle in that time, frequency must be halved, resulting in 75 kc (approx.).



TURNER Model 33

meets every requirement

for a RUGGED ALL-PURPOSE MICROPHONE

Packed with power to spare — built to take rough handling and bad climate conditions — engineered for smooth response to both music and voice pickups, the Turner Model 33 is an all-around microphone for recording, P.A., call system, studio, and amateur work. A professional unit for professional results. Ask your distributor or write.

Free Turner Catalog
Write for your copy

THE TURNER COMPANY

930 17th Street, N.E.
Cedar Rapids, Iowa

Licensed under U.S. Patents of the American Telephone & Telegraph Company, and Western Electric Company, Incorporated.
Crystals licensed under patents of the Brush Development Company



TURNER Microphones

LOOK at these
Performance Features

33X Crystal

- Moisture-sealed crystal.
- 90° tilting head.
- Wind and blast-proofed.
- Barometric compensator.
- Chrome finished case.
- Level -52DB.
- Range 30-10,000 cycles.
- Removable cable set.

33D Dynamic

- Heavy duty dynamic cartridge.
- 90° tilting head.
- Wind and blast-proofed.
- Chrome finished case.
- Level -54DB.
- Range 40-10,000 cycles.
- Removable cable set.
- Choice of impedances.

QUESTION


Why do so many television sets use Sprague KOOLOHM Resistors for all 5- and 10-watt wire wound power resistor requirements?

ANSWER

Because Koolohms far surpass other wire wound resistor types in the essential characteristic of resistance stability. Also because, being doubly insulated, Koolohms can be mounted anywhere—even directly against a metal chassis. Koolohms are highly heat- and moisture-resistant. One type—the standard type handles any job. No need to worry about choosing special coatings. Moreover, Koolohms cost no more than ordinary resistors, and are actually cheaper in many cases.

SERVICE HINT

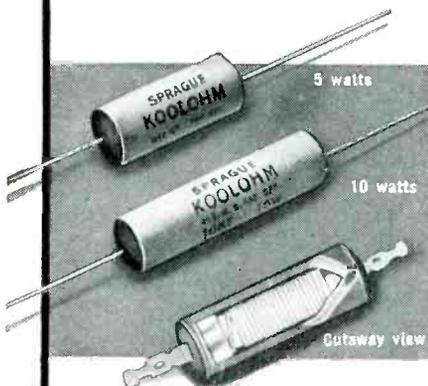Play safe by using Sprague Koolohms in all your work—not only in television, but wherever you want a really first class job. And remember: Koolohms can be used safely at their full wattage ratings, even in enclosed places. No need to buy a 10-watt resistor when the circuit only needs 5-watts. A 5-watt Koolohm dissipates a full 5 watts!



Wound with ceramic-insulated wire. More resistance in less space. Doubly protected, insulated and sealed by outer ceramic jacket. Highly resistant to moisture and heat.

SPRAGUE
KOOLOHM
(Reg. U. S. Pat. Off.)
WIRE WOUND RESISTORS

SPRAGUE PRODUCTS CO., North Adams, Mass.

(Jobbing distributing organization for products of Sprague Electric Co.)

Servicing Helps

by P. M. RANDOLPH

Selecting Coax Cables . . . Preamp Equalization

Service Notes on Philco, Crosley, Silvertone and G. E. Models.

IN AN ANTENNA installation coaxial cable acts as the transfer device between the antenna and the television receiver. In selecting the coaxial cable required for a job the TV installer must take into consideration three fundamental points:

- (1) The approximate amount of attenuation that can be tolerated at the highest frequency TV channel.
- (2) The potential difficulties of me-

chanically installing the coaxial cable selected.

- (3) The customer's acceptance of the coaxial cable (especially the larger cables) that must be run on or through the customer's premises.

Either 75- or 53-ohm coaxial cable may be installed for connection to 75-ohm TV receivers. A 170-ohm resistor across the 75-ohm input of a receiver will make a near perfect

Table A

Cable Type	Attenuation* in db Per 100'				Nominal Impedance	Outside Diameter	Application Data
	(Mc)	40	100	200			
RG5/U	1.6	2.65	3.85	9.6	52.5	.332	Flexible low loss cable used in master antenna systems. Also used in individual installations where low loss cable is required and RG8/U is not acceptable to the customer because of large outside diameter. ¹
RG8/U	1.2	2.1	3.3	8.5	52	.405	Tough low-loss cable used in master antenna systems. Used also in individual installations where there is no objection to large diameter cable. ¹
RG11/U	1.1	1.9	2.85	7.7	75	.405	Tough low-loss cable used in individual installations in fringe areas for direct connection to 75-ohm TV receivers.
RG17/U	.46	.85	1.3	4	52	.870	Lowest-loss cable used in fringe areas where several hundred feet of cable must be run between an antenna tower and a TV receiver. ¹
RG58/U	2.3	4.1	6.2	17	53.5	.195	High-loss coaxial cable used in primary signal areas where an extremely flexible coaxial cable is required. ¹
RG59/U	2.2	3.75	5.6	14.3	73	.242	High-loss coaxial cable used in primary signal areas for direct connection to a 75-ohm TV receiver.

¹Coaxial cable connects to 300-ohm TV receiver input through a trifilar matching transformer; RCA MI-6876-2. (See March, 1948, issue of SERVICE.)

*Attenuation data courtesy Amphenol.

match to the 73-ohm coaxial cable. The 53-ohm cable is preferred where a match must be made through a 50/300-ohm trifilar transformer. The 75-ohm cable may also be connected through the transformer with only minor losses.

To facilitate the selection of coaxial cables in accordance with above fundamentals a table of types of coax and related data has been prepared; table A.


Preamp Equalization*

IN THE DISCUSSION of preamp equalization last month, it was pointed out that if required, a low-frequency response can be maintained ± 2 db from 1,000 cycles to 50 cycles by changing the value of the 2,700-ohm resistor, R_{101} , feeding the second, 6SC7 to 12,000 ohms and the value of the .01-mfd capacitor, C_{103} , in series with this resistor to .03 mfd. This type of equalization provides a rise of 2 to 2.5 db at 300 cycles and a drop of 1 to 2 db at 50 cycles. Alternately, two compensation stages can be incorporated as shown at Fig. 1.

This effectively provides the full 6 db/octave and will produce an output curve which is flat within ± 1 db from 1,000 to 50 cycles. It is questionable whether or not the added parts required for Fig. 1 are justifiable since the improvement on the overall curve is only ± 1 db over the circuit shown as Fig. 2.

The insertion loss with either of the changes made will, of course, be increased, and additional gain is required after the preamplifier.

The high-frequency response of the cartridge when operating into the preamp-equalizer has been designed to be the most generally satisfactory. The 6,800-ohm resistor, R_{101} , in Fig. 3, limits the response to compensate for the pre-emphasis shown above the high-frequency cross-over point in Fig. 4. With the recordings now being made by one manufacturer the response at 10,000 cycles with the 6,800-ohm R_{101} will be up several db, and those of other manufacturers will range above and below this point. The normal variations which will be encountered from recording to recording should not be objectionable. Some recordings will sound more brilliant than others, but tone controls on the receiver should take care of this. If less needle scratch is desired R_{101} can be reduced to as low as 2,000 ohms, particularly in

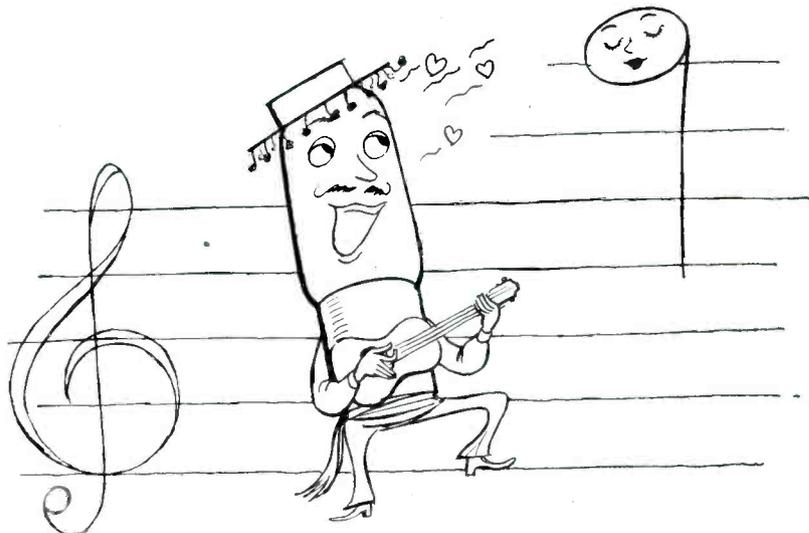

The little lamp that learned to love "high C"


A SOPRANO'S "high C" can be just too much for many dial lamps. Severe vibrations caused by such high notes are often sufficient to tear an old-style lamp filament apart. General Electric engineers found a simple way to minimize this cause of early lamp failure. By making the filament supports longer and moving the bead closer to the coil, they greatly reduced the effects

of vibration.

That's why G-E dial lamps have actually learned to like "high C"... and to give long life in spite of the continuous vibration.

For information on prices and types of G-E miniature lamps, call your nearby G-E Lamp office. Or write to General Electric Company, Div. 166-S2, Nela Park, Cleveland 12, Ohio.

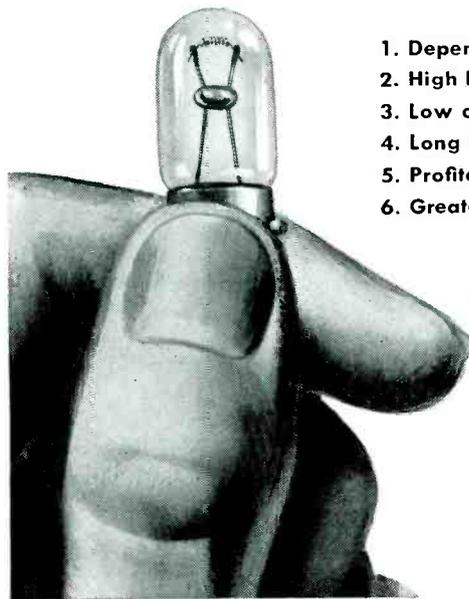1. Dependable, trouble-free performance.
2. High level of maintained light output.
3. Low current consumption.
4. Long life.
5. Profitable to handle.
6. Greater dealer acceptance.



G-E LAMPS

GENERAL ELECTRIC

SERVICE, FEBRUARY, 1949 • 35

*From notes prepared by N. S. Cromwell, G. E.

(Continued on page 36)

Everybody agrees
ATR VIBRATORS
are **TOPS!**

ATR

AUTO RADIO VIBRATORS
have Ceramic Stack Spacers



A COMPLETE LINE OF VIBRATORS...

Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction, featuring Ceramic Stack Spacers for Longer Lasting Life.

Backed by more than 17 years of experience in Vibrator Design, Development, and Manufacturing.

ATR PIONEERED IN THE VIBRATOR FIELD.

NEW VIBRATOR GUIDE FREE



ATR

"A" BATTERY ELIMINATORS

for DEMONSTRATING AND TESTING AUTO RADIOS

New Models... Designed for testing D. C. Electrical Apparatus on Regular A. C. Lines. Equipped with Full-Wave Dry Disc Type Rectifier, Assuring Noiseless, Interference-Free Operation and Extreme Long Life and Reliability.

NEW MODELS NEW DESIGNS
NEW LITERATURE

"A" Battery Eliminator, DC-AC Inverters, Auto Radio Vibrators

See your jobber or write factory

AMERICAN TELEVISION & RADIO CO.
Quality Products Since 1931
SAINT PAUL 1, MINNESOTA-U.S.A.

Servicing Helps

(Continued from page 35)

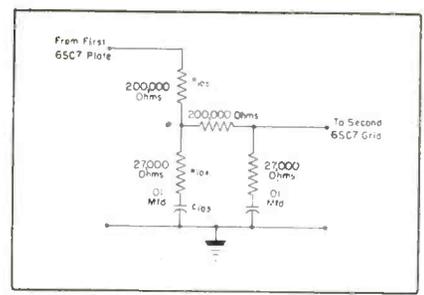


Fig. 1. Alternate If compensation circuit.

Fig. 2. The If compensation circuit of the preamp shown in Fig. 3.


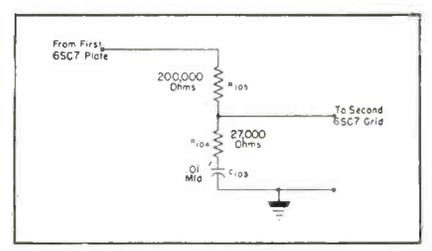


table model sets. Conversely, R₁₀₁ may be increased in value to 33,000 ohms, or omitted entirely for increased high-frequency response.

If still more high-frequency response is required, peaking can be added as shown in Fig. 5.

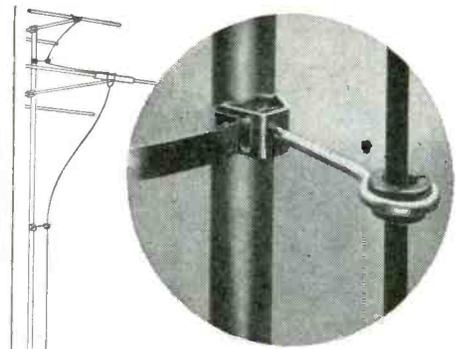The amount of high-frequency response provided by this circuit should be necessary only to make up for deficiencies in the amplifying system following the preamp, room acoustics, or the hearing ability of the user. Elimination of R₁₀₁ and addition of a 470-mfd capacitor across the 200,000 ohm resistor, R₁₀₅, will increase the 10,000 cycle over-all response about



Phoenix ANTENNA MAST STAND-OFF INSULATORS


- Attaches to any size mast in 10 seconds.
- Just pull strap through, then turn screw eye.
- No more swinging lead-ins with broken wires.
- A MUST for every good installation.

List Price **25¢** each

A complete line of Television Antenna Mounts. Send for literature.

At Leading Jobbers and Dealers - or Write to Phoenix Electronics Inc. Lawrence, Mass.


Fig. 4. Velocity characteristic of average present day recordings.

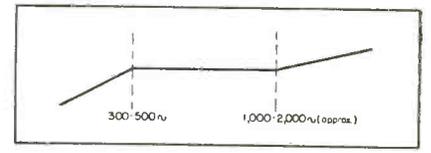

15-20 db. This is far in excess of any normal requirements.

It can be seen that modification of the preamp-equalizer to suit individual

Fig. 3. Schematic of preamp equalizer; G.E. SPX-001.

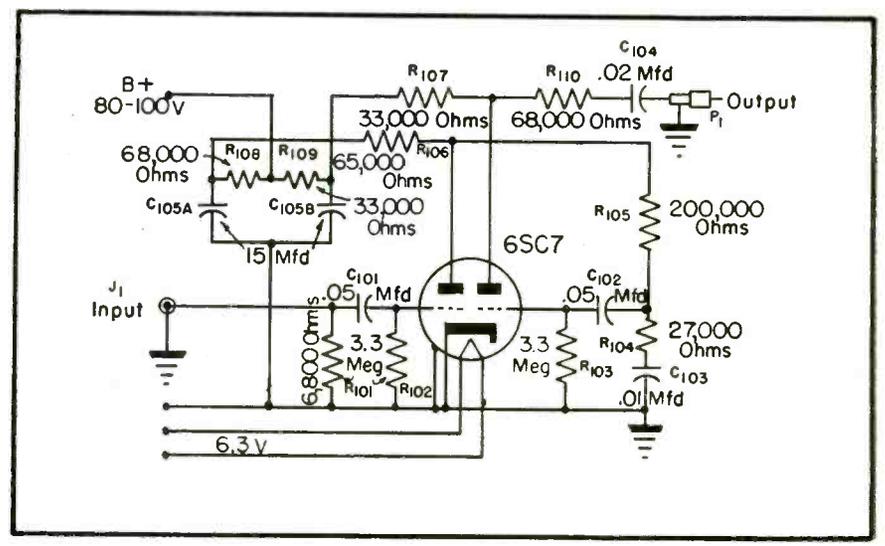

requirements is a relatively simple matter. Actually, the response as designed into the preamp is the best for the majority of applications.

A curve of the actual velocity response of the variable-reluctance cartridge is shown as Fig. 6. This curve cannot be traced from any of the popular and commercially available frequency records, since these records have frequency characteristics which cause incorrect test results.

If the zero db axis is shifted down 1 db, it can be seen that the curve is within ± 1 db of the ideal velocity response curve. The flat response and the absence of resonant peaks are the factors which allow equalization of the curve with simple circuits to suit the requirements of varied applications.

There are many other types of circuits which can be used to vary the response so that portions of the curve can be boosted or attenuated for special requirements. A sharp cut-off above 10,000 cycles is highly recommended for all applications and recordings, since little or nothing is lost in musical quality and much is to be gained in the elimination of noise components and high-frequency distortion from the recordings. A sharp cut-off at 5,000 to 7,000 cycles will improve the reproduction of many recordings greatly, and the musical quality will still be enjoyable.

Compensation circuits for other types of cartridge must be removed from the receiver or amplifier with which the variable reluctance cartridge is to be used. Such circuits will in-

(Continued on page 38)


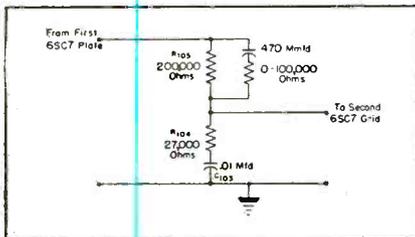


Fig. 5. H peak circuit developed for the preamp.

Fig. 6. Actual velocity response of the G.E. RPX-010 variable reluctance cartridge.

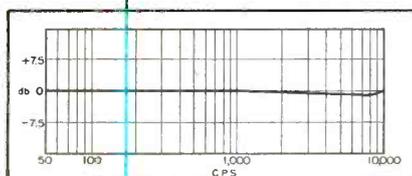

TRANSVISION

PRESENTS
THE NEW

MODEL 12CL TV-FM KIT

Brings the biggest and best in television within the reach of everyone.

GIGANTIC VALUE!

OVER

200

SQ. IN. PICTURE
VISIBLE from ALL ANGLES

With FM Radio
(De Luxe Continuous TV-FM Inputuner)

(Picture much bigger than a tabloid newspaper page.)
IMAGE IS EQUAL to that of a 20" tube—even sharper and clearer—and it is visible from all angles.

\$399⁰⁰

NET

Includes Kit, Cabinet, Lens, Table, Antenna and 60 Ft. of Lead-In Wire

EQUIVALENT OF \$1000.00 SETS!

Price of the new 12CL electromagnetic kit includes these outstanding features:

- 12½" picture tube with special fitted All-Angle Lens and color kit.
 - Beautiful select-grain cabinet and roto-table.
 - De Luxe continuous TV-FM Inputuner.
 - New all-channel hi-gain antenna and 60 feet of lead-in wire.
- Nothing else to buy.


TRANSVISION REMOTE CONTROL UNIT KIT

Will operate any TV receiver from a distance. Turns set on, tunes in stations, controls contrast and brightness, turns set off. Ideal for installations where the television receiver is inaccessible. Tuner unit is a high gain, all-channel unit with about 50 micro-volt sensitivity. Easy to assemble in about an hour.

Model TRCU, with 25 feet of cable... Net \$66.00
Without cabinet Net \$65.00

ASSEMBLE Your Own CABINETS

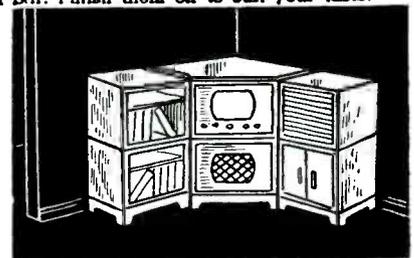Transvision's "MODULAR" Cabinets come in knock-down, unpainted units, offering an unlimited range of combinations, including even a bar. Finish them off to suit your taste.



Corner piece, shown above, has room for TV, Phono, Record Storage, and open Book Case. COMPLETE..... Net \$84.00

For other units and prices, write for "Modular" Catalog.

MODEL 12CL TV-FM KIT

- Features 12½" tube with fitted All-Angle Lens, giving over 200 sq. inch picture which is visible from anyplace in a room.
- Gives ideal long-range reception with CONTINUOUS TUNING on ALL CHANNELS. Has De Luxe continuous TV-FM Inputuner.
- COMPLETE with Cabinet, Lens, Roto-Table, Antenna, Lead-in Wire.
- A BIG PROFIT-MAKER for service dealers. This kit is TOPS—ideal for homes, clubs, taverns, and other commercial installations.

EASY TO ASSEMBLE . . .

NO TECHNICAL KNOWLEDGE REQUIRED
Transvision's simple step-by-step Instruction Sheet makes assembling a TV Kit a pleasure. Each kit comes complete with all-channel double-folded dipole antenna and 60 ft. of lead-in wire. *Nothing else to buy!*

TRANSVISION ALL-CHANNEL TELEVISION BOOSTER

To assure television reception in weak signal areas, or areas which are out of range of certain broadcast stations, Transvision engineers have designed this new booster. It increases signal strength on all television channels. Tunes all television channels continuously. Can be used with any type of television receiver. Unusually high gain in upper television channels. Model B-1.....LIST \$44.95

TRANSVISION COMPLETE LINE OF TELEVISION COMPONENTS

Essential units for building a quality television set . . . Transvision makes available a complete line of high quality parts competitively priced. Included in this line are Filter Chokes, all types of Transformers, Focus Coils, Deflection Yokes, Coils—and, of course, major units such as Picture Tubes, Antennas, Lenses, etc., etc.

WRITE FOR COMPONENTS FOLDER P-1

RADIOMEN . . . You Can GET INTO the
TELEVISION BUSINESS
IN A BIG WAY WITH THE
TRANSVISION DEALER PLAN
Write for Dealer Folder D-1

TRANSVISION, Inc. Dept. S New Rochelle, N. Y.

In Calif.: Transvision of California, 8572 Santa Monica Blvd., Hollywood 46
All prices 5% higher west of Mississippi; all prices fair traded. All Prices Subject to Change Without Notice

MERIT

news

New MERIT Vibrator Transformers


MERIT leads again!

For the first time a transformer company in the replacement field makes available to you, Vibrator Transformers in sealed-in cans, that fit exactly your specific applications, and made to Merit's high standards of quality.

These new Transformers are sealed in compound filled cases for interference or hash reduction, for operation from 6 V battery and vibrator.

Here is another outstanding development in MERIT'S sweet line of replacement transformers.

Buy them from your
Merit jobber today!

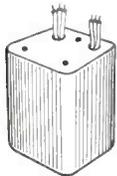


MERIT
Vibrator
Transformers
Mounting JT

Type No.	List Price	Sec. DC Volts to filter	Sec. Amp.
P-4069	\$6.75	150	40
P-4070	7.25	225	40
P-4071	7.50	250	50

DIMENSIONS

Type No.	H	W	D
P-4069	3"	2 ³ / ₈ "	2 ³ / ₁₆ "
P-4070	3"	2 ³ / ₈ "	2 ³ / ₁₆ "
P-4071	3"	2 ³ / ₈ "	2 ³ / ₁₆ "

PRODUCTS OF MERIT

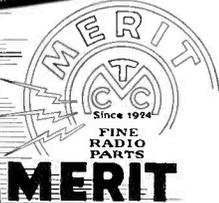

MERIT

COIL & TRANSFORMER CORP.

4455 NORTH CLARK ST., CHICAGO 40, ILL.

Servicing Helps

(Continued from page 37)

crease or attenuate portions of the response curve. All necessary compensation is done within the preamplifier, with the exception of the bass boost required within the amplifier or receiver to compensate for the deficiency of the human ear at lower volume levels. This latter compensation should be coupled to the volume control circuit for proper operation and is provided in most receivers built in the last 10 years or more.

Service Notes

Philco 48-1270: *Extreme weakness on radio, on all positions; phono okeh.* The 100,000-ohm resistor, R₃₀₆, in the screen circuit on the second *if* amplifier tube is undoubtedly defective. This *matchstick* unit is located close to the rear of the chassis, connected to pin 3 on the 7B7 socket. When it opens up entirely, screen voltage is removed. Bypass capacitor can be checked too for leakage.

Crosley 66TA: *Resistors smoking, coils melting, etc., and not a sound from speaker.* Look for short in small trimmer, 62 on schematic, which tunes the *rf* plate circuit. This will cause resistors 1 and 5 (3,300 and 1,000 ohms) to burn up. This condition could damage the *rf* interstage transformer. To remedy, the capacitor and resistor are disconnected from the right side of trimmer assembly and the assembly is turned upside down. An extra piece of thin mica, salvaged from the defunct *if* transformer is inserted between trimmer blades, and the unit reassembled.

Silvertone 101.802-1: *This battery set may have no volume at all or be very*

¹From notes supplied by Jack Darr.

weak. An open plate load resistor (1-megohm) in 1LD5 plate circuit is usually the trouble. It would be also wise to check the 3.3-megohm screen resistor on the same tube.

Philco CR-4, CR-6: *Intermittent operation after first two weeks or so of use.* The antenna trimmer, located on side of cabinet, is the trouble in most cases. This unit is in series with the antenna, and shorting either end will cause cut out and popping noises. The problem can be solved by bending connecting lugs to clear bracket, and inserting extra mica between blades if necessary. It's also wise to check the very small leads to oscillator coil. Often the plastic-covered wire on these coils will short to grounded lugs or adjacent wires, if overheated during assembly.

G. E. 250, 260: *No reception.* Flexible bands which connect the antenna in the lid with the terminals on the chassis may be broken. To remedy solder the ends together, being careful that they do not touch the case as the cover is opened.

Often in these models the quality will become fuzzy. In every case this trouble was traced to the bias cells. In use these will become loose and even drop out of their holders completely. If the holders are bent straighten them out so that they will have plenty of tension on the cells. The front panel must be removed to get at these cells.

Intermittent reception is another complaint with these sets. On two occasions this was found to be caused by the leads from the bypass capacitor mounted across the 1LC6 *rf* tube socket shorting to the socket lugs. To get at the chassis to make this repair it is necessary to remove the front panel, push button escutcheons, dial escutcheon, lid arms, and the right end panel. The latter is removed after


²From notes supplied by John Findarle.

telrex INC.
CONICAL ANTENNAS
RUTHERFORD AVENUE ON ROUTE 35
ASBURY PARK, N. J. PHONE: ASBURY PARK 1 0119

BOX 879A, ASBURY PARK, N. J.

- Hi-Gain Stacked Conical "V" Beam
- Channels 2 to 13 Plus FM
- Low Inception Angle
- Extremely High Signal to Noise Ratio
- 150 Ohm Non-varying Impedance
- Use 72, 150 or 300 Ohm Transmission Lines
- Universal Mounting Clamps

SEE YOUR DISTRIBUTOR

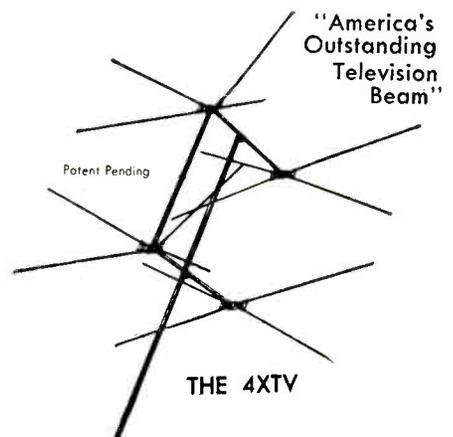

taking off three speed nuts used to hold it in place.

Silvertone 1670-U: If this set develops intermittent reception the .5-meg-ohm *arc* resistors should be checked for poor connections in the end terminals. These loosen with age and replacing them cures up the intermittent condition.

If the same set has poor tone, sensitivity, etc., an alignment job will do wonders.

Horizontal AFC

(Continued from page 33)

pulse waveform of output potential. This is not exactly true, for we need a sawtooth potential. This is obtained simply by connecting a .0022-mfd capacitor (61) across the output; a sawtooth is produced from a pulse. During the time that the tube is non-conductive, the capacitor is charging through a 120,000-ohm resistor (178). When the tube conducts, the capacitor discharges through the tube plate circuit. There is, as potential across the capacitor, a slow charging and a rapid discharging to produce the sawtooth waveform of potential required.

A study of the foregoing indicates that almost any component in the overall circuit is capable of some measure of frequency-control, and therefore is instrumental in thermal or aging-drift of the oscillator. Fortunately, the effects of all circuit elements do not cause drift in a single direction, and near cancellation is had, along with the control-tube plate resistor of high negative temperature coefficient.

The only component necessitating special attention to placement in the chassis are that resistor and the oscillator coil which is placed away from heat-radiating components.

The variable *horizontal lock* capacitor control permits the injection of increased control-tube signal in the event of high noise level, or weak signal, causing a decrease in capacity.

Next Month

THE CONCLUDING installment of the Lester L. Libby series on the alignment of the Bendix TV receiver will be presented in the March issue.

Donald Phillips will also continue his discussions of TV production changes in the March issue of *SERVICE*. In this issue will also appear an article on TV sync and inter-sync systems by Edward M. Noll.



Model 260 in all-bakelite roll top carrying case

There are more
Simpson 260
 high sensitivity
 Volt-Ohm-Milliammeters
 in use today than all others
 combined! Your Parts Jobber
 can tell you why

SIMPSON ELECTRIC COMPANY

5200 5218th St., Kinzie St., Chicago 44, Ill. In Canada: Bach-Simpson, Ltd., London, Ont.

RANGES at 20,000 ohms per volt DC, 1000 ohms per volt AC

VOLTS: AC & DC—2.5, 0, 50, 250, 1,000, 5,000

DC CURRENT: 10, 100, 200 MA—10 AMP—100 MICRO AMP

OHMS: 0-2,000 (12 center), 0-200,000 (1200 center), C-20 MEGOHMS (120,000 ohms center)

DECIBELS: (5 ranges) —10 to +52 DB


American Beauty

ELECTRIC SOLDERING IRONS

are sturdily built for the hard usage of industrial service. Have plug type tips and are constructed on the unit system with each vital part, such as heating element, easily removable and replaceable. In 5 sizes, from 50 watts to 550 watts.

TEMPERATURE REGULATING STAND

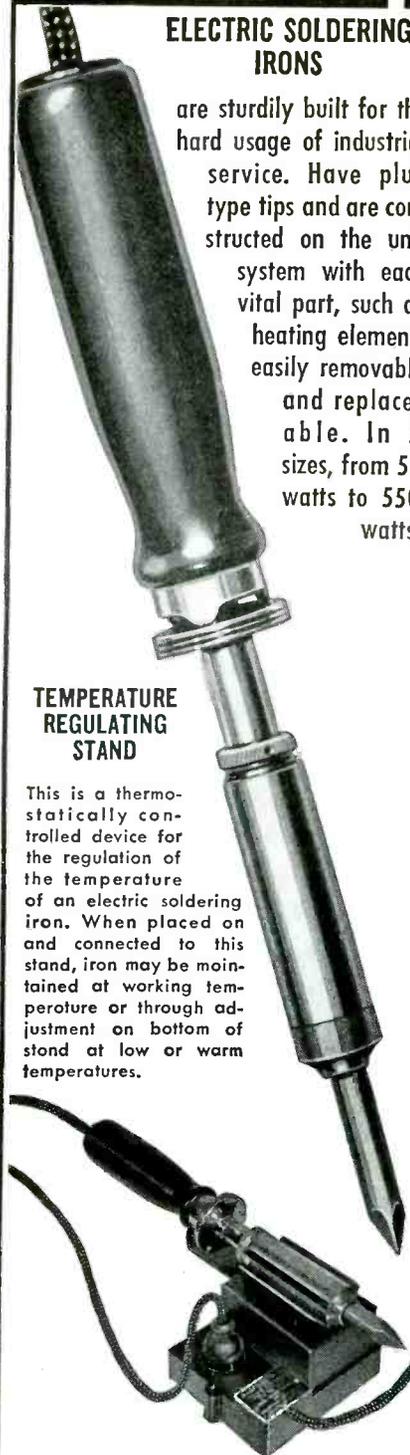This is a thermostatically controlled device for the regulation of the temperature of an electric soldering iron. When placed on and connected to this stand, iron may be maintained at working temperature or through adjustment on bottom of stand at low or warm temperatures.



For descriptive literature write

**AMERICAN ELECTRICAL
HEATER COMPANY
DETROIT 2, MICH., U. S. A.**

Ser-Cuits

(Continued from page 22)

sound *if* amplification are employed. These two stages are operated with their plates grounded while their cathodes are returned to the -140-volt buss. Thus, these two tubes form part of the divider system that splits the B voltage. Inductors L_{17} and L_{18} are 1" pieces of straight, tinned copper wire. They are employed in the cathode circuits of V_{13} and V_{14} to provide a decreased input conductance at the grids of these stages at 21.75 mc.

T_{10} in conjunction with a 6AL5 (V_{15}) forms a conventional ratio detector system that operates on a center frequency of 21.75 mc and has a peak bandwidth of approximately 500 kc.

Traps

Since the *if* frequency of the adjacent channel sound carrier and the *if* frequency of the received channel sound carrier are quite close to the frequencies passed by the picture *if* system, some means of attenuating these sound carriers must be provided in the picture *if*. Otherwise the carriers would pass through to the pix detector where they would be demodulated and passed on to the picture tube grid as video information. Once there, these signals would appear as interference in the observed picture.


Incidentally with the *rf* oscillator operating above the channel being received the *if* relation of the pix to sound carriers is the reverse of their *rf* relation.

To prevent this interference, trap circuits L_{34} , L_{37} , L_{41} and L_{42} are provided. L_{34} and L_{37} function as series traps in the plate circuits of V_2 and V_4 and are tuned to 27.75 mc, the *if* frequency of the adjacent channel sound carrier. The combined trapping action of these two stages is sufficient to keep the sound interference from this source at a negligible value. L_{41} and L_{42} are tuned traps inserted in the cathode circuits of the third and fourth pix amplifier. These traps are tuned to 21.75 mc, the sound *if* frequency. At this frequency, the voltage developed across these traps will function as a degenerative voltage opposing the 21.75 mc sound *if* signal at the grids of the respective stages. The combined attenuation offered by the pix amplifier stages is sufficient to suppress the 21.75 mc sound carrier before it reaches the pix detector. Inductors L_{39} and L_{40} are used to stabilize the pix amplifier stages.

FREE

SERVICE MEN
REPAIRMEN!

**WALDOM
REPLACEMENT
CONE
MANUAL**

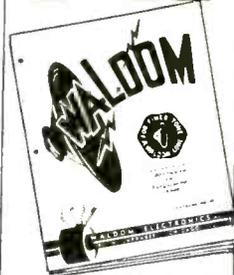

Just mail your name and address today for FREE copy of the big 20-Page WALDOM Replacement Cone Manual, listing replacement data for 69 different brands of speakers—from Admiral to Zenith! Manual also gives complete instructions, together with clear illustrations for installing cones properly. Invaluable reference guide for servicemen and repairmen. Get your copy FREE! Just send name and address.

FOR FINER TONE A WALDOM CONE

Waldom Replacement Cone Assemblies will satisfy the high standards of precision workmanship and performance set by you and by your customers because . . .

- **WALDOM CONE ASSEMBLIES** feature HAWLEY diaphragms with the patented thin, tapering edge that assures maximum speaker efficiency and true low frequency response.
- **WALDOM CONE ASSEMBLIES** are guaranteed unconditionally as to construction and performance. Only the very finest voice coils and spiders, precision made to exact specifications, are used.
- **WALDOM CONE ASSEMBLIES** carry full R. M. A. Warranty.



Write for Your FREE

REPLACEMENT CONE MANUAL! The big 20-Page WALDOM Manual puts every bit of replacement cone information at your fingertips, in seconds! It will speed your speaker repair work, and help you handle those jobs more profitably. Send your name, address for Free copy.

WALDOM ELECTRONICS, INC., Dept. S
911 N. LARRABEE STREET CHICAGO, ILLINOIS

Two detectors are employed at the output of the pix *if* system. One, a 1N34 crystal diode, is connected in the conventional manner to provide an output signal of negative polarity across its output load, while the other, a 6AL5 (V_{8A}), is connected to give an output signal of positive polarity across its load.

The video amplifier is a conventional two-stage system that is fed by the output of the 1N34 crystal detector. The frequency response of the amplifier extends to 4 mc while the overall voltage gain from the input grid to the output plate is approximately 60 times. The gain of the amplifier is variable by means of a 3,000-ohm unit (R_{60}), the picture control, in the cathode circuit of the 6AU6 first video stage, V_6 .

The video signal at the picture tube grid must be of such polarity that the sync and blanking pulses will drive the grid in the negative direction. For this reason, with the two-stage video amplifier, it is necessary for the output of the pix second detector, the 1N34 crystal diode, to be of the same polarity as that of the video signal required at the kinescope grid. With this arrangement, sync pulses drive the grid of the first video amplifier stage in the

negative direction. This stage, V_6 , is so designed that with normal signal input at its grid the tube works over most of its operating range. However, any large noise pulses above sync level will drive the grid beyond cutoff. This results in a desirable peak noise limiting action by the video amplifier that effectively improves the overall signal-to-noise ratio of the receiver.

Horizontal Deflection Circuits

The horizontal deflection and *afc* circuits in this set depart considerably from the conventional systems. The primary function of these circuits, as in other receivers, is to provide a stable, linear, deflection current in the horizontal yoke. Performance of this action results in framing the received picture in the horizontal direction.

The horizontal oscillator, V_{21} , is a conventional cathode coupled multi-vibrator. In actual operation the frequency of the oscillator is set near line speed by means of a horizontal hold control, R_{55} . The oscillator is then locked in sync by means of a *dc* control voltage which is applied to the grid (pin 7) of one of its triode sections. This control or *afc* voltage acts to speed up or slow down the oscillator until it operates at horizontal sweep frequency. The *afc* voltage is developed by a horizontal *afc* rectifier, V_{20} , and is the resultant of the phase error between the incoming horizontal sync pulses and the output of the horizontal oscillator which is coupled back to the rectifier by means of a 680-mmfd capacitor (C_{76}) and 3,300-ohm resistor (R_{100}).

The peaked sawtooth voltage used to drive the horizontal output stage is developed by the charge-discharge action of capacitor C_{76} and the peaking resistor R_{100} . A neon bulb (NE-2) acts as a regulator for the voltages applied to the multivibrator and as a result provides for increased stability of oscillator operation.

Horizontal Output

Most present-day receivers that employ magnetic deflection systems utilize transformer coupling between the horizontal output stage and the deflection yoke. In this receiver, however, no output transformer is used and the horizontal deflection yoke is directly connected to the plate of the output stage. Due to this fact, and to provide proper loading for the output stage, the inductance of the yoke is made quite high as compared to that of yokes used in conventional transformer cou-

(Continued on page 42)

Flexibility makes

"the Service Man's Line"

Brach antennas . . . long known for dependability . . . maximum reception . . . trouble-free operation . . . durability and ease of installation . . . new feature an added extra . . . Flexibility. Unique construction features aid the service man in making a more rapid installation to which future additions or modifications can be easily made.

1. FLEXIBILITY A complete line designed with basic antenna parts which are convertible to more complex arrays as required by location and reception problems.

2. COMPLETE KITS Each antenna model is independently designed and furnished in a completely packaged kit containing all necessary hardware, download (when desired) and the Universal Base Mount . . . ready for installation.

3. PRE-ASSEMBLY Each antenna is factory pre-assembled as far as possible, ready to erect. Complete and simple installation instructions. Saves valuable man-hours on the roof.

4. MECHANICAL STRENGTH Weather - tested for durability, Brach Antennas feature a husky steel mast, rigid connections, sturdy base mount, neat appearance. All parts corrosion resistant.


5. SUPERIOR RECEPTION Designed with engineering "know-how". All Brach antennas are factory pre-tuned, matched for 300 ohm transmission line with large diameter aluminum elements for better signal pick-up. Directivity patterns and standing wave ratios available upon request.

New! Tops in TV! HI-LO ROTATABLE Antenna

Here it is! A rotatable antenna to provide peak performance with any station at any time. Brach introduces the new "Superview" Rotatable, covering both high (174 MC to 216 MC) and low (88 MC to 108 MC) TV bands. High band extension available for easy addition to standard dipole array for separate orientation. No more multiple images. No more "weak" stations. Brach's Superview HI-LO assures television reception that's tops. Make sure and investigate the new Superview line today.

Write for Free Brach catalog showing complete line of TV and FM antennas and accessories.

SEND FOR CATALOG No. S304

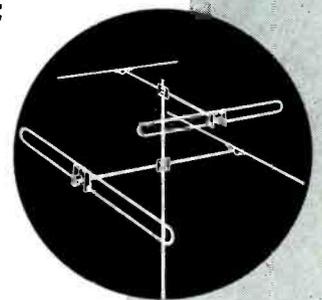

L. S. BRACH MFG. CORP.

200 CENTRAL AVENUE, NEWARK, N. J.

WORLD'S OLDEST AND LARGEST MANUFACTURERS OF RADIO ANTENNAS AND ACCESSORIES

Rooftop Definition with Table-Top Convenience!

NEW
ICA WASP
INDOOR ALL-CHANNEL
ANTENNA
FOR TELEVISION
AND FM

INSTALLED
IN AN INSTANT!

\$**6⁹⁵**



No rooftop climbing here! The ICA Wasp adjusts indoors—easily, and to all channels! For all receivers! Compactly designed, the Wasp features a smoothly engineered swivel base, combined with exclusive adjustable dipoles. Once adjusted, special spring action assures firm anchoring of dipoles and perfect electrical contact.

The heavily chrome-plated brass dipoles and antique bronzed swivel base blend well with living room décor. A non-scratch felt base protects furniture finish.

The Wasp is packaged with 8 feet of 300 Ohm lead.
19" high closed; base 3 5/8" diameter.

Latest Television Antenna and Accessory Catalog Available.



insuline CORPORATION OF AMERICA

INSULINE BUILDING • 36-02 35th AVENUE • LONG ISLAND CITY, N. Y.
West Coast Branch and Warehouse: 1335 South Flower Street, Los Angeles, Calif.



Picture width is controlled by means of R_{100} which varies the plate voltage (and thereby the output) of the horizontal stage. Small improvements in trace linearity are affected by means of the variable linearity control system placed in the plate circuit of the damper.

The Damper Circuit

When the plate current of the output stage is cut off by the negative portion of the voltage applied to its grid, the magnetic field in the deflection coil begins to collapse at a rate determined by the resonant frequency of the system. If permitted to go unchecked the circuit would oscillate. However, since this condition is undesirable, a damper stage, V_{26} , is placed across the horizontal yoke to prevent these oscillations. This stage is so arranged that a half cycle of oscillation (retrace) is permitted. At the end of the half cycle the damper conducts and causes the oscillatory currents in the yoke to decay in a linear manner and at a rate suitable for the visible trace. Very shortly after decay starts, the output stage begins to conduct and this additional current in conjunction with the decay current in the yoke produces an essentially linear trace motion of the electron beam.

Low Voltage Power Supply

A single 5U4G rectifier supplies approximately 330 volts *dc* at 220 ma to the receiver. A pair of 40-mfd capacitors, $C_{102A/B}$ together with filter choke L_{65} form a pi-type filter system for the supply. Additional 80-mfd filters are placed in the receiver chassis.

A unique system of *dc* voltage division and distribution is utilized.

The divider system is so arranged that the receiver chassis is 140 volts positive in respect to the minus leg of the supply; the total current requirements of the receiver are supplied through the focus coil system. The over-all design of the receiver circuits is such that the current requirements on the power supply are at a minimum for the number of tubes involved.

High Voltage Supply

An *rf* 10 *kv* high voltage supply system is utilized to provide the second anode potential for the kinescope. A twin triode with both sections connected in parallel functions as the *rf* oscillator. The voltage developed by the oscillator in its plate tank is stepped up in the secondary of the *rf* transformer, T_{15} , and applied to the high voltage rectifier. The operating frequency of the oscillator is approximately 190 kc.

HICKOK 5" CATHODE RAY OSCILLOGRAPH For Television

Seven to twenty times more sensitive than Comparable 'Scopes.

Phasing control with Hickok exclusive sinusoidal sweep. • Extra high gain amplifiers—.015 V per inch. • Synchronized linear FM sweep. • Wide band amplifiers for FM and Television to 1 megacycle.

Mail this ad for literature and free copy of our regular 50c Service Instruction Manual.

THE HICKOK ELECTRICAL INSTRUMENT CO.
10921 Dupont Avenue, Cleveland 8, Ohio

Ask for Model 195 B

Ser-Cuits

(Continued from page 41)

pled systems. Since horizontal retrace time is a function of the resonant frequency of the yoke and its associated circuit it is necessary to keep the shunt capacity across the yoke at a minimum value. However, due to the polarity of the deflection voltage, it is necessary to connect the filament of the damper tube directly to the plate of the output stage. This places the capacity of the damper tube filament transformer directly across the yoke. For this rea-

son transformer T_{10} was specially designed for low capacity between the damper tube filament winding and the rest of the assembly.

The majority of the output stage plate current is supplied through the damper while the remainder comes through a 5,000-ohm control (R_{100}) in series with a shunt feed choke, L_{62} . Since the inductance of L_{62} is large (as compared to that of the yoke) it presents a high impedance in the B+ line to the deflection voltage developed by the 6L6 output tube, V_{25} , and thus prevents the B supply from loading down the output stage.

TRY and BEAT THESE BUYS!

PUSHBACK WIRE



Below Mill Prices!
 2,000,000 feet—tinned copper—all 1st. class, double cotton serve, waxed finish. Available 1,000 foot rolls.
 22 gauge (6 colors) \$3.98 roll
 20 gauge (6 colors) 4.98 roll
 18 gauge (brown only) 6.49 roll

HERE'S A STEAL Tom Thumb RADIO CAMERA



A hit on the beach at picnics, etc. A combination reflex camera and portable battery radio. Former list \$29.95

OUR LOW PRICE
\$12.65 Less Batteries
 With batteries add \$1.84.

MIDGET I. F. TRANSFORMERS

Original List \$2.10
 At discounts up to 86%

NOW 36c EACH

400-500 Kc range
 1 1/4" square, 3" high hi-gain iron core.

INPUT—A826
 OUTPUT—A827

Specify Type
 Matched Pair 69c
 Dozen \$3.95
 Egg Crate of 100 \$29.00

1 meg. VOLUME CONTROLS

85% DISCOUNT
OUR PRICE 29c each

Universal with switch

ORDER INSTRUCTIONS
 Minimum order—\$2.00. 25% deposit with order required for all C.O.D. shipments. Be sure to include sufficient postage—excess will be refunded. Orders received without postage will be shipped express collect. All prices F.O.B. Detroit.

RADIO SUPPLY & ENGINEERING CO., Inc.
 86 ELDEN AVE. DETROIT 1, MICH.

New TV Parts . . . Accessories

PHILMORE TV KITS

A 30-tube TV kit, model P 30, featuring a 12-channel tuner, and assembled and prealigned picture and if sound stage units, has been announced by the Philmore Manufacturing Co., Inc., 113 University Place, N. Y. 3, N. Y.
 Kit, supplied with several large blueprints detailing top and bottom wiring, uses the basic RCA 630TS circuit. Supplied with a 10" picture, the receiver can be modified to use a 12" or 16" type tube.



TRANSVISION TV FIELD STRENGTH METER

A TV field strength meter, FSM-1, has been announced by Transvision, Inc., New Rochelle, N. Y.
 Meter consists of a high-gain receiver with a calibrated meter to indicate a signal level. Each unit is individually calibrated. Said to be capable of measuring field strength from 50 to 50,000 microvolts at 300-ohm input terminals.
 The instrument can also be used to measure losses or gain of various antenna and leadin combinations and check receiver reradiation (local oscillator).



MUELLER CLAMPIPE

A stand-off insulator for TV and FM antenna leadins, *Tenna-Clampipe*, that clamps onto the antenna mast or any other handy support, has been announced by the Mueller Electric Co., 1583 E. 31st St., Cleveland 14, Ohio.
 Clampipe is an assembly of the Mueller ground clamp and a screw-eye with a plastic, insulating grommet. All metal parts are weather-proofed.
 Offered in two types, for flat twin-lead and other for round cable.

RCA SPEAKERS

are quality-engineered for dependable performance



Check these important features!


- ✓ Moisture-resistant voice-coil suspension—unaffected by humidity changes.
- ✓ Felted cone for "flutter-free" response.
- ✓ Rugged mechanical construction with welded housing assembly.
- ✓ Exclusive clamping spring permanently locks Alnico V magnet in larger sizes of PM speakers.
- ✓ Mechanical filter ring in 12" speakers cuts needle scratch and 10-kc. whistle.
- ✓ Rugged—Dustproof—Rustproof.
- ✓ Adjustable voice-coil mounting in 12" speakers.
- ✓ Mounting designed to RMA standards.

Always keep in touch with your RCA Distributor

TURN TO NEXT PAGE

RCA ELECTRONIC COMPONENTS RADIO CORPORATION OF AMERICA HARRISON, N.J.

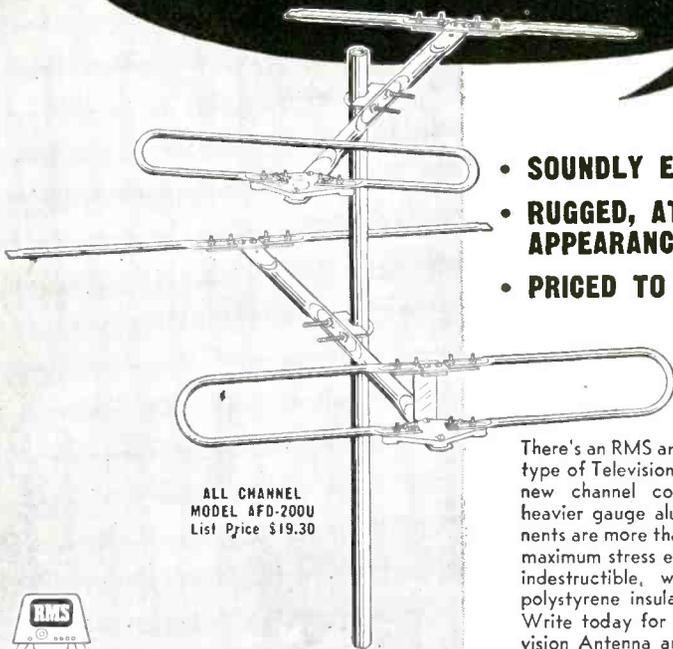Everybody's Talking About . . .
**THE NEW RMS
 TELEVISION ANTENNA LINE**



ALL CHANNEL
 MODEL 8FD-2000
 List Price \$19.30

- **SOUNDLY ENGINEERED**
- **RUGGED, ATTRACTIVE APPEARANCE**
- **PRICED TO SELL FAST**



There's an RMS antenna for every type of Television installation . . . new channel construction and heavier gauge aluminum components are more than adequate for maximum stress encountered . . . indestructible, weather-resistant polystyrene insulators.

Write today for new RMS Television Antenna and Accessories Catalog #215-S




RADIO MERCHANDISE SALES, INC.

550 WESTCHESTER AVENUE
 NEW YORK 55, N. Y.

JFD MAST LEADIN SUPPORTS

An assortment of mast-clamp screw eye polyethylene stand-offs for use in securing twin lead or RG type lines to masts or elements from 1/2" to 2" in diameter, has been announced by the JFD Manufacturing Co., Inc., 4117 Ft. Hamilton Parkway, Brooklyn 19, N. Y.

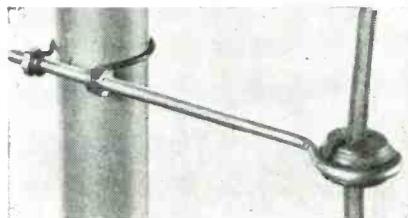
Screw eye lengths available are: 3 1/2", 5 1/2", 7 1/2", 12". Tempered spring steel mast clamps sizes are: 1/2", 3/4", 1", 1 1/2", 1 3/4" and 2".



DELSON WINDOW TV ANTENNA

A window antenna for TV and FM, the *Jiffy-Tenna*, of hard-drawn lightweight aluminum tubing with lucite insulation, has been announced by Delson Manufacturing Co., 126 11th Ave., New York 11, N. Y.

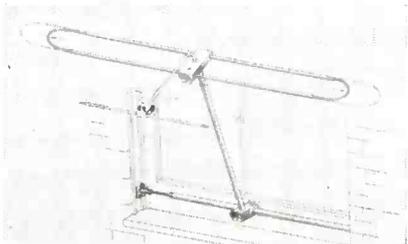
Can be adjusted to serve as a tunable folded dipole antenna. Has a sliding trombone feature. Dipole ends can be removed to provide single dipole and reflector on the low bands.



VEE-D-X CHIMNEY-VENT PIPE TV MOUNT

A chimney and vent pipe TV antenna mount which mounts inside the chimney or vent pipe, and can fit into openings, round, square, rectangular or oval, from 4" to 22", has been announced by the LaPointe-Plascomold Corp., Unionville, Conn. Will accommodate masts of 1", 1 1/8" and 1 1/4" diameter.

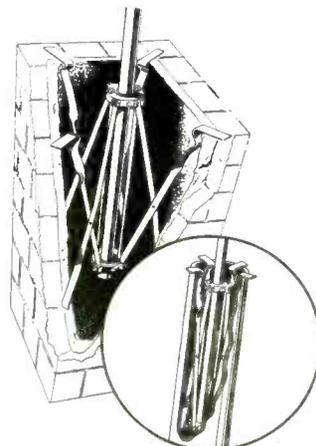Has 8 points of bearing. Unit is constructed of aluminum castings with cadmium plated steel arms.



The New *Mueller*

"TENNA-CLAMPIPE"

(Clampipe T. M. Reg. U. S. & Can. Pat. Off.)

A Stand-off Insulator that Clamps on Quickly-Easily-Almost Anywhere

for

Supporting TV and FM Antenna Lead-ins on Masts, Cross-arms, Basement Pipes or any other Handy Place.


SIMPLY TURN THE SCREW-EYE BY HAND FOR A SOLID, PERMANENT GRIP.

An assembly of the famous Mueller Clampipe Ground Clamp and a Screw-eye with plastic, insulating grommet. Offered for flat or round cable. **ASK YOUR JOBBER.**

Send for Free Sample & Catalog 810.

MUELLER ELECTRIC CO.

1565 E. 31st St. Cleveland 14, Ohio

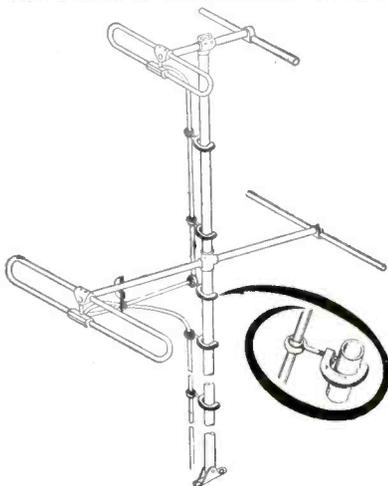

For Originality LOOK TO XCELITE QUICK-CHANGE REAMERS

For Your XCELITE Handles!

Detachable to fit your XCELITE No. 14 Nut Driver or "Combination-Detachable" Screw-driver! Short enough to get in where ordinary reamers can't! Enlarge holes in plastic, sheet metal, wood! See your dealer or supply jobber NOW!


"ANOTHER XCELITE FIRST"

PARK METALWARE CO., Inc.

DEPT. V ORCHARD PARK, N. Y.

Quality Tools PREFERRED BY EXPERTS

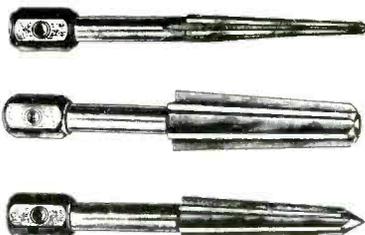FIRST TO USE PLASTIC FOR SCREWDRIVER HANDLES



Available in 3 sizes: 1/8 to 5/16, 1/4 to 1/2, 1/2 to 11/16. Shown above 1/2 actual size.

SERVICEMEN

Espey Radio Chassis are

Easy to Sell— Easy to Install—



#514 AMPLIFIER #513 TUNER

This New Deluxe Custom Built AM/FM Quality Chassis gives you increased Sales in the profitable Chassis Replacement market.

Here is exquisite high fidelity in chassis form that will grace the finest cabinet.

The 513 De Luxe Tuner is easy to install in any console cabinet, old or new, and embodies the latest engineering refinements for lasting high quality at a price that defies competition.

The Espey 513 Tuner employs 10 tubes plus tuning indicator in a super heterodyne circuit and features a drift compensated circuit for high frequency stability, tuned RF on AM and FM plus phono input provision, and separate AM and FM antennas.

Model 514 De Luxe Power Supply-Audio Amplifier is designed specifically to work in conjunction with Model 513 Tuner, and is also used wherever a high quality audio amplifier is required.

With an output of 25 watts, Model 514 features a parallel push-pull output circuit, self-balance phase inverter system, extended range high fidelity response, and inverse feedback circuit.

Write Dept. D2 for your free catalog.

Makers of fine radios since 1928.

ESPEY

TEL. BUTTERFIELD 8-2300

MANUFACTURING COMPANY, INC.

528 EAST 72nd STREET, NEW YORK 21, N. Y.

FOR T-V SERVICING

Investigate the Mega-line of instruments:

MEGA-SWEEP

MEGA-PIPPER

MEGA-MARKER

MEGA-MARKER SR.

Request Catalog

Kay Electric Company

19 Maple Ave., Pine Brook, N. J.

CHICAGO ISOLATION TRANSFORMERS

Three isolation transformers, with 50, 150, and 250-va capacities respectively, have been announced by Chicago Transformer Division, Essex Wire Corp., 3501 W. Addison St., Chicago 18, Ill.

Transformers are suitable either for adjusting high or low line voltages to operate radio, TV, and other equipment on a normal 115 volts, or promoting safer servicing or experimental work on electronic gear by isolating chassis grounds from line grounds. Particularly useful in eliminating shock hazard on ac/dc TV sets. Besides providing a standard 115 volts, the secondaries of these transformers will also supply 125 or 105 volts for use in locating faulty set components.

The units are mounted in compound-filled drawn steel cases, and have a 7' cord with male plug on primary, female plug on secondary.




* * *

TOWERS TV-FM MAST


A tubular, high-tensile, lightweight, alloy-steel mast with a universal mount for TV and FM antennas has been announced by the Towers Corp., 3332 E. 55th St., Cleveland 4, Ohio. Mast is five feet long and can be built to any height with five-foot extensions. Mast and extensions have telescoping ends for joining.

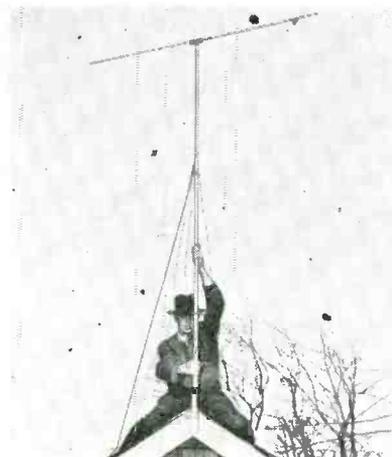Masts are packed individually with guy-wire ring and heavy cotter pin. An 11" base is packed separately; antenna mounting block is packed individually, complete with hardware. Mast and extensions are furnished in either 1" or 1 1/4" diameters, in either irco-sealed aluminum finish or baked black enamel. Hardware is zinc-plated.



RCA SPEAKERS

are priced for replacement needs

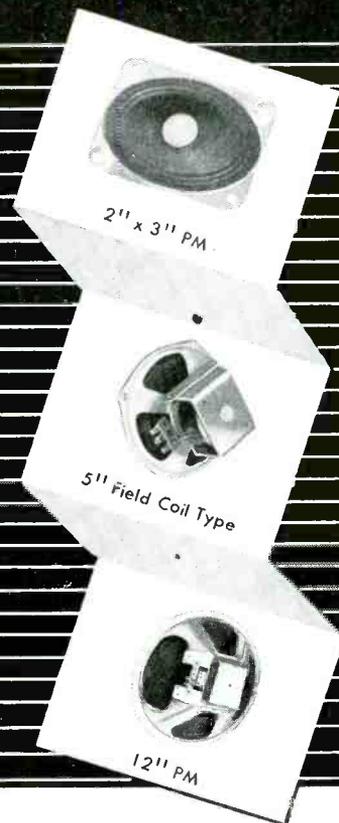

Engineered and manufactured by RCA—this quality line of RCA Speakers is competitively priced... easy to sell. Seventeen PM and field-coil types meet practically all replacement requirements.

When you replace with RCA Speakers, you build extra customer good will...at no extra cost!

Always keep in touch with your RCA Distributor

TURN TO NEXT PAGE



ELECTRONIC COMPONENTS
RADIO CORPORATION of AMERICA
HARRISON, N. J.

NOW

ESTIMATE REPAIRS ON THE SPOT!



- accurate
(Same as large generators)
- pocket size
- economical

A.M. Signal Generator Model #710 F.M. Signal Generator Model #720A

Here are TWO great units that will pay for themselves in 30 days. Helps locate faults quickly and accurately—estimate a repair job or do a complete alignment right on the spot.

Safe for A.C. or D.C. operation. Instrument cases and chassis are completely isolated from power supply. No chance of shock, short circuit, or burnout. Both units complete with individual trimmers for recalibration. Size: 3"x6"x2¾". Weight: 1½ lbs.

MODEL #710 Fixed frequencies of 1500-550-456-465 K.C. Complete with tubes, etc. \$17.95	MODEL #720A Calibration accurate within 1% for fixed frequencies of 9.1, 10.7, 88 & 108 mc. Complete with tubes, etc. \$19.95
---	---

WRITE FOR CATALOGUE 2 S

RADIO CITY PRODUCTS CO., INC.

152 WEST 25th ST NEW YORK 1, N. Y.

RESERVE SPACE NOW FOR THE MAY

Radio Parts and Electronic Equipment Show Issue of SERVICE

MAY 17-20, 1949
STEVENS HOTEL, CHICAGO

Hundreds of extra copies will be distributed at the Show—a valuable circulation bonus for advertisers at a time when buying interest is at peak.

LAST FORMS CLOSE APRIL 25

New Instruments ... Components ... Accessories

RCA MINIATURE TESTPOINT ADAPTER

A miniature test-point adapter, which permits tube-base tests to be made on the tube side of the radio chassis, has been announced by the RCA Tube Department.

Adapter which accommodates all types of 7-pin miniature tubes, is placed in the tube socket and the tube in turn is plugged into the adapter.

NEWCOMB PHONO AMPLIFIER

A 10-watt phono amplifier, P-10, has been announced by Newcomb Audio Products Co., 6824 Lexington Ave., Hollywood 38, Calif.

Power output is said to be 10 watts at less than 5%, over 9 watts at 50 cycles at less than 5%, over 90% of rated output at less than 2%. Frequency response: ± 1 db, 30 to 15,000 cycles. Input impedance, ½ meg; gain, 75 db. Bass tone control range 0 to + 16 db. Treble tone control range — 25 db to + 15 db. Output impedances: 4, 8, and 16 ohms to octal socket. Tubes: One 6SC7, one 6SF5, two 6V6GT and one 6X5GT.




KEMODE SOLDERING IRON

A no-flame, no-electric quick-shot soldering iron, which uses a cartridge for instantaneous working-temperature heating of the tip, that is retained for six to eight minutes, has been announced by the Kemode Manufacturing Co., Inc., 161 W. 18th St., N. Y. 11, N. Y.

Available with six types of tip sizes: pyramid (⅜" and ⅝"); chisel (⅜" and ⅝"); heavy duty (1" and 1½").

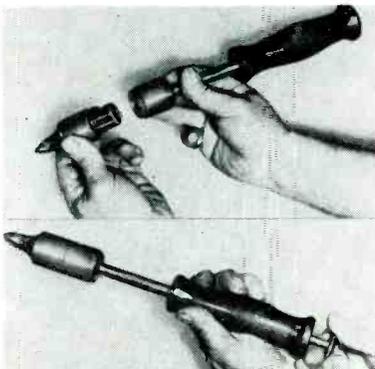In operation, a cartridge is inserted in tip, and a spring plunger in handle is pulled to activate the cartridge.



DUOTONE MICROGROOVE CUTTING NEEDLES

A microgroove cutting sapphire needle has been announced by The Duotone Company, N. Y. C.

ASTATIC EQUALIZER AMPLIFIER

Equalizer-amplifiers, the EA series, for use with the Astatic magneto-induction pickup cartridge, have been announced by the Astatic Corp., Conneaut, Ohio.


One model, EA-1, is for installation in receiver sets and audio amplifiers and provides the necessary equalization and preamplification and bass boost. Another model, EA-2, is self-powered and provides adjustable bass-boost, treble roll-off, and selection of turnover frequency. A third unit, EA-3, is also a self-powered unit, providing bass-boost and equalization.




E-V TORQUE DRIVE KIT

A sales and service kit of torque drive crystal pickup cartridges has been announced by Electro-Voice, Inc., Buchanan, Michigan.

Each kit contains 6 assorted cartridges with replaceable needles (which it is said can be used to replace any one of over 150 standard type cartridges); 4 extra needles and needle holders, and consumer pamphlet. Available in kit A (osmium-tip) and kit B (sapphire-tip).

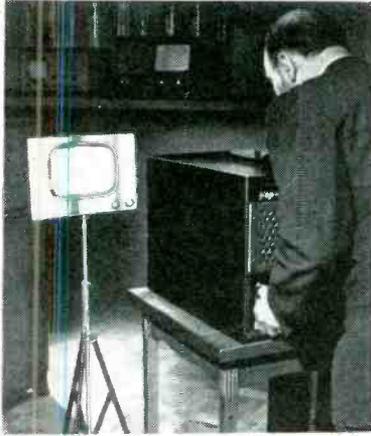FEDCO
MADE IN U.S.A.**POINTS THE WAY
TO NEW PROFITS
WITH THESE 3 TV NEEDS!****FEDCO Pictur-Vu**

Portable mirror and stand makes TV adjustments a simple one-man job. Unbreakable 10 x 14" mirror on an adjustable, collapsible stand. You stand behind the set while adjusting, yet you can see everything clearly in the mirror. Complete with protective bag \$6.00 for mirror
DEALERS' NET

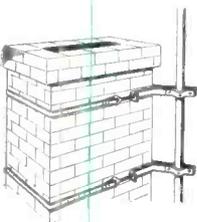
FEDCO**CHIMNI-MOUNT**

Fits any chimney, and accommodates any television antenna mast up to 1 1/2". Rigid, all steel construction, rust-proofed and weather-resistant. One man can easily install. Complete with hardware and strapping.

\$4.95 List

FEDCO**TENNA-MOUNT**

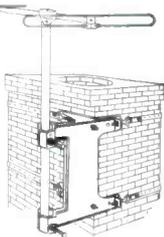One-piece hi-strength aluminum alloy. For high quality and fast installation of TV-FM antenna masts on chimneys, poles, corners. Simply wrap straps around the support and tighten nuts. No special holes needed. Easily installed with regular tools. With two 12-ft. straps, hardware, all rust-proofed.



\$7.50 List

Immediate Delivery!

FEDERAL ENGINEERING CO.

37 Murray Street, New York 7, N. Y.

SECOND ANNUAL**PENNY SALE!****PAY 1¢ MORE AND GET 2!**

For Example: 2 gang .00042mf St'd superhet RMA cut-plate with 2" pulley MV-217. Ship. wt. 1 lb. \$1.49—2 for \$1.50. 30mfd. 150v Electrolytic, new stock.

45¢—2 for 46¢

8mfd. 150v Electrolytic, new stock.

39¢—2 for 40¢

Send for complete **PENNY SALE LISTINGS** of electronic and radio mdse. Prices net f.o.b. our plant. Include postage and insurance.

Universal general corp.

301 CANAL ST. N. Y. 13, WA. 5-9642

NEWS**RCA PROMOTES ELLIOTT, TEEGARDEN, BAKER AND ORTH**

Joseph B. Elliott is now vice president in charge of all RCA Victor consumer products, and L. W. Teegarden has been appointed in charge of all RCA technical products.

Henry G. Baker has become general manager of the Home Instrument Dept., and Richard T. Orth has been named general manager of the Tube Dept.

* * *

CUNNINGHAM NOW SYLVANIA AD AND SALES PROMOTION DIRECTOR

Terry P. Cunningham has been named director of advertising and sales promotion for Sylvania Electric Products Inc. Cunningham will direct advertising and sales promotion for the lighting fixtures, lamp, radio tube and electronics divisions and the Wabash Corp.



* * *

C-D BUYS RADIART

Cornell-Dubilier has purchased from Maguire Industries, Inc., all of the stock of Radiart Corp., Cleveland, Ohio, manufacturers of auto radio vibrators and TV and automobile antennas.

New officers of the Radiart are: Octave Blake, president; L. K. Wildberg, vice president; Verne Mitchell, vice president, and C. A. Staub, treasurer and assistant secretary.

* * *

FRANK LESTER JOINS INSULINE

Frank Lester has been named chief engineer of the Insuline Corporation of America, 36-02 35th Ave., L. I. City, N. Y. Lester was formerly chief engineer for Electronic Corp. of America and Radio Wire & Television Inc.



* * *

HARRY SMITH HYTRON CONTEST GRAND PRIZE WINNER

Harry L. Smith, 25-56 Steinway Street, Long Island City, New York, who won the first prize at the start of the Hytron contest in May, was recently named winner of the grand prize, \$200 worth of U. S. Savings Bonds.



Harry L. Smith receiving the Savings Bonds from Bruce A. Coffin, president of Hytron Radio & Electronics Corp., while Everett Boise, Hytron's commercial engineer in the New York area, looks on.

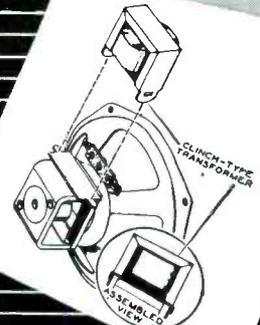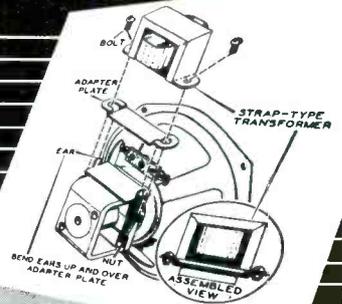
**RCA
SPEAKERS****are easy
to install**

Another RCA first, to speed your service work . . . the universal transformer mounting bracket. Saves time in mounting either clinch-type or strap-type output transformers. Included with all 4", 4" x 6", and 5" RCA PM speakers. Larger speakers include mounting holes on frame according to RMA standards.

Get the facts on RCA Speakers today. Ask for Bulletin 2F892.

**Always keep in touch
with your RCA Distributor****ELECTRONIC COMPONENTS
RADIO CORPORATION OF AMERICA
HARRISON, N. J.**

CHECK!

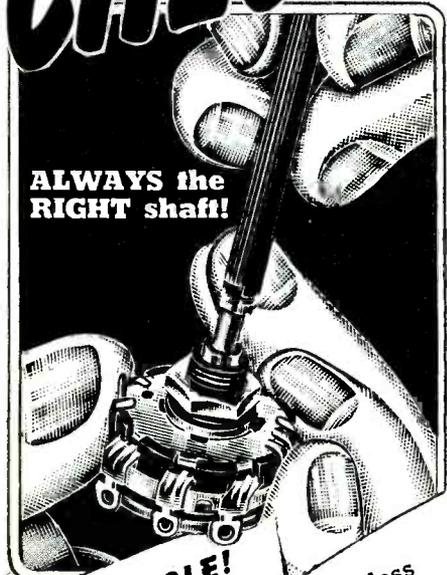

ALWAYS the RIGHT shaft!

NO WIGGLE! NO WOBBLE!
 Clarostat shafts are centerless ground. Fit snugly in bushing. Yet turn so SMOOTHLY!

EASY TO CUT!
 Clarostat shafts are of aluminum. That means easy and quick cutting to correct length.

YOU PICK IT!
 Select the right control — ohmage, taper, tap. Then select the right shaft. All for \$1.25. No extra charge for special shaft!

CLAROSTAT
 Ask your Clarostat jobber for latest catalog. Or write us.



Controls and Resistors

CLAROSTAT MFG. CO., Inc. • Dover, New Hampshire

In Canada: CANADIAN MARCONI CO., Ltd.
 Montreal, P.Q., and branches

JOTS AND FLASHES

FIVE RULES for visual comfort in viewing television were issued recently by the American Optometric Association: (1) receiver should be properly installed with particular attention to the antenna; (2) in tuning, tone setting should be adjusted before turning the picture up to the desired brilliance, and a comfortable balance between steadiness of image and brilliance selected since an unsteady image or too much light results in visual discomfort; intense darkness and bright light in a room with a television receiver should be avoided, a mild, indirect light being preferable (if the room is totally dark there will be too much contrast between the bright screen and its surroundings and if there are bright lights, they will distract); (3) sun glasses should not be worn for television because they adapt vision to unnatural conditions; (4) excessively long periods of close concentration on the screen should be avoided. . . . A three-speed record player which features two pickup arms, one for conventional records and the other for two speeds for 33 1/3 and 45 rpm has been developed by Scott Radio Laboratories, Inc., Chicago. . . . Publication of the *Aerovox Research Worker* has been resumed, and will appear soon. . . . The annual get-together of *Radio's Old Timers* will be held in the South Ballroom of the Hotel Stevens on Monday, May 16, during the Radio Parts Show in Chicago. John O. Olsen, 1456 Waterbury Road, Cleveland 7, Ohio, is president of the group. . . . Stewart-Warner Radio and TV set distribution and production will be handled by a newly created division, the Stewart-Warner Electric Division, which Sam Insull, Jr., will head and Edward L. Taylor will be general sales manager. . . . Henry C. L. Johnson is now with Benton & Bowles as account executive for the electronics group of Crosley. . . . The Video Corporation of America recently appointed five new distributors for their line: Milmar Sales Co., Chicago, Illinois; H. A. Gilliam Co., Houston, Texas; Stan-Burn Radio Electronics, Brooklyn, New York; Regal Radio, Inc., New York City; L. Zelkin, Beverly Hill, Calif, and Commercial Television Corp., Pittsburgh, Pa. . . . William W. Boyne is now general manager of Zenith Radio Corp., New York. . . . Samuel Olchak has been named commercial service manager of Air King Products, Brooklyn. . . . Henry P. Segel is now New England representative for Permoflux. William S. Lee and Paul H. Sweitzer will cover Michigan and Indiana, Illinois (except the Chicago metropolitan area), and western Kentucky, respectively, for Permoflux. . . . W. C. Johnson is now vice president in charge of sales of Admiral Corporation, Chicago. . . . C. S. Craigmile has been elected president of Belden Manufacturing Company, Chicago, succeeding Whipple Jacobs, who resigned to become president of Phelps-Dodge Copper Corporation. Arthur L. Wanner is now vice president and treasurer of Belden. . . . Col. Webster F. Soules, Electro-Voice sales manager recently participated in a month of active service at the Ft. Monmouth Signal Corps Laboratories, New Jersey. . . . The Wheeler Insulated Wire Company, Inc. has moved its plant from Bridgeport to Waterbury, Connecticut.


ADVERTISERS IN THIS ISSUE

SERVICE INDEX—FEBRUARY, 1949

ALLIANCE MFG. CO.	32
Agency: Foster & Davies, Inc.	
AMERICAN ELECTRICAL HEATER CO.	40
Agency: Dudgeon, Taylor & Bruske, Inc.	
AMERICAN PHENOLIC CORP.	30
Agency: Burton Browne, Advertising	
AMERICAN TELEVISION & RADIO CO.	36
Agency: Firestone-Goodman Adv. Agency	
L. S. BRACH MFG. CORP.	41
Agency: A. W. Lewin Co.	
CHICAGO TRANSFORMER DIV. ESSEX WIRE CORP.	28
Agency: George Brodsky, Advertising	
CLAROSTAT MFG. CO., INC.	48
Agency: Austin C. Leachoura & Staff	
CORNELL-DUBILIER ELECTRIC CORP.	Inside Front Cover
Agency: Reiss Advertising	
ELECTRO-VOICE, INC.	31
Agency: Henry H. Splitz Advertising	
ESPEY MFG. CO., INC.	45
Agency: Regent Adv. Agency	
FEDERAL ENGINEERING CO.	47
Agency: Shappe-Wilkes Inc.	
GENERAL ELECTRIC CO.	16, 17, 25
Agency: Maxon, Inc.	
GENERAL ELECTRIC LAMP DEPT.	35
Agency: Batten, Barton, Durstine & Osborn, Inc.	
THE HEATH COMPANY	4
Agency: G. Dean Arend, Advertising	
HICKOK ELECTRICAL INSTRUMENT CO.	42
Agency: White Adv. Co.	
HYTRON RADIO & ELECTRONICS CORP.	5
Agency: Henry A. Loudon, Advertising	
INSULINE CORPORATION OF AMERICA	42
Agency: S. B. Leon Co.	
KAY ELECTRIC CO.	45
Agency: George G. Felt	
KEN-RAD DIV. GENERAL ELECTRIC CO.	1
Agency: Maxon, Inc.	
P. R. MALLORY & CO., INC.	Inside Back Cover
Agency: The Aiken Kynett Co.	
MERIT COIL & TRANSFORMER CORP.	38
Agency: Symonds, MacKenzie & Co.	
MUELLER ELECTRIC CO.	44
PARK METALWARE CO., INC.	44
Agency: Melvin F. Hall Agency	
PHILMORE MFG. CO., INC.	29
Agency: Bas and Co., Inc.	
PHOENIX ELECTRONICS, INC.	36
Agency: Milton Richards	
RADIART CORP.	19, 27
Agency: Ohio Adv. Agency	
RADIO CITY PRODUCTS CO.	46
Agency: Jaman Advertising, Inc.	
RADID CORPORATION OF AMERICA	43, 45, 47, Back Cover
Agency: J. Walter Thompson Co.	
RADIO MERCHANDISE SALES, INC.	44
RADIO SUPPLY & ENGINEERING CO.	43
Agency: Claude E. Whipple	
JOHN F. RIDER PUBLISHER, INC.	23
Agency: Shappe-Wilkes Inc.	
HOWARD W. SAMS & CO., INC.	
Agency: George Brodsky, Advertising	
SIMPSON ELECTRIC CO.	39
Agency: Burton Browne, Advertising	
SPRAGUE PRODUCTS CO.	44
Agency: The Harry P. Bridge Co.	
SYLVANIA ELECTRIC PRODUCTS, INC.	8
Agency: Newell-Emmett Co.	
TELREX, INC.	38
Agency: Consuelo Evans, Inc.	
TRANSVISION, INC.	37
Agency: H. J. Gold Co.	
TRIPLETT ELECTRICAL INSTRUMENT CO.	7
Agency: Western Adv. Agency, Inc.	
TUNG-SOL LAMP WORKS, INC.	21
Agency: E. M. Freystadt Associates, Inc.	
THE TURNER CO.	33
Agency: W. D. Lyon Co.	
UNIVERSAL GENERAL CORP.	47
Agency: Van Diver & Carlyle, Inc.	
WALDOM ELECTRONICS, INC.	40
Agency: E. H. Brown Adv. Agency	

You Asked For It...

HERE IT IS!

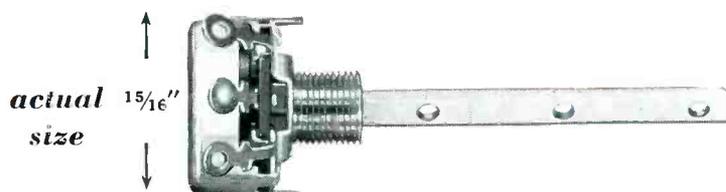

Mallory Midgetrol

The Control You Engineered

Check these points and you'll see why the Mallory Midgetrol has become the *first* control in the business!

- ✓ FASTEST OF ALL TO INSTALL
- ✓ SAVES TIME
- ✓ SAVES TROUBLE
- ✓ SAVES MONEY
- ✓ EASIEST SWITCH TO INSTALL
- ✓ ELIMINATES SAWING AND FILING

First In Quality... Best For Results!

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS
*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

Engineering leadership is behind every

Cunningham tube



RCA Laboratories, Princeton, N. J.
RADIO CORPORATION of AMERICA

CUNNINGHAM TUBES are far more than the end product of a factory. Behind every Cunningham tube are the vast engineering resources of the famed RCA Laboratories. It is here that continuing research in the fields of chemistry, metallurgy, and electron behavior helps to make *good* tubes *better*.

Engineering leadership is one of the reasons why you can be confident that every Cunningham tube

you install in a receiver meets the highest standards of quality and dependability.

Cunningham tubes have enjoyed customer acceptance for over 32 years. Whether it's metal, miniature, or glass, there's a Cunningham type to meet practically every service requirement. Your Cunningham Distributor keeps complete stocks on hand to meet your immediate needs.

SEE YOUR CUNNINGHAM DISTRIBUTOR TODAY



**A QUALITY PRODUCT OF THE
RADIO CORPORATION OF AMERICA**