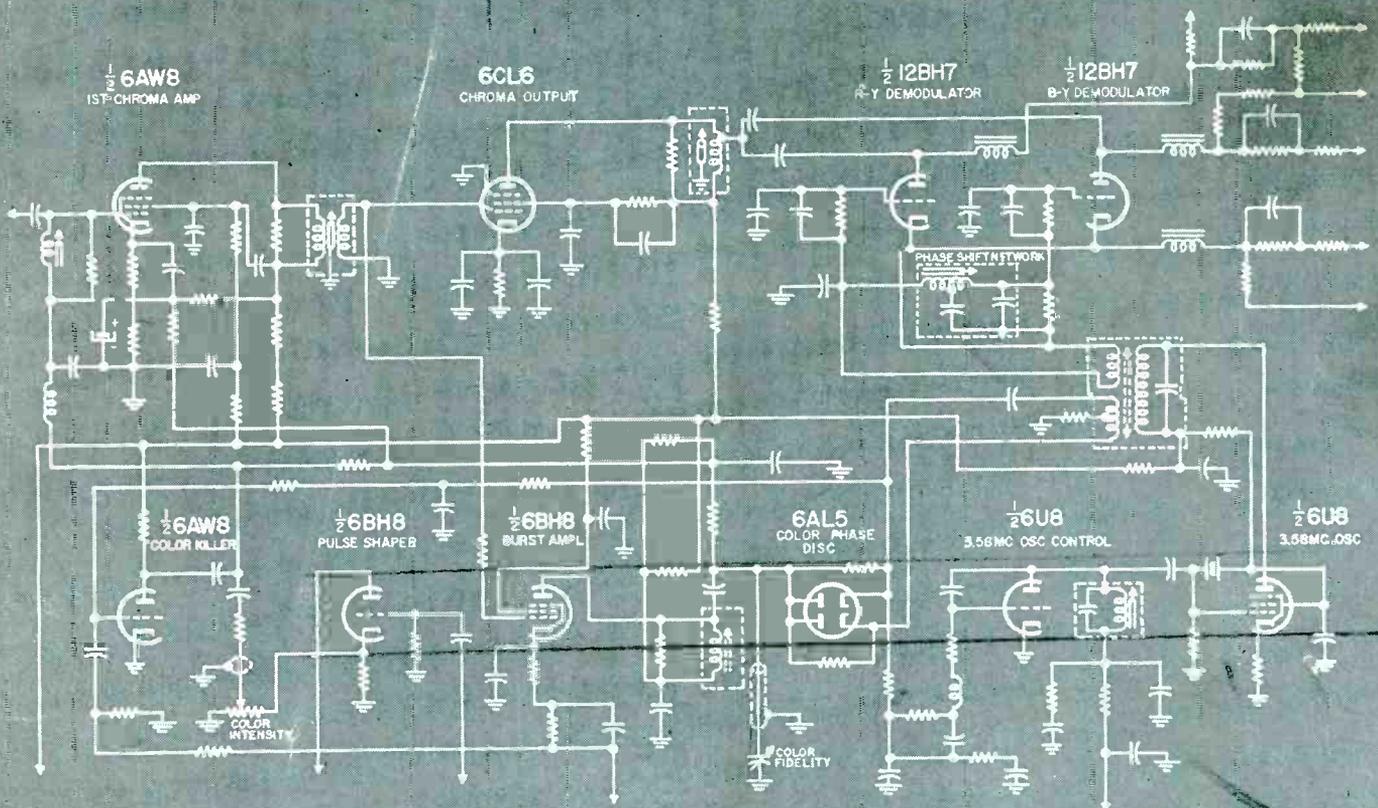


SERVICE

THE TECHNICAL JOURNAL OF THE TELEVISION-RADIO TRADE



Color-TV phase detector and sync color-killer circuitry.
See circuit analysis, this issue

2S 84H 9-
R TURSE
CLARIFHEW LANE
POMPTON LAKES, N.J.
10-57



AR 1 and 2



AR-22



TR-2



TR-4




TR 11 and 12



Everything You Need for Profitable Rotor Sales

CDR ROTORS have EVERYTHING

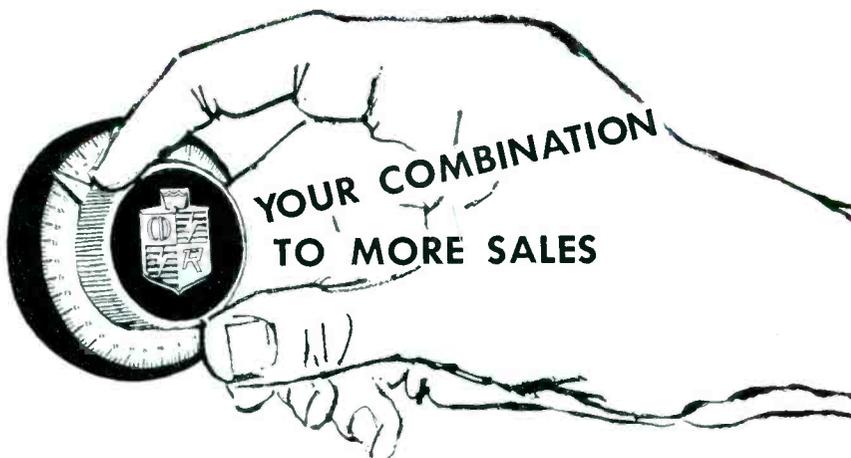

THE COMPLETE LINE
... a model for every need... whatever the application there is a CDR Rotor that meets the situation best!


PRE-SOLD FOR YOU!
The greatest coverage and concentration of full minute spot announcements on leading TV stations in every major rotor market is working for YOU...pre-selling your customers!




CORNELL-DUBILIER
SOUTH PLAINFIELD, N. J.



THE RADIART CORP.
CLEVELAND 13, OHIO

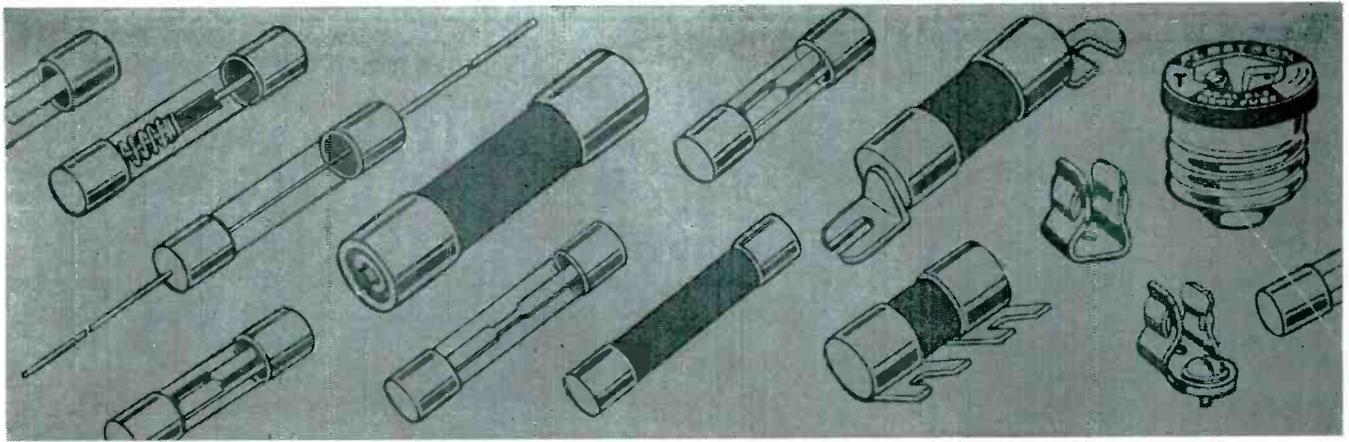

Whenever you need fuses...

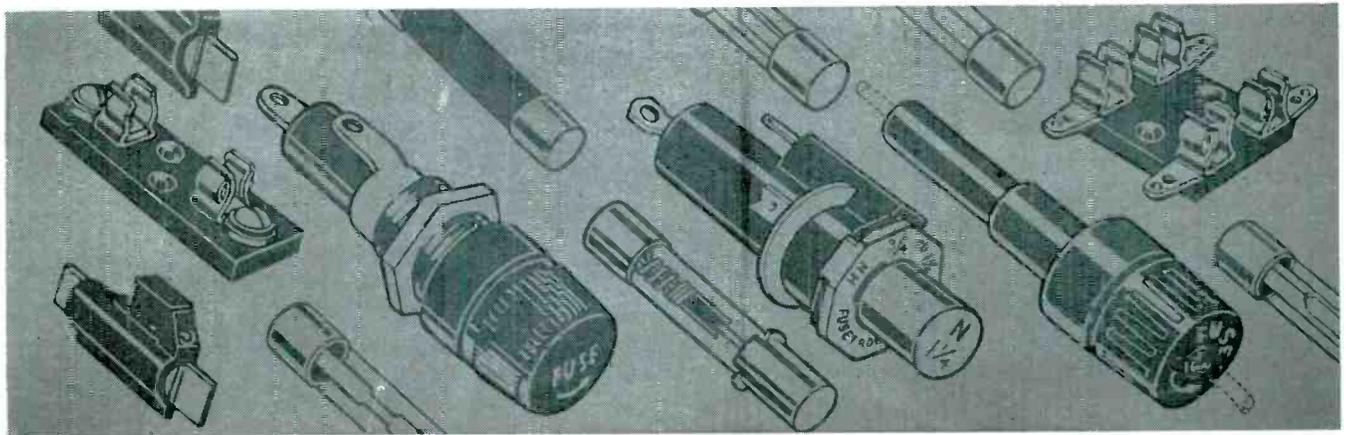

**you'll save time and trouble
by turning FIRST to BUSS!**



S-1156

Makers of a complete line of fuses for home, farm, commercial, electronic, automotive and industrial use.

By relying on BUSS as your source for fuses, you can quickly and easily find the type and size fuse you need. The complete BUSS line of fuses includes: Standard types, dual-element (slow blowing), renewable and one-time types . . . in sizes from 1/500 amp. up—plus a companion line of fuse clips, blocks and holders.

**BUSS fuses are made to protect—
not to blow needlessly**

When you sell or install BUSS fuses—you can be sure that users receive maximum protection against damage due to electrical faults. And just as important, users are safeguarded against irritating, useless shut-downs caused by faulty fuses blowing needlessly.

There are no kicks or complaints from your customers about the operation of BUSS fuses. Servicemen avoid costly, unnecessary call-backs. That's why it pays to rely on dependable BUSS fuses.

**Capitalize on the
BUSS trademark**



The universal trade and consumer acceptance of BUSS fuses is based on the millions upon millions of BUSS fuses used in homes, on farms and in industry over the past 42 years. Sales are easier to make when you handle BUSS . . . the *Known* brand of fuses.

For more information on BUSS and Fusetron small dimension fuses and fuseholders . . . Write for bulletin SFB.

BUSSMANN MFG. CO. (Division of McGraw Electric Co.)
UNIVERSITY AT JEFFERSON ST. LOUIS 7, MO.



ELECTRO DC POWER SUPPLY

0-32 V. up to 15 Amps.
Continuously Variable



**one...
for all**
these applications

6 Volts

Auto Radio Servicing*
Transistor Circuit Design
Plating Operations
Laboratory Work
Battery Charging

12 Volts

Auto Radio and Accessories
Servicing*
Marine and Aircraft Equipment
Mobile Communications
Equipment
Model Train Operation
Battery Charging
Transistor Circuit Design

18 Volts

Tank Mobile Equipment Servicing

24 Volts

Relay Operation
Telephone Circuits
Aircraft Ignition Servicing

28 Volts

Aircraft Equipment Servicing

32 Volts

Farm Radio Servicing
Railroad Mobile Equipment

*Both Transistor and Standard Sets

Special filter circuit broadens range in all low voltage applications. Has all EPL patented features, plus many new ones, available only in the "NFA."

\$195 net

Send for new bulletin today:

ELECTRO PRODUCTS LABORATORIES

4501-V Ravenswood Ave.,
Chicago 40, Ill.

Canada: ATLAS RADIO LTD., Toronto

633



Vol. 25 No. 11

SERVICE

NOVEMBER, 1956

The Technical Journal of the Television-Radio Trade

Including RADIO MERCHANDISING and TELEVISION MERCHANDISING.
Registered U. S. Patent Office.

COVER CIRCUIT

Color-TV Phase Detector-Sync Color Killer (Admiral 29Z1) 22

FEATURES

Editorial	Lewis Winner	9
Cures For Vertical Instability in TV Chassis	Jack Darr	12
How To Boost Low TV Set Voltages	Jess Dines	14
This Month In SERVICE		17
Special Tests For Tube Elements (Instrumentation Development Report)	E. A. Bramsen	18
Hi Fi Amps For PA (Audio Report)		20
Transistor-Tube Tester (Instrumentation Development Report)		21
Color-TV Chassis With New Phase Detector and Sync Color Killer (Cover: With Complete Circuit)	John Schumacher	22
Coax Cables For Community TV Systems	Robert Felber	26
Garage-Door Opener Receiver-Transmitter Circuitry (Service Engineering) ..		28
Traffic Appliance Servicing (Automatic Toaster Repair)	Milton Wallach	34
Replacing Picture Tubes With Aluminized Types (Service Helps)		38
Phono-Tape Repair Tips		59

CIRCUIT DIAGRAMS

Triode Blocking Vertical Osc.	12	Admiral 29Z1 Color-TV (Complete Circuit) ..	24,25
Vertical Integrator	12	Perma-Power Garage Opener Trans.	28
Twin Triode Vert-Osc Output	13	Transformer Phasing Test Circuit	32
Boost Circuit With Two 6V Filament Transf.	14	100-V Boost Circuit With 6V Transf.	33
DC V Output Boost Using Power Transf.	14	Selenium Doubler Conversion to Tripler ..	33
Pentode Output With Feedback	20	Resistive Controls in Toasters	35
Tubes Strapped as Triodes	20	Small Electrolytic Leakage Test-Forming Circuit	39
Ultra-Linear Amp.	20	Transistor Phono. Preamp. Mike Circuits ..	49
Eico 666 Transistor-Tube Tester	21	Perma-Power Garage Opener Receiver ..	51
Transistor Collector-Current Test Circuit ..	21	Unity-Coupled Amp.	55
Admiral 29Z1 Phase Detector	22	Ultra-Linear Cross-Coupled Amp.	55
Admiral 29Z1 LV Power-Fil Circuit	22	Variable Damping PA System	57

DEPARTMENTS

Catalogs, Leaflets and Books	40	Bench-Field Tools	52
Personnel	41	Latest in Audio	54-57
Ten Years Ago in SERVICE	45	TV Parts . . . Accessories	58
Association News	45	Instruments	62
Components	50	Industry News	63
		Tube News	64

Index to Advertisers

Entire Contents Copyright 1956, Bryan Davis Publishing Co., Inc.

Second-Class mail privileges authorized at New York, N. Y.; additional entry at the Post Office, Norwalk, Conn. . . . Subscription price: \$2.00 per year (\$5.00 for 3 years) in the U.S.A. and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.



EDITOR and PUBLICATION DIRECTOR

Lewis Winner

Associate Editor: David E. Pearsall II
Assistant Editor: Robert D. Wengenroth
Editorial Assistant: Eli Cohen
Editorial Assistant: Howard Jennings
Art Director: Anthony R. Alifi
Supervisor, Circuit Diagrams: Michael D. Bellezza
Editorial Production: Astrid Kelly

CIRCULATION DEPARTMENT

Circulation Manager: A. Goebel
Ass't Circulation Mgr.: A. Kiernan

ADVERTISING DEPARTMENT

Advertising Mgr.: Aaron L. Lafer
East-Central Rep.: James C. Munn
Pacific Coast: Leo Sands, Dist. Mgr.

Published Monthly by Bryan Davis Publishing Company, Inc.
52 Vanderbilt Ave., New York 17, N. Y.
Tel.: MUrray Hill 4-0170
B. S. Davis, Pres. Lewis Winner, Vice-Pres



Original components in these and other leading Radio and TV sets since 1948

Advertisement for Radio Receptor Company featuring logos for Raytheon, Crosley, RCA, Sparten, Sentinel, Motorola, Emerson, Hallicrafters, Admiral, GE, Olympic Television, and CBS TV Sets, centered around an image of a selenium rectifier component.

RADIO RECEPTOR

Selenium Rectifiers

That's why they're the best replacements in any Radio and TV circuit!

These famous trademarks represent a few of the many long-time users of RRco. Selenium Rectifiers. The complete list reads like a "Who's Who" in electronics.

Manufacturers' choice in so many models, RRco. "Safe Center" rectifiers are ideal replacements in any set. Your parts distributor can supply you with standard Radio Receptor replacements for sets of all radio and TV manufacturers. Demand "Safe Center" rectifiers and insure the quality of your repair work.



Semiconductor Division

RADIO RECEPTOR COMPANY, INC.


In Radio and Electronics Since 1922

240 WYTHE AVENUE, BROOKLYN 11, N. Y. • EVERGREEN 8-6000

Sprague Salutes the Independent Service Dealer

**ASK YOUR
INDEPENDENT
PARTS
DISTRIBUTOR**

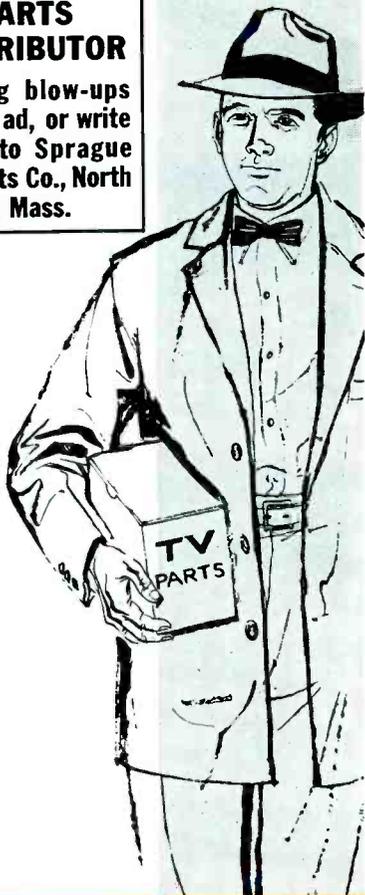for big blow-ups
of this ad, or write
direct to Sprague
Products Co., North
Adams, Mass.



HERE'S TO THE MAN

- ... who assures your enjoyment of the best entertainment in the land.
- ... who competently and conscientiously keeps your TV and radio in top operating condition.
- ... who has become a specialist in his chosen field like your doctor, lawyer, or dentist.
- ... who has the finest service equipment to operate his own business in your home community.
- ... who stands alone ... serving no other boss than you, the customer.
- ... who has earned your patronage, respect, and confidence as an important asset to the community he serves.

YOU CAN DEPEND ON THIS MAN

SPRAGUE®

WORLD'S LARGEST INDEPENDENT MANUFACTURER OF ELECTRONIC COMPONENTS

PROTECT YOUR REPUTATION!

Cut price TV tuners are surplus from a *special* run of a *special design* for one particular model of one particular manufacturer. Chances are overwhelmingly against your ever being able to use a surplus tuner properly—in the set for which it was designed. PROTECT YOUR REPUTATION—don't force match a "bargain" tuner to your customer's set—use only STANDARD APPROVED REPLACEMENT TUNERS (which are furnished you complete with schematic). These will cover over 90% of your service replacement needs. Designed exclusively for service by the manufacturer of more than 19,000,000 TV tuners in use today.

Tell the Customer

“ You should have a STANDARD APPROVED REPLACEMENT TUNER FOR UHF (ultra-high frequency) STATIONS. Often the older and larger stations known as VHF STATIONS (very high frequency) are too far away to give top quality pictures. The STANDARD APPROVED REPLACEMENT TUNER is *the* tuner specially built for UHF conversion. It will accommodate any of the 70 UHF TV Channels! UHF strips can be put into your tuner any time, and because it is so easy for the serviceman, it will cost less in service charges.”

At your jobbers in factory-sealed packages only.

Master
Specialists
in
Tuned Circuits

CHICAGO—LOS ANGELES—BANGOR, MICH.—NO. DIGHTON, MASS.

Export Agent: Scheel International, Inc., Chicago

ORIGINATORS of the Turret Style Tuner
ORIGINATORS of the Standard Cascode Tuner
ORIGINATORS of the Standard Pentode Tuner
ORIGINATORS of the New Neutrode Tuner

Master Specialists in Tuned Circuits
World's Largest Manufacturer of Electronic Components

Standard COIL PRODUCTS CO., INC.

CHANNEL MASTER PUTS NEW SELL IN

DEALERS HAVE SOLD MORE *CHANNEL MASTER* T-W AND SHOWMAN ANTENNAS DURING THE PAST 60 DAYS THAN ANY OTHER ANTENNA DURING ANY 60 DAY PERIOD IN TV HISTORY
Isn't it time you called your Channel Master distributor?

- ★ 2-Page Spreads
- ★ Full-Color Ads
- ★ Full-page Ads



Month after month... all thru the prime TV buying months... this continuing series of sales-stimulating ads is creating loads of lively new prospects... right in your own selling area.

55,000,000
ads building new
customers and sales for you!

NATIONAL ADVERTISING TV ANTENNAS!

"Showman" INDOOR ANTENNA FOR VHF OR VHF-UHF

This smartly styled antenna overcomes consumer objection to ugly "rabbit-ear" antennas. Exclusive "Metro-Dyre" electronic tuning brings in pictures sharp and clear on all channels. Tuning knobs with channel markings just like a TV set makes channel selection so easy. It's the most powerful indoor antenna ever developed . . . and it's backed with an **UNCONDITIONAL MONEY-BACK GUARANTEE**. Engineered for Black and White and **COLOR**.

model no.	description	type
3900	Nobogon & Cell	VHF
3901	Wood & Gold	VHF
3902	Gold & Silver	VHF
3905	Nobogon & Cell	VHF-UHF



Tremendous consumer response emphasizes desire for better TV antennas . . .

and there are no antennas on the market today that compare with these fabulous new Channel Master models.

T-W OUTDOOR ANTENNA

The revolutionary new T-W is the very first TV antenna to use the "Traveling Wave" principle. This unique design electronically reinforces signals . . . eliminates "ghosts" and "snow" . . . rejects all unwanted signals and interference. In gain, front-to-back ratio, and mechanical strength, the T-W is unequalled by any other Broad Band antenna. Engineered for Black and White and **COLOR**.

model no.	description
350	7-element
350-2	7-element stacked
351	5-element
351-2	5-element stacked
352	3-element
352-2	3-element stacked



CHANNEL MASTER CORP.

ELLENVILLE, N. Y.

WORLD'S LARGEST MANUFACTURER OF TV ANTENNAS AND ACCESSORIES

An Open Letter To Independent TV & Radio Service Dealers

Way back in the forties when you had only to combat the suspicion and mistrust of the public — a mistrust created through unfavorable and unfair criticism in press and magazine — the Raytheon Manufacturing Company, recognizing this threat to your existence, started the Raytheon Bonded Electronic Technician Program in a sincere effort to help you survive. This program has helped thousands upon thousands of independent service dealers from coast to coast to establish themselves as reputable businessmen, increase their profits and gain the full respect of their customers.

The program has been carefully controlled. Membership in the Raytheon Bonded Dealer group has been kept limited and selected for 2 reasons: (1) Raytheon wants only the finest service organizations to bear this proud distinction, and (2) it represents a substantial investment for every dealer registered.

Today, the growth of Manufacturers' Service Organizations creates new problems for you in maintaining and increasing the business you have worked so hard to earn. To help you win and keep customer confidence, we are going to lift the quotas on the number of Bonded Dealers we will back. We know that many of you operate to standards that will enable you to qualify for the Raytheon Bond. We recognize your need for this support and gladly offer this helping hand.

We regret that this offer can be made for a limited time only. If you are interested in getting the help of the Raytheon Bond, get in touch with your Raytheon Sponsoring Bonded Tube Distributor right now. He will be delighted to show you how the Bond will help you build your business. And helping you — the independent service dealer — to prosper is something we at Raytheon are dedicated to do.



Receiving and Cathode Ray Tube Operations
Newton, Mass.



The Tremendous Picture-Tube Replacement Market

OF THE 40-MILLION TV receivers in use today, nearly 16-million are three years or older. And 80 per cent of these sets are still using the original picture tube that no longer can provide satisfactory results. Pictures produced by most of these tubes are hazy and lusterless, regardless of the efforts to rejuvenate.

Few of the tubes in the older models were ever capable of providing really bright pictures because of their basic construction. This design problem, coupled with the operational defects resulting from years of usage, have affected the performance of these ancient tubes.

The majority of the tubes used in these early chassis, dating back to '50, are in the 16, 17 and 19-inch family, and today can readily be replaced with the aluminized types that are capable of providing truly brilliant pictures. How such replacements can be made are described in an exclusive technical report in this issue.* Of course, to obtain the best results from the new type picture tubes, the chassis must be in tip-top shape; thus it is important to make a thorough check of the complete receiver by testing every tube and all of the vital components and circuitry, and then replace any defective tubes or parts.

In addition to the need for replacements in the older sets, there is also a sizable market for replacement picture tubes in those receivers that have been installed since '53. The increasing number of hours spent by millions before TV sets has begun to take its toll on the picture tubes. With the long-day long-night schedule of viewing that has become so common, one no longer can expect a tube, with its normal 2000-hour life, to last for years and years.

*Based on the number of initial equipment tubes made for TV sets during the past three years, totaling over 30-million, it has been estimated that at least 5 to 6-million replacements will be required for this market during the next twelve

months. For this operation, the 17-inch tube will be most called-for replacement, followed by the 19 and 21-inch types.

Thus we find that there's a solid need for nearly 18-million picture tubes as replacements that Service Men can *sell* and *install*.

Vital Role of the Standard-Brand Tube

TO BE SUCCESSFUL in this enormous replacement market, there is one rule that must be carefully observed; only quality standard-brand tubes should be used.

Only in the standard-brand plants will we find the thorough engineering planning, development and design facilities; the painstaking production control; the rigid lab, factory and field test setups; and the tough final inspection checks that must obtain to produce the quality product.

The manufacture of picture tubes is so involved, because the tube is a precision display device that requires the utmost care in its assembly.

Even in the apparently simple step of envelope washing, strict adherence to critical chemical and optical specifications must prevail. Cleansing fluids must be absolutely pure; repeated washings must be made under controlled timing and temperature conditions to remove all impurities.

Racks of special mechanical, electrical and electronic test gear, under the supervision of experienced engineering personnel, must be used to check not only every element in the gun, but the glass bulbs, whose contours must be absolutely smooth and scratch-free. In addition, complete tubes must be subjected to a chain of checks that guarantee conformance with all performance standards.

There are terrific opportunities on tap for Service Shops everywhere who take advantage of the tremendous picture-tube-replacement market we now have, and sell and install *only* quality standard-brand tubes.—L.W.

**Servicing Helps*; page 38.

**AS MODERN
AS TOMORROW...**



the

WING →
DIPOLE

and

WING →
DIRECTOR

The **MOST POWERFUL** combination
ever designed

FOUND ONLY IN THE TRIO ZEPHYR LINE



POWER PACKED PAIR

FOR DISTANCE



Zephyr

POWER PACKED THREESOME

FOR EXTREME DISTANCE



ZEPHYR ROYAL

POWER PACKED FOURSOME



FOR THE MAXIMUM

Trio's Zephyr and Zephyr Royal, the leaders of the 1956 season, are brought to you in the 1957 models improved and perfected, and destined to remain the champions. This famous antenna family is expanded by the Zephyr-Mite, newest addition to the Zephyr family. Trio's Zephyr family features the "Wing" dipole—the composite dipole that brought the power of the Yagi to every channel! Add to this the "Wing" director, the revolutionary new director specifically

designed to enhance the power and sensitivity of the "Wing" dipole—and you have a combination that is unequalled in the TV antenna field today for the maximum in performance. The "Wing" dipole and "Wing" director are exclusive features of the Trio Zephyrs—features that make Trio "the choice antenna line."

Trio's recognized quality construction features the internationally famous Insta-Lok clamps—the clamps that 'protect' the element!

TRIO®

Manufacturing Company
GRIGGSVILLE, ILLINOIS

COPYRIGHT 1956 TRIO MFG. CO. EXPORT SALES DIV., SCHEEL INTERNATIONAL INC., 4937 N. Lincoln Ave., Chicago, U.S.A. Cable Address: HARSHEEL

NEW!

CATCHES ALL LEAKY CAPACITORS

IN-CIRCUIT
... CHECKS
ALL COUPLING
CAPACITORS
FOR
LEAKAGE


OUT-OF-CIRCUIT
... CHECKS
ALL CAPACITORS
FOR LEAKAGE
AND
CAPACITANCE

Simpson

MODEL 383A

CAPACOHMETER IN-CIRCUIT

CAPACITOR LEAKAGE TESTER

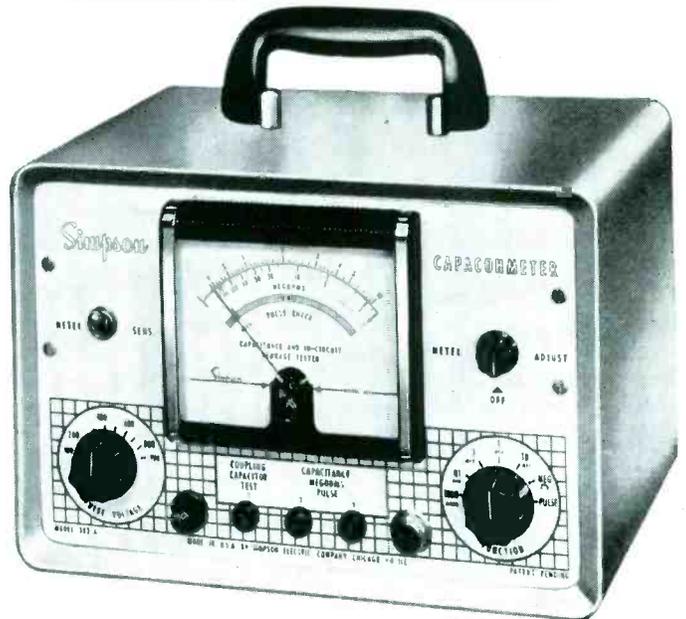

Here is the first *complete* "testing package" for all paper, mica, and ceramic capacitors. With this *one* instrument—the Simpson Capacohmeter—you can: (1) detect most borderline capacitors *in-circuit* by means of the exclusive Simpson *Pulse Test*; (2) measure leakage of defective capacitors, including coupling capacitors, in ohms; (3) determine the capacitance directly, of good capacitors, from 10.0 uuf to 10.0 uf.

With *this* instrument, most tests can be made *in-circuit*. *All* tests are made under load conditions. There is no fussing with bridge circuits and balancing controls. Readings are indicated on a large 4½" meter with better than 10% accuracy. But that's not all. You can use the Simpson Capacohmeter to test for leaky wiring, sockets, and transformers . . . to measure distributed capacitance of wiring to ground . . . to "high-pot" good components . . . and many other tests which you will discover.

Model 383A with leads and Operator's Manual . . . **\$89⁹⁵**

See your Jobber, or Write

SIMPSON ELECTRIC COMPANY

5200 W. Kinzie St., Chicago 44, Illinois
Phone: EStebrook 9-1121

In Canada: Bach-Simpson Ltd., London, Ontario

WORLD'S LARGEST MANUFACTURER OF ELECTRONIC TEST EQUIPMENT



Cures For Vertical

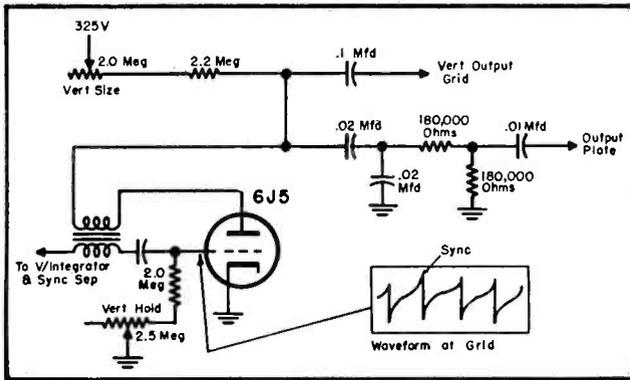


FIG. 1: A TYPICAL TRIODE blocking oscillator used as a vertical oscillator in many TV chassis.

ROLLING, FLIPPING or slow drifts vertically, have been found to be most prevalent on the fringe of the fringe areas, where signals are pretty weak at their best, and subject to fading at any time. This situation aggravates any troubles that might be caused by a vertical sync circuit.

Vertical sync circuits can be extremely simple, but there are some that are quite tricky.

A typical vertical oscillator circuit, with its associated sync feed, as used in '49-'50 TV sets, is shown in Fig. 1. The blocking oscillator uses a triode, 6J5 or its equivalent, and the output of this feeds a pentode output stage, which drives the yoke through an appropriate impedance-matching transformer. Sync pulses are taken from the output of a sync amplifier, fed through a vertical integrator network into the *bottom* end of the grid winding of the blocking-oscillator transformer. As the sync pulses arrive at the grid of the oscillator, they *trigger* the oscillator, so that it runs in sync with the pulses derived from the transmitted signal, locking the picture in place vertically.

The peculiar waveshape of the blocking oscillator lends itself admirably to this type of control; if the pulse arrives at the right time it *fires* the oscillator, so that it runs in sync with the pulses. Let us now assume that the vertical oscillator itself is basically okeh; that is, it can be *locked in sync* by hand, by moving

the vertical hold control. If this can be done, the oscillator and output stage themselves are alright; they are capable of making a 60-cycle wave of the proper frequency, and all they lack is the proper control. This is furnished by the incoming sync pulses. What we've got to do is get them onto the grid, at the proper amplitude. This is the function of the sync separator and (sometimes) the sync-amplifier circuits.

The source of the sync signals is usually the video amplifier plate circuit; from here the full video signal, sync and all, is taken off and fed through some coupling device to the input of the sync separators. (This varies somewhat in different sets.) In the sync separators, the horizontal and vertical sync pulses are separated and fed to their respective oscillators. While the horizontal pulses are usually differentiated and shaped in various filter networks, the slower vertical pulses are fed to the oscillator through a *vertical-integrator* network. This changes the basic pulse (as removed from the signal) to a sharp spike for better control of the oscillator.

Parts values for the integrator network have been standardized; the input resistor is a 22,000-ohm unit, the second and third resistors are of 8200-ohm value, while the capacitors are .002, .005, .002 mfd, from the input end. While *printed-circuit* integrator networks are used in the majority of

sets, some still use separate parts. Whatever shape you find them in, their function is the same; to shape the vertical pulse.

The vertical oscillator is triggered by a spike at just the proper time, to keep the picture locked in sync, vertically. Anything that interferes with the pulse, on its way to the grid, will upset sync and cause the picture to roll or flip. Because of the characteristics of this circuit, by turning the vertical hold control one should be able to roll the picture slowly *downward*; when the wide blanking bar between frames reaches a point about 3"-5" from the bottom of the screen (21-inch tube) it should suddenly snap out of sight. When the vertical hold control is turned the other way, the picture should *never* roll slowly upward; instead, it should suddenly break out, rolling upward so fast that you can see at least two frames on the screen (superimposed) at the same time. This is the normal reaction. Any set which will *not* behave in this fashion needs attention in the vertical sync circuits. Incidentally, this is one area that should be checked on every service call, whether that was the original complaint or not. It takes only four or five seconds and a slight movement of the vertical hold control to tell if the set is working alright. If any trouble is noted, the best thing to do is fix it then and there to avoid a callback. If nothing else, call the owner's attention to it

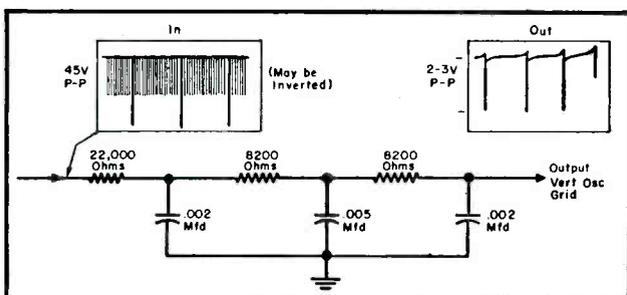


FIG. 2: STANDARD VERTICAL INTEGRATOR. This may be a complete assembly in printed-circuit form or made up of individual components. The output waveform shown appears with the vertical oscillator disabled, either by removing the tube or shorting out. If the signal is applied directly to the grid, this cannot be shorted without shorting out sync; in this case, the large bypass must be shunted from plate to chassis,

Instability In TV Chassis

by JACK DARR

and let him know that he is going to have trouble in that section soon. When it does occur, as it inevitably does, your reputation as a prophet will be considerably enhanced.

Typical Problems and Solutions

In one model, where a vertical-hold problem was encountered, a 6SN7GT served as the vertical sync amplifier and oscillator and a 6AQ5 as the vertical output amplifier. The picture floated up and down the screen, but could be *balanced* in place using the hold control; it would not stay there, however. The 6SN7 was checked and it was discovered that the sync-separator half of the tube was very weak, while the oscillator half was very good. Replacing the tube cured this one quickly.

Another chassis, offering the same symptoms, was found to be fairly stable when first turned on; but as it warmed up, the sync grew worse. This led to a suspicion of a tube with a *hot leakage*. Tubes were checked and replaced, but the trouble persisted. The blanking bar, when rolled into view, had a peculiar look; the normal *hammer-head* of the sync pulse was distorted and compressed. The set was removed from the cabinet and a 'scope was hooked in for a check. At the vertical oscillator grid the sync pulses were visible, but they were very small; they were so small that they were unable to trigger the oscillator with enough authority to make it hold. There was the trouble; now, how to find it.

Tracing the sync pulse, back through the integrator network to the video stage, showed a normal-appearing signal at the video plate and also at the integrator input. The pulse appeared to grow weaker as it passed through the integrator, especially at the second capacitor. This set used a network made up of individual resistors and capacitors; so they were

disconnected and checked. The second capacitor, (with a .002-mfd value) was found to have a very low insulation resistance, although the capacity seemed about normal. After checking a new capacitor *before* installation, replacement was made and the sync pulse popped up at the oscillator grid at least four times as large as before. For oscilloscopic observation of the sync pulse itself at the oscillator grid, the picture must be rolled down slightly with the hold control. If the picture is locked in sync, the pulse becomes part of the little spike above the baseline and will not be visible. The hold control should be set to roll the picture *very slowly* downward, and the 'scope sweep locked to hold the *sync pulse* stationary, while the oscillator waveform moves slowly to the left. In this way, the two will be seen easily and their comparative amplitudes easily checked. On a 5" 'scope, if the vertical oscillator waveform is set up so that it is about 3" high, the sync pulse should be at least 1/2" high for good trigger action.

Still another set with hold trouble had a *pec* integrator network and a

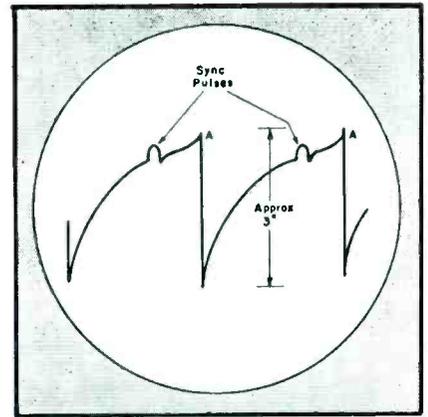


FIG. 3: NORMAL APPEARANCE of sync pulse at grid of vertical oscillator; waveform was made with picture out of sync to show height of sync pulses. With picture locked in, sync pulses will blend into peaks at point A, and disappear. Vertical hold should be adjusted to roll picture *very slowly* downward; 'scope should be locked in on sync pulses for best visibility. Note proportion of amplitude of sync to oscillator waveform.

twin-triode oscillator, using a blocking oscillator. The circuit was similar to that shown in Fig. 4. This time the picture acted peculiarly. Observation with the 'scope showed an oddly-shaped waveform, with a slight bend in the oscillator output. Sync pulses were apparently okeh, as far as height was concerned, but seemed to have little effect on the oscillator frequency.

In this circuit, the cathode of the vertical oscillator is returned to ground through the winding of the oscillator transformer, while the oscillator plate is *dc*-coupled to the output grid. Tracing the circuit with a 'scope showed an unusual curvature of the waveform. At this point the tube was checked. The trouble showed up immediately in the form of a very heavy heater-cathode leakage. Apparently

(Continued on page 49)



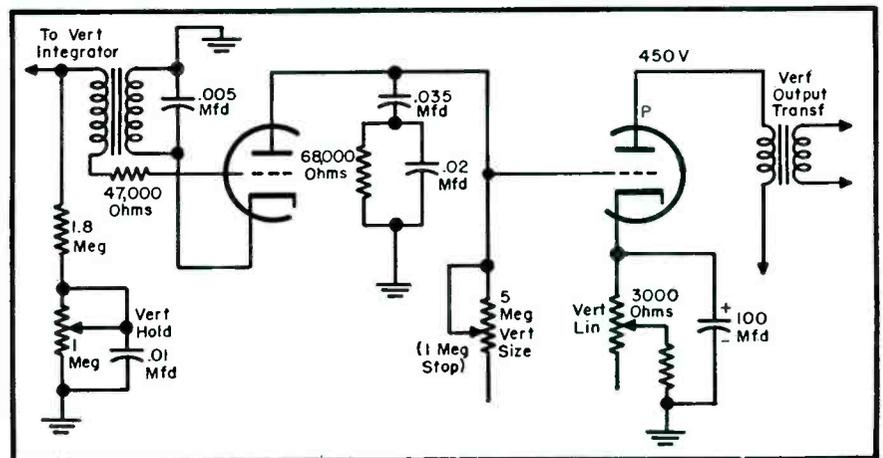


FIG. 4: A TYPICAL twin-triode vertical oscillator-output circuit using a 12BH7. Note that the cathode of the oscillator tube returns to ground through a winding of the vertical oscillator transformer, thus enabling the heater cathode leakage to affect sync.

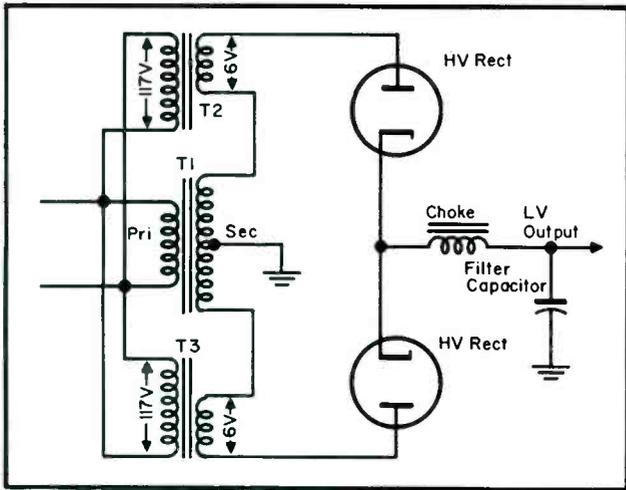

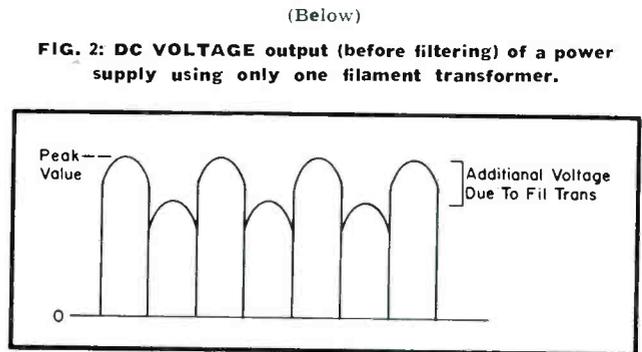(Left)
FIG. 1: TWO 6-VOLT filament transformers connected to a power transformer to produce an additional 10 volts dc.



How To Boost Low TV Set Voltages

By Using Separate Filament Transformers, Unused Power Transformer Windings or Through Alteration of Selenium Circuits

by **JESSE DINES**†

OCCASIONS ARISE where it becomes necessary to raise (or lower) the output of *dc* supplies. These problems occur in intercom systems where more power is needed to drive additional speakers; TV set conversions when increased height and width are needed; and low-voltage supplies which have lost some of their efficiency due to age and deterioration.

The standard methods of increasing *B+* include increase of the size of the input filter capacitor; use of a filter choke with a lower *dc* resistance, and application of buffer capacitors across the power transformer secondary. Other methods that have been found particularly effective include the use of separate filament transformers and unused power-transformer windings, and the modification of selenium rectifier circuits.

Separate Filament Transformers

A pair of small 6-volt filament transformers mounted next to the power

transformer, connected as shown in Fig. 1, can be used to boost low voltage. The 117-volt windings of the filament transformers are connected in parallel with the windings of the power transformer. And the 6-volt windings are connected in series with the secondary of the power unit. If a lower than anticipated voltage results, then phasing must be corrected by reversing leads of the 6-volt windings. (Reverse phasing may be used to advantage when a lower-than-normal *dc*

voltage is needed.) In effect, the use of the additional transformers provides an increase in the turns ratio of the power transformer; one connected to each side of the power transformer to insure proper balancing. The voltage increase which may be expected from such an arrangement is about 10 volts.

If an increase of more than 10 volts is desired, then 12-volt (or even higher voltage) filament transformers may be used. For a 12-volt transformer, twice the output of a 6-volt transformer will be obtained, or about 20 volts.

It is possible to omit one of the boosted transformers and obtain a boosted *dc* voltage output. Approximately the same voltage output can be obtained, since the filter capacitor will charge to a peak voltage value. But there is a disadvantage in this method; the power transformer saturates more and can overheat due to circuit imbalance. Thus, one should exercise caution and avoid this single-transformer method, since resulting excessive overheating can ultimately burn up the transformer.

Some power transformers have an additional 5- or 6-volt winding which

(Continued on page 32)

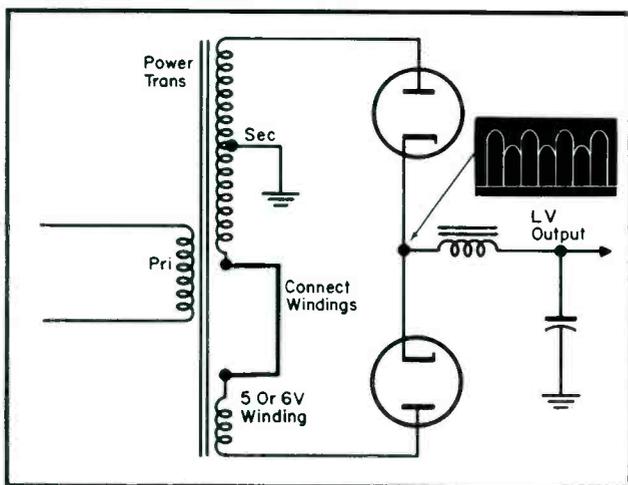



FIG. 3: POWER TRANSFORMER low-voltage winding added to the secondary to produce a greater *dc* voltage output.

†Author of *Servicing TV Sweep Systems*.

THOUSANDS OF SERVICE DEALERS

SATISFY CUSTOMERS
SAVE REPEAT CALLS

MAKE MONEY EVERY DAY with B&K

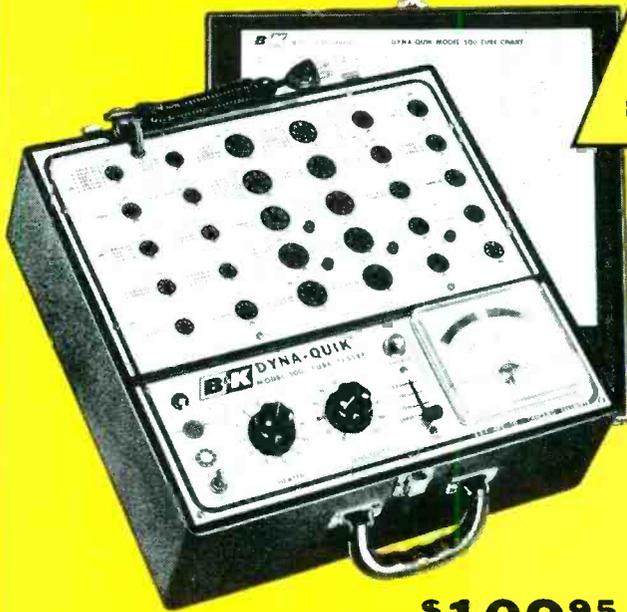

DYNA-QUIK MODEL 500 DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

Tests over 95%

OF ALL POPULAR TV TUBES*— IN SECONDS
It's easy and profitable to check all the tubes in a TV set with DYNA-QUIK—on every service call. Cuts servicing time. Creates more on-the-spot tube sales. Saves repeat calls, protects service guarantee.

DYNA-QUIK 500 *measures true dynamic mutual conductance*, completely checks tubes with laboratory accuracy under actual operating conditions right in the home.

Tests each tube for shorts, grid emission, gas content, leakage, dynamic mutual conductance and life expectancy. One switch tests everything. No roll charts. No multiple switching. Makes complete tube test in as little as 12 seconds. Large 4½-inch plastic meter shows tube condition on "Good-Bad" scale or in micromhos on scales calibrated 0-6,000 and 0-18,000. Used in home or shop, DYNA-QUIK is a proved money-maker!

*Including new 600 mll series tubes.


NET **\$109⁹⁵**

Dyna-Quik 500. Easily portable in luggage-style carrying case. Size: 15¼ x 14¼ x 5¼ in. Weighs only 12 lbs. Has 7-pin and 9-pin straighteners on panel.

DELUXE—PORTABLE

CRT MODEL 400

Tests and repairs
TV Picture Tubes

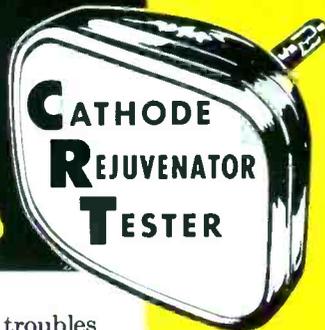

NET **\$54⁹⁵**

Deluxe CRT 400. With 4½-in. plastic meter. Weighs only 5 lbs. Luggage style carrying case. Size: 11 x 7¼ x 5".

Quickly spots and corrects picture tube troubles right in the home, without removing tube from set. Restores emission, stops leakage, repairs interelement shorts and open circuits. Life test checks gas content and predicts remaining useful life. Grid cut-off reading indicates picture quality customer can expect. Eliminates tube transportation, cuts service-operating costs. Also saves money on TV set trade-in reconditioning. Earns dollars in minutes—pays for itself over and over again.

Proved In Use by Servicemen Everywhere.

See your B & K Distributor or send for facts on "Profitable TV Servicing in the Home" and Informative Bulletins 500-400-S.



B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois

It's a *Landslide!*

SERVICE-DEALERS EVERYWHERE
AGREE IT PAYS TO STANDARDIZE ON



COLORTENNAS®

*NON COLOR-BLIND

Here are the reasons:

1. Model for model, JFD NCB Colortennas give finer, more usable performance.
2. Model for model, there is more dollar value in JFD NCB Colortennas.
3. There's a JFD NCB Colortenna for every purse, every purpose, every location.
4. Every NCB Colortenna on a home gives you a satisfied customer—a customer that respects and trusts you.
5. Your reputation goes up when you install JFD NCB Colortennas.
6. NCB Colortennas mark you as a discriminating installer—your customer a discriminating buyer.
7. There's that extra *plus* in JFD NCB Colortennas—performance, appearance, ruggedness, value, packaging, merchandising program, standardization.
8. NCB Colortennas prepare the home for color—give finer black and white.

And to top these reasons—JFD now offers you a fabulous extra—the Colortenna *Sell-A-Bration* Premium Program. Yes, you get extra profits in your pocket with every Colortenna you buy—you get your choice of over 900 brand name premiums... your choice of that long awaited vacation trip to any part of America or Europe.



Why compromise? Colortennas are the antennas for you. See your JFD antenna distributor or write to us direct for complete details.

 **ELECTRONICS INC.**

JFD CANADA LTD. • 51 McCormack Street, Toronto 14, Ontario
JFD INTERNATIONAL • 15 Moore Street, N. Y. C.

for deep-fringe areas
Wonder Helix
Model WX811
40 points

for near-fringe areas
Super-Helix
Model RX511
20 points

for fringe areas
Power-Helix
Model PX911
40 points

for local areas
Junior Helix
Model JX311
10 points

for deep-fringe areas
Shut-Out Helix
Model SX992-SX996
50 points

for fringe areas
UHF 4-Bow Helix
Model UX211
10 points

for fringe areas
Star-Helix
Model SX711
30 points

for local UHF areas
UHF Corner Helix
Model UX411
10 points

THIS MONTH IN SERVICE

NATIONWIDE EDUCATIONAL PROGRAM UNDER STUDY BY INDUSTRY TRADE GROUPS--A hard-hitting industry-sponsored educational plan, that would bring the country's best technical and business talent to service associations across the nation, has been blueprinted by special educational committees of RETMA and NEDA. . . Believing that the advent of color-TV, transistorized chassis and other new developments have created an urgent need for on-the-spot talks and demonstrations, the industry groups propose to provide a pool of speakers and equipment that will be shuttled around the country to every association, large and small. . . Those sparking the idea say that the intensive drive should be of significant value to Service Men, serving to resolve the many technical and business problems that they always face, enabling them to cope with neighborhood problems that will strengthen their position in their community. . . . A key role is being drafted into the plan for distributors because of their knowledge of local conditions and their public relations facilities that are available to promote the program. . . In view of the obligation all have to help the Service Man, the committee's spokesmen said, it is hoped that everyone in industry will support the campaign.

TRANSISTORIZED PORTABLE TV SETS EXPECTED WITHIN TWO YEARS--A bold forecast that industry can expect by '58 portable transistor-TV models that will operate on their own battery-supplied power source, was made recently by the prexy of RETMA. He felt that current problems, particularly in the development of transistor horizontal sweep and high-frequency circuits, should be overcome within the next twenty-four months. Now, he said, transistors operating from a low-voltage battery do not provide enough picture drive for full contrast pictures. . . According to one lab, it is now possible to transistorize vertical deflection systems and the sync circuits; it is claimed that both are practical and comparable to tube circuits in performance.

WIDE-ANGLE 110° DEFLECTION PICTURE TUBES DEVELOPED--The long-awaited aluminized 110° diagonal-deflection rectangular glass-type picture tubes, having an overall length of 14½ inches, will soon be on the market. . . Announcement of the finalized design of the tube was made a few weeks ago. . . The tube's overall length was said to compare with 20 inches for a tube having the same overall diagonal dimension, but with only 90° deflection angle. . . A feature of the new tube is the use of a straight gun with an improved electrostatic focusing-lens system and incorporating a pre-focus structure to maintain image sharpness over the complete screen area. The new gun was also said to eliminate the need for an ion-trap magnet. . . Another design feature of the tube is its neck diameter of 1⅛ inches, which makes possible the use of a deflecting yoke with an increased deflection sensitivity. . . The wide-angle tubes will be available in 14, 17 and 21-inch types.

UHF TV TRANSLATOR DEMONSTRATED--The new translator service that was recently authorized by the FCC to permit small, inaccessible communities to receive big-city TV, was demonstrated a few weeks ago in the 3500-population town of Quincy, Washington. . . The system, picking up a channel-4 signal, radiated 200 watts on channel 78 and delivered a three-millivolt signal 6½ miles away and nearly 2-millivolts 18 miles away. Engineers on the scene reported that the pictures were steady and did not suffer from any local interference. . . Translator systems are scheduled for installation in over 100 areas in the far west.

NEW ASSORTMENT OF COMPONENTS FEATURING FERRITES ON WAY--The unusual magnetic properties of ferrites that have made it possible to build highly-efficient antenna rods and TV fly-back transformers and deflecting yokes, will soon be identified with many new parts. Because of the material's high stability with respect to temperature changes and residual magnetic shock from high ac or dc magnetization and its high saturation, it will be widely used in wide-band transformers, tuners, miniature transformers, choke coils and recording heads. . . Isolators, using low-frequency ferrites, will also appear for use in ultrahigh color-TV to reduce ghost effects caused by reflected signals on the line between the TV set and the antenna.



Special Tests For

That Can Provide Vital Tube

TESTING TUBES for grid emission, often the cause of hard-to-find troubles in TV sets, mobile radio equipment and industrial electronic apparatus.

THE TUBE has been noted as the most frequent cause of failures of radio and TV sets and other electronic devices. How long a tube will last is difficult to guess and impossible to predict with accuracy. It is said that the burn-out of a tube is the most common cause of complete failure. However, filament burnout is not the most common tube failure, not by a wide margin. Most tubes are replaced because they no longer are capable of operating within specified electrical limits. Many tubes are unuseable because of loose elements, bad internal connections, short circuits between elements, gas, broken glass, leakage or grid emission.

To determine if a tube needs replacement, any or a combination of the following techniques are normally employed: (1) each tube is checked in a tube tester; (2) the tubes are left alone if the equipment seems to operate satisfactorily; (3) performance is observed as new tubes are substituted, one at a time; (4) certain tubes are replaced arbitrarily, based on previous experience with a particular type of set or equipment, or (5) as many tubes as the customer will pay for are replaced, on the assumption that the tubes have already been in use longer than their rated life.

When in doubt and cost is not a factor or labor cost to find the defect is greater than new tube cost, all tubes can be replaced. But will this fix the trouble? Not necessarily. Assuming that all new tubes in stock are good, which they seldom are, they are not all necessarily uniform

even if of like type numbers. Some new tubes will perform well in one application and not in another.

One television set manufacturer was recently reported to have a carload of tubes on hand which would not function in the TV sets then in production. They were of the right type number, but were of a different manufacture. The TV set had been designed around the characteristics of a particular brand of tube on hand. Allowance had not been made in a critical circuit for the unexpected variance between brands.

Of course, both brands were rated identically in the tube manuals. However, in mass production tube manufacturers cannot always maintain the closest tolerances without retarding production and raising costs. To overcome these problems the set manufacturer may really mean it when a label is stuck inside the cabinet which reads: "For best results use only X brand tubes".

Prechecking Tests

One test equipment manufacturer carefully prechecks each tube and advises its customers to do so too. A manufacturer of aviation electronic equipment issues a manual to its cus-

tomers which gives detailed instructions on how to precheck tubes, burn them in and then recheck them before installation.

In the interests of greater customer satisfaction and reduction of callbacks it behooves the Service Man to take a new look at tube testing, both old and new tubes.


First, what does a tube tester do? Is a tube tester supposed to be a tube merchandiser or an instrument with which one can determine with some accuracy the relative merit of a tube? It can be both. Only a well-designed tube tester is capable of testing most tube types with any degree of accuracy.

There are tube testers that measure emission, some indicate power output, and some are calibrated to read mutual conductance directly in micromhos.

Some testers measure the characteristics of dual triode tubes with the elements in parallel, on the assumption that both halves deteriorate almost equally, or that if the tube tests oke neither half can be far below allowable tolerances. In general, such a test may be adequate, but not so in critical circuits where each tube half is used independently or where both halves must be almost identical.

In one general-purpose tube tester being readied for production, dual triodes will be paralleled for grid testing, connected in series for emission test, or both halves can be checked independently if desired.

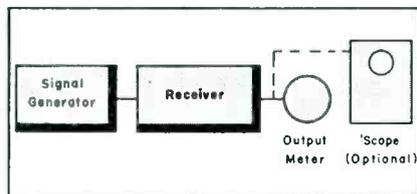It is a safe assumption that a tube rejected by a conventional tube tester as having low emission, mutual con-



TUBE TESTING system most applicable to communication receivers.

Tube Elements

Performance and Reliability Information

by E. A. BRAMSEN

Chief Engineer
Seco Manufacturing Company

ductance or power output should no longer be used. Even if it is still operative in the equipment in which it was used, the fact is that its performance is out of electrical limits and its future life expectancy is short. In addition to merit, most tube testers check for interelement shorts and some are provided with a gas test feature.

One method that is used for determining if a tube is nearing the end of its life is to test it first at rated filament voltage and again at 10% or more below rated filament voltage. If the merit reading is far below allowable limits at the lowered filament voltage, the tube should not be expected to last much longer.

If a tube checks out on a conventional tube tester as being satisfactory, it is not a positive indication that the tube will operate satisfactorily in all applications. For example, the tube's performance may taper off or a short may develop after extended use. Hence, a tube preheating rack on which tubes are warmed up before testing can be used to help detect such faults.

However there is another phenomenon which occurs in new tubes as well as old ones. It may be present as soon as the tube reaches operating temperature or after an extended period of operation. In some circuits it may not cause appreciable trouble; in others it may cause hard-to-find troubles and in some instances causes serious circuit malfunction.

This phenomenon is called *grid emission* and is common in high gain tubes like the 6AK5, 6KB6, etc. It

is a common trouble in TV sets, mobile radio receivers, electronic control devices and some types of computers.


The control grid in a high-gain tube is necessarily close to the hot cathode. Sometimes some of the cathode coating or impurities get on the grid. The hot cathode also warms up the grid and under some conditions the grid performs like a cathode and emits electrons too. This causes current to flow in the grid circuit in a reverse direction which can upset bias conditions and cause the tube to operate in an undesired portion of its characteristic curve and in some circuits to behave far from the intended manner.

In a TV receiver, a single tube with grid emission can cause instability, overloading and insensitivity. When a *vhf* mobile radio receiver loses sensitivity after a period of operation, the trouble can often be traced to a tube with grid emission. In fact, one tube with grid emission can affect the bias on several tubes tied to the same *agc* buss.

If the condition is very severe, it can sometimes be detected with a tube tester which has a gas test feature. However, this kind of test normally is not sensitive enough to find this fault. To take care of this problem a special type of tester for detecting grid emission has been developed.

The tester consists of a *dc* amplifier with an electronic eye as an indicator. Both the tube under test and the *dc* amplifier are biased to cutoff. If the tube has grid emission, the bias drops and causes the eye to open.

To cut down callbacks and to

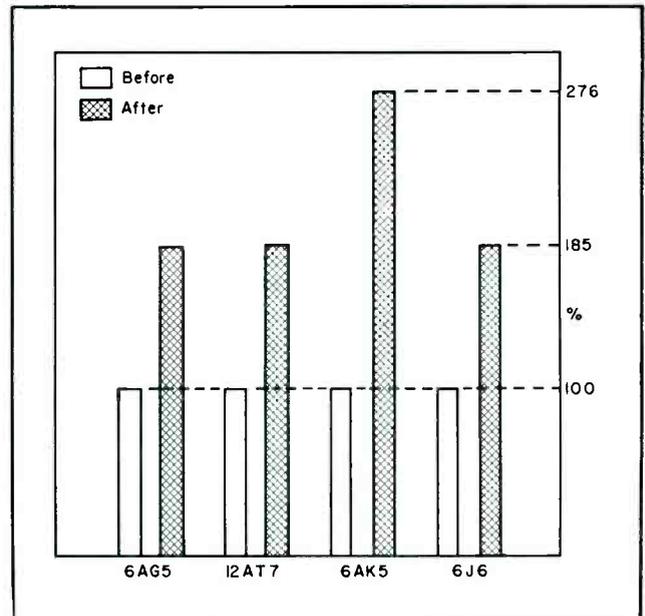

IMPROVEMENT in tube life can be attained by more rigid tube testing before placing new tubes in service, as shown in this bar graph. For example, when 6AK5s are pre-service tested for grid emission, the average life of the tubes, which test okeh when new, can be effectively extended 176%. New tubes with slight grid emission may operate satisfactorily when installed, but it has been found generally fail to last as long as tubes which do not have this defect.

build a better reputation with customers, more comprehensive tube testing is a good idea. It is time well spent because it really saves time that is often spent doing a job over.

As tubes are put into stock they can be checked for merit and shorts and applicable types can also be checked for grid emission. It might be smart to mark the tubes to indicate that they have been pretested.

Lab methods can be employed in the shop when servicing radio and TV receivers. After tubes have been checked on a standard tube tester for merit and shorts, applicable types can be checked for grid emission and interelement leakage with a grid circuit tester. Then to assure maximum performance, new tubes, known to be good, may be substituted one-at-a-time noting any change in performance, by observing a *vtvm* or scope tied into an appropriate receiver circuit. This is the best test, of course, of tube performance at any given time. After allowing the set to operate a couple of hours, a recheck of all applicable tube types for grid emission may reveal interesting results.

More critical and comprehensive tube testing is becoming a necessity as b-w TV set manufacturers try to get more performance out of fewer

(Continued on page 37)

Hi-Fi Amplifiers for PA: Features of Circuits For Small and Large Systems



IN COMMERCIAL SOUND, *quality* is of the essence, because any deviation from uniform response can develop the same kind of trouble as a poor loudspeaker or microphone.

However, this does not mean that amplifiers designed for *hi-fi* application are necessarily good public address amplifiers. Amplifiers for public address are really specialized equipment and, while many high-fidelity amplifiers suit the purpose admirably, one must exercise great care in making a selection.

It is important, initially, that the amplifier carry all of the facilities that will be necessary for public-address work. It should have microphone inputs of the correct impedance and level for the microphones to be used. You may elect to have a separate preamp and power amplifier, or a combined unit to serve the purpose, according to the kind of application in mind. If all the jobs you

(Right)

FIG. 1: STRAIGHT pentode output circuit with overall feedback. Amplifiers with this output are not satisfactory for commercial sound.

FIG. 2: TUBES strapped as triodes, as shown, are well suited for pa work; but the output from amplifiers with such a circuit may be inadequate for some jobs.

FIG. 3: THE ULTRA-LINEAR approach, which splits the difference between pentode and triode operation; it affords good power for the tubes used, and is well suited for pa work.

are likely to do call for a compact and readily portable arrangement, then the single unit is probably the best bet. But on some large installations it is an advantage to have a separate preamp so that the control

point need not be located in the same position as the power feed to the loudspeakers.

The control or preamp end of the amplifier should provide for independent gain control for as many microphone circuits that may be required; separate bass and treble control (there is usually no need for phono equalization in the detail required for high-fidelity systems); and possibly a master gain control.

The amplifier output should provide impedances of 4, 8 and 16 ohms, which are particularly suitable for small jobs and also a 70-volt constant-voltage line output. Variable damping is of no particular advantage to the public-address man. It is an additional control that can cause trouble by being incorrectly adjusted or overlooked. However, if the circuit is a good one, it is not a serious disadvantage; the variable damping control can simply be left at the maximum damping position and then dismissed from the control program.

Output Stage

The power output stage should supply sufficient power to handle all the jobs for which the amplifier is required. As to frequency, a deviation of as much as 1 db between 20 cps and 20 kc is quite acceptable.


However, amplifiers in which there are no specifications for frequency response or distortion may not be good enough; failure to provide such data often indicates that the manufacturer does not make a practice of measuring his frequency response or distortion. This can mean that the frequency response may be almost anything.

Fixed Damping Factors

If an amplifier has a fixed damping factor, it should preferably be greater than 5; although, provided the damping is relatively high, it is not critical for public-address work.

There are some amplifiers on the market that might appear to give a satisfactory performance according to the foregoing information; they may have a 70-volt line output provided. But the amplifier may really have been designed as a low cost model for the high-fidelity market and the

(Continued on page 54)

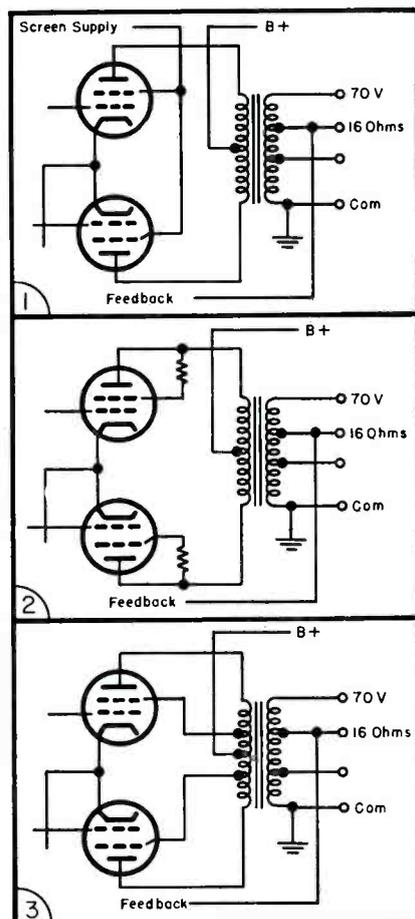

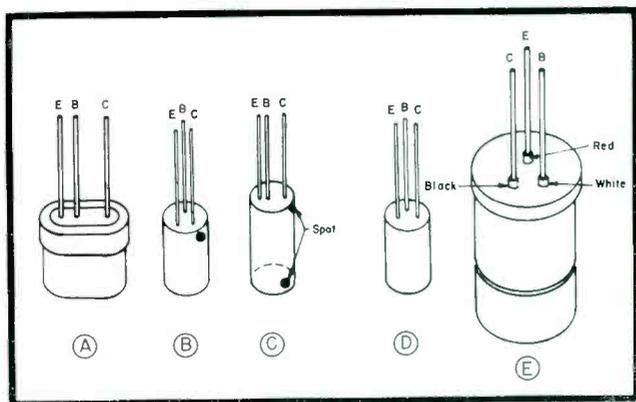


FIG. 1: ASSORTED TYPES of npn and pnp transistors. A = 2N34 type; B = 2N47/2N105 family; C = 2N37, 2N108, HD-398, CK-721, TS-161 group; D = 2N41/2N204 series and E = 2N156/2N158.

No LONGER can the transistor be considered as purely an experimental plaything or just a lab item. Stepped-up production of all-transistor portables and table-model radios, as well as, car radios and phono-amplifiers, have changed that picture.

This trend has resulted in the design of instruments that can check the variety of transistors now being used. The newly developed designs indicate that it is no longer feasible to use the ohmmeter as a transistor testing device, since they normally generate heavy currents (1000 milliamps on the R x I scale) and such current can permanently change the characteristics of a transistor under test. Another

inherent disadvantage of the ohmmeter check is that the transistor is a non-linear device and its apparent resistance can vary widely as a function of the voltage across it. Because of this non-linearity different readings will be obtained on different scales of the same meter or when the reading of one multimeter is checked against the reading of another.

Testers now available usually check for opens, shorts, and transistor gain. Some units incorporate separate battery supplies for the transistor test, while others utilize the main power source of the tube tester portion of the instrument. A tester¹ that uses line voltage is illustrated in Fig. 2. This instrument makes use of one of the most significant characteristics of a

¹Eico 666.

Transistor-Tube Tester

Provides Leakage Measurements of Transistor Collector Current and Direct Reading of Current Amplification Factor

transistor, namely the collector current that flows when the emitter is grounded and no signal is applied to the base. This current depends upon the temperature, resistivity of the germanium, the resistance from base to ground and the extent of contamination on the surface of the transistor; it is comparable to the grid current that flows in a tube and is equally undesirable. The circuits used for this test are shown in Fig. 3.

The figure of merit can also be measured; this is the common emitter current-amplification ratio. Various symbols are used to denote this quantity; β (beta), α_{cb} (alpha cb), h_{21} and h_{re} . Using beta as the quantity, we find that it is related to the common base current-amplifica-

(Continued on page 48)

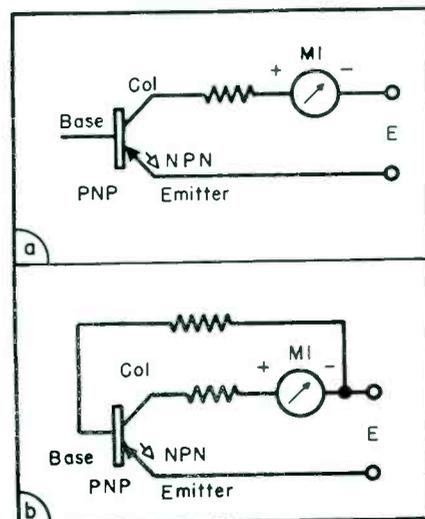
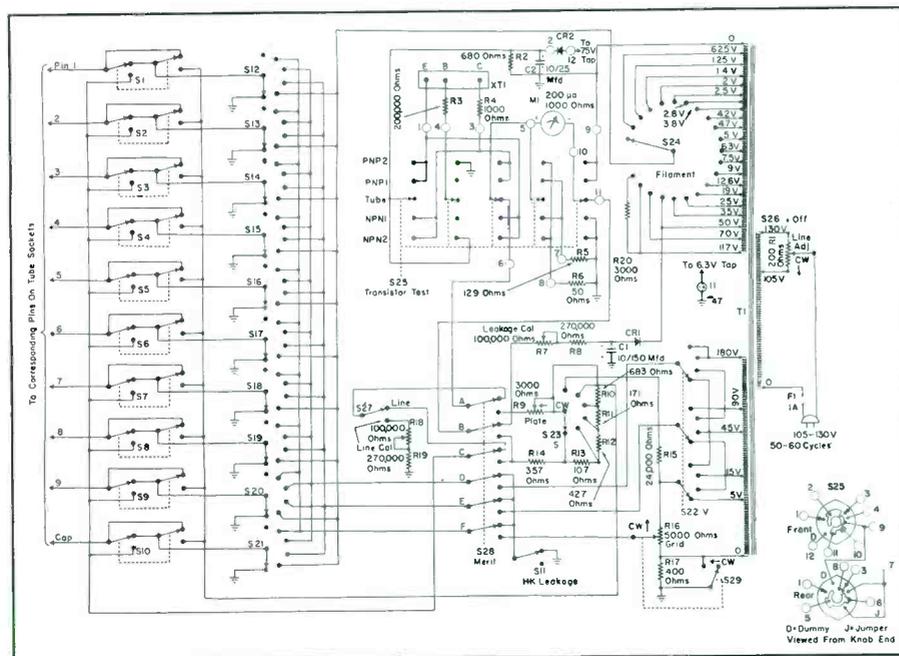


FIG. 2 (left): CIRCUIT of Eico tube-transistor tester.

FIG. 3 (above): Test circuits designed to reveal transistor collector-current information.

COLOR-TV Chassis with New Phase Detector and Sync Color Killer

[See Front Cover and Pages 24 and 25 for Complete Diagrams]

IN THE COLOR-SIGNAL producing circuits, changes are apparent in the subcarrier phase detector, oscillator control tube, and color killer circuits. A 6AL5 color phase detector included in our new line of color models¹ represents some new ideas in balanced phase detectors. It eliminates the balancing control, gives an output independent of any non-symmetry in the incoming burst signal and has twice the gain of the previous more conventional phase detectors. The previous phase detector consisted basically of two peak detectors fed by burst 180° out-of-phase, to which was added a common reference voltage from the sub-carrier crystal oscillator. This circuit (when viewed from its control voltage or output terminal; Fig. 1) shows that the two detectors and their loads are in parallel with one

by **JOHN SCHUMACHER**

Engineering Department
Admiral Corp.

another. Thus it is necessary that the loads for both detectors be matched or balanced, (original circuit had balancing control) and the output voltage should be equal to one-half the voltage difference between the two detectors. The new phase detector

This article, prepared as a supplement to the *Circuitry Report on the Admiral Color-TV Receiver*, published in March, 1956, SERVICE, which detailed the fundamental engineering principles behind the receiver, offers an analysis of a refinement of the original design that has been included in a new color chassis.

system also consists of two peak detectors; however, they are fed with single-ended burst and sub-carrier 180° out of phase, and when viewed from its control voltage or output terminal, (pin No. 1 of 6AL5) the two load resistors are seen to be in series to ground. These changes have been found to produce the following advantages:

- (1) The values of the load resistors no longer need to be balanced and thus no balancing control is needed.
 - (2) As the two loads are in series the output voltage is equal to the actual voltage difference between the two detectors.
 - (3) As the burst is fed single-ended into both plates of the two detectors, the system only
- (Continued on page 36)


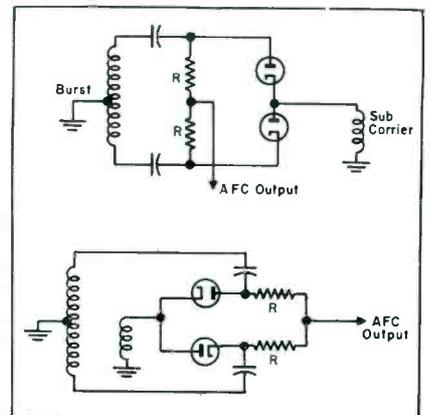


FIG. 1: PHASE DETECTOR circuits. Type shown below is standard, which when viewed from control voltage or output terminal reveals that the pair of detectors and their loads are in parallel with one another and must be balanced. At top, circuit of improved system is shown. Load resistor values do not have to be balanced here and thus no balancing control is required.

FIG. 2 (LEFT): LV power and filament supply circuit of Admiral 29Z1 color-TV receiver diagrammed on pages 24 and 25.

¹Admiral 29Z1

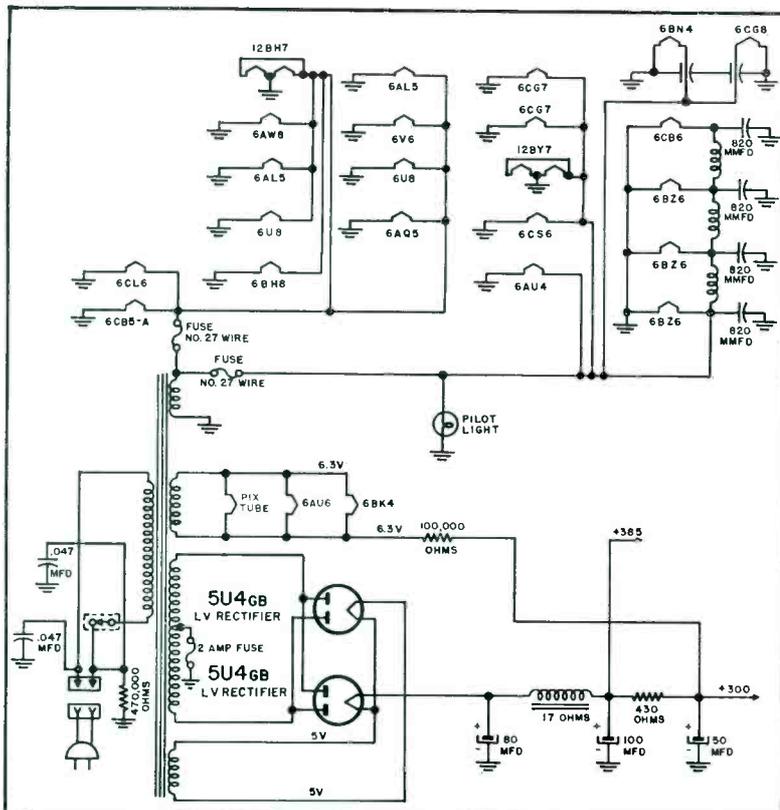


New gift idea!

... Terrific TV traffic-builder for Christmas!

remote CONTROL INSTANT TUNER for TV!

changes channels from your easy chair!

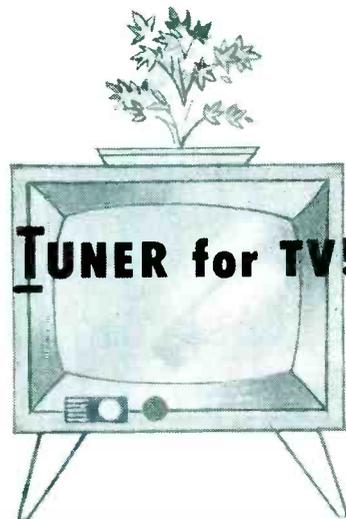

DON WILSON—RADIO AND TV'S GREATEST SALESMAN WILL BRING CUSTOMERS IN DROVES!

Don Wilson, one of America's long-time favorite radio and TV announcers, will lend his strong support to help you sell **I-T** Remote Control Instant Tuners on television. So place your order now for a big stock of **I-T's** and capitalize on this big advertising campaign . . . timed for Christmas.



Goes On Practically Any Set!

The **I-T** Remote Control Instant Tuner is engineered to go on practically any set—new or old. Your market is wide open!

No Installation Problems!

Customers can install **I-T** themselves in less than 3 minutes! It's easy—no tools needed—no electrical connections. And, there's no service problem!

HERE'S HOW **it** SELLS!

I-T sells like hot cakes! All you have to do is demonstrate it—and you'll sell **I-T's** by the bushel! Almost every TV set owner is a red hot prospect. IN ADDITION—**I-T** is the perfect gift for every occasion—Christmas, wedding, housewarming! You name it—and you'll sell **I-T**!



I-T IS SOLD AND FULLY GUARANTEED BY


THE ALLIANCE MANUFACTURING CO., INC., ALLIANCE, OHIO

(Division of Consolidated Electronic Industries Corp.)


In Canada—Alliance Motors, Schell Ave., Toronto, Ontario

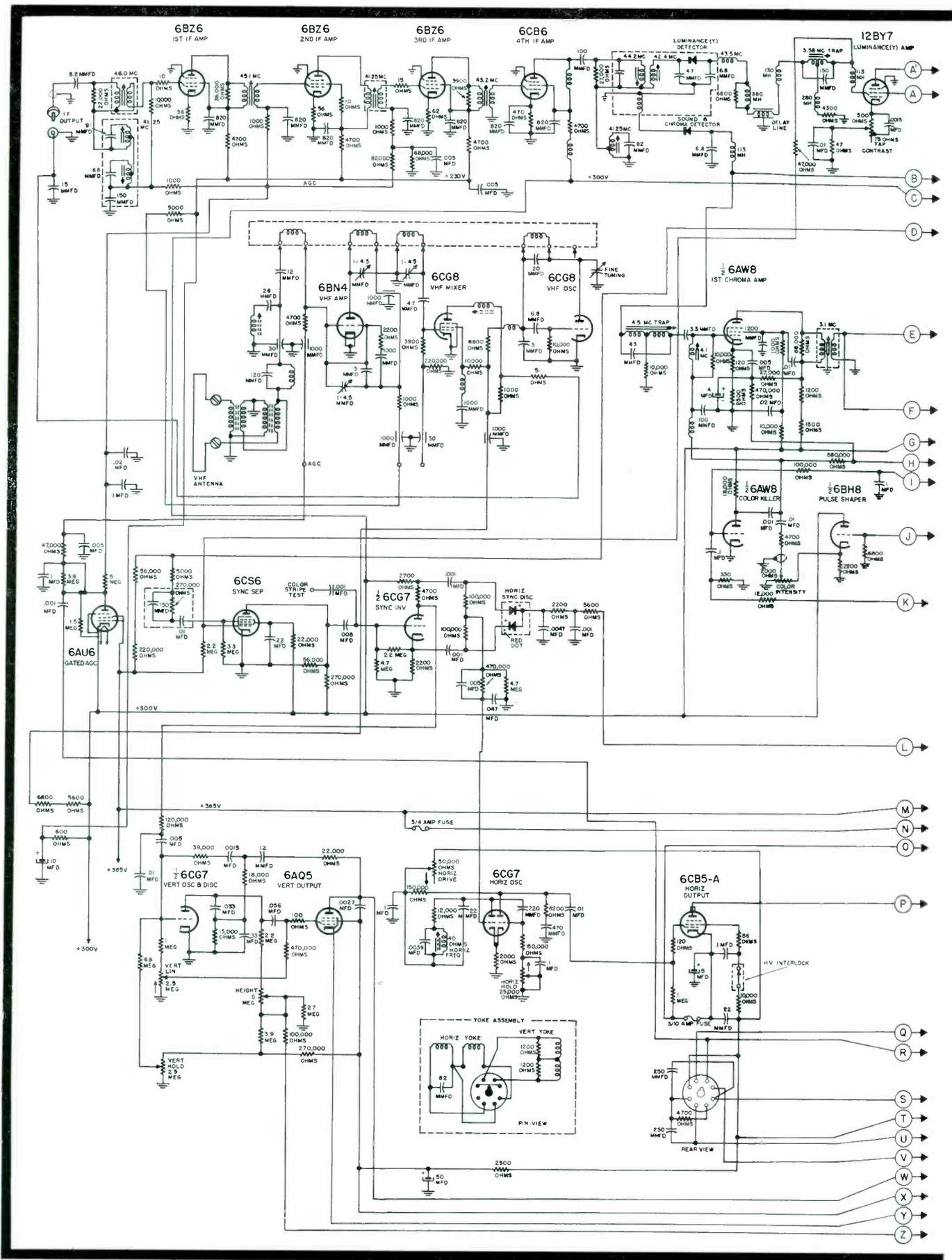WRITE, WIRE, OR CALL NOW FOR INFORMATION ON HOW YOU CAN ORDER and PROFIT with **I-T** Remote Control INSTANT TUNER!






COMPLETE CIRCUIT of Admiral 29Z1 which

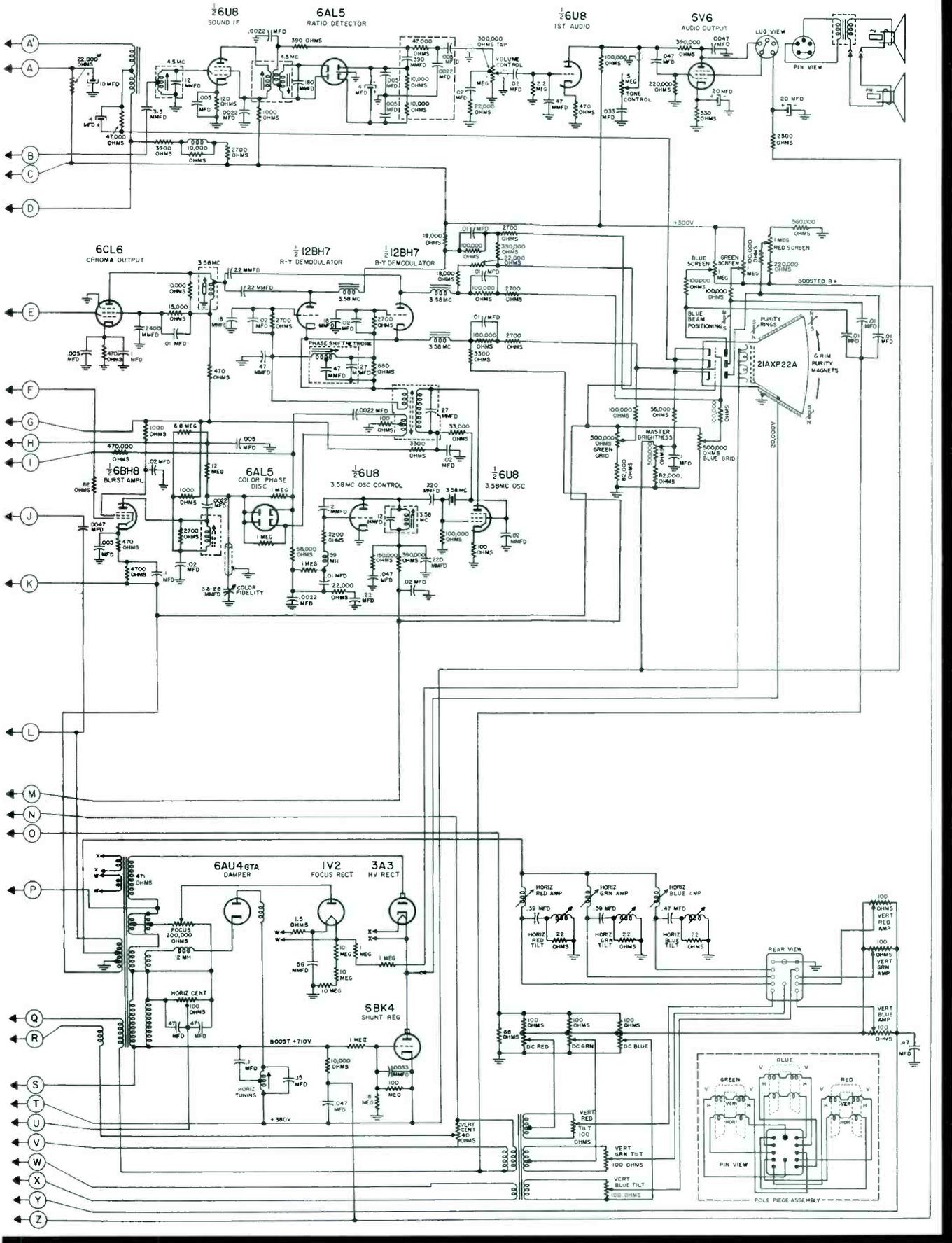

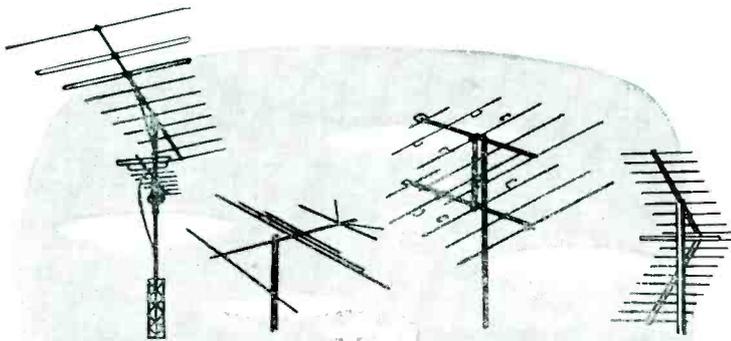features a new phase detector and sync color killer.



UHF-VHF ANTENNA DIGEST

DESIGN • APPLICATION • INSTALLATION • SERVICE

Coax Cables For Community-TV Systems

SEVERAL YEARS AGO, as the wonders of television became a household necessity for those in the larger metropolitan centers, residents of the fringe areas were still struggling with TV pictures that ran a poor second to the first motion pictures. Those who were willing to invest in an antenna system, which in many cases exceeded the cost of the receiver, were privileged to watch snowy, fading pictures, which often disappeared completely for a period of time ranging from minutes to days. Strangely though, certain persons in that same area were blessed with outstanding reception which their neighbors couldn't enjoy.

From a situation such as this sprang the first community-TV system. Ingenious Service Men were able to connect two or even three ad-

by **ROBERT FELBER**

*Products Manager, Community TV
Amphenol Electronics Corp.*

joining TV receivers to the same antenna system, and it wasn't long before the idea of a wired community took hold.

Hotel and apartment-house master antenna systems were already being installed in large metropolitan areas, with varying degrees of success. Why not use this principle for house-to-house TV signal distribution? With high hopes and a strong heart (and constitution), a few rugged individuals embarked on such a venture which was shortly to change the living habits of these people who lived

on the TV frontier, particularly those in hilly terrain where signals were usually blacked out.

Little did these Service Engineers realize the many problems with which they would be confronted. Nothing had ever been done on such a scale, particularly at these high frequencies and with a medium as fickle as television. Aside from the fact that the electronic equipment had not been designed for that specific application, cable problems which were previously unheard of, were met.

Having selected 75-ohm cables as the standard for a system, it was next necessary to select those which offered the lowest attenuation at a price which would make the operation financially practical. Since the signals were usually picked up outside

(Continued on page 42)



OUTDOOR CABLE test facilities where coax performance is studied.



COAX CABLE quality control lab.

CLIP FOR REFERENCE

MORE

HOTPOINT TV TUBE CHARTS


Hotpoint TV, America's newest major TV line, publishes this tube chart as a service to servicemen.

Complete service information on all Hotpoint TV sets is now available from Hotpoint TV Distributors. If you have not yet ordered yours, clip this chart for temporary reference, then contact your Hotpoint TV Distributor immediately.

*Published as a service
to servicemen by*


Hotpoint Co.

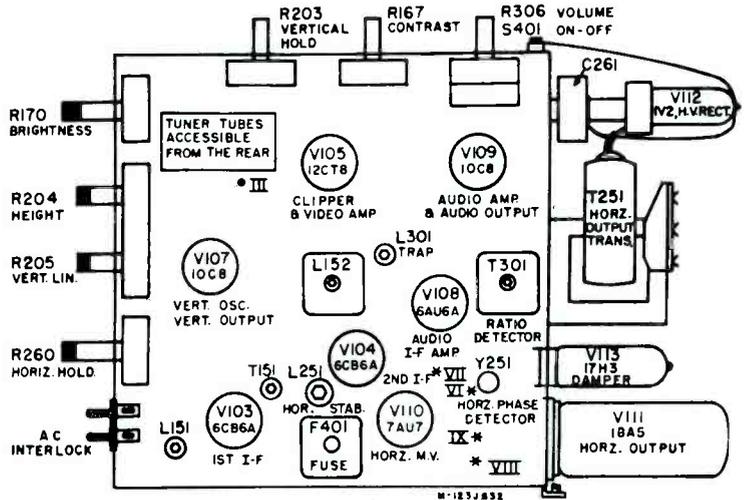(A Division of General Electric Company)
5600 West Taylor Street
Chicago 44, Illinois




CHASSIS HS-T-56—Covers Hotpoint TV Models 9S101 and 9S102.

this is the
Hotpoint
13½ lb. Portable

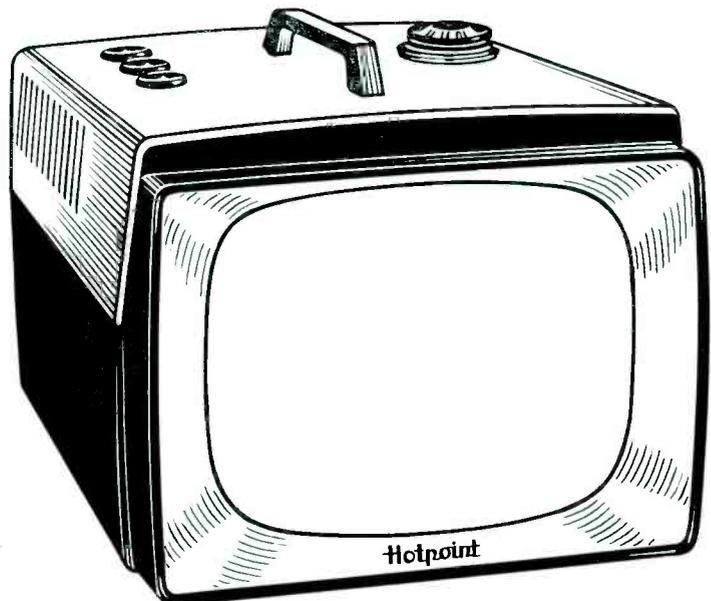

lightest of all
the TV Portables!

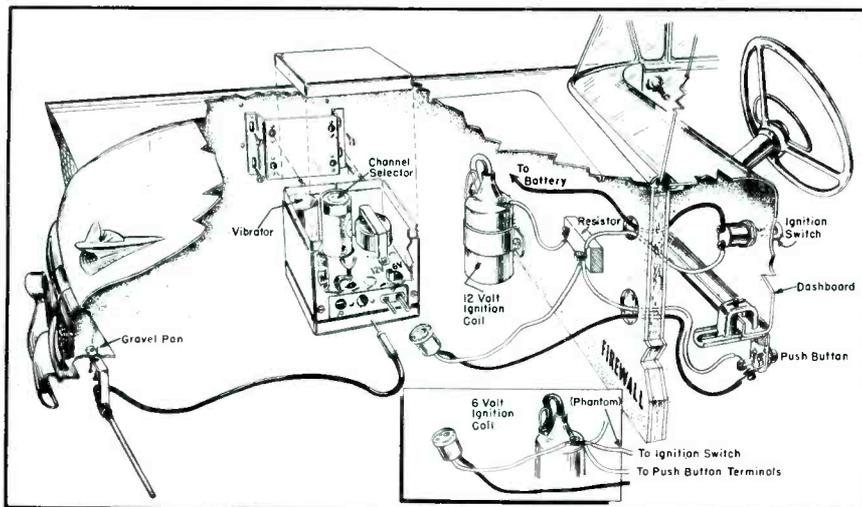Garage Door Opener Receiver-Transmitter Circuitry . . . Maintenance-Repair Notes




(Above)

DETAILED DRAWING showing position of the garage opener remote-control transmitter and accessories in car.

(Below)

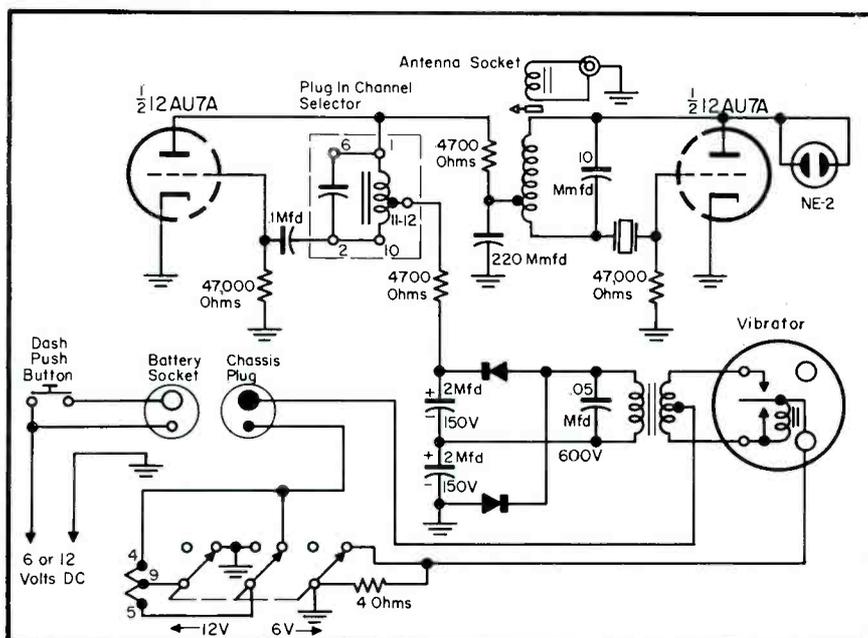COMPLETE CIRCUIT of the Perma-Power tone-modulated transmitter used in garage operator system.



(Continued on page 31)

THE INSTALLATION and maintenance of automatic radio-control devices for garage doors has become a flourishing activity among service shops.¹ The expanding interest has been prompted by the growing number of private garages and the development of soundly-engineered systems.

Properly installed, the controls will operate at any distance up to at least 75' from the garage. Depending upon installation and location the operating distance may be as great as 250'.

So that neighboring installations will not interfere with each other, one system² employs ten different channels or *keys*. A channel can be changed by means of plug-in channel selectors.


Two or more cars can be equipped to operate the same door. Additional cars may be equipped for remote control at any time without altering or adjusting the original installation.

By utilizing different channels, separate doors, side-by-side, can be controlled independently. Each car will then operate only its own door.

The remote-control unit in this system consists of a tone-modulated transmitter and a fixed frequency receiver operating in the class C Citizen's Band at 27.255 mc, as authorized by the FCC for such purposes. The carrier, transmitted with a frequency accuracy of $\pm .04\%$, is obtained by crystal control of an *rf* oscillator; the carrier is modulated at one of ten predetermined tone frequencies between 600 and 4700 cps. These tones are distributed between the foregoing limits on a logarithmic scale with a frequency ratio of 1 to 1.25 between any two adjacent tone channels. The modulating and detecting tuned audio circuits are pro-

¹See report by **John Sevec** in *September, 1956, SERVICE*.

²*Perma-Power RC 201.*

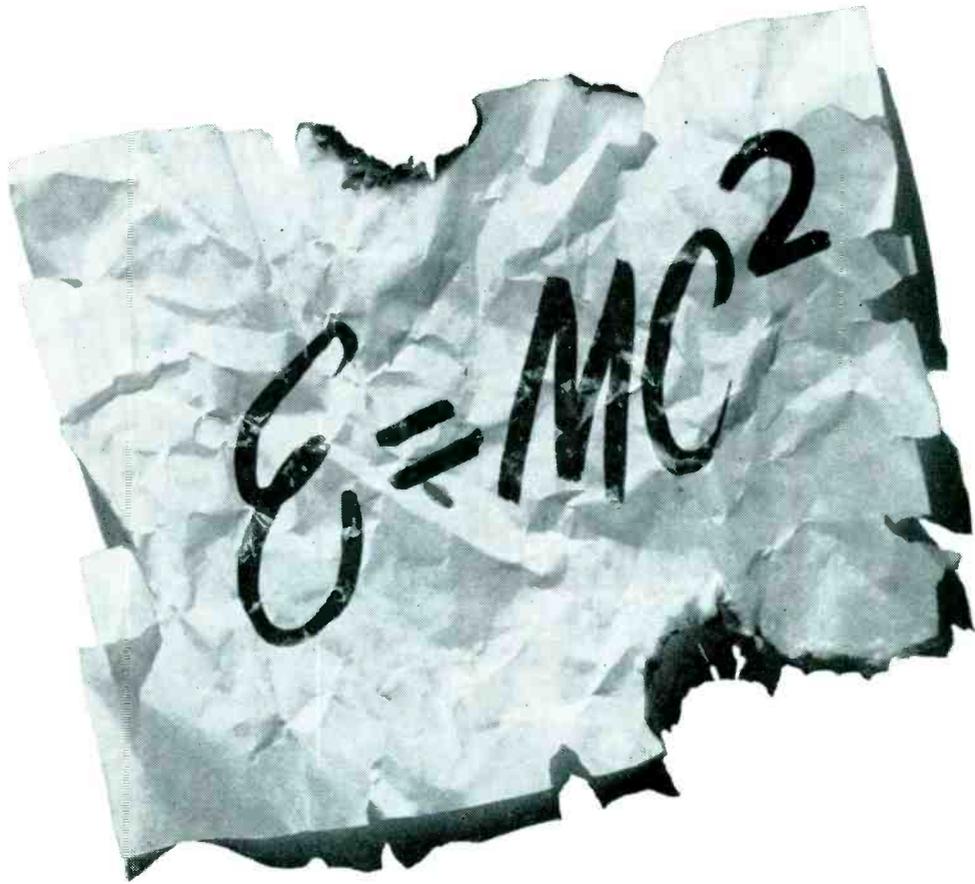

The Equation that Shook the World!

A hasty scrawl on a scrap of paper ushered in the Atomic Age. Through this equation, Dr. Albert Einstein revealed to mankind the awesome secret of atomic fission, with all of its tremendous power for good or evil.

This is the kind of a world we live in . . . a world where knowledge is power in a truer sense than ever before. It is an exciting world.

Univac® has added a new dimension to the world of science, processing data with a speed that crowds many lifetimes of research into a few hours.

Squarely in the midst of this exciting world are the engineers and scientists of Remington Rand Univac. Their potential for growth and achievement (and the rewards that go with them) is unlimited. *You can be one of them.*

Immediate Openings for:

FIELD LOCATION ENGINEERS with a college degree in a scientific or engineering field and experience in electronics. Extensive electronic background may substitute for some college. Many opportunities for rapid advancement.

FIELD LOCATION TECHNICIANS with technical school background and preferably some experience in electronics. These positions can lead to full engineering responsibility.

Send complete resumé to:

Remington Rand Univac


DIVISION OF SPERRY RAND CORPORATION

Mr. Phil Wilson

Dept. SN-28

1902 W. MINNEHAHA AVENUE • ST. PAUL W4, MINNESOTA

SERVICE, NOVEMBER, 1956 • 29

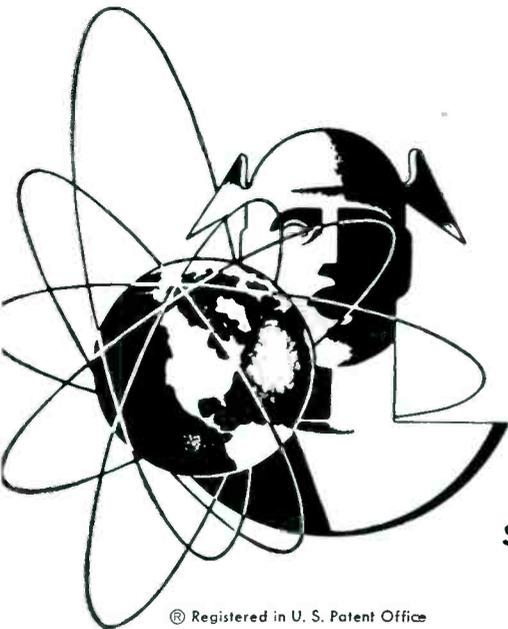


© Registered in U. S. Patent Office

1957 CROSLY SPECIALLY DESIGNED FOR TV SERVICEMEN EVERYWHERE!

... makes job easier, faster, more profitable!

**"90% of Crosley repairs
can be made
without removing chassis!"**

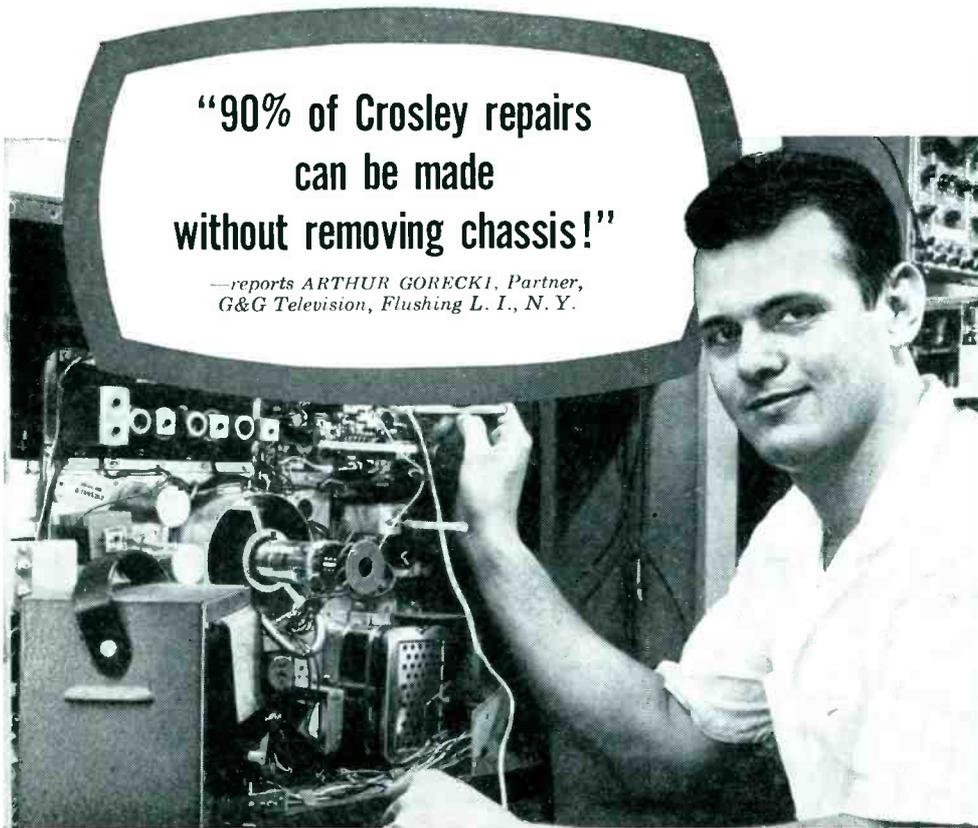—reports ARTHUR GORECKI, Partner,
G&G Television, Flushing L. I., N. Y.



Now, more than ever, the welfare and importance of the TV serviceman takes top priority with Crosley! By designing a TV chassis that's the easiest to service, Crosley makes it easier than ever for servicemen to make repairs in the home, cut repair time way down (for more profit per call) and drastically reduce shop time. With this amazing chassis you not only give faster service, but *better* service—eliminating costly call-backs and irate customers! Note the features described here . . . and see for yourself why Crosley is

KNOWN FOR THE NEWEST . . . RESPECTED FOR THE BEST!

Has all the features servicemen want—AND MORE!


- Printed circuit board is translucent. Just place light behind it to trace circuitry.
- Picture tube is removable from the front of set.
- Even filter capacitors and selenium rectifiers can be replaced without removing chassis!
- Transformers and chokes are screwed on—not riveted. Easy to service or replace!
- Special Crosley funnel-guide helps find oscillator adjustment. Cuts down probing time!

crosley and bendix
HOME APPLIANCES

DIVISIONS OF AVCO MANUFACTURING CORP., CINCINNATI 25, OHIO



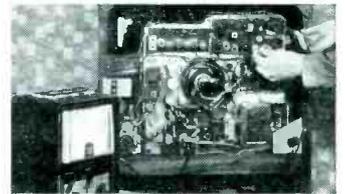Test points are labeled and easily available from the rear without removing chassis. Quick circuit analysis and trouble-shooting make for simplified servicing.



95% of all parts replaced without removing chassis, without touching a chassis bolt. Provision is even made for changing the power supply parts easily.



Find tube blowouts with a screwdriver. Open heater tubes are a cinch to locate with the marked special test points. All receiving tubes easily replaced.



Picture tube comes out with the chassis. The tube mounting is a part of the chassis assembly for quick handling. Replacement and set-up are quicker and easier.

Service Engineering

(Continued from page 28)

vided in plug-in form. Factory adjusted and sealed, they have a frequency stability of better than $\pm 1\%$.

The transmitter employs a single 12AU7A. One triode section serves as a crystal-controlled *rf* oscillator; it is plate modulated by the second triode section functioning as the tone oscillator in conjunction with a plug-in tuned circuit.

Plate power is obtained from a full-wave doubler circuit utilizing two selenium rectifiers. A transformer and vibrator provide for operation from the car's battery.


Accommodation of both 6 and 12-volt batteries is provided by a two-position slide switch mounted on the transmitter chassis. This switch connects the heater in series for 12-volt operation and in parallel for 6 volts; a dropping resistor is inserted in the power-transformer circuit in the 12-volt position.

Tuning Indicator

A novel feature of the transmitter's design is a built-in tuning indicator, which shows when the tank circuit is adjusted to resonance at the crystal frequency. The indicator consists of a miniature neon glow lamp connected to the high-potential terminal of the tank coil. Maximum *rf* voltage is indicated when the lamp glows brightest.

The indicator lamp also serves an important secondary purpose. It is well known that in crystal circuits of this type or of the similar tuned plate-tuned-grid type, the output (plate) circuit should be resonated at a frequency slightly higher than the crystal frequency. Although the output is then slightly less than when the tank is tuned to exact resonance at the crystal frequency, the oscillator is more stable, particularly with regard to *starting* when keyed *on-off*. This is so because the tank circuit must appear as an inductive plate load so that we have a negative conductance component of the tube input admittance to cancel the grid circuit losses and insure that oscillation will start. Once the oscillations have built up to a high value and are limited by non-linear tube characteristics, the tank circuit may be safely operated much closer to resonance at

(Continued on page 51)

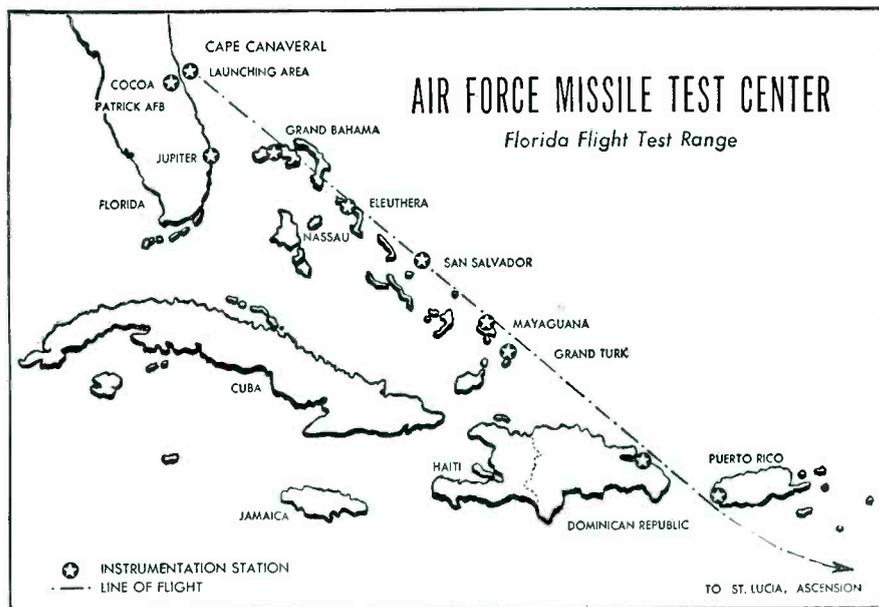

Engineers and Scientists:

INSTRUMENTATION SYSTEMS ENGINEERING for MILITARY APPLICATIONS

→ SALARIES UP TO \$14,000.

IN THESE NEW PROGRAMS AT THE MISSILE TEST PROJECT, FLORIDA

Have you as an engineer or scientist considered the problems and projects associated with the instrumentation and control of a long range missile, guided over a course that extends thousands of miles?

To achieve precision performance, missile launching and guidance require a vast network of instrumentation and control. New development programs have created challenging opportunities for Electronics Engineers and Scientists who are interested in data acquisition, transmission, recording and processing systems.

A world leader in electronics provides instrumentation for the Air Force Missile Test Center, which extends from Patrick Air Force Base, on the Central East Coast of Florida, to the Mid South Atlantic.

You will enjoy top salaries, liberal company-paid benefits, and ideal Florida living for you and your family. Relocation assistance, too.

→ TODAY . . . get complete information on arrangements for personal interview. Send a complete resume of your education and experience to:

PERSONNEL MANAGER
MISSILE TEST PROJECT—Dept. N-34L
P. O. Box 1226
Melbourne, Florida


MISSILE TEST PROJECT
Melbourne, Florida

What About Color TV?

There has been much talk about Color TV — and about whether or not available TV equipment is suitable for Color TV reception. Whatever other conditions prevail — one thing is certain . . .

ALL  TV PRODUCTS ARE ENGINEERED for COLOR

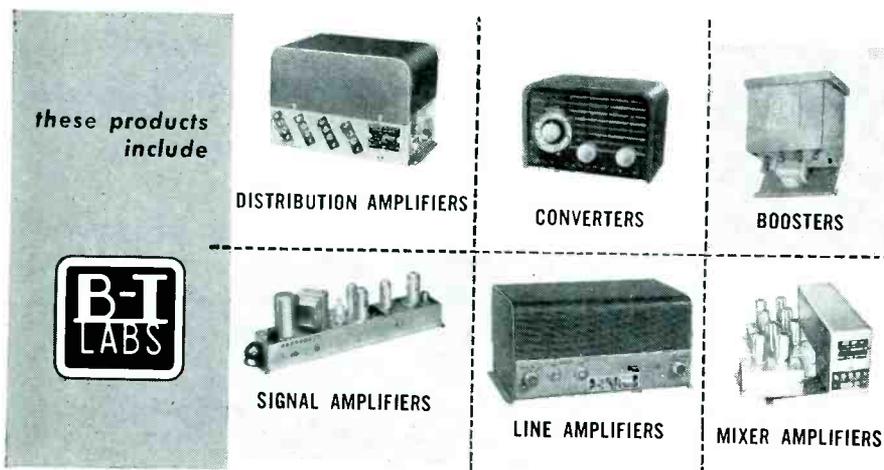Every piece of Blonder-Tongue equipment ever built, sold and in use — or ever to be used — is designed with color in mind . . . with the flat, broad output required for color.



. . . and all B-T impedance matching devices, equalizers, couplers, attenuators, connectors and tap-offs.

For example:

The  Model TV-42

is the only type approved by engineers for color — with a flat response from 0 to 900 mc.

Every  Master TV System now in operation is designed to meet the exacting demands of Color Television . . . today and tomorrow.

Keep abreast of the Latest Developments. Apply for your **FREE** subscription to the **B-T BULLETIN**.



Write today, to Dept. OL-8



BLONDER-TONGUE LABS., INC. Westfield, New Jersey

In Canada: Telequipment, London, Ontario

The largest manufacturer of TV Signal Amplifiers, UHF Converters and Master TV Distribution Systems.

Increasing TV Voltage

(Continued from page 14)

is not being used in the circuit. This winding can be connected in series with the power transformer secondary (Fig. 3; p. 14) to produce additional voltage. This circuit operates in approximately the same way as the set-up shown in Fig. 1; however, only one 6-volt filament transformer is used.

The output waveform shown will be the same as that obtained from the Fig. 1 system, where every other pulse of rectification is greater in amplitude than the alternate pulses. The additional *dc* voltage gain which can be realized in this circuit can be calculated by multiplying the voltage of the winding by 1.4. Thus, a 5-volt winding will produce a *dc* voltage gain of approximately 5×1.4 , or 7 volts.

Effective operation of this method centers on correct phasing. The 5- or 6-volt winding (or any other winding that may be used) must be properly connected to the power transformer. Otherwise, power transformer burnout may occur.

To obtain the correct phase all leads to the power transformer must be disconnected; Fig. 4. Any terminal of the unused filament winding (in the indicated case, terminal 4) must be jumped to one side of the power transformer secondary (terminal 3). With an *ac* voltmeter, the voltage measurement across terminals 2-5 should now be compared with that across 2-3. If the phase is proper, the former voltage will be greater than the latter. If the voltage across terminals 2-5 is less than that across 2-3, then phasing is improper and the connections to terminals 4 and 5 must be reversed.

A separate 6-volt filament winding may be used together with an unused filament winding of the power

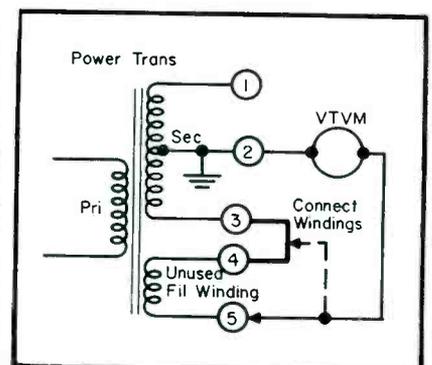


FIG. 4: METHOD OF determining phase of a power transformer unused winding.

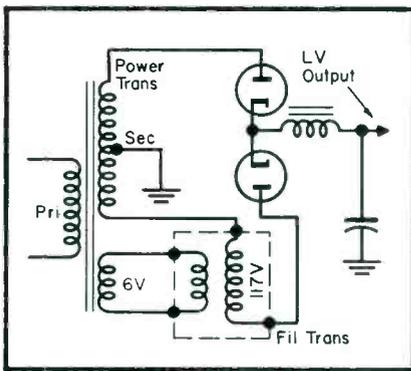


FIG. 5: SIX-VOLT FILAMENT transformer connected to power transformer to produce an additional 100 volts dc.

transformer to obtain a greater *dc* voltage. In this instance, the filament transformer 6-volt primary is connected across the 6-volt winding of the power transformer; the 117-volt secondary of the filament transformer is connected in series with the power transformer secondary, as indicated. Phasing is important here, too; the connections of the filament transformer must be in order to prevent power transformer burnout. To determine phase, the check procedure outlined for the previous boost method should be followed. A *dc* voltage increase of about 100 may be anticipated by using this method.

To increase the output of a selenium rectifier circuit, the circuit need only be converted into a tripler system. By adding a capacitor and rectifier, as shown by the heavy lines (and removing the ground, shown in dotted lines) in Fig. 6, a tripler circuit is established. A voltage increase of about 100 may be realized from this change.

To increase the *dc* to only about 15 volts, a 6-volt filament transformer may be connected so that the 6- and 117-volt windings are in series to form an autotransformer. If a *dc* voltage lower than the original results, then the connections to one of the transformer windings should be reversed.

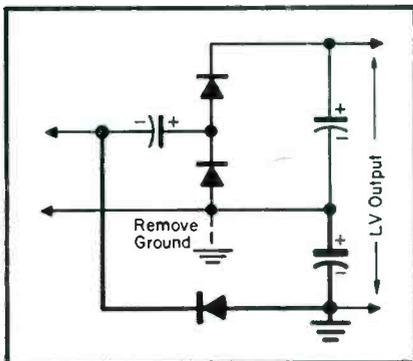


FIG. 6: FORMING A TRIPLER selenium-rectifier circuit from a doubler.

**AT LAST . . . one tester that does the whole job!
Faster—Easier—Better**

**NO OTHER
QUICK-TEST
TUBE CHECKER
IS SO
COMPLETE**



The Advanced, Improved,

ANKO TELETEST

TV and RADIO TUBE CHECKER

with the Exclusive Anko "Grid-Snooper"

that spotlights troubles

**CHECKS MULTI-SECTION TUBES—
UP TO 4 SECTIONS—
ONE SECTION AT A TIME—
WITHOUT ADDITIONAL
SWITCHING!**

A Necessity for Profitable Operation

The Anko-Teletest is so advanced in design that it not only accurately tests over 300 tubes in use today, but also has 10 spare sockets for new tubes that cannot be tested on presently wired sockets, so that it will fill your needs for years to come.

Tells the "inside story" of every set quickly and reliably—speeds bench work, pleases customers on service calls.

Simple to Use

No special skill or experience required—anyone can operate with speed and efficiency. A model of simplicity in spite of its advanced design.

Costs Little More But Worth It

You can own the all-inclusive Anko-Teletest for just a few dollars more than partial, inadequate testers, and have the benefit of top quality, serviceable equipment for years to come.

**Ask Your Jobber for
a Free Bench
Demonstration on
Your Toughest
Problem!**

1. Checks for shorts from any element to any adjacent element—requires no additional set-up. Special tests for gas, grid emission and grid shorts on all one and two section tubes.

2. Quick-test feature eliminates roll chart and multiple switching. Tests an entire set of tubes in minutes.

3. Dynamic loaded test puts tubes under fully loaded conditions.

4. Long life case—so light it can be carried anywhere, easily. Heavy duty wood case is covered with imported fabric that resists scratches and scuffing. Trimmed with genuine leather. Detachable hinged cover with firm holding catch.

Fully Guaranteed.

**90 day warranty on
all defective material
and workmanship.**

**ANKO MANUFACTURING
COMPANY, INC.**
5042 W. State St., Milwaukee 8, Wis.

Traffic Appliance Servicing

How To Repair Automatic Electric Toasters That Use Clock Timers And Clock-Thermostat Systems

by MILTON WALLACH

COUNTER in traffic-appliance service shop designed to expedite incoming-outgoing repairs and consumer part sales. Note variety of appliance types which this shop is authorized to service.



AUTOMATIC ELECTRIC household toasters are the most difficult type of portable appliance to service. We are faced with this problem because of the assorted types of pop-up and timing mechanisms employed and the number of different models some manufacturers make.

There are two basic groups of toasters. In one family are clock timers and in the second we have the clock-thermostat (bi-metal type) arrangements.

The clock timer pop-up mechanism



is found on many popular inexpensive toasters. In a simple arrangement a push down lever of the carriage assembly serves to actuate the clock. At a predetermined time, set by the manufacturer, the clock trips a lever which releases the carriage assembly. A dampening device consisting of springs or dashpot (cylinder) assembly prevents the toast from popping out of the unit.

In this type of toaster preheating is necessary before bread can be toasted properly. Also, since the toasting period is set by a non-automatic adjusting clock timer, the quality of

the toast varies depending on the texture of the bread; thus to obtain satisfactory results constant manual adjustment is required.

In the clock timer and thermostat arrangement, used on better-quality toasters, a number of refinements are included. The thermostat, which usually is a bi-metal type, is actuated by either reflector-element plates or resistance wires located directly in the toaster well. It compensates for heat and controls the speed of the clock, increasing the time element, when

(Continued on page 35)

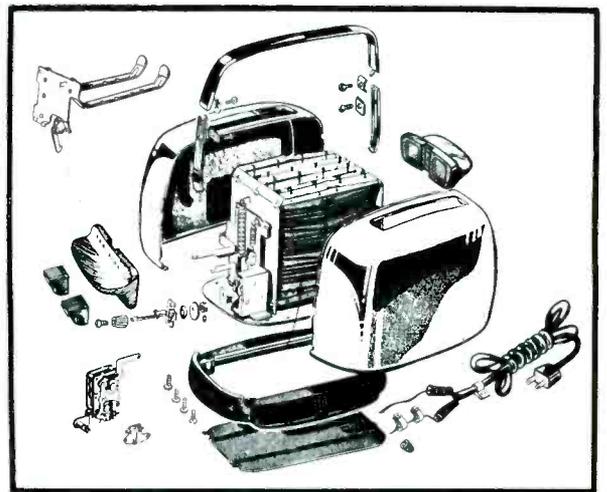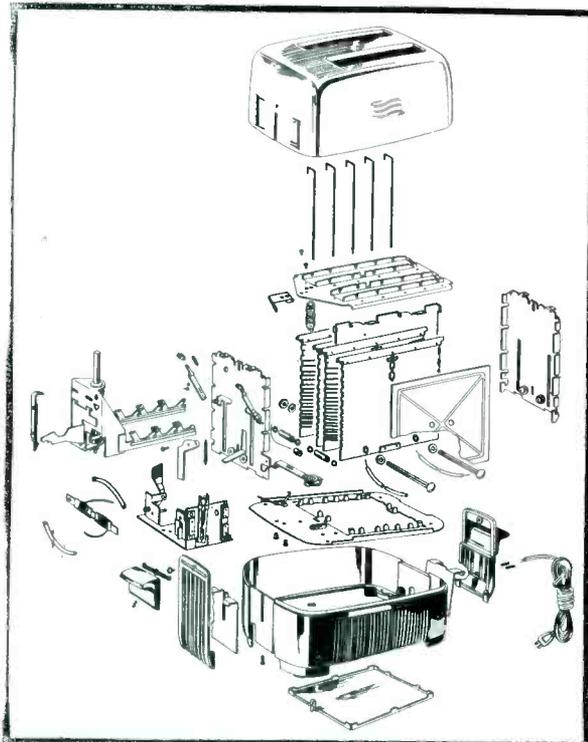

DETAILED drawings of clock type (above) and thermostat bi-metal type (left) toasters.

the specs are the proof . . .
the BEST BUYS are **EICO**[®]
 for COLOR & Monochrome TV servicing



NEW COLOR and Monochrome
DC to 5 MC LAB & TV 5" OSCILLOSCOPE
 =460
 Factory-wired and tested \$129⁵⁰
 Also available as kit \$79⁹⁵


• Features DC Amplifiers!

Flat from DC-4.5 mc, usable to 10 mc. **VERT. AMPL.**, sens. 25 rms mv/in; input Z 3 meg; direct-coupled & push-pull thruout; K-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. **SWEEP**: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); pre-set TV V & H positions (30 & 7875 cps); auto. sync. ampl. & lim. **PLUS**: direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; filter; bezel fits std photo equipt. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. Z-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control.



NEW TV-FM SWEEP GENERATOR & MARKER
 =366
 Factory-wired and tested \$119⁹⁵
 Also available as kit \$69⁹⁵

Entirely electronic sweep circuit (no mechanical devices) with accurately-biased inductor for excellent linearity. Extremely flat RF output: new AGC circuit automatically adjusts osc. for max. output on each band with min. ampl. variations. **Exceptional tuning accuracy**: edge-lit hairlines, 6:1 vernier. **Swept Osc.** Range 3-216 mc in 5 fund. bands. **Variable Marker Range** 2-75 mc in 3 fund. bands; 60-225 mc on harmonic band. 4.5 mc Xtal Marker Osc., xtal supplied. Ext. Marker provision. Sweep Width 0-3 mc lowest max. deviation to 0-30 mc highest max. dev. 2-way blanking. Narrow range phasing. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Cables: output, 'scope horiz., 'scope vertical.

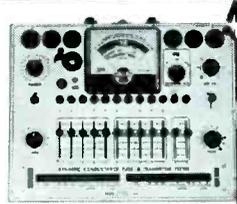

NEW DYNAMIC CONDUCTANCE Tube & Transistor Tester
 =666
 Factory-wired and tested \$109⁹⁵
 Also available as kit \$69⁹⁵

COMPLETE with steel cover and handle. **SPEED**, case, unexcelled accuracy & thoroughness. Tests all receiving tubes (& Color & Monochrome pic tubes with adapter). Composite indication of Gm, Gp & peak emission. Simultaneous sel of any 1 of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot). New series-string voltages: for 600, 450, 300 ma types. Sensitive 200 ua meter 5 ranges meter sensitivity (1% shunts & 5% pot). 10 SIX-position lever switches: free-point connection of each tube pin. 10 pushbuttons: rapid insert of any tube element in leakage test circuit & speedy sel. of individual sections of multi-section tubes in merit tests. Direct-reading of inter-element leakage in ohms. New gear-driven rollchart. Checks n-p-n & p-n-p transistors: separate meter readings of collector leakage current & Beta using internal dc power supply.

See the 50 EICO models IN STOCK at your neighborhood distributor. Write for FREE Catalog S-11. Prices 5% higher on West Coast

EICO BROOKLYN 11, N. Y.

Traffic Appliance Servicing

(Continued from page 34)

necessary, if the toaster is cold, or cold or moist bread are used. The timer element also decreases heat, when required, when the toaster is hot or the bread is dry or thin.

In the thermostat type of toaster the pop-up mechanism is controlled entirely by the thermostat. Most toaster thermostats, which are of the bi-metal type, are generally actuated by resistor wires wound around or near the bi-metal. This feature found on many popular brand toasters also compensates for heat and bread textures.

Repair Hints

In many cases the causes of inoperative units can be traced to dirty mechanisms due to an accumulation of bread crumbs, oils and sugar from sweet breads, corrosion, dirty and pitted contacts, bound carriage guides and rails.


In the initial inspection of a toaster to be serviced an electrical check must be made to determine whether there are any breaks in the circuit. This can be accomplished with a continuity tester and with the carriage assembly in toast position. If the circuit is open, one should check for breaks in the cord set (male plug), elements and connectors. Also the contact points should be checked, as a small particle of foreign matter can prevent

current from flowing through. Pitted contacts can be repaired by filing with an ignition file (not emery paper); they should not be filed flat, but rounded out so that a minimum of contact is made. Such filing will not only increase the contact life, by reducing excessive arcing, but also make it more difficult for foreign matter to collect between the contacts. If, up to this point the toaster appears

(Continued on page 39)

**HERE'S
ADDED
SERVICE
PROFIT**

at no extra expense

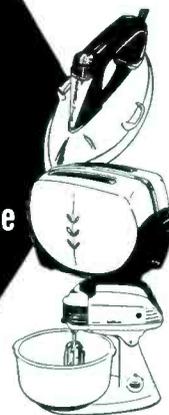

YOU can easily service small appliances as well as TV and radio for extra profits. You're in the home, so no extra call is required. Just inquire if there's an iron, toaster, mixer or other appliance that needs attention. You'll be surprised how many will say "yes" and be glad you mentioned it!

More Than 5 Million General Mills Appliances alone are in Daily Use!




Yes, aside from other makes, more than 5,000,000 GENERAL MILLS appliances have been sold to American homes. They are famous for their performance and satisfaction, yet through abuse and carelessness thousands of them need repair and service. You can get that business in your city.

We are exclusive national parts headquarters for all General Mills appliances. We have an attractive profit-proposition for you. Send the coupon today.

APPLIANCE SERVICE CO.
 1516 East Lake Street
 MINNEAPOLIS 7, MINN.

APPLIANCE SERVICE CO.
 1516 E. Lake Street, Minneapolis 7, Minn.
 Enclosed is 25 cents to cover cost of printing and mailing complete parts list and detailed instructions for servicing General Mills appliances.

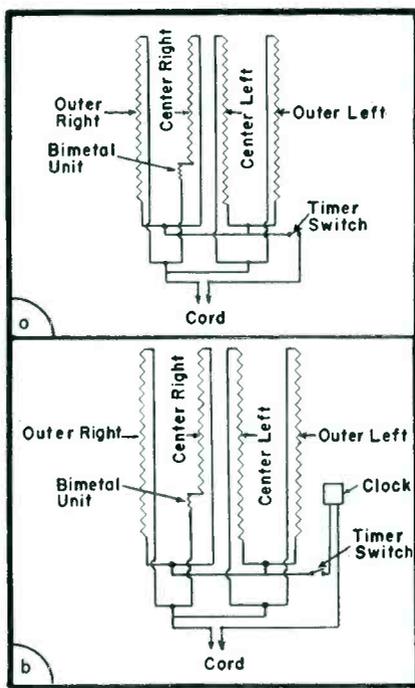Name.....
 Firm.....
 Address.....
 City..... Zone..... State.....



BI-METAL (a) and combined bi-metal/clock-type (b) resistive-element controls employed in automatic toasters.

Color-TV

(Continued from page 22)

conducts on one side of the burst signal and therefore, symmetry in the incoming burst signal is not important.

Both phase detector circuits also provide an output which is a measure of the amount of burst in the signal. This is the output of the detector which develops a negative voltage with respect to ground across its load resistor. This voltage applied through a voltage referencing network is connected to the grid of the first chroma amp as an automatic color-gain control or *acc*.

The changes in both the color killer circuit and in the oscillator control tube circuit are related and are the result of the use of sync color killers. In the past, color killers have been activated by one-half the output of the balanced phase detector, which when burst was present gave a comparatively high output, usually negative, and when no burst was present, gave a comparatively low output. This type of color killer has been found to present a problem; the bias voltage on the color killer must be so adjusted that it does not kill when there is still usable chroma present and at the same time kills the color circuits on a noisy monochrome transmission. To make a good compromise in this color killer bias, for widely divergent conditions met in the field, a color killer threshold control was used. To overcome these shortcomings and to eliminate a difficult adjustment, the sync color killer circuit was developed. This color killer makes use of the following properties of a balanced phase detector to obtain an actuating or sensing voltage. Whenever the two signals supplied to the phase detector are non-synchronous or exactly 90° out of phase, the output of the detector is zero. Whenever the signals are synchronous and not 90° out of phase, the output of the phase detector is some definite voltage, either positive or negative, depending on the phase difference between the two signals and the overall sensitivity of the control circuit. If the phase between the two signals could be so adjusted that the output of the phase detector was sufficiently negative when burst was present, (oscillator synchronized to burst), so that it would bias the color killer tube to cutoff, we would have a color sensing voltage practically immune to noise and other interfering signals in monochrome transmissions, and at the same

Little Devil COMPOSITION RESISTORS

Meet all MIL-R-11A requirements. Rated at 70C rather than 40C. Available in 1/2, 1, and 2-watt sizes in all standard RETMA values.

BROWN DEVIL® RESISTORS

Vitreous-enamelled. In 5, 10, and 20-watt sizes.

TYPE AB POTENTIOMETERS

Resistance material is solid-molded, noise-free. Rated at 2 watts.

FR-7.5 FUSE RESISTOR

For easy replacement in all television receivers. 1 1/2" Tinned wire leads.

WRITE FOR STOCK CATALOG

Be Right with

OHMITE®

DEPENDABLE RESISTANCE UNITS

Eliminate call-backs due to faulty replacements. Use Ohmite components.

AXIAL-LEAD RESISTORS

Vitreous-enamelled, power-type units designed to withstand high temperatures.

3 WATT SIZE
9/16" x 1/4"

5 WATT SIZE
1" x 11/32"

10 WATT SIZE
1-3/4" x 13/32"

OHMITE®

OHMITE MANUFACTURING CO.
3642 Howard Street, Skokie, Illinois

the **BEST** because...
Only the CLEAR PICTURE Comes Thru!

with the **NEW and AMAZING** *Dynamic* **FILTER TENNA**

with the **EXCLUSIVE** built-in **HI-PASS FILTER**
T. M. Reg. Pat. Pend.
THE FIRST TRULY ELECTRONIC INDOOR TV ANTENNA TO GIVE CLEAR FILTERED RECEPTION.

List **\$18.95**
SATIN BRASS, SATIN CHROME, SATIN COPPER FINISHES.

Beautiful!

The secret is in the filter! Automatically screens out electrical disturbances. Ghosts, fuzz, and distortion eliminated with a 12 position channel attenuator. Guaranteed to outperform all other indoor antennas, and most roof installations in urban areas... or money back!

ALSO, there is a **DYNAMIC** accessory or service aid for practically every need.



Model DF200 **\$9.50** List

Available at all distributors where quality electronics are sold. COMPLETE LINE FOLDERS ON REQUEST

Manufactured By... **DYNAMIC ELECTRONICS - NEW YORK, INC.**
Forest Hills, Long Island, New York



big reasons why QUIETROLE
Reg. U. S. Pat. Off.

is "The Choice of Better Service Dealers Everywhere"

- 1 MERIT
- 2 QUALITY
- 3 RELIABILITY

The original product for quieting noisy controls and switches . . . the universal lubri-cleaner for TV and radio . . .



Carried by recognized jobbers . . . everywhere!

Say "QUIETROLE" to your distributor . . . be sure you get it.
NO GUM!
NO GOO!
NO GRIME!

manufactured by




QUIETROLE COMPANY INC.
 Spartanburg, South Carolina

IN CANADA: Active Radio & TV Distributors
 58 Spodina Ave., Toronto 2B, Ont.

EBY AD-60



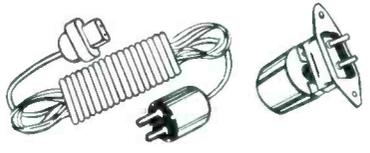UNIVERSAL CHEATER-PATCHCORD
 Compact - Lightweight



- The AD-60 is supplied in two parts - the adapter and the special cord.
- The adapter when used with any standard cheater cord converts same into a Zenith type of cord.
- Inserting the special cord into one end of the adapter, the AD-60 becomes a Zenith type of patch cord. Inserting the other end of the special cord into the adapter the AD-60 becomes a standard type of patch cord.

Carry your AD-60 and service all TV receivers.

List Price **\$2.25**

EBY SALES CO. of N. Y.
 130 LAFAYETTE STREET
 NEW YORK CITY 13, N. Y.

time would never kill on color signals unless the subcarrier oscillator could not be synchronized to burst, which would make the signal unusable for creating color. The difference in phase can be set up by adjustment of the oscillator control tube plate circuit. All of the foregoing, however, has not been accomplished without some disadvantages, since the oscillator control tube has been set up to operate with some negative voltage on its grid during color, and zero volts when no color is present. Therefore, the oscillator is not at burst frequency when monochrome is present and must be pulled into frequency by the burst on color transmissions. To aid pullin, a network has been added at the low side of the plate coil of the oscillator control tube to furnish a load to the low-frequency beat between burst and oscillator frequency, when the two signals are out of sync, so that this amplified beat can sweep the oscillator into sync with the burst. The addition of this network, together with a change in sensitivity of the oscillator control tube, produces color sync performance equal to the older system; at the same time we have lost none of the advantages of the synchronous color-killer circuit.

The circuit of this new chassis also offers another new feature: the B+ supply return is to tube rectifiers instead of selenium rectifiers. This has become possible, because of the use of a new power-transformer design, which through the use of a heat-conducting potting material enables the heat to be conducted away from the windings and core of the transformer.

Special Tests for Tubes

(Continued from page 19)

tubes. In color-TV sets, proper tube performance is of even greater significance.

The independent shop owner interested in developing mobile radio, computer or industrial electronics service business can profit by paying special attention to tube-testing methods. What worked for radio and television sets which operate only a few hours a day and are not used for returning a profit to the owners, may not work in industrial servicing. Besides industrial customers will not and cannot afford to tolerate frequent equipment failures. Since well over 90% of all electronic equipment failures are caused by tubes, here is the department which warrants the most consideration.



PILE UP PROFITS

by speeding up your service. Read CORNELL-DUBILIER'S pocket-size monthly magazine loaded with short-cuts and aids to servicing. PLUS a "Sell-Swap-Buy" section for your ad. Mailed FREE to your home every month for the asking.

CORNELL-DUBILIER ELECTRIC CORP.
 DEPT. S116 SOUTH PLAINFIELD, N. J.
 OK! Send me "The Capacitor"—Free

Name _____
Please Print!

Address _____

City _____ Zone _____ State _____

My occupation or job title is _____



SELL-SWAP-BUY

Turn your unneeded equipment into dollars. CORNELL-DUBILIER'S pocket-size monthly magazine gives you space for a Sell-Swap & Buy ad. The ad is FREE—the magazine is FREE. Mailed to your home every month for the asking—use coupon.

CORNELL-DUBILIER ELECTRIC CORP.
 DEPT. S116 SOUTH PLAINFIELD, N. J.
 OK! Send me "The Capacitor"—Free

Name _____
Please Print!

Address _____

City _____ Zone _____ State _____

My occupation or job title is _____

HICKOK

Model 675



PROFESSIONAL TV ENGINEERS' 5" SCOPE

- Illuminated Calibrated Screen.
- Flat response through 3.58 MC.
- New circuit technique eliminates band-width switching.
- Low capacity probe furnished.
- Includes New HICKOK Service-Instruction Warranty

THE HICKOK ELECTRICAL INSTRUMENT CO.

10521 Dupont Ave. • Cleveland 8, Ohio

STEAM IRONS NEED CLEANING TOO!

get **INSIDE** clean for **MORE** steam

SSS-T! STEAM IRON CLEANER

- EASY TO USE
- ODORLESS
- NON-ACID
- WILL NOT BURN
- ECONOMICAL
- MFR. RECOMMENDED
- FULL YEAR SUPPLY

FREE literature on request. Stores and shops only, request FREE sample on business letterhead.

Choice jobber areas available.



A NATURAL Over-the-Counter Seller!

Used and Sold in Leading Appliance Service Stations Coast-to-Coast!

Order from your **JOBBER** or write us for name of your nearest supplier.

Fast Chemical Products Corp.

65 Page Avenue
YONKERS 4, N. Y.

Servicing Helps

Replacing Metal Picture Tubes With Aluminized Glass

Types ‡ . . . Small Electrolytic Formation and Testing

THERE ARE MANY TV sets in the field with metal picture tubes suffering from diminished brightness. Improved picture quality can be obtained by replacing with aluminized glass types. The 21AP4 may be replaced by a 21ZP4B, and the 21MP4 by a 21YP4A.

To install a glass tube in place of the metal type, the chassis, yoke assembly, old picture tube, and the plastic mask must be removed; *one must wear safety goggles during this operation and handle picture tube with care.* All of the old metal tube retainer springs and high voltage contact should be snapped out from the mask. The plastic mask should be placed face down on a clean surface, and the new picture tube should be carefully set, face down, on the mask. There are two areas of interference near each corner that prevent the entry of the tube face. One should be sure that the tube is rotated so that the high-voltage connection is on the proper side, for the tube face may not be symmetrical. The areas of interference should be marked on the plastic with pencil for reference; then the tube should be set aside.

Now the interfering wall of the plastic mask should be ground away using a coarse wheel in a bench motor arbor, or electric drill and arbor held in a vise. One should check the removal of the plastic periodically with the picture tube until enough material has been removed to allow the picture tube face to enter easily and seat against the little bosses in the corners; do not force the tube in place. The contour of the tube is such that material needn't be removed all the way in to the mask face. By starting near the mask face and working back, a slip is less likely to cause damage. The mask should be held in the same plane as the grinding wheel, working laterally. The plastic tends to gum and smear, but cools rapidly to a brittle sponge which readily flakes away. The surface of the mask that

must be ground away is not visible in the set, so no skill or precision workmanship is required here.

The fitted mask (and safety glass) should be washed free of finger marks with a gentle detergent and reassembled into the cabinet.

The bracket suspending the yoke assembly from the top of the cabinet should next be moved exactly 1" to the rear. It is well to drill pilot holes for the screws to avoid splitting the wooden mounting block. Next, it is necessary to drill out the rivets which fasten the plastic cup to the set's rear cover. To space the cup approximately 1" away from the cover, 1½" No. 6 screws and three nuts (each) should be used.

The new picture tube face should now be cleaned and inserted in the mask. The yoke should be placed over the neck of the tube, attaching it loosely to the suspension bracket. The nuts on the diagonal pressure rods will be close to the end, so they should be checked to be certain that a safe minimum of three threads are engaged. All of the sets that have been converted have been found to have ample thread engagement; should one be encountered that does not, the rod brackets can be spaced out with ordinary washers to lengthen effectively the rods. The two diagonal rod and the suspension bracket nuts should then be tightened in a manner to center the yoke on the neck of the picture tube.

The high voltage lead wire should now be cut loose from the old metal tube contact spring. The insulation should then be stripped approximately 1½" back from the cut end; the tip should be tinned to prevent fraying, and the bare end formed into a loop which can be inserted into the picture tube *ultor* (high voltage) cavity cap.

Now the ion trap should be installed and adjusted, the picture sized, and then the rear set cover can be put on.

Small Electrolytic Forming

ELECTROLYTIC CAPACITORS employed in transistor equipment should be

‡Based on notes prepared by **Serge L. Krauss**, electronic product design engineer, C. G. Conn, Ltd.

formed and tested for leakage prior to use. A circuit such as shown by Fig. 1 may be employed. The battery (B) or one of less voltage than the rated working voltage of the capacitor should be used.

A current limiting resistance (R) must be placed in series with the capacitor and a microammeter. The total resistance should be enough to allow about 50 μ a maximum to flow during the forming and charge period if already formed. (A formed capacitor will discharge through its shunt resistance, and even in testing, the protective resistance must be used to safeguard the meter.) For 50 μ a to flow at 9 volts (a handy battery size) a 180,000-ohm resistor is required, as the following mathematical explanation reveals:

$$E/I = R$$

$$9/50 \times 10^{-6} = 1.8 \times 10^5 = 180,000 \text{ ohms.}$$

As the current becomes reduced, a shorting switch may be closed allowing the capacitor to form up to full battery voltage. The leakage at that voltage may be read directly on the meter. *Caution:* The meter must be kept on a higher range and one must switch to the microampere range after ascertaining that the current is low enough not to damage the meter movement.

Most capacitors run about .03 to .04 μ a per mfd per volt. At 9 volts, applied to a 10-mfd capacitor, we have

$$9 \times 10 \times .03 = 2.7 \text{ } \mu\text{a leakage.}$$

Or for the higher figure (.04) we have a leakage of 3.6 μ a.

Another factor that must be considered in choosing capacitors for duty with transistorized circuits is the working voltage versus rated voltage. The leakage increases rapidly as the working (applied) voltage approaches the rated voltage. Above the rated voltage, the capacitor may break down and have a high leakage thereafter; rated voltage should be greater than the battery voltage applied.

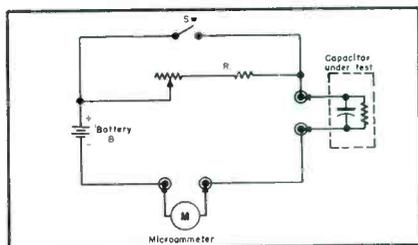


FIG. 1: LEAKAGE TEST and forming circuit for small electrolytics. The meter should be used on a higher range until you are certain of the current.

Appliance Servicing

(Continued from page 35)

to be electrically satisfactory, then a complete cleaning must be made. All of the foreign matter should be removed with a soft pencil type artist brush, being careful not to damage the nichrome element wires or disturb the compensating devices. Compressed air should not be used for this job as it will damage the toaster, particularly those using the mica-

wound elements. Greasy par be dissolved with a good non-oily solvent, such as carbon tet. Moving parts, such as the latch mechanism, carriage guides and rails should be relubricated with graphite oil. Any worn parts should be replaced. Clock timers, after a thorough cleaning, should be lubricated very lightly at the pivot or shaft points with silicon oil. In the final test stage the toaster should be assembled and bread tested, making all adjustments with the color control in medium position.

IF YOU REPAIR SMALL APPLIANCES...

... you'll want this new, different and complete Manual of parts and service.



**DON'T DELAY!
SEND 25c NOW**

STILL AVAILABLE

Every appliance repair shop needs this handy catalog. Regularly priced at \$1.50 . . . but for a limited time only it's yours for only 25c —stamps or cash (no check please) to cover cost of mailing.

128 PAGES!

SUPPLY IS LIMITED

**RETAIL
\$1.50**



"BELDEN"

**HEATER
CORD SETS**

The most profitable "plus" sale item for TV servicemen. Best quality replacement cord sets for your customers' electric appliances. HPD cord for irons, toasters, percolators, heaters, etc.

VG-8714 HPD heater cord set—7ft. long—No. 16-2, 10M cycle—black w/red and gold tracers—legs tightly and neatly fibre-glass wrapped—eyelets installed.

\$5600
per C

EA.—65¢ LOTS 25—60¢

VG-8484 Same as above except without eyelets—color pattern brown w/white tracer.

\$5200
per C

EA.—60¢ LOTS 25—55¢

ORDER FROM NEAREST JOBBER

ELECTRA-CRAFT APPLIANCE CO.
348 WEST 42nd ST.
NEW YORK 36, N. Y.

ELECTRIC SWEEPER SERVICE CO.
2034 EUCLID AVENUE
CLEVELAND 15, OHIO

BEST IN



SIGHT

The Tung-Sol Magic Mirror Aluminized Picture Tube captures every tone, every detail brilliantly to bring out the best in every set. It's your best insurance for loyal, satisfied customers. Tell your supplier you'd rather have Tung-Sol tubes.

Blue Chip Quality

 **TUNG-SOL®**

Magic Mirror Aluminized
PICTURE TUBES

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Columbus, Culver City, Dallas, Denver, Detroit, Melrose Park (Ill.), Newark, Seattle.

CATALOGS—LEAFLETS—BOOKS

NATIONAL APPLIANCE TRADE-IN GUIDE Co., 2105 Sherman Ave., Madison 4, Wis., has published the 1957 *Official NARDA TV Blue Book* containing latest trade-in values of sets produced by 47 manufacturers from 1947 to date. 152 pages; priced at \$5.

ELECTRO PRODUCTS LABORATORIES, 4500 Ravenswood Ave., Chicago 40, Ill., has released an illustrated catalog sheet describing the D612T 8 and 16 v dc power supply for servicing transistor, as well as tube model auto radios.

UNITED CATALOG PUBLISHERS, INC., 110 Lafayette St., New York 13, N. Y., has issued a 1546-page 1957 edition of the *Radio Electronic Master*. New edition lists more than 125,000 items of 350 manufacturers. Included are detailed descriptions, specifications and prices on tubes, test equipment, capacitors, resistors, relays, coils, antennas, transformers, recording and pa systems, hi-fi equipment, hardware, tools, transmitters, communication receivers, wire and cable, speakers, microphones, rectifiers, converters, amateur gear, switches and volume controls. Available through parts distributors.

HEATH Co., Benton Harbor, Mich., has released a 14-page illustrated brochure, *Heathkit 1956 Fall Flyer*, with specifications, descriptions and prices on 'scope voltage calibrator, voltmeter, multimeter, harmonic distortion meter, audio oscillator, signal generator, linearity pattern generator, cathode ray-tube and receiving tube checker, condenser checker, impedance bridge, battery eliminator, audio amplifier speaker, crossover and preamp kits.

PYRAMID ELECTRIC Co., 1445 Hudson Blvd., North Bergen, N. J., has issued an 18-page booklet, *TMR-1*, with data on *Twist-Mount* electrolytic capacitors.

ATLAS SOUND CORP., 1451-39th St., Brooklyn 18, N. Y., has released bulletin 756 describing a dispatcher and switchboard microphone support, neck-supported microphone stand and microphone foot switch. Also contains application information.

RCA SERVICE Co., INC., Commercial Service, Camden 8, N. J., has issued a reference book on the setup and servicing of *The 700 Series Color Television Receivers*, illustrated with 148 photos and diagrams. Contains a circuit-by-circuit description of the two types of chassis used in the 700 series receivers, an illustrated description of setup procedure and a section detailing step-by-step practical methods for analyzing, localizing and correcting malfunctions.

HOWARD W. SAMS AND Co., INC., 2201 E. 46th St., Indianapolis 5, Ind., has released a *Transistor Circuit Handbook* by Louis E. Garner, Jr. Contains more than 200 basic circuits with practical applications and data on transistor uses. Book is divided into four sections covering lab practice, basic circuits, circuit applications and reference material. 430 pages; priced at \$4.95.

AMERICAN TELEVISION AND RADIO Co., 300 E. Fourth St., St. Paul, Minn., has released a 6-page folder illustrating and describing an aluminized 21-inch 26-tube 41-mc TV model and a line of custom consoles available for the chassis.

BLONDER-TONGUE LABORATORIES, 526-536 North Ave., Westfield, N. J., has issued a general catalog covering TV distribution units, TV installation accessories and closed-circuit TV equipment. Illustrations, specifications and prices are included.

SHURE BROTHERS, INC., 222 Hartrey Ave., Evanston, Ill., has published a pocket-size replacement manual, *RM-56*, with complete information and technical data on ceramic and crystal pickup cartridges and magnetic recording heads.

PERSONNEL

ROBERT L. SHAW has been appointed national sales manager of the radio and television division of Sylvania Electric Products, Inc., 254 Rano St., Buffalo 7, N. Y. . . . THOMAS P. RYAN is now central regional sales manager with offices in Chicago. . . . RAYMOND B. HUEY has been promoted to western regional sales manager with headquarters in Los Angeles. . . . RICHARD M. KLEIN has been named product engineering manager of the electronic product sales department at 1740 Broadway, New York 19, N. Y.

DON LARSON has been appointed general manager of the Western Electronic Show and Convention. . . . Larson's former ad agency has changed its name to Bill West Advertising and BILL WEST has assumed agency operation.

A. R. HOPKINS has been named manager, commercial electronic marketing department, Radio Corporation of America, Camden, N. J.

HARRY STOCKMAN, H. PHILIP HOVNANIAN and E. JAMES JOHNSTON have announced the formation of Neutronics Research Co., 165 Lake St., Waltham, Mass.

JOHN SEARING has been named sales manager for insulated chokes, fixed composition and wire-wound resistors manufactured by International Resistance Co., 401 N. Broad St., Philadelphia 8, Pa.

JAY CARVER has been appointed ad and sales promotion manager of Electro-Voice, Inc., Buchanan, Mich. Carver was formerly ad manager of Cabinart.



Carver

Searing

Adkins

DAVID C. ADKINS has been named public relations manager of CBS-Hytron.

EDWIN B. HINCK, formerly sales manager, replacement tube division, Allen B. Du Mont Laboratories, has joined C & M Industries, Inc., 141 E. 44th St., New York 17, N. Y., as vice president.

PETER G. BUTTACAVOLI has been promoted to national service manager of the receiver division of Allen B. Du Mont Laboratories, Inc.

J. R. JOHNSON has been promoted to vice president in charge of sales and merchandising for Standard Coil Products, Co., Inc., 2085 N. Hawthorne Ave., Melrose Park, Ill.

NILS HILLSTROM has been named national sales manager of Newcomb Audio Products Co., 6824 Lexington Ave., Hollywood 38, Calif.

ROBERT B. CODY has been appointed district sales manager of the General Electric Co. tube department office at 106 W. 14th St., Kansas City, Mo. . . . D. J. WHALEN is now district sales manager of a new tube department office at Farmers Union Building, 1575 Sherman St., Denver, Colo. . . . E. D. TREANOR is now district sales manager in charge of a new office at Brown-Marx Building, Birmingham, Ala.

LAWRENCE LEKASHMAN has been named vice president in charge of sales for David Bogen Co., Inc., and Presto Recording Corp., both affiliates of Unitronics Corp. . . . DAVID PEAR is now manager of advertising and sales promotion for both companies.

BEST IN



SOUND

Made to the highest requirements of leading set manufacturers, Tung-Sol Tubes are perfect replacements for all sets. Bank on Tung-Sol's brand of quality—tops in the industry. It's the sure way to avoid callbacks that eat into profits. Tell your supplier you'd rather have Tung-Sol tubes.


Blue Chip Quality

TUNG-SOL[®]
RECEIVING TUBES

TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

SHOW ANY PICTURE or PATTERN

at any time — ON ANY TV SET

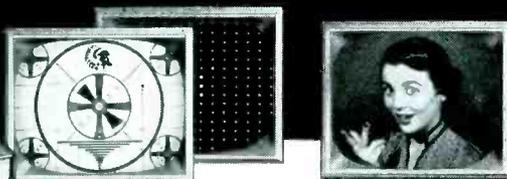


- For Servicing Black & White and Color TV
- For Merchandising and Advertising Promotions
- For Paging, Educational and Industrial Use

New
MODEL 1000

B&K DYNA-SCAN

PICTURE AND PATTERN VIDEO-GENERATOR

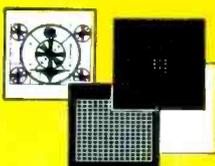

**3 SLIDE
TRANSPARENCIES
ARE SUPPLIED**

1. Indian Head Pattern
 2. White Dot Pattern
 3. White Line Crosshatch
- Plus One Clear Acetate

These are broadcast quality and assure high-definition TV images. You can also transmit slides of any subject you wish.



MODEL 950

See Your Distributor or Send For Bulletin 1000-S

Simplify and speed servicing with this unique, new, COMPLETE FLYING SPOT SCANNER. Produces composite video and sync signal that operates any standard VHF black and white or color TV receiver. Easily reproduces standard Indian Head test pattern or any other pattern—in home, shop or store—for proper TV set alignment; enables you to make all color TV static and dynamic convergence adjustments with stable White Dot and White Line patterns. Can be used with one or more standard TV receivers or fed into master antenna system. Reproduces from any film transparency. Transmits messages typed or written on clear acetate. Size: 16½ in. long, 10¾ in. high, 9½ in. wide. Net wt. 28 lbs. **\$199⁹⁵** NET

Model 950 Dyna-Scan Pickup and RF Generator Only

Make your own picture and pattern generator. Just connect Model 950 to any properly modified 10-inch TV set which acts as your external flying spot scanner. Size: 3½ in. high, 10½ in. wide, 5 in. deep. Complete with 3 slide transparencies and 1 clear acetate. Net wt. 5 lbs. **\$69⁹⁵** NET

B & K MANUFACTURING CO.

3726 N. Southport Ave. • Chicago 13, Illinois

Makers of DYNA-QUIK, CRT, CALIBRATOR and DYNA-SCAN



TO ELIMINATE coax failure due to cracking of jacket or core at extremely low temperatures, cables are subjected to a cold-bend test. Length of cable is conditioned at a temperature of -40 F for one hour in the cold box illustrated.

made. All amplifiers had been checked prior to installation, and a continuity check showed the cable circuits were intact. With a flick of the switch, channel 2 was viewed with clarity never before realized in this area. A twist of the channel selector and there was channel 4, another twist and nothing. What had happened to channel 5? If channel 2 and 4 were good, why not channel 5? Could the system be frequency sensitive? It could be and it was.

It was at this point that a cable phenomenon was noted. Heretofore, the relatively short cable lengths used never caused this condition to appear. But now, with cable measured in miles instead of feet it was found that a cable could have low response or *traps* at certain frequencies. Now the problem was presented to the cable manufacturer for solution.

An investigation was undertaken by our lab. The fact was eventually established that high attenuation peaks were directly related to minute irregularities in the extrusion of the cable core. As an example, any slight change in the core diameter will change the impedance of the finished cable at the point. If this change in diameter appeared at regular intervals along the length of the cable, the effect would be cumulative. In short cable lengths these slight variations would not be noticed since the total effect was still small, but now that the cable lengths were extremely long, their presence was very obvious. When these irregularities appeared at intervals, equal to a half wavelength of the frequency to be transmitted over the cable, the effect was such as to cause high attenuation at that point. Calculations of this attenuation

TV Antennas


(Continued from page 26)

of town on some tall hill or mountain, it was necessary to install a system which required little maintenance over these long, often inaccessible spans. For this application, low loss, large diameter cable¹ was selected. Although these low-loss cables are relatively expensive, this choice allowed a minimum of amplifiers to be used, and consequently maintenance service in this area would be at a minimum. Once the signal had

reached the edge of town, it was possible and desirable to resort to the higher loss, but less expensive RG-11/U type cable. From here on, maintenance service would be no unusual problem and since the signal would be distributed in many directions, amplifiers were a necessity. With this RG-11/U type cable strung from utility poles on streets and in alleys, house drops were made with the still less expensive but higher-loss RG-59/U type cable.

The great moment had arrived when the first system check would be

¹Such as Amphenol 21-125.

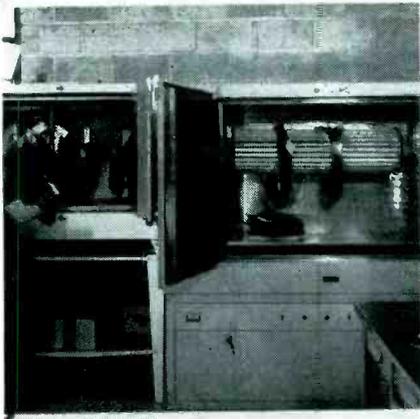


HEAT AGING OVEN. Samples of coax are placed in this oven and held at a temperature of 205° F for seven days.

involve factors such as the velocity of propagation of the cable, and in the case of more severe irregularities, a harmonic and subharmonic relationship.

In cable production, it is possible to control various parameters of extrusion to shift these irregularities outside of the range of a particular band of frequencies. However, an elaborate electronic control system has been devised to eliminate the variations entirely. Every foot of community-TV cable is subjected to sweep tests which require that the cable attenuation must remain within 5% of the nominal value at any given frequency in the entire *vlf* spectrum.

This is only one of the exacting requirements of cable such as is required for the distribution of TV signals. In addition, a minimum requirement has been established, following the standards set up by Washington in the specification covering *rf* coax cables; MIL-C-17B. Over a period of years, it has been found

(Continued on page 44)

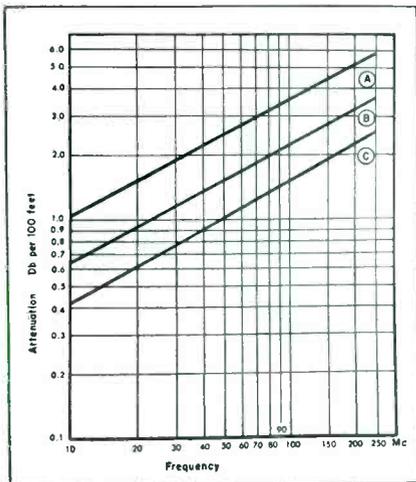

ATTENUATION VERSUS FREQUENCY plot for foam (c) and standard coax cables (a and b).

"SURE, I use **CLEAR BEAM** **Antenna Kits**...they've **doubled my installation business!**"

Using Clear Beam Antenna Kits makes sense right from the start! Attractive packaging and do-it-yourself label creates customer interest in a new or replacement antenna—makes it a cinch to sell complete installations.

Servicemen installing Clear Beam Antenna Kits have eliminated "loose stock" inventory problems and are now able to price installation jobs accurately and profitably due to fixed material costs!

Start doubling your installation business with Clear Beam Antenna Kits now. Display them in your shop—show them from your service truck—let Clear Beam's self-selling antenna kits clinch extra installation sales for you!





Kits for Conicals, Arrows, Yagis, Dipoles, UHF, VHF complete with mast, lead-in and all necessary hardware ready to install!



CLEAR ANTENNA CORP.,
BEAM CANOGA PARK, CALIF.

Warehouses in Seattle, Portland, San Francisco, Honolulu, Dallas, Kansas City, Detroit, Baltimore

SERVICE, NOVEMBER, 1956 • 43

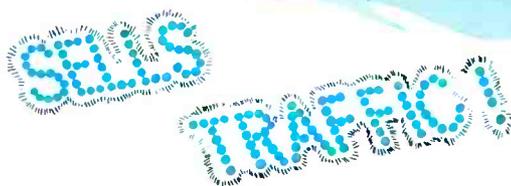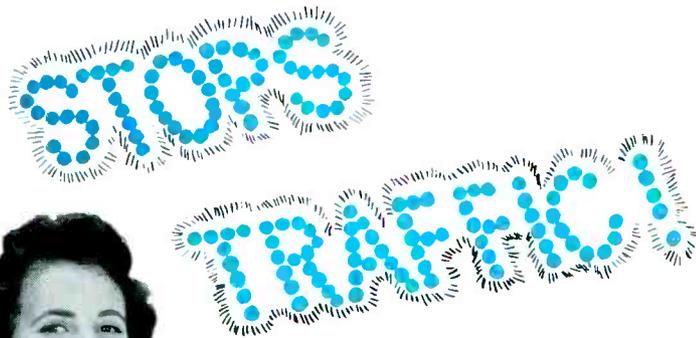

Capitalize on the growing two-set television market with this beautiful 5 color Telecoupler display.

Cash-in on the increased Christmas sales of both black & white and color tv sets by *displaying* and *selling* AMPHENOL's popular two-set coupler.



TELECOUPLER
by AMPHENOL

see your



distributor

TV Antennas

(Continued from page 43)

that this specification has satisfied the great majority of cable applications, and as a consequence they have been adopted as a minimum requirement, even for those cables which do not fall in the category of military nomenclature.


Such has been the case in the development of cables which use a semi-solid dielectric for the cable core. This dielectric is composed of minute particles of polyethylene, each of which contain an inert gas. These particles, when subjected to heat, will soften and enlarge as the gas expands. Upon cooling, the polyethylene again hardens, forming a permanent bubble, which in conjunction with millions of others, forms a solid, lightweight mass. This construction has been found to lend itself well to use as a cable core, since the volume of dielectric has been minimized. This, in turn, results in a cable with lower attenuation for a given size of cable inner and outer conductor.

The advantages of a foamed dielectric have long been recognized by cable manufacturers, but the control of this expanding dielectric during the extrusion process has presented a problem that has only recently been resolved. These foam-dielectric cables offer an opportunity to design a more passive system. The lower loss of these cables reduces the number of amplifiers required, thereby reducing the original system cost and the cost of subsequent maintenance.

Prior to the release of these cables, they are subjected to tests² in a

(Continued on page 46)

²Following the MIL-C-17B specification.

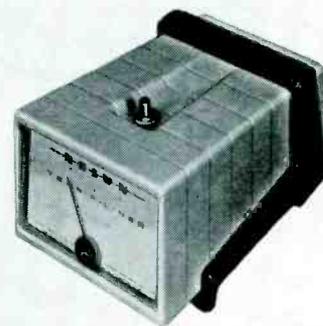

Antenna rotator control with dial designed to offer improved readability. Other features are said to be fingertip operation, and a positive action brake which is to prevent wind-milling and assure proper antenna alignment. (CAR6B Tenn-A-Liner; Crown Controls Co., Inc., New Bremen, O.)

Associations

ARTS, CHICAGO, ILL.

AT THE SEMI-ANNUAL business-election meeting of the Associated Radio and Television Servicemen, Chicago, Ill., *Howard Wolfson* was elected chairman for the '56-'57 fiscal year. *Joe Ehlinger* was named vice chairman; *Delmar Kotrba*, secretary-treasurer, and *George Neize*, sergeant-at-arms.

Member reps for the south, west, and north sections of the city were also appointed for the ensuing year. They are: *Martin Nebojsic*, *Anthony Bauman*, and *Yuki Minaga*.

RTASCV, Calif.

AL LIMBERATOS has been elected president of the Radio and Television Association of the Santa Clara Valley in California.

Newly elected board of directors include: *Bob Swift*, *Harold Kelly*, *Ben Floyd* and *Richard Kelso*. Reelected to the board for a second term were: *H. Lawrence Schmitt*, *Quentin Muchow*, *Tom Miner*, and *Jim Wright*.

Muchow was elected vice president and *Jim Wright* was reelected secretary. *Harold Kelly* is now sergeant-at-arms.

RTG, Long Island, N. Y.

AT THE FORTHCOMING electronics fair (Dec. 6-7-8) at the New York State University at Farmingdale, New York, under the sponsorship of the Radio and Television Guild of Long Island, over a dozen industry experts have been scheduled to appear.

Subjects to be covered include new developments in the Lawrence single-gun color tube, antenna design for b-w and color-TV, RCA color circuitry, the Sylvania color-TV receiver, test equipment for b-w and color-TV, and use of color test equipment and new transistor devices.

RTTA, Pasadena, Calif.


AT A RECENT MEETING of the Radio Television Technician Association, Pasadena, Calif. a proposed bill for licensing of Service Men and service dealers was presented. This bill is to be presented for enactment at the California State Legislature, under the auspices of the California State Electronics Association. At present, the measure is under discussion and consideration by allied groups of the state association. Copies of the proposed bill are being mailed to all members for study.

Installation of RTTA officers for '57 will be at a dinner-dance at the Altadena Country Club on January 12.

TEN YEARS AGO IN SERVICE

THE FIRST COMPLETE explanation of the TV service plans that would be set up by set makers, detailed during a TV clinic program arranged by *ye ed* at the Waldorf Astoria Hotel in New York City, appeared in an exclusive SERVICE report. *W. L. Parkinson*, speaking for G. E., and *W. L. Jones*, spokesman for RCA Service Company, disclosed that their companies would enter the contract business for installation and repair. *Ernest Marx*, commenting on the DuMont plan, said that the independent service shop would be used, but a contract arrangement might possibly be set up. Typical problems that would be encountered in the field, and time and material involved in making repairs, were covered by *George Duvall* of Television Technicians, Inc. . . . Webster-Chicago Corp. demonstrated a wire recorder offering 50 minutes of recording time. . . . FTR released a series of booklets and counter displays on its miniature selenium rectifiers. . . . *Kenneth C. Prince*, show manager of Radio Parts and Electronic Equipment Shows, Inc., announced members of the board for the May, 1947 show. Serving on the board were: *Jack Berman*, Shure Brothers; *Charles Golenpaul*, Aerovox; *Jerome J. Kahn*, Standard Transformer Corp.; *Sam Poncher*, Newark Electric; *Walter Jablon*, Hammarlund Manufacturing; *Robert C. Sprague*, Sprague Products; *R. J. Sherwood*, Hallicrafters; and *William L. Schoning*, Lukko Sales Corp.

what's a square foot

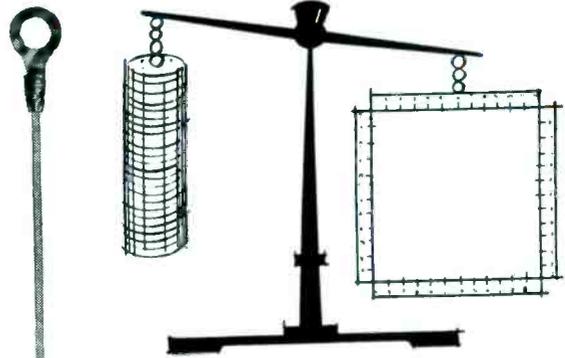

worth to you?

api can increase its
Trade Mark
productive value!

API's local inventory and service facilities can help you increase square foot floor space value for productive uses by eliminating heavy warehousing requirements.

At any of API's local inventory and service centers, you will find a wide variety of A-MP® Terminals, Connectors and Tools to meet all your service requirements. Order only the amount to satisfy your service needs. Call API's nearest branch office for inventory, service and technical assistance!

In addition to branch offices, API maintains a group of local telephone information centers for your convenience.

api
Trade Mark

dependability 2 ways

The product and the product knowledge of the API man who serves you.

AMERICAN PAMCOR, INC.

Subsidiary of Aircraft-Marine Products, Inc.
181 Hillcrest Ave., Havertown, Pa.


*Hawthorne, Calif.	*Minneapolis, Minn.	*Dayton, O.
*San Francisco, Calif.	*Kansas City, Mo.	*Portland, Ore.
*Washington, D.C.	*St. Louis, Mo.	*Philadelphia, Pa.
*Atlanta, Ga.	*Maplewood, N.J.	*Pittsburgh, Pa.
*Chicago, Ill.	*Albany, N.Y.	*Knoxville, Tenn.
*Indianapolis, Ind.	*Buffalo, N.Y.	*Dallas, Tex.
*Baltimore, Md.	*Charlotte, N.C.	*Richmond, Va.
*Boston, Mass.	*Cincinnati, O.	*Huntington, W. Va.
*Detroit, Mich.	*Cleveland, O.	*Milwaukee, Wis.

*Consult the yellow pages of your local telephone directory under AMERICAN PAMCOR, INC., for local telephone center number.

New! Revolutionary!

SECO TUBE TESTER

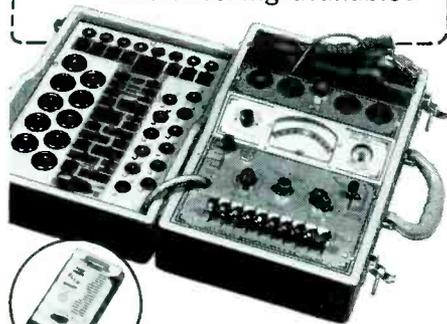offers most complete tube checking available!



New! Faster! Tube set-up chart for all current tubes.



Contained in handsome portable carrying case!

1. Grid-Circuit Test—all tubes
2. Dynamic Mutual Conductance Test on pre-wired panel
3. Cathode Emission Test by free point selector system

Outstanding performance and accuracy . . . wide range . . . saves you valuable time by eliminating call-backs due to obsolete or incomplete testing. Justifiably culls and sells more tubes for you.

Dynamic Mutual Conductance Test of all popular radio and TV amplifier tubes made on pre-wired chassis. Designed for speed — tube set-up data printed on panel. Master unit provides Cathode Emission Test for all tubes. Both units incorporate nationally accepted grid-circuit test developed by Seco. Handy new "flip-chart" lists complete tube set-up data. Fast . . . easy to use . . . operates like telephone index. Completely self-contained — mounted in handsome light green carrying case. Easily portable — only 13½" x 9" x 6" — weight 11½ pounds. Model 107 Tube Tester . . . \$139.50 Net



Dependable! Accurate! Quickly spots grid errors and leakage in critical amplifier tubes!

Model GCT-5 Grid-Circuit TUBE TESTER

Checks over 95% of all tubes subject to "control grid error." Saves valuable service time . . . electron ray tube indicates faults at a glance! Just 6½" x 6½" x 2½" . . . weight: 4 pounds.

Wired and tested . . . \$29.95 Net
Complete, easy to assemble kit . . . \$19.95 Net



No disconnecting! No charting! Checks complete horizontal coil circuit — not just individual components!

Model FB-4 FLYBACK CIRCUIT and INDUCTANCE ANALYZER

Nothing faster . . . 100% accuracy. Checks complete horizontal coil circuit . . . not subject to obsolescence due to variables in engineering design.

Model FB-4 . . . \$38.95 Net

WRITE TODAY! Clip and mail the handy coupon for complete information and descriptive literature on all Seco test instruments.



MANUFACTURING CO.
5015 Penn Ave. So., Minneapolis, Minn.

Name _____
Address _____
City _____ State _____


TV Antennas

(Continued from page 44)

quality-control laboratory. Upon completion of every 5,000 to 10,000 feet of continuous cable, a 110-foot sample is sent to the quality-control lab. After complete dimensional checks the cable is tested for such important quality factors as nominal impedance, velocity of propagation, attenuation at ultrahigh frequency, nominal capacitance, low capacitance unbalance, absence of cracks and fractures of dielectric and jacket after cold bend tests, close centering, minimum displacement of inner conductor after flow test, attenuation stability, capacitance stability and absence of corona effect at high voltage.

Many of these tests are of specific interest to the community-TV operator since they assure him of satisfactory cable performance under some of the conditions peculiar to his application. Since these cables will be exposed to the elements and will be subjected to a wide range of temperatures, the heat aging, flow and cold bend test are of considerable significance.

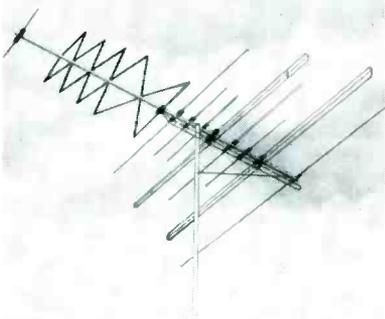In the heat-aging test, a sample of the cable is placed in the oven and held at a temperature of 98°C (205°F) for a period of seven days. At the conclusion of this period, the



Helix-type antenna designed for both color and b-w performance in deep fringe areas. On the low band the antenna utilizes a pair of double driven folded dipoles phased for signal addition. A reflector, director and deflector (director-reflector) are used to flatten the bandpass characteristic at a high level. Since the loading effect of these elements would bring the impedance down, the dipoles themselves are 600-ohm units said to make possible a close impedance match. By maintaining an inline yagi-type configuration construction, the dual receiving elements are shielded by reflectors to realize maximum back rejection and minimum wind resistance. The helical section is composed of individual non-linear additive collectors each tuned separately for a high band channel. (Wonder-Helix Colortenna; JFD Manufacturing Co., Inc., 6101 16th Avenue, Brooklyn 4, N. Y.)



NOW! INSTANT SOLDER GUN and COMPLETE "DO-IT-YOURSELF" KIT

FOR HUNDREDS OF RADIO, TV AND HOMECRAFT JOBS

SOLDER GUN ONLY — MODEL G14 \$7.95
BEST KIT VALUE! MODEL G14K \$8.95

Includes:

- ✓ 150-Watt Instant Solder Gun Model G14
- ✓ Cutting Tip for plastic tile, old putty, toys, etc.
- ✓ Smoothing Tip for furniture scratches, sealing, etc.
- ✓ Famous Kester TV-Radio Resin Core Solder
- ✓ Sandpaper for cleaning parts

"You'll like the way it HANDLES!"

COMBINES ALL THE ADVANTAGES OF THE SOLDER GUN AND THE CONVENTIONAL SOLDERING IRON. No waiting — press trigger and solder of once. Ideal tool for shop or home use. Takes only half the space of transformer guns in tool boxes.
120 Volts AC-DC ¼" Tip (also available ⅜" Tip)

COMPARE THESE FEATURES WITH ORDINARY SOLDER GUNS!

- POWER PACKED—150 Watts
- NO HEAVY TRANSFORMER — weighs only 8 oz.
- STURDY LIFETIME TIP — no soft fragile wire
- HEAT RIGHT IN TIP — new unique element design
- LONGER, THINNER REACH — EFFECTIVE SPOTLITE

HEXACON ELECTRIC COMPANY
594 WEST CLAY AVENUE, ROSELLE PARK, NEW JERSEY

Serving Craftsmen for a Quarter of a Century

NEW Senco TRANSISTOR CHECKER

NOW WANTED and NEEDED by EVERY SERVICEMAN!

Quickly and accurately checks all transistors and crystal diodes.

Provides these 4 important checks on transistors:
OPEN • SHORT
CURRENT GAIN
LEAKAGE


Checks forward to backward resistance of diodes

★ Complete set-up chart and instruction booklet attached to back

★ Will never become obsolete, with test leads, replaceable up-to-date set-up chart and gain control to vary battery voltage

★ Accurate and simple to operate — takes less than 30 seconds to test either TRANSISTORS or crystal diodes

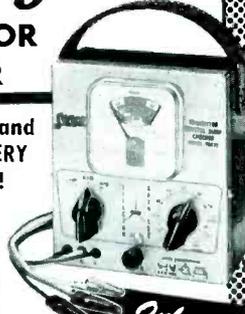★ Uses test leads which eliminates need of completely removing transistor from circuit
At leading distributors everywhere



Only \$15.95

DEALER NET
Approved by leading manufacturers

SERVICE INSTRUMENTS CO.
171 OFFICIAL RD • ADDISON, ILL.

cable is wound and unwound ten times from a test mandrel whose diameter is approximately 10 times the outside diameter of the cable. The jacket and core material must then show no loss of pliability or signs of cracking.


The flow test is also conducted in this oven, and its purpose is to assure minimum migration of the center conductor under extreme conditions. A length of cable is hung over a horizontal mandrel, whose diameter is 10 times the outer diameter of the cable. Specified weights are hung from each end of the center conductor and the assembly is then subjected to a heat of 98°C (205°F) for a period of 7½ hours. After this, the assembly is allowed to cool in position and then X-rayed to ascertain that any center conductor migration is within specified limits.

Low Temperature Tests

To eliminate the possibility of cable failure due to cracking of the jacket or core at extremely low temperatures, the cable is subjected to a cold bend test. First, a length of cable is conditioned at a temperature of -40°C (-40°F) for a period of one hour in a cold box. While still in the cold box, the cable is wound around a mandrel ten times the cable diameter, at a rate of 15 rpm. The appearance of cracks or fractures in either the core or jacket constitute reason for rejection of the entire cable run. Even after these tests, still another test is conducted just prior to placing the cable on shipping reels. In this case, a high voltage is applied between the shield braid and the outer surface of the jacket. Every foot of cable is so tested, and a puncture of the jacket by the applied voltage requires that the faulty cable be cut out and rejected.

Outdoor Tests

To evaluate further cable performance, there has been established an outdoor test facility where cables are actually strung on specially prepared utility poles for study under actual field conditions. One of the current projects is the determination of cable radiation characteristics which is of considerable interest to community-TV system operators, now that the FCC has issued specific regulations concerning same. Results of these tests will provide cable users added assurance that they can design systems to conform to applicable requirements.

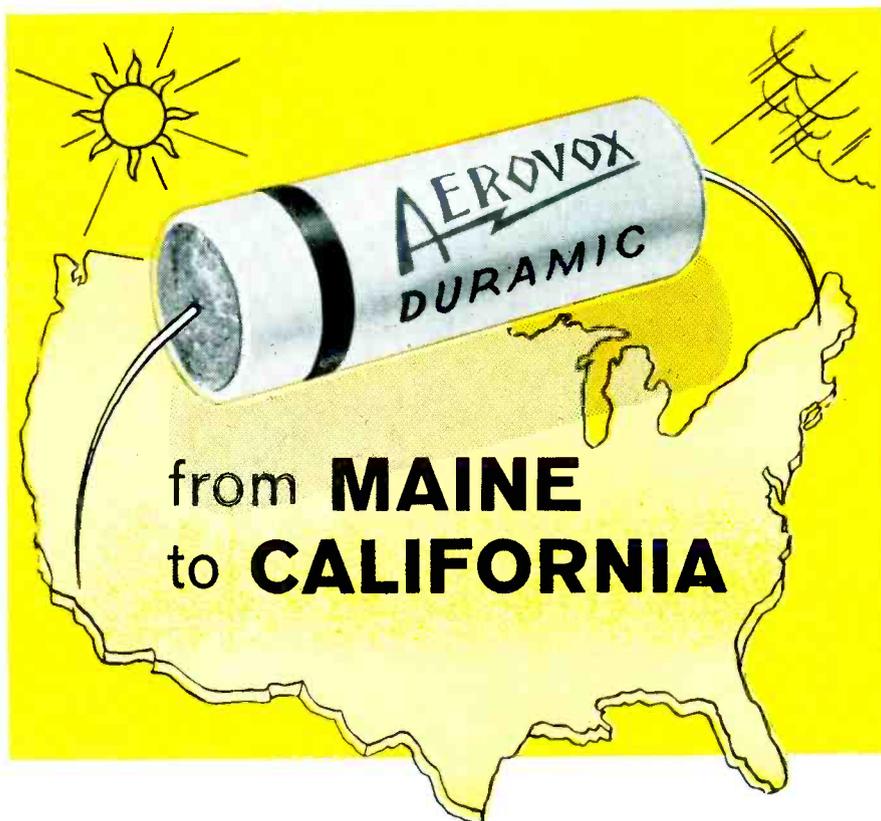

Servicemen everywhere are acclaiming the outstanding performance of Aerovox "DURAMICS"—ceramic-cased tubular capacitors. No matter what the weather conditions... hot-and-humid or cold-and-damp... these superior capacitors have provided outstanding performance without costly call-backs.

HERE ARE THE REASONS FOR SUCH OUTSTANDING PERFORMANCE CHARACTERISTICS:

- ★ Dense steatite case provides exceptional protection against humidity.
- ★ Terminal lead wires are firmly imbedded into the end seals and will not work loose or pull out under the most severe operating conditions.
- ★ Operating temperatures from -55°C to +85°C.
- ★ Exclusive Aerovox end-fill will not separate from case nor soften or flow at any rated temperature.
- ★ Excellent power-factor, insulation resistance and temperature coefficient characteristics.
- ★ Available in 10 standard voltage ratings from 200 to 15,000 VDC.

AEROVOX TYPE P84CM CAPACITORS are always in stock at your local Aerovox Distributor in a complete range of capacitance values and voltage ratings. Popularly priced. Write today for your copy of the latest Aerovox catalog or ask your distributor.




AEROVOX CORPORATION

DISTRIBUTOR SALES DIVISION,
NEW BEDFORD, MASS.

In Canada: AEROVOX CANADA LTD., Hamilton, Ont.
Export: Ad Auriema, 89 Broad St., New York, N. Y., Cable: Auriema, N. Y.

Mr. Electronic Service Technician

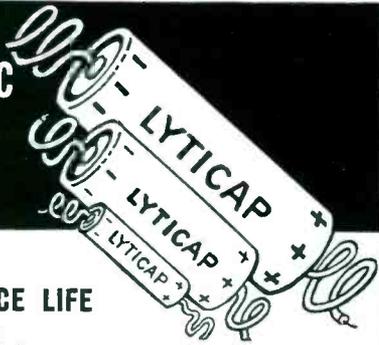

FOR LONGER SERVICE LIFE
you can rely on . . .

LYTICAP* ELECTROLYTIC CAPACITORS

You can recognize PLANET LYTICAPS by their shiny red cardboard jackets and their general neat workmanlike appearance. Available in all frequently used capacities from 3 to 500 volts, they are ideal for all types of service work—radio—television—industrial.

PLANET LYTICAPS are 100% tested for capacity and leakage; they receive a rigid mechanical inspection. Like all Planet products, they are fully guaranteed for one year. No wonder so many set manufacturers use them as original equipment!

Ask for PLANET LYTICAPS by name at your regular parts jobber.

*Registered

PLANET SALES CORP.
BLOOMFIELD, N. J.

XCELITE Hand Tools
PREFERRED BY THE EXPERTS

SOMETHING NEW (AND BETTER) IN FLUSH CUTOFF!

For your flush cutoff work in miniatures and subminiatures, the popular new XCELITE No. 62 Transverse Cutter gets into small spaces and can be operated with thumb and finger only. Its new coil return spring is out of the way, and permits sliding insulating sleeves on handles. Ask your supplier!



XCELITE
INCORPORATED
Dept. V
Orchard Park
New York

Canadian Representative:
Charles W. Pointon, Ltd.
6 Alcina Avenue
Toronto, Ont.



For Originality
LOOK TO **XCELITE**

Transistor—Tube Tester

(Continued from page 21)

tion ratio by the following expressions:

$$\beta = \frac{\alpha_{cc}}{1 - \alpha_{cc}} \quad \alpha_{cc} = \frac{\beta}{1 + \beta}$$

Either quantity may be specified by the manufacturer, depending upon the use for which the transistor is intended. In either case, present manufacturing tolerances are very broad; therefore even if a transistor falls outside of the indicated range, it may still be usable. In all cases considerable latitude should be given before a transistor is discarded as defective.

Collector-Base Amp Factor

In this test a small current is applied to the base by means of a 200,000-ohm resistor to permit the measurement of the collector-to-base amplification factor.

These tests will determine if the transistor is good or bad, but will not, of course, duplicate the factory tests of frequency response, input or out-

put resistance, collector capacitance and other characteristics that are necessary for specific grades of transistor.

This transistor tester also provides for tube tests for 4, 5, 6, 7-pin octal and loctal, miniature 7 and 9 pin, also subminiature 5, 6 and 7 pin (in

line base) and 8-pin (circular base) types.

Leakage Readings

Direct reading of interelectrode and cathode-to-heater leakage can be measured in ohms on a 0 to 20-megohm scale meter. A filtered *dc* voltage of -70 is obtained by rectifying and filtering 50 *v ac* obtained from the filament-winding tap. This voltage is applied between the tube element, isolated by its transfer switch and the remaining tube elements, whose lever switches are set at the plate, screen and grid voltage buses, which are grounded through the merit leakage switches at their normal positions. The current through the circuit is measured in ohms on the meter.

Emission Information

In general, each test furnishes a composite indication of cathode-emission capability and the ability of each grid to control the plate current, in accordance with the design of the tube, plus the ability of the plate to receive the regulated current. For diodes and rectifiers the test is an


**Don't just say
capacitors**

Ask For Sprague By
Catalog Number

Know what you're getting . . . get exactly what you want. Don't be vague . . . insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 61 Marshall Street, North Adams, Mass.


SPRAGUE
WORLD'S LARGEST
CAPACITOR MANUFACTURER

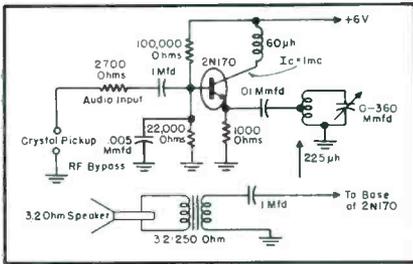emission test. To test properly a variety of tube types several plate, screen and grid voltage ranges are available from taps on the plate secondary winding of the transformer.




ABOVE: PHONO OSCILLATOR using 2N170 transistor. Range is 6" to 20". For a mike input, circuit at bottom should be used in place of crystal pickup and resistor.

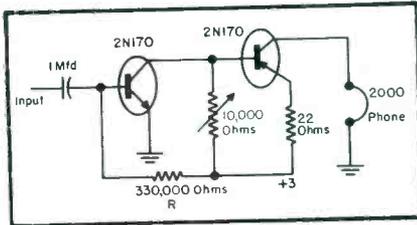BELOW: TRANSISTORIZED direct-coupled battery-saver amplifier. R must be adjusted for maximum results.



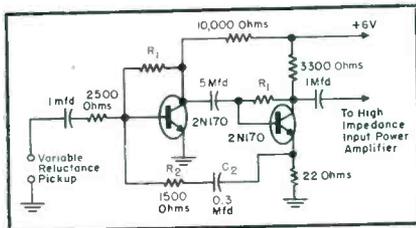BELOW: TRANSISTOR VARIABLE reluctance compensated preamp. R₁ (100,900 to 500,000 ohms) should be chosen to produce collector voltage of 2.5 to 3.5. Changing C₁ and R₂ will vary compensation curve. (Diagrams courtesy G.E.)



Vertical Instability Cures

(Continued from page 13)

the 60-cycle voltage impressed on the cathode through the leakage was overpowering the tiny sync pulses and causing the oscillator to lock at the local line frequency, instead of with the sync pulses.

One troublesome chassis with hold troubles, using two halves of a 6SN7 in sync amplifier stages, delivered an odd-looking vertical sync pulse, as seen on the blanking bar; it was weak and washed-out in appearance and quite distorted. The familiar hammer-head looked more like a geologist's rock-hammer. Checking the sync pulses at the oscillator stage con-



need a TV TRANSFORMER?



need an exact replacement?



wonder where to get it?



STANCOR TRANSFORMERS

are AVAILABLE from better distributors EVERYWHERE!

FREE

The latest Stancor TV Replacement Guide and Catalog listing replacements for over 9000 TV models and chassis.



CHICAGO STANDARD TRANSFORMER CORPORATION

3507 ADDISON STREET, CHICAGO 18, ILLINOIS


Export Sales: Roburn Agencies, Inc.
431 Greenwich St., New York 13, N. Y.

firmed a suspicion; they were very weak. Tracing them back through the two sync separator stages showed that these stages were apparently alright; there seemed to be plenty of video signal applied to them. At the video amplifier plate the scope picture seemed to be alright at first, but a comparison with the waveform shown on the schematic showed that there were differences, especially about the sync pulses, etc. At a glance the picture seemed to be fairly good, until the position of the contrast con-

trol was checked. It was turned all the way up. At this point the voltages were measured on all stages concerned and the video amplifier plate voltage was found quite low. Resistance measurements showed that the first peaking coil, a small unit wound on a 5000-ohm resistor, was open. This not only lowered the plate voltage, causing the picture on the screen to be washed out, but also lowered the vertical sync amplitude to the point where it no longer had control over the oscillator.

SAVE with SECURITY

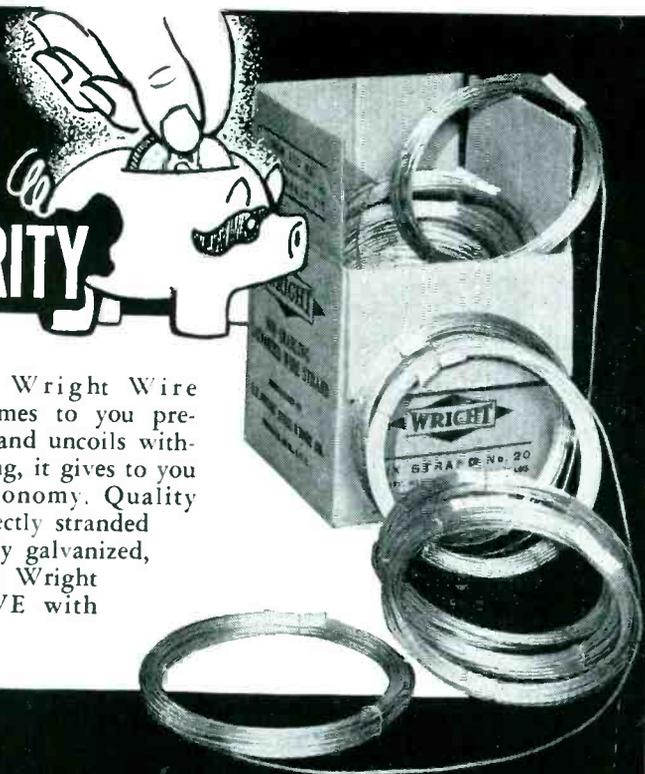Because Wright Wire Strand comes to you pre-measured and uncoils without snarling, it gives to you unique economy. Quality wire, perfectly stranded and heavily galvanized, the bright Wright way. SAVE with Wright.



Prompt deliveries from stocks in Worcester, Chicago, Atlanta, New Orleans, Houston, Dallas and Los Angeles.

G. F. WRIGHT STEEL & WIRE CO.
249 Stafford St. • Worcester, Mass.

for service and lab. work

Heathkit PRINTED CIRCUIT OSCILLOSCOPE KIT FOR COLOR TVI

① Check the outstanding engineering design of this modern printed circuit Scope. Designed for color TV work, ideal for critical Laboratory applications. Frequency response essentially flat from 5 cycles to 5 Mc down only 1½ db at 3.58 Mc (TV color burst sync frequency). Down only 5 db at 5 Mc. New sweep generator 20-500,000 cycles, 5 times the range usually offered. Will sync wave form display up to 5 Mc and better. Printed circuit boards stabilize performance specifications and cut assembly time in half. Formerly available only in costly Lab type Scope. Features horizontal trace expansion for observation of pulse detail — retrace blanking amplifier — voltage regulated power supply — 3 step frequency compensated vertical input — low capacity nylon bushings on panel terminals — plus a host of other fine features. Combines peak performance and fine engineering features with low kit cost!



MODEL
Q-10
\$695.00
Shpg. Wt.
27 lbs.



MODEL
TS-4
\$495.00
Shpg. Wt.
16 lbs.

Heathkit TV

SWEEP GENERATOR KIT ELECTRONIC SWEEP SYSTEM

② A new Heathkit sweep generator covering all frequencies encountered in TV service work (color or monochrome). FM frequencies too! 4 Mc — 220 Mc on fundamentals, harmonics up to 880 Mc. Smoothly controllable all-electronic sweep system. Nothing mechanical to vibrate or wear out. Crystal controlled 4.5 Mc fixed marker and separate variable marker 19-60 Mc on fundamentals and 57-180 Mc on calibrated harmonics. Plug-in crystal included. Blanking and phasing controls — automatic constant amplitude output circuit — efficient attenuation — maximum RF output well over .1 volt — vastly improved linearity. Easily your best buy in sweep generators.

Heath
COMPANY
A SUBSIDIARY OF DAYSTROM, INC.
BENTON HARBOR 11, MICH.

WRITE FOR FREE CATALOG
... COMPLETE INFORMATION

COMPONENTS

PRINTED WIRING ELECTROLYTICS

Hermetically-sealed electrolytic capacitors, EY, designed for printed-wiring boards and automatic assemblies, have been announced by Astron Corp., 255 Grant Ave., E. Newark, N. J.

Units are said to use pure foil and a high-grain etch process.

CLOCK-RADIO REPLACEMENT KNOBS

A line of clock radio replacement knobs, consisting of four types (including a metal jacket double-barrier style in gold), has been announced by Geelar Manufacturing Co., 400 S. Wyman St., Rockford, Ill.

Other knob styles are plastic and available in six colors; included in the line are single and double barrier and spring types. A kit, 1630, containing an assortment of 25 knobs is available through parts distributors.

PUSH-PULL SWITCH CONTROL

A push-pull switch control that serves to turn controls on or off at any given setting has been introduced by the Clarostat Manufacturing Co., Inc., Dover, N. H.

Unit can be combined with Series 47 composition element 15/16" diameter controls. Has concentric shaft which push-pulls for switching action and rotates for control setting, each function being independent of the other.

Switch is available in three types: Series AG-17 SPST, .5 amp 125 v dc or 1 amp 125 v ac; Series AG-18 SPST, .5 amp 125 v dc or 3 amp 125 v ac; Series AG-19 SPST, .5 amp 125 v ac.

UNIVERSAL REPLACEMENT KNOBS


A line of universal replacement knobs, featuring a variety of stem lengths and types, has been developed by Colman Tool and Machine Co., Amarillo, Tex.

Featured are a number of knob heads that can be assembled with any one of an assortment of stems. Available in stock assortments of two sizes and ten colors.

SILVERED MICA CAPACITORS

A replacement kit of TV-high-voltage silvered micas, No. 14, has been announced by Arco Electronics, Inc., 64 White St., N. Y. 13, N. Y.

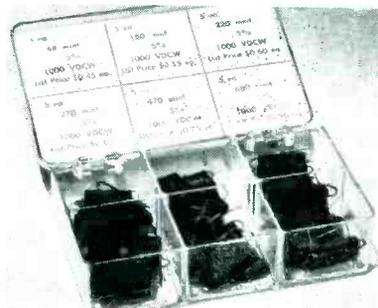Kit contains five each of 68,180, 220, 270, 470 and 680- mmfd capacitors. Supplied in plastic container.



Service Engineering

(Continued from page 31)

the crystal frequency. It is desirable, however, to provide a tuning indicator which will allow non-technical personnel to tune for maximum output.

The arrangement described has been found to achieve this, with no sacrifice in starting characteristic, by the non-linear behavior of the glow lamp. During the build-up period of starting oscillation, the rf voltage is below that required for the lamp to strike. The stray capacitance contributed by the lamp is slightly less under this condition, than when the lamp is glowing and therefore the tank circuit is tuned to a slightly higher frequency. Thus, starting is assured and, as the lamp strikes, the tank resonance is automatically shifted toward the highest output adjustment. Adjustment of the tank circuit to achieve proper starting is thus a natural consequence of resonating the tank for maximum brightness of the glow lamp.

Transmitter Antenna

The transmitter antenna consists of a short wire embedded in fibreglass and integrally connected to a coax cable and fittings for mounting and plugging into the transmitter. The entire assembly including the signal radiating surface has been designed for under-car installation. The fractional wavelength radiator is matched to the transmitter by the coax line.

The receiver uses a 6BA6, 12AU7A and 2D21;

(Continued on page 53)

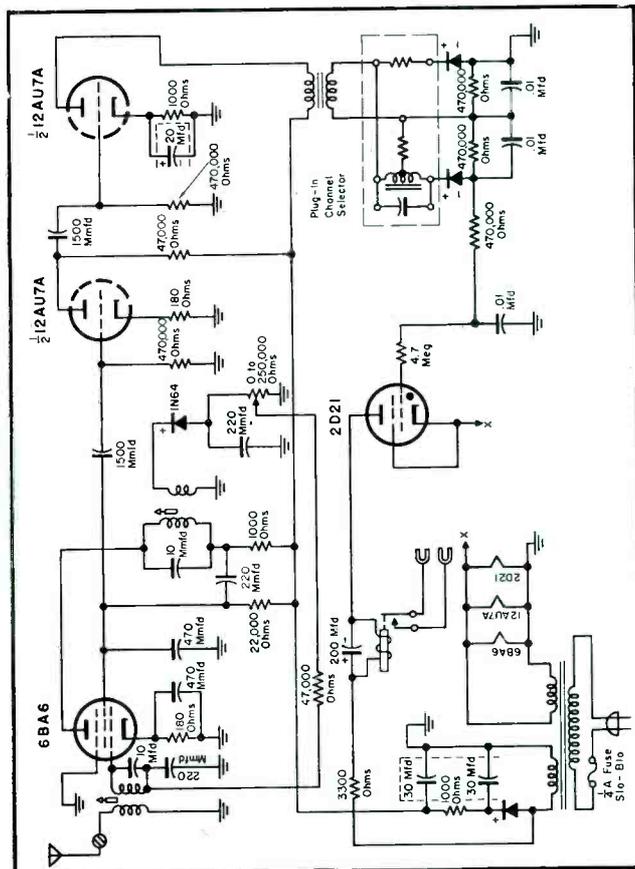


DIAGRAM of receiver developed for remote-control garage-door opener.

PHILCO

The World's Largest
Field Service Organization

WANTS

Electronic Engineers, Radar
and Communications Men at
All Levels and In All
Fields of Electronics

YOU FOR IMMEDIATE OPENINGS!



● As the Pioneer in the servicing of electronic equipment, PHILCO has an interesting variety of BOTH Commercial and Government operations to be serviced on a long range basis. To men who possess the ability and/or educational background necessary to Design, Maintain and/or Instruct others in the fields of Communication, Radar and Sonar equipment this combination provides BOTH challenging opportunities and employment security.

What's more . . . in addition to TOP PAY commensurate with your ability to do a better than average job, PHILCO has many valuable company benefits which are acclaimed as "THE BEST IN THE INDUSTRY." But, why not find out for yourself . . . TODAY!

WRITE NOW FOR OUR
NEW 22 PAGE, FULL COLOR BOOKLET
'FIRST In Employment Opportunities...'


Dept. 14A
PHILCO TECHREP DIV.
22nd & Lehigh Ave.
Philadelphia 32, Pa.

Please send me your booklet, "Philco TechRep Division, FIRST In Employment Opportunities The World Over."

NAME _____
ADDRESS _____
CITY _____
FIELD OF INTEREST _____

PHILCO TECHREP DIV.
22nd & Lehigh Avenue • Phila. 32, Pa.

KESTER

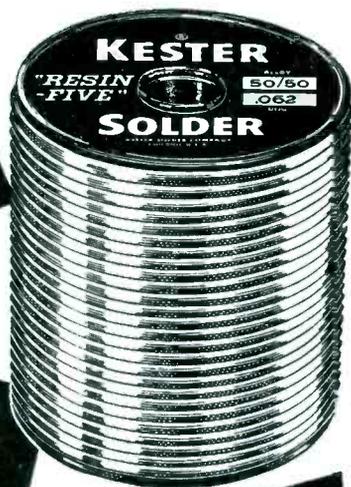

Absolutely non-corrosive and non-conductive, KESTER "RESIN-FIVE" CORE SOLDER contains an activated type of resin that gives you that fast, positive action on all your jobs . . . including the most difficult.



KESTER SOLDER COMPANY
4248 Wrightwood Avenue • Chicago 39, Illinois
Newark 5, New Jersey • Branford, Canada

SOLDER

BENCH-FIELD TOOLS

PW SERVICING KIT

A printed-wiring board servicing kit, 13-K, has been introduced by Walsco Electronics Corp., 3225 Exposition Place, Los Angeles 18, Calif.

Contains *solder-ease* tool with probe for tightening contacts and a fork on opposite end to handle wires while soldering; silicone resin lacquer; copper foil with thermoplastic backing; solder wires and washers with a flux layer; tweezers; fiberglass brush and solder solvent. Another kit, 12-K, includes an Ungar soldering iron, a special tip, a can of spray lacquer and a practice wiring board.



SELFHOLDING CONNECTOR TEST PROBE

An insulated probe equipped with a selfholding connector has been developed by E-Z Hook Test Products, 1536 Woodburn Ave., Covington, Ky.

Probe features hook type design. Has a built-in terminal board that can be used to assemble test probe setups.



SOLDERING/ELECTRICAL KIT

A soldering and electrical kit, 507, has been introduced by Ungar Electric Tool Co., 4101 Redwood Ave., Los Angeles 66, Calif.

Kit contains a heavy-duty pencil soldering handle, heavy work and precision tips, electrical terminals, trouble light, circuit tester, electrician's tape, resin core solder and a 20-page manual. Package is supplied with a protective slip cover.



THE PROFIT TRIO!

MAKES VISUAL ALIGNING
QUICK, SIMPLE, PROFITABLE



MODEL 983—Oscilloscope



MODEL 984—Sweep Generator



MODEL 985—Calibrator

Here are the three instruments that enable you to align by the WESTON *Simplified* method . . . the method that cuts alignment time in half, and thus makes this job highly profitable for servicemen. Ask your distributor for all the facts or write for the Test Equipment bulletin — R 36-A. WESTON Electrical Instrument Corporation, 614 Frelinghuysen Avenue, Newark 5, New Jersey. A subsidiary of Daystrom, Inc.

WESTON
TEST EQUIPMENT

The Quality Line

Service Engineering

(Continued from page 51)

a germanium diode (1N64) for signal detection; two small selenium diodes (1S1) in the tone selector network; and a selenium rectifier (H50B) in the power supply.

A simple half-wave (8' wire) antenna is connected to an input tuned circuit. The signal is amplified by a fixed frequency, screen-grid-neutralized 6BA6 stage.


Diode RF Detector

A germanium diode serves as an *rf* detector, with a potentiometer load resistance functioning as a sensitivity (distance) control. The detected signal is fed back to the 6BA6 grid along with the *avc* voltage and further amplified by reflex action with the screen-grid functioning as a triode plate.

Audio signal voltage from the 6BA6 screen is fed to a resistance-coupled amplifier ($\frac{1}{2}$ 12AU7A) and then to a transformer-coupled stage ($\frac{1}{2}$ 12AU7A), which drives the decoding or tone-selecting apparatus. The secondary of the transformer feeds the signal to the decoding circuit; this circuit operates in conjunction with the 2D21, which is used to actuate a relay connected in the plate circuit. The circuit operates in such a manner that a certain *yes-no* bandwidth is achieved where *yes* and *no* correspond to relay contacts closed and open, respectively. A tone corresponding to the frequency of the plug-in channel selector will cause operation of the relay. If the signal level rises to a value equal to twice the threshold level, the tone frequency will also cause operation of the relay when it is varied approximately at 3% of the exact channel frequency, but will not operate the relay at deviations greater than about 5% from the center frequency, even if the level goes up to the maximum that is obtainable when the signal is limited by *avc* action and saturation of the audio amplifier.

The signal from the secondary of the audio transformer is applied to two channels in the decoding network. One channel is essentially *all-pass*, and the other is a very selective band-stop filter. The output from each channel is rectified and combined in series in such a manner that the net output, when there is no at-

(Continued on page 61)

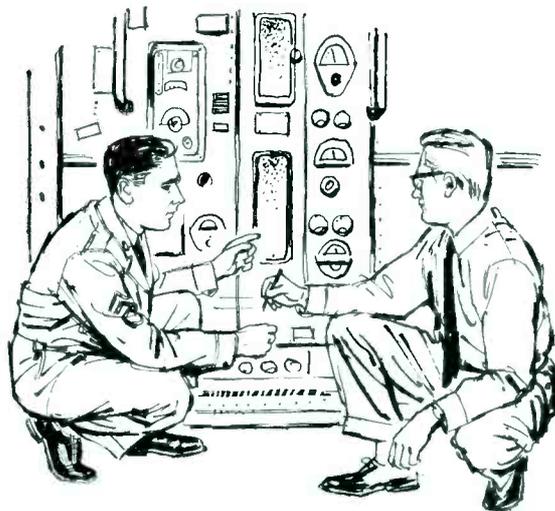

TODAY...

A TECHNICIAN

TOMORROW...

*AN RCA FIELD
ENGINEER!*

HOW ABOUT YOU? Many technicians have the knowledge and experience that can immediately qualify them as Field Engineers with RCA! Now is the time to find out whether you can make the big step up to Field Engineering with RCA.

As an RCA Field Engineer, you'll be responsible to advise and assist the military in the installation, maintenance and use of:

**HEAVY GROUND RADAR
AIRBORNE FIRE CONTROL RADAR
COMMUNICATIONS EQUIPMENT**

You may be assigned to one of many military installations in this country, or overseas. Liberal RCA benefit program adds security . . . a Tuition Refund Plan makes continued education easy . . . relocation assistance, too.

Arrange confidential interview with representative of RCA Engineering Management at a location convenient to you.



Please send complete resume to:
Mr. James Bell
Employment Manager, Dept. Y-11L
RCA Service Company, Inc.
Cherry Hill, Camden 8, N. J.

RCA SERVICE COMPANY, INC.

CERAMIC CARTRIDGES



LOADED with PROFIT

- Lightweight, miniature size, greater compliance
- New mechanical construction gives higher output
- New "throw-away" element
- Simple replacement, snap-in action
- Assorted stock orders totaled for maximum discount
- "Clearamic"—The "new look in good listening"

New Turnover Type



Response . . . 40-12,000 cycles
Output . . . 1-1.2 volts

New Single Needle Type



Response . . . 40-12,000 cycles
Output . . . 1-1.2 volts

Turnover type features "throw-away" element offering snap-in replacement of both element and needle assembly for essentially the price of a good replacement needle. Single needle type features simplified self-locating needle replacement.

Ask for the handy new "dispenser" assortment — meets almost all replacement needs.



ELECTRONICS DIVISION

ELGIN NATIONAL WATCH COMPANY

For Cartridges:

2435 N. NAOMI STREET,
BURBANK, CALIFORNIA

Sales representatives in principal cities.

Audio

(Continued from page 20)

70-volt tapping just provided so as to attract the public-address market.

Such an amplifier will work of course, but reasonably satisfactory performance of the amplifier may be dependent upon accurate loading, by using, say, 16 ohms on the 16-ohm tap. This amplifier would not be very satisfactory for use in public-address work, where maybe only 5 or 10 watts would be taken from the 70-volt line out of the amplifiers's maximum rating of, say, 25 or 30 watts.

Tube Types

Tube types represent a key design factor to study carefully before selecting a commercial sound amplifier. Some amps use a straight pentode output, either single ended or push-pull (most of the large power units, of course, being pushpull) with single overall feedback loop. This amplifier has a serious disadvantage for public address work; its stability characteristics are fairly critically, dependent upon the output being correctly loaded.

The amplifier may not oscillate with any value of load from nominal to open circuit, but this does not mean that its frequency response will be accepted under all these conditions, nor will its distortion necessarily maintain the low value given in the specification.

So, in selecting an amplifier for public-address work, it is important to examine the schematic and note the type of output used.

If a straight pushpull pentode with overall feedback, is used (Fig. 1;



"Oh, him, sir?
He's carrying the
JENSEN NEEDLES."

When . . . You Change Your Address

▶ Be sure to notify the Subscription Department of SERVICE at 52 Vanderbilt Avenue, New York 17, N. Y., giving the old as well as the new address, enclose address labels from your last SERVICE copy, and do this at least four weeks in advance.

▶ The Post Office Department does not forward magazines unless you pay additional postage, and we cannot duplicate copies mailed to the old address.

▶ We ask your cooperation.

THE NEW

No-Noise

TUNER-TONIC

Volume Control and Contact Restorer with Perma-Film

2 oz. bottle. Net to servicemen

\$1.00



Cleans, lubricates, protects not a carbon-tet solution. Still available in the new 6 oz. spray can.

Net to servicemen—\$2.25

"NO NOISE"

Also available in 8 oz. bottles and quart cans. At your nearest distributor.


with PERMA-FILM

Cleans, lubricates, restores all tuners including wafer type. Won't change or affect capacities, inductance or resistance. Won't harm insulations or precious metals, nor attack plastics. For television, radio and FM. Eliminates all noise, oxidation and dirt indefinitely.

Non-toxic, non-inflammable, insures trouble-free performance.

Extra economical because a small amount does the job!

\$3.25

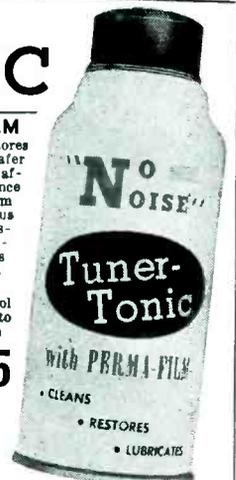

ELECTRONIC CHEMICAL CORP.


813 Communipaw Avenue

Jersey City 4, N. J.

p. 20), this amplifier should be avoided. If the output tubes are strapped as triodes, as shown in Fig. 2 (p. 20) the amplifier should be quite good for public-address work, provided it carries the required facilities.

However, the output stage need not necessarily use tubes strapped as triodes, because better output can be obtained for the corresponding plate dissipation by using the tubes some way as pentodes. To illustrate, the ultra-linear design is very good for a *pa* amplifier; Fig. 3 (p. 20). Unity coupled arrangements (Fig. 4) in which the tubes are essentially working as pentodes, but half the load is in the cathode and half in the plate, are also well suited for public-address work. Other useful arrangements are

(Continued on page 56)

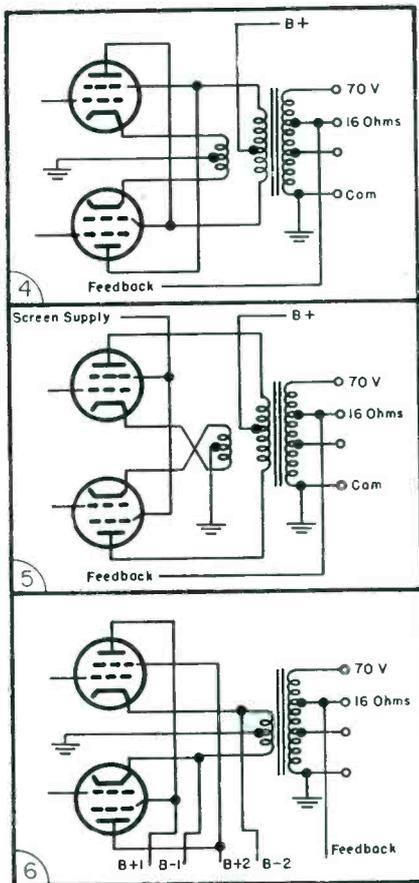


FIGS. 4, 5, 6.

FIG. 4: THE UNITY-COUPLED circuit, which uses pentodes in what may be viewed as semi-cathode-follower operation. This circuit is well suited for *pa* work.

FIG. 5: A CROSS-COUPLED variation of an ultra-linear circuit that is also well suited for commercial sound.

FIG. 6: CIRCLOTRON method, another effective *pa* circuit, which uses two separate $B+$ supplies.

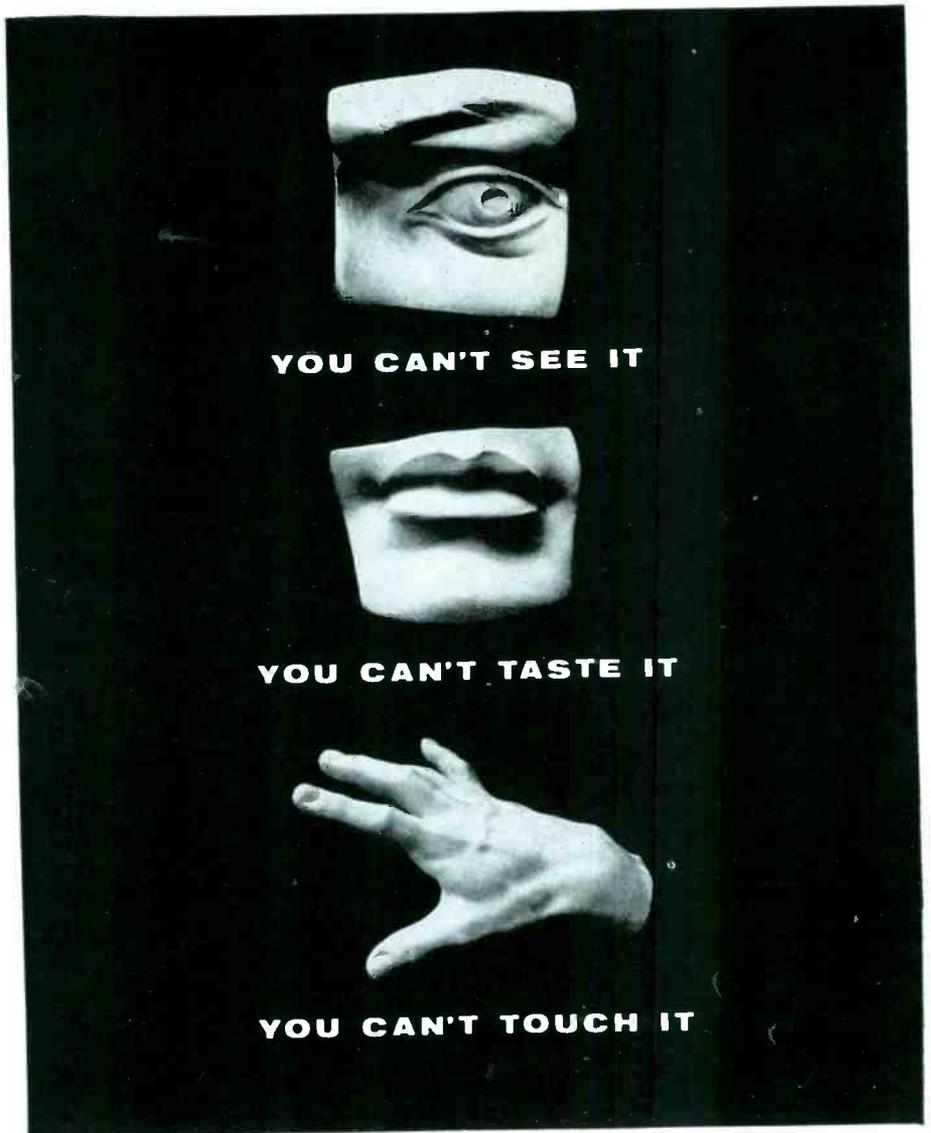

... But it's the most important asset a company can have

A modern plant, a well-stocked inventory, a good shipping department—these things are important. But, more important than all of these, is the *integrity* of a firm... that sense of moral responsibility that demands that you do your best and stand behind what you do.

Integrity starts at the top and filters down, enhancing everything it touches. It serves notice on its customers that every product bearing its label has a team of responsible people behind it.

And something happens to the *product* too! Integrity seems to be built right into it... in ways that you can see and in many more ways that you can't.

In addition to a close check on the quality of the various parts, we, at University, do not tolerate any "sweeping under the carpet." Even those parts which are completely enclosed and hidden from view are as carefully finished as the exposed parts, guaranteeing trouble-free performance.

That's why everyone is saying...

LISTEN

University sounds better




UNIVERSITY LOUDSPEAKERS, INC., 80 SOUTH KENSICO AVENUE, WHITE PLAINS, N. Y.

SERVICE, NOVEMBER, 1956 • 55

for the first time
 . . . a five-volt phono cartridge
 with response to 10,000 cps for
 improvement-replacement applications!

the new

SHURE
W9

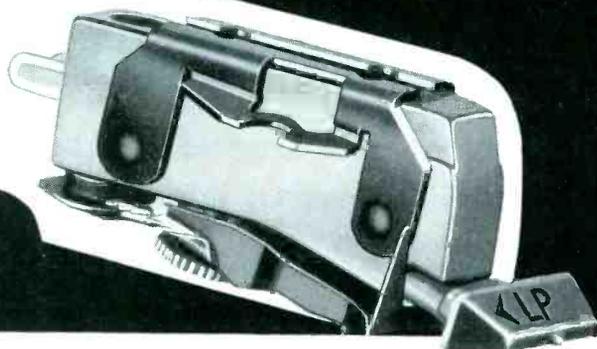

SPECIFICATIONS

Output: 5.0V for 78 rpm,
 3.5V for microgroove*

Needle Force: 9 grams

Response: 40-10,000 cps

Net Weight: 7 grams

List Price: \$9.50
 with two synthesized
 sapphire needles

*Model W9 has capacitor furnished
 as an accessory. With capacitor,
 output is 1.7V for microgroove,
 2.5V for 78 rpm.

This three-speed, dual-needle, dual-voltage crystal cartridge creates a whole new market for you! With the Shure W9, you can dramatically improve the sound of low-cost, low gain phonographs. The W9 replaces sixty-nine frequently used, high output cartridges of twelve manufacturers.

You can replace the needle of the W9 in a matter of seconds, without tools and without removing the cartridge from the tone arm.



The Mark of Quality

SHURE BROTHERS, INC.

Microphones ~ Electronic Components

204 HARTREY AVENUE • EVANSTON, ILLINOIS

"In Electronics since 1925"

Audio

(Continued from page 55)

the cross-coupled ultra-linear shown in Fig. 5 and the *circlotron* design illustrated in Fig. 6.

Source Resistance


All of these circuits yield a basic source resistance for the output stage, before the application of overall feedback, that is quite low; somewhere in the region around the nominal loading impedance. Such a circuit, with additional overall voltage feedback, will be found to be an effective public-address amplifier.

Variable Damping Control

The final consideration is the application of the variable damping control. If the amplifier does not use variable damping, this feature need not be considered; but if variable damping is included, it should be of one of the types shown at Fig. 7, in which control is achieved by varying the quantity of negative voltage and current feedback. This type of control can be turned to the maximum damping position, which is entirely voltage feedback with the current feedback short-circuited.

Alternate Damping Methods

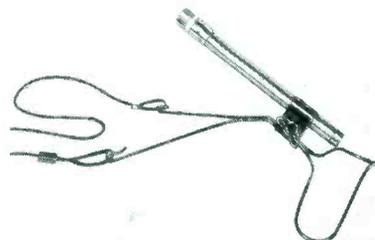An alternate variety of damping factor control uses positive or negative current feedback, as shown in



MICROPHONE CHEST support with a braided neck cord, phenolic adjustment slide, polished chrome goose neck, and black nickel-plated wire frame. Mike can be placed on speaker's chest, in hand, or on any flat surface such as a table. (Model NS-1; Atlas Sound Corp., 1451 39th St., Brooklyn 18, N. Y.)




CONTROL CENTER for hi-fi home music systems with eleven positions for bass and treble record equalization. Has five input channel selectors for tape, tuner, microphone, and two phono cartridges; and a master on-off switch, with volume control. (Model C-4; McIntosh Laboratory, Inc., 320 Water St., Binghamton, N. Y.)

Fig. 8. This design is not good for public-address work, because while public-address application requires a maximum damping factor, the maximum position of this control is not the best operating condition for the amplifier.

In some instances it may even go unstable with some load value. This means that an amplifier using this type of control will need careful adjustment for every different loading condition, which is obviously an undesirable feature for public-address application.

(Below)

FIG. 7: TWO VERSIONS of an acceptable form of variable damping for pa amplifiers. The control swings the feedback from all current to all voltage; minimum and maximum damping, respectively.

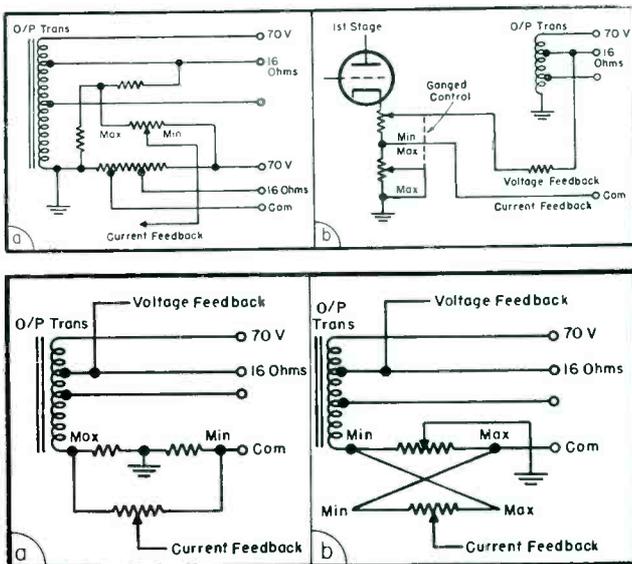

(Left, bottom)

FIG. 8: TWO VERSIONS of a type of variable damping control, not recommended for pa work. It uses variation between positive and negative current feedback.



A SPEAKER SELECTOR designed for temporary or permanent speaker coupling and comparison checks. Can be used in connection with any audio output for switching to up to 3 speakers at remote points. (Model DS77; Dynamic Electronics-New York, Inc., 73-39 Woodhaven Blvd., Forest Hills, Long Island, N. Y.)

There Is a Tremendous Difference

In the Quality of Diamond Needles

A cheap, poorly manufactured stylus can do more damage to a record than any worn one.

Diamond Needles manufactured by The

Tetrad Company—the oldest and largest producer of diamond needles—are unsurpassed in polish and follow cartridge manufacturers specifications exactly.

HERBERT KUPFERBERG

Record Editor
Herald Tribune

“Diamond-tip styli, I have found, give sharper reproduction than any other kind, and last far longer. Their durability is of particular importance to any one who plays records frequently, for although the other types are less expensive initially, the necessity for repeated replacement sends their cost soaring. It’s a pleasure to insert a new needle in a pick-up and to know that it will remain there for a long time.”



PLAY SAFE
PLAY DIAMOND

TETRAD

WORLD'S LARGEST
MANUFACTURERS
OF DIAMOND STYLI

For further information on Quality Diamond Needles write to:
The Tetrad Co., Inc., 62 St. Mary Street, Yonkers, N. Y.

hi-LOW

with ATLAS
high quality
low price



PAGING & TALK-BACK SPEAKERS
6 sizes and types.
All impedances
from 4 to 45 ohms.
From 5 to 15 watts.
From \$15.00 to \$24.00 NET.



WEATHERPROOF LINE MATCHING TRANSFORMERS
For constant impedance or constant voltage systems.
\$5.00 NET.



HIGH-POWERED PUBLIC ADDRESS SPEAKERS
Four sizes from 2 1/2' to 6' air column.
From \$10.00 to \$39.00 NET.



U-L APPROVED EXPLOSION-PROOF SPEAKERS
For hazardous applications.
Several sizes, all classes.
From \$66.00 to \$75.00 NET.



SUPER-POWER DRIVER UNITS
For all purposes, powers, frequencies.
From \$15.00 to \$30.00 NET.



MIKE STANDS & ACCESSORIES
All sizes and types: boom stands, desk stands, adapters, fittings, etc.



NEW! SWITCHBOARD MIKE SUPPORT
Adjustable 12" goose neck. Use as desk support, for dispatcher office, dais, table, etc.
#SB-1 ... \$7.80 NET.

New!

NEW! "CHESTY" NECK-SUPPORTED MIKE STAND

Quick, easy 3-way adjustment. Lightweight. Multiple uses.
#NS-1 ... \$3.00 NET.



New!



NEW! MIKE FOOT SWITCH
Hand, foot or knee operation—shielded, grounded, noise-free, dependable, damage-proof.
#FS-1 ... \$7.20 NET.



SEND FOR COMPLETE FREE CATALOG
ATLAS SOUND CORP.
1442 39th St., Brooklyn 18, N. Y.
In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

TV PARTS... ACCESSORIES

REPLACEMENT FLYBACKS

Replacement flyback transformers, EFR-124, designed for use in 109 Emerson TV models, have been announced by Rogers Electronic Corp., 43 Bleecker St., New York 12, N. Y.

Said to replace Emerson parts numbers 738091, 738096, 738099, 738100, 738106, 738107 and 738111. Included with each flyback is a schematic showing connection in Emerson circuit. Also listed on the data sheet are the 109 Emerson sets covered.

FUSE RESISTORS

Insulated fuse resistors, type FR, which function as a resistor under normal conditions and as a fuse under abnormal conditions, are now available from the International Resistance Co., 401 North Broad Street, Philadelphia 8, Pa. Recommended as a surge-limiting resistor in voltage doubler circuits for TV receivers.

70° DEFLECTION YOKE REPLACEMENTS

Exact 70° cosine deflection yoke replacements (MDF-78) for over 200 Motorola, Hoffman, and Hallicrafters chassis have been developed by the Merit Coil and Transformer Corp., 4427 North Clark St., Chicago 40, Ill.

For exact replacement in over 50 Motorola models and chassis, Merit has developed a MDF-79 cosine deflection yoke with plug.

Also available are exact replacement flybacks (HVO-59 and HVO-61) for G. E. parts RTO-125, 126, 127, and RTO-129, 130, respectively. Both feature an anti-corona ring and exact lead color coding.

DON'T JUST SAY CAPACITORS

Ask For Sprague By Catalog Number

Know what you're getting... get exactly what you want. Don't be vague... insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 61 Marshall Street, North Adams, Massachusetts.

SPRAGUE
WORLD'S LARGEST CAPACITOR MANUFACTURER

for SURE profits

Deal yourself a winning hand



RECOTON DIAMOND NEEDLES

For repeat sales and higher profits—sell **RECOTON DIAMOND NEEDLES**. Recoton has 100% consumer acceptance, insuring your fast turnover! Stick with the winner—**RECOTON**—famous for quality!

RECOTON CORPORATION

52-35 Barnett Avenue
Long Island City 4, N. Y.

STATEMENT REQUIRED BY THE ACT OF AUGUST 24, 1912, AS AMENDED BY THE ACTS OF MARCH 3, 1933, AND JULY 2, 1946 (Title 39, United States Code, Section 233) SHOWING THE OWNERSHIP, MANAGEMENT, AND CIRCULATION OF SERVICE, published monthly at New York, N. Y., for October 1, 1956.

1. The names and addresses of the publisher, editor, managing editor, and business managers are:

Publisher: Bryan Davis Publishing Co., Inc., 52 Vanderbilt Ave., N. Y. 17, N. Y.; Editor: Lewis Winner, 245 W. 107th St., N. Y. 25, N. Y.; Managing Editor: None; Business Manager: Lewis Winner, 245 W. 107th St., N. Y. 25, N. Y.

2. The owner is: (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 per cent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual member, must be given.)

Bryan Davis Publishing Co., Inc., 52 Vanderbilt Ave., N. Y. 17, N. Y.; B. S. Davis, Ghent, N. Y.; M. T. Davis, Ghent, N. Y.; J. C. Munn, 2253 Delaware Drive, Cleveland 6, Ohio; Lewis Winner, 245 W. 107th St., New York 25, N. Y.

3. The known bondholders, mortgagees, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.)—None.

4. Paragraphs 2 and 3 include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting; also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner.

(Signed) LEWIS WINNER, Editor

Sworn to and subscribed before me this 26th day of September, 1956.

(Seal) Beatrice E. Earley, Notary Public

PHONO-TAPE Repair Tips

IF THE NEEDLE setdown adjustment is correct for 10" and 12" records, but the needle lands outside of 7" 45 rpm records on Magnavox-Collaro changers, the pickup height should be backed off, adjusting shaft about 1/2 turn.

Stylus Installation

INCORRECT STYLUS REPLACEMENT often affects *hf* response. The results that can occur are illustrated in Fig. 1 (p. 60). Curve A represents a good response that should obtain when a high quality pickup is used with its correct stylus.

Use of an incorrect stylus may cause the dip and peak response of curve B. In some instances, the peak may be higher or the dip shallower, or perhaps the peak will not be so high and the dip will be deeper. This will depend upon the proportion of the stylus and the extent of the error in its dimensions.

Listening-Test Record Checks

The important thing to notice about curve B is that an unnatural effect occurs on the high-frequency response. One should listen carefully to the reproduction to check this, if it is not possible to take an actual frequency run with a test record.

One's first reaction, when listening to a disc played by a pickup producing the response of curve B, is that the high-frequency response is good. This will be so because the peak tends to accentuate the record surface noise.

You will probably find that the sound offers more surface noise, than a pickup with the A response, but careful listening will disclose that this surface noise has substantial coloration, and the general level of the higher frequencies in the program material is not as good as you would expect from the surface-noise level. This condition obtains, because the effective rolloff is really at a lower frequency than would first appear by the position of the peak, and the peak only *appears* to sustain the response.

A good response, as at curve A, gives the best reproduction of high-frequency components in the

(Continued on page 60)



Webcor Imperial Diskchanger 1631-21

The amazing new **WEBCOR**
"MAGIC-MIND" diskchangers select
33 1/3 and 45 rpm speeds—automatically!

For new installations . . . for replacements . . . here's the most sensational record changer since Webcor first developed a practical, low-priced diskchanger years ago!

Just stack any assortment of 33 1/3 and 45 rpm records . . . of all sizes . . . in any sequence. Turn on the MAGIC MIND Diskchanger . . . and it automatically selects the right turntable speed . . . as each record drops gently onto the turntable! What's more . . . regardless of record size . . . the tone arm sets down accurately on the starting groove!

It's sheer magic! For the first time—and only Webcor has the MAGIC MIND Diskchanger . . . it's possible to hear hours of recorded music . . . without raising a finger!

(Plays 78 rpm records, too, of course.)

SEE or CALL your Webcor distributor today. Have him give you the complete story on Webcor's new MAGIC MIND Diskchangers . . . designed to fit all standard wells. Mounting boards precut to exact dimensions of Webcor diskchangers.



WEBCOR VHF

Imperial Plug-In Fonograf
MODEL 1632-21

Finest diskchanger on the market! MAGIC MIND Automatic Speed Selector. GE Magnetic Cartridge with diamond, sapphire styli. Easy set-down adjustment. Adjustable counterbalance to regulate stylus pressure. Extra-heavy, weighted turntable with removable rubber mat. Many other features. In Chrome or Burgundy. Model 1632-1 with Webcor Ceramic Cartridge. Model 1632-27 with special plug-in head.

d&r
dependable & reliable

FLUTTER METER



- Eliminates all guesswork
- Saves time and increases production
- Makes satisfied customers

Model FL-3C... for measuring, testing and servicing Tape Recorders and Turntables

LOWEST PRICED INSTRUMENT... HIGHEST QUALITY

The rare case where the best costs less

Features:

- Simple operation—tape recorders—turntables
- Internal 3kc carrier oscillator
- Light weight—easily portable
- Regulated power supply

Specifications:

- Accuracy: $\pm 5\%$
- Bandwidth: 0.5 to 250 cps
- Input: 250,000 ohms; 0.7 rms full limiting
- Dimensions: 7"x 12"x 6" black case with gold trim


Complete 5-step instruction plate on top of case

Price \$185.00

Order direct or write us for name of nearest representative

404 East Gutierrez Street
P.O. Box 1500 • Santa Barbara, California

Telephone: WOODLAND 5-4511

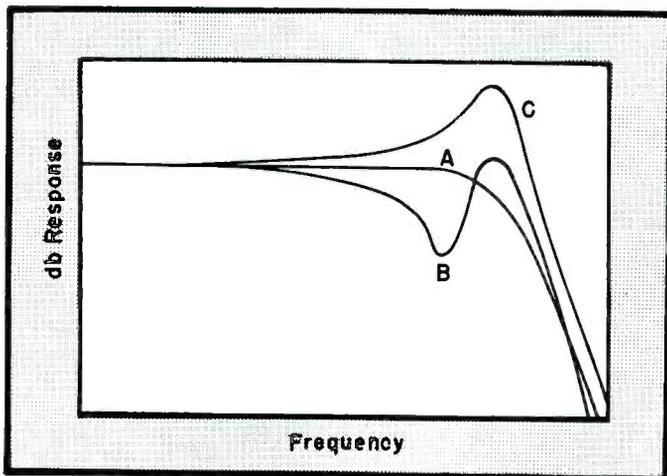

IDEAL AND POOR response curves found in phono systems: A is the ideal curve; B can be caused by improper combinations of needle and cartridge; C usually reflects loss of damping in the pickup, and indicates it is time to replace not only the stylus, but the cartridge, too.

Phono-Tape Repair Tips

(Continued from page 59)

program material, and at the same time minimizes the apparent surface noise.

Curve C shows a peak that can occur due to insufficient damping. The use of too long a stylus arm can produce insufficient damping for the tone-arm resonance. But this is not true of high-frequency resonance; if the stylus arm is too long, its increased mass will pull the frequency down and the peak will not as a rule be excessive. The peak shown in curve C can occur even when the correct stylus is inserted. This happens because, even in the best of cartridges, damping material deteriorates with age.

Checking Tape Capstan Speed

A strob disc (circular fan-like metal disc) placed on the metal drive capstan (for 7½ ips only), can be used to check capstan speed on tape recorders. When the recorder is operating, and the disc is viewed under a fluorescent light, spokes will appear to form on the disc as it spins. If the spokes seem to turn counter-clockwise the capstan is rotating too slowly. If they appear to turn clockwise, at a ratio greater than two revolutions per minute, the capstan is rotating too fast.

If the capstan speed is not correct, the condition of the drive idlers should be checked for cleanliness. Also the end play of the capstan flywheel should be checked. If it is too tight or too loose, the flywheel should be adjusted by tightening or loosening the adjusting set screw.

Other Causes of Improper Speed

Improper capstan speed can also be due to incorrect pressure on the pressure roller; the correct pressure is one pound. To adjust the roller, one should either stretch or remove loops from the pressure arm springs.

Slow Winding Speed

It is normal for a reel to start slowly when winding the tape towards a comparatively full reel. However, the recorder should pick up in speed soon after. When the winding continues to be slow, the rubber drive wheel under the reel chucks should be checked. If the rubber has shredded to any great extent, the wheel assembly should be replaced.

Service Engineering

(Continued from page 53)

tenuation in either channel, is zero (or slightly negative). The net *dc* output of the two channels is applied to the grid of the relay tube. The 2D21 thyratron is maintained non-conducting by *ac* bias from the heater winding of the power transformer applied to its cathode. A signal whose frequency is different than the band-stop frequency will suffer relatively little attenuation in either channel.

Bias Cancellation

However, if the signal is attenuated in the band-stop channel, the net *dc* output will be positive and cancel the bias, causing the relay to operate. The plug-in decoding network is factory adjusted to correspond to the modulating frequency of the transmitter and attenuates only that particular tone.

Capacitive Time Delay

To avoid possible operation from transients and interference, particularly that of the familiar *squeal* or *whistle* variety, a time delay of approximately one-half second is provided by a capacitor across the relay.

The *dc* power for the receiver is obtained from a half-wave rectifier and single section resistance-capacitance filter.

Premium Tubes

The remote-control units are designed for maximum tube life. However, for critical applications in commerce and industry or when extraordinary tube life is desired, the original *entertainment* type tubes may be replaced with *high-reliability* industrial types as noted below. These tubes may be directly interchanged with their entertainment type equivalents.

Entertainment Type	Equivalent High Reliability Industrial Type
6BA6	5749
12AU7A	5814A
2D21	5727

TABULATION of entertainment and equivalent high-reliability industrial type tubes that can be used for critical applications or when unusually long tube life is required.

THIS

DFF

PLUS THIS

LIFE

MEANS MORE OF THIS FOR YOU



DFF—Duotone Fidelity Focus is big—big as Life where it's being advertised in the biggest program of its kind in needle history. For DFF brings music out of the shadows into focus. It's the big needle news. Put it to work for you. It's the perfect door opener. So is the free DFF Needle Test Card. Lets you test customer's needle right in his machine. Then send test card to us (with 25¢ to cover handling); and we will rush you back a complete report on the customer's needle. Gives you chance for second visit—second sale. Ask us about free DFF Needle Test Cards and DFF Program—it's big—



SPECIAL SERVICE MAN'S KIT
The all-in-one needle repair kit with the famous four free extras. Includes free—one 50X microscope to check needle. Jeweler's screw-driver. Professional Tools. Plastic carrying case. 13 of the most used needles. List \$25.00.



DUOTONE T-V CLOTH
An extra on every service call. New especially treated cloth that removes T-V Smog like magic. Gives brighter picture. Reduces reflection glare. Keeps dust from clinging. A quick wipe by servicemen inside and outside of protective glass and on picture tube. Sell one for home use to remove fingerprints—keep off dust. \$1.00 list.

THE DUOTONE COMPANY Keyport, New Jersey

Here's A Business for EVERY AGGRESSIVE SERVICEMAN
Installing **RADIO CONTROLLED GARAGE DOOR OPENERS...**

and if you do, install the BEST!

Perma-Power


Here is the ultimate in design for remotely operating garage doors with maximum convenience and safety. All mechanism is concealed in a modern spun-aluminum fixture that beautifies as well as illuminates the garage interior. The motor is a 1/4 HP, 117 volt, capacitor-start type with ample power to operate the largest of modern residential garage doors. Also in the fixture is the radio receiver which turns on the motor when it gets a signal from the transmitter in the car.

The radio-control transmitter is crystal-controlled, sending out its signal on an FCC authorized frequency of 27.255 mcs. Being small, it mounts under the hood and operates directly from the 6 or 12 volt car battery.

INSTALLATION—Entire system was designed to make installation an easy one-man job. Simplified step-by-step instruction manual assures fast, professional results using common hand tools. Every part required is supplied including mounting materials.



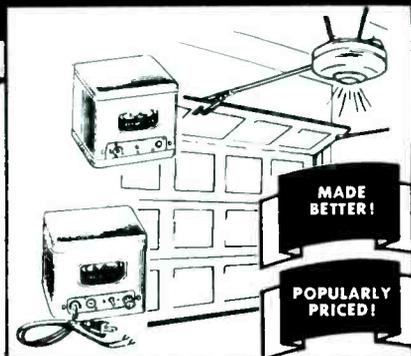Manufacturers of Electronic Equipment Since 1928



MAIL THIS COUPON FOR COMPLETE FACTS NO OBLIGATION

Perma-Power

COMPANY, 4727 N. DAMEN AVE. CHICAGO 25, ILL.

- Please send literature, including installation instructions
- Please send name of nearest distributor

Serviceman _____

Firm _____

Address _____

City _____

State _____

— DON'T DELAY! — MAIL ME TODAY! —



another
EXACT
REPLACEMENT
first



MDF-78 and MDF-80 for exact replacement in over 200 models and chassis of Motorola—Hoffman—Hallicrafters. Provides exact lead color coding and exact network. Two more in the exact replacement line of a company that has always led the industry with the most complete selection of transformers, yokes and coils. Merit replacement parts are actually better than original equipment because Merit is the only manufacturer of transformers, yokes and coils who has complete production facilities for all parts sold under their brand name.

MERIT


MERIT COIL AND TRANSFORMER CORP.
4427 N. CLARK ST., CHICAGO 40, ILLINOIS

INSTRUMENTS

VTVM


A vacuum-tube voltmeter, V-500-VTVM, featuring a single range and function control, has been announced by Anchor Products Co., 2712 W. Montrose Ave., Chicago 18, Ill.

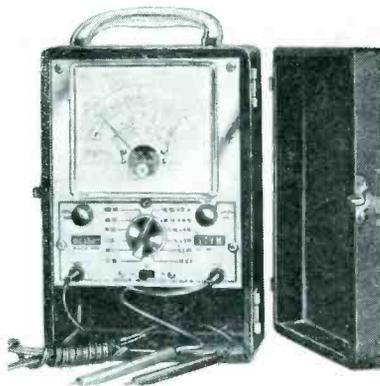Meter has a separate 3-volt *ac* scale; zero centering for TV and FM alignment and a 30 to 100-mc operation range. No batteries are used. Unit has an on-off indicator light, polarity-reverse switch, db scale and overload protection. Measures *ac* and *dc* voltages and resistances. Comes with test leads and isolation probe.



EXPANDED-SCALE VOLTMETERS

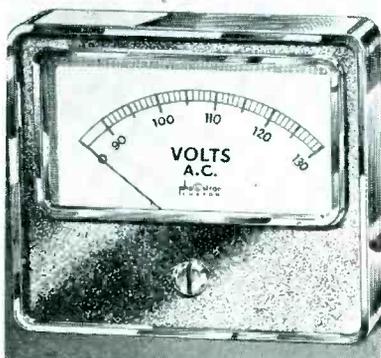Expanded-scale voltmeters, for both *ac* and *dc*, in a variety of ranges and case styles have been introduced by Phaestron Instrument and Electronic Co., 151 Pasadena Ave., S. Pasadena, Calif.



VOLTAGE CALIBRATOR

A voltage-calibrator (kit), VC-3, for producing square-wave signals of known amplitude, has been developed by Heath Co., 305 Territorial Rd., Benton Harbor, Mich.

Unit features 1% attenuator resistors and multivibrator circuit. Output frequency is approximately 1000 cps. Fixed outputs are .03, .1, .3, 1, 3, 10, 30 and 100 *v p-p*. Measurement of unknown signal amplitudes is said to be possible by comparing to known *p-p* output of calibrator on scope. Unit is also said to serve as a square-wave generator at 1000 cps for determining gain, frequency response or phase-shift characteristics of audio amplifiers.

"Mike"
Stands
by

Snyder
PHILADELPHIA

DESK
BANQUET
FLOOR &
PORTABLE
Models

SNYDER

SNYDER MFG. CO., PHILADELPHIA 40, U.S.A.
BELLEVUE TUBE MILL, INC., PHILADELPHIA
SNYDER ANTENN-GINEERS, LTD., TORONTO 14, CANADA
WORLD EXPORT: ROBURN AGENCIES, INC., N. Y.
VAN DER HOUT ASSOC., LTD., NEW TORONTO, CANADA
SNYDER ANTENN-GINEERS, INC., LOS ANGELES 58

ADVERTISERS IN SERVICE
NOVEMBER, 1956

	Page
Aerovox Corp.	47
Alliance Manufacturing Co., Inc.	14
Allied Radio Corp.	63
American Elite, Inc.	64
American Pamcor, Inc.	45
Amphenol Electronics Corp.	44
Anko Manufacturing Co.	33
Appliance Service Co.	35
Atlas Sound Corp.	58
Avco Manufacturing Corp., Electronics Div. TV	30
B & K Manufacturing Co.	15, 42
Blonder-Tongue Laboratories, Inc.	32
Bussmann Manufacturing Co.	1
Channel Master Corp.	6, 7
Chicago Standard Transformer Corp.	49
Clear Beam Antenna Corp.	43
H. G. Cisin	63
Cornell-Dublier Electric Corp. Inside Front Cover,	37
D & R, Ltd.	60
Duotone Co., Inc.	61
Dynamic Electronics-New York, Inc.	36
Eby Sales Co.	37
Electra-Craft Appliance Co.	39
Electric Sweeper Service Co.	39
Electro Products Laboratories	2
Electronic Chemical Corp.	54
Electronic Instrument Co., Inc. (EICO)	35
Elgin National Watch Co., Electronics Div.	54
Fast Chemical Products Corp.	38
Heath Co.	50
Hexacon Electric Co.	46
Hickok Electrical Instrument Co.	38
Hotpoint Co.	27
Jackson Electrical Instrument Co.	64
Jensen Industries, Inc.	54
JFD Manufacturing Co., Inc.	16
Kester Solder Co.	52
P. R. Mallory and Co., Inc. Inside Back Cover	62
Merit Coil and Transformer Corp.	62
Ohmite Manufacturing Co.	36
Perma-Power Co.	61
Philco Techrep Div.	51
Planet Sales Corp.	48
Quietrole Co., Inc.	37
The Radiart Corp. Inside Front Cover, Radio Corporation of America, Tube Div. Back Cover	37
Radio Receptor Co., Inc., Semiconductor Div.	3
Raytheon Manufacturing Co.	8
RCA Service Co., Inc.	31, 53
Recoton Corp.	58
Remington Rand Univac, Div. of Sperry-Rand Corp.	29
Seco Manufacturing Co.	46
Service Instruments Co.	46
Shure Brothers, Inc.	56
Simpson Electric Co.	11
Snyder Manufacturing Co.	62
Sprague Products Co.	4, 48, 58,
Standard Coil Products Co.	5
Tetrad Co., Inc.	57
Trio Manufacturing Co.	10
Tung-Sol Electric Co., Inc.	40, 41
University Loudspeakers, Inc.	55
Webcor, Inc.	59
Weston Electrical Instrument Co., Inc.	52
G. F. Wright Steel & Wire Co.	50
Xcelite, Inc.	48

INDUSTRY NEWS

CONELRAD WALL CHART

A wall chart, containing instructions on what to do in case of a Conelrad alert, has been made available for operators of base radio stations by Kaar Engineering Corp. Chart outlines procedures which must be followed to comply with FCC rules. Copies can be had by writing Kaar Conalert, P. O. Box 1320, Palo Alto, Calif.

NEW TUBE PLANT IN ALTOONA, PA.

Sylvania Electric Products, Inc., recently broke ground for a new receiving tube plant at Altoona, Pa. New manufacturing unit will contain 190,000 square feet of production space.

SALES-INCENTIVE CAMPAIGN

A national sales-incentive *Sell-A-Bration* program designed to spark replacement-antenna installations has been announced by JFD Manufacturing Co., Inc., 6101 16 Ave., Brooklyn 4, N. Y.

Based on a point system, Service Men will be given bonus points for each antenna of the Colortenna family sold; eleven antenna models are included in plan.

Merit points will be redeemable in over 900 premiums ranging from fishing rods to sports cars to national and overseas pleasure trips. Distributor salesmen will receive the same amount of merit points as his dealers.

Sales campaign features use of displays, streamers, newspaper mats and direct mail.

The promotion will end March 15, 1957.

DON'T JUST SAY CAPACITORS

Ask For Sprague By Catalog Number

Know what you're getting . . . get exactly what you want. Don't be vague . . . insist on Sprague. Use Complete radio-TV service catalog C-610. Write Sprague Products Company, 61 Marshall Street, North Adams, Massachusetts.

SPRAGUE

WORLD'S LARGEST
CAPACITOR MANUFACTURER

SHOOT TV TROUBLE FAST

With H. G. Cisin's Copyrighted RAPID "TV TROUBLE SHOOTING METHOD"

Without experience or knowledge, this guaranteed new method of servicing TV sets, enables you to DIAGNOSE TV troubles as rapidly as an expert. NO THEORY—NO MATH—you can locate all faults in record-breaking time regardless of make or model. "TV TROUBLE SHOOTING METHOD" is the most valuable aid to TV servicing ever written. Be a TV Trouble Diagnostician. Increase your present earnings. Open your own Profitable Business or get a high-paying skilled job.

It's all in this book . . .
Nothing more to Pay—Nothing else to Buy

85 picture troubles, over 58 raster and sound troubles. By this unique copyrighted method you know EXACTLY WHERE the trouble is; plus step-by-step instructions, including 69 RAPID CHECKS, enabling you to find the faulty part.

13 IMPORTANT PRELIMINARY CHECKS NEED NO INSTRUMENTS! Of the 69 Rapid Checks, OVER 65 ALSO REQUIRE NO INSTRUMENTS! Rapid checks include emergency checks for distorted pictures, defective tubes including PIX tube, plus 57 others. ALL EXPLAINED IN SIMPLE LANGUAGE. PERFORMED WITHOUT INSTRUMENTS. MANY CHECKS USE THE PICTURE TUBE AS A GUIDE.

H. G. Cisin the author, is the inventor of the AC/DC midset radio. He licenses RCA, APTK, etc. He has also trained thousands of technicians now owning their own prosperous TV service organizations or holding highly paid TV positions. His years of experience are embodied in this remarkable new book.

Guaranteed. Money Back in 5 Days if Not Satisfied!

ABSOLUTELY FREE with each order: H. G. Cisin's newest book "TV & RADIO TUBE SUBSTITUTION GUIDE." Gives direct replacements of set and picture tubes. Most valuable servicing aid! ACT NOW—get both books postpaid at cost of only one! **\$1** Postpaid

RUSH COUPON NOW!

H. G. CISIN, CONSULTING ENGINEER,
Amagansett, N. Y. Dept. S-33

Enclosed find \$1. Rush both books.

Name _____
Address _____
City _____ Zone _____ State _____



NEW

Build-Your-Own knight-kit TRANSISTOR & DIODE CHECKER KIT

only \$8.50

Save on this valuable new instrument! Checks leakage-to-gain ratio and noise level of all junction, point contact and barrier transistors. Can also check germanium and silicone diodes, and forward and reverse conduction of selenium rectifiers. Useful for continuity and short tests, as well as for noise level tests. Features: spring-return leakage gain switch, calibration control, full-vision meter, separate sockets for PNP and NPN type transistors. Complete kit with bakelite case, all parts, 22½v. battery and instructions. Shpg. wt., 2½ lbs. Model 83 Y 149. Net only **\$8.50**

Net F.O.B. Chicago

FREE



356-PAGE ALLIED CATALOG
Lists dozens of other low-cost quality Knight-Kit test instruments, plus the world's largest selection of parts and equipment for service work. Write for FREE copy.

ALLIED RADIO, Dept. 23-L-6
100 N. Western Ave., Chicago 80, Ill.

Send Kit described above. \$_____ enclosed
 Send FREE 356-Page ALLIED Catalog
Name _____
Address _____

Choose from these

JACKSON

3

"Service Engineered"


TUBE TESTERS

1 New Features!
Model 648A
Dynamic
\$129.95 net



Fastest Dynamic Tube Tester made, yet it's fully flexible for all receiving types, new and old. The set-up time is actually less than the warm-up time of the tube. New Variable Sensitivity Shorts Test shows leakage up to 2.0 megohms. Metered plate current shows tube condition. Meter calibrated in Good-Bad as well as Percent of relative micromhos. Automatic Line Voltage Indicator, Life Line Indicator, New Zig Zag Roll Chart locates tube types much faster. Twenty-three heater voltage settings cover all series-string tubes.

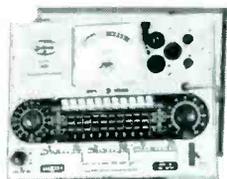
2 Low-Cost
Forty-Niner
with Plug-In
Accessories



\$49.95 net, Accessories extra

A good, basic tube tester, with plug-in accessories for performing a wide variety of additional tests. Accessories may be added any time, permit testing tubes for filament current and high resistance shorts, as well as checking selenium rectifiers. Lever action shows which pins are connected. Sensitive shorts test. Line Voltage Indicator. A tremendous value.

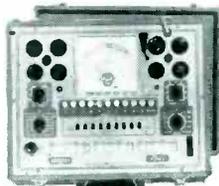3 New, Portable
Dynamic
Model 561
\$89.95, net



Employs famous Jackson Dynamic principle, applying separate voltages to each tube element. High voltage power supply for most accurate tests. Improved switching system gives simplified, fast operation. Filament voltages for the very latest TV types. Fully portable case finished in harmonizing gray and green, tough plastic fabric. Built-in roll chart, with free replacement service for one year.

Test Data on New Tube Types
for All Jackson Testers Appears
Monthly on Page 65 of PF Reporter

For more information, write:

JACKSON
ELECTRICAL INSTRUMENT CO.

"Service Engineered" Test Equipment

16-18 S. PATTERSON BLVD., DAYTON 2, OHIO
In Canada: The Canadian Marconi Company

Tube News

THE INCREASING popularity of TV portables has prompted the introduction of a number of 450-*ma* replacement tubes for these chassis.

Three types that have recently become available are the 6J6A, 6V6GTA and 8AW8A¹.

A fourth tube, announced as a replacement, is the 8CG7², a heater-cathode type medium-mu twin triode of miniature construction, designed for use as a vertical and horizontal deflection oscillator. The tube is identical to the 6CG7 except for its 450-*ma* heater rating.

Another reduced size type that has become available is the 6CD6GA³, a high-perveance glass-octal beam power tube, for horizontal-deflection amplifier use with 90° deflection-angle picture tubes. Utilizing a button-stem construction in a T-12 envelope, the 6CD6GA is smaller than the 6CD6G, and features a modified mount design. It has a maximum peak positive-pulse plate voltage rating of 7000 and a maximum plate dissipation of 20 watts. The tube is unilaterally interchangeable with the 6CD6G.

Also developed for the horizontal-deflection circuit is a damper diode, the 19AU4³ (half-wave rectifier) with an 18.9-v/600-*ma* heater.

Rated to withstand a maximum peak inverse plate voltage of 4500 (absolute), the 19AU4, it is claimed, can supply a maximum peak-plate current of 1050 *ma* and a maximum *dc* plate current of 175 *ma*.

Tube engineers have also been active in developing new types for audio and *ac/dc* chassis.

A beam power tube of the glass-octal type, the 6DG6GT³, has been designed for service as an output tube in audio amplifiers. Having a 6.3-v/1.2-*a* heater and a maximum peak heater-cathode voltage of ±90, but otherwise like the 25L6GT, the 6DG6GT is intended for the use in audio equipment requiring a power sensitivity and efficiency at relatively low plate and grid-No. 2 voltages.

For example, it is said, in a class A1 application, a single 6DG6GT operating at a plate voltage of 200 and a grid-No. 2 *v* of 25, will deliver 3.8 watts of power.

Another new audio tube recently announced is the 17C5², a heater-cathode miniature beam pentode. It was designed for use in the *af* power output state of *ac/dc* receivers, and is identical to the 50C5, except that it has a 450-*ma* heater rating.

¹Sylvania

²Raytheon

³RCA

Europe's Largest Selling
Electronic Tubes
Now Available
to the discriminating
American tube buyer
—at standard prices.



- Receiving Tubes
- Special Purpose Tubes



not just a
replacement—
but an
improvement



TELEFUNKEN

PIONEER IN ELECTRONICS
SINCE 1903

Write for your Telefunken Tube
Manual and for the name of your
nearest jobber.

Imported exclusively by

**AMERICAN
ELITE, INC.**

Dept. 8
7 Park Avenue
New York 16, N. Y.



...another
MALLORY
service-engineered
product

**More than
60 Million
Vibrators
worth of
experience
...to bring you
the best!**

Yes, it has taken 26 years of pioneering development . . . plus the manufacturing know-how gained by making more than 60 million vibrators—60 million units worth of experience—to bring you Mallory's long-lived, premium performance vibrators.

Unique Mallory features have reduced mechanical hum to levels thought impossible a few years ago. They have extended vibrator life, and established new standards of reliability and service.

As in the past, Mallory will continue to lead the vibrator field in design and development . . . bringing you the finest in performance . . . the utmost in economy and efficiency.

Give your customers *the best*.
Be certain you order Mallory from
your distributor.

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA


• Capacitors • Vibrators • Resistors • Controls • Switches
• Rectifiers • Power Supplies • Filters • Mercury Batteries

Advanced
engineering
and precision-
manufacture
build

LONG LIFE

into RCA

RECEIVING TUBES

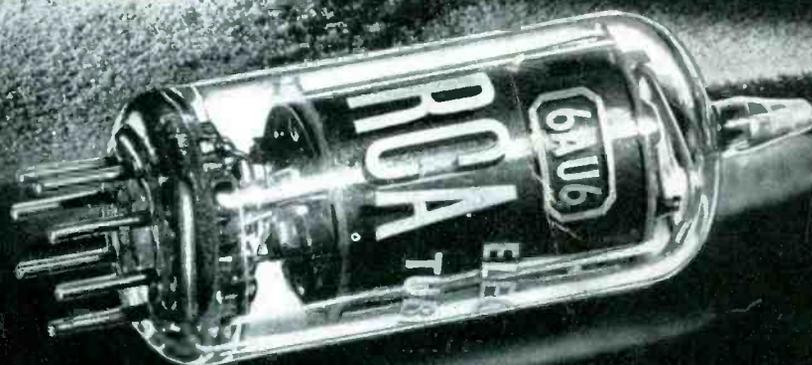

A receiving tube that delivers, and keeps on delivering at maximum performance levels doesn't just happen—it *has to be made to happen!*

Stringent quality control checks govern each part and each process in the manufacture of all RCA Receiving Tubes. Take the RCA-6AU6, for instance: The control grid is silver-plated to minimize grid emission and to give low contact potential; carefully processed cathode materials minimize leakage and mica support is specially treated to insure low inter-electrode leakage; result—Long Life! To insure noise-free performance—each tube is “receiver-tested.” Avoid costly callbacks—standardize on RCA. Tell *your* distributor to fill *your* tube order with RCA Tubes *only.*



RECEIVING TUBES
RADIO CORPORATION OF AMERICA