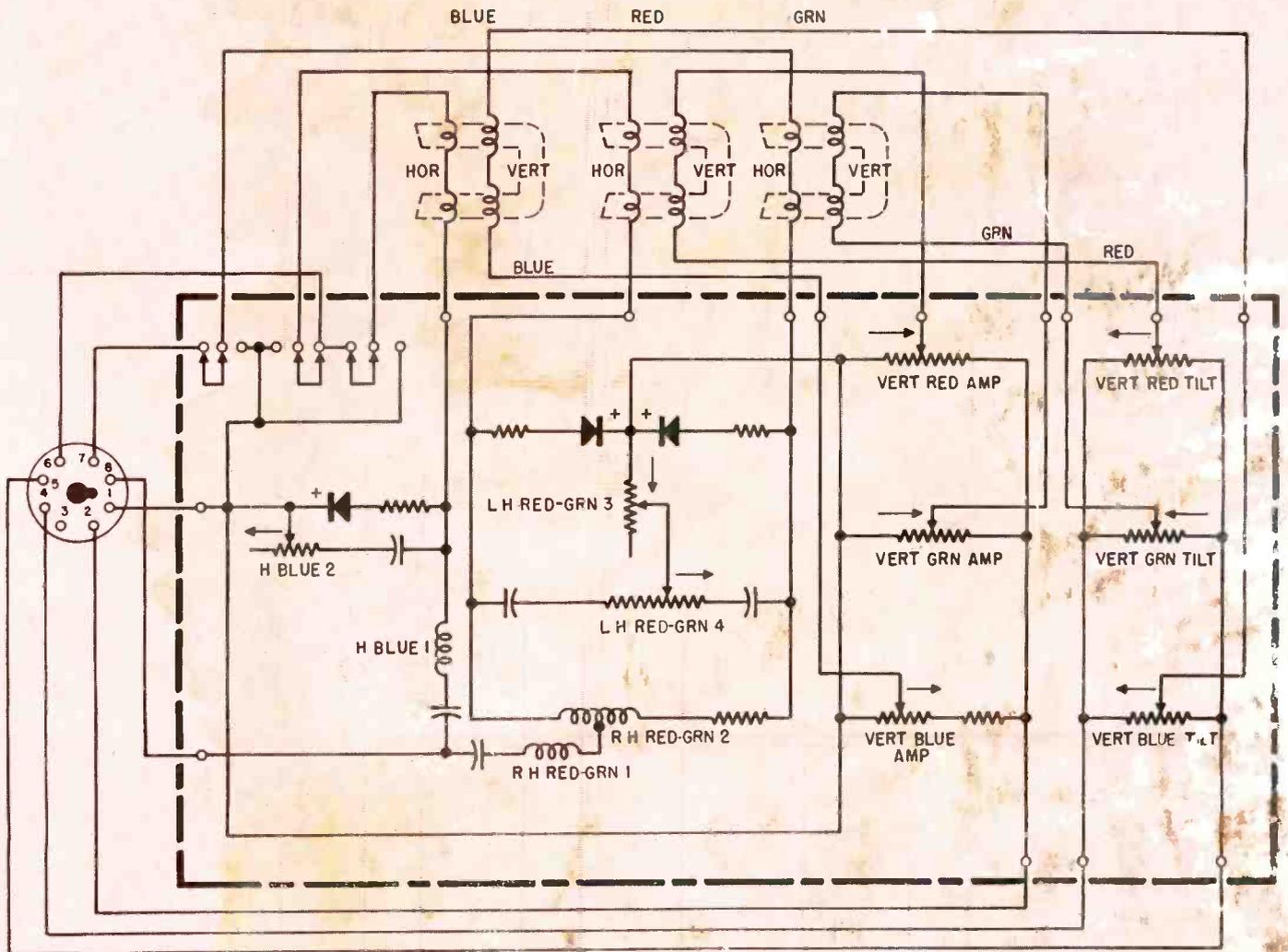


COLOR
TELE
VISION

OCTOBER, 1957

SERVICE

THE TECHNICAL JOURNAL OF THE TELEVISION-RADIO TRADE



Semiconductor dynamic convergence
circuit developed for glass 21-inch
tube color-TV receivers.

See circuit analysis, this issue

AL BRONSY
2-59
1962 SO STEARNS DR
LOS ANGELES 34, CALIF
25 SAR 1-10-56

MODEL 280SW (shown right)


• Double stacked array PLUS high frequency elements.

- All Aluminum Construction.
- Mounts on any mast up to 1 3/4".
- QUICK-RIG design for speedy one man installation.
- Complete with stacking bars.


MODEL 180SW same as 280SW only not double stacked.

MODEL 180 QUICK-RIG 8 element "Lazy-X" Conical.

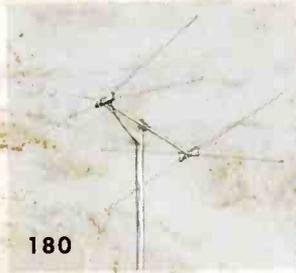
MODEL 280 QUICK-RIG double stacked "Lazy-X" Conical.



180

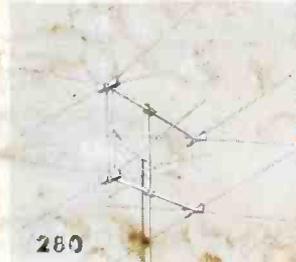

280

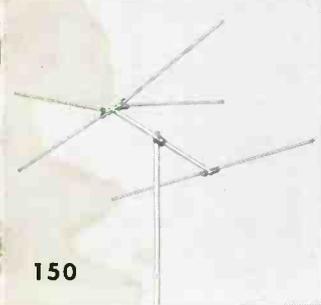


150


TV ANTENNAS

Proven Unquestionably . . .
 the best performing at
 the lowest possible price!

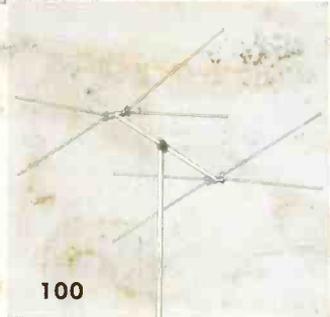RADIART . . . the name you can depend upon for QUALITY and VALUE . . . offers a COMPLETE and NEWLY ENGINEERED line of superbly performing TV antennas at an economy price. Carefully tested under all conditions . . . each of these new models is guaranteed to be the best performing at the lowest possible price.




100

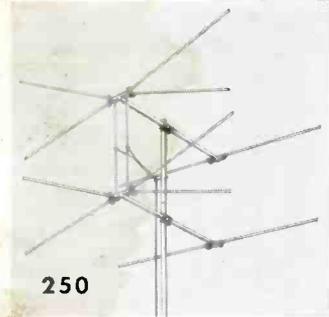

250

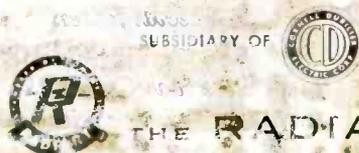
- LZX 100 single array
- LZX 101 single array, unassembled
- LZX 200 8 element conical completely assembled, stacked array
- LZX 201 8 element conical unassembled, stacked array
- LZX 150 single array
- LZX 151 single array, unassembled
- LZX 250 6 element conical assembled, stacked array
- LZX 251 6 element conical unassembled, stacked array



THE RADIART CORPORATION / CLEVELAND 13, OHIO

To install or service COLOR-TV...

you must have these 5 new Walsco tools

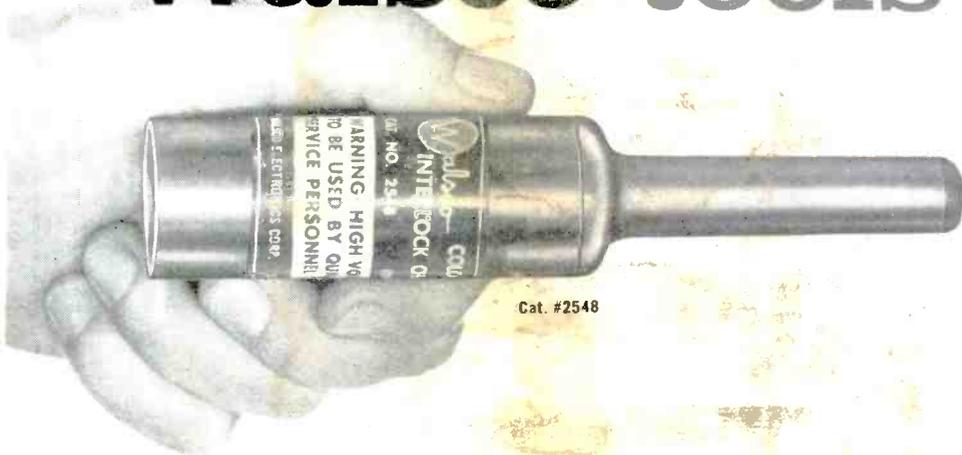

Cat. #2548

Specially designed... absolutely essential to make Color-TV servicing easy and profitable!

Cat. #2548 NEW WALSCO COLOR-TV INTERLOCK CHEATER.

Lets you service color sets with rear panel removed. Blocks grounding of high voltage supply. Special design permits safe insertion of high voltage probe. Net \$5.94

Cat. #2590 NEW WALSCO COLOR-TV DEGAUSSING COIL.

Required to eliminate stray magnetic fields prior to purity adjustments. Made to standard industry specifications; enclosed in molded plastic cover. Momentary switch safely de-energizes coil without pulling plug.

Cat. #2590 with momentary switch. Net \$16.90 Cat. #2591 without switch. Net \$14.90

Cat. #2589 NEW WALSCO COLOR-TV ALIGNMENT TOOL.


Adjusts and aligns all concentric controls on color, as well as black-and-white sets. Makes two separate adjustments at the same time: outer shaft aligns outer control shaft, inner shaft aligns inner control shaft. Net \$1.19

Cat. #2595 NEW COLOR-TV GRID GROUNDING BOX.

Essential for grounding controlled grids of color tube to permit convergence and matrix adjustments. Special "insulation piercing" terminals make application easy. Net \$5.10


Cat. #2596 NEW WALSCO TV COLOR VIEWER.

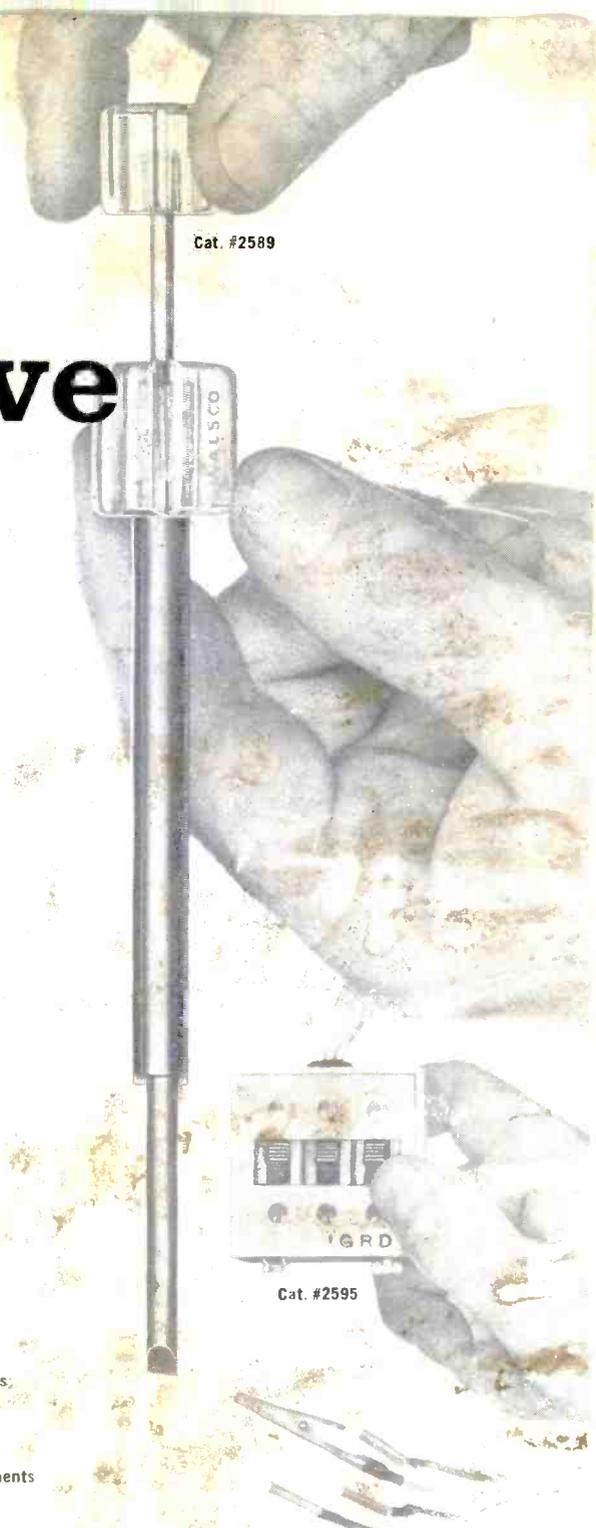Balanced optical filters speed accurate color phase and matrix adjustments on all color TV sets without using an oscilloscope. Net \$1.50



Cat. #2589

Cat. #2595

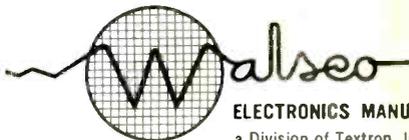

ELECTRONICS MANUFACTURING COMPANY

a Division of Textron, Inc.

100 West Green Street, Rockford, Illinois

Western Division:

3225 Exposition Place, Los Angeles 18, California

In Canada:

Altas Radio Corp., Ltd., 50 Wingold Avenue, Toronto, Canada



Cat. #2590



Cat. #2596

FREE!

Special folder

explaining how to use

these new Color-TV tools.

Ask your jobber or write direct.

26th YEAR
OF
CONTINUOUS
PUBLICATION

SERVICE

THE TECHNICAL JOURNAL OF THE TELEVISION-RADIO TRADE
Including RADIO MERCHANDISING and TELEVISION MERCHANDISING
Registered U. S. Patent Office

COVER CIRCUIT

Color-TV Dynamic Convergence Circuit For Glass Picture-Tube Chassis
(RCA 800 Series) 20

FEATURES

| | |
|--|----|
| Editorial | 17 |
| A Field Progress Report On Color-TV: Why The Television Service Man Should Be A Color-TV Booster C. E. Walter | 18 |
| Circuitry Report On 21-Inch Color-TV Chassis Using Glass Picture Tube J. A. May | 20 |
| Glass-Envelope 21-Inch Picture Tube For Color-TV L. B. Headrick | 24 |
| Installation Checks For Latest Color-TV Chassis J. R. Meagher | 26 |
| Improper Damping Cures . . . Checks For Multirange Ohmmeter Accuracy . . . Transistor Radio Repair Tips (Service Notes) | 28 |
| This Month In SERVICE | 32 |
| RF Amplifier Stages For VHF Tuners Wayne S. Rial | 35 |
| TV Antenna Replacement With All-Channel Types | 37 |
| Repeaters, Antennas, Test Equipment For 2-Way (Service Engineering) | 43 |
| Latest Developments In Semiconductors, FM Tubes And Wide-Angle Picture Tubes | 46 |
| Audio: Dropout and Modulation Noise Problems in Tape | 51 |
| Audio: Motel Sound-System Installation L. A. Randall | 56 |

CIRCUIT DIAGRAMS

| | | | |
|---|--------|--|----|
| RCA CTC7 (800 Series) Color-TV Block Diagram | 20 | Magnavox HV Transformer Circuit Modified For AGC Keying Pulse | 29 |
| RCA 800 Color-TV Chassis (Complete Diagram) | 22, 23 | Pentode-Tuner RF Amp | 35 |
| Color-TV Switching Circuits For Gun Biasing | 26 | Antenna Matching Networks | 35 |
| Motorola 918-919 Circuit Revised To Minimize Motor Noise | 28 | RCA 800 Color-TV Sound | 39 |
| Westinghouse Horizontal Sweep | 29 | RCA 800 Color-TV Dynamic Convergence (Cover) and Power | 40 |
| | | Stromberg-Carlson Amp For Motel Sound System | 60 |

DEPARTMENTS

| | | | |
|--------------------------------------|----|--------------------------------------|-------|
| Transistor-Radio Service Notes | 28 | Audio Installation and Service | 51 |
| Catalogs and Books | 30 | Radio-TV Components | 52 |
| Association News | 31 | Audio Developments | 56-63 |
| Ten Years Ago in SERVICE | 31 | Accessories | 64 |
| TV Antenna Digest | 37 | Test Instruments | 64 |
| Service Engineering | 43 | Bench-Field Tools | 65 |
| Transistor-Tube News | 46 | Personnel | 66 |
| Index to Advertisers | | | 65 |

© 1957 by Bryan Data Publishing Co., Inc. All rights reserved.

Second-Class mail privileges authorized at New York, N. Y.; additional entry at the Post Office, Norwalk, Conn. . . . Subscription price: \$2.00 per year (\$5.00 for 3 years) in the U.S.A. and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

**IMPROVE
your
AMPLIFIER
in 5 ways**



with the
**Amperex®
GZ34/5AR4
RECTIFIER**

A LOW-IMPEDANCE, INDIRECTLY HEATED, FULL-WAVE RECTIFIER WITH 250 MA OUTPUT CAPACITY

The unique AMPEREX GZ34 replaces without circuit changes, in the majority of amplifier circuits, an entire line of popular, heavy-duty 5-volt rectifiers—5U4G, 5V4G, 5T4, etc. — with the following benefits:

- Better voltage regulation due to lowered power supply impedance;
- Higher power supply output voltage for more power;
- Added filter condenser protection due to reduced surge;
- Cooler operation due to lower voltage drop;
- Protection of costly power output tubes through delayed warm-up.

OTHER Amperex TUBES FOR HIGH-FIDELITY AUDIO APPLICATIONS:

| | |
|-------------|---------------------------------------|
| EL84/6BQ5 | 9-pin power pentode; 17 W PP |
| GCA7/EL34 | High-power pentode; 100 W PP |
| EF86/6267 | Low-noise high- μ pentode |
| ECC81/12AT7 | Low-noise medium- μ dual triode |
| ECC82/12AU7 | Low-noise low- μ dual triode |
| ECC83/12AX7 | Low-noise high- μ dual triode |
| ECC85/6AQ8 | High- μ dual triode for FM tuners |
| EZ80/6V4 | 9-pin rectifier; cathode; 90 ma. |
| EZ81/6CA4 | 9-pin rectifier; cathode; 150 ma. |

At All Leading Electronic Parts Distributors



**Amperex
ELECTRONIC CORP.**
200 Duff Ave., Hicksville, Long Island, N. Y.



EDITOR and PUBLICATION DIRECTOR

Lewis Winner

Associate Editor: **David E. Pearsall II**
Assistant Editor: **Robert D. Wengenroth**
Editorial Assistant: **Arnold Gewirtz**
Editorial Assistant: **Howard Jennings**
Field Editor (Mid-West):
Rudolph T. Plemich
Art Director: **Anthony R. Aliff**
Supervisor, Circuit Diagrams:
Michael D. Bellezza
Editorial Production: **Astrid Kelly**


CIRCULATION DEPARTMENT

Circulation Manager: **A. Goebel**
Ass't Circulation Mgr.: **A. KJernan**

ADVERTISING DEPARTMENT


Advertising Mgr.: **Aaron L. Lafer**
Pacific Coast: **Leo Sands, Dist. Mgr.**
535 Ramona St.
Palo Alto, Calif.
Tel.: DAvenport 5-3716

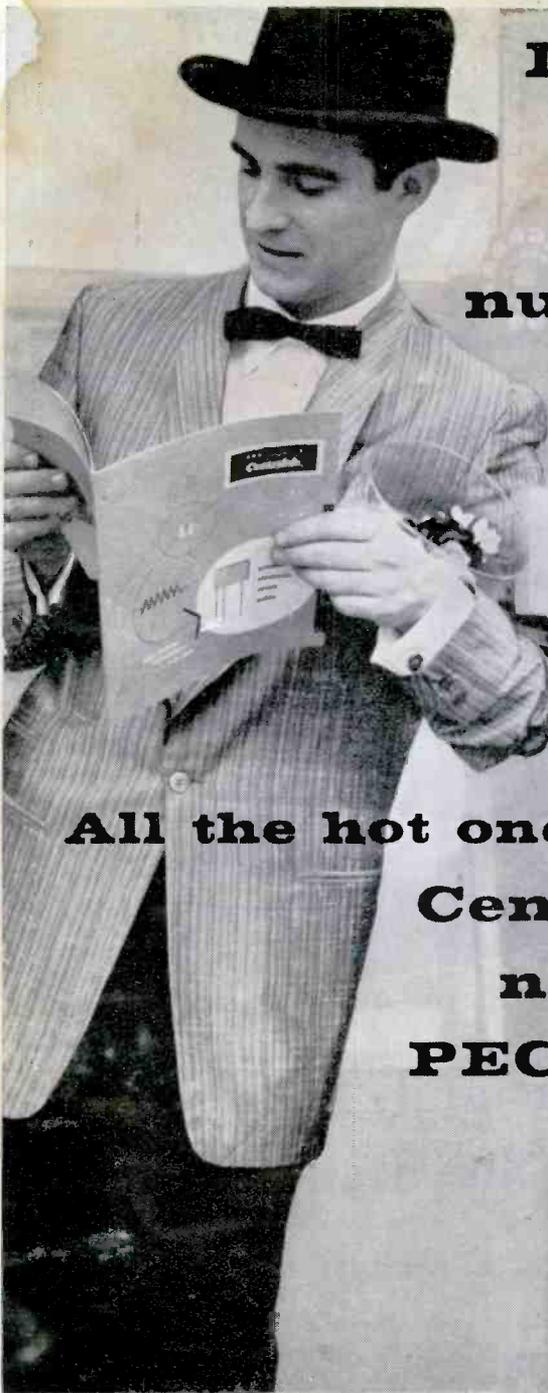Published Monthly by
Bryan Davis Publishing Company, Inc.
52 Vanderbilt Ave., New York 17, N. Y.
Tel.: MUrray Hill 4-0170
B. S. Davis, Pres. Lewis Winner, Vice-Pres.



**Looking
for
new
numbers?**

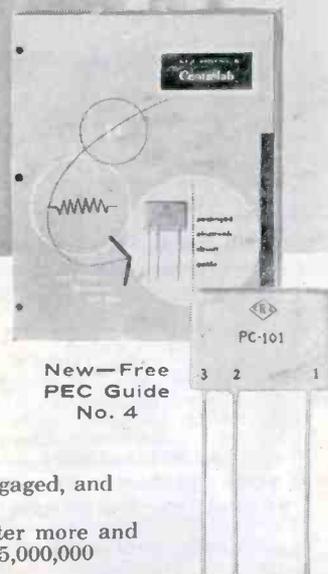**All the hot ones are in
Centralab's
new, free
PEC* Guide**



New—Free
PEC Guide
No. 4

Twenty-five fresh new beauties to choose from. Currently keeping company with the entertainment industry's most popular chassis.

Brand-new edition of the Discriminating Serviceman's Guide — loaded with vital statistics on both the old favorites and the new models. Gives practical techniques for testing — how to tell good ones from bad.


Get the lowdown on what models have been engaged, and where, by 130 radio and TV manufacturers.

These are facts it pays to have — you encounter more and more of these slim, trim PEC's every day. Over 75,000,000 now in circulation.

These beauties are waiting to be picked up at your Centralab distributor. Write us for your copy of PEC Guide No. 4.

Centralab A DIVISION OF GLOBE-UNION INC.
1-931 EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN

◀ Trademark

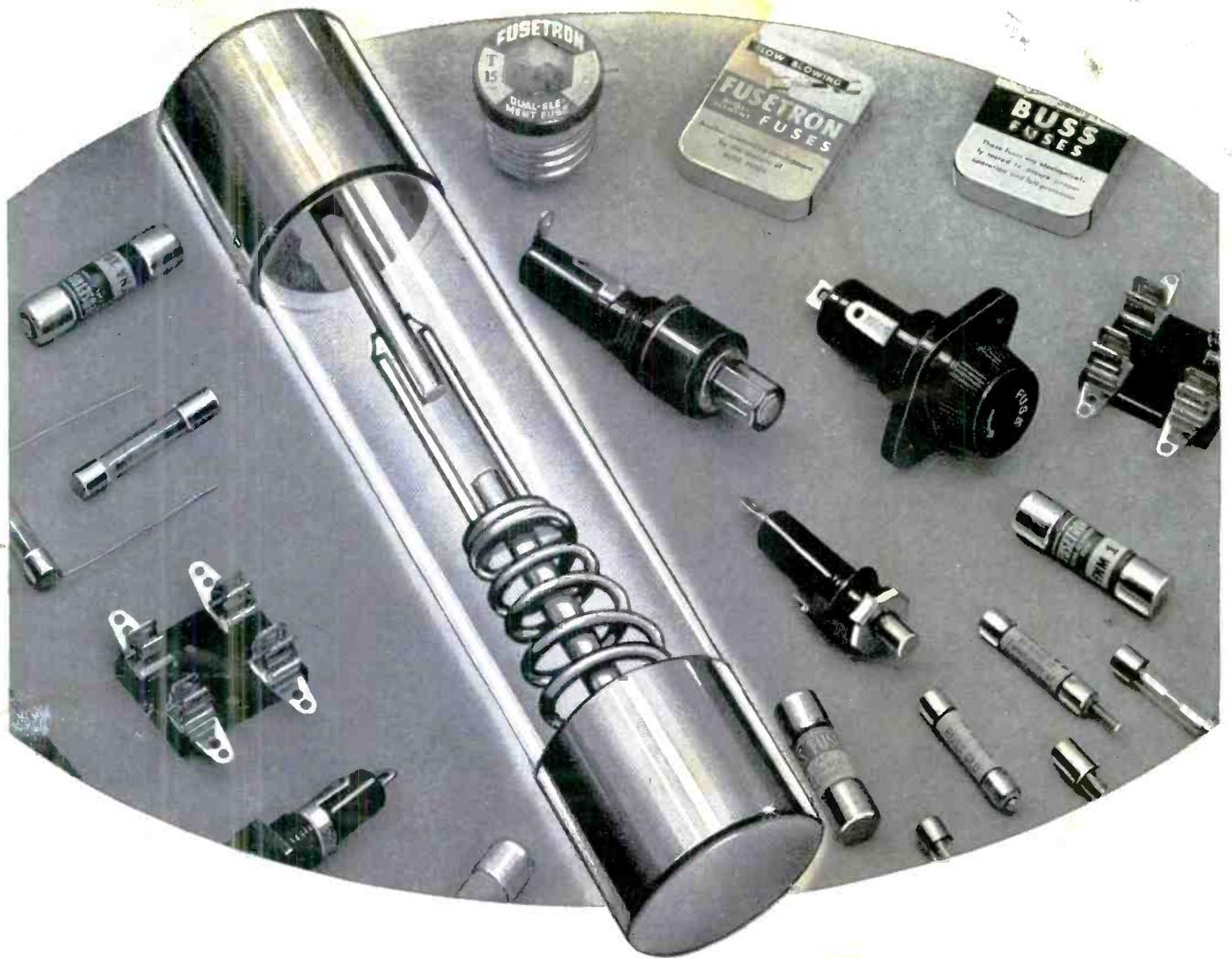

Save Time and Trouble by Standardizing on BUSS Fuses

YOU'LL FIND THE RIGHT FUSE EVERYTIME... IN THE COMPLETE BUSS LINE

By using BUSS as your source for fuses, you can quickly and easily find the type and size fuse you need. The complete BUSS line of fuses includes: dual-element (slow blowing), renewable and one-time types . . . in sizes from 1/500 amp. up — plus a companion line of fuse clips, blocks and holders.

**BUSS TRADEMARK
IS YOUR ASSURANCE OF FUSES OF
UNQUESTIONED HIGH QUALITY**

Over the past 43 years, millions upon millions of BUSS fuses have operated properly under all service conditions.

Thus, BUSS fuses have earned a reputation for accurate and dependable electrical protection.

To make sure this high standard of dependability is maintained . . . BUSS fuses are tested in a sensitive electronic device. Any fuse not correctly calibrated, properly constructed and right in all physical dimensions is automatically rejected.

LET BUSS FUSES HELP PROTECT YOUR PROFITS . . . The dependability of BUSS fuses helps you avoid 'kicks' and complaints that the fuses you sold or


installed failed to protect or blew needlessly. This safeguards you against costly adjustments and 'call-backs'. It pays to refuse to take a chance with anything less than BUSS quality in fuses.

For more information on BUSS and FUSETRON Small Dimension fuses and fuseholders . . . Write for bulletin SFB. Busmann Mfg. Division McGraw-Edison Co., University at Jefferson, St. Louis 7, Mo.

BUSS fuses are made to protect — not to blow, needlessly



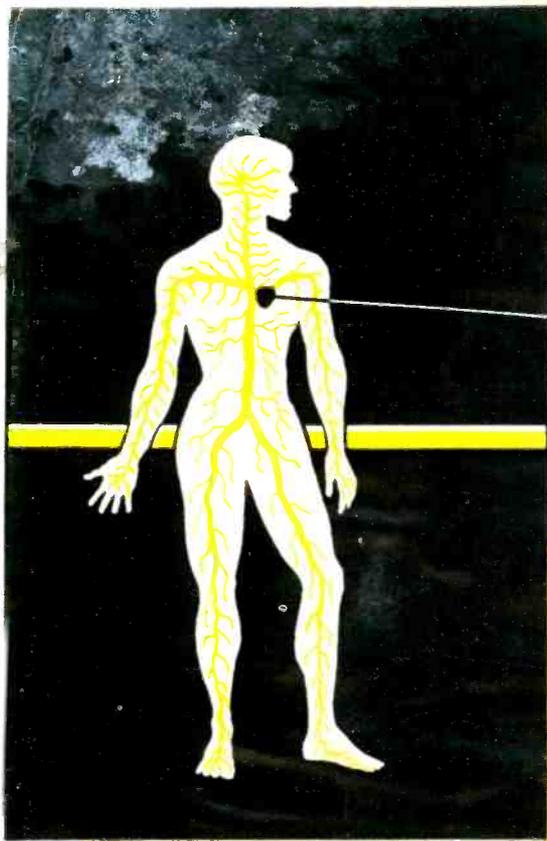
MAKERS OF A COMPLETE LINE OF FUSES FOR HOME, FARM, COMMERCIAL, ELECTRONIC, AUTOMOTIVE AND INDUSTRIAL USE.



THE
WING
DIPOLE




IS THE VERY
HEART
OF AN ANTENNA

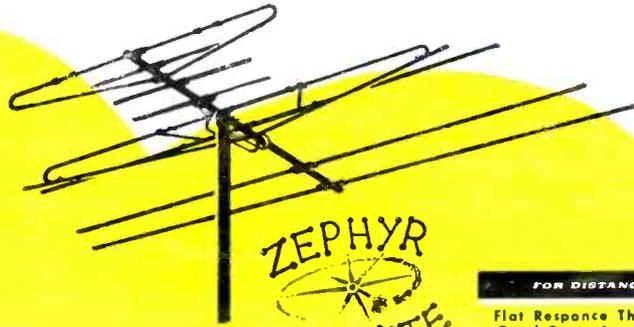

ZEPHYR
MITE

FOR DISTANCE
Flat Response That Gives
Good Reception on Both
Black & White & Color

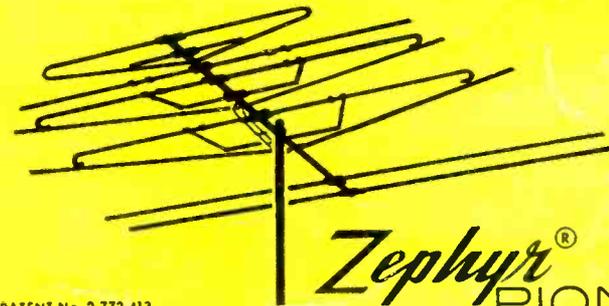EXTENDED "WING" DIPOLE
The Heart Of the Antenna
With The Increased Power and Sensitivity
Of The "WING" DIRECTOR
Exclusive Features Of The
TRIO ZEPHYR FAMILY ANTENNAS
THE LINE WITH PROTECTION



Zephyr[®]
PIONEER

U.S. PATENT No. 2,772,413
CANADIAN PATENT No. 541,670

ZEPHYR ROYAL[®]

FOR THE MAXIMUM

In TV Enjoyment

New
EXTENDED
"WING" DIPOLE

With The
"WING" DIRECTOR

COLLINEAR DIRECTOR

STAGGER - TUNED

THE NATION'S BEST PERFORMING ANTENNA ON BLACK & WHITE
EXCELLENT FOR COLOR RECEPTION



Export Sales Div., Scheel International Inc., 5909 N. Lincoln Ave., Chicago, U.S.A.

Cable Address: HARSHEEL

COPYRIGHT 1957 TRIO MFG. CO.

FOR EXTREME DISTANCE


Use: The

EXTENDED "WING" DIPOLE

And The

"WING" DIRECTOR

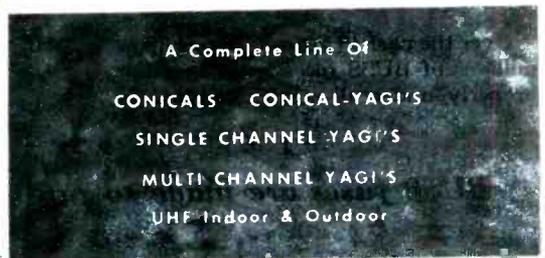
COLLINEAR DIRECTOR
for increased gain
on the highs



A Complete Line Of
CONICALS CONICAL-YAGI'S
SINGLE CHANNEL YAGI'S
MULTI CHANNEL YAGI'S
UHF Indoor & Outdoor

EPON[®] RESIN does it!

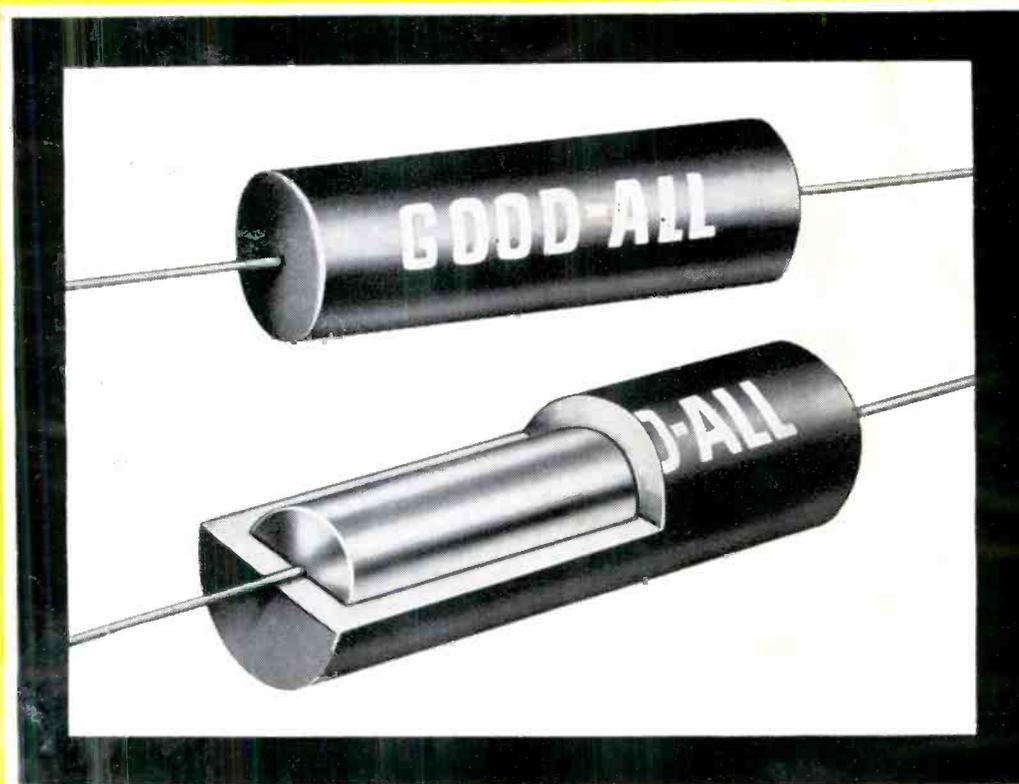Improved GOOD-ALL capacitors have low leakage, high stability—even in extremely humid climates



Here's how:

EPON RESIN is helping to set new standards of excellence in a line of 600 UE capacitors made by Good-All Electric Manufacturing Company, Ogallala, Nebraska.

Good-All reports that Epon resin offers superior moisture resistance . . . far better humidity protection than obtained with

conventional molding materials. These capacitors offer rugged, trouble-free performance because Epon resin assures high dielectric strength, low leakage, great resistance to chemical and corrosive attack, and handsome appearance.

For molding . . . for potting . . . for laminating, sealing and encapsulating . . . Epon resins are pre-

ferred because they offer an almost ideal combination of electrical and physical properties.

. . .

Write for complete information on the use of Epon resins in protective enamels, tool and die materials, etched circuit laminates, transformer and motor sealing compounds.

SHELL CHEMICAL CORPORATION

CHEMICAL SALES DIVISION, 380 Madison Avenue, New York 17, New York

Atlanta • Boston • Chicago • Cleveland • Detroit • Houston • Los Angeles • Newark • New York • San Francisco • St. Louis
IN CANADA: Chemical Division, Shell Oil Company of Canada, Limited • Montreal • Toronto • Vancouver



GOOD-ALL CAPACITORS



The "Capacitor of Tomorrow"

600-UE Mylar* Dielectric • Molded in Epoxy**

NEW to the replacement market! Widely used by leading equipment manufacturers.

The 600-UE is created by the skillful combination of new "wonder materials," and Good-All's advanced design, exclusive production technique and tight quality control. It is ideal for replacement use in today's modern circuitry.

FEATURES: • Low leakage • High stability • Long, trouble-free life • Rugged construction • Extremely reliable service in humid climates

SUPERIOR QUALITY • COMPETITIVE PRICE

DU PONT

***MYLAR**® is DuPont's trade name for their amazing space-saving polyester film. This thin, tough film makes an ideal capacitor dielectric. Its inherent electrical stability and exceptional dielectric strength contribute greatly to the trouble-free service of the 600-UE.

SHELL

****EPON**® is Shell's trade name for their epoxy resin wonder plastic molding compound base. Far superior to common molding materials, Epon forms an extremely rugged moisture-tight case. Leads adhere securely to the compound. High dielectric strength is also an attractive feature of this tough, dense material.



GOOD-ALL ELECTRIC MFG. CO.

Distributor's Division • 26 RITTENHOUSE PLACE • ARDMORE, PENNSYLVANIA

A wonderful offer
 from the
**RAYTHEON RECEIVING
 TUBE DISTRIBUTORS**
 who sponsor
 the Raytheon Bonded Dealer
 Program . . .

at no added cost . . .

GROUP
 for Raytheon
 who by preference

Now, Registered Bonded Dealers can gain personal security for themselves and their families — automatically increase their life insurance coverage, through their regular purchases of Raytheon Receiving Tubes. The amount of coverage is determined by the quantity of Receiving Tubes the dealer buys.

The New England Mutual Life Insurance Company has created a Group Life Insurance Plan for Raytheon Bonded Electronic Technicians — a plan offered exclusively by Raytheon Distributors who sponsor the Bonded Dealer Program. Any such Distributor who meets the necessary requirements for setting up a Group Life Insurance Plan for Bonded Dealers may give them this valuable protection without the necessity of a physical examination. Check with your Raytheon Sponsoring Distributor and see if he has it available to you.

If you're not at present a Raytheon Bonded Dealer, better see your Sponsoring Distributor as to whether you can qualify. You'll find being a Raytheon Bonded Dealer a real asset to you. You'll find using Raytheon quality receiving tubes is a big help, too.

**Administered and underwritten by New England Mutual Life Insurance Company*



| | | | |
|---|--|---|--|
| RAYTHEON MANUFACTURING COMPANY | | | |
| Receiving and Cathode Ray Tube Operations | | | |
| NEWTON 58, MASS. 55 Chapel Street | CHICAGO, ILL. 9501 Grand Ave. (Franklin Park) | ATLANTA 6, GA. 1150 Zanolite Rd. N.E. | LOS ANGELES 7, CALIF. 2419 So. Grand Ave. |
| Raytheon makes all these | | } Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes and Transistors, Nuclear Tubes, Microwave Tubes. | |
| | | |  Excellence in Electronics |

LIFE INSURANCE*

Bonded Electronic Technicians
use **RAYTHEON RECEIVING TUBES**




Snyder
PHILADELPHIA

TNT*

TORQUE TV TENNA®


EXPLODES the OUTDOOR MARKET!

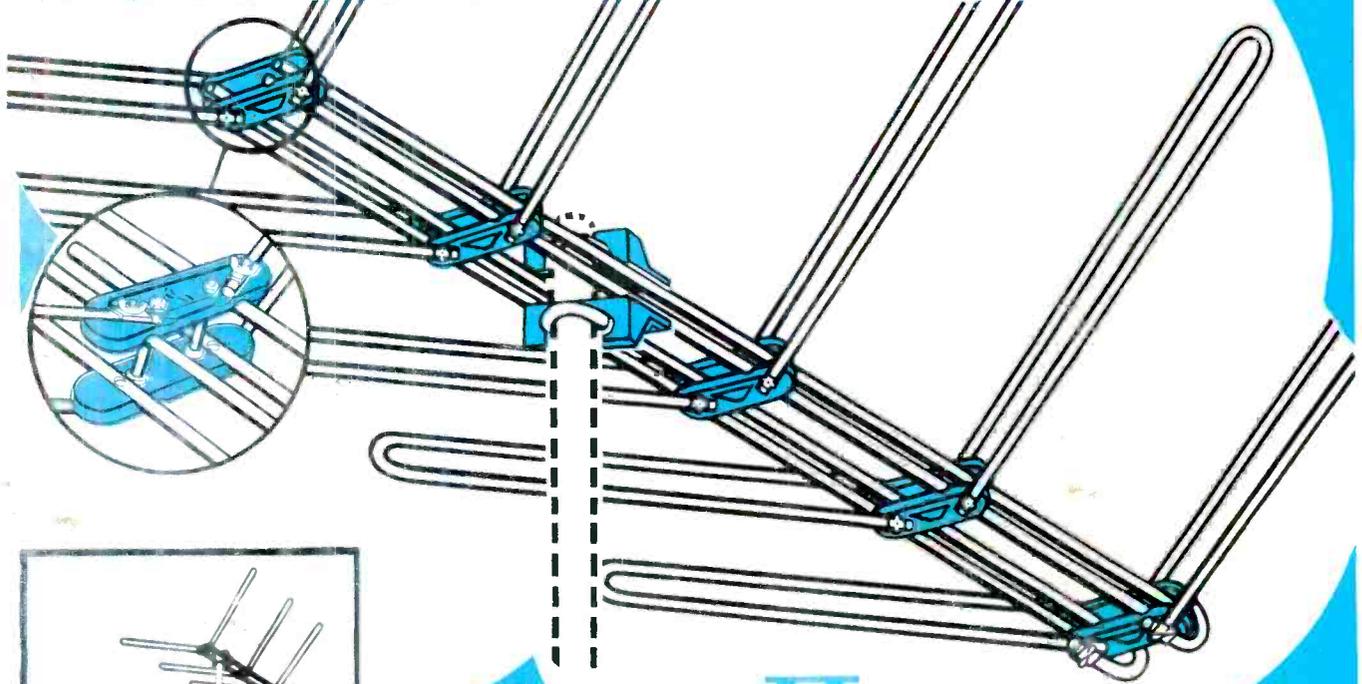

TNT V

NEW

***Torque-N-Tenna**

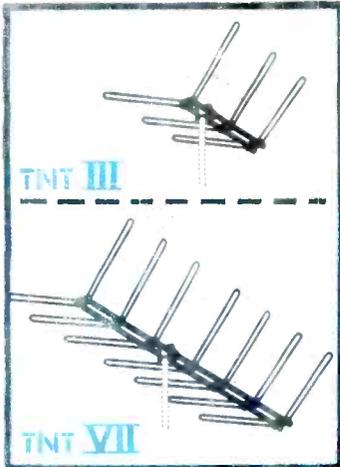


ALSO AVAILABLE IN
'DO-IT-YOURSELF'
KIT PACKAGES



gives you {
REPLACEMENT BUSINESS
BIGGER SALES
GREATER PROFITS

SNYDER

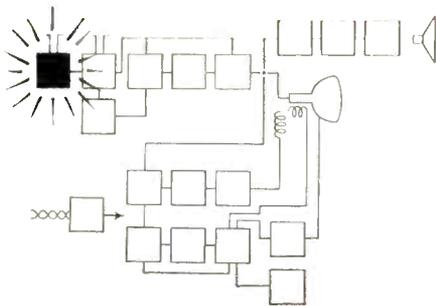MANUFACTURING CO.
PHILADELPHIA • TORONTO
EXPORT ROBURN AGENCIES, N. Y.
WAREHOUSES: LOS ANGELES, SEATTLE, DALLAS



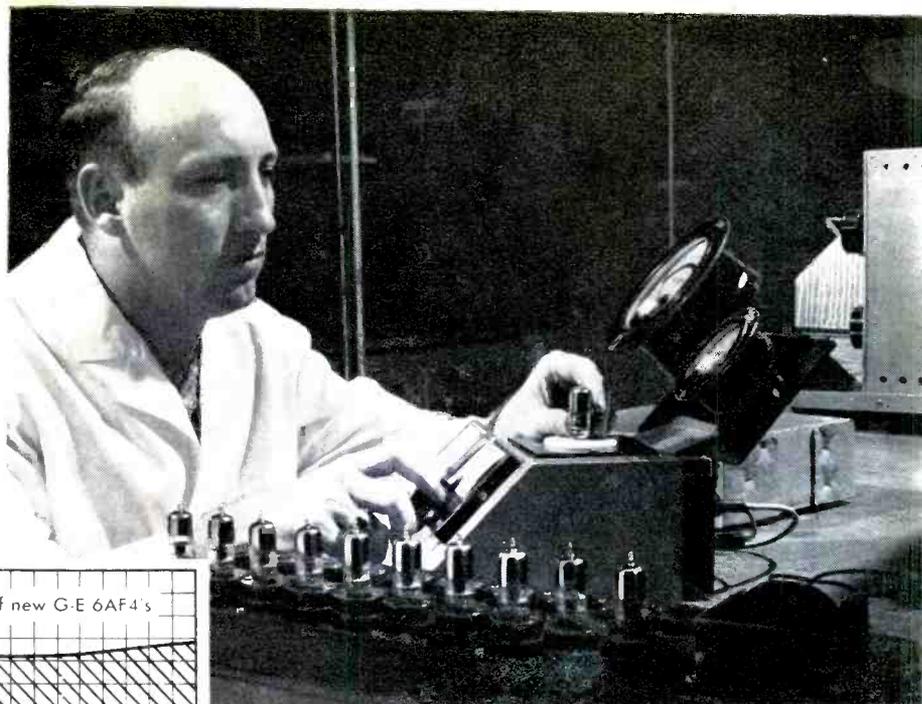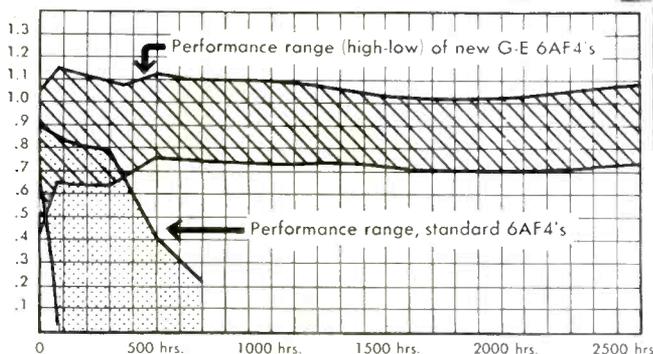Life-test comparison chart below shows oscillator activity versus hours of life of new G-E 6AF4's and standard 6AF4's.



ABOVE: General Electric Design Engineer J. G. Tucker checks, for oscillator activity, new G-E 6AF4 tubes that are undergoing life test. LEFT: Effect of tube operation over long periods on new vs. standard 6AF4's is shown by the chart. Tests of many thousand tubes are represented. Note that the oscillator activity of new G-E 6AF4's averages a straight horizontal line, whereas standard 6AF4's show a sharp, sudden drop . . . meaning rapid loss of picture quality.

Now . . . from General Electric . . . a long-life 6AF4 for sustained high-quality u-h-f TV reception!

Only General Electric can give you . . . in the long-life 6AF4 u-h-f oscillator tube . . . the tube industry's newest, most effective means for making friends of service customers. Installing a new General Electric 6AF4 cuts snow, brings a clear picture that will retain its high quality. Tests prove that after 2500 hours and more of service, this u-h-f oscillator tube performs just as well as one freshly taken from a carton!

Virtually no receiving tube is called on to undergo the same electrical "stresses" as a 6AF4. With small electrodes and close spacing to meet low-inductance, low-capacitance demands of up-to-900-mc operation, current density is 5 to 6 times that of other triodes.

Consequently, extremely high cathode emission is called for. The plate and grid, subjected to high tem-

peratures, must resist gas-forming tendencies that would destroy tube efficiency. Stiff requirements like these have meant short life for 6AF4's. Now General Electric, through creative design, combines new materials with new manufacturing and test methods to give TV-technicians and set-owners a 6AF4 that *for the first time* is fully as efficient and dependable as other tubes.

The same long-life performance is being built into General Electric's 2AF4, 2AF4-A, 3AF4-A, and 6AF4-A.

Outstanding examples like this of ever-higher quality, of design steadily improved, make General Electric tubes the best you can install. Phone your G-E tube distributor at your earliest opportunity! *Distributor Sales, Electronic Components Division, General Electric Company, Owensboro, Kentucky.*

Progress Is Our Most Important Product


GENERAL  ELECTRIC

161-1A10

how to pick up the chips in the



Non Color-Blind **HELIX**

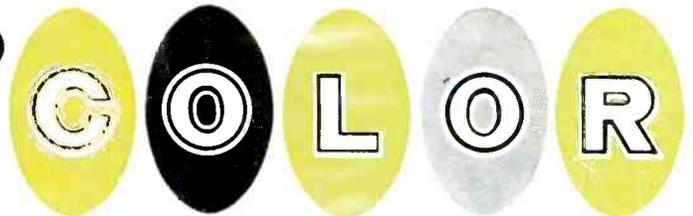

Yes Mr. Service Dealer

Your thousands of Colortenna orders and reorders prove it . . .

You like the idea of an integrated antenna line that assures you the right antenna answer for every reception problem . . .

You like the idea of the red helix which identifies the Colortenna to prospects as an outstanding performer in black and white and color . . .

You like the big prizes and trips you win in the fabulous Colortenna Sell-A-Bration . . .

You like the hard-hitting local advertising and promotion that pays off in Colortenna sales in your store . . .

You like the ready-made customer acceptance and confidence that Colortenna performance builds for you . . .

NOW WITH BRILLIANT ALCOA SPEC.

Color in 1958

You'll love the spectacular new JFD Colortenna line that will send your antenna profits rocketing to new highs. Put its dynamic selling power to work for you by seeing your JFD distributor now.

CASH IN ON THE SELL-A-BRATION SWEEPSTAKES!

Over \$100,000.00 worth of prizes given so far to TV dealers and servicemen!

3 GRAND PRIZES TO SERVICE-DEALERS

with highest totals for season, September 1, 1957—March 31, 1958.

Winners to be announced May 19, 1958

First Prize ALL-Expenses Paid Trip for Two to Paris

Second Prize ALL-Expenses Paid Trip for Two to Bermuda

Third Prize ALL-Expenses Paid Week-End for Two at the Waldorf-Astoria in New York

EVERY COLORTENNA COUNTS FOR FREE PRIZES!

Wallace 16 Pc. Tableware Set
Only 14 Power Helix—PX911S

12 Spalding GOLF Ball Set
Only 25 Star Helix—SX711


Chatham Orlon Blanket
Only 11 Wonder Helix—WX811S

Samsonite Ladies Case
Only 38 Wonder-Helix—WX811

Samsonite Men's "Quick-Tripper"
Only 40 Wonder-Helix—WX811

Aluminum Fishing Tackle Box
Only 11 Star Helix—SX711S

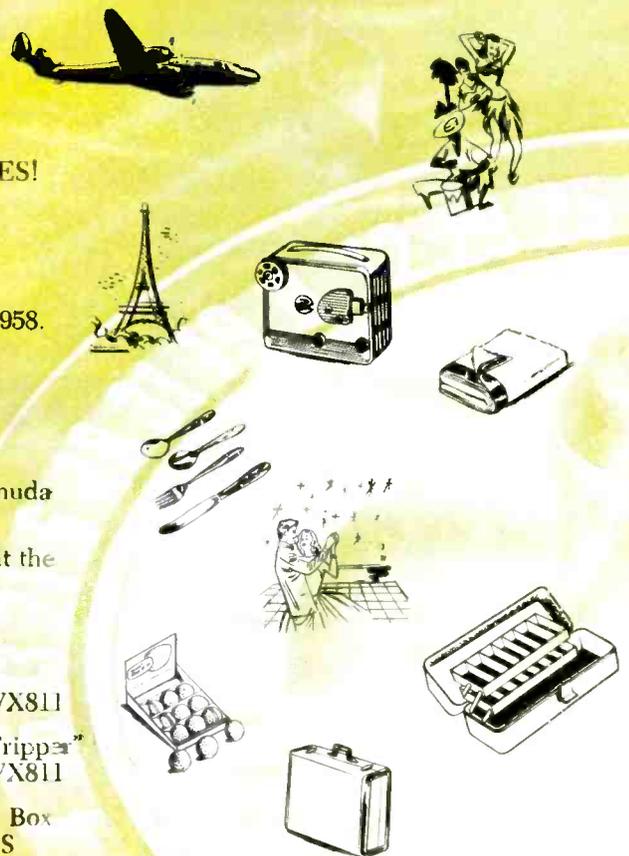PLUS HUNDREDS OF OTHER BRAND-NAME PRODUCTS



TV Antenna Market

TENNAS[®]

SUN-FAST GOLD ANODIZING!

GLEAMING GOLD ANODIZING GIVES YOU MORE TO SHOW!... MORE TO SELL!

New... new... new! *Gold* Colortennas with ALCOA Spec. fade-proof gold anodized finish that catches the eye and makes them buy.

NEW UNBREAKABLE "KRALASTIC" INSULATORS


You get the toughest, hardest, strongest insulators money can buy. Matchless electrical, physical and weathering properties for better performance all year, every year.

NEW RIGIDIZED REFLECTORS

Twice the strength—twice the rigidity. Every element over 30 inches long is now reinforced with 16 inch aluminum dowels in center. Never before so many dynamic selling features packed in one antenna.



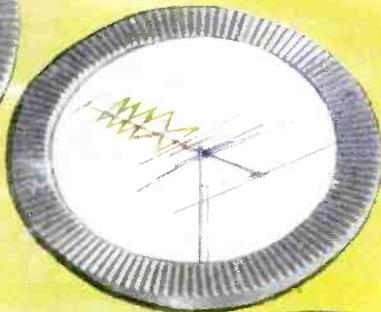WONDER-HELIX
model type
AX811 Gold Anodized
WX811 Regular





POWER-HELIX
model type
AX911 Gold Anodized
PX911 Regular



STAR-HELIX
model type
AX711 Gold Anodized
SX711 Regular

SUPER-HELIX
model type
AX511 Gold Anodized
RX511 Regular

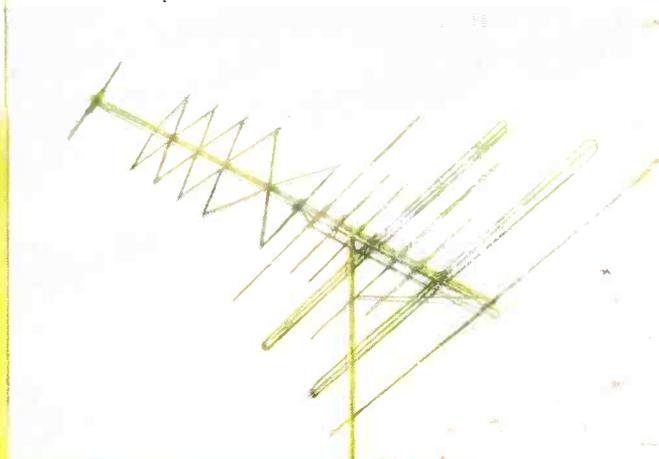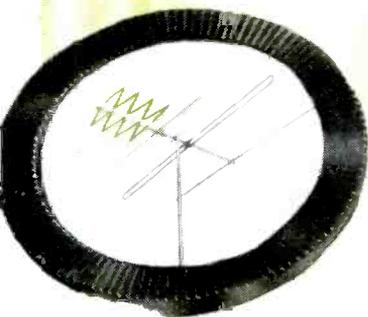JUNIOR-HELIX
model type
AX311 Gold Anodized
JX311 Regular



THE FUSE IS LIT! *Get Set* FOR
THE COLORTENNA BOOM in 1958

IN PROFITS!
PERFORMANCE!
PREMIUMS!
PROMOTION!



See your JFD distributor.

ELECTRONICS CORP.

Brooklyn 4, N. Y.

Pioneers in electronics since 1929



A merely insert card in slot

B flip power lever to "power-on" position

C press calibrate lever and adjust calibration control

simple as **A-B-C...**

NEW RCA WT-110A AUTOMATIC TUBE-TESTER

means more service profits!

Dollar for dollar, feature for feature, you'll find RCA's WT-110A the fastest, most accurate automatic punched-card tester you can buy today. It's a virtually *obsolescence-proof design* ... from the exclusive RCA 700-card capacity magazine file that always keeps the pre-punched cards in type number sequence, to the fully automatic circuit setup (including *all* operating voltages) and the easy, do-it-yourself punch card accessories available to keep the tube-card file up-to-date!

See and test the WT-110A at your local RCA Distributor. Prove to yourself what a boost in business, prestige, profits the RCA-WT-110A can mean!



**TEST EQUIPMENT
RADIO CORPORATION OF AMERICA**

Electron Tube Division, Harrison, N. J.




All this for
\$199.50


USER PRICE (Optional)
Prices higher in Hawaii and Alaska

- automatically sets up socket connections, and all operating voltages such as heater, signal, plate and screen voltages, and bias (both fixed and cathode).
- checks tubes for transconductance, gas, shorts, and leakage between elements.
- automatically selects correct conditions from 220 possible combinations of heater voltage (from 0.1 volt to 120 volts) at currents up to 4 amps., 10 bias voltages and 11 values of cathode resistors.
- tubes, such as rectifiers, tested under heavy load currents up to 140 ma per plate.
- high-and-low sensitivity ranges for leakage tests.
- 12 volt plate and screen supply for testing new auto-radio tubes.
- meter protected against burnout.
- test card provided for checking instrument.
- 239 pre-punched cards supplied with instrument cover 95% of currently active TV tubes. Pre-punched accessory cards available.
- active card magazine capacity—350; storage capacity—350...a total capacity of 700 cards.

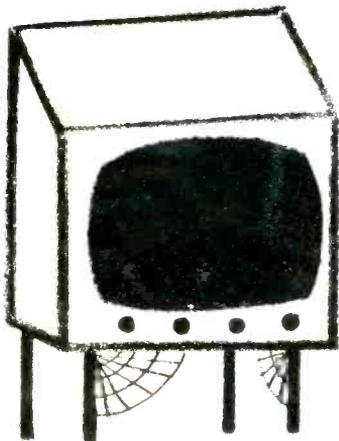Reputation Builder #2: it pays to be prompt



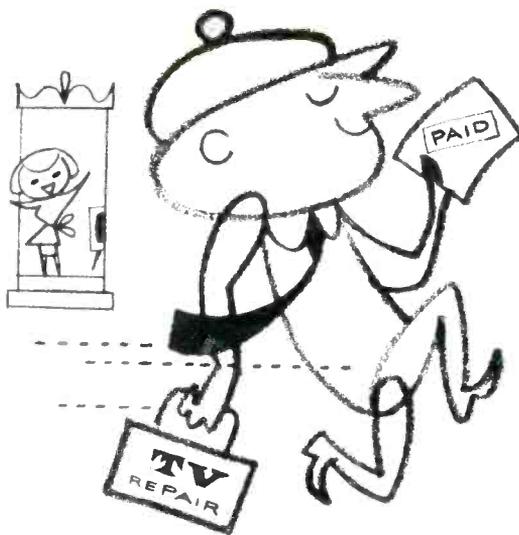- Only 51% of set-owners who wait 3 to 4 days for service are satisfied with the bill



- BUT . . . 69% of customers getting same-day service are satisfied with the bill

it pays to replace with Sprague Twist-Lok* Electrolytics



- Another way to build and hold a reputation is to insist on top quality replacement parts. Callbacks due to replacement failures not only cost you *money* . . . they also cost you *customers*! Replace with *less* than the best and you place your reputation at stake. In capacitors, the best is *Sprague*.

- Take the Twist-Lok 'lytic, for example. Sprague TVL's have everything! More exact ratings . . . higher quality to meet original equipment specifications. *Every* TVL for *every* voltage rating is made with expensive high-purity etched-foil anode construction—ultra stable film formation techniques. And etched cathodes meet the toughest ripple requirements. No wonder they're your first line of defense against callbacks!

- Get your copy of Sprague's latest radio and TV service catalog, C-455. Write Sprague Products Co., Distributors' Division of Sprague Electric Company, 61 Marshall Street, North Adams, Mass.

don't be vague...insist on

★ Trademark

SPRAGUE®

world's largest capacitor manufacturer

SPRAGUE RESEARCH IS CONSTANTLY PRODUCING NEW AND BETTER CAPACITORS FOR YOU

FULL COLOR TV



MODEL U-98—first and finest fully automatic rotator. Eye-appealing decorator colors—Ivory, Forest Green and Standard Mahogany Grain. Retail \$44.25



MODEL T-12—with exclusive Tenna-Teller Pointer—highly accurate. Striking modern design. Forest Green and Ivory or Standard Mahogany. Retail . . . \$34.25
Decorator Colors priced \$2.00 extra.

demands reliable



DON'T ASK VIEWERS TO PUT UP WITH A 'STAY-PUT' ANTENNA!

- TV authorities admit the higher sensitivity of color.*
- Viewers won't tolerate weak, washed out color!
- Maximum directivity with ALLIANCE TENNA-ROTOR is the best insurance for top antenna performance—for FULL COLOR!

Wherever you find Color TV, it will pay you to recommend Alliance!

• Every color TV buyer is a potential Tenna-Rotor sale . . . even in metropolitan areas. Because the "**fringe**" area for color is closer to the transmitter!

Viewers who might tolerate black and white TV that's "so-so", will **not** put up with irritating, "ghosty" color. And independent interviews **at point of sale** show that color TV customers find it **easy** to say Yes to Alliance Tenna-Rotor!

*Practically all TV authorities agree "color is critical"—more sensitive than black and white. "Chromatic gradation" with color that's ghosty, is harder on the eyes than black and white. Many recommend properly installed outdoor antennas with rotators, to improve directivity of the antenna, to help overcome interference and reduce annoying effects caused by the higher sensitivity of color, and the normal characteristic of color to "drop out" quicker.

Ride the Trend to Color . . .
and soak up those extra profits with Alliance! Tie in with the longest and strongest TV campaign in TV accessory history! Remember . . . Poor color is worse than no color . . . and Alliance Tenna-Rotor is the sensible answer!

**THE ALLIANCE
MANUFACTURING COMPANY, INC.**

(Division of Consolidated Electronics Industries Corp.)

ALLIANCE, OHIO

In Canada—ALLIANCE MOTORS, Schell Avenue, Toronto 10.

The Growing Stature of COLOR-TV

COLOR TELEVISION has reached a point of technical excellence and stabilization.

In the three years since its debut, color-TV has made truly remarkable progress, both technically and commercially, and is now firmly established as a mature business promising tremendous potentials for the alert Service Man.

Color-TV has forged ahead so rapidly because of the extensive experience gained in black-and-white developments, and engineering ingenuity. Measured by the rate of increase in retail sales, color has exceeded even the phenomenal rate of increase enjoyed by black-and-white during the comparable period of development.

The slow evolution of black-and-white chassis was dictated by tube-size problems. Many, many years elapsed before 21-inch tube chassis were available in quantities. But in color, the change from small to large tubes was swift; 21-inch models appeared very soon after a limited production of 15-inch sets. Today's receivers feature 21-inch glass-envelope picture tubes with brilliance great enough to permit satisfactory viewing in brightly-lighted rooms.

CIRCUIT-WISE, the advancements have been marked, too. The tube complements have been reduced substantially, semiconductors have been introduced in simplified networks and adjustments have been minimized. Controls regulating color—

and there are only two now—have been removed from the hidden panel and moved up next to the channel selector. One is a color control designed to bring color into the picture in varying intensity; the second is a tint control (formerly called hue) which shades the color to the viewer's personal taste.

The mystery in color has been removed. The supplementary color circuits present no problems to those who have a sound knowledge of black-and-white design.

COLOR RECEIVERS now being made generally arrive from the factory in ready-to-operate condition. But one must always be prepared—armed with sufficient knowledge of the chassis, and adequate test equipment and tools—to make adjustments, perhaps for color purity or convergence, to insure performance which will instill customer confidence.

THE GIANT STRIDES made by color-TV offer enormous opportunities to the Service Man in installation, repair and sales, too.

An exclusive progress report on the growing stature of color-TV appears in this issue on pages 18 to 27. Described for the first time are the circuits used in the latest glass-picture-tube chassis, new features of the viewing tube, test equipment required, and an analysis of the outstanding prospects in color-TV for every Service Man.

A Symbol of Value



A WELL-KNOWN SYMBOL is like a good reputation—difficult to establish and even more difficult to maintain.

During our daily activities, we come into contact with many trademarks which symbolize an assured measure of performance or quality.

Like its counterparts, the ABC symbol, shown above, signifying membership in the Audit Bureau of Circulations, provides you with a reliable measure of our publication standards.


To keep you as a subscriber—year after year—this publication must provide a service worth your money. Of course, the degree to which we hold

your interest—as verified in the ABC report, showing our paid circulation—is what interests our advertisers, too.

Thus the ABC symbol is a constant reminder that (1) your interests come first with us and that (2) our advertisers get what they pay for—your interest.

SERVICE, the only technical journal in the radio-TV trade which has maintained *unbroken* membership in the ABC for over twenty years, with a continuing record of the largest audited circulation in the field, is proud once again to salute the Bureau, during this, ABC month.

Why The Television

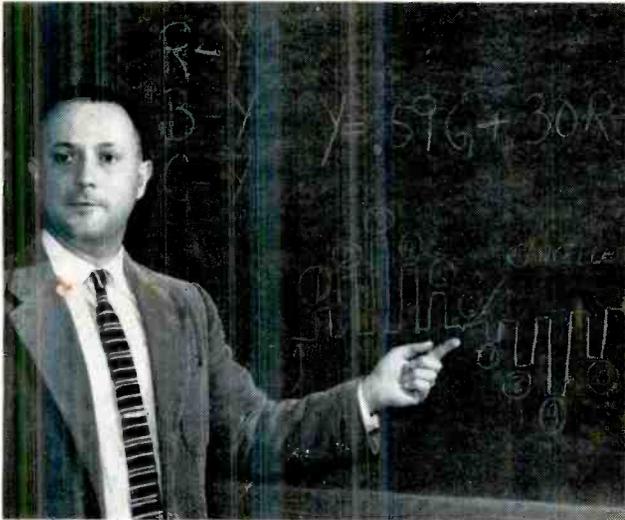

by C. E. WALTER, RCA Service Company, Inc.

C. E. WALTER, delivering a talk, one of a nation-wide series, on color-TV, at a recent association meeting.

THERE SURELY CAN BE no doubt in the mind of the average television Service Man that color-TV, as an entertainment medium, is second to none in its potential as a factor in his future business success. Why, then, should not the Service Man be a booster of color television? Most of the TV industry, manufacturers and distributors alike, have been taking every possible means to build a foundation for color-TV which could only provide one answer to that question; the Service Man should boost color at every opportunity. It will be his future, and the efforts to provide a firm basis for this future will be rewarded.

TV has meant a great deal to those of us associated with this miraculously growing industry. We see in it a future which will demand the best from the television Service Man, and it is obvious that those who can learn color now, who can gain invaluable experience, and who can invest in this future, will be the ones to benefit most. We have already seen color-TV receivers begin to move into customer's homes at a rapidly increasing rate. Thousands of Service Men have already had the opportunity to gain considerable experience and *know how*. This experience has proved several things: (1) The quality, dependability and performance of color-TV sets is definitely established as excellent; (2) the servicing industry is ready in many areas to handle the color installation and service demands, and (3) customers are ready to buy.

Service Charges

We might examine the pattern of charges for color-TV service. Gen-

erally speaking, Service Men are charging, and getting, more for the more specialized knowledge required for color installation and service. This is justified, though it is not a universal pattern. Some self-servicing dealers, who also sell television, are charging the same rates for color service as for black-and-white. At first, this was admittedly a *sales tool*, permitting the dealer to give a favorable answer to the customer who asked, "Don't you charge more for color television service?" After some months of operation under this policy, it was then evident that a few well-trained, well-equipped service organizations *could* handle color installation and service at black-and-white rates. It should be made clear that the Service Man who has invested a lot of his time, money, and effort into training and equipping himself for color television should be entitled to adequate compensation and a fair return. The proper installation, setup, and servicing of color television is somewhat more critical, and more time-consuming than for black-and-white.

The Service Man—Key to Color

Actually, it is the Service Man who is the key to successful color television sales efforts. The sale of a product does not automatically imply consumer satisfaction. With any product as complex as a television receiver, color or black-and-white, performance over a period of time is demanded. The quality of the installation is of particular importance — first impressions are created—and to the installing Service Man falls the honor of making or breaking the sale. Following a suc-

cessful installation, the burden of keeping the instrument sold falls upon the Service Man. It can truly be said that the role of the Service Man in color television is the most important single feature in achieving the ultimate goal — consumer satisfaction. Such a statement is probably subject to some debate, but story after story of successful dealer sales efforts in color television is being recorded, and each and every one of them stresses the importance and dependence placed upon the installing and servicing personnel.

Another of the important reasons why the Service Man should boost color, is that his name is then associated with color by his customers. Even though the customer may not be interested in color at this time, just a few favorable words by the Service Man may start Mrs. Jones thinking, and when Mrs. Jones is ready for color, she knows you are ready to help her. There have been instances when customers, believing that color service is more complex and more demanding than black-and-white, feel that the Service Man who advertises and boosts color must be better qualified on black-and-white than his competitor who sticks to black-and-white service, or who has a negative approach to color. This is entirely logical, and in many cases the competent Service Man who effectively services and installs color, also enjoys an increase in his black-and-white business.

In many communities there is a dealer or independent Service Man who has set himself up as *Mr. Color Television* in his area. This has been very effective. By advertising and

Service Man Should Be A COLOR-TV Booster

promoting the association between color and the Service Man, the consumers in the area will naturally turn to *Mr. Color Television* with their color questions and problems, and, as previously mentioned, will often bring black-and-white problems as well.

The color-television servicing specialist often finds himself in contact with the type of consumer who is financially more able to promptly pay for the service, or who may be interested in the purchase of additional equipment or appliances. Regardless of the type of customer, however, the Service Man is an excellent source of prospects for many types of home equipment. Many sales and service dealers will pay a commission to their Service Men who submit prospects resulting in sales. Many independent Service Men have similar arrangements with local retail dealers.

The Product

Color-TV receivers have come a long way—from the 15-inch picture tube, and complex circuitry of early 1954, to the 21" picture tube and simplified circuitry of today. The receiver quality is most satisfactory. This is a matter of statistical record. They are much easier to operate, to install and to service.

The specialized test equipment for proper installation and servicing of color is available. Service Men often bring up the question of test equipment obsolescence. While it is always difficult to *star gaze*, it is felt that there is no reason why the excellent test equipment available today should become obsolete in the foreseeable future. Some of it is expensive, to be sure, but it is of high quality and durability, and favorable terms are available from most distributors.

Training

Adequate training facilities are available to the majority of the industry. Manufacturers have been conducting training programs at dealer-Service Man level, and have produced thousands of well-trained Service

Men. We have been conducting field training lectures and workshops (practical do-it-yourself training) since early 1954, and have had a total Service Man attendance of more than 105,000. Many trade and vocational schools are now offering color-TV courses, and excellent correspondence course training is available at low cost.

At one time it was felt that there would be TV-antenna problems in color. We have now learned from experience that this is not so. In many installations indoor type antennas are being used, though the superiority of a high-quality outdoor antenna, properly installed, cannot be denied. This is another avenue of possible profit for the Service Man—a new antenna. Unfortunately, there is considerable mis-information in the field about antennas in general. The antenna requirements for color are slightly more critical than for black-and-white, as a result of the added transmitted signal components. However, any efforts by the Service Man to improve the quality of the color signal delivered to the receiver antenna terminals, will also result in improved black-and-white performance.

Most of the factors which were

advanced several years ago as reasons why color-TV could not be pushed are now things of the past. The quality of the product is high. Color receivers are easier to install and service. Retail prices are more favorable. Many banks or other lending institutions, recognizing the future of color television, have favorable financing terms for the purchase of receivers. The frequency and quality of color programming have advanced tremendously. Some television stations transmit practically all of their local programs in color. Many more stations are being equipped; there are now almost 300 stations equipped to rebroadcast network color and more than 100 of these are equipped to originate color.

The manufacturers of today's color receivers have solved practically all of the problems related to production and distribution. This directly benefits the Service Man and the consumer. Fortunately, the Service Man has had a say in the design of today's receivers, and the installation and servicing adjustments are easier to make and more effective than ever before. The quality and performance are better than ever before; those who are

(Continued on page 48)

SIMPLIFIED COLOR-TV TUNING controls in new glass picture-tube color receivers; color and tint controls mounted on the upper right side of the cabinet. Color brings color into the picture; tint shades it to the viewer's personal taste.



Circuitry Report On 21-Inch COLOR-TV

Complete Analysis of

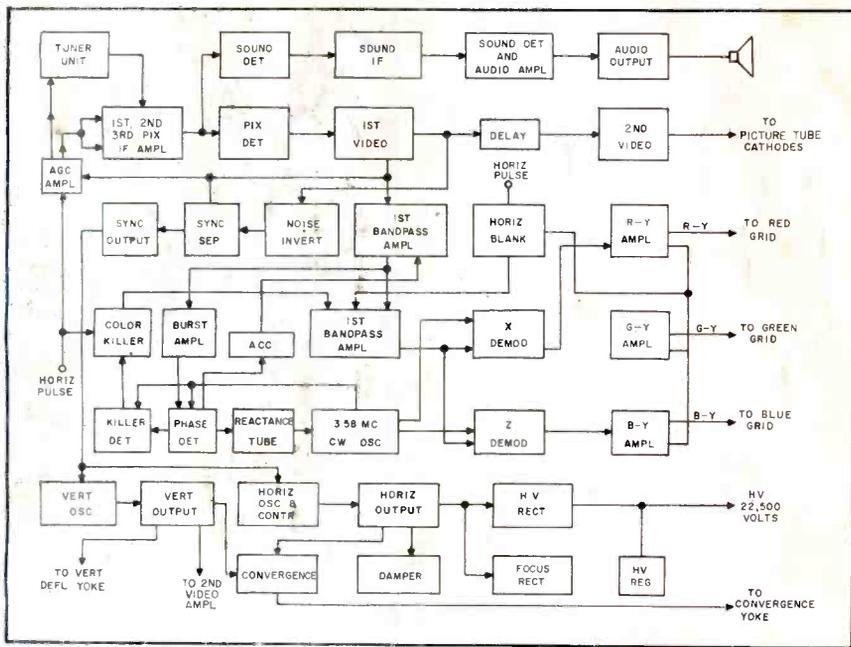


FIG. 1: BLOCK DIAGRAM of the complete RCA CTC7 color-TV chassis.

The 800 SERIES¹ COLOR-TV receivers¹ recently introduced by RCA include a number of features designed as conveniences not only for the consumer, but the Service Man.

A glass-envelope picture tube (21CYP22) with a viewing area of approximately 260 square inches is used in this new chassis.

Some of the customer features include improved picture brightness and contrast both for color and black-

and-white pictures, and convenient color-coded *tint* and *color* controls. These controls show, on an escutcheon, the direction of rotation for proper tuning to achieve the desired color effects on the viewing screen of the picture tube.

Other features of the CTC7 chassis include: Intercarrier FM sound system, quadrature-grid FM detector, separate picture and sound detectors, 4.5-mc sound trap and sound reject-

tion control in the input circuits of the video amplifier stages, *agc* control of the *rf* amplifier and the first and second picture *if* amplifier stages, an automatic noise-cancellation circuit, automatic-frequency phase control in the chrominance circuits, crystal-controlled 3.58-mc color subcarrier reference oscillator, stabilized *synchroguide* horizontal oscillator and control, an automatic chroma-control circuit, an automatic noise-immune color killer circuit, and continuously-regulated high-voltage to the ultor of the picture tube.

A feature of particular interest to the Service Man is the mechanical arrangement of the convergence circuits. The controls necessary to perform convergence adjustments are on a printed circuit in a mounting which is detachable from the cabinet. When removed from its normal mounting position it may be inverted and secured to two mounting screws provided on the rear of the cabinet, permitting adjustment from the front of the receiver.

The chassis contains six printed circuit boards. New type tube sockets are utilized on these boards and should prove a boon to the Service Man. From the top side of the printed boards each of the pin connections on the tube sockets are accessible through a guide opening. Thus, voltage measurements can be made quickly and easily whenever required.

Two types of tuner units are used in these receivers. The *vlf*-only tuners² use a new tube, 6BC8, in a driven grounded-grid circuit with *if* and FM traps in the input circuit. A



All of the deluxe models in this series use a new CTC7 chassis. Models are available with a *vlf*-only tuner, or optionally, a combination *uhf*-*vlf* head end; the *uhf*-*vlf* models have a U designation following the model number. *VHF* tuning in the U models is accomplished with a 13-position switch-type tuner; the 13th position automatically switches to a continuously variable tuning system which covers all 70-*uhf* channels.

FIG. 2: PICTURE-TUBE accessories required for the glass-tube color-TV models.

Chassis Using Glass Picture Tube

Circuits Used in RCA 800 Color-TV Line

by J. A. MAY, RCA Service Company, Inc.


6CQ8 triode-pentode is used as the local oscillator and mixer providing output in the 41-mc range. The *uhf-uhf* tuner uses a *vhf*³ and a *uhf* section⁴. The *uhf* section is similar to the type used in previous color receivers and consists of a 6AF4A local oscillator operating at fundamental frequency throughout the *uhf* range, and a 1N82 crystal mixer.

In *vhf* operation, the tuner, in the *vhf-uhf* combination, uses the same tubes and operates in the same manner as the *vhf*-only tuners. However, this tuner has an extra switch position. When switched into this position, the output of *uhf* unit is fed to the 6CQ8 which becomes a 4I-mc *if* amplifier for the *uhf* channels.

Three stages of picture-*if* amplification are used in bifilar-coupled stagger-tuned stages. The first and second picture *if* stages are *agc* controlled. The printed-circuit board⁵ for the picture *if* stages also includes separate detectors for picture and sound, a 4.5-mc trap, and a sound-rejection control. These features assist in minimizing the possibility of a 920-kc beat from appearing in the video during a color program; 920-kc is the difference-frequency resulting from the color subcarrier, 3.58-mc above the picture carrier, beating with the sound carrier, 4.5-mc above the picture carrier.

The sound system in this new color-receiver series differs from previous color receiver models in using a single stage of sound *if* amplification and a quadrature-grid FM detector—first audio stage similar to those used in current black-and-white receivers. A single 6AQ5A provides audio output and,

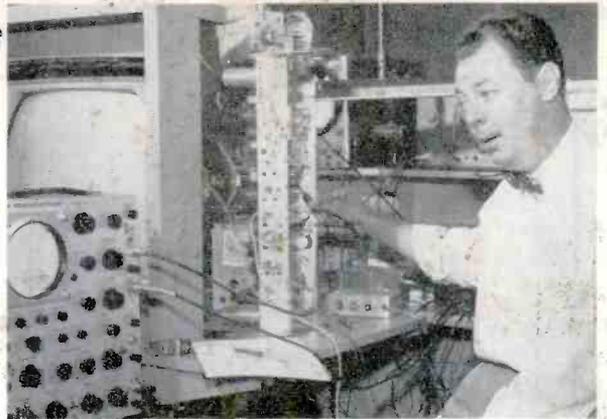(Right)
J. A. MAY in lab checking latest glass picture-tube color model.




in the cathode circuit, a secondary B+ source for other circuits in the receiver.

Two video amplifiers are incorporated, as in previous color receivers, with the first stage, the pentode section of a 6AW8A, serving as the signal distribution center for sync, *agc* and chroma information. A delay line, as is the normal practice, is in the grid circuit of the second video amplifier. A 12BY7A second video amplifier feeds the brightness component of

the color signal, or in the case of a black-and-white picture, the picture information to the cathodes of the picture tube through a dividing network. The dividing network is required because the phosphors in the picture tube, characteristically, have unequal light output efficiencies; thus, the dividing network supplies each cathode with the proper proportion of video signal during either black-and-white or color picture reception. The

(Continued on page 38)

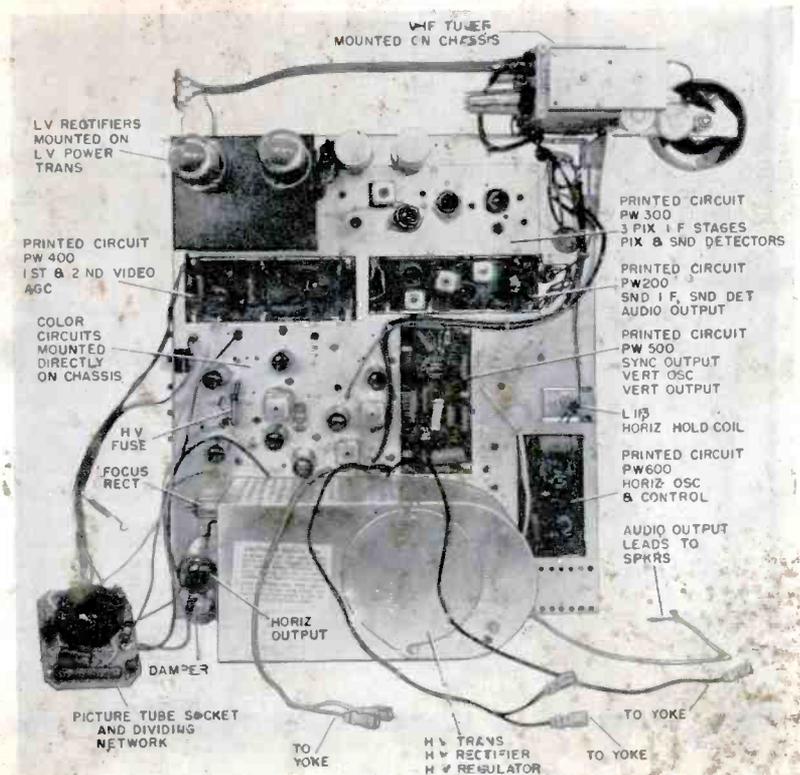

³KRK48A ⁴KRK49A ⁵KRK56D ⁶PW300

FIG. 3: TOP VIEW of color chassis showing key assemblies and components.

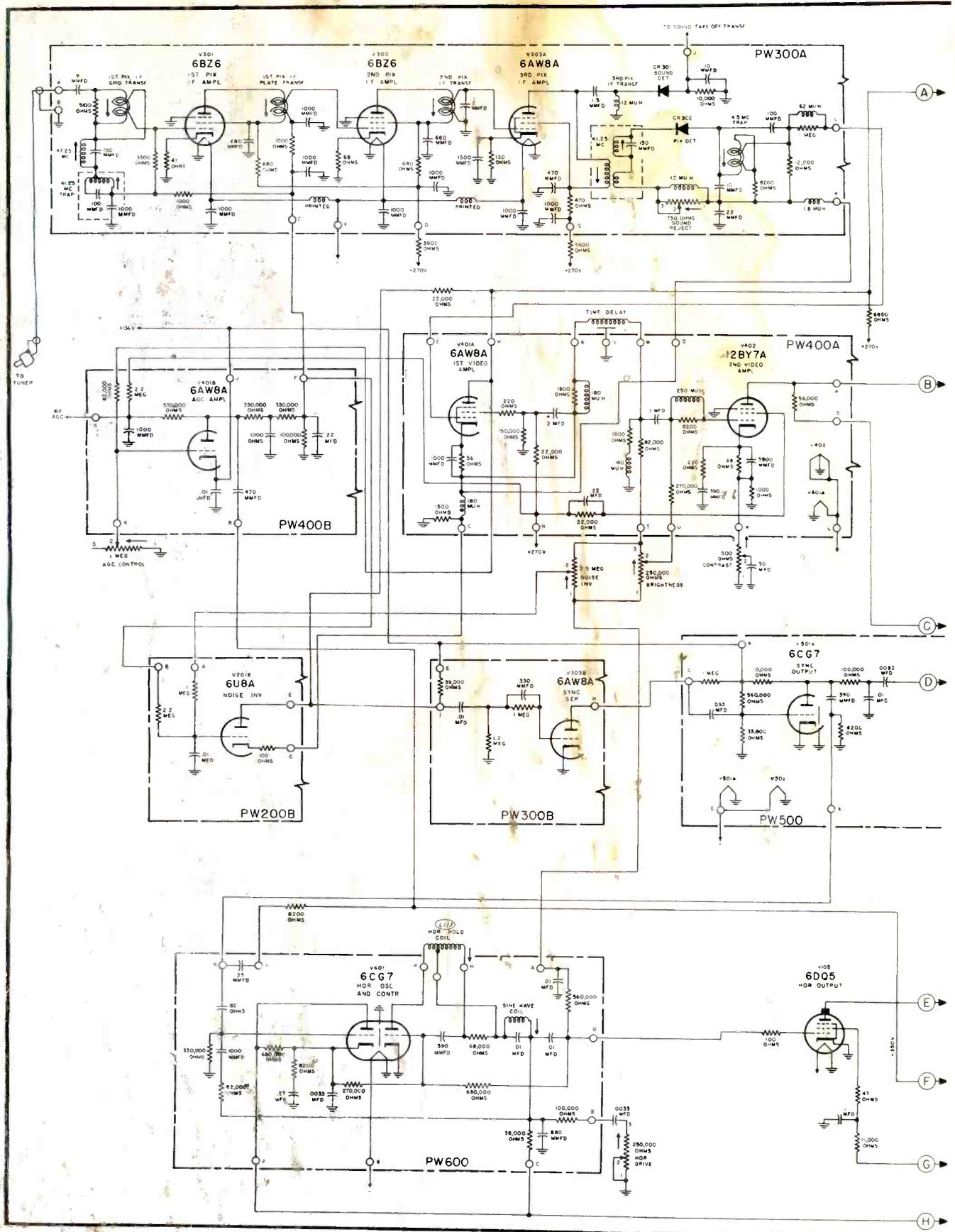



FIG. 4A

Circuit Diagram of 21-Inch Color-TV Chassis Which Features All-Glass Picture Tube. See Systems Used

Glass Envelope 21-Inch Picture Tube For COLOR-TV

by L. B. HEADRICK, Electron Tube Division, RCA

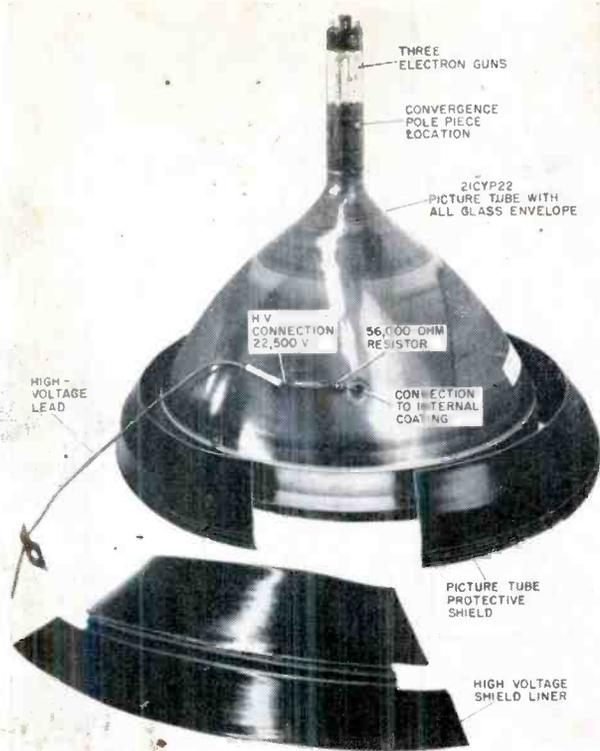New Three-Gun Tube Provides Increased Brightness and Contrast . . . Requires Less HV Insulation and Electric Shock Protection in Chassis



AN ALL-GLASS ENVELOPE¹ picture tube has been designed for use in color-TV receivers. It is a round, directly-viewed type having a graded-hole shadow-mask and an improved three-gun assembly. Because it has an all-glass envelope, the need for high-voltage insulation and electric-shock protection in the color receiver has been reduced. It is provided with an external conductive envelope coating, which with a portion of the internal conductive coating, forms a high-voltage filter capacitor.

The graded-hole shadow mask utilized in the new tube permits in-

creased light output from the screen. In addition, the light-filtering action of the face glass of the tube has been increased so that the picture has both improved contrast in a well-lighted room and higher brightness resulting in more vivid colors.


An average correction for the vertical component of the earth's magnetic field has been built into the tube so that a minimum of additional magnetic correction is required in the color receiver. Correcting magnets to provide both or either radial and

tangential beam motion in localized areas are shown in Fig. 1. Most of the tubes will not require any or only one or two of these magnets for good color purity; a few tubes may require up to six magnets. The magnetic shield placed around the faceplate end of the tube, as shown in Fig. 1, minimizes the effects of extraneous magnetic fields and contributes to the simplicity of magnetic correction adjustments required during the installation of a color-TV receiver in the home.

Additional Magnetic Shielding


Additional magnetic shielding, shown in Fig. 2, has been built into the electron gun to reduce the amount of dynamic convergence correction required by the deflecting yoke and picture-tube combination, as well as to reduce the interaction between the

(Continued on page 48)

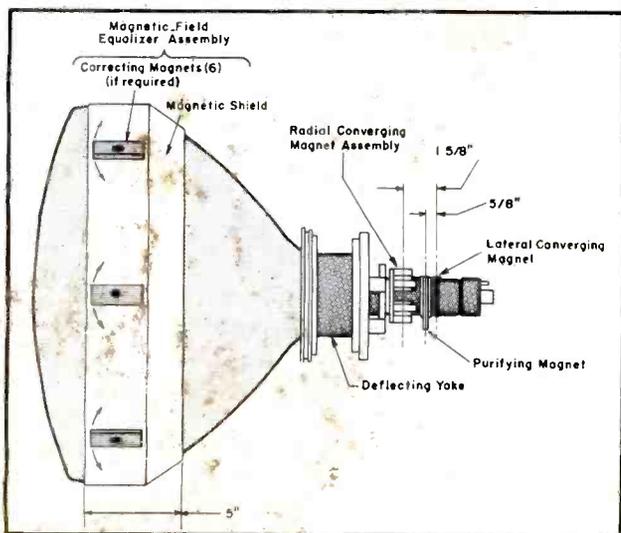

(Left)
FIG. 1: A CROSS-SECTIONAL view of glass-envelope color-TV picture-tube, illustrating correcting magnets in magnetic-field equalizer assembly, and the radial-converging magnets.

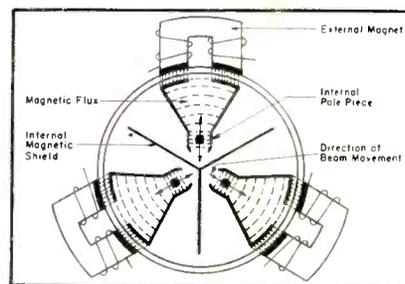(Right)
FIG. 2: ADDITIONAL MAGNETIC shielding built into the electron gun to reduce the amount of dynamic convergence correction required by the deflecting yoke and picture-tube combination.




FINCO® announces

MODELS UNLIMITED!

NOW . . . you can sell a TV Antenna designed for your area

| | | | |
|-------------------------|---------------------------|-----------------------------|--------------------------|
| | BUFFALO SPECIAL | SYRACUSE-ROCHESTER SPECIAL | DUO-DIRECTIONAL SPECIALS |
| | SAN DIEGO B-6 | CHICAGO SPECIALS | PITTSBURGH SPECIAL |
| LONGVIEW, TEXAS SPECIAL | VICKSBURG SPECIAL | FLORIDA, WEST COAST SPECIAL | GEOMATIC SPECIALS |
| | PATENTED FIDELITY PHASING | DETROIT-TOLEDO SPECIAL | MODEL B-8 |
| UHF-VHF SPECIALS | MODEL B-66 | | |
| MODEL B-7 | FRONT-TO-BACK SPECIALS | | |

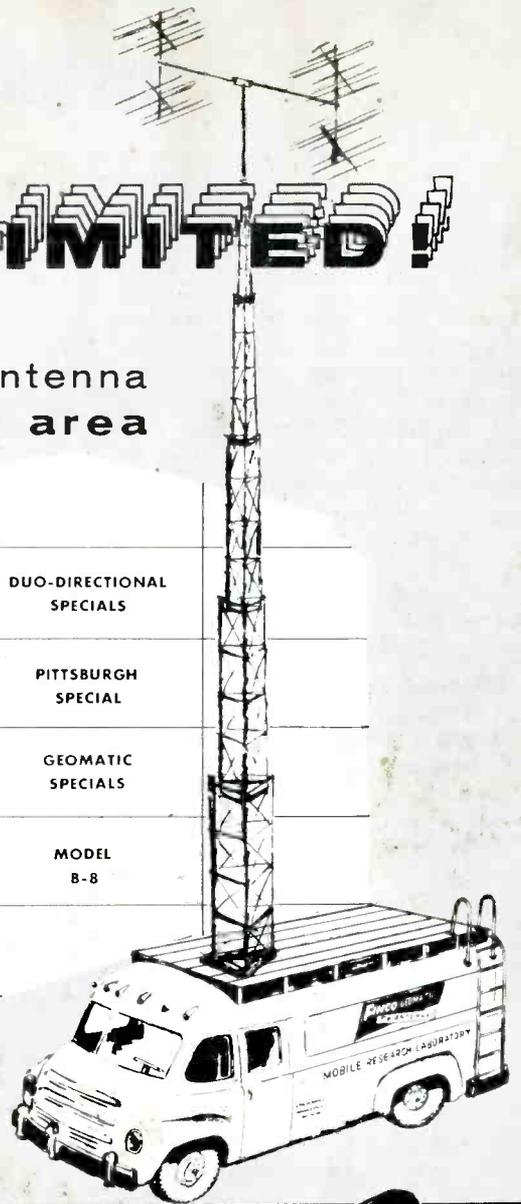

• IN SOLVING UNUSUAL, LOCALIZED RECEPTION PROBLEMS, FINCO has proved that the only positive way to develop the most efficient and economical TV Antenna is by actual MOBILE RESEARCH LABORATORY TESTS combined with Expert Topology and Channel Power Plotting.

If a distributor qualifies, Finco's research department assumes the task of studying the specific, local reception problems. If the problems can possibly be solved the result is an exclusive Red-Hot, High-Profit Hi-Performance Antenna For Your Area —

Hundreds of FINCO research projects are now in process or already completed, giving dealers and servicemen a big jump on their competition. The total cost to your Jobber IS HIS COOPERATION . . . urge Your Jobber to write, wire or call FINCO TODAY!

FINCO®

is often imitated . . . the leader always is!



FINCO®

THE FINNEY COMPANY • 34 West Interstate Street • BEDFORD, OHIO • Telephone: BEdford 2-6161

Copyright 1957, The Finney Co.

Form No. 20-199

Installation Checks For Latest

How To Test and Adjust New Receivers

SERVICE MEN who have had experience in installing the 600 and 700 series color receivers will find that the chassis in the new line are equally easy to install. In most cases it is necessary only to degauss the receiver. In a few cases it may be necessary to touch up the center-convergence or purity adjustments, as outlined in this report.

Installation and servicing of the new series receivers requires the same test equipment as earlier models:

A *degaussing coil* for purity correction.

A *dot-bar-crosshatch generator* for adjusting convergence.

A *color-bar generator* for checking demodulator phasing, for checking the relative gains of the R-Y, B-Y, and G-Y channels, and for other adjustments and troubleshooting applications.

A *wideband scope*, flat to 4 mc, for signal tracing and troubleshooting in the color circuits.

A *vvm* and a *high-voltage probe* for checking the adjustment and operation of the high-voltage regulator circuit.

Preliminary Steps

In preparing the receiver for checking, the chassis must be placed in the position and direction which it will finally occupy. The receiver *must* then be demagnetized with a degaussing coil to aid in obtaining good purity.

The following checks should be made on each installation job. These checks are in addition to the conventional checks for height, width, linearity, drive, centering, focusing, etc.

Any necessary adjustments should be made in accordance with the adjustment procedure in the manufacturer's service data for the particular receiver.

Purity Checks

One should first obtain a clean raster by removing the *if-link* plug

from the *rf* tuner, or by removing a tube from the *if* amplifier. The raster should be examined for impure (tinted or colored) areas. Impurities usually show up most prominently in the red field. The red field may be viewed by biasing off the blue and green guns with a switching device¹ diagrammed in Fig. 1.

If there are impure areas in the central portion of the red field, it will be necessary to adjust the purifying magnet, which is mounted on the neck of the picture tube. If there are impure areas at the edges, one must adjust the corresponding edge-purity magnets to eliminate the impure areas.

Edge-Purity Magnets

The edge-purity magnets in the new receivers are mounted around the picture tube, several inches in front of the deflecting yoke. Each magnet assembly consists of two magnetized *hairpins* which may be turned with respect to each other to alter the strength of the magnetic field, and both hairpins may be turned together to alter the direction of the field.

A *Z-axis* coil is used in the new chassis to aid in counteracting the *Z-axis* effect of the earth's magnetic field. This coil is energized momentarily by pressing a push button which connects a 50-mfd capacitor (charged to 270 v) to the coil. A center-tapped potentiometer, identified as the *Z-purity* adjustment, is

used to establish the direction and intensity of current through the coil.

Convergence Checks

In the first step in the convergence adjustment, one should tune in a black-and-white program. The picture should be inspected to see if there are any noticeable color fringes around the edges of objects and lettering.

If there are color fringes at the center of the picture, the center convergence should be adjusted. Four permanent-magnet adjustments are provided for this purpose. Three of these adjustments (one for the red gun, one for the blue gun, and one for the green gun) are in the converging-coil assembly which is mounted on the neck of the picture tube. The fourth magnet, identified as the *lateral* magnet, is also mounted on the neck of the picture tube.

Adjustment of center convergence is all that is required in the majority of installations to obtain good convergence over the entire picture, but if there is an objectionable amount of misconvergence in other areas of the picture after center convergence has been adjusted, it is necessary to adjust vertical or horizontal dynamic convergence.

For all convergence adjustments a suitable dot-bar-crosshatch pattern generator² should be used.

To check gray-scale tracking, it is also necessary to tune in a black-and-white program and examine the highlights and lowlights in the picture. The highlights should be untinted white; the lowlights should be untinted gray. If the highlights or lowlights are tinted, gray-scale tracking (red, blue, and green screen and background adjustments) should be adjusted in accordance with the procedure specified in the service data.

Color Operating Control Checks

Color receivers have only two new customer operating controls. These

¹RCA 226X1.
²Such as the RCA WR-46A.

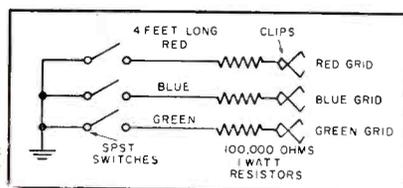


FIG. 1: SWITCHING CIRCUIT designed to permit biasing off of one or two guns in the color tube, when adjusting purity or convergence.

COLOR-TV Chassis

by J. R. MEAGHER, Electron Tube Division, RCA

controls are labeled *tint* and *color* in the new series; the tint control is equivalent to the hue control in earlier models.

Fine Tuning Control: The fine-tuning control should be turned in the direction which will put sound slightly into the picture, thus producing a .9-mc beat in the picture, and then the control should be turned in the opposite direction until the beat just disappears. If the control is turned too far in this direction, the colors will become weaker, and continued rotation in the same direction will cause complete loss of color.


Color Control: The color control should be adjusted to obtain a natural and pleasing intensity of color, neither too pale nor too vivid. It should be possible to overload and distort the colors by turning the color control fully clockwise.

Tint Control: The tint control should be adjusted to obtain natural flesh tones on faces of persons in the picture. If the tint control is turned slightly in one direction from its correct position, the flesh tones become bluish. If the tint control is turned slightly in the opposite direction, the flesh tones become greenish. Correct flesh tones should be obtained with the tint control set at approximately mid-position.

Killer-Threshold Adjustment Checks

In making these adjustments the receiver should be switched to an unoccupied channel. The contrast control and the color control should be turned fully clockwise. The killer-threshold adjustment should be turned to produce colored snow in the raster, and then this adjustment should be turned in the opposite

⁵Such as the RCA WR-61B.

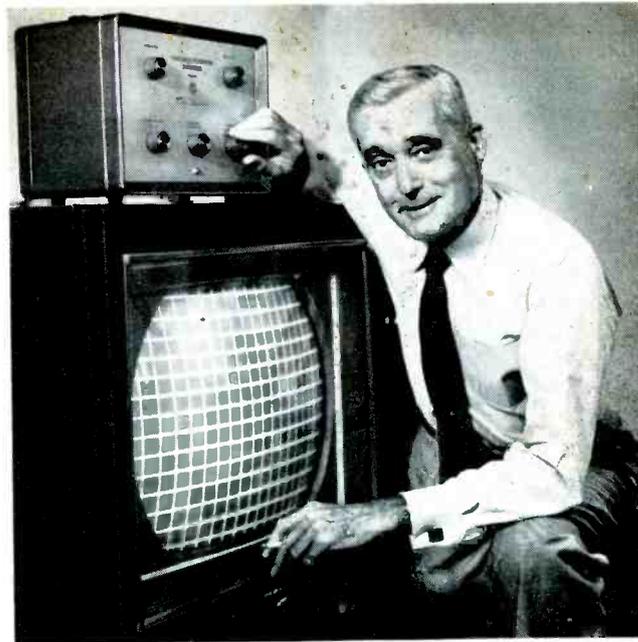

direction until the colored snow just disappears.

To check reception on each color channel, if color is missing or weak on one channel, but is satisfactory on other color channels, one should try orienting the antenna, or try a new antenna. Also any traps, stubs, branch lines, or inductive-type multiple-set couplers, which may be connected to the transmission line, should be disconnected.

If the existing antenna is falling apart from age, or if the transmission line is rotted, a new antenna and a new line should be installed, using a type of antenna recommended for color reception on the desired channels. An antenna rotor should be used in those areas where the stations are in different directions, and in areas of multi-path reception where reflections or ghosts are present.

If the receiver is operated from an indoor antenna of a type which has a tuning or switch control, or an adjustable stub, the adjustment usually has a marked effect on color reception.

HV Regulation Checks

To test the *hv* regulation, a black-and-white or color program should be tuned in, and the brightness and contrast controls turned over the

⁶The reader is referred to the recently published RCA Color Television Pict-O-Guide for illustrated information on adjustment and troubleshooting procedures.

ranges in which they are normally operated; the picture should not *bloom* or go out of focus. The high-voltage regulator circuit should maintain the uitor anode voltage substantially constant (at approximately 22,500 volts in the 800 series receivers) when the picture changes from all-dark to all-light scenes, or vice versa.

Phasing and Relative Gain Checks

In the unlikely event that the tints or hues in color pictures are not normal, it will be necessary to use a suitable color-bar generator⁷ to check the phasing of the demodulators and to check the approximate relative gains of the R-Y, B-Y, and G-Y channels. These checks can be made in the home, without using a scope, by means of the generator, as follows:

To check phase, the generator should be connected to the receiver, adjusting both the generator and the receiver to obtain a color-bar pattern on the picture tube.


Using the switching circuit shown in Fig. 1, the blue and green guns should be biased off, leaving only the red gun operating. The tint control should be adjusted so the center of bar number 6 has the same brightness as the adjacent spaces between the bars. The tint control should be left in this position.

Now the red and green guns should be biased off, leaving only the blue

⁷Continued on page 49)

SERVICE NOTES

FIELD AND SHOP

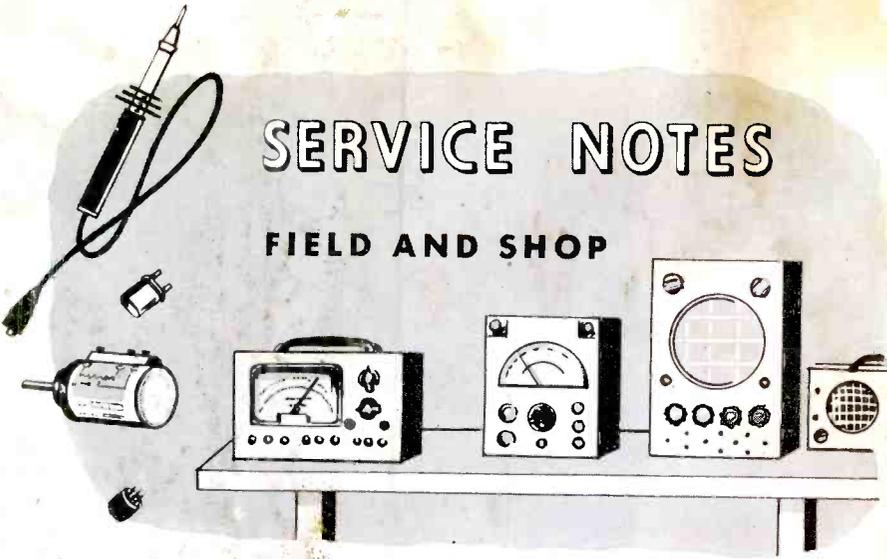

RF Chassis-Power Supply Modifications to Reduce Motor Noise . . .
 Cures for Improper Damping . . . Multirange Ohmmeter Accuracy
 Checks . . . Remedies for Weak-Strong Station Distortion in
 Transistor Radios . . . TV Tuner Repair

PRODUCTION CHANGES to reduce phono motor noise in Motorola chassis have been made in the *rf* chassis and power unit. The *rf* chassis and power units made prior to these changes are not interchangeable with those made after the alteration. The new chassis and corresponding power units have been color coded with a red dot and numbered as follows:

Model 918—serial number greater than 4600; models 919 and 919 HR—serial number greater than 11050.

An *rf* chassis which has a red dot on its power-cable connecting plug requires the use of a power unit that has a red dot adjacent to its power-cable receptacle, and vice versa. (If in doubt about the identification of a power unit, check the power-cable receptacle; if the power-cable receptacle has a grounding clip, then it is to be used with a red dot chassis, and conversely). When servicing these receivers, one must be sure that two

matching units are used (either color coded or non-color coded). If a non-color coded type is mistakenly used with a color-coded type, continuous fuse blowing will result.

In the modified receivers, the driver transformer (T_a) has been changed to a new type which has a tapped primary winding. The bottom section of this transformer is connected to the acceleration grid of the driver stage and injects an out-of-phase motor noise pulse into the primary of the driver transformer, thus eliminating the motor noise existing in the B+ line. Choke L_7 has been eliminated, and choke L_8 has been changed to a transformer-type and relocated into the power unit chassis; resistor R_{23} and capacitor C_{21} have been eliminated from the power unit chassis. A grounding clip has been added to the power receptacle on the power-unit chassis; the plug used on the power cable has been changed to a

water type and an insulated shell has been added to the plug. The plug was changed to accommodate the shell, which acts as an electrical shield.

In addition, new components have been added to the chassis as indicated in Fig. 1.

Improper Damping

THE FUNCTION of the damper tube is to eliminate the shock-excited oscillation that occurs in the horizontal output system during horizontal retrace. Since this function is performed immediately after each horizontal retrace, the linearity of the left side of the raster depends upon the damper operation.

In Westinghouse TV chassis, the horizontal linearity control (L_{401}) with capacitors C_{401} and C_{402} constitute a phasing network. When L_{401} is correctly adjusted, the phase of the *ac* component of the voltage from across C_{401} is such that the *ac* component, when applied to the plate of the output tube, compensates for any non-linearity in the output circuit. When C_{401} is open, this compensating voltage is removed, distortion results, causing non-linearity of the horizontal trace.


Resistor-Installation Notes

WHEN INSTALLING resistors on the terminal strip, one should allow sufficient length to the leads; this will prevent solder crystallization due to prolonged overheating. Spaghetti used on these leads should be of fiberglass or other heat-resisting material. One should never use the common soft plastic spaghetti, as it will not stand up under overheating.

Multirange-Ohmmeter Accuracy Checks

THE BEST WAY to estimate the accuracy of a multirange ohmmeter is to look at the pointer on the *dc* volt scale and see what 3% of the full scale reading corresponds to on the ohms scale. Broadly speaking, one can expect that the ohms reading to be accurate within $\pm 1\frac{1}{2}$ small divisions on the *dc*-voltage scale. This can readily be transferred from one scale to the other by eye, so as to estimate the accuracy.

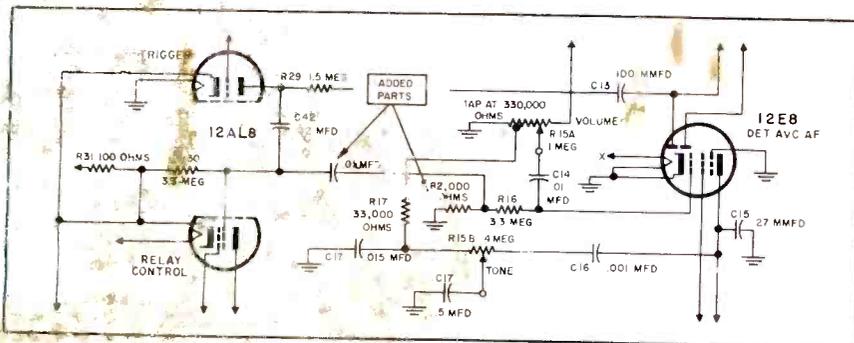For instance, if, on the direct scale the reading is 20 ohms, which is opposite to 150 on the *dc* volts scale, the accuracy will be between approximately 18 and 22 ohms, which is $\pm 10\%$. Moving further up the



(Left)
FIG. 1: REVISED CIRCUITRY of Motorola 918 and 919 HR chassis with added components to reduce phono motor noise.

scale to, say 60 ohms, the accuracy will be from approximately 53 to 68 ohms, which is even wider deviation. At the lower end of the scale, say a reading of 5 ohms, the accuracy will be within 4.3 to 5.7 ohms. This again is more than 10% deviation, and the maximum accuracy of the ohmmeter is seen to be at the midscale point, which is true of all ohmmeters.

A reading within $\pm 10\%$ at the best position on the scale does not sound very accurate, and it is for this reason that the accuracy of the ohms scale is often omitted. Information normally provided covers microammeter accuracy which, it is said, is within $\pm 2\%$ and shunt and multiplier accuracy, said to be within $\pm 1\%$. You are thus left to deduce the fact that the accuracy of all the ranges is somewhere within $\pm 1\%$ and $\pm 3\%$. However, a more critical examination will show that these accuracies combine to limit the ohms range to a value of $\pm 10\%$. This is true of all ohmmeter ranges, and the reading obtained should never be trusted to a greater accuracy than this. If resistors are to be checked to a finer percentage, such as 5% tolerance, the only solution is to use a proper resistance bridge for the measurement.

Tuner Repair

A RECENT ANALYSIS of in-warranty returns of Magnavox 700584-6 tuners has revealed that a number are returned as being *shorted*. Examination of these shorted tuners has disclosed that in a great many cases the short has been caused by one of the *rf* plate coils touching the low potential end of R_{50} , a 10,000-ohm resistor feeding +140 volts to the mixer stage. When this happens, the 2200-ohm (R_{501}) resistor (outside the tuner) burns. The repair necessary is to clear the short by bending the coil away and replacing R_{501} .

Hum and Buzz Remedies

A FEW EARLY Magnavox 21-01BB, 21-02, etc., chassis were produced with the high side of R_{307} connected to +270 v. This, under certain con-

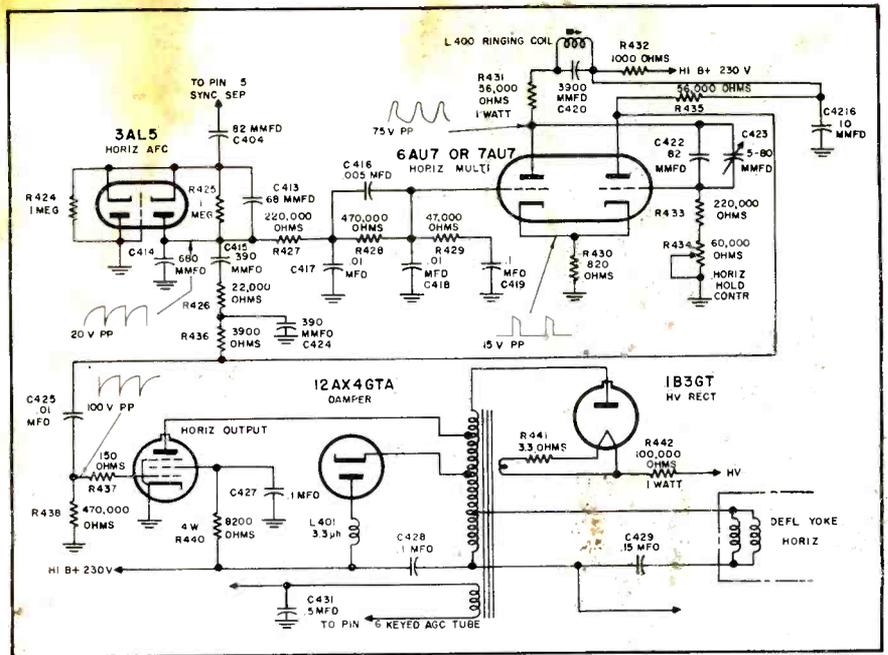


FIG. 2: WESTINGHOUSE horizontal sweep circuit.

ditions, can result in sync buzz being fed back from sync splitter to the *af* amplifier. If this condition is encountered the high side of R_{307} should be disconnected from +270 and reconnected to the junction of R_{215} and R_{210} .

A few cases of 120-cycle hum also have been reported. This has been found to be due to a change in value of R_{502} ; 680 ohms. If this resistor checks off value, it should be replaced.

Deflection-Yoke Failure

Yokes used in all current Magnavox chassis except the 19 series have been found to fail because of puncture of the insulation between leads and solder terminals.

These yokes can be repaired by splicing new leads in place of the burned sections and installing a 1" piece of insulated sleeving as shown in Fig. 4.

Cures for Weak or Strong-Station Distortion in Transistor Radios†

WHEN DISTORTION is present and varies with the strength of the sta-

tion signals, an abnormal condition obtains in the circuit of those transistors whose bias is *agc* controlled.

Distortion only on weak stations is most often due to unsatisfactory operation of the detector. The diode should have a slight initial forward bias. A check should be made for presence of this bias voltage, and one should also check to see that polarity does not reverse with signal and that *agc* voltage with signal is of proper polarity; base to emitter voltage should decrease with increase of signal.

Distortion on strong stations indicates that the transistors are being driven to cutoff by a strong *agc* voltage. On some pocket-size models an overload diode is used to reduce the gain of an *if* circuit only on strong signals. One should therefore check terminal voltages and the overload diode, if such is used.

Transistor radios will not handle large variations of signal as well as vacuum-tube radios, and it may be that on excessively strong signals the best solution is to turn the radio so

(Continued on page 55)


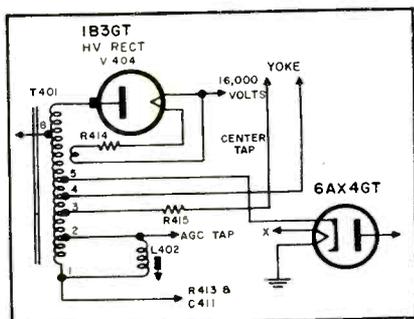


FIG. 3: MODIFIED HIGH-VOLTAGE TRANSFORMER connections in Magnavox chassis. The *agc* keying pulse is now obtained from the top of the horizontal width coil.

FIG. 4: REPAIRS required in Magnavox yoke to prevent lead-insulation puncture.

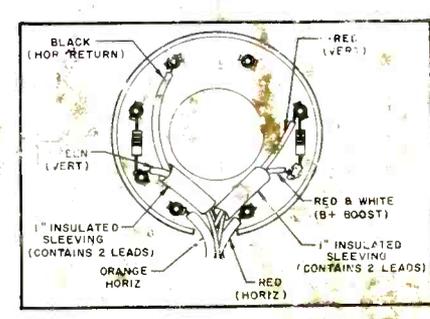

BEST BUILT



YET

That's our claim—backed up by a solid majority of independent set makers who use them. Built to one standard of quality—Blue Chip Quality—Magic Mirror Aluminized Picture Tubes mirror twice the light to create a picture twice as bright. Tell your supplier you'd rather have Tung-Sol!

Blue Chip Quality

TUNG-SOL®

Magic Mirror Aluminized

PICTURE TUBES

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Ga., Columbus, Ohio, Culver City, Calif., Dallas, Tex., Denver, Colo., Detroit, Mich., Irvington, N. J., Melrose Park, Ill., Newark, N. J., Seattle, Wash.

CATALOGS—BOOKS

SYLVANIA ELECTRIC PRODUCTS, INC., 1740 Broadway, N. Y. 19, N. Y., has released two booklets: *Industrial Tubes* and *Guide to Replacement*. The *Industrial Tubes* booklet describes the general characteristics of vacuum and beam power tubes, rectifiers, thyratrons, magnetrons, mercury vapor rectifiers and ignitrons. It also lists the maximum ratings of these types. In addition, there are sections devoted to reliable and ruggedized tubes. The *Guide to Replacement* booklet lists the basic designation, tube class and various manufacturers' type numbers for over one-hundred tubes in Sylvania's industrial line.

GENERAL ELECTRIC Co., Schenectady 5, N. Y., has published a 12-page booklet describing the why, where and how of industrial capacitor applications. Publication details units and equipments available; discusses problems and solutions in selection of industrial capacitors, and includes diagrams and pictures.

CENTRALAB, a division of Globe-Union, Inc., 900 E. Keefe Ave., Milwaukee 1, Wis., has issued a 121-page pocket control guide (No. 6) with listings on the latest replacement controls. Feature of guide are data on carbon and wire-wound controls listed by ratings and part numbers, together with taper curves. Guides are priced at 20 cents each.

ELECTRONIC INSTRUMENT Co., INC., 33-00 Northern Blvd., Long Island City 1, N. Y., has released a 6-page catalog (form A5) describing the EICO line of high fidelity equipment in both kit and factory-wired form. Contains specifications on master control preamp, 60-watt ultra-linear power amp, 50-watt ultra-linear power amp, 50-watt ultra-linear integrated amp, 20-watt ultra-linear Williamson-type integrated amp, 12-watt Williamson-type integrated amplifier and a two-way speaker system.

THE NATIONAL APPLIANCE Trade-In Guide Co., 2105 Sherman Ave., Madison, Wis., has released the 1958 issue of the *TV Blue Book* which features articles on servicing, advertising and merchandising.

HOWARD W. SAMS AND Co., INC., 2201 E. 46th St., Indianapolis, Ind., has issued volume nine in the Sams' *audio amplifier series*. Presents photo coverage, schematics, parts lists, voltage and resistance measurements and servicing information. Contains data on fifteen amplifiers, three preamplifiers, twelve tuners, and five custom radios produced during 1956. Contains 240 pages; priced at \$3.95.

GENERAL TRANSISTOR CORP., 91-27 138th Place, Jamaica 35, N. Y., has published bulletin G-120, which describes a line of *pnp* and *npn* transistors for radio, *rf*, and *if* applications.

TUNG-SOL ELECTRIC, INC., 95 Eighth Ave., Newark 4, N. J., and Minnesota Television Service Engineers, Inc., have published a 20-page *Radio-TV Apprenticeship Standards Guide*. Copies are free to all Service Men and associations. They may be obtained through local Tung-Sol jobbers or by writing to TTLB, Special Services Department, P. O. Box 1321, Indianapolis, Ind.

ALLIED RADIO CORP., 100 N. Western Ave., Chicago 8, Ill., has announced the release of a 404-page catalog listing over 27,000 items.

CLEVELAND INSTITUTE OF RADIO ELECTRONICS, 4900 Euclid Ave., Cleveland 3, O., has published a 24-page brochure and course outline describing electronic industry employment requirements and opportunities.

CBS-HYTRON, Danvers, Mass., has issued a 650-page handbook with data on over 1000 tubes along with 300 curves for current receiving and television picture tubes, regardless of make. Abbreviated data are included for seldom-used tubes of these types, as well as a variety of special-purpose tubes. Data and curves for CBS semiconductors are also given.

ASSOCIATIONS

TSA, Detroit, Mich.

THE SECOND ANNUAL MIDWEST Electronic Forum sponsored by Television Service Association, 8225 Woodward Ave., Detroit 2, Mich. will be held in February, 1958.

The forum will cover technical lectures on b-w and color television, radio, hi-fi, tape recorders and industrial electronics.

RTG, Long Island, N. Y.

THE FIRST FALL TECHNICAL meeting of the Radio and Television Guild was held recently.

Pete Langer of Sylvania was the featured speaker. He covered the *technical aspects of servicing Sylvania's 1958 TV receivers.*

At an earlier executive meeting, a group-insurance program was discussed. Tentative plans call for a study of accident, health, income protection and life forms of coverage for possible use by the guild and its membership.

ESFETA, New York

THE EMPIRE STATE FEDERATION of Electronic Technicians Associations, Inc., held a meeting recently in Ithaca, New York, with *Ben DeYoung*, representing Ithaca, acting as host member.

Among those at the session was NATESA eastern vice president *Bert Lewis*, representing Rochester.

George Carlson, ESFETA secretary, reported that Jamestown's self-certification program has been very effective where individual members advertised association membership, and general promotion of the plan obtained.

The next meeting of ESFETA has been scheduled for Nov. 10 in Rochester, N. Y. *Robert LeMay*, president of the Rochester group will be host.

TEN YEARS AGO IN SERVICE

THE RADIO TECHNICIANS GUILD of Rochester, N. Y., announced a two-day meeting featuring talks on FM, TV, tubes and business management. . . . The first organization meeting of the State of New York Federation of Radio Technicians has held. . . . A twice-a-month newspaper advertising campaign listing association members was set up by the Radio and Electronic Technicians Association of Indiana, Inc. . . . Officers of RETA were *John Lackman*, president; *John Davies*, vice president; and *Charles Palmer*, publicity director. *Robert Tate*, *Harold Gibson*, *Carlton Kindig*, *Charles Palmer* and *Claude High* were on the board of directors. . . . The Long Beach, Calif., Radio Technicians Association conducted a drive for old TV sets for use in apprentice training at schools and boys clubs. *Wes Farrell* was president of the association; *John J. Sawyer*, vice president; *Verne Preston*, secretary; and *Clare Reese*, treasurer. Directors included *P. N. Nibbelin*, *M. E. Mattox*, *H. M. McNeil* and *R. J. Hayden*. . . . The Radio Technicians Association of Huntington, W. Va., announced membership requirements: Two years' experience in active servicing and a written examination of ten questions where the passing grade was 80%. . . . First circuit report on *if* systems used in prewar and postwar TV receivers was published in SERVICE. . . . Over 100,000 TV receivers (mostly 10-inch type) were reported to be in operation. . . . *Les A. Thayer* of Belden Manufacturing Co. was elected chairman of the Association of Electronic Parts and Equipment Manufacturers in Chicago.

BEST FOR



EVERY SET

All Tung-Sol radio, TV or Hi Fi tubes are engineered to one standard of quality—Blue Chip Quality. Whether they're for famous set makers or leading service dealers, Tung-Sol Tubes are identical in design and performance. Tell your supplier you'd rather have Tung-Sol!

Blue Chip Quality

 **TUNG-SOL**[®]
RECEIVING TUBES

TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

THIS MONTH IN SERVICE

BOOM IN CLOSED-CIRCUIT TV OPERATION--The increasing use of closed-circuit TV, and its widening scope of application, is writing a new chapter on the television scene. . . . Today CC-TV, which basically concerns TV signals confined to cable circuits for reception by interconnected receivers, is serving many business, industrial, educational, entertainment, religious, professional, and municipal activities. Current interest in CC-TV ranges from apartment houses and banks, to theatres and toll-TV cable systems. . . . CC-TV is providing many schools and colleges with an economic means of giving graphic instruction to different classes, often in different buildings, at the same time. In several places, it is bringing educational programs from the schools to local community centers. . . . CC-TV business uses include facing and talking to representatives throughout the country without any of them leaving their home cities, linking stockholders' meetings in different cities, verifying signatures of bank customers, watching for poachers on parking lots, and even baby sitting. . . . Industrial CC-TV use covers inspecting manual and mechanical operations, watching heat and pressure gauges, detecting unnecessary chimney smoke, locating trouble in equipment, monitoring entrance gates and yard traffic. . . . In transportation, CC-TV applications are broad, too; railroads are using closed circuits to check car numbers and inspect freight-car running gear in switchyards, to speed issuance of reservations and tickets at passenger stations, and to police grade crossings. Airports employ CC-TV to check aircraft, watch planes take off and land and to provide waiting passengers with information about plane arrivals and departures. . . . A number of hotels and apartment houses now offer guests free non-broadcast video entertainment and other programs via closed circuit.

WHERE CC-TV OPERATION is confined to a single building, interior cables can be installed to connect up several rooms. Or it can be strung outside to link a group of buildings. In more extended operations, because of the cost factor, the cable is not usually buried in the ground, as are most of the common carrier coax lines. In such cases, the private cable is, under a mutual rental or other arrangement, normally suspended on the same poles which carry local power and telephone lines, or on poles erected for the purpose.


ASSOCIATIONS COOPERATING IN UHF FIELD TESTS--Affiliated groups in NATESA are cooperating with TASO (Television Allocations Study Organization) in a series of home-observation field tests, which began a short while ago in the south and midwest. . . . In the south, a team of association members have been helping crews check reception from two Baton Rouge TV stations--WABF-TV, operating on channel 28, and WBRZ (TV) operating on channel 2. . . . In these studies measurements of field strength outside the home are taken at the same time that observations in the home are being made by Service Men and the viewer, in an attempt to find a correlation between the strength of TV signals as actually measured and the degree of satisfactory service received on typical home receivers. . . . The tests in the midwest were conducted in Madison, Wisconsin.

PICTURE-TUBE LIFE STUDY UNDER WAY BY STANDARD-BRAND MANUFACTURER--An investigation of the life and performance efficiency of standard-brand picture tubes as compared to other types is now being conducted by a leading tube maker. . . . Preliminary tests have indicated that the extreme precautions taken by standard-brand plant research, production and test result in not only a substantial increase in tube life, adding thousands of hours in many cases, but performance values, too.

TUBES-TESTED-BY-EXPERTS PROMOTION SET--A promotion campaign, aimed at helping independent Service Men inform the public about the importance of having tubes tested by experts has been introduced. . . . This campaign will stress that only a trained Service Man using reliable electronic test equipment can make an accurate analysis of the conditions of receiving tubes. . . . The promotion points out that unskilled attempts of radio and TV set owners to fix it themselves can result in damage to the receivers.

YOU'LL be on your way to a "POT OF GOLD"

by walking Kraeuter's New Rainbow Line

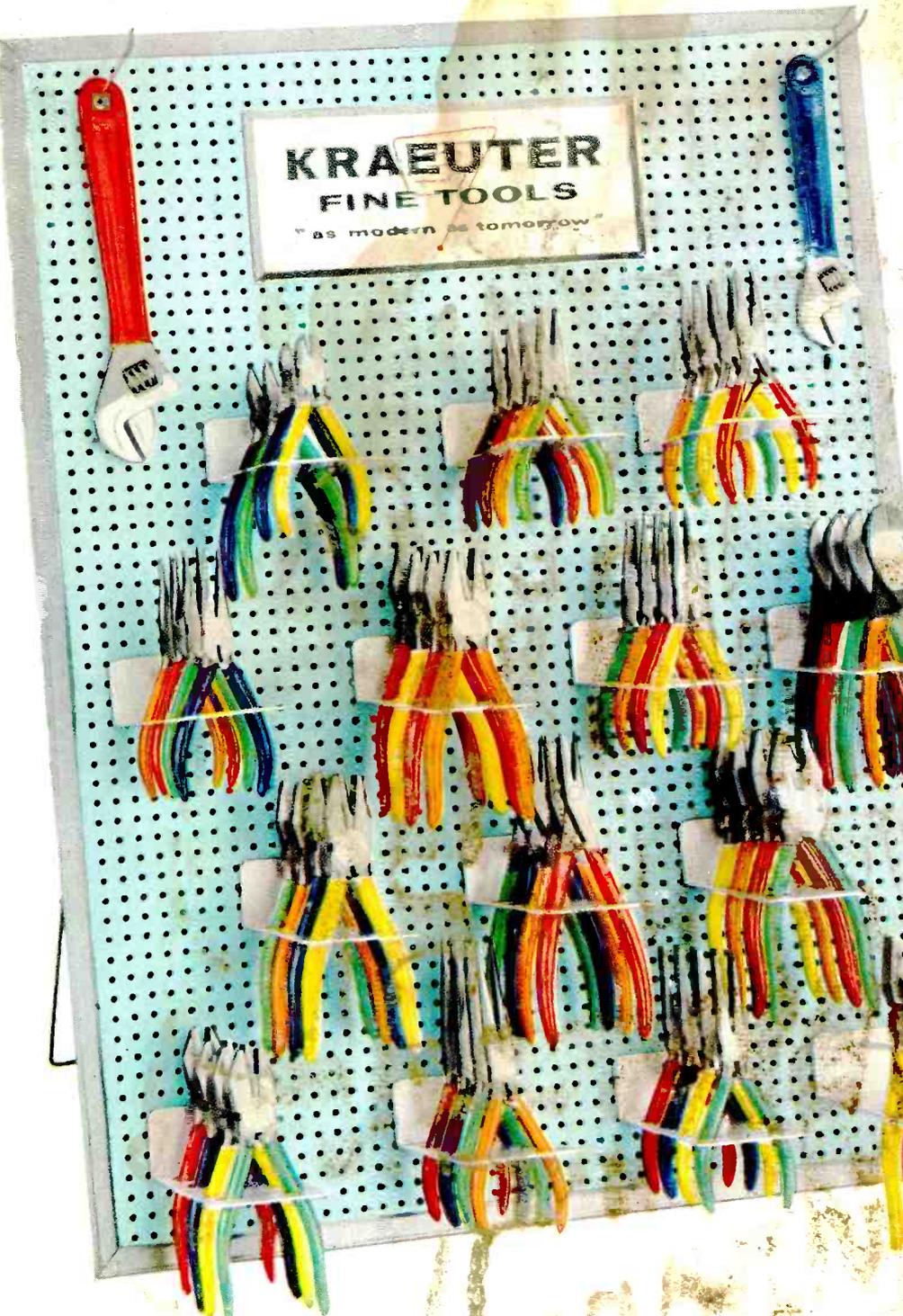

The Rainbow Line route is loaded with treasures

Look at them!

1. Selection of 3 each of 4 or 6 each of any 7 fast moving tools all with colorful cushion grips—all at regular prices.
2. Colorful Free Display Board.
3. Complete set of multiple hanger peg board brackets free with every Rainbow Line Display purchase—Brackets valued at \$12.00—

Don't miss taking this treasure route of the Rainbow Line

BUY THE FINEST BUY KRAEUTER BUY AMERICAN

AS MODERN AS TOMORROW

kraeuter & co., inc

FOR 100 YEARS THE FINEST IN HAND TOOLS 1860-1960 NEWARK, N. J.



Take Your Pick

of Krauter Rainbow Displays

There's a
"Pot of Gold"
 with every one



BUY THE FINEST
 BUY KRAUTER
 BUY AMERICAN



AS MODERN AS TOMORROW

Krauter & co., inc

FOR 100 YEARS THE FINEST IN HAND TOOLS 1500-1960 NEWARK, N. J.

RADIO & ELECTRONICS

| | | List each | Total List |
|---|---------|-----------|------------|
| 3 ea. of Short Jaw Nose Cutting Pliers 71 | 8 R* | 3.95 | 11.85 |
| " " " Long Needle or Snipe Nose Pliers 1621 | 6 Y | 2.85 | 8.55 |
| " " " Curved Needle or Snipe Nose Pliers 1631 | 5 1/2 G | 3.25 | 9.75 |
| " " " Short Chain Needle Nose Pliers 1641 | 5 R | 2.85 | 8.55 |
| " " " Long Chain Needle Nose Pliers 1661 | 6 B | 3.15 | 9.45 |
| " " " Radio & Ignition Nose Cutting Pliers 1663 | 6 Y | 3.25 | 9.75 |
| " " " Tongue-N-Groove Joint Pliers 710 | 10 R | 3.60 | 10.80 |
| " " " Extra Long Chain Nose Pliers 1781 | 7 O | 3.75 | 11.25 |
| " " " Electricians' Side Cutting Pliers 1830 | 7 Y | 3.25 | 9.75 |
| " " " Diagonal "Oblique" Cutting Pliers 4501 | 4 1/2 B | 2.50 | 7.50 |
| " " " Diagonal "Oblique" Cutting Pliers 4501 | 5 O | 2.75 | 8.25 |
| " " " Diagonal "Oblique" Cutting Pliers 4501 | 6 R | 3.10 | 9.30 |
| " " " Heavy Duty Diagonal Cutting Pliers 4610 | 7 G | 3.10 | 9.30 |
| " " " Diagonal Cutting Pliers-Needle Point 5601 | 5 R | 3.50 | 10.50 |

List 134.55
 Cost to retailer 89.70
 Profit to retailer 44.85
 Peg Board Display & 14 Brackets FREE

MILL SUPPLY

| | | List each | Total List |
|---|---------|-----------|------------|
| 3 ea. of Short Chain Needle Nose Pliers 1641 | 5 R* | 2.85 | 8.55 |
| " " " Long Chain Needle Nose Pliers 1661 | 6 B | 3.15 | 9.45 |
| " " " Long Chain Needle Nose Pliers 1671 | 6 G | 2.60 | 7.80 |
| " " " Extra Long Chain Nose Pliers 1781 | 7 O | 3.75 | 11.25 |
| " " " Linemen's Side Cutting Pliers 1801 | 8 1/2 Y | 4.50 | 13.50 |
| " " " Electricians' Side Cutting Pliers 1830 | 6 1/2 O | 2.90 | 8.70 |
| " " " Electricians' Side Cutting Pliers 1830 | 8 B | 3.70 | 11.10 |
| " " " End Cutting Nippers 1850 | 7 R | 3.60 | 10.80 |
| " " " Diagonal "Oblique" Cutting Pliers 4501 | 4 1/2 B | 2.50 | 7.50 |
| " " " Diagonal "Oblique" Cutting Pliers 4501 | 5 O | 2.75 | 8.25 |
| " " " Diagonal "Oblique" Cutting Pliers 4501 | 6 R | 3.10 | 9.30 |
| " " " Heavy Duty Diagonal Cutting Pliers 4610 | 7 G | 3.10 | 9.30 |
| " " " Tongue-N-Groove Joint Pliers 710 | 10 R | 3.00 | 9.00 |
| " " " "Griptite" Combination 356 | 6 O | 2.30 | 6.90 |

List 131.40
 Cost to retailer 87.60
 Profit to retailer 43.80
 Peg Board Display & 14 Brackets FREE

HARDWARE

| | | List each | Total List |
|---|---------|-----------|------------|
| 3 ea. of Short Chain Needle Nose Pliers 1641 | 5R* | 2.85 | 8.55 |
| " " " Long Chain Needle Nose Pliers 1661 | 6B | 3.15 | 9.45 |
| " " " "Griptite" Combination Pliers 356 | 6 O | 2.30 | 6.90 |
| " " " Extra Long Chain Nose Pliers 1781 | 7 O | 3.75 | 11.25 |
| " " " Linemen's Side Cutting Pliers 1801 | 8 1/2 Y | 4.50 | 13.50 |
| " " " Electricians' Side Cutting Pliers 1830 | 6 1/2 O | 2.90 | 8.70 |
| " " " End Cutting Nippers 1850 | 7 R | 3.60 | 10.80 |
| " " " Diagonal "Oblique" Cutting Pliers 4501 | 4 1/2 B | 2.50 | 7.50 |
| " " " Diagonal "Oblique" Cutting Pliers 4501 | 5 O | 2.75 | 8.25 |
| " " " Diagonal "Oblique" Cutting Pliers 4501 | 6 R | 3.10 | 9.30 |
| " " " Heavy Duty Diagonal Cutting Pliers 4610 | 7 G | 3.10 | 9.30 |
| " " " Gripping & Cutting Pliers 2018 | 7 1/2 R | 3.50 | 10.50 |
| " " " Button's Pattern Pliers 1841 | 8 O | 2.90 | 8.70 |
| " " " Tongue-N-Groove Joint Pliers 710 | 10 R | 3.00 | 9.00 |

List 131.70
 Cost to retailer 87.80
 Profit to retailer 43.90
 Peg Board Display & 14 Brackets FREE

*Color code:
 R-Red, Y-Yellow, G-Green,
 B-Blue, O-Orange

Alternate Packages are available in 6 each of any 7 tools listed in the Hardware, Mill Supply and Radio-Electronics assortments.

RF Amplifier Stages For VHF TV Tuners

How Pentode-Tuner Amplifiers Operate . . . Circuit And Tube Conditions Which Affect Cascode And Pentode RF-Amplifier Performance

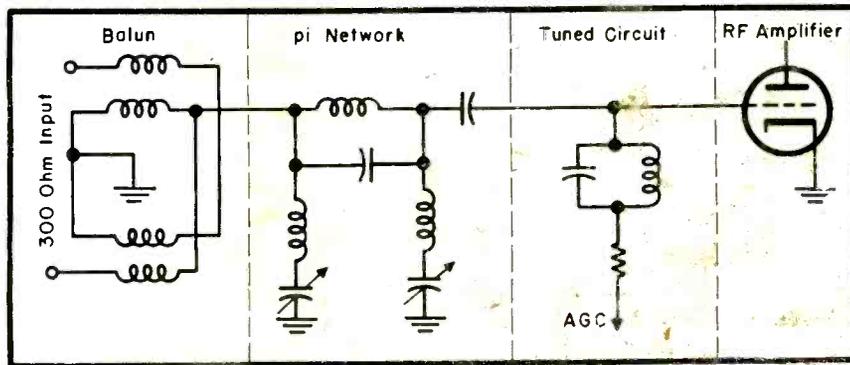


FIG. 1: ANTENNA matching network and its relation to tuner circuitry.

by WAYNE S. RIAL

Application Engineer, Electronic Tube Div.,

Westinghouse Electric Corp.

TUNED CIRCUITS in series-cascode amplifiers, which employ a *pi-network*, obtain this net by way of the output capacity-to-ground of the grounded-cathode stage, the coil, and the input capacity-to-ground of the grounded-grid stage. Most tuner manufacturers select a value of coil inductance such that the *pi* network will resonate slightly above the highest *vlf* channel.

Another peculiarity, typical to series cascode amplifiers, is the method of establishing grid bias on the grounded-grid stage. Several circuit configurations are used.

Another condition, peculiar to the series-cascode circuit, is that dual triodes containing very low heater-cathode leakage must be used, because the cathode of the grounded-grid stage is above 100-v positive

with respect to the heater. With modern dual triodes designed for cascode use, this problem has not been serious.

Several types of sharp cutoff triodes are available for cascode operation; cascode transconductances vary between 8,000 and 10,000 umhos at -1-v bias on the input section. These tubes are the BQ7A, BZ7, BK7A and BS8 in the order of magnitude of increasing cascode *GM*'s. Also a remote cutoff cascode tube (the BC8) is available with a -1-v bias cascode *GM* of near 10,300 umhos. The larger tuner manufacturers require a sharp-cutoff cascode tube, because most tuners are to be used with TV receivers employing simple *agc* bias systems. Also, tuner designers say that less variation of cascode stage input-conductance occurs with sharp

cutoff tubes, although this statement has never been truly evaluated.

Recently two new dual-triodes have been announced for cascode-tuner use; these have been especially designed for low *B+* operation (cascode *B+* of 125 volts). These tubes (the 4BX8 and 6BX8) are of great value where high gain, low noise, tuner *rf* amplifiers are desired for low *B+* operation.

Pentode-Tuner Amplifiers

The main reasons for using pentode-tuner *rf* amplifiers, are cost and available supply voltage. Pentodes are only used in low-cost *B+* receivers. As stated earlier, the principal disadvantage of tuner pentodes is no output.

Some other inherent characteristics of the pentode are:

- (1) They operate at high gain.
- (2) Neutralization is not required.
- (3) Stable operation with tuned grid circuits can be achieved.
- (4) The input impedance varies greatly with *agc*-voltage variation.
- (5) They are noisier than triodes.

One noise source in a pentode (as in a triode) is due to shot effect. The pentode has an additional noise source called *partition* noise which is due to irregularities in the division of

(Continued on page 54)

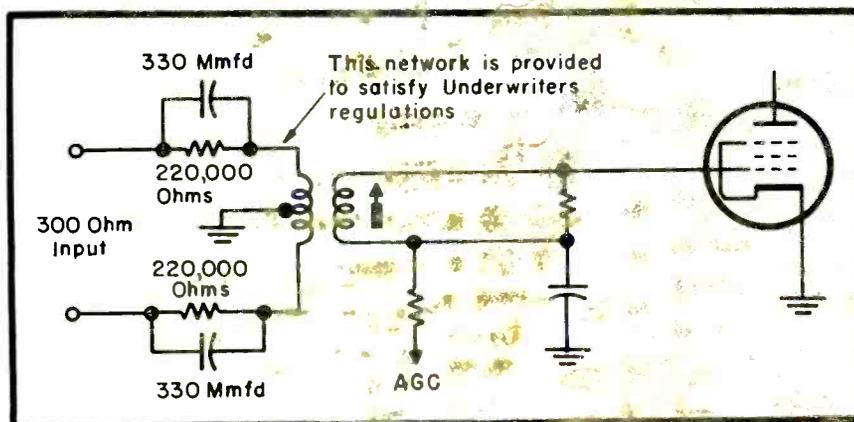


FIG. 2: TYPICAL TUNER input circuit using a matching transformer.

'VHF RF Tuner Amplifiers: SERVICE, August, 1957.

ASTRON *"Staminized"* CAPACITORS ARE


born -- protected

TO INSURE REAL STAYING-POWER AFTER INSTALLATION

From the first conception of design, Astron's protection insures highest capacitor quality and reliability.

Only the very finest of raw materials pass Astron's "Selected Purchasing System." Time-proven production techniques assure "surgically clean" assembly. Meticulous quality controls are strictly enforced . . . over 10 separate production line tests are performed, **plus a 100% final inspection of every unit before shipment!**

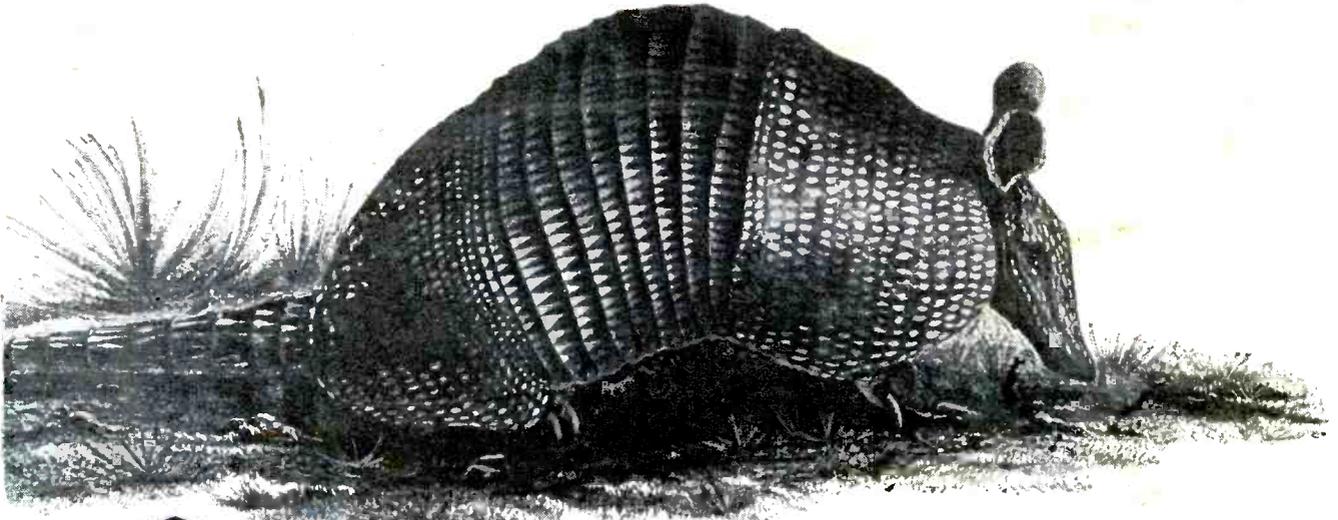Astron's climatic protection processes are many . . . each designed to guard the quality of Astron capacitors against moisture and temperature long after installation.



The Astron "Staminizing" method of manufacture guarantees you a "no-call-back" capacitor with real staying power!

Remember your reputation is our business. Build it, guard it, protect it . . . Buy Astron Capacitors . . . they're born-protected.



FREE Servicing Aid

Save time, use handy Astron pocket-size Replacement and Pricing Guide (AC-4D)
Write Today!

*Trade-mark




Export Division: Rocke International Corp., 13 East 40th St., N. Y., N. Y.

ASTRON
CORPORATION
255 GRANT AVENUE EAST NEWARK, N. J.

In Canada: Charles W. Pointon, 6 Alcina Ave., Toronto 10, Ontario

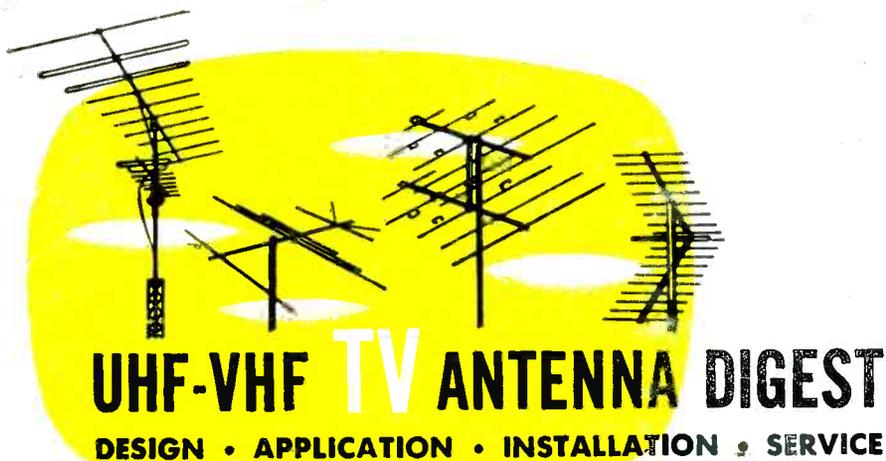TV Antenna Replacement With All-Channel Types†



SEVERAL MONTHS AGO a field-engineering crew conducted a study investigating the replacement of old worn-out antenna installations with exact-replacement antennas.¹ This study revealed that severe performance deterioration takes place in an antenna installation over a period of from four to six years, and that marked improvement can be achieved through replacement of the antenna, leadin and allied accessories.


The exploratory tests showed that exact replacements, antenna type for antenna type, provided substantial increases in gain, e.g., 7 db for channel 3 and 3.2 db for channel 8. The two TV stations involved in this performance check were slightly over fifty miles from the reception point.

The original, as well as the replace-

ment antennas, employed in the *old-versus-new* project were 5-element yagis for the lowband station and 10-element yagis for the highband station, with separate leadins for each antenna and manual selection used to switch from one antenna or the other. Installations of this type were very common up to approximately four or five years ago.

Shortly after this survey was completed, it was decided to find out what improvements would obtain if the existing cut-for-channel antennas were replaced with an all-channel model which could provide not only more gain, but *full coverage* of the stations now in the area, and prepare

TACO Report, SERVICE, July, 1957.

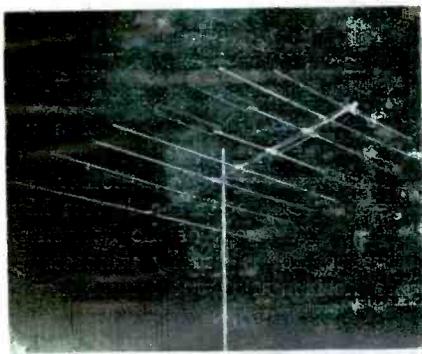

ANODIZED TV ANTENNA now available in single or stacked arrays. Anodizing is said to provide long-term sealing of the aluminum surface pores against corrosive elements. Antennas incorporate an improved paddle design on the driven dipoles for greater bandwidth. (Models G2540, G2550, G2560 and G2570; Technical Appliance Corp., Sherburne, N. Y.)

MOBILE TEST laboratory with all-channel vhf antenna used to study results obtained with newer types and cut-for-channel installations made several years ago.

†Based on an investigation conducted by the field-engineering department of the Technical Appliance Corporation.

for reception of additional channels that might be allotted.

A single *all-channel* antenna was selected for the test and installed on the same site location as the cut-for-channel array used previously.

Superior results were immediately noted. Not only was it possible to tune in more stations with consistency, but the quality of pictures from the familiar stations was better and the signal strength from the others was very satisfactory.

Not only did the study disclose that improved performance resulted when new type antennas were installed, but other advantages prevailed, too. It was possible to eliminate antenna switching, since one antenna provided multi-station pickup. The single antenna also removed the complex and unattractive multiple system setup; the mast now could be supported more firmly.

The original cut-for-channel installation had used a chimney mount to provide sufficient rigidity for the top-heavy installation. When the elements and feed contacts of the old antenna were inspected they were found to be heavily coated with soot which had begun to erode the metal. It was also found that the high-mast chimney installation often vibrated so violently that the vibration rumble was transmitted to all the walls of the house.

To overcome these problems the single antenna was mounted directly

(Continued on page 53)



SPECIALY PRICED DURING OCTOBER

**TIMED RIGHT
FOR YOUR
BIG TV
SERVICE
SEASON!**



No. 8666X

G-C SPRA-KLEEN

2 CANS FOR \$1.89 DEALER NET

VALUE \$2.40

special this month

2 CANS \$1.89

SEE YOUR G-C JOBBER NOW!

NOW, WHEN YOU NEED IT, is the time to stock up on G-C SPRA-KLEEN . . . the easy-to-use electrical contact cleaner and lubricant in the power spray can. Brushless, clean, convenient . . . SPRA-KLEEN makes servicing easier. Buy now and save during this special sale!

FREE G-C CATALOG . . . send postcard today!

GENERAL CEMENT MFG. CO.

Division of Textron Inc.

400 SOUTH WYMAN STREET

ROCKFORD, ILLINOIS

21-Inch Color-TV

(Continued from page 21)

voltage-dividing network is on a separate mounting board to which the picture-tube socket is also attached.

The sync circuits are fed from the plate circuit of the first video stage and consist of a sync separator and a sync-output stage which perform normal functions. As in past deluxe models, these color receivers employ a noise inverter circuit to insure sync stability.

Sync information is led from the

plate of the first video amplifier to the grid of the sync separator. Any noise impulse appearing in the video plate circuit will also appear in the cathode circuit. The cathode of the noise inverter is connected to the first video amplifier cathode; thus, when the grid voltage of the noise inverter is preset by the noise-inverter control any noise appearing at the cathode will appear amplified (above the preset level) at the plate of the noise inverter. This is opposite in polarity to the same noise pulse appearing at the plate of the first video amplifier. The output of the noise inverter

and the output of the first video amplifier are connected to the grid of the sync separator, and since the polarities of the two noise pulses are opposite at the common point, the noise is cancelled. As mentioned, the noise inverter control sets the level at which the noise inverter operates. It should be adjusted so that over-cancellation does not take place. This would affect sync and cause the set to lock-out of synchronization.

The *agc* circuit uses the triode section of the 6AW8A first video amplifier. The tube is keyed into conduction by a pulse from the horizontal output transformer. AGC voltage is applied to the grids of the first and second picture *if* amplifiers and the grid of the *rf* amplifier.

Preset AGC System

The *agc* system in this new line differs from previous color receivers in that the *agc* control is preset at the factory and normally requires no adjustment. If adjustment should be required it is recommended that a meter or other indicating device be connected to terminal *D* of the printed circuit video board[®] and the *agc* control adjusted to show a reading of 10 volts p-p at this point. If the *agc* control is not adjusted in this manner it is possible to degrade color renditions.

The horizontal oscillator and control stages consist of a modified *synchroguide* circuit using a 6CG7 dual triode. A stabilizing pulse is applied to this circuit from the *agc* pulse line from the horizontal output transformer. Horizontal hold is controlled by adjusting the core of the horizontal-frequency coil.

The 6DQ5 horizontal-output tube incorporates, in its grid circuit, the bias supply for the noise inverter and brightness controls. Horizontal drive is regulated by a 250,000-ohm potentiometer in the output circuit of the horizontal oscillator. Another convenience feature for the Service Man is that adjustment of the horizontal-drive control is usually unnecessary. The horizontal-output transformer is the source for horizontal pulses for *agc*, color killer, horizontal convergence, horizontal retrace blanking, burst keying in the chrominance circuits, and horizontal-sweep deflection. Other functions in the horizontal output circuit include; High voltage (22,500) for the picture-tube ultor anode, through a 3A3 rectifier and a 6BK4 shunt regulator tube; a focus-rectifier type IV2, and the 6AU4GTA damper. B+ boost voltage is also supplied from the horizontal-sweep output circuit. Adjustment for high



Picture of a smart TV technician making a dollar a minute on his way back from lunch

*
"Naturally... it's the GOLD Twilight Antenna by Winegard Co. Dept. E-10 BURLINGTON, IOWA"

21-inch Color-TV

(Continued from page 39)

signal information (the region of 3.58-mc above the picture carrier) and pass the color-signal information to the demodulators. The demodulator section uses a 12AZ7 dual triode.

The chrominance signal is fed from the second bandpass amplifier to the grids of the two triodes. Each triode operates independently, with one section as the X demodulator and the other as the Z demodulator; X and Z are arbitrary designations given to the demodulation axes, which in this instance are separated by 57.5°.

By the process of synchronous detection the modulator plate voltages vary in amplitude, continuously proportional to the amplitude and phase of the chrominance signal.

The output of the X demodulator is fed to the grid of the R-Y matrix

amplifier, one triode section of a 12BH7A, and from plate of this tube to the red grid of the picture tube. The output of the Z demodulator is applied to the B-Y matrix amplifier, one triode section of a 12BH7A, and from the plate of this tube the blue color difference signal is applied to the blue grid of the picture tube. By applying a portion of the output of both demodulators to the cathode of the two mentioned matrix amplifiers, and adding a third triode having its grid at ac ground potential, and a common cathode resistor for the three matrix amplifiers, the G-Y color difference signal is developed in the plate circuit of the third triode. The G-Y (green) color difference signal is applied to the green grid of the picture tube.

In order for the demodulators to operate, a locally-developed subcarrier reference signal must be applied.

This is accomplished by the crystal controlled 3.58-mc oscillator, a 6UA. Output from this oscillator is applied to the cathode of the demodulators, the proper phase being determined by the crystal and the reactance control tube.

Color synchronization is obtained by developing a signal which matches, exactly in frequency and phase, the color synchronization signal (burst). This is accomplished by feeding the first signal from the output of the first bandpass amplifier to the grid of the burst amplifier. A horizontal pulse from the horizontal-output transformer is delayed to coincide with burst time in the composite transmitted signal. This follows the horizontal sync pulse at a predetermined time; thus by delaying the pulse fed to the burst amplifier grid, the tube conducts only at the time burst is present. Burst is then ampli-

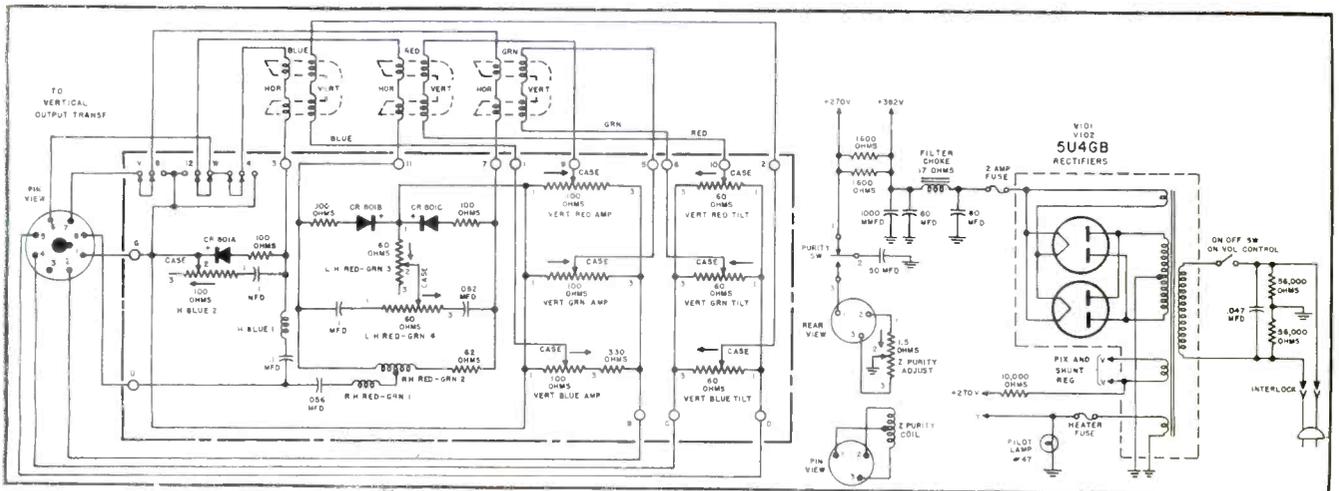


FIG. 6: DYNAMIC CONVERGENCE and power supply circuitry of RCA CTC7 color-TV chassis.

fied and fed through a transformer to the phase detectors, two diode sections of a 6BN8. At the same time, a portion of the subcarrier-reference signal from the local 3.58-mc oscillator is fed to the phase detectors. Any variation between the phase of burst and the phase of the local 3.58-mc oscillator results in an error voltage across R_{T1} and R_{T2} . The error voltage is fed to the reactance control tube which effects the necessary phase correction in the 3.58-mc oscillator. As the 3.58-mc oscillator is driven to the correct phase (to match burst phase), the correction voltage in the phase detector drops to zero and the color signals are demodulated in proper phase. When this happens, color synchronization takes place because the phase of burst and the phase of the locally-generated 3.58-mc subcarrier are the same; thus the color signal information can be demodulated to produce the original colors transmitted. All colors will appear in the picture in the same places and proportions as they do in the scene being televised.

Automatic control of the chrominance level is effected by applying a rectified version of the amplified burst signal to the grid of the first bandpass amplifier. Operation of the automatic chroma control circuit can be compared roughly with *agc* operation. As the burst signal increases in amplitude, the burst voltage from the output of the burst amplifier increases. This increased burst voltage, when rectified by one of the diodes of the phase detector, produces an increase in the bias voltage that is applied to the grid of the bandpass amplifier, and as a result, the stage provides less gain and thus limits the amplification of the color signal to the predetermined level.

A decrease in the received burst level would result in the opposite effect. Less burst would result in less bias at the grid of the first bandpass amplifier, more gain in this stage, and the color signal would be amplified to the predetermined level.

By this means, the color picture remains at a constant level regardless of variations in the strength of the transmitted burst signal.

The color killer circuit in this new chassis cuts off the second bandpass amplifier during the absence of the color synchronization signal (burst); thus color will appear in the picture only when a color signal is being received.

A portion of the output of the 3.58-mc subcarrier oscillator is fed to the

(Continued on page 44)



Don't Juggle a Heavy Chassis

WHEN A FINGER TIP WILL DO THE JOB FOR YOU . . .

How many times have you had to lift and turn a big chassis in order to get the light correctly focused so that you could make a solder connection . . . or look for a broken lead? All this extra work can now be eliminated if you put a LUXO LAMP above your bench.

This remarkable lamp directs *all* the light where you want it. With just the touch of a finger, you can raise, lower, turn or tilt it to any angle . . . get just the desired focus, direction and intensity of light. Comfortable to work under, too, because it eliminates reflections and disturbing shadows . . . and provides glare-free illumination.

APPROVED BY UNDERWRITERS LABORATORIES, INC.

Ask for LUXO—if you want the BEST!

YOUR JOBBER HAS IT

LUXO LAMP CORPORATION • TUCKAHOE, N. Y.
SAN FRANCISCO, CAL. • MONTREAL, QUEBEC

MORE ACTIVE! EFFECTIVE!



KESTER "RESIN-FIVE" CORE SOLDER

THE BEST FOR TV-RADIO WORK . . .
EVERYTHING ELECTRICAL—Kester "Resin-Five" Core Solder is better and faster than any solder ever developed. It has an activated flux-core that does a perfect job on all metals including zinc and nickel-plate. The flux residue is absolutely non-corrosive and non-conductive.

Available in all practical Tin-Lead Alloys; 40/60, 50/50 and 60/40 in diameters of $\frac{1}{32}$ ", $\frac{1}{16}$ ", $\frac{3}{64}$ ", $\frac{1}{8}$ " and others.

Printed Circuit Soldering On Copper-etched boards use 60% Tin-40% Lead Alloy . . . for those that are Silver-surfaced use 3% Silver-61½% Tin-35½% Lead

KESTER SOLDER COMPANY

4248 Wrightwood Avenue, Chicago 39, Illinois • Newark 5, New Jersey, Brantford, Canada

YOUR INSTALLATION VOLUME CAN BE GREATER!

If you're *not* a Channel Master Dealer you are probably not getting your share of the *really profitable* antenna installation business. Hundreds of dealers have doubled and even tripled their antenna sales *in less than one year* when they

switched to Channel Master and featured the famous T-W antenna. In fact, far more T-W antennas are bought than any other fringe area antenna. There must be good reasons for this. Below are listed but a few of them.

How much installation business are you losing every week? ...because you don't feature the CHANNEL MASTER® T-W

Put these extra selling advantages to work for you!

Superior PERFORMANCE! Outperforms any all-channel antenna ever made! Revolutionary "Traveling Wave" design delivers highest front-to-back ratios (better than 10:1) — top gain over the entire VHF range.

Stronger CONSTRUCTION! Super-strong in every detail of construction: Twin-Boom — the only antenna with 2 full length crossarms; 2 Super-Nests — the most powerful grip that ever held an antenna to the mast; Line-Lok — absorbs all transmission line tension; 7/16" dia. elements.

Bigger NATIONAL ADVERTISING! More than 75,000,000 advertising messages in America's leading national magazines. Now saturation coverage with big-space ads blanketing 173 prime outdoor antenna markets.

LIVE LEADS galore! Tens of thousands have already responded to Channel Master's Free "Antenna Check-Up Kit" offer — repeated in new national ads. Based on experience, 50% — and more — of these leads are converted into actual sales


Local CO-OP ADVERTISING! The most liberal advertising allowance in the industry — so you can run your own local promotions. Channel Master dealers have the widest array of mats, radio and TV spots, and display materials.

Promoting ANTENNA REPLACEMENTS! Channel Master's national advertising hammers home the theme of antenna obsolescence — opening new markets for you!

Call your Channel Master distributor now!

© Reg. U.S. Pat. Office and Canada

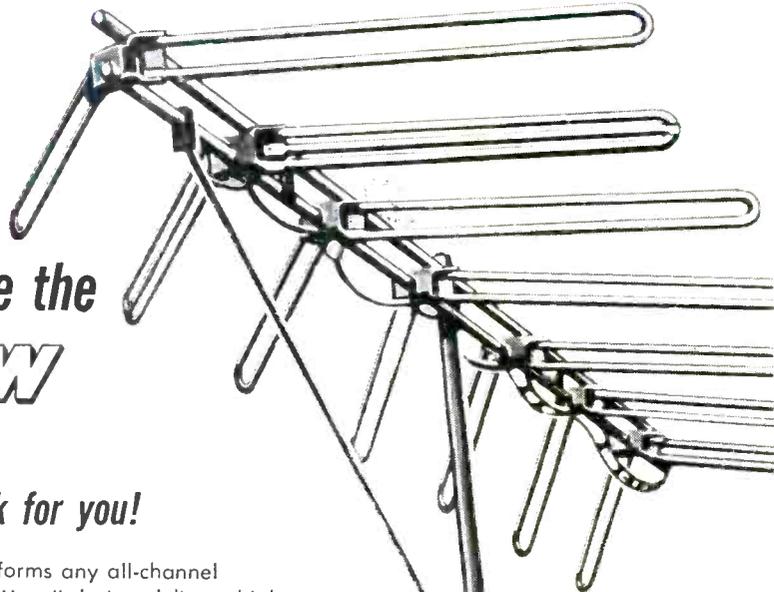7-element
model no. 350
5-element
model no. 351
3-element
model no. 352



model no.
354-1

including: • 2-element T-W
• Combination 4 ft. x 1 1/4" aluminum mast and Universal Tripod Mount • 3 Mounting Nails with Neoprene sealing washers • 50' 80 mil wire • 6 - 3/2" Standouts • 1 Standout Strap.

A COMPLETE
ANTENNA
INSTALLATION
IN ATTRACTIVE
3-COLOR
DISPLAY CARTON

NEW "INSTALL-IT-YOURSELF" ANTENNA KIT featuring new 2 ELEMENT T-W ANTENNA

Designed for top performance in suburban and metropolitan areas. Powerful "Traveling Wave" principle provides the 2-element T-W with better all around performance than a stacked conical.

Promotionally Priced at \$29⁹⁵ list



CHANNEL MASTER CORP.

ELLENVILLE, N. Y.

Copyright 1973 Channel Master Corp.

WORLD'S LARGEST MANUFACTURER OF TV ANTENNAS AND ACCESSORIES

service engineering

INDUSTRIAL
ELECTRONICS

Repeater Stations, Antennas and Amplifiers for Microwave Systems . . . Test Equipment Facilities for Two-Way Installations

SINCE MICROWAVE PROPAGATION is essentially limited to line-of-sight paths, it is frequently necessary to repeat the signals. When communications are not required at repeater stations its equipment takes a very basic form. In this case the received video signal is simply reshaped and retransmitted in the same direction. Frequently, however, it is desirable to terminate some of the channels at a repeater station. The terminations may be on a party-line basis, in which case the demodulated information is reinserted into the system for further use; or the termination may be complete, in which case the channel is free to be used in the rest of the system for other purposes. The repeater with multiplex and termination units is similar to two microwave terminals connected back to back. The only additional equipment required here is called a blanking and switching unit, an electronic gate synchronized by the multiplex equipment. The gate is used to remove selected channel pulses from the train of through video pulses. It is also used to reinsert new pulses in the same channel positions with the same or new modulation for further use in the system.

Power Amplifier Operation

Power amplifiers designed for microwave applications are usually 100% grid modulated by the amplified pulses from multiplex modulators. In the output are short bursts of *rf* energy at about 20 to 30 watts peak

power. These correspond to .5 micro-second pulses spaced about 4 micro-seconds apart which are generated, synchronized, and pulse-position modulated in the multiplex. The transmitter-modulator circuits contain pulse-shaping stages which assure that all pulses will be uniform in shape and amplitude, and free from noise. This feature is of great importance when the same pulses are repeated through many stations. Noise accumulated in transmission and reception is effectively removed at each repeater before transmission.

A single antenna is almost always used for both transmission and reception. These two signals are sep-

arated by a pair of band-pass filters called an *rf* duplexer. At 2000 mc the receive and transmit filters are coupled through a single coax transmission line to a dipole radiator backed up by a parabolic reflector. The reflector concentrates the radiated energy in the desired direction with an efficiency that leads to effective power gains of approximately one thousand.

Two-Way Test Equipment

IN TWO-WAY service, tube testing is extremely important. Accordingly one must select instruments required for such tests with great care. The emission type will not do; testers should measure dynamic mutual conductance. Even after testing all tubes in a high-grade tube tester, substitution of tubes one-at-a-time often reveals tubes which will not provide optimum performance under actual operating conditions.

Most tube testers fail to detect grid emission, a significant cause of two-way receiver malfunction. Special grid-circuit tube testers, or general-purpose tube testers with built-in grid emission testing features, will show up tubes which are apparently okeh, but which detract from receiver performance.

Two-way equipment manufacturers generally sell special test meters for use with their equipment. These test meters plug directly into the mobile unit enabling measurement of various voltages and currents without exposure of the bottom of the chassis. Some shops, servicing several makes of mobile equipment, have built universal test meters for this purpose.

Besides adequate test equipment, more rigid servicing techniques and ingenuity are essential. Mobile radio equipment is subjected to environmental conditions far more severe than electronic devices installed at fixed locations. While most receivers employ very stable frequency control circuits, some have been known to drift off frequency when subjected to unusually high or low temperatures.

Although it is not economically feasible for a service shop to install a temperature chamber, some reports of malfunction of two-way equipment have been traced to frequency drift attributed to exposure to extreme temperatures. A mobile unit whose frequency checks out in Chicago on a spring day could be off frequency in the middle of July, as well as in January, because of the wide variance in temperature. It can be extremely

(Continued on page 48)



CHECKING TRANSMITTER tuning with a grid-dip meter. The circuit tracer to the right of the marine radiotelephone serves to check receiver circuits.

(Photo by Cyril Glunk)



TWIN LEAD HANKS

...make your Job Easier!

AMPHENOL job-size hanks make your selling job, your installing job easier! Pre-assembled with lugs on one end, attractively packaged in convenient 25, 50, 75 and 100 foot lengths, AMPHENOL hanks are easy to use for new and replacement installations, easy to sell to the "do it yourself" market. No bulky spools to handle, just job size hanks for every twin lead applicator!

Lighten up your work load, boost your sales with AMPHENOL Twin Lead hanks!



50 FEET GENUINE



no. 214-056
FLAT TWIN LEAD



**PREASSEMBLED!
WITH LUGS ON ONE END!**

AMPHENOL ELECTRONICS CORPORATION
CHICAGO 30, ILLINOIS

SEE OTHER SIDE

| Part No. | Description | Wastage in Hanks of | | | |
|------------------------|---|---------------------|--------|--------|---------|
| | | 25 ft. | 50 ft. | 75 ft. | 100 ft. |
| 214-318 | Indoor - 60 mil. 28 pure copper cond. | ✓ | ✓ | ✓ | ✓ |
| 214-056 | Standard - 60 mil. 28 pure copper cond. | ✓ | ✓ | ✓ | ✓ |
| 214-559 | Standard - 72 mil. 28 copper-weld cond. | | ✓ | ✓ | ✓ |
| 214-298 | Indoor - 72 mil. 28 pure copper cond. | | ✓ | ✓ | ✓ |
| 214-106 | Standard - 100 mil. 28 pure copper cond. | | ✓ | ✓ | ✓ |
| Now Available in Coils | | | | | |
| 214-271 | Air-Core - S. Pat. 2543696 - 28 pure copper cond. | | ✓ | ✓ | ✓ |

Remember
for finest quality, virgin polyethylene is used in all AMPHENOL Twin Leads.

PRE-ASSEMBLED
with lugs on one end!



AMPHENOL ELECTRONICS CORPORATION
Chicago 30, Illinois

21-Inch Color-TV

(Continued from page 41)

plate and grid of the triode section of the 6BN8 killer detector. When burst is present in the received signal, as mentioned previously, the phase detector will operate. A portion of the burst signal applied to the phase detector is also applied to the cathode of the killer detector.

When the signal applied to the plate and grid of the killer detector is in phase with the signal applied to the cathode, the tube conducts and a voltage is developed at the grid of the color killer tube. This voltage overcomes the normal bias on the grid of the color killer and causes this tube to stop conducting. The output of the color killer is applied as a bias to the grid of the second bandpass amplifier; thus, when the color killer is conducting, the second bandpass amplifier is cut off. When the second bandpass amplifier is cut off, no signal is applied to the grids of the X and Z demodulators and as a result color picture presentation on the picture tube is not possible.

When the color-killer tube does not conduct, the second bandpass amplifier is free to operate and amplify any signal present in its grid circuit.

Thus, the voltage developed by the killer detector (happening only during the time burst is present) overcomes the killer bias, the second bandpass amplifier operates, and a color picture will be shown on the picture tube. When burst is not present, only the signal from the 3.58-mc subcarrier oscillator will be present at the plate and grid of the killer detector. The tube will not conduct, since only when burst is present will there be sufficient cathode bias to cause conduction, and the color killer will apply bias to the grid of the second bandpass amplifier sufficient to cut off its operation. In this manner, since the phase of burst and the phase of the signal from the 3.58-mc subcarrier oscillator are the determining factors for operation of the killer circuit, noise impulses cannot cause the second bandpass amplifier to operate and the black-and-white picture will be free of color caused by impulse noise. The operating level of the color killer circuit is preset by the killer-threshold control.

Horizontal-retrace blanking is accomplished by applying a horizontal pulse to the grid of one triode section of a 12BH7A, the horizontal blanking amplifier. This pulse, amplified, is applied to the cathode of the

second bandpass amplifier, causing this tube to be cut off during horizontal retrace time. In addition, the amplified pulse is coupled to the cathodes of the three matrix amplifiers. This causes these tubes to draw large currents during retrace and thus reduces their plate voltage and cuts off the picture tube. It also causes these tubes to reset the *dc* level of the color signals.

The new glass-envelope picture tube introduced in the 800 series color receivers is similar in many respects to the previously used metal-envelope tube. It features magnetic-sweep deflection, electrostatic focus and magnetic convergence.

An internal conductive coating, similar to black-and-white picture tubes, is used as a supplementary filter capacitor for the high voltage. In these receivers, high voltage is regulated at 22,500 volts.

The picture-tube accessories, which include the deflection and convergence yokes, lateral beam-positioning and purity magnets, are installed in conventional positions on the neck of the tube. Two other features are edge purity magnets and the Z purity coil.

In previous color receivers the edge purity magnets were called *color-equalizing magnets*. They were installed about the periphery of the face of the picture tube and were used for correcting color impurities caused by stray magnetic fields near the outer edges of the tube. The new edge-purity magnets perform a similar function, but are installed on the picture-tube pull-up ring mounting assembly near the bell end; these edge-purity magnets are hairpin-shaped magnetized bars which are rotated on insulated mountings to achieve the desired corrective effect near the edges of the picture tube.

An auxiliary purity device is the Z purity coil. This coil consists of a few loops of heavy wire at the periphery of the picture tube. Its purpose is to correct color impurity effects caused by stray magnetic fields affecting the Z axis (lengthwise from faceplate to socket) of the picture tube.

A momentary-control push-button switch on the rear of the chassis discharges a capacitor through the coil to achieve a magnetization of metal components which will give the desired purity improvement.

Convergence Circuitry

The convergence circuits used with the glass picture-tube chassis have been designed for greater ease and accuracy of convergence. One of the most noteworthy features of the system is that convergence in the center area of the viewing screen is *clamped* at a *dc* reference level. This is accomplished by rectifying a portion of the horizontal convergence voltage and applying it to the horizontal-dynamic convergence coils. By this means the center of the screen will remain in convergence, with regard to horizontal dynamic convergence. Once adjusted, adjustment of horizontal dynamic convergence at either side of the screen can be made without materially affecting convergence at the other edge of the screen. Convergence at the center of the screen is accomplished by permanent magnets, which are in adjustable sliding mounts on the convergence yoke assembly, which is mounted over the pole piece assembly in the neck of the picture tube.


Simpson

announces

NEW

HANDISCOPE

model 466

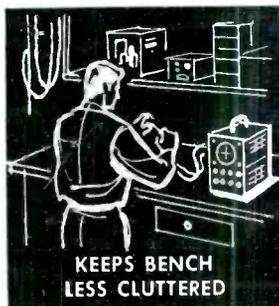

perfect for:

- Hi-Fi troubleshooting
- Industrial maintenance
- Production line tests
- Communications equipment checks
- AM & FM radio servicing
- Useful for black and white TV, too

MEASURES ONLY 8" x 12 1/4" x 16 1/2"—Use this rugged little instrument for the 101 jobs where a big specialized scope isn't needed. It brings you quality features such as a filter type graticule, universal-fit bezel, and 5" screen, yet is economically priced. And like other Simpson test equipment, Model 466 is built to give you years of hard service.

Frequency Response of Vertical Amplifier:
From 15 cycles/sec to 100 Kc/sec, flat within ± 1 db; 6 db down at 250 Kc/sec; useable to 1 Mc/sec.

Maximum Vertical Deflection Sensitivity:
30 Millivolts RMS/inch.

Frequency Response of Horizontal Amplifier:
From 15 cycles/sec to 20 Kc, flat within ± 1 db; 6 db down at 100 Kc/sec.

Maximum Horizontal Deflection Sensitivity: 0.7 volt RMS/inch.

Z-Axis Sensitivity (Voltage Required to Extinguish Beam): 20 volts RMS.

Calibrating Voltage (at 117.5 VAC power source): 1 volt P-P $\pm 10\%$.

Maximum Input Voltage: 400 volts peak.

Input Resistance: 0.1 Meg (at atten. x 1); 0.5 Meg (at atten. x 100).

Input Capacitance: 40 uuf (at atten. x 1); 35 uuf (at atten. x 100).

Sawtooth Sweep Range: 15 cycles/sec to 80 Kc/sec.

Power Consumption (at 117.5 volts AC): 50 watts.

Model 466 with Lead, Operator's Manual.....

\$144⁹⁵

See your Electronic Distributor, or write


SIMPSON ELECTRIC COMPANY

5200 W. Kinzie Street • Chicago 44, Illinois • Phone: EStebrook 9-1121

In Canada: Bach-Simpson Ltd., London, Ontario



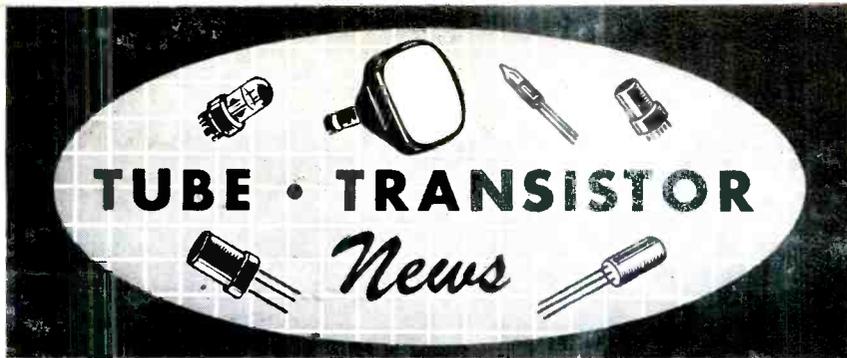WORLD'S LARGEST MANUFACTURER OF ELECTRONIC TEST EQUIPMENT



Latest Developments in Semiconductors (Diodes and Transistors) . . . Hi-Mu Triodes for FM . . . 17"-24" Wide-Angle Picture-Tube Replacements

WELDED, HERMETICALLY-SEALED, high temperature, medium-current diffused silicon - diode rectifier replacements¹ (1N253, 1N254, 1N255 and 1N256), particularly suited to rectifier applications where high inverse voltages, high forward conductance, very low leakage current and extremely high rectification efficiency are required, are now available.

The 1N253 has a peak-inverse rating of 95 v, and an average rectified current of 1 a. The 1N254 has a peak-inverse rating of 190 v and an average rectified current of 400 ma. The 1N255 has a peak-inverse rating of 380 v and an average rectified current of 400 ma, while the 1N256 has a peak-inverse rating of 400 v and an average rectified current of 200 ma.

High-Frequency Transistor

ANOTHER NEW SEMICONDUCTOR development² is a hermetically-sealed junction transistor of the germanium *pn*p type (2N274), designed primarily for *rf* amplifier service in compact mobile and communications equipment, and in entertainment-type receivers operating at frequencies covering the AM broadcast band and up into the short-wave bands. This transistor is also suitable for use as an *if* amplifier or as a mixer-oscillator.

The 2N274 utilizes shielding to minimize interlead capacitance between the collector lead and the base lead and to minimize coupling to adjacent circuit components. The resultant advantages of such shielding are of primary importance in critical high-frequency circuits where low

feedback capacitance is a major design consideration.

The 2N274 also features low collector transition capacitance (1.7 mmfd) which makes possible satisfactory gains in the AM broadcast band without the use of a neutralizing network, a collector dissipation of 35 milliwatts maximum, and a power gain of up to 45 db at 1.5 mc and 24 db at 10.7 mc when used in a unilateralized common-emitter circuit with base input.

Junction Transistor

FOR HIGH-VOLTAGE *on-off* control applications, such as in neon-indicator circuits, relay-puller circuits, incan-

¹RCA. ²International Rectifier Corp.



A 450-MA, 6.3-V TV-picture tube heater for portable receiver picture tubes which incorporates control of both warm-up time and current. Wound from a straight piece of tungsten, the heater is a double helical coil which is said to make possible the same cathode coating temperature achieved in 600 ma, 6.3-v tubes. Unlike conventional 450-ma heaters whose coils are wound from a spiral section of tungsten wire, this heater boasts a rigid mechanical structure with little tendency to sag away from the cathode cap. (Sylvania)

descent lamp driver circuits, and direct indicating counter circuits of electronic computers, a junction transistor (2N398) of the germanium *pn*p alloy type² is now available.

The 2N398 features a maximum voltage rating of -105 v for collector-to-base breakdown and for collector-to-emitter punch through. This value permits the design of neon-indicator circuits in which the transistor can switch the full firing voltage of the indicator lamp. Because the 2N398 has a minimum *dc* current transfer ratio of 20, neon indicating circuits can be designed to perform the functions of a logic circuit without the use of a separate logic stage.

Silicon Diodes

SILICON DIODES³ claimed to be comparable in cost and electrical ratings to the 1N91, 1N92 and 1N93 germanium diodes used in power supply applications, have been announced.

The diodes (SD-91, SD-92 and SD-93) are of all-welded construction, hermetically sealed, and feature a peak-inverse-rating range of from 100 to 300 v. Maximum rectified *dc* ranges are from 100 to 150 ma at 85° C ambient. The rectifying barrier of this silicon diode is formed by the fused junction principle. Pig-tail leads are welded to the terminals of an all-welded, shock-proof housing.

High-Mu Twin Triodes

HIGH-MU TWIN TRIODES (6DT8 and 12DT8) of the 9-pin miniature type², have been developed for application as combined oscillator-mixers and *rf* amplifiers in cathode-drive or grid-drive circuits of FM tuners.

The two units of each type are isolated from each other by an internal shield having a separate base-pin terminal. This shielding arrangement affords a reduction in antenna radiation.

Wide-Angle Picture Tubes

A WIDE-ANGLE RECTANGULAR glass television picture tube (24AHP4), having a 24" diagonal envelope, has been added to the RCA line.

The new tube has an overall length of 15½" and a weight of 28 pounds. Compared to tube types having the same size faceplate and 90° deflection, the 24AHP4 is 5¼" shorter and seven pounds lighter.

In addition to its wide deflection angle and short length, the tube also features a neck diameter of 1¾",

(Continued on page 53)

¹Raytheon.


how long would it take you to solve this service problem?

PHOTOFACT

helps you lick problems
like this in just minutes
for only *2½¢ per model!

SYMPTOM:

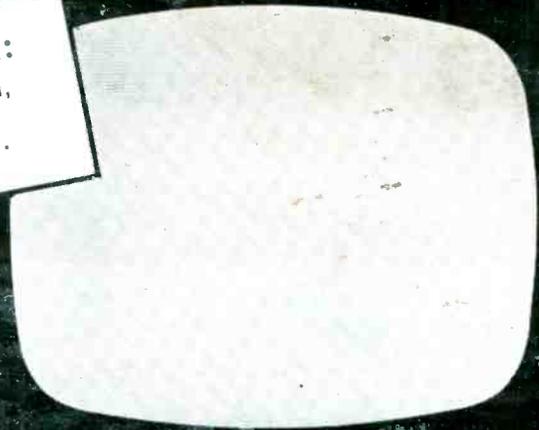Raster, No Sound,
No Picture,
and No Snow ...




Let's take a look at this problem: A condition such as this can exist only when there is no signal reaching the picture tube or the audio output stage. Using the Tuner Service data (found in every PHOTOFACT TV Folder), first isolate the trouble by connecting an amplitude-modulated signal to the mixer-grid test point "D." The appearance of one or more black bars on the face of the tube would indicate that the trouble is probably in the tuner. So look for the following possible causes:

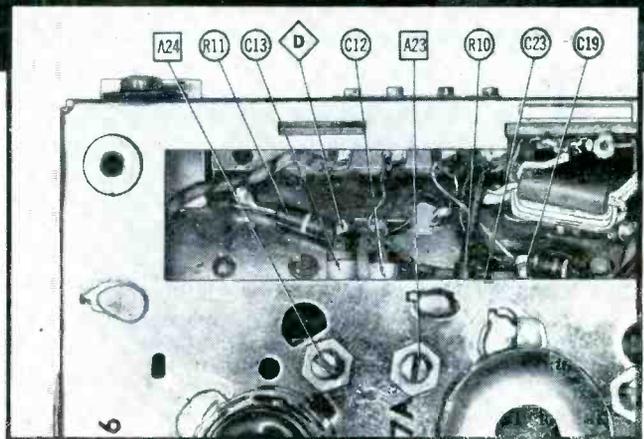1. Defective oscillator-mixer tube
2. Defective RF amplifier tube
3. Open plate-load resistor in the oscillator stage
4. Failure of the feedback capacitor in the oscillator stage
5. Open decoupling resistor
6. Dirty or faulty contacts
7. Cold solder joint

Using the applicable PHOTOFACT Folder you can troubleshoot and solve this problem in minutes. Here's how:

Check the oscillator-mixer and RF amplifier tubes. Tubes okay?—then: Check voltages on the tube pins (they're right on the schematic) for open oscillator plate-load



(Based on an actual case history taken from the Howard W. Sams book "TV Servicing Guide")

resistor, open RF decoupling resistor, faulty feedback capacitor, dirty switch contacts or cold solder joints.

Every PHOTOFACT Television Folder contains complete detailed information on Tuners, including separate Schematics, separate Keyed Chassis Photographs, Parts Lists, Alignment Points, Test Points, and Field Service Adjustments that will help you quickly locate the proper parts to replace and tell you how to do a touchup or thorough alignment job after making the necessary repairs. These features are a *plus* exclusive in PHOTOFACT.

Whatever your problem or favorite servicing procedure may be—you will always find all of the information you need at your fingertips in PHOTOFACT. For only *2½¢ per model, PHOTOFACT helps you solve your service problems in just minutes—helps you service more sets and earn more daily!

*Based on the average number of models covered in a single set of PHOTOFACT Folders.



**MONEY BACK
GUARANTEE!**

Got a tough repair? Try this—at Howard W. Sams' own risk: see your Parts Distributor and buy the proper PHOTOFACT Folder Set covering the receiver. Then use it on the actual repair. If PHOTOFACT doesn't save you time, doesn't make the job easier and more profitable for you, Howard W. Sams wants you to return the complete Folder Set direct to him and he'll refund your purchase price promptly. **GET THE PROOF FOR YOURSELF—TRY PHOTOFACT NOW!**

FREE



**FOR SERVICE
TECHNICIANS ONLY**

Fill out and mail coupon today for Free subscription to the Sams Photofact Index—your up-to-date guide to virtually any receiver model ever to come into your shop. Send coupon now.

HOWARD W. SAM'S & CO., INC.

Howard W. Sams & Co., Inc.
2207 E. 46th St. Indianapolis 5, Ind.

Put me on your mailing list to receive the Sams Photofact Index and Supplements. My (letterhead) (business card) is attached.

I'm a Service Technician: full time; part time

My Distributor is: _____

Shop Name _____

Attn: _____

Address: _____

City _____

Zone _____ State _____

... another
MALLORY
 service-engineered
 product



MALLORY VIBRATORS


to meet every service requirement

1

FOR THE VERY BEST IN PERFORMANCE...

Mallory Gold Label Vibrators are the result of over 27 years of vibrator pioneering and leadership. Employing the exclusive Mallory buttonless contact design, they eliminate problems of sticking contacts... insure positive starting... provide far longer life... are unbelievably quiet. For utmost dependability, and to build your reputation for service, make Mallory Gold Label Vibrators your standard of quality.

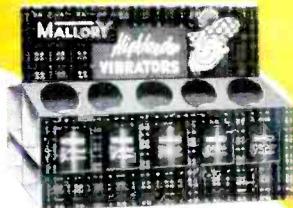Depend on Mallory
 for vibrator dependability
 —for any job



2

FOR ECONOMY JOBS...

The Mallory Highlander is a new line designed expressly for the jobs that must be done at a lower price. It delivers trouble-free service longer than any vibrator in its price class—second only to the Gold Label line. Ask your Distributor for the new Mallory Highlander—in the handy new 10-pack carton.

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc. INDIANAPOLIS 6, INDIANA

- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Mercury and Zinc-Carbon Batteries
- Controls
- Switches
- Rectifiers
- Filters

Service Man and Color-TV

(Continued from page 19)

waiting for color to be perfected are in for a considerable surprise. They are missing out on a good thing, and have been for some time. All the excuses and reasons for knocking color have been removed, and the only legitimate reason at this time could be: "We aren't ready or prepared for color." Now is the time to become prepared; the rest of the industry is forging ahead—don't be left behind.

Glass Envelope Color Tube

(Continued from page 24)


convergence correcting fields for the three different beams. This new feature makes possible the attainment of optimum convergence over the entire picture, with fewer successive approximation adjustments of the components.

Service Engineering

(Continued from page 43)

hot inside of the trunk of an automobile out in the sun on a summer day and very cold, especially when a two-way unit is first tuned on in mid-winter.

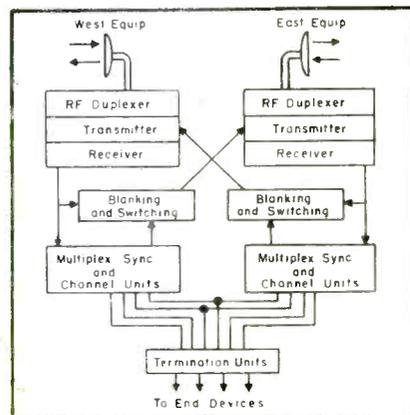Thus, it would be a good idea to check equipment at room temperature and at the highest and lowest temperature, as well as other environmental conditions to which 2-way equipment will be subjected.



REPEATER with multiplex and termination units. Additional equipment required for this phase of operation is a blanking and switching unit.

Color-TV Checks

(Continued from page 27)

gun operating. The center of bars number 3 and 9 should be at the same brightness level as the adjacent spaces between the bars. In the next step, the red and blue guns should be biased off, leaving only the green gun operating. The center of bars number 1 and 7 should be at the same brightness level as the adjacent spaces between the bars.

If phasing is not correct, phasing should be adjusted in accordance with the procedure given in the service data.

If the phasing is correct, the approximate relative gains should be checked in the following manner:

The red and green guns should be biased off, leaving only the blue gun operating. Then the pedestal-amplitude control on the generator should be turned fully clockwise to 10 (100%). The contrast or color-saturation controls on the receiver should then be adjusted so that the center of bar number 6 has the same brightness as the adjacent spaces between the bars.


The next step involves biasing off of the blue and green guns, leaving only the red gun operating. Now the pedestal-amplitude control must be turned counterclockwise to the position at which the center of bar number 3 has the same brightness as the adjacent spaces between the bars. This condition should be obtained with the pedestal-amplitude control set at approximately 5.5 (55%).

Finally the blue and red guns should be biased off, leaving only the green gun operating. The pedestal-amplitude control should now be turned counterclockwise to the position at which the center of bar number 10 has the same brightness as the adjacent spaces between the bars. This condition should be obtained with the pedestal-amplitude control set at approximately 3.4 (34%).



ALL-GLASS picture tube used in latest color chassis.

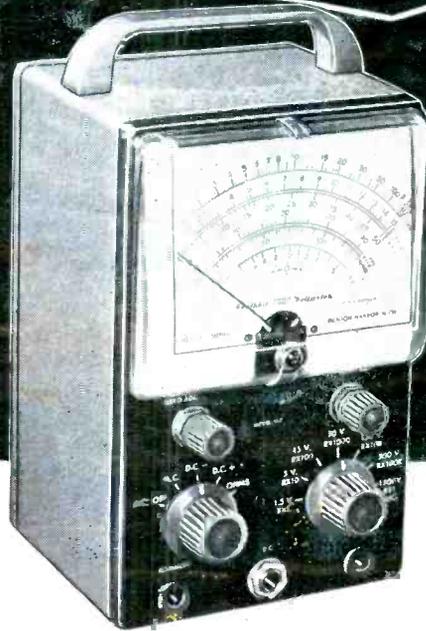look what **\$24⁵⁰** buys
in test equipment!



**HEATHKITS
GIVE YOU
TWICE AS MUCH
equipment for
every dollar
invested**

The famous model V-7A Vacuum Tube Voltmeter is a perfect example of the high-quality instruments available from Heath at 1/2 the price you would expect to pay! Complete, only **\$24⁵⁰**



Get the most out of your test equipment budget by utilizing HEATHKIT instruments in your laboratory or on your production line. Get high quality equipment, without paying the usual premium price, by dealing directly with the manufacturer, and by letting engineers or technicians assemble Heathkits between rush periods. Comprehensive instructions insure minimum construction time. You'll get more equipment for the same investment, and be able to fill your needs by choosing from the more than 100 different electronic kits by Heath. These are the most popular "do-it-yourself" kits in the world, so why not investigate their possibilities in your particular area of activity! Write for the free Heathkit catalog now!



Contains detailed descriptions of Heathkit models available, including VTVM's, scopes, generators, testers, bridges, power supplies, etc.



Also describes Heathkit ham gear and hi-fi equipment in kit form. 100 interesting and profitable "do-it-yourself" projects!

FREE catalog

Mail coupon below for your copy—Now!

HEATH COMPANY
A SUBSIDIARY OF DAYSTROM, INC.,
BENTON HARBOR 11, MICHIGAN

Name _____

Address _____

City & Zone _____

State _____



Have YOU Given Your Service Business Its COLOR Transfusion?

This TV service-dealer is "hep". He's getting ready now for healthy, wealthy business. "Doctor", of course, is his RCA Tube Distributor. And he'll give you your "booster shot", the new RCA PICT-O-GUIDE for COLOR TV, with your order for RCA TUBES—free of extra charge!

Written by RCA's well-known TV-service authority John R. Meagher (who also wrote the famous RCA Pict-O-Guide series for black-and-white TV), this volume is profusely illustrated with full-color photos, packed with step-by-step alignment and trouble-shooting instructions, and loaded with labor- and time-saving short cuts for profitable color-TV servicing. See for yourself what other service technicians have learned—color-TV servicing has been simplified! See your RCA TUBE DISTRIBUTOR with your order today!

RCA COLOR-TV PICT-O-GUIDE CONTAINS SECTIONS ON:

Color Mixing • RCA Compatible Color TV System • Purity • Convergence • Gray-Scale Tracking
Color Operating Controls • Antenna Considerations • RF-IF Bandpass Alignment • Color Test Equipment • Color-Bar Patterns • Troubleshooting • Signal Tracing • Interference • "Green Stripe" Test Signals



RECEIVING TUBES

RADIO CORPORATION OF AMERICA
© Electron Tube Division Harrison, N. J.



AUDIO

INSTALLATION AND SERVICE

Phono • Tape • PA
Cartridges • Needles • Amplifiers • Speakers

FM, Drop-Out and Modulation Noise Problems in Magnetic Tape†

Tape noise present during strongly recorded portions (modulation noise) is much greater than that occurring during periods when there is no recorded signal (background noise). Since this modulation noise varies with signal intensity, it is usually masked by the signal and therefore goes unnoticed.

However, if the modulation noise is sufficiently intense, it may be heard in the background of the recorded program. This is particularly true in the case of sustained tones or sine wave test signals. While modulation noise is perhaps not the most serious problem in magnetic recording, it most certainly deserves attention.

Surprisingly enough, two of the most troublesome forms of modulation noise are not magnetic in origin at all, but arise from mechanical con-

siderations. They are frequency-modulation noise and drop-out noise.

Frequency-Modulation Noise

Tape is usually driven past the recording heads by a mechanical drive system. The free span of tape between the capstan drive and the idler roller represents a highly resonant mechanical body which is easily excited into longitudinal vibration by friction as it slides over the heads. The resultant fluctuations in tape motion cause frequency modulation of

From a report prepared by R. A. Von Behren, Research and Development Manager, Magnetic Products Division, Minnesota Mining and Manufacturing Company.

the recorded signal which may be audible as noise.

This type of noise can be demonstrated by recording a sine wave tone of about 3 to 5 kc and listening for the background noise. The fact that the origin of the noise is motion flutter can be verified by placing a small roller in contact with the tape near the point of contact with the recording or reproducing head. In most cases a sharp drop in background noise results, and the signal is noticeably clearer.

While the small amount of FM noise present in most recording systems is not usually a problem on program material, an abnormal condition such as a sticking idler, or the tape binding in the guides may increase greatly this effect and cause it to become objectionable.

It is well known that anything which interrupts momentarily the intimate contact between the recording heads and the tape usually causes a corresponding momentary reduction in signal intensity. This interruption may be caused by an irregularity in the tape coating itself, but it is more often caused by dust and other contaminants. In some cases, a small dent in the tape can cause a drop-out. Almost without exception, a defect of this sort will cause a click or pop to appear in the recording due to the sharp drop in signal.

There is an important distinction between these noises and background noise in that, if a non-magnetic drop-out happens to occur in the erased tape, there will be no resultant noise pulse.

Modulation Noise Causes

The conventional modulation noise is caused by rapid fluctuations in signal amplitude. These are believed to result from local disturbances of the recorded magnetization in the tape due to the fact that the coating is composed of small, discrete particles rather than a continuous phase. Small structural defects in the coating, such as agglomeration and the like, and gross variations due to the coating process.

The noise contribution of the latter effect is usually quite negligible, because of the long wavelengths involved which represent sub-audible frequencies in most systems.

The particle-size effect seems to be rather inherent in the nature of magnetic materials, for even if a continuous magnetic medium such as a metallic plating were employed, the

(Continued on page 58)

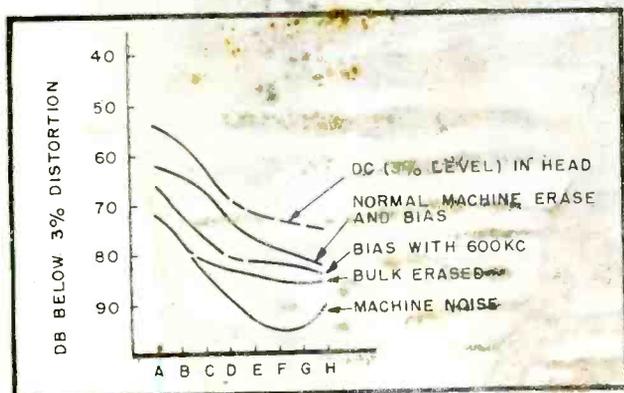


FIG. 1: PLOT OF various degrees of tape noise which obtain during several stages of erasure. A = 20-75 cps; B = 75-150 cps; C = 150-300 cps; D = 300-600 cps; E = 600 cps - 1.2 kc; F = 1.2-2.4 kc; G = 2.4-4.8 kc; H = 4.8-10 kc.



**MERIT DOES NOT
carry water
on both shoulders
MERIT SELLS**

its entire Production to
*Independent Electronic Parts
Distributors for re-sale to
Independent Service Dealers!*

MERIT

MERIT COIL & TRANSFORMER CORP.
4427 N. CLARK ST., CHICAGO 10, ILLINOIS

RADIO AND TV
SERVICEMEN

make more money with this



SECO Model 107
TUBE TESTER

3 complete tests in one handy instrument

Here's the tube tester every serviceman has been asking for! Designed for outstanding performance and accuracy—provides 3 important tests: Dynamic Mutual Conductance Test of all popular radio and TV amplifier tubes—Cathode Emission Test for all tubes by free point selector system—nationally accepted Grid Circuit Test developed and patented by Seco. Saves you valuable time—quickly pays for itself by justifiably culling and selling more tubes for you!

Completely self-contained in compact portable carrying case. Furnished with handy flip-chart for fast, easy tube set-up data. **\$139.50** net


SECO Write today for free literature
MANUFACTURING CO.
5015 Penn. Ave. So., Mpls., Minn.

COMPONENTS

CERAMIC-CAPACITOR REPLACEMENT KITS

THREE CERAMIC-CAPACITOR replacement kits, CK-2, CK-3 and CK-4, have been introduced by Sprague Products Co., North Adams, Mass.

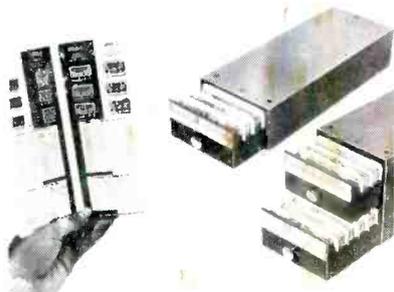CK-2 contains 150 *Cera-mite* disc capacitors with ratings from 5 mmfd to .01 mfd in a two-drawer miniature cabinet. CK-3 includes 75 units with ratings from 10 mmfd to .01 mfd in a one-drawer miniature cabinet. CK-4 contains three each of four different *Universal* ceramic capacitors.



SUBMINIATURE ELECTROLYTICS

SUBMINIATURE ELECTROLYTIC capacitors, *EE* and *EM*, designed for transistorized circuits and miniaturized low voltage *dc* equipment, have been announced by Astron Corp., 255 Grant Ave., E. Newark, N. J.

Units feature low leakage characteristics for minimum battery drain. *EE* has epoxy end fill; *EM* has a spun end with rubber bushing. Both are hermetically sealed. Available in voltage ratings of 1, 3, 6, 8, 16, 26 and 50.

Also now available is a miniature *mylar* metallized capacitor, *RQL*, said to be reliable at temperatures up to 125° without derating. Units are hermetically sealed.

Garage Door Operator



RADIO-CONTROLLED GARAGE-DOOR operator using a limited range low-frequency principle, which it is said eliminates the need for FCC licensing and the requirement for a commercial operators license for installation, repair or maintenance. (Genie Lift-A-Door; Alliance Manufacturing Co., Inc., Alliance, O.)

REPLACEMENT VIBRATORS

A LINE OF REPLACEMENT VIBRATORS, *Gold Label*, have been developed by P. R. Mallory and Co., Inc., 3029 E. Washington St., Indianapolis 6, Ind.

Units feature buttonless contact construction.



SILICON RECTIFIER CONVERSION KIT

A SILICON RECTIFIER conversion kit (M-500), said to provide additional B voltage (20 r in doubler) has been announced by Sarkes Tarzian, Inc., 415 N. College Ave., Bloomington, Ind.

Service notes describing application of the rectifiers as half and full-wave voltage doublers and in half-wave (line voltage) and step-up transformer circuits have been prepared by Sarkes Tarzian, Inc.

FLYBACK REPLACEMENTS

TWO REPLACEMENT flyback transformers, *EFR* 196 and *EFR* 197, for use in Motorola TV receivers, have been announced by Rogers Electronic Corp., 49 Bleecker St., New York 12, N. Y.

EFR 196 replaces Motorola part number 24K736488; *EFR* 197 replaces part number 24C736487. Both units are packaged in hermetically-sealed plastic containers.

Parts Show Gavel Ceremony



CHARLES GOLENPAUL, new president of the Electronic Industry Show Corporation, accepting gavel of office from outgoing president, Wilfred L. Larson. Golenpaul, vice president of Aerovox Corp., will serve for a year, heading operations for the 1958 Electronic Parts Distributors Show to be held May 19-21 in the Conrad Hilton Hotel in Chicago.


Tube-Transistor News

(Continued from page 46)

which makes possible the use of a deflecting yoke having high deflection sensitivity and permits deflection of the beam through the wide deflection angle with only slightly more power than is required to scan a tube with a 90° deflection angle.

Another design feature of the 24AHP4 is its electron gun, which is of the straight type designed to minimize deflection distortion and to eliminate the need of an ion-trap magnet.

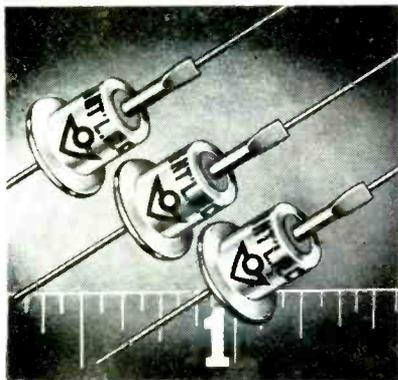The 24AHP4, of the low-voltage electrostatic-focus and magnetic-deflection type, has a spherical filter-glass faceplate, an aluminized screen measuring 21 7/16" by 16 1/2" with slightly curved sides and rounded corners, and a minimum projected screen area of 332 square inches.



SILICON DIODES designed as alternates for germanium 1N91, 1N92 and 1N93 diodes. (International Rectifier Corp., El Segundo, Calif.)

TV Antennas

(Continued from page 37)

to the ridge of the roof by means of a roof mount combined with an anchoring system.


Strap Standoff



(Left)
UNIVERSAL STRAP STANDOFF that accommodates Nos. 8 or 9 standard wood screw eyes. Features a buckle which utilizes a double-seated thread lock to exert two separate tensions on the wood screw as it's tightened. This progressively increases the pressures of the outer thread and inner thread locks. Buckle is made of heavy-gauge zinc-coated steel with electro-galvanized or stainless steel strap. (Imp: JFD Manufacturing Co., Inc., 6101 16th Ave. Brooklyn 4, N. Y.)

(Right)
INDOOR TV ANTENNA developed for mounting on back of console, table model or portable, which can be concealed when not in use or extended when desired. Supplied with Twin-X cable. Features two 4-section staffs which can be moved in any direction via a 360° swivel adjustment. (Model PT-R [Tuk-It Hideaway]; Snyder Manufacturing Co., 22d and Ontario, Philadelphia, Pa.)

Indoor TV Antenna

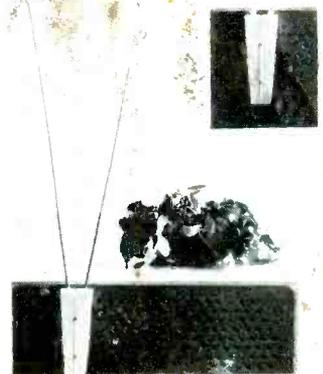


STOP CB WITH C-D

*CALL BACKS CAN BE STOPPED. Insist on "CORNELL-DUBILIER" when you buy Ceramic Capacitors. They're the finest—yet cost no more than the run-of-the-mill grades. That's because C-D Ceramics are made, from start to finish, in one huge C-D plant devoted to ceramic capacitor fabrication. Every ingredient, every operation is scrupulously supervised and controlled by specialists. A C-D Ceramic is truly "the ceramic with the Million Dollar Body". Ask your Distributor for Catalog 616 and Extract 200D-3C or write direct to Dept. S-107, Cornell-Dubilier Electric Corp., South Plainfield, New Jersey.

stop call backs...insist on
CORNELL-DUBILIER CAPACITORS

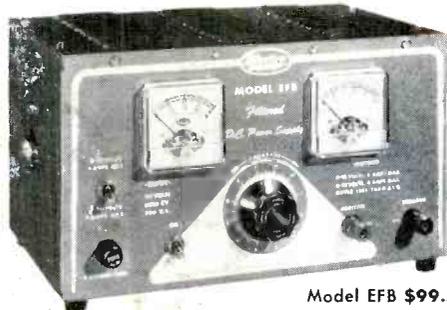SOUTH PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER & CAMBRIDGE, MASS.; PROVIDENCE & HOPE VALLEY, R. I.; INDIANAPOLIS, IND.; SANFORD, FUGAY SPRINGS & VARINA, N. C.; VENICE, CALIF.; & SUBS: THE RADIART CORP., CLEVELAND, OHIO; CORNELL-DUBILIER ELECTRIC INTERNATIONAL, N. Y.



Model EFB \$99.50 Net

New! Super-Filtered DC for transistor design work

Less than 15 millivolts AC ripple up to max. load

DC Power... for precision laboratory and design work

- Dual range — 0-32 volts up to 4 amperes
0-16 volts up to 8 amperes
- Internal Impedance: 4 ohms at 32 volts
2 ohms at 16 volts
- Smooth voltage control with continuously variable carbon brush-type auto transformer
- Long-life selenium rectifiers—patented heat sink cooling

Model EB dual range DC Power Supply, same as above except 5% ripple.



Model D-612T \$44.95 Net

First to service all 3:

1. Transistor and hybrid auto radios
2. Transistor portable radios
3. Tube auto radios

Improved D-612T... better than ever — same low price

- Dual range — 0-8 volts, 0-16 volts, continuously variable
- Up to 22½ volts available for transistor portable radio loads
- 1/10% AC ripple for low current loads — ½% AC ripple up to 5 amperes
- 10 amperes continuous duty up to 12 volts
- 20 amperes intermittent service

ELECTRO PRODUCTS LABORATORIES



4501-V North Ravenswood,
Chicago 40, Ill.

Canada: Atlas Radio Ltd., Toronto



See your jobber or
send today for new bulletins

47589

RF Amplifier TV Stages

(Continued from page 35)

current between the plate and screen. Pentodes are about 3 to 5 times noisier than the same tube connected as a triode.

Pentode operation in *vlf* tuners function the same as pentode operation in any other *rf* amplifier application, except that at high frequencies, the effect of tube parameters upon circuit operation is exaggerated.

Sharp cutoff pentodes are also desired for tuners, again because of the available simple *agc* system voltage as found in inexpensive, low B+ receivers.

Typical tuner pentode amplifier tubes used today are the 3 and 6BC5, the 3 and 6CB6, and the 3 and 6CE5.

Parameters Affecting Cascode and Pentode Operation

Several important circuit and tube parameters affect both cascode and pentode amplifier performance; input impedance and cathode-lead inductance, contact potential, and cathode interface resistance.

A wide variation of input impedance in a tuner-input stage (*rf* amplifier) with *agc* variation causes the antenna-matching device to have various matching impedances looking towards the antenna from the input-tube grid. These variations in matching impedances cause various mismatches (and thus various voltage standing-wave ratios) on the antenna transmission line which gives rise to ghost images on the TV screen. These effects can be reduced by maintaining a very low grid-to-cathode capacity and low lead-inductance of the input section of the tuner *rf* amplifier.

The antenna-input matching device to the *rf* amplifier grid is usually either a balun (transformer type circuit which converts 300-ohm balanced input to single-ended unbalanced 50-ohm output) or a transformer. The purpose of each device is the same, i.e., to match a balanced 300-ohm antenna input to an unbalanced output of different impedance feeding the *rf*-amplifier grid circuit. This device should not only provide a good match to the antenna transmission line over a wide frequency range (54 to 216 mc for *vlf*); but some selectivity in combination with the input tuned circuit, and possibly some voltage gain. The typical antenna balun has a 300-ohm balanced input and a 50-ohm unbalanced output. A device (*pi network*) is usually placed between the balun output and the grid of the *rf* amplifier to raise the impedance of the tuner-input network looking in from the *rf* amplifier grid.

The antenna transformer is a simpler matching device that requires no *pi network* following it, because the transformer output impedance is high. The matching transformer does not have a constant input and output impedance over the *vlf* bands and therefore is more critical in respect to transmission line matching. Thus, *rf*-amplifier tubes, which have wide variations of input impedance, should not be used with matching transformers.

It has been found that pentode *rf* amplifiers have a wider variation of input impedance than do cascode stages with the same change in *agc* voltage.

Input impedance of a stage is composed ordinarily of a capacity in parallel with a resistance appearing between grid and cathode of the stage. The value of the input capacity is fairly independent of frequency and is determined principally by tube interelectrode capacities and stage gain. The input capacitance will be minimum when the impedance in the plate circuit of the stage is zero and maximum when the plate impedance is very high. Also since *rf*-amplifier stage gain varies widely with the applied *agc* voltages, the tube-input capacitance will vary somewhat with *agc* and thus

cause varying loading upon the tuned input circuit, which consequently has a degenerative or regenerative effect upon the incoming signal at various frequencies within the pass band of the tuner. This results in a distortion or tilt of the curve of gain versus frequency.

In pentodes, the variation of input capacitance may be as much as 3:1 from zero bias to cutoff bias, while in triodes the input capacitance variation may only be 2:1 from the zero bias to cutoff condition. This phenomenon is true at any frequency, but it is especially important at *ohf* where the tube-capacity parameters form a large part of the tuned circuits. Thus pentodes will have a larger variation of the capacitive-reactive component of its input impedance than do triodes under similar conditions.

Service Notes

(Continued from page 29)

that the antenna will pick up less of the incoming signal.

An *if* transistor having exceptionally high gain may cause regeneration on weak signals. The correction for this difficulty is to interchange the two *if* transistors or to replace if only one *if* transistor is used; realignment is advisable after any change of transistors in the *if* circuit.

If a type 2N140 transistor is used in place of a type 2N139 transistor, regeneration may occur; one should check for type of transistor.

Regenerative squeal has been found to be due to high internal battery resistance; a new battery will correct the trouble. In RCA model 7-BT-9 the size of the first filter capacitor (C_{15}) was increased from 25 to 45-mfd and later, two 45-mfd capacitors in parallel were used to eliminate squeal.

High-resistance riveted connections at battery leads on printed board can also cause regeneration; this can be overcome by soldering the rivets to the printed wiring.

Still another source of trouble are high-resistance connections at chassis mounting spacer. This condition is evidenced by a change in the frequency and intensity of the squeal when the tuning capacitor mounting screws are first loosened and then tightened. The spacer and the mounting screws are in the tuning capacitor ground circuit and electrolytic action between the copper wiring and the die-cast zinc spacer results in corrosion and high resistance joints. A 3-point wire jumper should be soldered between the three copper areas at the tuning capacitor mounting screws.

In cases of *no signal* in a transistor radio, the first step is to check battery voltage with the set turned on. New batteries are rated at 9 v, but transistor radios will operate on batteries with outputs as low as 6 v. If the battery is okeh, the terminal voltages should be checked. There can be short-circuits in transistor radios just as in any other radio. One significant difference is that in a transistor radio, there is insufficient power to burn out a resistor. Transistors have no filaments to burn out, but lead wires can be broken. Battery leads and phone jack leads are the most likely source of such trouble. Transistors themselves should be the last item suspected.


If a quick check of terminal voltages indicates that a short-circuit is not the cause of trouble, it is suggested that signal injection be used to localize the defect as being in one specific stage. There can be breaks in printed wiring which would cause signal stoppage; but any such breaks, which would not materially affect terminal voltages, are highly unlikely.

†Based on service notes prepared by the RCA Service Co., Inc.

LEARN MORE! EARN MORE!

WITH H. G. CISIN'S TV SERVICE BOOK

New! Guide To BASIC ELECTRICITY

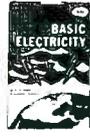

Learn electricity at home this easy way, without time-wasting correspondence. Information you need and want is at your fingertips, clearly explained and illustrated. First two vols. just off the press. Send for these two new books at once. We guarantee you will be more than satisfied.

Vol. 1 (No. E1) 50c
Vol. 2 (No. E2) 50c

TV TUBE LOCATORS Vol's 1 & 2



TROUBLE INDICATING TUBE LOCATION GUIDES for thousands of TV models from Admiral to Zenith. Tell which tubes to replace to cure every trouble due to tube defects. Vol. 1 covers 1947 to 1953 models. Vol. 2, just off press, covers 1954 to 1957 sets including newest portables.

Vol. 1 (No. K1) \$1.50
Vol. 2 (No. K2) \$1.50

ABC of COLOR TV



This easily understood new book takes the mystery out of Color TV. Fully illustrated. Covers basic color principles, color transmission and reception, the color signal, color tubes. Helps you cash in on this profitable new field.

No. R1 \$1

New Edition RAPID TV TROUBLE SHOOTING METHOD



Novel TV servicing method enables a novice to diagnose TV troubles as rapidly as an expert. Pix, raster and sound troubles are listed and given code numbers. When combined they tell exact location of trouble.

No. T1 \$1

TV CONSULTANT



The TV serviceman's silent partner. New rapid methods of pinpointing faults. Tells WHAT to do and HOW to do it. Includes UHF, COLOR and use of test instruments. NO MATH. NO THEORY. NO FORMULAS. Just practical servicing instructions on all types of sets.

No. L1 \$2

SHOOT TV & RADIO TROUBLE FAST



Quickest radio & TV trouble shooter locates radio & TV faults in record-breaking time, regardless of make or model. Section on printed circuits. Only book containing radio & TV trouble tracing in one volume.

No. T2 \$1.50

RCA & ADMIRAL TROUBLE INDICATING TV TUBE LOCATION GUIDES




These two books contain the most complete compilation of RCA and ADMIRAL tube location guides ever published. The RCA volume includes all TV models from the earliest 1947 sets to latest models, more than any 5 ordinary tube chart books.

The ADMIRAL book includes over 1500 Admiral TV models from the earliest sets to the newest 1956 models. Also contains PICTURE GUIDE to TV tube troubles.

RCA GUIDE—No. A1 \$1 ADMIRAL GUIDE—No. M1 \$1

TV PIX GUIDE

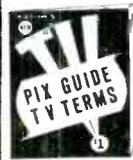

Pictures show oft-recurring faulty TV conditions. Probable causes are explained and logical cures suggested. A second section clearly defines and explains technical TV terms. Over 70 illustrations.

1957 Edition

No. G1 \$1


TV DOCTOR



Just the info needed to start TV servicing. Includes: How to recognize and remedy TV troubles; How to replace defective tubes including Pix tube; Easy TV trouble checks; Color TV; Antenna Know-How; How to combat interference, ghz's and snow; VHF installation and servicing; How to read schematics and much other valuable TV info for beginners.

No. D5 \$1

TV TUBE SUBSTITUTION GUIDE

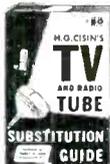

Tube replacements for TV & radio sets. All fit same sockets and need NO CHANGES IN WIRING. Book also contains complete data on PICTURE TUBE replacements, many directly, others with only slight changes.

No. S1... Only 50c

TV TROUBLE TRACERS

Six volumes, different TROUBLE INDICATING TUBE LOCATION GUIDES in each. Hundreds of popular TV models. Each vol. has over 70 illustrations. 40 most common TV troubles illustrated.

Vol. 1 (No. TT1)—Older sets
Vol. 2 (No. TT2)—'52-'53 sets
Vol. 3 (No. TT3)—'53-'54 sets
Vol. 4 (No. TT4)—'54-'55 sets
Vol. 5 (No. TT5)—'55-'56 sets
Vol. 6 (No. TT6)—New PORTABLES & '57 RCA sets

Each Volume 50c

FREE: \$2 WORTH OF BOOKS—FREE—with every purchase of entire CISIN TV LIBRARY of 19 valuable TV service books listed above. Regular Price \$16.50—yours for only \$14.50!

If Jobber is out of stock mail "No Risk" Trial Order Coupon 5-day Money Back Guarantee


H. G. CISIN, Dept. S-39, AMAGANSETT, N. Y.

Enclosed find \$..... RUSH POSTPAID following books:

K2—\$1.50 A1—\$1 T2—\$1.50 TT2—50c
 K1—\$1 M1—\$1 T1—\$1 TT3—50c
 L1—\$2 G1—\$1 S1—50c TT4—50c
 D5—\$1 R1—\$1 TT1—50c TT5—50c
 E1—50c E2—50c TT6—50c

Enclosed find \$14.50. Send entire CISIN TV LIBRARY listed above.

Name
Address
City Zone State

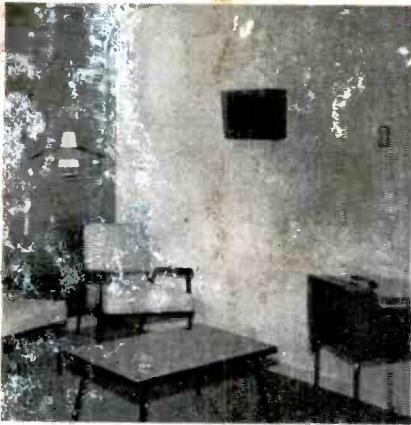

GUEST ROOM at the Trenholm Motor Lodge, near Rochester, N. Y. equipped with a tile-type surface-mounted speaker, five-program selector and off switch, with individual room volume-control switch.



COMPLETE SOUND SYSTEM recessed in one cabinet in the wall behind the reception counter of the Trenholm Motor Lodge. Note bank of four individually-controlled AM-FM radio receivers. At the left of the counter is a paging microphone.



INSTALLING TUNER-AMPLIFIER in sound-system cabinet used in Trenholm system.

Motel Sound-System Installation

by L. A. RANDALL

Special Products Div., Stromberg-Carlson,
Division of General Dynamics Corp.

THE ADVENT OF FLEXIBLE SOUND SYSTEMS capable of providing multiprogram channel music and paging facilities has expanded the uses of such networks. Today, such systems have been installed in a wide variety of places, including a growing number of motels. Just south of Rochester, New York, near a New York State Thruway interchange is an interesting example of a recent new-look motel sound-system installation which provides five program channels (four radio and one record changer) to each of 44 guest room and 9 public-room speakers, or group of speakers, as in the restaurant. Voice paging to the public rooms and parking lot speakers originates at the registration desk from the microphone. Operation of a microphone switch provides direct current to a relay that cuts off all program lines to the public room speakers, and connects the output of the paging amplifier to all the public room speaker lines. To avoid music in the parking lot the speakers are connected directly to the output of the paging amplifier.

In the preliminary stages of developing a sound package of this type, careful planning in selecting equipment and an analysis of the installation problems are necessary. Those handling sales must consult with the installation-service crew, whose experience regarding pitfalls that might be encountered, and suggestions concerning the best equipment to provide the required services, will enable an accurate estimate to be prepared and will gain customer confidence.

The installing crew can make a better estimate of the cost of their portion of the project after they have reviewed the plans and specifications. They can determine adequate speaker

coverage, location of antenna conduit for lead-in, space required at the equipment cabinet location for proper installation and service, ventilation and possible future expansion. They can review the input and output conduit and offer suggestions for terminating the conduit in the floor beneath the equipment cabinet, or at the top of the cabinet, for an installation that is neat, rather than one with terminal boxes at the rear of the cabinet with lossy connections due to loose and unsightly flexible cables.

In the Rochester-area installation all cabinet-assembly equipment was analyzed for technical and physical features. An AM-FM radio tuner-amplifier² was selected because of its wide FM frequency response (20 to 20,000 cps) and AM response of 20 to 7500 cps. Other features of this unit are an interstation whistle filter providing 29-db rejection at 10 kc. Antenna connections include FM (72 to 300 ohms) for use with a dipole antenna and AM (high impedance) for a short antenna. In addition to tuning and selector controls, the unit has a bass control providing 15-db boost and 20-db droop at 30 cps and a treble control which provides 12-db boost and 20-db droop at 10,000 cps. Also included in this combination tuner-amp is a loudness control that gives gradual increasing bass and treble boost as loudness is decreased to compensate automatically for normal hearing deficiencies at low volume levels so essential in a motel installation.

Drift has also been found to be a very important factor affecting quality of reception, particularly where no attendant is available to retune the radio section as in a motor court system. Accordingly, this fact was considered, too, before the tuner-amp was selected. The model chosen has been designed to minimize drift so that no retuning is necessary. Also the unit meets RETMA (now EIA) specifications and the proposed FCC regulations to prevent interference with other services using the air channels.

Other tuner-amplifier factors that had to be studied, were output regulation which could provide absolute

(Continued on page 60)


¹Trenholm Motor Lodge.

²Stromberg-Carlson SR-405.

TO BRING OUT THE BEST
IN EVERY HI-FI SYSTEM...



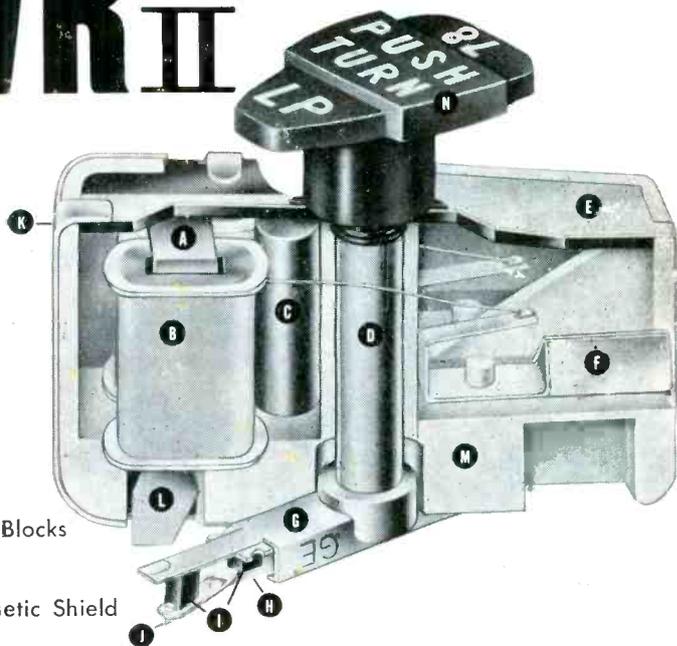Sell and install the NEW G-E VR_{II} cartridge



- Ⓐ Highly permeable laminations
- Ⓑ Hum-cancelling wound coils
- Ⓒ Alnico V Magnet
- Ⓓ Pivot Post
- Ⓔ Electrostatic Shield
- Ⓕ Plug-in Terminals
- Ⓖ "T"-Channel
- Ⓗ VR II Clip-In-Stylus
- Ⓘ Special G-E Damping Blocks
- Ⓝ Stylus Jewel
- Ⓚ Mu-Metal Electromagnetic Shield
- Ⓛ Magnetic Pole Pieces
- Ⓜ Plastic Body
- Ⓝ Triple Play Knob

Only a genuine G-E VR_{II} gives your customers all this:

New Full-Range Reproduction—General Electric's new VR II makes faithful reproduction from 20 through 20,000 cycles a glorious reality!

New 4-Gram Tracking Force—Lateral compliance has been extended to 1.7×10^{-6} cm per dyne, permitting a tracking force of only 4 grams to minimize record and stylus wear.

Instant Clip-In-Tip Stylus—Stylus replacements can be made at home without removing cartridge from tone arm. There's no need to discard an entire dual assembly when only one tip is worn.

New Electrostatic Shielding—New shield prevents pickup of electrostatic interferences and hum; also

grounds stylus assembly so that electrostatic charges cannot build up from record surface.

New Lightweight Construction—Reduced in size and weight—with new stylus guard, terminals and knob—the General Electric VR II will withstand continued use under the most exacting conditions.

The new G-E VR II cartridge is being announced to the public in a heavy schedule of advertisements now running in major Hi-Fi and general magazines. Do you have enough stock to meet the demand?

Specialty Electronic Components Dept., Section HFS10, West Genesee Street, Auburn, N. Y.

In Canada: Canadian General Electric Company, 189 Dufferin Street, Toronto 3, Canada.

Progress Is Our Most Important Product

GENERAL  ELECTRIC


Ask "The Man on the Roof" why he prefers

South River



How valuable is a Serviceman's time? 5¢ a minute?
7¢ a minute? . . . 10¢ a minute?

South River's New Ratchet Type Chimney Mount Saves 10 Minutes Per Installation!

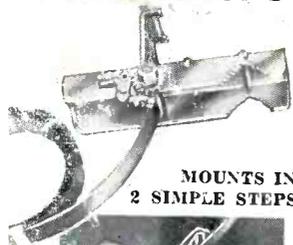

MOUNTS IN
2 SIMPLE STEPS

1. Encircle chimney with banding and thread through slotted shaft.



2. Tighten banding with wrench.



RATCHET GUY WIRE TIGHTENER

Eliminates turn-buckles! Fastens to wall or roof with screws. Extra space between tightening shaft and base permits large tightening capacity. Same sturdy construction as ratchet chimney mount.

It's the fastest, simplest, most convenient ever manufactured!

Mounting is factory assembled with band attached. No assembly of eyebolts, banding, banding clips, nuts, etc., is necessary for chimney mounting.

South River's New Ratchet Type Chimney Mount is 8 WAYS BETTER:

1. Heavy gauge steel construction.
2. Banding naturally unwinds for easy mounting. No troublesome watchspring effect!
3. Embossed and welded for extra rigidity and strength!
4. Ratchet of aircraft type aluminum, forged and heat-treated for maximum toughness and strength.
5. Fine ratchet teeth insure positive tightening of banding.
6. Banding is factory assembled to mounting.
7. Zinc plated, golden iridite finish.
8. Available with galvanized banding (Model RT) or stainless steel banding (Model RT-ST).



HIGH STRENGTH ALUMINUM GUY CABLE, HIGHLY CORROSION RESISTANT

Special 56S Alclad alloy. 7 strands, 17 gauge specially tempered and normalized. Special tight weave. Will not rust or stain. Specifically for guying use. Breaking strength: approx. 500 lbs. pull. Boxed in 100 ft. coils or ten 100 ft. coils, interconnected, 1000 ft. to box.

South River

METAL PRODUCTS CO., INC.

South River, New Jersey

PIONEER MANUFACTURER AND OUTSTANDING PRODUCER OF THE FINEST LINE OF ANTENNA MOUNTING ACCESSORIES

Audio

(Continued from page 51)

inevitable magnetic domain structure would result in some considerable degree of graininess. This fact has been borne out by experiences with metallic wire, the noise problems of which are well known.

It is in the microstructure of the magnetic coatings that the greatest strides have been made in the reduction of noise in magnetic tapes.

Early tapes manufactured in this country employed a paper base

which, owing to the porous and fibrous surface, were a rather poor support for a magnetic coating. The coarse microstructure of coatings on paper gave rise to high modulation noise level.

The next significant advance came with the introduction of plastic film base. Early acetate base tapes with unoriented coatings were some 10 db improved over the paper tape. It is interesting to note that noise in the highest frequency bands actually increased in going from paper to plastic base, presumably because of the im-

proved head contact and playback resolution.

Since about 1950, particle orientation has been employed to reduce the modulation noise level and increase the sensitivity of magnetic tape. The decrease in modulation noise averages about 5 db for oriented tapes.

Thus far we have dealt only with modulation noise which appears when signals are recorded on the tape. The problem of background noise is perhaps of much greater concern in magnetic recording. In the absence of any recording on the tape, noise in the system is, of course, much more noticeable.

The best of current theories on tape background noise indicates that it is due principally to the random orientation of the spontaneously-magnetized domains in the tape. In the usual case, these domains are actually the particles of magnetic oxide in the coating. There is much experimental evidence to corroborate this theory.

Erasure Problems

The matter of preventing the tape from subsequently becoming magnetized requires some considerable care. The most frequently encountered troubles involve residual magnetization in the heads and guides. These are well known offenders, and the practice of periodic demagnetization of heads and other machine parts is well established in the industry. However, for the highest quality work, it would be well to check these very carefully.

One quick test for a magnetized playback head is to turn up the playback gain to maximum and tap the head gently with the fingernail, or the wooden part of a pencil. If a click is heard in the play channel, the head is magnetized and is responding to magnetostrictive modulation of its own field.

Another quick test for playback head magnetization is to play a paper leader tape across the head and listen for magnetostrictive noise as described above. Other parts of the machine can be tested by passing a few inches of bulk-erased tape over the part and comparing the relative noise levels. By application of these tests, it is often discovered that the method being used to demagnetize heads and guides is not accomplishing its purpose, and other techniques can be tried.

The problem of adequately erasing tape and preserving the zero signal portions in a neutral state during recording is not easily solved. This is illustrated in Fig. 1 (p. 51). The same

GET YOURS NOW!



ULTRA-LINEAR speaker systems said to feature room-balanced design, permitting installation either in a corner or flat against a wall. (University Loudspeakers, Inc., 80 South Kensico Ave., White Plains, New York.)

standard tape¹ with plastic base and oriented coating was used throughout, and the conditions of erasure of the tape varied to give the results plotted.


The tape was first bulk erased and played on the machine to determine the *lowest* background noise level. The tape was then erased and biased on a properly adjusted commercial recording machine (with no input signal and the gain turned back to zero) and the noise level was seen to rise about 10 db.

Upon further investigation of this phenomenon, it was determined that both 60-cycle and 100-ke bias frequency were recorded on the tape. The 60-cycle recording was audible and could be easily verified by speeding up the tape. Incidentally, the application of only the erasing function (recording head disconnected) also resulted in the recording of some 60-cycle signal. It was suspected that the 60-cycle signal was coming through as a modulation on the bias-erase signal.

Recent advances in the art of video recording indicate that much shorter wavelengths can be recorded than formerly supposed. Moreover, short-wavelength magnetization may actually be recorded in the tape without necessarily being detected because of limitations in the reproduce head.

In order to verify the fact that the 100-ke bias was being recorded, an external bias source of 600 kc was also tried. This lowered the noise level by some 4 db, indicating that some improvement could be gained by going to a higher bias frequency. Some 60-cycle signal was recorded, however, in spite of precautions taken in the
(Continued on page 63)

¹Scotch No. 111.

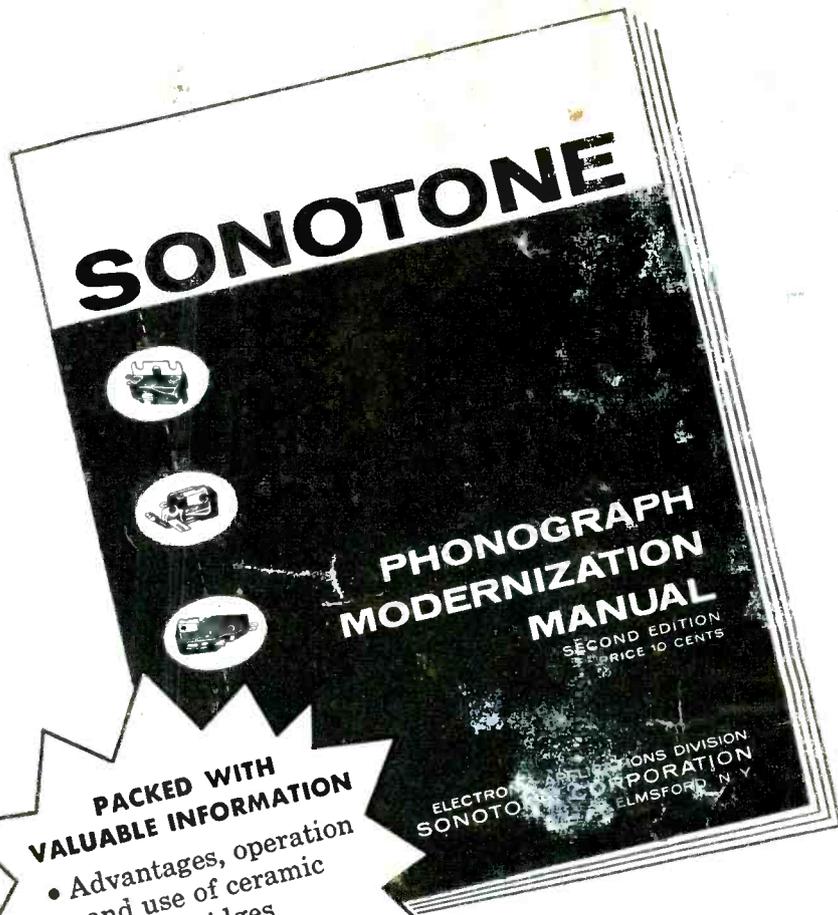

PACKED WITH VALUABLE INFORMATION

- Advantages, operation and use of ceramic cartridges
- Replacement data

IT'S FREE!

This handy booklet will help you make proper and intelligent use of the amazing new Sonotone Ceramic Cartridges. It will enable you to make profitable replacements, modernizing your customer's phonograph. It will give him extra satisfaction and bring you prestige.

Be sure to get your up-to-date manual.

Just fill in the coupon and mail to Sonotone. Attach to a postcard if you wish.

SONOTONE® Corporation

Department CS-107
Elmsford, N. Y.

Please send me, without cost or obligation, a copy of the newly revised "SONOTONE Phonograph Modernization Manual."

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Motel Sound-System Installation

(Continued from page 56)

stability with any combination of resistive, capacitive or inductive output loading, since the number of guest and public room speakers in operation at any one time can vary greatly. The output impedances must be such as to provide the correct output tap for the distribution lines so that the speaker-line transformer will draw the correct amount of audio power to operate the speakers at the desired level.

Experience has proved that on an average about 50% of the guest room speakers are in use at one time and as a rule the speakers operating are equally divided between the program channels provided. On this basis, since 50% of the 44 guest room speakers equals 22 and five channels are involved, the average number of guest speakers on any one channel at one time is 4 or 5. When highly efficient speakers and line transformers with minimum loss are used, the maximum allowable audio power drawn by a guest room speaker is approximately $\frac{1}{4}$ watt; this wattage has been found to be loud enough for the room, but not too loud to annoy those in adjoining rooms. Therefore, with an average of five guest room

speakers operating at one time, $\frac{1}{4}$ watts minimum has been found to be adequate for each program channel. The tuner-amplifier chosen has a 12-watt (undistorted) output, providing ample audio power for the guest rooms, plus the public space speakers. When special events are broadcast, such as important news events, political conventions, world championship boxing or world series ball games, and the speaker load on any one channel would exceed the average, two or more radio tuners can be tuned to the same broadcasting station and the speaker load divided among the distribution channels.

To secure the $\frac{1}{4}$ -watt power at each guest room speaker or a little more audio power for the public-room speakers the following computations can be applied:

$$\frac{\text{Ohms at the Amplifier}}{\text{Ohms at the Speaker}} \times \text{Audio Output} = X$$

In this motel project the 16-ohm output tap of the tuner-amplifier and the 625-ohm primary tap of a line

³Stromberg-Carlson TR-13. ⁴Stromberg-Carlson AU-58.

transformer³ were selected. From the foregoing equation, we have:


$$\begin{aligned} 16/625 \times 12/1 &= X \\ 192/625 &= X \text{ or } .307 \end{aligned}$$

Two 25-watt amplifiers⁴ were selected for use as the phonograph and paging amplifiers. Using the 16-ohm output tap and the 625-ohm primary tap of the speaker transformer, and the amp-speaker formula, the speaker draw will be found to a little over .60 watt. The difference between the .30 watt drawn from the tuner-amplifier is 3-db, and hardly noticeable, but even this difference can be adjusted by an input gain control on the amplifier.



The equipment cabinet assembly has been supplied with a monitor speaker panel with meter and selector switches so that the output of each program channel can be checked and monitored for volume and quality before individual switches are connected to send the programs to the channel transmission lines. Below this panel were located four AM-FM tuner-amplifiers, a record changer, and phono and paging amplifiers; the paging amplifier has been equipped with a low-impedance microphone input transformer. At the bottom of the cabinet is a power on-off panel with indicating lamp.

Included in the assembly is a timer that turns the power to the system on-off at times designated by manage-

(Continued on page 62)

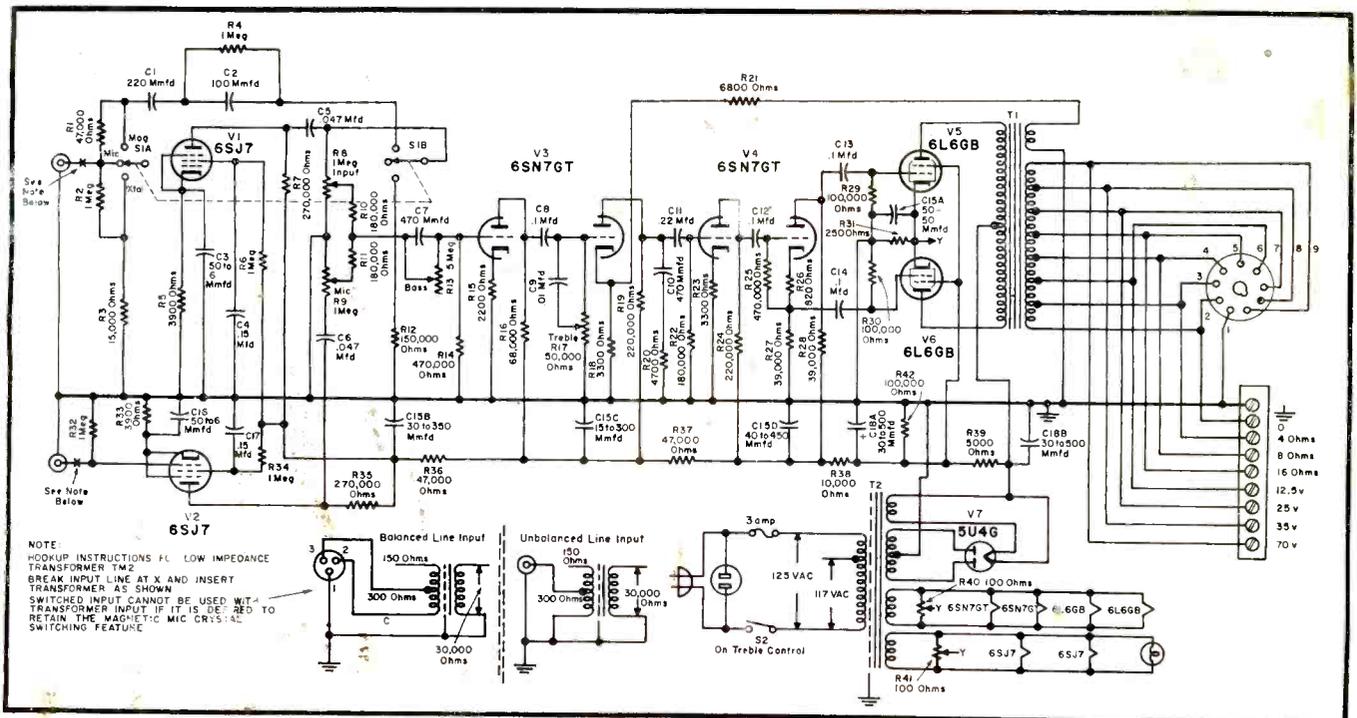

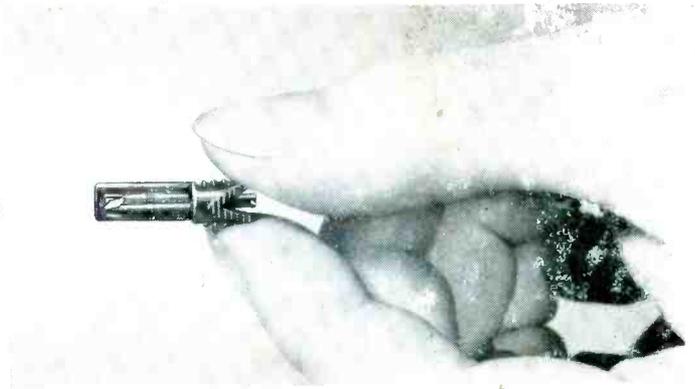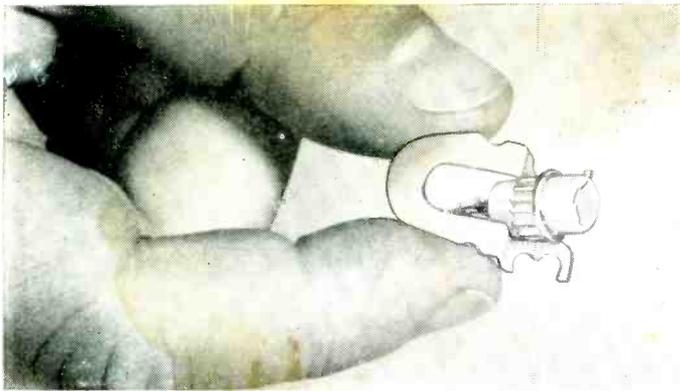SCHEMATIC OF STROMBERG-CARLSON amplifier included in Trenholm sound-system installation.



FOR CONTINUING PROFITS, INSTALL

Electro-Voice® POWER-POINT®

ONE Installation Instead of Many WITHOUT a Drop in Cartridge Replacement Business!

•
NO Problem of Obsolescence!

•
NO Need to Invest Heavily in Burdensome Inventory!


•
THREE POWER-POINT Mounts, SEVEN Color-Coded POWER-POINT Needle-Cartridge Units—That's ALL YOU NEED!

Put the profit back in cartridge-replacement business but eliminate the headaches involved in old-fashioned phonograph servicing. Install a POWER-POINT just ONCE and let your CUSTOMER install replacement cartridge-needle units! *You get the profit without problems!*


POWER-POINT (U.S. Patents D108347, 2793254) is the unique miniaturized unit containing BOTH a fresh ceramic cartridge and jeweled playing tips. You sell a POWER-POINT for less than the cost of a separate cartridge or comparable needles alone! Most Models, \$3.95 list.

Only $\frac{3}{4}$ " long and less than $\frac{1}{2}$ " in diameter, POWER-POINTS are color-coded, blister packed in plastic to keep them fresh, clean and easy to handle.

These are the POWER-POINT mounts:

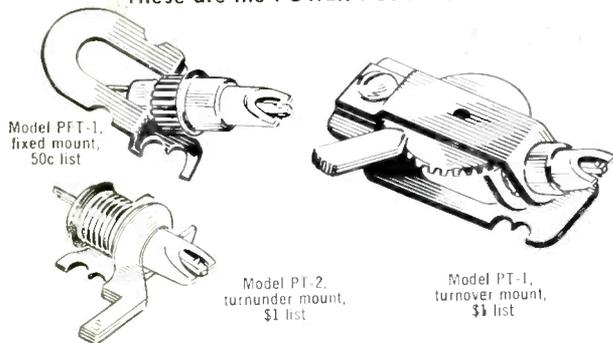

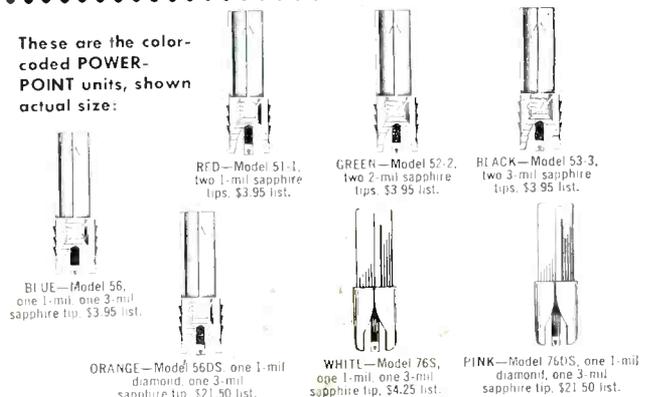These are the color-coded POWER-POINT units, shown actual size:



THE MARKET IS BIG: MORE THAN TWO MILLION NEW PHONOGRAPHS USE POWER-POINTS AS ORIGINAL EQUIPMENT! The Profits are BIG—and E-V helps you sell with fact-cramped folders and colorful envelope-stuffers. Write Dept. S-710 and ask for Bulletins No. 223 and 225.

CALL YOUR E-V DISTRIBUTOR TODAY!

Electro-Voice

ELECTRO-VOICE, INC., BUCHANAN, MICHIGAN

Export: 13 E. 40th St., New York 16, U.S.A. Cables: ARLAB

Time for
REPLACEMENT?



Specify

**OXFORD
SPEAKERS**

Why gamble when you can be assured of the finest line of replacement speakers . . . OXFORD. Now specified by more manufacturers of original equipment than ever before during our more than twenty-five years of producing the best speakers. Your choice . . . from 2" to 15" with guaranteed faster delivery . . . better service . . . more extensive and complete line.

TIME for REPLACEMENT . . . specify OXFORD SPEAKERS . . . you'll be glad you did.

OXFORD Components, Inc.

Subsidiary of Oxford Electric Corp.

354 West Monroe Street • Chicago 6, Illinois

In Canada: Atlas Radio Corp., Ltd., Toronto

Export: Roburn Agencies, New York City



Motel Sound System

(Continued from page 60)

ment, so that under ordinary conditions the system requires no attendant. A small-power supply provides 24 v dc to energize the paging relay, equipped with a suppressor across the coil terminals to reduce objectionable clicks in the public-room speakers when the relay is energized by the paging microphone.

The paging relay has sets of break-make spring combinations. In normal or non-operative position, the make

contacts to swingers are connected to the output of the program amplifiers; the swingers are connected to the individual public-room transmission lines, and the make springs are connected to the output of the paging amplifier. In non-operative position the output of the program sources is connected to the channel distribution lines. In operative position the program source is broken and the distribution lines connected to the output of the paging amplifier.

Internal wiring features the use of twisted-pair shielded with overall insulation for balanced line operation.

Separate output terminals are provided for guest room and public room transmission lines.

Antenna Systems

Another problem in any installation is the choice of the antenna and its location. Neither the architect nor the owner want the antenna on the roof, normally the location for strongest signal pickup, claiming such an installation is unsightly. However, the fact that the right location for an antenna is a very important link in providing quality and noise-free reception must be stressed, with fact, of course. Both architect and motel operator can be convinced that only a rooftop-installation is the logical approach.

In this project an omnidirectional FM antenna and a 50' flat top for AM pickup were located on the roof and a lightning arrester grounded to a cold water pipe. An antenna transformer, as recommended by the antenna manufacturer, was located in the flat-top antenna; leadin from both antennas was RG-59/U coax.

Leadin from the FM section was connected to the FM terminal at the tuner-amplifier and the shield to ground on the chassis. The flat top leadin was connected to the hi-antenna connection on the chassis through a 25-mmfd capacitor, the shield being brought to the chassis ground. Six twisted pair cable (one spare) were installed for program lines to the speakers.

Guest room speakers⁵ were surface mounted and equipped with a six-position (5 on, 1 off) selector switch and volume control; both the selector switch and volume control rotate 360°. The speaker cabinet, of the tilt-type is equipped with a cone speaker⁶, having an 8" cone and a frequency response of 55 to 13,000 cps. The line transformer is rated at 2.5 watts with 2 and 8-ohm tapped secondary and a tapped primary in steps of 3 db at 312, 625 and 1250 ohms.

Public space speakers using 8" cone units are surface mounted, with a frequency response of 45 to 14,000 cps.

In the lobby, a floor-standing cabinet employing an *acoustical labyrinth* is used. The speaker, a coax type⁷, has a 12" low-frequency radiator and a 2" tweeter with a dividing

⁵Stromberg-Carlson RS-81D. ⁶Stromberg-Carlson BC-27.

⁷Model RF-471. ⁸Model TR-20.



TRANSISTOR TESTER

A TRANSISTOR TESTER, TT-2 (kit or wired), for checking transistors and diodes, has been introduced by Century Electronics Co., Inc., 111 Roosevelt Ave., Mineola, N. Y. Unit is said to check transistors for off current, leakage, opens, shorts, cut-reverse current gain. Power supplied by 6-v battery.

AN RF POWER METER, PM-1 (kit), for sampling f field in the vicinity of transmitter antenna. Provides a continuing indication of transmitter power. Detects dropping off of transmitter power by comparing past meter indication with that obtained at any other given time. Operates with transmitter having output frequency between 100 kc and 250 mc. Sensitivity is .3 v rms full scale, with an adjustment control on the panel. Meter is a 200 μ a unit.

RF POWER METER

A MULTIRANGE MIRROR-SCALE VOM, 120M, said to eliminate parallel, has been announced by Precision Apparatus Co., Inc., 70-31 84th St., Glendale 27, N. Y. Unit has $\frac{1}{2}$ % tolerance multipliers and a separate function selector position for $-dc$ volts and $-dc$ milliamperes. Polarity switching is accomplished by changing the function selector; test leads need not be reversed. Sensitivity is 20,000 ohms/volt dc and 5,000 ohms/volt ac . Has 44 ranges; range selection is accomplished with 18-position, positive-detenting selector equipped with low resistance, silver-plated contacts. Accessories available include a 30 kv safety probe, TV-2B; leather instrument case, LC-3; and snap-on foldaway tilt stand, ST-1.

MIRROR-SCALE VOM

TEST INSTRUMENTS



PORTABLE PLUG-IN INVERTERS

PORTABLE INVERTERS, which plug directly into the cigarette lighter receptacle of autos or other vehicles, have been introduced by American Television and Radio Co., 300 E. Fourth St., St. Paul 1, Minn. Units are designed for operating standard ac dictating machines, record players, incandescent lamps, and electronic test equipment. All units have 110 v ac 60 cycle output with output wattages ranging from 30 to 150 watts.

A DEGAUSSING COIL for demagnetizing color picture tubes and chassis, has been announced by Bushnell Electric Co., Bushnell, Ill. Coil has 425 turns of No. 20 hf magnet wire bound with plastic tape. Comes with a 10' type sv cord with feed-through switch.

DEGAUSSING COIL

RECOTON CORPORATION
 52-35 Barnett Ave., Long Island City 4, N. Y.
 In Canada: Quality Records, Ltd., Toronto

REPLACEMENT NEEDLES

RECOTON

you'll find whatever they ask for in RECOTON'S REFERENCE GUIDE!
 that's why it's easier to sell

The Customer is Always Right!

| | | | | | | | | | |
|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|
| 410 | 409 | 408 | 407 | 406 | 405 | 404 | 403 | 402 | 401 |
| 392 | 382 | 372 | 362 | 352 | 342 | 332 | 322 | 312 | 302 |
| 292 | 282 | 272 | 262 | 252 | 242 | 232 | 222 | 212 | 202 |
| 192 | 182 | 172 | 162 | 152 | 142 | 132 | 122 | 112 | 102 |
| 92 | 82 | 72 | 62 | 52 | 42 | 32 | 22 | 12 | 2 |

ACCESSORIES

TV TUBE RESTORER
 TV TUBE RESTORER K-10, has been announced by Prima-Power Co., 3100 Madison Ave., Chicago 12, Ill. Claimed to local and correct an cathode heater-cathode short, grid control grid-cathode short, screen and combinations of these



UHF CONVERTER
 UHF CONVERTER, UH-2 Champion, featuring continuous tuning over the entire uhf band, has been developed by Granco Products, Inc., 38-07 20th Ave., Long Island City 5, N. Y. Unit features preselection, vernier tuning and coax frequency control.

ADVERTISERS IN SERVICE

OCTOBER, 1957


| | Page |
|---|--------|
| Alliance Manufacturing Co..... | 16 |
| Amperex Electronic Corp..... | 2 |
| Amphenol Electronics Corp..... | 44 |
| Astron Corp..... | 36 |
| | |
| B&K Manufacturing Co..... | 39 |
| Bussmann Manufacturing Co..... | 4 |
| | |
| Centralab, A Div. of Globe-Union, Inc.. | 3 |
| Channel Master Corp..... | 42 |
| H. G. Cisin..... | 55 |
| Cornell-Dubilier Electric Corp. <i>Inside Front Cover,</i> | 53 |
| | |
| Dynamic Electronics-New York, Inc..... | 65 |
| | |
| EICO..... | 63 |
| Electro Products Laboratories..... | 54 |
| Electro-Voice, Inc..... | 61 |
| | |
| The Finney Co..... | 25 |
| | |
| General Cement Manufacturing Co..... | 38 |
| General Electric Co., Electronic Components Div..... | 11 |
| General Electric Co., Specialty Electronic Components Dept..... | 57 |
| Good-All Electric Manufacturing Co..... | 7 |
| | |
| Heath Co..... | 49 |
| | |
| Jensen Industries, Inc..... | 63 |
| JFD Electronics Corp..... | 12, 13 |
| | |
| Kester Solder Co..... | 41 |
| Kraeuter & Co., Inc..... | 33, 34 |
| | |
| Luxo Lamp Corp..... | 41 |
| | |
| P. R. Mallory & Co., Inc..... | 48 |
| Merit Coil & Transformer Corp..... | 52 |
| | |
| Oxford Components, Inc..... | 62 |
| | |
| Philco Corp., Accessory Div. <i>Inside Back Cover</i> | |
| | |
| The Radiart Corp..... <i>Inside Front Cover,</i> | 53 |
| Radio Corporation of America, Components Div..... | 14, 50 |
| Radio Corporation of America, Electron Tube Div..... <i>Back Cover</i> | |
| Raytheon Manufacturing Co..... | 8, 9 |
| Recoton Corp..... | 64 |
| | |
| Howard W. Sams & Co., Inc..... | 47 |
| Seco Manufacturing Co..... | 52 |
| Service Instruments Corp..... | 65 |
| Shell Chemical Corp..... | 6 |
| Simpson Electric Co..... | 45 |
| Snyder Manufacturing Co..... | 10 |
| Sonotone Corp..... | 59 |
| South River Metal Products Co., Inc..... | 58 |
| Sprague Products Co..... | 15 |
| | |
| Sarkes Tarzian, Inc., Rectifier Div..... | 66 |
| Trio Manufacturing Co..... | 5 |
| Tung-Sol Electric, Inc..... | 30, 31 |
| | |
| Waage Manufacturing Co..... | 65 |
| Walsco Electronics Manufacturing Co..... | 1 |
| Winegard Co..... | 40 |

BENCH-FIELD TOOLS

TUBE CADDY

A TUBE CADDY, TC-5 (24" w x 16½" h x 8½" d), with a separate removable tool tray, has been introduced by Argos Products Co., Genoa, Ill.

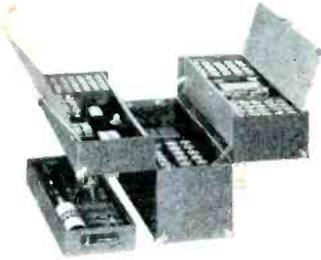Designed to hold not only tubes, but tools, soldering gun, meter and accessories.



SERVICING LAMP

A SERVICING LAMP, Magna-Lite, with a magnetic base that permits placement on metal surfaces or flexible-joint arm, has been announced by R-Columbia Products Co., Inc., Highwood, Ill.

Available in two models: 300 with standard shade, plug and bulb; and 350 with flood shade and standard plug (less bulb).

WOOD TOUCH-UP FINISHES

PUSHBUTTON, AEROSOL-TYPE, satin-finish stains, said to permit spraying of a matching touch-up color on damaged wood furniture, have been developed by Press-N-Spray Div., Saco Chemical Corp., 527 Lexington Ave., New York, N. Y.

Four colors are available: Brown and cordovan mahogany, walnut and blonde.

ADJUSTABLE HIGH-INTENSITY LAMP

AN ADJUSTABLE INCANDESCENT flexible lamp, Kold, for close work requiring a high light intensity, has been introduced by the Faries Lamp Div., General Lamps Manufacturing Corp., Elwood, Ind.

Constructed with a flue effect said to draw off heat with a fast up current. Lamps extend from a minimum of 12" to a maximum of 38".

ALUMINUM SAFETY-STEP LADDERS

ALUMINUM LADDERS, with steps made of extruded aluminum, have been announced by Ballymore Co., West Chester, Pa.

Ladders have ball-bearing casters which automatically retract when ladder is stepped on. Handrails are offered on 3- and 4-step models.

SPARE TIME PROFITS

enjoyed by Radio-TV shops handling small appliance repairs. These jobs picked up on regular service calls and repaired at the shop during slack periods.

For complete catalog RW-58 on Appliance Parts, Switches, Testers, Toaster and Percolator Elements, Supplies, etc., contact your nearest parts jobber. If he cannot supply you, write us giving jobber's name and address.

WAAGE MFG. CO. 632R N. ALBANY AVE.
CHICAGO 12, ILL.

BETTER HI-TI

Dynamic
**ELECTRONIC
COMPONENTS - ACCESSORIES**

AMPLIFIERS



7
AS
A
\$39.

"QUADRAURAL" SPEAKER SYST

TRADE MARK REGISTERED

RECORD COMPENSATORS
RUMBLE FILTERS
HI-PASS FILTERS
LOW-PASS FILTERS
SPEAKER SELECTORS
TRI-SET COUPLERS
MOLDED-ON CONNECTORS
DUO-JACK ADAPTERS
FILTER-TENNA

Sold by Better Distributors Everywhere
SEND FOR CATALOG SHEETS
ON ALL DYNAMIC PRODUCTS
"UNMISTAKABLE THE FINEST"

Manh. City, Ill.
DYNAMIC ELECTRONICS-NEW YORK, INC.
Forest, Long Island, N. Y.

SENCORE

Handy "36"

R-C

Substitution Unit

Another
Sencore
Time-
Saver

"36"

Most
Often
Needed
Components
At YOUR
Fingertips!



3 pole, 12 position switch individually selects one of the "36" components for direct substitution.

Contains:

- * 12-1 watt 10% resistors from 10 ohms to 5000 ohms
- * 12-½ watt 10% resistors from 10K ohms to 5.0 meg ohms
- * 10-500 volt capacitors from 100-mmf. to .5mf.
- * 1-10mf., 450V Electrolytic
- * 1-40mf., 450V Electrolytic

ONLY
\$1275
DEALER NET

Completely isolated

★ For Shop, Lab, or outside service
AVAILABLE AT ALL PARTS
DISTRIBUTORS!

SENCORE SERVICE
INSTRUMENTS CORP.
471 OFFICIAL RD., ADDISON, ILL.

- POPULAR
SENCORE
PRODUCTS
- Transistor Tester
 - Leakage Checker
 - Filament Tester
 - Voltage Regulator
 - Bias Supply


Cut out this ad now for further information.

M-500
SARKES
FOR TELEVISION

M-150
M-150
FOR ALL RADIOS

2 Types Silicon Rectifiers Replace 95% of All Selenium Types Used in Radio and Television Sets

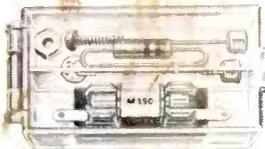- Save Shelf Space
- Save Mounting Time
- Lower Inventory Investment



Simplify rectifier replacement by using Sarkes Tarzian Silicon Rectifiers... Get better performance, too, at no additional cost... Send for Service Notes No. 1 and No. 4 for complete details.

Sarkes Tarzian RECTIFIER DIVISION
INC.

DEPT. S-2, 415 NORTH COLLEGE AVE., BLOOMINGTON, INDIANA

IN CANADA: 709 WESTON RD., TORONTO 9, TEL. ROGERS 2-7535
EXPORT: AD AURIEMA, INC., NEW YORK CITY

PERSONNEL

GEORGE GEMBERLING, former general district manager of The Alliance Manufacturing Co., Inc., Alliance, O., is now sales manager for the consumer products division. . . . *Ray Buhrman*, advertising manager, has been named assistant sales manager for the consumer products division and still retains his duties as ad manager.



Gemberling

Buhrman

CONRAD R. ODDEN has been appointed to a newly created post of manager, general quality control, RCA Victor Radio and Victrola Division. Odden has been serving for the past three years as manager of commercial service for the RCA Service Company, Inc.

BROCK P. HAYES has been named Syracuse district manager for the CBS-Hytron Sales Corp., Danvers, Mass. *Ray A. Juusola* is now manager, marketing administration, of CBS-Hytron.

LARRY STINEMAN is now chief engineer of Gramer-Halldorson Transformer Corp., 2734 N. Pulaski Road, Chicago, Ill. *Stineman* was formerly chief engineer for Merit Coil and Transformer Corp.

ROGER A. SWANSON has been appointed a sales engineer for the semiconductor division of Sylvania Electric Products Inc., 1740 Broadway, N. Y. 19, N. Y.

LYNN LOCKWOOD has joined the Finney Co., 34 W. Interstate St., Bedford, O., as a special factory rep. *Donald Wells* has been named special development engineer for Finney. *Richard Linnert* is now a special sales engineer for Finney.

C. GRAYDON LLOYD has been named general manager of the General Electric specialty electronic components department, Auburn, N. Y.

RICHARD G. FREEMAN has been elected vice president of Todd Products Co., Inc., Mt. Vernon, N. Y. *Freeman* was formerly vice president and director of purchasing of Empire Coil Co.

BOB HODGES has been named sales engineer of the catalog products division of Chicago Standard Transformer Corp.

ROBERT E. GIANNINI has been appointed western regional manager for distributor sales of General Electric electronic tubes and other components. The regional office has been moved to the Los Angeles headquarters at 11840 Olympic Boulevard.

Mr. Service Dealer...



PHILCO 7100A—Newest Philco Universal Color and Dot Bar Generator

BUILT-IN QUALITY FEATURES

- 4 crystals for maximum accuracy.
- Crystal controlled sound carrier, picture carrier, sync circuitry and color display.
- Visual marker signal to identify color bars.
- Regulated power supply.
- Separate R.F. and video attenuators.
- Positive and negative video signals for localizing trouble.
- Complete with R.F. and video cables.
- Tube complement of 14 tubes: 7-12AT7, 1-12AU7, 2-6CS7, 1-6CL6, 1-513, 2-OD3.

PHILCO is the Best Buy in Color Servicing



The new Philco Universal Color and Dot Bar Generator, like all Philco Test Equipment, was designed by expert engineers who know service work best. Built by trained technicians to meet the highest and high-quality standards for more dependable, more accurate work on the job.

For Sure Success in Color Servicing

Philco Test Equipment is designed to help your profits grow by being faster and more accurate in solving every service problem. This latest Philco Universal Color Bar and Dot Bar Generator combining both services in one compact, lightweight case eliminates the nuisance of using separate instruments. Improved convergence signals are provided and a "white-raster" display is included to speed up accurate "purity" adjustments.

Now, it's no longer necessary to disable the set by removing a tube or changing circuit to obtain the "quiet", snow-free raster required. Halves the work time and eliminates old-fashioned methods requiring you to handle hot tubes. Front panel of etched aluminum with black knobs and easy-to-read etched markings. 15 lbs. light. Dimensions: 13 $\frac{3}{8}$ " wide, 11 $\frac{1}{2}$ " high, 9 $\frac{3}{4}$ " deep.

Get the full story from your local **PHILCO DISTRIBUTOR** on how the Philco Universal Color Bar and Dot Bar Generator can streamline color servicing.

PHILCO

Accessory Division • Philadelphia 34, Penna.



OR MAIL THE COUPON TO:
PHILCO CORPORATION ACCESSORY DIVISION
 "A" Street and Allegheny Avenue
 Philadelphia 34, Pa.

Please send me information on Philco Universal Color Bar and Dot Bar Generator with supply, accuracy and speed.

Name _____

Address _____

City _____ State _____

QUIET

**Trouble-
shooter
at
work**



Here's how Microscopic Inspection by RCA helps reduce costly callbacks...

A bad tube, or a potential trouble-maker—can it get by this gal? Not likely. She's part of the specially trained RCA group of inspectors whose important job it is to find trouble and help prevent it from happening to you.

RCA Quality-Control Procedures include MICROSCOPIC INSPECTION OF POPULAR TV RECEIVING TYPES! These types are closely examined for possible poor welds, weld splatter, bad crimps, damaged stems, improper assembly, and many other factors that can affect top quality, long-term performance. Though the tubes may pass all electrical tests, such defects could slip by and mean the difference between a profitable service call and a costly callback.

You can have valuable assurances from this *extra* care: (1) that popular TV receiving tubes shipped to RCA Tube Distributors have had the *extra* benefit of the MICROSCOPIC INSPECTION PROGRAM and (2) that you can always service your customers with the confidence that RCA TV Receiving Types are top quality replacement tubes.

When you order—tell your distributor "RCA only" and watch your profits grow.



RECEIVING TUBES

RADIO CORPORATION OF AMERICA

Tube Division, Harrison, N. J.

