


SHORT WAVE CRAFT

DEC 30 - JAN 31 Edited by
HUGO GERNSBACK

ARTICLES BY

- Dr. Alfred N. Goldsmith, Ph.D.
- C. H. W. Nason
- Dr. Fritz Noack
- A. Binneweg
- R. Wm. Tanner
- Beryl B. Bryant
- Dr. J. Fuchs
- Frank Sobiech
- Clyde A. Randon

Dec. — Jan.

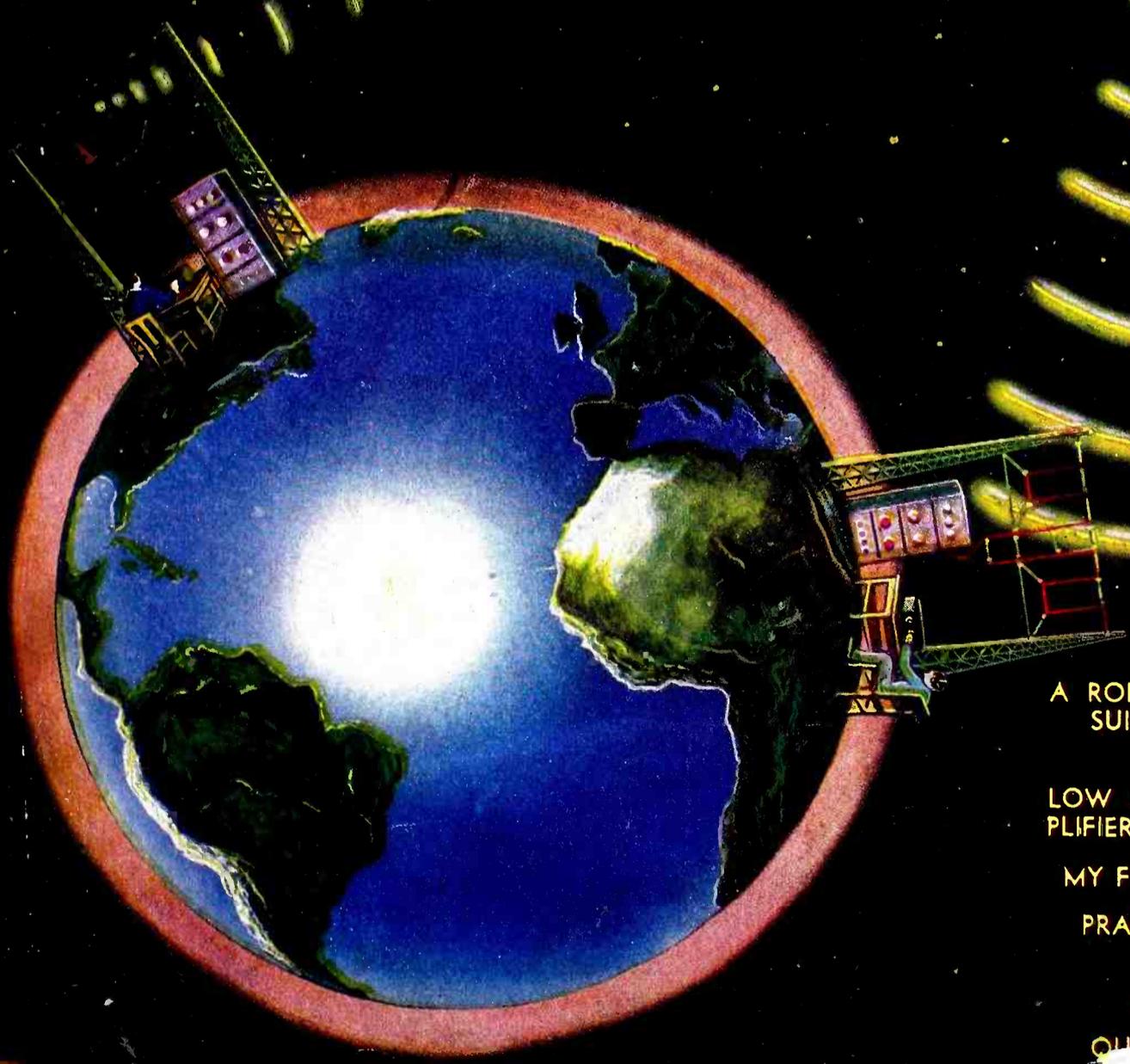

- IN THIS ISSUE
- "WHEN TO LISTEN IN"
 - HOW TO BUILD S-W "TELEVISION" TRANSMITTER
 - THE FUTURE OF SHORT WAVES
 - SUPER-HETS FOR SHORT WAVES
 - 85 METER PHONE TRANSMITTER
 - A ROLLS-ROYCE S-W RECEIVER—SUITABLE FOR "TELEVISION" RECEPTION
 - LOW POWER OSCILLATORS, AMPLIFIERS AND CRYSTAL CONTROLS
 - MY FAVORITE AUDIO AMPLIFIER
 - PRACTICAL S-W HINTS AND HOOK-UPS
 - AMONG THE HAMS
 - QUESTIONS AND ANSWERS
 - 150 ILLUSTRATIONS
 - 75 HOOK-UPS AND

50c

5,000

Radio Service Men Needed Now!

The replacing of the old battery operated receivers with all-electric Radios has created a tremendous country-wide demand for expert Radio Service Men. Thousands of trained men are needed quick!



30 Days of R.T.A. Home Training

... enables you to cash in on this latest opportunity in Radio

\$40 to \$100
a week
Full Time
\$3.00 *an hour*
Spare Time

Ever on the alert for new ways of helping our members make more money out of Radio, the Radio Training Association of America now offers ambitious men an intensified training course in Radio Service Work. By taking this training you can qualify for Radio Service Work in 30 days, earn \$3.00 an hour and up, spare time; prepare yourself for full-time work paying \$40 to \$100 a week.

hour spare time or \$40 to \$100 a week full time, this R. T. A. training offers you the opportunity of a lifetime.

More Positions Open Than There Are Trained Men to Fill Them

If you were qualified for Radio Service Work today, we could place you. We can't begin to fill the requests that pour in from great Radio organizations and dealers. Members wanting full-time positions are being placed as soon as they qualify. 5,000 more men are needed quick! If you want to get into Radio, earn \$3.00 an

We furnish you with all the equipment you need to become a Radio Service Man!

Radio Service Work a Quick Route to the Big-Pay Radio Positions

Radio Service Work gives you the basic experience you need to qualify for the big \$8,000, \$10,000 to \$25,000 a year Radio positions. Once you get this experience, the whole range of rich opportunities in Radio lies open before you. Training in the Association, starting as a Radio Service Man, is one of the quickest, most profitable ways of qualifying for rapid advancement.

If you want to get out of small-pay, monotonous work and cash in on Radio quick, investigate this R. T. A. training and the rich money-making opportunities it opens up. No special education or electrical experience necessary. The will to succeed is all you need.

Mail Coupon for No-Cost Training Offer

Cash in on Radio's latest opportunity! Enroll in the Association. For a limited time we will give to the ambitious man a No-Cost Membership which need not . . . should not. . . cost you a cent. But you must act quickly. Filling out coupon can enable you to cash in on Radio within 30 days, lift you out of the small-pay, no-opportunity rut, into a field where phenomenal earnings await the ambitious. You owe it to yourself to investigate. Fill out coupon NOW for details of No-Cost Membership.

The Radio Training Association of America
4513 Ravenswood Ave. Dept. SWC-12 Chicago, Ill.

THE RADIO TRAINING ASSOCIATION OF AMERICA
4513 Ravenswood Ave., Dept. SWC-12, Chicago, Ill.
Gentlemen: Please send me details of your No-Cost training offer by which I can qualify for Radio Service Work within 30 days. This does not obligate me in any way.

Name.....
Address.....
City..... State.....

10.4

AERO SHORT-WAVE Automatic TUNING UNIT

(Protected by patents pending)

Exclusive Features

W. H. Hoffman and Don H. Mix, than whom there are no better known short-wave experts, are the designers of this tuner.

Automatic range, 15 to 90 meters; full range, up to 200 meters.

No plug-in coils used in automatic range.


Easiest tuning device known.

Tunes even more slowly than broadcast receiver.

Special attachment enables it to reach 200 meters.

Anyone can operate it.

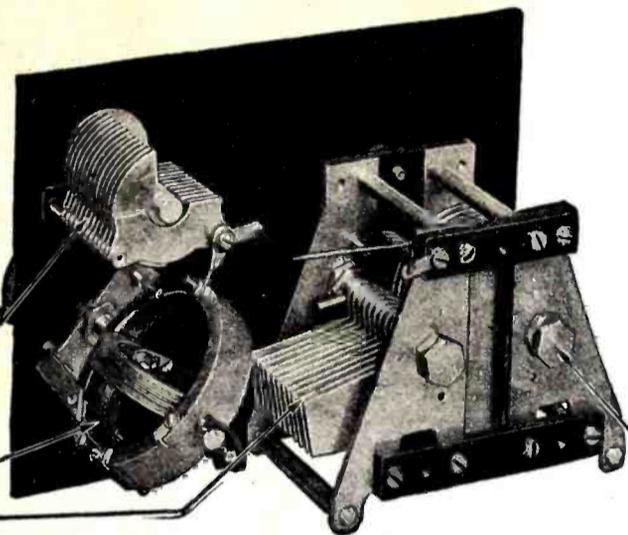The days of fooling with plug-in coils are over. Amateurs can now have a real thrill by this new automatic tuning device. Read the complete story in February QST and May RADIO-CRAFT, and then mail your order to Aero Products for the complete built-up unit. Be first to use this remarkable short-wave apparatus.



SHIFT DIAL SET APPROXIMATELY HALF WAY 65°

TUNING DIAL AT 100° WAVELENGTH APPROXIMATELY 50 METERS

A Marvelous Improvement

NO PLUG-IN COILS

Range 15 to 90 meters. Easiest tuning short-wave receiver known. The tuning unit consists of two controls. The right-hand control, which will be termed the shift control, and the left-hand control, the actual tuning device. In addition to these two controls it will, of course, be necessary to have a regeneration control.

For those who desire to employ it for television or the upper phone band, a special attachment may be secured.

OPERATION

The tuner is operated in the following manner. As a specific example, with the right-hand dial set at nine degrees, revolving the left-hand dial through 180 degrees, you will cover from 19.1 to 22.6 meters. The next step will be to move the shift dial to 13 and tuning over 180 degrees, as before, this time covering from 21.9 to 25.7 meters. This process is continued through 180 degrees on the shift dial until you have reached the maximum automatic wave length, which is 90 meters.

You will note that the tuning dial, in the first instance when tuned through 180 degrees, covers only 3½ meters, whereas ordinarily when using plug-in coils your tuner, when passing through 180 degrees, generally covers at a minimum of 25 meters. This same speed of tuning is maintained throughout the entire short-wave spectrum, and it is for this reason that this tuning arrangement surpasses any known method.

This unit is furnished completely assembled to the amateur, and may be built into either a short-wave converter or receiver.

For those desiring to go from 90 to 200 meters a special device may be had, making its range then from 15 to 200 meters. Net price of attachment, \$5.90 extra.

A general chart is furnished with each unit specifying the settings for the shift dial, which will enable you to approximate the wave length for each setting on the shift dial.

This tuner is not sold through the usual trade channels, but is sold to amateurs only direct from factory at special low net price. Be sure to send post office or express money order for \$19.50 with your order. Shipments will be made in order received. Be first to order. Attach your money-order to coupon below and mail today — NOW!

AERO PRODUCTS, INC.
 4611 E. Ravenswood Ave., Dept. 2650, Chicago, U. S. A.

Dear Sirs:
 I want to be one of the first to secure the new Aero Short-Wave Automatic Tuning Unit. Enclosed is money order for \$19.50 which is your low opening net price to amateurs only.

Name

Street and No.

City..... State.....

PRICE ONLY

\$ 19.50

NET

AERO PRODUCTS
 INCORPORATED
 4611 E. Ravenswood Avenue
 Dept. 2650
 Chicago, Illinois, U. S. A.

HUGO GERNSBACK, Editor

H. WINFIELD SECOR, Managing Editor

CONTENTS**DECEMBER-JANUARY, 1930-31 ISSUE***In This Issue: Prominent Short Wave Authors***Goldsmith - Randon - Tanner - Nason - Noack - Binneweg****FEATURES:**

- Looking Ahead With Short Waves, by Alfred N. Goldsmith, Ph.D., Vice-president and General Engineer of the Radio Corporation of America
Newspaper Page Reproduced via Short Waves...
Short Wave Radiophone Keeps Fireboat in Touch With Shore
Can We Radio the Planets? by Hugo Gernsback..
How to Convert A Broadcast Receiver to A S-W Super-Het, by Clyde A. Randon.....
A New Short and Long Wave Receiving Set, by H. Winfield Secor.....
"Rolls-Royce" Short Wave Receiver, by C. Sterling Gleason
- The Short Wave, Screen Grid Craft Box, by Beryl B. Bryant
- Short Waves Trail Criminals to Their Lair.....
Propagation of Radio Waves, by Dr. J. E. Fuchs..
An 85 Meter Phone Transmitter, by R. Wm. Tanner, W8AD
- Oscillator, Amplifier and Crystal, by A. Binneweg, Jr.
- Can We Use Ultra Short Waves and Infra Red Waves for Communication, by Dr. F. Schröter
- Television on Short Waves—How to Build an Amateur Transmitter, by C. H. W. Nason...
A 19 Tube Short Wave Receiver for Trans-Atlantic Reception, by Dr. Fritz Noack (Berlin)
How to Build and Raise a 60 Foot Wood Tower, by Richard Carman

SHORT WAVE RECEIVERS:

- Short and Long Wave Receiving Set..... 276
The Amateur's "Short Wave" Special, by Frank Sobiech
- "Rolls-Royce" Short Wave Receiver..... 278
The Short Wave, Screen Grid Craft Box..... 282
The New Hammarlund Short Wave Receiver..... 285
The Screen Grid Five, by Edward G. Ingram..... 300
A 19 Tube Short Wave Receiver for Trans-Atlantic Reception
- A Sensitive and Selective Short Wave Receiver, by R. Wm. Tanner, W8AD..... 304
Measuring Wave Length of a Coil and Condenser 312

SHORT WAVE TRANSMITTERS:

- An 85 Meter Phone Transmitter..... 292
The Hartley Short Wave Transmitter, by Lester C. Kirsch
- Explaining the Simple Relation of the Oscillator, Amplifier and Crystal..... 296

TELEVISION SHORT WAVE SETS:

- A "Rolls-Royce" Short Wave Receiver—Suitable for Television Reception..... 278
Television Transmission for the Amateur..... 301

REGULAR MONTHLY DEPARTMENTS:

- Short Waves for the Broadcast Listener..... 271
A Short Wave Experimenter..... 277
The Short Wave Beginner..... 281
Among the "Hams"..... 288
Ultra Short Waves..... 299
When to Listen In—Time Table of Short Wave Stations
- Short Wave Question Box..... 310

SHORT WAVES FOR THE BROADCAST LISTENER:

- Converting the Broadcast Receiver Into a Short Wave Super-Het. 271
A New Short Wave Converter, by McMurdo Silver 275
A New Short and Long Wave Receiving Set.... 276

IN OUR NEXT ISSUE

The Coast Guard's Best Short Wave Receiver.
How to Learn the Code.
Transmitting On 10 Meters.
Ultra Short Waves—by Dr. F. Noack.
A 5 Meter Transmitter and Receiver, by E. T. Somerset, G2DT.

A Phone Transmitter for the Beginner, by R. Wm. Tanner, W8AD.
Improved Audio Amplifiers for Short Wave Receivers.
How to Operate Short Wave Receiver, by Arthur G. Green.
W9XAA—The "Short Wave" Voice of Labor, by Maynard Marquardt, Chief Engineer of WCFL and W9XAA.

SHORT WAVE CRAFT—Bi-monthly. Entered as second class matter May 7, 1930, at the post office at Mount Morris, Illinois, under the act of March 3, 1879. Trademarks and copyrights by permission of H. Gernsback, 98 Park Place, N. Y. C. Text and illustrations of this magazine are copyright and must not be reproduced without permission. SHORT WAVE CRAFT is published on the 15th of every other month. Six numbers per year. Subscription price is \$3.00 a year in the United States and possessions. Canada and foreign countries, \$3.50


a year. Single copies 50c. Address all contributions for publication to Editor, SHORT WAVE CRAFT, 96-98 Park Place, New York, N. Y. Publishers are not responsible for lost manuscripts. Contributions cannot be returned unless authors remit full postage. SHORT WAVE CRAFT is for sale at all principal newsstands in the United States and Canada. European agents: Brentano's, London and Paris. Printed in U. S. A. Make all subscription checks payable to Popular Book Corporation.

COPYRIGHT, 1930, BY H. GERNSBACK

Published by **POPULAR BOOK CORPORATION**

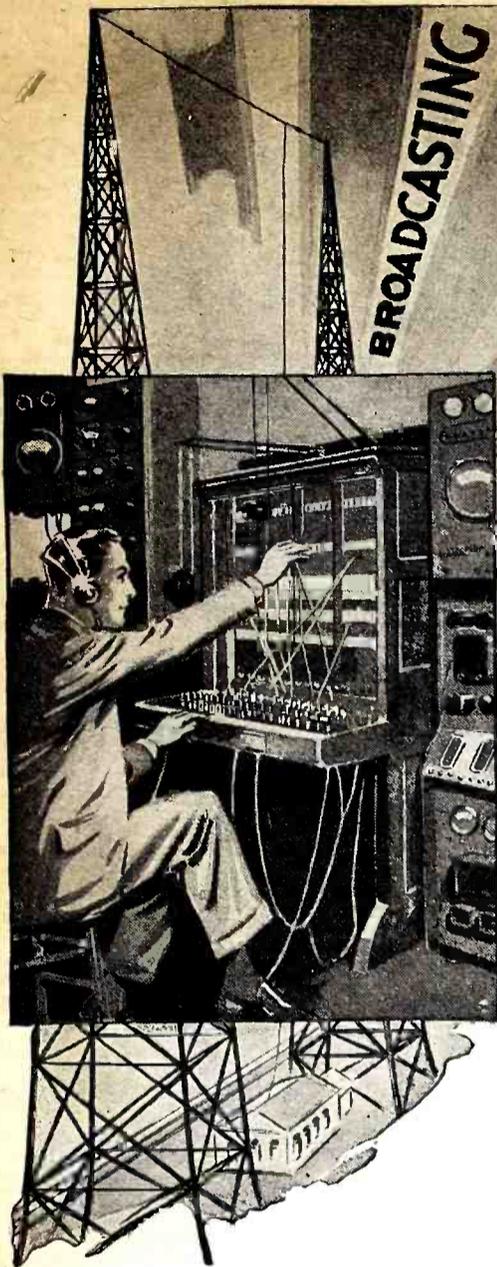H. GERNSBACK, President - H. W. SECOR, Vice-President

Publication Office, 404 N. Wesley Avenue, Mount Morris, Ill.
Editorial and General Offices, 96-98 Park Place, New York, N. Y.



BROADCASTING

TELEVISION

TALKING PICTURES

WIRELESS OPERATING

WIN FAME and FORTUNE in RADIO!

Don't spend your life slaving away in some dull, hopeless job! Don't be satisfied to work for a mere \$20 or \$30 a week. Let me show you how to make real money in Radio—the fastest-growing, biggest money-making game on earth!

THOUSANDS OF JOBS ARE OPEN
Paying \$60, \$70 and on up to \$200 a Week

Jobs as Designer, Inspector and Tester, paying \$3,000 to \$10,000 a year—as Radio Salesman and in Service and Installation Work, at \$45 to \$100 a week—as Operator or Manager of a Broadcasting Station, at \$1,800 to \$5,000 a year—as Wireless Operator on a Ship or Airplane, as a Talking Picture or Sound Expert—THOUSANDS of JOBS Paying \$60, \$70 and on up to \$200 a WEEK!

Learn Without Lessons *in* 60 Days

You learn ALL branches of Radio at Coyne—in 8 short, pleasant weeks—NOT BY CORRESPONDENCE, but by actual work on actual Radio, Television and Sound equipment. We don't waste time on useless theory. We give you just the practical training you will need—in 8 weeks' time.

No Books - No Lessons
All Practical Work at Coyne

Coyne is NOT a Correspondence School. We don't teach you from books or lessons. We train you on the greatest outlay of Radio, Television and Sound equipment in any school—on scores of modern Radio Receivers, huge Broadcasting equip-

ment, the very latest Television apparatus, Talking Picture and Sound Reproduction equipment, Code Practice equipment, etc. You don't need advanced education or previous experience. We give you—right here in the Coyne Shops—all the actual practice and experience you'll need.

TELEVISION *Is on the Way!*

And now Television is on the way! Soon there'll be a demand for THOUSANDS of TELEVISION EXPERTS! The man who learns Television NOW can make a FORTUNE in this great new field. Get in on the ground-floor of this amazing new Radio development! Learn Television at COYNE on the very latest, newest Television equipment.

Talking Pictures *A Great Field*

Talking Pictures and Public Address Systems offer thousands of golden

opportunities to the Trained Radio man. Here is a great new field of Radio that has just started to grow! Prepare NOW for these marvelous opportunities! Learn Radio Sound Work at Coyne, on actual Talking Picture and Sound Reproduction equipment.

Coyne is 31 Years Old

Don't worry about a job! Coyne Training settles the job question for life. You get Free Employment Help as long as you live. And if you need part-time work while at school to help pay expenses we'll gladly help you get it. Coyne is 31 years old! Coyne Training is tested—proven beyond all doubt. You can find out everything ABSOLUTELY FREE. JUST MAIL COUPON FOR MY BIG FREE BOOK.

H. C. Lewis, Pres.

Radio Division

Founded 1899

Coyne Electrical School

500 S. Paulina Street Dept. 11-2K Chicago, Illinois

H. C. LEWIS, President
Radio Division, Coyne Electrical School
500 S. Paulina St., Dept. 11-2K Chicago, Ill.


Send me your Big Free Radio Book and all details of your Special Introductory Offer. This does not obligate me in any way.

Name

Address

City..... State.....

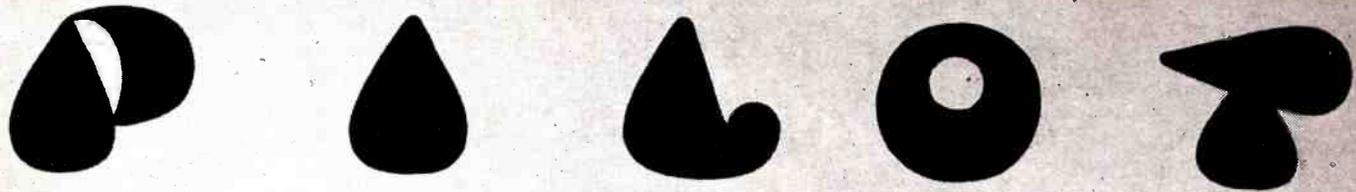THE LINE OF RADIO PARTS YOU CAN *finish* WITH AS WELL AS *Start* WITH



KITS • PARTS • ACCESSORIES

Now occupying the largest factory in the world owned and operated by a radio manufacturer, Pilot Radio & Tube Corporation offers the service man, custom set builder and amateur set builder assurance of a future supply and service on every item necessary for replacement for years to come. • Pilot Super-Wasp Kits are the best known short wave apparatus throughout the world. Pilot power supply units, transformers, fixed condensers, resistances, and other accessories are only second to the Super-Wasp in international fame.

• Pilot Broadcast Receiver Parts, coils, variable condensers, shields, etc., are in use in more home and custom built receivers than any other brand. • Pilotron Radio Tubes are depended on in more different countries for constant radio contact over immense distance than any other tubes.

Pilotrons are the only radio tubes all of which give as good results in short wave work as on broadcast wavelength.

Pilot short wave experience has taught Pilot tube engineers the value of manufacturing practices not yet generally known, with the result that Pilotrons are unexcelled in uniformity of design and consistency of operation.



PILOT RADIO & TUBE CORP.


Chicago Office 234 S. Wells Street LAWRENCE, MASS. San Francisco Office 1278 Mission Street
New York Office—525 Broadway

OFFICES IN PRINCIPAL COUNTRIES OF THE WORLD



TUBES

POWER SWITCHES

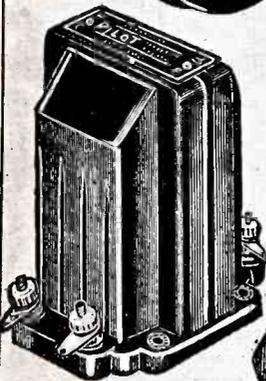


TRANSFORMERS AND CHOKES




COILS




JACKS

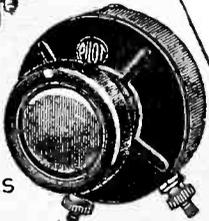


REOSTATS

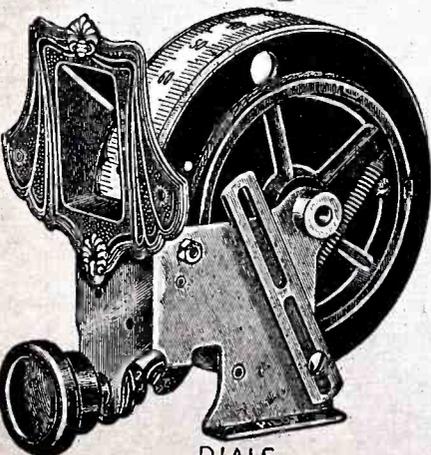

DIALS

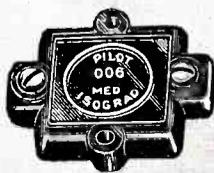


FIXED CONDENSERS

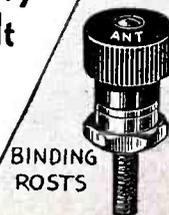


BINDING ROSETS




POWER PACKS

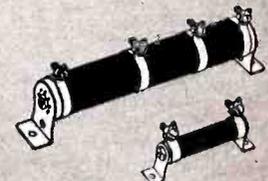


FIXED RESISTORS

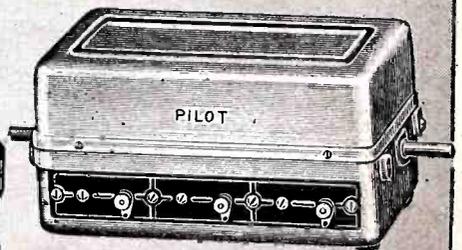

VAULT-TYPE "VARIABLE CONDENSERS

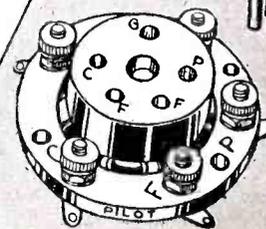

TUBE SOCKETS

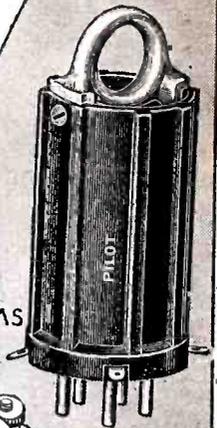

COIL FORMS



KITS

Here are a few examples of the kind of money I train "my boys" to make

Started with \$5. Now has Own Business



"Can't tell you the feeling of independence N.R.I. has given me. I started in Radio with \$5, purchased a few necessary tools, circulated the business cards you gave me and business picked up to the point where my spare time earnings were my largest income. Now I am in business for myself. I have made a very profitable living in work that is play."

HOWARD HOUSTON, 512 So. Sixth St., Laramie, Wyo.

\$700 in 5 Months Spare Time

"Although I have had little time to devote to Radio my spare time earnings for five months after graduation were approximately \$700 on Radio sales, service and repairs. I owe this extra money to your help and interest. Thanks for the interest shown me during the time I studied and since graduation."



CHARLES W. LINSEY, 537 Elati St., Denver, Colo.

\$7396 Business in two and one-half Months




"I have opened an exclusive Radio sales and repair shop. My receipts for September were \$2332.16—for October, \$2887.77 and for the first half of November, \$2176.32. My gross receipts for the two and one-half months I have been in business have been \$7396.25. If I can net about 20% this will mean a profit of about \$1500 to me."

JOHN F. KIRK, 1514 No. Main St., Spencer, Iowa.

My Free book gives you many more letters of N. R. I. men who are making good in spare time or full time businesses of their own



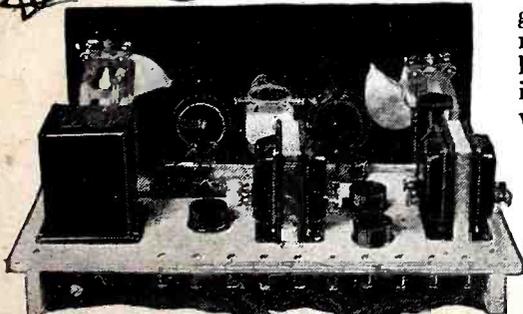Rear view of 5-tube Screen Grid Tuned Radio frequency set — only one of the many circuits you can build with my parts.



You'll get practical Radio Experience with my new 8 Outfits of Parts that I'll give you for a Home Experimental Laboratory!

My course is not all theory. You use the 8 Outfits I'll give you, in working out the principles, diagrams and circuits used in modern sets and taught in my lesson books. This 50-50 method of home training makes learning easy, fascinating, interesting. You get as much practical experience in a few months as the average fellow who hasn't had this training gets in two to four years in the field. You can build over 100 circuits with these parts. You experiment with and build the fundamental circuits used in such sets as Crosley, Atwater-Kent, Eveready, Majestic, Zenith, and many others sold today. You learn how these circuits work, why they work, how they should work, how to make them work when they are out of order.

I will show You too how to start a spare time or full time Radio Business of Your Own without Capital



J. E. Smith, Pres., National Radio Institute

The world-wide use of receiving sets for home entertainment, and the lack of well trained men to sell, install and service them have opened many splendid chances for spare time and full time businesses. You have already seen how the men and young men who got into the automobile, motion picture and other industries when they were young had the first chance at the key jobs—and are now the \$5,000 \$10,000 and \$15,000 a year men. Radio offers you the same chance that made men rich in those businesses. Its growth is opening hundreds of fine jobs every year, also opportunities almost everywhere for a profitable spare time or full time Radio business. "Rich Rewards in Radio" gives detailed information on these openings. It's FREE.

So many opportunities many make \$5 to \$30 a week extra while learning

Many of the ten million sets now in use are only 25% to 40% efficient. The day you enroll I will show you how to do ten jobs common in most every neighborhood, that you can do in your spare time for extra money. I will show you the plans and ideas that are making as high as \$200 to \$1,000 for others while taking my course. G. W. Page, 107 Raleigh Apts., Nashville, Tenn., writes: "I made \$935 in my spare time while taking your course."

Many \$50, \$60 and \$75 a week jobs opening in Radio every year

Broadcasting stations use engineers, operators, station managers, and pay \$1,800 to \$5,000 a year. Radio manufacturers continually need testers, inspectors, foremen, engineers, service men, and buyers for jobs paying up to \$15,000 a year. Shipping companies use hundreds of operators, give them world-wide travel at practically no expense and pay \$85 to \$200 a

month. Radio dealers and jobbers are continually on the lookout for good service men, salesmen, buyers, managers, and pay \$30 to \$100 a week. Talking Movies pay as much as \$75 to \$200 a week to the right men with Radio training. My book tells you of other opportunities in Radio.

I will train you at home in your spare time

Hold your job until you are ready for another. Give me only part of your spare time. You don't have to be a high school or college graduate. Hundreds have won bigger success. J. A. Vaughn jumped from \$35 to \$100 a week. E. E. Winborne seldom makes under \$100 a week now. The National Radio Institute is the Pioneer and World's Largest organization devoted exclusively to training men and young men, by correspondence for good jobs in the Radio industry.

You Must Be Satisfied

I will give you an agreement to refund every penny of your money if you are not satisfied with my Lessons and Instruction Service when you complete my course. And I'll not only give you thorough training in Radio principles, practical experience in building and servicing sets, but also train you in Talking Movies, give you home experiments in Television, cover thoroughly the latest features in sets such as A. C. and Screen Grid.

My 64-Page Book Gives the Facts

Clip and mail the coupon now for "Rich Rewards in Radio." It points out the money-making opportunities the growth of Radio has made for you. It tells of the opportunities for a spare time or full time Radio business of your own, the special training I give you that has made hundreds of other men successful; and also explains the many fine jobs for which my course trains you. Send the coupon to me today. You won't be obligated in the least.

Get my new book It points out what Radio Offers You



J. E. SMITH, President Dept. ON-90 National Radio Institute Washington, D. C.

THIS COUPON IS GOOD FOR ONE FREE COPY OF MY NEW BOOK

mail it TODAY

J. E. SMITH, President, National Radio Institute, Dept. ON-90 Washington, D. C.

DEAR MR. SMITH:—Send me your book. I want to see what Radio offers. I understand this request does not obligate me and that no agent will call.

Name.....

Address.....

City..... State.....

Get the facts on my Lifetime Employment Service to all Graduates

KEEP STEP WITH RADIO PROGRESS!

RADIO is one of the real marvels of this modern age. Its development has been phenomenal. It is growing, changing, evolving new principles which require constant study. The demand is for technically trained men—men who keep pace with the unfolding revelations of this mighty and promising industry.

The International Correspondence Schools Course in Radio, prepared and constantly supplemented by outstanding authorities in the field, is specifically designed to meet the requirements of the radio industry for technically trained radio men. The manufacturer, the distributor, the dealer, Communication and Steamship Companies, the U. S. Government, all insist upon up-to-date, expert training. Recognized for its completeness and practicability, an I. C. S. Radio Course provides this training.

Authorities responsible for the preparation of the I. C. S. Radio Course include: H. H. Beverage, Radio Corporation of America; George C. Crom, American Transformer Company; Keith Henney, author of "Principles of Radio"; Malcom

E. Gager, Instructor at the Massachusetts Institute of Technology; E. V. Amy, consulting radio engineer, formerly with R. C. A.; H. F. Dart, authority on radio tubes; Julius C. Aceves, consulting radio engineer, formerly of Columbia University, and others.

The I. C. S. Radio Course is complete, from the foundational principles of radio to the most advanced stages, thoroughly and scientifically covering every department of this vast industry. It is a modern education in radio, a valuable guide of advancement for men engaged professionally in the radio business. Experimenters will find the I. C. S. Radio Course extremely useful. A thorough understanding of the principles underlying radio communication as presented in the Course will lead to more intelligent undertakings, more systematic work, and more fruitful results. Ample material for experimentations is now available in the ultra-high frequency field and in television.

Mark and mail the coupon. We will send you all details. This act may be the real beginning of your career in radio!

INTERNATIONAL CORRESPONDENCE SCHOOLS,
Box 2877, Scranton, Penna.

Without cost or obligation, please tell me all about the
COMPLETE RADIO COURSE

Name
Street Address
City..... State.....

If you reside in Canada, send this coupon to the International Correspondence Schools Canadian, Ltd., Montreal, Canada.

HUGO GERNSBACK

EDITOR

DEC.-JAN.

1930-1931



H. WINFIELD SECOR

MANAGING EDITOR

VOLUME 1

NUMBER 4

Short Wave Advances

By HUGO GERNSBACK

AT NO other time, perhaps, throughout the entire development of the art of short waves, has there been such rapid advancement as during the past year.

Several books could be written on the great advances which have been made during this time, and the present discussion is only a resumé of more important advances. One of the most important, if not the most important, of recent developments, is the announcement that our larger broadcasters, including the National Broadcasting Company, are seeking permission from the Radio Commission to take on commercial programs to be sent out over short waves. This is indeed great news because, if this does happen, it is certain that short waves will become as universal as the regular long waves are today. All of the big interests now realize that, by means of short waves, they can broadcast to the entire world instead of being satisfied to cover only the United States and Canada and, perhaps, Mexico. At the present time, practically all licensees for short waves have only experimental licenses and none of the broadcasters are broadcasting regularly on schedule on short waves.

All of this, as I have often predicted, will soon change; and broadcasting will no doubt go out on regular schedules on the short waves, just as it is done now on the longer waves. Of course, at the present time the big broadcasters who are operating on the short waves have no income whatsoever from the short-wave transmissions, and the expenses of these are defrayed out of the broadcaster's own pocket. Soon, however, this will be a thing of the past; for there is no question that scheduled commercial broadcasting will soon be heard on short waves. Then we will have the usual sponsored and paid-for programs on short waves, too; and, once the Americans start this, it is certain that the rest of the world will not wish to stay behind.

The set manufacturers have already seen the light; and at least one such manufacturer is now producing commercial broadcast sets that can be used for the short waves as well as regular waves.

During the next few years, it is certain that all receiving set manufacturers must follow suit. All sets, sooner or later, will be equipped for short-wave reception.

Of course, at the present time we have separate short wave sets or, more frequently, our converters to be attached to the broadcast sets. Both of these are more or less makeshifts which, sooner or later, will be replaced by the complete universal construction whereby both sets of waves can be tuned in. Up to now, short-wave reception was no sinecure for the public at large. The difference in tuning-in between short waves and regulation waves is enormous, as every short-wave fan knows only too well. On account of the more-than-

hairbreadth closeness of tuning, the short-wave enthusiast must first acquire a tuning technique; but I predict that our technicians will overcome this trouble during the next few years by means of a special condenser-and-vernier arrangement, so that it will be possible to tune a short-wave set with the same ease as the ordinary broadcast set.

I am fully aware that the short-wave "shark" will immediately contradict me and say that, even though the problem may be solved, so far as the tuning is concerned, the vagaries of short waves will still remain; and that, if you do succeed in tuning at a certain point of the dial, the station will not be heard because of the Heaviside-layer effects, fading and other troubles which are supposed to be beyond control in short-wave receivers.

This bugaboo may be dismissed from our minds immediately. While it is true that such reasoning holds true today; they will not do so in the future. The solution of the problem is contained in one word—POWER. Once short-wave broadcasters begin to broadcast with 50 or 100 kilowatts, the fading and skip-distance effects will not be nearly as formidable as they are now. It used to be the same in long-wave broadcasting; when, in 1922 and 1923, we tried to pick up a 500-watt broadcast station 300 or 400 miles distant, if conditions were just right, we could get the station. At other times, it simply could not be heard, no matter what we did. But present-day conditions do away with all these troubles and, when we think of the amount of power that some of the broadcasters now use (as compared to what they did use in 1922) we are apt to laugh at our former disappointments.

Recently, station KDKA announced that they are ready to broadcast on a power of 1,500 kilowatts whenever authorized; and the end is not yet. It is, therefore, probable that history will repeat itself in short-wave progress as well; and I am positive that the time will come when it will be as simple for the layman to receive a short-wave station as it is today for him to receive the present high-power broadcast stations.


In the meanwhile, a tremendous amount of research work remains to be done; but during the next few years there will be indeed a paradise for the short-wave experimenter who is interested in getting results and getting distance. The old days cannot even be compared remotely with what is taking place now. It was one thing to hear a station 300 miles away on earphones in 1922, and it is quite another to receive an antipodal station on the loud speaker today.

And then there is, of course, television too on the short waves. This is coming along so rapidly that, before we realize it, we will be able to "look in" on the entire world; and the time that it will take until we do this is much shorter than you may imagine.

SHORT WAVE CRAFT IS PUBLISHED ON THE 15th OF EVERY OTHER MONTH

THE NEXT ISSUE COMES OUT JANUARY 15TH

LOOKING

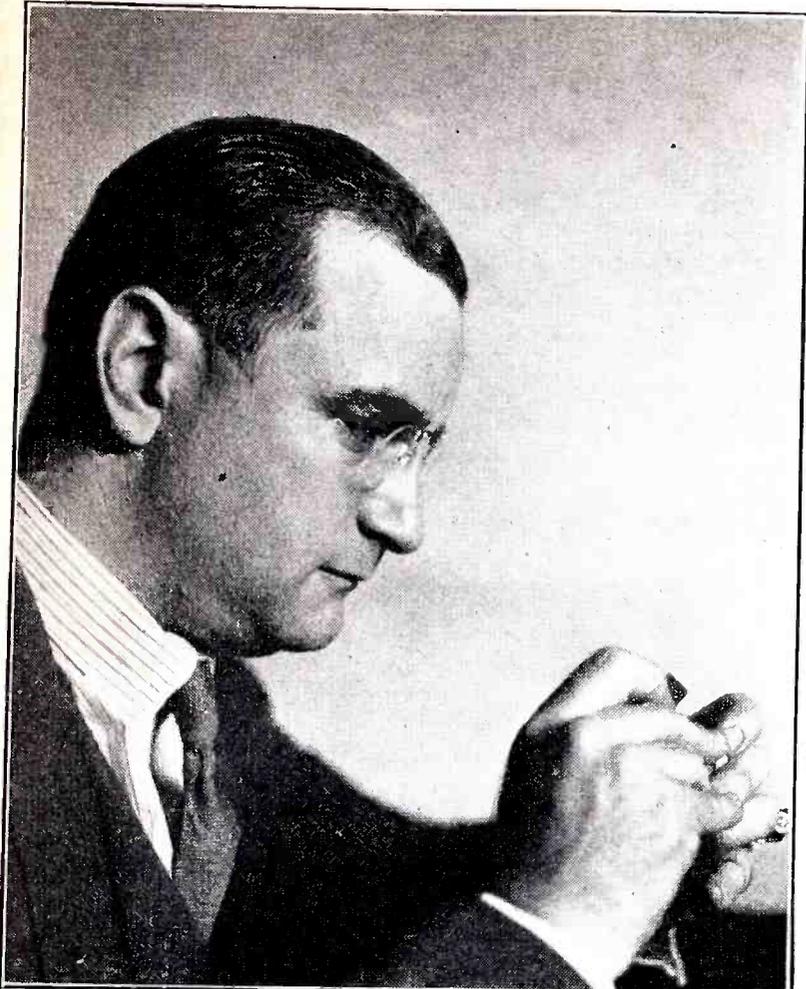

Photograph Copyrighted by Robert H. Davis

Dr. Alfred Norton Goldsmith, Ph. D.

ALFRED NORTON GOLDSMITH—American electrical and radio engineer, was born in New York City on September 15, 1887. He was graduated from the College of the City of New York in 1907 with the degree of Bachelor of Science and Phi Beta Kappa honors. In 1911, he received his Ph.D. from Columbia University. Upon his graduation from the College of the City of New York, he accepted a position as instructor in electrical engineering at that institution.

Dr. Goldsmith became Consulting Radio Expert for the United States Department of Justice in 1912. While teaching at the College of the City of New York, Dr. Goldsmith took a keen interest in the development of radio telephony, and finally persuaded the authorities of the college to establish a course in wireless. He thus gained the distinction of presiding over the first course of this nature ever offered by a collegiate institution of learning in the United States.

From 1915 to 1917, Dr. Goldsmith, in addition to his teaching duties, was Consulting Engineer and Correspondent for the General Electric Company, and in this capacity he cooperated with Dr. Ernst F. W. Alexanderson in the development of vacuum tube radio telephony equipment. In 1915, his work in connection with radio telephony attracted the attention of the American Marconi Company, and two years later he came to this organization as Director of Research.

With the formation of the Radio Corporation of America in 1919, Dr. Goldsmith became Director of Research for the new organization, and devoted much of his time to a study of transmitting and receiving problems. It was not until broadcasting became popular, however, that Dr. Goldsmith came into his own. His researches in radio telephony qualified him superbly for the post of Chief Broadcast Engineer, which he was appointed to fill in 1922, and on January 1st, 1929, he was made Vice-President and Chief Broadcast Engineer. On April 19, 1929, his title was changed to Vice-President and General Engineer. Prominent among Dr. Goldsmith's contributions to the field of science are investigations in simplex and duplex radio telegraphy and telephony, tape recorder for high-speed radio reception, the electric phonograph, the photophone or recording of sound on motion picture films, precision radio measurements, high power broadcast transmission, and international relay broadcasting. With the formation of the National Broadcasting Company in 1927, Dr. Goldsmith became Chairman of the Board of Consulting Engineers. He is also Vice-President in charge of technical matters for RCA Photophone, Inc.

IN the present short-wave activities, we have all the uncertainties, thrills and opportunities which once existed in radio broadcasting. Just so long as broadcasting was an experiment, it had much charm for those of an experimental turn of mind. When broadcasting technique attained a sound engineering basis, however, followed by standardization and mass production of popular-priced receivers for living rooms and lay hands, the thrill of experimentation gave way to the sheer joy of practical entertainment.

Present-day short-wave radio, as far as we have gone, is much the same story. Today it has its thrills and trials and tribulations. Tomorrow, when it is reduced to standardized practice for lay as well as professional uses, it will find its place in the growing field of home entertainment. And the experimenters, not to be denied their rights, will turn to still shorter wavelengths which will then represent the frontier of practical radio communication.

Short and Long-Wave Receivers

The question is frequently asked: Why do the leading set manufacturers overlook short-wave receivers in their offerings? Do they realize the interest in and the demand for short-wave sets?

Set manufacturers fully appreciate short-wave possibilities and probabilities—as well as difficulties. The facts, that short-wave reception is the happy hunting ground of "experimenters," and that short-wave reception by simple apparatus is highly erratic, are the main

reasons why set manufacturers have purposely avoided the mass production of popular short-wave sets. When and if short-wave reception is reduced to a fool-proof practice, when and if the layman can tune in stations with the same ease as in broadcast reception, and when positive results may be obtained day in and day out, then, and only then, will short-wave sets find their way into the average living room. The practical will then replace the experimental; the main fun will be in tuning in distant, foreign programs, with certainty and genuine entertainment value, rather than in the tuning gymnastics and infinite patience of today. We are very far from this achievement as yet.

The Term "Short-Wave" Is Relative

Let us note that short-wave radio is a relatively recent development, and the term, "short-wave," is a purely relative one. A decade ago, anything below 500 meters was looked upon as short-wave practice. Yet broadcasting made the 200-550 meter band commonplace, and the frontier of radio communication was pushed far down below 200 meters; stopping first at 100 meters, then continuing down to 50, and it is now down to 15 meters in everyday work. The frontier of practical radio communication is now close to 5 meters, and already the wavelengths below that point are being explored. Some experimenters are working even below 1 meter. Obviously, then, short-wave radio is purely relative. In the future we shall have an entirely different conception of real short-wave

communication, for the trend is steadily towards shorter wavelengths.

The Heaviside Layer and "Skip-Distance" Effects

The past half-dozen years have served to eliminate much of the uncertainty of short-wave communication, although by the use of elaborate and expensive commercial equipment. The erstwhile pranks of high-frequency signals, once believed unavoidable, have by now been reduced to fairly definite laws or, if you prefer, rules of conduct. The general theory which governs the peculiar behavior of short-wave signals is known as the "Heaviside-Kennelly Layer Theory," which assumes that very short waves do not follow the curvature of the earth (as assumed in the case of longer waves) but are rather reflected, or refracted, by some medium in the upper atmosphere. This medium is held to be a stratum of rarefied air, existing about 100 miles above the earth's surface, and electrically conductive because of its ionized condition.

The height of the ceiling of this upper stratum rapidly changes, as the sun's rays act to vary the "electrical density" of the ionized condition. A low ceiling or ionized atmosphere tends to reduce the distant energy in a radio wave; so that such a wave may disappear entirely after traveling a hundred miles or even less from the transmitting antenna.

The radio wave is thought to be composed of two components; one a *ground wave* which travels along the curvature

AHEAD *With* Short Waves

Virtually a virgin field, high frequency radio affords an ideal opportunity to the experimentally inclined

By ALFRED N. GOLDSMITH, PH.D.

*Vice-President and General Engineer,
Radio Corporation of America*

of the earth, and the other a *sky wave* which is projected to the upper ionized stratum or Heaviside Layer. The sky wave is presumably reflected from (or refracted by) the under surface or ceiling of the ionized layer, at an angle towards the earth; this reflection being compared with the reflection of a beam of light by a mirror.

Thus, while the ground wave of a given radio station may be practically absorbed, a short distance from the transmitter, the reflected sky wave may reach the earth at certain points hundreds and even thousands of miles away, thereby accounting for real DX reception. It is this reflection of sky waves which accounts for the so-called *skip distance* in short-wave communication. This phenomenon, fortunately, varies according to the frequency or wavelength employed, the time of day, and the location of the transmitter. It becomes more noticeable at higher frequencies, within limits; and it is also dependent somewhat upon the seasons, the time of day, and the transmission path.

Variations in Wave Reflections Carefully Studied

The reflection by the Heaviside Layer is a matter which has received no end of attention from our commercial radio engineers. The R.C.A. engineers have spent years on short-wave transmission and reception conditions. Transmission and reception records and logs have been kept day in and day out, week by week, month by month. Variations during the twenty-four hours of the day, from season to season, and from year to year, over various circuits, have been carefully noted. Out of these trying and costly observations have been evolved the practical engineering facts of today; whereby engineers know precisely what frequency to employ for a given radio circuit at any time of the day or night, and for any season. The engineers are provided with carefully-computed tables, indicating the frequency most generally suitable for any hour or day of the year. These charts govern the frequency changes at

our transoceanic short-wave transmitting stations.

It is common practice to employ a plurality of frequencies for a given transoceanic radio circuit during the twenty-four hours of the day; in order to maintain the desired skip distance between transmitter and receiver. Transmitters are transferred from one circuit to another, in keeping with daylight, twilight, night, and dawn. Precise engineering data, in large measure, supplant the guesswork and just plain "good luck" of the past. Ample safety factors are employed at every possible step in transmitting and receiving practices. Nothing is left to mere chance. That is

SHORT-WAVE RADIO, the experimental field of today, is bound to become the practical field of tomorrow. The short-wave art is rapidly being reduced to standardized practice, based on sound engineering knowledge. In everyday communication, we have harnessed short waves down to 15 meters. Even the shorter waves are now being studied with promise of early commercial application. And, as the frontier of everyday radio is pushed back steadily, down the wavelength scale, the experimenter is always certain to find plenty of opportunities to pioneer and blaze the trail beside the engineers and commercial minds that follow along somewhat different paths, all leading to the continuous progress of radio.

Dr. Alfred N. Goldsmith.

why short-wave radio is playing such an important rôle in the handling of R.C.A. transoceanic traffic. It has proven practical quite as well as economical.

Why Commercial Stations Receive European Short-Waves Best

Yet, from the standpoint of amateur and lay application, short-wave radio is still largely an interesting experiment. Take the matter of transatlantic radio programs, for instance. Many wonder why programs from England, Holland and Germany are not received direct, by means of short-wave sets, rather than through the intermediary of the R.C.A. short-wave receiving station at Riverhead, on Long Island, and the N.B.C. networks. Unfortunately, few realize the elaborate preparations and equip-

ment necessary for the practical reception and rebroadcasting of overseas radio programs.

Years have gone into the preparation for present-day rebroadcasting of European radio programs. Reception tests have been conducted month after month, during many years. Quantitative measurements of intercepted signal strength have been made and filed for reference, under all manner of conditions. Many types of receivers have been designed, built and tried, until the present equipment represents the result of a rigid elimination contest.

Today, overseas programs are received under conditions fairly closely approaching the ideal, so far as our short-wave technique is concerned. The receiving station is located at a carefully-selected site, representing the best compromise between maximum intercepted signal strength and minimum local interference. Further to increase the signal-interference differential, directional antennae, virtually aimed at the distant transmitters, are employed.

Again, in order to combat troublesome fading common to transoceanic short-wave signals, the "diversity antenna" system is used, with a plurality of antennas and receivers; so that one is likely to score a fair average for the intercepted signal strength, at all times, fading or no fading. Finally, an automatic receiver selector (for the best signal at each instant) together with an automatic volume control insures the maintenance of the output at a given level. Is it any wonder, then, that the overseas programs are picked up with sufficient volume, clarity, and uniformity to be broadcast over the N.B.C. networks, while the short-wave fan can at times hardly pick up the same original signals with his own short-wave equipment?

From the standpoint of pure experimentation, overseas programs are a welcome challenge to the radio experimenter. They test his skill, resources, and

(Continued on page 313)

Newspaper Page Reproduced Via SHORT WAVES Across the Country



Recently a successful experiment was conducted between the short wave station W6XN at Oakland, Calif., and Schenectady, New York, when the front page of a San Francisco newspaper was reproduced by a new photo transmission and reception system. Photo at left shows Dr. E. F. W. Alexanderson with C. J. Young, who developed the system, both of the General Electric Company.


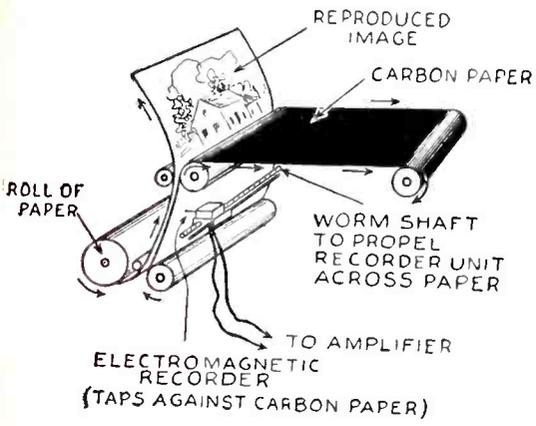




Diagram at left shows method used to translate short wave radio signals into facsimile of newspaper page in recent test over 2,500 miles distance between Oakland, Calif., and Schenectady, New York. The reproduced newspaper page is made up of three strips, the recording machine using paper 8 inches wide. A magnetic recorder taps against the carbon paper, giving an impression on the white paper.

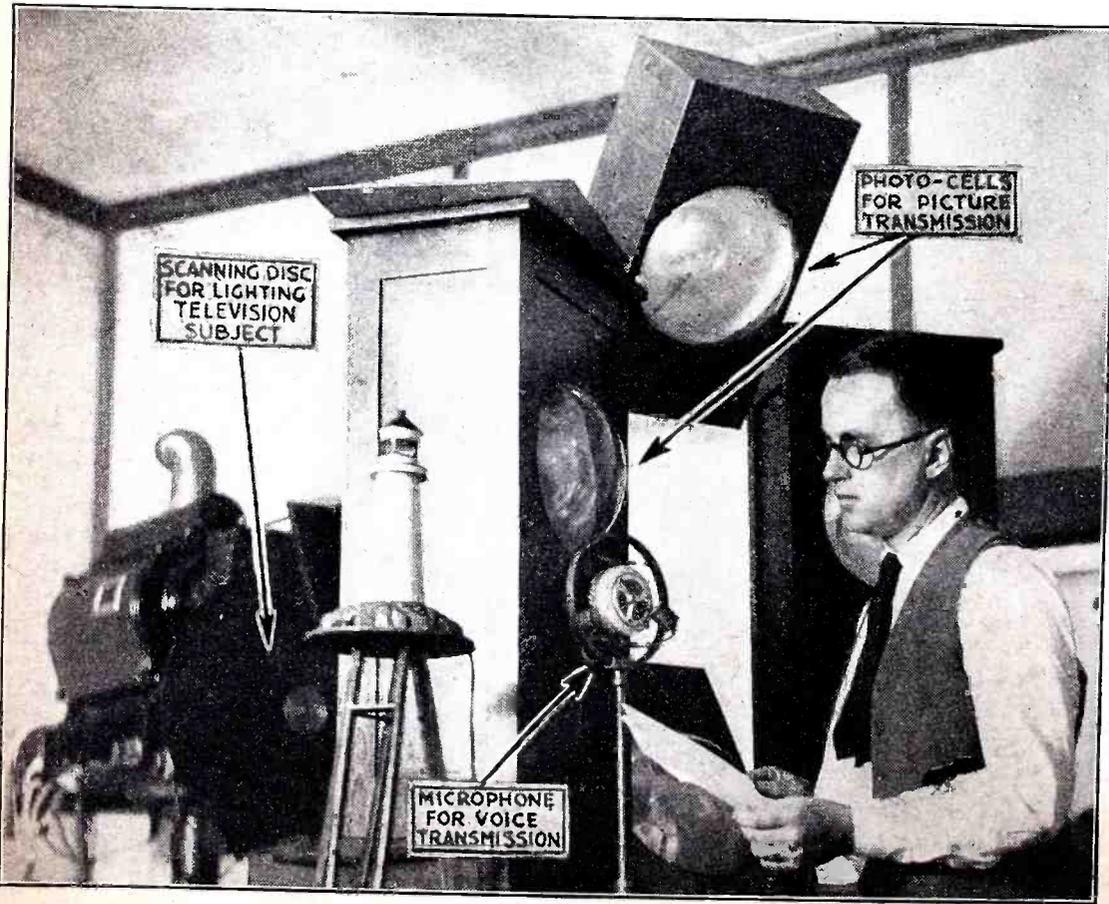



Simultaneous Sound and Image Transmission

BOSTON recently witnessed one of the most successful demonstrations of the simultaneous transmission and reception of the television image, together with the accompanying voice. The apparatus responsible for this demonstration is illustrated at the left. "Big Brother" Bob Emery had the pleasure of appearing before the televising transmitter, the large photo-electric cells of which are observed in the picture. Behind the photo-electric cells there is a rapidly revolving scanning disc containing a spiral of holes, which causes a pencil of light from the arc lamp shown at the left of the photo, to traverse the speaker's face from top to bottom in rapid fashion many times a second. The speaker's voice was picked up by the microphone seen standing just in front of him. The sound waves were transmitted by Station WEEI on one wavelength, while the television image waves were transmitted by Station W1XAV.

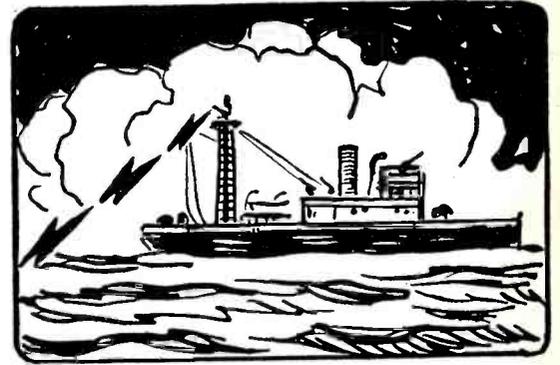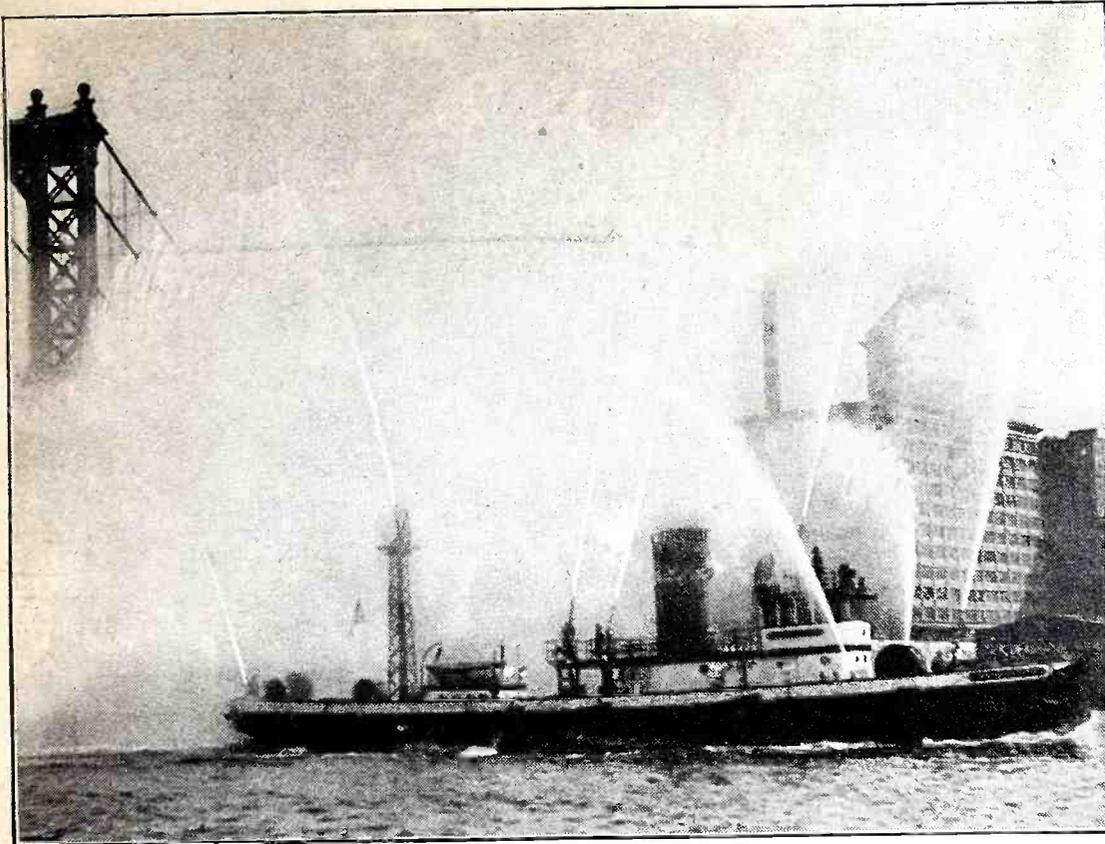Short Wave Radiophone
Keeps
FIREBOAT
in Touch with
SHORE




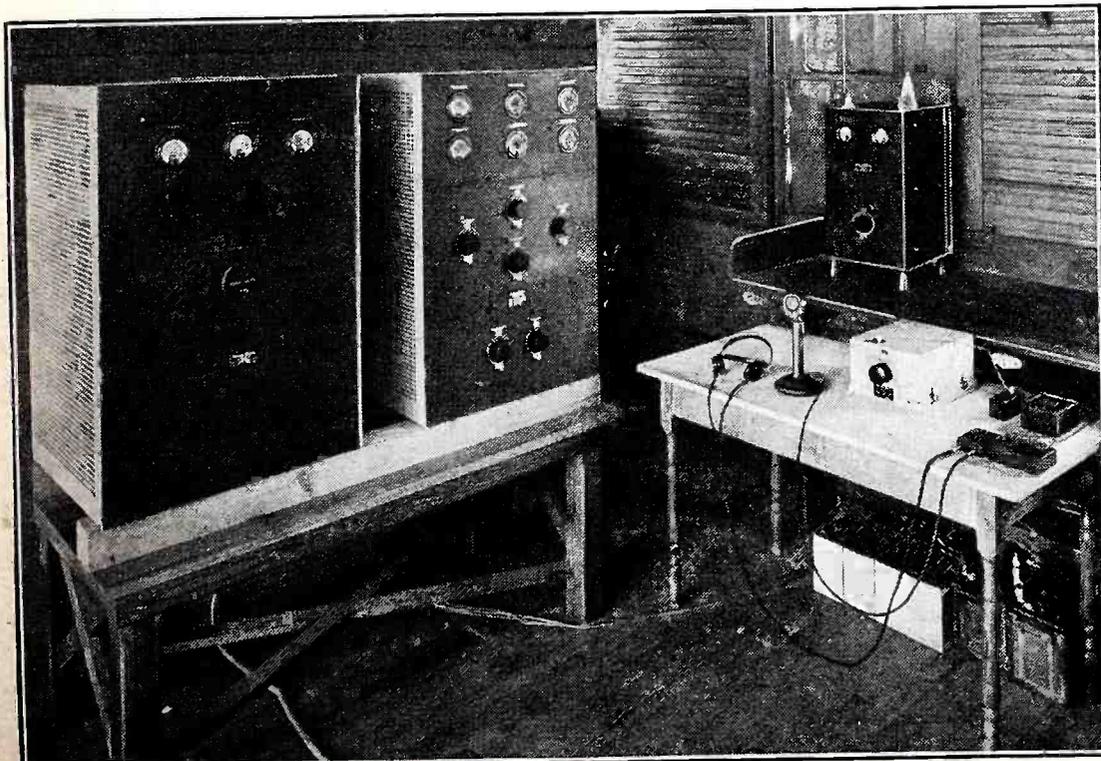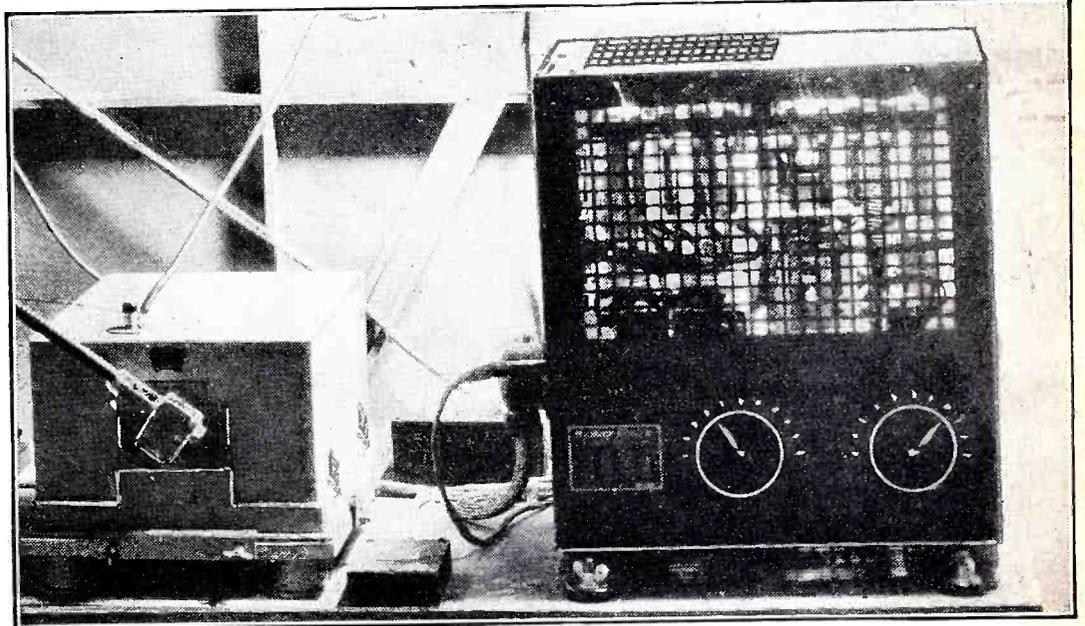SUCCESSFUL tests were recently carried out with the newly installed short wave radiophone transmitter and receiver installed aboard the New York City fireboat "John Purroy Mitchell." The above radio station which communicates with the fireboat, as she cruises around the harbors and rivers adjacent to New York City, is located at the Marine Fire



Top photo shows radiophone equipped New York City fireboat "John Purroy Mitchell." Photo above shows Short Wave transmitter and receiver aboard the fireboat, while photo at the left shows shore radiophone apparatus installed at Marine Fire Department Headquarters.

Department Headquarters at the Battery, and has been assigned the call WCS. The radiophone transmitter aboard the fireboat is located below decks and has remote control wires leading to the pilot house above. The photo at the center of the page shows receiver and transmitter used on board the fireboat. Both stations employ a wavelength corresponding to a frequency of 1596 kilocycles (188 meters). The recent tests were very successful and the fire chief's voice was picked up aboard the fireboat as she cruised around the harbor and was reproduced on the loud speaker in the pilot's cabin so that everyone could hear
(Continued on page 320)

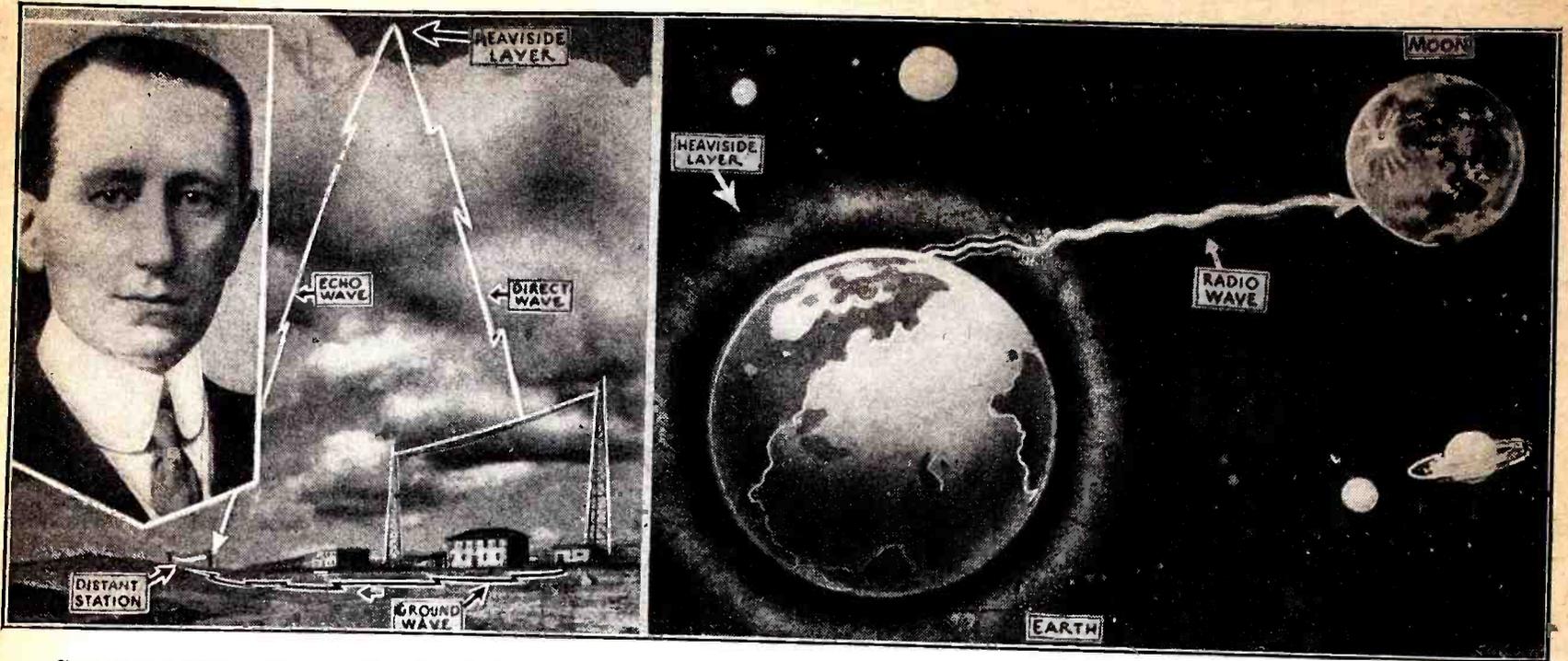

Guglielmo Marconi recently stated that he believes directed "beam" waves can and do penetrate the Heaviside layer, reaching out into space to distances as great as 48,000,000 miles. Picture at left shows "earth-bound" ground and echo waves, the latter reflected by the Heaviside layer.

CAN We RADIO the

A New Use for Amateur Radio

IF someone had made the statement, forty years ago, that you could send a message clear around the world without the use of wires, even the greatest electrical experts of the day

would have strongly doubted the sanity of the man making such an assertion.

We are getting rapidly over the wonderment created by radio and are becoming accustomed to the impossible.

In the February, 1927, issue of RADIO NEWS (of which I then was the publisher) appeared an illustrated article written by myself and entitled "Can We Radio the Planets?" which is reproduced at the end of the present article.

The 1927 article is chiefly interesting because it came in for a good deal of ridicule at that time; while today Marconi, in conjunction with many other scientists, has reached the conclusion that it will not be long now before it will indeed be possible to send radio signals to the heavenly bodies.

As I said in my former article, again I do not wish to have the meaning misconstrued when I speak of signaling the planets. There is no idea in my mind, at the present time, of communicating with imaginary inhabitants of the Moon, Mars or Venus. The purpose of sending signals is purely for scientific research which will, in due time, give us a much better understanding of radio waves. It is admitted today that we know practically nothing of what happens to the radio wave after it leaves the transmitting aerial and until it impinges on the receiving aerial.

The thoughts which I advance here, I believe to be new so far as radio amateurs are concerned, and I also believe that in due time something will come of them.

No doubt, the radio amateurs will remember that I am the one who in 1910 fought their battles in Washington; and an editorial which I published in the February, 1912, issue of MODERN ELECTRICS became the basis of the present radio law, whereby the radio amateurs

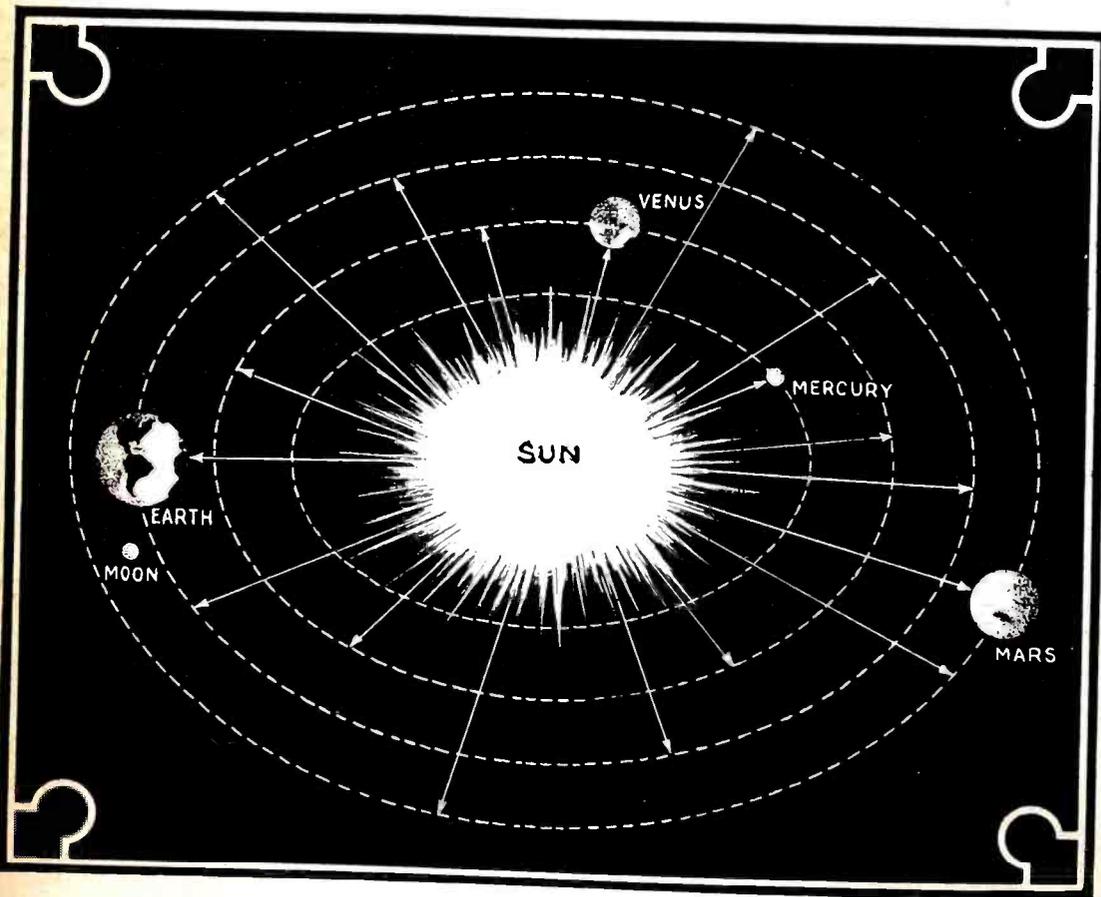


Fig. 2—A "celestial" vacuum tube, in which the sun gives off the electronic stream in the direction of the arrows. The various planets may be taken respectively as plates and grids in a multi-element tube; while the atmospheres of the planets are analogous to the gas adhering to the plate and grid, as shown in Fig. 1.

THE author of this article presents some new views on how radio amateurs, with modest equipment, can now actually experiment by sending signals to the Moon, which, reflecting the radio waves, should make it possible to have other amateurs receive them at another point on our planet.

Our front cover depicts this idea graphically. While revolutionary, the idea is by no means new, and recent scientific investigations tend to show that it may already have been accomplished.

Scientists have believed until recently, that the so-called Heaviside layer would serve as a barrier to any radio waves which might try to leave the earth. Recent research and experiments, however, have shown that certain short-wavelengths apparently penetrate the Heaviside layer and are reflected by some heavenly body, or possibly by streams or bands of electrified particles in space, for the simple reason that the signals were received after an unduly long time. There are other theories as to where the delayed signals may have spent their time, but the most plausible is, that they actually penetrated the Heaviside layer, sped outward into space where they struck some heavenly body, for example, and were reflected on a long journey back to earth, where a receiving instrument recorded them.

PLANETS?

By HUGO GERNSBACK


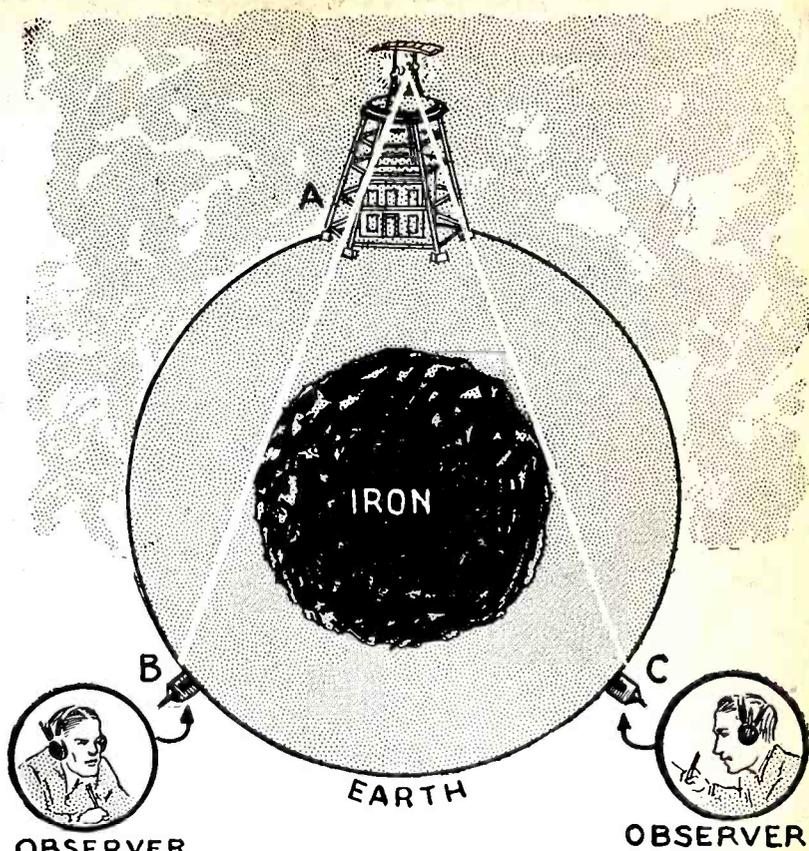


Fig. 4 shows a radio beam-transmitter "A" at some point on the globe, transmitting a beam to "B" or "C". As the angle of the beam is varied, the respective observers will get the signal either strongly or not at all. By this system it will be possible to explore the interior of the earth, to ascertain the size of the earth's iron core.

were allotted the territory below 200 meters. At that time, the authorities in Washington thought this was a good joke on the amateurs; because no one knew what to do with wavelengths below 200 meters and they were thought then to be of little use.

It may well be that history will repeat itself and interplanetary signalling will open up avenues totally unsuspected today.

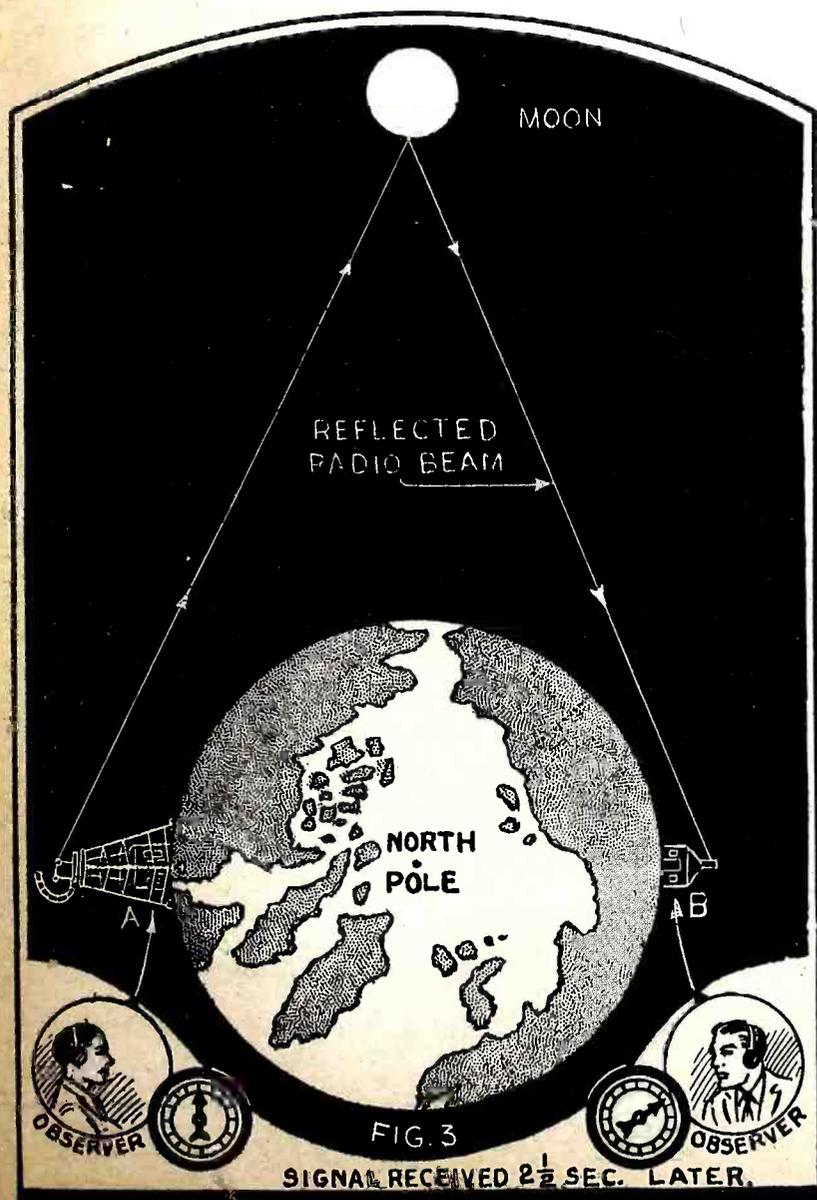

Fig. 3 shows how, by means of a powerful beam transmitter, located at some point "A" on our globe, we can send a beam of radio waves to the moon, which, being more or less metallic, will reflect the beam at the same angle. An observer, located at "B" on the opposite side of the earth, will receive the signal back from the moon, a distance of 238,000 miles, in two and a half seconds after it leaves the transmitter "A".

I need not tell the transmitting amateur that with very little power it is possible today to literally radio around the world. Five- and seven-and-a-half-watt short-wave transmitters have been heard half-way around the world, repeatedly. Of course, we still have the old "Heaviside layer" bugaboo to contend with; it is even doubted by some authorities that it is possible for any sort of short wave to penetrate the Heaviside layer and leave our planet. I emphatically disagree with these authorities for the following simple reasons: radio waves are electromagnetic waves, like light. Little proof is required that light waves from regions of other worlds do pass through, not only the Heaviside layer, but the atmospheric layer as well. It is admitted that light waves in their passage through these layers are refracted; and this refraction is the counterpart of the "reflection" of radio waves in the Heaviside layer.

When, however, radio waves become sufficiently short, I do not believe that the Heaviside layer will stop them, any more than it stops the light or heat waves. Indeed, we have already joined, in the electromagnetic spectrum, radio waves and heat waves; so that no longer is it possible to distinguish between them, since they merge at some indefinable point.

No one knows, at the present time, what kind of short radio waves will penetrate the Heaviside layer; they may be waves of 5 meters or of 5 centimeters or 5 millimeters. No one knows, because no one has as yet tried it; and here is where

(Continued on next page)

the radio transmitting amateur comes in. The problem is not as difficult as we might believe. We know from experience that even minute power makes it possible to communicate over great distances on earth by means of short waves. If the right wave is finally selected, I sincerely believe that, with power from 100 watts upwards, it may be possible to

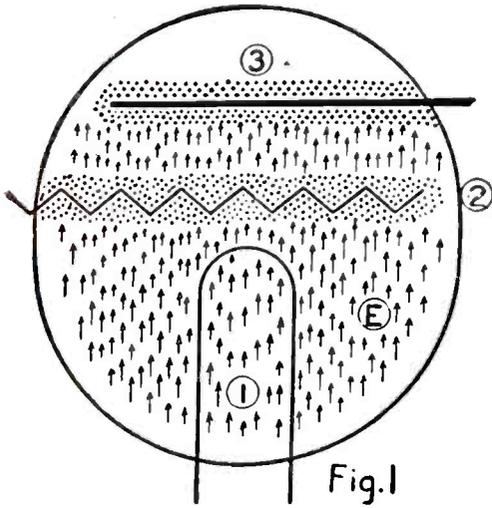


Fig. 1 shows the interior of a vacuum tube where (1) is the filament, E is the stream of electrons going in the direction of the arrows, (2) is the grid, (3) is the plate. The small dots surrounding the grid and plate indicate a layer of gas always adhering to metals, a miniature Heaviside layer, which the electrons must pierce.

send a wave to the Moon, and have it reflected back to earth without undue difficulties.

If this belief is correct, it will then be possible for a group of amateurs to do the following: the system used in Fig. 3 can easily be used. The transmitting amateur, let us say at some point in North America, by means of a direct aerial (as shown also on the front cover of this magazine) directs the radio wave at the Moon when it is at the proper elevation. The Moon, as well as most of our planets, is partly metallic in substance. The Moon, therefore, will serve as a gigantic reflector and, if the wave leaves the earth and penetrates the Heaviside layer, and is enabled to travel the distance of some 240,000 miles, the wave will then be reflected; just as the sun's light rays are reflected from the Moon, making it possible for us to see the Moon.

If, now, another amateur stationed on the other side of the globe, let us say Australia or South America, has also a directive aerial pointed to the Moon overhead, he should be able to record the signal, if this theory is correct.

If the transmitting and receiving amateurs are possessed of chronometers and signals are sent out, let us say, at the beginning of every minute on a pre-selected day, the receiving amateur will note the incoming signals, which should be received by him in about 2½ seconds. The reason is that radio waves, like light waves, travel at the rate of 186,000 miles a second. A little calculation will show, therefore, that for them to go out to the

Moon, some 238,854 miles, and return, will take a trifle over 2½ seconds. If a great number of observations are made in this manner, it is possible to come to an exact result; and we will be enabled to learn a lot more about radio than we know today.

I would advise amateurs making these tests that everything is not as simple as it might seem from this rough outline. One thing the amateur should realize is that he should have the assistance of a competent astronomer, who will guide him in minor problems that come up during these experiments. One of the problems, for instance, is that neither the earth nor the moon is at rest, with regard to the other, and that they move constantly. All this must be taken into consideration when tests are made. Another point to remember is that, while ultra-short waves may pierce the Heaviside layer, yet they will be affected by it by some sort of refraction, just as light waves are refracted through the atmosphere. Unless these factors are compensated, serious errors are liable to creep up; and, not only that, signals may be missed entirely, because they may never reach the Moon, which is the target, and therefore they cannot be reflected or received.

Yet, the cost of these experiments is not prohibitive, even to the modest amateur; and the fame that will come to him and his co-workers, when sufficient proof is received that signals have actually been sent to the Moon and back, will compensate them for all the time, money and effort that have been expended on the experiments.

Just what benefits we will derive from turning the trick, no one can even remotely perceive today. It is certain that, sooner or later, man will travel, not only to the Moon, but to other planets, by means of space-fliers; and before that happens, science should certainly be in a position to say whether it will be possible or not to communicate with such fliers, once they have left the confines of the earth.

Can We Radio the Planets?

By HUGO GERNSBACK

Member of American Physical Society

WHEN Jan Lippershey built his first telescope in 1608, he came in for severe condemnation, because it was argued that such an instrument of the devil could never do any good. When our own Percival Lowell first propounded his theory of the Martian canals and Mars as the abode of life, he, too, was greatly ridiculed as a visionary; and even today orthodox astronomers do not share his views. When the first telescope was built, the then intelligentsia could not see any good in it, except as an instrument of the devil; so when I ask the question, "Can we radio the planets?" I know that I shall be subjected to not a little ridicule.

The telescope and spectrum analysis have opened the heavens to us to a tremendous extent, and enriched our scientific knowledge immeasurably. Spec-

trum analysis has shown us that stars, millions of light years removed from us, are constituted of identically the same matter as that found in our own earth; making it, therefore, reasonably certain that the entire universe is composed of practically identical matter, with little possibility of exception.

As you will see further on, when I propound the question, "Can we radio the planets?" I do not necessarily imply that in doing so we can send intelligence to Mars or to Venus, or to the Moon, with the expectation of getting an answer—although the latter may not be as impossible in a hundred years as it is now. I am simply trying to show that, by making a start, the greater the art of radio and our knowledge thereof will become.

The largest telescopes have been made possible through the generosity of our wealthy people, and it is, therefore, not impossible to hope that what has been done in building telescopes can be duplicated in building super-power stations for radio for research purposes. I might say, right here, that the benefits derived from such a super-power radio station will no doubt be vastly greater than from building a telescope, and for the following reasons:

The telescope is useless when it comes to exploration of our own earth. It is built to explore the heavens. A super-power radio plant can be used, not only to explore the heavens, if I may call planetary space such, but also for tremen-

(Continued on page 314)

TABLE OF VIBRATIONS		WHOSE EFFECTS ARE RECOGNIZED AND STUDIED	
		Number of Vibrations per Second	
1st Octave	2	
2nd "	4	
3rd "	8	
4th "	16	
5th "	32	
6th "	64	
7th "	128	
8th "	256	SOUND
9th "	512	
10th "	1,024	
15th "	32,768	
20th "	1,047,576	UNKNOWN
25th "	33,554,432	
30th "	1,073,741,824	ELECTRICITY
35th "	34,359,738,368	
40th "	1,099,511,627,776	
45th "	35,184,372,088,832	UNKNOWN
46th "	70,368,744,177,664	
47th "	140,737,468,355,328	HEAT
48th "	281,474,976,710,656	
49th "	562,949,953,421,312	LIGHT
50th "	1,125,899,906,842,624	CHEMICAL RAYS
51st "	2,251,799,813,685,248	
57th "	144,115,118,075,855,872	UNKNOWN
58th "	288,230,376,151,711,744	
59th "	576,460,752,303,423,488	X-RAYS
60th "	1,152,921,504,606,846,976	
61st "	2,305,843,009,213,693,952	
62nd "	4,611,686,018,427,389,904	UNKNOWN

In this table, beginning at the 25th octave and ending with the 45th, we have what may be termed the radio band of vibrations. It is thought that, as we approach wavelengths or frequencies near those of heat, it will be readily possible to pierce the Heaviside layer.

Short Waves for the Broadcast Listener

How to Convert an Ordinary Broadcast Receiver Into A S-W SUPER-HET.

By CLYDE A. RANDON

The Superheterodyne is occupying the attention of leading short wave fans today and in the present article by Mr. Randon we are taken through a complete course on just how the superheterodyne works, and how we may apply its principle in conjunction with our standard broadcast receiver for the reception of short wave stations. Constructional and winding data for the short wave coils are given. This system allows you to use the high quality audio amplifier in your broadcast receiver.

FOR the broadcast listener there are thrills galore on the short waves. The reception of broadcast programs in the ordinary broadcast range becomes monotonous to experimenters, due to the sameness of the programs, and those who desire to


mitter. Short waves, however, have the peculiar property of returning to earth at a distance with better signal strength, due to a so-called "skip-distance" effect which becomes more pronounced as the wavelength is shortened.

If the reader has had any experience at all with distance reception, he will realize that nearby stations often cause difficulty in the reception of distant programs on an average receiver. The stations on the short waves are comparatively few and, if one is properly located, one can experiment to his heart's content until the station is finally tuned in. That is one advantage, but there is another and more important one.

For distance work in the broadcast range it is desirable to stay up late at night. Some don't mind so much, but others who prefer sleep to DX (we all do after we lose enough of the former) find that late hours and work the following day simply do not agree. The short waves give exceptional distance even in daytime, to say nothing of the early evening hours, which are undoubtedly those when the experimenter desires to try his luck. It is not uncommon to hear over three thousand miles in daytime (at noon) at a wavelength of 20 meters. The short waves, therefore, are of considerable interest to DX fans.

An important motive which keeps many

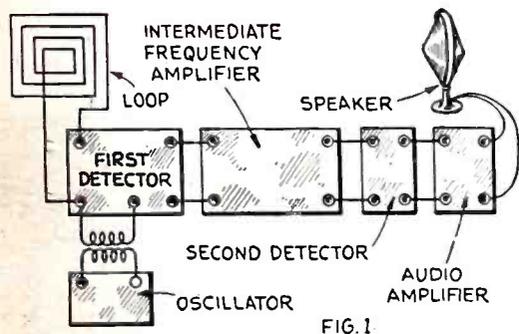
people away from the short waves is that they simply do not care to put out additional money for short-wave radio sets. Yet the broadcast set you now have can be used in its entirety for short-wave reception, by connecting ahead of it a simple frequency-changer, the construction of which will be described.



Arrangement of the units comprising an ordinary superheterodyne receiver.


receive distant stations are often disappointed because only under the most unusual conditions is a station thousands of miles away heard in the broadcast range. However, on the short waves the reception of stations from very great distances is the rule rather than the exception, because distance work is more favorable to waves of short length.

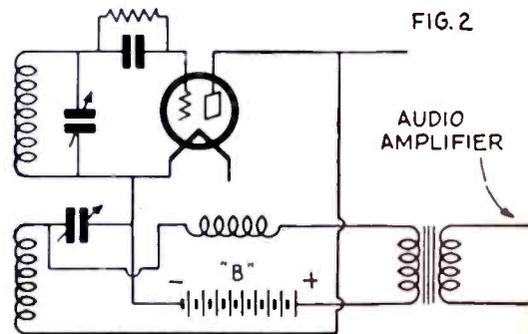At ordinary broadcast frequencies the waves return to earth nearer the trans-




Circuit diagram of ordinary short wave, regenerative detector system; this is the essential arrangement for an ordinary short wave adapter.

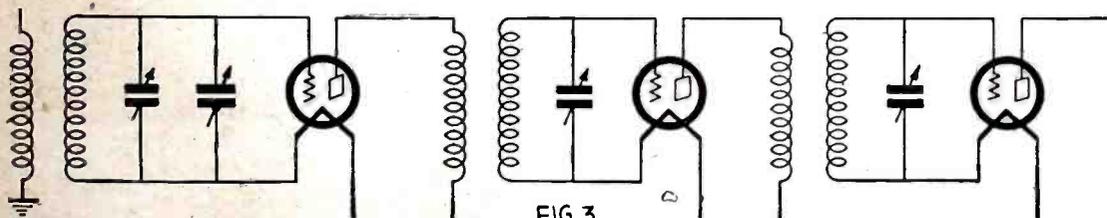This, by the way, is not an ordinary adapter, but a simplified *superheterodyne* arrangement by means of which all the tubes in your present broadcast receiver can be used to the greatest advantage. Many foreign stations can be brought in on the loud speaker at the hour when



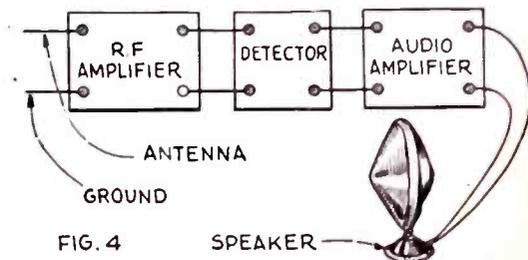Typical connections of a tuned radio frequency amplifier for the reception of broadcast wavelengths. Such an amplifier can be utilized as an intermediate frequency amplifier of a short wave superheterodyne, in the manner clearly explained by the author.



Set-up of an ordinary broadcast receiver; for short wave reception it is too difficult to change both the R.F. and detector units, so usually the detector tuning unit is changed.

reception is best from the particular country.

Various Receiver Arrangements

The superheterodyne arrangement for reception is the most sensitive yet devised. A good superheterodyne will receive on a loop aerial what an ordinary set requires a full-length outside aerial for.

The units comprising a superheterodyne receiver are shown in Fig. 1, while in Fig. 2 the essential connections of an ordinary adapter are shown. The tube used as detector in the latter will depend upon the tube used in the detector socket of the broadcast receiver. A.C. tubes can be used if desired, the fundamental connections remaining the same. In the detector circuit shown the regeneration is controlled by means of a variable bypass condenser. Some arrangements use resistance control of regeneration; both schemes have their advantages and disadvantages. Unless a variable resistor of high quality is available, the condenser scheme of control is ordinarily to be preferred.

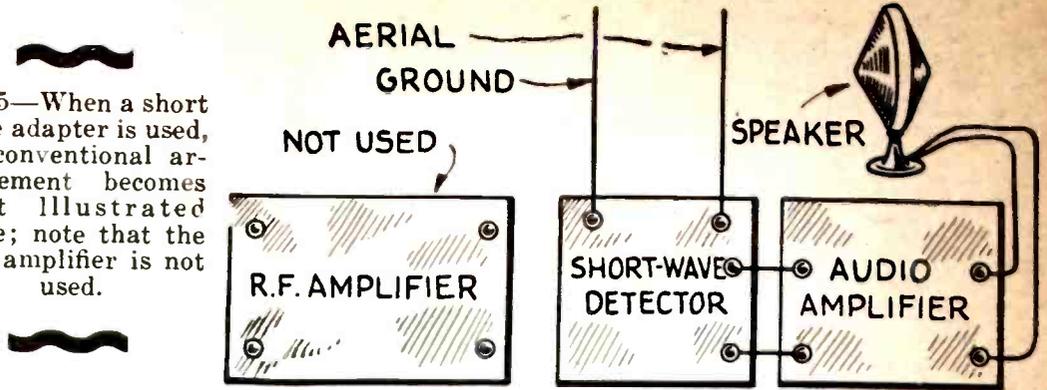


Fig. 5—When a short wave adapter is used, the conventional arrangement becomes that illustrated above; note that the R.F. amplifier is not used.

In Fig. 6 an ordinary broadcast receiving set is indicated at A. When the frequency-changer is put ahead of it, the R.F. amplifier becomes the intermediate-frequency amplifier of the short-wave superheterodyne, as indicated at B. The detector unit of the broadcast set then becomes the second detector and the audio amplifier of course remains the same. Compare this arrangement with Fig. 1.

The short-wave detector of Fig. 2 (construction described later) is converted

With one additional tube (in the form of a Hartley oscillator) more than is required for an ordinary adapter, the R.F. tubes of the broadcast receiver are utilized as the intermediate-frequency amplifier. Thus, adding only one tube results, really, in the addition of a whole R.F. amplifier (which may be as much as four tubes in some sets). It is readily apparent, therefore, that the additional oscillator is well worth while.

Almost all short-wave sets require two controls. Note that the superheterodyne arrangement uses the same number—one on the oscillator and one on the tuned circuit of the "first detector." The results with an arrangement like this are simply surprising. In some sets the proper conditions do not exist for the short-wave detector when it is plugged in. By using the frequency-changer ahead of the set itself, the conditions can be chosen correctly for the type of tube employed.

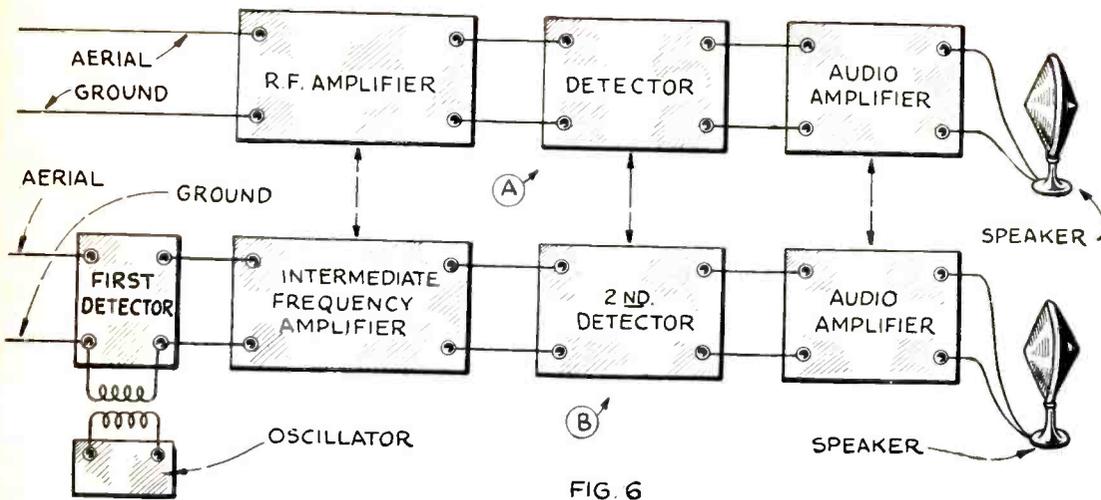


FIG. 6

This diagram shows clearly the development of a short wave superheterodyne receiver from an ordinary broadcast receiving set.

Fig. 3 shows the essential connections of an R.F. amplifier for broadcast work. With an ordinary detector-adapter for short waves, this amplifier is not employed, only the audio channel being used.

When an ordinary adapter arrangement is plugged into the detector socket of a broadcast receiver, one is simply substituting a short-wave detector for the detector ordinarily employed. Evidently the R.F. stages in the broadcast receiver (like those of Fig. 3) are not employed because they do not tune to short waves. The aerial and ground are therefore connected directly to the short-wave receiver.

Fig. 4 shows the arrangement in a typical broadcast receiver "chain," and Fig. 5 the same broadcast outfit after the short-wave detector has been plugged in.

Advantages of the Frequency-Changer

By using a superheterodyne arrangement in front of the entire broadcast receiver, it is possible to use all its R.F. stages, thus building up the signal greatly before impressing it upon the detector.

into the first detector of the superheterodyne, while the oscillator is a separate Hartley arrangement which will be discussed later.

The arrangement shown was designed only for short-wave broadcast reception, but it may be used, with special adjustment, for code work, for which it is necessary to provide a regenerative second detector. A broadcast receiver already provided with a regenerative detector will be best for this purpose; such, of course, can be used for music also.

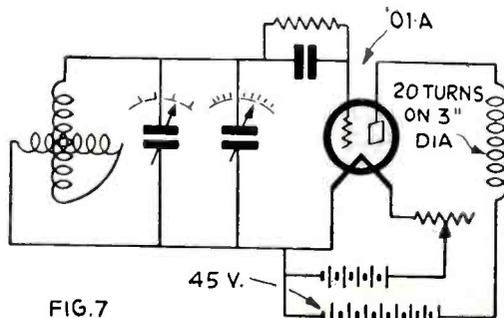


FIG. 7

Detector unit using a variometer with two midget variable condensers, the larger one being used for rough tuning.

Simplicity of the Circuit

The first detector is just an ordinary detector unit consisting of a suitable tube and a tuned input circuit. This detector is non-regenerative and therefore no tickler is required. Since no regeneration condenser or tickler coil are used, the unit is really very simple. The regeneration-control condenser, normally used with an adapter, is now incorporated in the oscillator, so that, all in all, the only extra apparatus required is one lone tube in the oscillator.

Since no tickler is necessary, the arrangement (if plug-in coils are used) can be simplified greatly. There need only be two connections to the coil and thus the plug-in attachments are extremely simple in construction. There is, also, no bother in obtaining the correct directions for winding the coils.

While ordinary small plug-in coils wound on tube bases are easy to construct and use for the experimental sets,


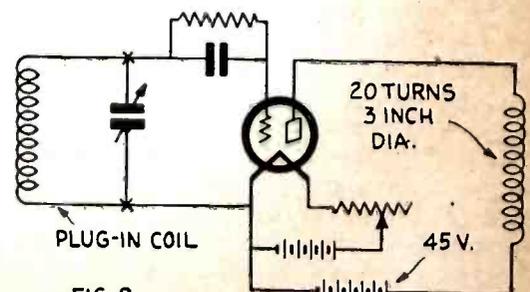


FIG. 8

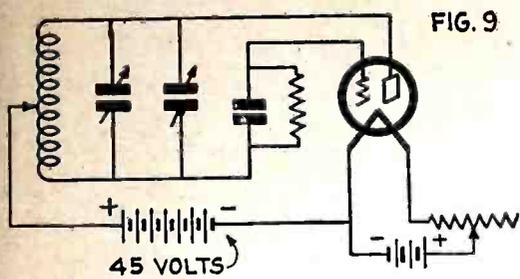First detector arrangement, using plug-in coils; the plate coil is not necessary in some cases.



Circuit diagram of oscillator used with the short wave superheterodyne receiver.

The experimenter will find real enjoyment in experimenting with different values; to change the intermediate frequency the dial of the receiver is simply turned to the desired value. It will be found that by simply changing the aerial connections one can turn from locals to short-wave stations. This is a very interesting stunt to perform on visitors. It is really a spectacular stunt to be able to pull in a very distant station in broad daylight.

are wound on UX tube-bases, and the condenser used is 30 mmf.

Turns	Range in meters
8	17-25
11	24-34
17	34-43
22	44-64
55	63-100

If coils 2 inches in diameter are used the number of turns will be less for a given range. It is desirable in any case, of course, to have overlapping ranges, to obtain a continuous tuning scale.

It is unnecessary to provide a coil for coupling the oscillator and first-detector together. There will be sufficient pick-up from the oscillator, even at a considerable distance, to give good results. The input circuit of the first detector is tuned to the short-wave station and then the oscillator-dial is operated until the fundamental frequency of the oscillator (or one of its harmonics) differs from that of the broadcast station by the value of the frequency to which the broadcast receiver is tuned. If, for example, the receiver is tuned to 1,000 kilocycles (299.8 meters) and it is desired to receive a 30-meter broadcast station, it will be necessary to tune the oscillator until its fundamental (or harmonic) differs in frequency from the 30-meter wave by 1,000 kilocycles (also called one megacycle). Thirty meters is 9,994 kc., to be exact; the oscillator is adjusted to either 8,994 or 10,994 kc. It is better to tune to the "long-wave side."


Since the two frequencies, beating together, produce a third frequency equal to the exact difference between the two original frequencies (as in any superheterodyne receiver) there will exist in the plate circuit of the first detector a 1,000 kc. signal. Since the broadcast R.F. amplifier is tuned to this frequency, the signal will be amplified still further, and finally appear at the loud speaker with good volume.

Design of the Oscillator

There are some important points regarding the design of the oscillator (Fig. 9, and suggested baseboard layout in Fig. B). An ordinary tube oscillator has ample power for all ordinary purposes; consequently, if any useful result is ob-

Coils Readily Made

A variometer arrangement may be finally used, but for experimental purposes the average experimenter will use an ordinary plug-in arrangement like Fig. 8 (a suggested baseboard layout is shown in Fig. A). This will not be particularly troublesome, because of the simplicity of the input circuit to the first detector. A midget condenser of about 50 mmf. will give good results, and the tuning will not be very sharp. Of course, the smaller the condenser the less the range covered, so the stations will be spread out better on the dial. A vernier dial can be used with the larger condensers, with good results. A very small condenser will require a larger number of coils to cover a given

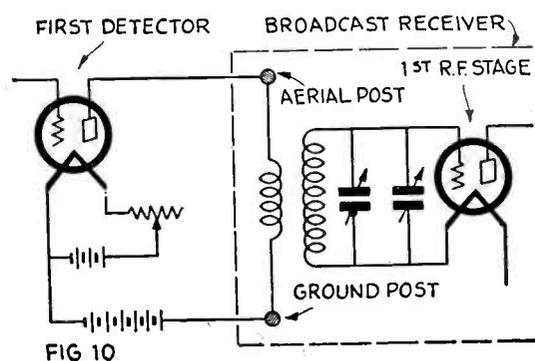

Typical input circuit to first R.F. stage of broadcast receiver, with connections to first detector shown.

range; a 30-mmf. midget variable condenser will usually give good all-around results.

Although the exact coil sizes will depend upon the tubes used and factors of construction, the following data will be approximately correct for the bread-board arrangement of Fig. A. The coils

the reader may desire to use a variometer (See Fig. 7) so that the entire short-wave range can be covered without changing coils. Some of the large variometers formerly used for broadcast work will be suitable for this purpose after some of the turns are removed from both the rotor and the stator. Often it will be necessary to remove both windings entirely and rewind them with spaced turns, in order to keep the losses within reason at high frequencies.

Of course, the ideal construction would be a rotor and a stator with spaced windings, on skeleton forms. The best results will be obtained with a good separation between the windings, because of the capacitive effects, but this should not be too great.

For experimental work one naturally uses the parts available, so that no exact variometer specifications are given. The dimensions also depend upon the detector unit employed. It is well to remember that, when the two windings in a variometer are aiding, the inductance is given by the sum of the windings plus twice the mutual inductance between the two windings. The inductance of a coil increases as the square of its turns. The ratio between the number of turns in the coil and the wavelength to which the circuit tunes is therefore direct. Knowing the approximate sizes required when using ordinary single-layer coils and the simple rules of inductance variation, one can get fairly close even without trying.

Choice of Frequency Simple

The object to be attained by a first detector is to create, in the plate circuit, an intermediate frequency, lying in the broadcast band, and which should be so chosen so that no station is operating at this frequency. Otherwise, in spite of the fact that the antenna is connected to the first detector, the signals will "ride through" the set, and interference will result between short-wave and ordinary broadcast stations. Especially is this true of powerful locals.

One can easily find on the receiver-dial some point at which there is no station, or may tune the set between two stations should it be desired to use an intermediate frequency in this vicinity. Some receivers give a greater gain in the R.F. amplifier at the lower broadcast wavelengths, due to regenerative effects, so that if a lower wavelength is used the amplification in the intermediate-frequency section will be greater. However, there are also advantages in using the higher wavelengths.

Simple switching arrangement utilizing two single-pole, double-throw switches, either of the knife or cam variety, which permit rapid switching of either short wave or broadcast receiving set on to aerial and ground connections.

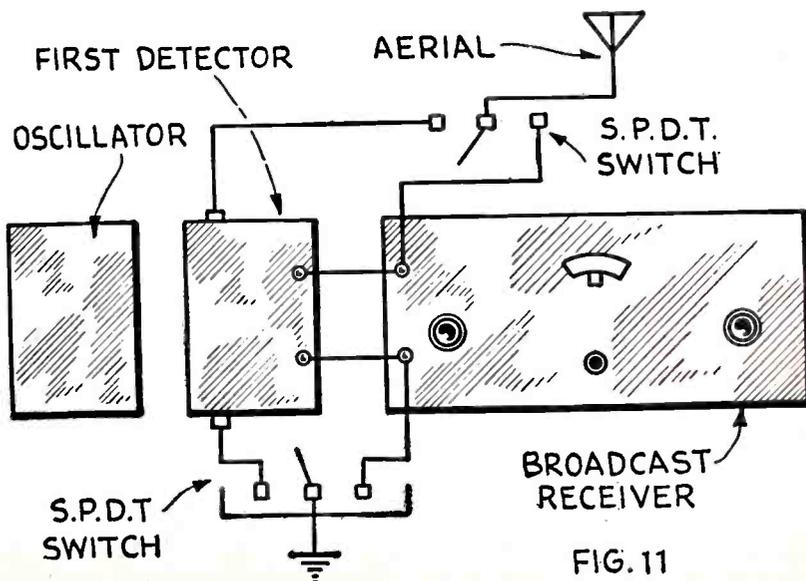



FIG. 11

tained by operating it below maximum efficiency, it is desirable to do so. The only objection (besides that of extremely sharp tuning) to the use of a very large condenser in a short-wave tuned-circuit is that the high capacity results in low efficiency, because of the relatively large currents in the tuned circuit. To apply high voltage between filament and grid of a receiver, a relatively high value of inductance is desirable.

However, an oscillator designed for lower efficiency can be made to cover a very wide range with but a single coil in the oscillator circuit. Naturally the tuning will be sharp, but (as shown in Fig. 9) a vernier can be used for finer adjustment. This vernier should be, preferably, 50-mmf. size, because the range covered by a given vernier is less when the capacity in parallel with it is higher. If the oscillator is shielded, no extension handles will be necessary.

An ordinary 23-plate condenser can be used in the oscillator. It is convenient to mount the oscillator on a baseboard, or in a separate cabinet, so that it can be used for a variety of tests, or wave-meter calibration, in conjunction with the broadcast receiver.

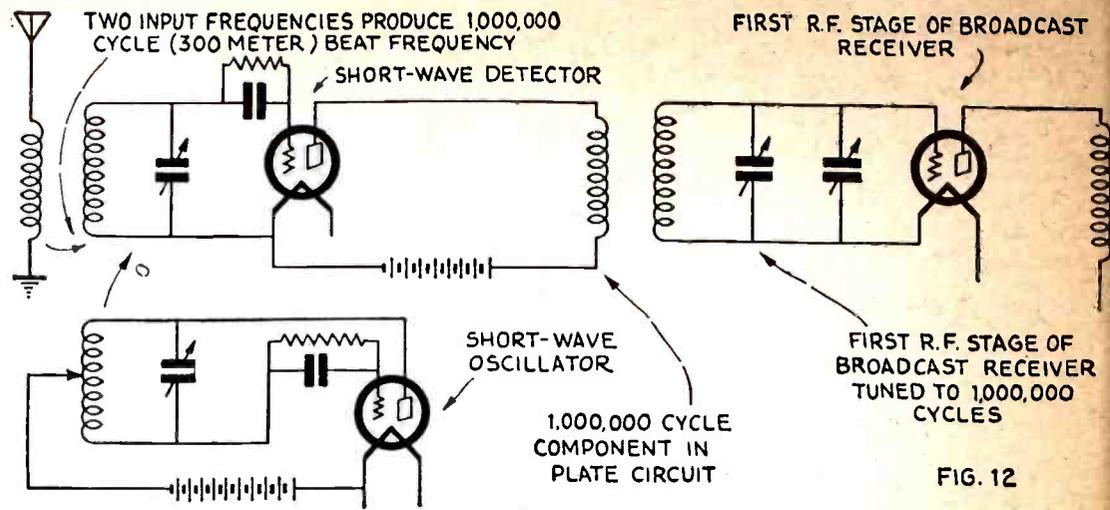If the condenser values mentioned above are used, a 3-turn coil, on a 3-inch diameter, will cover the lower short-



Circuit connections for a sensitive short wave superheterodyne receiver; all the tubes in the broadcast set are used with this arrangement.

additions, or a small filament-transformer which gives the desired 2.5 volts at the proper current value is employed.

The oscillator condenser, if provided with a suitable vernier, can be made to cover a rather large range. If a smaller range is desired, without a vernier, the coil sizes suggested for the receiver will serve. If a .00035-mf. receiving condenser is used in an oscillator (a 23-plate size, often found in the junk box, will cover a larger range), coils two inches in diameter will cover the follow-

Turns	Range (Meters)
50	270-560
33	200-280
17	100-230
9	50-140
3	17-55

These values are suggested also for a wavemeter to cover the lower ranges.

Coupling the Output to the Broadcast Receiver

Of course, the input circuits to different broadcast receivers differ so much that one should find out the circuit from a nearby radio store, if it is not already known. Service Men usually keep files of the circuits of common radio receivers. Remember, in any case, that the object to be obtained is simply to couple the "broadcast signal" into the broadcast receiver.

The frequency-changer has simply changed the short-wave signal into an ordinary broadcast signal; the object is to impress it into the first R.F. stage. A typical input connection for an ordinary broadcast receiver is shown in Fig. 10. If the first R.F. stage has a primary coil, as shown, it will not be necessary to wind a special coil for this purpose.

In some sets a separate coupling-coil will be necessary. Leads are then run into the set and this coil is set near the coil of the first stage. Any changes in the tuning that may occur and caused by so doing are compensated by means of the trimming condenser.

MIDGET CONDENSER

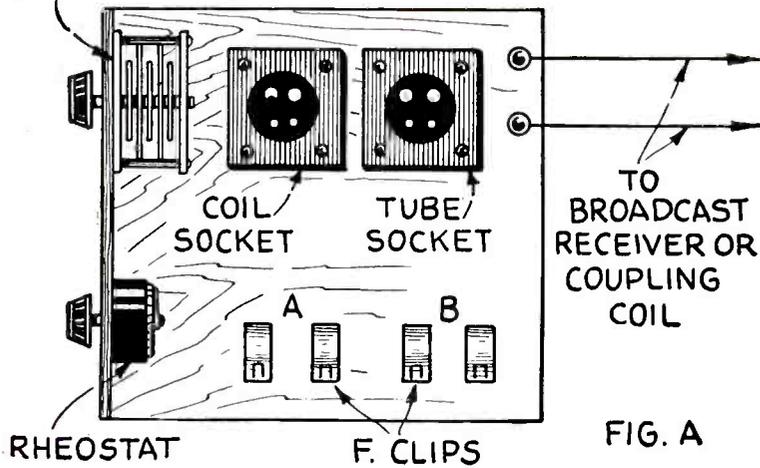


Fig. A, at the left, shows a suggested baseboard arrangement for short wave first detector, employing plug-in coils. It is important to see that all leads are kept as short as possible and the layout shown will be found to work very well, says the author.

wave ranges, and a 10-turn size will give a complete coverage. It may be necessary to modify these values, slightly, in some constructions. An ordinary grid leak and condenser are used in the oscillator.


This Hartley circuit, by the way, is better adapted for use in a superheterodyne oscillator than all others which have been tested. Some require choke coils, and consequently "dead spots" are discovered at some points. This is very objectionable in receiving work, especially in the oscillator, where a continuous range is highly desirable.

The circuit of Fig. 9 requires no choke coil; notice that the battery is connected between the center-tap on the inductance and the filament.

The tube may be a '99, an 01-A, or (if A.C. is used) a '27. In the latter case the filament supply can be taken from the broadcast set by suitable wiring

ing ranges, if the effective capacity in parallel with the tuned circuit is kept reasonably low:


Fig. B, at the right, shows a convenient arrangement of the oscillator parts on the baseboard, which will enable the constructor to use the shortest leads in connecting various component parts. Wood baseboards are commonly used, but when one has constructed such an instrument as this and has it working well, it would be a good idea to use a bakelite or similar baseboard.

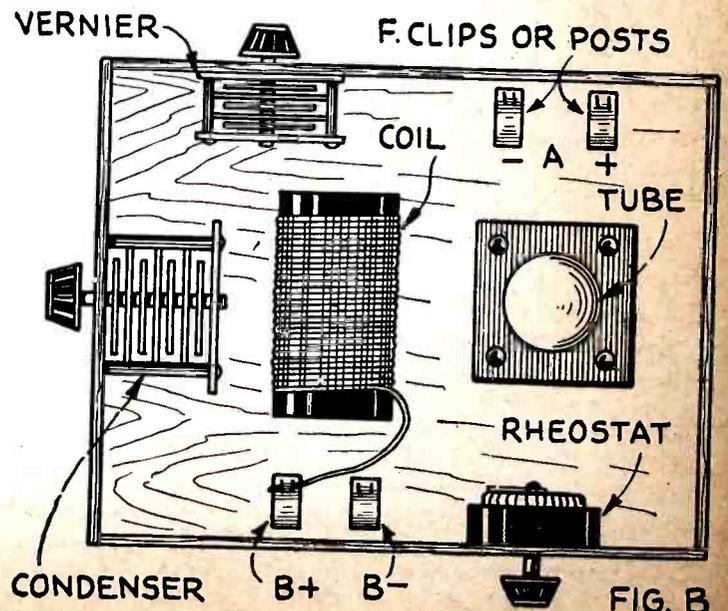

How You Can Convert YOUR BROADCAST RECEIVER


For Short Wave Reception

By McMURDO SILVER*

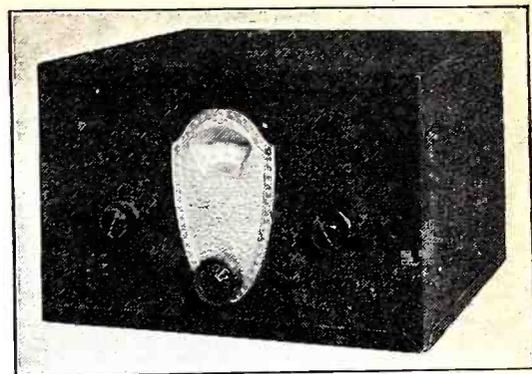


Front view of new Silver-Marshall S-W "Converter"

The author explains how to build a new design of converter, which, when connected to your broadcast receiver, enables you to hear short-wave phone stations as well as code signals. The cost of building the converter is low and it has its own plate and filament supply, all from the A.C. lamp socket; no batteries. The converter and your B.C. set form a superheterodyne, most sensitive and selective of receivers.

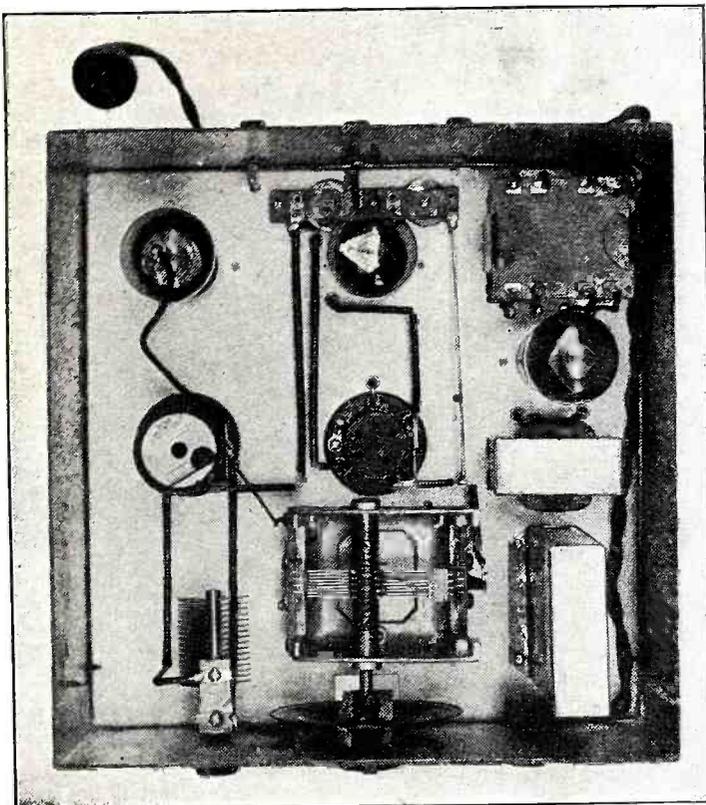

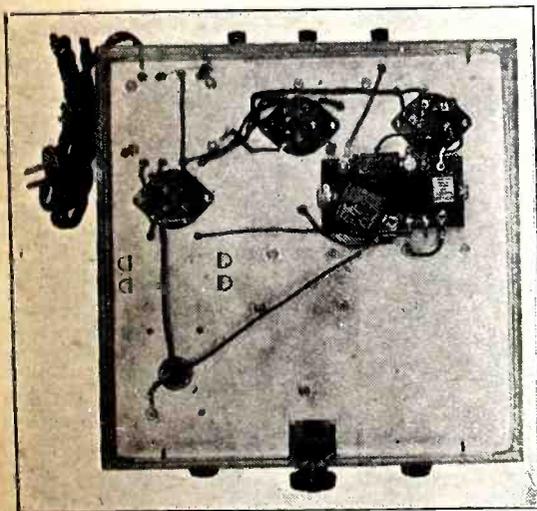Top view of S-W converter, which has its own A, B and C supply.



Bottom view of S-W converter.

FOR short-wave reception, the superheterodyne system, though sometimes regarded as complicated, unquestionably provides the best and most satisfactory type of receiver. It is the only system permitting any high order of amplification; since practically insurmountable problems are involved in the design of a short-wave R.F. amplifier, with which it is almost

impossible to obtain either any fair order of amplification, stability, practically satisfactory or reasonable commercial simplicity. With the superheterodyne, on the other hand, almost any desired order of amplification can be obtained on short waves, and a high order of simplicity attained; since, where it is re-


quired to cover a wide frequency band, only two coils need be changed for each band and there is no difficulty of circuit ganging involved.

Herewith is illustrated and diagrammed a short-wave converter, consisting of an oscillator and first detector; which, when placed before an ordinary broadcast receiver, employs the R.F. amplifier of the latter as an intermediate-frequency amplifier, and turns the whole combination into a superheterodyne. This converter is in distinct contrast to previous short-wave converters, which usually consisted of only a regenerative short-wave detector designed to be plugged into the detector socket of a tuned radio-frequency or other set, and utilized only the audio amplifier of the latter. With this converter, all of the amplification of the T.R.F. receiver, with which it is used, is fully utilized, and slightly augmented by the gain resulting from the frequency conversion.

Parts Necessary

The converter consists of a '24 first detector, with plug-in coils which are tuned by a .00014-mf. vernier or midget type of condenser. It was not thought desirable to bring the condenser control out to a vernier dial; since it is not particularly critical in setting, and operation may be more easily mastered when the first detector's tuning is regarded as a

(Continued on page 324)

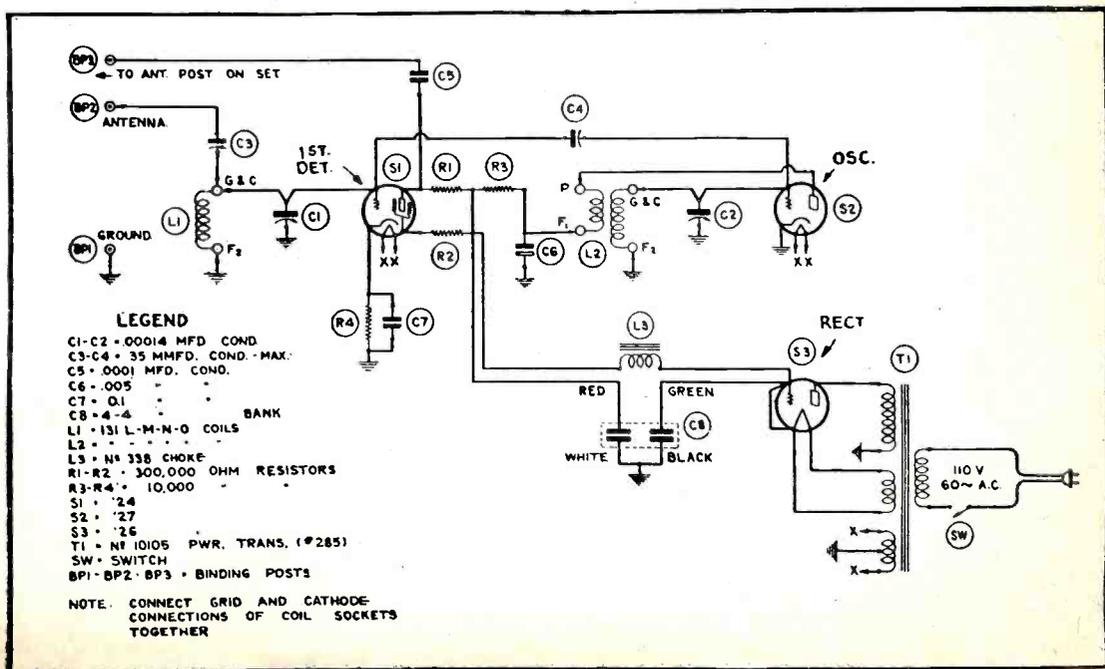

Wiring diagram of the Silver-Marshall S-W converter. It plugs into any A.C. socket.

* President of Silver-Marshall, Inc.



A COMBINATION SHORT and LONG WAVE SET

By H. WINFIELD SECOR

The new Colin B. Kennedy broadcast receiver contains a short-wave set which operates in conjunction with the radio and audio frequency units in the broadcast receiver. Plug-in coils are eliminated by a clever switch device.

Handsome appearance of the new Colin B. Kennedy combination long and short-wave receiver—the first receiver of this type and showing the future trend of receiver design. The wave set has one stage of untuned R.F. ahead of a regenerative detector; and the dynatron oscillator uses a S.G. tube as well. The receiver is not of the super-heterodyne type, but uses a dynatron

THE combination short and long-wave receiver just simply had to come, and it has remained for one of the leading builders of high quality receiving sets to point the way. This receiver excited a lot of attention at the recent New York Radio Show as the first instrument of its kind to be shown. Before another year has passed we will undoubtedly see plenty of combination long and short-wave receivers being commercially marketed.

Three short wave coils, covering a band of from approximately 15 meters to 100 meters are provided; two coils being permanently built in and shielded, while the third is of the plug-in type, which permits the owner of the set to remove this coil and insert others.

The long-wave receiver unit employs 4 tuned stages with shield grid tubes, a power detector, 1 resistance-coupled A.F. stage, with the second A.F. stage using 2 '45 tubes in push-pull. As the diagram shows, a dual switch connects the antenna with the long or short-wave set.

The special switch connecting the various short-wave coils into circuit is a three-pole, three-way affair, operated by a single knob on the exterior of the cabinet. The short-

Semi-sectional view of the new Kennedy broadcast receiver which is also fitted with a short-wave set; 1—Station Tuning Knob; 2—Wave Band Switch; 3—Regeneration and volume control; 4—Power Pack; 5—Broadcast Wave Receiver Control; 6—Dynamic Loud Speaker.


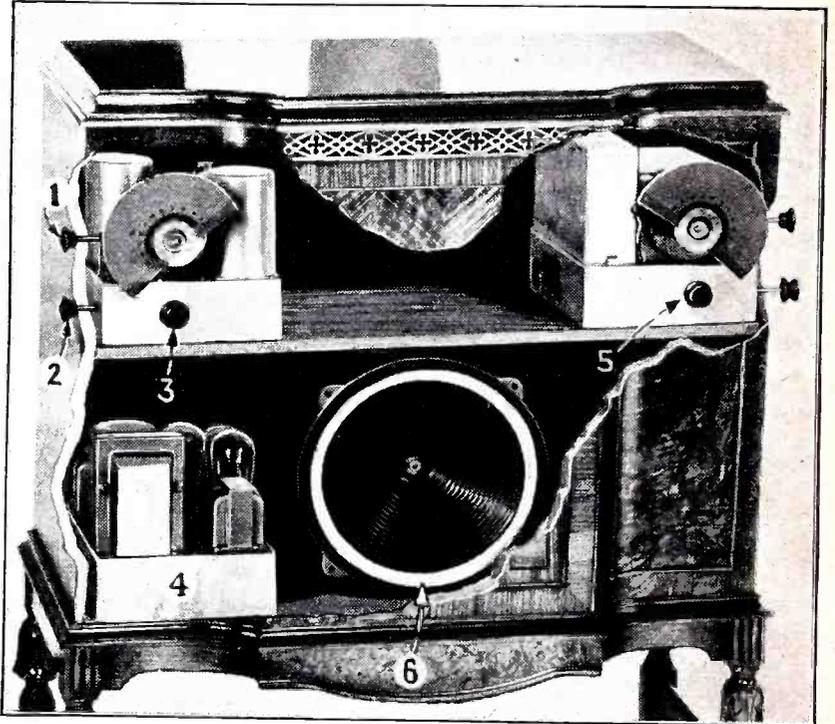


Diagram of short-wave set used in the Kennedy "combination receiver". This is not a superheterodyne—but a dynatron oscillator is used; the short-wave set feeds into the primary of the first tuned stage of the long-wave set.

oscillator, the output being taken from the screen of this tube through a condenser as shown. The frequency of the oscillator is fixed at approximately 1530 K.C., but can be varied.

For short wave reception it is only necessary to once set the dial of the long wave receiver at the output frequency of the short wave oscillator, and then tune the short wave receivers' single dial, as well as operate the regeneration control.

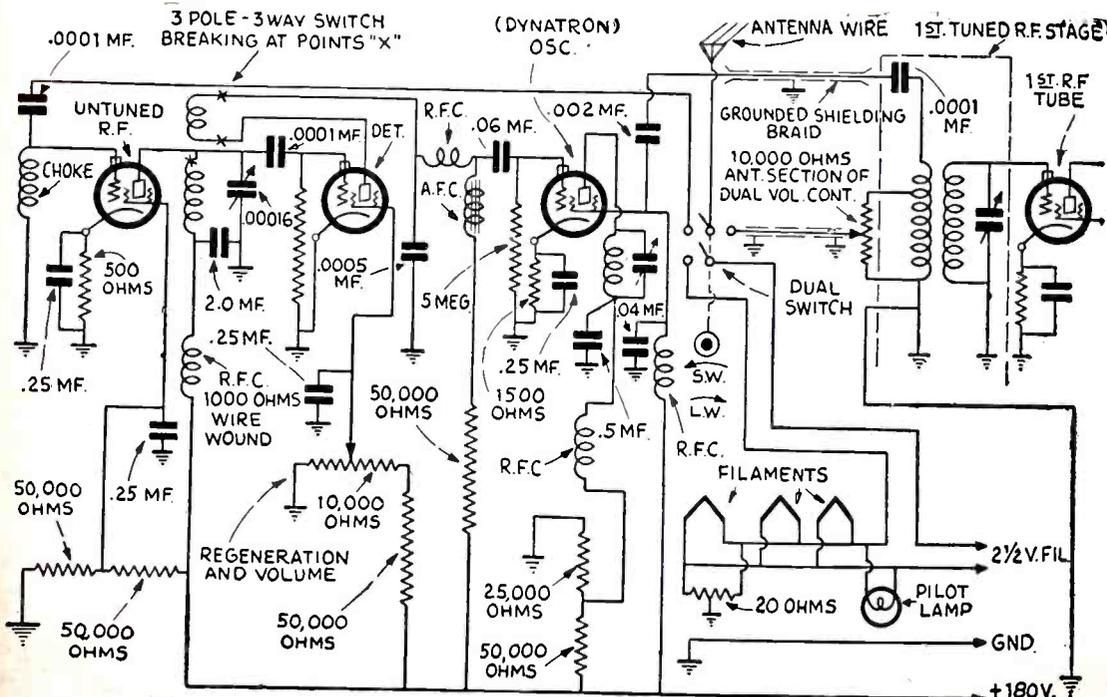This long and short wave receiver thus employs a total of six screen grid tubes, four being tuned amplifier tubes and thus producing a tremendous overall amplification of the short wave signals. Including the audio stages, a total of 11 tubes are employed for short wave.



The Short Wave Experimenter

The Amateur's "Short Wave" Special

By FRANK SOBIECH

THE two tube receivers illustrated here is one of the simplest types that can be built. It is, however, a thoroughly practical one, which can be depended upon to give readable signals, when conditions permit, even over the greatest distances.


Apparatus Required

- Three UX type tube sockets.
- C-1 mf., Tobe by pass condenser.
- C1-50 mmf., tuning condenser (straight line frequency).
- C2-100 mmf., midget variable condenser.
- C3-100 mmf., Sangamo fixed grid condenser.
- C4-Antenna coupling condenser; two $\frac{1}{2}$ " square brass plates, about $\frac{1}{8}$ apart.
- C5-2,000 mmf., Sangamo, fixed by-pass condenser.
- R- $\frac{1}{2}$ ampere ballast resistor (Amperite).
- R1-2 or 4 megohm grid-leak.
- R3-0.1 megohm fixed, grid-leak type resistor.
- R2-50,000 ohm variable resistor.
- L1-L2-Tube base coils.
- One good audio-frequency transformer.
- SW—One battery switch.
- Base Board measuring 11" x 6".
- Bakelite panel 12" x 6 $\frac{1}{2}$ ". One binding post strip.
- Phone jack, resistor mounting, miscellaneous wood screws, machine screws, brass strip, etc.

From the circuit diagram it can be seen that two variable condensers are used in series across the secondary L1. The condenser C1 is the main tuning control, and is a high grade condenser of 50 mmf. capacity. The midget condenser C2 is of 100 mmf. capacity. It is used in series with the main tuning condenser to reduce the capacity range of the latter, so that almost full scale coverage can be obtained on any of the amateur

bands. When the receiver is operated on the 1,715 or 3,500 kc. bands, the midget condenser is set near its maximum capacity, the exact position being determined experimentally, so that the capacity range of the tuning condenser will be limited to the value necessary to give full scale coverage on those bands. For the 7,000, 14,000 and 28,000 kc. bands, the midget condenser is set at lower values; each value being predetermined

Condenser C5, is a radio frequency by-pass condenser, across the audio frequency transformer. Its use is very important: without it the detector could be made to oscillate only by using an abnormally large tickler or very high voltage. The most satisfactory plate voltage for the detector is about 22 $\frac{1}{2}$. It might be thought from the diagram that 45 volts is used in this set. This is not so, however, since the resistance of R2 at

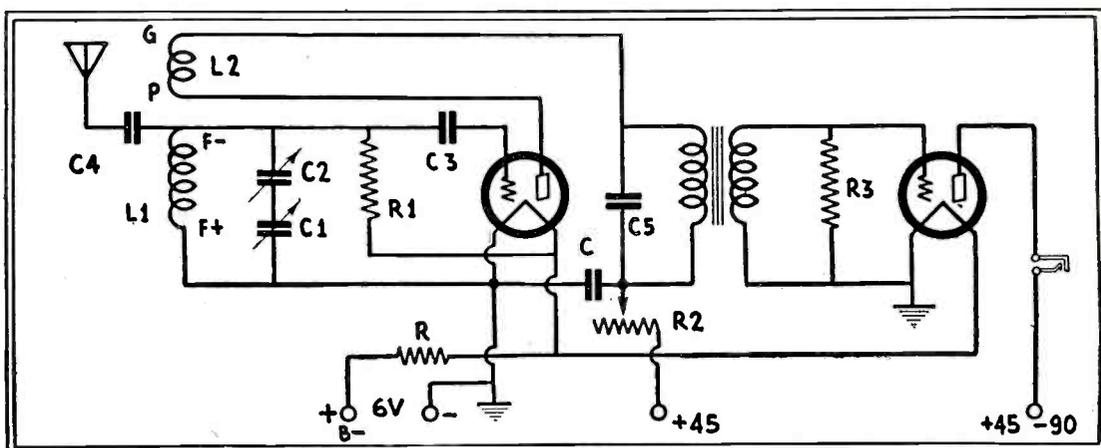

One of the features of this short-wave receiver designed by Mr. Sobiech is that a midget condenser, C-2, of 100 MMF capacity is used in series with the main tuning condenser C-1, to reduce the capacity range of C-1 and give greater wavelength coverage.

experimentally, so that the effective capacity range of the tuning condenser is progressively lower for the higher frequency bands.

The Coils

The short wave coils are wound on bases taken off burnt-out tubes. The exact number of turns needed, will depend to some extent on the placement of the apparatus and the arrangement of the wiring.

The tickler coil L2 is fixed in its position with respect to coil L1, and is wound on the same tube base, about $\frac{1}{4}$ " from the filament end of L1. The tube bases are long enough to accommodate the required number of turns of wire for the first four coils; but the fifth base, however, must be fitted with an extension that will make it about three inches long.


about half-scale setting, is sufficient to drop the voltage to the point where only about 22 $\frac{1}{2}$ volts are placed on the detector plate.

The fixed resistor R3 is connected across the secondary of the audio-frequency transformer to eliminate a howl or squawk, which is often produced at the point where the detector starts oscillating.

FOR BEGINNERS!

In the next Issue—
ARTHUR G. GREEN
will tell

"How to Operate a Short
Wave Receiver."

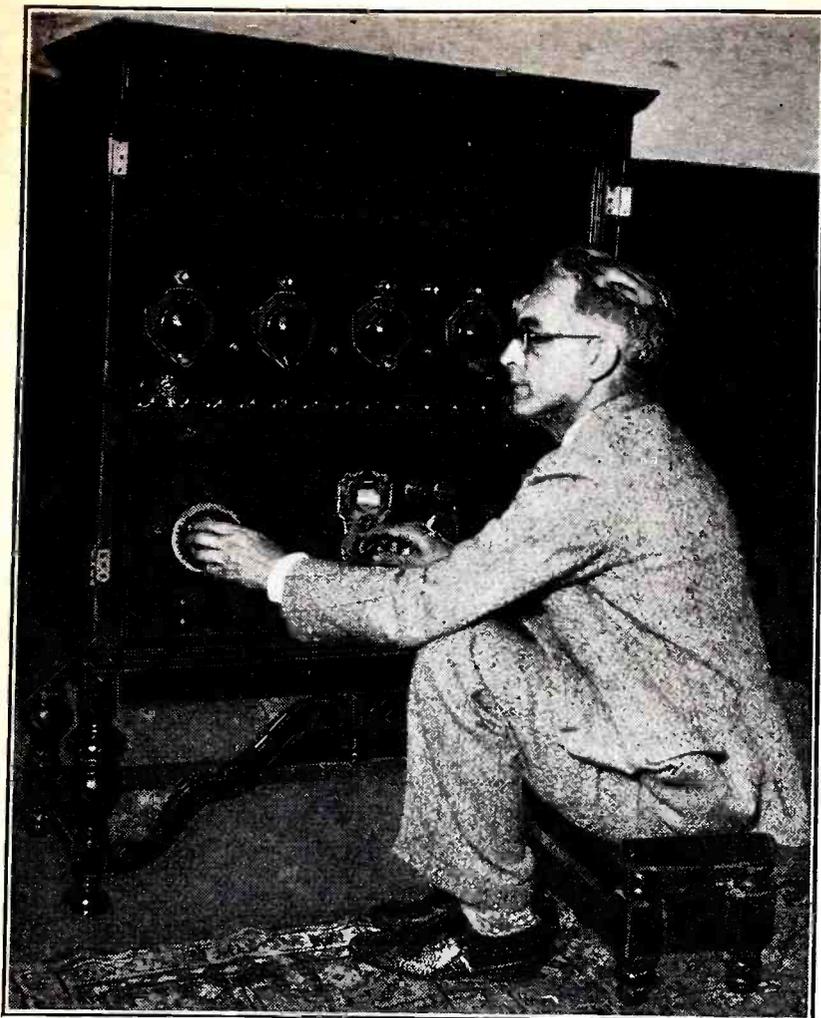

Mr. Lee tuning the "Rolls-Royce" receiver.

A "Rolls-Royce" SHORT WAVE RECEIVER

By C. STERLING GLEASON

This short wave receiver was specially designed for the superior reception of Television signals and it employs five stages of resistance coupling; these stages being so designed as to pass a wide band of frequencies, essential for the reproduction of a clear television image. This receiver also makes an excellent voice amplifier.

AMONG broadcast receivers, the Rolls-Royce type of set has become fairly common in this day of single-dial control and straight-tuned radio-frequency. In the realm of short-wave outfits, however, the lowly three-tube flivver still holds sway. Few builders have mastered the intricacies of multi-stage radio-frequency amplification at the extremely high frequencies; and even the screen-grid tube, which holds out such alluring possibilities, has not been exploited to the extent that it deserves. Nevertheless most constructors undoubtedly long for a receiver of the Rolls-Royce class—for a set above the ordinary in sensitivity, with a reserve of power which may be opened up upon occasion—just as the flivver owner may yearn for the smooth powerful pull of a twin-six motor beneath the hood.


Such a receiver, designed and built by Gilbert C. Lee, a Los Angeles engineer, is the most successful *de luxe* short-wave set that has come under the writer's observation. It is the result of two years' experimentation toward a receiver which would not only yield performance on the short waves comparable with that attained by the best multi-tube broadcast

receivers, but would also meet the requirements of television.


Seven tubes are employed; it was considered better to use a larger number of tubes than is common in short-wave receivers, rather than attempt to exact maximum performance out of a smaller number, all of which must be worked at all times to the limit. Especially in television is a large reserve of power desirable, because of the large momen-

tary demands made upon the amplifier by scanning peaks. With each tube normally delivering a good deal less than its maximum output, a comfortable reserve of power is always available, and distortion from overloading is avoided.

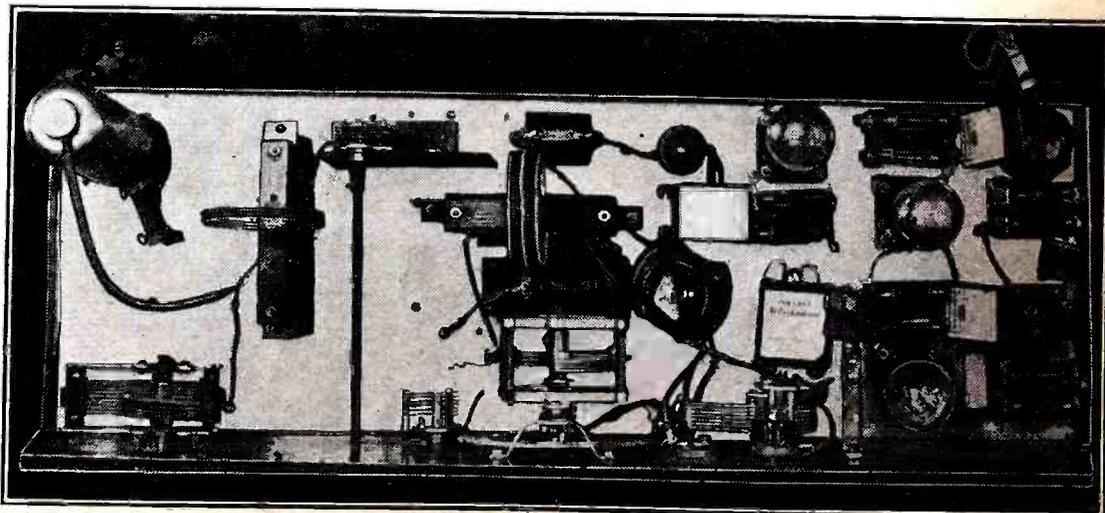Since the receiver was designed especially for use in television reception, particular attention was given to the peculiar requirements of visual signal transmission. The wide sideband that



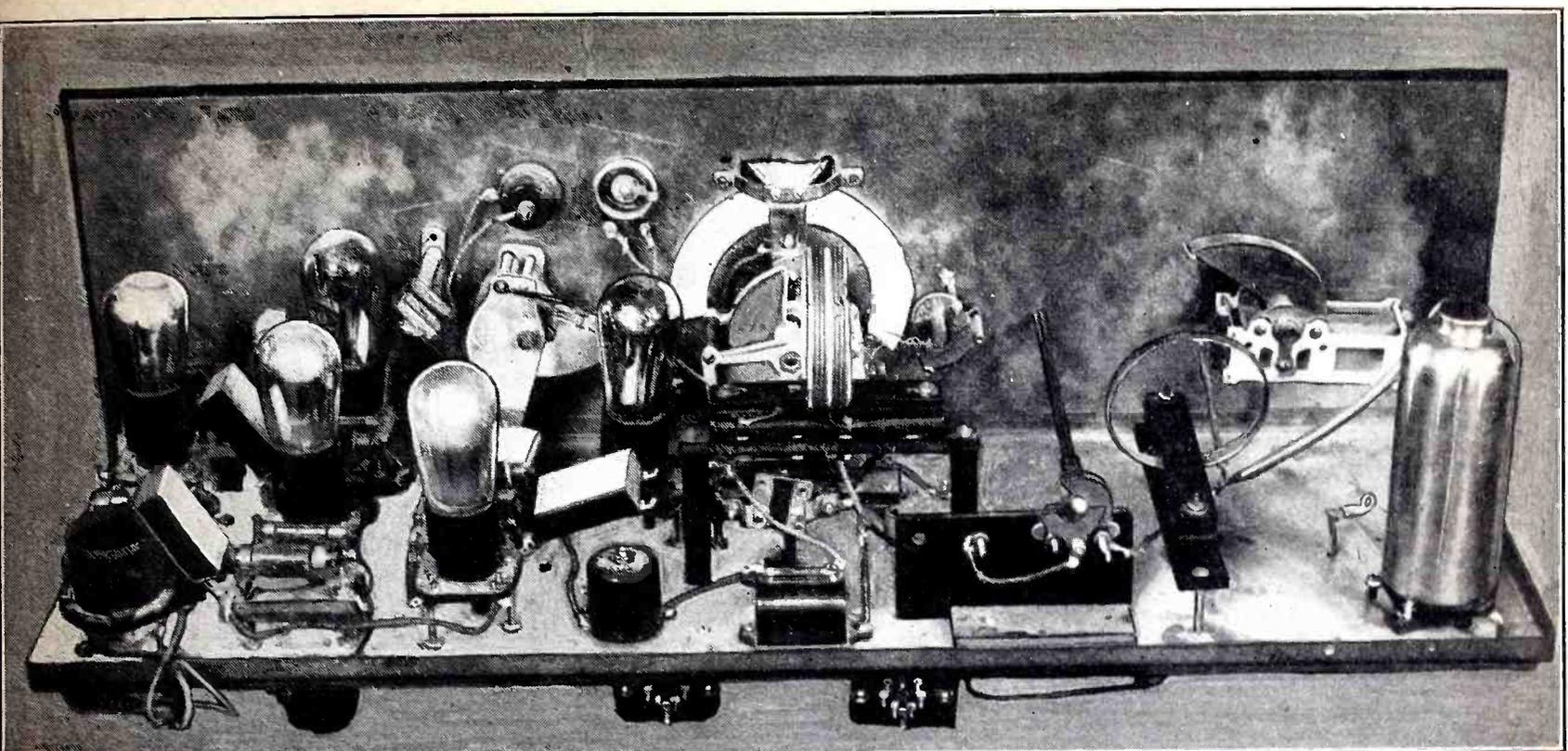Top view of "Rolls-Royce" short wave television and voice receiver.



Rear view of "Rolls-Royce" receiver, showing resistance coupled stages, short wave coils, condensers, etc.

must be transmitted, if good detail is to be obtained, precluded the use of multi-stage cascaded radio-frequency, with the attendant number of tuned circuits. A single stage of high-gain amplification, followed by a detector of sufficient power-handling capacity, and a number of stages of resistance-coupled audio, was deemed the best combination. The temptation to secure single-dial control by gang-condenser tuning was resisted, because of the relatively large loss of efficiency at high frequencies which would be occasioned by a slight inaccuracy in tuning, and the danger of cutting sidebands, with the attendant loss of picture detail.

Coupling to the antenna is obtained through a small variable condenser which can be adjusted to fit the particular antenna, and left. With this condenser properly set, the tuning range is free from "holes," due to resonance at harmonics of the antenna circuit; at the same time, the tuning of the radio-frequency stage is broadened somewhat by the closer coupling of the antenna resistance into the tuned circuit, flattening to a certain extent the "hump" of the resonance peak. This load has also a slight stabilizing effect on the rather exuberant screen-grid tube, which yields the desired high gain of this stage.


Flexibility of adaptation to various wavelength bands, as well as a favorable L/C ratio and a well-distributed tuning range, is secured by the use of plug-in inductances and small tuning condensers. The construction of R.F. transformers is vastly simplified, and performance improved, by feeding the output from the screen-grid stage directly into the grid of the detector, thus combining primary and secondary windings into one. Since the plate voltage is applied to the lower end of the common winding, the grid leak must be connected from the grid across

to the filament, lest the high positive potential of the "B" battery reach the grid. The R.F. current in the grid coil finds a filament return through a 0.25-mf. condenser. The detector circuit thus requires only two windings—grid coil and tickler—which are mounted close together in fixed relation. A "throttle condenser" allows control of feedback, and a 500,000-ohm variable resistor is provided for adjustment of detector "B" voltage to suit the requirements of various frequency bands. On the lower waves a rather high voltage is allowed to reach the plate but, as the higher wavelengths are approached, more resistance can be cut in and smooth operation will be obtained with lower plate voltages. A type '12A tube is used as de-


detector (VT2) and is followed in turn by a '40, an '01A, two '71A's, and a '10.

Five Resistance-Coupled A.F. Stages

In order to get the high signal output desirable for bright, clear pictures, a multi-stage audio amplifier was indicated. Because the television signal where much detail is transmitted consists of many grays and intermediate tones, producing a frequency band of components far above the customary 5,000-cycle range of musical reproduction, transformer amplification was out of the question. Impedance coupling also was regarded by Mr. Lee as less suitable, because at the higher frequencies the distributed capacity of the impedances by-passes much of the signal energy and produces marked

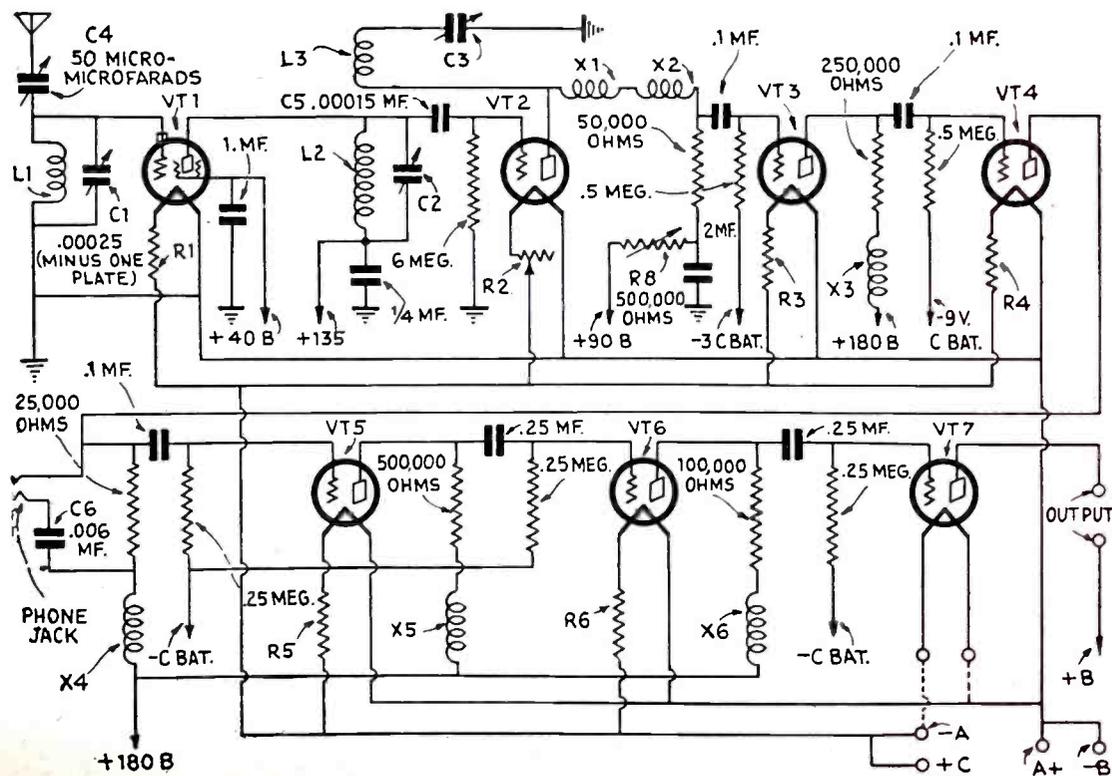

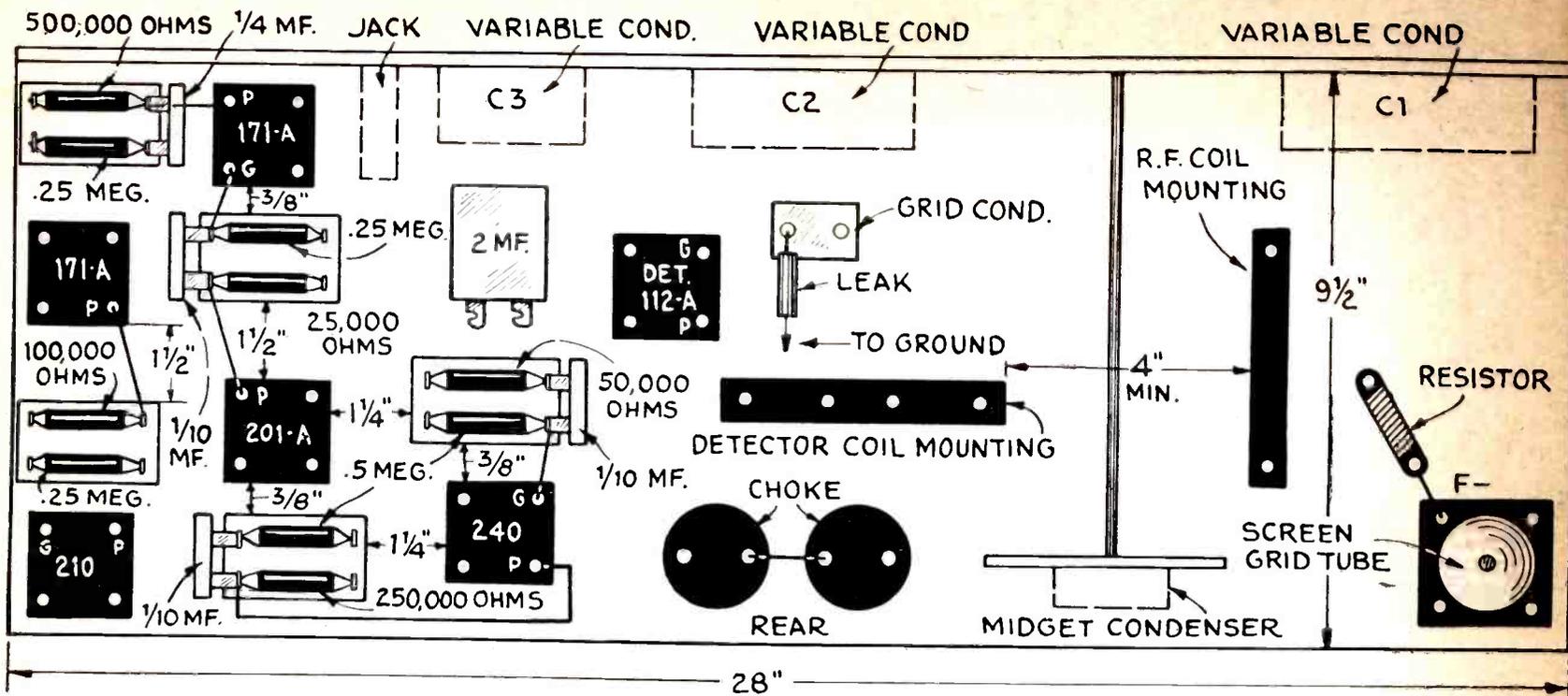Hook-up of television and voice receiver.



Layout of parts in "Rolls-Royce" S-W receiver suitable for television or voice reception.

attenuation of the higher components essential to pleasing pictorial quality. Multi-stage transformer and impedance coupling in cascade are both difficult to handle, because of interaction between the relatively intense fields surrounding the windings.

Resistance coupling was therefore selected, not only because of the diminished trouble with inductive feed-back, but also because of the fact that the reactance of the coupling condenser, falling as it does with frequency, results in a rising frequency-characteristic peculiarly adapted to the needs of television.

Few experimenters have had the temerity to attempt to operate as many as five stages of audio frequency without either individual stage shielding or special layout with unusually wide separation of equipment. Mr. Lee has, however, succeeded in constructing such an amplifier with perfect freedom from oscillation and with no trouble as regards motor-boating or any of the other common ailments of resistance coupling. This result was attained only after much experimentation and careful checking by listening in to each stage individually. Stability of operation is assured, not only by careful design and layout, but also by working each tube at a level well below its maximum output. Coupling through the "B" supply is eliminated by a choke placed in series with each amplifier plate lead. Several engineers have built this set after Mr. Lee's specifications, and have been markedly successful when the layout for the stages was followed implicitly; however, deviation from the placement of parts in the amplifier has generally proved disastrous.

The recipe for success with this amplifier is not new; the secret is merely to have short leads, not parallel, and to keep well in the clear from conductors which may cause stray couplings. No interstage shielding has been found necessary. The panel is shielded by a sheet

of copper and the sub-panel also is shelved with copper. All tube sockets, resistor mountings, condensers and wiring are kept clear of the shielding. The sockets and resistor mountings are placed on "stilts" 1½ inches high. It was found that when the apparatus was mounted directly on the sub-panel, the induced currents in the copper floor were sufficient to upset the whole amplifier and throw it into uncontrollable oscillation. A 1½-inch elevation of all parts eliminated this trouble.

In television, freedom from set noises is particularly important for a clean screen, since irregular pulses show up as spots flickering across the picture. For this reason, wire-wound resistors are used in the plate circuits of all resistance-coupled stages. The resistors are placed with the grid and plate ends of the mountings directly opposite the corresponding socket terminals; and the condensers are mounted on end, supported by their terminals, which are soldered directly to the mounting terminals. Thus the length of the leads is reduced to a minimum.

List of Parts

The parts required for the circuit are:
 3 variable condensers: 2 tuning (C1, C2); 1 regeneration (C3). Values may be chosen by the constructor;
 1 panel, 9 x 29 inches; 1 sub-panel, 9½ x 28 inches; and sheet copper to cover panel and sub-panel;
 3 dials;
 4 sub-panel brackets;
 1 battery cable or cable terminal plug;
 1 "midget" variable condenser (C4), capacity 50 mmf.; and 1 bakelite shaft extension to reach to panel;
 Hammarlund space-wound tubing stock—at least 60 or 70 turns—and mountings to fit coils (see text below);
 1 fixed condenser (C6), cap. .006-mf.;
 1 fixed condenser (C5), cap. .00015-mf.;
 1 6-megohm grid leak and pair of mounting clips;

1 25-ohm rheostat (R2);
 1 series resistor (R1) for '22 tubes;
 4 Amperites (R3 to R6 inclusive) to suit tubes used;
 1 tube shield for screen-grid tube;
 7 cushion sockets;
 1 Clarostat (R8), 500,000 ohms;
 1 phone jack for headphones (if desired);
 Output jack or binding posts;
 5 resistance-coupled stage mountings;
 5 wire-wound resistors, values as follows: 25,000, 50,000, 100,000, 250,000, and 500,000 ohms;
 5 grid resistors: two 0.5-megohm and three 0.25-megohm;
 8 fixed condensers of reliable make and reasonably high working voltage: three 0.1-mf., three 0.25-mf., one 1.0-mf., and one 2.0-mf.;
 3 1.5-mh. chokes (X1, X2, X4);
 1 85-mh. choke (X3);
 2 chokes, home-made (X5, X6; see text);
 7 tubes: one '22 (VT), one '12 (VT2), one '40 (VT3), one '01A (VT4), two '71A (VT5, VT6), and one '10 (VT7).

Mounting and Wiring

In laying out the apparatus, the disposition of parts upon the panel is not particularly important, except that reasonable care should be exercised to keep as much separation as possible between parts about which there is likely to be a strong radio frequency field. The sub-panel shield may be bent up around the edges to form a shelf, if desired. The bakelite base panel underlying the copper shield may be omitted if the shield has sufficient mechanical strength to support the load; however, the bakelite gives a much more rigid layout. All shielding is, of course, connected to ground, and much wiring can be saved by bearing in mind that the shielding is a common circuit between "A+," "B—" and one side of all tube filaments. It is very important to remember that the detector tuning condenser will be at "B+135"

(Continued on page 326)

The SHORT

By BERYL BAKER BRYANT

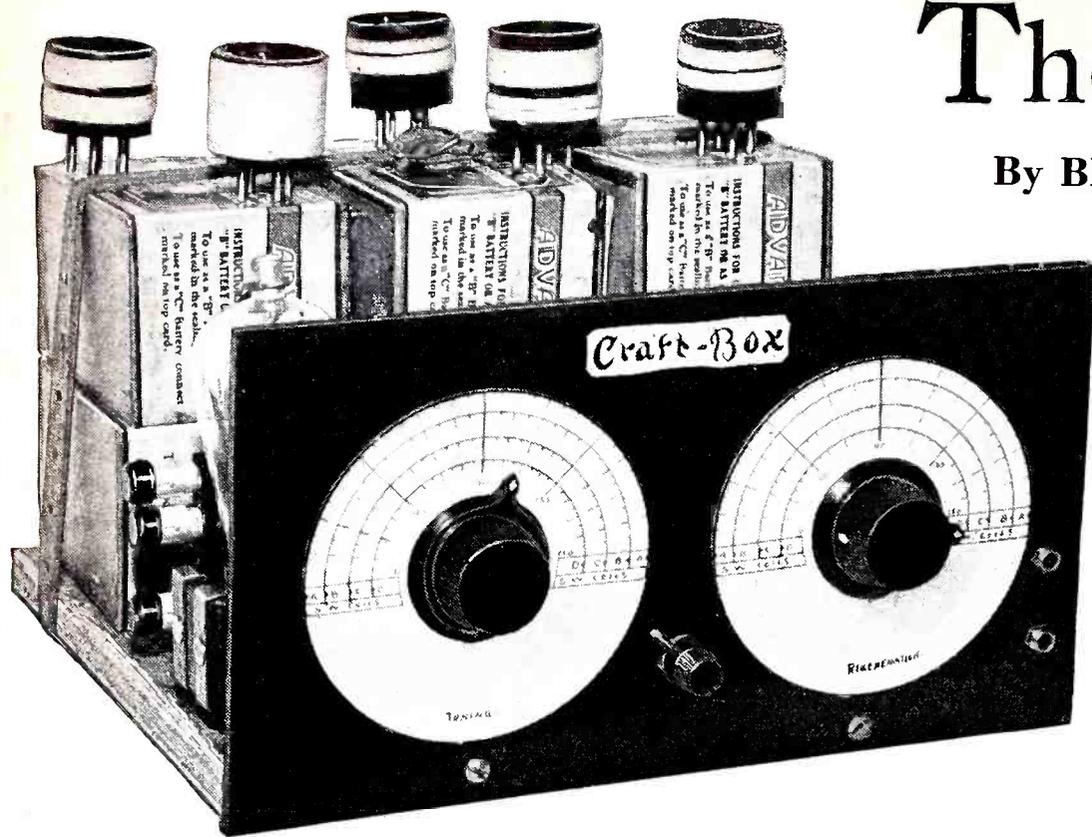


Fig. A. Front view of "The Short Wave Screen-Grid Craft Box." The dials were made for four coils, but five coils eventually were used; dial cut-outs for a five-coil job appear in these columns.

This "Junk Box" short wave receiver is a compact little job and well suited to the average experimenter's pocket-book. It utilizes one '22 screen grid tube and two '99 tubes; two "C" batteries supply the filament current.

- 2 mica fixed condensers, .006-mf. (C4, C5).
- 1 mica fixed condenser, .0001-mf. (C6).
- 2 grid-leak mountings.
- 1 grid leak, 2-megohm (R1).
- 1 grid leak, 5- or 6-megohm (R4).
- 3 binding posts.
- 2 cord-tip jacks (J).
- 1 filament resistor, 15-ohm wire, tapped at 5 ohms to provide grid bias for the '22 R. F. tube (R2, R3).
- 1 resistor, 10-ohm wire, for the '99 filaments (R5).
- 5 old tube bases, to be used for coils.
- No. 28 D.C.C. magnet wire, ¼ pound, to be used for coils.
- 1 wooden baseboard, 10 inches long, 9 inches wide, and ½-inch thick.
- 1 hard-rubber (or bakelite) panel, 10

THE unusual development of radio over a brief span of time has left the "junk-box," or drawer, of many radio experimenters well filled with obsolete parts which can no longer be used with any degree of satisfaction in a modern broadcast receiver. These parts have become obsolete not because of their lack of efficiency, but because of the alteration of broadcast conditions.

The vogue of short-wave code and broadcast transmission offers a purpose wherefore the experimenter or short-wave enthusiast may resurrect many of the parts he had relegated to his own private junk heap. With care of design and construction a short-wave receiver may be fashioned that will equal the performance and appearance of apparatus constructed of specially-designed and costly parts.

Junk-Box Craft

With this purpose in mind the author set about to design and construct a real short-wave receiver. The old junk box was fished out of the closet and its contents dumped on the floor. (A word of advice, place papers on the floor first; as this will preserve peace of mind later.) After a few minutes spent in selection of parts that might be used, the following were chosen:

- 2 seven-plate midget variable condensers, 32-mmf. capacity, with knobs, C1, C2 (formerly used as compensating condensers in a broadcast receiver).
- 4 UX-type sockets. (Not necessary that they match.)
- 1 unmounted A. F. transformer, vintage of 1922. (Although any of recent manufacture might work better) (TR).
- 1 85-millihenry R. F. choke. (There was

some doubt as to the probable efficiency but, in any event, it proved without "dead spots"; as regeneration was obtained over all the short-wave bands. The inductance need not be as great as that used, but may be as low as five or ten millihenrys.)

- 1 battery or filament switch (S.W.).

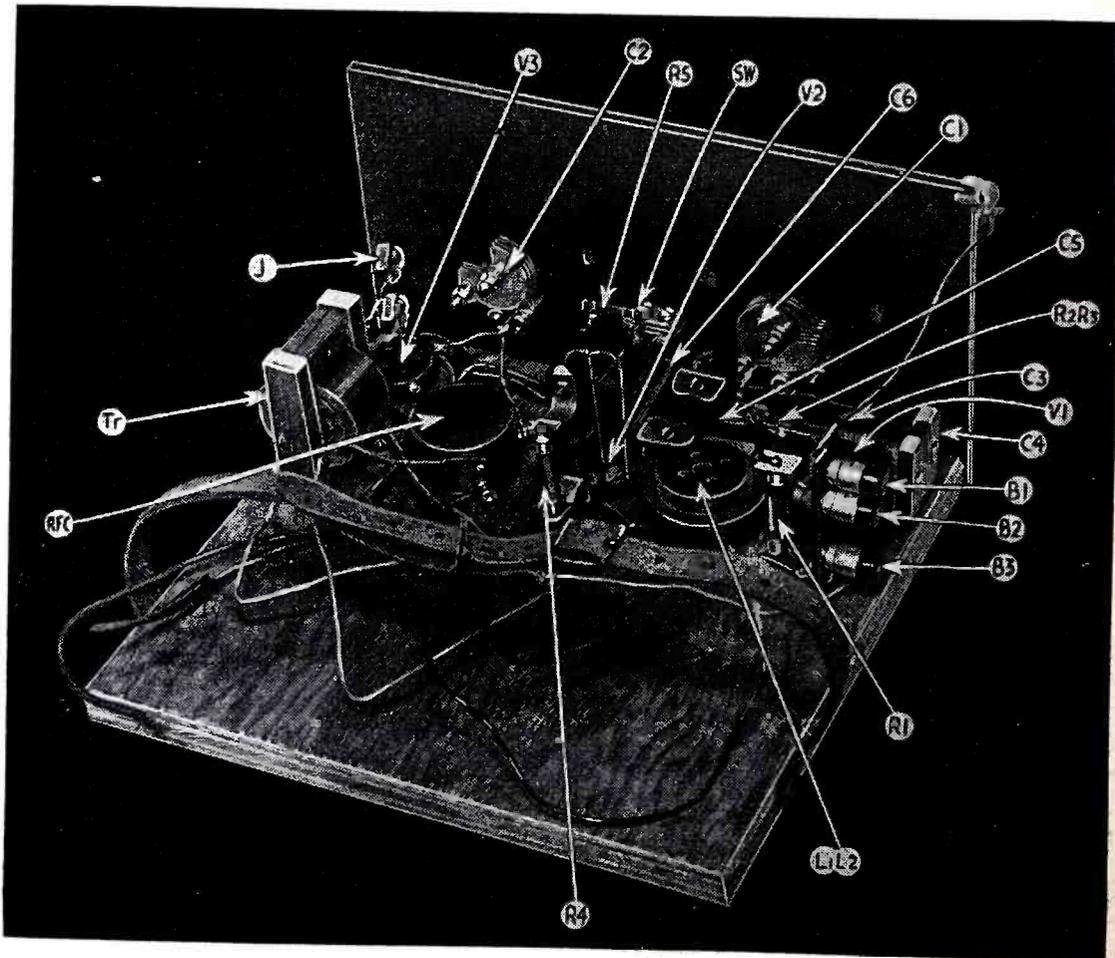


Fig. B. Rear view of the "Craft Box." All the parts, few in number, are easily seen. What parts would YOU use?

WAVE SCREEN GRID CRAFT BOX

inches long, 7 inches wide by $\frac{1}{8}$ -inch thick.

- 1 '22 screen-grid tube (V1).
 - 2 '99 tubes (V2, V3).
 - 5 small "B" batteries, 22½-volt portable.
 - 2 "C" batteries, 4½-volt, for filament supply.
- Hook-up wire, wood screws and other necessary hardware.

After the parts have been selected the constructor should carefully clean, inspect and tighten all parts as well as test the various parts for shorts or open circuits. Denatured alcohol and ether mixed in equal parts will remove dirt, oil or grease, when applied judiciously with a small, stiff bristle brush. If the parts are not thus inspected and cleaned before assembling into the complete receiver, trouble is apt to appear.

The Short-Wave Circuit

Inspection of the circuit diagram will show the circuit used for this short-wave receiver to be the same old standby—a single circuit regenerative detector preceded by a screen-grid R. F. stage, and followed by a conventional transformer-coupled A. F. stage. In regard to the latter, it was not deemed necessary to use two stages of A. F., as phones would be employed, and for this purpose sufficient volume would be obtained with one. The grid circuit of the R. F. stage is untuned, having a 2-megohm grid leak (R1) connected from the control grid cap to the bias tap on the series filament resistor (R2-R3); the grid leak serves only as a means of blocking the R. F. from the ground circuit, forcing the signal to be impressed on the control grid, while providing a means of applying the 1½-volt "C" bias to the control grid. (Otherwise, a negative charge would accumulate on the control grid, causing the tube to block.) The antenna

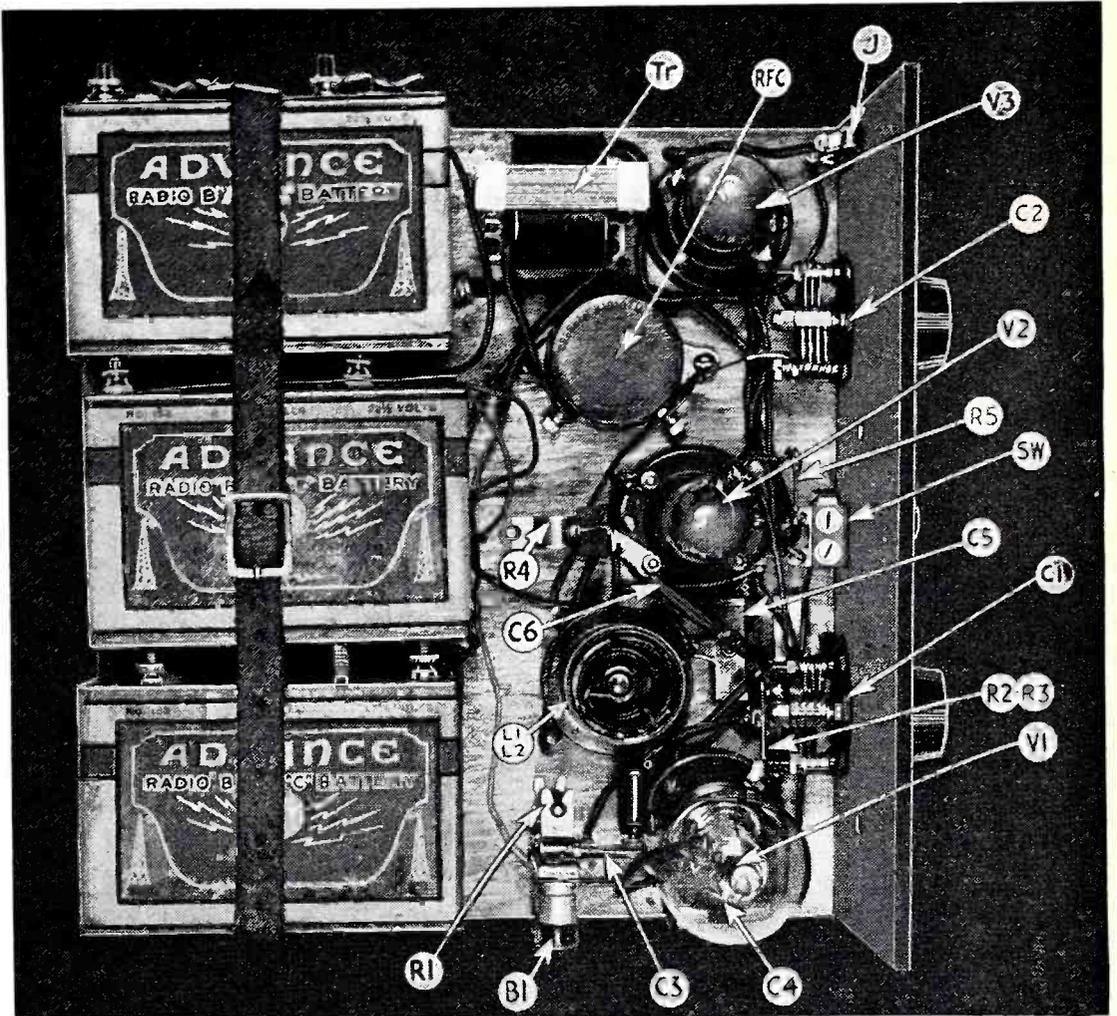


Fig. C. Batteries in place; all leads connected; tubes in their places; with the aerial and ground attached, we are "rarin' to go," whither our old "Craft Box" will take us.

may be coupled direct or through a small semi-variable homemade condenser (C3), to the control grid of the R. F. tube; the choice will depend upon the antenna used.

Construction of Coils

The short-wave coils are of the plug-in type; five are used to cover the band from 25 to 100 meters. They are constructed from old tube bases; five of

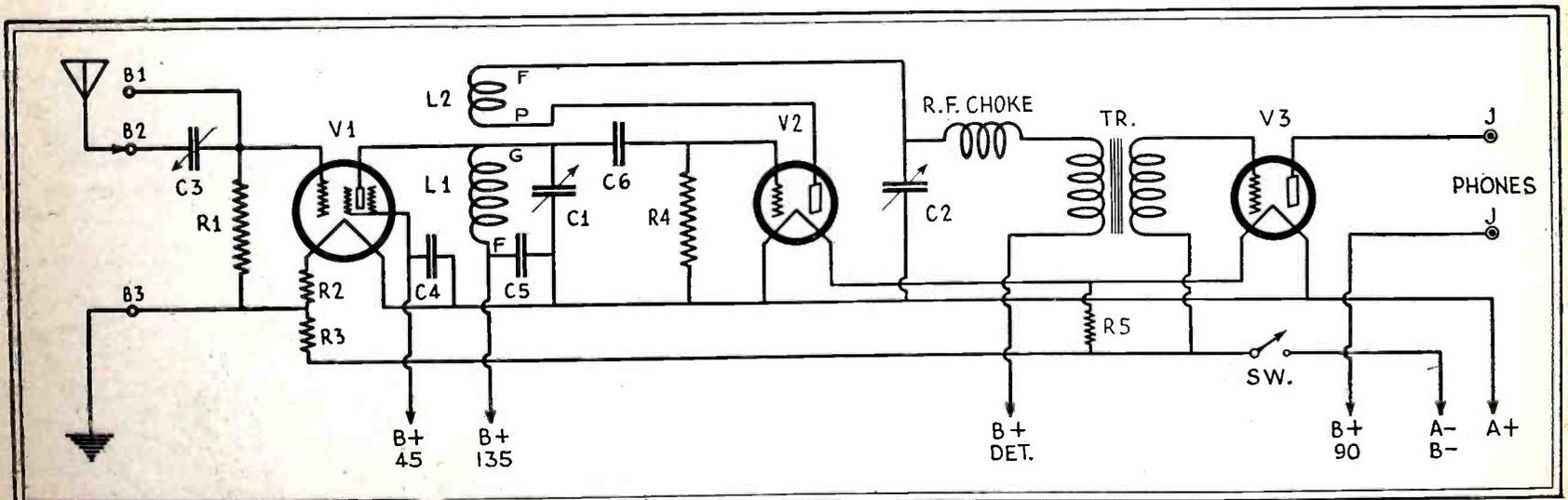


Fig. 1. Schematic circuit to be followed by those who want to dig into their junk box and ride the short waves via the "Craft Box." As 90% of construction is getting started, "it's up to you"; we have eliminated all the mechanical difficulties.

the UX type as listed above. There are two types of tube bases, the short and the long; if possible, the long should be obtained (especially for the "E" coil) as otherwise it will be difficult to accommodate the required turns on the base. If it should prove impossible to obtain the long type, thin cardboard may be wrapped and cemented around the short base to give the required winding space. Follow the winding specifications:

Coil A: Grid winding, 7 turns; tickler winding, 7 turns; shortest band, approximately 18 to 25 meters.

Coil B: Grid winding, 10 turns; tickler winding, 10 turns; tuning range, approximately 25 to 35 meters.

Coil C: Grid winding, 15 turns; tickler winding, 14 turns; tuning range, approximately 35 to 45 meters.

is readily determined approximately as $48\frac{1}{2}$ turns of No. 28 D.C.C. wire may be wound in one inch of space.

To start the grid winding, the end of the wire is passed through the hole drilled at the top of the base, then passed down through the grid prong and soldered. The proper number of turns is wound, breaking the wire but leaving about six inches free. The insulation is removed to within $\frac{1}{2}$ -inch of the point where the wire enters the hole; the wire is passed through the hole and down through the filament prong on the same side as the grid prong. Start the tickler winding $\frac{1}{8}$ -inch from the end of the secondary; the wire is again passed through the hole and soldered to the remaining filament prong and the proper turns are wound. Remove the insula-


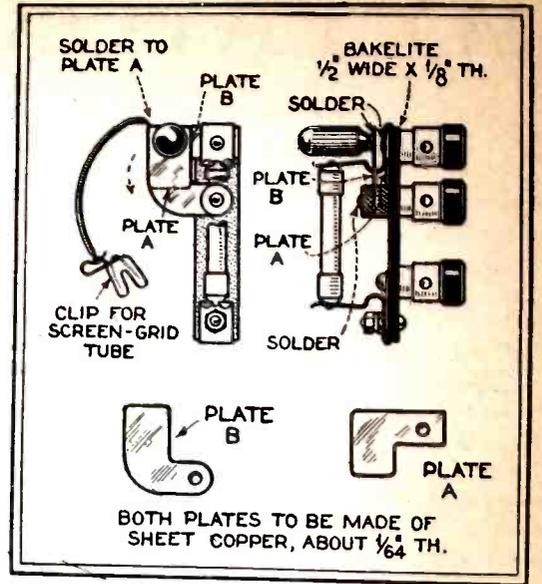


Fig. 2. Detail of the binding post plate in conjunction with which is the antenna variable series capacity.

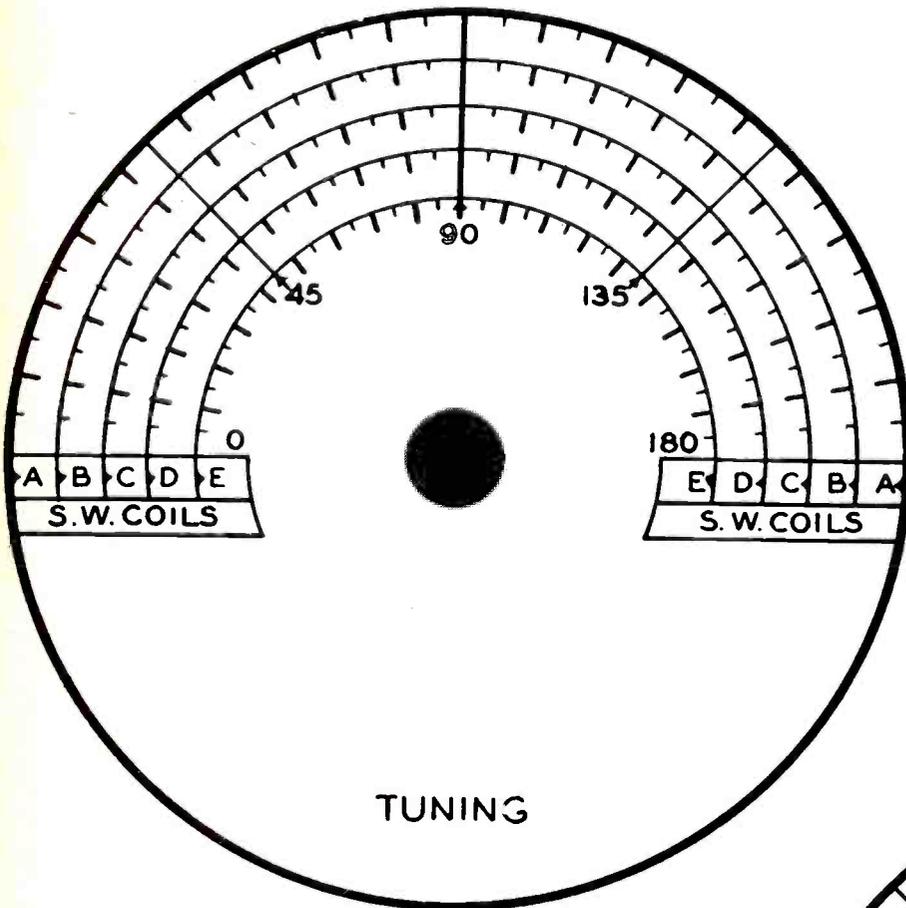

Dial for the "Craft Box." Copy, cut out and paste on panel. "Regeneration" dial appears below. A red ink dot on the right line and stations are quickly retuned in.

tion as before and pass the wire through the lower hole, through the plate prong, and solder.

The tickler of the "D" coil is wound double-layer. The tickler for the "E" coil is wound on a small length of cardboard tubing which is placed inside the secondary winding. Care should be taken that the beginning of the tickler winding is connected to the filament prong on the side of the plate prong.

Parts Assembly

The hard-rubber or bakelite panel is first drilled for the mounting of the two midget variable condensers, the filament switch and the two cord-tip jacks. Two holes are also drilled near the lower edge for fastening the panel to the base-board, which may be done at this time.


(Continued on page 331)

Coil D: Grid winding, 20 turns; tickler winding, 18 turns; tuning range, approximately 45 to 65 meters.

Coil E: Grid winding, 50 turns; tickler winding, 50 turns on a cardboard tube fitted inside the secondary winding; tuning range, approximately 63 to 100 meters.

The cement and glass are removed from the tube bases. (This may be done very easily with a sharp penknife.) Starting about $\frac{1}{16}$ -inch from the top edge of the form the grid winding (L1) is started and wound for the required number of turns; $\frac{1}{8}$ -inch space separates it from the tickler winding (L2). It is a good plan to prepare the bases before winding by drilling the holes to anchor the winding ends, which are also to be soldered to the prongs. The solder and wires should previously be removed from the prongs by the application of a soldering iron and a sharp knock. The distance at which the holes should be drilled

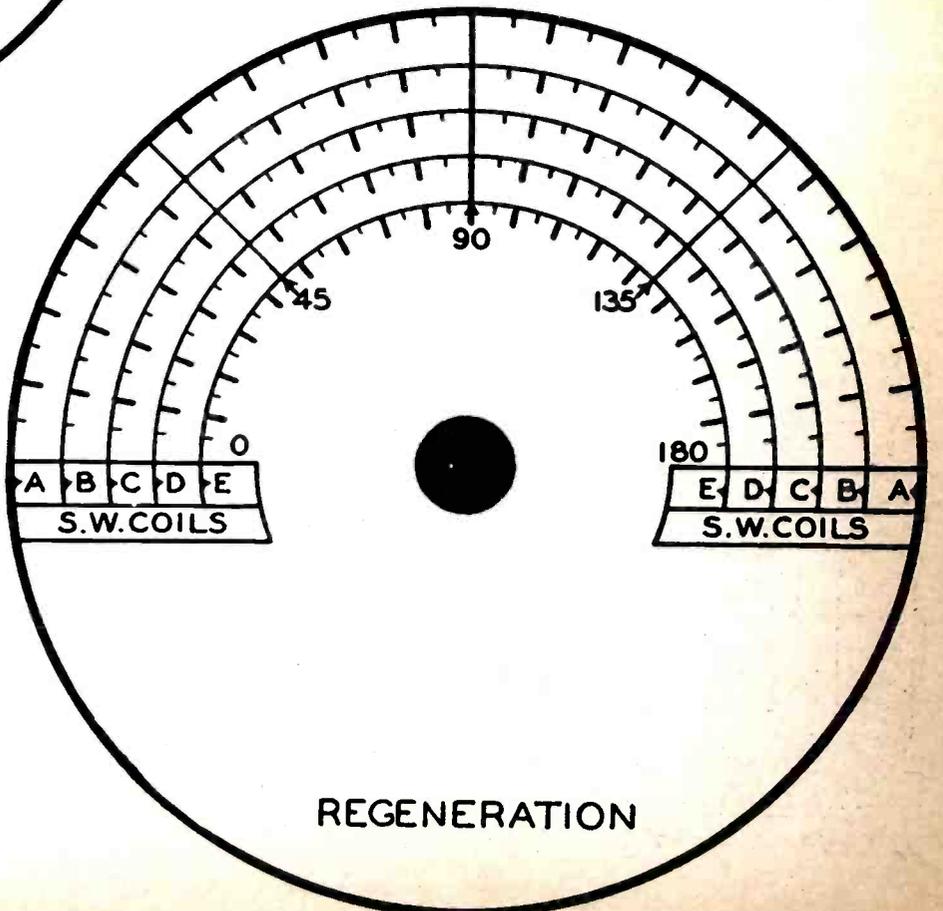This is the design for the second dial of "The Craft Box." Trace, cut around outside edge and then paste the dial so made on the receiver panel. "Tuning" dial appears above.



REGENERATION

MY FAVORITE AUDIO AMPLIFIER

By MANDER BARNETT

AN audio amplifier must, if it is to be used with a short-wave tuner, possess as many as possible of the following features: A really high step-up gain and positively no audio fringe howl; it should be as compact as possible, and should have a really flat amplification curve over the whole audio frequencies. In my favorite audio amplifier, which is used in conjunction with a regenerative detector, an attempt has been made to make it conform to the above ideals as closely as possible. The circuit diagram is shown in Fig. 1. The amplifier itself, of course, comprises only V2 and V3, but, because the first audio tube is resistance-capacitively coupled, a screen-grid detector is used, as shown by V1.

By analyzing the above features set out for our ideal audio amplifier of a short-wave receiver we find that this amplifier has a relatively high gain, considering the small number of tubes used. V1 with the resistance-capacity coupling units R1-C2 and R3 produces a high gain—higher than that obtained with an ordinary tube as detector, of course—and a high-ratio transformer (7:1) can be used between V2 and V3 without detrimental effects on quality. The step-up gain, then, is possibly higher than it would have been if two transformer stages had been used, and the quality is better.

Battery coupling in an audio amplifier can be very annoying and cause motor-boating, as well as fringe-howl effects. So that battery coupling shall not take place between the detector and the audio amplifiers, the detector plate supply is de-coupled from the rest of the circuit

by means of R2 and C1. R2 has a value of about 20,000 ohms, and C1 about 2 mf.

The plate resistance R1 is about 80,000 ohms or higher, but if a higher value is used it must not be forgotten that R2 is also in series with it, and this

smooth over noisy batteries and also keeps R.F. currents out of the batteries; it has a value of 2 mf. C4 keeps R.F. currents out of the output leads; its value is .001-mf. A larger condenser would tend to cut off the higher audio notes.

The tubes, of course, are all battery

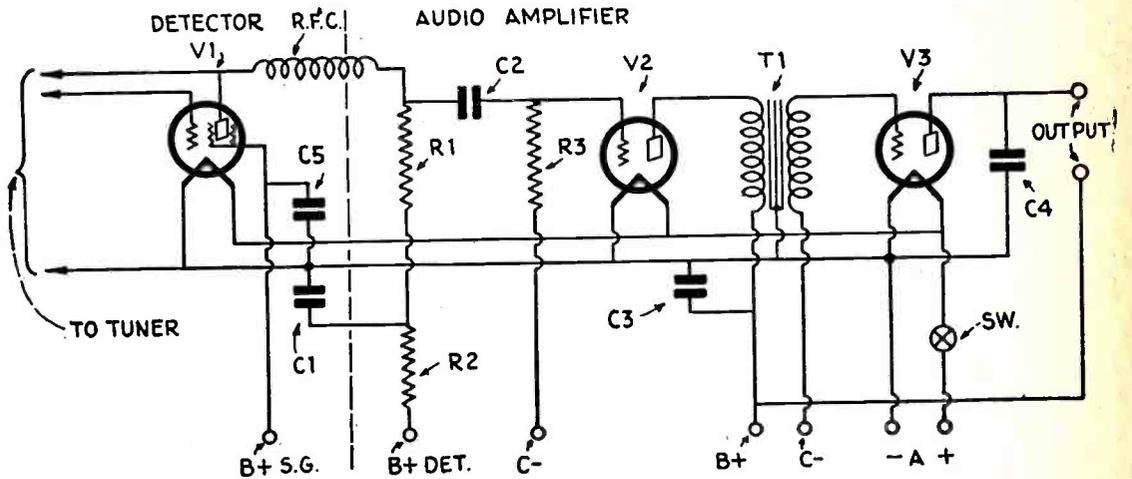


Diagram above shows Mr. Barnett's favorite audio amplifier hook-up for use in short-wave reception. Note that resistance coupling is used in the first audio stage to prevent "fringe howl".

will help to lower the plate voltage so that a higher plate potential than usual will be necessary.

RFC, of course, is an ordinary short-wave R.F. choke. C2 has a value of .004-mf., which is not too large and not too small to pass audio currents. R3 is about 0.5-megohm, but the resistance is not very important and a 2-megohm leak will do, if one is on hand. C3 helps to


tubes, V1 being a screen-grid tube, V2 a general-purpose tube, and V3 a small power tube. This amplifier is, of course, built in a metal case along with the tuner.

In practice it will be found that this amplifier actually does fill most of the ideals set out and is certainly a very useful audio channel for use with any type of short-wave tuner.

New Hammarlund S-W Receiver

By LEWIS W. MARTIN

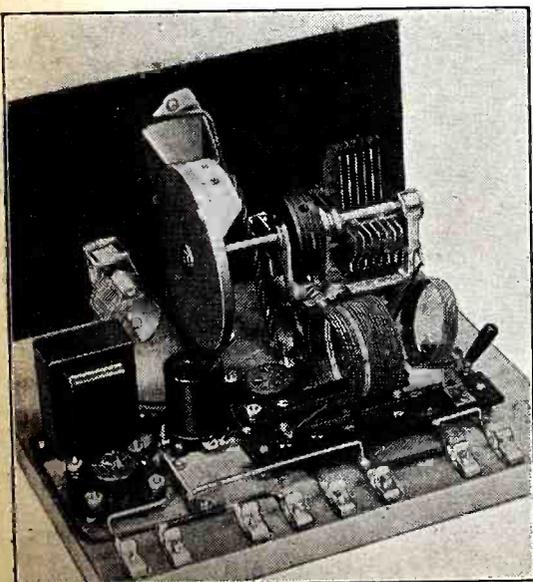Where in broadcasting, elaborate transmitters and receivers must be used



"The Hawk" S-W receiver.


for best results, in short-wave work, ultra simplicity reigns. No banks of tubes, selector systems, multiple amplification methods, need be used. And by simplicity, we not only mean few tubes, but only a major tuning control. Especially is this true with the advent of the new two volt, 230 type tubes. Thus simplicity and efficiency is merged with economy of operation, for only a pair of dry cells are needed.

In the detector circuit, L¹ is a variable primary, affording maximum transference of energy throughout the entire spectrum. Tuning the secondary L² is a .000125 mfd. variable condenser of special design. This condenser uses non-corrosive Midline shaped, brass plates 1/32" thick, which are double spaced. With a full floating rotor mounted in adjustable cone bearings, positive and permanent capacities, and absence of any plate vibration, are assured. A specially developed insulation "Parmica" which most closely approximates the efficiency

of dry air, is used as the insulation medium in this condenser, accordingly reducing the dielectric losses to less than 10% of the ordinary short wave tuning condenser. Further a constant impedance, double wiping contact eliminates all objectionable inductive reactance of the conventional pigtail.

As will be noted, the detector is a regenerative one, using the condenser parallel feed method, the most effective sys-

(Continued on page 328)

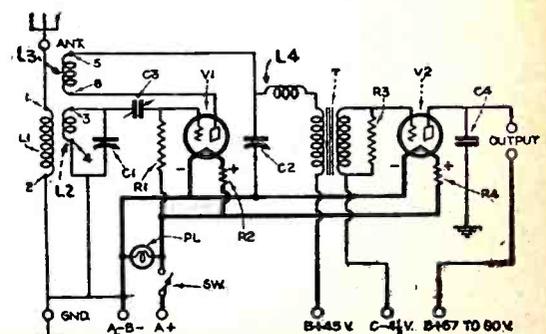

Hook-up of "The Hawk" S-W receiver.




Two Los Angeles officers of the law ready for business—note the loud speaker mounted on the wind shield and which connects with a short-wave receiver.

SHORT WAVES are rapidly coming to the front in police work. They are very useful for broadcasting alarms, either general or special, the reports being picked up easily by short-wave receivers installed on automobiles carrying "cruising" patrols, fire and police boats, etc. Eventually the officer on beat or traffic duty will pick up important alarms by means of a small short-wave receiver carried on his person, or perhaps installed at convenient spots where he is likely to notice a visual signal for attention or else hear it. Important alarms could be indicated by a special signal which would command instant attention by all policemen, wherever seen or heard. A traffic officer might be very busy but if he heard the "Attention" code signal, denoting a special alarm being broadcast, he would concentrate on the message.

General Installation Features

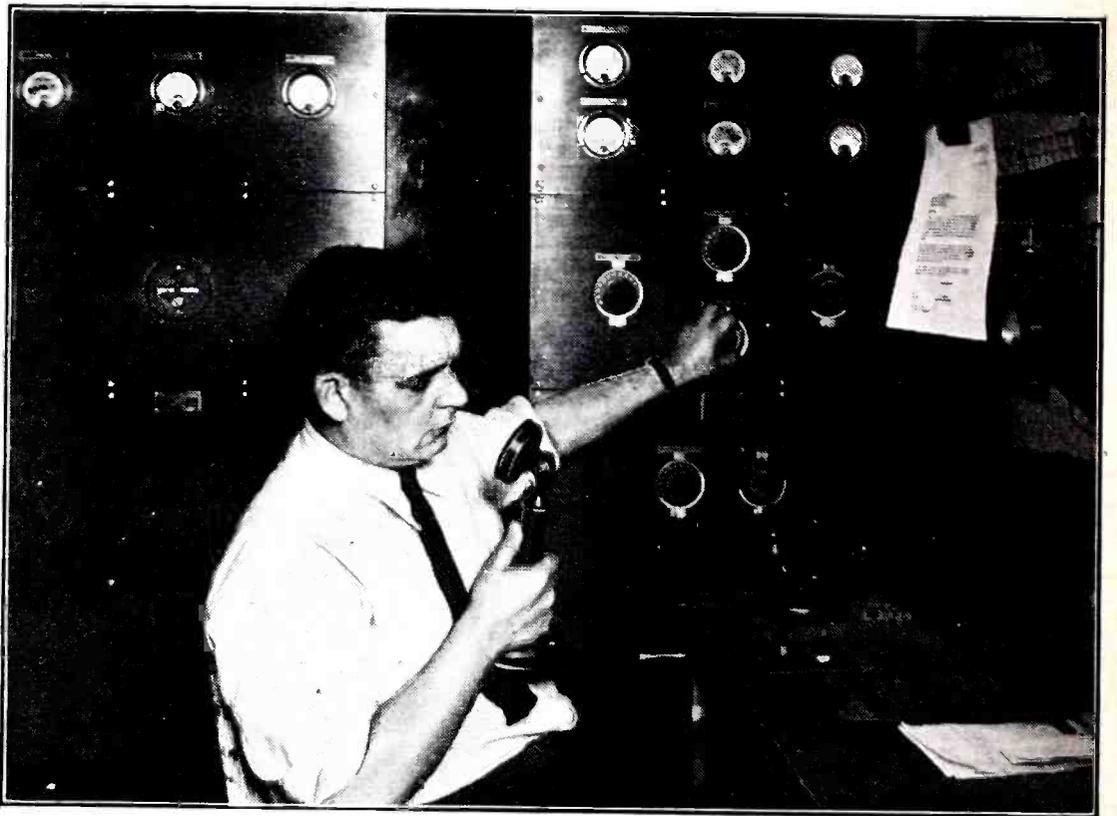The first thing to decide when making a police radio installation is the type of




Sending out an alarm from a short-wave transmitter at Los Angeles police headquarters.

The Delco short-wave police radio receiving set which is fitted in a convenient location on an automobile.


aerial to be used. The following instructions are given by the makers of the Delco police radio apparatus:

Closed Car Aerial—To install an aerial on a closed car, the headlining must be removed so that the aerial screen wire can be fastened under the bows. Use copper screen wire and keep six inches from the metal of the car. Solder a cross wire to the screen at the point where the lead-in is attached.

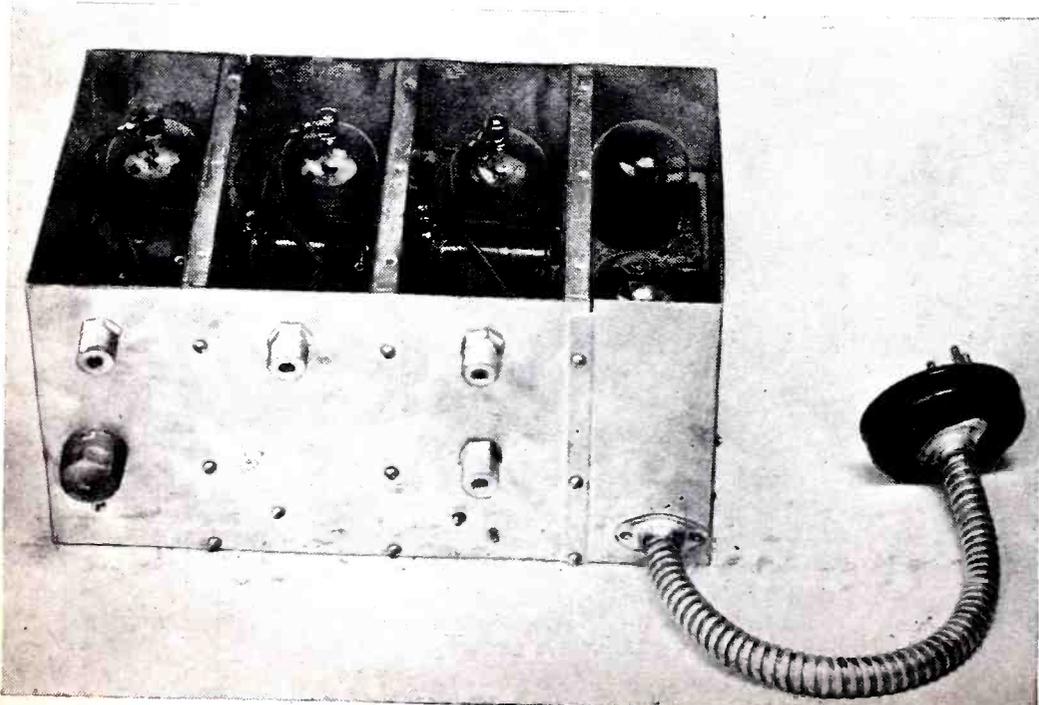In car tops where wire netting is used as part of the construction, the netting should be connected to a cross wire, soldering each wire to the cross wire. Make sure that the netting is *not grounded*. This may be determined by connecting a lead to the wire netting and touching it to the battery side of the ammeter; if no spark occurs the wire



WAVES TRAIL the CRIMINAL TO HIS LAIR

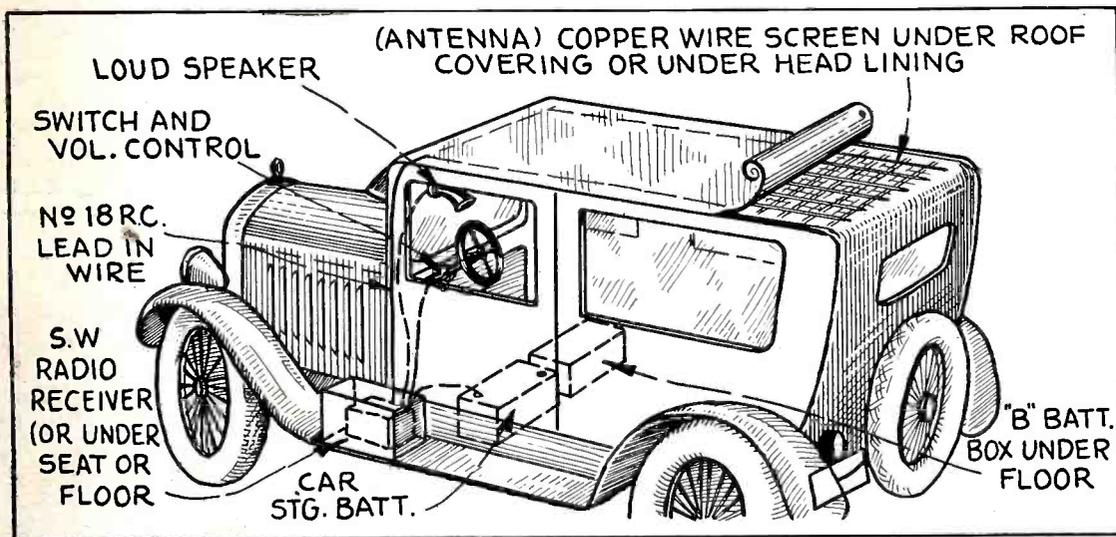


made by mounting the set on the running board, in which case a special waterproof case is furnished with the set. The switch and volume control are mounted on a special panel which is fastened to the steering column.

Install a spark plug resistor in series with each spark plug and a coil resistor in series with the high tension coil lead.

A condenser is used to eliminate spark interference, and should be fastened under the generator cutout relay bracket screw. The lead on the generator condenser should be fastened to the main brush relay terminal. Tubes: 3—224's; 1—112A and 1 Pentode.

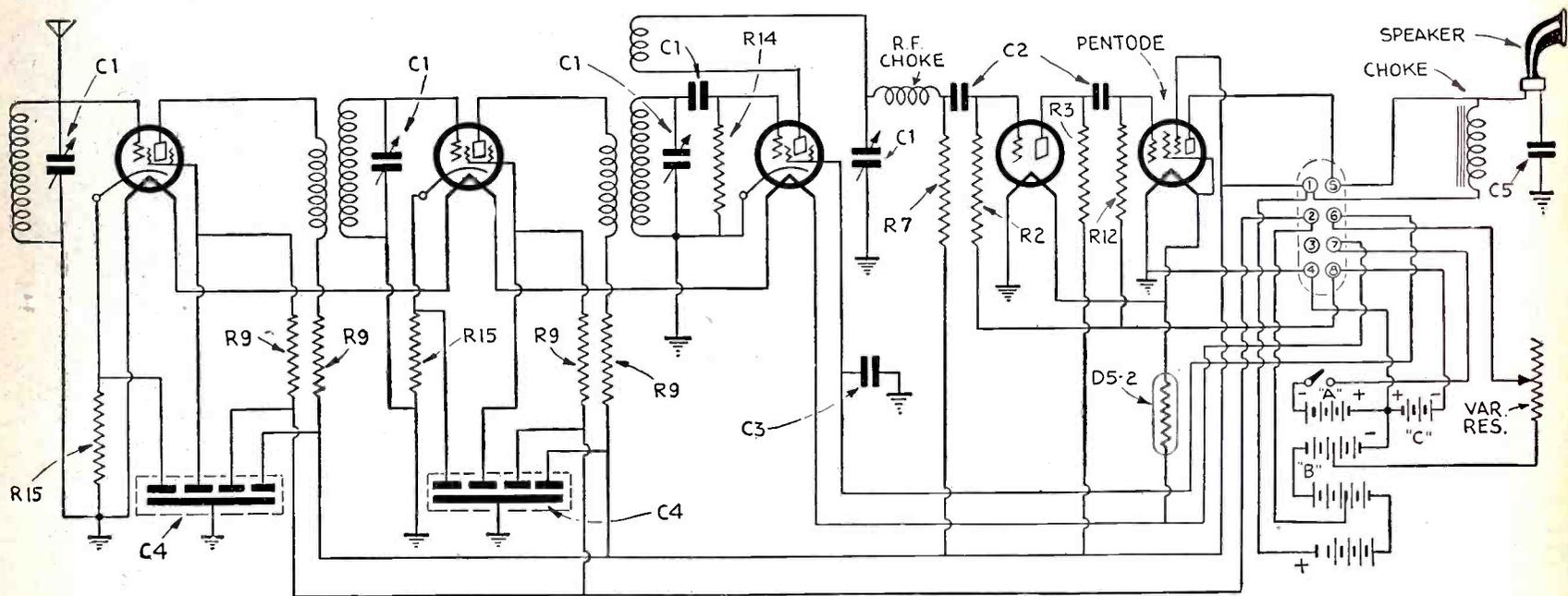← Arrangement of short-wave receiver and antenna on police automobile.



Above: Hook-up for Delco short-wave police receiver, which uses a Pentode tube in the last amplifier stage. Values of Resistors: R2—1 meg.; R3—250,000 ohms.; R7—500,000 ohms.; R9—10,000 ohms.; R12—2 megs.; R14—5 megs.; R15—400 ohms. Condensers: C1—.0001 m.f.; C2—.002 m.f.; C3—.25 m.f.; C4—four .25 m.f.; C5—1.0 m.f.


is not grounded and is suitable for use as an aerial. If it is grounded, the top deck must be removed and the wire investigated to determine the point at which it touches the metal of the car.

In cases where the netting wire construction is used, it must be used as the aerial. Never attempt installation of a different type of aerial.

Open Car Aerial—Use copper screening, placing it over the bows and under the top deck. Fasten the front end to the front cross bow and the rear end to the rear bow. Solder a cross wire to the screen at the point where the lead-in is attached.

Lead-in Wire—Use rubber covered insulated No. 18 wire for lead-in. Connect the lead-in to the aerial at a point nearest the location of the aerial terminal on the radio set. The wire should be just long enough to reach the set and should be kept as far away as possible from other wires.

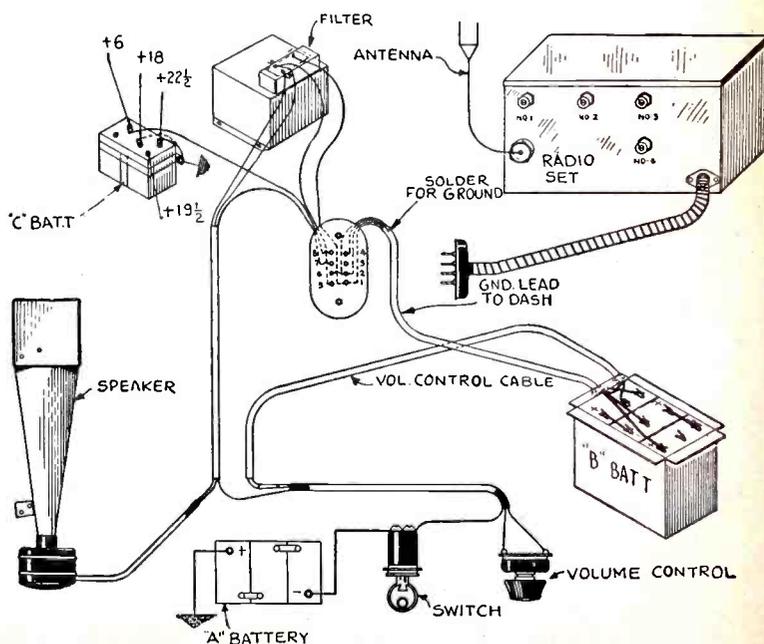Radio Set—The set may be installed in almost any location on the car, depending upon the design. A very efficient installation is



AMONG THE "HAMS"

Station W3CDQ Operated by Miss Elizabeth M. Zandonini



Miss Zandonini's transmitter is a 50-watt Hartley, with mercury arc rectifier; receiver employs detector and 2 stages of A.F.



Miss Elizabeth M. Zandonini, 3320 19th St., N. W., Washington, D. C., operates this very business-like looking station, licensed under the call letters W3CDQ. This station is heard in all corners of the world.

YOUNG HAMS, NOTE

Editor, SHORT WAVE CRAFT:

I have received the following stations on the "Composite Short-Wave Receiver" (described in the February issue of *Radiocraft*): Winnipeg, Canada, is back upon their old wave of 25.60 meters and their call is CJRX. PHI, Huizen, Holland, comes in here with good volume. A new station in New Jersey is W2XAM, New Brunswick, on a wavelength of 35 meters and also heard around 46 meters, testing with Montreal on Tuesdays and Fridays. W6XN is on 23.34 meters, or 12,850 kc., on Tuesday and Friday from 8 P. M. to 2 A. M. W3XAL, Bound Brook, New Jersey, puts over a terrific signal. G5SW doesn't seem so loud lately for some unknown reason. Monday, April 7th, I had G2IV of the S.S. *Majestic*; they were calling G2IR. They are also on during the evenings, around 66 meters. W2XAM is also heard testing around 4 and 5 o'clock in the evening with VE9AP of Drummondville, Canada, who is on around 23 meters. On Sunday, April 2nd, I picked CGA of the Canadian Marconi Company at Drummondville, Quebec, Canada, on 16.501 meters, and also VZA on 23.7 meters at 11 P. M. Their 16.50-meter transmitter shut off at this time. The two were giving music and news reports to GBK at Bridgewater, England, and GLDJ of the *Homeric* on the route from Southampton to New York. They continued until noon.

I trust this will help other fans. I would like to correspond with any short-wave fan of my age (15) or older.

RALPH WYMER,
1438 Chester Street,
Toledo, Ohio.

(Here is a typical letter from a young ham. This is the kind of a letter the editor likes to receive and we can't get too many of them. It is the kind of information that is needed to keep other readers posted. How about it, hams? Send in your letters!—Editor.)

FROM PORTO RICO

Editor, SHORT WAVE CRAFT:

Your previous activities as an editor in the radio field were a success. I refer of course to your writings. I venture to predict that SHORT WAVE CRAFT under your leadership will be just that, this time also. A magazine devoted entirely to short waves was greatly needed in the whole world. The lack of extensive information on this field, especially for the lay public, not only for the amateur, or the veteran enthusiast, to be found in an exclusive magazine, was plain. Therefore, your sentence in the last paragraph of your editorial "The Short Wave Radio Field," in Vol. 1, No. 1, page 5, in your June-July number, "I pledge my word that . . . SHORT WAVE CRAFT will contain 100 per cent short wave material—nothing else," is a good policy.

The first number is splendid. I con-

gratulate you for this achievement. If the U. S. is leading the world as a broadcaster (for local consumption) I do not see a good reason why it should not lead, too, in short wave broadcasting, if we have the three things needed for the attainment: the engineer, the laboratory, and the money. Short waves belong to the world, and the nation that is prepared in the future to penetrate the homes of the neighbors (and the five continents will be neighbors) with short wave broadcasting, will lead in the selling of all necessities in the foreign commerce.

R. DEL VALLE SARRAGA,
Vice-President, Radio Club,
P. O. Box 935,
San Juan, Porto Rico, W. I.

(As our correspondent states, short waves belong to the world, and these are exactly our feelings. We aim to cover the entire short wave field from every angle. If our correspondent keeps on reading SHORT WAVE CRAFT he will find that all of his desires, as far as his short wave inclinations are concerned, will be fulfilled.—Editor.)

FROM AN OLD TIMER

Editor, SHORT WAVE CRAFT:

Congratulations and sincerest wishes for the success of your latest new magazine, SHORT WAVE CRAFT.

The writer has been a charter subscriber to each and every new magazine you brought out from *Modern Electrics* since

1908 and each new magazine has been outstanding in its field and much enjoyed.

May I suggest a subject that I would like to read about in the next issue, namely, some experimental information, medical data, and suggestions on "Ultra Short Waves from the medical point of view."

The General Electric Company and many of the college and medical research laboratories are carrying on studies in this field, and if only some inkling of this data written from the experimenter's point of view could be presented, who knows but what it may lead to another amateur's triumph such as the present short wave success in telephony and telegraphy.

HARRY W. KRUG,
873½ Dewey Ave.,
Rochester, N. Y.

(Here is a real old-timer who has been in the game since the coherer and spark gap days, and he may be presumed to know his stuff. It is a pleasure to hear from our old friends. Incidentally, Mr. Krug's request has already been fulfilled. We are going to have more to say about "Ultra Short Waves from the medical point of view." A tremendous amount of this kind of work is now being done in Germany and we are getting a good supply of articles right along.—Editor.)

MORE HAM STUFF

Editor, SHORT WAVE CRAFT:

I want to offer you my heartiest congratulations for starting such a wonderful radio magazine as SHORT WAVE CRAFT is. It is the best short-wave magazine ever published, in my opinion. I have a few suggestions to offer. Why not have the section "Among the Hams" enlarged to a full page or even more? Very few magazines have ever published constructional details for a real good short-wave super-heterodyne. Why not publish a few of these? In closing, I wish to say that I am sure that a great many short-wave enthusiasts hold the very same opinion that I hold in regard to your magazine and will back it up from the start.

ALBERT SOBEL,
9 Cuthbert Place,
Kew Gardens, L. I.

(Well, Albert, your wish has been fulfilled. Here we are with two whole pages and we hope it makes you happy. We will have, with your help and the help of other hams, a page or more a month, but it is up to you to keep on shooting the material to us. Remember, this is your own page, but we can't publish it unless you shoot along the dope. As to the short-wave superheterodyne, you will notice we have published several articles along this line already and will continue to publish more.—Editor.)

English Amateur 5-Meter Station, G2DT



Mr. E. T. Somerset, English short wave amateur, operates this station G2DT, and experiments with wavelengths as low as 5 meters. Left to right—5 meter receiver; G.R. frequency meter type 558-P; full dial spread 9 to 90m receiver; 20 meter Hartley HI-L transmitter; frequency monitor; 40 meter Hartley transmitter; 5 meter transmitter (not visible in photo); M-L dynamotor; D.C. power supply.

MORE DOPE

Editor, SHORT WAVE CRAFT:

WSBN, the S.S. *Leviathan*, is now on about 75 meters.

G2GO, the S.S. *Americ*, is on 70 meters. This station was testing with WOO, May 20th, and was 400 miles off shore. It came in with good volume and cut right through a lot of code interference.

WOO, at Deal, N. J., is now on 62 meters.

A Drummondville, Canada, station on 62.70 meters came in here with plenty of volume. They were sending a program to the S.S. *Larentic* and the S.S. *Duchess of Richmond*. I could not understand the call letters and I think they were in French. I would like to know the call letters of this station. If anyone understood them I will appreciate it if a fellow reader will send them to me.

W. GOSCH,
296 Peck Street,
New Haven, Conn.

(This is the kind of dope that the hams want, and again we say, keep on shooting it in. We will publish as much of it as space permits.—Editor.)

Station Photos Wanted!
Send in photos of your short-wave station and one of yourself. Give brief description of apparatus used and results achieved.

"RED" BROADCASTS!

Editor, SHORT WAVE CRAFT:

I enjoy your magazine very much. I think it is the very best radio magazine published. I would like to correspond with short wave fans, especially constructors of the Super-Wasp. I will answer all the letters I receive.

RICHIE THOMAS (RED) HEPBURN,
Rogers, Ohio.

(No comment needed on the above, either. Now, you hams, get busy and snow-under "Red" with your letters and postal cards. Serves him right.—Editor.)

HE WANTS TELEVISION ON S. W.

Editor, SHORT WAVE CRAFT:

I have read the first copy of SHORT WAVE CRAFT and I kind of think I'd like to get it regularly, so you'll find a money order for a dollar and a half to cover a year's subscription.

The first number is fine, except that I couldn't find any television, but there will probably be some in the subsequent numbers—I hope so. Maybe there will even be an article or two on facsimile. Why is it that there is so little reading matter on these two interesting subjects?

I'm very glad to find that I am a "S. W. P. H.," having sent some dope to *Radio Craft* some time ago.

Yours for the best of success with your new enterprise, I am.

PAGE TAYLOR,
3790 Ashland Ave.,
Detroit, Mich.

(Continued on page 334)

The Influence of the Earth's Atmosphere on the PROPAGATION of RADIO WAVES

IF THE radio waves coming from the earth, which penetrate the ionosphere, are there deflected, and return again to the earth at a distant point, actually follow this path, according to this diagram they should not be

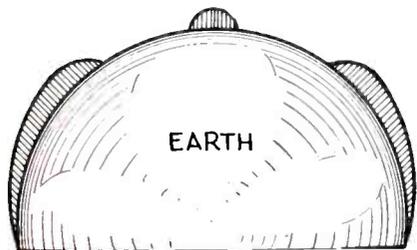


Fig. 6

The principle of the behavior of short waves.

By DR. J. FUCHS

PART II—Conclusion.

Dr. Fuchs, famous European expert on short-wave phenomena, explains in an interesting way such important subjects as—Skip Distances—The Echo Problem—What Wave Velocity Shall We Use?—Signals That Encircle the Earth Three Times.

same reason already so great that a really dead zone, where nothing at all is heard, no longer exists. The effect is shown merely by a slight decrease of the signal-strength, but it disappears al-

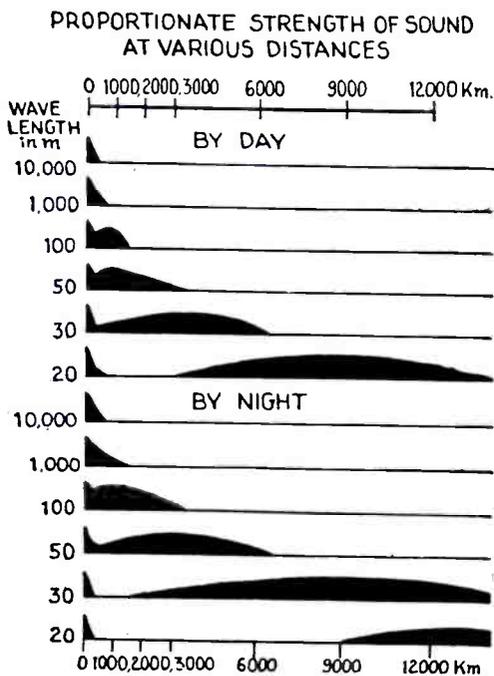


Fig. 7.

The audibility of short waves under various conditions.

most entirely in the case of still greater wavelengths. In the case of telephonic wavelengths of a few hundred meters it is still marked, as appears from a work by Captain Round (Fig. 8).

From Fig. 7, moreover, there is another conclusion to be drawn, of practical significance: if wireless communication is to be kept up over a certain distance for the 24 hours of the day, it will be necessary to change the wavelength at least once. For a distance of 4,400 miles—for instance, that from Vienna to New York—one will use by day the waves under 20 meters, but by night the 30-meter wave will provide the greatest energy at the place of reception. It is a practical advantage, of using

the wavelengths under 100 meters, that by this means one may cover longer and shorter distances equally well, merely by the correct choice of the wavelength, without having to alter the power of the transmitter, while in using waves above 100 meters, increases in range can be attained only by increasing the energy.

Aside from the proved dependence of the extent of the dead zone upon the wavelength and time of day, it is dependent also upon the time of year. In general, the deflection in summer is much greater than in winter, because of the strong solar radiation, and consequently the dead zones are much smaller. The propagation conditions on a summer night are, occasionally, the same as those on a winter day. For this reason Fig. 7 represents also very well the difference in propagation on a summer night and a winter night.

The Echo Problem

Very remarkable situations and phenomena occur if still shorter wavelengths are used for transmission. It is to be expected, from studies of other wavelengths, that in such a case the deflection by the influence of the ionized atmosphere will be a slight one. The wave will, accordingly, remain a very long time in the higher atmosphere before coming down again; the dead zone will become larger, and the question now arises whether—with even shorter wavelengths—the dead zone would not become so large that the wave simply could not return to the earth at all, but would circle above it, be lost in space.

Through observations made in the last few years this problem has suffered a very peculiar complication.

If the wavelength is shortened to 20 meters, the dead zone and with it the range as well become so great that the signals of station A (Fig. 9) are heard

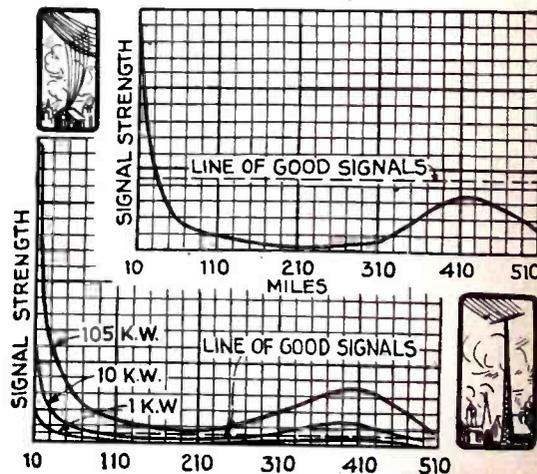


Fig. 8.

The audibility of radio waves at various distances.

detectable at a place on the earth lying on the line between the transmitter and the receiver. Under certain conditions this is the case. Fig. 6 shows the curve of the signal-strength under such circumstances. In the immediate vicinity of the transmitter we have great signal-strength; then for a certain distance they are not to be detected, since they are high up in the strata of ionized air, while further on the intensity of the signal begins to rise again, reaches a maximum, and then slowly but finally decreases.

Here the same phenomenon occurs that is found in the propagation of sound; namely, a "dead zone," also called a "zone of silence." The area of this dead zone often varies extraordinarily for all possible reasons, but from the previous explanations we know that a change of the dielectric constant is at the bottom of them all.

The figure No. 7 shows conditions which may occur, for instance, during a winter night. From this, one can plainly deduce that the location of the dead zone is governed by the time of day as well as of the wavelength. By day the ionization is greatest. This corresponds to a great difference between the angle of incidence and the angle of reflection; accordingly a wide deflection. The waves cannot reach great heights, but come down again instead after a short distance. Therefore, the dead zone is always smaller by day than by night.

If, for example, we compare the dead zone of the 20-meter wave by day and at night, we plainly see a marked difference, for it is a matter of thousands of miles. But a dependence on the wavelength is also plainly evident in this case. In fact, for the same time of day the dead zone becomes wider as the wavelength used is shortened.

In the case of wavelengths of more than 50 meters, the deflection is for the

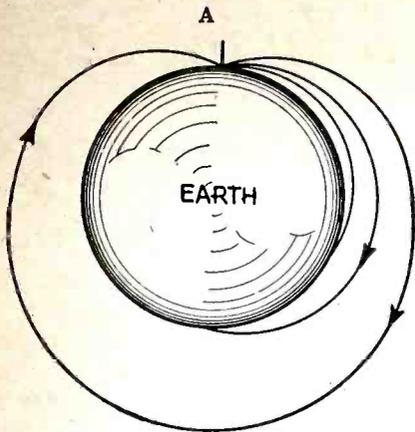


Fig. 9.

Radio waves which encircle the entire earth.

not only at the antipodes, but also are heard again at A after a complete circuit of the earth. This fact was first observed in the year 1926.

Signals Encircle Earth Three Times!

An observer in the vicinity of station A will therefore first receive the direct signal sent out from the station and about one-seventh of a second later the signal which has encircled the entire earth. In the case of later and more exact investigations, it was possible to establish the fact that signals were also perceptible two-sevenths, and even three-sevenths, of a second after the main signal. These were signals which had gone around the earth two and three times and were nevertheless still strong enough, in spite of the great distance traveled (some 75,000 miles), to be recorded at the receivers.

The multiple arrival of such signals is very undesirable for radio telegraphers. The signal arriving later has, of course, the same character as the first signal (being therefore either a dot or a dash) and acts exactly like an acoustic echo. Under certain conditions of rapid telegraphic transmission, it can happen that the signals run into each other and become impossible to read. Because of its correspondence to acoustic echo, this electrical phenomenon is called "echo." It corresponds to a single, double or triple echo, according as the signal has encircled the earth once, twice or three times.

In Fig. 10 you see such an echo signal, which was received by means of a cathode-ray oscillograph. One plainly recognizes the principal signal, then the first and the second succeeding signals. As a time marker a 500-cycle alternating current is impressed on the record, by which one can measure exactly the interval of time between the main signal and the echo.

Another kind of echo formation, shown in Fig. 11, indicates the conditions under which (as, for example, in the winter months daily at about 3 o'clock) the signals of American transmitters, operating on about a 20-meter wavelength, can be heard with a very strong echo effect. One impulse of the New York transmitter comes on the direct path across the Atlantic, its dead zone and its range, however, being relatively small, since the whole distance is in daylight.

The part of the wave which goes around the other side of the earth, however, finds night there; its dead zone and range are then so great that it too reaches Vienna, but somewhat later than the direct one. The result is the formation of an *echo*.

Another echo occurs if the original wave can again be propagated further over the dark side of the earth and afterward be received again in Vienna from the same direction. One speaks of direct and indirect echo in terms of the direction of the principal path.

For the interval of time between the main signal and the first echo, it makes a difference whether the radio wave has traveled at great heights or close to the earth, because great differences in the distance covered may result. Attempts have been made to calculate, from the actually-measured time and the velocity of light, the average height at which the

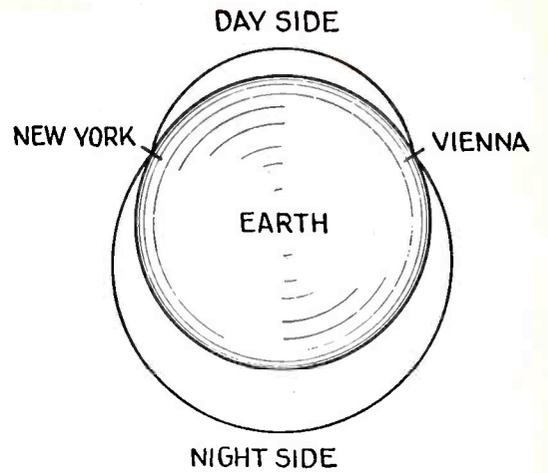


Fig. 11.

How the "echo" occurs.

is 240,000 kilometers (150,000 miles) a second; in winter, 269,000 kilometers (168,000 miles); there therefore appears to be a dependence on the time of year. These figures agree well with Lambert's, so that probably there can be little doubt about the whole matter.

The reason for this interesting fact, as already mentioned, can be now assigned; it is that radio waves travel in very high strata of the terrestrial atmosphere, which makes the velocity of propagation come out smaller. In the case of Lambert's figure, however, these waves must have penetrated to a height of about 3,000 kilometers (over 1,800 miles), which would seem very improbable in view of all we formerly thought we knew.

There is a further possibility of explanation in the fact that radio waves en route from transmitter to receiver have to do some work, be absorbed, and therefore suffer a diminution of their velocity. In the past three years increased attention has been directed to this question, and work upon it has been characterized by two conceptions long current in other fields of physics: phase velocity, and group velocity.

The Group Velocity

We can only measure the *group velocity*. Therefore Lambert's result, that the propagation of radio waves occurs at a velocity of 247,000 kilometers (154,000 miles) a second, is at any rate a group velocity, even if we do not yet know how it has come about. The group velocity is that which controls the transfer

(Continued on page 331)

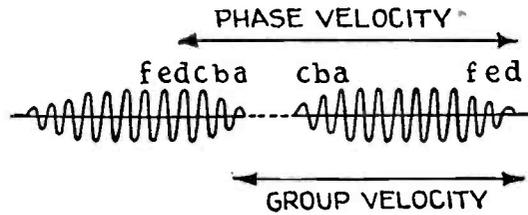


Fig. 12.

Illustrating phase velocity and group velocity.

radio waves had followed their course over the surface of the earth. There resulted an estimated height of 120 miles. Although this figure fits in with our previous considerations, it cannot be regarded as a confirmation of them, however.

What Wave Velocity Shall We Use?

It is in fact highly questionable whether one can use for this purpose the figure obtained for the speed of light waves in a vacuum (the latest value is 299,790 kilometers, or 186,282 miles, a second). A. Lambert, by very extensive research, has been able to confirm and re-determine the conclusion that the speed of radio waves differs considerably from that of light waves, amounting in fact to 247,000 kilometers a second plus or minus 9,000 (that is, from 160,000 to 149,000 miles a second). Independently of this, the Japanese, M. Hasimoto, has moreover calculated that the velocity of propagation in summer

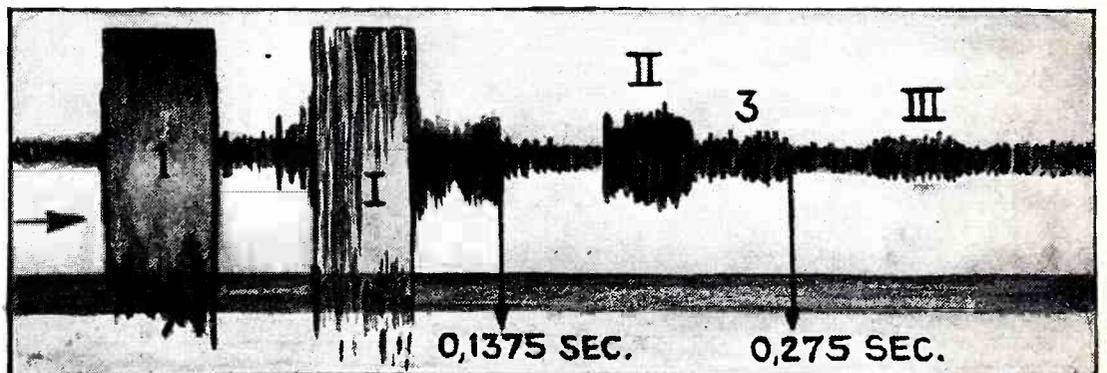


Fig. 10.

Oscillogram of a triple echo.

AN 85 METER PHONE TRANSMITTER

By R. WILLIAM TANNER, W8AD

This 85 meter phone transmitter operates without a crystal control. The output is 15 to 25 watts; range up to 1,000 miles; 100 per cent modulation possible; bias-variation system of modulation employed. Master oscillator-power amplifier system used, ensuring freedom from swinging antenna effects. Cost of complete transmitter, including tubes and microphone, can be held down to \$70.00.

NO DOUBT many of the experimentally-inclined broadcast listeners using short-wave receivers have tuned in on amateur 'phone stations and wished that they too could transmit by voice. The greatest obstacle

When designing this efficient little transmitter, the writer took into consideration the many types of circuits available. Considerable experimenting was done to determine the best layout for one not familiar with the radiation of

ates any effect of a swinging antenna upon the frequency of oscillations. The oscillator employs a '12A tube in a "high C" Hartley circuit tuned to half the frequency of the emitted wave. The second harmonic excites the grid of a '12A fre-

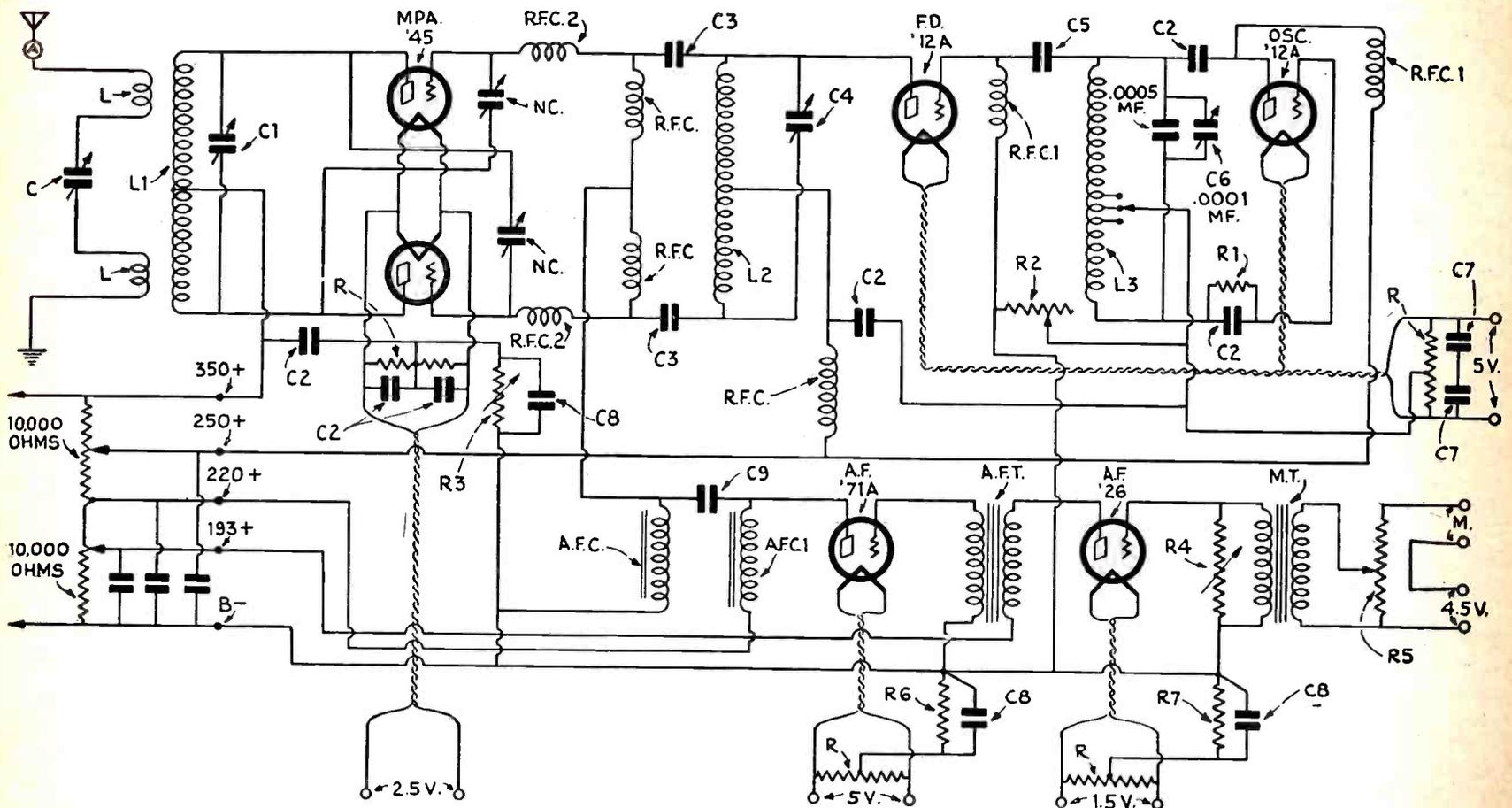


Fig. 1—Shows complete hook-up of 85 meter phone transmitter, with microphone modulator circuit in lower right hand part of diagram, the microphone being connected to terminals marked M.

to the beginner is the lack of really authoritative data on the subject.

The purpose of this article is to submit sufficient details to enable the novice, who is capable of constructing a successful multi-tube broadcast receiver, to build and operate a phone station.


It should first be impressed upon the mind of the would-be operator that, before placing any type of transmitter on the air, it will be necessary for him to obtain both a station and an operator's license from the district Supervisor of Radio.

electromagnetic waves. The circuit shown in the diagram (Fig. 1) proved to be comparatively simple in construction and operation, giving a high output at a relatively low cost. The tubes required are all of the receiving type, and the plate supply is obtained from an '80 rectifier. The power output to be expected is in the neighborhood of 15 to 25 watts on the modulation peaks. Under favorable conditions, distances up to 1,000 miles may be covered.


The circuit is a self-excited master oscillator-power amplifier, which elimin-

frequency-doubler, operated considerably below the plate current cutoff. The output of this tube is amplified by a pair of '45 tubes, connected in a push-pull arrangement, the grid-plate capacities being neutralized to prevent oscillations. The constancy of frequency with this combination is comparable to that of a crystal-controlled outfit, and due mainly to the second-harmonic oscillator.

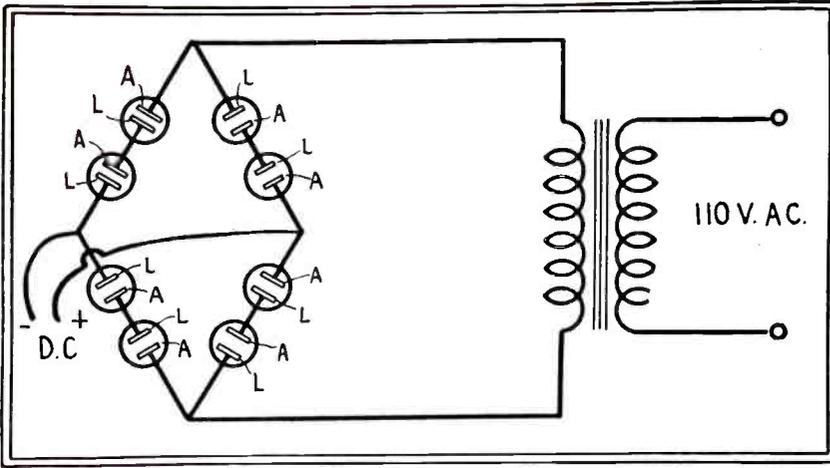The bias-variation system of modulation, developed by the writer about two years ago and described in *QST*, is employed. Properly adjusted, 100 per cent.



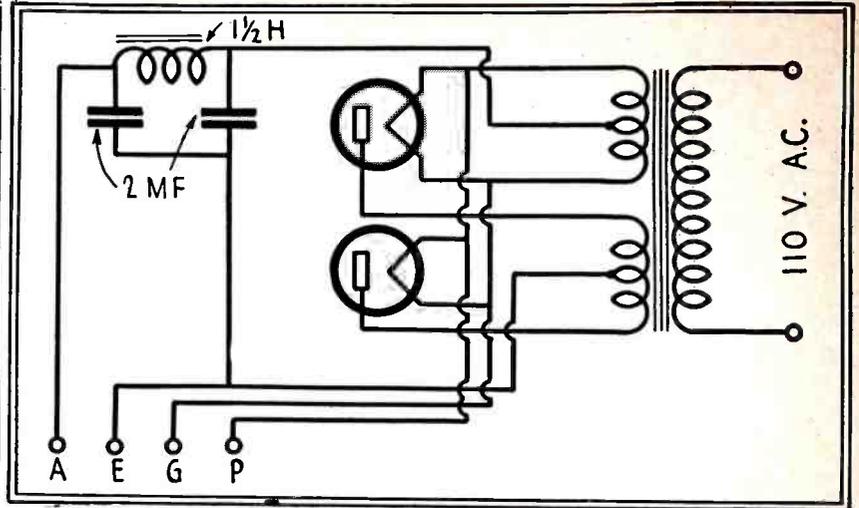For the plate supply 20 rectifier jars are required for 500 volt transformer, connected in bridge fashion as indicated.



Optional full-wave rectifier hook-up employing two vacuum tubes of the half-wave type.

The Hartley Short Wave Transmitter


By
LESTER C. KIRSCH

HERE is a short-wave transmitter that will cover a great distance, and can be built out of old parts lying around on your work bench. It is used for code work. The inductance can be made out of copper gas tubing 1/4-inch in diameter, or copper ribbon. The primary inductance (4) consists of eight turns; the secondary inductance (5) of two and two-thirds turns, 5 inches in diameter and 6 inches long, spaced about 1/4-inch. The choke coil (1) can be constructed by winding 150 turns of No. 28 or No. 30 D.C.C. wire on cardboard or wooden tubing 3/4-inch in diameter. An '01A or a '10 tube may be used in this transmitter.

Power Supply

If the builder contemplates using the '10 type of tube, it would be best to use a step-up transformer and some scheme of rectification, instead of trying to employ "B" batteries. The '10 tube draws approximately 60 milliamperes at 350 volts on the plate and it would be much

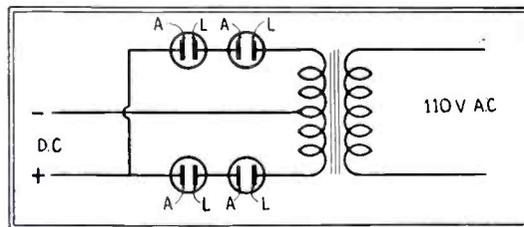better to use rectified alternating current for the plate supply instead of batteries, as the batteries will not stand up under





Center—Tap transformer with electrolytic rectifiers to give full wave rectification.

this heavy drain for a considerable length of time.

If it is desired to work the '10 tube at full capacity, it will be necessary to have a power transformer with a center

tap on the secondary so that 500 volts are supplied on each half of the secondary. The rectifier tubes can be of the UX-216B or UX-281 type, or any other which will satisfactorily handle this voltage and current. The filament secondary winding is used to supply the current for the filament of the rectifier tubes and the oscillator tube. This winding is tapped in the center as shown in figure. Voltmeters may be connected so as to indicate the A.C. filament voltage and the D.C. plate voltage respectively. These may or may not be used; however, they are valuable adjuncts to the power-supply set.

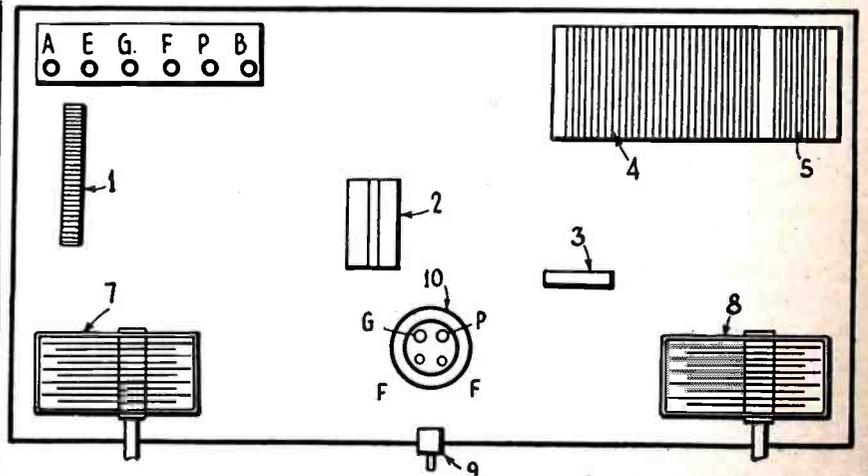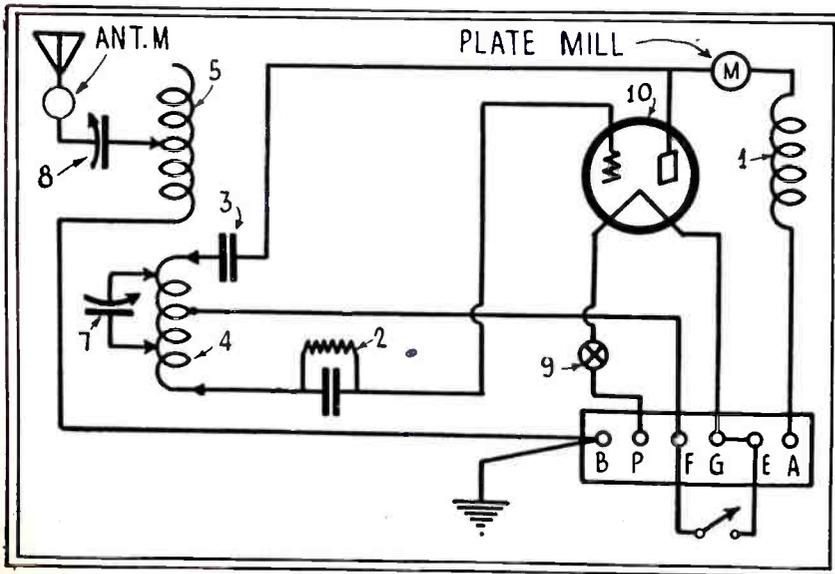The audio-frequency choke coil shown in diagram and marked 1 1/2 H should have an inductance of 1 1/2 henries and be capable of carrying 150 milliamperes. The filter condensers may be either 2- or 4-mf. capacity and must be capable of operating above 500 volts. The whole power supply can be mounted as a separate unit; or you may build the power supply and use jars for a rectifier, which



At Left—General hook-up of short wave transmitter to aerial and ground. Right—Suggested arrangement of apparatus on sub-panel.

saves rectifier tubes and serves the same purpose. The jars can be glass tumblers, or ½- or ¼-pint size mayonnaise jars. The aluminum can be cut from an old aluminum kettle (be sure to clean the aluminum with sand paper) or shields out of an old radio set may be used. The lead should be sheet lead. If you have a transformer that puts out 500 volts, or less, use the bridge-type rectifier.

When you have finished the rectifier and turned on the power, watch your transformer and do not let it get hot, or a burn-out is probable.

Use a '01A and put five volts on the filament and from 90 to 425 volts on the plate; if you use 400 volts on the plate of the tube a great distance can be covered.

Baking soda can be used for the solution in the rectified jars, 1½ tablespoonsful to one gallon of water. The aluminum plates will form white. If a transformer puts out 500 volts, twenty jars should be used.

List of Parts

- (1) Radio-frequency choke coil;
- (2) .001-mf. grid condenser (receiving type) and one 5,000-ohm "Lavite" transmitting grid leak;
- (3) .002-mf. plate condenser, receiving type;
- (4) Primary inductance;

- (5) Secondary inductance;
- (6) Two brass angle supports for inductances;
- (7) .0005-mf. variable condenser (receiving type will do);
- (8) .0005-mf. variable condenser (receiving type may be used);
- (9) Filament switch;
- (10) UX-type socket.

Power Supply

- (1) Step-up transformer;
- (2) Audio-frequency choke, 1½ henries, 150 milliamperes;
- (3) Two- or four-mf. filter condensers;
- (4) Rectifiers;
- 20 glass jars;
- 20 lead strips;
- 20 aluminum strips;

Aluminum and lead strips should be one inch wide and as long as the depth of the jar.

Assembly and Wiring Data

Just a word regarding a few of the parts which may not show up very clearly: one terminal of the choke coil (1) is soldered directly to the lug of binding post A on the binding-post strip. This will rigidly support this coil.

The grid condenser (2) and the plate blocking condenser (3) are elevated from the baseboard by means of short, stiff wires to which they are connected.

The inductance coils (4 and 5), are fastened to the baseboard by means of brass brackets. It is necessary for the builder to realize that, although they are mounted in one unit, they are in reality two separate coils. The one with the greater number of turns of wire (4) is mounted towards the left; this is the primary or closed-circuit coil. The other coil (5), which has a small number of turns, is the secondary or antenna coil. Connections to these coils are made by means of the clips supplied with leads of flexible rubber covered wire.

The wire coming from the binding post (B) is permanently soldered to the inside turn of the inductance coil (5). In like fashion, the wire coming from the condenser (3) is soldered to the inside turn of coil (4). All other connections to the coils are made with flexible wire and clips, so that they may be shifted from turn to turn, to correspond to the wavelength required.

All wiring except that going to the inductance clips should be made with bus-bar wire of the usual type, and covered with black cambric tubing or spaghetti.

For the low-power tube, a thermocouple radio-frequency meter reading 0-to-100 or 0-to-500 milliamperes will be satisfactory. But if a '10 tube is used, it is necessary to employ a 0-to-1 thermocouple radio-frequency ammeter, and a plate D.C. milliammeter of 0-to-100 ma.


How to Use Short Wave Wavemeters

By A. Binneweg, Jr.*

TO greatly facilitate the location of proper dial settings for foreign broadcasting stations and thus popularize the new all-electric A.C. receiver kits recently placed on the market, the Delft Radio Co. is manufacturing a special inexpensive short-wave wavemeter. This was briefly described in the last issue of SHORT-WAVE CRAFT. However, due to the fact that few short-wave listeners understand how to operate a wavemeter, its use will be described here in more detail. The wavemeter, representative of a good design, is shown in the illustration herewith.

A wavemeter in its simplest form is a calibrated tuned circuit. To use it, couple it closely to the tuned-circuit of the detector (which must be oscillating weakly for most accurate results). When the dial of the wavemeter is varied (and the proper plug-in coil is used so that the wavemeter will tune to the wavelength of the receiver), the detector tube will stop oscillating when the wavemeter is tuned exactly to it. By varying the coupling between receiver and wavemeter coils, a very sensitive position is soon found which yields very accurate results.

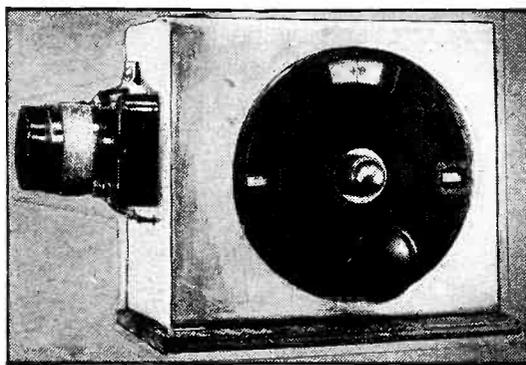As soon as the point at which the wavemeter causes a click in the receiver (as heard in the head phones or loud-speaker) is found, the dial of the wave-



The Delft short wave wavemeter.

meter is read and the wavelength to which the receiver is tuned is thus accurately found.

Although changes within a short-wave receiver may influence to considerable extent its dial settings, the calibration of a wavemeter is constant and always ready for use.

If an accurate wavemeter is desired, it must be calibrated from accurate standards. To design one of these instruments to cover the range of 15 to 125 meters with the required overlap between coils, and such that the calibration remains constant, is a problem for specialists with the required laboratory apparatus. Careful shielding is also necessary to prevent hand-capacity effects.

Users of wavemeters should take care to see that the detector tube is oscillating. Be sure to couple to the secondary coil in the detector otherwise no results will be obtained. It would be of no use to couple the wavemeter to coils in the R.F. amplifier because the sensitive condition does not obtain there.


Wavemeter Problems

Suppose that you wanted to locate beforehand a certain receiver dial-setting so that you could hear a certain station when it came on. This is the reverse process of finding the wavelength to which your receiver is tuned.

First look up the wavelength of the station in SHORT-WAVE CRAFT. Next select the particular coil which, when plugged into the wavemeter, will allow the wavemeter to tune to this wavelength. Then set the dial of the wavemeter to that wavelength. Bring the wavemeter close to the secondary of the receiver and vary the receiver dial until you get the familiar click. When obtained, your receiver is tuned exactly to the proper wavelength and the desired station is then heard. It sounds long, perhaps, but its all very easy, especially if you have a good wavemeter to start with and all necessary instructions.

The technical and practical considerations, as well as the matter of popular price have here been admirably met.

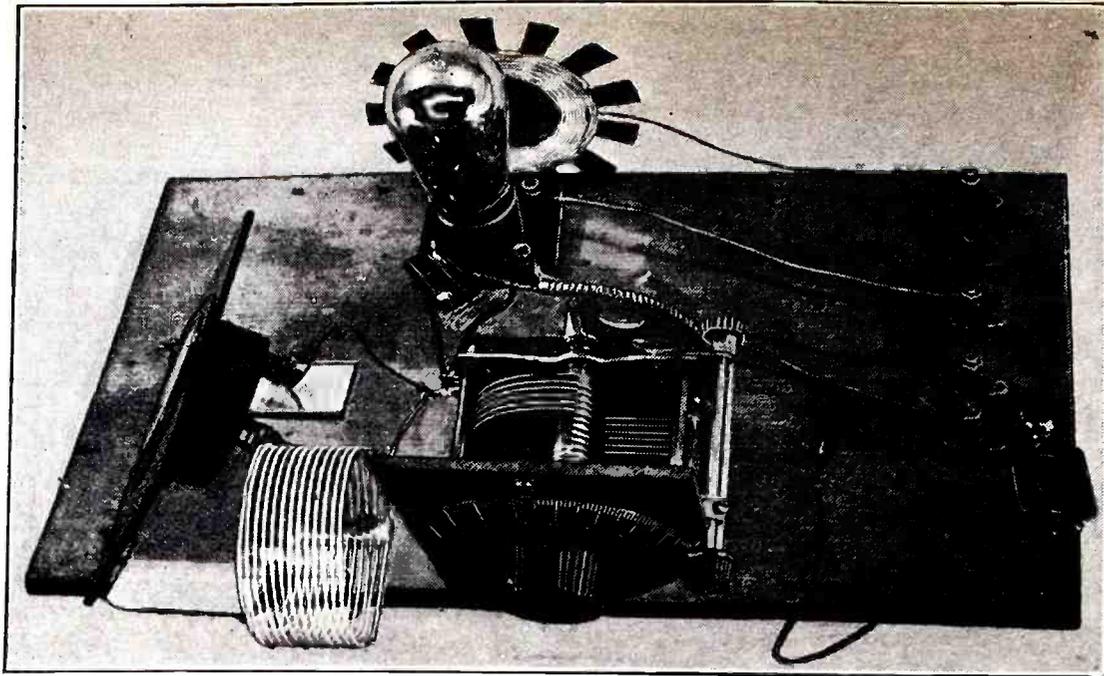* Short-Wave Radio Engineer, Delft Radio Co.



Inexpensive power-amplifier for 80 meter operation. The clip connects with the oscillator inductance.


Explaining the Simple Relation of the Oscillator, Amplifier and Crystal

By A. BINNEWEG, JR.

ONE of the most important considerations in the design of modern transmitters is that the frequency must remain constant within narrow limits. The days of "climbing" and "frequency-modulated" signals are over. A low-power transmitter, properly operated and adjusted, is better than a high-power rock-crusher that takes up too much space. The use of screen-grid tubes in short-wave receivers has made the low-power transmitter unusually effective.


We are not insinuating that high power is not good. High power is a wonderful thing—if you know how to use it—but the great majority of transmitters will be of necessity low powered. A good low-power outfit is another wonderful thing.

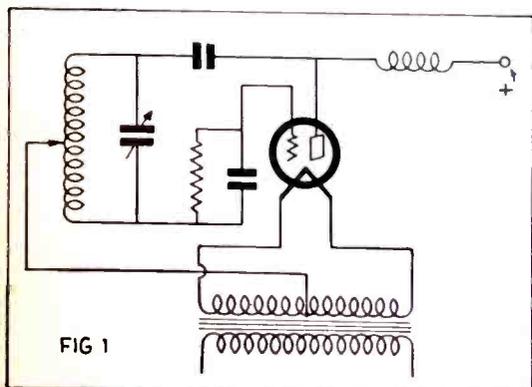There are two requirements, therefore, for a story that will interest the majority of "hams." These are: first, a constant-frequency transmitter, and, sec-



Hartley circuit used in the master oscillator.

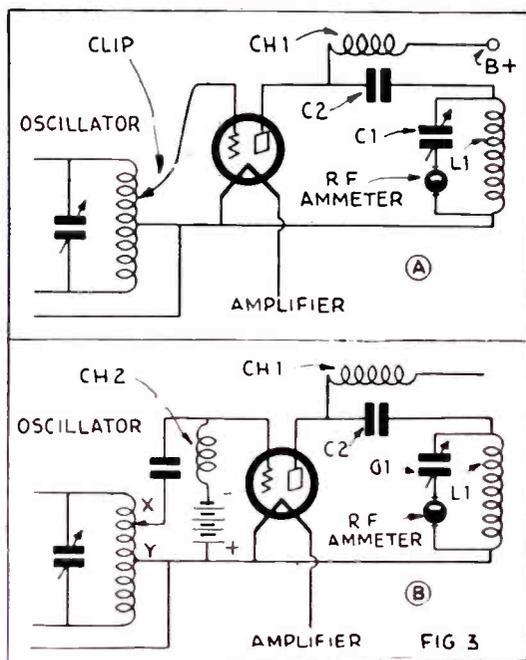What is a master oscillator? A power amplifier? How does one connect a quartz crystal control to provide constant frequency transmission?



Developing a suitable amplifier for transmitting a constant-frequency signal.

only, low power. The practical sets discussed here are not only low-powered, but they furnish a remarkably constant frequency and are simple to adjust and operate. Circuits are developed which can be used with any power, of course.

"Constancy" Is Relative

When one speaks of "constant frequency," a little grain of salt must be consumed, for there is no such thing. What we are thinking of is the most constant frequency that can be economically obtained, within the limits allowed by the state of the art. That makes reasoning simpler from the start. Self-excited oscillators are all right, but to get a good, steady signal out of them for a certain length of time is often a tricky occupation. A good master oscillator with a power amplifier is even better (who said they are more complicated?). Crystal control (discussed later) is even better, but let's start with the master oscillator-power amplifier, which is less expensive, though when we speak of master oscillators we mean good ones.

A master oscillator is simply an oscil-

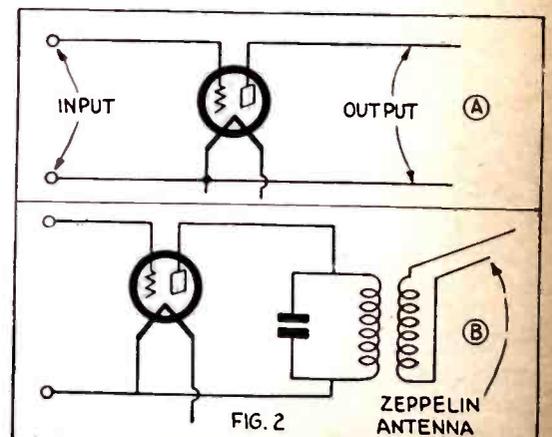


Fig. A—Simple amplifier. Fig. B—Theoretical amplifier feeding a Zeppelin antenna.


lator that behaves. It is separated from the transmitting antenna by an R.F. amplifier and there are, therefore, certain advantages similar to those obtained by introducing an R.F. amplifier between the detector and the antenna in a short-wave receiver. (We assume that the reader can read circuit diagrams backwards. Most amateurs shy at the terms "master oscillator" and "power amplifier." A master oscillator is simply an ordinary good oscillator, and a power amplifier is simply an R.F. amplifier.)

Having cleared up the most obvious difficulties, we can make it even simpler. Fig. 1 shows about the simplest circuit that one can assemble; this is our master oscillator. In order that its frequency shall remain constant, during prolonged CQ's, a relatively large amount of capacity must be used in the oscillating circuit, and the blocking condensers must be small. This means that a good .0005-mf. receiving condenser will serve for 40- and 80-meter operation; such a condenser will require for an inductor about eight turns of copper tubing, on a 2-inch diameter, at 40 meters (or its equivalent, as will appear later) and about twice the number of turns, or equivalent inductance, for 80-meter operation. Work at 20 meters requires about three turns. Blocking condensers of 100 mmf. capacity are needed; the grid leak is 10,000 ohms. A type '10 tube and socket, and the choke about finish the oscillator. Use about two hundred turns of No. 26 wire, on a 1½-inch diameter, for the choke; a hundred turns either way won't make enough difference to worry over, at these frequencies.

Operating a Power Amplifier

A power amplifier simply amplifies the signal from the master oscillator, which should, of course, be of constant frequency. Fig. 2A shows the simplest tube amplifier; it is not exactly what we want but stirs the imagination. Fig. 2B is more nearly what we want, because it has a tuned circuit in the plate circuit,

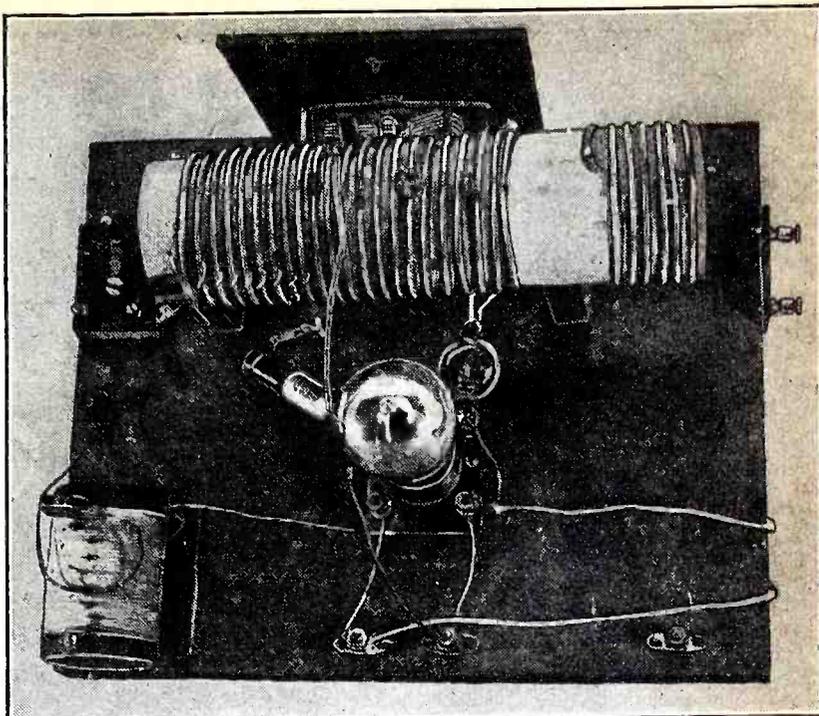Appearance of a low-power master-oscillator designed for 80 meter operation.



circuiting the power supply. When C2 is added, a choke, Ch1, must be used so that the plate can be supplied with high voltage without shorting the R.F. generated by the tube; the choke keeps the R.F. energy out of the power supply.

It will be found that a clip on the grid lead to the power amplifier, as shown in Fig. 3A, is very convenient. The filament-lead to the amplifier connects with the filament clip of the oscillator.

Let's start playing with the set and get it to work right; much in general is learned about practical procedure by trying everything, within limits and within reason, that you have time for.

We connect the amplifier to the oscillator as shown in Fig. 3A and turn on the power. Wow! The amplifier plate certainly is red! What's the trouble? We quickly turn off the power and draw a circuit diagram and investigate. We locate the trouble; the grid is at filament potential with respect to D.C., so the tube draws a heavy plate current. (Easy enough—after you try it!)

Anyway, let's bias the grid; hot plates are unnecessary. We try it again; this time, no results at all, no deflection in

things over before we have to study. But watch your step.

A Practical Amplifier Design


Now that we know something about these interesting sets, let's connect up a practical one and put some power into a transmitting antenna. Following the circuit diagram and using the sizes of parts already suggested above, we construct the 80-meter master oscillator-power amplifier, shown in Fig. 4.

The coil consists of 22 turns of No. 10 copper wire wound on a piece of cardboard tubing. Strips of celluloid (from an auto side-curtain) are first laid lengthwise, then the turns of wire are wound over these and cemented to the celluloid with collodion. Another convenient method is also suggested at the left of the coil in Fig. 4; the turns can be "sewed" in place with string. Taps should be provided at each turn for experimental purposes; pieces of thin copper are soldered to scraped positions along the wires; there are two rows of taps and the distance between successive taps is two turns, to allow space for the clips.

The baseboard arrangement suggested by Fig. 4 is very convenient and efficient; all parts can be readily reached and all leads are short and direct. Two vertical uprights support the oscillator inductor.

A tapped choke was used in this oscillator, so that the best value of turns may be selected at any wavelength employed; this looks good but it isn't absolutely necessary. A good mica fixed condenser must be used for plate blocking. The heavy leads at the right are for filament supply.

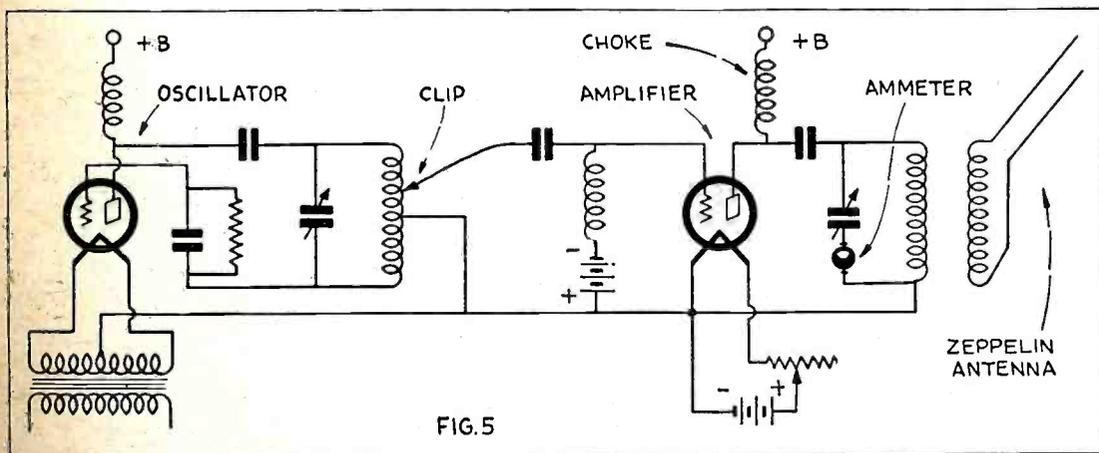Of course, if one has already a perfectly good oscillator, built to modern specifications (about the only difference between old and modern sets is the L/C ratio in the tuned circuit, the size of the blocking condensers and the design of the R.F. choke coil), it will not be necessary to build up a new set; use the one you have, though it may need adjustment, and add a power amplifier to it.




Our first master-oscillator, power amplifier that put power into an antenna.

gives fair amplification and can be coupled readily to a Zeppelin antenna without any special arrangements at all. Like all theoretical arrangements, Fig. 2B has to be modified when we put it into our amateur station. Let's do this.

It will be necessary to add the condenser C2 (Fig. 3A) to prevent short-

the plate circuit R.F. ammeter. The choke, Ch2 (Fig. 3B), was forgotten. We also find that the combination is more stable when we use fewer turns between "X" and "Y" on the oscillator inductance.

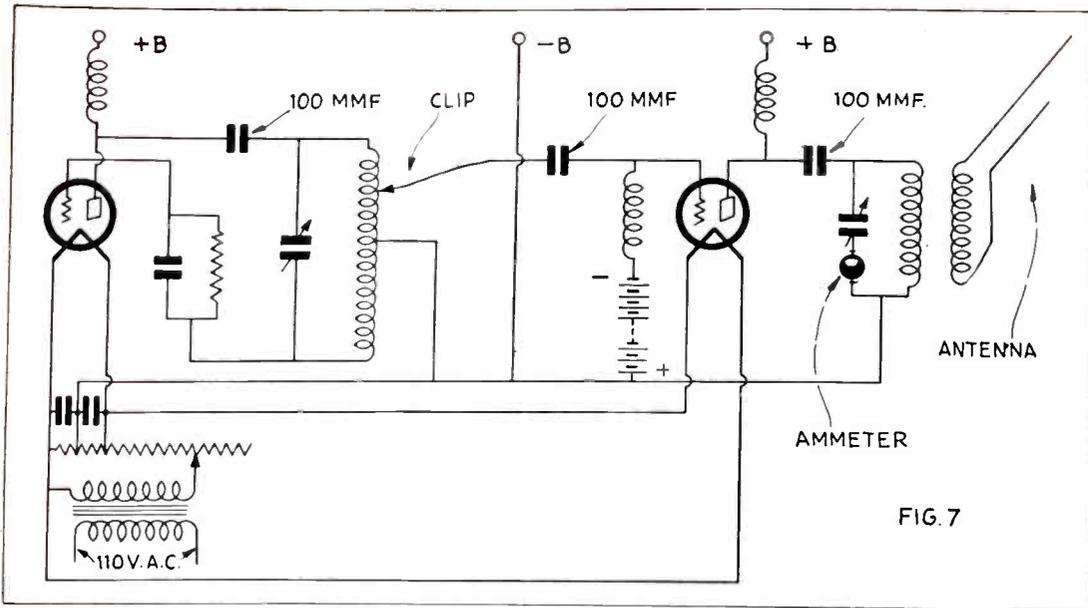Don't for a minute think that we are dumb; we are just in a hurry to get



Complete master-oscillator power-amplifier transmitting circuit.

Fig. 5 shows how a power amplifier can be added to a simple Hartley oscillator for preliminary adjustments and experiment. A storage battery is used to supply the filament of the amplifier. This is the one we used first to feed a Zeppelin antenna.

A Very Good Layout

A suggested power amplifier arrangement is shown in Fig. 6. This experimental set gave remarkably constant signals, compared to those from the usual self-excited oscillators, when a good master-oscillator was used. An ordinary 13-plate condenser and a space-wound coil can be used if low power is employed.

The R.F. ammeter reads the current in the plate tuned-circuit of the power amplifier. The plate choke used is a spider-web coil, although a single-layer winding gave results as good. The "C" battery (45 volts gave good results with 350 volts D.C. on the plate of both tubes) and grid choke are not shown in this picture. The grid condenser is necessary to prevent short-circuiting the "C" battery. The clip connects with a tap on the oscillator inductance. A good mica condenser should be used for plate blocking.

Fig. 7 shows complete connections for the low-power master-oscillator and power amplifier. Both tubes use the same filament transformer. A center-tapped 300-ohm resistor is shunted across the filament to provide a center-tap independent of rheostat setting.

Adjustment is simple. The same voltage can be applied to both plates for simplicity. With the grid clip in place, a few turns from the center tap connection, tune the amplifier plate circuit until the R.F. current in the plate tuned-circuit is at maximum. If the oscillator becomes overloaded and stops, use fewer turns between filament tap and grid clip and less grid excitation.


The antenna is coupled to the plate coil of the amplifier in the usual way. Meters can be used in the oscillator if desired. The plate meter will show an increase when either the amplifier plate circuit or the antenna consumes power,

but even a small neon lamp can be used to adjust a set like this. The antenna circuit is now removed from the oscillator and cannot affect its frequency.

Applying Crystal Control

Crystal control is the last word when it comes to constant-frequency transmission. A crystal oscillator is quite simple in principle. If you know anything about radio at all, you know why a tube oscillates. The plate circuit supplies sufficient energy not only to excite the grid, but to keep things going in general.

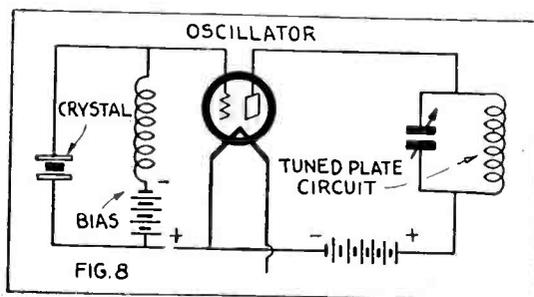A tuned plate-tuned grid circuit is a good example of an oscillator for the



Simple quartz crystal-oscillator circuit.

purposes of illustration. An ordinary crystal oscillator is simply a tuned plate-tuned grid oscillator in which the grid circuit is "tuned" mechanically instead of electrically. The crystal has its own natural, mechanical vibrating period just as, in an ordinary tuned plate-tuned grid

circuit, the grid tuned circuit has its own natural electrical vibrating period. The advantage of a quartz crystal is that the frequency furnished is extremely steady. By the mechanical vibration of the crystal, alternating electrical charges which operate the grid are produced.

Thus one can replace the grid tuned circuit by a crystal and still have an oscillator with a very constant frequency. A simple crystal oscillator is shown in Fig. 8.

Let's add a power amplifier to the crystal oscillator of Fig. 8. A crystal cannot be used directly in a high-power oscillator; one always requires amplifiers to give higher-power signals. High voltages will cause a crystal to vibrate with excessive amplitude, soon destroying it. With care it is possible to use 350 volts on a crystal-oscillator tube, although 250 volts is usually a safe maximum. If a lower voltage is used than 350 (assumed here as the voltage applied to the amplifier tube) a series resistor in the plate lead will reduce the voltage to the crystal tube.


Fig. 9 shows a crystal oscillator with power amplifier. The adjustment is simple; it is otherwise the same as for the master oscillator-power amplifier arrangement previously discussed for operation at the fundamental of the crystal. It is usual, however, to tune the amplifier plate to the second harmonic of the crystal for several obvious reasons.

For example, a 160-meter crystal will furnish a 160-meter wave to the grid of the crystal-controlled oscillator; the plate circuit is tuned to the same frequency. The power amplifier plate circuit is tuned to 80 meters, and so is the aerial for 80-meter operation. For operation at 40 meters with an 80-meter crystal, the procedure is similar; another stage of amplification will be required to operate at 40 meters with a 160-meter crystal. It is usually best to purchase a crystal having a fundamental as near to the desired operating frequency as possible, which saves apparatus and expense.

WANTED!

Articles on Short Wave Transmitter and Receiver Ideas.

Have you some?

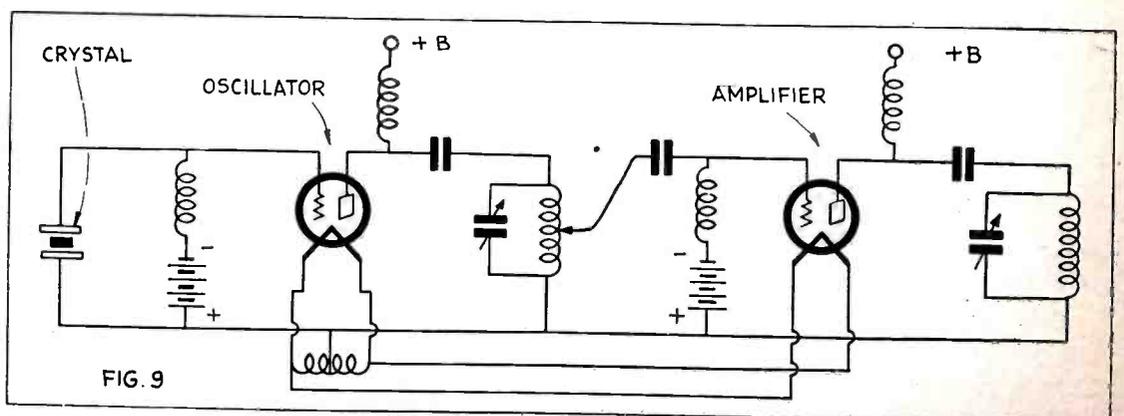

Quartz crystal oscillator with power-amplifier.

Ultra Short Waves

Can We Use Ultra Short and Infra-Red Rays for Communication?

SHORT wave communication has already won for itself a considerable share of the communication field. In the main, the band from 20 to 100 meters is in question; still shorter waves have been known for years and have occasionally been tested experimentally, but thus far they have not been given serious use for communication purposes.

It now seems as though the band from .7 of a meter to 8 meters might also be especially suitable for communication. For these very short waves other physical laws are in part valid than for longer "short waves". While the longer waves are reflected by the Heaviside layer, which is a partial explanation for their extraordinarily high efficiency for long-distance transmission, this is manifestly not the case with waves less than 8 meters in length. Since these are radiated from the antenna in straight lines, they can (unless there is a very good conduction for the ground wave) only extend to distances lying within the horizon of the transmitter.

It is especially noteworthy that these very short waves, for which Dr. Schröter proposes the designation "quasi-optical waves", lie in the spectrum in which Heinrich Hertz made his classic discoveries. These very short waves are very strongly absorbed by the atmosphere.

It seems as though the band from 8 meters down to about 10 centimeters, and the infra-red short wave band, between about 2.4 microns and .7 of a micron are in particular the ones which can be given practical use. The former band is produced by electron tubes and spark gaps (macroscopic dipoles), the infra-red band by radi-

By DR. FRITZ SCHRÖTER

(Based on a lecture by Dr. Fritz Schroter at the meeting of the Electro-technical Society and the Heinrich Hertz Society.)

The transmitters and receivers for ultra short waves as well as infra-red rays are discussed and some of the possible applications of these systems to everyday problems.

ators of heat (molecular dipoles). Between these two bands lie the waves which are produced by the so-called mass-radiators of Frau Glagdeva-Arkadieva, in the form of tiny sparks made between fine metal filings. Hereby are attained over-oscillations which already extend into the field of heat-ray producers, for example the highly charged mercury vapor lamp.

IN THE NEXT ISSUE:
New Work in Germany
on
Ultra-Short Waves
by
Dr. Fritz Noack

The wave band from about 8 meters down to 1 meter has been especially investigated by Dr. Schröter, Dr. Michelssen, and W. Ludenia, of the Telefunken concern, in order to get practical applications for radio "lights" (radio beacons, rotary direction indicators), which particularly in the case of fog, are intended to replace optical signals. Since the wave lengths are in this case relatively small, the rays can be gathered into pencils by groups of dipoles or by reflectors and therefore concentrated. Consequently the watt-power of the transmitter can be small, still being used in the

sharply directed radiation needed in navigation. Even a locally limited radio operation (*i.e.* by several stations), in which pencils of rays of the same wave length can operate close at hand without interference, is directly possible, at least if the horizons of the individual transmitters do not cut each other.

Likewise at the receiving end the apparatus needed is not very complicated. For telegraphy the very sensitive super-regeneration can be used, which for radio telephony has to be replaced by other proper systems on account of its extreme noisiness.

For the production of waves less than a meter in length, there comes into question either the Barkhausen-Kurz Bremsfeld hook-up or the Hull magnetron-tube hook-up. Moreover, spark-gaps can be used, which can be built extremely simple, but which send out only damped waves; to make up for that, they have a very intensive radiation effect. The resulting arrangement is similar to the classic, basic arrangement of Hertz. Dipole and spark-gap are set in the focal axis of a parabolic mirror of small dimensions. It is with such a hook-up that Dr. Schröter was able to give a demonstration in his lecture, transmitting audible telegraphy and radio.

In the similarly arranged receiving mirror there is used either a crystal detector or a vacuum tube operating in the Barkhausen-Kurz hook-up.

In telephonic transmission the spark-gap is fed by a modulated tube generator, the sending power being about .1 of a watt. Analogous with the Hertz experiments, with this hook-up one can nicely

(Continued on page 328)

THE SCREEN GRID FIVE SHORT WAVE RECEIVER

By EDWARD G. INGRAM

WHILE marked progress has been made recently in short wave receiver design, those who have had experience with the performance of receivers meant primarily for the reception of distant phone stations will admit there still is room for further improvement. It is not an easy matter to obtain sufficient volume and sensitivity for consistent loud-speaker reception of distant stations in Europe and other foreign countries without too much complication and expense.

This short-wave receiver described in detail by Mr. Ingram is designed to operate on A.C. and employs the '24 screen grid tube for R.F. detector and first A.F. stages; fringe howl is eliminated by resistance coupling.


In the audio-frequency end of the receiver, also, difficulty was experienced because of the effect of the first stage on

loss in amplification due to the low gain of the resistance stage.

Advantages of '24 Tube

Recently attention has been focused on the A. C. tube for short wave work, and improved results have been obtained; but, in the writer's opinion, the full possibilities of the type '24 screen-grid tube have not been taken advantage of, and this is the chief reason for the present article.

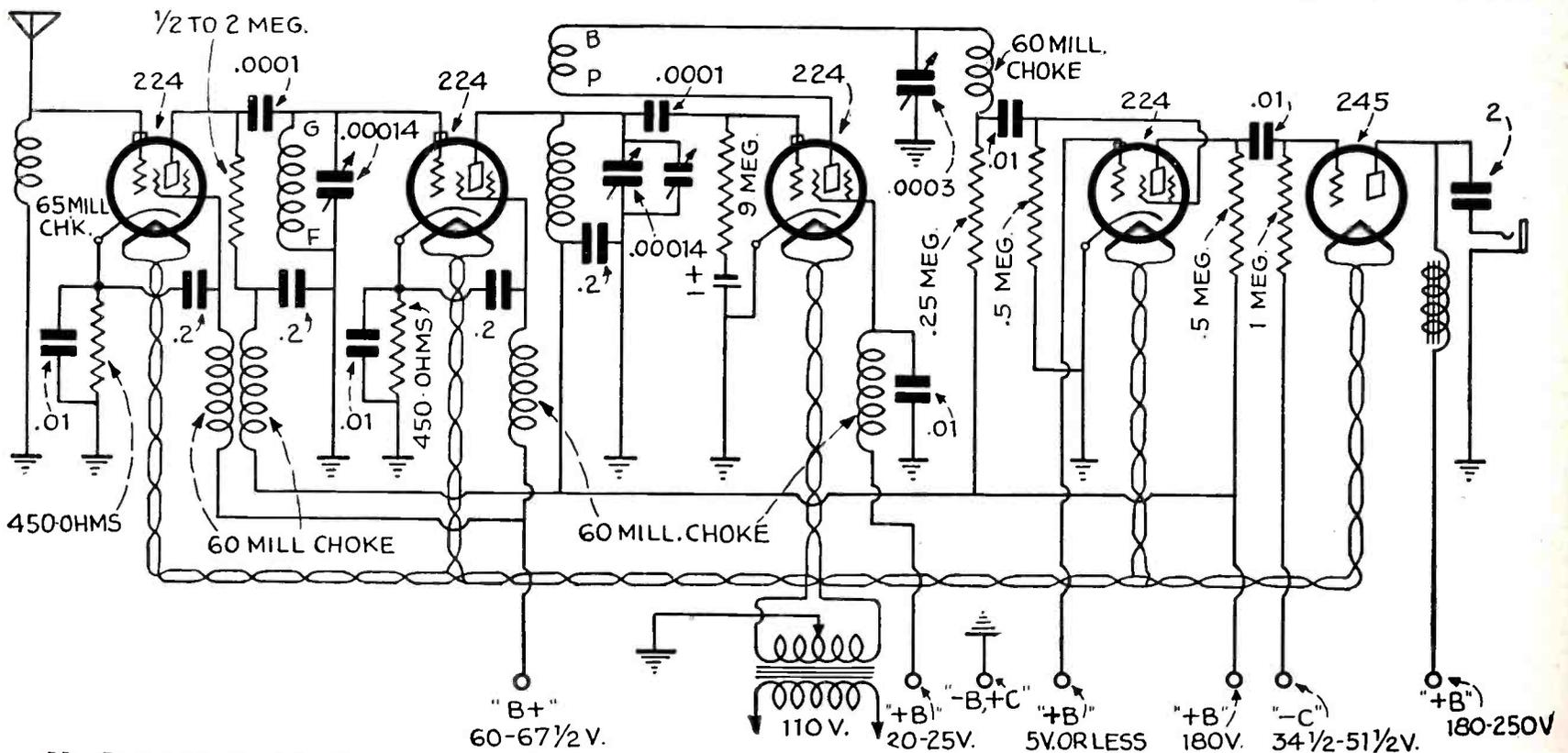The '24 screen-grid tube, used as a radio-frequency amplifier, has an ampli-



Mr. Ingram's novel hook-up, showing '24 type screen grid tubes in R.F., detector and first A.F. stage, last being connected as a space charge amplifier. Second audio stage uses '45 tube with choke and condenser output filter.

While foreign stations often are received with good loud-speaker volume on very simple sets (such as those with an untuned R. F. stage, a regenerative detector and two stages of A. F. amplification), frequently reception conditions are such that the need of more amplification keenly is felt.

Until recently all of the developmental work on short wave receivers has been done with D. C. tubes. The advent of the '22 type D. C. screen-grid tube with its low grid-plate capacity made stable, R. F. amplification at high frequencies a possibility and brought about a marked gain in sensitivity. But the gain with one tuned stage of radio frequency was still not enough, and the addition of more stages required too many controls; for ganging of the tuning condensers was not found very practicable.

what is known as "threshold oscillation" in the detector tube. Threshold oscillation, or "fringe howl," is the rasping howl which sets in just as the detector goes into oscillation when advancing the regeneration control. This usually occurs when the detector is worked into a transformer stage of audio frequency amplification. It can be prevented frequently by the use of a certain amount of resistance across the secondary of the transformer; but if this has to be less than 500,000 ohms, as usually is the case, sensitivity is impaired. The best solution is to make the detector work into a resistance-coupled stage of amplification, which is now done extensively. With the detector plate potential supplied through a high resistance, the oscillation difficulty is overcome; but unfortunately there is a

fication constant of 420 as against 300 for its D. C. companion; this means greatly increased sensitivity. The A. C. type '27 tube shows some superiority over D. C. tubes (like the '01A) for the detector and audio stages; so that sets recently placed on the market, with '24s in the tuned R. F. stages and '27s in the detector and audio stages, show a very marked improvement in performance over like sets with D. C. tubes.

But human nature is not easily satisfied and we still seek for further improvement. The resistance-coupled stage, even with a '27 tube, is still a weak point in the A. F. end of the receiver; and if this could be improved upon, and a further gain also obtained in the radio frequency-detector without additional controls, we would be approaching a type of receiver with a

(Continued on page 330)

Possibilities in Amateur

Television on Short Waves


By C. H. W. NASON

The Transmitter—how to use small photo cells and details of the amplifier to pass a wide band of frequencies.

I BELIEVE that there will be none to contradict me when I say that none of the major radio developments have come out of the research laboratories of the larger corporations. Television offers an unparalleled opportunity to the amateur investigator, not only as regards satisfaction from results obtained, but also from pecuniary return.

Regardless of the present state of the art, television will sooner or later become an integral part of the nation's entertainment. When that time arrives, the field will undoubtedly be controlled, as broadcasting is now, by some few large interests who will be willing to purchase any patents belonging to independent investigators and the lack of which might lay them open to suit in the prosecution of their plans. Regardless of all that has been said of the helplessness of the little fellow, it has been proven, time and again, that the larger organizations would much rather pay a fair price for a valuable idea than to risk the loss of a suit or the loss of the public's good will through the adverse publicity which might result.

There are two reasons why the amateur should be interested in the problems of television transmission. The obvious one is that ideas, which might be developed in the field of transmission, might need experimental research with equipment readily available; the other is that, in developing an idea regarding reception of the television signal, it is not always possible or convenient to utilize the signals available. By this I do not mean

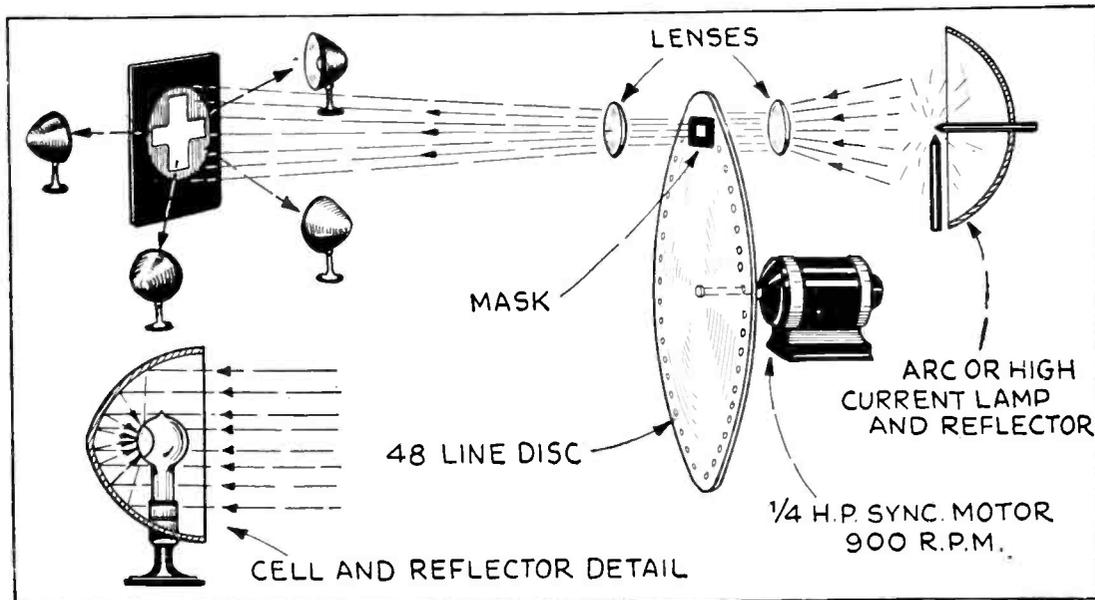

The author shows us how to utilize four small photo-cells instead of large ones at the Television transmitter. Fig. 1.

that an actual carrier must be propagated; for the same results may be attained by modulating a low-powered oscillator not capable of reaching beyond the walls of the laboratory, or by wire-line transmissions within the walls of the laboratory.

Contrary to the general view, the best medium for the amateur is not the transmission of film but the actual pick-up of persons or objects. The equipment necessary for the construction of an "indirect pick-up" or beam-scanning system is far simpler mechanically than that required for the transmission of film, where an arrangement to provide a constant speed of advance for the film is required. For amateur work, other than in the most pretentious installations, the employment of "direct pick-up," where the subject is brilliantly lighted and we scan an image projected on the disc by a high-quality photographic lens, is entirely out of the question, because of the highly developed lighting system required.

Amount of Amplification Required

It is not necessary to employ large and expensive photoelectric cells in such an installation; as exceedingly fine work can be done with smaller cells placed at the focal point of fairly large parabolic reflectors. An elementary arrangement for such a system is shown in Fig. 1. The voltage output from the cells, under normal conditions of lighting, will be in the neighborhood of 5 microvolts. This means that, in order to modulate a low-powered transmitter, or operate a neon tube for monitoring purposes, we must employ amplifiers having a combined gain of about twenty million. Without recourse to any calculations, the writer hazards the estimate that this might be done with about eight stages of amplification.

Shielding for such a system (except for that mechanical shielding found necessary in avoiding microphonic disturbance) would not be difficult; and the normal method of accomplishment would be through the use of a photo-cell amplifier of two stages, an intermediate or low-level amplifier of three stages, and a main amplifier employing another three stages. These would, preferably, be separately shielded and provided with their own power sources. No great difficulty would be experienced in operating the final amplifier from A.C.

In order to avoid picking up extraneous disturbances, it is advisable to employ a low-impedance tube in the output of each of these amplifiers; so that the leads interconnecting them will constitute a low impedance circuit and be less apt to pick up strays. The amplifier circuit

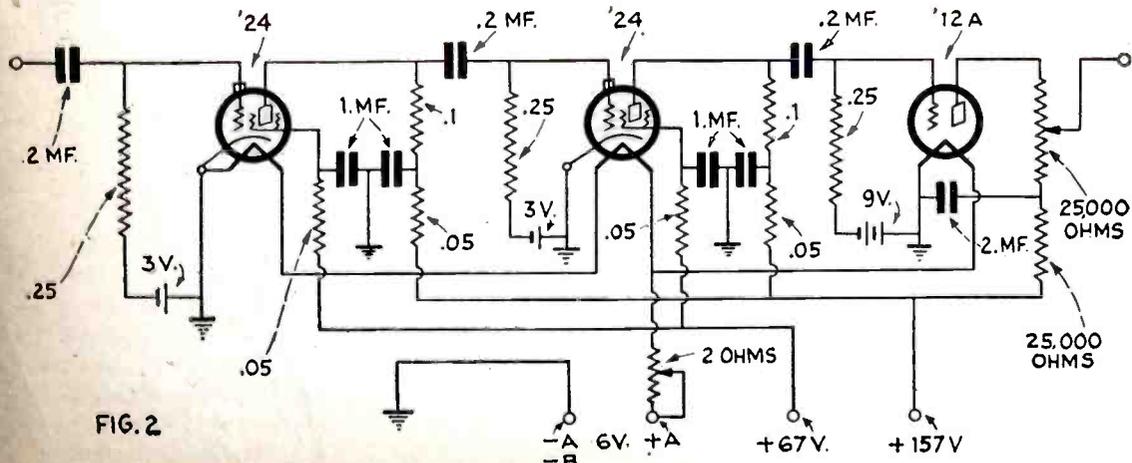


FIG. 2

Fig. 2.—Resistance coupled amplifier suitable for use with Television transmitter.

(Continued on page 319)

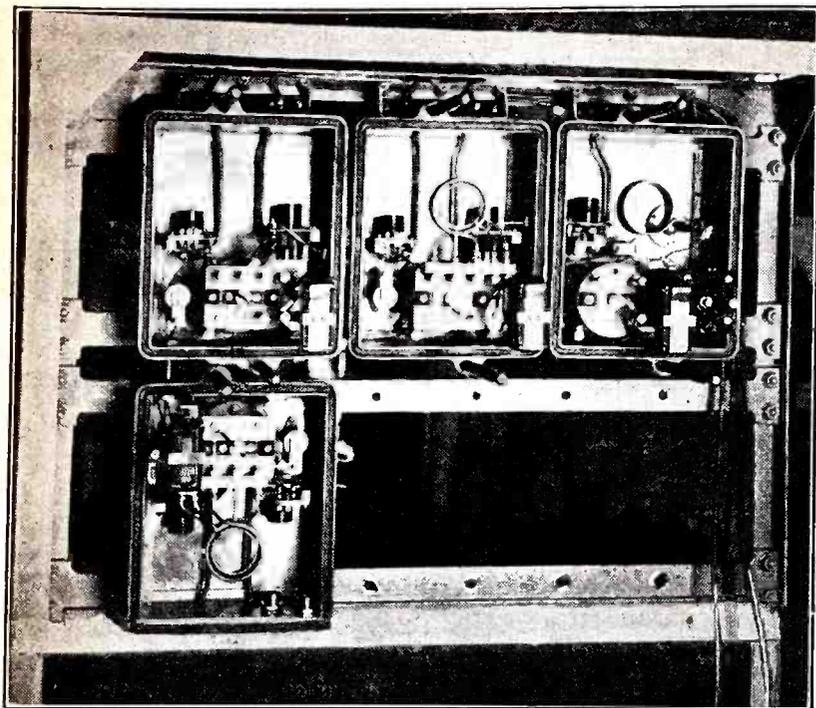


Fig. 2—Rear view of the four short-wave, radio frequency stages in their separate stage shields.

A 19 TUBE SHORT WAVE RECEIVER

Used for
TRANS-ATLANTIC
RECEPTION

By DR. FRITZ NOACK
(Berlin)

Interesting details of German Commercial S-W Receiver, used for phone, code and picture reception. It has trans-Atlantic range and many novel points of value to all S-W students.

four stages B-I-II-III-IV, which are tuned to 300 kilocycles; these stages are separately shielded by copper boxes; and the coupling filters pass a band of 6,000 cycles, so that the audio frequencies ac-

(Continued on page 317)

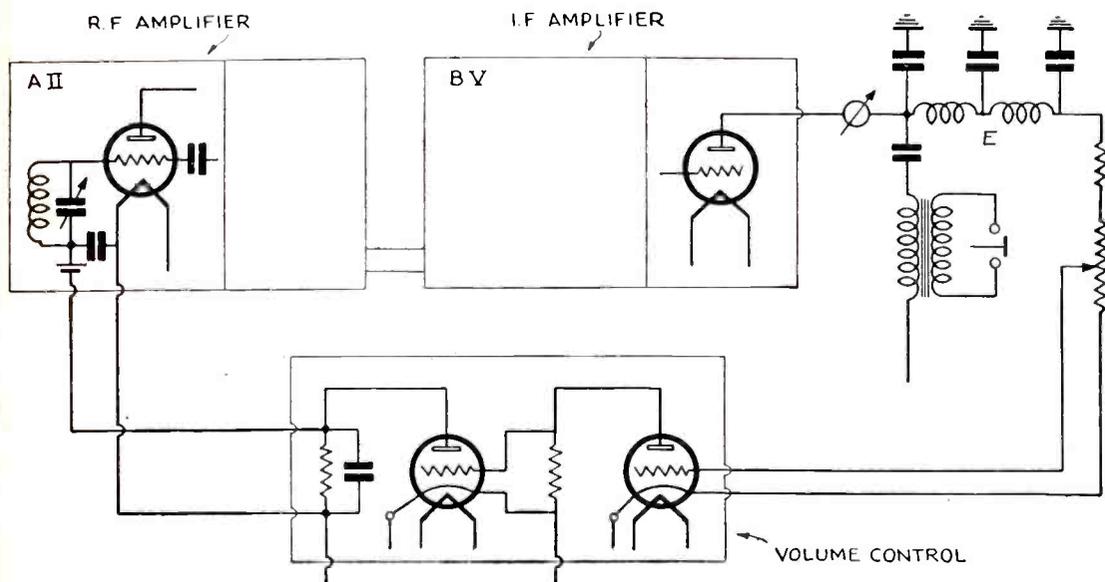


Fig. 5—Circuit of automatic volume control as used in 19 tube S-W receiver.

IN a preceding issue of SHORT WAVE CRAFT the writer gave a brief account of the new receiver which has been developed by the Telefunken Co., for overseas radio traffic. This set, a super-heterodyne with four stages of short-wave R. F. amplification ahead of the first detector, and four stages in the intermediate-frequency amplifier, is intended to amplify the lowest perceptible signals to full volume; while an automatic volume control compensates for unduly loud signals and gives an even output. In addition to this, a special device brings out code signals strongly while interference is suppressed.

This very interesting receiver is illustrated here, and its schematic circuit is shown for the interest it will arouse in all short-wave enthusiasts—whether they will attempt so ambitious a feat of construction or not. Fig. 1 is a front view of the complete receiver, and Fig. 2 shows the radio-frequency amplifier in its separate stage shields.

The schematic circuit is shown in Fig. 3, and the keying arrangement used for

telegraphy in Fig. 4; while the connections of the automatic volume regulator control used for phone work are given in Fig. 5.

Frequency-Changing System

The first R. F. stage, A-I takes the signal from the antenna; whence it passes through the succeeding three R. F. stages, A-II-III-IV, to the first detector A-V, and is then modulated with the local frequency generated by the oscillator unit A-VI. Each of the latter stages, like the R. F. stages illustrated, is cased in a separate large bronze shield can.

The unit A-VI comprises two tubes, connected in parallel and operated from a small oscillator, whose radio-frequency energy is amplified by them; while a neutralizing connection prevents feedback into the oscillator, which might affect the constancy of its frequency. The coupling from the unit to the first detector is variable, for better adjustment of the over-all amplification of the receiver.

The intermediate-frequency output of the first detector is then amplified by the

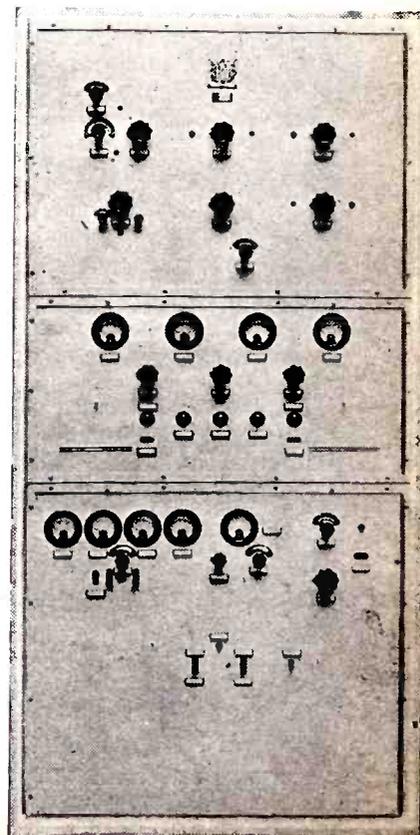


Fig. 1—Front view of 19 tube trans-Atlantic S-W receiver.

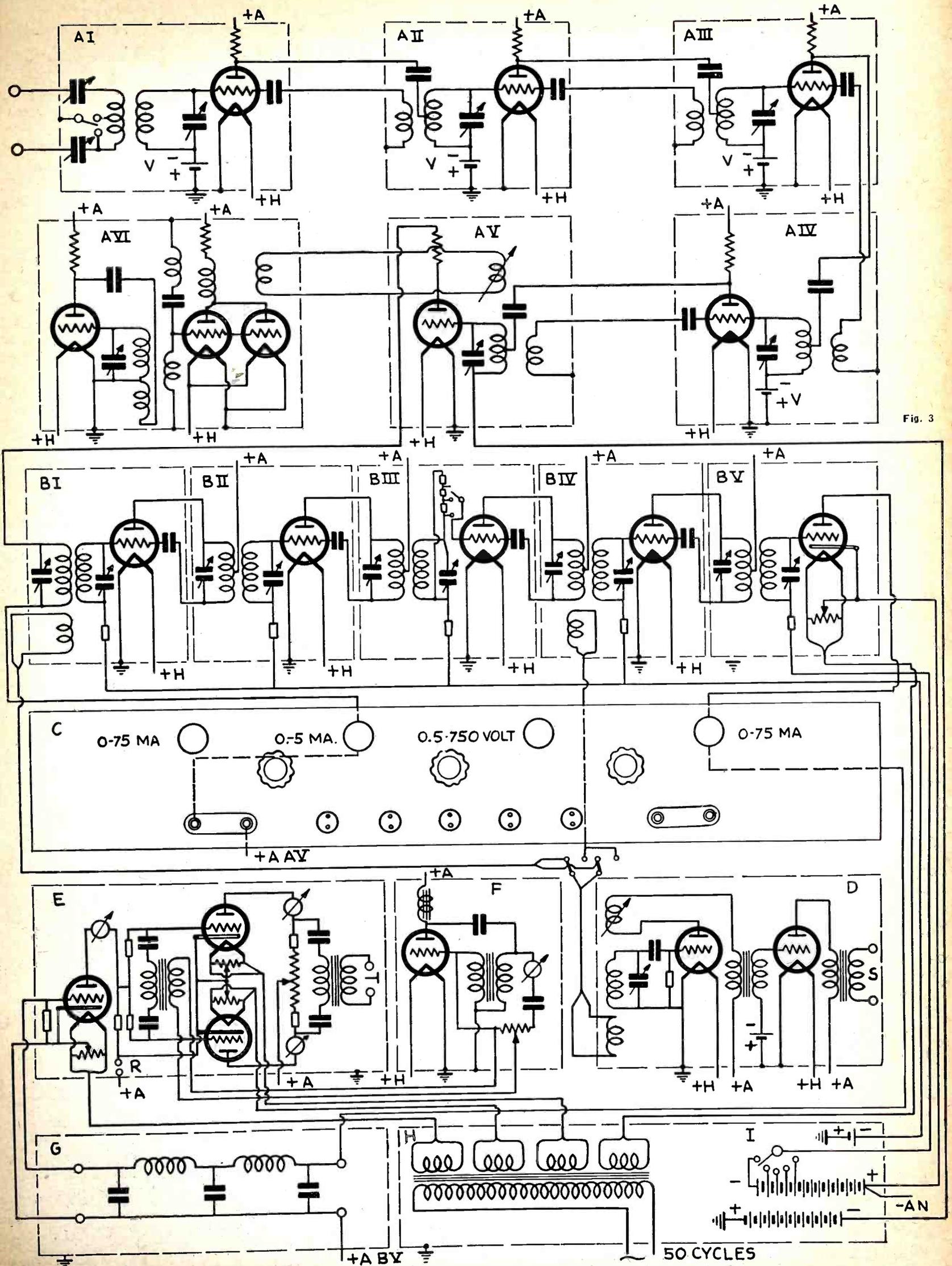


Fig. 3

Short-wave radio frequency amplifier, 4 stages A I, II, III, and IV. First detector at A V; oscillator at A VI; four intermediate amplifier stages B I, II, III, and IV with second detector at B V; control panel at C; listening circuit at D; E—photo recorder and amplifier; F—tone generator; G—band pass filter; H—transformer supplying heater current; I—C—bias battery; —AN is B—.

A Sensitive and Selective Short Wave Receiver

By R. WILLIAM TANNER (W8AD)

Mr. Tanner, well-known designer and builder of short-wave transmitting and receiving sets, here presents us with one of his newest ideas—a short-wave receiver provided with switches for changing to the various wavelength bands instead of having to bother with plug-in coils. This set has a stage of shield grid R. F. amplification ahead of the detector to improve the sensitivity. The wavelength range of this set is 15 to 550 meters. The set is designed for A.C. operation.

ONE of the most sensitive and selective short wave receivers ever built by the writer consisted of only four tubes with a screen grid tube as a regenerative space charge detector. In place of the usual set of four to five plug-in coils, an arrangement of stationary inductances was employed, shifting to the various bands being accomplished by means of multi-point switches. In order to be of the greatest possible service, a two section variable condenser was used for tuning, regular 200 to 550 meter broadcasting being received on the largest inductance by connecting both sections in parallel.

The experimenter who desires a receiver capable of tuning from 15

to 550 meters and giving good quality, sensitivity and selectivity with incomparable ease of adjustment will do well to consider this outfit. For the benefit of such experimenters a detailed description will be given.

First let it be stated that shielding will not improve the operation in the least except, possibly, to decrease the pickup of the coils, wiring, etc. Stage shielding is needed ONLY when the R.F. amplifier is tuned.

In the diagram in Fig. 1 is depicted the complete schematic circuit. It will be noticed that this is an A.C. hookup. If good standard makes of tubes are employed, the amount of hum present in the phones or loud speaker will be neg-

ligible. The first tube is a type 224 in an untuned stage with a variable grid bias resistor for controlling volume, a necessity in the broadcast band. The second tube is the space charge detector. A high degree of selectivity is obtained by connecting the R.F. plate to taps on the main coils. A close examination of the coil arrangement will reveal the fact that only one coil is in circuit at a time, thereby overcoming the old horror of dead-end losses.

General Features

The detector employs plate detection to improve the tone quality of broadcasting, and also to increase selectivity by raising the input impedance of the tube. The

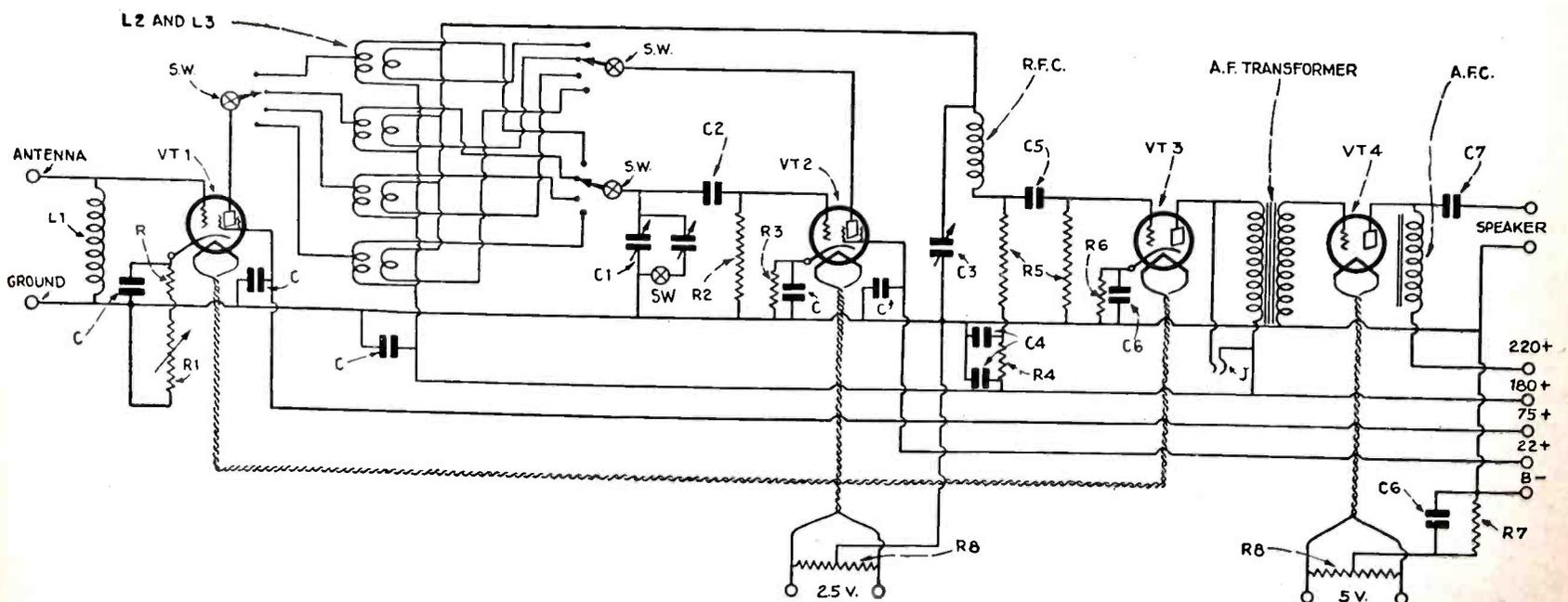


Fig. 1, above, shows complete wiring diagram of Mr. Tanner's sensitive and selective short-wave receiver comprising one stage of untuned radio-frequency amplification, regenerative detector and two stages of audio amplification.



negative bias is not great enough to appreciably effect the sensitivity. Regeneration is obtained by the "throttle" or bypass condenser method and, when the screen grid voltage is of the correct value, is very smooth, in fact, it is almost impossible to notice the oscillation point due to the absence of regenerative hiss, so prominent in other detectors. The space charge connection is superior to the screen grid connection from tone quality standpoint although slightly less sensitive. Regeneration can be obtained down to approximately 15 meters. Below that the tube becomes rather unstable due to the high plate to screen grid capacity.

The detector output is resistance-coupled to a type 227 first A. F. stage. The A. F. transformer coupling this tube to the 171A power stage has a telephone jack across the primary to provide headphone operation, always desirable in short wave receivers. A "motor-boating" preventer is used in the B positive lead to the detector and is quite an important item although not absolutely necessary in all sets. This consists of a resistor R⁴ and two bypass condensers C⁴.

All of the parts are mounted on a 7" by 18" metal panel and a 17" by 8" wooden baseboard 1/2" thick. A cabinet was not used on the original model but one is desirable to keep out dust. A pair of 1" bakelite sub-panel brackets are employed to allow space underneath for the bypass condensers, resistors, etc., for the sake of compactness and ease of wiring.

The antenna R. F. choke L1 is easily wound by the constructor. It consists of 350 turns of No. 36 enamel wire scramble wound on a common thread spool 3/4" or 1" in diameter. The 500 ohm resistor R limits the bias to a low value of approximately 2 volts. The variable 50,000 ohm resistor R1 controls volume by increasing the bias. All of the bypass condensers C have a capacity of .1 mfd. It will be noted that no R. F. choke is shown in the R. F. screen grid or B positive leads. It has been worked out in practice that such chokes in a single R. F. stage, whether tuned or untuned, are unnecessary. The

Fig. 2 shows how windings for radio-frequency transformer are placed on the supporting tubes, together with brass brackets for mounting the coils.

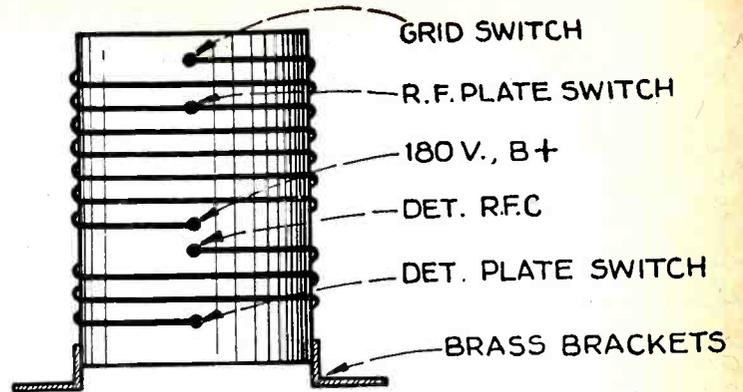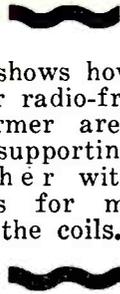

only effect of their absence would be feedback in the detector and increasing regeneration. If these items are not needed, then why use them?

The Short-Wave Coils

The four coils are, perhaps, the most difficult parts of the whole receiver to construct. Three 4 point switches and four 1 1/2" bakelite tubes are needed together with a small quantity of wire, a few brass machine bolts, soldering lugs, eight small brass angles and two 1/8" bakelite plates 5" square. In the interest of economy the four coil forms are of different lengths. These are given in the coil table accompanying this article. A 6 1/4" length may be purchased and cut to the required sizes by the individual.

The grid coils are wound first, slightly spacing the turns of the 20 and 40 meter coils. The ticklers are started 1/8" from the grid windings and close wound with No. 30 enamel wire. Detuning effects of the regeneration control will then be considerably less than if large

wire was used. The coils are assembled on the base with the grid ends up so that the grid leads to the switches will be short and direct. The layout for the three band switches is shown in Fig. 3B. Exact dimensions cannot be given as so many types and sizes are available. The levers should have a radius of not more than 1 1/4". Both plates have holes drilled in the corners for four 3/8" brass pillars, which are drilled and threaded for 8/32 bolts. This unit is assembled, after the wiring is finished, by placing a pillar at each of the four corners.

Tuning Condenser

Now for the tuning condenser. The back section of a two-gang .00035 mfd condenser is cut down to the required capacity by removing some of the rotor plates. The exact number needed will depend upon the size of the plates; however three will usually be sufficient, the resulting capacity then being in the vicinity of .000125 to .00016 mfd. To connect the two sections in parallel for broadcast reception,

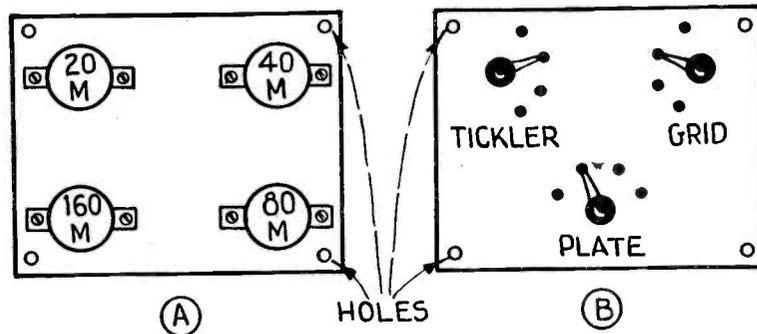


Fig. 3 shows how tapped coils are mounted and the wavelength change switches arranged.

wire was used. The windings should not come within 3/8" from the edges of the forms in order to allow sufficient space for the connecting screws and angle brackets. The leads are soldered to lugs held to the forms with machine bolts. Details are shown in Fig. 2.

The layout of the four coils is

merely cut a slot and drill a hole in a brass strip 3/8" wide to fit over the terminal posts of each section.

The detector bias resistor R3 has a value of 10,000 ohms and may well be semi-variable to provide smooth oscillations. A 25 watt Truvolt resistor fitted with a slider is ideal for this purpose. The

higher the resistance the greater will be the number of turns required for each tickler.

Now for just a word in regard to the choice of the .0005 mfd regeneration condenser C3; oscillations are more easily controlled if this is of the straight line capacity type rather than of the modern straight line frequency type due to the slower capacity increase at the high end of the scale. Then tuning in on short wave broadcasts or other telephone stations, zero beat tuning is sometimes beneficial towards both sensitivity and selectivity. For this work the advantages of a vernier dial on the regeneration condenser is readily apparent.

or speaker filter consists of a 30 Henry B-eliminator choke and a 2 mfd, 600 volt condenser. A negative bias of 13 volts is applied to the grid of the 227 by taking the voltage drop across R6, of 2000 ohms resistance, in the cathode load. This is bypassed with a 1 mfd condenser. The 171A obtains a bias of approximately 40 volts from a 2100 ohm resistor, also bypassed by a 1 mfd condenser, connected from the center tap of the 5 volt filament resistor to B negative.

A suggested arrangement of parts is shown in Fig. 4. All of the bypass condensers, resistors (except the resistance coupler) and detector R. F. choke are located

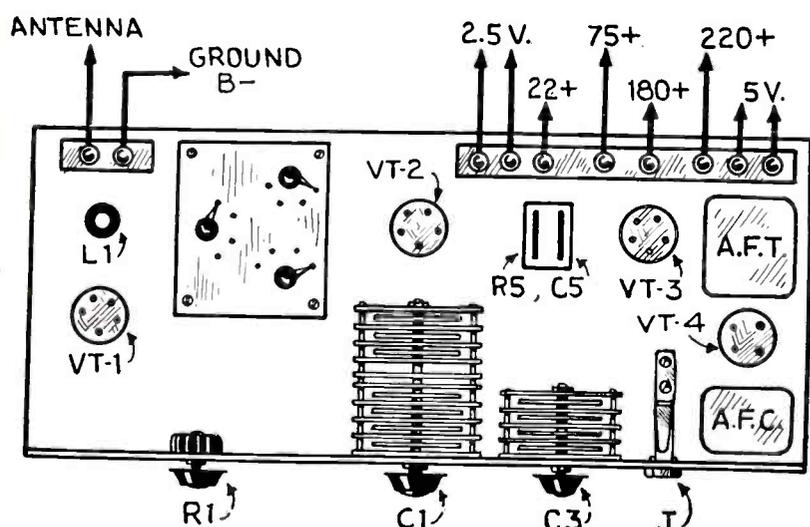


Fig. 4 shows the author's arrangement of the various instruments comprising the sensitive and selective short-wave receiver described in the accompanying article. The wavelength change switch box and its coils are shown at the rear left of sub-panel.

The R. F. choke RFC, used to keep the R. F. currents out of the audio amplifier, should have an inductance of approximately 85 MH. The resistor R4 and condenser C4 comprise the audio filter and is very effective in preventing motor-boating, a condition which causes much trouble when employing a screen grid tube as a detector in a short wave receiver. A resistor of 25,000 ohms with 2 mfd bypass condensers are about the right values.

Audio Amplifier Details

The two stage audio amplifier is of the conventional type, the first stage using a 227 tube resistance coupled to the detector. The last stage is transformer coupled and employs a 171A for loud speaker operation. An open circuit telephone jack is connected across the primary to allow the use of headphones when desired. The output

under the baseboard. It is a good plan to run all R. F. current carrying wires first, making them as short and as direct as possible. Then run the filament, B and C wires wherever they will fit in without coming too close to R. F. wires. In the model it was found unnecessary to use twisted pair for the filaments, however, it seems to be good practice to do so.

After the parts are all mounted and the wiring completed, the tubes may be inserted in their respective sockets and the external connections made. As all brands of tubes do not have exactly the same characteristics, it will probably be necessary to modify the tickler coils somewhat but first turn on the filaments and test the plate voltages at the terminal posts. The values should be very close to those specified in the diagram in Fig. 1.

Checking Up Regeneration

To determine if the ticklers have the correct number of turns, first throw the switches to the 20 meter coil and set the tuning condenser C1 at maximum capacity with only the small section in circuit and slowly increase the capacity of the regeneration condenser. If oscillations start below 50 degrees on the dial, the tickler is too large and one turn must be removed or else audio howling will be the result when C3 is increased. One turn will be enough to take off from this coil.

The same procedure is followed with the other coils. If the tube refuses to oscillate with any of the four coils when C3 is at maximum, the tickler leads may be reversed. If such is not the case more turns will have to be added. It will take a pretty poor detector tube to refuse to oscillate at some point on the regeneration condenser with the tickler turns as specified, providing the connections are correct. In order to provide sufficient regeneration with the largest of the coils in conjunction with both sections of C1 for broadcast reception, oscillations may start below 50 degrees on the regeneration dial when only the small section is used, however, audio howling should not be troublesome at these waves.

If it is at all possible to vary the detector screen grid voltage, regeneration can be made very smooth. This is not extremely critical but requires a little care in getting the right value.

Alternating current hum should be at a very small minimum even when using headphones on the low waves. A fixed condenser of from .006 to .01 may be found necessary connected across one-half of the 2.5 volt filament resistor. The hum should not increase at the point of oscillation if good tubes are employed.

Tuning is accomplished in the usual manner, however, with the space charge detector, the resulting sensitivity is rather high, and selectivity may be improved by setting the volume control at a high value. Then tune in the station with the detector oscillating. Reduce the regeneration control to

(Continued on page 329)

Short-Wave Stations—When to Listen

Kilo-Meters	Cycles	Station Name	Location	Time
4.97-5.35	60,000-56,000	Amateur Telephony and Television.		
5.83	51,400	W2XBC	New Brunswick, N. J.	
7.32	41,000	W8X1	East Pittsburgh, Penna.	
8.57	35,000	W2XCU	Ampere, N. J.	
1.67	34,600	W2XBC	New Brunswick, N. J.	
9.68	31,000	W8X1	Pittsburgh, Pa.	
9.96	30,105	Golfo Arancé	Sardinia. Telephone to Rome.	
10.51	29,190	PK313	Sourabaya, Java, Wed. and Sat. 5:50-7:50 a.m.	
11.55	25,960	G5SW	Chelmsford, England Experimental.	
11.67	25,700	W2XBC	New Brunswick, N. J.	
12.48	24,000	W6AQ	San Mateo, Calif.	
(Several experimental stations are authorized to operate on non-exclusive waves of a series, both above this and down to 4 meters.)				
13.04	23,000	W2XAW	Schenectady, N. Y.	
13.92	21,540	W8XK	Pittsburgh, Pa.	
13.97	21,460	W2XAL	New York.	
14.01	21,400	WLO	Lawrence, N. J., transatlantic phone.	
14.06	21,320	Div	Nauen, Germany.	
14.15	21,130	LSN	Monte Grande, Argentina.	
14.50	20,680	LSN	Monte Grande, Argentina, after 10:30 p.m. Telephony with Europe.	
		FMB	Tamatave, Madagascar.	
		PMB	Bandoeng, Java.	
		FSR	Paris-Saigon phone.	
14.62	20,500	W9XF	Chicago, Ill. (WENR).	
14.89	20,140	DGW	Nauen, Germany. Tests 10 a.m.-3 p.m.	
15.03	19,950	LSG	Monte Grande, Argentina. From 9 a.m. to 1 p.m. Telephony to Paris and Nauen (Berlin).	
		DH	Nauen, Germany.	
15.07	19,906		Monte Grande, Argentina. 8-10 a.m.	
15.10	19,850	WMI	Deal, N. J.	
		SPU	Rio de Janeiro, Brazil.	
15.12	19,830	FTD	St. Assise, France.	
15.40	19,460	FZU	Tamatave, Madagascar.	
15.45	19,400	FRO	FRE, St. Assise, France.	
15.50	19,350		Nancy, France, 4 to 5 p.m.	
		VK2ME	Sydney, Australia.	
15.55	19,300	FTM	St. Assise, France. 10 a.m. to noon.	
15.60	19,220	WNC	Deal, N. J.	
15.85	18,920	XDA	Mexico City, Mex. 12:30 to 2:30 p.m.	
15.94	18,820	PLE	Bandoeng, Java. 5:40-6:40 a.m. and from 2:40 a.m. Tues. and Fri.; 8:40-10:40 a.m. Tues. Also telephony.	
			Saigon, Indo-China.	
16.10	18,620	GBJ	Bodmin, England. Telephony with Montreal.	
16.11	18,610	GBU	Rugby, England.	
16.30	18,400	PCK	Kootwijk, Holland. Daily from 1 to 6:30 a.m.	
16.35	18,350	WND	Deal Beach, N. J. Transatlantic telephony.	
16.38	18,310	GBS	Rugby, England. Telephony with New York. General Postoffice, London.	
		FZS	Saigon, Indo-China, 1 to 3 p.m. Sundays.	
16.44	18,240	FRO	FRE, St. Assise, France.	
16.50	18,170	CGA	Drummondville, Quebec, Canada. Telephony to England. Canadian Marconi Co.	
16.54	18,130	GBW	Rugby, England.	
16.57	18,120	GBK	Rugby, England.	
16.61	18,050	KQJ	Bolinas, Calif.	
16.70	17,950	FZU	Tamatave, Madagascar.	
16.80	17,850	PLF	Bandoeng, Java ("Radio Malabar").	
		W2XAO	New Brunswick, N. J.	
16.82	17,830	PCV	Kootwijk, Holland. 3 to 9 a.m.	
16.87	17,780	W8XK	Pittsburgh, Pa.	
16.90	17,750	HSIPJ	Bangkok, Siam. 7-9:30 a.m., 1-3 p.m. Sundays.	
17.10	17,350	G2IV	S.S. "Majestic."	
		G2GN	"Olympic."	
17.34	17,300	W2XK	Schenectady, N. Y. Tues., Thurs., Sat. 12 to 5 p.m. General Electric Co.	
		W8XL	Dayton, Ohio.	
		W6XN	Oakland, Calif.	
		W6AJ	Oakland, Calif.	
		W7XA	Portland, Ore.	
		W7XC	Seattle, Wash.	
		W2XCU	Ampere, N. J.	
		W9XL	Anoka, Minn., and other experimental stations.	
17.52	17,110	WOO	Deal, N. J. Transatlantic phone.	
18.10	16,560	G2AA	ship phone.	
18.37	16,320	VLK	Sydney, Australia. Phone to England.	
18.40	16,300	PCL	Kootwijk, Holland. Works with Bandoeng from 7 a.m. Netherland State Telegraphs.	
		WLO	Lawrence, N. J.	
18.50	16,200	FRE	Saigon, Indo-China.	
18.56	16,150	GBX	Rugby, England.	
18.80	15,950	PLG	Bandoeng, Java. Afternoons.	
19.50	15,375	F8EZ	French phone to G2GN.	
19.56	15,340	W2XAD	Schenectady, N. Y. Broadcasts 1:30 pm., relaying WGY.	
19.60	15,300	OXY	Lynby, Denmark, Experimental.	
19.63	15,280	W2XE	Jamaica, N. Y.	
19.66	15,250	W2XAL	New York, N. Y.	
19.72	15,210	W8XK	(KDKA) Pittsburgh, Pa. Tues., Thu., Sat., Sun., 8 a.m. to noon.	
19.83	15,120		Vatican City (Rome).	
19.99	15,000	CM6XJ	Central Tuluoco, Cuba.	
		LSJ	Monte Grande, Argentina.	
20.00	14,990	VK6AG	Perth, Australia.	
20.50	14,620	WMI	Deal, N. J.	
20.70	14,480	W8XK	East Pittsburgh, Pa.	
		GBW	Rugby, England.	
		WNC	Deal, N. J.	
20.80	14,420	VPD	Suva, Fiji Islands.	
20.90	14,340	G2NM	Sonning-on-Thames, England. Sundays 12:30-2 p.m.	
20.97-21.26	14,300-14,100	Amateur Telephony.		
21.50	13,940		Bucharest, Roumania, 2-5 p.m. Wed., Sat.	
21.59	13,890		Mombasa, East Africa.	
22.20	13,500		Vienna, Austria.	
22.38	13,400	WND	Deal Beach, N. J. Transatlantic telephony.	
22.50	13,325	G2IV	S.S. "Majestic."	
		G2GN	S.S. "Olympic."	
23.00	13,043	OBE	La Punta, Peru. Time Signals 2 p.m.	
			"Radio-Maroce," Rabat, Morocco, 8-9 a.m. Tues., Thurs., Sat.	

All Schedules Eastern Standard Time: Add 5 Hours for Greenwich Mean Time.

Kilo-Meters	Cycles	Station Name	Location	Time
23.35	12,850	W2XO	Schenectady, N. Y. Antipodal program 9 p.m. Mon. to 3 a.m. Tues.; noon to 5 p.m. on Tues., Thurs. and Sat. General Electric Co.	
		W6XN	Oakland, Calif.	
		W2XCU	Ampere, N. J.	
		W9XL	Anoka, Minn., and other experimental relay broadcasters.	
24.41	12,280	GBU	Rugby, England.	
24.46	12,250	FTN	Ste. Assise (Paris) France. Works Buenos Aires, Indo-China and Java. On 9 a.m. to 1 p.m., and other hours.	
		KIXR	Manila, P. I.	
		GBS	Rugby, England.	
24.63	12,280	Airplane.		
24.68	12,150	GBS	Rugby, England. Transatlantic phone to Deal, N. J. (New York).	
		FQO	FQE, Ste. Assise, France.	
24.89	12,045	NAA	Arlington, Va. Time signals, 8:55-9 a.m., 9:55-10 p.m.	
24.98	12,000	FZG	Saigon, Indo-China. Time Signals, 2-2:05 p.m.	
			Oporto, Portugal.	
25.10	11,945	KKQ	Bolinas, Calif.	
25.24	11,880	WBXK	(KDKA) Pittsburgh, Pa. Tues., Thu., Sat., Sun., noon to 5 p.m., and Sat. night Arctic programs. Television Mon. and Fri. 2:30 p.m., 60 lines, 1200 r.p.m.	
		W9XF	Chicago (WENR).	
		W2XAL	New York (WENR).	
25.34	11,840	W2XE	Jamaica, New York (WABC).	
25.36	11,820	KIXR	Manila, P. I., 5-6 p.m., 11:15 a.m.-12:15 p.m., 2-4 a.m., and (except Monday) 5-10 a.m.	
			Calcutta, India.	


(NOTE: This list is compiled from many sources, all of which are not in agreement, and which show greater or less discrepancies; in view of the fact that most schedules and many wavelengths are still in an experimental stage; that daylight time introduces confusion and that wavelengths are calculated differently in many schedules. In addition to this, one experimental station may operate on any of several wavelengths which are assigned to a group of stations in common. We shall be glad to receive later and more accurate information from broadcasters and other transmitting organizations, and from listeners who have authentic information as to calls, exact wavelengths and schedules. We cannot undertake to answer readers who inquire as to the identity of unknown stations heard, as that is a matter of guesswork; in addition to this, the harmonics of many local long-wave stations can be heard in a short-wave receiver.—EDITOR.)

Kilo-Meters	Cycles	Station Name	Location	Time
31.36	9,560		Konigswusterhausen, Germany. 10 to 11 a.m., 11:30 a.m. to 2:30 p.m., and 3 to 7:30 or 8:30 p.m. Relays Berlin.	
		NAA	Arlington, Va.	
		KIXR	Manila, P. I.	
		ZL2XX	Wellington, New Zealand.	
31.48	9,530	W2XAF	Schenectady, New York. Mon., Tues., Thurs. and Sat. nights, relays WGY 5:30-11 p.m., daily. General Electric Co.	
		W9XA	Denver, Colorado. Relays KOA.	
			Heisingfors, Finland.	
31.56	9,500	OZ7RL	Copenhagen, Denmark. Around 7 p.m.	
31.60	9,490	OXY	Lynby, Denmark. 1 p.m.	
31.80	9,430	XDA	Mexico City, Mex.	
			Posen, Poland. Tues. 1:45-4:45 p.m.; Thu. 1:30-8 p.m.	
32.00	9,375	EH90C	Berne, Switzerland. 3-5:30 p.m.	
		OZ7MK	Copenhagen, Denmark. Irregular after 7 p.m.	
		SUZ	Melbourne, Australia.	
32.06	9,350	CM2MK	Havana, Cuba.	
32.13	9,330	CGA	Drummondville, Canada.	
32.40	9,250	GBK	Bodmin, England.	
32.50	9,230	FL	Paris, France (Eiffel Tower) Time signals 4:56 a.m. and 4:56 p.m.	
		VK2BL	Sydney, Australia.	
32.59	9,200	GBS	Rugby, England. Transatlantic phone.	
32.80	9,110	SUS	Cairo, Egypt.	
33.23	9,010	GBS	Rugby, England.	
33.81	8,872	NPO	Capite (Manila) Philippine Islands. Time signals 9:55-10 p.m.	
34.50	8,690	W2XAC	Schenectady, New York.	
		HKF	Bogota, Colombia.	
34.68	8,650	W2XCU	Ampere, N. J.; W9XL, Chicago.	
		W3XE	Baltimore, Md. 12:15-1:15 p.m., 10:15-11:15 p.m.	
		W2XV	New York City.	
		W8XAG	Dayton, Ohio.	
		W6XN	Oakland.	
		W4XG	Miami, Fla.	
			And other experimental stations.	
34.74	8,630	WOO	Deal, N. J.	
35.00	8,570	RB15	Khabarovsk, Siberia. 5-7:30 a.m.	
35.02	8,560	G2GN	SS. "Olympic."	
		G2IV	SS. "Majestic."	
35.54	8,440	G2AA	shore-to-ship phone.	
35.48	8,450	WSBN	SS. "Leviathan."	
36.00	8,330	3KAA	Leningrad, Russia. 2-6 a.m., Mon., Tues., Thurs., Fri.	
36.74	8,160		Mombasa, East Africa.	
37.02	8,100	EATH	Vienna, Austria. Mon. and Thurs. 5:30 to 7 p.m.	
		HS4PJ	Bangkok, Siam. Sunday 8-10 a.m.	
37.36	8,030	NAA	Arlington, Va. Time signals 8:55-9 a.m., 9:55-10 p.m.	
37.43	8,015	Airplanes.		
37.65	7,980	VK2ME	Sydney, Australia.	
37.80	7,930	DOA	Doberitz, Germany. 1 to 3 p.m. Reichpostzentralamt, Berlin.	
38.00	7,890	VPD	Suva, Fiji Islands.	
38.30	7,830	PCV	Kootwijk, Holland, after 9 a.m.	
38.60	7,770	FTF	St. Assise, France.	
		PCK	Kootwijk, Holland. 9 a.m. to 7 p.m.	
39.15	7,660	FTL	St. Assise.	
39.70	7,550		SS. "Bremen."	
40.00	7,500		"Radio-Touraine," France.	
40.20	7,460	YR	Lyons, France. Daily except Sun., 10:30 to 1:30 a.m.	
40.50	7,410		Eberswalde, Germany. Mo., Thu. 1-2 p.m.	
			Riobamba, Ecuador.	
41.00	7,310		Paris, France ("Radio Vitus") Tests. Moscow, USSR. 7-7:45 a.m.	
41.46	7,230	DOA	Doberitz, Germany.	
41.50	7,220	HB9D	Zurich, Switzerland. 1st and 3rd Sundays at 7 a.m., 2 p.m.	
41.70	7,190	VK6AG	Perth, West Australia. Between 5:30 and 10 a.m.	
42.12	7,120	OZ7RL	Copenhagen, Denmark. Irregular. Around 7 p.m.	
42.50	7,060		Liakov Islands (north of Siberia).	
42.70	7,020	EAR125	Madrid, Spain. 6-7 p.m.	
42.80	7,000	F8KR	Constantin, Algeria.	
43.00	6,980	EAR 110	Madrid, Spain. Tues. and Sat., 5:30 to 7 p.m., Fri. 7 to 8 p.m.	
		CTIAA	Santos, Portugal, Friday, 4-5 p.m.	
43.50	6,900	IMA	Rome, Italy, Sun., noon to 2:30 p.m.	
43.60	6,875	F8MC	Casablanca, Morocco. Sun., Tues., Wed., Sat.	
		D4AFF	Coethen, Germany, Sundays 4-6 a.m.; Tuesdays, Fridays, noon-2 p.m.; Thursdays 4-6 p.m.	
44.40	6,753	WND	Deal, N. J.	
44.60	6,720	VRV	Georgetown, British Guiana. Wed and Sun., 7:15 to 10:15.	
45.00	6,600		Berlin, Germany.	
45.20	6,635	WSBN	SS. "Leviathan."	
46.05	6,515	WOO	Deal, N. J.	
		W4XG	Miami, Fla.	
46.70	6,425	W2XCU	Ampere, N. J.; W9XL, Anoka, Minn.; and others.	
47.00	6,380	CT3AG	Funchal, Madeira Island. Sat. 5-7 p.m.	
		HCIBR	Quito, Ecuador, 8-11 p.m.	
47.35	6,335	W10XZ	Airplane Television.	
		VE9AF	Drummondville, Canada.	
48.00	6,250		"Radio-Maroce," Rabat, Morocco.	
48.30	6,205	HKC	Bogota, Colombia. 9:45-11:30 p.m.	
48.62	6,170	HRE	Teucucalpa, Honduras. 8:15-11 p.m., Mon., Wed., Fri., Sat. Int. S. W. Club program. Sat. 11:30-12 p.m.	
48.74	6,155	W9XAL	Chicago, Ill. (WMAC) and Airplanes.	
48.83	6,140	KIXR	Manila, P. I. 3-4:30, 5-9 or 10 a.m., 2-3 a.m. Sundays.	
		W8XK	East Pittsburgh, Pa. Hu., Thu., Sat., Sun., 5 p.m. to midnight.	
48.99	6,120		Motala, Sweden, "Rundradio." 6:30-7 a.m., 11-4:30 p.m. Holidays, 5 a.m.-5 p.m.	
		NAA	Arlington, Va.	

How to Make and Raise A 60 Ft. Wood Tower

By RICHARD CARMAN

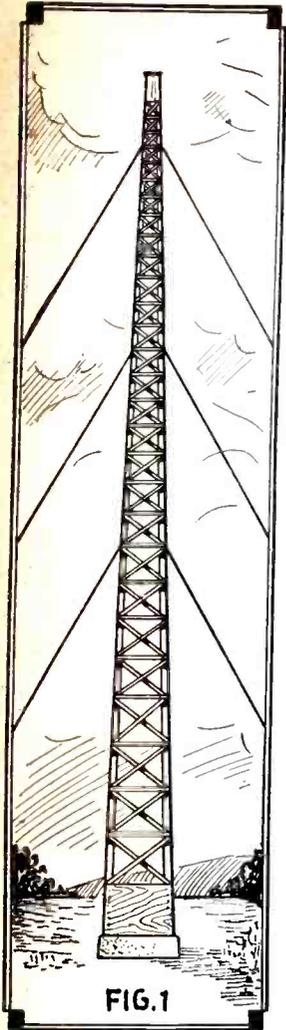This tower, constructed of light wood strips, is surprisingly strong and easily erected. Shorter towers of the same design can readily be built. Suitable rope guys should be fastened to the tower to steady it during high winds.



Appearance of the finished 60 foot radio tower. Of course the tower can be built in any size desired. Rope guys can be used.

HOW many amateur radio operators look at, or hear about, somebody's 60-foot wooden mast with a great deal of awe and admiration, and yet hesitate to make one because of the supposed difficulties in building and erecting it? As a matter of fact, it is a quite simple, inexpensive and easy job, and one which you can be justly proud of when completed. The advantages of a wooden mast are, of course, obvious and much to be desired by the amateur who is collecting those real DX cards.




The mast consists of four longerons, each 60 feet in length, made up of 2 x 1 inch clear pine, and is braced with ordinary lath or wood of similar dimensions, and some of the 2 x 1 pieces are shown in Fig. 3. The highest five feet of the mast are covered with plywood and with one piece of wood at the top, as shown in Fig. 4; this is made as waterproof as possible. It is advisable to paint the entire mast with creosote or some tar-content roof paint. It will simplify the painting very much if the longerons and each section are painted as they are completed. A concrete base must be (or should be) prepared for the mast to rest on, and should extend well below the frost line, be absolutely level and mixed to procure the hardest stone possible.

The first operation in making the mast is to build up the longerons. Secure 2 x 1-inch lumber, dressed and knot-free, and 15 feet long. Take one 15-foot piece and cut it exactly in half; take another piece 15 feet long and place it side by side with the first, even at one end, so

that the two form a combined piece of wood 2 x 2 inches. Nail them firmly together. (If possible, it will produce a much better job to glue and nail them together.) Note Fig. 2.

From this start, build up the entire length of the spar, lapping one piece of wood over the other till you have the 60 feet. At the top you will be able to use the other 7½-foot piece of wood that you sawed off to start the bottom section of

other. Now establish two string lines on each longeron and pull tight, so that you will have a guide to keep the tower absolutely straight as you build up the braces. Nail temporary braces every few feet up the mast to assist in keeping the longerons in the proper position as you nail and glue the permanent braces. At the bottom of the mast fit a board 1 inch thick by 15 inches wide for a base, as shown in Fig. 5, and then put on the

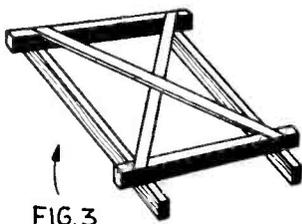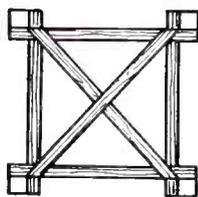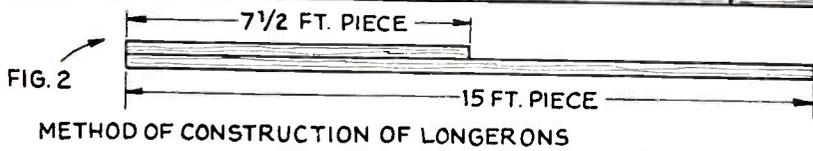

CONSTRUCTION OF SQUARE BRACES

FIG. 4
CONSTRUCTION OF TOP

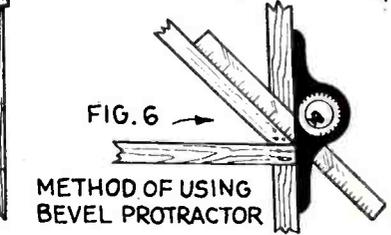
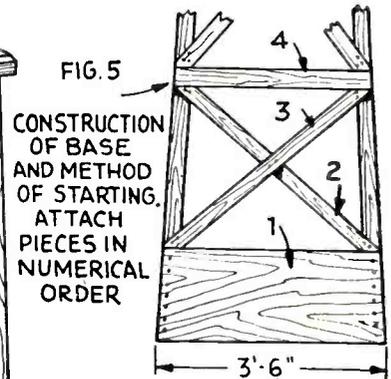
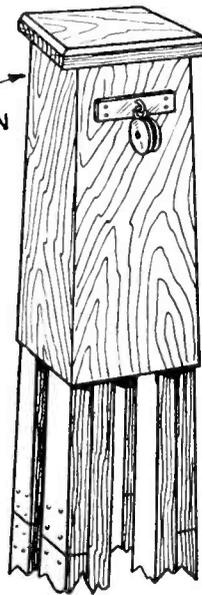


FIG. 6
METHOD OF USING BEVEL PROTRACTOR

Fig. 2 above shows how longerons are lapped; other details of construction are shown by Figs. 3, 4, 5 and 6.

the longeron. Make four of these spars 60 feet long. If you use glue, be sure to clamp them together long enough for them to set.

When the four are completed, take two of them and lay them on something as flat as possible, such as a sidewalk or a series of wooden horses that are absolutely level with one another. Place the bottom ends 3 feet 6 inches apart, measuring from the outermost sides, and place the tops 2 inches apart from each

braces by gluing and nailing them. Put them in in the order numbered, and thus up the entire length of the mast, except the last 5 feet, which will be braced with a single piece of plywood.

A very simple way to keep the mast absolutely symmetrical all the way up is to use a bevel protractor. Make the first "criss-cross" brace as nearly square as possible; then set your protractor to this angle, as shown in Fig. 6. By using the protractor for a guide for the "criss-


crosses" along the entire length of the mast, you will obtain a very perfect looking job. When you have criss-crossed up to within 5 feet of the top, fit a piece of plywood over the remaining distance, as shown in Fig. 4. When this is completed you have finished one section of the mast.

Assembling the Two Sections

Now take the other two longerons and duplicate exactly the section you have just completed. When these sections are finished and painted stand them on their sides, absolutely parallel to each other, with the braces facing outward. Establish temporary braces and string lines the entire length of the mast, so that when you nail and glue the braces on the sides they will exactly duplicate the sides you have just completed. At the bottom place a brace, as shown in Fig. 3, using pieces of the 2 x 1 for the square braces and the laths for the criss-cross. Place one of these at the bottom, and others approximately every 8 feet, all the way up. These braces will look better if you space them evenly with one of the horizontal braces between the "criss-crosses" each time.

When you have placed all the "square-braces" you are ready to fit your board on the bottom on one side and proceed up to the top as before with the horizontal braces and the "criss-crosses." When you have finished this side, turn the mast over and finish that side. When you have thus completed the four sides, finish off the tip with plywood (which may be taken from an old packing box). Glue and nail this in place and finish off the top as shown in Fig. 4.

Now take a ring bolt long enough to

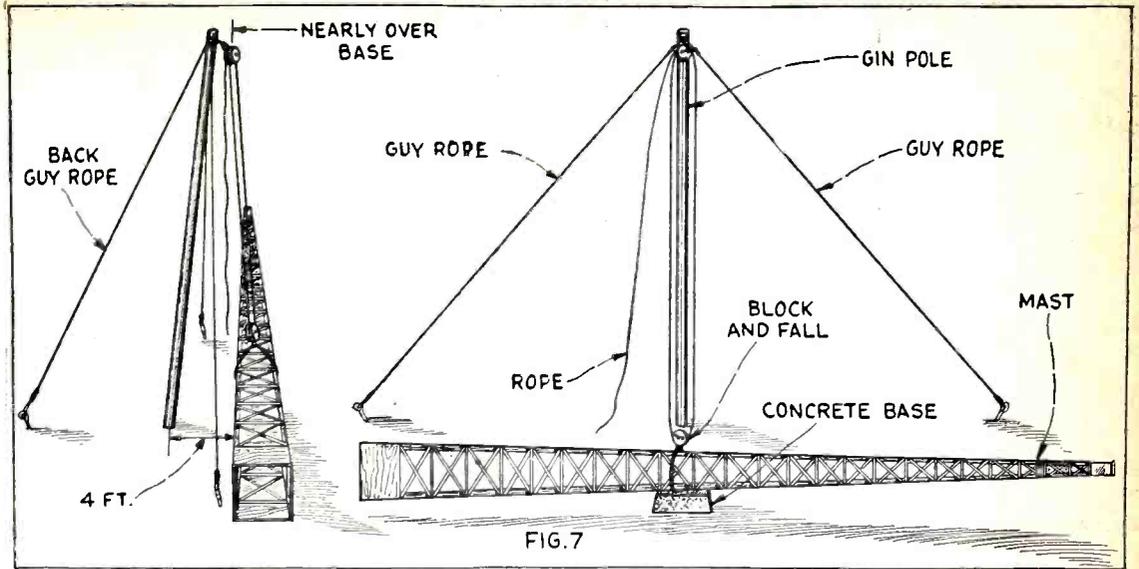

Above we see the author's suggested method of raising the 60 foot tower by means of a gin pole.

reach through the top of the mast, and reinforce its hold with a brass or metal strip which will extend far enough to get the support of the longerons. Drill one hole in the strip to pass the bolt, and several small holes so that you may place small screws into the plywood to make it fast. Now attach the best weatherproof pulley that you can buy, and through this pass the rope (also of excellent quality) to be attached later to your antenna. Finish painting the mast.

Guy wires or ropes must be used, either two or three sets, according to the amount of bad weather in your particular locality. They are secured directly around the longerons at a point where the square braces are in place. The top guys need not be attached any higher

The concrete should extend well below the frost line and must be perfectly level. The mast may be fastened to it by placing pieces of 2 x 4 wood around its base and nailing these to the mast, and using anchor bolts to hold the 2 x 4's to the concrete base.


Another method is to put several bolts or pieces of metal bracing in the original base and let the concrete harden with the bolts protruding at points that will not interfere with the mast coming to rest on the concrete. Be sure the base of the mast is well waterproofed; then place it on the concrete base and pour concrete around the edges and center and let it harden. The protruding bolts or braces will then firmly hold it in place.

Raising the Mast

There may be many ways in which to raise a tall mast or tower, but the easiest and safest is described below; this is known as the "gin-pole method." Not only is it very easy, but only two or three persons are needed to operate the entire equipment. At no time is the mast in danger of slipping or getting beyond control, as may happen with other methods of erecting it.

Place the mast so that the center of balance is directly over the base on which it is to rest. Attach all the guy wires, and place the rope in the pulley, being sure that all are sufficiently long. Now place the gin pole (which must be at least 2 feet taller than the distance between the center of balance of the mast and the base of it) with its foot at a point about 4 or 5 feet away from the concrete base, and its top almost over the concrete base. Fasten the base of the pole so that it will not slip; then place the three guy wires or ropes so that the two on the side are well forward of the base (as shown in Fig. 9) and the rear one is back far enough so that the gin pole will be held in place quite firmly with no danger of slipping. Now place a block and fall at the top of the gin pole, and attach the other end to the mast by passing a rope around the body of the mast two or three times.

(Continued on page 316)

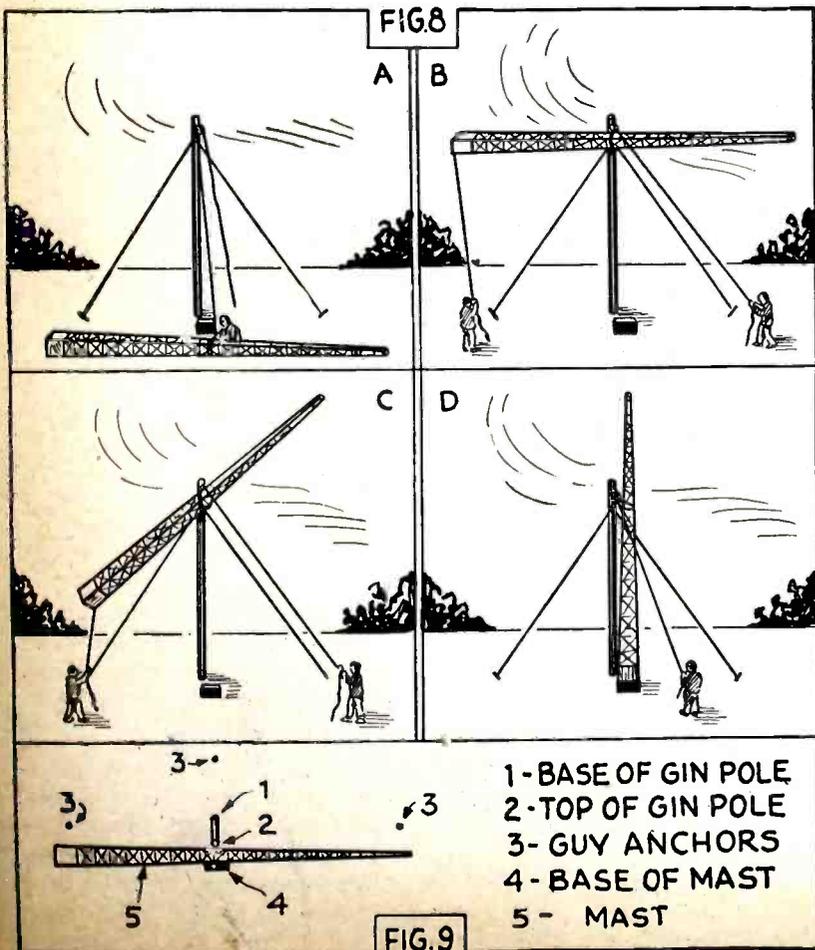

Figs. 8 and 9 here show progressive stages in the raising of the 60 ft. radio tower. When the tower has been hoisted by the means of block and fall as at B, the rope attached to the base is used to pull the mast to the vertical position in D.

SM


Foreign Programs in Your Own Living-Room!

The S-M 738 is a self-contained converter that makes a powerful short-wave superheterodyne when attached to any broadcast set.

There is nothing that the finest commercial short-wave receiver (costing three times as much) will do, that the 738 will not duplicate and beat if your broadcast receiver has any punch at all.

Under favorable weather and local receiving conditions, it will give you every American short-wave broadcaster and the principal foreign stations—for to every bit of the sensitivity and selectivity of your broadcast set is added the additional power of a 224, and a 227 tube!

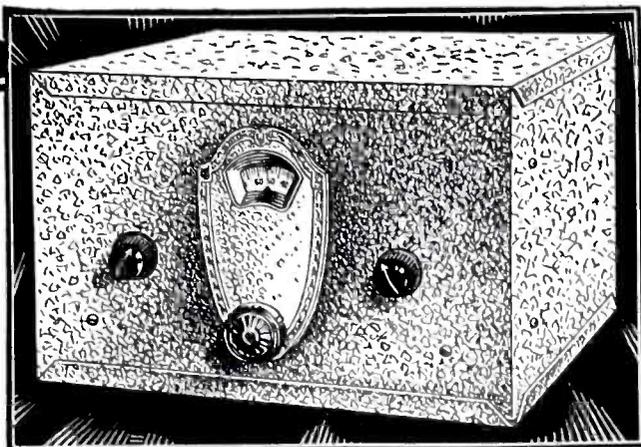The 738 Converter is built in a beautiful black crystalline case with a hammered silver dial escutcheon—a credit to any living-room.



The wired model can be hooked up in three minutes—you merely remove the antenna lead from the broadcast receiver and connect it to the antenna post of the converter; then run two leads from the 738 to the antenna and ground posts of the broadcast set. That's all.

It tunes by a single dial, (which tunes the oscillator circuit) and an auxiliary

midget condenser.

It will give, in addition to short-wave broadcasting, phone and i.c.w. where there is any carrier modulation at all.


Included in the list price are eight coils (four pairs) which cover the wave length range of from 18 to 206 meters. Tubes required: 1-'24, 1-'26, 1-'27.

Price, completely factory-wired, tested and RCA licensed, less only tubes.....\$69.50 List
Component parts total.....\$59.50 List

S-M 737 Bearcat

The Bearcat is a self-contained, a. c., short-wave receiver that is a bearcat. Operated with an S-M 850, 870 or any other above-average speaker, it will give loud-speaker code and short-wave broadcast programs ranging up to 5,000 or even 10,000 miles, depending on weather and local receiving conditions.

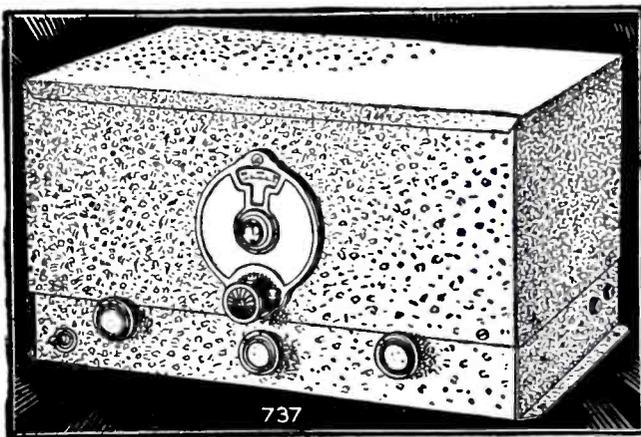The Bearcat consists of one stage of tuned a. c. screen-grid r. f. amplification using a '24 tube followed by a '27 detector of the regenerative type. The detector is resistance-coupled to a '24 screen-grid first audio tube which in turn feeds through a stage of resistance to a '45 power output tube. The power supply, operating from any 105-120 volt, 50-60



5,000 to 10,000 Miles

cycle alternating current lighting circuit, uses an '80 rectifier and provides all A, B and C power for the receiver.

One of the 737's outstanding points of superiority is the built-in midget condenser that allows spreading of the amateur bands over 180 degrees by a turn of the wrist. In addition, it gives very satisfactory vernier control on short-wave broad-

casting—particularly foreign stations that are so difficult to tune in on the average short-wave receiver.

Price, completely factory-wired, tested and RCA licensed, less tubes and speaker.....\$139.60 List
Component parts total.....\$119.50 List

And Superheterodyne Broadcast Receivers

Ask your nearest jobber about the two finest broadcast receivers ever built—the nine-tuned-circuit 724 superheterodyne and the eleven-tuned-circuit 714 superheterodyne tuner—or write for your copy of the new SILVER-MARSHALL GENERAL PARTS CATALOG.

The Radiobuilder, Silver-Marshall's official publication, tells the latest news of the great S-M laboratories. Fill in the coupon for a sample copy. If you are a custom-builder or a radio dealer you should be an Authorized S-M Service Station. It costs you nothing and is invaluable to you.

SILVER-MARSHALL, Inc.
6457 West 65th Street • Chicago, U. S. A.

Silver-Marshall, Inc., 6457 W. 65th St., Chicago, U. S. A.
.....Send your NEW 1931 CATALOG with sample copy of the RADIOBUILDER. Also Data Sheets as follows: (Enclose 2c for each Data Sheet desired.)
.....No. 21. 737 Short-Wave Bearcat.
.....No. 23. 738 Short-Wave Superhet Converter.
.....No. 24. 724 Screen-Grid Superhet Receiver.
.....No. 25. 714 Screen-Grid Superhet Tuner.

Name.....
Address.....

Measuring the Fundamental Wavelength of A Coil or Coil and Condenser

By

MELVERN H. BERRY

EVERY Radio Fan has known of a time when he would give a portion of his anatomy to have some means to test the fundamental wavelength of his coils before placing them in his set to see what they would do. For real accurate results it is impossible to obtain the information without some laboratory testing apparatus.

Most every radio fan has an oscillator and a wave meter. If you have a calibrated oscillator, it will be much better.

fundamental wave-length can be read right from the curve.

If your oscillator is not calibrated it will be necessary to employ a wavemeter to get the wave-length of your coil. This can be done by bringing your wavemeter (absorption type) close to the coil to be measured, and when the resonance of the meter is adjusted to coincide with the frequency of the


in double hump resonance,—the indicating device will register at two different wave lengths quite close together. To remedy this it is only necessary to loosen the coupling until the two resonance points merge into one. (It might be of interest to point out that this phenomenon is harnessed to furnish the circuit selectivity of the Hammarlund Hi-Q29 receiver, where the coupling has been reduced to one per cent.)

Instead of the 25-ohm potentiometer diagrammed, it is suggested that a 300- or 400-ohm one be used if a battery type tube is used rather than one of the A.C. type.

Also, the oscillator may work more smoothly if the grid leak connects to filament of the tube. The negative "A" is the correct side for an oscillator.

The .002 mfd. fixed condenser must be of high grade as the "B" potential is impressed on it at all times.

It must be remembered that loose coupling must be maintained between coils, if maximum accuracy is to be realized. As it is necessary to have a frequency or wavelength standard from which to work, such a standard must be built or purchased. A simple method for calibrating a home-constructed unit is to use the tuned circuit as an absorption trap in conjunction with a regular radio set, setting the eventual wavemeter so that it "tunes out" the carrier of a broadcast station using crystal control; these stations can be depended upon to be adjusted to their assigned frequency. Once the dial readings for these frequencies have been determined, the rough calibration of a "wavemeter" has been accomplished. Plotting these values on graph paper will supply intermediate values. — (Courtesy Radio-Craft.)

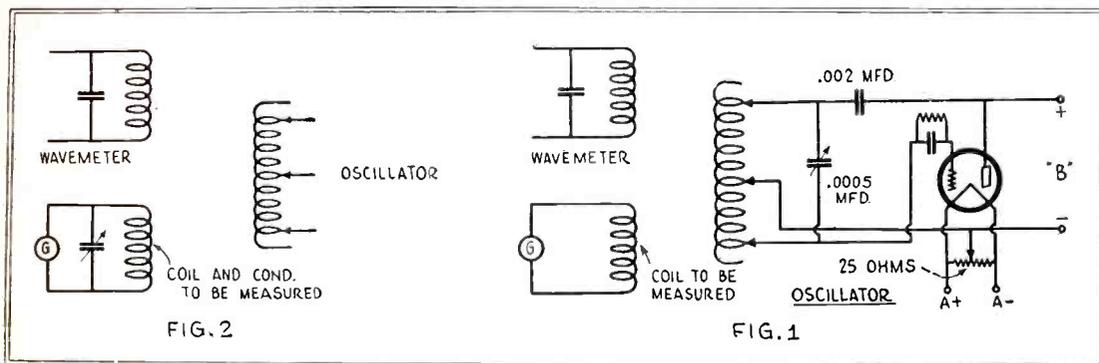

The two schematic arrangements above indicate the proper connections and coil relations to be observed when determining the wavelength range of a particular coil, or coil-and-condenser.

A neat and accurate galvanometer can be made for a few cents by winding a few turns of fine wire on a form one inch square. Hang this solenoid between the poles of a horseshoe magnet, allowing the ends of the coil to support it.

Place the galvanometer across the ends of the coil to be measured, Fig. 1, and bring the coil in close proximity to the coil of the oscillator. Rotate the dial of the oscillator until there is resonance between the two coils. When the wave-length of the oscillator is the same as that of the coil to be measured a current will be noted to flow in the galvanometer. The indication may be very slight. The amount of deflection of the galvanometer depends upon its sensitivity and the coupling of the two coils. If your oscillator is calibrated the

oscillator there will be a second deflection of the galvanometer towards zero. The actual maximum fundamental can be read directly from the meter or from the curve.

When using as a test for the wave-length of a coil and condenser combination, refer to Fig. 2.

It will be necessary to put a radio frequency choke coil in the lead from "B" plus to plate. Otherwise, the battery resistance would probably be so low there would not be sufficient radio frequency voltage drop to cause circuit oscillation. This choke may be of any convenient size. On an ordinary thread spool, 250 turns of 30 to 36 gauge wire with almost any kind of insulation would work well.

It must be noted that incorrect coupling of the absorption circuit to the circuit under test will result

Looking Ahead With Short Waves

By DR. ALFRED N. GOLDSMITH

(Continued from page 265)

patience. Most assuredly he wants to tune in the overseas signals direct, without the intermediary of the R.C.A. and N.B.C. facilities. But from the standpoint of enjoying the overseas programs, as *reliable programs*, there can be no other choice than the retransmitted signals available to all broadcast listeners tuned in on the N.B.C. networks.

Can Short Waves Extend Over Broadcast Spectrum?

Another moot point is that of using short-wave signals for multiplying the number of broadcast channels. At a glance, the suggestion appears logical. Upon study, however, it represents many and serious drawbacks. While a few suitable channels might be added directly below the present 200-meter broadcast band, the shorter waves are hardly applicable to broadcast requirements. Thus, with standard broadcast wave lengths, engineers can closely determine the coverage of a transmitter. Range, service area, and probable number of listeners become subject to mathematical computation. And, since a broadcaster lives by the audience he commands, such precise information is much to be desired. With short waves, however, it is entirely different. There is the skip distance. There is absorption. There is the echo effect. There is a dead local area. In fact, practically nothing is certain about the service range of a short-wave transmitter employed for mass communication purposes. Ostensibly, the field of short-wave radio (between 15 and 100 meters) is for radio relays or connecting links between broadcasting systems, as a means of interchanging programs.

Future of Short Waves for Television

In radio television, short waves are certain to be employed in the future as well as at present. Where else can the television broadcaster hope to find the

necessary elbow room for his necessarily wide signals? Here again, short-wave transmission presents many problems.

Thus, the higher frequencies are quite unsuitable for an area nearer than a hundred miles. Signals approaching the broadcast band must be employed for the purely local area; while shorter waves might be used to reach distant points. Then, it is necessary to employ carefully chosen wavelengths to overcome excessive absorption of signals, particularly in crowded localities. Different wavelengths may be employed during different hours of the day and night for distant work. Today, queer "echo" effects or double images, due to the reflection of the signals by the Heaviside layer, are obtained at the receiving end.

The idiosyncrasies of the higher-frequency signals are not the least of the many practical difficulties that stand in the way of radio television progress beyond the purely experimental status of today. And yet the very short waves below 10 meters may show extremely practical capabilities for television after further research.

Short-wave radio, the experimental field of today, is bound to become the practical field of tomorrow. The short-wave art is rapidly being reduced to standardized practice, based on sound engineering knowledge. In everyday communication, we have harnessed short waves down to 15 meters. Even the shorter waves are now being studied with promise of early commercial application. And, as the frontier of everyday radio is pushed back steadily, down the wavelength scale, the experimenter is always certain to find plenty of opportunities to pioneer and blaze the trail beside the engineers and commercial minds that follow along somewhat different paths, all leading to the continuous progress of radio.

How to Gain Detector Sensitivity

By MANDER BARNETT


(Continued from page 281)

antenna as loosely coupled as may be consistent with good results. This will also help to smooth out "dead spots" in the tuning, which are caused by the natural wavelength of the antenna. This trouble, of course, does not appear in receivers using a screen-grid tube in front of the detector.

In the accompanying diagram is shown a super-sensitive detector circuit in which every effort has been made to make it as smooth working as possible. R1 is a 2-meg. grid leak, and R2 is the 200-ohm potentiometer. C1 is a small by-pass condenser, about .0002-mf.; a larger capacity would possibly by-pass R. F. currents better, but would cause a cut-off in the

notes of the higher musical scale. C2 is a 2-mf. condenser and this, together with the 20,000-ohm resistor, effectively decouples the detector circuit from the other audio and R. F. stages. C3 is merely for R. F. by-passing purposes and must be kept very small—.0002-mf. will do again here. This must be kept very small or otherwise it would tend to cancel out the effects of C2. Both R. F. and A. F. stages may, of course, be added to this detector circuit as required, and the owner of such a receiver will have the satisfaction of knowing that he is, at least, getting the best possible results from his detector stage, provided, of course, that high-quality components are used.

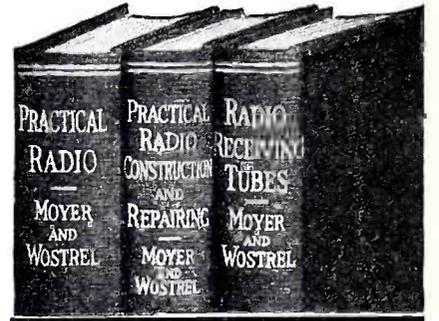The answers to your questions on building, testing and repairing radio sets



The three volumes of this library cover the entire field of building, repairing and "trouble-shooting" on modern radio receivers. The Library is up-to-the-minute in every respect and is based on the very latest developments in the design and manufacture of equipment. The rapidly-growing interest in *short-wave reception* is thoroughly covered in a complete section which deals with the construction of this type of apparatus.

Radio Construction Library

By JAMES A. MOYER and JOHN F. WOSTREL

Faculty, University Extension, Massachusetts Department of Education

Three Volumes — 993 Pages, 6x9
561 Illustrations

VOLUME I: presents the fundamental principles of radio so clearly and simply that anyone of average training will be able to read, understand and apply them. In one chapter alone, it gives actual working drawings and lists of materials for the construction of eight typical sets.

VOLUME II: fully discusses all of the elementary principles of radio construction and repair. An explanation of the necessary steps for "trouble-shooting," repairing, servicing and constructing radio sets successfully. Practical data is also given on antenna systems, battery eliminators, loud speakers, chargers, etc.

VOLUME III: covers the essential principles underlying the operation of vacuum tubes in as non-technical a manner as is consistent with accuracy. It discusses the construction, action, re-activation, testing and use of vacuum tubes; and an interesting section is devoted to remote control of industrial processes; and precision measurements.

EXAMINE these books for 10 days FREE
This Library is not only a thorough home-study course, but a handy means of reference for the more experienced radio experimenter, repair man, and radio shop-owner. To these men, as well as to those who desire to advance in the radio profession, this offer of a 10 days' Free Examination is made.

Simply clip, fill in, and mail this coupon

McGRAW-HILL
FREE EXAMINATION COUPON

McGRAW-HILL BOOK COMPANY, INC.
370 Seventh Avenue, New York.

Gentlemen: Send me the new RADIO CONSTRUCTION LIBRARY, all charges prepaid, for 10 days' Free Examination. If satisfactory I will send \$1.50 in 10 days and \$2.00 a month until \$7.50 has been paid. If not wanted I will return them at your expense.


Name

Home Address

City and State.....

Position

Name of Company.....SWC-12-30

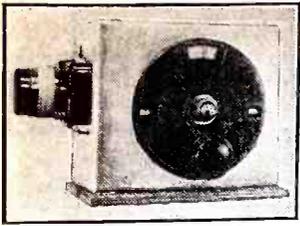

DELFT All-Short-Wave Wavemeter


This fine sturdy wavemeter is for finding foreign short-wave broadcasting stations on your short-wave receiver without wasting time hunting for them. Instructions for finding any station come with it. It stops guessing at wavelengths. Requires nothing else for its use with your set. Long distance is easy with a wavemeter. First

you look up the station wavelength in the magazine. Next you set the wavemeter to that wavelength. (This is easy because all the wavelengths are marked right on the dial.) Then all you have to do is to tune your short-wave receiver to the wavemeter. The desired station will then be heard in your set without further trouble if it is there at all. The wavemeter tunes from 15 to 125 meters so any short-wave station is easily found. It is totally shielded so there is no hand-capacity. It comes complete with extra, sturdy plug-in coils, wavelength calibrations charts and full, simplified instructions telling how to operate the wavemeter to get best results with any kind of short-wave receiver. Complete Wavemeter only \$6.95 Postpaid. Others charge from \$12 to \$20. Why pay more? Easy to operate.

Special Amateur Band Wavemeter

You can use the above wavemeter with a transmitter also. But we have a special amateur-band wavemeter which looks just like the one above but gives the required accuracy (1/4 of 1%) demanded by the government. For \$5.55 postpaid, you get the complete wavemeter, all instructions, and calibrated coil for any one amateur band with this accuracy. For each extra band, add \$1.50 for the extra required calibrated plug-in coil.

DELFT Coil Winding Kit

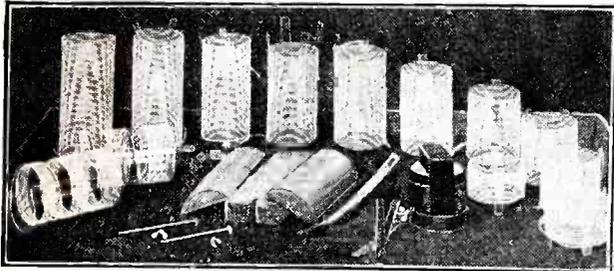

This new coil winding kit makes perfect short-wave coils in no time. The special threaded type form gives exact spacing between turns. It is 2 inches in diameter—the best size for all short-wave coils. It makes broadcast and transmitting coils too. When a coil is finished, the form collapses and slips out, leaving a perfectly-spaced low-loss coil on a thin skeleton celluloid frame. You can't buy coils better than these at any price. The kit contains a Delft form, discs, low-loss cement, plenty of wire, brushes, 40 ft. of cord, skeleton celluloid frames and full instructions showing condenser and coil sizes necessary for different short-wave and broadcast wavelengths. Complete and ready to use—nothing else required. Why pay \$10 for a single set of coils? You can make all you want with this kit. The form never wears out. Order now! You'll be surprised. New complete Kit, \$1.89 postpaid. We are originators and sole manufacturers.

DELFT Short-Wave R.F. Amplifier Kits

Kits supply all parts (panel, baseboard, everything) for construction of sensitive R.F. receiver amplifiers. Connect ahead of your present set, regardless of its make, and build (or "boost") the received music loudness up, even before it reaches your set. This set will give you good loud-speaker volume even on distance. Comes complete with layout, hook-ups, directions, showing how to connect it to any short-wave set. Easy to build. Uses the power supply from your present detector unit. Complete 2 tube Kit, battery operation, \$7.95, less tubes, (takes all power from your present detector unit). Complete 2 tube Kit, for A.C. operation, \$9.45, less tubes, (separate filament supply transformer needed for A.C. operation), \$2.50 (but takes B supply from your detector). Complete One Tube Kit, battery operation, \$5.95, less tube. Complete one Tube Kit, A.C. operation, \$7.45, less tube. (requires above transformer at \$2.50, but takes B supply from your detector). (For both one-tube Kits, state whether or not you want a long panel (same price) so you can add another tube later). These kits postpaid. Tubes: \$1 for D.C., \$1.50 for A.C., (tested)—sold only with above kits.

WARNING! Guaranteed Plug-In Coils

Our engineers have tested every type plug-in coil. Many of them don't work in your set, because they were built for some other special purpose. They also tune up to the broadcast range, but there is nothing from 100 to 200 meters. Why buy useless coils? Some firms don't say their coils have no tickler windings, so you can't use them when they come. Be careful to buy where they are shown in the photo of the wavemeter in this ad, but have finger handles that don't pull out. All coils are tested in a short-wave set. Tube-base coils (fit into a UX- or I-prong socket, use, 15 to 125 meters, using either a .0001, .00014 or .00015 condenser, Set of 3 (with finger handles), \$1.35. Same kind of coils but having tickler windings also (for detector), Set of 3, \$1.95. Guaranteed.

SOME DELFT SPECIALS:

TRANSMITTING AERIAL KIT—(Good condenser, copper ribbon coupling coil, wire cut to right size, insulators—and full instructions—\$3.50. (State which band you use); **R.F. Choke Coil** (Special 3 section winding; eliminates dead spots on transmitter, as telephone Transmitter—\$1.00—microphone not supplied. Kit for building a complete short-wave adapter kits have instructions; also postpaid).


NOTICE that our items are sent postpaid. You thus save postage, collection and money order fees. Others do not mention postage. When your parts come, the actual cost is much more. We sell cheap and save you plenty on postage too. Send money in bills, small amounts in stamps, if you wish; wrap well, register the letter if necessary.

DELFT
Phone: Higate 0748

524 Fairbanks Avenue,
OAKLAND :: CALIFORNIA

SHORT - WAVE
RADIO
SPECIALISTS

DELFT Short-Wave Transmitter Kit

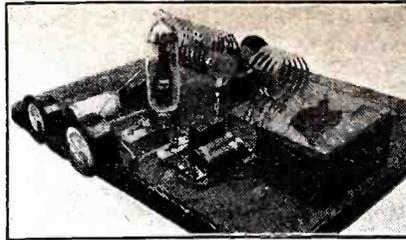

Build this fine modern transmitter. The Kit supplies absolutely all transmitting parts, except baseboard, to build this set. Meters not necessary to operate it, so not included. No tube or power supply is supplied because users want to transmit with a receiving tube and add big tube later. Uses batteries or plate supply from your receiver. Batteries or A.C. as desired. Six pages of instructions, all circuits, layout, aerial sizes, filters, rectifiers, coil sizes various wavelengths (coils furnished with it for 20, 40 and 80 bands), all adjusting dope, etc. No license required to experiment with it. Ham license easy after you know how! Use it on the air later. Complete Kit, \$8.45 postpaid. This set works at least all districts with a 5-watt tube.

DELFT All-Electric Short-Wave Receiver Kits


Never Before at Such Prices!!



This kit supplies all parts (including panel, baseboard, etc.) for a neat short-wave receiver, consisting of sensitive detector and stage of high-gain audio amplification. Brings in stations directly from 3,000 miles away regularly and often much farther. You can add to it later for even greater distance so nothing is wasted. You get all parts, also a Delft coil winder so you can make all the coils you want for any wavelengths. Also full, simplified instructions (giving values for different wavelengths, etc.), circuit diagrams, layout, adjusting information—6 pages giving all you need to know about short-wave receivers. Easy to build, in a short time. All kits below are similar. Complete 2 tube Kit, for battery operation, \$10.95 postpaid (with tubes, \$12.95). Good set of head phones, \$1.50. Complete 3 tube Kit (2 stages audio), for battery operation, \$11.95 postpaid (with tubes \$14.95). Complete 2 tube Kit, for A.C. operation, \$12.95 postpaid (with tubes \$15.95). Complete 3 tube Kit (2 stages of audio), for A.C. operation, \$14.95 postpaid (with tubes, \$19.45). Filament Transformer (eliminates A battery), for 2 tube A.C. Kit ('27 tubes), \$2.50. Filament Transformer, with ample capacity for either 2, 3 or 4 tubes (either type '27 or screen-grid), \$3.00. 3 or 4 tubes operates a speaker (all kits on the market do not include tubes). Suppose you want a Complete 2 tube A.C. Set: Kit alone, \$12.95, F. Transf. (will serve when you add more tubes), \$3.00; 2 tubes at \$1.50 makes \$3; Total, \$18.95. You can operate an A.C. set with one \$1 B-battery temporarily, and buy an inexpensive B-eliminator later, making the set entirely all-electric. Phones, tubes, transformers, not sold separately. These are the lowest prices anywhere!

DELFT Code Practice Set

Something Entirely New and Novel! !

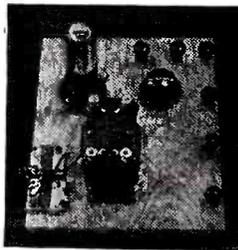

This inexpensive Code Practice Set gives a Natural Code Tone like actual radio signals. Simply connect head phones and key. But can be used without a key. Requires no B batteries. Takes 2 dry cells to operate it. Used for sending and receiving. Practice Set, without tube (with full operating Instructions and experiments), \$3.85.

Postpaid. Get one Now!

Can We Radio the Planets?

By HUGO GERNSBACK

(Continued from page 270)

dously important radio research work between points on our own planet.

Penetrating Short Waves

I am fully aware of the criticism that will at once be raised, that it is not possible for us to send a radio beam beyond the confines of our own atmosphere, due to the so-called Heaviside reflecting layer effect, which is supposed to exist a hundred or so miles above the surface of the earth. According to the researches of the eminent scientist, Oliver Heaviside, the upper layers of our atmosphere are supposed to be so conductive electrically, due to the ionizing effect existing at such heights, that the radio waves are reflected; and it would thus seem impossible that we could project a radio beam outside of the confines of the earth.

This may be perfectly true when it comes to the usual radio waves, such as have been used in the past varying from some 15 meters up to 25,000 meters; although I maintain, along with many other physicists, that the Heaviside effect has never been proven conclusively. I am equally certain that at lower wavelengths, say from two meters downwards, entirely different conditions appear, for the following reasons:

We know that radio waves are nothing but an electromagnetic activity, the same as light waves or heat waves. It is believed that, the lower down we go in the wavelength scale (that is, the higher the frequency), the easier it becomes to penetrate the Heaviside layer, if we grant its existence at all. Light comes to us, from the sun and the planets, through the Heaviside layer; so we know that the Heaviside layer cannot stop light waves. To be sure, the frequency of light waves is enormously higher than that of even the shortest radio waves; but it still seems reasonable that for waves of the length of two meters, or even less, the Heaviside layer should not cause us undue worry.

Incidentally, interplanetary conditions are about the same as we find in our present vacuum tubes. Fig. 1 shows a vacuum tube, in which (1) is the filament; (2) the grid; (3) the plate. Electrons are given out by the filament (1), and shoot in the direction of (3); but, surrounding the grid and the plate, there is a miniature Heaviside layer, composed of a slight amount of gas, which surrounds all metallic and other matter, and which the electrons must first pierce before they can reach the grid or the plate.

In the Interplanetary Vacuum

Given a reasonably strong bombardment of electrons, this internal tube "Heaviside layer" can be broken down as is well known. Conditions on earth seem to be similar. If we employ the right radio wave, with sufficient power behind it, it should be possible to pierce the supposed Heaviside layer and shoot the waves out into free space. In this we would be assisted by the force of the solar radiation itself. This is made plain

in Fig. 2, which shows that our own planetary system is nothing but a vacuum-tube arrangement on a large scale. We have the sun in the center, with the planets outside, which in this case become the plate and grid of our celestial vacuum tube.

It will be noted that the solar radiation is in the direction of the arrows. It would seem, therefore, that a beam of the correct radio wave sent, let us say, from the earth to Mars, when in "conjunction," would stand a better chance of being transmitted than vice versa. For that reason, it would seem that a supposed signal emanating from Mars earthward would find it necessary to work against the stream of solar emanations, and encounter more resistance than if the case were reversed and the signal were sent from earth to Mars.

Marconi, in his recent researches, has shown that it is possible to conserve a great deal of energy by using his so-called "beam system." The beam system is nothing but a reflector arrangement whereby practically all of the energy is sent in one direction to the exclusion of other directions.

A Super-Reflector

Suppose we should now erect a tremendous power plant, which would use, let us say, 100,000 kilowatts, radiating the power on a wavelength of 2 meters or less, using the beam system of reflection. What would happen if such a tremendous amount of energy were let loose into the ether, we do not know today.

The question of sending intelligible messages to Mars or Venus need not be dealt with here at all, although it opens up interesting speculations. To the contrary, this discussion confines itself to practical scientific research, as will be apparent from a study of Fig. 3. It is known that radio waves can be reflected, just as light can be reflected, by means of a mirror. Hertz was the first to point this out, and Marconi is making use of the system by reflecting his beam, using metallic-screen reflectors to do so.

Scientists today are pretty well agreed upon the fact that the interior of the earth is composed largely of iron; practically every meteor that falls from the heavens is composed of iron; and practically every star investigated shows a large proportion of iron in its makeup. The conclusion, therefore, may be drawn that the moon, for instance, must therefore be largely composed of iron. It would therefore make an excellent reflecting medium.

Suppose now, that we proceed to erect our 100,000-kilowatt radio beam-transmitter at a point somewhere, indicated at A, on our globe. It will now be possible to direct a beam towards some point on the moon, where the angle of incidence will be suitable. The radio beam reflected, therefore, would come back to earth somewhere, shown at point B. It would be a simple matter for an astronomer to calculate the exact angle at which the beam should be sent, and it should be possible for an observer at B to detect

the reflected beams, if reflected they are. This could be easily proven as follows: The distance between the earth and the moon is, on the average, 238,854 miles.

Radio waves travel at the rate of, roughly, 186,000 miles each second. If both observers, at A and B, were using chronometers, and if a signal were sent from A at a certain time, the signal going out to the moon and reflected from it would be found to return to the earth in a little more than two and a half seconds. This would afford, therefore, a complete proof of the theory.

The same method might be used, perhaps, with other heavenly bodies, such as Mars or Venus; and would be of tremendous assistance to science in general, if found practical. What immediate benefits would be derived, in dollars and cents, I am in no position to state; although I believe many valuable discoveries, incidental to the effects produced, would no doubt be made sooner or later.

It has often been proposed to use the well-known Goddard rocket to explore the heavens, and have this rocket equipped with radio instruments which could send back a signal, thereby proving or disproving the Heaviside theory. It is possible, by means existing today, to construct such rockets. Indeed, the Society for the Exploration of the Universe, which is now being founded in Vienna, Austria, proposes to build such a rocket. Dr. Franz Hoeff, the noted Viennese scientist, and chief promoter of the plan, states that the first experiment, which is to be followed by others, can best be carried out with the rocket containing several kilograms of explosive flashlight as the only load. The shock accompanying the landing on the moon would bring the flashlight to explosion and, with the help of the modern telescopes, the explosion would be noticeable from the observatories of the earth.

It would seem quite simple to incorporate a radio set in such a rocket, at no excessive cost. Of course the radio set would no doubt be smashed to atoms when the rocket landed on the moon; but this need not worry us. The experiment is supposed to be made only to prove or disprove the Heaviside theory; and the signals, providing the apparatus functioned properly, could be sent back to the earth for a distance of some 238,000 miles, until the rocket actually struck the surface of the moon, when the signals would cease.

Analyzing the Earth's Interior

Aside from its utility in exploring the heavens, our super-power radio beam plan may, in addition, be used for terrestrial radio work; as the beam could, of course, be sent horizontally for scientific radio purposes. Important experiments could be carried out for underground radio by reflecting the beam earthward, as shown in Fig. 4. If, as many scientists have conjectured, the interior of the earth is an iron core, as shown in this illustration, the following important experiments can be made:

HEADQUARTERS for HEADSETS

Even during the rapidly progressing years of radio there still remains need, for broadcast and testing purposes, experimental work and short wave reception, of headsets of precision manufacture and quality workmanship. The products presented below are made by the largest manufacturers of radio headsets in the world—products that have been recommended for years and years and need no introduction to the radio trade.

BRANDES and CANNON-BALL Products



BRANDES Matched Tone Headsets
Standard and reliable since 1908. Brandes Headsets have been used continually through these long years and have given remarkable service. They still occupy first position among headsets used throughout the world.
Superior, 2000 Ohms Resistance— **\$4.50**
List Price.....

CANNON-BALL Headsets
The popularity of Cannon Ball Headsets is a tribute to their high quality. Aluminum cases, double magnets and double poles. Quality built. Popular priced.
Dixie, 1800 Ohms Resistance— **\$2.25**
List Price.....
Senior, 2000 Ohms Resistance— **\$3.00**
List Price.....
Master, 2200 Ohms Resistance— **\$3.50**
List Price.....

CANNON-BALL Single Phone
Used principally with Crystal Sets. Low in price and gives very satisfactory reproductions.
Dixie Single, with 4½ ft. cord and braid headband. List Price..... **\$1.50**
Dixie Single, with 4½ ft. cord without headband. List Price..... **\$1.25**

PANDORA Crystal Set



Selective and efficient. Receives broadcast reception loud and clear from stations within a radius of 25 miles. Of metal construction and enameled in various colors.
List price, with Crystal, **\$2.50**

Cannon & Miller Co., Inc.
Springwater New York

Look! Look!



A Real Compass

A genuine Belgian Stoppani Compass; solid bronze, Parkerized; graduated in 1/10; Ruby Jewelled. Has surveyor's elevated sights; 4 inches square; hardwood case; set screw in corner to hold needle rigid when not in use. Said to have cost U. S. Government \$29.00. Sportsmen can never hope to equal this wonderful value. Complete, \$6.00; 2 in one shipment, \$10.00.

AMMUNITION CASE

For belt. Solid cowhide, plush lined, with clasp flap; weatherproof; 3 1/2 inches deep, 2 1/2 inches wide. One dollar value anywhere. Only 25 cents. If money is sent in advance, we pay postage in the United States.

Here is a **NEW** and **BETTER PORTFOLIO**—*more beautiful, more practical, lighter in weight*



(WEIGHT 1/2 POUND)

The Daisy Portfolio is as far ahead of the old style brief case as a modern plane over a canal barge. With this beautiful portfolio under your arm, you present a *neat appearance* and you don't look like a school boy. If you want to take some papers or samples from the bag and show them to your prospect, you don't take up his time *fussing around with two buckles and a lock*. One pull of the *patented slide fastener* and your samples and papers are out—another pull and they are *securely locked*.

May be used by Radio Engineers, Consultants, Architects, Advertising Solicitors, Bank Messengers, Brokers, Buyers (to carry order pads, circulars, samples), Collectors, Engineers (to carry blueprints), Salesmen (to carry samples), Teachers, College Students.

Price \$2.50 P. P. Prepaid. Send check or money order to

Gold Shield Products Co.
102 WC Chambers St., N. Y. C.

For many reasons it is desirable, today, to know the exact composition of the interior of our planet. If there is an iron core at the inside of the earth, as tentatively shown in Fig. 4, a power plant shown at A could project a beam in the direction of the arrow, emerging at B. By pointing the beam in various directions, it should be possible to ascertain the thickness of the metallic core quite accurately.

Many other important facts, would surely be discovered through experimentation of this kind on a large scale; and might, in time, be translated into dollars and cents, bringing great returns to the builders.

And last, but not least, the subject of communication between the planets can then be undertaken in earnest. If we find out, by experiment, that we can reflect a radio beam from the surface of the moon, we can be reasonably certain that, given sufficient power, the same beam system can be used to send signals to either Mars or Venus; as these two planets hold forth the greatest hope of being the abode of some sort of life.

I am of the opinion that, if interplanetary communication by radio waves becomes possible, it will be only through the instrumentality of short waves. I do not believe that our present radio instruments have been brought to such a state of perfection that they can intercept such signals; but I do believe that, during the next fifty years, the sensitivity of short-wave receivers will be made so great that it will be possible to receive the necessarily faint signals, which may have their origin millions and hundreds of millions of miles away.

At the present time it would seem no more foolish to build such a radio plant for the benefit of the radio art, than to build one of our tremendous telescopes.

How to Make a 60-Foot Wood Tower

By **RICHARD CARMAN**

(Continued from page 309)

You now tie to the base of the mast a light rope or clothesline long enough so that, when the mast is pulled up to the top of the gin pole, you may pull the base down to the ground and swing it to the concrete base.

Now pull up the mast to the top of the gin pole, with one person guiding the rope attached to the base. When it is at the top of the gin pole, pull the rope attached to the base and gently place it in position on the concrete base. Fasten the base down, and stay the guy wires for the mast itself.

If you cannot easily secure a gin pole strong enough (about 6 x 6, or two floor beams 2 x 8 inches nailed together in the same manner as your longerons of the mast), you may use a substantial ladder or extension ladder as a gin pole.

The writer will gladly give you any information you desire if you will address him, care of this magazine, and **ENCLOSE A STAMPED AND ADDRESSED ENVELOPE.**



Short-Wave Reception for \$5

**It Can Be Done—
It Has Been Done!**

EVERYWHERE you go you hear talk about short-wave reception. The old-timers in radio are interested in it, more so now than ever before. The new-timers are thrilled. All know that foreign reception is obtainable, a joy denied on broadcast receivers.

It has been possible for eight years or more to build devices that will enable the reception of short waves, and will give good results. But such devices were rather expensive.

How about \$5 as a fair price for the privilege of enjoying short-wave reception any time you so desire? That's different, you'll agree.

You might be willing to spend \$100 to be able to bring in short-wave stations, but you wouldn't mind enjoying the privilege of the same reception in that same fascinating band if the price were only \$5, now, would you?

All you need do, therefore, is to find out how it can be done. You don't want some theoretical description, but the facts, cold facts or hot facts, but above all, the facts. You can have them.

One dollar will bring you Radio World, the first and only national radio weekly, for eight weeks, starting with the November 8th issue. In the November 8th and 15th issues you will find all the fundamentals of the secret, and the solution to the problem, while subsequent issues will present operating sidelights. Full revelation of parts to use, parts that cost only \$5, including data on winding your own coils, is in the November 8th and 15th issues.

Moreover, you will get a blueprint showing the schematic wiring diagram and the pictorial wiring as well, full-size. And the size of the device is so small you can put the short-wave gadget in your overcoat pocket.

**MAIL THIS COUPON!
Penetrate the Mystery!**

RADIO WORLD,
145 West 45th Street,
New York, N. Y.

Just East of
Broadway

Enclosed please find \$1.00, for which please send me:
 Radio World, postpaid, for eight weeks, beginning with the November 8th issue.
 A blueprint of the Short-Wave Gadget, both schematic and pictorial diagrams, full-size, with coil winding data, postpaid.

Name
Street Address
City..... State.....

A 19 Tube S-W Receiver

By DR. FRITZ NOACK

(Continued from page 302)

cepted are sufficient for telephone communication.

While a much narrower band would suffice for telegraphic work, the same coupling is used for this purpose; particularly as added certainty of reception is thus afforded, and also because telegraphic transmission of pictures is also contemplated. If desired, the frequency-band passed by these filters can be widened by adjusting the coupling of the individual filter circuits; for which purposes a calibration is provided.

Surplus Amplification Provided

The amplification factor of the R. F. amplifier is from 600 to 6,000 times, and that of the intermediate amplifier about 20,000; so that, under the most unfavorable signal conditions, the over-all amplification before the second detector is about 12,000,000. To permit a coarse adjustment of the factor of amplification, a potentiometer which can be turned completely off is incorporated in the in-


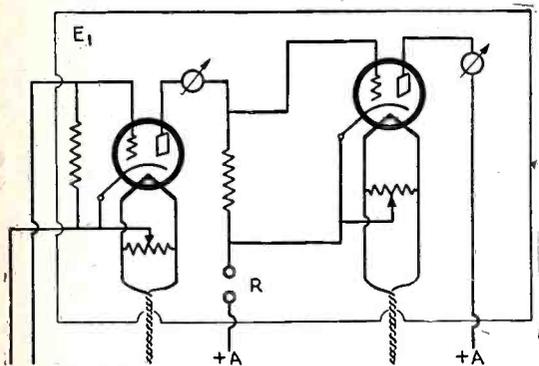


Fig. 4. For receiving code this circuit is used, with two tubes direct coupled, which work in opposite phases. Automatic high speed recorders are used, one being connected at R.

intermediate stage B-III; by means of this, a signal strength varying from 30 to 50 volts is maintained on the grid of the second detector B-V. The direct-current intensity of the detector output is then about 6 milliamperes. For telephone reception, the potentiometer is so adjusted that the detector is relieved of half this load.

The R. F. amplifier uses interchangeable coils, each set covering a frequency band in the ratio of about 1:1.4; that is, the respective ranges are from 10 to 14, 14-20, 20-29 and 29-41 meters. To make the change, the covers of the shield cans are taken off; each coil is fixed to its mounting by the use of five thumbscrews. These coils are of the usual short-wave type, in number of turns.

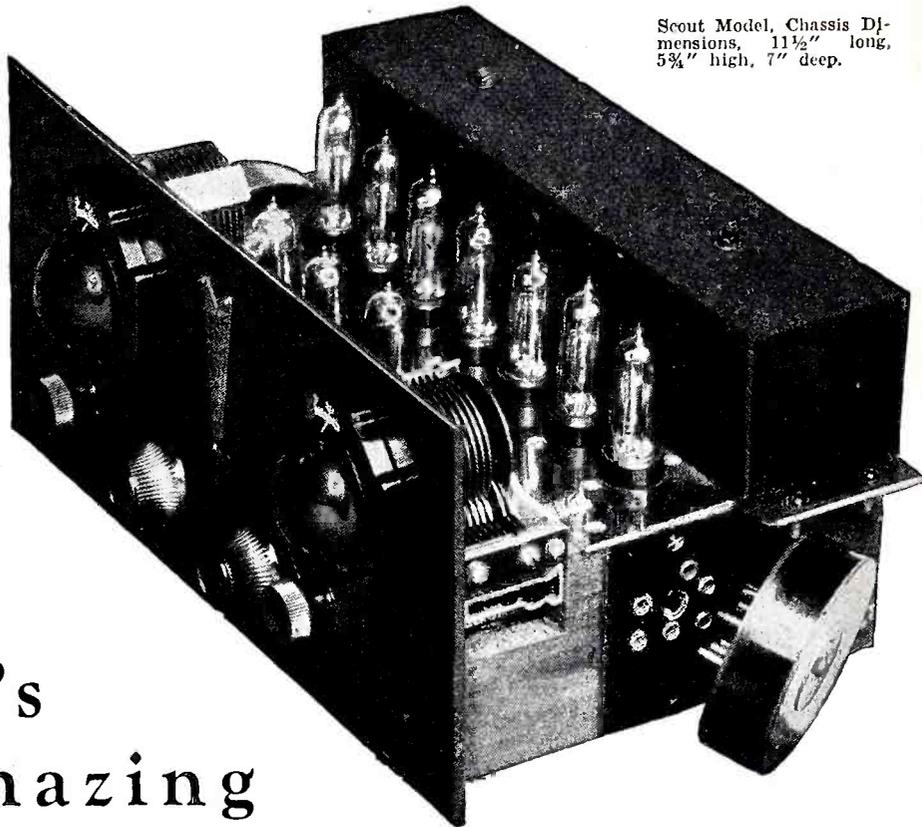From the second detector, the output is led to the relay unit E. For telephony, or picture reception, the switch "E-Bild" (picture) is used; for code, the key "E-Telegraphie" (Fig. 4). The former employs a final stage of push-pull amplification, the latter two direct-coupled tubes, which, because of their connection,



Scout Model, Chassis Dimensions, 11 1/2" long, 5 3/4" high, 7" deep.


It's
amazing
what you get on the
MERCURY "S-W" SCOUT!

NOT A KIT
The MERCURY Scout comes completely assembled ready to operate from either rectifier or batteries. Each receiver individually assembled and tested for D-X in our own laboratory.

What we say here is true fact. With the MERCURY Scout Receiver you will consistently pick up short-wave broadcast, telephone conversations and code from distant countries like Australia, Central and South America, Java, England, Holland and Russia right in your own home! This is possible only because of the way in which the MERCURY is designed, using 10 tubes in an improved Superheterodyne circuit. The MERCURY is the most powerful set made for its size and operates from either power apparatus or batteries.

Tuning Range 13—550 Meters

The MERCURY S-W Scout is a combination short-wave and broadcast receiver. Four sets of low-capacity "plug-in" coils are supplied, covering all classes of stations from 550 meters DOWN to 13 METERS! On ultra-short bands (9-22 and 22-32 meters) advantage is taken of a special split condenser arrangement allowing even spacing of stations over entire range of receiver. Separation on Standard-wave band—12 to 15 Kilocycles.

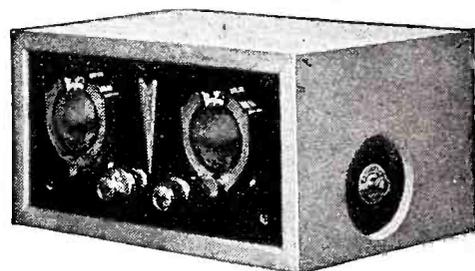

The Most Compact Short-wave and Standard Broadcast Receiver Conceivable. Cabinet Dimensions only 12 1/2"x9"x6 3/4".

Here is the Secret of the MERCURY'S Power



MERCURY "The Messenger of the Gods"

The MERCURY circuit uses TEN R215A Tubes (known as the "N" tube in the U. S. and standard equipment with United States Signal Corps) providing 4 Stages of Intermediate Frequency Amplification and 2 Stages of Audio Amplification. Current consumption of all TEN Tubes is but 1/2 ampere at approx. 5 volts. Milliamperage drain is very low, being 12 milliamps. The R215A Tube is used exclusively in MERCURY receivers, and is exceedingly rugged, having a long period of efficient operation.

Mail this Coupon—Get this Short-Wave Book FREE

THE H. M. KIPP COMPANY, Ltd., SWC-4
447-A Yonge St., Toronto, Ont., Canada.
Send me FREE your 16-page Short-wave Booklet giving prices and describing in detail the MERCURY Short-wave Receiver.
Name
Address
City..... State.....

RADIO'S GREATEST VALUES!

ALL merchandise listed is BRAND NEW and is shipped in the original, factory sealed cartons and carries the same guarantee of ABSOLUTE SATISFACTION! Due to the demand for this seasonal merchandise actually exceeding the available supply, ACT IMMEDIATELY! (We reserve the right to return remittances, as soon as the

supply of any one item is exhausted.) In most instances, our SALE PRICES ARE LOWER THAN THE ACTUAL MANUFACTURERS' COST! Join the ever swelling ranks of our 100% SATISFIED CUSTOMERS—WE HAVE YET TO RECEIVE OUR FIRST COMPLAINT.


Stewart-Warner Magnetic Chassis



New 1930 Self-Baffled Dyphonic Type. Do not confuse with earlier and cheaper models. An ultra-sensitive, loud speaker. Produced by one of radio's greatest companies. Extremely sensitive, tremendous volume without distortion or rattling. Reproduces with absolute fidelity. Speaker uses a power action unit avoiding chattering even under unusual volume. Oversize magnet. We guarantee satisfaction. Cone diameter 9 in. In factory sealed carton. Shipping weight 6 lbs.

List Price \$10.00.
YOUR SPECIAL PRICE..... \$2.75

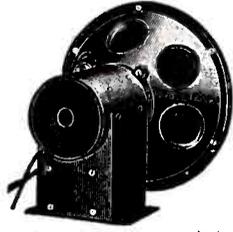Utah Dynamic A.C. Power Speaker—Model 33A



110-volt, 60-cycle A.C. light socket supply for field excitation using Westinghouse dry rectifier. 9 in. high, 9 1/2 in. wide, 7 1/2 in. deep. Speaker comes packed in wooden crate. Weight 19 lbs. It is one of the most powerful as well as best re-

9-inch cone.
producers in the market.
List Price \$50.00.
YOUR SPECIAL PRICE..... \$7.50

Peerless 15" 110 Volt D.C. Concert Dynamic Speaker



The largest and most powerful dynamic speaker made! Gives tremendous volume—deep and sonorous, as well as fully vibrant over entire musical register. Contains push-pull output transformer (adapts speaker to any receiver output!) and two D.C. field coils, one 800 ohms and the other 4,000 ohms.

Ideal for use with Webster amplifier listed below. Shipping weight 25 lbs.
List Price \$75.00.
YOUR SPECIAL PRICE..... \$16.95

R.C.A. Loud Speaker 103



A beautiful speaker in appearance. Superb in its ability to reproduce music and speech most faithfully. The frame and pedestal are mounted to resemble hand-carved oak, while the beautiful tapestry medallion conceals the mechanism and completes the decorative design of the

instrument. Magnetic unit. Corrugated cone. Height 15 in., width 13 1/2 in., depth 6 1/2 in. In factory sealed carton. Shipping weight 14 lbs. List Price \$22.50.
YOUR SPECIAL PRICE..... \$5.20

R.C.A. Filter Condenser and Output Choke No. 8346

This unit has 7 condensers and an output choke. Condenser values include four 0.5-mfs. capacities and three 2-mfs. capacities—total 8-mfs. Used in Radiola No. 60. Size 6 x 4 x 3 inches. Shipping weight 5 lbs. List Price \$16.50.
YOUR SPECIAL PRICE..... \$5.75



R.C.A. Double Filter Chokes (No. 8336)

This heavy-duty, extremely strong, double filter choke can be used for all types of filter circuits, experimental work, power amplifiers, receivers, eliminators, power packs, converted sets, etc. Known as R.C.A. replacement part for all Radiola models, particularly Nos. 33, 17 and 18. Each choke D.C. resistance, 500 ohms. Connected in parallel, these double filter chokes have a rating of 30 Henries at 160 Mills; connected in series, 60 Henries at 80 Mills. Fully shielded in heavy metal case with special insulating compound. Size 5 1/4 x 3 3/4 x 2 1/4. Shipping weight 6 lbs.



List Price \$10.05.
YOUR SPECIAL PRICE..... 95c

R.C.A. 600 Volt Replacement Condenser Block (No. 8333)

For Radiolas 18, 33 and 51. Over a half a million of these different types of Radiola receivers are on the market. Every serviceman needs these blocks, but they can of course be used for other purposes, such as experimental or converting battery sets for power. Size 3 3/4 x 2 3/4 x 3 1/2 inches. Shipping weight 4 lbs. List Price \$7.40.
YOUR SPECIAL PRICE..... \$1.45



R.C.A. Filter Cond. No. 8289

This condenser unit of 6 condensers includes two 1.0-mfs., two 3.5-mfs., a 2-mf., and a 3-mf. condenser—total capacity 14-mfs. Used in Radiola No. 17 and Radiola No. 50. Size 6 x 4 x 3 inches. Shipping weight 4 1/2 lbs. List Price \$19.20.
YOUR SPECIAL PRICE..... \$5.75

Loftin-White Direct Coupled 2-Stage Power Amplifier



A very fine phonograph or radio tuner amplifier. Gives auditorium volume! Uses one 224, one 245, one 280 tubes. 6 1/2 x 8 1/2 x 9 inches. Self-contained power supply— for 110 volt, 60 cycle, A.C. Shipping weight 20 lbs.

List Price \$35.00.
YOUR PRICE..... \$16.50

2 1/2 Volt A.C. Fil. Transformer



Two windings, both center tapped. One "lights" six 227 or six 221 2 1/2-volt tubes, and the other lights two 245 tubes (not used with Webster amplifier). Total: 14 amps. For 110 volt, 60 cycle, A.C. Size 4 1/4 x 2 5/8 x 3 1/4 inches. Shipping weight 6 lbs.

List Price \$10.00.
YOUR SPECIAL PRICE..... \$2.75

1 1/2-2 1/2-5 V. A.C. Transformer

Lights five 226, two 227 (or 224) and two 171 A.C. tubes. Permits conversion of battery sets to A.C. operation, using Raytheon type "B" eliminator. For 110 volts, 60 cycles, A.C. Shipping weight 5 lbs.
YOUR SPECIAL PRICE..... \$3.95

Dry Electrolytic Condensers



Mount in any position! Guaranteed never to blow out! Remarkably compact and very inexpensive, permitting generous use of filtering systems. The greater the mfd. capacity employed, the less A.C. hum remains. 500 volt peak rating. Ideal for all 171A - 245 power packs—use two of each capacity desired for 250 power packs (1,000 volt peak thereby assured).

Mfd.	Numb.	Diameter	Length	YOUR PRICE
1	1	3/4 in.	2 1/4 in.	28c
2	1	1 in.	2 1/4 in.	45c
4	1	1 1/2 in.	2 1/4 in.	85c
8	1	1 3/4 in.	4 1/2 in.	\$1.25
16	2	3 in.	4 1/2 in.	2.12
24	3	3 in.	4 1/2 in.	2.75
32	4	3 in.	4 1/2 in.	3.75

GUARANTEED (6 MONTHS) "REXTRON" TUBES




Sold on a 6 month FREE REPLACEMENT GUARANTEE BASIS, IF THEY PROVE UNSATISFACTORY! All tubes are carefully meter-tested before shipment, and carefully packed. Do not confuse these HIGH QUALITY TUBES with any other "low priced" tubes—"Low Price" tubes are usually "seconds."

Choice of	Choice of	Choice of	Choice of
226	201A-112A	224	222
227	200A-199UX	245	210
171A	199UV-120	280	250
			281

\$1.00 each \$1.00 each \$1.00 each \$2.95 each



Replacement Power-Pack Condenser Blocks

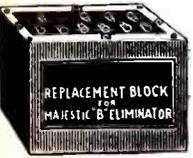

Exact duplicate, physical size, placement of connection terminals, and electrical specifications of original blocks. For Majestic 171 type receivers...
\$5.85

Shipping weight, all types, 7 lbs.

For Majestic 250 type receivers... **\$5.85**

For Majestic 245 type receivers... **\$5.85**

For Majestic "B" Eliminators... **\$2.90**

The above can be used with any similar power packs—fully guaranteed for ONE YEAR! (All other types can be supplied. Write for prices.)

245 A.C. Power Transformer



For five 224 (or five 227), two 245, one 280 A.C. tubes, OR ANY COMBINATIONS OF 2 1/2-VOLT TUBES. All secondary windings CENTER TAPPED. 600-VOLT HIGH VOLTAGE SECONDARY. 75 WATT CAPACITY. Size 5 1/4 x 4 1/4 x 3 1/4 inches. For 110 volt, 60 cycle, A.C. Shipping weight 12 lbs.

List Price \$15.00.
YOUR SPECIAL PRICE..... \$4.45

600 Volt Condenser Sections

Impregnated in pitch. Flexible lead terminals.
5 mfd. 25c 2 mfd. 40c
1 mfd. 30c 4 mfd. 60c

Freed-Eisemann Block

Contains 1-4 mfd.; 2-1 mfd.; 2-1 mfd.; 1-5 mfd.; 1-2 mfd. 5 1/4 x 3 1/2 x 2 1/2 inches. Flexible leads. Shipping weight 6 lbs. **YOUR PRICE..... \$1.95**

Webster Push-Pull Power Amplifier and "B" Supply



Uses two 226, two 210 and one 281 tubes! Super powerful PUSH - PULL amplifier. GIVES AUDITORIUM VOLUME! Also furnishes 110 volt D.C. speaker field voltage (A.C. speakers can also be used) and 15, 67, 90, 135 volts "B" current. FOR USE AS PHONOGRAPH, SPEECH AND RADIO TUNER AMPLIFIER! 16 in. long, 10 1/2 in. wide, 6 1/2 in. high. Use 2 1/2-volt A.C. filament transformer shown at left to supply "A" current to tubes in tuner, to which it will be coupled. FULLY GUARANTEED! For 110 volt, 60 cycle, A.C. Shipping weight 40 lbs. List Price \$100.00.
YOUR SPECIAL PRICE..... \$20.25


250 Push-Pull A.C. Power Transformers




Ideal for use in short wave transmitters, public address amplifier systems, super-power amplifiers, A.C. receiver power packs, etc. EMPLOYS HIGHEST GRADE MATERIALS AND LABOR—FULLY GUARANTEED! Has FOUR CENTER TAPPED secondary windings: 2 1/2 volts, 8.75 amps.—7 1/2 volts, 2 1/2 amps.—7 1/2 volts, 2 1/2 amps.—1200 volts; designed for two 281, two 250 and five to six 2 1/2-volt A.C. tubes (224's or 227's) or 226 tubes if a suitable resistance is used. FULLY SHIELDED! Soldering lug terminals. CAPACITY: 135 WATTS. Size 6 1/4 x 4 1/4 x 4 1/4 inches. For 110 volt, 60 cycle, A.C. Shipping wgt. 18 lbs. List Price \$20.00.
YOUR SPECIAL PRICE..... \$5.65

Earl Power Transformer

Make money reworking the old battery set. This power transformer used in Earl Model 22 receiver supplies "A," "B" and "C" potentials for: two '27's (or screen - grid '24's), three '26's, two '71A's and one '80 rectifier; total current output of high-voltage winding at maximum output (about 200 volts) is 80 ma. High-voltage secondary, filament winding for '27's, and for '71A's are center-tapped. May be used in any number of combinations. Suitable resistors, a couple of 4-mf. filter condensers, two 30-henry chokes and by-pass condensers complete fine power pack. Size 3 3/4 x 3 x 2 3/4 inches. 16 long leads and full wiring directions. Shipping weight 5 lbs. List Price \$7.50.
YOUR SPECIAL PRICE..... \$1.75

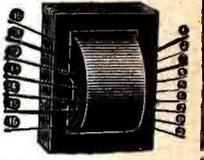

Victor Push-Pull Input-Output Unit

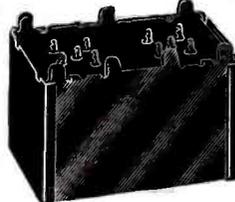

Housed in one metal case. For 171A, 245, 250 tubes. Electrostatically shielded—impregnated in dielectric sealing compound. Output matches moving coil on all dynamic speakers. Solder lug terminals. TREMENDOUS VALUE! Shipping weight 6 lbs.

YOUR PRICE..... \$2.50

A.C. Phonograph Motor

SYNCHRONOUS—revolves EXACTLY 80 turns per minute despite any voltage variations. Most compact made—only 1 1/4 in. thick—mounts in any limited space. For 110 volt, 60 cycle, A.C. Complete with turntable. Shipping wgt. 10 lbs. List Price \$15.00.
YOUR SPECIAL PRICE..... \$4.45



Pacnet "Phonovox" Pick-up



One of the best and most powerful electric phonograph pick-ups made. Balanced tone arm, unusually sensitive.

Shipping weight 7 lbs.
YOUR PRICE..... \$4.85

A-B-C Eliminators



B-C Unit Dispenses with all batteries—no new tubes required. "A" unit (bone-dry) furnishes 6 volts at 2 1/2 amperes; "B-C" unit furnishes 180 volts "B" (and all lower plate voltages) and up to 40 volts "C"—requires 280 rectifier tube. For all push-pull amp. receivers, or any type battery set. Shipping weight 12 lbs.
"A" UNIT..... \$11.45

"B-C" UNIT, with 280 tube. Shipping weight 12 lbs..... \$10.75

WE ARE A WHOLESALE HOUSE AND CANNOT ACCEPT ORDERS FOR LESS THAN \$3.00. If C. O. D. shipment is desired, please remit 20% remittance, which must accompany all orders; balance on delivery. If the full cash amount accompanies the order, you may deduct 2% discount. Send money order—check—U. S. stamps (any denominations).

Radio Trading Co.
246A Fifth Avenue
New York, N. Y.

Should you wish goods shipped by parcel post, be sure to include sufficient extra remittance for same. Any excess will be refunded. We have no catalog—order from this page; you will find special offers from time to time in this magazine. Prompt shipments will be made.

A 19 Tube S-W Receiver

(Continued from page 317)

work in opposite phases. That is to say, in one the plate current flows on the signals, and in the other on the "spaces"; so that the signal output of B-V is recorded on two sets of automatic high-speed instruments, at a uniform amplitude. This makes for the most favorable operating conditions.

Remote-Control Operation

Since the output of the second detector B-V is pulsating direct current, a local oscillator is provided at the operating (remote-control) station. If the wire lines between the receiver and operating station are not suitable for this purpose, the D. C. output must be changed to alternating current. For this purpose the special audio-frequency oscillator F (Fig. 3) is provided; this is operated by one of the tubes of the telegraph unit. The signals are then sent out over the line as an audio-frequency current of constant amplitude.

To prevent key noises from being carried over the line, the second stage of the "E-Bild" relay apparatus is constructed in push-pull. There is also provided a filter system G, so tuned that no stray modulating current can escape from the second detector B-V into the relay unit.

Telephone reception is accomplished through an audio transformer, the primary of which is connected into the plate circuit of B-V. To effect suitable equalization of the signal, an automatic volume control (Fig. 5) is connected in the plate circuit of B-V; the choke coils G (see Fig. 3) block the audio frequencies, so that only direct current passes, and the output voltage of the volume control,

which varies with the strength of the received signal, is applied to the grids of the amplifier tubes. The result is to give constant reception strength at the output of the second detector, regardless of fading in the signal.

To facilitate the operation of the receiver, and observe the characteristics of the received signal, a monitoring device D is provided; this (Fig. 3) consists of a regenerative detector and a stage of audio-frequency amplification, which can be connected ahead of the second detector B-V by a switch. This apparatus can be used also for observation of the characteristics of the first detector's output, by connecting it into the output of this tube, by another adjustment of the switch.

Batteries and Tubes Employed

The receiver contains also a filament transformer H and the grid-biasing battery I. The plate potentials are taken from batteries. Since the plate potentials of the various tubes differ, and some are specially coupled, it is necessary to use three separate batteries ("A," "B" and "C") for each tube or pair of tubes.

The tubes used (*German types*) are RE-194 types, except for B-V and in the relay apparatus, where four REN-1104 types are used. The former are battery-operated, using 0.2 ampere at 4 volts across the filaments, and drawing 5 milliamperes each at 100 volts on the plate. The latter are A. C. tubes, using 1.1 amperes at 4 volts of 50-cycle A. C. current on their heaters; and drawing 10 milliamperes with 100 volts on the plate.

Possibilities in Amateur Television

By C. H. W. NASON

(Continued from page 301)

shown in Fig. 2 is typical of the circuits employed; this is the intermediate amplifier specified above.


The photo-cell amplifier should have but one stage of screen-grid amplification, and the output tube employed in the final amplifier feeding the modulator tube, or the neon monitor, should be a '50 type. With these two exceptions the three circuits for the amplifiers are identical.

The amplifier circuit as shown has a gain-frequency characteristic essentially flat from fifteen to thirty thousand cycles, which is correct for 48-line images, since the highest frequency encountered does not exceed this figure. Where experimental arrangements require amplifiers of higher quality, this may be taken care of by the introduction of tuned chokes into the plate circuits of the various stages. For the time, these would be unnecessary complications.

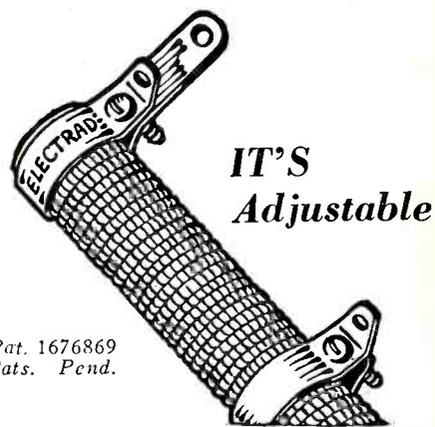Problems of Illumination

To return to the mechanical arrangements for the scanning mechanism it might be well to go into detail as to the apparatus required. If a second-hand motion-picture arc housing is available, it would serve our purpose better than anything else obtainable at a reasonable price on the open market. With the changes that have been made in motion-picture theater equipment within the past few years, such arcs should be available at a very reasonable figure. Care must be taken in ventilating the arc housing; for the gases given off by the arc are extremely injurious to health.

The scanning disc employed may be a regular receiving disc of the requisite proportions. If motion-picture projection lenses are available, they will serve admirably for the optical portion of the apparatus. A study of the dimensions of a standard projector will give some



U. S. Pat. 1676869
and Pats. Pend.

TRUVOLT

Accurate "B" and "C"
Voltages

For Short Wave Receivers

For greatest short wave efficiency—you must have correct "B" and "C" voltages. Delivering exactly the right voltages to tubes often adds many miles and greater thrills to your short wave adventures.

The sliding clip—an exclusive TRUVOLT feature—permits exact adjustment of resistance. Clips can be added as desired to make dividers.

Patented air-cooled winding assures stable operation—longer life. Made in all usual sizes.

For Quiet Control of Volume ELECTRAD Super-TONATROL

Not a scratch when you adjust the volume with the super TONATROL, Electrad's 5-Watt, long life volume control. For this better volume control is stepless. Pure silver 8-point floating contact assures positive connection with the resistance element. Shielded all-metal construction. 7 types for all usual requirements, \$2.40 to \$3.50.

Mail Coupon for
Technical Data

ELECTRAD

ELECTRAD, INC., Dept. SC-4,
175 Varick Street, New York, N. Y.

Please send technical data on TRUVOLT and Super-TONATROL. Check here for technical data on all products.

Name

Address

idea as to the positioning of the disc and lenses.

The disc would, preferably, be built so that the dimensions of each frame are those of a standard motion-picture film. That is — .720-inch by .969-inch or, roughly, three-quarters of an inch by an inch. A mask should be provided in close proximity to the disc, to limit the light transmitted to these dimensions at the scanning point. In positioning the subject the disc should be held motionless while the lenses are adjusted, until the image of the disc aperture as projected on the scanned object is sharply defined.

The photocells should be mounted on a rack quite close to the scanned scene, and no attempt should be made to accurately position the reflectors until the apparatus is functioning and an image of a geometric figure, drawn on a large piece of paper, is visible in the monitoring televisor. Then the reflectors (which may be automobile headlamp mirrors or parabolic mirrors such as are obtainable from scientific supply houses) may be adjusted for the best received image. These reflectors will operate in the same manner as the mirrors used by photographers in obtaining highlights; and some adjustment may be necessary before the maximum signal with the mini-

mum shadow is obtained. In connection with these mirrors, it might be well to mention that the chromium-plated reflectors now obtainable are less subject to breakage and are more efficient in reflecting blue light than are the old-style glass mirror.

The action of the Federal Radio Commission in opening up the 1715-2000- and 56,000-60,000-kilocycle bands to amateur television and facsimile experimentation has failed to produce the required stimulus. Without any doubt the amateur who first gets "on the air" with a creditable television signal is going to find considerable of a path beaten to his proverbial doorway. It stands to reason that the transmission of a television signal is not for the tyro. Only those who have become familiar with the operation of high-quality 'phone equipment may expect success in such an undertaking. The writer has been out of the field of amateur transmission for some years, but has spent considerable time in the development of commercial television systems; and he has employed an arrangement such as that shown with considerable success.

No attempt has been made here to show structural details as the sole purpose of this paper is to stimulate a degree of interest in the problem, sufficient

to warrant the work which would be necessary in preparing a series of articles covering the entire problem.

It may be noted that the lower frequency band, mentioned above, borders on that used by the commercial television services. Receivers constructed or purchased for the reception of the commercial transmissions will be capable of receiving the amateurs also. Your attempts, then, will reach, not a limited few amateurs, but the entire television audience within the range of your equipment.

Short - Wave Radiophone Keeps Fireboat In Touch With Shore

(Continued from page 267)

it distinctly. The shore station has a power output of 1 kilowatt; the receiving set is a standard aircraft type, having three stages of screen grid R.F. amplification. A microphone and headphone sets form part of the equipment.

The fireboat's radiophone transmitter is of the aircraft type and has a power rating of 100 watts. For receiving purposes aboard the fireboat, headphones are supplied as well as a loud speaker.

Special

Combination offer

REGULAR PRICE \$3.00

OUR SPECIAL PRICE 2.00

SAVING ~ ~ \$1.00

"THEORY OF RADIO COMMUNICATION"

By John T. Filgate

Formerly Instructor at U. S. Army Signal School

Published with the approval of U. S. War Department, this is the first public printing of the officers' radio manual used by U. S. Army Signal Corps. A splendid technical textbook for advanced Radio Amateurs. 250 pages, 200 illustrations.

AND TWO YEARS' SUBSCRIPTION TO

RADIO DESIGN

OFFICIAL ORGAN OF THE RADIO INTERNATIONAL GUILD


which also includes membership in the RADIO INTERNATIONAL GUILD "Theory of Radio Communication" sells regularly for \$2.00 alone. Now you can have it together with two years' subscription to "Radio Design" all for \$2.00.

MAIL THIS COUPON WITH \$2.00

RADIO DESIGN PUBLISHING CO., Inc., Lawrence, Massachusetts, U. S. A.

Enclosed is remittance of \$2.00 for which please send me "Theory of Radio Communication". Also credit me with 2 years' subscription to Radio Design and 2 years membership in the Radio International Guild.

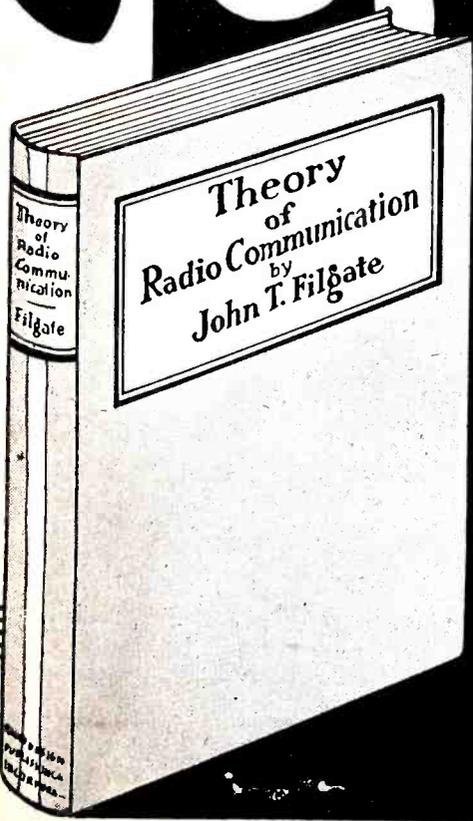NAME.....ADDRESS.....
CITY.....STATE.....



THERE ARE A LIMITED NUMBER OF THESE BOOKS AVAILABLE. YOU MUST ACT QUICKLY IF YOU WISH TO TAKE ADVANTAGE OF THIS WONDERFUL OPPORTUNITY.

An 85 Meter Phone Transmitter

By R. WM. TANNER, WSAD

(Continued from page 293)

be wound first with 5 turns, spaced slightly. When this is done, start the plate coil 1 inch from the last turn of the antenna coil, and continue space-winding for 22 turns. A tap is taken off at the exact center for connection to the positive of the high voltage. The other antenna coil, having the same number of turns as the first, is wound 1 inch from the plate coil. The coupling between each antenna coil and the plate coil must be exactly the same, or the push-pull amplifier will be unbalanced, with one tube supplying most of the energy.

The leads are soldered to lugs which are fastened to the form with 1/2-inch, 8/32 machine-screws. If the turns have a tendency to run together, a little collodion applied now and then will keep them in their proper position. Details of this unit are shown in Fig. 2.

An engineer would, in all probability, hold up his hands in horror at the use of fixed one-inch coupling. However, it has been worked out in practice that with such small coil diameters one-inch coupling is sufficient. Therefore, why not make it fixed and simplify the adjustment and operation processes?

The plate inductance is tuned by means of an .0001-mf. midget condenser (C1). The neutralizing condensers (NC) have each a maximum capacity of .000025-mf. An .001-mf. mica bypass condenser (C2) is connected between the "B+" and the center of the filament resistor.

The antenna tuning condenser (C) is of the receiving type, with a capacity of .0005-mf. maximum. Although not absolutely necessary, an 0-to-1 amp. hot-wire or thermocouple ammeter (A) may be placed in the antenna lead to indicate resonance.

The center-tapped resistors (R) shunted across the filaments are 60-ohm, and bypassed with .001-mf. (C2) and .002-mf. (C7) fixed condensers.

Audio (Speech) Amplifier

Now we come to the audio amplifier, upon which the quality of the transmitted speech depends almost entirely. The microphone and a 4.5-volt battery are connected directly across a 200-ohm potentiometer (R5) employed as a gain control. The contact lever goes to one side of the primary of the modulation transformer (M.T.). The secondary, across which is a 250,000-ohm grid-leak-type resistor (R4), feeds the grid of the '26 tube. A negative bias is supplied through a 1,500-ohm resistor (R7) bypassed with a 1-mf. condenser (C8). A voltage of 135 to 180 is applied to the plate.

The audio transformer (AFT) is a high-quality type, with a 3 1/2:1 ratio; this furnishes voltage sufficient to swing the grid of the '71A stage to full output.

A Special — While They Last!

\$100.00 PHOTOPHONE




12-Inch
Dynamic

SPEAKERS

Brand New
in Original Cases
Order Today

\$15

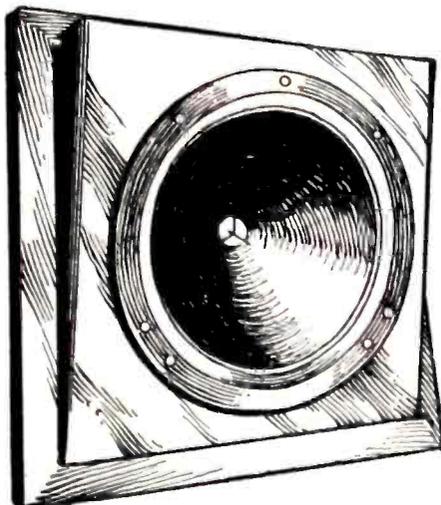

Never before was such an astounding value offered. Every carnival owner, motion picture house, theatre, church, fair, American Legion Post, club, sound engineers and radio experimenters will want one. Only limited number.

12-inch Dynamic Field Supply; 110 volts D. C.; Field Resistance, 1000 Ohms; Voice Coil, 8 Ohms; Mountings, Steel Angle Frame. For adaptation to A.C. operations. \$6.50 additional.

M. & H. Sporting Goods Co.

512 Market Street, Philadelphia

Send for Catalog.

Terms: 25% with order; balance C. O. D. or Sight Draft. Specify Express or Freight.

Deepest Cut Prices!

- .00035 mfd. single Masterpiece variable condenser; brass plates; shaft extending front and rear. Built-in brackets permit subpanel mounting. Order Cat. 3-SIN @ \$0.30
- .00035 mfd. double (two-gang) Masterpiece variable condenser; brass plates; shaft extending at front only. Order Cat. 3-DOU @ .60
- .00015 mfd. tuning condenser for short waves. Order Cat. SWC-15 @ .60
- .00025 mfd. tuning condenser for regeneration in short-wave circuits. Order Cat. SWC-25 @ .60
- Flexible insulated coupler for uniting coil or condenser shafts of 1/4-inch diameter. Provides option of insulated circuits on both sides. Order Cat. FL-C @ .26
- Brach relay, for making the switch in a set with battery-operated filaments turn on the trickle charger when set is turned off, and turn charger off when set is turned on; also will make set switch turn B eliminator off when set is turned off. Order Cat. BR-REL @ .69
- Antenna coil for .0005 mfd. Order Cat. ANT-5 @ .45
- Three-circuit tuner for .0005 mfd. Order Cat. 3-CT-5 @ .75
- Antenna coil for .00035 mfd. Order Cat. ANT-3 @ .47
- Three-circuit tuner for .00035 mfd. Order Cat. 3-CT-3 @ .79
- Screen grid RF transformer, for .0005 mfd., to couple screen grid tube to next tube. Order Cat. SG-5 @ .45
- Screen grid RF transformer, for .00035 mfd., to couple screen grid tube to next tube. Order Cat. SG-3 @ .47
- AC electric motor and turntable, for playing phonograph records. A synchronous motor. 60 cycles; 80 turntable revolutions per minute. Order Cat. SYN-M @ 4.45
- A-battery switch (Benjamin). Order Cat. A-SW @ .13
- A-eliminator or dynamic speaker transformer (Jefferson), 20-volt secondary. Will pass 2 1/4 amps. Order Cat. 20-V-T @ .49
- 30-henry shielded choke for B supply filtration or filtered speaker output. Will stand 100 ma. Order Cat. OS-30IIS @ 1.65
- 60-henry shielded center-tapped choke (30 each side of center) for B supply filtration or filtered output of push-pull tubes. Will stand 100 ma. Order Cat. OS-60ICT @ 1.95

GUARANTY RADIO GOODS CO.

143 WEST 45TH STREET

(Just East of Broadway)

NEW YORK, N. Y.

EVERY new issue of SHORT WAVE CRAFT brings out the most important developments in short wave radio—both American and European improvements. Contributions of renowned short wave experts are found among the pages of every issue of SHORT WAVE CRAFT.

"Official" RADIO SERVICE MANUAL

and Complete Directory of all Commercial Wiring Diagrams

IN LOOSE-LEAF FLEXIBLE, LEATHERETTE BINDER

OVER 1,000 ILLUSTRATIONS, DIAGRAMS, Etc.

352 PAGES 9" x 12"
Weight 2½ lbs.

HUGO GERNSBACK, *Editor*
CLYDE FITCH, *Managing Editor*

Prepared Especially for the Radio Service Man!

NEVER in the history of radio has there ever been published a service manual, so complete, as this new OFFICIAL RADIO SERVICE MANUAL. It is a veritable encyclopedia of service information—worth several times its price. It is invaluable not only for the Service Man, but for everyone interested in radio.

\$3.50 A COPY

There has been collected for this manual wiring diagrams and data of nearly every commercial set, of which there is any available record, manufactured since 1927, and many earlier ones.


The OFFICIAL RADIO SERVICE MANUAL is made in loose-leaf form in a handsome, durable, flexible leatherette binder and contains 352 pages of the large size, 9 x 12.

Additional service data for new receivers, as they appear on the market, will be published and supplied at a trifling cost so that the MANUAL may be kept up-to-date at all times. But that is not all.

SERVICE INFORMATION

The OFFICIAL RADIO SERVICE MANUAL contains also a most comprehensive instruction course for the radio Service Man, giving practical information from every angle on how to service the set. Here are only a small number of the articles mentioned:

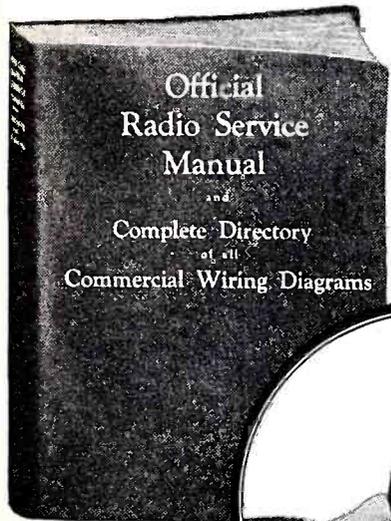- Amplifiers (Audio and Radio)
- Automotive Radio
- Antennas
- Condensers
- Detectors
- Eliminators
- Meters
- Power Supply Systems
- Radio Phonograph Equipment
- Resistors
- Short-Wave Sets
- Speakers
- Tubes



MAIL COUPON TODAY—

GERNSBACK PUBLICATIONS, Inc., SWC-12
96-98 Park Place, New York, N. Y.

As per your special offer, I enclose herewith \$3.50 for which you are to send me postpaid, one copy of the OFFICIAL RADIO SERVICE MANUAL.

Name

Address

City..... State.....

You simply cannot realize what a tremendous work this is until you have held a copy in your hands and have gone through its 352 pages.

Over 1,000 illustrations, diagrams, etc.

WHAT THEY SAY

NOTHING CAN COMPARE WITH IT
I have received my copy of the OFFICIAL RADIO SERVICE MANUAL. I expected it would be good for I think you know as much as any of them what the average radio man wants, but I'll wager not very many expected to receive a book comparable to this one. I think you deserve a lot of credit for being the first to put out a real service manual that the amateur or professional can make good everyday use of. It's a good practical book and one that every service man will be proud of.—E. D. HANA, Haslett, Mich.

BEST BOOK IN THE FIELD
I received your book OFFICIAL RADIO SERVICE MANUAL and I find it is as yet the best book I have found in this field of radio. You are well justified in that this is the peer of service manuals. I wish you all the success possible in the publishing of future books on radio which are sure of great necessity.—WILLIAM R. BROWN, Brown Radio Service, 1010 Buckingham Street, Toledo, Ohio.

WORTH A GREAT DEAL MORE
Received your copy of OFFICIAL RADIO SERVICE MANUAL and am greatly pleased with same. It is worth a great deal more than it costs.—HAROLD AIGUIER, 41 Rutland Ave., Arlington, N. J.

"SHE IS A BIRD"
Just to let you know we received my MANUAL this A.M. and—OH BOY!! She is sure a BIRD! You sure did strut your stuff, AND HOW!!—V. H. HERNDON, Herndon's Radio Shop, Odon, Indiana.

EXTREMELY PLEASED
I acknowledge receipt of the OFFICIAL RADIO SERVICE MANUAL and I am extremely pleased with it.—EDW. JOHN SMITH, 337 E. 26th St., Erie, Penna.

A VERITABLE GOLD MINE
I received the OFFICIAL RADIO SERVICE MANUAL. I am well pleased. It is a veritable gold mine for the Service Man.—EUGENE BINFORD, Arkansas City, Kansas.

MAGNIFIQUE
Received my copy of the OFFICIAL RADIO SERVICE MANUAL this A.M. "She is what you call him? Magnifique! Exquisite!" A timely aid for the troubled sets. Thanks.—E. BOICE, 1118 W. Dauphin, Philadelphia, Pa.

FINEST THING
Just received the RADIO MANUAL. It sure is the finest thing I have seen.—E. J. SCHWARM, 405 Eddy Road, Cleveland, Ohio.

IT ASTOUNDED THEM
Everywhere I have exhibited the MANUAL it has taken the boys by surprise and its completeness has astounded them. For instance, Saturday morning last I had occasion to run into the service plant of the Madenzie Radio Corp., New York District Distributors for Zenith Radio, in connection with replacement units, and when I showed the Service Manager, Mr. Wandelt, the MANUAL, he was agreeably surprised and called the men to see the work. Delightedly yours, and always a booster for Gernsback Publications, of which I read practically all, and study them.—IRA C. HALDERMAN, 44 Leroy Place, Ridgewood, N. J.

An 85 Meter Phone Transmitter

(Continued from page 293)

The 2,000-ohm resistor (R6) biases the grid of the '71A; this is also bypassed with a 1-mf. condenser (C8).

Either a transformer or a choke-condenser combination may be used in the output of the audio amplifier, to apply the amplified speech currents to the modulated power amplifier; but, as an extremely high voltage is not necessary, better quality will result with the choke-condenser arrangement.

Two chokes will be needed: one (A.F.C.1) with an inductance of 30 henries at 20 ma. for the plate circuit of the '71A audio stage, and one (A.F.C.) of 50 to 100 henries (low current) for the grid circuit of the modulated power amplifier. The coupling condenser (C9) cannot be too large, or the higher audio frequencies will be cut off; a capacity of approximately .01-mf. will suffice.

The grid choke is connected from the "B—" to the common lead to the grid R.F. chokes, as clearly shown in Fig. 1. The biasing voltage for the modulated power amplifier is rather critical, and is supplied through a 4,000-ohm adjustable resistor (R3) bypassed with a 1-mf. condenser (C8). Battery bias is preferable with a potentiometer for fine adjustment, if cost is not a consideration.

Power Supply

Very little will be said about this, for some constructors may prefer to use a manufactured unit, which costs practically the same as one of home construction. The high-voltage winding should supply 700 volts, center-tapped to the '80 rectifier. As the total current drain is about 100 ma., the filter chokes must be able to carry this amount. The power transformer, usually, has a 2.5- and a 5-volt winding, which can be used for the R.F. filaments. Another 5-volt winding is needed for the '71A, and should be supplied from a separate transformer which also gives 1.5 volts for the '26 tube.

Mounting and Wiring

The diagram in Fig. 3 shows the layout of parts for the oscillator, frequency-doubler and modulated power amplifier. All R.F. chokes, blocking and bypass condensers, grid leak, etc., are placed underneath the baseboard. The two biasing resistors (R2 and R3) are on top where they are readily accessible. A 1½-inch wooden baseboard, 20 x 10 inches, will just about hold all the parts without overcrowding. The three tank condensers (C1, C4 and C6) are mounted on a bakelite panel 6 x 20 inches. The radiation meter, if one is used, may also be placed on this panel. Vernier dials are not necessary; plain ones serve the purpose just as well.

It is advisable first to run all wires carrying R.F. currents, in order to keep them as short and direct as possible. The connecting wires in both halves of the push-pull amplifier must be of equal length.

The layout of parts for the A.F. unit is shown at the right; the baseboard is 10 x 6 inches. As in the R.F. unit, the resistors and bypass condensers are placed underneath. Both baseboards are mounted on bakelite sub-panel brackets, 2 inches high.

Adjustment and Operation

The initial adjustments of this transmitter are rather complicated, but if they are made in accordance with the following directions no trouble should be experienced. Before going into details it is well to call attention to the fact that the unusual voltages required for the plates of the various tubes are not generally available from manufactured "B" substitutes. It is advisable to connect two 10,000-ohm, 75-watt "Truvolt" resistors in series across the output terminals, and disregard the regular taps. Three sliders will be needed to supply the intermediate voltages. The sliders should be bypassed to the "B—" by 0.5-mf. condensers.

First connect an 0-to-100-ma. meter in the "B+" lead to the oscillator, and light the filaments of all tubes except the audio amplifier. (Leave all "B+" but the oscillator disconnected.) Place the oscillator filament tap on the sixth turn on L3, and vary C6 to the desired wave (twice the working wave) as determined by means of a wavemeter. Now listen-in on an oscillating receiver for one of the many C.W. "squeals" that will be found in the 80-meter band. Reduce the number of turns between grid and filament until the squeal has the least amount of A.C. modulation. Under these conditions the oscillator plate current will be from 10 to 12 ma.

Now set the slider on R2 to nearly full resistance, and connect the "B+" together with the milliammeter to the frequency-doubler. Tune C4 slowly, until the plate current takes a pronounced dip downward and then increases as C4 is increased. The center of this dip indicates resonance and is the correct adjustment of C4.

Remove the milliammeter and place it in the "B+" lead to the modulated power amplifier. Do not connect the high voltage at this time, but set R3 at about two-thirds its resistance, and couple three turns of bell wire in series with a 2.5-volt flashlight bulb to one end of L1. Tune C1 so that the bulb lights brightest, and then vary both neutralizing condensers *together* until the light goes out. Readjust C1 slightly. If the bulb shows no signs of light, the tubes are completely neutralized, and the high voltage may now be connected and C1 tuned for the plate current dip, exactly as done with the frequency-doubler. It is well to use a low voltage on this stage when making initial adjustments, for detuning C1 may cause the tubes to draw excessive plate current.

The antenna and counterpoise may now be connected. Each should have a

Short-Wave

TRANSMITTERS
and
RECEIVERS

Absolutely

Require the
BEST CONDENSERS

That is why

FLECHTHEIM
SUPERIOR CONDENSERS
Are Used Exclusively

BY AN

EVER

INCREASING
NUMBER

Of AMATEURS
EXPERIMENTERS
TECHNICIANS
SERVICE MEN, etc.

"Over 50% of the Broadcasting Stations in the U. S. A.

Use *Flechtheim Superior Condensers*"



250 v.
to
5000 v.

Type VM 200, 2 Mfd., 5000-v. D.C.
(3300 rms. RAC)

Catalog No. 22 Sent on Request

A. M. FLECHTHEIM & CO.,
Inc.

132 Liberty St. New York, N. Y.

SEND FOR NEW 1931

Radio and Electrical
Wholesale Trade Catalog

IT IS FREE

Royal-Eastern's New 1931 General Wholesale Trade Catalog has been compiled to place before you a most comprehensive line of high-grade nationally advertised merchandise, at lowest wholesale prices. Every worth-while radio, electrical and sporting goods item is featured at lowest wholesale prices. Being the largest radio and electrical mail order house in the East, we can serve you best. We buy no seconds. We have no job lots. Only fresh and clean products in original factory cartons. Same day shipping service—and, Royal-Eastern never substitutes. With our large warehouses and a background of thirty-three years of service to the trade, we are in a position to render the same service to you as has been our custom in the past. Official authorized headquarters for New Hammarlund HiQ31, Silver-Marshall and Pilot Products.

BEST CREDIT RATING!

Our Banking Affiliations and Depositories

The National City Bank of New York, N. Y.
Irving Trust Co., New York, N. Y.
Brooklyn National Bank, Brooklyn, N. Y.
Bank of Manhattan, Long Island City, N. Y.
Huguenot Trust Co., New Rochelle, N. Y.

33 Years Service to the Trade | Send for Catalog Today! | 33 Years Service to the Trade
IT'S FREE!

Royal-Eastern Electrical
Supply Company

15 West 21st Street New York, N. Y.
BRANCH WAREHOUSES:
Brooklyn, N. Y. Long Island City, N. Y.
New Rochelle, N. Y.

WORLD-WIDE SHORT WAVE RECEIVER
Span the World with this Set!

ONLY \$6.45

A new radio thrill for you! Listen in DIRECT to London, Paris, Berlin, Buenos Aires and other broadcasting stations throughout the world via short waves. Enjoy unique foreign programs from strange lands. Your ordinary receiver cannot tune in these low wave stations. WORLD-WIDE RECEIVER gets 14 to 550 meter stations with surprising clarity. SEND NO MONEY! Just write your name and address on a postcard and ask us to send you this wonderful guaranteed short wave set. Pay postman \$6.45 plus a small delivery charge. All orders West of the Rockies must be accompanied by \$1.00 deposit. Foreign countries must remit in full. Write today!

CHAS. HOODWIN CO.

Dept. A-17

4240 LINCOLN AVE. CHICAGO

NUBOR
FLASHES

We have so many good items at such attractive prices in Standard Radio Parts, that even a full page advertisement could not do them justice, therefore send for our Big 16 page catalog and pick the winners.

NUBOR WHOLESALERS

Dept. C.

12 Warren St. New York, N. Y.

length of approximately 65 feet, and the antenna should, of course, be as high as possible. The condenser C is varied for maximum radiation; as it is tuned to resonance, the power amplifier's plate current will increase.

Now readjust R2, C6, C4, C1 and C for greatest output. At this time the audio unit may be connected. With the microphone idle, decrease the resistance of R3 until the increased antenna current with additional reduction is negligible. Then set the bias at a value which gives half the plate current obtained at the point of maximum antenna current. Under these conditions, modulation will be symmetrical and 100 per cent. on the peaks. It will be found that the plate current is around 40 ma., depending upon the exact value of plate voltage.

The microphone may now be spoken into with the assurance that good quality will be transmitted.

Parts List

- C—.0005-mf. antenna tuning condenser;
C1—.0001-mf. midget amplifier tuning condenser;
C2—.001-mf. bypass condensers;
C3—.00025-mf. coupling condenser;
C4—.0001-mf. midget "tank" condenser;
C5—.0001-mf. coupling condenser;
C6—.0005-mf. oscillator tuning condenser (fixed) and .0001-mf. midget;
C7—.002-mf. bypass condensers;
C8—1-mf. bypass condensers;
C9—.01-mf. condenser;
R—60-ohm filament resistors;
R1—5,000-ohm grid leak;
R2—2,250-ohm, 25-watt "Truvolt" frequency-doubling biasing resistor;
R3—4,000-ohm, 75-watt "Truvolt" M.P.A. biasing resistor;
R4—250,000-ohm grid-leak type resistor;
R5—200-ohm gain control;
R6—2,000-ohm biasing resistor;
R7—1,500-ohm biasing resistor;
RFC—R.F. chokes (see text);
RFC1—R.F. chokes (see text);
RFC2—R.F. chokes (see text);
AFC—50-henry grid choke;
AFC1—30-henry plate choke;
AFT—Silver-Marshall type 255 (3½-1) audio transformer;
MT—Silver-Marshall type 255M modulation transformer;
Tubes, sockets and miscellaneous hardware.

Converting Your Broadcast Receiver for S-W Reception

By McMURDO SILVER

(Continued from page 275)

vernier or trimmer adjustment rather than as a regular tuning control. The oscillator circuit, however, is extremely sharp; employing a somewhat similar coil to that of the first detector, it is tuned by a .00014-mf. condenser controlled by a vernier dial. A '27 tube is the oscillator, and power supply for both tubes of the converter is obtained from a small, self-contained power unit.

While it might be feasible to obtain all power for the converter directly from the receiver by which it is employed, this would involve pulling leads out of the

Leading Circuits
for Short Waves

NATIONAL 5-TUBE THRILL BOX—A remarkably sensitive short-wave outfit, noted for reception of foreign stations. (Front view illustrated above.) This outfit costs money, but the results are there. It is so good it is standard equipment on planes of several passenger air lines, besides being the standby of amateurs and custom set builders. If you've an appetite for short waves, the Thrill Box is your meat. Uses 224 RF, 221 detector, 227 first audio, 227 push-pull second audio. A separate A and B supply is required. See below. Standard set of four pairs of coils included (21.2 to 2.61 megacycles). Humless operation, even on earphones. Single tuning control. No grunting, no backlash, no hand capacity. Product of National Co., makers of the finest parts. Order Cat. AC-SW-5, list price, less tubes, less B supply, \$79.50; net price\$46.74

WIRED MODEL AC THRILL BOX—Order Cat. AC-SW-5-W. Tested for performance, using foreign stations only. List price, \$89.50, less tubes, less power unit; net price\$52.62

NATIONAL SW POWER UNIT—Furnishes heater voltage and B voltage for the AC Thrill Box. Uses 280 rectifier. Comes in wired form only. Licensed under RCA patents. Order Cat. 5880, list price, less tube, \$34.50; net price\$20.28

BATTERY MODEL THRILL BOX—This uses the new 2-volt tubes; two 232 screen grid, three 230 and one 231, in same general circuit. Order Cat. DC-SW-5, list price, \$75; net price\$44.10


WIRED MODEL BATTERY THRILL BOX—Order Cat. DC-SW-5-W. Tested for performance, using foreign stations only. List price, \$85, less tubes; net price.....\$49.96

HAMMARLUND SW TUNER—For one stage of RF and detector; battery operation; uses two 230 tubes or any other pair of battery-operated general purpose tubes. Coils cover 15 to 105 meters. Order Cat. SWR-2, list price \$36, less tubes; net price.....\$21.15

Guaranty Radio Goods Co.

143 West 45th Street
New York, N. Y.

BACK NUMBERS
Of All Issues of Short Wave Craft
Available at 50 Cents each. Prepaid

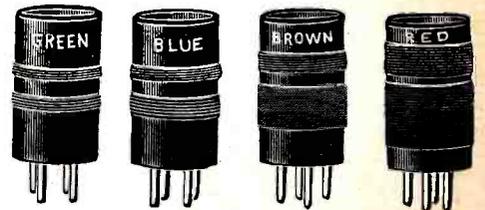New Style
SHORT WAVE PLUG-IN COILS

THESE new style coils are moulded in genuine bakelite to fit UX sockets. Coils come in different colors bakelite, as indicated in illustration, for quick identification. Smallest and most efficient coils produced as yet. Wound with special wire to avoid all possible losses.

Set includes four coils to cover range from 15 to 210 meters when used with a .0001 midget condenser. Just plug coil into UX socket.

Every radio amateur, every experimenter, requires a set of these fine coils. Sizes: 2¼ in. overall by 1¼ in. Coil dimension: 2½ x 1¼ in.

List Price, \$3.75 per set of 4 coils.

YOUR SPECIAL PRICE, \$1.90
POSTPAID.....

RADIO TRADING CO.

246 A Fifth Avenue New York City

latter, and thereby complicate the connection of the converter to the set; it has been felt, therefore, that it is wiser to incorporate a complete power supply unit directly in the converter for simplicity and, particularly, in view of its low cost.


A '26 tube is used as a rectifier, being fed by a small transformer which also supplies filament current for the '24 detector and '27 oscillator. Filtration is provided by one high-inductance choke and two 4-mf. dry-electrolytic, semi-self-healing condensers.

The whole construction and design of the converter is so ridiculously simple that little comment is necessary; the circuit diagram is self-explanatory, as are the photographs. The antenna is coupled to the first detector through a small trimmer-type condenser which, upon installation, is initially set to provide the most satisfactory results; as also is the similar small trimmer condenser used to couple the oscillator to first detector grid circuit. The first detector is coupled to the antenna binding post of the broadcast receiver through a 300,000-ohm resistance and a .0001-mf. fixed condenser.

How to Connect Converter to Your B.C. Set

To install the converter, it is necessary only to insert its power-supply plug into a 110-volt, 50- or 60-cycle light socket, remove the antenna lead from the receiver and connect it to the antenna post of the converter; then connect the two posts on the converter to the antenna and ground posts of the receiver. To disconnect the converter, it is necessary simply to shift the antenna lead from the converter back to the receiver's antenna post. In operation, the receiver's volume control is used exclusively; since it is contemplated that the converter will be placed on top of, or beside, the regular broadcast receiver which, in turn, is tuned to some low frequency (around 600 kc.) on which normally no station can be heard. If, when the converter is used, the receiver tuning dial is always set at exactly the same position, the oscillator dial on the converter may be logged definitely; which will be, of course, a great convenience.

In actual operation, it has been found that the results obtained from this converter, in conjunction with a good broadcast receiver, were distinctly superior to those obtained from any short-wave receiver which it has been the writer's privilege to play with—including a number of short-wave superheterodynes. The selectivity is extremely satisfactory, indeed, and the television problem (image-frequency selectivity) is not troublesome. This is due, first, to the use of a very high intermediate frequency—that to which the broadcast receiver is tuned, which generally places the image-frequency 1,000 kc., or further away from the wanted station; coupled with the fact that the short-wave channels upon which the converter will be operated, are not as crowded as are the American broadcast channels. Consequently the possi-

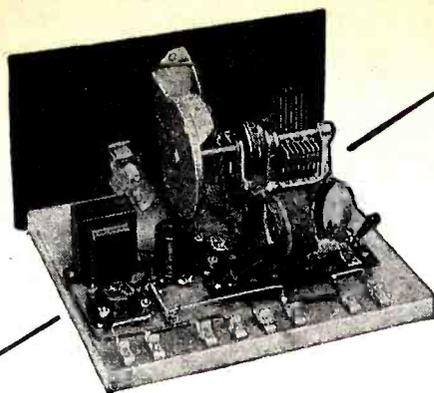

The IDEAL RECEIVER for SHORT WAVES

A remarkably efficient two-tube distance getter, with regenerative detector and one audio-stage. Easily constructed from the Hammarlund kit, containing all parts, as illustrated. Covers the range of 15 to 105 meters.

It includes the famous Hammarlund Drum Dial, the new Hammarlund wide-space short-wave "Midline" Condenser and the improved Hammarlund Space-Wound Plug-in Coils. Interchangeable coils are available for higher wave bands. Makes a wonderful tuning unit for the short-wave experimenter.

HAMMARLUND MANUFACTURING CO.
424-438 West 33rd Street, New York

For Better Radio
Hammarlund
PRECISION
PRODUCTS

Write Department SW-4 for details of
Hammarlund Short-Wave Equipment

Right Now!!

Send for Our

NEWEST CATALOG

Largest Assortment and Biggest Bargains in
RADIO SETS AND PARTS

All Merchandise at Wholesale!

S. HAMMER RADIO COMPANY

142 Liberty Street, N. Y. City Dept. G Hitchcock 1152

**KEEP
POSTED
ON RADIO
PROGRESS**

Fill in and mail the coupon and 50c. and get your first copy of RADIO DESIGN, membership button, identification card and lithographed membership certificate.

Join the Radio International Guild

... the international organization of 60,000 members which exchanges information, kinks and tips invaluable to experimenters, custom set builders and service men. Also—personal news of individual members together with short wave news and gossip from all over the world.

Members receive RADIO DESIGN—official organ of the guild, in which prominent radio writers tell of the progress being made in SHORT WAVES, TELEVISION and other new and interesting phases relating to the various applications of radio.

Four big issues yearly. Articles on new circuits and receivers with illustrations and working diagrams. The radio news of the world in interesting form.

RADIO INTERNATIONAL GUILD - Box SW-12 LAWRENCE, MASS.
Enclosed find 50 cents for which please enroll me as a member of the Radio International Guild and send me the button and Radio Design for one year.

Name _____
Address _____

Book Prices Slashed!

AS LONG AS THE SUPPLY LASTS—

Sent Prepaid
to You

35c the Copy 3 for \$1.00

All of these books sold for 50c. a copy up to now. But in order to clean our stock we are selling them at 35c. a copy AS LONG AS THE SUPPLY LASTS.

If you ever wanted a fine book at a big bargain, here is your last chance.

NO FICTION


POPULAR BOOKS aim to educate you and entertain. They never contain fiction. They are all on SPECIAL SUBJECTS. Each book is compiled by EXPERTS. Every book contains far more matter than the usual \$2.00 book, and gives you a wealth of material for the price of a high-class magazine.

All books are uniform in size—the large (9 x 12-inch) page which is a favorite with readers; heavy and durable paper only is used, and the type is selected for its readability. The covers are always in four colors and varnished to keep from soiling.


Large 9" x 12" in size—4 colored cover—100 pages per book

The majority of POPULAR BOOKS are profusely illustrated. **FILL IN THE COUPON AND ORDER TODAY.** We accept money orders, U. S. Stamps or cash.

POPULAR BOOK CORP.
93L PARK PLACE NEW YORK

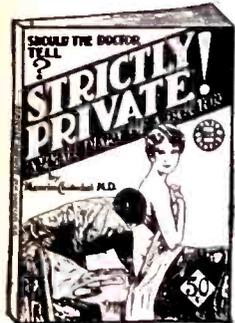

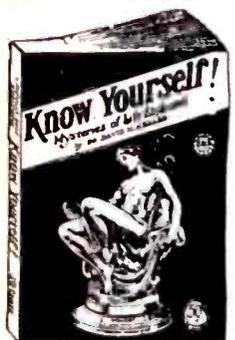
No. 1
Here you will read the interesting and unusual experiences that happen behind the closed doors of a doctor's inner office. Written in diary form by Maurice Chidekel, M.D. Unbelievable but true.




No. 5
Dr. David H. Keller, M.D., discusses such important topics as Sexual Physiology of the Young Man, Love and Marriage, The Normal Sex Life, Psychology of the Young Girl, Companionate Marriage and dozens of other important topics from a scientific standpoint. Contains the best and most advanced thoughts on Life and Reproduction of interest to everyone — enlightenment on every page.



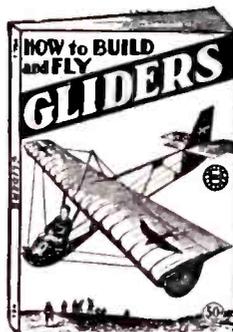
No. 4
So few people today know the schemes introduced by the racketeers—and the astounding success with which they extract tremendous sums of money from people. Only government inspectors and agents are familiar with their methods of extortion—the baffling ways of the racketeers. In RACKETEERS dozens of outstanding schemes and the names of the leaders are exposed.



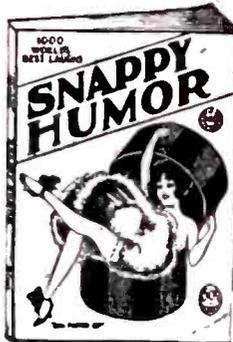No. 2
The first complete book in the English language. Gliding is a sport that can be practiced by everyone. It is the easiest, quickest and cheapest means of learning to fly. This book enables you to build and fly your own glider with little work and small expense. Written by expert gliders.



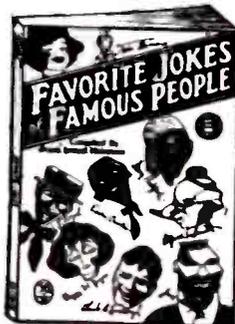No. 3
SNAPPY HUMOR is a collection of the world's best wit, culled from periodicals of every language. It contains the cream of the world's mirth, French, German, English, etc., etc., with rich and snappy illustrations, also many varied stories. Over 750 Original Illustrations. Plenty of laughs — thrills on every page.



No. 6
READ 'EM AND LAUGH—The pet story of each of a hundred world-famous celebrities, personally interviewed by the author. Each person is introduced by a comic introduction followed by an uproarious caricature by the author.

bility of image-frequency interference is much less than on a superheterodyne operating in the broadcast band.

This short-wave converter may be employed with a broadcast band superheterodyne receiver, in which case the resultant combination might be termed "double-suping," due to the fact that two intermediate frequencies are employed—one in the broadcast band, that to which the superheterodyne broadcast receiver would be initially tuned, and the other the superheterodyne's L.F. amplifier.

How to Hear C. W. Signals

When the converter is adjusted, in conjunction with the broadcast receiver, for reception of short-wave telephone or broadcast signals, it does not permit the reception of short-wave C.W. signals. It is a very simple matter, however, to adapt it to C.W. telegraph reception by the simple process of so tuning the broadcast receiver, with which the converter is used, that it is set very close to a local broadcast station; which is then used as a local oscillator to heterodyne the short-wave telegraph signals. It is assumed, however, that the broadcast receiver is sufficiently sensitive to pick up at least one high-wave local station, either directly upon its coils or on the small length of connecting wire between its antenna post and the converter. Of course, if preferred, a separate local oscillator, set to beat with the intermediate frequency or the wave to which the broadcast receiver is tuned, may be used for short-wave reception and, since this will be unmodulated, it is somewhat preferable to the use of a local broadcast signal as a heterodyne.

A Rolls-Royce Receiver By C. STERLING GLEASON

(Continued from page 280)

potential, and hence must not be allowed to come into contact with the shielding. This condenser is the exception to the general rule that condenser rotor plates go to filament circuits.

The sub-panel allows considerable latitude in layout, so far as the R.F. stage and detector are concerned—care being taken, of course, to mount the coils at right angles and as far apart as possible. The screen-grid tube with its enclosing shield is well placed at the extreme left-hand corner at the rear. The antenna coupling condenser should be at the back and, if adjustment from the panel is desired, it may be regulated by means of a bakelite extension shaft running to the front.

The most exacting part of the set is the resistance-coupled amplifier. The layout diagram for this portion of the receiver must be followed exactly; deviation is almost certain to make trouble. The "stilts" may consist of 2-inch screws or of threaded rod of corresponding length, placed so that they elevate all parts of the resistance-coupled amplifier at least 1½ inches above the metal sub-panel. The chokes in the plate leads may be placed beneath the sub-panel, care being taken to insulate the wire well when passing it through the copper base, as this is at filament potential and

POPULAR BOOK CORPORATION,
93L Park Place, New York, N. Y.

Dept. SWC-12

Please send me the book (or books) selected below. I have enclosed the numbers I desire. I enclose remittance for \$ at the rate of 35c a copy or 3 books for \$1.00. You are to send the books to me postpaid (CANADA and FOREIGN 5c extra postage per book).

I have selected the following books: 1 2 3 4 5 6

NAME
ADDRESS CITY AND STATE.....

the entire 180 volts is therefore in danger of short-circuit at this point. Two 1.5-mh. chokes are placed in series in the lead coming directly from the detector plate; since the purpose of these is to keep the R.F. out of the amplifier and force it instead back through the tickler circuit, these two should be close to the detector circuit and preferably above the sub-panel.

The two home-made chokes, X5 and X6, are wound as follows: Upon a form 1 inch in diameter, with a piece of bakelite or celluloid clamped on each side to make the width of the winding 1/4-inch, wind at least 150 turns of No. 32 wire. "Scramble-winding" is best, because it results in less distributed capacity than layer-wound coils. The exact number of turns should be determined by experiment, and one may stop at the 150th turn and test or may wind on more turns and then strip them off until the optimum value is found. Factory-made chokes may be utilized, but different values may profitably be tried.

Coil Values Are Optional

Unless only a small range of tuning is desired, plug-in inductances are necessary. Any set of factory-made coils of appropriate tuning ranges may be used; the variable condensers in such a case being chosen to match. As used by Mr. Lee, the coils are cut from Hammarlund 3-inch coil stock, which comes in 30-inch lengths and may be cut up into sections of any desired size. The coils are clamped between pieces of bakelite, and the leads run to pin-plugs extending from the under side of the clamps. The detector coil should be of a piece long enough to include both grid and plate windings, plus one extra turn. The wire is cut between the two sections, care being taken not to injure the celluloid body of the stock; and a single turn is care-

fully unwound between the two segments, leaving a slight separation between the plate and grid windings thus formed. When the coils are thus arranged, the correct relationship for regeneration is assured if the outer ends of the two coils go to plate and grid respectively. The mounting strip, bearing the pin jacks into which the coils fit, is a single piece of bakelite mounted upon bakelite pillars which should be several inches high.

The following turn values are employed in the set of coils used by Mr. Lee to cover the short waves:

R.F. Coil	Detector Winding	
	Grid	Plate
2 turns	2 turns	1 turn
3 "	3 "	3 turns
4 "	4 "	4 "
8 "	8 "	4 "
15 "	15 "	6 "

If higher wavelength ranges are desired smaller coils are advisable, since the bulk of the larger coils is considerable if this space-wound stock is used. If the above values are used, one plate should be removed from the detector tuning condenser.

Television the Proof of Quality in the Amplifier

The audio stages are supplied with filament voltage through Amperites, and the screen-grid tube operates through a series fixed resistor (R1) which drops the six volts to the specified value. Only the detector tube has a rheostat. The automatic control for the audio circuits is more satisfactory than hand adjustment, because the temptation to use the filament rheostat as a volume control is conducive to reduced filament emission which will produce distortion, especially on peaks—an effect very undesirable in television reception.

Book Review

RADIO SERVICE MAN'S HANDBOOK WITH ADDENDA DATA SHEETS. Flexible covers, size 9" x 12", pages 200, price \$2.00. Published by Gernsback Publications, Inc.

This remarkable book contains several hundred illustrations with wiring diagrams and charts covering every conceivable subject, including radio sets, tubes, etc. The book is strictly up-to-date and contains the newest practical information which every radio man must absolutely have.

THE ELEMENTS OF RADIO-COMMUNICATION, by O. F. Brown, M.A., B.Sc. Cloth covers, size 9" x 5 1/2", pages 216, illustrations 146, price \$3.50. Published by Oxford University Press.

An authoritative treatise which explains in plain English with practically no mathematics, the properties of high frequency alternating current; oscillations and radiations; transmission of damped waves; crystals and thermionic valves; receiving circuits; generation of oscillation by vacuum tubes; radio telephony; reproduction in radio telephony; directional reception; with a chapter on "short wave" transmission and reception; and the propagation of waves through space.

FUNDAMENTALS OF RADIO, by R. R. Ramsey, Professor of Physics, Indiana University. Cloth covers, size 5 1/2" x 6", pages 372, illustrated, price \$3.50. Published by The Ramsey Publishing Company.

Dr. Ramsey gives us a very refreshing treatment of the fundamentals of radio, including battery and dynamo action; alternating currents; inductance; vacuum tube constants; aerials of different kinds and how they operate; radio frequency instruments and apparatus; audio amplification and receivers in general.

RADIO TELEGRAPHY AND TELEPHONY, by R. L. Duncan and C. E. Drew. Cloth covers, size 9 1/2" x 6", pages 950, illustrations 468,

price \$7.50. Published by John Wiley & Sons, Inc.

This 950 page book forms indeed a most complete treatise on radio facts. The authors treat thoroughly the magnetic circuit; Ohm's law; transformers and induction; motor generators and starters; storage batteries; alternating currents; capacity and inductance formulae. Other chapters cover thoroughly vacuum tubes as detectors and amplifiers; oscillographs; radio compass; wavelength measurements and "short wave" receivers.

DRAKE'S RADIO CYCLOPEDIA, by H. P. Manly. Cloth covers, size 6" x 9", pages 1035, profusely illustrated, price \$6.00. Published by Frederick J. Drake & Co.


This massive cyclopedia covers radio apparatus; 1,735 subjects in alphabetical order ranging from A-battery to Zero-beat. The volume contains 1,110 illustrations, diagrams, etc. There are 414 illustrations and articles on the building and designing of radio sets, alone; 110 articles with 383 illustrations on the methods of repair, service and adjustment of radio sets. Every conceivable type of amplifier is given. Short wave receivers are also covered.

RADIO TRAFFIC MANUAL AND OPERATING REGULATIONS, by R. L. Duncan and C. E. Drew. Flexible covers, size 9" x 6", pages 186, price \$2.00. Published by John Wiley & Sons, Inc.

This valuable hand book starts off with instructions on how to learn the code in considerable detail, with a list of abbreviations. Then comes operating rules and regulations of the Radiomarine Corporation of America with operator's report forms; followed by the rules of the International Radiograph Convention; United States Radio Act of 1927 and the Ship Act of 1912.

(Continued on page 333)

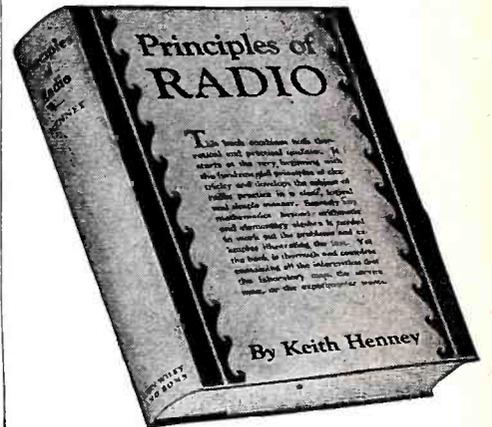Radio Men Everywhere—ENDORSE KEITH HENNEY'S "RADIO"



PRINCIPLES of RADIO

By Keith Henney

Formerly, Director of the Laboratory Radio Broadcast Magazine

Keith Henney's book on Radio scored an immediate "hit" on its publication a few months ago. Thousands have already purchased it and are enthusiastic about the valuable material which the author has made available.

This book brings together within one cover the kind of information on radio which will appeal to the practical interest of every radio experimenter, technician, engineer, and fan. It contains the latest data and the most modern methods. It treats in a thoroughly practical way everything from the production of radio currents to their reception and transmission. Scarcely any mathematics beyond arithmetic and elementary algebra is needed for a complete understanding of the theory and applications.

See a Copy on Ten Days' Approval Price, \$3.50

A Wiley Book

JOHN WILEY & SONS, Inc., 440 Fourth Avenue, New York.

Gentlemen: Kindly send me on approval Henney's "Principles of Radio". I agree to remit the price (\$3.50) within ten days after its receipt or return the book post-paid.

Name
Address
Reference

SWC 12-30



END CARD FOR FREE COPY

TRANSMITTING and RECEIVING PARTS and TUBES . . .

Biggest Discounts to Amateurs

Every make of AC and DC parts, kits, accessories, and cabinets of merit always in stock . . . 12 brands of tubes.

Free Technical Information and Advice by Experts.

Buy in Seattle at Chicago and New York Prices

WEDEL COMPANY

SEATTLE, WASH.

RADIO and ELECTRICAL JOBBERS SINCE 1888

SHORT WAVE ENGINEERING

We manufacture to order Monitors, Wavemeters, Short Wave A.C. Sets, Transmitters of any wattage rating, Power Supply Units, and any special instruments. All orders are individually treated. Estimates gladly given.

Monitors. Completely shielded in aluminum cases. Coils to cover 20, 40, and 80 Meter bands. Complete with batteries and tube—\$12.50; calibrated \$16.50.

Wave meters. Fully shielded in aluminum cases. Have a very sensitive neon bulb for indication. Calibrated for 20, 40, and 80 meter bands. Complete—\$9.50. Accuracy within 1%.

ENGINEERING DEPT.

COLUMBIA SPECIALTY CO.

1038 LONGWOOD AVE., NEW YORK CITY

CAN WE USE Ultra Short and Infra Red Rays?

(Continued from page 299)

demonstrate the sharply directional rays gathered in pencils.

For producing modulated infra-red rays, which for giving signals are necessarily from other sources of light and heat, we can use the ordinary technical sources of light which radiate heat, such as arc lights or glow lamps. In this case the light is directed through light disks or light valves, or else is interrupted. We can also use discharges of gas, for example in potassium. Telephonic modulation is done by modulating the amplified frequency in the feed-circuit, an arrangement which was demonstrated by Dr. Schröter in his lecture with striking success.

As detectors for modulated infra-red rays the Telefunken experts uses specially designed, highly-sensitive devices, for example, very thin-layered selenium-tellurium cells or thalofide cells.—*Das Funkmagazin.*

New Hammarlund S-W Receiver

By LEWIS W. MARTIN

(Continued from page 285)

tem for efficient, consistent results. The tickler, L³, is a fixed one, a .0001 mfd. midget variable condenser tuning the plate. With this system, the tuning is very smooth and gradual over the entire scale. There are no dead spots or tuning dips.

In the standard set, four plug-in coils are provided, these covering the 14 to 105 meter range. These coils, known as the 20, 30, 40 and 80 meter coils, are all built along the lines just mentioned, their difference being in the number of turns and size wire used. The variable primary, however, which is a part of the base, is accordingly the same for all wavelengths.

To provide steady grid control, a special grid condenser having a variable capacity of from 20 to 100 mmfd. is used, in conjunction with a 3 megohm grid leak, R¹.

To isolate the plate circuit, and thus afford better reproduction a radio frequency choke is used, L⁴.


We now enter the audio channel, where a special type low ratio audio frequency transformer is used, this feeding into a 230 type tube. It will also be noted that this circuit is well by-passed.

PANELS TUBING & RODS

FORMICA, BAKELITE AND HARD RUBBER—STANDARD OR SPECIAL SIZES

Cut While You Wait

Drilling, Engraving and Special Work

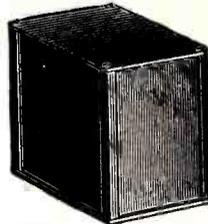

All Sizes of ALUMINUM

CANS, PANELS AND CHASSES Made and Cut to Order

Neutralizing Screw Drivers, Short or Long Sizes



COUPLINGS in Brass and Bakelite for 1/4 inch Shafts

INSULATING BUSHINGS for all size Shafts



TEL. CORTLANDT 4885

Mail Orders Filled Immediately

United Radio Mfg. Co.
191 Greenwich St. New York

Back Numbers Available at 50c each, Prepaid.
SHORT WAVE CRAFT
98 Park Place, New York City

SPECIALS

WESTERN ELECTRIC HAND MICROPHONES

Switch in handle. Very sensitive. Just the thing for that Home Recorder, Transmitter etc. Brand New! Only **\$3.95**

FRESHMAN 125 WATT POWERS TRANSFORMERS

Delivers 375 Volts, 7 1/2 center-tapped and 7 1/2 Ct. Complete power supply for 210 Amplifier or Transmitter. **\$3.70**

RCA OUTPUT OR 3:1 AUDIO TRANSFORMERS

90c each. Four for **\$3.00**

FARADON FILTER CONDENSER BLOCK 1 1/2 Mfd. 1000 Volt and 2 Mfd. 600 Volt (DC Working). Excellent for power packs, etc. SPECIAL AT..... **\$1.45**

SEND FOR OUR BARGAIN BULLETIN!! IT WILL SAVE YOU MONEY!

HARRISON RADIO CO.
Dept. C.
189 FRANKLIN ST. NEW YORK CITY

PATENT YOUR INVENTIONS Register Your Trademark

If your invention is new and useful it is patentable. I PROTECT your rights by U. S. and Foreign Patents. Call or send me a sketch or model of your invention. Consultation free.

Z. H. Polachek
Reg. Patent Attorney, Consulting Engineer. One Two Three Four Broadway, N. Y.



1234 Broadway
New York City

A Sensitive and Selective S-W Receiver

By R. WM. TANNER, W8AD

(Continued from page 306)

just below the oscillation point and increase the volume to the desired audibility by means of the volume control.

LIST OF PARTS

- L1..... Antenna R.F. choke
- L2, L3... Tuning inductances
- C..... .1 mfd bypass condensers
- C1..... 2-gang tuning condenser (see text)
- C2..... .00025 mfd grid condenser
- C3..... .00035 or .0005 mfd regeneration condenser
- C4..... 2 mfd filter condensers
- C5..... .01 mfd audio coupling condenser

- C6..... 1 mfd bypass condensers
- C7..... 2 mfd. speaker coupling condenser
- VT1.... Type 224 screen grid tube
- VT2.... Type 224 screen grid detector tube
- VT3.... Type 227 first audio tube
- VT4.... Type 171A power audio tube
- J..... Open circuit phone jack
- R..... 500 ohm R. F. bias resistor
- R1..... 50,000 ohm volume control
- R2..... 1 megohm detector grid leak
- R3..... 10,000 ohm detector bias resistor
- R4..... 25,000 ohm audio filter resistor
- R5..... 500,000 ohm plate and grid resistors
- R6..... 2,000 ohm bias resistor 10MA
- R7..... 2,100 ohm bias resistor 20MA
- R8..... 60 ohm filament resistors center tapped

COIL TABLE

Band	Grid	Tickler	Plate Tap	Length of Form
20	7 #18 enamel	6 #30 enamel	6	1 1/4"
40	13 #18 "	8 #30 "	10	1 1/2"
80	25 #22 "	11 #30 "	20	1 3/4"
100-550	53 #28 "	21 #30 "	35	2"

Short-Wave Stations—When to Listen

(Continued from page 307)

Meters	Kilo-cycles	Station	Meters	Kilo-cycles	Station
49.15	6,100	W3XAL, Bound Brook, N. J. (WJZ, New York), 5-6:30 p.m., 11 p.m.-1 a.m.	92.50	3,256	W9XL, Chicago, Ill.
49.17	6,095	VE9GW, Bowmanville, Ontario, Canada. Daily, 1:45-5 a.m., noon to 7 p.m. Sundays, 5 a.m. to 7 p.m. Gooderham & Woris, Ltd.			W6XBA, S.S. Metha Nelson, Fox Film Corp. And other experimental stations.
49.26	6,090	Copenhagen, Denmark.	94.76	3,166	WCK, Detroit, Mich. (Police Dept.)
49.31	6,080	W2XCX, Newark, N. J. Relays WOR. W9XAA, Chicago, Ill. (WCFL). 6-7 a.m., 7-8 p.m., 9:30-10:15, 11-12 p.m. W6XAL, Westminster, Calif. HS2PJ, Bangkok, Siam. 6-6:30 a.m.	95.48-97.71	3,142-3,070	Aircraft.
49.40	6,070	UOR2, Vienna, Austria. 5-7 a.m., 5-7 p.m. Tues. and Sat., 9-10 a.m. Thu.	96.03	3,124	WOO, Deal, N. J.
49.46	6,065	SAI, Motala, Sweden. 6:30-7 a.m., 11 a.m.-4:30 p.m.	97.15	3,088	W10XZ, Airplane Television.
49.56	6,060	W8XAL, Cincinnati, Ohio. Relays WLW. 6:30-11 a.m., 1:30-3 p.m., 6 p.m.-1 a.m., daily. W9XU, Council Bluffs, Iowa. Relays KOIL. W3XAU, Byberry, Pa., relays WCAU.	97.53	3,076	W9XL, Chicago, Ill.
49.67	6,040	W9XAA, Chicago, Ill. (WMAQ). W2XAL, New York. PK3AN, Sourabaya, Java. 8-9 a.m.	98.95	3,030	Motala, Sweden. 11:30 a.m.-noon, 4-10 p.m.
49.80	6,020	W9XF, Chicago, Ill. W2XBR, New York, N. Y. (WBNY).	101.7	to 105.3	meters—2,850 to 2,950 kc. Television. W3XK, Wheaton, Md., 8 to 9 p.m. except Sunday; W2XR, New York, N. Y.; W9XR, Chicago, Ill.
49.97	6,000	ZL3ZC, Christchurch, New Zealand. 10 p.m.-midnight, Tuesdays, Thursdays and Fridays. HRB, Tegucigalpa, Honduras. 9:15 p.m.-midnight, Mo., Wed., Fri. From 11 p.m. to midnight Sat., Int. S. W. Club programs. EAR25, Barcelona, Spain. Sat. 3 to 4 p.m. RFN, Moscow, Russia. Tues., Thurs., Sat. 8 to 9 a.m. Eiffel Tower, Paris, France Testing 6:30 to 6:45 a.m., 1:15 to 1:30, 5:15 to 5:45 p.m., around this wave.	104.4	2,870	Milan, Italy. After 2 p.m.
50.23	5,970	Vatican City (Bome).	105.3	to 109.1	meters—2,750 to 2,850 kc. Television. W2XBA, Newark, N. J. Tues. and Fri. 12 to 1 a.m.; W8XAV, Pittsburgh, Pa.; W1XB, Somerville, Mass.; W7XAO, Portland, Ore.; W9XAP, Chicago, Ill.; W2XAP, Jersey City, N. J. W2XCR, Jersey City, N. J. 8-10 p.m., Mo., Wed., Fri., 3-5 p.m. W2XB0, Long Island City, N. Y.
51.40	5,833	HK7, Barranquilla, Colombia. 8:30 to 10:30 p.m., exc. Sun.	110.2	2,722	Aircraft.
52.00	5,770	AFL, Bergedorf, Germany.	124.2	2,416	W7XP, Seattle, Wash., Police and Fire Depts.
52.72-54.44	5,690-5,510	Aircraft.	125.1	2,398	W9XL, Chicago, Ill.; W2XCU, Ampere, N. J. And other experimental stations.
54.02	5,550	W8XJ, Columbus, Ohio.	128.0-129.0		Aircraft.
54.51	5,500	W2XBH, Brooklyn, New York City (WBBC, WCGU).	129.0	2,325	W10XZ, Airplane Television.
56.70	5,300	AGJ, Nauen, Germany. Occasionally after 7 p.m.	130.0	2,306	SS "Bremen" and "Europa" testing.
58.00	5,170	OKIMPT, Prague, Czechoslovakia, 1 to 3:30 p.m., Tues. and Fri. PMB, Sourabaya, Java. LL, Paris, France.	135.0	2,220	Stockholm, Sweden. Oslo, Norway.
60.90	4,920	Paris, France.	136.4	to 142.9	meters—2,100 to 2,200 kc. Television. W2XBS, New York, N. Y., 1,200 R.P.M., 60 lines deep, 72 wide. W1XAV, Boston, Mass. W2XCW, Schenectady, N. Y. W3XAD, Camden, N. J. W3XAK, Bound Brook, N. J. (Portable.) W2XR, Long Island City, New York. 4-6:30, 7:30-10 p.m., daily. W8XAV, Pittsburgh, Pa., 1,200 R.P.M., 60 holes, 1:30-2:30 p.m., Mon., Wed., Fri. W2XBU, No. Beacon, N. Y. (1-2 p.m.) W2XCD, Passaic, N. J. 8-10 p.m., exc. Sat. and Sun. W8XAV, Pittsburgh, Pa. W9XAA, Chicago, Ill. W9XAC, Chicago, Ill. W9XG, West Lafayette, Ind. W10XU, Wheaton, Md. (Airplane.)
61.22	to 62.50	meters—4,800 to 4,900 kc. Television. W8XK, Pittsburgh, Pa.; W1XAV, Lexington, Mass.; W2XBU, Beacon, N. Y.; WENR, Chicago, Ill.	142.9	to 150	meters—2,000 to 2,100 kc. Television. W1XAE, Springfield, Mass. W1XY, Lawrence, Mass. W2XB0, Long Island City, N. Y. W3XK, Wheaton, Maryland. 8-10 p.m., Mo., Wed., Fri., 3-5 p.m. W2XBU, No. Beacon, N. Y. (1-2 p.m.) W2XCD, Passaic, N. J. 8-10 p.m., exc. Sat. and Sun. W8XAV, Pittsburgh, Pa. W9XAA, Chicago, Ill. W9XAC, Chicago, Ill. W9XG, West Lafayette, Ind. W10XU, Wheaton, Md. (Airplane.)
62.56	4,795	W9XAM, Elgin, Ill. W3XZ, Washington, D. C. W9XL, Chicago, Ill. And other experimental stations.	150	2,000	RA72, Smolensk, USSR.
62.69	4,785	Aircraft.	149.9-174.8	2,000-1,715	Amateur Telephony and Television.
62.70	4,785	VZA, Drummondville, Canada.	174.0	1,723	ZL2XS, Wellington, New Zealand.
62.80	4,770	ZL2XX, Wellington, New Zealand.	175.2	1,712	WKDU, Cincinnati, Ohio. (Police Dept.) WMP, Framingham, Mass. 11 a.m., 1 and 5 p.m. daily. Music and police reports. WRBH, Cleveland, O., (Police Dept.) KGJX-Pasadena, Calif., (Police Dept.) St. Quentin, France. F8FY, Cannes, France. 5 p.m. Wed.; 4 a.m. Sunday.
63.13	4,750	WOO, Deal, N. J.	176.5	1,700	Orly, France.
65.22	to 66.67	meters—4,500 to 4,600 kc. Television. W6XC, Los Angeles, Calif. DOA, Doberitz, Germany. 6 to 7 p.m., 2 to 3 p.m., Mon., Wed., Fri. OHK2, Vienna, Austria. Sun., first 15 minutes of hour from 1 to 7 p.m.	178.1	1,684	WDKX, New York, N. Y. (Police Dept.)
70.00	4,280	OHK2, Vienna, Austria. Sun., first 15 minutes of hour from 1 to 7 p.m.	180.4	1,662	Michigan State Police.
70.20	4,273	RB15, Khabarovsk, Siberia. 5-7:30 a.m. G2GL, S.S. "Homeric." G2GN, SS. "Olympic." G2IV, SS. "Majestic."	186.6	1,608	W9XAL, Chicago, Ill. (WMAQ) and Aircraft Television. W2XY, Newark, N. J. W2XCU, Wired Radio, Ampere, N. J. W2XCD, DeForest Radio Co., Passaic, N. J. 8-10 p.m. Ornskoldvik, Sweden. And other experimental stations.
71.77-72.98	4,180-4,100	Aircraft.	187.0	1,604	W2XCU, Wired Radio, Ampere, N. J. W2XCD, DeForest Radio Co., Passaic, N. J. 8-10 p.m. Ornskoldvik, Sweden. And other experimental stations.
72.87	4,116	WOO, Deal, N. J.	187.9	1,596	WRBC, New York, N. Y. (Fire Dept.) WKDT, Detroit, Mich. (Fire Dept.) W7XP, Seattle, Wash. (Police and Fire Depts.)
74.72	4,105	NAA, Arlington, Va. Time signals 8:55-9 a.m., 9:55-10 p.m.	196	1,530	Karlskrona, Sweden. (Standard Television scanning, 48 lines, 900 R.P.M.)
80.00	3,750	F8KR, Constantine, Tunis, Africa. Mon. and Fri. I3RO, Rome, Italy. Turin, Italy.			
82.90	3,620	DOA, Doberitz, Germany. (Television.)			
84.24	3,580	OZ7RL, Copenhagen, Denmark. Tuesday and Fri. after 6 p.m.			
84.46-85.66	3,550-3,500	Amateur Telephony.			
86.50-88.00	3,490-3,460	Aircraft.			


DEALERS AND SERVICEMEN



Radio Bargain News
 Write for Your **FREE** Copy of this **BIG** Catalog
40 PAGES
OVER 1,000 ITEMS
OF REPLACEMENT PARTS FOR ALL STANDARD SETS

Free Write Now
Federated Purchaser
 16 Hudson St., N. Y. City

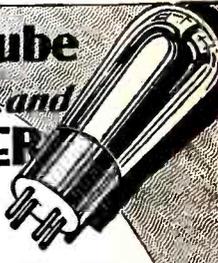Makes Any Tube Last LONGER and Perform BETTER



By automatically keeping voltage exactly right for each tube, AMPERITE lengthens tube life and improves reception. *Never wears out.* Insist on AMPERITE. A type for every tube—A.C. or D.C. \$1.10 with mounting (in U. S. A.) At all dealers.

AMPERITE Corporation
 661 BROADWAY, NEW YORK

FREE—"Amperite Vest Pocket Tube Chart." Write Dept. SW-4

AMPERITE
 The "SELF-ADJUSTING" Rheostat

1931
LOWEST WHOLESALE PRICES!

FREE RADIO CATALOG

Everyone interested in RADIO should have this Catalog. Solid with "Specials" from cover to cover. Teeming with values... every item a feature. All latest sets and equipment. Screen Grid, A. C., Humless, all electric sets... also battery operated sets and direct current sets. Dynamic speakers, beautiful consoles, kits and parts. Wholesale prices. Astounding savings. Get this FREE bargain book today.

Chicago Salvage Stock Store
 509 S. State St. Dept. 640 Chicago

BARGAINS

THORDARSON Input and Interstage Transformers




A Transformer possessing a ratio of 2 to 1. Built primarily for use with 210, 250 and 245 types of power tubes in push-pull stage. Size 3 1/2 x 3 x 3 3/4. Weight 3 1/2 lbs. List, \$12.00

Your Price, \$3.95

B.B.L. GIANT ELECTRIC

Motor Speaker Chassis

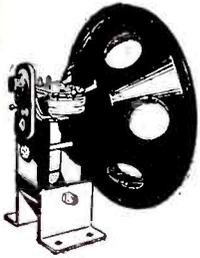

Contains a GIANT MODEL UNIT. Note the HUGE MAGNETS. Surpasses all other magnetic speakers, and most dynamics. Every note and tone in the musical register is faithfully reproduced, with no distortion or rattles. MUSIC AS IT SHOULD BE. Equipped with switch arrangement offering choice of 3 impedances to match any amplifier output characteristics—an exclusive feature. No field current required—no rectifiers. Shpg. wt., 10 lbs.

No. 421-E-2. 9" DIAPHRAGM. List, \$14.00

Your Price, \$7.25

ANALYZER and TUBE TESTER



Our Special Price
\$11.95

This reliable meter selling for considerably less than many others on the market meets the demands of every service man most efficiently. Its sturdy construction and accuracy in testing voltages, tubes, open circuits, etc., assures you satisfaction and long use. This meter is identical in construction and resembles others which wholesale from \$60 to \$100.

WHAT IT DOES FOR YOU!

Shows A.C. and D.C. Filament Voltages

Tests Plate and Grid Voltages (also Screen Grid Voltages)

Indicates Plate Current and Line Voltage

Shows Open Circuits and Grounds


Tests A.C. and D.C. Tubes

This exceptionally fine meter makes every essential test on the radio set.

At the tremendously low prices at which the merchandise below is offered, every radio dealer, service man or mechanic should equip himself with stock for future use. It is probable that such low prices will not prevail for long.

SONORA CABINET

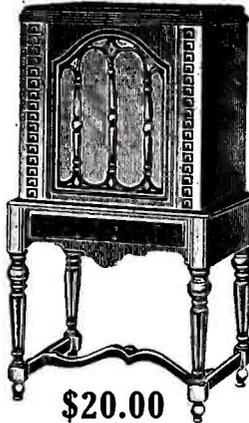with Peerless 12-inch Auditorium Dynamic Speaker



positively the last word in the most efficient and powerful reproducer model. As a fitting companion, it is housed in a truly exquisite deep two-tone walnut console, of rare beauty and craftsmanship! To properly baffle the ultra-powerful Peerless chassis, a chamber 12" deep, 17 3/4" wide and 18" high houses same. Front baffle of 3/4" thickness! Ideal for use with the most powerful public address amplifier. NO RATTLING, NO DISTORTION — JUST PERFECT REPRODUCTION! For that matter it is equally suited with ordinary sets, employing the average type of audio amplification systems, using as low as 90 volts "B" current! Will work with any set, regardless of output characteristics. Overall dimensions: 40" high, 24" wide, 15" deep. For 110 volt, 50-60 cycle A.C. Shpg. wt., 60 lbs. No. 408-A-50. List, \$155.00.

\$20.00

DRY ELECTROLYTIC CONDENSERS



No. 1006



No. 1007-8-9




No. 1003-4-5

Absolutely dry—mount in any position! SELF HEALING—NEVER BLOW OUT! High voltage rating—occupy surprisingly small space, considering high microfarad capacity. Much less expensive than paper dielectric condensers! Clever mounting facilities. IDEAL FOR REPLACEMENT PURPOSES, as well as installation in new power packs! 500 volt D.C. PEAK rating. (Use two of each capacity desired for 250 tube power packs.)

	An-				YOUR
No.	Mfd.	odes	Dia.	Length	PRICE
1003.	1	1	3/4"	2 1/4"	.55
1004.	2	1	1"	2 1/4"	.90
1005.	4	1	1 1/2"	2 1/4"	1.70
1006.	8	1	1 3/4"	4 1/2"	2.50
1007.	16	2	3"	4 1/4"	4.25
1008.	24	3	3"	4 1/4"	5.50
1009.	32	4	3"	4 1/4"	7.50

COMBINATION "A.B.C." POWER PACK

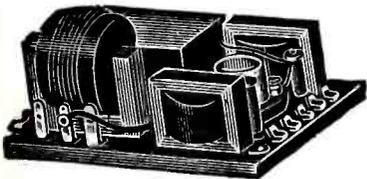

WIRED READY FOR USE Built with high-grade parts. Supplies "A.B.C." Voltages for 5-226's, 2-227's, 2-171-A's, 1-280 105-120 Volts — 50-60 Cycle Delivers over 125 Mills and up to 300 volts "B" power. The Power Transformer is designed to take care of a D.C. DYNAMIC SPEAKER, two connections being provided on the pack for same. It need not be used if not wanted, but may come in handy at some future date.

Price Now \$6.75

All products shipped C.O.D. immediately upon receipt of order.

GRENPARK TOOL CO. 245 Greenwich Street New York, N. Y.

The Screen Grid Five By EDWARD G. INGRAM

(Continued from page 300)

uperlative degree of efficiency. Now, with regard to the first audio-frequency stage of the receiver, recent research has revealed that, if the '24 type

tube is used as a space-charge amplifier (that is, with the two grid connections reversed so that the signal is impressed on the outer screen grid) with resistance

coupling the extremely high gain of about sixty can be obtained.

The use of an untuned stage of radio-frequency amplification has been found very desirable in short-wave receivers; for it provides better coupling to the antenna, so that variations in the lengths of the latter are unimportant, and also gives a distinct gain in amplification without adding any controls. For this reason, the first radio-frequency stage incorporated in the receiver is of this type, provided with choke-coil coupling and a '24 type tube. This is followed by a tuned radio frequency stage, a regenerative detector and a resistance coupled audio stage, all provided with type 24 screen-grid tubes, the audio frequency tube being used as space charge amplifier with the grid connection reserved for this purpose.

The second audio-frequency stage also is of the resistance type, but provided with a type '45 power tube.

Thus, by the addition of an untuned R.F. stage and a screen-grid detector we greatly increase the sensitivity of the set, as compared with the usual modern short-wave receiver with a single tuned stage, without increasing the number of controls; and, by the use of a screen-grid resistance-coupled audio stage, we increase the audio-frequency amplification without losing the stable regenerative control obtained with resistance coupling.

Biases for the R.F. tubes are obtained through resistors, by-passed with fixed capacities. The detector gets a positive bias by means of a 1 1/2-volt battery; the negative battery terminal being grounded.

Maximum amplification from the '24 audio tube is obtained when no biasing resistor is connected between the cathode and ground. Unless a separate transformer winding is used to supply the filament of the power tube, the grid bias must be furnished by "C" batteries. The correct voltage is 34 1/2, with 180 volts on the plate, or 51 1/2 with 250 volts on the plate.

The plates of the first three tubes may be operated on 180 volts. While a detector plate voltage of 180 sounds high, it is not; for this tube may be operated on even 200 volts to advantage.

The screen grids of the R.F. tubes should be supplied with 60 to 67 1/2 volts. For the screen grid of the detector, 20 to 25 volts is enough. The space-charge grid of the first audio tube should be kept at 5 volts, or less.

A little experimenting may be necessary with the resistance values used in this stage. The plate resistor should be from 1/4 to 1/2 meg., and the grid resistor from 1/10 to 1 meg.

The writer expects to supply the plates of all but the power tube from a 180-volt storage battery. Plate current for the power tube will be taken from a "B" power unit. Separating the two sources of plate supply has the advantage of eliminating the possible danger of inter-stage coupling. Also, when using ear-phones on the first stage, freedom from line noises is assured.

The Short-Wave S-G Craft Box

By **BERYL BRYANT**

(Continued from page 284)

A metal tab is soldered directly to the clip of the grid leak as shown in Fig. C. A similar piece is made and drilled with a hole in the tab to pass a 6-32 brass machine screw. A hole is drilled $\frac{3}{4}$ -inch from the screw fastening the clip to the bakelite mounting strip of the grid-leak mounting. The second strip is now arranged in such manner as to be variable in the surface exposed to the fixed strip, being pivoted by the same screw used for the mounting of the binding post as shown (Fig. 2). The binding post (B1), used to connect the antenna directly to the grid of the R. F. tube, is fastened to a screw soldered to the one which fastens the clip to the bakelite strip. The ground binding post (B3) is mounted on the bakelite strip in the same manner as the series-condenser binding post (B2) and its screw is soldered to the lower clip of the mounting. On the rear of the baseboard should be left a space $1\frac{1}{4}$ inches wide by 9 inches long for the "A" and "B" batteries, which are held in position by a strap of fibre or "fish" paper. This strap should be an inch wide and strong enough to prevent tearing.

Adjustment and Operation

To operate the receiver the batteries are first placed on the rear of the baseboard but not fastened down until connected; all are connected in series, to provide 135 volts. Two $4\frac{1}{2}$ -volt "C" batteries connected in parallel are used for the "A" battery, or, if longer life is desired, three dry cells connected in series may be used. "A—" and "B—" are connected together and to the lead from the filament switch. The "A+" is connected to the "A" battery, "B+ Det." and the R. F. screen-grid lead to 45 volts positive. It was found by experiment that a slight increase (not over $67\frac{1}{2}$ volts) on this grid improved signal strength to a noticeable figure. The "B+90" and "B+135" are also connected to the proper battery terminals.

Caution: do not connect the batteries, especially the "B" batteries, until the constructor is positive that all connections have been properly made in the receiver.—*Radiocraft*.


Propagation of Radio Waves

By **DR. J. FUCHS**

(Continued from page 291)

or in a vacuum, is equal to that of weak radio signals in receiving apparatus.

(To be concluded)

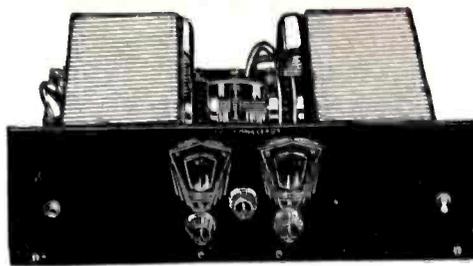

Now you can get the whole wide world!

Any short-wave station in the world. The new ship-to-shore type coils and the scientific precision of this new set give revolutionary results.

I. C. A. CONQUEROR SHORT-WAVE RADIO KIT

Here is the thrill of thrills. Tune in on the whole world and get them all. Even novices get Europe and South America at the first try. The I.C.A. Conqueror (A.C. or battery model) is the last word in high power, stabilized short-wave reception.

The coils and circuit are the combined achievement of I.C.A. engineers and a foremost ship-to-shore short-wave expert. The I.C.A. Conqueror will do all that the most expensive custom-engineered sets will do and far out-performs the popular sets on the market, yet the Conqueror sells at a popular price—in kit form, complete with all coils, quickly assembled.


The I.C.A. Conqueror A.C. model uses a 224 screen-grid in the R.F. One 227 for detector and two 227's and one 245 in

the transformer-resistance-transformer-type audio. For broadcast-band reception, special coils of scientific design are used.

Although any A and B power supply may be used for the I.C.A. Conqueror A.C. Model, we recommend the I.C.A. Conqueror Power Pack, scientifically designed to be extremely constant in voltage flow.

Dealers, professional set builders and servicemen make real money assembling and selling the I.C.A. Conqueror. A splendid opportunity for part or full time profits. Some territories still open. Order from jobber or mail order house. If they can't supply, send direct. List Price of Kit \$65—Net \$39. A.C. Power Pack, List Price \$34.50—Net \$19.75. Catalog and full information on request.

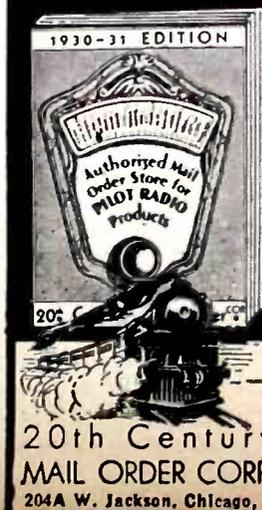INSULINE CORP. OF AMERICA, 78-80 Cortlandt St., New York, N. Y.



Send for this **FREE CATALOG** of Radio Bargains and get **FREE RADIO GIFT!**

Make 20th Century your headquarters for everything in radio. Lowest prices assured. Every article guaranteed. Complete equipment for regular and short wave receivers and transmitters. Sets, Parts, Kits, Pilotron Tubes and other Pilot Radio products. Send for catalog NOW.

GENUINE PILOT PRODUCTS

GUARANTEED RADIO TUBE SALE

All Tubes Guaranteed for 6 Months

FOR THE FIRST TIME, a standard brand of radio tubes is sold at extraordinarily low prices, yet each and every one of the tubes is guaranteed in all respects for 6 months.

All tubes are date stamped and any tube that fails to make good for ANY reason will be replaced free of charge within 6 months.

Radio tube users have become wary of so-called cheap tubes. Such tubes are nearly always "seconds"; that is, tubes that have failed to pass the manufacturer's tests. These tubes do not give good service and therefore are never guaranteed for any length of time.

REXTRON tubes are manufactured by one of the oldest, reliable Eastern tube manufacturers and we have made special arrangements for this unparalleled sale. You will find here tubes that you cannot buy elsewhere, yet the price is low when you figure the long service that these tubes will give you. There are no better tubes made than REXTRON, regardless of price.

Order from this page and please note particularly the following terms.

No orders accepted for less than \$3.00.


All prices are F. O. B. New York.

No replacements after six months.


If you wish a tube replaced, it is necessary to return it to us and we will send you a new one immediately.

It is not necessary to send full amount of cash with order, so long as you send 20% of the value with your order.

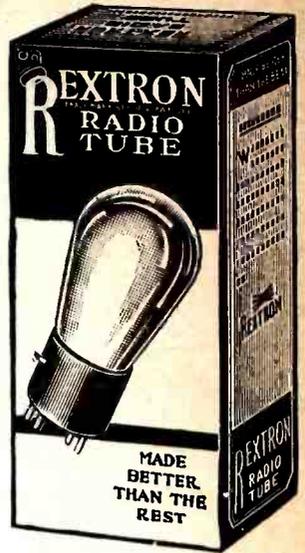Shipment will go forward to you by express collect.



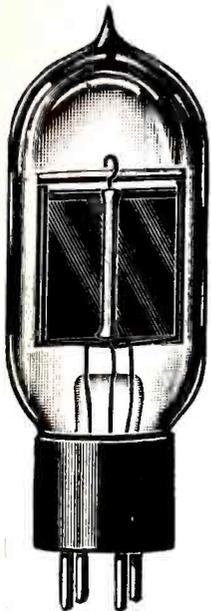All tubes come in this attractive carton.



Telion Television Tube \$3.85



2-Inch Photo-Electric Cell, \$4.50



High Grade (Hi Mu) 201A Type—better vacuum—works and fits in any set. \$1.00



A.C. Adapter Tubes to convert battery sets into A.C. Electric sets—furnished for 226, 227, 171A. \$1.00.




Switch Tube \$1.00
Switch is used when one filament burns out, tube therefore has twice normal life. With switch on acts as 171 or 112 Power Tube— with switch off it is 201A Tube.

Tubes Shipped Immediately


TYPE	PRICE
UX-201A—Amplifier or Detector—Standard for all purposes.....	\$1.00
UX-226 —Used as amplifier tube for A.C. operation.....	1.00
UY-227 —Used as detector amplifier for A.C. operation.....	1.00
UX-171A —Power output amplifier for A.C. or D.C. operation, 1/4 amp.....	1.00
UX-171 —Same characteristics as the 171A on tungsten filament, 1/2 amp.....	1.00
UX-240 —Designed for impedance and resistance coupling.....	1.00
UX-120 —Power amplifier used in last stage of audio frequency of battery set using dry cells.....	1.00
UX-199 —Detector and amplifier tube, long prongs.....	1.00
UV-199 —Same characteristics as UX-199 only short prongs.....	1.00
UX-112 —Power amplifier tube, 1/2 amp.....	1.00
UX-112A —Power amplifier tube for low current consumption, 1/4 amp.....	1.00
UX-200A —Detector tube recommended for weak signals and good reception.....	1.00
UY-224 —Screen grid, four-element, used as frequency amplifier and linear power detector in special circuits.....	1.00
UX-245 —Power amplifier tube used in last audio stage—for low plate voltage.....	1.00
201A—Quadrode 5-prong, for special circuits.....	1.00
200A—Special detector tube, a supersensitive detector.....	1.00
201A—Special radio frequency, a supersensitive detector.....	1.00
201A—Special audio frequency, a supersensitive detector.....	1.00
171 —Special A.C. 1/2 amp, extra coated filament—good for electric sets.....	1.00
T-14 (201A High Mu), high emission.....	1.00
Switch tube, 201A or 112 or 171, double life.....	1.00
226, 227, 171A—Adapter tubes, to convert battery sets into A.C., each.....	1.00
UX-210—For power amplifier, high voltage.....	2.95
UX-250—Power amplifier used in last stage of audio frequency.....	2.95
201A—All bakelite shield tube.....	2.00
UX-222—Screen grid tube for D.C. operation. Radio frequency amplifier.....	2.10
Telion television tube.....	3.85
Photo-electric cell—2 inches.....	4.50

RECTIFIER AND CHARGER BULBS

125 mil. rectifying tube (B. H. type).....	2.00
2 amp. old and new type charger bulbs (list \$4.00), our price.....	2.85
5 and 6 amp. old type charger bulbs (list \$8.00), our price.....	4.95
UX-280—Used as a fullwave rectifier tube for high emission.....	1.00
UX-281—Characteristics similar to the 280, but used as half-wave rectifier of high emission.....	2.95
Freshman rectifying tube, especially designed for use with Freshman Master "B" Eliminators, UV brass base, limited quantity.....	1.00

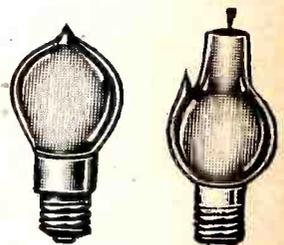

2-Ampere Charger Bulbs. \$2.85.

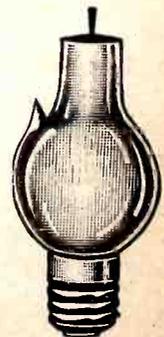

5 and 6-Amp. Charger Bulbs. \$4.95.




5-Prong 201A \$1.00

RADIO TRADING CO., 246A Fifth Ave. NEW YORK

SHORT-WAVE COILS

Tube Socket Models

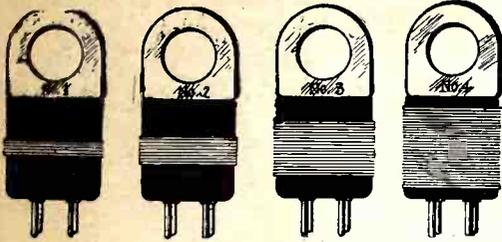

Coils fit in standard UX (4-prong) tube sockets, for .00014 mfd. tuning. Four coils to a set (15 to 150 meters; use .00014 mfd.). Order Cat. FHC @ \$1.50. The coil forms are equipped with finger handles.

CONVERTERS

A.C. model short-wave converter (Cat. AP-AC-CON) includes drilled, socketed panel, cabinet, two Hammarlund .0005 mfd. SFL, two National VB dials, five precision de luxe coils (Screen Grid Coil Co.), filament transformer, everything else (less three 227 tubes required). Price \$24.70.

- Hammarlund .0005 SFL tuning condenser (Cat. H-SF-5) \$3.30
- Heath Radiant .00014 tuning condenser (HR-4) 1.25

GUARANTY RADIO GOODS COMPANY

143 West 45th Street New York, N. Y.
(Just East of Broadway)


GUARANTY RADIO GOODS CO.,
143 West 45th Street, New York, N. Y.
(Just East of Broadway)

Enclosed please find \$..... for which please ship:

- Cat. FHC@ \$1.50
- Cat. AP-AC-CON@ 24.70
- Cat. H-SF-5@ 3.30
- Cat. HR-4@ 1.25

Your Name
Street Address
City..... State.....(SWC)

Aluminum Box Shields

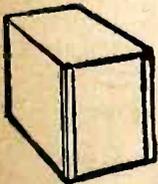

Beautiful silver dip finish, 5x9x6 inches, \$1.89. We make any sizes to order in 24 hours.
4x4x5 inch knockdown coil shield (like picture on left), \$1.00.

.25 Sprague Midget Cond., 59c; 7-Plate Midget Cond., 50c; 4 and 5 prong plug-in coil forms, grooved for wire, 45c. Drum dial drive cable by foot or mile. Include sufficient postage for shipment.

BLAN, The Radio Man, Inc.
89U Cortlandt St., New York, N. Y.

Book Review

(Continued from page 327)

TELEVISION TO-DAY AND TO-MORROW, by S. A. Moseley, and H. J. B. Chapple. Cloth covers, size 8" x 5½", pages 130, profusely illustrated, price \$2.50. Published by Isaac Pitman & Sons.

This up-to-the-minute work on television describes in detail the apparatus used by Baird. The student will learn all about scanning discs; the best type of motor; reverse effects and how to overcome them; isochronism and synchronism; various ways of synchronizing the receiving discs; photocells and neon tubes; radio receivers for television signals; noctovision. The author handles the subject of Television in a comprehensive and interesting manner.

RIDING THE AIR WAVES, with Eric Palmer, Jr. by himself. Cloth covers, size 7½" x 5½", pages 328, price \$2.00. Published by Horace Liveright.

Short Wave Fans cannot miss reading this highly entertaining and informative book which tells the story of youthful Mr. Palmer and his remarkable achievements in amateur radio. "Around the World with 5 watts" and many other interesting subjects appear between the covers of this book. The author also handles the subject of short wave transoceanic rebroadcast; the recognition of amateur radio service by the government, etc.

A POPULAR GUIDE TO RADIO, by B. Francis Dashaill. Cloth covers, size 5½" x 8½", pages 286, profusely illustrated, price \$3.50. Published by The Williams & Wilkins Company.

The author starts off with an excellent section on electricity and magnetism; the use of radio aerials and grounds; the fundamental principles of radio; the electron tube and crystal rectifiers—how they work; the principle of radio amplification; radio inductance coils and condenser; fundamental radio receiving circuits; electrical reproduction of sound; the atmosphere and radio phenomena, etc. The subject matter is adequately handled by the author and makes very interesting and informative reading matter.

RADIO RECEIVING TUBES, by Moyer and Wostrel. Cloth covers, size 7½" x 5½", pages, 298; illustration, 181; price \$2.50. Published by McGraw-Hill Book Company, Inc.

Every radio student or operator cannot do without this authoritative book on the radio vacuum tube. The various chapters include construction of vacuum tubes; electrical fundamentals; elementary action taking place in the vacuum tube with graphs; reactivation of tubes; testing of tubes including determination of amplification factor; plate resistance; grid resistance, etc. Other valuable chapters cover detector action; V. T.'s as amplifiers; oscillation generators; followed by specifications for vacuum tubes and their industrial application in many rôles.

ELEMENTS OF RADIO COMMUNICATION, by Professor John H. Morecroft. Cloth covers, size 9" x 6", pages 270, illustrations 170, price \$3.00. Published by John Wiley & Sons, Inc.

Professor Morecroft explains in an authoritative and clearly understood manner, such important radio phenomena as—current flow in circuits containing capacity and inductance; propagation of radio waves; vacuum tubes as detectors and amplifiers; fading of radio waves and its causes; neutralization; "superheterodynes for short waves," etc.; audio frequency amplifiers; how filters work.

RADIO MOVIES, by C. Francis Jenkins. Cloth covers, size 9" x 6", pages 144, profusely illustrated, price \$2.50. Published by Jenkins Laboratories, Inc.

An absorbing history, handsomely illustrated, of the Jenkins system of transmitting and receiving movies by radio. One of the chapters give constructional details and drawings for building your own radio-visor or machine for making the radio movies visible in your home. Diagrams of amplifiers are given with much other valuable information.

OFFICIAL RADIO SERVICE MANUAL, by Hugo Gernsback, Editor; Clyde Fitch, Managing Editor. Flexible covers, size 9" x 12", profusely illustrated, pages 352, price \$3.50. Published by Gernsback Publications, Inc.

Commercial wiring diagrams for all the regularly manufactured receiving sets are included in this manual and no radio service man or student who builds and repairs radio sets can be without this tremendously useful compilation of circuits and their descriptions. This book is worth \$100.00 to anyone who has a use for it. The Manual is indexed so that any commercial receiving circuit can be found instantly. One of the most valuable radio books ever published.


RAWNER RADIO & TELEVISION CO.

Dept. S.W., 142 Liberty St.
NEW YORK CITY, NEW YORK
Hitchcock 4780-4781

Write for FREE CATALOG

DEPOSIT WITH ALL C.O.D. ORDERS—INCLUDE POSTAGE—OTHERWISE SHIPMENT WILL GO FORWARD BY EXPRESS. ORDER FROM THIS PAGE—WE MAKE 24-HOUR SHIPMENTS!

Loftin-White Tuners

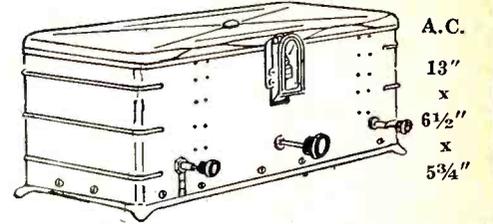

May Be Connected to Any Kind of Amplifier

Calibrated Tuning Dial—"razor edge" selectivity—uncanny sensitivity. Antenna stage, micrometer tuned, by compensating knob on panel. This tuner, and its circuit, is famed the world over! Actually used in SONORA \$895.00 RECEIVER!


REQUIRES
3-224, 1-227
AC TUBES **\$17.95**

SPECIALS

- THORDARSON
- R-245 Compact\$11.90
- R-171 and 210 Compact 4.89
- 250 Push-Pull Power Transformer. 5.50
- For 2-250, 2-281, 5-227
- 250 M.A. Double Choke..... 6.95
- 2½-Volt 12 Amp. Transformer.... 3.75
- 1½-2½ 5-Volt Transformer..... 3.95
- Silver-Marshall Output Filter..... 3.95
- S.M. No. 255 Phono Equalizing Trans. 2.95
- 245 A. B. C. Power Pack..... 16.50
- Same, with 2-Stage Push-Pull (2-245) Amp. Uses 1-227, 2-245, 1-280.... 19.85
- (Also furnishes 12 Amps. 2½ Volt A.C. and "B" Voltage for Tuner.)
- A.C. Synchronous Phono Motor..... 4.45

RADAX

ROUND THE WORLD
SHORT WAVE SET

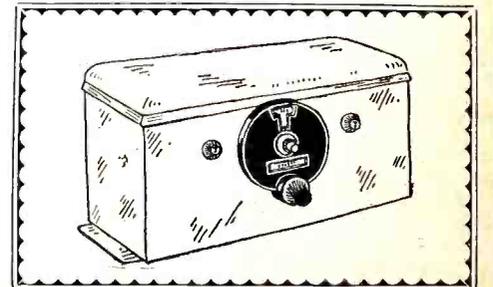

\$15.95 Complete

"Round the World Reception." Housed in fully shielded aluminum case. Single, calibrated tuning dial. Uses precision plug-in coils (furnished) covering 10 to 200 meters! Fully assembled and wired. Uses 1-222 SCREEN GRID DETECTOR, 1-201A (1st A.F.) and 1-112A (2nd A.F.).

S-I-O-P!

NOW that you have seen SHORT WAVE CRAFT, we know that you don't wish to do without a copy. To new subscribers we have a special offer that will be void after December 10th.

Those who believe in this publication and wish to receive their copy every other month, NOW have the opportunity to subscribe at a considerable saving. You will receive SHORT WAVE CRAFT at a 33 1/3% reduction from the regular subscription rate—also the three first issues GRATIS.

Fill out the coupon and rush it in before you forget it. IT IS A CHANCE YOU WILL NEVER GET AGAIN.

Short Wave Craft,
93L Park Place, New York City.

Gentlemen:
Please enroll me as a subscriber to SHORT WAVE CRAFT for which I enclose herewith \$2.00 for one year's subscription, and am to receive the three first issues GRATIS. (\$2.50 CANADA AND FOREIGN.) I understand that the full subscription price is \$3.00 a year.

NAME
ADDRESS
CITY AND STATE

With
BYRD at the SOUTH POLE

AN album containing authentic views of the BYRD ANTARCTIC EXPEDITION. Each of the seventeen actual photographs presents a thrilling story of the hazardous life at the far end of the world.
Send twenty cents, stamps accepted, for your copy of this interesting album of the greatest expedition of all times.

GREN PARK COMPANY
245-C Greenwich St.
New York New York

SIGNAL
Wireless
PRACTICE
SET LIST \$3.40



For practicing the code. Equipped with high grade key and high frequency buzzer. Each set complete with booklet "Fundamentals of Wireless Telegraphy." If your dealer cannot supply you write direct—
SIGNAL ELECTRIC MFG. CO.
MENOMINEE, MICH.

Among the Hams

(Continued from page 289)

(Our correspondent will have noticed that his demand has already been granted. We have had several articles on television on short waves, beginning with the second issue, and we will have some more right along. All we want of you hams and short wave enthusiasts, including "S. W. P. H.," is to let us know what you want to read, and it will be published if it can be secured. Remember, the editor has no preference as to the various articles; he is not publishing the magazine for himself but for you fellows. So shoot along the suggestions and you will find we will pay close attention to them.—Editor.)

STATEMENT OF THE OWNERSHIP, MANAGEMENT, CIRCULATION, ETC., REQUIRED BY THE ACT OF CONGRESS OF AUGUST 24, 1912.

Of Short Wave Craft, published bi-monthly at Mt. Morris, Illinois, for Oct. 1, 1930.

State of New York, County of New York, ss. Before me, a Notary Public, in and for the State and county aforesaid, personally appeared Hugo Gernsback, who, having been duly sworn according to law, deposes and says that he is the editor of the Short Wave Craft and that the following is, to the best of his knowledge and belief, a true statement of the ownership, management (and if a daily paper, the circulation), etc., of the aforesaid publication for the date shown in the above caption, required by the Act of August 24, 1912, embodied in section 411, Postal Laws and Regulations, printed on the reverse of this form, to wit:

1. That the names and addresses of the publisher, editor, managing editor, and business managers are:

Publisher, Popular Book Corporation, 98 Park Place, N. Y. C.; Editor, Hugo Gernsback, 98 Park Place, N. Y. C.; Managing Editor, H. Winfield Secor, 98 Park Place, N. Y. C.

2. That the owner is: (if owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding one per cent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a firm, company, or other unincorporated concern, its name and address, as well as those of each individual member, must be given.)

Popular Book Corporation, 98 Park Place, N. Y. C.; D. Gernsback, 98 Park Place, N. Y. C.; H. Winfield Secor, 98 Park Place, N. Y. C.

3. That the known bondholders, mortgagees, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.)

None.

4. That the two paragraphs next above, giving the names of the owners, stockholders, and security holders, if any, contain not only the list of stockholders and security holders as they appear upon the books of the company but also, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, is given; also that the said two paragraphs contain statements embracing affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner; and this affiant has no reason to believe that any other person, association or corporation has any interest direct or indirect in the said stock, bonds, or other securities than as so stated by him.

5. That the average number of copies of each issue of this publication sold or distributed through the mails or otherwise, to paid subscribers during the six months preceding the date shown above is (This information is required from daily publications only).

H. GERNSBACK.

Sworn to and subscribed before me this 30th day of September, 1930.


(Seal.) ROZELLA BENNETT,
(My commission expires March 30, 1931.)

Free AVIATION Course

Study in a few simple lessons!

In the current issue of AVIATION MECHANICS appears two complete courses in Aviation, written by Jack Stinson of flying fame and Morton Schwam, motor expert. So thorough are these courses that you will be well instructed in the most important points of flying and airplane construction. The country looks to junior aviation enthusiasts as the heroes of the future—get an early start—your training should begin NOW.

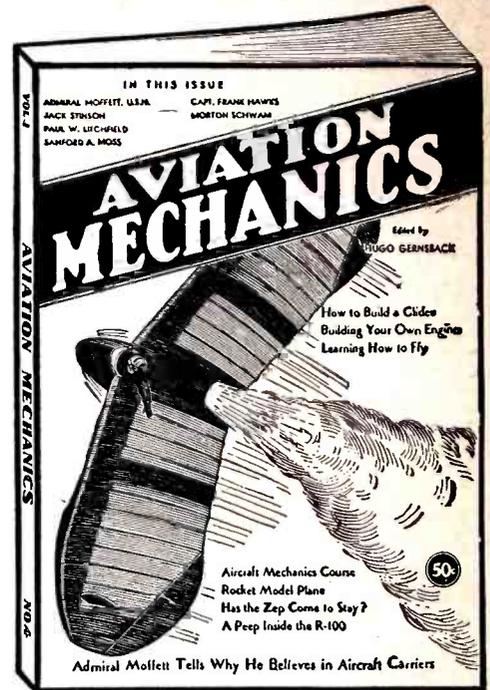On All Large Newsstands . . . 50c the Copy



OVER 200 ILLUSTRATIONS

Features in This Issue . . .

- Building Your Own air-Cooled Engine
- Model Rocket Plane That Flies
- How to Build a Primary Glider Learning How to Fly
- Shooting Trouble on Plane and Engine
- Questions and Answer Box
- Dirigibles
- Tail-less Planes
- Latest Inventions

also many practical hints on motors, instruments, wings and construction—replete with over 200 illustrations, diagrams and working drawings. Instructors as well as thousands of junior aviation enthusiasts read AVIATION MECHANICS—it is an excellent guide in their work, a simple easy reference.

Each issue contains complete description and photographs of all the latest types of planes.


SPECIAL OFFER—The regular subscription price of AVIATION MECHANICS is \$3.00 per year. If you act quickly, and send in \$1.80 in cash, check or money order, you will receive this magazine for one full year, also the first and second issues gratis. Or to acquaint yourself with this magazine send 25c for a sample copy.

Published on the 15th of every other month

AVIATION MECHANICS
93L PARK PLACE, NEW YORK, N. Y.

FOR BOOKS to read during your spare time, we suggest that you turn to page 326 of this issue. On that page you will find many books to complete your hours of pleasure.

WORLD'S BEST RADIO BOOKS

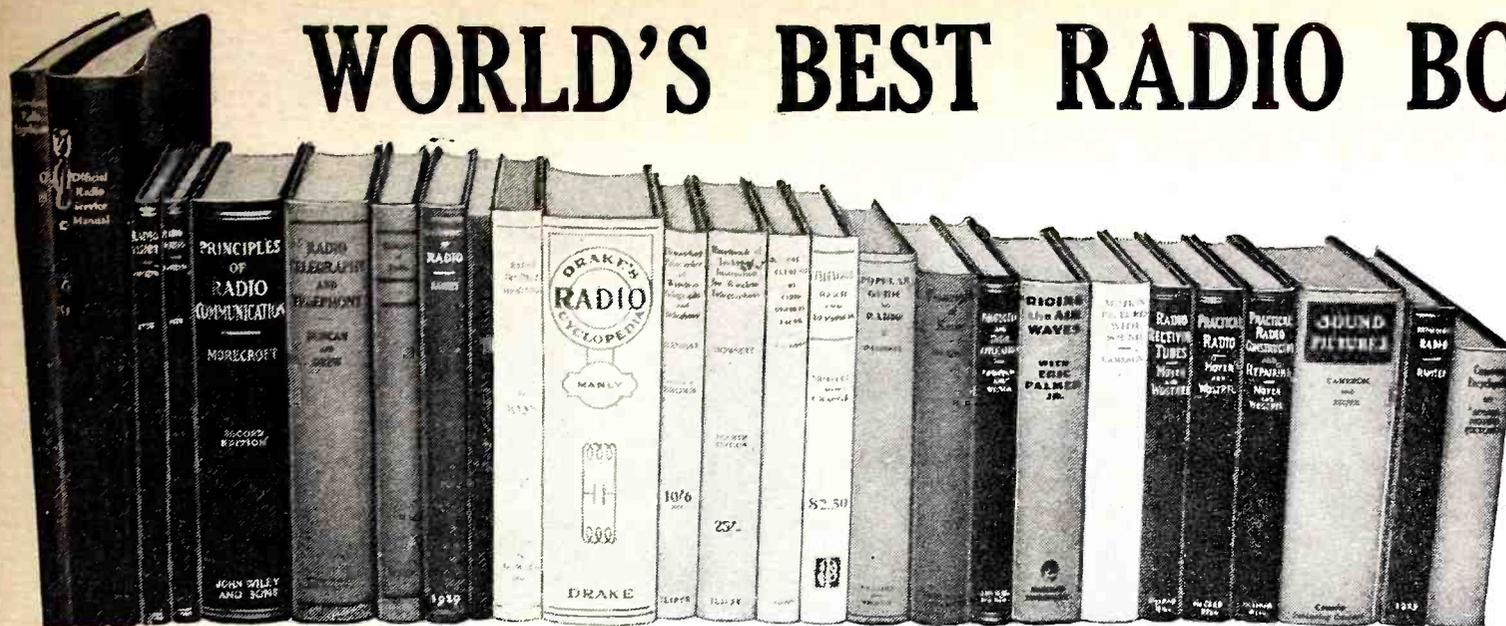

ORDER DIRECT FROM THIS PAGE

WE herewith present to the readers of **SHORT WAVE CRAFT** the most complete collection of recent important radio books. We have, after an exhaustive study, selected these volumes because they represent the foremost radio books of their kind in print today. There is such a great variety that we are sure it will satisfy any taste as well as any requirement that the student of radio might have.

We publish no catalogue and ask you to be kind enough to order direct from this page. Prompt shipments will be made to you direct from the publishers. We merely act as a clearing house for a number of radio book publishers and **OUR PRICES ARE AS LOW OR LOWER THAN WILL BE FOUND ANYWHERE.** Prompt shipments will be made.

Remit by money order or certified check. If you send cash, be sure to register it. If you wish to get any other radio book, please write us.

EXPERIMENTAL RADIO. by R. R. Ramsey, Professor of Physics, Indiana University. Cloth covers, size 7½x5½", 256 pages, 168 illustrations. Price, postpaid **\$2.75**

This book by Professor Ramsey is written in the nature of an experimental radio course and contains 128 experiments, illustrated and described in a clear and interesting style. The experiments cover such valuable subjects as: A test on a loud speaker; the impedance of coils; construction of a filter, screen grid tube; beat note audio oscillator; etc.

PRINCIPLES OF RADIO COMMUNICATION. by J. H. Morecroft, Prof. of Electrical Engineering, Columbia University. Cloth covers, size 9½x6", 988 pages. Profusely illustrated. Price **\$7.50**

A radio classic, indeed, is Professor Morecroft's very complete text-book which covers such important radio phenomena as: the action in condensers; self and mutual induction in a circuit; phase and phase difference; effect of condensers and coils on wave shape; resonance frequency of coupled circuits; skin effect in coils; antenna resistance; transformers; vacuum tubes; radio frequency alternators; modulation and circuits; amplifiers and filters.

RADIO TRAFFIC MANUAL AND OPERATING REGULATIONS. by R. L. Duncan and C. E. Drew. Flexible covers, size 9x6", 186 pages. Price **\$2.00**

This valuable handbook starts off with instructions on how to learn the code in considerable detail, with a list of abbreviations. Then comes operating rules and regulations of the Radiomarine Corporation of America with operators' report forms; followed by the rules of the International Radiograph Convention; the United States Radio Act of 1927; the Ship Act of 1912; etc.

PHOTOCELLS AND THEIR APPLICATION. by V. K. Zworykin, E.E., Ph.D., and E. D. Wilson, Ph.D. Cloth covers, size 5½x8", 210 pages, 97 illustrations. Price **\$2.50**

Photocells today occupy a very important place in radio and talking pictures, as well as other branches of applied science, and these two experts have provided the very latest information as to the action taking place in various types of photocells. The theory on which these different cells operate, including color sensitivity, together with amplifier and scanning discs used in picture as well as television transmission, etc.

PRINCIPLES OF RADIO. by Keith Henney, M.A. Cloth covers, size 8x5½", 478 pages, 306 illustrations. Price **\$3.50**

The author is well known in radio and he has here provided a very complete and clearly written discussion of radio circuits and apparatus, including such important topics as: condensers; transformers; determination of inductance;

vacuum tube action, including Screen Grid and Pentode; wave meters, their calibration and use; modulation; amplifiers; long wave receivers; and different types of rectifiers.

HOW TO PASS U. S. GOVERNMENT RADIO LICENSE EXAMINATIONS. by R. L. Duncan and C. E. Drew. Flexible covers, size 9½x7", 170 pages, 92 illustrations, appendix. Price **\$2.00**

The authors are thoroughly conversant with their subject and all of the most important information including hook-ups; types of antennae and receivers with wiring diagrams of both small and large receivers and transmitters of commercial type, including ship sets are given.

RADIO RECEIVING TUBES. by Moyer and Westrel. Cloth covers, size 7½x5½", 298 pages, 181 illustrations. Price **\$2.50**

No radio student or operator can do without this authoritative book on the radio vacuum tube. The various chapters include construction of vacuum tubes; electrical fundamentals; elementary action taking place in the vacuum tube, with graphs; reactivation of tubes; testing of tubes including determination of amplification factor; plate resistance; grid resistance, etc.

PRACTICAL RADIO—INCLUDING THE TESTING OF RADIO RECEIVING SETS. by James A. Moyer, S.B., A.M., and John F. Westrel. Cloth covers, size 8x5", 378 pages, 223 illustrations. Price **\$2.50**

Everyone will find this volume of the utmost practical value as the authors have explained in text and diagrams, for the practically-minded student, such interesting subjects as telephone receivers and crystal sets; various types of aerials; current sources for vacuum tubes; audio and radio frequency amplification with hookups; loud speakers and how they work; various radio receiving sets with diagrams and just how they work.

PRACTICAL RADIO CONSTRUCTION AND REPAIRING. by J. A. Moyer, S.B., A.M., and J. F. Westrel. Cloth covers, size 8x5", 354 pages, 163 illustrations. Price... **\$2.50**

This handbook is one that every radio set tester and general student will want to read carefully. These experts have given a very complete description of instruments used to test and repair modern radio sets, together with complete diagrams of many modern receiving sets, with explanations on how to test the radio and audio frequency stages for faults.

ELEMENTS OF RADIO COMMUNICATION. by Professor John H. Morecroft. Cloth covers, size 9x6", 270 pages, 170 illustrations. Price... **\$3.00**

Professor Morecroft explains in an authoritative and clear manner such important radio phenomena as current flow in circuits containing capacity and inductance; propagation of radio waves; vacuum tubes as detectors and amplifiers; fading of radio waves and its causes; neutralization; superheterodynes for short waves, etc.; audio frequency amplifiers; how filters work, etc.

RADIO TELEGRAPHY AND TELEPHONY. by R. L. Duncan and C. E. Drew. Cloth covers, size 9½x6", 950 pages, 468 illustrations. Price **\$7.50**

This 950 page book forms indeed a most complete treatise on radio facts. The authors treat thoroughly the magnetic circuit; Ohm's law; transformers and induction; motor generators and starters; storage batteries; alternating currents; capacity and inductance formulae. Vacuum tubes as detectors and amplifiers; oscillographs; radio compass; wavelength measurements and short wave receivers.

RADIO SERVICE MAN'S HANDBOOK WITH ADDENDA DATA SHEETS. Flexible covers, size 9x12", 200 pages, 200 illustrations. Price, prepaid **\$1.75**

This remarkable book contains several hundred illustrations with wiring diagrams and charts covering every conceivable subject, including radio sets, tubes, etc. The book is strictly up-to-date and contains the newest practical information which every radio man absolutely must have.

OFFICIAL RADIO SERVICE MANUAL. by Hugo Gernsback and Clyde Fitch. Flexible covers, size 9x12", over 1,000 illustrations, 352 pages. Price, prepaid **\$2.98**

Commercial wiring diagrams for all the regularly manufactured receiving sets are included in this manual and no radio service man or student who builds and repairs radio sets can be without this tremendously useful compilation of circuits and their descriptions. This book is worth \$100.00 to anyone who has a use for it. The Manual is indexed so that any commercial receiving circuit can be found instantly. One of the most valuable radio books ever published.

Howtoorder
We cannot make C.O.D. shipments. Our prices are net, as shown on this page. You will note that some of the books include postage. Those that do not will be shipped by express collect if you do not wish to include a sufficient amount of postage.

FUNDAMENTALS OF RADIO. by R. R. Ramsey, Professor of Physics, Indiana University. Cloth covers, size 9½x6", 372 pages, illustrated. Price, prepaid **\$3.50**

Dr. Ramsey gives us a very refreshing treatment of the fundamentals of radio, including battery and dynamo action; alternating currents; inductance; vacuum tube constants; aerials of different kinds and how they operate; radio frequency instruments and apparatus; audio amplification and receivers in general.

RADIO TROUBLE SHOOTING. by Ennor R. Haan, E.E. Flexible covers, size 6x9", 323 pages, 257 illustrations. Price **\$3.00**

This is a well illustrated and intensely practical handbook for all radio service men and operators, as well as set builders and testers. Some of the practical problems illustrated and discussed are: interference and noise problems—how to locate and remedy them; antenna circuit troubles and their effect on radio; batteries, chargers and eliminators.

DRAKE'S RADIO CYCLOPEDIA. by H. P. Manly. Cloth covers, size 6x9", 1035 pages, profusely illustrated. Price **\$6.00**

This massive cyclopedia covers radio apparatus—its operation and maintenance, the various subjects being alphabetically arranged. There are 1735 subjects in alphabetical order ranging from A-battery to zero-beat. This volume contains 1110 illustrations, diagrams, etc. There are 414 illustrations and articles on the building and designing of radio sets, alone; 110 articles with 383 illustrations on the methods of repair, service and adjustment of radio sets.

S. GERNSBACK'S RADIO ENCYCLOPEDIA. by S. Gernsback. Stiff leatherette covers, size 9x12", 168 pages, profusely illustrated. Price **\$1.45**

Radio apparatus, inventors and terms are all illustrated and described in this remarkable book which required the efforts of several engineers in its compilation. The subjects are alphabetically arranged and the illustrations are especially fine and clear.

TELEVISION TO-DAY AND TOMORROW. by S. A. Moseley and H. J. B. Chapple. Cloth covers, size 8x5½", 130 pages, profusely illustrated. Price, prepaid **\$2.50**

This up-to-the-minute work on television describes in detail the apparatus used by Baird. The student will learn all about scanning discs; the best type of motor; reverse defects and how to overcome them; isochronism and synchronism; various ways of synchronizing the receiving discs; photocells and neon tubes; radio receivers for television signals; noctovision.

SOUND PICTURES AND TROUBLE SHOOTER'S MANUAL. by Cameron and Rider. Cloth covers, size 8x5½", 1120 pages, profusely illustrated. Price **\$7.50**

This useful volume will appeal to all radio as well as "talkie" trouble-shooters. The first chapters deal with fundamentals of electrical circuits, including Ohm's law, A.C. and D.C. circuits, rectifiers, amplifiers, mixers and faders; various types of loud speakers and how to arrange them; photocells; electric motors; various types of talkie projectors; also commercial amplifiers with diagrams are given.

RIDING THE AIR WAVES, WITH ERIC PALMER, JR. by himself. Cloth covers, size 7½x5½", 328 pages. Price **\$2.00**

Short wave fans cannot miss reading this highly entertaining and informative book which tells the story of youthful Mr. Palmer and his remarkable achievements in amateur radio. "Around the World with 5 Watts" and many other interesting subjects appear between the covers of this book.

A POPULAR GUIDE TO RADIO by B. Francis Dashiell. Cloth covers, size 5½x8½", 236 pages, profusely illustrated. Price, prepaid **\$3.50**

The author starts off with an excellent section on electricity and magnetism; the use of radio aerials and grounds; the fundamental principles of radio; the electron tube and crystal rectifiers—how they work; the principle of radio amplification; radio inductance coils and condensers; fundamental radio receiving circuits; electrical reproduction of sound; the atmosphere and radio phenomena, etc.

RADIO VISION. by C. Francis Jenkins. Cloth covers, size 9½x6", 144 pages, profusely illustrated. Price, prepaid **\$1.25**

A beautifully printed and interesting illustrated history of transmission of images by radio; particularly covering the apparatus and successful demonstrations of the Jenkins system. Other apparatus illustrated and discussed are the Braun tube receiver; the R. C. A. Photo-radio apparatus; the A. T. & T. Company system; and the Bell machine.

RADIO MOVIES. by C. Francis Jenkins. Cloth covers, size 9½x6", 144 pages, profusely illustrated. Price, prepaid **\$1.25**

An absorbing history, handsomely illustrated, of the Jenkins system of transmitting and receiving movies "via radio." One of the chapters gives constructional details and drawings for building your own Radiovisor or machine for making the radio movies visible in your home. Diagrams of amplifiers are given, with some other very valuable information.

BIG SCOOP

MESCO Keys

Standard for 20 years. Lists from \$3 to \$5. We just bought a big quantity. Better get them while they last at these special prices.



No. 101

No. 101..... 95c
No. 103..... \$1.75
No. 244..... 1.75




No. 244



No. 103

THORDARSON DOUBLEFILTER CHOKES

Contains Two 18 Henry 250 Mill Chokes

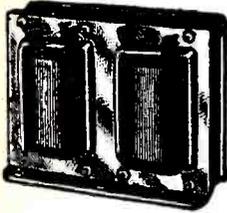

Model T-2458

Heavy duty, rugged double Filter Reactor for Filter Circuits in Transmitters, Power Amplifiers, "B" Eliminators and various other purposes. Each Choke has a 2000 Volt insulation and the D.C. resistance of each Choke is 108.5 ohms. When connected in series this Filter Reactor has a capacity of 36 henries at 250 mils. and when connected in parallel 18 henries with 500 mils. carrying capacity.

Special, \$6.25

GEN. RADIO WAVEMETER

TYPE 558 AMATEUR BAND



Type 558 Amateur-Band Wavemeter, a fixed air condenser is connected in parallel with the variable condenser. This arrangement spreads a narrow band of frequencies over the entire wavemeter scale which greatly increases the accuracy of reading. Five coils are used, covering the following amateur bands:

Coil A 4.6 to 5.4 Meters
Coil B 9.4 to 10.9 Meters
Coil C 18.5 to 21.5 Meters
Coil D 37.0 to 43.0 Meters
Coil E 75.0 to 86.0 Meters

The accuracy of calibration is to within 0.25%.

Type 558 Amateur-Band Wavemeter \$18.00

LEEDS

The Home of RADIO

45A VESEY STREET
NEW YORK

New York's Headquarters for
Transmitting Apparatus

When in Town Visit Our Store

Everything in
ACME JEWELL WESTON PYREX
BRADLEY FLERON
THORDARSON
ELECTRAD NATIONAL
LYNCH SIGNAL
FLECHTHEIM
NATIONAL RECTOULB
GENERAL RADIO
CARDWELL
SAMSON EVEREADY
KINO AND TELEVISION CELLS
In Stock



Type PL571

Dubilier High Voltage Filter Condenser

4 Mfd. D.C. Working Voltage 600 V.

These Filter Condensers are designed for use in filter circuits in Transmitters, and all high Voltage Socket power devices and Power Packs. Special \$1.80



DUBILIER CONDENSERS

400 Volts D. C. Working Voltage

Type 902-3 Mfd.—5" high, 2" wide, 2 1/4" deep. \$1.35
List \$4.50. Special..

7 Mfd.—5" high, 2" wide, 4 1/2" deep. List \$7.50. Special..... \$1.75

GOOD NEWS

We have added 100% more space to our store. Our stocks are bigger than ever and our service continues par excellence.

A C M E

Variable Ratio Audio Transformer


Ranges from 2 to 1 up to 20 to 1 ratio. Ideal for the short-wave set for high gain. Useful in the lab. for all kinds of experimental work. List \$1.65 price \$7.00 each. Special.....

MESCO Half Inch Spark Coil



The coil of a 101 uses. Can be used as a peaked audio choke, with fixed condensers, etc. Many other uses will suggest themselves to the experimenter. Reg. 7. Special \$1.50

THORDARSON TRANSFORMER

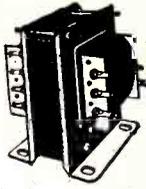

150 watts, 400 volts each side of centre tap at 375 M. A. 5 volt filament, centre tap. Fine for power supply for 7 1/2 watt or for crystal control power supply. Specially priced for a short time only. each..... \$3.50



FILTER CHOKE

30 Henry, 150 Mill—special heavy choke, good for filter circuits for transmitters up to and including one UX852, or as a modulation choke on medium power transmitters. Specially priced at..... \$3.25


LEEDS RADIO LABORATORIES

Precision Custom Built Short Wave Receivers and Transmitters

This department under the supervision of the Short Wave Specialist Jerome Gross. We design, construct and advise on any material for the "Ham" Broadcasting station or laboratory. Write Jerry Gross for advice on any of your problems.

The LEEDS 1930 SPECIAL

A short wave receiver that's got them all beat. Best circuit design and finest mechanical construction. Praised by "Hams" everywhere as the greatest short wave receiver ever made. The secret of the success of the Leeds Short-wave Receiver is due to its marvelously smooth regeneration control. Ease of handling through this perfect control of the detector tube is the outstanding feature of this receiver.

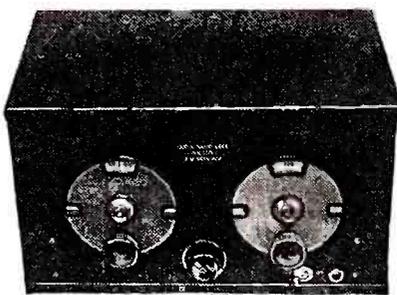

In use by a constant host of Hams from coast to coast. 3-tube Receiver—detector—2 audio, using three 201-A tubes. Universal type, continuous range 15 to 100 meters; amateur type covers Ham bands 20-40-80 meters with generous spread on the dial.


Special Offer, Net \$37.50

3 Coils as illustrated \$6.50

Leeds Listening MONITOR



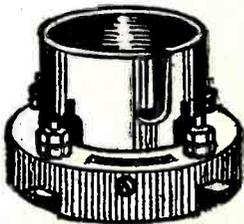For checking your note, its stability and whether D.C. or not. THE ONLY SURE CHECK. Give you an accurate idea as to what your signal sounds like to the other fellow. The Leeds Monitor is encased in an aluminum shield 5"x6"x9" overall. Completely shielded, with batteries self contained. Supplied with A. & B. batteries, but without 1-UX 199 tube. Special \$15.00



By Insistent Demand


LEEDS 50-watt socket, positive contact; heavy phosphor bronze springs, heavy brass shell; highest grade porcelain insulated base; will hold your tube in one position. Specially priced.

Make your own transmitting and receiving coils. Copper tubing transmitting inductance.

Size of tubing		
2 1/8"	9c	1 1/8"
2 3/8"	9c	1 1/4"
3 1/8"	10c	1 1/2"
		1 3/4"
		1 7/8"
		2"

Prices per turn

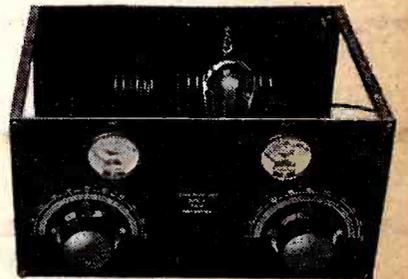New LEEDS The 1930 7 1/2-Watt Transmitter, That Has Set the Country Talking



—kit \$55. Completely constructed \$70. \$57.50*
Special Offer, completely constructed....

NEON GLOW LAMPS



Made by General Electric Co., type G. 10, standard base, 101 uses, as illustrated in QST May Issue, page 17. Price only 65c
Standard electric socket for tube... 15c

WIRE

No. 14 Enamel 3/4c Foot
No. 12 " 1c "
No. 10 " 1 1/2c "
Any length up to 1000 feet

PLEASE PRINT YOUR NAME AND ADDRESS PLAINLY TO AVOID DELAY. WRITE FOR SPECIAL PRICE LIST.

Important! You may deduct 2% cash discount with any order taken from this page, provided you mention SHORT WAVE CRAFT.


MAIL ORDERS FILLED SAME DAY
10% Deposit Must Accompany All C. O. D. Orders

LET RCA INSTITUTES START YOU ON THE ROAD TO . . . SUCCESS IN RADIO

Radio needs you... That's why the entire Radio industry is calling for trained men... That's why thousands of men who answered these advertisements are now earning from \$2,000 and up a year. Radio is highly interesting work... with opportunities that are yet unlimited. Manufacturers and broadcasting stations are now eagerly seeking trained RCA Institute men... Aviation and radio in the movies also provide innumerable opportunities... Millions of sets need servicing... thousands of ships require experienced operators... Never before was there an opportunity like this in Radio.



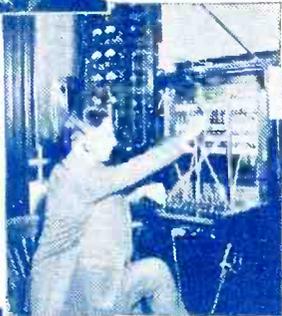Radio Mechanic and Inspector \$1800 to \$4,000 a Year.



Broadcast Station Mechanic \$1800 to \$3600 a Year.



Land Station Operator \$1800 to \$4000 a Year.



Broadcast Operators \$1800 to \$4800 a Year.

This is the Only Course Sponsored by Radio Corporation of America

RCA sets the standards for practically the entire Radio industry... The RCA Institutes' Home Laboratory Training Course enables you to learn more than the mere ABC's of Radio... In your spare time, in only an hour or so a day, you can obtain a thorough, practical education in Radio... You get the inside information, too, because you study right at the source of all the latest, up-to-the-minute developments. RCA, the world's largest Radio organization, sponsors every single detail in this course.

You learn Radio by actual experience with the remarkable outlay of apparatus given to every student. You learn the "How" as well as the "Why" of every Radio problem, such as repairing, installing and servicing fine sets. That's why every graduate of RCA Institutes has the experience, the ability and the confidence to hold a worthwhile Radio job.

Practical Instruction for You to Study in Your Own Home

RCA Institutes offers four different courses... certainly instruction that you need. A complete serviceman's and repairman's technical course... advanced course... complete course without code... and a complete course including code. And practical instruction with each course. Courses that teach construction, repairing, service, broadcasting and ship operating.

Graduates of RCA Institutes Find It Easier to Get Good Jobs

They are closest to the source of Radio's greatest achievements because so much of the progress of Radio is measured by the accomplishments of the great engineers in the huge research laboratories of the Radio Corporation of America.

Students of RCA Institutes get first-hand knowledge, get it quickly and get it complete. Success in radio depends upon training and that's the training you get with RCA Institutes. That's why every graduate who desired a position has been able to get one... That's why graduates are always in big demand.

Study Radio at the Oldest and Largest Commercial Training Organization in the World

Send for our Free Book... it will explain our practical methods of training that has prepared hundreds of men for success in Radio. Remember that you, too, can be successful... can speed up your earning capacity... can earn more money in Radio than you ever earned before. The man who trains today will hold down the worthwhile Radio job of the future. Come in and get our free book or send for it by mail. Everything you want to know about the opportunities in Radio. Forty fascinating pages, packed with pictures and descriptions of brilliant opportunities in this gigantic, world-wide profession.

See for yourself why graduates of RCA Institutes now occupy thousands of well-paid positions. These positions are usually available in from 3 to 10 days after graduation for men who can qualify. RCA Institutes will back you up to the limit. Our catalogue is yours free... SEND FOR IT TODAY!

Clip this Coupon NOW!



RCA INSTITUTES, Inc.
Dept. S.W.C.12, 75 Varick St., N. Y.

Gentlemen: Please send me your FREE 40-page book which illustrates the brilliant opportunities in Radio and describes your laboratory-method of instruction at home!

Name.....

Address.....

State.....

RCA INSTITUTES, INC.

A Division of the
Radio Corporation of America

SPONSORED BY



The Greatest Thrill in Radio . .

WORLD WIDE SHORT WAVE RECEPTION



The Best Short Wave Reception Unit

• PILOT Super-Wasp

(A. C. OR D. C. SHORT WAVE KIT—14 TO 500 METERS)

It is not only home set builders who are buying the thousands of Super-Wasps Pilot is shipping every week. The fellows who relay messages all over the world for the sheer joy of it—the *Licensed Radio Amateurs*—are also adopting Super-Wasp as their official outfit for receiving broadcasts, talk and code.

These experts, who developed short waves before any manufacturer knew anything about them, know why Super-Wasp is superior. They are convinced that the feature Pilot pioneered of putting a Screen Grid, TRF stage ahead of the detector gets more stations than their own old straight regenerative sets. They know too that in a few hours they can produce a neater receiver for their operator's table with the inexpensive Super-Wasp Kit than if they bought expensive separate parts and experimented till they worked right.

You can tell a leader by how many followers he has. Pilot Super-Wasp's success is proved by its many imitators. Remember, Pilot Super-Wasp covers from 14 to 500 meters, giving you practically all the regular broadcasting channels as well as short waves. And don't overlook the fact that Pilot products are known *personally* to more users throughout the world than any others and that every single Pilot product is made in the largest factory in the world owned and operated by a radio manufacturer.

BATTERY SETS
IN KIT FORM

\$29.⁵⁰

Kit K-110: The battery-operated Super-Wasp. Batteries and Tubes extra.



A. C. SETS
IN KIT FORM

\$34.⁵⁰

Kit K-115: The A.C. Super-Wasp. Use your own ABC pack or Pilot K-111, specially designed for the Super-Wasp. Power Pack and Tubes extra.

PILOT RADIO & TUBE CORP.

OFFICES IN PRINCIPAL COUNTRIES
OF THE WORLD



FACTORIES: LAWRENCE, MASS.

Chicago Office
234 S. Wells Street
New York Office—525 Broadway

San Francisco Office
1278 Mission Street

PILOT SUPER-WASP RADIO
FOR LONG AND SHORT
WAVE RADIO RECEPTION

ALASKA
CANADA
GREENLAND
MEXICO
COSTA-RICA
GUATAMALA
HONDURAS
PANAMA
SALVADOR
BERMUDAS
CUBA
WEST INDIES
HAITIAN
REPUBLIC
COLOMBIA
GUIANA
VENEZUELA
ARGENTINA
BRAZIL
URUGUAY
BOLIVIA
CHILE
ECUADOR
ENGLAND
IRELAND
FRANCE
BELGIUM
GERMANY
HUNGARY
SWITZERLAND
POLAND
RUSSIA
GIBRALTAR
ITALY
PORTUGAL
SPAIN
BULGARIA
RUMANIA
TURKEY
ARABIA
PERSIA
INDIA
CEYLON
JAVA
PHILIPPINE
ISLAND
SIAM
CHINA
JAPAN
ALGERIA
EGYPT
MOROCCO