

RADIO & TELEVISION

FORMERLY
S SHORT WAVE & TELEVISION



TELEVISION

"SIGHT EFFECTS"

SEE PAGE 710

In This Issue —

Frequency Modulated Receiver

What is the Rhumbatron?

Television Course

International Radio Review

All-Wave 8-tube Receiver

Universal Test Meter

Radio Test Quiz




**HUGO
GERNSBACK**
EDITOR

RADIO EXPERIMENTING AMATEUR RADIO

25¢
IN U.S. AND
CANADA

**APRIL
1939**

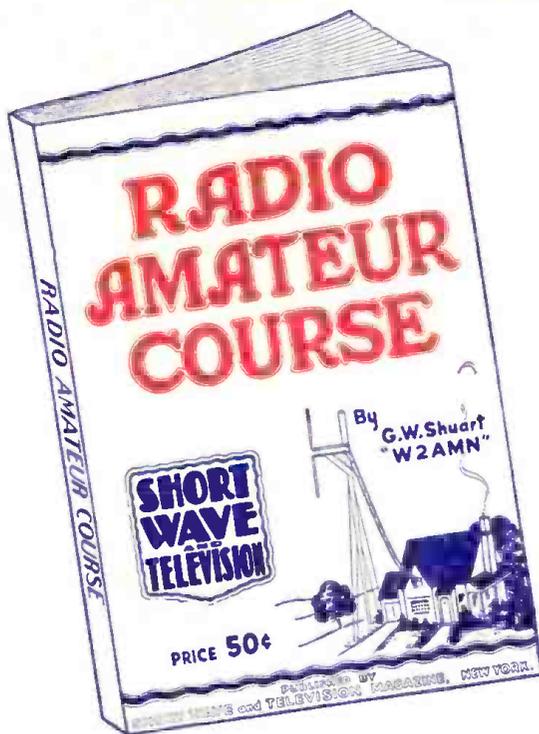

Your Money Back—

IF THE RADIO AMATEUR COURSE DOES NOT REPRESENT THE GREATEST BOOK VALUE EVER OFFERED TO THE RADIO "FANS" FOR 50¢

TO convince you that there isn't a better book buy today, the publishers of the **RADIO AMATEUR COURSE** make the sensational offer of a money-back guarantee on such a low-priced book. Stop in at any of the many dealers listed at the right and examine this volume. See for yourself if the **RADIO AMATEUR COURSE** isn't just the book you've always wanted.

Printed on the finest quality paper—well illustrated attractive 4-color cover—complete with radio information you must have. It contains a step-by-step program for obtaining a short-wave radio education.

*Written by George W. Shuart, W2AMN,
foremost short-wave authority*

148 PAGES

6¼ x 9½ INCHES

**OVER 150 RADIO DIAGRAMS
and TECHNICAL PHOTOGRAPHS**

RADIO AND TELEVISION

99 Hudson Street, New York, N. Y.

**All Prominent RADIO DEALERS
Ready to Show You This Big Book!**

- ARIZONA**
Sam's Cigar Store,
127 N. First Ave., Phoenix.
- CALIFORNIA**
Scott Wholesale Radio Co.,
344 E. Fourth Street, Long Beach.
Offenbach Electric Co., Ltd.,
1452 Market Street, San Francisco.
Zack Radio Supply Co.,
1426 Market Street, San Francisco.
- COLORADO**
Auto Equipment Co.,
4th at Lawrence, Denver.
- CONNECTICUT**
Radio Inspection Service Co.,
277 Asylum Street, Hartford.
Stern Wholesale Parts, Inc.,
210 Chapel St., Hartford.
- GEORGIA**
Wholesale Radio Service Co., Inc.,
430 W. Peachtree St., N. W., Atlanta.
- ILLINOIS**
Allied Radio Corporation,
833 West Jackson Blvd., Chicago.
Newark Electric Company,
226 W. Madison Street, Chicago.
Wholesale Radio Service Co., Inc.,
801 W. Jackson Blvd., Chicago.
- INDIANA**
Van Sickle Radio, Inc.,
84 West Ohio Street, Indianapolis.
- MASSACHUSETTS**
Greater Boston Distributors,
49 Waltham St., Boston.
H. Jappe Co., 46 Cornhill, Boston.
Wholesale Radio Service Co., Inc.,
110 Federal Street, Boston.
Springfield Radio Co.,
377 Dwight Street, Springfield.
H. Jappe Co.,
87 Mechanic Street, Worcester.
- MICHIGAN**
Rissl Brothers, Inc.,
6027 Hamilton Ave., Detroit.
- MISSOURI**
Modern Radio Company,
409 No. Third Street, Hannibal.
Burstain-Applebee Co.,
1012-14 McGee Street, Kansas City.
Van Sickle Radio Co.,
1113 Pine Street, St. Louis.
- NEBRASKA**
Radio Accessories Company,
2566 Farnam Street, Omaha.
- NEW JERSEY**
Arco Radio Co.,
227 Central Avenue, Newark.
Wholesale Radio Service Co., Inc.,
219 Central Avenue, Newark.
- NEW YORK**
Wholesale Radio Service Co., Inc.,
542 E. Fordham Rd., Bronx.
Wholesale Radio Service Co., Inc.,
90-93 166th Street, Jamaica, L. I.
Llan, The Radio Man, Inc.,
64 Dey Street, New York City.
Eagle Radio Co.,
84 Cortlandt Street, New York City.
Federated Purchaser, Inc.,
25 Park Place, New York City.
Harrison Radio Co.,
12 West Broadway, New York City.
Sun Radio Co.,
212 Fulton Street, New York City.
Terminal Radio Corp.,
80 Cortlandt Street, New York City.
Thor Radio Corp.,
60 Dey St., New York City.
Try-No Radio Co., Inc.,
85 Cortlandt Street, New York City.
Wholesale Radio Service Co., Inc.,
109 Sixth Avenue, New York City.
Radio Parts & Equipment Co.,
244 Clinton Avenue No., Rochester.
M. Schwartz & Son,
710-712 Broadway, Schenectady.
- NEW HAMPSHIRE**
Radio Service Laboratory,
1187 Elm Street, Manchester.
- OHIO**
News Exchange,
51 So. Main Street, Akron.
Canton Radio & Supply Co.,
1140 Tuscarawas Street, W., Canton.
United Radio, Inc.,
1103 Vine Street, Cincinnati.
The Hughes-Peters Electric Corp.,
178-180 N. Third Street, Columbus.
Standard Radio Parts Co.,
135 East Second Street, Dayton.
- OREGON**
Portland Radio Supply Co.,
1300 W. Burnside Street, Portland.
- PENNSYLVANIA**
Radio Distributing Co.,
1124-26 Market Street, Harrisburg.
M. & H. Sportin' Goods Co.,
512 Market Street, Philadelphia.
Cameradio Co.,
963 Liberty Ave., Pittsburgh.
- RHODE ISLAND**
W. H. Edwards Co.,
32 Broadway, Providence, R. I.
- TEXAS**
Amarillo Electric Co.,
111 East 8th Avenue, Amarillo.
- UTAH**
O'Loughlin's Wholesale Radio Supply,
315 South Main Street, Salt Lake City.
Radio Supply, Inc.,
46 Exchange Place, Salt Lake City.
- WASHINGTON**
Spokane Radio Co., Inc.,
611 First Avenue, Spokane.
- WISCONSIN**
Radio Parts Co., Inc.,
536-538 W. State Street, Milwaukee.
- AUSTRALIA**
McGill's Agency,
183-184 Elizabeth Street, Melbourne.
- CANADA**
The T. Eaton Co., Ltd.,
Winnipeg, Manitoba.
Canadian Electrical Supply Co., Limited,
285 Craig Street W., Montreal, Que.
Metropolitan News Agency,
1248 Peel Street, Montreal, Que.
- CUBA**
The Diamond News Co.,
Palacio Asturiano, Por San Jose,
Habana.
- ENGLAND**
Gorrings' American News Agency,
9a. Green Street, Leicester Square,
London, W.C.2.
- HOLLAND**
Radio Peeters, Van Woustraat, Amster-
dam, Z.
- INDIA**
Empire Book Mart,
Box 631, Bombay.
- MEXICO**
American Book Store, S. A.,
Avenida Madero 25, Mexico City.
Central De Publicaciones,
Avenida Juarez, 4, Apartado 2430,
Mexico, D. F.
- NEW ZEALAND**
Te Aro Book Depot, Ltd.,
64 Courtenay Place, Wellington.
- SOUTH AFRICA**
Technical Book Co.,
147 Longmarket Street, Cape Town.

If this book is not at your dealer's, send your order directly to us. We will credit your dealer with the sale of this book. To order your copy of RADIO AMATEUR COURSE, fill in coupon below and mail.

RADIO AND TELEVISION, 99 Hudson St., New York, N. Y.
Gentlemen: I enclose herewith my remittance of Fifty Cents (50¢) for which please send me **POSTPAID**, my copy of the **RADIO AMATEUR COURSE**. (Remit by check or money order; register letter if you send cash or unused U. S. Postage Stamps.)

Name

Address

City State R&T-439

A FREE LESSON SHOWED BILL HOW HE COULD MAKE GOOD PAY IN RADIO

BILL, YOU'RE ALWAYS FOOLING WITH RADIO -- OUR SET WON'T WORK -- WILL YOU FIX IT?

I'LL TRY, MARY, I'LL TAKE IT HOME TONIGHT

I CAN'T FIND OUT WHAT'S WRONG -- GUESS I'LL MAKE A FOOL OF MYSELF WITH MARY

HELLO BILL -- GOT A TOUGH ONE TO FIX? LET ME HELP YOU

HELLO JOE -- WHERE'VE YOU BEEN LATELY -- AND WHERE DID YOU LEARN ANYTHING ABOUT RADIO?

I'VE BEEN STUDYING RADIO AT HOME, BILL, WITH THE NATIONAL RADIO INSTITUTE. YOU OUGHT TO TAKE THEIR COURSE. I'VE GOT A GOOD RADIO JOB NOW. LET'S MAKE A CIRCUIT DISTURBANCE TEST -- STARTING WITH THE AUDIO OUTPUT STAGE AND TESTING EVERY STAGE RIGHT BACK TO THE ANTENNA. LISTEN FOR THE CLICKS WHEN I TAP THE GRID LEADS

SAY -- WHERE DID YOU LEARN THAT TEST? IT'S A GOOD ONE

HERE'S THE TROUBLE, BILL, IN THE FIRST I.E. AMPLIFICATION STAGE. I LEARNED THAT TEST EVEN BEFORE I STARTED TAKING THE COURSE, BILL. IT'S DESCRIBED IN A FREE LESSON WHICH THE NATIONAL RADIO INSTITUTE SENDS YOU WHEN YOU MAIL A COUPON FROM ONE OF THEIR ADS

I'VE SEEN THEIR ADS BUT I NEVER THOUGHT I COULD LEARN RADIO AT HOME -- I'LL MAIL THEIR COUPON RIGHT AWAY

I'M CONVINCED NOW THAT THIS COURSE IS PRACTICAL AND COMPLETE. I'LL ENROLL NOW

AND THEN I CAN MAKE REAL MONEY FIXING RADIO SETS

OR INSTALL AND SERVICE LOUD SPEAKER SYSTEMS

OR GET A JOB WITH A RADIO BROADCASTING OR TRANSMITTING STATION

AVIATION RADIO, POLICE RADIO, TELEVISION, ELECTRONIC CONTROLS -- RADIO IS SURELY GOING PLACES. AND THE NATIONAL RADIO INSTITUTE HAS TRAINED HUNDREDS OF MEN FOR JOBS IN RADIO

I will send you a Lesson on Radio Servicing Tips FREE TO SHOW HOW PRACTICAL IT IS TO TRAIN AT HOME FOR GOOD JOBS IN RADIO

Clip the coupon and mail it. I will prove I can train you at home in your spare time to be a RADIO EXPERT. I will send you my first lesson FREE. Examine it, read it, see how clear and easy it is to understand -- how practical I make learning Radio at home. Men without Radio or electrical knowledge become Radio Experts, earn more money than ever as a result of my training.

Why Many Radio Experts Make \$30, \$50, \$75 a Week

Radio broadcasting stations employ engineers, operators, station managers and pay well for trained men. Fixing Radio sets in spare time pays many \$200 to \$500 a year -- full time jobs with Radio jobbers, manufacturers and dealers as much as \$30, \$50, \$75 a week. Many Radio Experts open full or part time Radio sales and repair businesses. Radio manufacturers and jobbers employ testers, inspectors, foremen, engineers, servicemen. In good-pay jobs with opportunities for advancement. Automobile, police, aviation, commercial Radio, loud speaker systems are newer fields offering good opportunities now and for the future. Television promises to open many good jobs soon. Men I trained have good jobs in these branches of Radio. Read how they got their jobs. Mail coupon.

Many Make \$5, \$10, \$15 a Week Extra in Spare Time While Learning

The day you enroll I start sending Extra Money Job Sheets; show you how to do Radio repair jobs. Throughout your training I send plans and directions that make good spare time money -- \$20 to \$50 -- for hitherto, while learning. I send you special Radio equipment to conduct experiments and

build circuits. This 50-50 method of training makes learning at home interesting, fascinating, practical. I devote more than 10 Lesson Texts exclusively to Television methods and applications, and cover Television fundamentals thoroughly in my Course.



I Also Give You This Professional Servicing Instrument

Here is the instrument every Radio expert needs and wants -- an All-Wave, All-Purpose, Set Servicing Instrument. It contains everything necessary to measure A.C. and D.C. voltages and current; to test tubes, resistance; adjust and align any set, old or new. It satisfies your needs for professional servicing after you graduate -- can help you make extra money fixing sets while training.


Get Sample Lesson and 64 page Book FREE -- Mail Coupon

In addition to my Sample Lesson, I will send you my 64-page book, "Rich Rewards in Radio." Both are FREE to anyone over 16 years old. My book points out Radio's spare time and full time opportunities and those coming in Television; tells about my Training in Radio and Television; shows you letters from men I trained, telling what they are doing and earning; shows my Money Back Agreement, or Paste it on a penny postcard.

J. E. Smith, Pres., National Radio Institute Dept. 9DB3, Washington, D. C.



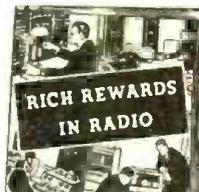J. E. SMITH
President
National Radio Institute
Established 25 years
He has directed the training of more men for the Radio Industry than anyone else.



YOU CERTAINLY KNOW RADIO SOUNDS AS GOOD AS THE DAY I BOUGHT IT.

THANKS! IT CERTAINLY IS EASY TO LEARN RADIO THE N.R.I. WAY. I STARTED ONLY A FEW MONTHS AGO, AND I'M ALREADY MAKING GOOD MONEY.

THIS SPARE TIME WORK IS GREAT FUN AND PRETTY SOON I'LL BE READY FOR A FULL TIME JOB

OH BILL -- I'M SO GLAD I ASKED YOU TO FIX OUR RADIO. IT GOT YOU STARTED THINKING ABOUT RADIO AS A CAREER. AND NOW YOU'RE GOING AHEAD SO FAST

OUR WORRIES ARE OVER. I HAVE A GOOD JOB NOW, AND THERE'S A BIG FUTURE AHEAD FOR US IN RADIO

J. E. SMITH, PRESIDENT, DEPT. 9DB3 NATIONAL RADIO INSTITUTE, WASHINGTON, D. C.

Dear Mr. Smith: Without obligation, send me a sample lesson and your free book which points out spare time and full time Radio opportunities, and shows how I can train for them at home in spare time -- about the N.R.I. Set Servicing Instrument you give. (Please write plainly.)

Name Age

Address

City State

14X-1

RADIO & TELEVISION

The Popular Radio Magazine

APRIL — 1939
Vol. IX No. 12

HUGO GERNSBACK, Editor
H. WINFIELD SECOR, Manag. Editor
ROBERT EICHBERG, Assoc. Editor

FLASH!

Television Sight Effects

See page 710

In This Issue

GENERAL FEATURES

Antennas—Past, Present and Future—Harold H. Beverage, Chief Research Engineer, RCA Communications	709
Television "Sight Effects"—H. W. Secor	710
What Is a Rhumbatron?	712
World-Wide Radio Digest	713
International Radio Review	716
Radio Test-Quiz—Robert Eichberg	719
The Martian Flash—H. Gernsback	720

CONDENSED FEATURES

New York and London Mayors Talk by Short Wave	713
The 50,000 Hour Tube	715
Fire-Fighting at the Fair	715
Facsimile Reaches the Public	715
Vertical or Horizontal Television Doublets?	716
Electronic Musical Instruments	717
Reducing Hum in S. W. Receivers	718
Circuit Breakers Protect Tubes	718
Simple Radio Time Switch	718
Baffling for High Fidelity	718
New Pick-Up Feed	718

INSTRUCTION

Radio Test-Quiz	719
The Radio Beginner—Lesson 6—Martin Clifford, W2CDV	724
Electronic Television Course—Henry Townsend	725
Question Box	740

TELEVISION

Television "Sight Effects"	710
Television's Interference Problem	713

Cover composition by H. Gernsback and Thomas D. Pentz.
Television "Sight Effects" staff at work. Photos courtesy N.B.C.

RADIO & TELEVISION—Published monthly on the tenth of the month. Entered as second-class matter Feb. 15, 1938, at the post office at Springfield, Mass., under the act of March 3, 1879. Trademarks and copyrights by permission of H. Gernsback. Text and illustrations are copyright and may not be reproduced without permission. Subscription price \$2.50 a year in the United States and possessions and Canada, \$3.00 in foreign countries. Make all subscription checks payable to Popular Book Corporation.

Published by Popular Book Corporation. Publication Office—29 Worthington St., Springfield, Mass. Editorial and Executive Offices—99 Hudson St., New York, N.Y. HUGO GERNSBACK, President; H. W. SECOR, Vice-President; EMIL GROSSMAN, Director of Advertising. European Agents: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, Fleet St., London, England; Brentano's—London and Paris. Australian Agents: McGill's Agency, 179 Elizabeth St., Melbourne.

Copyright 1939 by H. Gernsback

CONSTRUCTION

Frequency Modulation Receiver	721
Ultra High Frequency Antennas	731
Antenna Systems for Hams	731
Radio Kinks	733
6-Tube 1.4 Volt Superhet for Hams and Fans—Harry D. Hooton, W8KPX	734
An All-Wave 8-Tube Receiver—Range 7 to 2306 Meters—Herman Yellin, W2AJL	736
Universal Test Meter, 2500 Volt Range	738
A New Communications Receiver—McMurdo Silver	742

General Electric Answers Television Questions	713
Vertical or Horizontal Television Doublets	716
Separating Video and Audio Signals	717
Television Course	725

MISCELLANEOUS

The Rhumbatron	712
The Martian Flash—"Fips Returns"—H. Gernsback	720
Ultra-High Freq. Antennas	722
What Do YOU Think?	723
Elementary Radio Lessons	724
World Short Wave Stations	726
"Let's Listen In" with Joe Miller	727
Tenth Silver Trophy Award for Best "Ham" Station Photo	729
Radio Kinks	733
Question Box	740
New Ham Licenses	741
! Cover the Pacific Coast	744
New Radio Apparatus	755
Short Wave League—"On the Ham Bands"—Elmer R. Fuller	764

Next Month

DeLuxe Transmitter—"Beam Power 3"—H. G. McEntee, W2FHP
A High Efficiency 6L6 Exciter—Harry D. Hooton, W8KPX
An Exceptional 4-Tube Receiver—Francis J. Bauer
Push-Button Remote Control Unit for Your Receiver—C. W. Palmer, E.E.
A 2.5, 5 and 10 Meter U.S.W. Converter—Herman Yellin, W2AJL
How To Build A Television Receiver



Certified Circuits

When you see this seal on a set it is a guarantee that it has been tested and certified in our laboratories, as well as privately in different parts of the country. Only construction—experimental sets are certified.


You need not hesitate to spend money on parts because the set and circuit are bona fide.

This is the only magazine that renders such a service.




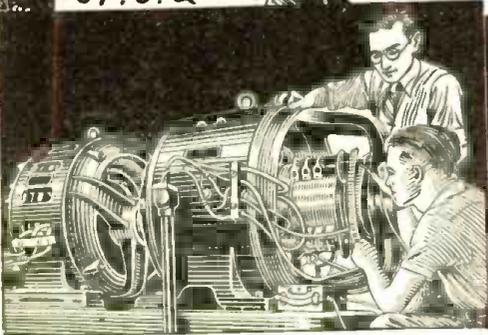H. C. Lewis

QUICK, EASIER WAY To TRAIN FOR **ELECTRICITY** 12 Weeks *Practical WORK* IN MY CHICAGO SHOPS



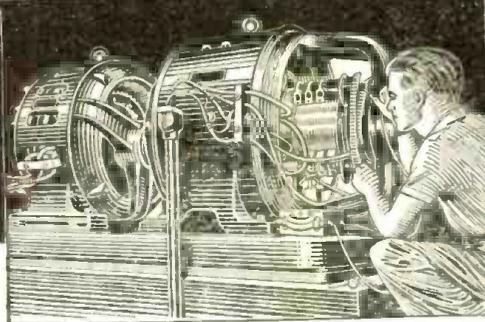FIRST—You are told and shown how to do it.



THEN—You do the job yourself.



HOUSE WIRING
only one of the many
branches you
"Learn By Doing."

WANT TO EARN MORE MONEY?

Have you ever dreamed of holding down a steady, good pay job? Have you ever dreamed of doing the work you really like in a job that holds promise of a real future in the years ahead?

Well, we all know that you can't get the good things in life by just dreaming about them. Hundreds of fellows are today holding down mighty fine jobs with prospects of a bright future. They are filling these jobs because they had the foresight to equip themselves with the right kind of training. Most of these men were only average fellows a short time ago, but the proper training helped to lift them out of the low pay ranks of unskilled workers. The same opportunity is now offered to you.

The great fascinating field of ELECTRICITY offers a real future to many men and young men who are willing to prepare for a place in this giant industry.


Here at my school in Chicago, the world's Electrical Center, you can get 12 weeks' Shop Training in ELECTRICITY, that can help give you your start towards a better job.

You will be trained on actual equipment and machinery and because of our method of training, you don't need previous experience or a lot of education. Many of my successful graduates never even completed Grammar School.

Here in my school you work on generators, motors, dynamos, you do house wiring, wind armatures and do actual work in many other branches of electricity and right now I'm including valuable instruction in Diesel, Electric Refrigeration and Air Conditioning at no extra cost. Our practical shop methods make it easier to learn—First the instructors tell you how a thing should be done—then they show you how it should be done—then you do the actual work yourself.



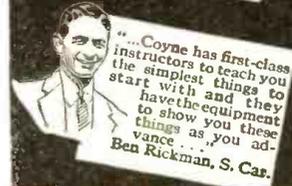"...Everything was just as stated in literature. And by Coyne methods plenty of instructorstotake care of every- thing, easy to learn. I really was satisfied with Coyne Training."
J. Halyk, Canada



"...Coyne has first-class instructors to teach you the simplest things to start with and they have the equipment to show you these things as you advance..."
Ben Rickman, S. Car.

I'LL FINANCE YOUR TRAINING

You can get this training first—then pay for it later in easy monthly payments, starting 60 days after your 12 weeks' training period is over—then you have 12 months to complete your payments.

If you need part time work to help out with expenses while training in my shops, my employment department will help you get it. Then after graduation this department will give you valuable lifetime employment service.

Send the coupon today for all details. When I get it I'll send you my big free book containing dozens of pictures of students at work

H. C. LEWIS, President

COYNE ELECTRICAL SCHOOL
500 S. Paulina St., Dept. 49-81, Chicago

in my shops. I'll also tell you about my "Pay After Graduation" plan, how many earn while learning and how we help our students after graduation. Fill in, clip coupon, mail it today for your start toward a brighter future.



H. C. LEWIS, President
COYNE ELECTRICAL SCHOOL
500 South Paulina Street, Dept. 49-81, Chicago, Ill.


Dear Sir: Please send me free your big catalog and full particulars of your present offer, also your "Pay-Tuition-After-Graduation" Plan.

NAME _____
ADDRESS _____
CITY _____ STATE _____

Please say you saw it in RADIO & TELEVISION

...THESE OUTSTANDING SHORT WAVE BOOKS ARE NOW AVAILABLE AT YOUR DEALER!

YOU buy parts, tubes, kits, accessories from your local radio dealer—that's what countless thousands of short-wave fans do. Now through a nation-wide distribution service our numerous books are available at your favorite radio dealer—right where you buy other radio equipment. It's more convenient, saves time and you can inspect the books before you buy. Ask your dealer to show you all the books advertised on this page—they're always in stock.

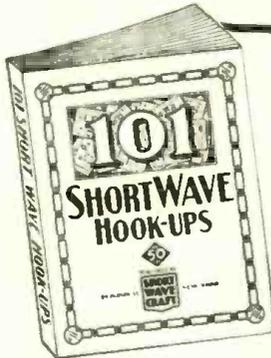

101 SHORT WAVE HOOK-UPS

Compiled by the Editors of RADIO & TELEVISION

Here is a worthwhile book that every short wave listener, every short wave fan, and every short wave amateur has wanted for a long time. It gives you the 101 best short wave hook-ups which have appeared heretofore.

100 Illustrations
72 Pages

50c

HOW TO BUILD AND OPERATE SHORT WAVE RECEIVERS

This is the best and most up-to-date book on the subject. It is edited and prepared by the editors of RADIO & TELEVISION and contains a wealth of material on the building and operation, not only of typical short wave receivers, but short wave converters as well.

150 Illustrations
72 Pages

50c




TEN MOST POPULAR SHORT WAVE RECEIVERS

HOW TO MAKE AND WORK THEM

The editors of RADIO & TELEVISION have selected ten outstanding short wave receivers and these are described in the new volume. Each receiver is fully illustrated with a complete layout, pictorial representation, photographs of the set complete, hook-up and all worthwhile specifications.

75 Illustrations
40 Pages

25c

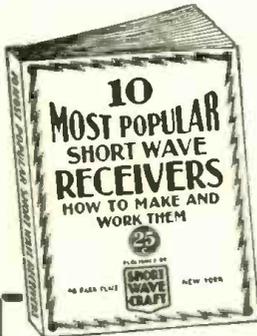

HOW TO GET BEST SHORT WAVE RECEPTION

M. HARVEY GERNSBACK tells you everything you have ever wanted to know about short wave reception. The author, a professional radio listener and radio fan for many years, gives you his long experience in radio reception and all that goes with it.

40 Illustrations
72 Pages

50c




HOW TO BECOME AN AMATEUR RADIO OPERATOR

By Lieut. Myron F. Eddy, whose experience in the amateur field has made him pre-eminent in this line.

If you intend to become a licensed code operator, if you wish to take up phone work eventually—this is the book you must get.

150 Illustrations
72 Pages

50c

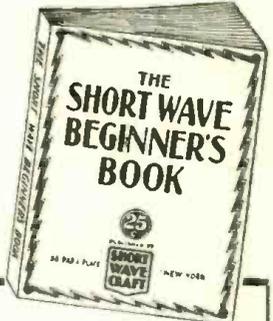

THE SHORT WAVE BEGINNER'S BOOK

Here is a book that solves your short wave problems—leading you in easy stages from the simplest fundamentals to the present state of the art as it is known today. It is the only low-priced reference book on short waves for the beginner.

75 Illustrations
40 Pages

25c

LOOK FOR YOUR NEAREST DEALER

For convenience the publishers list below dealers in all parts of the world where our books are available. On your next shopping trip be certain to examine these volumes. You're sure to want them for your technical library.

- | | | | |
|---|--|--|--|
| <p>ALABAMA
Walther Bros., Montgomery</p> <p>ARIZONA
Sam's Cigar Store, Phoenix</p> <p>CALIFORNIA
Electric Supply Co., Oakland
Radio Supply Company, Los Angeles
Radio Television Supply Co., Los Angeles
Pacific Radio Exchange, Inc., Los Angeles
Western Auto Supply, Los Angeles
Zack Radio Supply Co., Los Angeles
Wronan's Book Store, Pasadena
Western Radio & Elec. Co., San Diego
Offenbach Electric Co., San Francisco
Technical Book Co., San Francisco
Zack Radio Supply Co., San Francisco
Radio Specialties Co., San Jose</p> <p>COLORADO
Auto Equipment Co., Denver
Interstate Radio Supply, Denver</p> <p>CONNECTICUT
The Edward P. Judd Co., New Haven</p> <p>DELAWARE
Wilmington Elec. Spec. Co., Inc., Wilmington</p> <p>FLORIDA
Radio Accessories Co., Orlando</p> <p>GEORGIA
Wholesale Radio Service Co., Inc., Atlanta</p> <p>ILLINOIS
Allied Radio Corporation, Chicago
Walter C. Braun, Inc., Chicago
Chicago Radio Apparatus Co., Chicago
A. C. McClure & Co., Chicago
Midwest Radio Mart, Chicago
Newark Electric Co., Chicago
Sears, Roebuck & Co., Chicago
Max Stein & Co., Chicago
Montgomery Ward & Co., Chicago
Wholesale Radio Service Co., Inc., Chicago</p> | <p>INDIANA
Van Sickle Radio, Indianapolis</p> <p>MASSACHUSETTS
DeWolfe & Fiske Co., Boston
The Personal Book Shop, Boston
Wholesale Radio Service Co., Inc., Boston
Library Book House, Springfield
Tremont Elec. Supply Co., Boston</p> <p>MICHIGAN
Rissl Brothers, Detroit</p> <p>MINNESOTA
St. Paul Book & Stat. Co., St. Paul</p> <p>MISSOURI
Burstein-Applebee Co., Kansas City
Radio Labs., Kansas City
Walker Ashe Radio Co., St. Louis
Van Sickle Radio Co., St. Louis</p> <p>NEW JERSEY
Radio Apparatus Co., Newark
United Radio Co., Newark
Wholesale Radio Service Co., Inc., Newark</p> <p>NEW YORK
Fort Orange Radio Dist. Co., Albany
Wholesale Radio Service Co., Inc., Bronx
Wholesale Radio Service Co., Inc., City
Harrison Radio Co., New York City
Jamieson, L. J., American News Co., New York City
Baker & Taylor Co., New York City
Blair, the Radio Man, New York City
David Boren & Co., New York City
Federated Purchaser, Inc., New York City
Radio Circular Co., New York City
G. E. Stecher & Co., New York City
The Stelker Co., New York City
Sun Radio Co., New York City
Thor Radio Corp., New York City
Try-Mo Radio Co., New York City
Van Riemsdyck Book Stores, New York City
Wholesale Radio Service Co., Inc., New York City
H. W. Wilson Co., New York City
Radio Parts & Equipment Co., Rochester
M. Schwartz & Son, Schenectady</p> | <p>OHIO
College Book Exchange, Toledo</p> <p>OREGON
J. K. Gill Co., Portland</p> <p>PENNSYLVANIA
Radio Electric Service Co., Philadelphia
Cameradio Co., Pittsburgh</p> <p>WASHINGTON
Seattle Radio Supply Co., Seattle
Wedel Co., Inc., Seattle
Spokane Radio Co., Spokane</p> <p>WISCONSIN
Radio Parts Co., Milwaukee</p> <p>ARGENTINA
Radio Revista, Buenos Aires</p> <p>AUSTRALIA
McGill's Authorized Agency, Melbourne</p> <p>BELGIUM
Emil Arens, Brussels</p> <p>CANADA
T. Eaton & Co., Winnipeg, Man.
Electrical Supplies, Ltd., Winnipeg, Man.
Wholesale Radio Supply, Winnipeg, Man.
Canadian Electrical Supply Co., Ltd., Toronto, Ont.
Radio Trade Supply Co., Ltd., Toronto, Ont.
Canadian Electrical Supply Co., Ltd., Montreal, P. Q.</p> <p>BRAZIL
Agencia Soave, Sao Paulo</p> <p>CHINA
China News Co., Shanghai
International Booksellers, Ltd., Shanghai</p> <p>CUBA
Diamond News Co., Havana</p> <p>ENGLAND
Goringe's Amer. News Agency, London</p> <p>FRANCE
Toute La Radio, Paris</p> <p>GERMANY
Rehr G.M.B.H. SW15, Berlin NW No. 7</p> | <p>HOLLAND
Radio Peeters, Amsterdam, Z.</p> <p>INDIA
Empire Book Mart, Bombay</p> <p>MEXICO
American Book Store, Mexico, D. F.
Central De Publicaciones, S. A., Mexico, D. F.
Jaques Salvo, Mexico, D. F.</p> <p>NEW ZEALAND
Johns, Ltd., Auckland
James Johnston, Ltd., Dunedin
Te Aro Book Depot, Ltd., Wellington</p> <p>SOUTH AFRICA
Technical Book Co., Cape Town
Central News Agency, Johannesburg
International House, Johannesburg
South African Radio Publications, Johannesburg</p> |
|---|--|--|--|

IF YOUR DEALER DOES NOT CARRY THESE BOOKS, ORDER DIRECT FROM US. FILL OUT COUPON BELOW. SHIPMENT WILL BE MADE IMMEDIATELY.

POPULAR BOOK CORP. R&T-4-39
99 Hudson Street, New York City.

Gentlemen: I enclose herewith my remittance for _____ for which please send me the following books:

.....

.....

.....

Name _____

Address _____

City _____ State _____

(Send remittance in form of check or money order. If letter contains cash or unused U. S. postage stamps, register it.)

POPULAR BOOK CORPORATION • Publishers • 99 HUDSON STREET • NEW YORK, N. Y.

ANTENNAS—*Past, Present* *and Future*

Harold H. Beverage

Chief Research Engineer, R.C.A. Communications, Riverhead, L. I., N. Y.

● MARCONI, during his early work with wireless telegraphy in 1895, used a simple *dipole* oscillator similar to those used by Heinrich Hertz in his classical experiments eight years earlier. Marconi soon discovered that he could greatly increase the range of transmission by connecting one side of the dipole oscillator to earth and the other side to an elevated plate. By using structures of greater and greater elevation to support his antenna, he found that the range of transmission increased. Since the wavelength emitted by this early equipment was a function of the length and size of the antenna, it is evident that Marconi's success quickly set a trend toward the use of longer and longer wavelengths as well as larger and higher antennas. When Marconi had the famed letter "S" transmitted from Poldhu to Newfoundland in 1901, the antenna at Poldhu was supported by masts about 200 feet high, and it is probable that the wavelength was between 2000 and 3000 feet. During the next 20 years, it is not surprising that the trend toward the use of longer wavelengths continued, which in turn called for higher antennas to increase the efficiency of radiation, and antennas of larger area to hold the voltage down to reasonable values when the antennas were energized by the hundreds of kilowatts found necessary for reliable communication over great distances. By 1921, it was not unusual to find some *long wave* transmitting antennas supported by towers 800 feet high, and other types of antennas over a mile long. The Alexanderson multiple tuned antenna is a familiar example of the latter type.

During this period, the bugbear to *long distance* communication was atmospheric disturbances, more commonly known as "static." It was found that static originated mostly over land masses, so that, in general, on transoceanic circuits, the static originated in a direction more or less opposite to the direction from which the signals were arriving over their ocean path. Consequently, it was possible to greatly reduce the effects of static by using *directive reception*. Numerous arrangements were used with varying degrees of success, such as the uni-directional "loop-vertical" combinations of Pickard, the ground wires of A. Hoyt Taylor, and the long antennas supported on poles, such as Weagant's antenna and the "Wave Antenna." The voltages induced in these long antennas traveled at nearly the velocity of light, so that very



Harold H. Beverage, well-known for his researches in antenna design.

long antennas could be used effectively, the usual length being 8 to 10 miles for the transoceanic wavelengths in general use at that time.

The Wave Antenna was the first antenna to utilize the *traveling wave* principle, as distinguished from *standing waves*. Its effectiveness was due in large part to its simplicity which eliminated the critical adjustments which were required in its predecessors which depended upon some sort of a balancing arrangement.

The second era of long distance radio communication started with the discovery during the early 1920's, that short waves below 100 meters were useful for long distance communication in the daytime, as well as at night. For these short wavelengths, it was practical to return to the Hertzian dipole as a radiator. It also became feasible to use *directivity* in the transmitting antenna to project a large propor-

tion of the radiated power in the desired direction. It was logical that the first directive antennas should consist of arrays of dipoles with reflectors. Very effective arrays were developed as exemplified by the British Marconi Beam antenna, the German Tannebaum antenna, and the arrays developed in America by the A. T. & T. Company and the RCA. These antennas, however, were relatively expensive to construct and maintain, and as the number of short wave circuits rapidly increased, it was necessary to develop less expensive types of antennas. Economical and effective antennas were devised consisting of wires several wavelengths long orientated in such a way as to concentrate the radiation in the desired direction. Typical antennas of this general classification which have found wide use are the harmonic wire antenna, the V-shaped antenna with reflector, the Rhombic antenna, and the Marconi Series-Phase antenna. The latter two are generally terminated in a dissipative network equivalent to their surge impedance, so that they employ *traveling waves* rather than *standing waves*.

The early short wave receiving antennas were frequently arrays similar to the transmitting arrays, but less costly receiving antennas were eventually developed by the operators of radio communication services. In America, the antennas most generally used for transoceanic services are the Rhombic antenna and the Fishbone antenna, both of which are of the traveling wave type.

The short waves have been very useful as a means for studying the characteristics of the ionosphere and the mechanism of radio transmission in general. This knowledge has been useful in connection with studies of propagation in the broadcasting spectrum. The anti-fading service area of broadcasting stations has been approximately doubled by antennas designed to suppress the radiation at high angles above the horizon.

We are now entering upon the third era of radio communication, the development of the ultra-short waves. These waves do not ordinarily travel via the ionosphere and are limited in their reliable range to distances not greatly in excess of the horizon. This quality is an advantage in many ways since it makes it possible to duplicate the use of these frequencies without interference at points on the order of

(Continued on page 752)

Twenty-sixth of a series of
"Guest" Editorials.

Television "Sight"

● THE *sight effects* expert promises to be a mighty busy man once television has become an everyday entertainment feature—which it is scheduled to do this Spring.

William C. Eddy, a member of the NBC engineering staff, has already developed a number of extremely interesting *sight effects* for television shows. Some of these effects, such as books which turn their own pages, candles which mysteriously extinguish themselves, and "talking frogs," have already been worked out and used in a number of television plays which have been produced for experimental broadcasts during the past few months.

The accompanying pictures show some of the very interesting and unusual sight effects produced by Mr. Eddy and his staff.

In one elaborate marine scene built up especially for television broadcasts, a tank measuring about 12 feet square was filled with water, and the television viewer saw on his receiving screen a parade of warships circling around the harbor of a small seaport. A tugboat with a string of barges puffed along so realistically that the viewer would never dream that this whole scene was being staged with miniature ships built from cork and other odds and ends. The ships were caused to move around a prescribed path, thanks to a circular guide track submerged in the water. The ships were moved by a chain fitted with couplings, all driven by a motor. The puffs of smoke from the stack of the tugboat were produced periodically by squeezing a rubber bulb connected to a smoke tank and a tube leading to the bottom of the tug's stack.

The water in the harbor was colored so as to hide the mechanical devices used for moving the ships. Incidentally, the water was colored by placing some dye on the back of a small turtle and allowing it to swim around in the "harbor."

All the buildings used in these miniature scenes are built from wood and other materials by Mr. Eddy and his staff, and painted in colors to suit the particular scene and locality.

In one television scene it was necessary to build an animated frog, and as one of the pictures shows, the eyes and jaws of the frog were caused to move by means of flexible shafts passing out through the "tail" of the frog. The stomach of the frog was caused to pulsate by means of a rubber bag placed inside it, this bag being connected to a rubber hose and a bulb which

was periodically squeezed. The voice of the frog came from a loud speaker.

To cause a candle to extinguish itself while the television camera was focused upon it was a simple trick for Mr. Eddy—he merely placed a metal tube up the rear of the candle and when the candle was to go out, a quick squeeze on a rubber bulb, connected with the metal tube, snuffed out the flame.

In producing television plays, many cut-backs from the main television studio to the *sight effects* laboratory, two floors above, take place. In one of the scenes, a candle suddenly goes out—next, the tele-

from top to bottom, or bottom to top.

Some of these effects are created by using a lightly silvered sheet of glass placed at an angle so that the first title is seen through the sheet of glass, while the second title is picked up as a reflected image from the surface of the glass. The change from one title to the other is caused by manipulating dimmers so that while one light is being slowly decreased in strength, the light behind the other title is being gradually increased.

The leaves of a large book had to *turn themselves* while the television camera's eye was focused upon the book—this was

easily accomplished by attaching a flexible wire shaft to each page so that by turning a knob, each leaf could be turned by the operator who was outside the focus of the camera.

In another scene, a pile of books was supposed to fall on a bottle of acid and upset the bottle. Sounds simple—but suppose that this scene had to be repeated several dozen times? Here's what Mr. Eddy and his staff did. The books were guided in their fall by means of bent wires; the bottle was secured with a hinge so that it would always fall in the same direction when hit by the falling books. The fumes from the acid in the bottle were produced by blowing smoke into the bottle through a rubber tube passing through a hole drilled through the bot-

tom of the glass bottle.

Several of the accompanying pictures show a television miniature scene where the camera moves along a street and picks up images of different signs pertaining to the dramatic story at hand. As the camera nears the end of the street (containing, incidentally, a number of cleverly constructed miniature trees and bushes), the television viewer sees a white picket fence which is used as a cue or connecting link; next the television viewer sees the front of the house shown in the photo. This view is picked up by a second television camera, which is moved in slowly toward the house until the front door appears the same size as does the image of a real *full sized* door being viewed by another television camera. A *live* actor, supposedly a doctor in this case, opens the door and removes letters from the mail box. The switch-over from one television camera to the other is done so adroitly that the viewer never knows that in the first part of this scene he has actually been

(Continued on page 753)



Painting a miniature building for use in a Television scene.

viewer sees a pair of hands fumbling with a match. In the next scene the candle refuses to light—but what the viewer does not know is that while a cut-back was made showing the hands fumbling with a match, a candle dipped in a fire-proofing solution was substituted for the original one.



To get the effect of a candle slowly going out, the wick was gradually pulled down inside the previously drilled out candle.

The *flight of time* was one of the effects that Mr. Eddy was asked to produce and a photo shows how this was accomplished. A set of progressive calendar leaves were specially printed for the year in which the scene was to take place. These leaves were then placed on top of a frame so that when a rubber roller was rotated, the leaves slid down a pair of bent wire guides rapidly. The television camera recorded a *flutter of passing dates* with a very artistic effect.



A very ingenious titling machine has been devised by means of which one title can be caused to dissolve slowly into another; in other effects titles appear to be "wiped off"

Effects''

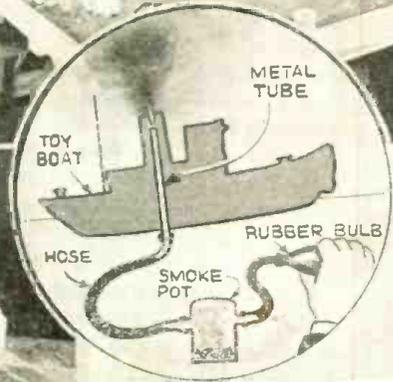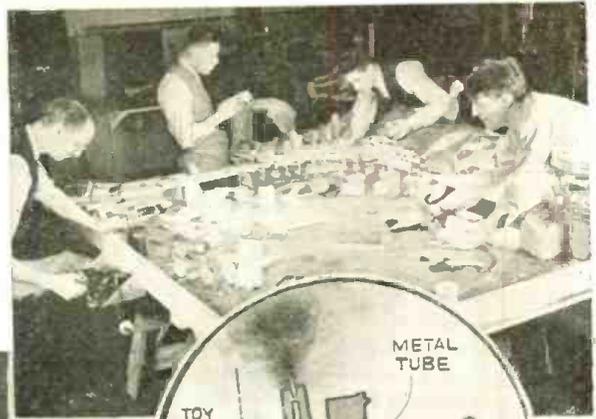Frogs that talk—books that turn their own pages—spiders that "obey orders"—all these and many others are produced by the television "sight effects" man.





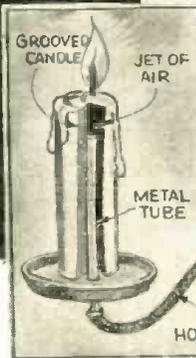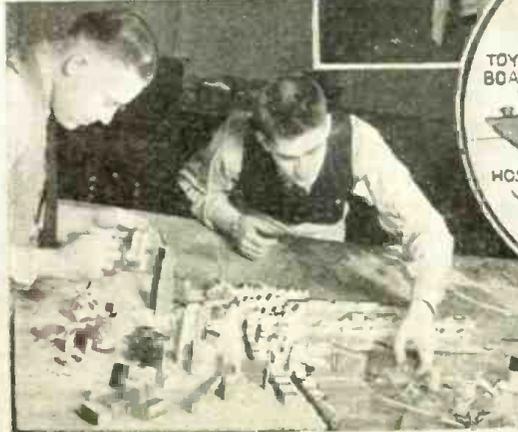Above—Model ships were maneuvered around model "harbor," by means of a moving chain. Method of pumping smoke out of ship's stack is shown in circle.






Above—How pages of a book are turned by flexible cables, the operator keeping out of camera range. Right—candle is extinguished by squeezing rubber bulb.

VOICE FROM LOUDSPEAKER

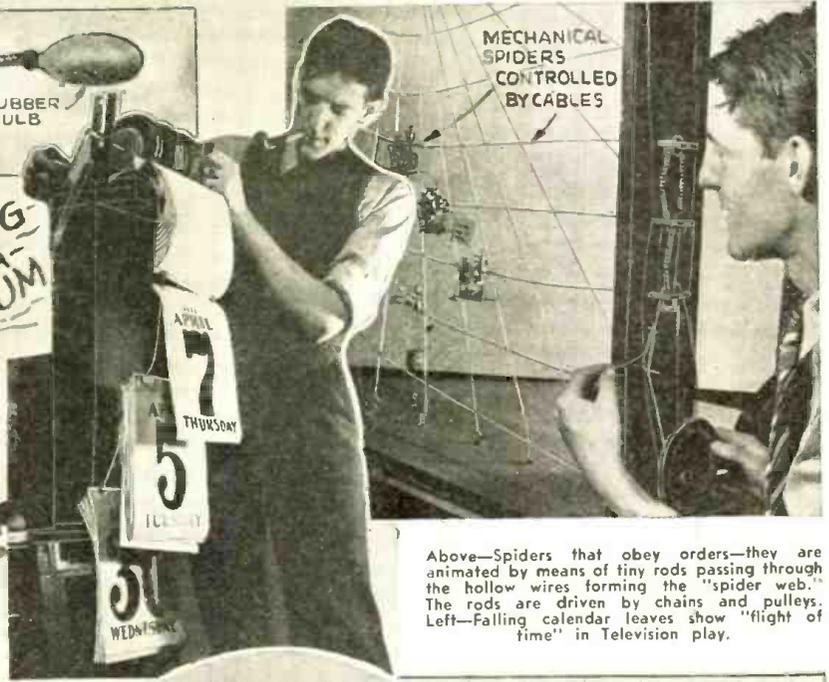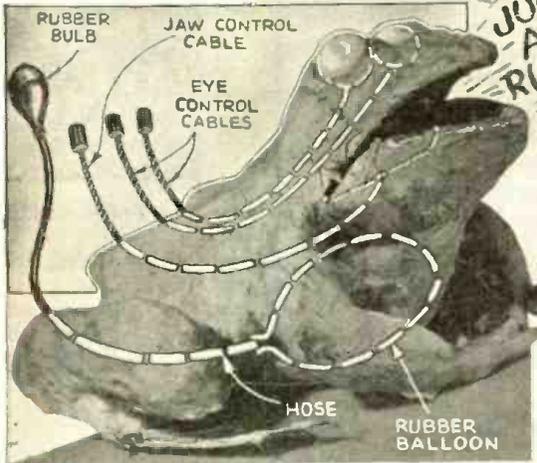

Above—Spiders that obey orders—they are animated by means of tiny rods passing through the hollow wires forming the "spider web." The rods are driven by chains and pulleys. Left—Falling calendar leaves show "flight of time" in Television play.

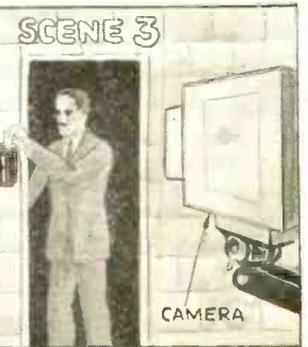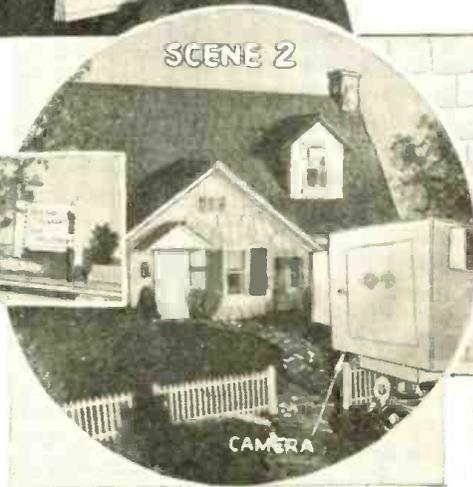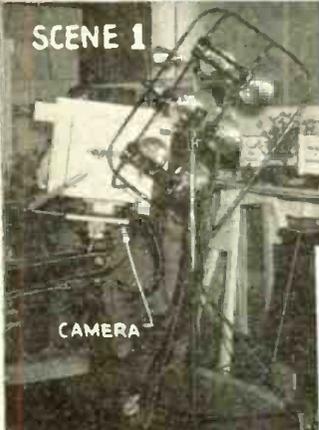Television animals not always what they seem. Above—animated frog in which the eyes, mouth and stomach move at the will of the operator.



Camera (scene 1) moves from left to right and picks up image of street and signs along the way; second camera is focused on the house, Scene 2. White picket fence is cue for change in scene and the camera pick-up.

Camera No. 1 shifts to actor in full-size door, and takes up action when door image in Scene 2 has been "panned up" to full size.



Prof. William W. Hansen tuning the 10 cm. Klystron transmitter in the Physics Laboratory at Stanford University

Russell Varian, credited with the Rhumbatron's invention, inspects his work, with Prof. Hansen.

● EXPLAINING the Rhumbatron and Klystron, R. E. Gillmor, president of the Sperry Gyroscope Company, says:

"The widespread possible application of the Rhumbatron and the Klystron in the development of new safety devices for avia-


Some sketches to show what the Rhumbatrons in the Klystron will do—and how they do it!

Electrons "Swing It" in the Rhumbatron

Waves only 10 cm. (4 inches) long may guide airplanes through use of high-power tube using new principle of "dancing electrons".

tion was called by the Bureau of Air Commerce to the attention of the various organizations cooperating with it in the development of a blind landing system."

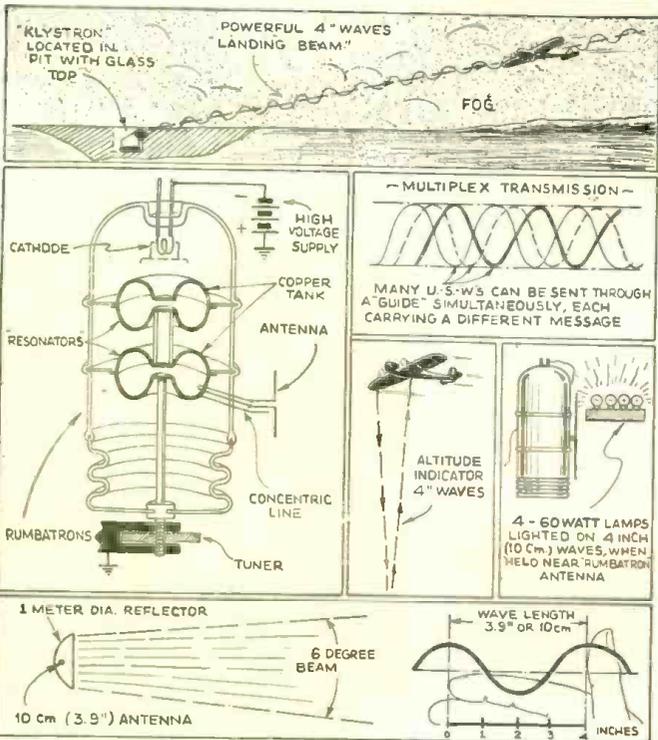Before continuing with Mr. Gillmor's discussion, pause a moment to study the following editorial item which appeared in the *M. I. T. Technology Review*. This item comments upon an address given by Prof. David L. Webster, head of the Physics Department of Stanford University,



before a recent colloquium of M. I. T.'s Department of Electrical Engineering, and says in part:

What is a Rhumbatron? "In the Klystron a beam of electrons representing a constant current is sent through two resonant metal containers known as *Rhumbatrons*. In the first Rhumbatron is an oscillating electric field, parallel to the stream and of such strength as to change the speeds of the electrons by appreciable fractions of their initial speed, accelerating some and slowing down others. After passing this Rhumbatron, the electrons with increasing speeds begin to overtake those with decreased speeds which are ahead of them. This motion groups the electrons into bunches separated by relatively empty spaces. A considerable fraction of the energy of these groups can then be converted into power of high frequency oscillation by passage of the stream through the second Rhumbatron, within which is an oscillating electric field so changing synchronously as to take energy away from the electrons in the bunches.

"If the first Rhumbatron (which is called the *buncher*) is driven by an external source of power such as an antenna receiving radiation and the electrons are strong enough to give the second Rhumbatron (which is called the *catcher*) more power than the antenna gives to the buncher, the Klystron is acting as an *amplifier*.

"If the buncher is driven by power received through a coupling loop or otherwise from the catcher, the Klystron is acting as an *oscillator*. And finally, if the buncher is driven by power from both of these sources at once, the Klystron is acting as a *regenerative amplifier*."

Blind Landing: Continuing with his explanation of the Klystron's purpose, Mr. Gillmor says:

"This new blind landing system (Continued on page 756)

Television's Interference Problem

Interference, due to the ignition systems of motor cars, is becoming a major problem among British television users. "Thermion," feature writer for *Practical and Amateur Wireless*, reports that Government departmental vehicles may soon be equipped with spark suppressors, and that motor manufacturers are rumored soon to make similar use of such devices. He further suggests that everybody engaged in radio and television install suppressors and that they be sold to all purchasers of television equipment. However, "Thermion" has said that nearly five million vehicles are already on the road there and that no legislation is likely to be introduced until television is far more widespread. "Thermion" suggests that the real solution of the problem is to allocate higher wavelengths for television transmissions.

The British writer seems to have overlooked the fact that high frequencies are particularly suited to wide-band transmissions.

Cabaret Televised

Engineers of the National Broadcasting Company took television transmission equipment to the Café Français in Rockefeller Center to pick up the floor show as presented to guests. Among those who performed before the television camera, according to the *New York Times*, were: Sheila Barrett, mimic; Frank Gaby, ventriloquist; Fats Waller, pianist, and several skating acts.

The report further stated that an NBC executive says, "It is not likely that advertisers generally will become interested in television as an advertising medium until there are perhaps 400,000 receivers in this area. There are now only a few hundred television receivers in the same locality."

WBRK Joins Three Chains

The eight-months-old station, WBRK, Pittsfield, Mass., became affiliated with the Yankee, Colonial and Mutual networks on March 1st.

The station brings the Mutual complement to 110 stations, as of February 15.

To Broadcast Yankee Clipper's First Flight

A shortwave relay broadcasting transmitter and associated equipment are installed on the Pan-American Airway's *Yankee Clipper No. 17*. This apparatus will be used during its initial flight to Europe, the program being broadcast over the Columbia Broadcasting System.

Clyde Houldson, CBS field technician, will act as announcer and operator in the flight. The airplane's station, WCBN, has received an F.C.C. license for eight special frequencies within the 1600 kc. to 23 mc. band, with an output of 100 watts.

The equipment is installed in the lower compartment of the plane's nose and is remote-controlled from the radio room on the upper deck. Its weight is below 1000 pounds, including spare parts, spill-proof batteries and measuring equipment.

A preliminary test of the equipment was given during the plane's test flight from Seattle to Washington. It was completely successful.

WORLD WIDE RADIO DIGEST

New Mystery Station

British listeners are reporting the reception of signals from an unlicensed transmitter located in the Ukraine (U.S.S.R.). The station, according to *Practical and Amateur Wireless*, broadcasts propaganda in Polish, Ukrainian and German, daily at G.M.T. 06:45 and 17:00 on channels varying between 28 and 36 meters.

Sixteen Tongues on Italian Stations

Beginning the first of this year, the radio stations of Italy have considerably increased their foreign language broadcasts, particularly on the short waves, according to *Practical and Amateur Wireless*.

The stations now transmit news bulletins and propaganda in 16 languages.

General Electric Answers Questions

Many queries about television are answered in a new booklet, "A Miracle Begins," by Dr. W. G. R. Baker of the General Electric Company.

Among the facts which are brought out is that transmission range is limited to a radius of 40 or 50 miles and that no economical system in interstation linkage is yet feasible. (It has been rumored that the National Broadcasting Company will announce trans-continental television by the end of March.—*Editor*)

Picture sizes, according to Dr. Baker, will range from 2.4 x 1.8 inches to 9.5 x 7 inches. Receivers will probably cost from \$150.00 to \$1000.00.

HIS HONOR THE MAYOR TALKS WITH HIS HONOR THE MAYOR



Seated in his horse-drawn coach on a London street, Major Sir Frank Henry Bowater, Lord Mayor of London, conversed with Mayor Fiorello H. LaGuardia, Mayor of New York. Their two-way trans-Atlantic telephone conversation was re-broadcast over the National Broadcasting Company network.

Mayor LaGuardia normally uses his equipment to keep in constant touch with the police and fire departments.

The major portion of the conversation was on how pleased the two mayors were to be able to talk to each other and to hear each other so clearly. They also exchanged views as to the hours, it being 2:55 p.m. in London and 9:55 a.m. in New York.

Mayor LaGuardia invited the Lord Mayor to attend the N. Y. World's Fair.




(Continued from preceding page)

Flag-Pole Antenna

Because the Bell System's transmitting station at Norfolk, Va., is located in a residential section a few blocks from the beach, an inconspicuous antenna was desired. Therefore shunt excitation was used, making it possible to employ a standard steel flag pole.

As seen in the picture, a diagonal transmission line connects to a carefully selected point on the antenna, the base of which is connected to a radial ground system buried in the earth.

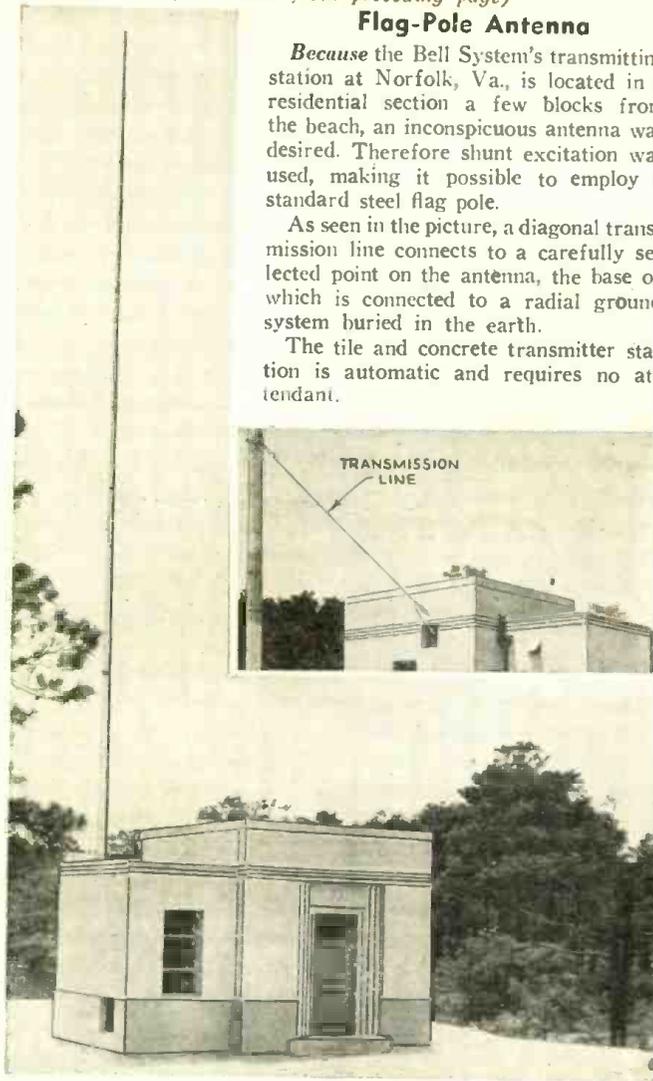The tile and concrete transmitter station is automatic and requires no attendant.



Shock of the Esso Baytown

When the New York-Bermuda plane crashed in the Atlantic Ocean, she sent out wireless calls for aid. These were received by shore stations; among them Radiomarine's WSC at Tuckerton. This station, as did others, promptly sent out calls for aid to ships at sea, and it was a call of this sort rather than one direct from the airplane that was received by the *Esso Baytown*.


The operator on the Standard Oil tanker was off duty at the time, but he had recently installed an automatic alarm which rings a bell when SOS signals are received, calling the operator to his



shack, a picture of which is printed herewith. The result was that radio had saved ten more lives. On Jan. 1, 1939, there were 1134 U. S. vessels equipped with the alarm system.

WORLD WIDE

S-W to Catch Crooks

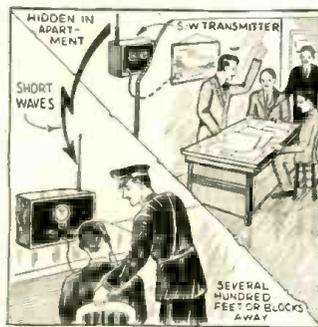


According to General Hugh S. Johnson, writing for Scripps-Howard newspapers, the police are now experimenting with a miniature battery-operated radio transmitter, small enough to be concealed in a brief case.

This outfit, installed in anyone's room or car, will transmit conversations taking place in its vicinity over distances of several hundred feet. Thus, police in a nearby room or following in another car can overhear whispered conversations.

New York's Fireboats Get 2-Way Voice

Two-way communication between ship and shore has been made possible with the installation of General Electric short-wave

transmitting and receiving equipment on New York City's ten fireboats, as well as on the mainland. Lt. John H. Reagan is shown here using the handset of the new 50-watt, ultra-high-frequency transmitter recently installed on the *Firefighter*, new \$1,000,000 addition to the Fire Department's fleet. The boat's receiver is a medium-high-frequency set tuned to pick up all messages sent from the department's 500-watt transmitter on the mainland.

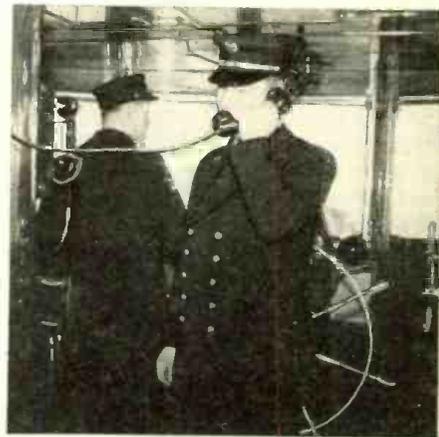

The boat's receiver is a medium-high-frequency set tuned to pick up all messages sent from the department's 500-watt transmitter on the mainland.

Regulations in Germany

Those who aspire to become radio artists broadcasting over German stations must pass official examinations. To enter these examinations, they must show at least two years of study in the entertainment field or have had professional experience. Of the 2,478 persons recently examined, only 1,125 passed the stringent tests.


(Wonder if there aren't any amateur hours or quiz programs in the Third Reich?)

New regulations on Government licenses are also expected in Germany. It is believed that the license fee will be reduced to 1 reichsmark for certain classes, and that free licenses will be more liberally issued.

Those who now get free licenses in Germany include the Diplomatic Corps, The Hitler Youth Homes, the Hitler Youth Schools, the Radio Departments of the Youth organization, the offices of the Ministry of Propaganda and of the Post Office and Defence Forces—the latter when the sets are being used in the defence of the nation. This is said to amount to several thousands.

RADIO DIGEST

That 50,000 Hour Tube!

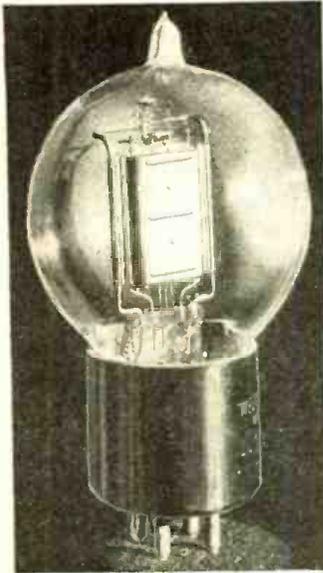

The long-life tube pictured here was developed in the Bell Telephone Laboratories to meet the peculiar needs of telephonic communications. These include low-power consumption, uniformity permitting replacement without readjustment of associated apparatus, reliability against interruption of service, and continuous operation twenty-four hours a day. This tube operates from a battery, the electrons being emitted from a coated filament. It is not adapted to A.C. or D.C. power line use. This, plus the fact that the average radio tube of today lasts about as long as the set, should provide an answer to those who have asked, "Why aren't 50,000 hour tubes used in radio receivers in the home?"

To "Look In" on Next Inauguration

When R.C.A. television was demonstrated in Washington, the *New York Times* reports, Minnesota's Senator Lundeen, appearing before the microphone, asked the announcer whether the Presidential inauguration of 1941 was to be telecast. An NBC official then admitted that plans were on foot to do so.

New Service Suggested

A British writer suggests that in addition to time signals and weather forecasts, it would be a valuable service if radio stations were to broadcast barometric readings. Many homes have barometers which are usually somewhat out of adjustment due to the lack of any available standard with which to calibrate and check.

Fire-Fighting at the Fair

To minimize fire hazards at the 1939 New York World's Fair, a fire chief's car, which will patrol the grounds, is being equipped with two-way radio.



In the accompanying illustration, the fire chief is speaking into the handset of the General Electric's 15-watt ultra-high-frequency transmitter. A superhet in the car picks up all messages broadcast from the headquarters station. Appropriately enough, the background in this picture is a Communications Building mural. Note "mikes" at left.

Facsimile Reaches the Public

The Crosley Corporation, long pioneers in various branches of the radio industry, have announced a facsimile receiver for sale to the public. The new receiver, licensed under Finch patents, reproduces type and pictures on a strip of paper approximately 3 3/8" wide (printing space). While the facsimile reproducer can be operated from any standard radio receiving set, the manufacturer suggests the use of a special receiver and a doublet antenna. He also believes that more satisfactory operation will be obtained




Reproducer and special set.

if an automatic time-switch is used to turn the facsimile equipment on any time during the day when transmissions take place and off at the time they terminate. Reproduction is achieved by means of an electrochemical process, current passing through sensitized paper which, in-

identally, will be sold at \$1.00 per roll! A stylus at the end of a moving arm which sweeps over the sensitized paper, marks each dot to be imprinted when the current passes from the




Inventor inspects work.

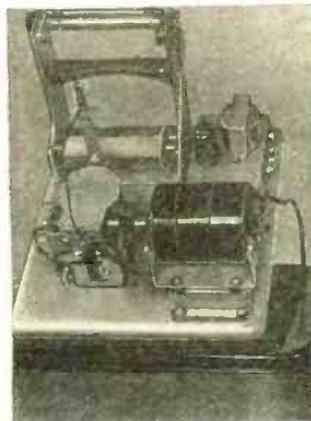

Facsimile chassis exposed.

stylus to a roll behind the paper, thus oxidizing the sensitized coating.

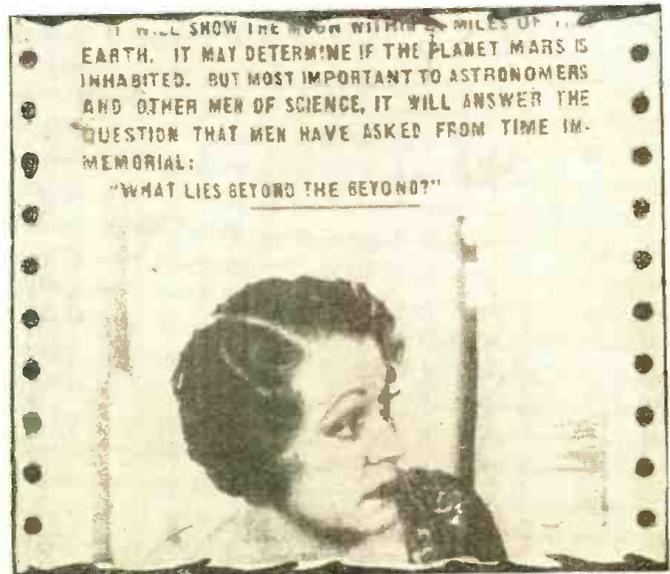Transmission is at the rate of approximately three feet of paper per hour. Station WLW is on the air with such transmissions between the hours of 1 A.M. and 6 A.M. Many other stations are likewise sending facsimile material.



Unretouched reproduction of transmission—Actual width is 4 11/16 inches overall. Width of type is 3 3/8 inches.

What the Experts Are Saying About Radio and Allied Arts Here and Abroad



Vertical or Horizontal Television Doublets

1 H. L. KIRKE, head of the Research Department of the B.B.C., raised the question of the desirability of vertical or horizontal polarization for television aerials, in an address made to the Royal Society of Arts. He said that in England Vertical polarization has been used while in America, horizontal polarization is favored, because interference from automobile ignition systems affects the latter system less.

He is quoted by *Wireless World* as saying, "It is probably simpler to design an aerial system with symmetrical radiation in the horizontal plane using vertical polarization. Recent experiments have shown, however, that at any rate, in certain circumstances, a considerable improvement in signal strength has been obtained by the use of horizontal polarization."

However, a change-over in the British system would necessitate altering all their television receiving antennas (estimated between 2,000 and 10,000) now in use.

Mr. Kirke concluded his statement say-

ing, "Experiments have shown that for the O.B. radio link, horizontal polarization is considerably the better, and with a suitable design of transmitting and receiving array, a gain of six to twelve decibels in signal strength over the present arrangement is expected, in addition to the improvement obtained by the reduction of general interference from motor cars."

Noise Suppression Circuits

2 AS Fig. 2A shows, a burst of static or other extraneous noise may override a signal greatly, with much distress to the listener. However, if the noise peaks are reduced, as shown in Fig. 2B, it is barely noticeable.

In noise limiters, the noise impulse is rectified and used to supply a negative bias, generally to the I.F. amplifiers. While this is an ideal system for commercially-made sets, it is hard to add to sets which have already been completed, due to time lag factors, etc. However, a noise suppressor circuit of the total cut-off type may easily be added to the A.F. stages of any set. Two such circuits are shown in Figs. 2C and 2D.


In 2C, the suppressor is connected directly in the output of the final tube and it is particularly adapted for headphone operation. The two anodes of the diode are at a potential of $1\frac{1}{2}$ volts negative, this bias being obtained from "C" batteries. When a noise peak occurs, it causes one of the anodes to go positive, thus short-circuiting the phones for the duration of the noise.

Fig. 2D, also taken from *Wireless World*, is a modification, in which the suppressor circuit is inserted in the detector's anode circuit, and the only components required are a center-tapped A.F. choke and a diode tube. Bias may be obtained either from batteries or from the cathode circuit of one of the A.F. stages. A small variable resistor of 50 to 100 ohms in series with the bias resistor of the A.F. cathode will supply the necessary voltage.

Simple Crystal-Controlled Oscillator

3 TWO simple circuits for crystal-controlled oscillators are found in a recent issue of *Wireless World*, a British publication.

Fig. 3A illustrates the simplest form of this type of apparatus. The values in this

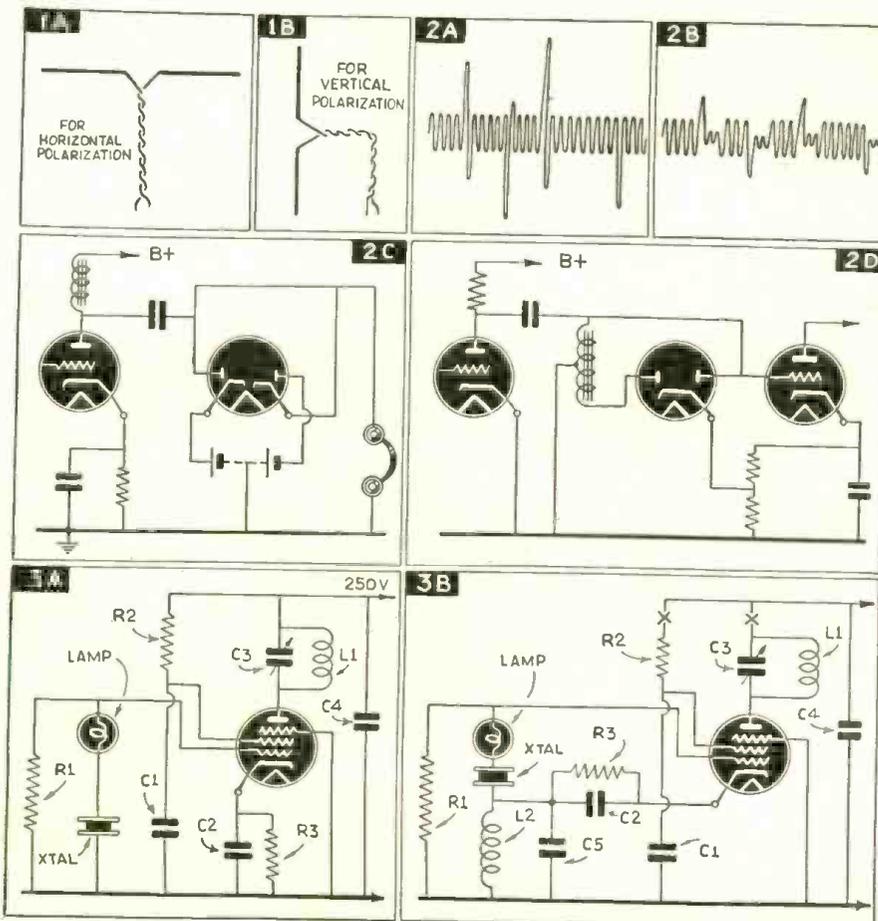



circuit are R1—50,000 ohms; R2—5,000 to 10,000 ohms; while the values of C1, C2, C3, C4 and L1 are determined by the frequency of the crystal oscillator.

Fig. 3B uses a few more parts, enabling the operator to make use of harmonics for multi-band operation.

C5 in this diagram is often made variable, but need not be, as once the adjustment has been found, it can be left "set." If the circuit is tuned to resonate at a frequency slightly lower than double that of the crystal, it functions satisfactorily. The points marked "X" indicate connections for a jack into which a milliammeter may be plugged.

Use for Magic Eye

4 A CIRCUIT using a magic eye tube for a frequency meter is indicated in Fig. 4. According to the description in *Practical and Amateur Wireless*, this instrument is far more sensitive than one employing a thermo-ammeter, and also tunes more sharply. In addition, indication is instantaneous; the absence of lag being particularly valuable when tuning is subject to rapid fluctuation.

While this apparatus can be added to any existing frequency meter, it will alter original calibration. The addition of a rectifier would increase its sensitivity, but the self-rectifier shown is sufficiently sensitive. Although an external rectifier improves the unit somewhat, it complicates the apparatus and raises its cost.

Electronic Musical Instruments

5 OLD headphone magnets may be utilized to build home-made electronic musical instruments, as described in *Practical and Amateur Wireless*.

Fig. 5A shows the principle. In this arrangement, a single stretched metal "string" vibrates between the poles of the two coils, which should be spaced as close as possible without permitting the string to touch them on its maximum vibration. The coils are in series, their free ends being connected to the input of an amplifier.

Fig. 5B shows how the unit may be assembled with a single stick of wood in order to make a one-string fiddle.

Fig. 5C shows a multiple unit, as designed for a guitar. The unit is mounted on a piece of mahogany and the strings stretched above it, each positioned accurately over its pole-piece. Various notes other than fundamentals are secured by sliding the

finger along the string, just as in playing standard instruments.

Overcoming Instability

6 WHEN a radio frequency receiver is used, oscillation or instability is often noticed before maximum volume is obtained. Two simple ideas, illustrated in Fig. 6, were described in *Practical and Amateur Wireless*.

The first idea is to "short" the reaction choke in the detector stage. If this stops the instability, the position of the choke should be changed or a shielded choke used. In some cases, the addition of a fixed condenser across the r.f. choke will prove effective, as shown in the r.f. stage of the diagram.

If neither of these tests prove effective, there is something radically wrong with the layout or wiring of the set, the article concludes.


Separating Video and Audio Signals

7 AS shown in Fig. 7, incoming television signals with their associated sound are applied across the terminals T and T1 to the control grid of a pentode, together with local oscillations from a source "S."

According to a patent recently granted to Ferranti, Ltd., and G. M. Tomlin, if the picture signals are transmitted on a carrier of 45 megacycles and sound on 41.5 megacycles, a local frequency of 32 megacycles is used. In the anode circuit A, the tuning of which is broadened by a slant resistance R, a difference frequency of 13 megacycles (45-32) is produced and transferred to the i.f. stage A1 of the picture channel.


A second tuned circuit, B, is connected to the screen grid, and is decoupled by a resistance R1 and condenser C. Here the second difference frequency of 9.5 megacycles (41.5-32) appears and is passed

(Continued on following page)

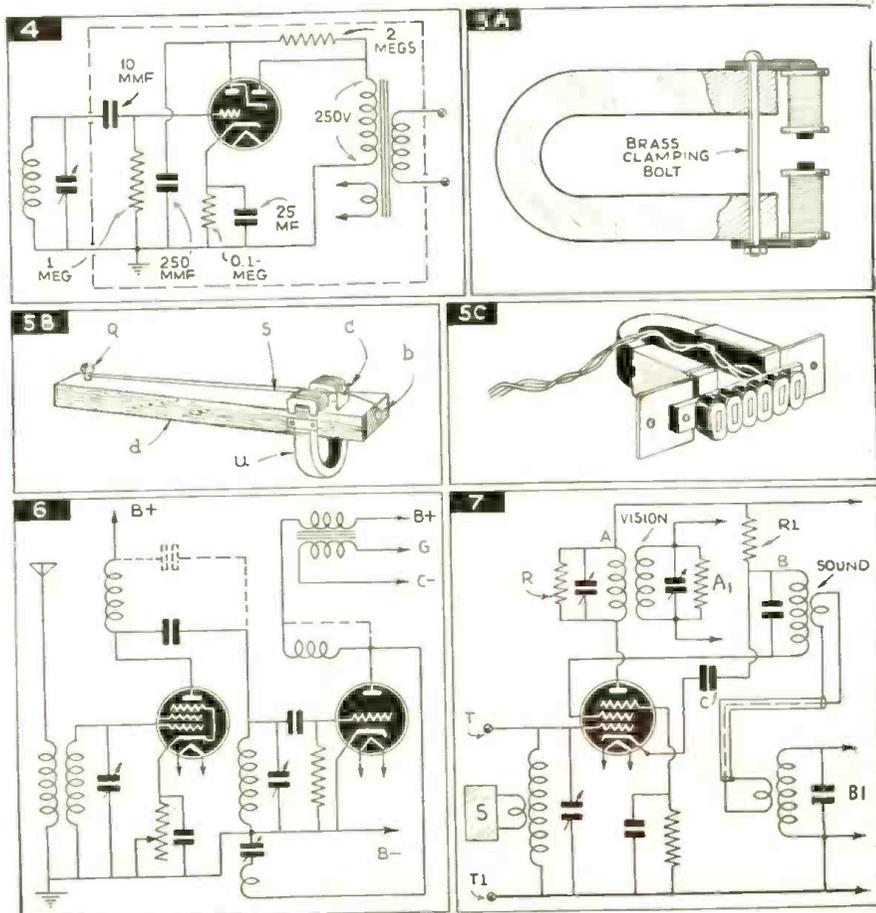

INTERNATIONAL RADIO REVIEW

(Continued from preceding page)

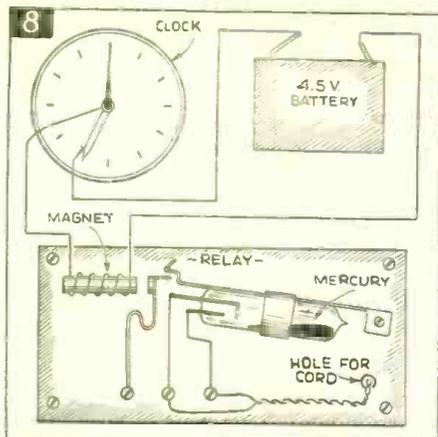


through a separate amplifier, B1, to the sound channel. The arrangement avoids cross-modulation and prevents undue attenuation of either set of frequencies.

Simple Radio Time-Switch

8 A TIME-SWITCH which can be made from a common clock and little other apparatus is described in *Popular Radio* of Denmark.

As Fig. 8 shows, one contact is made direct to the hour hand of the clock, while the other is made to a contact which may be positioned at any spot on the dial. In series with these two points is an electro-magnet (which may be removed from an ordinary ten-cent store door bell) and a 4½ volt flashlight or "C" battery.

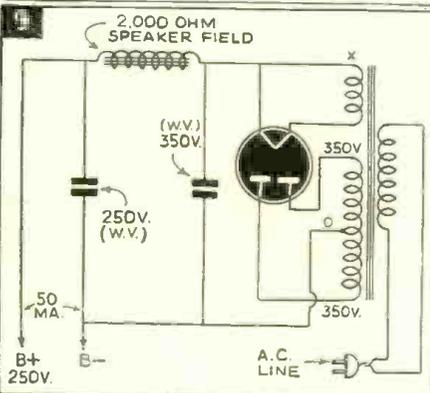This electro-magnet operates a trigger to trip a switch which is in series with the power line to the set.



Reducing Hum in S.W. Receivers

9 ACCORDING to *Practical and Amateur Wireless*, the simplest way to determine the cause of hum is to check the output of the detector stage, which may be done with a pair of headphones. This stage is most likely the source of the trouble.

While equipment of adequate size to carry the complete current for the plate of a multi-tube set must be rather heavy and therefore expensive, it is comparatively cheap to supply additional filtering for the detector stage. The diagram in Fig. 9 indicates this, the point from which a separate detector supply may be taken being marked X. A standard audio choke may be connected at this point. Better clarity will be obtained if a condenser network is used with the choke.

Circuit Breakers Protect Transmitter Tubes

10 AN article by Rene Jourdan, F8LO, appearing in *Le Haut Parleur "8"*, describes an interesting means of protecting transmitter tubes by means of simply constructed relays and a mercury switch. The variable resistance R is inserted in the circuit to permit careful adjustment of the relay, A1. When normal current is flowing into this circuit it energizes A1.

This permits the circuit S to be closed. If excess current flows in the circuit S, the relay A2 is actuated, opening the mercury switch. Oil is provided in the switch to prevent arcing.

Baffling for High Fidelity

11 AS no speaker can be better than its baffle arrangement, an article by M. McGowan, VK2MZ, in the *Australasian Radio World*, is particularly interesting.




The speaker used had a comparatively

flat response from 40 to 9000 cycles. As shown in Fig. 11A, the unit is mounted at the center of a 3-foot panel which forms the front of a box 12 inches deep. The box is lined with cotton batting and a back provided. At the center of the back, a one inch hole was drilled to prevent compression of the imprisoned air. A view showing this is given in Fig. 11B, for a complete plan.

For such readers as may wish to experiment with this type of baffling, further data is given at 11C.

New Pick-Up Feed

12 A NEW and improved Italian pick-up is described in the German publication *Radio Mentor*. The speaker is easier to load and to discard needles from than any other unit hitherto seen. As shown in Fig. 12A, a used needle is discarded merely by loosening the screw S. When the handle H is pulled down, the needle slides along it and falls into the needle container C. The needle is replaced by being inserted from the top, as shown in Fig. 12B.

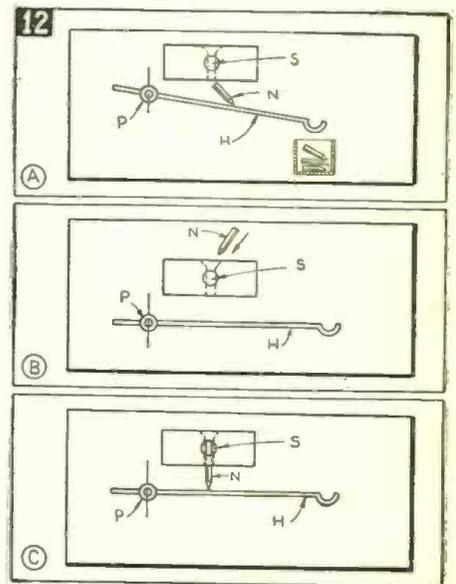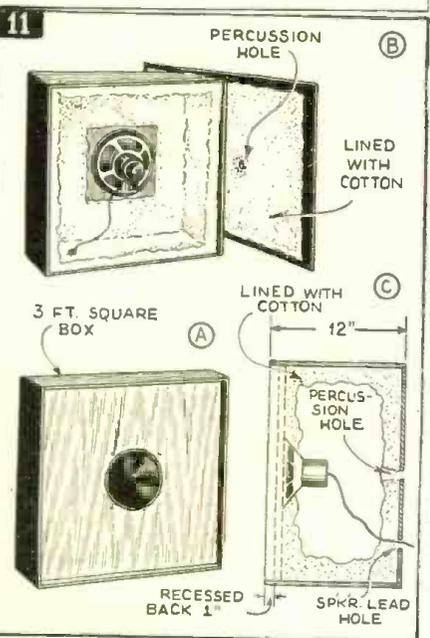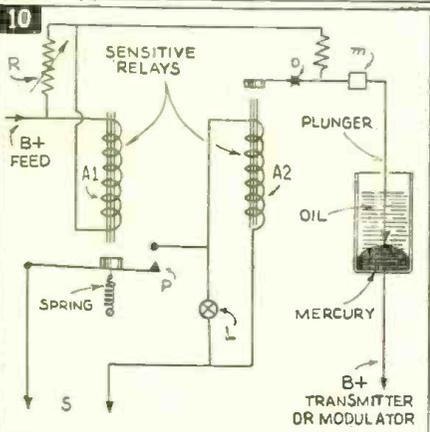

You will notice the handle, pivoted at B, returns to position so that, as shown in Fig. 12C, it forms a gauge permitting the needle to extend the correct distance and no further.

A Letter from London

In the January issue of *RADIO & TELEVISION*, it was stated that the Birmingham-Manchester co-axial cable had been abandoned for television use and would be used for telephone conversations. In reply

(Continued on page 751)

Radio Test-Quiz

For each question answered fully, count 10 points; half right, 5 points; etc. A perfect score is 170; a good score is 110; below 60 is poor.

1. Radio programs are generally loyal to the theme music, which identifies them year after year—but early in 1939, which of the following changed its theme music?

- a. *The Good Will Hour.*
- b. *Easy Aces.*
- c. *The Jack Benny Show.*
- d. *The Oak Bucket Boys.*



WHICH CHANGED ITS THEME MUSIC?

2. According to the latest complete FCC report (July 1, 1938) there were six broadcast frequencies, each of which had more than 50 stations on it. Match the frequency with the number of stations using it, in the table below.

- | | |
|-------------|-------|
| a. 1200 kc. | A. 65 |
| b. 1210 kc. | B. 51 |
| c. 1310 kc. | C. 59 |
| d. 1370 kc. | D. 53 |
| e. 1420 kc. | E. 64 |
| f. 1500 kc. | F. 60 |

3. The simplest way to make a volume expander is to

- a. *increase the "B" voltage on the R.F. stages.*
- b. *reduce the "C" voltage on the output stage.*
- c. *connect a pilot light across the loud-speaker voice coil.*
- d. *connect a 110-volt, 60-watt light bulb in series with the negative "B" lead.*

4. In making recordings—perhaps for veris—on acetate blanks, the proper depth of the cut is

- | | |
|----------------|----------------|
| a. 0.015 inch | d. 0.0025 inch |
| b. 0.025 inch | e. 0.005 inch |
| c. 0.0015 inch | f. 0.0005 inch |

5. And the ratio of the depth of cut to width of cut should be

- | | |
|--------|---------|
| a. 5:1 | d. 1:2 |
| b. 2:1 | e. 1:5 |
| c. 1:1 | f. 1:7½ |

6. Of the following features, introduced some time ago, which is not used as much as formerly in radio receivers?

- | | |
|--------------------|-------------------|
| a. <i>A.F.C.</i> | d. <i>A.T.C.</i> |
| b. <i>A.P.C.</i> | e. <i>A.V.E.</i> |
| c. <i>Q.A.V.C.</i> | f. <i>P.-B.T.</i> |

7. Since the public learned of "long life" tubes, which give 50,000 hours of operation in telephone service, there has been some discussion as to their availability for broadcast reception. Which of the following has or have been given as reasons why these tubes have not been made available to the public?

- a. *they cost 15 times as much as ordinary tubes.*
- b. *they would ruin dealers' replacement business.*
- c. *ordinary tubes usually last about as long as average receiving sets.*
- d. *receiving set circuits change too rapidly.*

8. As this goes to press, motion picture producers are agitating to keep movie stars from broadcasting. Which of the following broadcasters have appeared in motion pictures?


- a. *Fannie Brice.*
- b. *Walter Winchell.*
- c. *Ben Bernie.*
- d. *Amos 'n' Andy.*
- e. *Robert Benchley.*
- f. *Rudy Vallee.*

9. Some of the new concentric cable has the space between the inner and outer conductor filled with gas under pressure. The purpose of this is to

- a. *increase the capacity between the two conductors.*
- b. *keep moisture out.*
- c. *provide a method for detecting electrical leaks in the outer conductor.*
- d. *raise the inductance of the cable.*

10. The aerials used to radiate the NBC television signal from atop the Empire State Building in New York are

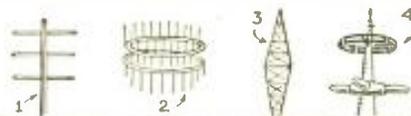- a. *horizontal rod dipoles.*
- b. *vertical wire dipoles.*
- c. *skeleton masts.*
- d. *torpedo shaped.*



WHICH IS THE LATEST TELEV. AERIAL?

11. If you are a short wave listener in Chicago, and the time is 8:00 p.m. where you are, what will be the approximate time in the following places whose stations you tune-in?

- | | |
|--------------------------|---------------|
| a. <i>Rio de Janeiro</i> | A. 3:00 p.m. |
| b. <i>Manila</i> | B. 5:00 p.m. |
| c. <i>Rome</i> | C. 11:00 p.m. |
| d. <i>Nome</i> | D. 7:00 a.m. |

- c. *Yukon*
- f. *Bombay*


- E. 3:00 a.m.
- F. 10:00 a.m.

12. The glamorous feminine comedienne of a certain broadcast is called "Stinky" by the orchestra leader of the show. Can you find their names in this list?

- | | |
|------------------------|-----------------------------|
| a. <i>Fannie Brice</i> | A. <i>Skinney Ennis</i> |
| b. <i>Martha Raye</i> | B. <i>Peter Van Steeden</i> |
| c. <i>"Honeychile"</i> | C. <i>Meredith Wilson</i> |
| d. <i>Gracie Allen</i> | D. <i>Kaye Kyser</i> |

13. Of the following stations, one is the farthest west station of the basic Blue network; another the farthest west of the basic Red network. Identify these two stations.

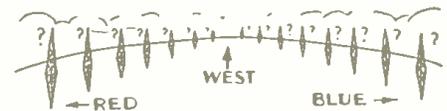- a. *San Francisco—KGO—KPO*
- b. *Salt Lake City—KUTV—KDYL*
- c. *Denver—KID—KOA*
- d. *Omaha—KOIL—W'OW*
- e. *St. Louis—KWK—KSD*



RED & BLUE, WHICH ARE FARTHEST WEST?

14. Of all the various bands, which of the following is the highest wavelength allocated to television in the United States?

- | | |
|-------------|------------|
| a. 500 kc. | d. 50 mc. |
| b. 1000 kc. | e. 70 mc. |
| c. 2000 kc. | f. 100 mc. |

15. When hooking up a double-button carbon microphone for "home broadcasting," the best way to connect it is

- a. *directly across the grid and cathode of the detector tube.*
- b. *directly across the grid and cathode of the first audio amplifier tube.*
- c. *to the grid and cathode of the detector tube through a special coupling transformer.*
- d. *to the grid and cathode of the first audio amplifier tube through a special coupling transformer.*

16. A line noise filter ordinarily consists of

- a. *A.F. choke coils.*
- b. *R.F. choke coils.*
- c. *fixed condensers.*
- d. *variable condensers.*

17. The Purple Network is the name for

- a. *the Mutual Broadcasting System chain.*
- b. *the Columbia Broadcasting System chain.*
- c. *the combined Red and Blue chains of the National Broadcasting Company.*
- d. *the Intercity Broadcasting System chain. (See Answers, page 757)*

The Martian Flash

An Inter-Stellar Magazine for all Radio Enthusiasts.

Published:—When Interplanetary Conditions Permit.

Interplanetarian Pub. Co., (Very) Ltd.

Fips—Editor

Subscription Price for All Planets—Priceless.

The Editor accepts no contributions of any kind, neither cash nor literary. This entire publication is read at your own risk. The Editor is not responsible for either the contents or your own reactions.

Martian Office—

698743209 K K K 9 Street,
Martolus, Mars.



Fips, the Office Boy, who tells us the latest happenings on Mars.

April, 1939

EDITORIAL

● MANY of our readers have written in asking for in-

formation as to how the Martians, as illustrated in the previous issues of *The Martian Flash*, got that way. In other words, why the telescope eyes, the barrel chests, the elephantine nose and the web feet?

The answer is simple. The atmosphere on Mars is so thin that it actually compares with the tops of the highest mountains on Earth. Mars, being much smaller than the Earth, lost most of its atmosphere through the ages and now has very little left. Indeed, it would not have much at all if the Martians themselves did not replenish it continually by artificial means. When I first came here I had continuous nose-bleeds and I was continually gasping for air. Now I am equipped at all times with a simple pocket apparatus which automatically gives me a sufficient amount of oxygen, without which I could not live at all on Mars.


Down through the ages the Martians had to adjust themselves to the rarefied atmosphere and that is why they must have enormous lungs (which require a large chest) to compensate for the rarefied air.

Scents and smells travel poorly in a

rarefied atmosphere. For this reason the Martian nose grew longer and longer so that it could get toward the source of the smell rather than have the smell come to it.

The telescopic eyes are also due to evolution because the Martians, using their eyes continually, found it necessary to grow eyes which could accommodate themselves better to their complex mode of living than fixed eyes. There is nothing new in all of this. Barrel chests are already in existence among certain inhabitants of the South American Andes. Another example is the elephant's nose. The peculiar shape is necessary because its huge bulk hinders it in kneeling down. Therefore the long, flexible nose has been evolved. Pop eyes are not new either. Snails and certain fishes have had them for millions of years, not to speak of Eddie Cantor!

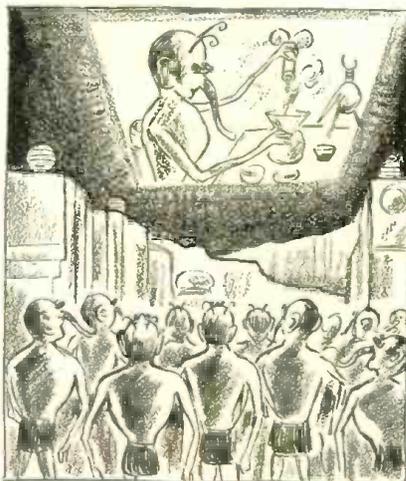As for the web feet, you know that gravitation on Mars is very low. For instance, my weight on Earth is 160 pounds, but is only 60 pounds on Mars! Consequently, to get a better foothold for the large proportioned body, the web feet were evolved by nature. The antennae on the Martian's forehead are not so new either because your insects on Earth have had them for many millions



"—the upper atmosphere served as a sort of mirror screen for television images—"

of years. So, you see, there is nothing new under the sun, and the grotesque—to you—is after all not so grotesque as you imagined.

MARTIAN TELEVISION

By Ulysses Mohammed Fips

* * Martian Star Reporter * *

EVER since my articles have appeared in *The Martian Flash* there seems to be an intense interest among the readers regarding the present status of television on the planet Mars.



A close-up of Earth 1,250,000 years ago, showed ape-like beings, but no men.

Let me say that, as you can probably imagine, television has been here for many millions of years and therefore it is somewhat different from what you would expect it to be.

To begin with, at the present time it is quite unnecessary for Martians to have any television receiving apparatus. Like many other things on Mars, all forms of communication have been personalized in the Martian himself. At first this was not the case and television was received on screens similarly to yours on Earth. Refinements then brought pocket television receivers and, much later, television receivers which could be strapped to the wrist; still later they got so small that by means of a special lens, you could view excellent images on a small finger ring and get the sound as well. Still later, huge television images were projected into the rarefied upper Martian atmosphere similar in principle to Northern Lights on Earth. These images were so colossal, yet of such excellent quality, that the upper atmosphere served as a sort of mirror screen and standing on the surface of Mars you could enjoy television in full colors any night of the year. As there are practically no clouds on Mars at any time, good television views were always to be had in this manner. These images were from 9 to 15 miles above the surface of Mars and you may imagine how huge these images must have been in order to see them plainly from Mars' surface. While such television exhibitions are still being used, especially for extraordinary occasions, nowadays the television images are received directly on the retina of the Martian's eyes. The reception comes over the Martian's antennae and the special wave motions are conducted directly toward the back of the eye. All one has to do is close one's eyes and see the transmitted television

(Continued on page 762)

Ultra-High Frequency Antennas

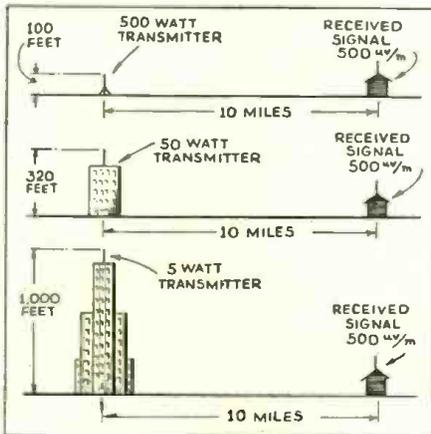


Fig. 1 shows the quantitative importance of the antenna height. In the three cases, the transmitter power is adjusted to give equal signals at a fixed distance for three heights of 100 feet, 320 feet and 1,000 feet. The respective transmitter powers required are 500 watts, 50 watts and 5 watts. In so far as the listener is concerned, the effectiveness of the three stations is the same although there is a great difference in power. Effective power is proportional to the square of the altitude or height.


Coaxial Antenna

● AN ideal antenna for ultra-high frequency applications is one which uniformly radiates the strongest possible signal along the surface of the earth. To attain this objective, it must be mechanically designed for easy mounting at the top of a high pole to take full advantage of height, and further it must be electrically designed to radiate most efficiently in horizontal directions for the greatest utilization of the radio power.

The coaxial antenna (Fig. 2) represents a practical form of this antenna utilizing certain new principles that attain the desired objective. Its slender proportions, short length, light weight and coaxial symmetry enable it to be applied easily to high steel poles of standard construction. Its superior radiating capabilities make it the most modern approach to the idealized radio antenna.

The ultra-high frequency radio antenna may be considered as somewhat similar to a beacon light except that it emits polarized radiations of a longer wavelength. It, too, must be placed high above the earth if it

Fig. 2. Method of terminating lower end of coaxial antenna in a very high impedance.

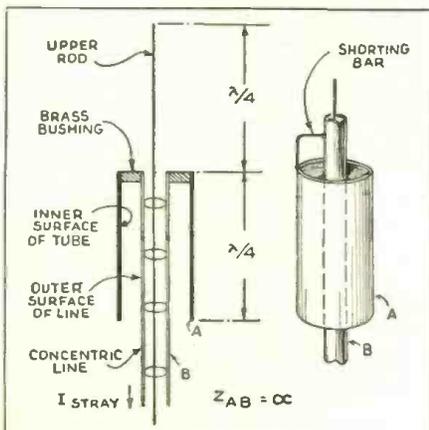

is to be effective in transmitting over long distances.

In most practical cases the radio equipment is located at ground level in a building and is connected to the high antenna by means of a transmission line. In this discussion a low-loss concentric type transmission line will be assumed. In this line the useful current at ultra-high frequencies is carried by two paper-thin metallic conducting surfaces; first, the skin surface of the quarter-inch copper inner conductor which may be considered as the outgoing conductor and secondly, the inside skin surface of the seven-eighths inch copper sheath which may be considered as the return conductor.

The outer surface of the seven-eighths inch copper sheath plays no part in this transfer of useful energy in the idealized case. By reference to Fig. 2 which shows a cross-section of an elementary form of a coaxial antenna a new circuit element is evident. The enclosed sheath of the transmission line acts in conjunction with the inner surface of the larger surrounding tube to form a short-circuited quarter-wave concentric line. The characteristics of this shorted section of line cause an extremely high impedance to be created across points A and B. By simple analogy this is equivalent to a high Q anti-resonant circuit which isolates the pole below point B from the antenna and reduces the stray pole current to a minimum.

When this antenna is supplied with power, the center of the antenna is at minimum potential, the top is at a high potential and the bottom of the tube is at a high potential. The presence of the high Q anti-resonant circuit element at the bottom of the tube allows this high potential to exist even in the immediate proximity of the transmission line.

The concentric line which feeds the antenna is a standard seven-eighths inch diameter gas tight line and is placed for mechanical strength inside a heavy brass supporting pipe approximately 2 inches in diameter both terminating in a solid brass bushing at the feed point, i.e., center of the antenna. A three-inch diameter coaxial tube is attached solidly to this bushing at the feed point and elsewhere is kept insulated from the 2-inch pipe by internal ring insulators. The quarter-wave rod projects through a sturdy insulator at the feed point and is connected at the feed point to the inner conductor of the transmission line.

Electrically, this coaxial antenna is a center-fed doublet and consequently closely matches the surge impedance of a standard seven-eighths inch concentric line. The doublet or dipole antenna consists of the quarter-wave rod and the outer surface of the three-inch tube which is also one-quarter wave long, making a total active radiator length of one-half wave.

At a frequency of 35.6 megacycles, a coaxial antenna was substituted directly for a "J" type antenna and comparative field intensity measurements of the signals were made in two directions and at two distances away from the station. The measurements in this case showed an 8 db. increase in signal strength in favor of the coaxial antenna for equal power input. To obtain a similar increase in signal strength from a 500 watt station by changing the carrier power alone would require an increase in the power of the station to 3 kilowatts!—Courtesy "Pick-Ups," Western Electric Co. publication.

Rotating Beam Loop

For Ham & SWL Use

● SINCE very little seems to have been done (or at any rate published, beyond bare specifications) with folded aeri-als, these appeared to offer the best field for experiment, and possessed many obvious advantages when it came to considering 56 mc. propagation. Long aeri-als are clumsy, unless one lives in the depths of the country, and are certainly unsightly.

The problem soon boiled down to one of mechanical difficulties, and it is the simple solution of these that is offered now.

A rotating beam was indicated, as narrow as possible, provided compass points were marked on the dial. The Reinartz double loop is compact, easily pushed up beyond trees or chimney pots, and it seems could be made very light; no small consideration this, when it has to be lifted 40 feet up. Wind resistance could also be reduced to a minimum.

No claim for electrical efficiency is made so far as experiments are being carried out with feeder lines, but it gives an 18 per cent increase over a dipole, and 6-1 ratio from back to front. For reception, car interference with a low dipole is a very serious problem, but is reduced by an amazing amount when using this method.

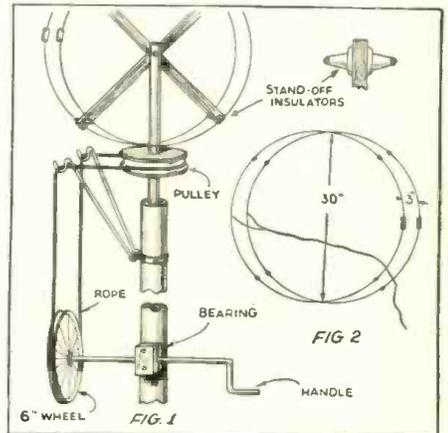


Fig. 1. The construction of the 56 Mc. Rotating Beam.

Fig. 2. The loops used for the 56 Mc. Rotating Beam.

A coaxial cable would solve feeder problems nicely, and several types of such cable are now available on the market.

Construction

A 30-inch cross of 1 1/4 in. by 1 in. pine was made by halving at the center, and a slot cut in an 18-inch support of 2 in. by 2 in. (Fig. 1). By shaping the bottom of the slot with a file, and pinning at the center, a tight fit with no play was obtained. A half-inch hole 12 in. long was drilled in the bottom to fit over a length of pipe, driven 6 inches into the top of the mast. One metal washer gave a smooth bearing. An old ebonite lead-in tube 18 in. by 2 in. with 1/2 in. walls was used, but wood is as good for the support.

Three discs of 1/2 in. wood, one soft 6 in. in diameter and two oak 7 1/2 in. in diameter, were fitted 2 in. from the bottom of the support, with a screw at each end of a diameter to hold it tight. This forms the pulley for a continuous rope to rotate the loops.

(Continued on page 763)

What Do You Think?

A "Ham" Replies to "SWL Punk"

Editor,

I would like to answer Mr. Austin Wardman's very interesting letter in the February issue and give my opinion of the QSL situation from a "Ham's" point of view, which may or may not be representative.

First, I would consider the SWL and Ham hobbies two very interesting but distinctly different ones. To be a successful SWL DXer takes a great amount of time and effort. Hours must be spent identifying new stations well enough to get confirmations. In the end, success is the reward. "Ham" radio, on the other hand, requires much time and effort, but in a different way. I don't think either of these hobbies, to be successful, can spare much time for the other. I'm quite sure Hams almost never have time to listen anywhere but on the particular band they are working; in fact, I have managed to keep very busy on about 100 kc. of the forty meter band for a year and a half.

Many prospective amateurs have in mind to go on fone only when they get their "tickets," and consider code just a "necessary evil." I know because I was that way myself, but now I think that is all wrong and after 1½ years "on the air" I have no desire to go on fone. The fone end is O.K., but a fellow should become a really good C-w operator first, in my opinion. That means to be able to send code and receive accurately at least 25 wpm. and also know correct operating procedure. Mr. Wardman. Ham radio welcomes fellows like that and you will have plenty of contacts.

The prospective Ham should buy, if possible, a really good "communications" type receiver, provided with a beat oscillator, of course. An audio oscillator is not needed if you don't wish to build one for keying practice, as you can place your key in series with the head fones to receiver and use almost any station to key on their beat note. Many short wave commercials have their carrier on the air continuously and WWV (5000 kc.) transmits a 400 cycle note continuously from 4 p.m. to 2 a.m., which is good for keying.

Of course, I won't go into the building of "rigs" as that is always well covered in the magazines. However, I might say that even a single 6L6 and a good antenna with about 25 watts input will give you much pleasure. Many fellows work "all over the world" with a little rig of that type. I used a single 6L6 for some time with very fine results.

The perfection of code technique is a very fascinating game, and I would suggest that Austin become an enthusiastic CWL (continuous wave listener). I'm sure the boys on CW would more readily QSL, as they would consider a fellow interested enough to copy call letters worthy of a card. Most of the SWL's looking for cards from Hams are naturally sending their cards to the boys on 20 meter fone. Many of these boys may have received an initial bunch of cards years ago, used them all and never bought any new ones since. So how could you expect to get a card from them? Then again they may have a few cards but save them for their unusual two-way contacts. I used to get cards from CWL's and was always very happy to send them a card in return but lately, I haven't received one card from CWL's. Guess I'm slipping, hi!

I have had over 1500 two-way contacts in my 1½ years on the air, but as I look over the QSL card situation, I find only about 300 cards there. That has kept me quite busy though, and I fear I would need a secretary here to QSL 100%. I can say that the Hams I have sent cards to have QSL'd practically 100%.

Austin wishes to know why the Hams are in this game anyway. I would say a vast majority are in it to improve their operating technique, and to carry on an interesting conversation on the air, not merely to say,

Herman Ruppert, 226 East 81 St., N. Y. City, is this month's prize winner—1 yr's subscription to R&T

Amateur station of Ota- kar Halas, Brno 2, Krizova 44, Czechoslovakia. Call OK2RR.

Honorable mention—six months' subscription, to Domenick Ferrari.

Famous S-W Fan—D.R.D. Wadia, 203 Walkeshwar Rd., Bombay, India. (Pres. of India Radio Amateurs' League.)

"Pse qsl es cul." Some of the old-timers don't get on the air, for they are afraid of finding "Lids" there, hi!

So all you fellows get on the air and show them—there are some fine operators coming up.

Well, here is wishing all the SWL DXers the best of luck. Incidentally, I could use a little luck here myself as I need a couple of states for W.A.S. and Africa for W.A.C.

So 73, es I'll bennu soon "on the air."

RADIO W2KSL,
WM. GORDON,
Apt. 3-C,
3140 Kingsbridge Ave.,
Bronx, N. Y. City.

He Likes Our Television Articles!

Editor,


I have been a reader of your very FB magazine for four or five years and I can sincerely say that I find it very interesting and helpful in all branches of radio. I am a student of commercial radio and television in Kansas City, Mo. Your articles on commercial radio and television are very


helpful to me; I also like your *International Radio Review* and I never pass over *What Do You Think?* without getting a great "kick" out of it.

My receivers are a Raco Super Clipper and a Doerle five-tuber. I have only a few veris because I spend most of my time experimenting with new receiving circuits, amplifiers, photo-cells and cathode-ray tube circuits. Some of this equipment can be seen in the photo. I am proud to be a member of the *Short Wave League*.

More power to your magazine under its new name. (See photo herewith.)

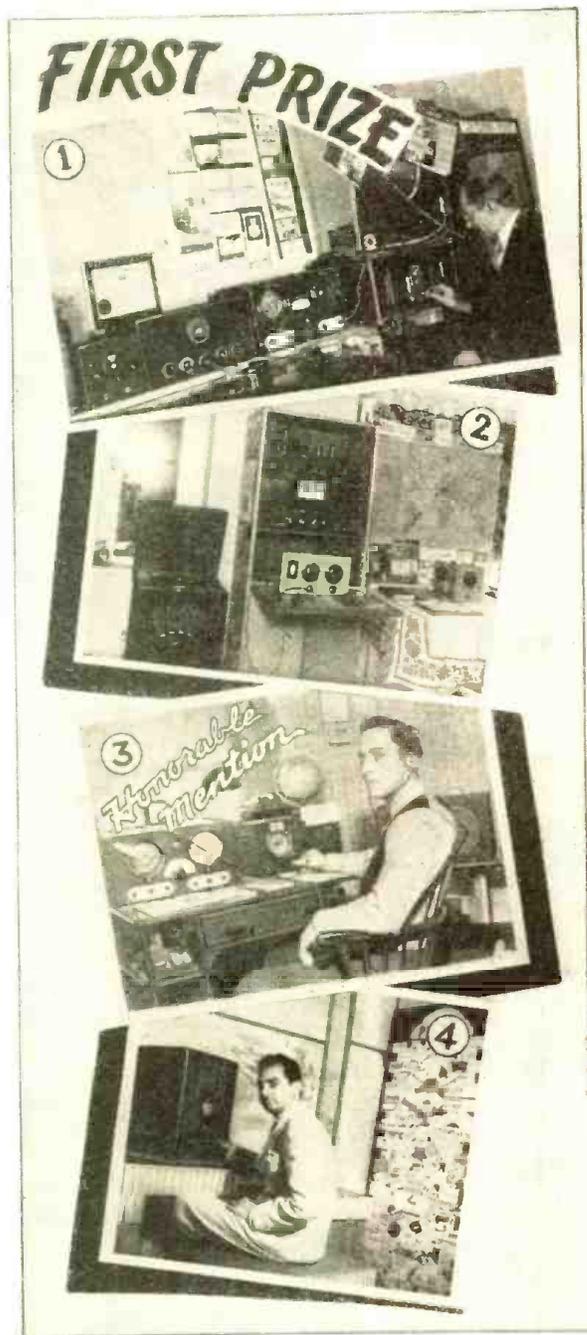DOMENICK FERRARI,
617 Smith Ave., N.W.,
Canton, Ohio.



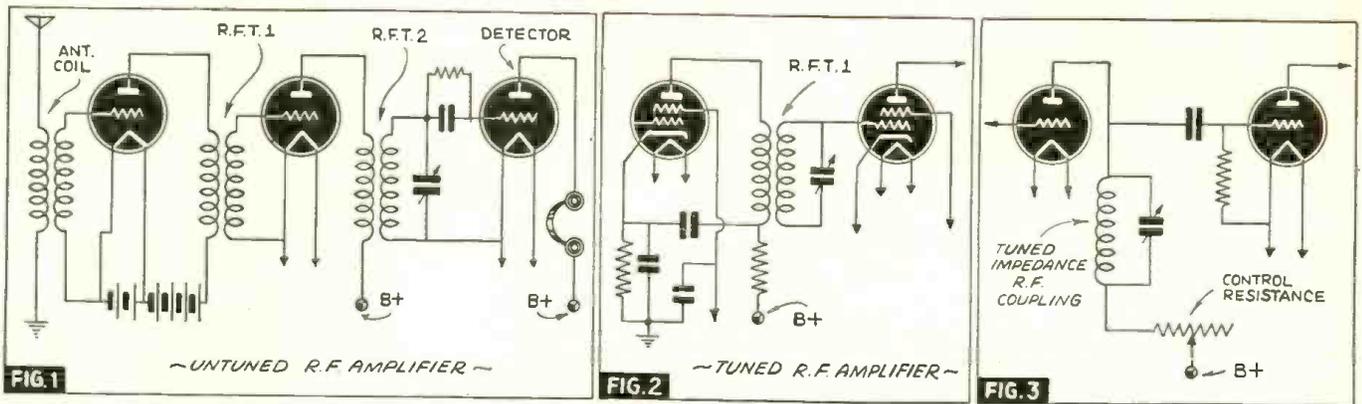

Diagrams above show untuned R.F. amplifier, tuned R.F. stage and tuned impedance R.F. coupling.

The RADIO BEGINNER

Lesson 6—

Radio Frequency Amplifiers

● WE can, for the sake of convenience, mentally divide a radio receiver into three separate parts. One of these, the section pertaining to *detection*, has already been considered in a previous article. The other two are the *audio frequency* amplifying and the *radio frequency* amplifying sections. It is with this latter part that we are now concerned.

We have already learned, during our consideration of vacuum tube operation, that the detector tube takes oscillations of radio frequency and turns them into direct current impulses. It might be thought that the output of this detector tube would vary in direct proportion to the input voltage applied to the grid. However, as the grid voltage is lowered a certain point, known as *cut off grid voltage*, is reached, below which there will be no effect in the plate circuit of the detector. In other words, the signal supplied by the antenna (that is, the radio frequency oscillations) must be of a certain order of magnitude before a response will be secured from the detector. The use of one or more stages of *radio frequency* amplification enables the signal to be built up to such a value that detector action can definitely be secured. This amplification ahead of the detector tube makes it possible to receive stations which would otherwise be inaudible. When a potential greater than cut-off grid voltage is applied, the output in the plate circuit of the detector increases more rapidly than the square of the input voltage.

Untuned R.F. Amplifier

Figure 1 shows a multiple stage *untuned radio frequency amplifier*. The very small alternating, high frequency wave received by the antenna causes a current (of the same frequency) to flow in the antenna circuit, comprising the antenna itself, the antenna coil, and the ground. The current, flowing through the antenna coil (or the primary) creates a magnetic field which in turn causes a potential of the same frequency to be induced across the secondary of the coil. Note, however, that this sec-

Martin Clifford, W2CDV

ondary is in the grid circuit of the first tube, and hence this potential is impressed on the grid. We recall from our discussion of the vacuum tube that a small potential on the grid can control a comparatively large current in the plate circuit. This current flows through the primary of the radio frequency transformer (marked RFT-1). Once again, as in the antenna coil, we have magnetic action and consequently a voltage induced across the secondary of the coil, and impressed on the grid of the next tube. A sufficient number of radio frequency (abbreviated R.F.) stages can be used until the signal is of such strength that it can be detected.

It should be observed that the voltage amplification is sometimes secured only by means of the tubes. The purpose of the R.F. transformers is to obtain an alternating voltage across the secondary (or on the grid of the tube) from the varying plate current of the preceding tube. We also secure a voltage step-up having the secondary wound with more turns of wire than the primary. There is a tendency in such an inductance for the amplification to increase as the frequency increases. This would mean that the amplification would not be constant over a wide range. Such a coil arrangement would tend to make the circuit unstable, since there would be the possibility of *feedback* through the tube capacity. Where the primary and secondary of an R.F. transformer are of the same size, amplification, although somewhat lower, is fairly constant over a wide range, and with less feedback. By *feedback* we mean that condition whereby a tube begins to act as an oscillator or a generator of radio frequency energy. A tube, designed to act as an R.F. amplifier, and behaving as an oscillator, causes howling, squealing and loss of efficiency in reception.



We have so far considered a type of R.F. amplifier rarely used today. An untuned system of transformer coupling will cover

only a very limited range of frequencies and is unsatisfactory. The purpose of an R.F. amplifier should be not only to increase signal strength, but also to increase *selectivity*.

Tuned R.F. Amplifiers

When we deal with an R.F. amplifier, we must handle waves that vary from a few hundred thousand cycles per second to several million cycles. In order to secure greater efficiency from our R.F. transformers, we place *variable condensers* across the secondaries of these coils, thus enabling us to tune in the particular frequency we want. See Figure 2. This type of circuit is known as a *tuned radio frequency amplifier* and (Continued on page 748)

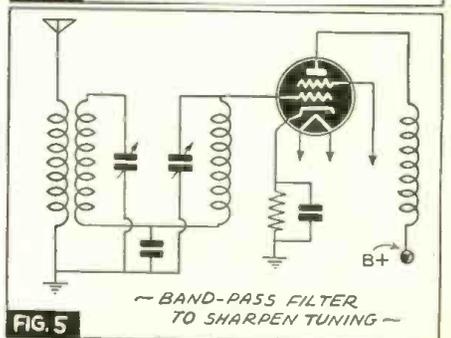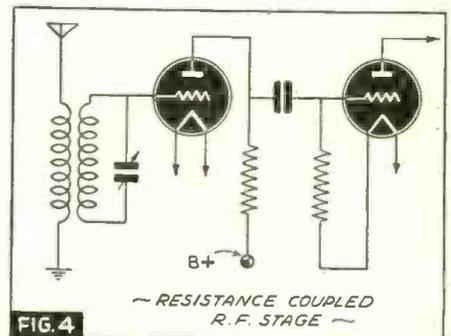These diagrams show resistance-coupled R.F. stage and band-pass filter or tuner to increase selectivity.



Electronic Television Course

Henry Townsend

Lesson 2—Photo Cells, Iconoscope, Image Dissector

● **PHYSICISTS** in their experiments with the alkali metals have found that light falling upon these metallic films produced enough energy to dislodge electrons from these surfaces. These electrons were collected by a positively charged electrode and currents of small magnitude were able to be passed through the tube. The alkali metals which show this photo-electric effect are Lithium, Potassium, Sodium, Rubidium and Caesium. Caesium and its compounds, when deposited upon other metallic films, respond to that particular part of the light spectrum which nearly approximates the response (or sensitivity) of the human eye and also shows the greatest *photo-electric* effect for a given amount of visible light of any of the photo-electric metals; consequently it is most commonly used as photo-electric material in television transmitting picture tubes.

A *photo-electric cell* consists of a cathode (coated with a photo-electric material, such as Caesium) and a positive electrode called the *anode*, located in front of the photo-electric surface to collect the electrons which are emitted from the cathode when light is caused to fall on this surface. See Figures 1-A and 1-B.

The *Iconoscope* (Fig. 2-A) is a cathode-ray tube in combination with a photo-electric screen consisting of millions of tiny photo-electric cells, each cell constituting a condenser. This screen is commonly referred to as a *Mosaic screen*, and when light is caused to strike these tiny photo cells (or Mosaic), in the form of an image, a charge of electrical energy is picked up by the cells where the light of the image strikes. (See Fig. 2-B.) This charge is discharged through the cathode beam as it traverses this Mosaic screen in the process of scanning point by point

The accompanying pictures show at 1-A and 1-B, a photo cell; 2-A—Fundamental action of the Iconoscope; 2-B—Iconoscope pick-up; 3—Image dissector; 4—Typical Television Transmitter Line-up; 5—Form of scanning pulse; 5-A—How interlaced scanning takes place.


and line by line. This discharge is then amplified by a series of amplifiers to a level where it may be transmitted over a co-axial cable and modulate a television transmitter.

The invention of the iconoscope is credited to Dr. Vladimir Zworykin of the RCA Laboratories. Prior to this, Philo T. Farnsworth was the first inventor to show a successful electronic picture tube, which he called the Farnsworth Image Dissector. This image dissector, shown in Figure 3, also incorporates a photo-sensitive cathode at one end, upon which an image is focused, similar to a photographic camera. This image causes a flow of electrons where light strikes it, and some distance away from the cathode we have an image in the form of an electronic stream corresponding to the light and dark portions of the image. This electronic image is then moved past an aperture in both a vertical and horizontal plane and the electrons are collected by a positively charged electrode in the proper sequence, then amplified as in the case of the iconoscope.

Still another type of picture tube used today is called a *monoscope* because it will only transmit or reproduce one image, namely, the image deposited in carbon on a target electrode, usually made of aluminum. This tube operates by virtue of the fact that carbon is a poor emitter of electrons. It consists of an electron gun, focusing electrodes, and electrostatic or electromagnetic means of moving a beam of electrons across this printed image, plus a collecting electrode to collect the secondary electrons which are emitted from that portion of the target which is not covered by the carbon deposit forming the image. This tube has an exceptionally high output and is used chiefly for testing or demonstrating television transmitting and receiving equipment. Various types of images can be printed on the target electrode, such as human figures, test charts, etc. When received, these establish the fidelity of a television transmitter and receiver.

It is presumed that the reader is familiar with the fact that in

(Continued on page 757)

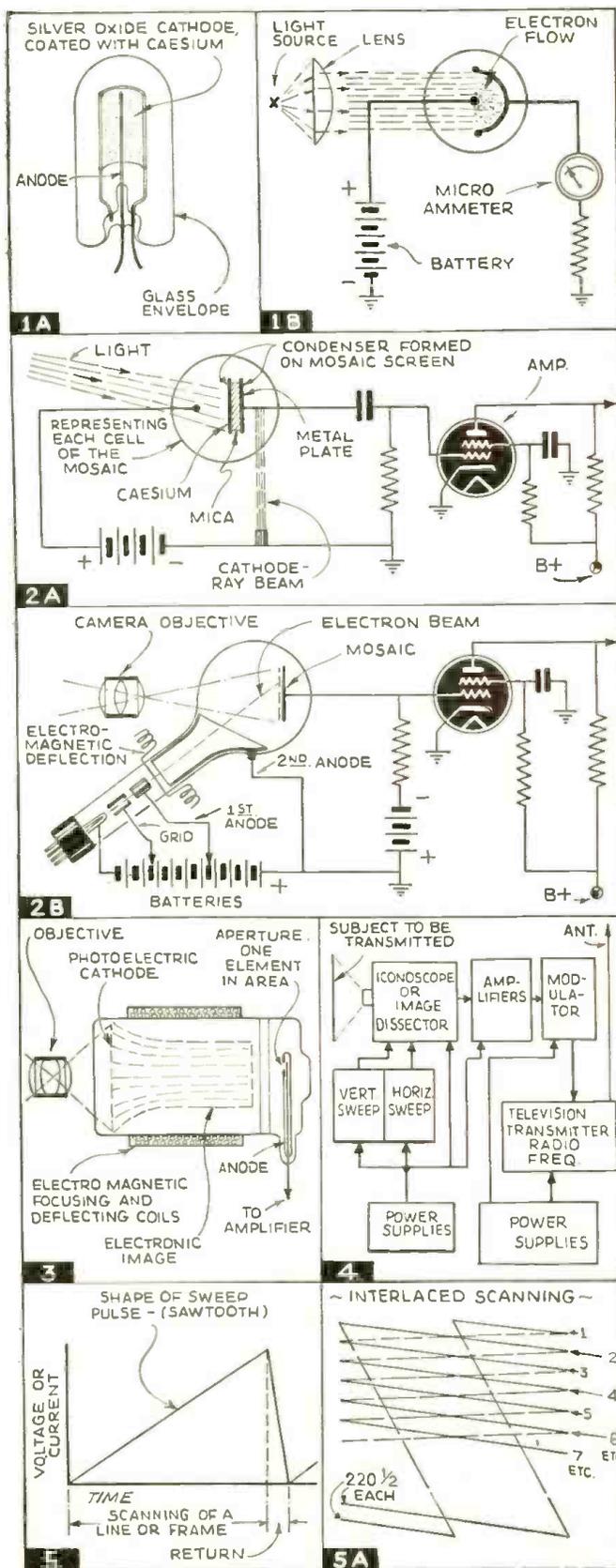

World Short Wave Stations

Revised Monthly

Complete List of SW
Broadcast Stations

Reports on station changes are appreciated.

Mc.	Call	Mc.	Call	Mc.	Call			
31.600	WIXKA	BOSTON, MASS., 9.494 m., Addr. Westinghouse Co. Daily 6 am.-1 am., Sun. 8 am.-1 am. Relays WBZ.	21.470	G5H	DAVENTRY, ENG., 13.97 m. (See 21.550 mc.), 5:45-8:50, 9 am.-noon.			
31.600	WIXKB	SPRINGFIELD, MASS., 9.494 m., Addr. Westinghouse Co. Daily 6 am.-1 am., Sun. 8 am.-1 am. Relays WBZ.	21.450	DJS	BERLIN, GERMANY, 13.99 m., Addr. Broadcasting House. 12.05-5.30 am.			
31.600	W3XEY	BALTIMORE, MD., 9.494 m., Relays WFBR 4 pm.-12 m.	19.020	H56PJ	BANGKOK, SIAM, 15.77 m. Mondays 8-10 am. See 15.23 mc.			
31.600	W2XDV	NEW YORK CITY, 9.494 m., Addr. Col. Broad. System, 485 Madison Ave. Daily 6-11 pm.; Sat. and Sun. 1:30-6, 7-10 pm.	18.480	H8H	GENEVA, SWITZERLAND, 16.23 m., Addr. Radio Nations. Sun., 10.45-11.30 am.			
31.600	W9XHW	MINNEAPOLIS, MINN., 9.494 m. Relays WCCO 9 am.-12 m.	16 Met. Broadcast Band		15.330	W6XBE	SAN FRANCISCO, CALIF., 19.57 m., 3-9 am.	
31.600	W3XKA	PHILADELPHIA, PA., 9.494 m., Addr. NBC. Relays KYW 9 am.-10 pm.	17.845	HVJ	VATICAN CITY, 16.81 m. Heard 12 n. on Wednesday.	15.320	OLR5B	PRAGUE, CZECHOSLOVAKIA. 19.58 m. Addr. (See 11.840 mc.) Sun., Wed., Sat. 5-5.10 pm.; Mon., Tues., Thurs., Fri. 6.55-9.55 pm.
31.600	W5XAU	OKLAHOMA CITY, 9.494 m., Sun. 12 n.-1 pm., 6-7 pm. Irregular other times.	17.840	DJG	BERLIN, GERMANY, 16.82 m., 10.35 am.-1 pm.	15.320	OZH	SKAMLEBAK, DENMARK, 19.58 m., Sun. 8 am.-1:30 pm.
31.600	W4XCA	MEMPHIS, TENN., 9.494 m. Addr. Memphis Commercial Appeal. Relays WMC.	17.820	ZROB	ROME, ITALY, 16.84 m., Addr. (See 2RO, 11.81 mc.) 5-7.30 am. Relays 2RO to 6 pm. irregularly.	15.310	GSP	DAVENTRY, ENG., 19.6 m., Addr. (See 17.79 mc.) 3-5.15 am., 1.45-4 pm.
31.600	W8XA1	ROCHESTER, N. Y., 9.494 m., Addr. Stromberg Carlson Co. Relays WHAM 7.30-12.05 am.	17.810	GSV	DAVENTRY, ENGLAND, 16.84 m., 5.45-8.50 am., 12.20-4 pm.	15.300	YDB	SOERABAJA, JAVA, N. E. I. 19.61 m. Addr. NIRM. 10 pm.-2 am.
31.600	W8XWJ	DETROIT, MICH., 9.494 m., Addr. Evening News Ass'n. Relays WWJ 6-12.30 am., Sun. 8 am.-12 m.	17.810	TPB3	PARIS, FRANCE, 16.84 m. Addr. (See 15.245 mc.) 9.30-11 am.	15.300	XEBM	MAZATLAN, SIN., MEX., 19.61 m., Addr. Box 78, "El Pregonero del Pacifico." Irregularly 9-10 am., 1-2, 8-10 pm.
31.600	W9XPD	ST. LOUIS, MO., 9.494 m., Addr. Pulitzer Pub. Co. Relays KSD.	17.800	OIH	LAHTI, FINLAND, 16.85 meters, 4-9 am.	15.300	ZRO6	ROME, ITALY, 19.61 m., Addr. (See 2RO, 11.81 mc.) 10 am.-2:30 pm.
26.550	W2XGU	NEW YORK CITY, 11.3 m. Relays WMCA.	17.790	GSG	DAVENTRY, ENG., 16.86 m., Addr. B.B.C., London. 5:45-8:50, 9:10-1:15 am., 12:20-4 pm.	15.290	VUD4	DELHI, INDIA, 19.62 m., 9:30-11:30 pm.
26.450	W9XA	KANSAS CITY, MO., 11.33 m., Addr. Commercial Radio Eqpt. Co. Testing	17.780	W3XL	BOUND BROOK, N. J., 16.87 m., Addr. Natl. Broad. Co., 9 am.-5 pm. to Europe, 5-11 pm. to So. Amer.	15.290	LRU	BUENOS AIRES, ARG., 19.62 m., Addr. El Mundo. Relays LRI, 7-9 am.
26.400	W9XAZ	MILWAUKEE, WIS., 11.36 m., Addr. The Journal Co. Relays WTMJ from 1 pm.	17.770	PHI2	HUIZEN, HOLLAND, 16.88 m., Addr. (See PHI, 11.730 mc.) Daily 7:40-9:10 am. Mon & Thurs. 7:40-9 am. Sun. 6:25-9:45 am.	15.280	DJQ	BERLIN, GERMANY, 19.63 m., Addr. Broadcasting House. 12.05-11 am., 4.50-10.50 pm. Also Sun. 11.10 am.-12.25 pm.
26.300	W2XJ1	NEW YORK, N. Y., 11.4 m., Addr. Bamberger Broad. Service, 1440 Broadway. Relays WOR 12 n.-6 pm.	17.760	DJE	BERLIN, GERMANY, 16.89 m., Addr. Broadcasting House. 12.05-5.50, 6-7.50 am.	15.270	HI3X	CIUDAD TRUJILLO, D. R., 19.65 m. Relays HIX Sun. 7.40-10.40 am. Tues. and Fri. 8.10-10.10 pm.
26.100	W9XJL	SUPERIOR, WIS., 11.49 m. Relays WEBC daily.	17.755	Z8W5	HONGKONG, CHINA, 16.9 m., Addr. P.O. Box 200. Dly. 11.30 pm.-1.15 am., 5-10 am., Sun. 9 pm. (Sat.)-1.30 am., 5-9.30 am. Operates irreg.	15.270	W3XAU	PHILA., PA., 19.65 m. (Addr. See 21.52 mc.) 3-7 pm.
26.050	W9XTC	MINNEAPOLIS, MINN., 11.51 m. Relays WCTN 9 am.-1 pm., 7 pm.-12 m.	End of Broadcast Band		15.270	W2XE	NEW YORK CITY, 19.65 m., Addr. (See 21.570 mc.) 1-3 pm. Sat. & Sun. 1:30-2:30 pm.	
26.050	W9XH	SOUTH BEND, IND., 11.51 m., Addr. South Bend Tribune. Relays WSBT-WFAM 2.30-6.30 pm., exc. Sat. and Sun.	17.730	W2XGB	HICKSVILLE, L. I., N. Y., 17.33 m., Addr. Press Wireless, Box 296. Tests 9.30-11.30 am. except Sat. and Sun.	15.260	GSI	DAVENTRY, ENG., 19.66 m., Addr. (See 17.79 mc.) 3-5.15 am., 12.20-1.30 pm.
25.950	W6XKG	LOS ANGELES, CAL., 11.56 m., Addr. B. S. McGlashan, Wash. Blvd. at Oak St. Relays KGFJ 24 hours daily. DX tips Mon., Wed. and Fri. 2:15 pm.	17.280	FZE8	DJIBOUTI, FRENCH SOMALILAND, 17.36 m. Test XMSN 1st Thurs. each month 8-8.30 am. Next B.C. April 6.	15.250	WIXAL	BOSTON, MASS., 19.67 m., Addr. University Club. 2:30, or 4 pm., ex. Sat. and Sun.
25.950	W9XUP	ST. PAUL, MINNESOTA, 11.56 m., Relays KSTP evenings.	15.550	CO9XX	TUINICU, ORIENTE, CUBA, 19.29 m., Addr. Frank Jones, Central Tuinicu, Tuinicu, Santa Clara. Broadcasts irregularly evenings.	15.245	TPA2	PARIS, FRANCE, 19.68 m., Addr. 98 Bis. Blvd. Haussmann. "Paris Mondial" 6-11 am.
21.630	W3XAL	BOUND BROOK, N. J., 13.8 m., Addr. N.B.C., N. Y. C. 9 am.-4 pm.	15.510	XOZ	CHENGTO, CHINA, 19.34 m. Daily 9.45-10.30 am.	15.230	HS6PJ	BANGKOK, SIAM, 19.7 m. Irregularly Mon. 8-10 am.
21.570	W2XE	NEW YORK CITY, 13.91 m. (Addr. CBS, 485 Madison Ave., N. Y. C. Daily 7.30-10 am. Sat., Sun. 8 am.-1 pm.)	15.370	HAS3	BUDAPEST, HUNGARY, 19.52 m., Addr. Radiolabor. Gyali Ut 22. Sun. 9-10 am.	15.230	OLR5A	PRAGUE, CZECHOSLOVAKIA, 19.7 m. Addr. (See OLR4A, 11.84) Mon.-Fri. 7.50-10.55 pm. Sat. and Sun. 5-5.15 pm., Sun. 5.55-8.55 pm., Tues. 4.40-5.15 pm.
21.565	DJJ	BERLIN, GERMANY, 13.92 m., Addr. Broadcasting House, 6-7.50 am.	15.360	DZG	ZEESEN, GERMANY, 19.53 m., Addr. Reichspostzentralamt. Tests irregularly.	15.220	PCJ2	HUIZEN, HOLLAND, 19.71 m., Addr. N. V. Philips' Radio Hilversum, 3-4.30 am. Tues., 9.30-11.30 am. Weds. Daily 7.25-8.25 am.
21.550	GST	DAVENTRY, ENG., 13.92 m., Addr. (B.B.C., London) Irregular at present.	15.360	—	BERNE, SWITZERLAND, 19.53 m. Irreg. 6.45-7.45 pm.	15.210	W8XK	PITTSBURGH, PA., 19.72 m., Addr. (See 21.540 mc.) 9 am.-1 pm.
21.540	W8XK	PITTSBURGH, PA., 13.93 m., Addr. Grant Bldg. Relays KDKA 6.45-9 am. Also Sunday, 6 pm.	19 Met. Broadcast Band		15.200	DJ8	BERLIN, GERMANY, 19.74 m., Addr. (See 15.280 mc.) 8-9 am., 4.50-10.50 pm. Also Sun. 11.10 am.-12.25 pm.	
21.530	GSJ	DAVENTRY, ENG., 13.93 m., Addr. (See 21.550 mc.) 5.45-8.50 am.	15.340	DJR	BERLIN, GERMANY, 19.56 m., Addr. Brdcast'g House, 12.05-11 am.	15.195	TAQ	ANKARA, TURKEY, 19.74 m., 5.30-7 am., 9.30-11 am., Relays 2RO irregularly Afts.
21.520	W3XAU	PHILA., PA., 13.94 m., Addr. Col. Broad. Syst., 485 Madison Ave., N. Y. C. 1-2.30 pm.	15.330	W2XAD	SCHENECTADY, N. Y., 19.56 m., Addr. General Electric Co. Relays WGY, 12.15-7 pm.	15.190	OIE	LAHTI, FINLAND, 19.75 m. Addr. (See OFD, 9.5 mc.) 1:05-4 am, 9 am.-5 pm.
21.500	W2XAD	SCHENECTADY, N. Y., 13.95 m., General Electric Co., 8 am.-12 n.			15.190	Z8W4	HONGKONG, CHINA, 19.75 m., Addr. P. O. Box 200. Irregular. 11.30 pm. to 1.15 am., 3-10 am.	


(Continued on page 728)

All Schedules Eastern Standard Time

Let's Listen In with

Joe Miller

"DX" Editor

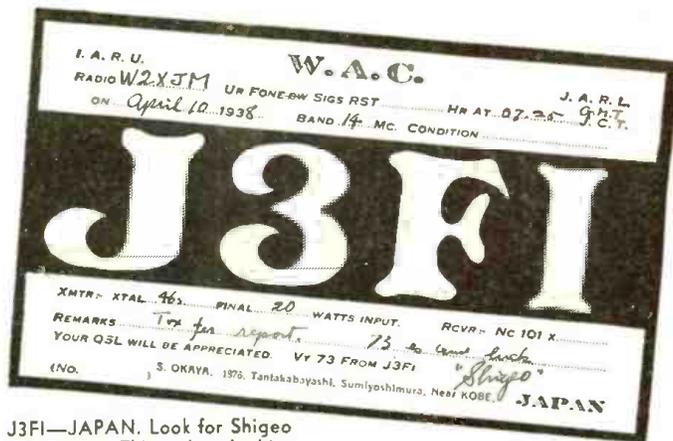

J3FI—JAPAN. Look for Shigeo this Spring. This red and white QSL is well worth earning!

● **SPRING** is here, and along with this most welcome of seasons arrives the international amateurs' DX contest, timed to take place when DX conditions for worldwide reception on the amateur bands, especially 20 meters, reach an optimum.

Our interest, and that of most of DXers, will, of course, be centered in the phone contest, which is scheduled to begin on March 17, at 7:01 p.m., E.S.T., and end on March 26 at 6:59 p.m., E.S.T. In these 9 days, it will be possible to hear many fine DX catches, as amateurs from all over the world will participate and offer all DXers a grand opportunity to add many fine DX logs to their present total. A note here for C.W. DXers and C.W. Hams is that the code section of the A.R.R.L. Contest begins on March 3rd at 7:01 p.m., E.S.T., and ends March 12th at 6:59 p.m., E.S.T.

Last year we "cleaned up" on a good deal of very fine DX, especially from Asia, using a W8JK beam directed North over the Pole to cover the eastern half of Asia, and we do hope that many of you OM's have a similar beam antenna constructed, and measured for 20 meters, as that will be the band, and we would like to have everyone ready to take the fullest possible advantage of the wealth of DX to be heard before, during and after the contest.

Further particulars, as to when to tune for best reception from each continent, etc., will be found in our *Ham Stardust* column.

Again we must mention the subject, a rather important one for us SWL's, of QSL cards, and of correct reports. This seems to be a somewhat sore topic for a number of DXers, but the necessity for some sort of a code of ethics for SWL's is becoming more apparent than ever.

There is, for one thing, entirely too much of the "I heard you, pse QSL" type of report being sent to amateurs, which tends to give them the impression that most SWL's are ignorant boys who collect cards just for the fun of it, and are not at all interested in giving the "ham" a report of some value to him, as to how well his signals came over, giving him a word-by-word report of his transmission, how good his modulation was, what stations were QRMing him, and every other detail one could ascertain of possible value to the station being reported. The amateurs appreciate such reports very much indeed, and, judg-

ing from some of our replies, it would seem that our report, being fully detailed, was considered exceptional, if only because of our pains to make it complete.

So, fellows, let's work together, and do the right thing. If you are making a report to a "ham," do your job as well as it can be done, or don't do it at all. Try to give our brother radio buffs, the amateurs, a better impression of us DXers, and your combined efforts should result in more QSL's, as there will be less amateurs "fed up" with the SWL's reports.

A word about postage. If a DXer expects a card for his report, he not only should, he must enclose a coupon with his report. Many "hams" have ceased QSLing, due to the many reports sent merely on cards, of course with no return postage. Why should an amateur spend many dollars monthly for postage to QSL SWL's when he can use that same money to purchase some much needed equipment?

Dan Malan, ZS4H, a popular amateur in South Africa, whose phone signals are well known in the States, writes us and requests us to publish his plea that SWL's enclose return postage if they wish QSL cards, adding that he's "no millionaire." Certainly, very few amateurs are! Dan has, like the grand fellow he is, been sending his cards to many SWL's who didn't send postage, when he was in no way obligated to do so, not counting the many amateur contacts he had to QSL, all this running into quite some bill.

During the past month conditions have been fair, but by March, DX should be very much better, this month commencing the spring DX peak.

INDIA

VUD4, on 15.29 mc., Delhi, is a new addition to the chain of excellent Asiatic broadcasters in India, and may be heard almost daily between 9:30-11:30 p.m., E.S.T., along with its sister station, VUD3, 15.16 mc., but with different programs on each. Reported by G. C. Gallagher, and I.D.A.

Also Masud Akhtar of New Delhi has been kind enough to send along a late copy of the "Indian Listener," an Indian radio magazine, with the latest data on the 60 meter band VU Broadcasters.

Reallocations place the stations on these new freqs.: VUC2, 4.84; VUB2, 4.88; VUM2, 4.92; and VUD2, 4.96 mc., these changes probably occurring during early December.

Regarding an item here a few months back about the failure of the Indian stations to QSL reports, which failure we personally experienced along with quite a number of our reporters (but which has evidently been since corrected), OM Masud tells us in his interesting letter that he made a personal call to the offices of All India Radio (A.I.R.) and was shown the files of reports from listeners, all of which were marked as answered, fully satisfying Masud that such a condition no longer exists.

Evidently our first reports were received before the station was fully equipped to handle reports, and

send confirmations. The Station Director assured Masud that all reports will be answered, but that listeners should send reply postage. Many thanks to you, Masud, for your FB help!

VWY2, 17.51 mc. (taken from veri) Poona, was heard during an inverted speech contact with a Rugby fone at 8:15 a.m. recently.

VUB2, 9.55 mc., Bombay, and VUD3, are reported from 10-10:30 p.m., with FB reception by Daryl Sebastian, W8.

IRAQ

The station lately reported as YIJG, this call from an English listener, is proven to have the call Y15KG, and was mistakenly heard over the air, Y15KG, on 7.20 mc., with 1 kw., is on the air daily from 7:30 a.m.-3 p.m., one hour earlier than previously reported, all this from an actual veri received from Mr. I. Hassan.

Another transmitter of 400 watts is on 6.90 mc. from 9:30 a.m. onward; closing time not given, but probably also 3 p.m. Another transmitter has been ordered, and will be used as a commercial job.

This complete plant is owned by Iraq royalty, H. R. H. Crown Prince Faisal Ghazi, and the title of the broadcasting center is "Qasr el Zehoor" Broadcasting Station, Baghdad, Iraq. Reports may be sent to this QRA, or to that of the previous one recently given (S.W.M., England).

ETHIOPIA

IABA, 9.65 mc., and known as "Stazione Di Addis Abeba," in that city, is being operated by the Italian Gov't from 11 a.m.-1 p.m. daily, rather a difficult time to log this fine African catch. (I.D.A.)

ALBANIA

ZAA, "Radio Experimental Tirana," at Tirana, is reported as being on from 12:30-2 p.m., E.S.T., on 7.4875 mc., making it rather too early to be heard well, if at all, in the U. S. Another freq., 9.9875 mc., will also be used, both of these freqs. being intended for European reception, and 15.765 mc., no schedule as yet, for America. QRA (address) ZAA, Radio Exp. Tirana, Directorate General of Posts and Telegraphs, Tirana, Albania. (I.D.A.) (S.W.M.)

PHILIPPINES

KZIB, now 9.49 mc., Manila, moved from 9.503 mc. to avoid being QRM'd by VK3ME, and is heard daily 6-9:05 a.m., with good signal. (I.D.A.) The QRA (address) is I. Beck Ind., Crystal Arcade Bldg., P.O. Box 440, Manila, P.I.

KZRM, 9.57 mc., Manila, is reported being operated by a new organization "The Far Eastern Broadcasting Co.," and owned by same, per W. G. Layton, from a recent veri. Schedule is: Mon.-Fri.: 4:30-6 p.m.; 5-9 a.m.; Sat.: 4:30-6 p.m.; 5-10 a.m.; and Sun.: 4-10 a.m. He also reports KZIB, KZGF, 5.47 mc., Manila, reported phoning KZGH, 5.44 mc., Iloilo, near 9 a.m., often, by Jack Hartley, W2.


CHINA

XGRV, reported on 11.38-11.42 mc., Chungking, the wartime capital being its location, according to a letter received by Jack Wells, W4, from H. K. Tong. Schedule is given as 1:135 a.m., when news is given in Chinese and Japanese, and 8-8:35 a.m., when it is given in English and French.

Mr. Tong, who is Chairman of the China Information Committee, P.O. Box 90, Hankow, states that XTJ, replaced by XGRV, has been moved to the interior to avoid damage from war activities. G. C. Gallagher, W6, reports XGRV.

XGRV, 15.19 mc., Chungking, is reported irregular 7-9 p.m. (I.D.A.)

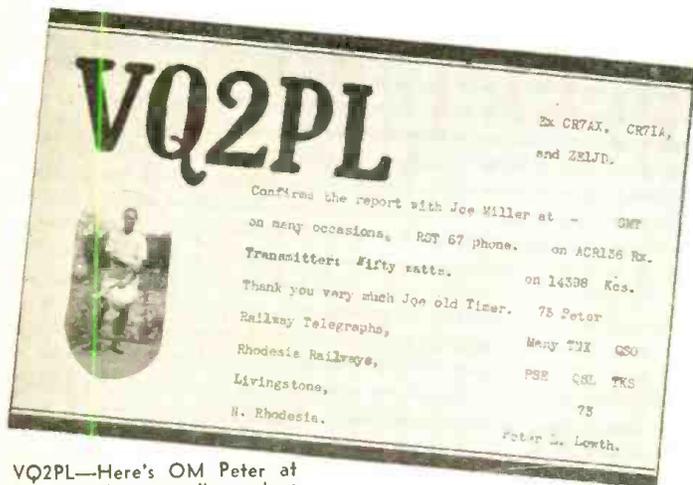XGAP, 9.56 mc., Peking, is heard 4-9 a.m., daily, and QRA is: S. Yoshimura, Director Peking Central Station, Hsi-eh-an-Chieh, Peking. (Continued on page 759)



VQ2PL—Here's OM Peter at home in this eternally verdant land.

Mc.	Call	Station	Time	Mc.	Call	Station	Time	Mc.	Call	Station	Time
15.166	LKC	OSLO, NORWAY, 19.78 m. Re-ported Suns. 10.30 am. on.		11.900	—	HANOI, FRENCH INDO-CHINA. 25.21 m. "Radio Hanoi", Addr. Radio Club de l'Indochine. 3.45-4.15 am., 7-9.30 am., 150 watts.		11.740	SP25	WARSAW, POLAND, 25.55 m., 6-9 pm.	
15.160	XEWV	MEXICO CITY, MEXICO, 19.79 m., 12 n.-12 m., irregular.		11.900	XEWI	MEXICO CITY, MEXICO, 25.21 m., Addr. P. O. Box 2874. Mon., Wed., Fri. 3-4 pm., 9 pm.-12 m. Tues. and Thur. 7.30 pm.-12 m., Sat. 9 pm.-12 m., Sun. 12.30-2 pm.		11.740	COCX	HAVANA, CUBA, 25.55 m. P. O. Box 32. Daily 8 am.-1 am. Sun. 8 am.-12 m. Relays CMX.	
15.160	VUD3	DELHI, INDIA, 19.79 m., Addr. All India Radio. 1.30-3.30 am., 9.30-11.30 pm.		11.885	TPA3	PARIS, FRANCE, 25.24 m., Addr. (See 15.245 mc.) 2-5 am., 11.15 pm.-6 pm.		11.740	HVJ	VATICAN CITY, 25.55 m. Testing irregular. Wed. 2.30-3 pm.	
15.155	SM5SX	STOCKHOLM, SWEDEN, 19.79 m., Daily 11 am.-5 pm., Sun. 9 am.-5 pm.		11.885	TPB7	PARIS, FRANCE, 25.24 m. (See 15.245 mc.) 9.30 pm.-mid., 12.15-2 am. Irregular.		11.730	PHI	HUIZEN, HOLLAND, 25.57 m., Addr. N. V. Philips' Radio. Daily 6.15-6.45 pm. Sat. 7.15-7.45 pm.	
15.150	YDC	BANDOENG, JAVA, 19.8 m., Addr. N. I. R. O. M. 6-7.30 pm., 10.30 pm.-2 am., Sat. 7.30 pm.-2 am., daily 4.30-10.30 am.		11.880	VLR3	MELBOURNE, AUST., 25.25 m., 3.30-7.15 pm., 9 pm.-3 am. week-days. Suns. mid.-3 am.		11.730	WIXAL	BOSTON, MASS., 25.57 m., Addr. World-Wide 8'cast'g Foundation, University Club. Daily exc. Sat. and Sun. 9-11 pm.	
15.140	GSF	DAVENTRY, ENG., 19.82 m., Addr. (See 17.79 mc.) 3-5.15 am., 5.45-6.50 am., 9 am.-noon.		11.870	W8XK	PITTSBURGH, PA., 25.26 m., Addr. (See 21.540 mc.) 1-11 pm.		11.730	LKQ	OSLO, NORWAY, 25.58 m. 4.30-9 am., Suns. 2.30-9 am.	
15.130	TPB6	PARIS, FRANCE, 19.83 m., Addr. "Paris Mondial," 98 Bis Blvd. Haussmann, 7-9.15 pm.		11.865	—	BERNE, SWITZERLAND, 25.28 m. Irreg. 8-9 pm. to No. Amer.		11.720	CJRX	WINNIPEG, CANADA, 25.6 m., Addr. James Richardson & Sons, Ltd. Daily 6 pm.-12 m., Sat. 6 pm.-Sun. 4 am.	
15.130	WIXAL	BOSTON, MASS., 19.83 m., Addr. World-Wide 8'cast'g Foundation, University Club. 10-11 am., Mon.-Fri. Sun. 10 am.-1 pm.		11.860	GSE	DAVENTRY, ENG., 25.30 m., Addr. (See 11.75 mc.) 3-5.15, 5.45 am.-10.30 am. Sun. 1-1.30 pm.		11.720	ZPI4	VILLARICA, PARAGUAY, 25.60 m. 7.07-9.07 pm.	
15.120	SP19	WARSAW, POLAND, 19.84 m., 6-9 pm.		11.855	DJP	BERLIN, GERMANY, 25.31 m., Addr. (See 15.280 mc.) Irregular. 7.15-10.50 pm. to No. Amer.		11.718	CR78H	LAURENCO MARQUES, PORTU-GUESE E. AFRICA, 25.6 m. Daily 12.05-1, 4.30-6.30, 9.30-11 am., 12.05-4 pm., Sun. 5-7 am., 10 am.-2 pm.	
15.120	HVJ	VATICAN CITY, 19.83 m., 10.30-10.45 am., Tues only. Suns. 1-1.30 pm.		11.850	C81185	SANTIAGO, CHILE, 25.32 m. Sat. 6-11 pm. and irreg.		11.715	TPA4	PARIS, FRANCE, 25.61 m., (See 15.245 mc.) 7-9.15 pm., 9.30 pm.-12 m. to No. America.	
15.110	DJL	BERLIN, GERMANY, 19.85 m., Addr. (See 15.280 mc.) 12.05-2, 8-9 am., 10.35 am.-4.25 pm., Sun., also 6-8 am.		11.850	OAX2A	TRUJILLO, PERU, 25.32 m. Testing on this freq. (See 12.200).		11.710	YSM	SAN SALVADOR, EL SALVADOR, 25.63 m., Addr. (See 7.894 mc.) 1-2.30 pm.	
15.080	RKI	MOSCOW, U.S.S.R., 19.87 m. Works Tashkent near 7 am. Broad-casts Sun. 12.15-2.30 pm. Daily 7-9.15 pm.		11.840	KZRM	MANILA, P. I., 25.35 m. Addr. Erlanger & Gallinger, Box 283. 9 pm.-10 am. Irregular.		11.710	—	SAIGON, FRENCH INDO-CHINA. 25.62 m., Addr. Boy-Landry, 17 Place A. Foray. 7.30-9.15 am.	
End of Broadcast Band											
14.960	—	MOSCOW U.S.S.R., 20.25 m., 1st of month, 6 pm. Dutch program.		11.840	OLR4A	PRAGUE, CZECHOSLOVAKIA, 25.34 m., Addr. Czech Shortwave Sta., Praha XII, Fochova 16. Daily 1.55-4.30 pm. Mon. to Fri. 7.55-10.55 pm., Sun. 5.55-8.55 pm.		11.705	SBP	MOTALA, SWEDEN, 25.63 m., 1.20-2.05, 6-9 am., 11 am.-1 pm., Sat. 1.20-2 am., 6 am.-1.30 pm., Sun. 3 am.-1.30 pm. Wed. and Sat. 8-9 pm.	
14.940	PSE	RIO DE JANEIRO, BRAZIL, 20.08 m., Broadcasts Wed. 3.45-4.15 pm.		11.830	W9XAA	CHICAGO, ILL., 25.36 m., Addr. Chicago Federation of Labor. Irregular 7 am.-6 pm.		11.700	HP5A	PANAMA CITY, PAN., 25.65 m. Addr. Radio Teatro, Apartado 954. 10 am.-1 pm., 5-10 pm. Sun. 6-10 pm.	
14.920	KQH	KAHUKU, HAWAII, 20.11 m. Sats. 1-1.30 am., 11-11.30 pm.		11.830	W2XE	NEW YORK CITY, 25.36 m., Addr. Col. Broad. System, 485 Madison Av., N.Y.C. Mon.-Fri. 3.30-6, 6.30-10 pm. Sat., Sun. 3-6, 6.30-11 pm.		11.700	C81170	SANTIAGO, CHILE, 25.65 m. Addr. P.O. Box 706. Relays C889 10 am.-2 pm., 3.30-11 pm.	
14.600	JVH	NAZAKI, JAPAN, 20.55 m. Broad-casts irregularly 5-11.30 pm. Works Europe 4-8 am.		11.826	XEBR	HERMOSILLA, SON., MEX., 25.37 m., Addr. Box 68. Relays XEBH. 9.30-11 am., 1-4 pm., 9 pm.-12 m. (See 11.75 mc.) Irregular.		End of Broadcast Band			
14.535	HBJ	GENEVA, SWITZERLAND, 20.64 m., Addr. Radio Nations. Broadcasts Sun. 10.45-11.30 am., Mon. 4-4.15 am.		11.820	GSN	DAVENTRY, ENG., 25.38 m., Addr. (See 11.75 mc.) Irregular.		11.676	IQY	ROME, ITALY, 25.7 m. Relays 2RO 1.35-2.25, 6-9 pm.	
14.440	—	RADIO MALAGA, SPAIN, 20.78 m. Relays Salamanca 5.40-8.40 am. Sometimes 2-4 pm.		11.810	2RO4	ROME, ITALY, 25.4 m., Addr. E.I.A.R., Via Montello 5. Daily 4.40-8.45 am., 10 am.-12 n.		11.535	SPD	WARSAW, POLAND, 26.01 m., Addr. 5 Mazowiecká St. 6-9 pm.	
14.430	HC1JB	QUITO, ECUADOR, 20.79 m. 10-10.30 pm. except Mon. 9-9.30 pm. and irreg.		11.805	OZG	SKANLEBAK, DENMARK, 25.41 m. Addr. Statsradion. Irreg.		11.402	HBO	GENEVA, SWITZERLAND, 26.31 m., Addr. Radio Nations. Sun. 7-7.45 pm., Mon. 1-1.15 am., 7-8.30 pm.	
14.166	PIIJ	DORDRECHT, HOLLAND, 21.15 m., Addr. (See 7.088 mc.) Sat. 12 n.-12.30 pm.		11.801	DJZ	BERLIN, GERMANY, 25.42 m. 4.50-10.50 pm.		11.040	CSW2	LISBON, PORTUGAL, 27.17 m., Addr. Nat. Broad. Sta. 9.30 am.-Noon. 2-5.30 pm.	
13.997	EA9AH	TETUAN, SPANISH MOROCCO, 21.43 m. Apartado 124. 5.15-6.15 pm., 6.30-7.30 pm., 9-10 pm. Re-lays Salamanca from 5.40 pm.		11.800	COGF	MATANZAS, CUBA, 25.42 m., Addr. Gen. Befancourt 51. Re-lays CMGF. 2-3, 4-5, 6 pm.-Mid.		11.000	PLP	BANDOENG, JAVA, 27.27 m. Re-lays YDB. 6-7.30 pm., 10.30 pm.-2 am., 4.30-10.30 or 11 am. Sat. until 11.30 am.	
13.635	SPW	WARSAW, POLAND, 22 m. Daily 6-8 pm. Sat. & Sun. 6-9 pm.		11.800	JZJ	TOKYO, JAPAN, 25.42 m., Addr. Broadcasting Co. of Japan, Overseas Division. 7-7.30, 8-9.30 am., 2.30-4, 4.30-5.30, 8-8.30 pm., 12.30-1.30 am.		10.950	—	TANANARIVE, MADAGASCAR, 27.40 m., Addr. (See 9.38 mc.) 12.30-4.5, 10-11 am., 2.30-4 am., exc. Sun.	
12.862	W9XDH	ELGIN, ILL., 23.32 m. Press Wire-less. Tests 2-5 pm.		11.795	DJO	BERLIN, GERMANY, 25.42 m. 4.50-Addr. (See 15.280 mc.) 11.30 am.-4.25 pm., 4.50-10.50 pm. Ir-regular.		10.670	CEC	SANTIAGO, CHILE, 28.12 m. Irregular.	
12.486	HIN	TRUJILLO CITY, DOM. REP., 24.03 m. 7.10-10.10 pm.		11.790	WIXAL	BOSTON, MASS., 25.45 m., Addr. (See 15.250 mc.) Daily 4.55-6.30 pm., Tues., Thur., 4.40-6.30 pm., Sat. 1.45-6 pm., Sun. 5-6.30 pm.		10.660	JVN	NAZAKI, JAPAN, 28.14 m. Broad-casts daily 1.50-7.40 am. Works Europe irregularly at other times.	
12.460	HC2JB	QUITO, ECUADOR, 24.08 m. Daily exc. Mon. 8-10.30 pm.		11.780	HP5G	PANAMA CITY, PAN., 25.47 m., Addr. Box 1121. 6-10 pm.		10.600	ZIK2	BELIZE, BRIT. HONDURAS, 28.30 m., Tue., Thurs., Sat. 1.30-2, 8.30-9 pm.	
12.235	TFJ	REYKJAVIK, ICELAND, 24.52 m. Works Europe mornings. Broad-casts Sun. 1.40-2.30 pm.		11.780	OFE	LAHTI, FINLAND, 25.47 m. Addr. (See OFE, 9.5 mc.) 1.05-3 am., 5-6.20, 10 am.-12.30 pm.		10.535	JIB	TAIHOKU, TAIWAN, 28.48 m. Works Japan around 6.25 am. Broadcasts, relaying JFKF 9.05-10 am., 1-2.30 am. Sun. to 10.15 am.	
12.200	—	TRUJILLO, PERU, 25 m., "Rancho Grande," Address Hacienda Chiclin. Irregular.		11.770	DJD	BERLIN, GERMANY, 25.49 m., Addr. (See 15.280 mc.) 11.30 am.-4.25 pm., 4.50-11 pm.		10.400	YSP	SAN SALVADOR, EL SALVADOR, 28.85 m., 1-3, 6.30-11 pm.	
12.000	RNE	MOSCOW, U.S.S.R., 24.88 m. Daily 6-7 am., 12 n.-2 pm., 3-6, 10.15-11 pm., also Tues., Thurs. 8.30-9 pm., also Sun. 6-10.30 am., 12 n.-5 pm., 6-6.30, 8.30-9, 10.15-11 pm.		11.760	TGWA	GUATEMALA CITY, GUAT., 25.51 m. (See 17.8 mc.) Irregular 10-11.30 pm. Sun. 6-11.30 pm., ir-regular.		10.350	LSX	BUENOS AIRES, ARG., 28.98 m., Addr. Transradio Internacional. Tests irregularly.	
11.990	CB1180	SANTIAGO, CHILE, 25.02 m. 7-11 pm.		11.760	XETA	MONTEREY, MEX. 25.51 m., Addr. Box 203. Relays XET. n.-3.30 pm. and evenings.		10.330	ORK	RUYSELEDE, BELGIUM, 29.04 m. Broadcasts 12.30-2 pm. Works OPM 1-3 am., 3-5 pm.	
11.970	H12X	CIUDAD TRUJILLO, D. R., 25.07 m., Addr. La Voz de Hispaniola. Relays H1X Tue. and Fri. 8.10-10.10 pm.		11.760	OLR4B	PRAGUE, CZECHOSLOVAKIA, 25.51 m., Addr. (See 11.840 mc.) Irregular.		10.290	TIEMT	SAN JOSE, COSTA RICA, 29.15 m., 4.30-8 pm.	
25 Met. Broadcast Band											
11.935	T12XD	SAN JOSE, COSTA RICA, 25.12 m. La Voz del Pilot. Apartado 1729. 10 am.-n., 4-10 pm.		11.750	GSD	DAVENTRY, ENG., 25.53 m., Addr. B.B.C., London. 3-5.15 am., 9 am.-noon, 12.30-6 pm., 6.20-8.30 pm., 9.20-11.20 pm.		10.290	DZC	ZEESEN, GERMANY, 29.16 m., Addr. (See 15.360 mc.) Irregular.	
11.910	CD1190	VALDIVIA, CHILE, 25.2 m., P. O. Box 642. Relays C869 10 am.-1 pm., 7-10 pm.									

(Continued on page 730)

Tenth SILVER TROPHY Award

For Best HAM Station Photo of the Month

Awarded to *L. W. "Bud" Preston, W9VXL*
Savanna, Ill.

● HEREWITH is a photo of myself and station for your contest. My transmitter is a Collins 301FXB with some alterations of my own. The receiver is a Patterson PR15.

I built a new R.4 unit and a new power supply for the final stage. I run either 250 or 400 watts phone and prefer the ten meter band. The tube lineup in the new R.F. unit is a 42 oscillator, 807 doubler, 809 buffer and a T125 final.

The speech lineup is a Shure 701A mike into the standard Collins 7C speech amplifier, driving a pair of ZB120's Class "B." The remote control box on the desk contains the filament, plate, stand-by and push-to-talk switches. The switches on the transmitter panel provide a means of applying plate voltage to each stage individually when tuning up. The antenna used for ten is a rotatable Johnson Q and reflector. The control wheel may be seen on the left-hand corner of the desk. An antenna change-over relay shifts the beam from the transmitter to the receiver, which is a PR15.

The room measures eleven by twelve feet and is built into one end of the attic. It is constructed of heavy celotex and has double walls to provide a dead air space. The floor is covered with an insulating material under the carpet. The room is perfectly sound-proof and dx contacts may be held at any time of day or night.

Thirty-nine countries have been "worked" in the six months I have been on the ten meter band.

In closing, let me congratulate and thank you for a very fine magazine. I have every issue from 1934 and refer to them many times.

Sincerely yours,

L. W. "BUD" PRESTON, W9VXL,
Savanna, Ill.

This beautiful silver trophy stands 11 $\frac{3}{4}$ " high and one is awarded monthly by RADIO & TELEVISION magazine for the best photo of a Ham station. The silver statue stands on a handsome bakelite base on which is a silver plate. The name of the winner will be engraved on this plate before the trophy is sent to him.

Silver Trophy Award

Note These Important Rules

The photos must be sharp and clear and preferably not less than 5" x 7".

The pictures will be judged for the general layout of the station, the quality of workmanship exhibited, and the appearance of the photograph itself. The judges will also consider neatness as an important point.

When you submit the photograph of your Ham station, send along a brief description not longer than 300 words, describing the general line-up of



the apparatus employed, the size, type and number of tubes, the type of circuit used, name of commercial transmitter—if not home-made, watts rating of the station, whether for c.w. or phone or both, etc., also name of receiver.


State briefly the number of continents worked, the total number of stations logged or contacted, and any other features regarding the station which you think will be of general interest to the reader. Mention the type of aerial system used, especially any unique or new features about it, and which type of aerial you use for transmitting and receiving; also what type of break-in relay system, if any, is used.

Important—Don't forget to send along a good photograph of yourself, if your likeness does not already appear in the picture!

Note that you do not have to be a reader of RADIO & TELEVISION in order to enter the contest. Pack all photographs carefully and the description had best be mailed in the same package with the photos. The Editors will not be responsible for photos lost in transit.

Do not send small, foggy-looking photos because they cannot be reproduced properly in the magazine. If the picture you have or may take of your station is not thoroughly sharp and clear and at least 5" x 7", it would be best to have a commercial photographer take a picture of your station. If you cannot do this, you most probably have a friend who owns a good camera and who can arrange to take the photograph. You are not limited to one picture, but may submit as many different views as you like.

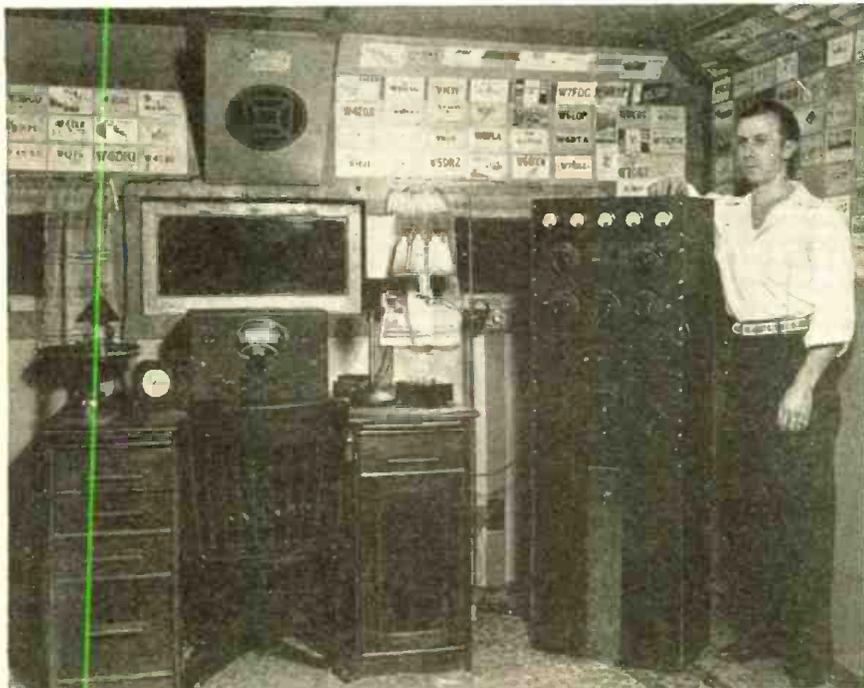Address all photos and station descriptions to Editor, Ham Station Trophy Contest, c/o RADIO & TELEVISION, 99 Hudson Street, New York, N. Y.



Prize-Winning "Ham" Station this month—L. W. Preston, Savanna, Ill.

Mc.	Call	
10.100	—	DEUTSCHE FREIHEITS SENDER, 29.70 m., loc. in Germany, under-cover. 4-5 pm.
10.042	DZB	ZEESEN, GERMANY, 29.87 m., Addr. Reichspostzenstralmf. Irregular.
9.995	COBC	HAVANA, CUBA, 30.02 m., Addr. P. O. Box 132. Relays CMBC 6.55 am.-1 am.
9.920	JDY	DAIREN, MANCHUKUO, 30.24 m. Relays JQAK daily 7-8 am. Works Tokyo occasionally in early am.
9.892	CPI	SUCRE, BOLIVIA, 30.33 m., 11 am.-n., 7-9 pm.
9.860	EAQ	MADRID, SPAIN, 30.43 m., Addr. Post Office Box 951. 7.30-8, 8.40-9 pm.
9.830	IRF	ROME, ITALY, 30.52 m. Works Egypt afternoons. Relays ZRO, 6-9 pm.
9.805	COCM	HAVANA, CUBA, 30.60 m. Addr. Transradio Columbia, P. O. Box 33. 8-1 am. Relays CMCM.
9.760	—	SAIGON, INDO-CHINA, 30.72 m., Addr. 17, Place A. Foray. "Radio Boy-Landry." Heard 6-9.15 am.
9.753	ZRD	DURBAN, SOUTH AFRICA, 30.75 m. Addr. S. A. Broadcasting Corp., P. O. Box 4559, Johannesburg. Daily exc. Sat. 11.45 pm.-12.50 am. Daily exc. Sun. 3.30-7.30, 9-11.45 am., Sun. 5.30-7, 9-11.30 am., also 4-5 am. on 3rd Sun. of month.
9.735	CSW7	LISBON, PORTUGAL, 30.82 m. Addr. Nat. Broad. Sta. n.-2 pm., 6-9 pm. for No. Amer.
9.708	COCO	HAVANA, CUBA, 30.90 m. Addr. 25 No. 445, Vedado, Havana, 7-1 am. Sun. 6.55 am.-1 am.

31 Met. Broadcast Band

9.705	—	FORT DE FRANCE, MARTINIQUE, 30.92 m., Addr. P. O. Box 136.
9.690	T14NRH	HEREDIA, COSTA RICA, 30.94 m., Addr. Amando C. Marin, Apartado 40. Sun. 7-9 am., Tues., Thurs., Sat. 9-10 pm.
9.690	LRA	BUENOS AIRES, ARG., 30.94 m., 6-9 pm.
9.685	TGWA	GUATEMALA CITY, GUAT., 30.96 m. Daily 10-11.30 pm.; Sun. 7-10.45 pm.
9.680	ZHP	SINGAPORE, MALAYA, 30.98 m. Sun. 5.40-9.40 am., Wed. 12.40-1.40 am., Mon.-Fri. 4.40-9.40 am., Sat. 12.25-1.40 am., 4.40-9.40 am., 10.40 pm.-1.10 am. (Sun.)
9.675	DJX	BERLIN, GERMANY, 31.01 m., Addr. (DJD), 11.77 mc.) 10.35 am.-4.25 pm.
9.670	W3XAL	BOUND BROOK, N. J., 31.03 m. Addr. NBC, N. Y. C. 5 pm.-1 am.
9.665	—	ROME, ITALY, 31.04 m. Relays ZRO 12 n.-6, 7.30-9 pm.
9.660	LRX	BUENOS AIRES, ARG., 31.06 m., Addr. El Mundo. Relays LRI, 6-6.45 am., 9.15 am.-10.05 pm.
9.650	W2XE	NEW YORK CITY, 31.09 m. (See 21.570 mc. for addr.) 10.30-11.30 am. exc. Sat. and Sun.
9.650	CS2WA	LISBON, PORTUGAL, 31.09 m., Addr. Radio Colonial. Tues., Thurs. and Sat. 4-7 pm.
9.645	HH3W	PORT-AU-PRINCE, HAITI, 31.1 m., Addr. P. O. Box A117. 1-2, 7-9 pm.
9.640	CXA8	COLONIA, URUGUAY, 31.12 m., Addr. Belgrano 1841, Buenos Aires, Argentina. Relays LR3, Buenos Aires 7 am.-m., Sat. to 2.15 am.
9.636	JFO	TAIHOKU, TAIWAN, 31.13 m. Relays JFAK irreg. 4-10.30 am.
9.635	ZRO	ROME, ITALY, 31.13 m., Addr. (See 11.810 mc.) 12.05-9 pm.
9.630	HJ7ABD	BUARAMANGA, COL., 31.14 m. 5.45-6.30, 11.30 am.-1 pm., 6-11 pm.
9.618	HJ1ABP	CARTAGENA, COL., 31.20 m., Addr. P. O. Box 37. Daily 9 am.-1.30 pm., 4.30-10.15 pm., Sun. 4.30-9 pm.
9.615	ZRK	KLIPHEVAL, SOUTH AFRICA, 31.2 m., Addr. P. O. Box 4559, Johannesburg. Daily. exc. Sat. 11.45 pm.-12.50 am. Daily exc. Sun. 3.20-7.20, 9-11.45 am., Sun. 3.30-4.30 or 4-5, 5.30-7, 9-11.45 am.

Mc.	Call	
9.607	HP5J	PANAMA CITY, PANAMA, 31.23 m. Addr. Apartado 867. 12 n. to 1.30 pm., 6-10.30 pm.
9.600	RAN	MOSCOW, U.S.S.R., 31.25 m. Daily exc. Sun. 6-10 pm. Sun. 6-7, 9.15-10 pm.
9.595	H8L	GENEVA, SWITZERLAND, 31.27 m., Addr. Radio Nations. Irregular.
9.590	VUD2	DELHI, INDIA, 31.28 m. Addr. All India Radio, 1.30-3.30 am., 7.30 am.-12.30 pm., 8.30-10.30 pm.
9.590	PCJ	HUIZEN, HOLLAND, 31.28 m., Addr. (See 15.220 mc.) Sun. 2-3, 7-9.25 pm. Tues. 1.45-3.40, 7.15-8.45, 9-10.30 pm., Wed. 7.15-8.30 pm., Fri. 8-9 pm.
9.590	VK6ME	PERTH, W. AUSTRALIA, 31.28 m., Addr. Amalgamated Wireless of Australasia, Ltd. 6-9 am. exc. Sun.
9.590	VK2ME	SYDNEY, AUSTRALIA, 31.28 m., Addr. Amalgamated Wireless of Australasia, Ltd., 47 York St., Sun. 1-3 am.; 5-11 am.
9.590	W3XAU	PHILADELPHIA, PA., 31.28 m. (Addr. See 21.52 mc.) Mon. and Thurs. 7.30-11.30 pm. Sat. 7.30-10.45 pm.
9.580	GSC	DAVENTRY, ENGLAND, 31.32 m., Addr. 8, 8, C., Portland Pl., London, W. 1, 12.20-1.15, 4.15-6, 6.20-8.30, 9.20-11.25 pm.
9.580	VLR	MELBOURNE, AUSTRALIA, 31.32 m. Addr. Box 1686, G. P. O. Daily 3.30-8.30 am. (Sat. fill 9 am.) Sun. 12.01-7.30 am. Also daily exc. Sat. 9.25 pm.-2 or 2.15 am. Sat. 5-10.30 pm.
9.570	KZRM	MANILA, P. I., 31.35 m., Addr. Erlanger & Galinger, Box 283. Sun. 3-10 am. Daily exc. Sat. 4.30-7 pm., 11.15 pm.-12.15 am. Daily exc. Sun. 4-10 am.
9.570	W1XK	BOSTON, MASS., 31.35 m., Addr. Westinghouse Electric & Mfg. Co. 7 am. to 1 am. Sun. 8 am.-1 am.
9.560	XGAP	PEKING, CHINA, 31.38 m., 9 am.-2 pm.
9.560	DJA	BERLIN, GERMANY, 31.38 m., Addr. Broadcasting House, 12.05-11 am., 4.50-10.50 pm.
9.550	HVJ	VATICAN CITY, 31.41 m., Sun. 5-5.30 am.
9.550	TPBII	PARIS, FRANCE, 31.41 m. Addr. (See 15.245 mc.) 2-5 am., 11.15 am.-6 pm.
9.550	W2XAD	SCHENECTADY, N. Y., 31.41 m., General Electric Co., 7:15-10 pm. to So. Amer.
9.550	OLR3A	PRAGUE, CZECHOSLOVAKIA, 31.41 m. (See 11.840 mc.) Mon. 4.40-5.10 pm.
9.550	XEFT	VERA CRUZ, MEX., 31.41 m. 10.30 am.-4.30 pm., 10.30 pm.-12.30 am.
9.550	YDB	SOERABAJA, JAVA, 31.41 m., Addr. N.I.R.O.M. Daily exc. Sat. 6-7.30 pm., 4.30 to 10.30 am. Sat. 4.30-11.30 am.
9.550	VUB2	BOMBAY, INDIA, 31.41 m., Addr. All India Radio. 9.30-10.30 pm., 1-3.30 am.
9.540	DJN	BERLIN, GERMANY, 31.45 m., Addr. (See 9.560 mc.) 12.05-11 am. 4.50-10.50 pm. to So. Amer.
9.540	HJ5ABD	CALI, COLOMBIA, 31.45 m., Addr. La Voz de Valle. 12 n.-1.30 pm., 5.10-9.40 pm.
9.538	VPD2	SUVA, FIJI ISLANDS, 31.46 m., Addr. Amalgamated Wireless of Australasia, Ltd. 5.30-7 am., exc. Sun.
9.535	JZI	TOKYO, JAPAN, 31.46 m., Addr. (See 11.800 JZJ) 2.30-4, 4.30-5.30 pm. 8-9.30 am.
9.535	—	BERNE, SWITZERLAND, 31.46 m., 1-2 pm. exc. Mon. and Tues.
9.530	W2XAF	SCHENECTADY, N. Y., 31.48 m., Addr. General Electric Co. 4 pm.-12 m. Sat. 1 pm.-12 m.
9.530	VUC2	CALCUTTA, INDIA, 31.48 m. Addr. All India Radio. 2.06-4.06 am.
9.526	XEDQ	GUADALAJARA, GAL., MEXICO, 31.49 m., n.-4.30 pm., 8-11.30 pm.
9.526	ZBW3	HONGKONG, CHINA, 31.49 m., Addr. P. O. Box 200. 11.30 pm. to 1 am., 3-10 am.
9.525	LKC	JELOY, NORWAY, 31.49 m., 4.30-10.30 am., Sun. 2.30-10.30 am.
9.523	ZRH	ROBERTS HEIGHTS, S. AFRICA, 31.5 m., Addr. (See ZRK, 9.608 mc.) Daily exc. Sun. 5-7.30 am.; Sun. 5.30-7 am.

Mc.	Call	
9.520	OZF	SKAMLEBOAEK, DENMARK, 31.51 m., Addr. Statsradiofonien, Heibergsgade 7, Copenhagen, 8-9.30, 9.30-11 pm. to No. Amer.
9.520	YSH	SAN SALVADOR, EL SALVADOR, 31.51 m., Addr. (See 7.894 mc.) Irregular 6-10 pm.
9.510	GSB	DAVENTRY, ENGLAND, 31.55 m., Addr. (See 9.580 mc.—GSC) 10.30 am.-12 n., 1.30-4, 4.15-6, 6.20-8.30, 9.20-11.25 pm.
9.510	HJU	BUENAVENTURA, COLOMBIA, 31.55 m., Addr. National Railways. Mon., Wed. and Fri. 8-11 pm.
9.510	H56PJ	BANGKOK, SIAM, 31.55 m. Thursday, 8-10 am.
9.510	—	HANOI, FRENCH INDO-CHINA, 31.55 m. "Radio Hanoi" Addr. Radio Club de L'Indochine. 12 m.-2 am., 6-10 am. 15 watts.
9.503	KZ18	MANILA, PHIL. ISL., 31.57 m., 7-9.05 am.
9.503	XEWV	MEXICO CITY, MEX., 31.57 m. Addr. Apart. 2516. Relays XEW. 9 am.-12.30 am.
9.500	VK3ME	MELBOURNE, AUSTRALIA, 31.58 m., Addr. Amalgamated Wireless of Australasia, 167 Queen St. Daily except Sun. 4-7 am.
9.500	OFD	LAHTI, FINLAND, 31.58 m., Addr. Finnish Brct. Co., Helsinki. 12.15-5 pm.
9.490	OAX5C	ICA, PERU, 31.61 m., Radio Universal, 8-11.30 pm.
9.488	EAR	MADRID, SPAIN, 31.6 m., Addr. (See 9.860 mc.) 7.30-8.30 pm. Mon., Tues., Thurs., Sat. at 9.30 pm. also.

End of Broadcast Band

9.465	TAP	ANKARA, TURKEY, 31.70 m., 1.20-5 pm. Irreg.
9.445	HCODA	GUAYAQUIL, ECUADOR, 31.77 m., 8.15-10.15 pm., exc. Sun.
9.437	COCH	HAVANA, CUBA, 31.8 m., Addr. 2 B St., Vedado. 8 am.-9.30 pm. Sun. 8 am.-12 m.
9.380	—	TANANARIVE, MADAGASCAR, 31.96 m. Addr. Le Directeur des PTT. Radio Tananarive, Administration PTT. 12.30-12.45, 10-11 am., 2.30-4 am., exc. Sun.
9.370	XOY	CHENGTO, CHINA, 32.02 m., 9.45-10.30 am.
9.355	HC1ETC	QUITO, ECUADOR, 32.05 m., Addr. Teatro Bolivar, Thurs. until 9.30 pm. 8-11 pm. Sats.
9.350	COCD	HAVANA, CUBA, 32.08 m., Addr. Box 2294. Relays CMCD 10 a.m.-11.30 pm. Sun. 10 am.-9 pm.
9.345	H8L	GENEVA, SWITZERLAND, 32.11 m., Addr. Radio Nations. Sun. 8-8.45 am., Mon. 6.45-8.30 pm.
9.340	OAX4J	LIMA, PERU, 32.12 m., Addr. Box 1166, "Radio Universal." 12 n.-3 pm., 5 pm.-1 am.
9.300	XGX	SHANGHAI, CHINA, 32.26 m., 8-9.05 am. Varies between 9.180-9.300.
9.300	HIG	CIUDAD TRUJILLO, D. R., 32.28 m. 7.10-9.40 am., 11.40 am.-2.10 pm., 3.40-9.40 pm.
9.200	COBX	HAVANA, CUBA, 32.59 m., Addr. San Miguel 194, Alfors. Relays CM8X 7 am.-12 m.
9.165	HC2CW	GUAYAQUIL, ECUADOR, 32.74 m., 7-11.30 pm., Sun. 3.30-6 pm.
9.125	HAT4	BUDAPEST, HUNGARY, 32.88 m., Addr. "Radiolabor." Gyali-ut, 22. Daily 7-8 pm., Sat., 6-7 pm.
9.100	COCA	HAVANA, CUBA, 32.95 m., Addr. Galiano No. 102. Relays CMCA 9 am.-12 m.
9.091	PJC2	CURACAO, D. W. INDIES, 33 m., 6.36-8.36 pm., Sun. 10.36 am.-12.36 pm.
9.030	COBZ	HAVANA, CUBA, 33.32 m., Radio Salas Addr. P. O. Box 866. 7.45 am.-1.15 am. Sun. 7.45 am.-12 m. Relays CM8Z.
8.965	COKG	SANTIAGO, CUBA, 33.44 m. Addr. Box 137, 9-10 am., 11.30 am.-1.30 pm., 3-4.30, 5-6, 10-11 pm., 12 m.-2 am.
8.841	HCJB	QUITO, ECUADOR, 33.5 m., 7-8.30 am., 11.45 am.-2.30 pm., 5-10 pm., except Mon. Sun. 12 n.-1.30 pm., 5.30-10 pm.

(Continued on page 732)

Antenna Systems for HAMS

Herman Yellin, W2AJL

1. Half-Wave Hertz Single-wire Untuned Feeder

● IT IS generally realized that a good antenna requires much lower transmitter power than a poor antenna for equal effectiveness; effectiveness being measured in signal strength at a distant point. Therefore, a series of articles has been prepared, of which the following is the first, describing amateur antennas and containing constructional data and tuning hints.

One of the simplest antennas is the half-wave Hertz with a single wire untuned feeder. For greatest efficiency, the antenna should be used on only one amateur band and should be cut for a half wavelength. If operation is desired on only one frequency, the antenna should be cut for that frequency, whereas if operation is desired over the entire band, the antenna should be cut for the center of that band. The following formula will determine the antenna length:—

$$\text{LENGTH (feet)} = \frac{468,000}{\text{frequency (KC.)}}$$




All untuned transmission lines or feeders have a definite surge impedance determined by the feeder's mechanical characteristics. If the feeder is terminated at the antenna in an impedance equal to its surge impedance, there will be no reflections from the antenna and no standing waves along the line to cause radiation from the line. A single wire line has an impedance of between 500 and 600 ohms. The impedance of a half-wave Hertz antenna varies from about 70 ohms at its center to about 2000 ohms at its extremities. At a distance from the center equal to 1/7 the length of the antenna, this antenna has a 500-600 ohm impedance, and so if the single wire feeder is coupled to the antenna at this point, no

standing waves will occur. For best results, a little experimenting should be done by varying the position of the feeder tap. The correct position will be indicated by a constant value of R.F. current along the line which may be any length up to several hundred feet. An R.F. ammeter can be placed at several points along the line, or several neon bulbs placed along the line, and the antenna tap adjusted until the current is the same at all points along the line. When tapped at the correct point, there will be minimum or no detuning of the final amplifier tank when the feeder is clipped thereon, and this is a simple method of adjustment. On long lines there will be a slight but steady diminution of current. The feeder should be at right-angles to the antenna for a distance equal to about 1/3 the length of the antenna to prevent interaction between antenna and feeder.

Coupling the feeder to the transmitter can be simply accomplished by clipping the feeder onto the final plate coil, starting at the point of minimum R.F. potential (ground) and going up the coil until the tube draws the desired plate current. If direct current is flowing through the coil a fixed condenser of .001 mf. or more should be placed in series with the feeder to keep D.C. out of the antenna. Otherwise, if the antenna were accidentally grounded, the power supply would be shorted. Also unfortunate accidents may result if some unsuspecting neighbor should come in contact with the antenna.

A more desirable method of coupling, resulting in elimination of any harmonics, is shown in Fig. 1b. The LC circuit should tune to the transmitter frequency while the feeder is adjusted on the coil in the same manner as before.

When this type of system is operated on

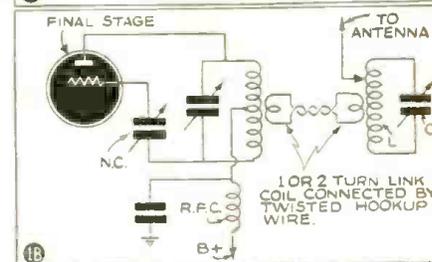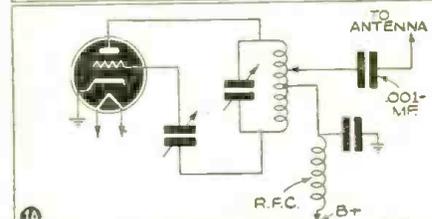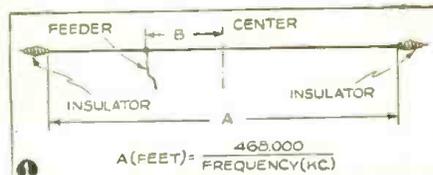

The half-wave Hertz Antenna, with single wire untuned feeder, showing different methods of coupling.

a harmonic, the feeder will have standing waves along it and will radiate. However, where it is impossible to erect more than one antenna and multi-band operation is desired, the antenna should be cut for the lowest operating frequency. The feeder should be tapped on the antenna so that distance "B" on the diagram is 1/6 the length of the antenna. Although not a perfect match on the highest wave band, a better match is afforded on the lower wave bands. Better results will be had with this multi-band antenna if the feeder is a multiple of a quarter wavelength long.

NEXT MONTH—Half-wave doublet with twisted pair feeders.

Ultra-High Frequency Antennas

● BRITISH radio listeners have had far more experience with the problems of ultra-high frequency reception than has the average American experimenter, for television has become part of the Briton's daily life. In this article, two engineers of the British branch of General Electric Co. discuss their findings.


Television Aerial and Input Circuit

Owing to the relatively high level of radiated interference in the region of 7 meters it is an advantage in almost all cases to use a frequency selective aerial fed by a correctly matched low impedance line to the receiver input.

The interference is thereby substantially limited to the frequency range necessary for reception, and as the aerial is of relatively small dimensions it can be situated in a position of minimum interference.

The most satisfactory aerial of this type is the center-fed dipole, shown in Figs. 1 and 2, tuned by adjustment of its length to the mean sound and vision wavelengths.

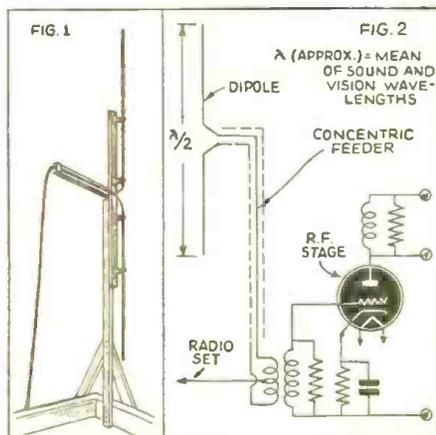The impedance of this varies from a maximum of several thousand ohms at its ends to about 80-100 ohms at the center. Transmission lines of this characteristic impedance can easily be obtained of compact construction in the form of a concentric



Center-fed dipole aerial used in England to pick up television and sound signals.

feeder, using a minimum of low-loss insulating material.

The feeder used for this purpose is shown in Fig. 1. It has an overall diameter of about 1/2 inch, and is protected externally from climatic conditions by a layer of insulating material. The characteristic im-

pedance is approximately 90 ohms, with attenuation at 45 mc. of approximately 1.0 db. per meter.

In positions of very weak signal strength, it is therefore possible to obtain improvement by using a higher aerial position, provided the vertical signal strength gradient is greater than about 1.0 per cent per meter.

At the receiver end, the line is terminated in a step-up transformer to match it to the input circuit of the first tube. This transformer also serves the purpose of reducing the effect of any direct pick-up on the feeder.


Since the aerial is used to receive both sound and vision signals, the secondary is tuned to 44 mc. by the grid-ground capacity of the R.F. amplifier tube (pentode) and damped by a terminating resistance to cover the necessary band-width of both the sound and vision channels. In the case of the combined television and broadcast receiver, the aerial coil is center tapped and connected to the aerial terminal of the broadcast receiver without the use of any switches. The feeder line is thereby used directly as an aerial for the broadcast receiver without modification, see Fig. 2.—*Excerpt from article "Television Receivers," by Espley and Edwards, in the Journal of the Television Society, London.*

Mc.	Call	Location, Distance, and Schedule	Mc.	Call	Location, Distance, and Schedule	Mc.	Call	Location, Distance, and Schedule
8.700	HKV	BOGOTA, COLOMBIA, 34.46 m. Tues. and Fri. 7-20 pm.	6.630	HIT	CIUDAD TRUJILLO, D. R., 45.25 m., Addr. "La Voz de la RCA Victor," Apartado 1105. Daily exc. Sun. 12.10-1.40 pm., 5.40-8.40 pm.; also Sat. 10.40 pm.-12.40 am.	6.170	W2XE	NEW YORK CITY, 48.62 m., Addr. Col. B'cast System, 485 Madison Ave. Mon., Fri. 12 m.-1 am. Sat. & Sun. 11.30 pm., 1 am.
8.665	COJK	CAMAGUEY, CUBA, 34.64 m., Addr. Finlay No. 3 Altos. 5.30-6.30, 8-11 pm., daily except Sat. and Sun.	6.625	PRADO	RIOBAMBA, ECUADOR, 45.28 m. Thurs. 9-11.45 pm.	49 Met. Broadcast Band		
8.665	W2XGB	HICKSVILLE, N. Y., 34.64 m., Addr. Press Wireless, Mon. to Fri. News at 9 am. and 5 pm.	6.610	YNLG	MANAGUA, NICARAGUA, 45.39 m. Emisora Ruben Dario. 1.30-2.30, 6-10.15 pm.	6.156	YV5RD	CARACAS, VENEZUELA, 48.71 m. 11 am.-2 pm., 4-10.40 pm.
8.580	YNPR	MANAGUA, NICARAGUA, 34.92 m. Radiodifusora Pilot.	6.558	HI4D	CIUDAD TRUJILLO, D. R., 45.74 m. Except Sun. 11.55 am.-1.40 pm.	6.153	HI5N	MOCA CITY, D. R., 48.75 m. 6.40-9.10 pm.
7.894	YSD	SAN SALVADOR, EL SALVADOR, 37.99 m., Addr. Dir. Genl. Tel. & Tel. 7-10.30 pm.	6.550	X8C	VERA CRUZ, MEX., 45.8 m. 8.15-9 am.	6.150	VPB	COLOMBO, CEYLON, 48.78 m., 7-11 am.
7.870	HCIRB	QUITO, ECUADOR, 38.1 m. La Voz de Quito. 8.30-11.30 pm.	6.550	TIRCC	SAN JOSE, COSTA RICA, 45.8 m., Addr. Radioemisora Catolica Costarricense. Sun. 11 am.-2 pm., 6-7, 8-9 pm. Daily 12 n.-2 pm., 6-7 pm., Thurs. 6-11 pm.	6.150	CJRO	WINNIPEG, MAN., CANADA, 48.78 m., Addr. (See 11.720 mc.) Daily 6 pm.-12 m., Sun. 5-10 pm.
7.854	HC2JSB	GUAYAQUIL, ECUADOR, 38.2 m. Evenings to 11 pm.	6.545	YV6R	BOLIVAR, VENEZUELA, 45.84 m., Addr. "Ecos de Orinoco." 6-10.30 pm.	6.150	ZPI4	VILLARRICA, PARAGUAY, 48.78 m. 4-6 pm.
7.797	HBP	GENEVA, SWITZERLAND, 38.48 m., Addr. Radio-Nations.	6.520	YV4RB	VALENCIA, VENEZUELA, 45.98 m. 11 am.-2 pm., 5-10 pm.	6.147	ZEB	BULAWAYO, RHODESIA, S. AFRICA, 48.8 m. Mon., Wed., and Fri. 1.15-3.15 pm.; Tues. 11 am.-12 n.; Thurs. 10 am.-12 n. Sun. 3.30-5 am.
7.614	CR6AA	LOBITO, ANGOLA, 39.39 m., Mon., Wed., Sats. 2.45-4.30 pm. Also 7.177.	6.516	YNIGG	MANAGUA, NICARAGUA, 46.02 m., Addr. "La Voz de las Lagos." 1-2.20, 8-10 pm. Except Sundays.	6.145	HJ4ABG	MEDELLIN, COL., 48.79 m. 11 am.-12 n., 6-10.30 pm.
7.510	JVP	NAZAKI, JAPAN, 39.95 m., 8-9.30 am.	6.500	MIL	CIUDAD TRUJILLO, D. R., 46.13 m. Addr. Apartado 623. 12.10-1.40 pm., 5.40-7.40 pm.	6.140	W8XK	PITTSBURGH, PA., 48.83 m., Addr. Westinghouse Electric & Mfg. Co. Relays KDKA 11 pm.-12 m.
7.450	T12R3	SAN JOSE, COSTA RICA, 40.27 m. "Radioemisora Athena", 9.30-11 pm., exc. Sun.	6.480	HIIL	SANTIAGO DE LOS CABALLEROS, D. R., 46.28 m., Addr. Box 356. 9.40-11.40 am., 7.40-9.40 pm.	6.137	CR7AA	LAURENCO MARQUES, PORT. E. AFRICA, 48.87 m. Daily 12.05-1, 4.30-6.30, 9.30-11 am., 12.05-4 pm., Sun. 5-7 am., 10 am.-2 pm.
7.410	HCJ84	QUITO, ECUADOR, 40.46 m., 7-9.30 pm. Irregularly.	6.470	YNLAT	GRANADA, NICARAGUA, 46.36 m., Addr. Leonidas Tenorio, "La Voz del Mombacho." Irregular.	6.133	XEXA	MEXICO CITY, MEX., 48.93 m., Addr. Dept. of Education. Daily 8-11 am., 2.30-4 pm., 7.30 pm.-12.45 am. Sun. 1.30 pm.-12.45 am.
7.410	YDA	TANDJONGPARIK, JAVA, 40.46 m., Addr. N.I.R.O.M., Batavia, 10.30 pm.-2 am.; Sat. 7.30 pm.-2 am.	6.465	YV3RD	BARQUISIMETO, VENEZUELA, 46.37 m. Radio Barquisimeto, irregular.	6.130	VP38G	GEORGETOWN, BRIT. GUIANA, 48.94 m. 9-10 am., 2.15-6.30 pm., Sun. 5.30-11.30 am., 3-5 pm.
7.380	XECR	MEXICO CITY, MEX., 40.65 m., Addr. Radio Foreign Office. Sun. 7-8 pm.	6.450	HI4V	SAN FRANCISCO DE MACORIS, D. R., 46.48 m. 11.40 am.-1.40 pm., 5.10-9.40 pm.	6.130	TIEM	SAN JOSE, COSTA RICA, 48.94 m. "El Mundo", Apartado 1049. 11 am.-11 pm., Sun. 10 am.-6 pm.
7.220	HKE	BOGOTA, COL., S. A., 41.55 m. Tues. and Sat. 8-9 pm. Mon. and Thurs. 6.30-7 pm.	6.400	TGQA	QUEZALTENANGO, GUATEMALA, 46.88 m., Mon.-Fri. 9-11 pm. Sat. 10 pm.-1 am. Sun. 1-3 pm.	6.130	CHNX	HALIFAX, N. S., CAN., 48.94 m., Addr. P. O. Box 998. Mon.-Fri. 7 am.-11.15 pm., Sat. 11 am.-11 pm., Sun. 12 n.-11.15 pm. Relays CHNS.
7.200	YNAM	MANAGUA, NICARAGUA, 41.67 m. Irregular at 9 pm.	6.384	ZIZ	BASSETERRE, ST. KITTS, W. INDIES, 46.99 m. 4.4-4.45 pm. Wed. 7-7.30 am.	6.130	LKL	JELOY, NORWAY, 48.94 m. 11 am.-6 pm.
7.177	CR6AA	LOBITA, ANGOLA, PORT. WEST AFRICA, 41.75 m., Mon., Wed., and Sats. 2.45-4.30 pm. Also see 7.614 mc.	6.340	HIIX	CIUDAD TRUJILLO, D. R., 47.32 m. Sun. 7.40-10.40 am., daily 12.10-1.10 pm., Tues. and Fri. 8.10-10.10 pm.	6.125	CXA4	MONTEVIDEO, URUGUAY, 48.98 m., Addr. Radio Electrico de Montevideo, Mercedes 823. 8 am.-Noon. 2-10 pm.
7.100	FOBAA	PAPEETE, TAHITI, 42.25 m., Addr. Radio Club Oceanien. Tues. and Fri. 11 pm.-12.30 am.	6.335	OAXIA	ICA, PERU, 47.33 m., Addr. La Voz de Chiclayo, Casilla No. 9. 8-11 pm.	6.122	HJ3ABX	BOGOTA, COL., 49 m., Addr. La Voz de Col., Apartado 26-65. 12 n.-2 pm., 5.30-11 pm.; Sun. 6-11 pm.
7.088	PIIJ	DORDRECHT, HOLLAND, 42.3 m., Addr. Dr. M. Hellingman, Technical College. Sat. 11.10-11.50 am.	6.324	COCW	HAYANA, CUBA, 47.4 m., Addr. La Voz del Radio Philco, P. O. Box 130. 6.55 am.-12 m. Sun. 9.55 am.-10 pm.	6.122	HP5H	PANAMA CITY, PAN., 49 m., Addr. Box 1045. 10 am.-1 pm., 5-11 pm.
7.050	FG8AA	POINT-A-PITRE, GUADELOUPE, F.W.I., 42.55 m., 6-7 pm., also 9-10.30 pm. Irregular. P.O. Box 125.	6.310	HIZ	CIUDAD TRUJILLO, D. R., 47.52 m. Daily except Sat. and Sun. 11.10 am.-2.25 pm., 5.10-8.40 pm. Sat. 5.10-11.10 pm. Sun. 11.40 am.-1.40 pm.	6.122	FK8AA	NOUMEA, NEW CALEDONIA, 49.00 m., Radio Noumea, Addr. Charles Gaveau, 44 Rue de l'Alma., Wed. & Sats. 2.30-3.30 am.
6.990	XEME	MERIDA, YUCATAN, 42.89 m., Addr. Calle 59, No. 517, "La Voz de Yucatan desde Merida." Irregular.	6.300	YV4RD	MARACAY, VENEZUELA, 47.62 m. 6.30-9.30 pm. exc. Sun.	6.117	XEUZ	MEXICO CITY, MEX., 49.03 m., Addr. 5 de Mayo 21. Relays XEFO 9 am.-1 pm., 7 pm.-2 am.
6.977	X8A	TACUBAYA, D. F., MEX., 43 m. 9.30 am.-1 pm., 7-8.30 pm.	6.295	OAX4G	LIMA, PERU, 47.63 m., Addr. Apartado 1242. Daily 7-10.30 pm.	6.115	OLR2C	PRAGUE, CZECHOSLOVAKIA, 49.05 m. (See 11.40 mc.)
6.805	HI7P	CIUDAD TRUJILLO, DOM. REP., 44.06 m., Addr. Emisora Diaria de Comercio. Daily exc. Sat. and Sun. 12.40-1.40, 6.40-8.40 pm. Sat. 12.40-1.40 pm. Sun. 10.40 am.-11.40 am.	6.280	HIG	TRUJILLO CITY, D. R., 47.77 m. 7.10-9.40 am., 11.40 am.-2.10 pm., 3.40-9.40 pm.	6.110	GSL	DAVENTRY, ENGLAND, 49.1 m., 6.20-8.30, 9.20-11.20 pm.
6.790	PZH	PARAMIRABO, SURINAM, 44.16 m., Addr. P. O. Box 18. Daily 6.06-8.36 am., Sun. 9.36-11.36 am. Daily 5.36-8.36 pm.	6.270	YV5RP	CARACAS, VENEZUELA, 47.79 m., Addr. "La Voz de la Philco." Daily to 10.30 pm.	6.110	XEGW	MEXICO CITY, MEX., 49.1 m., Addr. La Voz de Aguila Azteca desde Mex., Apartado 8403. Relays XEJW 11 pm.-1 am.
6.775	HIH	SAN PEDRO DE MACORIS, DOM. REP., 44.26 m. 12.10-1.40 pm., 7.30-9 pm., Sun. 3-4 am., 4.15-6 pm., 4.40-7.40 pm.	6.255	YV5RJ	CARACAS, VENEZUELA, 47.18 m. 5.30-8 pm.	6.108	HJ6AB	MANIZALES, COL., 49.14 m., Addr. P. O. Box 175. Mon.-Fri. 12.15-1 pm.; Tue. and Fri. 7.30-10 pm.; Sat. 2.30-5 pm.
6.750	JVT	NAZAKI, JAPAN, 44.44 m., Addr. Kokusai-Denwa Kaisha, Ltd., Tokyo. Irregular.	6.243	HIN	CIUDAD TRUJILLO, D. R., 48 m., Addr. "La Voz del Partido Dominicano." 12 n.-2 pm., 6-10 pm.	6.100	YUA	BELGRADE, JUGOSLAVIA, 49.18 m. 1-3, 6.30-8.30 am., Noon-6.30 pm.
6.730	HI3C	LA ROMANA, DOM. REP., 44.58 m., Addr. "La Voz de la Feria." 12.30-2 pm., 5-6 pm.	6.235	HRD	LA CEIBA, HONDURAS, 48.12 m., Addr. "La Voz de Atlantida." 8-11 pm.; Sat. 8 pm.-1 am.; Sun. 4-6 pm.	6.100	W3XAL	BOUND BROOK, N. J., 49.18 m., Addr. Natl. Broad. Co.
6.720	PMH	BANDOENG, JAVA, 44.64 m. Relays N.I.R.O.M. programs, 4.30-11 or 11.30 am. Also Sat. 9.30 pm.-1.30 am.	6.225	YVIRG	VALERA, VENEZUELA, 48.15 m. 6-9.30 pm.	6.097	ZRK	KLIPHEUVEL, S. AFRICA, 49.2 m., Addr. S. African Broad. Co., Johannesburg. Daily 12 n.-4 pm., Sun. 12 n.-3.20 pm.
6.690	TIEP	SAN JOSE, COSTA RICA, 44.82 m., Addr. Apartado 257, La Voz del Tropico. Daily 7-11 pm.	6.210	---	SAIGON, INDO-CHINA, 48.28 m., Addr. Radio Boy-Landry, 17 Place A. Foray. 4.30 or 5.30-9.15 am.	6.097	ZRJ	JOHANNESBURG, S. AFRICA, 49.2 m., Addr. S. African Broad. Co. Daily exc. Sat. 11.45 pm.-12.50 am.; Daily exc. Sun. 3.15-7.30, 9-11.30 am. (Sat. 8.30-11.30 am.) Sun. 3.30-4.30 or 4-5 am., 5.30-7, 9-11.30 am.
6.675	H8Q	GENEVA, SWITZERLAND, 44.94 m., Addr. Radio-Nations. Off the air at present.	6.205	YV5R1	CORO, VENEZUELA, 48.32 m., Addr. Roger Leyba, care A. Urbina y Cia. Irregular.	6.095	JZH	TOKYO, JAPAN, 49.22 m., Addr. (See 11.800 mc., JZJ.) Irregular.
6.672	---	--- 44.94 m., relays Salamanca, Spain, 7-9.45 pm.	6.200	HI8Q	CIUDAD TRUJILLO, D. R., 48.36 m. Irregular.	(Continued on page 758)		
6.672	YVQ	MARACAY, VENEZUELA, 44.95 m. Irregular.	6.190	TG2	GUATEMALA CITY, GUAT., 48.4 m., Addr. Dir. Genl. of Electr. Commun. Relays TGI Mon.-Fri. 6-11 pm., Sat. 6 pm.-1 am. Sun. 7-11 am., 3-8 pm.			
6.635	HC2RL	GUAYAQUIL, ECUADOR, S. A., 45.18 m., Addr. P. O. Box 759. Sun. 5.45-7.45 pm., Tues. 9.15-11.15 pm.	6.185	HI1A	SANTIAGO, D. R., 48.5 m., Addr. P. O. Box 423. 7 am.-5 pm.			

All Schedules Eastern Standard Time

First Prize Winner Pilot Lights Replace Meters

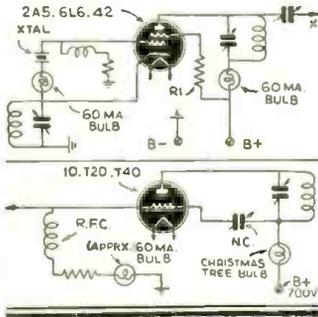Visitors to Ham shacks often frown around with the variable transmitter settings. Then, when the transmitter is put into operation, the buffer or amplifier stage draws excessive current which damages the tube unless battery bias is used. My rig at W8QKA has cheap meters which cannot




be used in circuit while the rig is in operation. Purchasing pilot light mountings fitted with colored jewel windows, I mounted these on the panel. I inserted one in the crystal circuit of the oscillator with a 60 ma. bulb in its socket. This enables me to watch the crystal current at all times for overheating. I wired another in series with the B positive lead to the final stage and put a Xmas tree bulb in the socket. When the amplifier is tuned, the bulb barely glows, but if excitation fails or the tank is detuned, etc., the bulb glows brightly and attracts the eye immediately.

Recently, I put a bulb into each stage, which makes tuning of individual stages easier and more precise. A Xmas tree bulb is the correct size for such tubes as 10's, 801's and their equivalents.—Operator, W8QKA.

Fancy Glass Panel

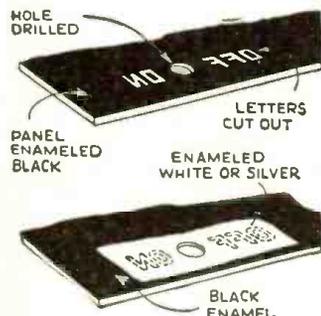A neat and attractive panel may be made by taking a sheet of double-strength window glass the required size and drilling the




necessary holes in it. If a mixture of camphor and turpentine is used, the glass will drill easily. Drills may be made from old three-cornered files ground

Radio Kinks

Each month the Editor will award a 2 year subscription for the best kink submitted. All other kinks published will be awarded eight months' subscriptions to RADIO & TELEVISION. Look over these kinks; they will give you some idea of what is wanted. Send a typewritten or ink description with sketch of your favorite to the Kink Editor.

down to a three-cornered point on a grinding wheel. After drilling the holes, clean the glass thoroughly and apply a coat of black enamel to the back of the panel. Allow this to dry, then scrape the paint off the back of the panel with a razor blade where the lettering (such as AVC. ON, OFF, etc.) is to appear. Paint over the back in white or silver where the lettering was cut out. The finished job has a mirror-like appearance and will improve the looks of your receiver or transmitter.

—Wayne Hawley.

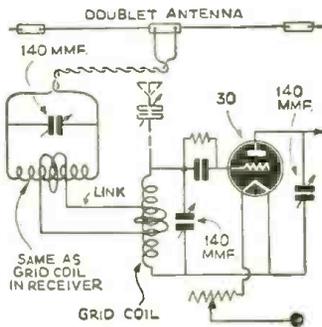

Doublet Coupling


Here is a method of increasing the sensitivity of a small radio receiver.

Procure a coil form the same size as that used in the first stage of the set and wind a coil on it of the same size wire and number of turns as the grid coil of the set. Remove the antenna trimmer condenser, connect the coil, as shown in the accompanying diagram. Coupling to the grid coil of the set, is made with two single turn coils of ordinary hook-up wire. The condenser used to tune the coil you have wound should be of the same value as the main tuning condenser in the set. In the diagram the dotted line represents the original antenna connection, which has been removed.

I find a doublet works better than an inverted L to pull in weak signals.—Frank Smith, Jr.

Shielded Cable Connector

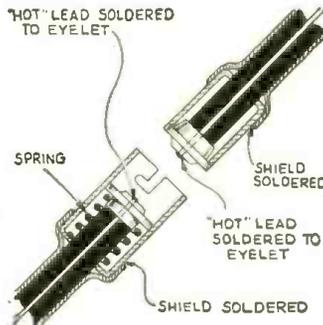Connections between long sections of one-wire shielded cable,




for microphone or phonograph pick-up, can be easily and quickly made with male and female parts of an auto antenna connector. The wires are soldered to the insulated plugs. The shield is soldered to the case of the units.

—Raymond T. Stephens.

Electric Heater For Soldering Iron

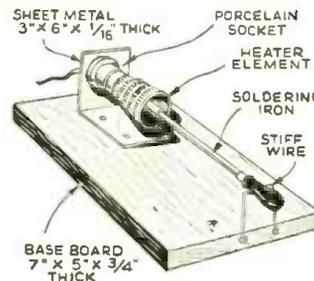
An electric heater, that brings any cheap soldering iron to operating temperature and maintains it at working heat, can be made from parts bought at the 10-cent store. The base of this iron heater is a piece of wood about 5" x 7" x 3/4". To this I screwed a



piece of 1/16" metal, the dimensions of which are shown in the sketch. On this metal I mounted a porcelain socket to hold an electric heating element in a horizontal position, and opposite the opening of the heating element I mounted a piece of stiff wire to serve as a rest for the handle of the iron. The head of the iron is inserted into the heating element and the current switched on to bring the iron to working temperature. The foot of the sheet metal must be mounted so that it comes between the heater and the wooden base in order to prevent scorching.—Carvil Mason.

Improvised Neutralizing Condenser

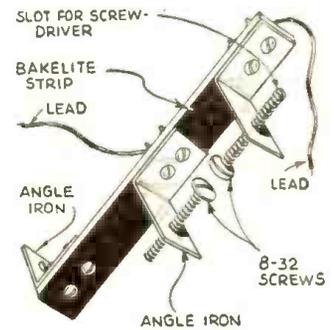
A simple neutralizing condenser, convenient for neutralizing a 6L6 beam power tube, is




easily constructed from workshop scrap. The essentials are: two 8/32 screws, two small angle irons and a strip of bakelite. One hole in each of the angle irons is threaded to take the screws. The irons are then mounted on a bakelite strip, as shown in the diagram, and are thus insulated from each other. The screws are then mounted as shown and a slot cut into the end of the upper one, so that it may be adjusted by a screwdriver. Lock nuts may be used on the screws to prevent their shifting, if desired. If the unit is to be baseboard mounted, a third angle iron can be used at one end of the bakelite strip, as shown.—Charles Allen.

Tank Coil Terminals

In low-powered transmitters, tank coils are usually wound on standard coil forms. The following kink has been used to provide a way to connect antenna feeders neatly to the coupling coil. Two grid caps from a pair of defunct tubes were obtained and drilled out to pass small bolts. They were then bolted to opposite sides of a standard coil form. The ends of the coupling coil were connected to the grid caps on the inside of

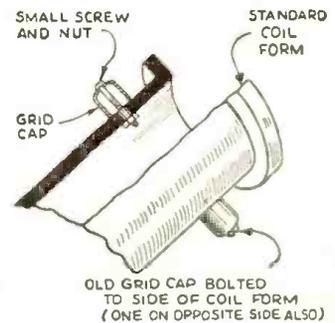

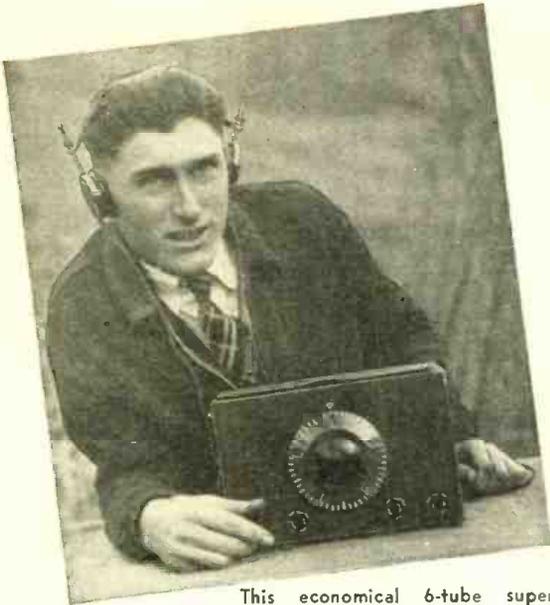the coil. All that is necessary when changing coils is to pull the feeders, which are terminated in insulated grip cap connectors, yank the coils and substitute the new ones. —Richard L. Kile, K6QPG.



This economical 6-tube superhet, which will appeal to Hams and Fans alike, will operate a loud speaker.

A 6-Tube, 1.4 Volt for the "Ham"

This battery-operated 6-tube super has surprising sensitivity and selectivity. The circuit employs a regenerative mixer, an oscillator, I.F. amplifier, regenerative detector, B.F. oscillator and A.F. output tube. Operation is very economical, the total filament drain being only .3 ampere.


● THE fine results obtained with the 1.4 volt "Economy Three" T.R.F. receiver described in the February issue induced the writer to try out the new tubes in a superheterodyne circuit. The results far exceeded his expectations and the six-tube

The circuit, as is shown below, consists of a 1A7-G regenerative mixer, a 1N5-G oscillator, a 1N5-G 460 kc. I.F. amplifier, a 1N5-G regenerative detector, a 1N5-G beat-frequency oscillator and a 1A5-G

receiver to be described here. so far as sensitivity and selectivity are concerned, is the equal of many standard A.C. "communications" type receivers using the same number of tubes.

audio output amplifier. The tubes used are all of the new economical 1.4 volt type, the total filament drain being only 0.30 ampere and the measured "B" drain less than 0.02 ampere at 90 volts. The R.F. gain (sensitivity) in the 1A7-G circuit is tremendously increased by making the mixer regenerative. The method of introducing feed-back is novel but extremely simple

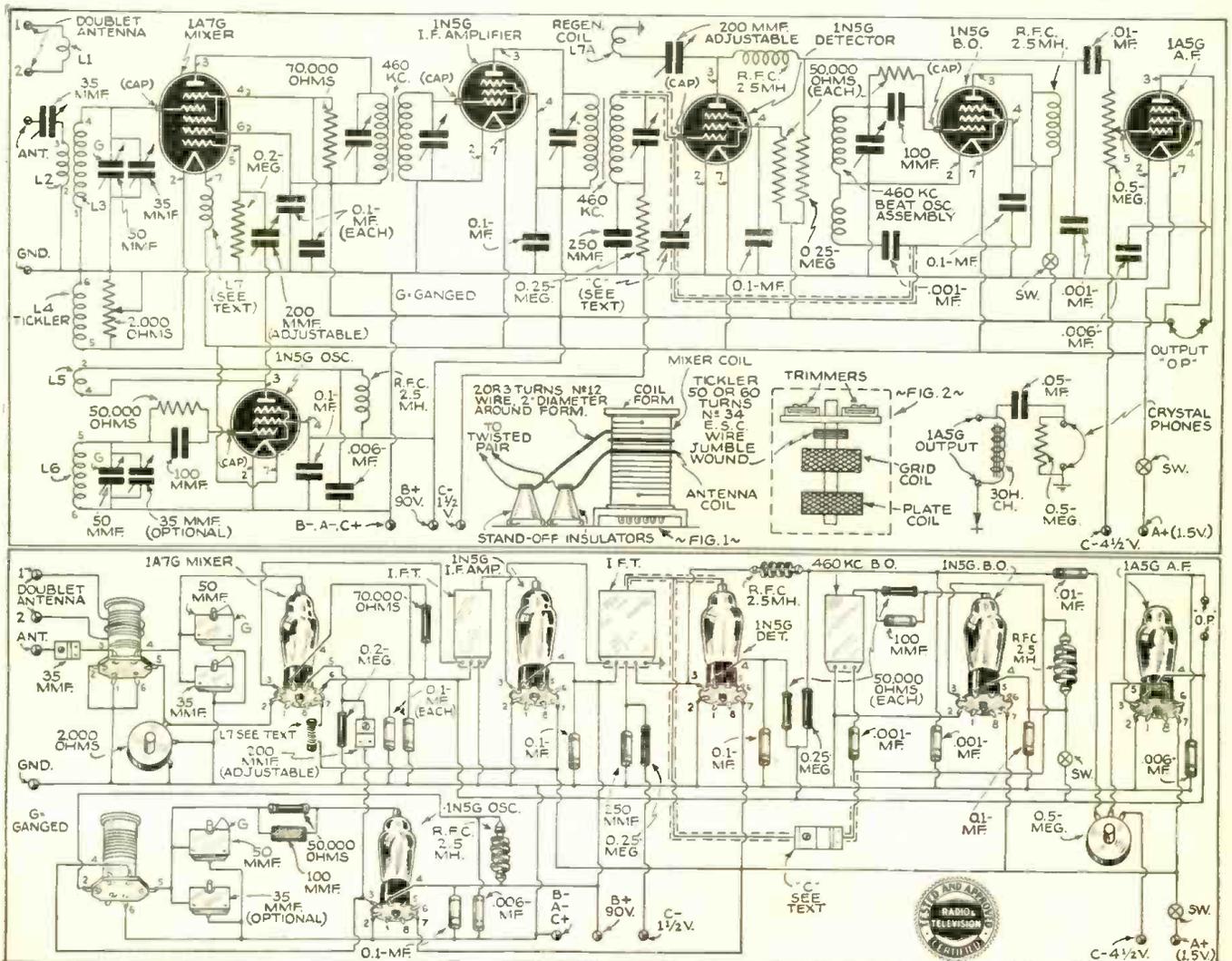Wiring diagrams, both schematic and pictorial, for the superhet are given below.



SUPER-HET or S-W Fan

Harry D. Hooton,
W8KPX



and effective—a small home-made R.F. choke (L7) consisting of about 25 to 30 turns of No. 26 enameled wire is wound on an old broadcast R.F. choke spool (one-half inch diameter) and inserted in the positive leg of the 1A7-G filament return, close to the tube socket, as shown in the diagram. The other (negative) filament lead is returned to ground through the tickler winding, L4. A 2,000 ohm potentiometer shunted across L4 permits the feed-back to be varied over a considerable range. The oscillator is of the conventional type, the R.F. output being taken from the plate of the tube through a small adjustable coupling condenser. Although better screening between the oscillator coupling grid, G1, and the mixer elements could be obtained by returning the anode grid, G2, to ground, it has been connected to the positive 90 volt plate return, in order to take advantage of the higher conversion gain thus made possible.

The I.F. transformers are of the iron-core, air-trimmed type which gives the maximum gain in this circuit. The tickler winding in the detector circuit, L7A, consists of about 50 or 60 turns of No. 34 E.S.C. wire jumble wound on the I.F. transformer core, about one-fourth inch from the grid coil, as shown in the drawing. The direction of the winding is not important as the leads can be reversed until oscillation is obtained. It should be emphasized at this point that the detector is *not permitted to oscillate*; the feed-back condenser, in series with the tickler coil, is adjusted so that the 1N5-G is operating *just below the point of oscillation* at all times. A separate beat

oscillator is used for the reception of c.w. code signals when this is desired. This method of operation greatly facilitates the reception of the weaker signals, which would be lost in the noise if the detector circuit was allowed to oscillate. However, if a great increase in I.F. selectivity is desired, or if the set is to be used for c.w. code reception only, the detector can be permitted to oscillate and the output I.F. transformer adjusted to cut off one side-band, giving the effect of "single signal" reception. Alignment details will be found farther on in this article.


The mechanical construction of the receiver is not at all complicated or difficult. As the photos and drawings show, the various parts are mounted in the National "C-One-Ten" steel cabinet, no separate chassis being used. The dial and tuning condenser assembly is the National "PW-2" type, which spreads the tuning scale over 500 degrees on the dial. The photograph of the sub-base assembly, taken before the receiver was wired, shows how the tuning condensers, the I.F. transformers, the coils and the tubes are placed. For exact dimensions, refer to Fig. 3.

In wiring the circuit, keep the "hot" grid and plate leads as short and direct as possible. Place these leads right against the metal sub-base in order to limit their external fields; it may be necessary to

shield the plate and grid leads from the I.F. transformers and the 1A7-G and 1N5-G mixer and I.F. tubes to eliminate oscillation at the I.F. level. Place the bypass condensers right on the socket terminals themselves in order to obtain a short, low-impedance path to ground for the R.F. and I.F. currents. Use solid No. 14 tinned copper bus wire for making the

(Continued on page 754)

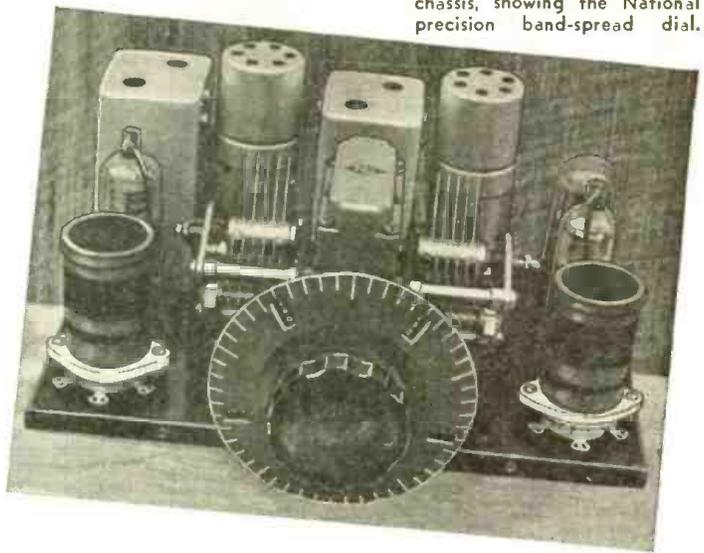Front view of the superhet chassis, showing the National precision band-spread dial.



Parts List, 1.4 Volt Super

NATIONAL CO.

- 1—PW-2 tuning unit (50 mmf. per section, double-spaced)
- 2—Iron-core I.F. transformers, 450-550 kc.
- 1—"C-One-Ten" cabinet, with panel and sub-base
- 1—R-201 R.F. choke, 12 mh.
- 1—R-100 R.F. choke, 2.5 mh.
- 1—Set XR-5 coil forms (see text)
- 2—5-prong isolantite sockets
- 4—8-prong isolantite sockets
- 2—UM-35 tuning condensers (35 mmf.)
- 3—No. 8 grid clips
- 1—Beat-frequency oscillator transformer, 450-550 kc.
- 1—M-30 padding condenser (30 mmf. max. capacity)

HAMMARLUND

- 2—Adjustable padding condensers, 220 mmf. max. capacity
- 2—Aluminum tube shields

SPRAGUE

- 6—Paper dielectric tubular condensers, 0.1 mf., 600 volts
- 2—Mica condensers, 0.006 mf.
- 2—Mica condensers, 0.0001 mf.
- 2—Mica condensers, 0.001 mf.
- 1—Mica condenser, 0.00025 mf.
- 1—Mica condenser, 0.01 mf.

I.R.C. (Resistors)

- 1—Fixed resistor, 200,000 ohms, ½ watt
- 3—Fixed resistors, 50,000 ohms, 1 watt
- 2—Fixed resistors, 250,000 ohms, 1 watt
- 1—Fixed resistor, 70,000 ohms, 1 watt

(Volume controls)

- 1—Volume control, 2,000 ohms, with DPST switch (regeneration)
- 1—Volume control, 500,000 ohms (audio volume)

BRUSH

- 1—Pair crystal headphones, or loudspeaker

RAYTHEON (Tubes)

- 1—1A7-G tube
- 4—1N5-G tubes
- 1—1A5-G tube

CROWE

- 4—Pointer knobs

WRIGHT DECOSTER


- 1—Permanent magnet dynamic speaker with universal transformer

EVEREADY (Batteries)


- 2—No. 386 "B" batteries
- 1—4½ volt "C" battery
- 1—1½ volt dry cell or 1½ volt "A" pack

MISCELLANEOUS

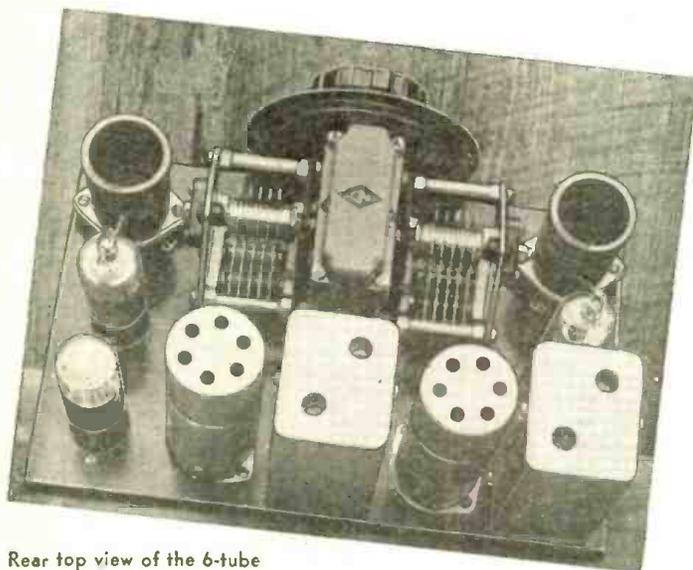- Hook-up wire, solder, machine screws, etc.



Rear top view of the 6-tube receiver.

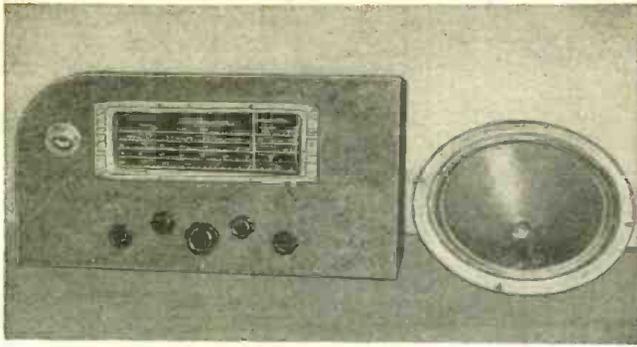

Front View of All-Wave 8-tube Super-het receiver.

How to Build An All-Wave 8-Tube




This unusual 5-band super-het, with range of 7 to 2,306 meters, employing 8 tubes for loud-speaker reception, can be built with 5 tubes for head-phone use. It has band-change switch, beat oscillator, noise-limiter and built-in power-supply.

● MANY Hams and SWL's would like a receiver covering not only the complete *short-wave* spectrum, but the *broadcast* band and the *long waves* as well. A receiver covering such a wide range presents rather impressive difficulties in the coil arrangement. Naturally one must have *coil switching*, but this presents quite a problem in designing the necessary coils and still greater difficulty in getting the coils for each band to "track" properly. Fortunately the problem has been solved by the availability of an efficient multi-wave coil assembly designed by the Meissner company. This coil assembly covers the frequency spectrum between 132 kc. and 42.5 megacycles in five bands. Designed to be used

with a 3-gang, 410 mmf. tuning condenser, the coil assembly comes already aligned at the factory so that only slight readjustment is necessary for efficient operation.


The set built around this coil unit by the writer contains a

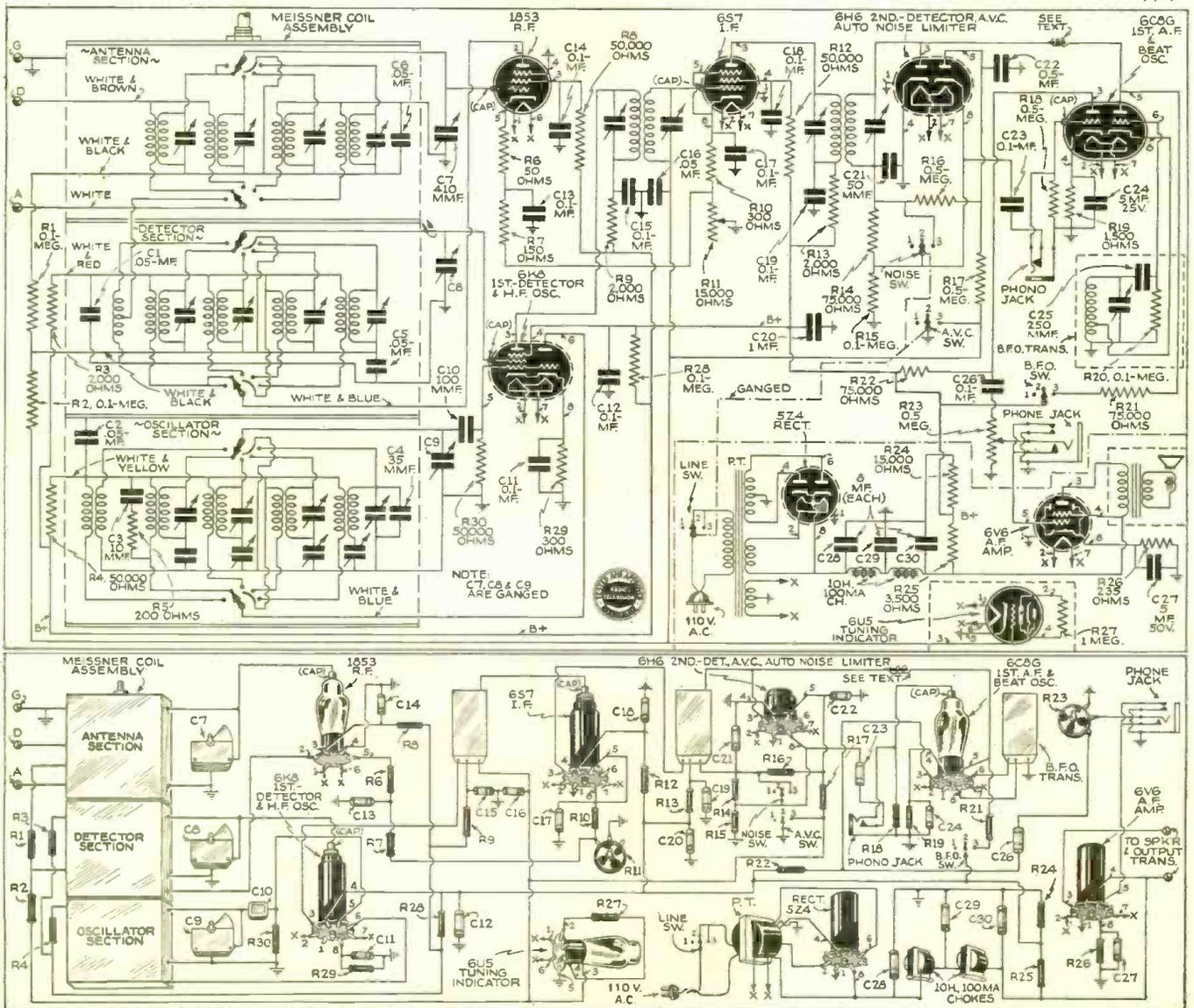Hook-up of 5-band 8-tube receiver: it can be built with 5 tubes for head-phones, eliminating power A.F. stage, "magic-eye", and "B" supply.



Herman Yellin
W2AJL

Receiver

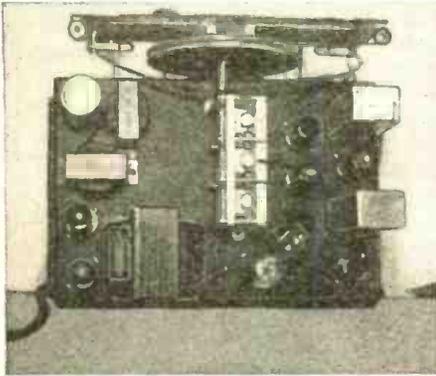

Top view of 8-tube super-het.

total of eight tubes, but the constructor can easily omit the power audio stage, the rectifier and power supply, and the "magic-eye" tuning indicator. Thus if the builder already has a power supply and amplifier, only five tubes need be used.

The complete receiver was assembled on a chassis factory-punched with the necessary holes, so that only a few small holes had to be drilled. Construction is thereby greatly facilitated. Incidentally, the large slide-rule type dial should be supported at its ends by a pair of simple brackets which can be obtained with the dial.


For the R.F. stage, the new variable-mu high frequency pentode, the 1853, was employed. Even on the lower frequencies, the increased gain over the standard 6K7 was noted. On the high frequencies, of course, the increase was more marked. Unfortunately, when using such a large value of tuning condenser, the use of an R.F. stage results in an actual loss instead of a gain on the very highest frequency band, so that on this band the R.F. stage is omitted. The sensitivity on this band is still adequate, however. It will be noted that only a portion of the 1853 cathode resistor is bypassed. This is done in order to minimize changes in input capacitance and input conductance with changes in plate current. Also note that the suppressor is connected directly to ground and *not* to the cathode.

Combination 1st Det. & H.F. Oscillator

A 6K8 tube is used as a combination first detector and high-frequency oscillator. This tube is equivalent to a 6L7-6C5 combination and has a much higher conversion efficiency than the old converter tubes. In the single I.F. stage is a 6S7 which is somewhat like a 6K7 except for its higher amplification and lower screen voltage. Its filament current is only 0.15 ampere. Following the 6S7 is a 6H6 which performs a multitude of functions. First, it operates as the second detector; second, it provides AVC; and third, (Continued on page 743)

Ultra-Modern

The
NEW

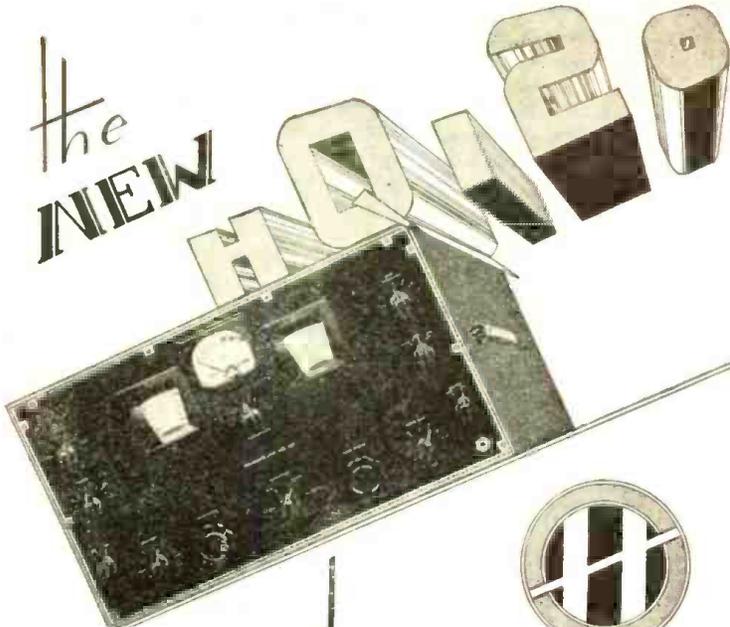

Tuning range—31—54 mc.

- ★ Full range selectivity in the crystal filter makes the "HQ-120" ideal for either phone or C.W. operation.
- ★ Over 310 degrees spread for each amateur band. Direct calibration in megacycles allows the amateur to check frequency with marked accuracy.
- ★ Due to uniform R.F. gain and constant crystal filter output, the calibrated "S" meter provides an accurate check on signal strength.
- ★ Special 15-gang condenser, 6-gang main tuning, and 9-gang band spread, provides uniform band spread and high efficiency on all bands.
- ★ Efficient noise limiter for reducing automobile ignition QRM and similar disturbances.
- ★ Antenna compensator permits perfect circuit alignment with all types of antennas. Also provides maximum image rejection.

Write Dept. RT-4 for Booklet

HAMMARLUND

424 N 33 ST NYC CITY NY

Canadian Office: 41 W. Av. No., Hamilton

- #### FEATURES
- SIMPLICITY
 - PERFECT CONTROL
 - SEMI-AUTOMATIC
 - EASE OF OPERATION



MARTIN FLASH

The greatest VALUE ever offered

STURDY CONSTRUCTION

Single lever. Two pairs of coin silver contact points . . . one for dots, the other for dashes.

Designed especially to meet the demands of amateur operators. Beautiful black crackle finish. This key is a "winner." Weight, 2 pounds. Base, 6x3x3/8. New low list, each **\$6.95**

Discount to Amateurs 40%

Ask your dealer to show you the FLASH Key. If he cannot supply you, send your order direct to us.

Write for complete catalog illustrating and describing all models.


MARTIN RESEARCH & MFG. CORP.

98 PARK PLACE

Dept. RT-4

NEW YORK CITY

This Universal Test Meter

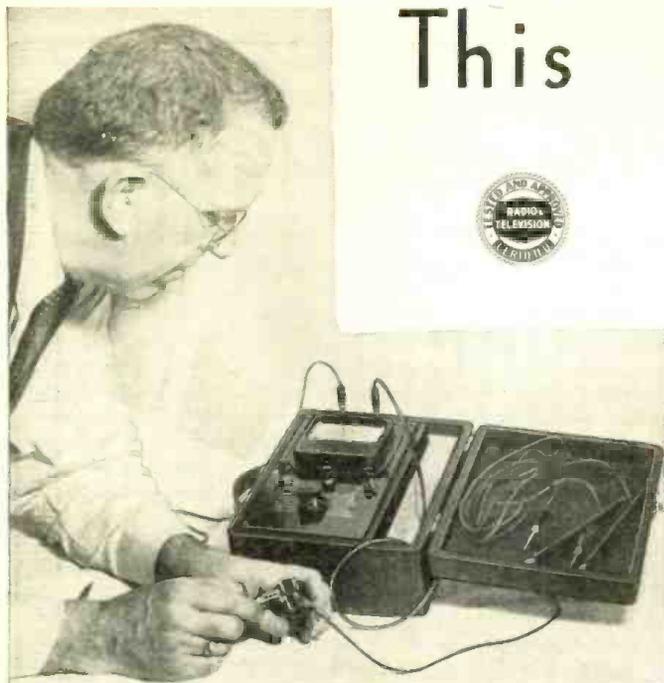

This test meter can be built at nominal cost. It has A.C. and D.C. ranges of 0-10, 50, 250, 1000 and 2500 volts. Current ranges are 1, 10, 50, 250 ma. Three resistance ranges are incorporated. Special scale to fit standard meter accompanies this article.

Owing to the fact that a switch quickly converts the meter for the different ranges, tests of many kinds may be made rapidly with this instrument.

rectifier for reading voltages. If a meter with a lower maximum current reading were used, it would be necessary to shunt the meter for A.C. and use separate sets of multipliers for direct and alternating current.

● WHILE the necessity for a universal type of test meter is agreed upon by all experimenters, the form which it is to take is a matter of wide disagreement. Practically everyone will agree as to the desirability of having as great a meter sensitivity as practicable. However, the greater the meter sensitivity, the larger the size of the multipliers for a given range and so the higher the cost.

There is one school of technicians that leans toward the use of carbon or metallized resistors as multipliers, thereby greatly reducing the cost. However, carbon resistors tend to undergo changes in resistance with age and also have a tendency to change in value when subjected to overload. Therefore, an instrument which reads accurately when new may become quite

inaccurate after being in use for some time. Unless checked with a reliably accurate instrument, the owner will remain blissfully unaware of any errors in his cheap test meter.

Medium Priced Meter Used


The writer is of the opinion that an instrument having a resistance of 2000 ohms per volt is of sufficient sensitivity for all ordinary purposes, and at the same time will result in multiplier resistor values which are economically feasible.

The universal test meter described herein was built around a 4" Triplet 500 microampere meter. One reason for the choice of the 500 microampere unit was that this was about the lowest current meter which would operate satisfactorily with a meter



Front view of the handsome test meter described in this article.

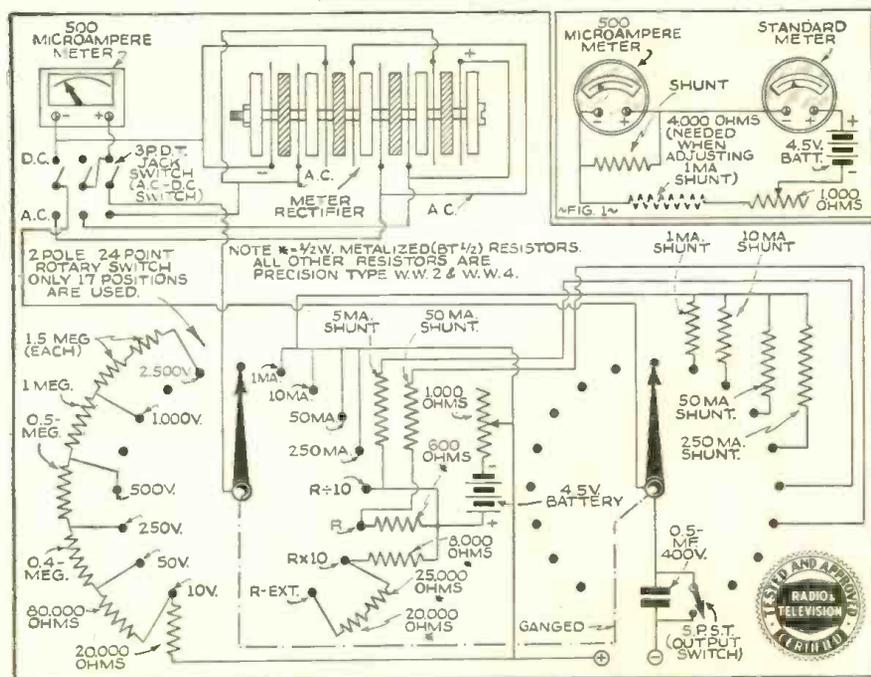Wiring diagram for the all-around test meter, which, with its rectifier, permits A.C. and D.C. tests.



Measures Both A.C. and D.C.


This meter has both A.C. and D.C. ranges of 0 to 10, 50, 250, 1000 and 2500 volts at a sensitivity of 2000 ohms per volt. Current ranges are 1, 10, 50 and 250 milliamperes d.c. Three resistance ranges are incorporated in the instrument using a built-in 4½ volt battery and provision has been made for connecting an external 22½ volt battery for reading very high resistance values. All these values can be read directly from the meter scale.

New Meter Scale Provided

Since no ready-made scale was available, it was necessary to have one drawn especially for this instrument. A full size facsimile is reproduced and can be cut out and pasted over the regular metal scale. When removing the regular metal scale, be extremely careful not to bend the meter pointer. Paste the new scale over the metal scale, being careful not to have any wrinkles in it and replace in the meter. This operation should be performed some place where there are no air currents, as a little dust in the meter movement will cause some stickiness.



Easily and cheaply built by anyone

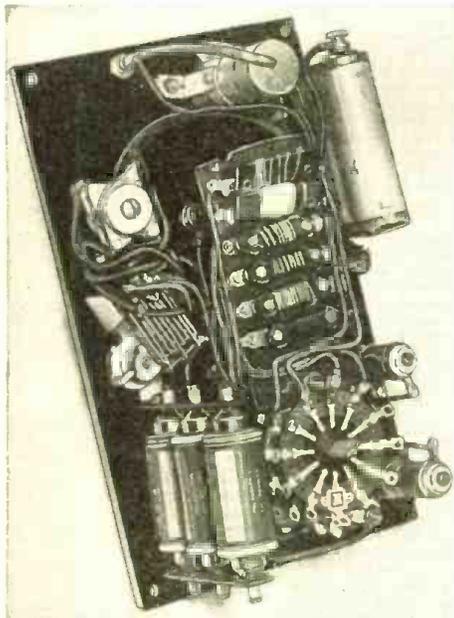

Rear view of the test meter, showing the resistance units.

The panel size shown in the drawing is about the minimum possible and need not be strictly adhered to. If a cabinet of different dimensions is already available, use a panel to fit it and re-arrange the parts to make a well balanced layout.

Not Necessary to Change Test Leads

As reference to the diagram will show, there are only two tip jacks, obviating the necessity of moving test leads to different jacks when it is desired to change from voltage to current or to output or to ohms. The two small switches under the meter are an A.C.-D.C. three-pole, double-throw jack switch used for connecting in the meter rectifier for reading A.C. voltages and the single-pole, single-throw jack switch which shorts out the built-in .5 mf. condenser used in measuring receiver output voltages. Between these two switches is the zero ohms adjuster. Incidentally, the resistors in the ohmmeter circuit are of the 1/2 watt metallized type, since they are not required to maintain the rated resistance values. The ohms adjuster takes care of any deviation from the correct and needed value. The main selector switch is a special Mallory 2-pole, 24-point rotary switch, not all of whose contacts are used, leaving several for any additional ranges to be added at some future time.

Reference to the photos will show the method of mounting the various components. The .5 mf. condenser and the 4 1/2 volt battery are fastened down by means of large size fuse clips or Mallory FPM-14
(Continued on page 745)

Now! **ALLIED'S New Spring Catalog** Brings you everything new in Radio **AT LOWEST PRICES**
DEALERS • SERVICEMEN • AMATEURS • BUILDERS • SOUND SPECIALISTS
Get Your Copy Today!



NEW SETS!

Now in ALLIED's brand new Spring Catalog, see the new Knights, with Push-Button Tuning, "Air-Magnet" built-in aerials, newest features—at prices never before possible! 60 Models, some as low as \$6.95—AC, AC-DC, 1 1/2 Volt, 6 Volt, 32 Volt, portable and auto sets—and radio's biggest line of Phono-Radios, phonographs, and record players! All backed by an ironclad guarantee! See many "specials"—"Pee Wees," "Magic Wireless" record players, etc. For real radio profits, send coupon now!



AIR-MAGNET RADIO




LOW-COST AUTO-RADIO

NEW P.A.



8 to 65 watts—standard and de luxe—permanent, portable and mobile—Monitor Speakers, Remote Control—also complete recording equipment, discs, accessories; read all about the new low-priced "Flex-disc"!

NEW AMATEUR GEAR!

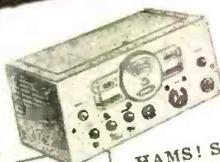

HAMS! See all the new station-checking equipment to meet new FCC regulations: Rotary Beam Antenna gear, new Hallicrafters National, Howard, R.M.E. models—all leading lines, at lowest prices! Everything for the Amateur!


NEW BUILDERS' KITS!

Dozens of new kits! Melssner 1, 2, 3 Tube Kits, "Pee-Wees," "Mystery" Phono and Mike kit, Photo Cell, etc. Write for Free Parts Lists!

Send for HANDBOOK

A new and different book, tells how to select circuits, read diagrams, build sets, etc. Packed with valuable data. Only 10c—see coupon. Get your copy now!

NEW TESTERS!

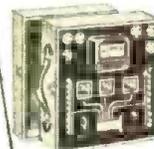

New equipment with provision for new Loctal Tubes, etc.—all leading lines of tube checkers, set testers, analyzers, oscillographs, etc.—and over 14,000 parts at lowest prices, in ALLIED's new catalog!

ALLIED Radio CORPORATION

ALLIED Radio Corp. Dept. 3-D-9
833 W. Jackson Blvd., Chicago, Ill.

() Send me your new FREE Radio Catalog for spring.

() Enclosed find 10c (plus 3c postage) for Radio Builders' Book.

Name

Address

City State

See Pages 752, 758 and 766 for Interesting Subscription Offers!

SOLAR gives you **MORE** for your money **MINICAP**

Catalog upon request
SOLAR MFG. CORP., 599 Broadway, New York

BRUSH HIGH LEVELER SERIES MICROPHONES

Range in price from \$22.50 to \$32.50

New Brush Headphones

Write for your Brush catalog today
THE BRUSH DEVELOPMENT COMPANY
3326 PERKINS AVENUE
CLEVELAND, OHIO

Question Box

Vertical Antenna

? Unfortunately, I have moved into a new location where I find it impossible to erect an outside antenna. Can one of the new type vertical antennas be employed?—Larry Hamsley, Hoboken, N. J.

A. There is no reason why such an antenna cannot be used. In fact, a prominent radio manufacturer has recently brought out a vertical antenna for home use. It consists of a 12-foot vertical rod. Attached to one end are two special insulators and metal straps. The straps are so constructed that they may be easily strapped or clamped around the roof top vent pipe or any similar protrusion. Also it is possible to mount the clamps on the outside of the building.

A single wire connected to the vertical connects it to the radio receiver and lightning arrester. Connection to the radio receiver is made through a 2000 mmf. condenser in order to isolate any charge picked up by the vertical. At the same time it allows radio frequencies to pass freely to the receiver. The arrester and coupler are shown.

The 99,000 ohm resistor acts as a leak for any static charge which might build up on the antenna and lead-in. The value of the resistance is sufficiently high so as not to affect signals picked up by the antenna proper. A gap-type arrester connected across the resistor discharges the antenna on large static charges to ground.


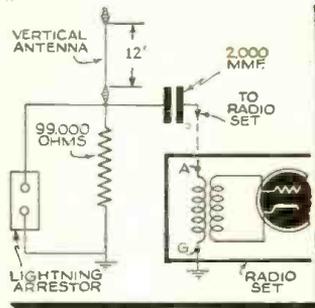


Diagram for Vertical antenna, No. 1174.

Remote Record Player

? Is it possible for you to print a diagram for a remote record player? This player should have a crystal pickup and at least one tube as amplifier.—Harold Morgan, Saginaw, Michigan.

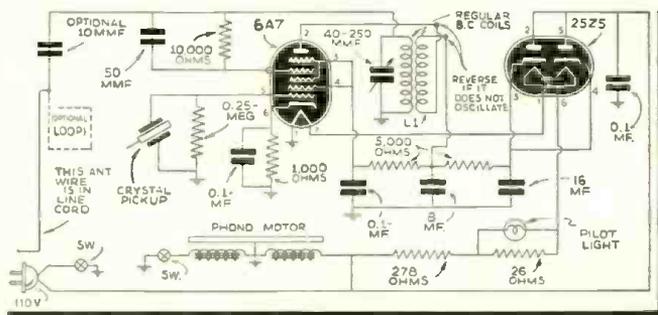A. A schematic of such a player unit is shown here. A crystal pickup feeds its audio output into the Number 1 grid of a 6A7. Grid Number 2 has a positive voltage applied to it through a 5000 ohm resistor. The remaining elements are so arranged as to become an oscillator, operating in the range from 540 to 740 kc. The coils L1 are used to determine the frequency of oscillation, tuning being accomplished by a 40-250 mmf. trimmer. Contained



Hook-up for remote "record player", No. 1175.

in the line cord is a length of wire which extends from the cord a few inches from the plug end. The other end of the wire is coupled to the grid of the oscillator circuit through a 10 mmf. condenser. This wire serves to radiate energy generated by the oscillator.

A 2525 is used to supply power to the 6A7. The rectified voltage is capacity-resistor filtered. The phono-motor is shown at the lower left.

To operate the unit, tune any receiver to 540 kc. With the unit in operation, carefully adjust the 40-250 mmf. condenser until

the record being played is heard through the receiver. This adjustment should be made carefully so that the oscillator is exactly in tune with the receiver. In cases where the receiver cannot tune to 540 kc., any other clear channel up to 740 kc. may be used.


Where sufficient signal is not received at the receiver, due to undue static or stormy weather, couple an insulated wire from the set antenna post to the free lead on the record player line cord. Do not make positive contact with this line cord wire, merely twist the two insulated leads together.

2 1-2 Meter Transceiver

? Will you please publish a diagram of a 2½ meter transceiver, one using the two volt type tubes namely, a 30 and a 49. The transceiver should be for battery operation and should show all the necessary parts needed.—Walter Maaken, Winnipeg, Manitoba, Canada.

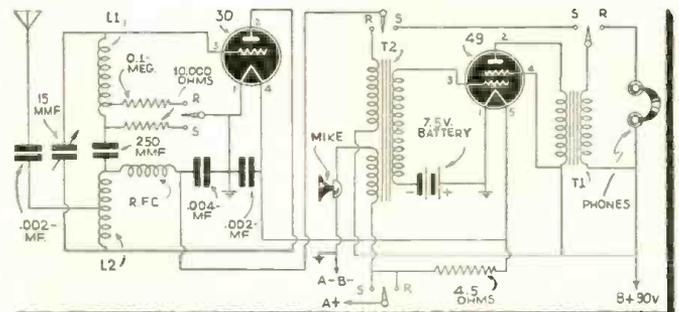A. Here is a diagram of a 2½ meter transceiver. It can be built into a compact carrying case. Miniature dry batteries can be used and in spite of their small size they should give approximately 8 hours continuous service. A 4-pole double-throw anti-capacity switch changes the circuit from SEND TO RECEIVE.

Two-volt type tubes are used: a type 30 and a 49. The circuit diagram shows the values of the parts needed. From the circuit diagram it is seen that the 30 tube is used as a super-regenerative detector in the receiving position or as a modulated



Transceiver for 2.5 meter communication, No. 1176.

oscillator in the transmitting position. The 49 tube serves as a tetrode audio amplifier for receiving and a modulator tube for transmitting purposes. Transformer T1 serves as a modulation transformer for transmitting and an output transformer for receiving. The R.F. choke is the 2½ meter conventional type. The tuning coils needed are L1 and L2. L1 consists of 4 turns of number 12 wire tapped at turn 1. L2 consists of 4 turns number 12 wire and tapped at the center.

Veri Cards

? How does one go about getting "veri" cards from foreign stations?—L. J. Hanos, Brooklyn, N. Y.

A. Merely make a note of the time, date and character of the program received. This, together with an International Postal Reply coupon should be sent to the station, together with a request for verification.

Response Range of Hi-Fi Set

? Can you inform one of your ardent readers what is the response range of a so-called high-fidelity receiver?—M. K. Laboting, St. Louis, Mo.

A. A high-fidelity radio receiver should be capable of reproducing frequencies from about 30 to 8000 cycles or higher. The RMA defines such a receiver as one that has a frequency range of from 50 to 7500 kilocycles, with not more than 5% harmonic distortion.

A fee of 25c (stamps, coin or money order) is charged for letters that are answered by mail. This fee includes only hand-drawn schematics. We cannot furnish full-size working drawings or picture layouts. Letters not accompanied by 25c will be answered on this page. Questions involving considerable research will be quoted upon request. Names and addresses should be clearly printed on each letter.

New HAM Licenses

COMPILED FROM THE LATEST RECORDS OF THE FEDERAL COMMUNICATIONS COMMISSION

THERE are now approximately 50,000 licensed radio amateurs in this country. And dozens of new amateurs are being licensed every month.

Heretofore no publication has listed the names and addresses of the new licensees as issued. RADIO & TELEVISION Magazine now provides this unique service, and publishes a list of newcomers in every issue. Check the names carefully so that you will be able to get in touch, not only with amateurs in your neighborhood and vicinity, but also with those distant amateurs whom you wish to contact either by mail or by radio.

This list contains 85 names of newly licensed amateurs. YLs' names appear in blackface type.

- | | |
|---|--|
| <p>W7FAK Victor B. Ross, Coliseum Apts., Apt. M, Juneau, Alaska.</p> <p>WILSC Leonard Rubin, 16 Almont St., Malden, Mass.</p> <p>WILSD Wm. A. True, 97 Myrtle St., Waltham, Mass.</p> <p>WILSE Harvey J. Jacobson, 35 Homestead St., Roxbury, Mass.</p> <p>WILSF Joseph W. Sheehan, 436 Sea St., Quincy, Mass.</p> <p>W2BEC John A. Friel, 134-03 95th Ave., Richmond Hill, L. I., N. Y.</p> <p>W2LUC Wm. Weingart, 201 Allen St., New York, N. Y.</p> <p>W2LUD Gideon Van W. Stivers, West Main St., Riverhead, N. Y.</p> <p>W2LTW Sylvester Montecucollo, 97 St. Pauls Ave., Jersey City, N. J.</p> <p>W3HWX Howard M. Shade, 7 Russell Rd., Alexandria, Va.</p> <p>W3HWY Calder C. Murlatt, Jr., 2008 Swatara, Harrisburg, Pa.</p> <p>W3HXA Norman Tulp, 7025 Clinton Rd., Upper Darby, Pa.</p> <p>W3HXB Joseph H. Snyder, Elm Ave., East Millstone, N. J.</p> <p>W3HXE George E. Schellhas, 726 Grantley St., Baltimore, Md.</p> <p>W4ACO Robert Van Sleen, 221 S. Marietta St., Gastonia, N. C.</p> <p>W4FUB Jones C. Tipton, 809 Lamar Ave., Charlotte, N. C.</p> <p>W4FUD John H. Turner, 254 Church St., Macon, Ga.</p> <p>W4FUE George Wentz, R.F.D. No. 3, Hickory, N. C.</p> <p>W4SY Samuel Saylor, 10 S. 3rd St., Fernandina, Fla.</p> <p>W5HPO Earl E. Ordway, Unit 3, Sec. 8, U.S.N.R. c/o Nat'l Guard Armory, Ardmore, Okla.</p> <p>W5HPQ Walter M. Mayer, 2106 Frio City Rd., San Antonio, Texas.</p> <p>W5HPS Clarence Scott, 131 S. St. Patrick St., New Orleans, La.</p> <p>W5HQA Clarence T aylor, Kemah, Texas.</p> <p>W6EJD Kenneth M. Curtis, 27-13th St., National City, Calif.</p> <p>W6GKR Clifford L. Johnson, Oakland Way, Emerald Lake, near Redwood City, Calif.</p> <p>W6LYL Jay D. B. Lattin, Signal Corps Unit, New Men's Gym, Univ. of Calif., Berkeley, Calif.</p> <p>W6QQM Walter Nestler, 2055 Del Mar Ave., San Marino, Calif.</p> <p>W6QQN Stanley C. Hall, Trustee, Mission Radio Club, 1394 Villa St., Mountain View, Calif.</p> <p>W6QQP Hubert Woods, 2625 Carlton Place, Riverside, Calif.</p> <p>W6QQQ Edwin S. Reiten, 1947 W. 43rd St., Los Angeles, Calif.</p> <p>W6QQR Leonard F. Melsha, 8416 San Carlos, South Gate, Calif.</p> <p>W6QQX Rexford R. Haslam, 1071 N. Angeleno Ave., Burbank, Calif.</p> <p>W6QQY Charles W. Worman, 140 N. Louise St., Glendale, Calif.</p> <p>W6QUA William Sharp, 731 S. Chapel St., Alhambra, Calif.</p> <p>W6QUB Robert Ullery, Rt. 1, Neal Rd., Paradise, Calif.</p> <p>W6QUC Francis D. Wells, 340 Hayes St., San Francisco, Calif.</p> <p>W6QUE Lon M. Hildebrand, 682 N. Central Ave., Stockton, Calif.</p> <p>W6QUF LeRoy W. Jillson, 811 East F St., Colton, Calif.</p> <p>W6QUG Richard E. Fricks, 4534 Idaho St., San Diego, Calif.</p> <p>W6QUT Freeman F. Gosden, 900 N. Alpine Dr., Beverly Hills, Calif.</p> <p>W7AAQ Jack W. Worley, 5616 N. Wall St., Spokane, Wash.</p> <p>W7H5 Oscar A. Schwartz, S. 3010 Lamont, Spokane, Wash.</p> <p>W8IPO Joe H. Van Wie, 5534 Marlborough, Detroit, Mich.</p> <p>W8JZH John F. O'Shea, 1057 Albert, Toledo, Ohio.</p> <p>W8SRL George M. Hudimar, 1597 Hopkins Ave., Lakewood, Ohio.</p> | <p>W8SSE Ernest Oney, 617 Herrick Ave., Wellington, Ohio.</p> <p>W8SSM John E. Kimar, 2060 W. 41, Cleveland, Ohio.</p> <p>W8SSN Stephen A. Hoynos, 848 Dana St., Warren, Ohio.</p> <p>W8SSP George Reinhart, 210 Main St., Stroudsburg, Pa.</p> <p>W8SSQ James B. Sackrider, 529 Clark Ave., Owosso, Mich.</p> <p>W8SSR Gregory W. Sawmiller, 121 E. Corning Ave., Syracuse, N. Y.</p> <p>W8SSS John J. Schueler, 32 Worcester Pl., Buffalo, N. Y.</p> <p>W8SST Thaddeus F. Dudek, 6722 Fullerton, Cleveland, Ohio.</p> <p>W8SSU Russell E. Geiger, R.F.D. No. 4, Youngstown, Ohio.</p> <p>W8SSW Ralph L. Archbold, 1195 E. 146th St., Cleveland, Ohio.</p> <p>W8SSX George Weinrich, 306 W. McClellan, Flint, Mich.</p> <p>W8SSY Corby Stone, 518 Rawlins St., Port Huron, Mich.</p> <p>W8SSZ Kenneth Huggett, 22 Reading Ave., Hillsdale, Mich.</p> <p>W8STA Herbert F. Keith, Wanakena, N. Y.</p> <p>W8STB Ralph F. Studt, 4927 Dearborn St., Pittsburgh, Pa.</p> <p>W8STC Windsor F. Hemenway, 130 N. Erie, Mercer, Pa.</p> <p>W9AAP Jesse W. Foster, 6834 Roberts, University City, St. Louis, Mo.</p> <p>W9BMY James W. Justice, 5803 A Michigan, St. Louis, Mo.</p> <p>W9EBD Elliot D. Full, 529 Hawthorne Lane, Winnetka, Ill.</p> <p>W9ESB Homer C. Cutler, 818 S. Marion St., Carbondale, Ill.</p> <p>W9JPF Charles F. Pippen, 15 W. 12th St., Anderson, Ind.</p> <p>W9JZH Clifford E. Johnson, 1409 5th Ave., Des Moines, Ia.</p> <p>W9NOQ Carl M. Leidholdt, Trustee, Chippewa Q.R.R. Club, 10 1/2 Jefferson Ave., Chippewa Falls, Wisc.</p> <p>W9NPK Anthony T. Maruca, 4827 18th Ave., Kenosha, Wisc.</p> <p>W9NQU Roland R. Petersen, Iota 9&10, Block 3, Flaxton, N. Dak.</p> <p>W9NRC Vernon E. Rardin, 212 Lombard Ave., Muscatine, Iowa.</p> <p>W9NRL H. Louis Robinson, 1306 Waverly Ave., Kansas City, Kans.</p> <p>W9NVU Robert H. Oberman, 1303 San Pedro, Trinidad, Colo.</p> <p>W9NWX Clarence Rasmussen, 656 Utica St., Waukegan, Ill.</p> <p>W9NXB Peter P. Viezbicke, 111 11th St., So., Virginia, Minnesota.</p> <p>W9OAV Robert Wm. Yeager, 30 N. 3rd St., Madison, Wisc.</p> <p>W9OBP Edwin P. Westbrook, N. W. corner 2nd S & Swift Sts., Winnebago, Ill.</p> <p>W9OBZ Chester D. Walters, 701 Prospect Ave., Wausau, Wisc.</p> <p>W9OCF Cyril Strehlon, 499 Grotto, St. Paul, Minn.</p> <p>W9ODC Robert J. Spellman, 2586 Crown Point, Omaha, Nebr.</p> <p>W9ODM Bennett L. Jackson, C.C.C. Co. 3541 Camp S.C.S. 5, Walton, Ky.</p> <p>W9O EZ George Zurian, 13641 Chatham St., Blue Island, Ill.</p> <p>W9OGR Clifford F. Susag, 415 7th Ave., East Alexandria, Minn.</p> <p>W9OPX Helen M. Kolar, 59th & Marion, R.F.D. No. 2, Downers Grove, Ill.</p> <p>W9OQZ Wm. C. Haggard, Jr., 1605 Joesting, Alton, Ill.</p> |
|---|--|

*Freeman Gosden (W6QUT) is known to millions of radio listeners as the "Amos" of "Amos 'n' Andy".

CORRECTION NOTICE

The call of F. V. Frost, 4548 47th Ave., Seattle, Wash., was incorrectly given as W7HCO in the March issue of R & T. Mr. Frost's call should have been listed as W7HCU.



NEW EDITION OF THE
Greatest Catalog in Radio
BIGGER THAN EVER!

— it's brand new!

Completely revised and enlarged Spring edition of the greatest catalog in radio—out now. Send for your copy at once. It's FREE! Tear off coupon below and mail.

NEW P.A.
with more SELL!



With this issue Lafayette announces a great new line of sound systems for 1939. Here is revolutionary P.A.—new in smoother, finer performance, new in streamlined styling, new in operating economy. And for the first time, 3 distinct lines for you to choose from—Economy, Standard and DeLuxe. Truly Lafayette can offer this year a sound system for every purse and purpose. Complete range in all three lines from 5 to 70 watts. If you sell or rent sound systems, or if you've ever considered this highly profitable field, be sure to see what Lafayette has for '39. Send for FREE catalog today.



Hams—FOR YOU
there's a section packed solid with up-to-the-minute gear at down-to-earth prices. Plus the scoop of the year—Frank Lester's revolutionary new 5-10 converter. Tear off coupon and mail at once.

IN ADDITION—60 stunning new radio models, kits, parts, tubes. Mail the coupon. **YOUR FREE COPY IS WAITING!**

LAFAYETTE RADIO CORP.
AND **WHOLESALE RADIO SERVICE CO. INC.**
NEW YORK, N. Y. • CHICAGO, ILL. • ATLANTA, GA.
100 SIXTH AVENUE • 901 W. JACKSON BLVD. • 265 PEACHTREE ST.
BOSTON, MASS. • BRONX, N. Y. • NEWARK, N. J. • JAMAICA, L. I.

Rush New FREE Radio Catalog No. 76.

Name..... PLEASE PRINT

Address.....

City.....State.....

LAFAYETTE RADIO CORP.
Dept. 4D9—100 Sixth Ave., New York, N. Y.

PASTE COUPON ON PENNY POSTCARD

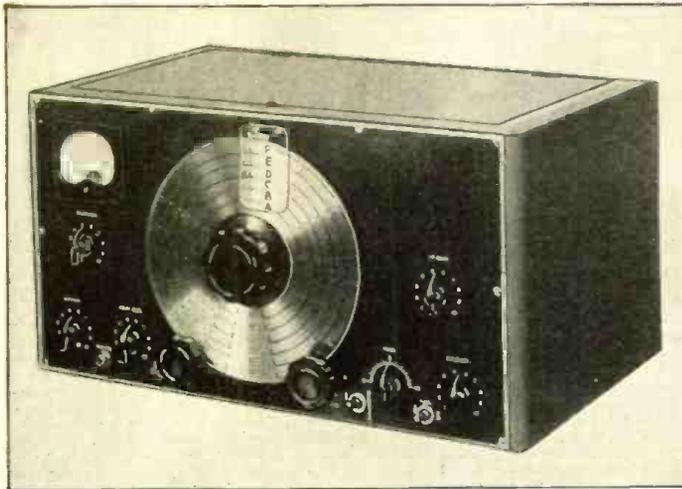


Fig. 1. Panel view of the new Silver Super. Complete control of all functions is provided.

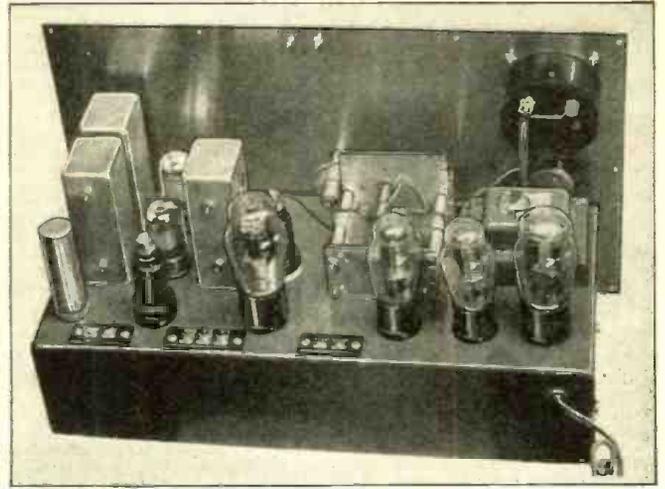


Fig. 2. Top of Chassis. Points to note include attractive layout and geared tuner.

A New Type of COMMUNICATIONS Receiver

McMurdo Silver

Built from standard parts, or wired from a factory-assembled kit, this receiver introduces many new features.

● THIS new communications receiver follows closely the designs prescribed by the A.R.R.L. as the means of providing the maximum of results at a minimum cost. It goes considerably beyond these earlier designs in that it includes a new *noise limiter* which is as effective as it is simple, covers the full range of 5 through 550 meters with sensitivity of about 1 microvolt absolute throughout, has the highest signal-to-noise ratio of any receiver the writer has ever operated, is completely free of "warm-up" drift, is both "portable" (battery operated) and "permanent" (A.C. operated) in the same unit, can be expanded into anti-fading dual-diversity reception at no increase in size, yet can be built to "battleship" ruggedness by even a novice to use from three to eight tubes with maximum complete chassis cost below \$50.00. Capable of being built from standard parts, it is also available as a completely assembled 8 tube kit, requiring only a couple of hours to wire and test. It can be aligned and tested without any service gear whatsoever, although a test oscillator (borrowable from, or usable at


any local service shop) makes the task most easy and sure-fire.

When this receiver also has A.V.C., six low-C tuning bands, uses the newest all-glass "Loctal" tubes, has nearly twenty-two inches of effective dial length per band readable to one part in 5000—which can be stretched to eleven feet per band at slight extra cost—selectivity continuously variable from 12 kc. "high-fidelity" right up to sharper than the 1 kc. necessary to single-signal c.w. reception, 4.25 watts undistorted power output, and appearance and controllability which are outstanding even among very expensive communications receivers, it comes close to being the ideal. Yet this is what numerous Chicago amateurs, young and old, who have tested the new "Silver Super," have found it to be.

Regeneration Put to Work

All of this is made possible through regeneration, amazingly neglected considering its tremendous benefits by factory-built (Continued on page 749)

Fig. 3. Wiring diagram of Silver Super. It can also be assembled as a "3-tube set", as described herewith.

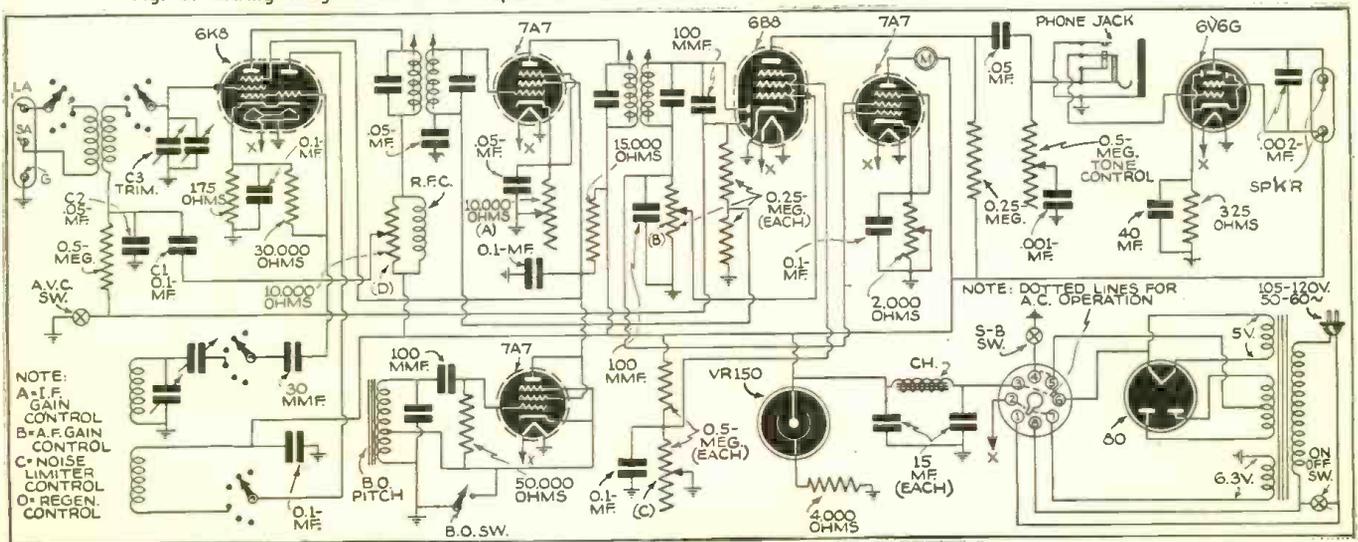

All-Wave 8-Tube Receiver

(Continued from page 737)

half of the tube acts as an automatic noise-limiter of the modified Dickert type. This type of noise limiting is very effective on noise pulses whose amplitude is greater than the desired carrier signal. Two degrees of noise limiting have been made available; one for use in copying cw (telegraph) signals and the other for listening to phone signals. This is switched in automatically when operating the combination AVC-BFO switch, about which more later.

1 Tube Acts as 1st Audio and B.O.

A 6C8G dual triode is used as a first audio stage and as a beat oscillator to enable the listener to copy cw telegraph signals and to facilitate locating weak dx stations. The BFO transformer comes complete with a built-in grid condenser and resistor. The condenser shown coupling the plate of the BFO half of the 6C8G to the plate of the 6H6 detector is made by merely wrapping about five or six turns of hookup wire around the lead running from the r.f. transformer to the 6H6 plate.

Getting back to the rather unusual method of AVC-BFO switching: a single 4-pole, 3-position rotary switch is used for controlling all the various features of the receiver. The 110 volt A.C., the AVC, BFO, and the degree of noise suppression. As the diagram shows, in position 1 the receiver is disconnected from the 110 volt line; in position 2 the set is connected to the line, AVC is switched in, BFO switched off and the noise-limiter adjusted for action on voice signals. In position 3 the AVC is cut off, the BFO turned on and the noise-limiter adjusted for its greater limiting action for use on cw (telegraph) signals.

Head-Phone and Phono Jacks Provided

The 15,000 ohm potentiometer simultaneously controls the gain of the 18S3 and the 6S7 tubes, providing effective control against overloading the detector by any strong "local" signals. A phono jack has been incorporated so that the audio section of the receiver can be used with a phonograph pickup. A half megohm "pot." permits complete variation of audio power.

When a pickup is plugged into the phono jack, the R.F. section is automatically disconnected from the audio. Another jack located on the rear of the chassis permits the listener to use headphones. The 6V6 audio power tube is automatically disconnected when listening-in with phones.

The r.f. transformers are of a rather unconventional type. Instead of the trimmer condensers being adjustable, the transformers have fixed condensers and adjustable inductance coils. This is an extremely valuable feature for the ordinary type of adjustable mica trimmer varies in capacity with temperature, humidity and vibration. By varying the position of the Poliron cores in the coils, the inductance is adjusted to the proper value and, once set, the r.f.'s will remain permanently aligned.

Switch Coil Assembly

All the r.f. coils, mounted on a six gang, 5-band switch, are adjusted to exactly the proper value of inductance at the factory and the trimmer condensers are adjusted for correct "tracking" in the receiver. However, a little readjustment will be necessary in the individual receiver. Although complete coil information is given in the chart, it is inadvisable for the constructor to attempt to make these coils himself, because of the great difficulty in getting the coils for each band to have the proper inductance to "track" properly. So the purchase of the complete coil assembly is strongly advised. Incidentally, the small variable trimmer condensers shown in the diagram across each coil are of 12 mmf. maximum value. Between the antenna and r.f. sections and between the r.f. and oscillator coil sections a metal shield is placed.

Aligning the Receiver

Lining-up the receiver is not particularly difficult, even without a signal generator. First, the two r.f. transformers must be aligned to 456 kc. Without touching any of the trimmers on the r.f. coil assembly, tune in a station emitting a signal of approximately constant amplitude; an aviation

(Continued on following page)

COIL CHART

Band	Antenna	Detector	Oscillator
13.5-42.5 mc. (22.2 to 7 meters)	None	3 1/2 t. No. 14 spaced to 1/2" length on 3/8" dia. (air wound) 1 turns	grid coil 3 1/2 t. No. 14 spaced to 7/16" plate coil 4 turns No. 36 SSE interwound with grid coil coils 1/2" dia.
5.85-18.2 mc. (51 to 16.4 meters)	prim. 3 1/2 t. No. 36 DSC interwound at ground end of sec. secondary 10 1/2 turns No. 18 spaced 3/4" 3/4" diam. form.	sec. 10 1/2 t. No. 18 spaced to 3/8" prim. 7 1/2 t. No. 36 DSC interwound at ground end of secondary 3/4" dia. form	grid coil 10 1/2 t. No. 18 spaced to 3/4" plate coil 6 turns No. 36 DSC at grid end of grid coil
1.74-6.45 mc. (172 to 46.48 meters)	prim. 10 1/2 t. No. 36 SSE sec. 3 1/2 t. No. 28 both coils close wound and separated by 3/8" wound on 3/4" dia.	prim. 15 1/2 t. No. 36 SSE sec. 3 1/2 t. No. 28 enamel 3/4" dia. form	grid coil 30 1/2 t. No. 28 enamel plate coil 10 1/2 t. No. 36 SSE both close wound 3/4" dia. form
530-1800 kc. (565 to 166.6 meters)	prim. 254t No. 38 SSE sec. 91 t. 3 5/44 SSE universal wound on 3/4" dia. form	prim. 528 t. No. 38 SSE sec. 93 t. No. 3 5/44 SSE coils spaced 3/16" wound on 3/4" dia. form	grid 62 t. No. 32 SSE 3/32" wide plate 30 t. No. 32 SSE 3/32" wide both coils close together universal wound on 3/4" dia.
132-405 kc. (2306 to 740 meters)	sec. 492 t. No. 3-41 * SSE prim. 715 t. No. 38 SSE each coil 3/4" wide wound on 1/2" dia form universal wound	prim. 1305 t. No. 38 SSE 3/16" wide sec. 492 t. No. 3-41 SSE 3/4" wide coils spaced 5/16" apart universal wound on 1/2" dia.	grid 217 t. No. 32 SSE 3/16" wide plate 69 t. No. 32 SSE 3/16" wide coils close together universal wound on 1/2" dia.

NOTE: No. 3-41 SSE and 3 5/44 SSE wire is Litz (stranded) wire.



RESISTANCE ANALYZER and INDICATOR

FOR USE WHEREVER RESISTANCE MEASUREMENTS ARE MADE

An indispensable radio instrument for every ham, serviceman and experimenter. Fuse protected, fool-proof, guaranteed. Dozens of uses. Determines resistance values; estimates tapers and values of controls; serves as voltmeter multiplier, rheostat or potentiometer; voltage divider; calibrated gain control or attenuator, etc., etc. Direct reading dial. Only 1 knob adjusts resistance from 0 to 1.0 megohm. Bakelite case 4 1/4" x 3 1/4". Three fuses. Interesting 16-page instruction manual supplied with each Analyzer.

Net Price (complete) . . . \$4.95



All Metal
11" long x
5 1/2" deep x
5 1/2" high

RADIO'S HANDIEST PARTS CABINET

This new All-Metal IRC RESIST-O-CABINET contains the first really balanced resistor assortment. Supplied complete with 59 famous IRC Resistors in practically every type and range commonly used in service work. You pay only the standard prices for the resistors. The cabinet is yours at not one cent of extra cost. The 59 resistors include popular ranges in 1/2- and 1-watt Insulated Metallized Resistors; also 10-watt fixed and adjustable wire wounds, the latter giving every range from a few ohms up to 10,000 ohms. Cabinet contains four large drawers with seven compartments in each. Designed to stack solidly, one atop the other.

List Value of Resistors \$15.16 (The Cabinet is included)

NOTE: Resist-O-Cabinet not sold empty.

INTERNATIONAL RESISTANCE CO.

401 N. Broad St., Phila., Pa.



By the makers of
INSULATED Metallized RESISTORS

STANDARD OF QUALITY EVERYWHERE

HOWARD

presents

DX ON 10 METERS

with

ELECTRIC BAND SPREAD



THE SCOOP
of the
NATIONAL
A.R.R.L.
CONVENTION

29.95
NET

*Here's the greatest value in the communication field for only \$29.95. A hand-built Howard with the custom-parts, fine engineering and spectacular performance features of communications receivers selling for twice the price or more. Check these outstanding features; 4 Band—broadcast to 10 meters inclusive, Ceramic Coils, Iron Core I.F. Transformers, Electrical Band Spread, Excellent 10 Meter performance and eleven additional communications features.

How Can We Do It?

Participating in volume buying on Howard Household Receivers—making more of our own parts than competitors.

Send (on coupon) for complete technical information and name of the nearest jobber where set may be inspected.

*Pacific Coast and export prices slightly higher.

AMERICA'S OLDEST RADIO MANUFACTURER

FREE For Complete Technical Details Send this Coupon

HOWARD RADIO COMPANY
1735 BELMONT AVE., CHICAGO, ILL.

Gentlemen: () Send me Booklet No. 430.
() I desire a demonstration.

My name is

Address

City State

All-Wave 8-Tube Receiver

(Continued from preceding page)

beacon station is ideal. Then merely adjust the i.f. coils until the signal is at a maximum. To line up the front-end of the set, start with the lowest frequency band. Tune in a signal at the high frequency end of the band, preferably a signal of known frequency, and adjust the oscillator alignaire (trimmer) so that the frequency of the signal corresponds to the frequency printed on the dial scale. Adjust the antenna and detector coil trimmers for maximum response. Then tune in a signal at the low frequency end of the band and adjust the oscillator padding condenser while rocking the tuning condenser to obtain maximum response. The oscillator padder is the condenser in series with each oscillator coil. The above procedure should be repeated for each band. On the highest frequency band there are no aligning or padding condensers, the coils being adjusted by spacing the end turn to give the desired amount of inductance for tracking.

Parts List

INTERNATIONAL RESISTANCE CO.


- 1—15,000 ohm potentiometer, type 14-118
- 1—500,000 ohm potentiometer, type 11-133
- 3—500,000 ohm, 1/2 watt BT 1/2
- 5—100,000 ohm, 1/2 watt BT 1/2
- 3—75,000 ohm, 1/2 watt BT 1/2
- 4—30,000 ohm, 1/2 watt BT 1/2
- 3—2,000 ohm, 1/2 watt BT 1/2
- 1—1,500 ohm, 1/2 watt BT 1/2
- 1—235 ohm, 10 watt type AB
- 1—3,500 ohms, 20 watts
- 1—15,000 ohm, 20 watts
- 2—300 ohm, 1/2 watt BT 1/2
- 1—150 ohm, 1/2 watt BT 1/2
- 1—50 ohm, 1/2 watt BT 1/2

RCA RADIOTRONS

- 1—1853
- 1—6K8
- 1—6S7
- 1—6H6
- 1—6C8G
- 1—6V6
- 1—5Z4
- 1—6U5

SPRAGUE PRODUCTS COMPANY

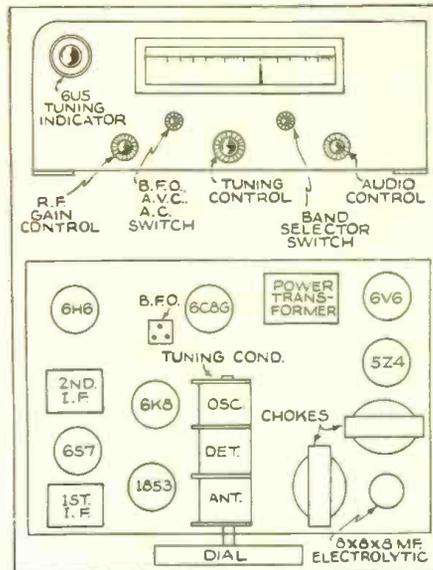- 10—.1 mf. 600 volt paper condensers type TC-1
- 1—.05 mf. 600 volt TC-15
- 1—.5 mf. 600 volt TC-5
- 1—8 x 8 x 8 mf. electrolytic PLS-888
- 1—5 mf. 50 volt electrolytic TA-55
- 1—5 mf. 25 volt electrolytic HC-5
- 1—1 mf. 450 volt electrolytic RE-1
- 1—.0001 mf. mica 1FM-31
- 1—.00005 mf. mica 1FM-45



Layout of panel and sub-base.

MEISSNER COMPANY

- 1—All-wave coil assembly 13-7600
- 1—3 gang tuning condenser 410 mmf. No. 21-5141B
- 1—9" Slide-Rule dial with brackets No. 23-8206
- 1—Standard chassis No. 11-8226
- 1—Panel No. 11-8221
- 1—Cabinet No. 11-8221
- 4—Ceramic octal sockets No. 25-8437
- 3—Bakelite octal sockets No. 25-8209
- 4—1 1/2" knobs No. 25-8224
- 1—1 1/2" knob No. 25-8225
- 1—Magic eye socket assembly No. 19285

ALADDIN RADIO INDUSTRIES

- 1—465 kc. I.F. transformer type P-101
- 1—465 kc. I.F. transformer type P-200
- 1—BFO transformer, 465 kc. type C-350

CINAUDAGRAPH CORPORATION

- 1—10" P.M. speaker type NZ10-10 (with 5000 ohm output transformer)

P. R. MALLORY

- 1—4-pole, 3-position rotary switch shorting type No. 3143
- 1—2 circuit midget jack type A-2A
- 1—2 circuit jack type No. 15

JEFFERSON TRANSFORMER CO.

- 1—350-350 volt transformer No. 463-431
- 2—10 henry 100 ma. chokes No. 466-410

I COVER THE PACIFIC COAST!

This column has been added as a new service to readers of RADIO & TELEVISION. Cooperation of Pacific coast listeners and any reports of reception will be greatly appreciated. Please address any reports or other correspondence to Lyle M. Nelson, RADIO & TELEVISION, 99 Hudson Street, New York, N. Y.

(All time is Pacific Standard)

● INCREASED activity among short-wave stations in the far East has been reported from all parts of the Pacific Coast during the last few months. Stations in Asia and Oceania have always, particularly during this time of the year, occupied the major part of Pacific Coast pxing.

A New Zealand station has been reported testing on 6.95 mc. by many listeners. According to these reports the call letters are ZL2ZB and the address is announced as: Hope Gibbons Building, Dixon Street, Wellington, C1. New Zealand. The station is heard in the early morning hours with best reception near 3 a.m.

According to W. T. Choppen of Timaru, New Zealand, new transmitters to be installed at Wellington will be ZLT1 on 6.085 mc., ZLT2 on 9.54 mc., ZLT3 on 11.78 mc., ZLT4 on 15.28 mc., ZLT5 on 17.77 mc., and ZLT6 on 25.91 mc.

The mysterious Chinese station on 11.40 has finally been identified as XGRV of Chungking. This popular broadcaster is very well received every morning from 4 to 4:30 and sometimes later.

Two other new Chinese stations to appear on the air during the last month are XGXA on 6.98 mc. and XGXB (possibly XGXC) on 7.02 mc. Both stations come through to the Pacific Coast with good volume. XGXA is on the air from 6 to 7:20 a.m. daily. Occasionally it has been reported as early as 4 a.m. XGXB (or G), although heard very well, is rather irregular in schedule. It can usually be picked up in the mornings from 5 to 7.

Portable transmitters located somewhere in the jungles of Belgian Congo and New Guinea have been reported on the 20 meter amateur band during the mornings and late evenings by George Goehring of Oakland, California.

A new station in Siam has been putting a fair signal through to the coast. The station works on 6.11 mc. from 5:10 to 7 a.m. on Wednesday. It has also been reported broadcasting irregularly on other weekdays. According to word from Siam the call of HS8PJ has been changed to HS6PJ.

Application has been made by "Radio Burma" of Rangoon for permission to use the call letters XYZ and XZZ on 6.012 and 3.79 mcs., according to John Cavanaugh of Oregon City. The latest schedule for "Radio Burma" is from 2:45 to 5:30 a.m. and from 5:30 to 7 p.m. with best reception during the morning broadcast, he reports.


Station RV15 of Khabarovsk, U.S.S.R., is back on 4.27 mcs. after various reports had placed it on 6.05 and 6.82 mcs. Latest developments seem to indicate that the stations heard on the latter frequencies were new stations and not RV15 as believed.

ROUND 'N' ABOUT—from listeners' reports. VPD of Suva has added a number of new frequencies. It can now operate on 15.16, 11.89 and 6.13 mcs. with a power up to 10,000 watts. . . . "Radio Hanoi" is using additional frequency of 11.91 mc. from 10 p.m. to 4 a.m. Station still very weak on 9.51 mc. . . . New station TAQ of Ankara, Turkey, coming through weakly on 15.20 mc. from 2:30 to 4 p.m. . . . New TAP on 9.465 also reported on the air during afternoons. . . . Prague is now on 11.84 mc. from 4 p.m. to 6:15 with good volume. . . . New Spanish Loyalist station "Radio Norte," EA4RM, on 9.49 after 6 p.m. with weak signal on coast. ZBW on 9.53 mc. is still very well received from 5 to 7 a.m. . . . PCJ coming through very well on 9.59 mc. during evenings.

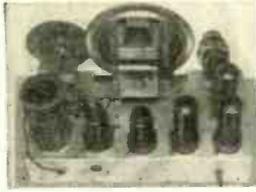H. G. CISIN'S FAMOUS KITS

1939 Senior Metal Tube SPACE EXPLORER

All-Wave All Electric Beam Power 5 Tube Communications Receiver



SEVEN NON-SKIP OVERLAPPING BANDS—Four 2000 meters. Professional Band Spread. Beam Power. Communications Set.

POWERFUL SENSITIVE, SELECTIVE—Ultra-Modern Features include Beam Power Output, Built-in Full Toned Electro-Dynamic Speaker, Patented Cisin A.C. P.C. Circuit, Low-loss Air Dielectric

Band Spread on all bands. Self-Contained Power Supply Precision Filtered to eliminate hum. Full Vision Dial. Antenna Control. Headphone Jack. Dual Regeneration Control. Beam Power tube furnishes over 2 watts undistorted power to dynamic speaker giving Full Loud Speaker Volume. Studio Tone Quality, stunning drilled metal chassis. Verified foreign reception reported by many owners. Gives professional results, but plans are so clear anyone, even a novice, can build this set successfully.

Uses 100% Metal Tubes rather than low-priced "type" type tubes in carefully engineered circuit as follows: one metal tube 6J7, one metal tube 6C3, one metal tube 25L6, one metal tube 25Z6, one metal tube K-55-A, as tuned screen grid pentode regenerative detector, powerful 1st audio amplifier, 2nd audio two-watt Beam Power Output, Half-wave rectifier and automatic ballast stage.

Complete Senior Space Explorer Kit of all chassis parts, Power Supply and clear, simplified wiring diagram (unwired, less tubes, coils and speaker) \$5.95
Five Matched Metal Tubes \$2.75; Four S.W. Coils \$1.40 to 200 meters \$1.20; Two B'cast Coils 200 to 625 m. \$1.20; Long Wave Coil 550 to 2000 meters \$1.20; Full Toned Dynamic Speaker \$1.95; Attractive two-toned wood cabinet \$1.50; Wired and tested \$2.25 extra. Shipping weight 7 lbs. Send stamp for Circular. 25% deposit on all C.O.D. orders.

SPECIAL—Senior Space Explorer, Complete Assembled, Wired, Factory-tuned Chassis, with all coils \$1.40 to 625 meters, set of matched metal tubes, built-in dynamic speaker, ready to use \$15.35

'39 JR. SPACE EXPLORER 4-TUBE RECEIVER



SEVEN BANDS—10 to 2000 meters. Junior Band Spread Professional Communications Set.

MODERN, SENSITIVE AND SELECTIVE! Ample Volume. Reception from as many as 39 foreign stations in a single evening reported and verified by many owners.

Uses one 6C6, one 70, one 12A7 (Twin-Tube) and one metal K-105-A; as tuned screen grid regenerative detector, powerful two-stage pentode audio amplifier, half-wave rectifier and automatic ballast stage. Self-contained power supply operates on 105-120 volts any frequency A.C. or D.C. interchangeably. Built-in Chromatic Speaker, phone jack, antenna control, full vision dial, hand spread variable dual regeneration control, sturdy drilled metal chassis. Clear explanatory diagram simplifies wiring. Ideal for the beginner.

COMPLETE JUNIOR SPACE EXPLORER KIT \$4.95 or all chassis parts, Power Supply and Dia. (unwired, less tubes, coils and speaker)

Four Matched Tubes \$2.45; Four Short Wave Coils 10 to 200 m. \$1.20; Two B'cast Coils 200 to 600 meters \$1.20; Long Wave Coil 550 to 2000 meters \$1.20; Tru-Fidelity Chromatic Magnetic Speaker \$1.45; Tru-Fidelity Chromatic P.M. Dynamic Speaker \$1.95; Attractive Two-toned Wood Cabinet \$1.50; Wired and factory tested \$2 extra. Shipping Weight 6 lbs. No circulars available on this model.

SPECIAL—Junior Space Explorer, Complete Assembled, Wired, Factory-tuned Chassis, with all coils 10 to 2000 meters, set of matched tubes, built-in Tru-Fidelity Chromatic P.M. Dynamic Speaker, ready to use \$13.95

H. G. CISIN'S All-Wave Air Scout Jr. THREE-TUBE All Electric All Wave Model 3AE Receiver

A powerful sensitive all-wave set. Holds wonderful records for foreign reception. Also brings in police calls, amateur, eedc. Transatlantic phone and broadcast entertainment. Excellent volume. Works from any A.C. or D.C. house current. Easiest set to build. Employs newest metal ballast tube as one of the tubes. Speaker mounts on attractive panel. Range 9.5 to 610 meters or to 1500 meters with special long wave coil. Complete Kit includes: Carbon 50c. Antenna Kit, 10 to 200 meter coil. Panel, Chassis, High Grade Variable Condenser, Potentiometer, Antenna Trimmer, Dial, Sockets, Knobs, Wire, Resistors, Condensers, and all other required parts including instructions and diagram. **\$3.20** With Phone (Less 25cmm. ONLY) tubes, unwired)

Following Auxiliary Parts are available: 9 1/2 to 20 meter coil (foreign) 25c; 15 to 45 meter coil (foreign) 25c; 40 to 80 meter coil (foreign) 25c; 5' Fine-tune Loud Speaker \$1.20; Complete Antenna Kit 50c; Wood Screw Kit 10c. Tubes for Model 3AE each. 40c. Long Wave Unit and coil \$1. Double Earphones \$1.50. Bandspread Attachment 75c. Air Scout Jr. model 3AE wired extra \$1.00. NOTE: If you already have earphones, two extra foreign coils may be substituted in model 3AE.

H. G. CISIN, CHIEF ENGINEER Allied Engineering Institute, Dept. S-54 98 Park Place, New York, N. Y.

This Universal Test Meter

(Continued from preceding page)

quently the point at which this voltage is measured also contains direct current, it is necessary to use a .5 mf. condenser to block out the d.c. component. The SPST jack switch shorts out this condenser for all measurements except for output measurements.

DECIBELS—It is not generally known that a decibel meter is merely an A.C. voltmeter. A chart has been prepared which can be fastened inside the meter case cover and which gives the number of decibels corresponding to the A.C. voltage measured across a 500 ohm line. For measurements across any other impedance line use the following formula:—

$$DB = 10 \log \frac{E^2}{R}$$

E=Measured A.C. voltage

R=Line impedance

$$\text{Also WATTS} = \frac{E^2}{R}$$

Parts List

INTERNATIONAL RESISTANCE CO.
1 each—20,000, 80,000, 400,000, 500,000 ohms—type WW-4
1—1 meg., type WW-2
2—1.5 meg., type WW-2
1 each—600 ohms, 8000 ohms, 20,000 ohms, 25,000 ohms. 1/2 watt, type BT-1/2

TRIPLET ELECTRICAL INSTRUMENT CO.
1—500 microampere 4" meter, type 421
1 each following slunts—1 ma., 5 ma., 10 ma., 250 ma.
2—50 ma. shunts
1—Full-wave meter rectifier, type C-4

P. R. MALLORY & COMPANY
1—1000 ohm potentiometer, type C1MP
1—Special 2-pole, 24-point tap switch No. 13124
1—S.P.S.T. jack switch, type No. 10
1—3-pole, 2-throw jack switch, type 763
1—Pair (1 black and 1 red) insulated tip jacks, type No. 523

CUSTOM AUTO TRUNK CO.
1—Special meter cabinet

MISCELLANEOUS
1—5" x 8 1/2" bakelite panel
1—4.5 volt battery
(Engraving optional). Lines can be scratched in bakelite and filled with China white.

More About Frequency Modulation

(Continued from page 721)

conditions, frequency modulation is the only system which is worthy of consideration."

Some of the critics of the new Armstrong modulation system have stated that ordinary transmission by amplitude modulation on the ultra short waves is so static and noise-free that it compares favorably with the Armstrong method, but in a recent letter to the *New York Times*, Major Armstrong challenges his critics to state (or to demonstrate) how they can produce the static and noise-free transmission with their system comparable to that obtained by his frequency modulation method.

Through the courtesy of the General Electric Company, we present herewith the wiring diagram and receiving antenna data on the new 12-tube frequency modulation receiver.

(Experimenters might try connecting a high frequency T.R.F. or other type R.F. receiving unit ahead of the second detector, instead of the superhet line-up shown in the standard diagram, incorporating of course the demodulator tube shown in the present diagram. In any event, it is highly important that the various stages be properly "lined up" with an oscillograph, if possible, as otherwise there is likely to be quite an amount of distortion.—Editor.)

The Model GM-125 receiver is a de luxe instrument designed solely for the purpose of receiving and reproducing programs transmitted by the frequency modulation system. By special electrical and acoustic treatment, this receiver will reproduce program material with the exceptionally realistic fidelity that is characteristic of this method of transmission and reception.

Antenna and Ground

Since this receiver operates at a relatively high radio frequency, it is very essential to construct a good antenna and ground system in order to obtain maximum results.

For distances up to within thirty miles from the transmitter, a simple horizontal di-pole as shown in Fig. 1 should give excellent results. It should be located free from all obstructions and placed as high from the earth as possible. Make sure it is run approximately at right-angles to the direction of the transmitter; i.e., if the transmitter is located due west, run the horizontal doublet in a north and south direction. The horizontal flat top has an effective antenna length of 10 feet 8 inches and consists of No. 12 or No. 14 bare copper wire (preferably stranded), cut in the middle and the two halves insulated by glass insulators. A twisted lead-in wire is then soldered to each side of the doublet as shown, and the other two ends of the transmission line are connected to the No. 1 and No. 2 terminals on the receiver chassis. The lead-in transmission line may be of any length up to 100 feet and should consist of low loss antenna lead-in wire. A good ground connection to a water pipe is connected to the terminal marked "G."

Somewhat better results may be obtained by constructing the antenna shown in Fig. 2. This varies somewhat from the di-pole antenna and is more efficient due to the fact that the transmission line has very little loss.

The antenna proper consists of a 10 foot 8 inch length of 1 inch diameter copper pipe supported at the middle by a pole lo-

Tube Voltage Table

Tube	Application	Plate to Gnd Volts	Screen to Gnd Volts	Cathode to Gnd Volts	Cathode Cur. MA	Filament Volts
6SK7	RF	240	90	0	7.5	6.4
6K8	Conv.	238	90	0	8.0	6.4
	Osc.	188				
6SK7	1st IF	238	90	0	8.1	6.4
6SK7	2nd IF	230	83	0	6.1	6.4
6SK7	3rd IF	225	83	2.9	6.1	6.4
6S17	4th IF	65	65	0	7.2	6.4
6Q7G	1st Audio	65	—	—	—	6.4
6J5G	Inverter	48	—	1.7	2.0	6.4
(2) 6L6G	Output	267	285	—	112	6.4
5U4G	Rectifier	350/350	—	—	180	50

RMS
Line Voltage—120

No signal input

cated as high above the ground as possible. The transmission line is made up of two No. 12 or No. 14 copper wires, spaced about 2 inches apart and transposed every two or three feet. The antenna end of the transmission line is soldered 13½ inches each side of the center of the copper pipe and should form a triangle, 27 inches on all sides. As in the previous installation, the horizontal flat-top should run approximately at right-angles to the direction of the transmitter.

For greater distances, somewhat better results may be obtained by using a reflector in conjunction with the antenna described and shown in Fig. 2. A suggested system is to use a 1-inch diameter copper pipe similar to the antenna, running parallel to the regular antenna and located farthest from the direction of the received signal. Fig. 3 shows a diagram looking from top and dimensions should be followed very carefully. By experimenting, however, with the distance between reflector and antenna, improvement in the individual installation may be noted.

Note—The reflector is a floating copper bar and there are no external connections. Connect and install the regular antenna as shown in Fig. 2.

Operation

The receiver has three operating controls, as follows:

Volume Control and Power Switch.

The control marked volume (left-hand control) also actuates the power switch for the receiver. When the control is in the extreme counterclockwise position, the receiver power is off. From this position, slight rotation in the clockwise direction will turn the receiver on and the volume will be at a minimum setting. Further clockwise rotation will increase volume until full output is attained.

Tone Control

This control (right-hand control) is continuously variable from bass to full-range to treble. The proper setting depends largely upon the tone most pleasing to the listener and upon the type of program being received.

Tuning Control

The tuning control is the large drum located above the volume and tone control knobs. To tune the receiver merely rotate the drum dial with the thumb. The scale is calibrated in megacycles so as to approximately locate the desired station.

When a station is located, a final adjustment is made by leaving the drum dial set at the point of minimum noise background. This point of exact tune is very important as it is only when the receiver is tuned to the position that the full, rich tones are available.

Circuit Alignment

I.F. Amplifier

Due to the good stability of components and the wide band characteristics of this amplifier, alignment should be unnecessary under normal operating conditions. Should it become imperative that an I.F. alignment is desirable, it will be necessary to use a cathode ray oscilloscope in conjunction with a 3.0 megacycle signal generator with a superimposed ± 300 kc. sweep frequency. This generator may be built up by constructing an oscillator with the tank condenser semi-fixed and variable, the variable portion being designed to be rotated by a motor and of proper capacity to give ± 300 kc. variation of the 3.0 megacycle mid-frequency. Connect the vertical plates of the oscilloscope across the resistor R-15 of the 4th I.F. stage and align transformers T-7, T-6, T-5 and T-4 in a progressive step by step method.

YOUR QUESTIONS ANSWERED by

THORDARSON GUIDES

The way to Easier, more Efficient

- Transmitter Construction
- Amplifier Building
- Radio Servicing

Thordarson engineers tell you how—simply, accurately. You benefit by their constant and up-to-date laboratory developments in these fields.

Transmitter Guide, No. 344—48 pages on transmitter design and operation—from portable and beginners models up to kilowatt rigs—fully described with circuit diagrams, parts lists and photographs.

Sound Amplifier Guide, No. 346—32 pages of value to every sound man. Circuits, constructional details and parts lists for amplifiers up to 120 watts output.

Radio Service Guide, No. 342—32 pages full of charts, tables and shortcuts, which are always useful; together with information on how to build a 32 volt power supply; an improved condenser analyzer and impedance bridge.

COMPLETE MANUAL

All three guides, plus the Thordarson Replacement Transformer Encyclopedia, No. 243; complete catalogs; and latest Thordarson bulletins are combined in an attractive loose-leaf binder—the *Thordarson Transformer Manual, No. 340*—price 50c (postpaid).



Get your copies today—
from your distributor or
from factory postpaid
at prices indicated. Ad-
dress Dept. RT. 94.

THORDARSON ELECTRIC MFG. CO.

500 W. HURON ST., CHICAGO, ILL.

Frequency Demodulator

With the same oscillator and sweep signal as used above, connect the vertical oscilloscope plates across the resistors, R-18 and R-19, then align the transformer T-8 for a cross-over curve as shown in Fig. 4. Proper alignment of trimmer C-51 is indicated when the curve crosses about mid-way in a vertical plane. Proper alignment of C-50 is indicated when the sides of the curve near cross-over are nearest to a straight line.

Note—Keep signal input high enough so that noise limiter is functioning. This point is indicated when an increase in signal input no longer changes the size of the curve.

R.F. Alignment

Make sure the last division on the low frequency end of the drum dial coincides with the escutcheon mark when the gang condenser is completely closed; then, proceed as follows:

1. Connect a high resistance 0-10 V. D.C. voltmeter across R-15.
2. Apply a 42.8 megacycle unmodulated signal to the antenna terminal board.
3. Set dial scale so it is tuned to 42.8 megacycle and peak oscillator trimmer C-4 for maximum voltage reading on the meter.
4. Peak the antenna (C-2) and R.F. (C-3) trimmers for maximum voltage output on meter.

Electrical Specifications

Volts	115-125
Frequency	50/60 Cycles
Watts Consumption	160
Tuning Frequency Range	37-44 mc.
	8.1-6.81 meters

Intermediate Frequency

Mid-frequency	3.0 M.C.
Band Width	300 K.C.

Electrical Power Output

Undistorted	12.0 Watts
Maximum	15.0 Watts



SILVER SUPER KIT

WE are proud to announce what we believe to be the first 100% communication receiver kit. Designed by McMurdo Silver, it incorporates and goes beyond the design principles laid down by the A.R.R.L. Handbook, QST and practically every technical magazine.

Fully assembled and with complete detailed instructions, it can be wired and tested by even the novice to produce the maximum of results for the very minimum of cost.

See it at your jobbers . . . or write Dept. RT 1 for full details of this and many other new items.



RADIO INSTRUCTION

YOU CAN BECOME A CODE EXPERT!

Learn the *Quick Candler Way!*

Candler doesn't care if you're just a beginner or if you've tried to develop your speed without success. If you follow the simple Candler System you will learn code right, with the correct fundamentals. It's a mental process; you must learn sound consciousness, and this Candler will teach you as he has taught thousands upon thousands of others, including such operators as T. R. McElroy, World's Champion and World's Record Holder.

In a short time after you've started Candler training you'll find yourself reading code as easily as you read the printed page, without strain or conscious effort. A few weeks of Candler training are equivalent to months of undirected practice. Write today for FREE "Book of Facts." Learn how the Candler system works. Read what highly paid commercial operators say about the Candler system. Send for your copy today!

CANDLER SYSTEM CO.

Box 331, Dept. S-4, Asheville, No. Carolina, U.S.A.
British Address: Rm. 56, Craven House
Kingsway, London, W.C.2



YOUR FUTURE IN

RADIO TELEVISION

● These growing industries need trained men for sales, service, operation. Your chance for employment and advancement depends on thorough training. National Schools offer you time-tested training. Complete, modern facilities and equipment in the largest trade school in the West. Est. 1905.

NATIONAL SCHOOLS

4000 S. Figueroa Street, Los Angeles

NATIONAL SCHOOLS, Dept. 4-RT, Los Angeles
Please send free Radio and Television Booklet.

NAME _____ AGE _____
ADDRESS _____
CITY _____ STATE _____

LEARN CODE RIGHT

Always ready—no weather interference—beats having someone send to you. Speed range 5 to 40 W.P.M. Radio or Morse. **STANDARD** with 10 tapes and book of instructions without oscillator \$20.25 **JUNIOR** with 5 tapes and book of instructions (not rented), without oscillator \$12.00 Complete oscillator equipment, less battery \$6.50 **RENTAL** Standard with 10 tapes and books of instructions \$3.00 first month, \$2.25 each additional month. With transformer and tube socket 25c per month more. With key and head phones \$0c per month extra. \$10 deposit or business references required. Write for details today.



INSTRUCTOGRAPH COMPANY
Dept. SW-4, 912 Lakeside Place, Chicago, Ill.
Representatives for Canada:
Radio College of Canada, 863 Bay St., Toronto

LEARN RADIO TELEVISION

500 LICENSED graduates placed in past 7 years in shipping, broadcasting, aviation, police, etc.; we also teach radio servicing and repairing; new beginners' class now forming; 62-page catalog free; oldest, largest and best equipped.

MASS. RADIO SCHOOL

18 BOYLSTON ST., BOSTON Est. 1899

RADIO ENGINEERING

broadcasting, aviation and police radio, servicing, marine radio telegraphy and telephony, Morse telegraphy and railway accounting taught thoroughly. 48 weeks' Engineering course equivalent to 3 years of college radio work. All expenses low. Catalog free. School established 1874.

Dodge's Institute, Turner St., Valparaiso, Ind.

The Radio Beginner

(Continued from page 724)

radio sets employing it are known as T.R.F. receivers. The action of such an amplifier is the same as the one already described. Plate current, flowing through the primary of the transformer, by magnetic action causes an alternating voltage to be placed on the grid of the following tube. In this instance, however, the secondary is tuned to resonance at the frequency desired by means of the variable condenser connected across it. Sometimes the primary is also tuned in this fashion. It should be observed in Figure 2 that use was made of *screen grid* tubes, in this way avoiding *feedback* through tube capacities, a situation difficult to overcome with the triodes shown in Figure 1, except through the use of an external *neutralizing* device.

In receivers employing R.F. amplification, the T.R.F. (tuned radio frequency) amplifier has found the widest application, but it should not be thought that the circuits described so far are the only ones in use.

Tuned Impedance R.F. Coupling

In the *tuned impedance coupled* R.F. amplifier, shown in Figure 3, we obtain a *voltage drop* across an impedance and apply the changes in voltage across this impedance to the grid of the next tube through a fixed condenser. The coupling device consists of a coil and condenser placed in parallel (or shunt) and inserted between the plate of the tube and the source of voltage; that is, in the plate circuit. In rotating the variable condenser, the coil-condenser combination is tuned to resonance with the frequency to be received, and in so doing offers the greatest possible impedance to that frequency. The plate current meeting this maximum impedance produces the highest possible voltage drop across the coil-condenser combination. The voltage changes are applied to the grid of the following tube by means of the fixed condenser connected to the impedance. The size of the coil and the capacity of the variable condenser are so chosen that they tune over the desired bands of frequencies. In a circuit of this type, difficulty is often experienced with feedback, since it cannot be controlled by neutralization. Resistors to control oscillation are placed in the positive voltage lead. Generally speaking, such R.F. amplifiers are seldom multiple staged, due to oscillation tendencies.

Resistance Coupling

Another type of amplifier is known as the *resistance coupled* R.F. amplifier, and is shown in Figure 4. This circuit is now seldom used for amplification before the detector stage, but has found wide use as an audio frequency amplifier and will be described in a future article on audio amplifiers.

Band Pass Filters

Sometimes certain undesirable effects known as *cross-modulation* and *second harmonic generation* are present in receivers. In order to avoid this effect, a *band pass filter* or *band selector* is used, as shown in Figure 5. The purpose of such a filter is simply to present a high impedance or resistance to all unwanted frequencies and at the same time allow the reception of those frequencies it is desired to receive. Since the *band-pass* filter couples the antenna to the grid of the first tube through a number of tuned circuits, a sufficiently high order of selectivity is obtained so that a strong signal, after passing through the filter, will not be strong enough to cause the R.F. tube to act as a detector.

RADIO INSTRUCTION

FASTEST WAY TO LEARN CODE

Easy, Fascinating, LEARN BY EAR
To Be a GOOD OP.

The New All Electric Master Teleplex Code Teaching Machine is exactly what thousands are looking for. No experience needed. Ideal for beginners—steps up WPM for ALL Ops. There is no guess work with Master Teleplex, because it records your sending in visible dots and dashes. You SEE and HEAR exactly how you are making your signals. You learn code the way you'll be using it—by SOUND. That's why practically every school teaching code uses TELEPLEX. Complete course included at no extra charge. Used by many schools for teaching code. Low cost; easy terms. MONEY BACK GUARANTEE. Send now for booklet S4, no obligation. Post card will do.



TELEPLEX CO.—67-69 PARK PLACE—NEW YORK
In Canada, Write
Canadian Electronic Inst., Toronto, Ont.

RADIO ENGINEERING

● Complete Radio Engineering Course in 96 weeks. Bachelor of Science Degree. Radio (television, talking pictures and the vast electronic field) offers unusual opportunities for trained radio engineers. Courses also in Civil, Electrical, Mechanical, Chemical, Aeronautical Engineering; Business Administration and Accounting. Tuition, living costs low. World famous for technical two-year courses. Special preparatory department for those who lack required high school work. Students from all parts of the world. Enter June, September, January, March. Write for catalog.

2449 COLLEGE AVE. ANGOLA, IND.

TRI-STATE COLLEGE

Insure your future!

You can train now for a better job in

PRACTICAL RADIO ENGINEERING

Always good jobs for good men . . .

● HERE is the opportunity for you to train yourself for a better Radio Job—at home in your SPARE TIME. CREI has trained hundreds of ambitious men for important positions in broadcasting, aviation, marine and police radio. Constant improvements demand better men for the important, high-paying jobs . . . and that means a better job for YOU—if you TRAIN NOW! Write for FREE BOOKLET!

CAPITOL RADIO ENGINEERING INSTITUTE

Dept. ST-4 3224-16th St. N.W., Wash., D. C.

RADIO ENGINEERING

RCA Institutes offer an intensive course of high standard embracing all phases of Radio and Television. Practical training with modern equipment at New York and Chicago schools. Also specialized courses and Home Study Courses under "No obligation" plan. Catalog Dept. SW-39.

RCA INSTITUTES, Inc.

A Radio Corporation of America Service
75 Varick St., New York, 1154 Merchandise Mart, Chicago

BE A RADIO SERVICE EXPERT

Modern receivers require men with modern training for service work. **LEARN AT HOME**
Our home instruction method and service equipment offer starts you earning money almost at once. Up to \$3 an hour easy in a short time. Write for free book.
Radio Training Ass'n of America
Dept. RT-94
4525 Ravenswood Ave., Chicago

AMATEUR RADIO LICENSES

Day and evening classes in code and theory
Home Study Courses

Hundreds of students now on the air. Results guaranteed. Reasonable, efficient and thorough.

AMERICAN RADIO INSTITUTE
1123 BROADWAY NEW YORK, N. Y.

New Type Communications Receiver

(Continued from page 742)

receivers, yet recommended in every receiver described in the *A.R.R.L. Handbook*. Originally advocated, it is believed, by the writer in 1932-33 as the easiest means in an I.F. amplifier of obtaining single-signal selectivity, its inclusion in first detector circuit also gives the high R.F. gain before frequency conversion, so essential to good signal-to-noise ratio, as well as tremendously increasing effective image frequency selectivity. In this particular design the I.F. regeneration knob is no more critical than any variable selectivity control—actually simpler to operate than usual crystal filter controls—while R.F. regeneration, once set, need never be touched again. Thus no criticism of possible complexity of operation in the hands of amateur or short-wave experimenter is justified, while the gain from the intelligent use of regeneration is amazing.

One particular advantage is the elimination of tubes which regeneration makes possible. This reduces cost and power drain, but even more important, cuts circuit noise to a surprisingly low minimum. Actually in the "Silver Super" inherent noise is only 2 milliwatts at 1 microvolt absolute sensitivity. In his experience of designing hun-

to the receiver. At the center is the 7 $\frac{3}{4}$ " dial, accurately calibrated for six wavebands from 540 to 61,000 kc., inclusive. It can be turned fast by its center knob, or at 15 to 1 reduction by the knob at its lower right. The outer edge of this dial carries 500 vernier divisions with 0-10 decimal indicator. Where greater band-spread is desired a simple 12:1 gear train can be slipped over the condenser shaft behind the panel, and projecting through a panel hole beneath the right center of the main dial, carries an 0-200 degree, 4" band-spread dial which then "peeks out" at the upper right of the main dial to be read against a second decimal vernier indicator to give eleven feet of dial length per hand with a readability of one part in 21,600.

Band-Switch

At the lower left of the dial is the wave-change knob operating four separate switches insulated with the new "X2B" beneath the chassis. These have double-spaced contacts spread over a full 360 degrees to give short connecting lead lengths and the lowest possible inter-circuit capacity. R.F. and oscillator circuits are simultaneously

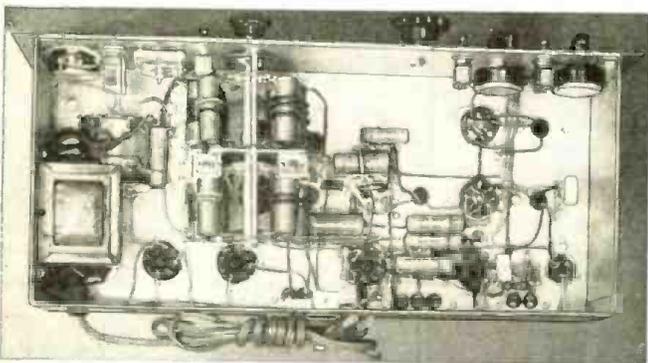


Fig. 4. Sub-chassis view. The coil and switch unit is factory-assembled.

dreds of receivers over nearly three decades, the writer has never before been able to attain such a quiet yet super-sensitive circuit.

Noise Limiter Included

Following closely the low cost single-signal super-het described in the October, 1938, and February, 1939, QSTs this new set uses one 6K8 regenerative first detector-oscillator, one 7A7 "Loctal" regenerative I.F. amplifier, 7A7 audio beat oscillator, 6B8 second detector, A.V.C. first audio amplifier and new type noise limiter, 6V6 beam power output tube, 80 rectifier, and one VR150 automatic voltage regulator tube. Including A.C. power supply, it mounts on a chassis 1/16" thick for absolute mechanical rigidity. This pan is only 15 $\frac{3}{4}$ " long, 7" deep and 3 $\frac{1}{2}$ " high, with control panel 17" by 9 $\frac{1}{2}$ ". A steel cabinet with hinged lid and removable back is available. 9 $\frac{1}{2}$ " high, 17 $\frac{7}{8}$ " long and 12" deep—with plenty of room behind the chassis to carry a 6-volt battery power supply or dry "A" and "B" batteries for portable operation, or the improved form of the Diversity Coupler recently described in *RADIO & TELEVISION* which turns the "Silver Super" into a full-fledged dual diversity receiver to minimize fading and its accompanying noise. The simplicity of parts layout, resulting in the extremely short and direct leads so essential to maximum efficiency, are clearly illustrated in Figs. 2 and 3.

Fig. 1 shows all of the controls essential

switched, with all unused coils short-circuited to prevent dead-end or absorption losses, which can become very serious at short wavelengths. All coils, including the extreme high frequency coil, are mounted on the wave-change switches themselves, as are the oscillator high-frequency padding condensers which set dial calibration. These padding condensers are compression mica on ceramic bases, not air-trimmers. Through special secret processes, these particular condensers (Guthman No. C45) are actually as stable as good air-dielectric condensers, and of very low loss design. R.F. coil sizes are such as to produce optimum Q versus shield proximity.


At the upper left of the panel is the calibrated S-meter, with below it the noise limiter knob, the extreme upper right knob being the beat oscillator pitch control. Along the bottom, left to right, are tone control, head-phone jack, antenna trimmer, beat oscillator on-off switch, wave change switch, vernier tuning, send-receive switch, audio volume control, A.V.C. on-off switch and I.F. selectivity control. Attention is called to the antenna trimmer knob: manual control of circuit tracking is provided in order to insure the very best possible results, and to take no chances of differences in antennae or adjustments of first detector regeneration upsetting circuit tracking, in line with recent trends in this direction in the newer communication receivers.

Fig. 3 shows a 6K8 tube used as detector.

(Continued on following page)

Your Complete RADIO TRAINING

GET IT ALL FOR \$4

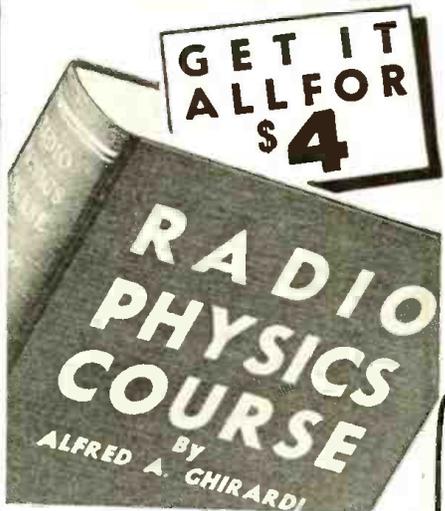

Complete in 1 Big Book

Just think! Packed into this one large \$4 volume is YOUR complete Radio Education. You can start learning at once, for Ghirardi's RADIO PHYSICS COURSE is a self-training book, which you can read at home, in spare time.

Master the Fundamentals of Radio —AND TELEVISION TOO!

Here's what you learn:

- Sound, Speech and Music
- Electricity
- Electric Current
- Electric Units and Circuits
- Resistance
- Ohm's Law
- Capacitance
- Magnetism
- Electromagnetism
- Transformers
- Inductance
- Condensers
- Alternating Current Circuits
- Filters
- Electrical Measuring Instruments
- Radio Waves
- Radiations
- Broadcast Stations
- Receiving Equipment
- Vacuum Tubes
- Radio and Audio Frequency
- Amplification
- Superheterodynes
- Loud Speakers
- Battery Operated Receivers
- Power Supply Units
- Electric Receivers
- Automobile and Aircraft Receivers

So complete is the training this book gives you that you learn not only Radio, but also about Electricity, Sound, Cathode-Ray Tubes, and Television as well. It's the equivalent of 36 different self-study books in one!

SO EASY IT'S AMAZING!

You will be surprised and delighted at your rapid progress once you start reading Ghirardi. No previous training is necessary. Ghirardi has an uncanny knack for making everything crystal-clear. That's why this book is used by more radio schools and students than any other radio text in the world.

USE IT 5 DAYS—OUR RISK!

Fit yourself at home for a good-paying radio job, this quick, inexpensive, most popular way. Send the coupon for your copy at once. You risk nothing; your money is automatically refunded if you decide to return the book within 5 days. The whole fascinating field of Radio lies ahead of you—set into it NOW!

TEAR OUT - MAIL NOW!

- Phonograph Pick-ups
- P. A. Systems
- Short-Wave Receivers
- Phototelevision
- Antennas and Grounds
- Testing and Servicing Receivers
- Sound Motion Pictures
- Appendixes
- Review Questions
- Plans for Self-Study
- DOZEN'S OF OTHER SUBJECTS!

972 pp. 500 illus. \$4

RADIO & TECHNICAL PUBLISHING CO., Dept. R&T-49
45 Astor Place, New York

Here is \$4 (\$4.50 foreign) for my copy of RADIO PHYSICS COURSE. SHIP POSTPAID at once with 3-day Money-Back Guarantee.

NAME _____

ADDRESS _____

CITY _____ STATE _____

Send free descriptive literature

LEARN RADIO THE Easy WAY

Your Inquiries Invited

When you need amateur equipment it is to your advantage to write to me. You get personal attention; 6% terms financed by myself so you buy with less cost and more convenience; fair trade-in value for your equipment; ten day trial of all receivers; and my cooperation in every way to see that you are 100% satisfied. For any equipment, the latest information and technical help, write to W9ARA.

Compare My Terms with Others

Model and Receiver	Cash Price	Down Payment	12 Monthly Payments
Skyrider SX-23	115.50	23.10	8.15
RME-70	\$138.60	\$27.72	\$9.79
HQ-120X & NC101X	129.00	25.80	9.11
NC100A	120.00	24.00	8.48
NC80X and NC81X	99.00	19.80	6.99
Breting 49 and S16	99.00	19.80	6.99
Howard 438	49.95	9.99	3.53
NC-44 and S-20	49.50	9.90	3.49
Sky Buddy	29.50	5.90	2.08

Also HRO, Breting 9, Howards, Sargents, all others

Similar terms on Hallicrafters, National, Harvey, RCA, RME, Temco transmitters and Thordarson, National, U.T.C., Utah, Kits.

All orders and inquiries attended to by Bob Henry, W9ARA; active amateur for 14 years; graduate M.I.T.E.E.; owner of Henry Radio Shop selling amateur supplies for ten years.

Bob Henry
W9ARA

BUTLER, MISSOURI

New Type Communications Receiver

(Continued from preceding page)

oscillator. Numerous tests of many different combinations of different tubes, single and separate, showed the 6K8 to be definitely the best converter available today in terms of stable oscillator output right down to 5 meters, maximum conversion gain, and freedom for interaction between first detector and oscillator circuits. Regeneration is independent of wavelength, and permanently set upon installing the receiver, is adjusted by the potentiometer connected to the feed-back condenser C1. Stable and permanent regeneration is secured in a manner new to receivers. An R.F. choke, R.F.C., in the plate return lead provides R.F. voltage which is fed back from the arm of a potentiometer across R.F.C. to the grid circuit A.V.C. return through C1. At first this may look inoperative, but consideration of the capacity ratios of C1 and C2 should make it clear that regenerative feed-back does occur. Tuning condenser capacity is 140 mmf.—amply low for maximum gain, and far lower than is found in most all-wave or even communication receivers. C3 is the antenna trimmer, adjustable from the front panel. High impedance antenna primaries prevent differences in antennae upsetting regeneration or circuit tracking, but no chance is taken with hard-to-get signals and C3 is made manually variable. It is not critical and can be forgotten except when the weakest of signals must be pulled through.


I.F. Amplifier

The I.F. amplifier uses two permeability-tuned high-Q I.F. transformers. These are the most stable types known today, for their tuning capacities can not vary, being "Silvercons," in which silver is directly plated onto mica, so that capacity cannot change. They are really fixed condensers. Tuning is effected by micrometric adjustment of powdered R.F. iron cores inside each I.F. coil. These two transformers represent much research and experiment to allow them to be regenerated without any frequency shift. Ordinary 455 kc. transformers used in a regenerative I.F. amplifier will show up to 10 kc. frequency shift for different degrees of regeneration, and this is, of course, highly undesirable, if not intolerable. Careful adjustment of coupling and stray capacities results in the "Silver Super" showing no measureable frequency shift at any degree of regeneration. The I.F. tube is the new 7A7, all-glass "Loctal" type. In this new tube, element leads enter a flat base or stem, instead of running up through the usual 1½" long stem tube and so providing harmful capacity and inductance. Having no molded bakelite base, but rather contact pins set directly in the glass itself, base losses are a thing of the past. A small metal socket aligning-cap shields the base so that both grid and plate leads come out the same end—the new "single-ended" type of R.F. pentode construction. Gain is higher than for the older 6K7, for the "Loctal" idea makes real sense in tube design. A second 7A7 is the beat oscillator, coupled to the second detector by capacity provided through judicious parts placement, and tuned from the front panel by a knob controlling its powdered iron core so as to permit optimum choice of beat note for single-signal selectivity, zero beating for broadcast reception, or different beat note pitches to reduce heterodyne interference—which is noticeably absent due to the extreme selectivity possible. I.F. regeneration—selectivity and gain control—is through cathode bias with feed-back

A PROFESSIONAL SLIDE RULE

PRACTICAL, EDUCATIONAL, TIME SAVER

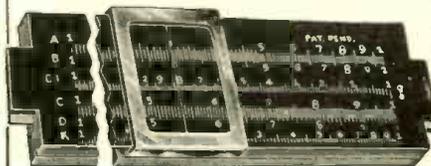
Features: Nickel Silver framed indicator with integral friction springs, scales calibrated directly on well-seasoned wood. Retains accuracy regardless of temperature or humidity changes. Instructions and illustrations of primary operations clearly printed on reverse side of rule for ready reference or teaching. Each rule with a durable pocket carrying case for convenience and protection.



We offer an eight inch, white wood, accurate slide rule with A, B, C, D, CI and K Scales, a 20-page Book of Instructions, How to Use a Slide Rule, a 36-page Book of 300 Examples and Answers, a two-toned Facsimile of the Declaration of Independence, suitable for framing, and an 8-page catalog illustrating and describing indoor games and many unusual items, all five prepaid anywhere in the United States and Canada for

50c

STURDY BINDERS

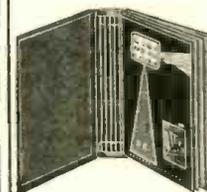

for any size magazines. Covered with black corrugated fibroid. Has two stamped metal ends with 12 Spring Wire separators. Magazines can be inserted and removed in a jiffy. 12 1/2 x 7 3/4" fits R.&T. Radio News, etc., \$1.00 10 3/4 x 7" with 3" back, fits QST, Radio, Popular Mechanics, Popular Science, etc. Prices on binders, P.P. prepaid.

STOPPANI COMPASS

A Precision Instrument made in Belgium. Purchased by the U. S. Government at more than \$30.00 each. Ideal for Radio Experimenters Laboratory, also may be used as a Galvanometer for detecting electric currents in radio circuits. Ruby jeweled, solid bronze. 4 inches square, fitted in a hardwood case. Also used by hunters and surveyors.



Our price prepaid \$4.50 each

Send for catalog containing full descriptions of these and many other interesting items.

GOLD SHIELD PRODUCTS

Dept. RT-4-9 350 Greenwich St. New York

FREE!

Our new Catalog describing over thirty-two books in the "How to Make More Money" field has just come off the press. This catalog describes each book in detail. It enables you to select one or more books which will meet your requirements in an attempt to improve yourself financially.

Many of the books in the NATIONAL PLANS INSTITUTE catalog tell you how to start a spare- or full-time business of your own.

Write today for your FREE copy of the "NPI" Book Catalog—address a one-cent postcard to Dept. RT-439—and mail it today.

NATIONAL PLANS INSTITUTE
246-T FIFTH AVENUE, NEW YORK, N. Y.

MIDWEST FACTORY SALE!



SAVE UP TO 50% NEW!

IT'S easy to put this big new 14-tube world-wide Midwest chassis in your cabinet and get exciting world-wide reception. Midwest makes a radio to suit every purse...6-tube to 17-tube, 5-band models. Prices start as low as \$10.95. As Much As 540 TRADE-IN ALLOWANCE on the beautiful 17-tube, 5-band Model "D" shown on left. Money-back guarantee. Write for new FREE 1939 catalog.

MIDWEST RADIO CORP., Dept. 14-LL, Cincinnati, O.

Do you need BINDING POSTS?



The XL PUSH POST with its Spring Action assures Constant Contact and quick connection. Manufactured in All Aluminum Type M at 10c each. Aluminum Body, Bakelite Top Type B1 at 15c each. Type B1 completely insulated with Bakelite Insulating Shell type C1 at 20c each and proven by 240 hr salt Spray Test AS NON CORROSIVE our Types CP or NP at 28c each.

Manufacturers and Dealers Liberal Discounts

X. L. RADIO LABORATORIES
420 West Chicago Ave., Chicago, Ill.

through slightly augmented grid-plate capacity of the 7A7 I.F. amplifier.

A.V.C. Switch Provided

The diode second detector and A.V.C. of the 6B8 is essentially conventional with optimum values chosen and the switch provided to cut out A.V.C. without affecting detector action when desired, as for code reception. A 7A7 is used as a V.T. voltmeter, fed from the diode load, for super-sensitive tuning meter operation. The pentode of the 6B8 is used for first audio stage—not so much for its high gain as to provide the simplest possible noise limiter. Varying the screen voltage on a pentode controls its plate current—in effect, controls its "saturation" or the strength of the signal it can handle. This characteristic allows noise louder than signal to be held down to no louder than signal by variation of screen voltage. This can be done automatically, which does not give most satisfactory results in operation, for then the system becomes a true "hole-puncher" silencing reception when noise appears. So operated, such automatic silencer is so effective that loud noise will actually shut off reception during its duration. A manual control is obviously more desirable, and so is provided. By permitting noise to be held down to signal volume, it gives the impression of having almost completely eliminated noise, so great is its seeming reduction. This noise limiter is equally effective on all types of noise, at all wavelengths.

Audio gain control is in the 6B8 grid circuit, with tone control and head-phone jack in its plate circuit, which is followed by a 6V6 beam power output tube for loud-speaker operation—and this set will "rattle the speaker" on almost any signal that can be heard. Power supply is essentially conventional, with chassis-mounted power transformer of ample size for good heat radiation, large, very high effective inductance filter choke and plenty of sealed-in-metal-can dry electrolytic capacity of generous voltage rating for extreme safety. Sockets are provided for the VR150 automatic voltage regulator tube for the user who desires the frequency stability usually associated only with a fine frequency meter, but seldom with receivers. This tube is not essential, but is a distinctly worthwhile refinement.

"Send-Receive" Switch

In line with attaining extreme stability, the send-receive switch is used in a new way. Instead of breaking only one or two plate circuits to mute the receiver during transmission, the S-R switch cuts the entire "B" supply to all tubes, including power to the filter. Thus, the operator, desiring a taste of real receiver frequency stability for a change, may leave the on-off switch on all the time—or turn it on in the morning before an evening of operation—so that tubes and set will have reached stable temperature by evening and there just won't be any frequency drift.

Still another refinement is the eight-prong socket and dummy plug just before the filter. Pulling the plug opens the filament and B-supply circuits so that with a live plug another source of power—dry batteries, dynamotor or vibrator "B" and battery "A" can be connected to the set. It is thus substantially independent of power sources, and can be operated A.C. or battery.

For the amateur who cannot afford to immediately buy all parts for the receiver as described, a distinct convenience exists in that he can buy parts for everything except the power supply, 6V6 power output

Complete RADIO TRAINING for \$1.95

Regular \$39.00 RADIO TECHNICAL INSTITUTE Course



AN UNUSUAL OFFER

A limited quantity of R.T.I. \$39.00 radio servicing courses have been reprinted and are offered to you at only \$1.95. These are the latest 1937 courses, complete in every detail with all supplementary material, and exactly

the same as the originals. Radio is the present-day opportunity field. Hundreds of men with no special talents have studied Radio Servicing for a short time and are now making twice and three times as much money. R.T.I. unique radio training brings rich rewards; you can get ready quickly, inexpensively, easily, and in your spare time for a good job in radio.

ACCEPTED BY INDUSTRY

Forty large radio manufacturers have helped to prepare the R.T.I. course. Just think what this backing by the radio industry means to you. R.T.I. Practical training will give you facts and real data you will need on the job. Hundreds of diagrams and illustrations will help you. You will pass quickly from lesson to lesson and in a surprisingly short time will be ready to do real radio servicing.

COMPLETE IN ALL DETAILS

No special previous education or experience is needed. R.T.I. course will give you all the training you need. The lessons are clear, interesting, easy to master and use. Fellows who knew nothing about radio before taking the R.T.I. course are now the leading servicemen in their communities. This is your chance to obtain this excellent course for only \$1.95.

From the very start you are introduced to practical servicing equipment and practices. You are told how to open your own shop or radio store. Lesson 15, "The Radio Servicing Business," will give you many practical ideas and hints. The course is so planned that you will be able to earn spare-time money before you have reached your tenth lesson. The special \$1.95 price of the complete course can be earned in a single evening's work.

YOUR GUARANTEE

You are completely protected. We guarantee these courses to be exactly as the original \$39.00 Radio Technical Institute courses. Money back guarantee. References: Liberty National Bank, Chicago.

THREE COURSES IN ONE

R.T.I. course is really three complete essential courses combined. You get training in (1) Practical and Applied Radio; (2) Fundamentals of Radio Principles; and (3) Advanced Specialized Training. This is the training that will place you above the average radio servicemen—and you get this training for only \$1.95.

There are over 32,000,000 radio sets in use. Over 4,500,000 auto radios alone. You should cash in on this gigantic money market. The R.T.I. easy practical course will pave the way to your success in Radio work.

TELLS HOW TO USE INSTRUMENTS

The training is complete. Everything from simple facts to complex alignment problems. Many servicemen have found that R.T.I. training is excellent for brush up and study of modern servicing methods. This is the best buy in a radio education. Take advantage of the bargain price today.



LATEST DATA

Yes, in the R.T.I. course you will find a complete explanation of A.V.C., how to use an oscilloscope, sound feed-back, resonance phenomenon . . . every possible fact you must know to be the best servicemen. You get a real radio training. One of the BEST radio courses is yours for only \$1.95.

LIMITED QUANTITY

Hurry your order to us today. There is but a small quantity of the courses left at the special price. You are completely protected with our guarantee. Send total remittance with order, or we will ship C.O.D. Postal money orders, checks, currency, unused stamps accepted. Answer today.

SUPREME PUBLICATIONS, Agents
3729 W. 13th Street, Chicago, Ill.

Please send the complete R.T.I. radio course at the special \$1.95 price.

I am enclosing \$1.95, send prepaid.

Send C.O.D. I will pay mailman \$1.95, plus a few cents postage.

NAME

ADDRESS

stage, beat oscillator, tuning meter and voltage regulator tubes. He can then assemble a 3-tube set—regenerative detector—oscillator, regenerative I.F. amplifier, second detector, A.V.C., audio amplifier and noise limiter that on headphones, with batteries or "junk-box" power unit, will give performance which will amaze the hard-boiled operator who sniffs at any communication receiver costing less than \$200.00. The user can then add on as he can afford to, until in the full-sized eight tube set he has something that has banished his receiver worries for a long time to come.

The writer will gladly answer questions, or give complete parts list and full "how-to-build-it" details to any who may care to write to him in care of this magazine.

Photos and description courtesy of Edwin I. Guthman & Co., Inc.

A Letter from London

(Continued from page 718)

to a letter from the editorial department of the *British Broadcasting Corporation*, asking further information, J. R. T. Hopper writes: "We would like to make it clear that the cable has been installed by the Post Office primarily for multi-telephone work, and that the suggestion that it may be used for television has been purely incidental. As a matter of fact, decision on the possibilities and method of extending television beyond the London area lies with the Television Advisory Committee, and so far no official announcement has been made."



for
**Assemblies
that MUST
LAST!...**

• Performance far beyond normal expectation accounts for the growing popularity of AEROVOX condensers and resistors. Likewise AEROVOX predominance in most assembly specifications. So be guided accordingly if you seek the LONGEST service at the LOWEST cost.

DATA: Latest catalog available at local AEROVOX supplier, or from us direct. Ask for details regarding our monthly RESEARCH WORKER publication.

AEROVOX
CORPORATION
NEW BEDFORD, MASS.
IN CANADA: AEROVOX CANADA, Limited, Hamilton, Ont.



Astonish YOUR FRIENDS!

Pass
500,000 Vts.
Thru the
Body!
Light
Lamps, etc.

DATAPRINTS SHOW YOU HOW!

20c Each in Order for 10 TESLA-LOUDIN HI-FREQ. COILS
(Data and Drawings only)

- 36" Sp'k Tesla-Loudin Coil.....40c
(1 K.W. Exc. Trf. Data. Included FREE!)
- 8" Sp'k Tesla-Loudin Coil.....40c
(1/4 K.W. Exc. Trf. Data. Included FREE!)
- 3" Sp'k Loudin; 110 Vt. "Kick Coil" type.....40c
- 3" Sp'k Tesla Works on Ford Sp'k Coil.....40c
- 1" Sp'k Violetta Hi-Freq. Coll.....40c

FREE with order for \$1.00 or more—20 Tricks with Hi-Freq. Coils* (40c separate)

Television Hook-ups—"Sight & Sound" .. 40c

20 ELECTRIC PARTY AND LODGE TRICKS! Loads of Fun!

How to Shock 'em!.....40c
Order with other prints; see special price below and save.

Solenoid & Magnet Data—Get Our List!

20 Telephone Hook-ups—Build Your Own .. 40c

RADIO CONTROL FOR MODEL BOATS. PLANES. ETC.
Circuit data40c

S-W DIATHERMY (Artificial Fever)
Dataprint giving Constructional data for Small, Medium and Large size App. (All 3) ..40c

Induction PIPE & ORE LOCATOR
Construction Data40c

You NEED these DATAPRINTS !!
40c Each.

- Electric Pipe Thawer. Rewinding Armatures.
 - 100 Mechanical Movements. Einthoven String Galvanometer.
 - 20 Motor Hook-ups. Resistance Measuring
 - Welding Transformer. Bridge.
 - 2 K.W.
- Special Prices: 4 prints \$1.00; 10 for \$2.00; 40c each, single orders.

The **DATAPRINT Co.**

Lock Box 322A RAMSEY, N. J.

Antennas—Past, Present and Future

Harold H. Beverage
(Continued from page 709)

200 miles or so apart. It is interesting to note that there are as many cycles between 5 meters (60 megacycles) and 10 meters (30 megacycles) as there are in the entire radio spectrum above 10 meters. The services that will undoubtedly develop in the ultra-short wave spectrum may eventually become as important, or even more important, than the services now existing in all of the rest of the radio spectrum. For example, the ultra-short wave band is the only part of the spectrum suitable for high definition television. Bands of 6 megacycles width in this spectrum have already been ear-marked by the Federal Communications Commission for experimental television transmission.

We have seen that in the transition from the long waves to short waves, there was a radical change in the type of antennas that were found useful and necessary for the new services. Will the development of the ultra-short wave spectrum see a radical change in antenna structures such as we do not dream of today?

In the long distance use of short waves, a limit was found in the concentration of the radio beam that could be used successfully. To obtain a high power gain, it was necessary to concentrate the radiation into a narrow beam in the vertical plane as well as the horizontal plane. It was found that there is no single vertical angle at which the radiation can be launched that will be effective over a considerable period of time. The classic work of the Bell Laboratories in the development of the MUSA system indicates very clearly that the signals may travel over several bundles of rays, but that these paths are quite variable and require a wide range of vertical angles to obtain reliable communication over a considerable period of time. This phenomenon sets a limit on the usable concentration of the radiated or received radio energy. As a practical matter, an antenna with a concentration which produces a power gain of 100 is probably close to the useful limit. Will a similar limitation in the concentration of power be found on the ultra-short waves? No such limitation is known today, and as the wavelength becomes shorter it is practicable to build antennas that will highly concentrate the radio beam. Will we see strange contraptions with power gains of 1000 or more on relay chains carrying television network programs and multiplexed mass communication? If power gains of a high order can be used, the transmitter power required will decrease in proportion so we may see a miniature "acorn" tube transmitter associated with an enormous directive antenna structure. The possibilities of using radio repeaters even smaller than telephone type repeaters, and concentrations of energy that reduce the attenuation over a given path to a very low value are indeed intriguing to the imagination.

Another factor that will affect the antenna design for the ultra-short waves is the necessity for providing antennas covering an extremely wide band for high definition television. We have already seen some radical departures from familiar forms of antennas in this field in the television antenna recently erected on the Empire State Building in New York. Here we see radiator elements looking like Indian clubs projecting from an expanding throat, appearing somewhat like the stream-

FREE- REAL ELECTROPLATING OUTFIT



Now
You Can ELECTROPLATE Easily with a BRUSH!

SOMETHING new for amateurs, fans, set builders—something which gives you the opportunity with which to experiment. Here's an ELECTROPLATING KIT amazingly simple to operate—you just Electroplate with a Brush! Requires only one single dry cell.

NOT A TOY

You can electroplate for profit, hundreds of things in the household—ashtrays, fixtures, water faucets, worn brackets, door knobs, musical instruments, jewelry and silverware and other articles. It's an indispensable piece of equipment to you for plating articles in hotels, apartments, office buildings, medical and dental offices, factories, schools, laboratories, etc. Exactly the same outfit (but larger) is used professionally by electricians, radio service men, automobile repair shops, etc. And for radio work, you can electroplate tarnished receiver parts, chassis, contacts, worn radio parts and accessories.

Put this REAL ELECTROPLATING KIT to use immediately—make it the most useful article in your lab or work bench. And, you can get it absolutely FREE (except for slight mailing cost).

Send your subscription today to RADIO AND TELEVISION for One Year (12 issues) and receive absolutely FREE one of these REAL ELECTROPLATING KITS—New subscribers are accepted or you may extend your present subscription another twelve months under this offer. Mail your remittance of \$2.50 (Plus 10c for shipping charges on kit) to the publishers of RADIO AND TELEVISION. (Canada and foreign \$2.85.) You will promptly receive your FREE REAL ELECTROPLATING OUTFIT by return mail. Use the coupon below to order your subscription.

RADIO AND TELEVISION

99 Hudson Street New York, N. Y.

RADIO AND TELEVISION

99 HUDSON STREET, NEW YORK, N. Y.

Gentlemen: Enclosed you will find my remittance of \$2.50 for which enter my subscription to RADIO AND TELEVISION for One Year (12 issues). Send me promptly my FREE REAL ELECTROPLATING OUTFIT. (Canada and foreign \$2.85.) In U.S. add 10c additional to cover shipping charges on kit.

() NEW SUBSCRIBER
() EXTEND PRESENT SUBSCRIPTION

Name

Address

City State

(Send remittance by check, money order or unused U. S. Postage stamps. Register letter if you send cash or stamps.)

RT-4-39

PLUG-IN COIL FORMS



Especially Recommended For All Home-Constructed Receivers And Low-Power Transmitters.

Molded from natural color bakelite, these eight-rib forms are made in the 4, 5, and 6 pin types, and in three diameters—1 1/4", 1 1/2" and 2 3/4". Easily drilled and readily removable from socket without disturbing winding. Priced from 18c to 60c net at your BUD dealer. For free catalogue RT-49 write

BUD RADIO, Inc.

5205 Cedar Ave. Cleveland, Ohio

lined nacelle of a modern air liner. By this unusual design, a radiator is obtained which, electrically, looks like a resistance over the complete octave of frequencies from 30 to 60 megacycles, many times wider than any omni-directional (all-directional) antenna known to the prior art. In other words, this antenna has a flat characteristic over a range 30 times as wide as the normal broadcasting band.

As we learn how to use shorter and shorter wavelengths we may well expect to see increasingly radical antenna designs which have little resemblance to the antennas that have been familiar to us in the long wave and short wave fields.

Television "Sight Effects"

(Continued from page 710)

looking at a miniature house. And what a house!—the shingles were even cut on a taper, and every detail of the full-sized door, even down to the doctor's nameplate, was accurately reproduced in the miniature. The chimney of this model house was constructed of lumps of sugar suitably painted with water colors.

In one of the interesting scenes, an animated spider's web was desired, and here the spiders—which were made in the studio specially for the purpose—were caused to move by a series of small rods rotating inside hollow tubes forming part of the web. These rods were geared together by means of a chain and driven by a motor.

Some of the books used in the television scenes are made of plaster of Paris, suitably painted to resemble actual books.

The writer was quite astonished to learn at what speed some of these objects were constructed and painted. Warships in miniature are made in a jiffy, as also are models of certain animals desired, not to mention artificial flowers and trees, miniatures of people in any style of dress or uniform, etc.

In making motion pictures, such effects as those here described are very easy to produce, for the camera can be stopped while certain changes are made in the objects or in the scene before the camera; but in television, the action of the scene cannot be stopped to permit such changes being made and the action must be continuous. Thus, an entirely new method of procedure had to be worked out by Mr. Eddy and his associates.

NOTICE

In reviewing the Thordarson Electric Mfg. Co.'s "Sound Amplifier Guide," we neglected to mention that the price of this bulletin (No. 346-D) is 15c, direct from the manufacturer, or through jobbers at the usual trade discounts.


Third of the new series
"Getting Started in Amateur Radio,"
by C. W. Palmer, E.E., in the next issue.

BOOK REVIEW

RADIO-FREQUENCY ELECTRICAL MEASUREMENTS. Hugh A. Brown, M.S., E.E., 384 pages, illustrated, size 6" x 9". Published by McGraw-Hill Co., Inc., New York and London.

Mr. Brown, who is Associate Professor of Electrical Engineering at the University of Illinois, has done a masterly work, covering his subject most thoroughly. Not only does he give the necessary formulae for use in various types of measurement work, but also gives diagrams of apparatus and lucid explanations on procedure. The book is very well illustrated with circuits and schematics, as well as a number of very interesting graphs, etc. The principal chapter headings are: Measurements of Circuit Constants; Measurement of Frequency; Antenna Measurements; Electromagnetic-Wave Measurements; Measurement of Electron-Tube Coefficients and Amplifier Performance; Electromotive Force; Current Power; Measurement of Wave Form; Modulation, Receiver and Piezo-Electric Crystal Measurements. The index is particularly ample and easy to use.

MARINE and COMMERCIAL-TYPE RECEIVERS

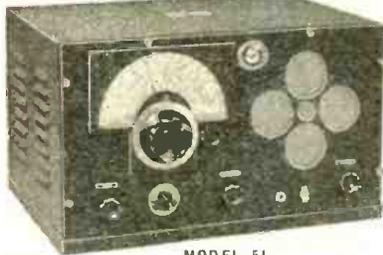


MODEL 51

- 13 Tube Performance (10 used)
- Isolate Insulation
- Iron Core I.F.
- Band Spread
- C.W. Pitch Control
- R.F. and Det. Panel Trimmers
- Push-Pull Audio
- A.C.-D.C. Circuit
- Full Wave A.C. Rectification
- High voltage, oiled paper filter condensers—no electrolytics
- Both Power lines fitted and shielded, moisture-proof bypasses

An AC-DC, communication-type superhet, built to highest standards. Continuous tuning range 9.7 to 3.750 meters in Model 51-MK covers time signals, weather and airplane beacons, 600 meters, broadcast, police, yacht phone, amateurs and short wave broadcast. Dial fully calibrated with all amateur, broadcast and ship bands marked. Regenerative input gives almost complete image rejection, brings up weak signals that are undecipherable without it. A rugged, dependable communication receiver afloat or ashore. A go-Getter for DX. ALWAYS IN ALIGNMENT. No need to depend upon line-up adjustments made in a factory thousands of miles away. R.F. and detector trimmers, on the panel, allow the operator to align the receiver perfectly for any frequency. Built of the best materials. No electrolytics or deteriorating parts except the tubes.

MODEL 51 NET PRICES

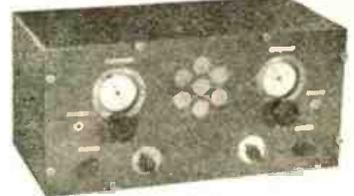Model 51-AK, 9.7-550 meters, 110 volts AC-DC net \$157.00
Model 51-MK, 9.7-3,750 meters, 110 volts AC-DC net \$175.00
Battery model also available.



MODEL 11 9.5 TO 20,000 METERS—

Continuous tuning from the ultra highs to the audio frequencies—the greatest tuning range of any advertised receiver. An exceptional CW receiver but good also for phone and broadcast. Designed for the operator whose interests are not confined to any one set of frequency bands. Flexible, quiet, easy to operate, ultra-sensitive. Employs tuned R.F. and regenerative detector circuit—believed by many to be most sensitive C.W. receiving circuit ever developed. Selectivity compares favorably with larger multi-tube sets. Features: Model 11 has coil switching, band spread, calibrated dial, break-in switch, phone jack, built-in speaker and power supply. Flexible, available in any voltage and for A.C., D.C. or battery, in 3 tuning ranges. An accepted standard in this field since 1936.

MODEL 11 NET PRICES

Model 11-AA, 9.5-550 meters, \$52.00
Model 11-MA, 9.5-3750 meters, \$57.00
Model 11-BA, 9.5-20,000 meters, \$77.00
Immediate Delivery. Prices include power supply, speaker and RCA tubes.

AMATEURS—STREAMLINER '39—

2 stakes I.F. give that extra kick lacking in so many 5 tube receivers, 9.5 to 550 meters, a knock-out on 10 meters, 5 tube amateur superhet. Write for details. Net price, complete \$33.90. Equals performance of sets selling for many times the price.

E. M. SARGENT CO.

212 9th St. Oakland, Calif.

ATTENTION!

WE PURCHASED THE ENTIRE QUANTITY OF 1,000 RADIO COIL WINDING MACHINES FROM THE WORLD FAMOUS ATWATER KENT MFG. CO. AND OFFER SAME SUBJECT TO PRIOR SALE AT LESS THAN 10% OF THEIR ORIGINAL COST.

200—Power Transformer Coil Winding Machines. Paper Layer Type. Will wind series of coils up to 12 and 13½" by 3" dia. Sizes of machines 31" and 35" long by 15" wide by 8" high. Price, each \$25.00
Weight 100 to 110 pounds.

25—Small Paper Layer Type. Will wind coils up to 3¼" wide by 1½" dia. Size 14" long, 8" wide x 5½" high. Weight 30 pounds. Price, each \$15.00

200—Field Coil Winding Machines. Wind 1 coil at a time. Size of spindle ¾" dia. x 4" long. Flange 2½" dia. and 3½" dia. Machine has automatic stop. Size 16" long x 10" wide x 7" high. Weight 30 pounds. Price, each \$7.50

75—Resistor Coil Winding Machines. Winding spindles 2¼" and 5" wide. 4 winding spindles extra free with every machine with different size threads. Size of machines, 13" and 15" long x 5" and 6" wide x 6" high. Weight 17 and 25 lbs. each. Price, each \$10.50

150—L.F. and R.F. Coil Winding Machines. Straight winding arranged with turn counter and automatic stop. Size 12" long x 9" wide x 7" high. Weight 20 pounds. Price, each \$11.50

25—Hand Coil Winding Machines. Arranged with turn counter and 3" winding spindle. Can be replaced with any length winding spindle. Size 10" x 6" x 6". Weight 12 lbs. Price, each \$6.50

Extra Gears to fit any of the above machines at 50c each. Also carry extra parts for above machines.

All machines overhauled and guaranteed in working condition or money refunded within 30 days.

Space does not permit to list all items. Your inquiries are solicited for machinery of every description.

Terms: 1/3 with order, balance S.D.B.L., F.O.B., N. Y.

M. M. LEVINE

Phone Worth 2-8655

84 Warren St., New York City



EVERYTHING IN RADIO!

A COMPLETE SOURCE FOR YOUR RADIO NEEDS
Our immense stock of radio sets, parts and supplies enables you to purchase your entire needs on one order. You will find all your Nationally Known Favorites in this big book which is FREE by the asking. Practically every order is shipped the same day it is received.
WRITE FOR BIG NEW CATALOG

BURSTEIN-APPLEBEE CO.

1012-14 McGee St., Kansas City, Mo.

I believe...

that a fair and square deal, every time, is the only way to keep up a successful business. That must be right, because since 1925 more and more men have been buying their radio equipment from me.

You, too, will find it to your advantage to deal with me whenever you want to buy a new receiver, transmitter, or any other equipment.

My personal attention to your wishes, fair trade-in allowances, reasonable terms for your convenience, prompt safe delivery, and above all—a sincere desire to give you full co-operation—is your assurance of complete and lasting satisfaction.

Be sure to write to me.

73

Bill Harrison, W2AVA

TIME PAYMENTS?

Check these easy terms—

Receiver	Cash Price	Down Payment	Monthly Payments 8 OR 12
NC-101-X			
HQ-120-X	\$129.00	\$19.96	\$14.21 \$9.66
NC-100A	120.00	18.48	13.22 9.00
S-16, Breting 49, NC-91-X, NC-80-X	99.00	15.34	10.90 7.41
New SX-23, speaker	127.50	19.40	14.06 9.58
SX-16, speaker	123.00	19.60	13.47 9.16
SX-17, speaker	149.50	22.60	16.53 11.25
RME-69	152.88	24.10	16.78 11.41
RME-70	138.60	21.10	15.31 10.41

I can change these terms to suit your convenience.

Also terms on all Halliflaters, Hammarlund, National, RME, Howard, Sargent, Breting, Patterson, Temco, RCA, Thordarson, Utah, etc., Receivers, Transmitters and Kits.

OUR USED DEPT

has many good reconditioned and guaranteed trade-in Receivers and Transmitters at attractive prices. Good values! Send stamp for list.

HARRISON RADIO CO.

12 West Broadway, New York City

PRECISION CRYSTAL CONTROL FOR ALL AMATEUR BANDS

BLILEY CRYSTALS Now \$3.35 UP
BLILEY ELECTRIC CO., ERIE, PA.

CLEARANCE SALE!

Rockbottom Prices on Surplus, and Army and Navy Merchandise

When prices are low we buy! They're low now—LOWER THAN THEY EVER WILL BE—hence this sale. Most of the merchandise is new—never used; some of it reconditioned. 100% satisfaction on each transaction or your money refunded.

ORDER FROM THIS PAGE. Use the convenient coupon below. Be sure to include sufficient extra remittance for parcel post charges, else the order will be shipped express, charges collect. Any excess will be refunded. C.O.D. shipments require a 20% deposit. If full remittance accompanies order deduct 2% discount. Send money order—certified check—new U. S. stamps. No C.O.D. to foreign countries.

ORDER TODAY QUANTITIES LIMITED QUICK SHIPMENTS ASSURED

BEAUTIFUL KOLSTER RADIO



Brand New! Never been used before! Packed in their original crates. Beautiful walnut highboy cabinets designed for the one-time expensive Kolster battery receivers models 6D, 6G and 6H. In fact the R.F. tuners, never used, are still in them and go with them. A modern midge receiver chassis installed in one of these beautiful cabinets would certainly compare favorably alongside a modern console radio. Three compartments are available: one for the R.F. tuner, one for the speaker and one for the last tier. Want a cabinet for building a combination radio-phonograph or a TELEVISION RECEIVER? Plenty of room for a cathode ray tube. Measurements: 54" high, 27" wide, 18" deep. Shp. Wt. 164 lbs.

ITEM NO. 32
Your Price \$4.95


WESTINGHOUSE WATTHOUR METER

Completely overhauled and ready for immediate service. Designed for regular 110-volt, 60 cycle 2-wire A.C. circuit. Servicemen use in their shops to check current consumption of sets, soldering irons, etc. Costs down if dismantled, the parts alone would bring the price. The elaborate four train could be used as a counter on machines of various kinds. Simple to install: 2 wires from the line and 2 wires to the load. Sturdily constructed in heavy metal case. Size: 8 1/2" high, 6 3/4" wide, 5" deep. overall. Shp. Wt. 14 lbs.



ITEM NO. 33
Your Price \$4.50

WESTINGHOUSE MODEL "WN" ELECTRIC HEATER

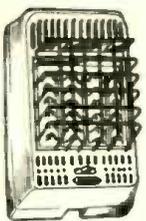

115-Volts, 1250-Watts
Radiant, clean Electrical heat—always there at the flip of a switch. Use it in the bathroom, the living room, the den, anywhere—leaves no dirt, no ashes, no soot. It is designed for permanent installation on any wall surface. Heating element is mounted on a special heater brick and protected by a cadmium-plated guard. Not a fire hazard! A special baffle and back panel protect the wall. Sturdily constructed on a white-enameled iron frame. Size: 15" high, 10" wide, 4 1/2" high overall. Shp. Wt. 23 lbs.

ITEM NO. 34
Your Price \$5.49

WESTON MODEL 562 A.C.—D.C. AMMETER

Designed by Weston for the Eastman Kodak Co. It is a precision-built magnetic-vane type ammeter which, with suitable shunt, can be used as a milliammeter too. It is 2" in diameter and designed for panel mounting. Bakelite base and black-enameled cover. Shp. Wt. 2 lbs.



ITEM NO. 35
Your Price \$1.25

U.S. ENGINEER DEPT' MAGNETIC COMPASS



Designed to the high precision standards of the U.S. Government by Herschelt. The extremely sensitive needle is mounted on a jeweled bearing and has a sliding weight on one side for maintaining an accurate balance. A metal scale around the periphery has a finely graduated scale permitting actual readings of all points of the compass. Students of electricity can use it as a galvanometer by wrapping a few turns of wire around it. Excellent for boy and girl scouts, forest rangers, hikers, campers, trailer homes, etc. The entire instrument is recessed into a mahogany case. Shp. Wt. 2 lbs.

ITEM NO. 36
Your Price \$2.65

SPERRY GYROSCOPE LIQUID COMPASS

Made for U.S. Signal Corps: sensitive and accurate. Quick readings easily made from top; accurate readings of graduations through focusing magnifying lens on side of instrument. Complete with level sights and russet leather carrying case. Excellent for boats, boy scouts, campers, hikers, etc. A few turns of wire around its case makes it usable as a galvanometer. Shp. Wt. 3 lbs.



ITEM NO. 12
Your Price \$1.85

VARIABLE SPEED UNIVERSAL MOTOR FOR 110 VOLTS, A.C. OR D.C.

Made for Dictaphone machines by American Gramophone Co. Used, but in excellent condition. Special lever control permits variable speeds up to 3000 r.p.m. 1/2" shaft extends from both sides of motor. Measures 7 1/2" x 3 1/2" diam. overall. Shp. Wt. 6 3/4 lbs.

ITEM NO. 11
Your Price \$2.55

FAMOUS VACUUM CLEANERS

Rebuilt Like New

Guaranteed for 6 Months


We give you new brushes, bags, handles, belts and other parts. The chassis is replated. All moving parts overhauled. Money back if not satisfied.

ELECTROLUX NO. 11—Radical design, cylinder type motor. Complete with all attachments. Foot control switch. Has 101 uses: cleaning upholstery, walls, draperies, curtains, mattresses, etc. Shp. Wt. 18 lbs. List price, \$69.75.


ITEM NO. 30
Your Price \$16.48

HOOVER NO. 105—Motor driven brush. Foot control switch. Black enameled steel motor housing. 12-inch nozzle. Shp. Wt., 24 lbs. List price, \$63.50.

ITEM NO. 28
Your Price \$13.95

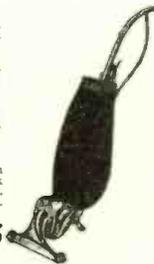

NEW FUEL PUMPS

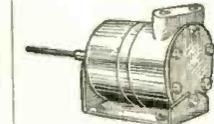

Brown & Sharpe pumps. Brand new; never been used. Can be used for gasoline, oil, kerosene, and other fuels. Not good for water. Takes standard thread 1/2" input and output pipes. Has 1/4" drive shaft. Measures 4 x 3 3/4 x 3 3/4" diam. overall. Shp. Wt. 8 1/2 lbs.

ITEM NO. 24
Your Price \$4.45

PORTABLE TELEGRAPH AND BUZZER FIELD SETS



Made for military use by Western Electric. A wonderful buy if only for the parts it contains. Never been used. Good for code practicing, signal communications, etc. Contains 2-tone, high-frequency buzzer with platinum contacts, telegraph key, telephone switches, earphone, condensers, transformers, chokes, etc. A \$50 value easily. Complete in wooden case with diagrams and instructions. Shp. Wt. 12 lbs.

ITEM NO. 16
Your Price \$5.45

WE HAVE NO CATALOG. ORDER FROM THIS PAGE.

HUDSON SPECIALTIES - 40-T West B'way - N.Y.C.

IT'S EASY TO ORDER—CLIP COUPON—MAIL NOW

HUDSON SPECIALTIES CO., 40-T West Broadway, New York, N. Y. RT-439

I have circled below the numbers of the items I'm ordering. My full remittance of \$..... (include shipping charges) is enclosed.

OR my deposit of \$..... is enclosed (20% required), ship order C.O.D. for balance. (New U.S. stamps, check or money order accepted.)

Circle Item No. wanted: 11 12 16 24 23 30 32 33 34 35 36

Name Address

City State

Send remittance by check, stamps or money order; register letter if you send cash or stamps.

6-Tube, 1.4 Volt Superhet.

(Continued from page 735)

various connections in the R.F. circuit; the filament, I.F. and A.F. circuits are wired with the stranded push-back hook-up wire.

The I.F. circuit should be aligned from the 460 kc. signal of a test oscillator if possible. However, in lieu of a test oscillator routine, the following procedure may be used. Plug in a pair of coils covering the 7 mc. amateur band and tune for one of the "dotter" stations usually heard in this region. A weak, steady signal is best for alignment purposes. Turn up the mixer regeneration control about three fourths way full-on and rotate the R.F. (mixer) trimmer condenser for maximum sensitivity. Now with an insulated screw-driver or neutralizing tool, beginning with the output I.F. transformer, adjust each I.F. trimmer screw for maximum signal strength.

The beat-frequency oscillator is built on a separate 4x3x1 1/2 inch chassis and is coupled to the 1N5-G detector control grid as indicated in Fig. 1. Condenser "C," indicated on the diagram, consists of two pieces of insulated hook-up wire about one inch long, loosely twisted together. The lead from the oscillator must be shielded right up to the point where it connects to condenser "C"; otherwise, the oscillator signal will get into the I.F. amplifier, causing the detector to block on strong signals.

If the receiver is to be used for c.w. code reception only, the beat-frequency oscillator may be omitted and the receiver aligned as follows: First, tune a "dotter" signal as outlined above and, with the detector out of oscillation, adjust the I.F. trimmers for maximum volume. Adjust the mixer regeneration control just below the point of oscillation and rotate the mixer and oscillator trimmers for greatest sensitivity. Now, while tuning back and forth across a signal, turn the output I.F. transformer grid trimmer screw to the right or left until the signal can be barely heard. Adjust the detector regeneration condenser until the 1N5-G is oscillating and advance the I.F. trimmer, still rotating the dial back and forth across the signal, until a point is found where one side-band is almost completely cut off.

The set will operate a loudspeaker with fairly good volume on most stations. When purchasing a speaker it is advisable to get a permanent magnet dynamic type fitted with a universal output transformer, which will permit accurately matched output from the 1A5-G audio amplifier. When using crystal headphones, an A.F. choke of about 30 henries, 15 ma. rating and an .05 mf., 600 volt condenser should be connected to the 1A5-G plate as shown in Fig. 1. Be sure that the coupling condenser is not leaky and is of good quality.

Either a doublet or single-wire antenna may be used with the receiver.

Coil Data

Grid Coil Spacing	Tickler Wire	Mixer Wire	Di.	Band
L3 4 turns 1"	L4 3 turns 20 E. 1"			10 meters
12 turns 1 1/2"	4 turns 20 E. 1"			20 meters
17 turns 1 3/4"	6 turns 22 E. 1 1/2"			40 meters
37 turns 1 3/4"	9 turns 26 E. 1 1/2"			80 meters
58 turns 1 3/4"	14 turns 28 E. 1 1/2"			160 meters
	L2 same wire and number of turns as for tickler.			

Oscillator Coils

Grid Coil Spacing	Tickler Wire	Mixer Wire	Di.	Band
L6 4 turns 1"	L5 3 turns 20 E. 1"			10 meters
12 turns 1 1/2"	4 turns 20 E. 1"			20 meters
15 turns 1 3/4"	6 turns 22 E. 1 1/2"			40 meters
32 turns 1 3/4"	9 turns 26 E. 1 1/2"			80 meters
52 turns 1 3/4"	16 turns 28 E. 1 1/2"			160 meters

All coil forms are 5-prong types. All ticklers close-wound on "cold" or ground end of form.

NEWEST RADIO APPARATUS

New Band-Switching Pre-Selector

● A NEW 5-band pre-selector, which has continuous coverage from 5 to 185 meters (1.6 to 64 mc.) with band-switching, has been announced by the Browning Laboratories, Inc.


The unit employs an 1852 tube as regenerative r.f. amplifier. Image rejection ratios of 500 or more are obtainable, while the use of a high-Q tuned antenna system affords marked gain in the signal-to-noise ratio. r.f. amplification may be as high as 800, even on the 5 and 10 meter bands, depending upon the amount of regeneration used. The main tank condenser with electrical band-spread, used for tuning, is provided with a dial calibrated for each of the five bands.

The unit, which is known as model No. BL-5DX, includes a filament transformer so that it may be used with any receiver. It may be had either in kit form or completely assembled.

refinements in its "gun" structure to obtain better focus and modulating characteristics. The electron gun is operated at the same potentials and in the same manner as other tubes of corresponding type and screen diameter.



New Set Tester

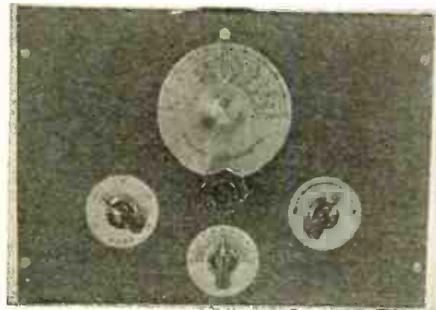

Full Line of Dual Atoms

● THE Sprague midget line now includes a full line of dual combinations which, according to the manufacturer, are the only small duals having common negative leads. The new line includes a



450 V. 8-8 mf.; a 50 V. 10-10 mf.; 200 V. 16-16 and 8-16 mf. units; a 250 V. 6-18 mf.; and 450 V. 8-16 mf. The condensers are hermetically sealed.

New Resistor Line

● A NEW line of carbon fixed resistors of solid molded construction, permanently bonded into one compact unit, has been announced by Consolidated Wire & Associated Corporations. These resistors are guaranteed within 10% plus or minus and variation is maintained within a 5% average. They are completely moisture-proof and non-inductive, having no capacity effect, and maintaining resistance value over an extremely wide temperature range.

The same company also announces an iron core, double-tuned, band-expanding I.F. transformer. Their new transformer line includes air core and iron core I.F. transformers, mica-trimmed, permeability-tuned, double and triple-tuned units; antenna, r.f., and oscillator coils; chokes, replacement primary windings, etc. These coils are pre-aligned and checked to assure their ready interchangeability and easy installation. Each is treated with a special moisture proof compound to insure permanence in the original adjustment.

Intensifier Type Cathode-Ray Tube

● A NEW type of television tube, called the "Intensifier," is considered by its manufacturers as "the first fundamental improvement affecting sensitivity since the inception of cathode-ray tubes 40 years ago."

The intensifier electrode takes the form of one or two metallic deposit rings near the screen end of the cathode-ray tube, and serves to accelerate the electrons after deflection, to afford increased brilliance without corresponding loss in deflection sensitivity.


The DuMont 54-9-T five-inch tube is provided with the intensifier feature, as well as several

● A NEW set tester, which indicates the presence of a signal throughout all sections of a receiver, draws no current from the circuit at any time. There are four input connections, one of which is a co-axial cable for use on ultra-high frequencies. The input impedance consists of approximately 5 muf. Three of the inputs operate on AC, and one on AC or DC.

The circuit incorporates electronic rather than radio engineering principles, and makes use of four 6E5's, two 6F8's and one 76, AC output.

The instrument, known as the "Million Signalyzer," simulates the functions of a vacuum tube voltmeter, output indicator and potential measuring device. It permits any 4 sections of a set to be checked simultaneously and a service man can learn its use in five minutes, its sponsors say.

New Type of Switch

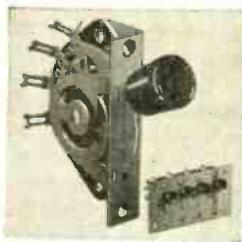

● A LOW capacity lever-action switch has just been announced by the Centralab concern. The switches are similar to toggle switches in their action, as far as the operating lever is concerned, but the contacts are more like those of the familiar rotary switches. They take up an

extremely small amount of space on the panel, and multiple mounting plates are provided so that they may be conveniently grouped.

Coaxial Cable for Hams

● A NEW type of coaxial cable is being produced by the Transducer Corporation. This cable consists of a length of braided tinned copper sheath, a length of tinned copper cable and a large number of ceramic insulated beads of unique shape. The amateur makes his own coaxial cable by stringing the beads on the cable and then forcing them through the braided copper sheath. When the sheath is clamped to the end beads, the cable is ready for permanent use. It is flexible so that it may be employed for antenna lead-ins, cathode-ray tube uses, P.E. cell connections, etc. Its capacitance is 10 mmf. per foot and its characteristic impedance, 150 ohms.



they
actually
work



C-D Quietone RADIO INTERFERENCE FILTERS

Like all C-D products—Quietone Radio Interference Filters were tested under exaggerated "life" conditions before being introduced to the industry. That's why we can say with confidence . . . "THEY ACTUALLY WORK."

Don't overlook this opportunity to increase your sales with little or no effort. Extremely simple to install, unobtrusive in appearance and available in three colors to match room interiors. On your next call demonstrate Quietone—and see how easy it is to increase your profit on each and every call.

Remember—for new profits demonstrate C-D Quietones, the filters backed by the twenty-nine year C-D seal of quality. Attractively priced to retail from \$1.00 up. Cat. No. 166A on request.

Product of the world's largest manufacturer of capacitors



CORNELL-DUBILIER
ELECTRIC CORPORATION
1027 Hamilton Blvd., So. Plainfield, N. J.
Cable Address: "CORDU"

New Style and Performance to Modernize Your Equipment at Amazing Low Cost!

New TURNER Torpedo Crystal Microphone



MODEL 55C

Slide open cover. 15 ft. cable. Level -50DB. 50-7000 cycles. Free wiring diagrams.

It's easy and inexpensive to give your equipment up-to-date good looks and top-quality performance with the new Turner Torpedo. Impressive full-plated finish. Streamline design and absolute absence of peaks reduce feedback. Guaranteed to out-perform many mikes selling for 50% more! Works directly into grid of almost any amplifier. Order today.

Write for Bulletin 41-A. Learn all about the latest developments in microphones. Details and applications of all models given in Free Bulletin 41-A. Know your stuff about mikes: write for your copy today!

\$1595
LIST

THE TURNER CO.

CEDAR RAPIDS, IOWA

Licensed Under Patents of the Brush Development Co.

NEW 1939 CATALOG

● 248 PAGES ●

SHOWING ALL LATEST
NATIONALLY ADVERTISED
RADIO PARTS
AND EQUIPMENT
FOR EXPERIMENTERS
AND AMATEUR RADIO OPERATORS

Our 1939 Catalog Mailed Free on Request

CAMERADIO

963 LIBERTY AVE.
PITTSBURGH, PA.

30 TWELFTH ST.,
WHEELING, W. VA.

Established 1919

AMERICA'S MOST POPULAR RADIO BOOKS

We herewith present a selected collection of recent important radio books. We have selected these volumes because they represent the foremost radio books of their kind in print today. We publish no catalog. Order direct from this page. Prompt shipments will be made to you. Remit by money order or certified check. Register all letters containing cash.

RADIO ENGINEERING HAND BOOK , 850 pages, latest.....	\$4.90
PRACTICAL TELEVISION , 223 pages, 127 illus.....	\$3.69
ELEMENTS OF RADIO COMMUNICATION , 286 pages, 241 illus.....	\$2.98
RADIO PHYSICS COURSE , 992 pages, 510 illus.....	\$4.00
THE RADIO AMATEUR'S HANDBOOK , 448 pages, 126 illus.....	\$1.97
MODERN RADIO ESSENTIALS , over 200 pages, and over 100 illus.....	\$1.95
FOUNDATIONS OF RADIO , 145 illus.....	\$2.47
PHOTOCELLS AND THEIR APPLICATION , 332 pages, 180 illus.....	\$2.88
ELECTRONICS , 134 pages, 45 illus.....	\$1.95
SHORT WAVE RADIO HAND BOOK , 128 pages, 150 illus.....	\$1.00
PRINCIPLES OF RADIO , 478 pages, 306 illus.....	\$3.46
EXPERIMENTAL RADIO , 256 pages, 168 illus. Prepaid.....	\$2.69
MODERN RADIO SERVICING , 1300 pages, over 700 illus.....	\$4.00
RADIO TROUBLE-SHOOTER'S HANDBOOK , 518 pages, 134 illus.....	\$3.00
Both Books	\$6.50
DRAKE'S CYCLOPEDIA OF RADIO AND ELECTRONICS , 1050 pages, 1178 illus.....	\$4.88

FUNDAMENTALS OF RADIO , 426 pages, illustrated. Prepaid.....	\$3.46
HOW TO PASS RADIO LICENSE EXAMINATIONS , 1938 Edition, 201 pages, illustrated.....	\$2.00
RADIO CONSTRUCTION AND REPAIRING , 444 pages, illustrated.....	\$2.50
THEORY OF VACUUM TUBE CIRCUITS , 226 pages, 226 illus.....	\$3.00
PRINCIPLES OF RADIO COMMUNICATION , 988 pages, profusely illus.....	\$7.35
RADIO ENGINEERING , 813 pages, 475 illus.....	\$5.50
EXPERIMENTAL RADIO ENGINEERING , 346 pages, 250 illus.....	\$3.46
RADIO OPERATING QUESTIONS AND ANSWERS , 427 pages, 106 illus.....	\$2.50
OFFICIAL RADIO SERVICE HANDBOOK , over 1,000 pages, over 1,000 illus. Prepaid.....	\$3.92
OFFICIAL SHORT-WAVE RADIO MANUAL , 240 pages, many illustrations. Vol. 1 (1934) Prepaid.....	\$2.00
Vol. 2 (1935) Prepaid	\$2.50
OFFICIAL RADIO SERVICE MANUAL , Volume 4, 2,000 illus., over 400 pages Prepaid.....	\$3.43
OFFICIAL RADIO SERVICE MANUAL , Volume 5, over 3,000 illus., over 1,000 pages. Prepaid.....	\$6.86
OFFICIAL RADIO SERVICE MANUAL , Volume 6, over 1,200 pages, over 2,500 illus. Prepaid.....	\$6.86

15 HANDY-POCKET-SIZE RADIO BOOKS

Here are 15 up-to-date books on radio and air conditioning. Modern in every sense. ALL BOOKS UNIT-FORM—they contain 64 pages, 50 to 120 illustrations. All books written by well-known authors. Order by Number.

2. MODERN VACUUM TUBES
3. THE SUPERHETERODYNE BOOK
5. HOW TO BECOME A SERVICE MAN
6. BRINGING ELECTRIC SETS UP TO DATE
8. RADIO QUESTIONS AND ANSWERS
9. AUTOMOBILE RADIO AND SERVICING
10. HOME RECORDING AND ALL ABOUT IT
12. PUBLIC ADDRESS INSTALLATION AND SERVICE
13. ABC OF AIR CONDITIONING
14. POCKET RADIO GUIDE
15. ABC OF REFRIGERATION
16. PRACTICAL RADIO CIRCUITS
17. SERVICING WITH SET ANALYZERS
18. POINT-TO-POINT RESISTANCE ANALYSIS
19. PRACTICAL RADIO KINKS AND SHORT CUTS

PRICE PREPAID EACH BOOK..... **50c**


HOW TO ORDER

No C.O.D. orders. Our prices are not, as shown. Some of the books sent prepaid (in U.S. only). Those that are not thus listed are shipped collect if sufficient postage is not sent. Add 7% of price for postage.

RADIO PUBLICATIONS, 97 HUDSON ST., NEW YORK, N. Y.

Westinghouse Power Generator

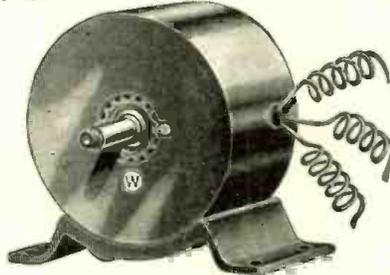Manufactured for U. S. Signal Corps
200 Watt. 110 V. AC



A. C. ELECTRICAL POWER

from a Windmill, from available Waterpower, from your Automobile, from your Motorcycle, from your Bicycle. Foot-pedals or Handcrank (for transportable Radio Transmitters, Strong Floodlights, Advertising Signs); do you want to operate AC Radio sets from 32 V. DC farm light systems; operate two generators in series to get 200 V. AC; obtain two phase and three phase AC, etc., etc.

There Are Over 25 Applications
Some of which are:

A.C. Dynamo lighting from eight to ten 20 Watt 110 Volt lamps. Short Wave Transmitter supplying 110 Volts AC for operating "Ham" transmitter. Operating 110 V. AC 60 Cycle Radio Receiver in DC districts. Motor Generator. Public Address Systems. Electric Sirens on motor boats, yachts, etc. Camp Lighting. Short Wave artificial "fever" apparatus. Television. Pelton Waterwheel for lighting or other purposes. Airplane: for lighting strong searchlights or electric signs. Laboratory work, etc., etc. ¼ to ½ H.P. needed to run generator.

BLUE-PRINT 22 x 28 in. and Four-Page 8½ x 12 in. INSTRUCTION SHEETS FREE with Generator.

Generator, as described, including four replacement carbon brushes. Blue-print and instructions..... **\$7.90**

Send \$2.00 deposit, balance C.O.D.


Shipping weight 18 lbs. (Replacement carbon brushes bought separate \$1.50 per set of four. Set of instructions bought separate \$1.00.)

MONEY-BACK GUARANTEE

WELLWORTH TRADING COMPANY

560 West Washington Blvd., Dept. RT-439, Chicago, Ill.

Radio Men Find This Book Handy

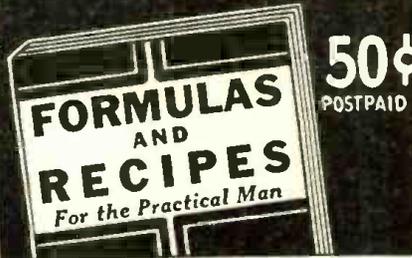

Here Is the Contents of the Book

1. Adhesives: Glues, Cements, Gums, Mucilages, Lubricants. 2. Cleansing: Stain Removers, Paint Removers, Bleaches, Cleaning Fluids. 3. Metal Craft: Coloring, Oxidizing, Plating, Repairing, Welding, Polishes, Alloys, Solders, Amalgams. 4. Paints: Colors, Stains, Varnishes, Enamels, Laminous Paint, Washable Paint; Paint-Removing, Waterproofing, Fireproofing. 5. Glass-Working: Cutting, Drilling, Boring, Bending, Blowing, Etching, Engraving, Frosting, Silvering, etc. 6. Wood-craft: Fillers, Fireproofing, Acid-proofing, Waterproofing, Furniture Polishes, Finishes, etc. 7. Inks: Recipes, Eradicators, Ink Stain Removers, Special Inks, Colored, Indelible, Sympathetic, Invisible, Hectograph. 8. Photography: Developers, Emulsions, Fixers, Sensitizing, Toning, Printing, Photographic Paper, Blueprint Paper. 9. Antidotes for Poisons, Remedies for Burns and Scalds, Disinfectants, First-Aid in Accidents, Emergency Remedies, Home Remedies. 10. Preparation, Manipulation, Handling, Mixing, Measuring, Weighing, Filtering, Straining Solutions; List of Technical Substances; Emulsifying; Use of Hydrometer, Use of Thermometer; Tables of Weights and Measures, Decimal Systems, Useful Tables.

TECHNIFAX, Division RT-439
560 W. Washington Blvd., Chicago, Illinois

TECHNIFAX, Division RT-439
560 W. Washington Blvd., Chicago, Illinois
Gentlemen: Enclosed please find 50c (check, money order, coin or unused U.S. stamps accepted) for which send me POSTAGE PREPAID. One Copy of FORMULAS AND RECIPES for the Practical Man.

Name.....
Address.....
City..... State.....

Rhumbatron

(Continued from page 712)

is based on some original ideas of Irving Metcalf of the former Bureau of Air Commerce.

"When Mr. Metcalf and John Easton, Chief of the Aircraft Section, Bureau of Air Commerce, first studied the principles of the Klystron and the Rhumbatron at the invitation of the Stanford authorities, they saw immediately a broad general field of application embracing, in addition to the blind landing system, a number of other projects including obstacle detection, collision prevention, traffic control, en route guidance, position fixes, and others.

"The Sperry Gyroscope Company, as one of the collaborators in the Metcalf blind landing development and as a manufacturing unit, assumed the responsibility of developing the Klystron in order to make sure that the finished product would fit the needs of the Bureau's blind landing system.

"Sperry's interest in this blind landing problem is very logical. The gyroscopic instruments, especially the directional gyro and the gyro-horizon have added very considerably to the safety of en route blind flying. The Metcalf blind landing system involves the application of modified gyroscopic instruments as well as considerable new radio technique.

"The research program surrounding this development has been conducted at Stanford University under the direction of Prof. D. L. Webster, executive head of the physics department. Other scientists who have played prominent roles include: R. H. and S. F. Varian, who are brothers; Prof. W. W. Hansen, associate professor of physics at Stanford; and Mr. John Woodyard, research associate in the physics department."

"Buncher" and "Catcher" = Klystron

Two rhumbatrons, called the "buncher" and "catcher," together with other apparatus, make the Klystron. Its name comes from the Greek verb "klyzo," denoting the breaking of waves on a beach. This is roughly descriptive of the action of the device, for in the buncher Rhumbatron is an oscillating electric field, parallel to a stream of electrons passing through it. The field is of such strength as to change the speeds of the electrons by appreciable fractions, accelerating some, slowing down others. After passing through the buncher, the electrons with increased speeds begin to overtake those with decreased speeds which are ahead of them. This motion groups the electrons into bunches separated by relatively empty spaces. By passing the stream through the catcher rhumbatron, within which is an oscillating electric field changing synchronously so as to take energy away from the bunched electrons, a considerable fraction of the power of the electron-bunches is converted into power of high-frequency oscillations.

Advantages of the Klystron principle are threefold. It produces strong waves; they are at stable frequencies; and they have strong amplification at the receiving end. The present working minimum wavelength employed by airlines in radio work is about one meter. But the Stanford Klystron produces waves one-tenth that length. Such waves, when emitted from a reflector one meter in diameter, would radiate within a narrow angle of only six degrees. The Klystron's inventors believe wavelengths considerably less than 10 centimeters can be reached, thereby still further narrowing the angle of radiation.

Electronic Television Course

(Continued from page 725)

order to transmit an image by television, we must pick up this image point by point and line by line, and transmit each point rapidly enough so that the eye may receive each complete picture in rapid enough succession to give the illusion of motion. Motion pictures in our theaters, when projected on a screen, are repeated at the rate of 24 pictures per second and each picture is interrupted twice by a shutter incorporated in the projecting apparatus, so that the eye receives 48 periods of light and 48 periods of dark for each second that we view the

radio frequency television transmitter, suitably coupled to an antenna for radiating the electrical impulses picked up and produced by the picture tube. The deflection circuits mentioned in the above paragraph serve to deflect the electronic cathode beam in a vertical and horizontal direction, while it sweeps the mosaic screen or target electrode, as the case may be. The vertical deflection circuit causes the beam to move from top to bottom 60 times per second and the horizontal deflection circuit causes the beam to move from left to right 13,230 times per second. The sequence in which the picture is scanned is as follows: lines, No. 1, 3, 5, 7, etc., to 220½ are scanned in the first 1/60th of a second (see Fig. 5-A). The beam then returns and scans lines Nos. 2, 4, 6, 8, etc., in other words, the beam scans one-half of the picture, then returns and scans the space between the lines previously scanned, giving us 60 half-frames or 30 complete frames or pictures per second. This process of scanning each picture twice, is called *interlaced scanning* because each pair of odd lines is interlaced by an even line. This is analogous to the motion pictures in the theater where each picture on the film is projected upon the screen twice while standing still in the projection aperture.

Interlaced scanning reduces the amount of flicker in a picture when viewed, because the eye receives two impulses of light; whereas in sequential scanning (scanning lines 1, 2, 3, 4, 5, 6, 7) the eye would perceive each picture but once and consequently the apparent projection rate would be slower and cause more flicker. During the interval of time that the vertical deflection circuit is sweeping the beam downward, the horizontal deflection circuit is moving the beam from left to right rapidly enough to scan 220½ lines. It might be well to mention at this point that the electronic beam moves in both directions; top to bottom and left to right in a linear manner, and when reaching the end of a line or frame returns to its starting point in 1/10th of the time that it took to travel the line or frame, as illustrated in Figure 5. It will be perceived that the voltage or current wave-forms assume the shape of a *saw-tooth* and it is for this reason that oscillators producing this wave shape are often termed *saw-tooth* oscillators. This quick return of the electronic beam causes a large signal in the output of the pick-up tube which is used at the receiving end for a synchronizing pulse. When delivered to the grids of the sweep circuit oscillators it causes them to keep in step with those of the transmitter, thus giving perfect synchronization between transmitter and receivers.

Due to the fact that the television signal is transmitted *negatively* (the carrier of the transmitter increases in amplitude for the black portions of a picture and decreases in amplitude for the whites), these synchronizing impulses represent the highest modulation capabilities of the television transmitter and when received they represent in the picture what may be termed "blacker than black" and consequently are of no significance, as far as the eye is concerned when viewing an image.

In Chapter No. 3, we shall discuss the radio and video frequencies involved in the transmission and reception of television images, the elements of cathode ray receiving tubes, electro-static and electro-magnetic deflection, and the modulation of a cathode ray electronic beam by the transmitted picture impulses.

Feature Articles April, 1939 RADIO-CRAFT

- Radio Abroad in 1938—A Review
- Manufactured Speech
- At Long Last—Static-Free Radio!—Part I
- Announcing the "Novachord"—Electronic Music's New 163-Tube "Baby"
- A Modern Amplifier for Recording and Playback
- An Easily-Built 3-Tube Midget Broadcast Superhet.
- A Home-Made String-Music Pickup
- Making a Shop-Type A.C. to D.C. Power-Supply
- How the "Beam-a-Scope" Works!

picture. In modern television, we have stepped up this rate of projection to 30 complete frames or 60 half-frames per second.

Television standards in the United States, as agreed upon by the Radio Manufacturers' Association *Television Committee*, standardized 441 lines per picture, 30 pictures per second, interlaced (i.e., 60 half-frame pictures), an aspect ratio of 3 to 4 (3 units in height to 4 in width) negative transmission and 10% of each line and frame allotted to synchronizing impulses. These standards and their relation to the transmission and reception of television images will be more fully explained in this and subsequent chapters of this course.

Figure No. 4 shows in block diagram the essential apparatus required for the transmission of a television image. It consists of an iconoscope, monoscope or image dissector, vertical and horizontal deflection circuits, amplifiers, power supplies, and a

Answers to QUIZ on page 719

1. b
2. aC, bE, cA, dF, eD, fB
3. c
4. c, minimum; d, maximum
5. d
6. a—too costly
7. c & d
8. all—though not all are classed as movie stars, their major activities being in other fields.
9. b
10. d
11. aC, bF, cE, dA, eB, fD
12. cA
13. d—KOIL, Blue; WOW, Red
14. c—experimental
15. c
16. Most often c or b; sometimes b & c; almost never a or d
17. b

for April, 1939

Please say you saw it in RADIO & TELEVISION

SPRAGUE ATOMS "Mightiest Midgets of All"

ECONOMICAL CONDENSERS

... for those
Economical Jobs

Just because they're the smallest midget dry electrolytics on the market—just because they're priced so amazingly low does not mean that Sprague ATOMS are cheap. Not by ten Juffula! And they've got more features than any other similar unit—more sizes—more voltages—more real "guts." They'll build up to higher surges with lower leakage and lower power factor. The exclusive Sprague vent **ABSOLUTELY GUARANTEES** against "blow-ups." ATOMS are self-supporting. You can mount 'em like paper tubulars, use 'em for any replacement job.

DUALS, TOO!

ATOMS are made in almost any needed dual combination—dual A or dual B—with common negative leads to simplify wiring. They fit in anywhere—and they're a whole lot better than most old style condensers many times their size. An 8 mfd. 450 V. ATOM lists at only 60¢—a dual 8-8 at only \$1. Ask your jobber today! Write for new Sprague Condenser Catalog.




SPRAGUE
450 VOLTS

SPRAGUE
PRODUCTS CO.
North Adams, Mass.

KORROL ALL METAL UTILITY CABINETS

Indispensable for keeping under lock and key all VALUABLE Parts including your QSL or SWL cards. Top drawer has 10 compartments for small parts. In the 6 and 8 drawer cabinets, the two lower ones are made into one unit to hold tubes, crystals, meters, pick-ups, camera lenses, films, micrometers, slide rules, etc. In the smaller compartments you can keep resistors, condensers, bolts, nuts, washers, etc., from being "borrowed".

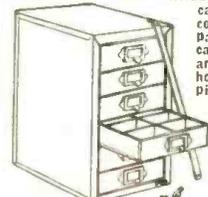

	Height	Depth	Width	List
6 drawers	9"	8 1/2"	6"	3.50
8 drawers	11 1/2"	8 1/2"	6"	4.50
Bar with lock and key				.50

Finished in wrinkle, olive green.
Amateur's Discount, 40%. Write for complete catalog.
Ask your dealer to show you a sample. If he has none, send your order direct.

KORROL RADIO PRODUCTS CO.
35D Greenwich St., Dept. 439, New York City

If It's a CANNON-BALL It is a GOOD HEADSET



Scientifically Built
Heavy bar magnets greatly increase their efficiency.

For clarity of tone use Cannon-Ball sensitive phones. Assure dependable performance. Guaranteed to give absolute satisfaction. Write Headset Headquarters for folder T-4 illustrating complete line.

C. F. CANNON COMPANY
SPRINGWATER, N. Y.

Mc.	Call	Station
6.090	CRCX	TORONTO, CAN., 49.26 m., Addr. Can. Broadcasting Corp. Daily 7.45 am.-5 pm., Sun. 10.30 am.-12 n.
6.090	ZBW2	HONGKONG, CHINA, 49.26 m., Addr. P. O. Box 200. Irregular.
6.083	VQ7LO	NAIROBI, KENYA, AFRICA, 49.31 m., Addr. Cable and Wireless, Ltd. Mon., Fri. 5.30-6 am., 11.15 am.-2.15 pm., also Tues. and Thurs. 8.15-9.15 am.; Sat. 11.15 am.-3.15 pm.; Sun. 10.45 am.-1.45 pm.
6.081	YVIRD	MARACAIBO, VEN., 49.32 m. 6-11 pm.
6.080	W9XAA	CHICAGO, ILL., 49.34 m., Addr. Chicago Fed. of Labor. Relays WCFL Irregular.
6.079	DJM	BERLIN, GERMANY, 49.34 m., Addr., Broadcasting House. 4.50-11 pm.
6.077	OAX4Z	LIMA, PERU, 49.35 m. Radio National 7 pm.-1.30 am. Except Sun.
6.075	VP3MR	GEORGETOWN, BRI. GUIANA, 49.35 m. Sun. 7.45-10.15 am.; Daily 4.45-8.45 pm.
6.070	CFRX	TORONTO, CAN., 49.42 m. Relays CFRB 7.30 am.-12 m., Sun. 10 am.-12 m.
6.070	VE9CS	VANCOUVER, B. C., CAN., 49.42 m. Sun. 1.45-9 pm., 10.30 pm.-1 am.; Tues. 6-7.30 pm., 11.30 pm.-1.30 am. Daily 6-7.30 pm.
6.069	—	TANANARIVE, MADAGASCAR, 49.42 m., Addr. (See 9.53 mc.) 12.30-12.45, 3.30-4.30, 10-11 am., Sun 2.30-4.30 am.
6.065	SBO	MOTALA, SWEDEN, 49.46 m. Relays Stockholm 4.15-5 pm.
6.060	—	TANANARIVE, MADAGASCAR, 49.5 m., 12.30-12.45, 3.30-4.30, 10-11 am.


World S-W Stations

(Continued from page 732)

Mc.	Call	Station
6.060	W8XAL	CINCINNATI, OHIO, 49.5 m., Addr. Crosley Radio Corp. Relays WLW Tues., Fri., Sun. 5.45 am.-12 n., 11 pm.-2 am.; Wed. 5.45 am.-12 n., 9 pm.-2 am.; Mon., Thurs., Sat. 5.45 am.-2 am.
6.060	W3XAU	PHILADELPHIA, PA., 49.5 m. Relays WCAU Tues., Fri., Sun. 1 pm.-Mid. Wed. 1-10 pm.
6.057	ZHJ	PENANG, FED. MALAY STATES, 49.51 m. 6.40-8.40 am., except Sun., also Sat. 11 pm.-1 am.
6.054	HJ6A8A	PEREIRA, COL., 49.52 m. 9.30 am.-12 n., 6.30-10 pm.
6.050	GSA	DAVENTRY, ENGLAND, 49.59 m., 10.45 am.-12 n., 12.20-4, 4.15-6 pm.
6.050	HJIABG	BARRANQUILLA, COL., 49.65 m., Addr. Emisora Atlantico. 11 am.-11 pm.; Sun. 11 am.-8 pm.
6.050	HP5F	COLON, PAN., 49.59 m. Addr. Carlton Hotel. Irregular.
6.045	RV15	KHABAROVSK, U.S.S.R., 49.63 m. 2-11 am.
6.045	XETW	TAMPICO, MEXICO, 49.6 m. Irregular 7-11 pm.
6.040	W4XB	MIAMI BEACH, FLA., 49.65 m. 1-3 pm., 9 pm.-12 m. Relays WIOD.
6.040	W1XAL	BOSTON, MASS., 49.65 m. Addr. University Club. Irregular.
6.033	HP5B	PANAMA CITY, PAN., 49.75 m., Addr. P. O. Box 910. 10.30 am.-2, 6-10 pm.
6.030	VE9CA	CALGARY, ALTA, CAN., 49.75 m. Thur. 9 am.-1 am.; Sun. 12 n.-12 m.

Mc.	Call	Station
6.030	RV59	MOSCOW, U.S.S.R., 49.75 m. 5-6, 10-11 pm. Irregular.
6.030	OLR2B	PRAGUE, CZECHOSLOVAKIA, 49.75 m. (See 11.875 mc.) Off the air at present.
6.023	XEUW	VERA CRUZ, MEX., 49.82 m., Addr. Av., Independencia 98. 10 pm.-1 am.
6.020	DJC	BERLIN, GERMANY, 49.83 m., Addr. (See 6.079 mc.) 1-4.30 pm.
6.017	H13U	SANTIAGO DE LOS CABALLEROS D. R., 49.85 m. 7.30-9 am., 12 n.-2 pm., 5-7 pm., 8-9.30 pm.; Sun. 12.30-2, 5-6 pm.
6.015	PRA8	PERNAMBUCO, BRAZIL, 49.84 m., Radio Club of Pernambuco, 4-9 pm.
6.010	OLR2A	PRAGUE, CZECHOSLOVAKIA, 49.92 m., Addr. (See OLR, 11.84 mc.) Wed., Thurs., 4.40-5.10 pm.
6.010	COCO	HAVANA, CUBA, 49.92 m., Addr. P. O. Box 98. Daily 7.55 am.-12 m., Sun. until 11 pm.
6.010	VK9MI	S. S. KANIMBLA, 49.92 m. (Travels between Australia and New Zealand.) Sun., Wed., Thurs. 6.55-7.30 am.
6.010	CJXC	SYDNEY, NOVA SCOTIA, 49.92 m. Relays CJCB 7 am.-1 pm., 4-8 pm. 1.30 pm. 8.30 pm.
6.007	ZRH	ROBERTS HEIGHTS, S. AFRICA, 49.94 m., Addr. (See ZRK, 9.606 mc.) Daily exc. Sun. 10 am.-3.30 pm.; Sun. 9 am.-12 n., 12.15-3.15 pm. Daily exc. Sat. 11.45 pm.-12.50 am.
6.007	ZRJ	JOHANNESBURG, S. AFRICA, 49.94 m., Addr. S. African Broadcast. Co., 3.30-4 pm. exc. Sun.
6.005	HP5K	COLON, PAN., 49.96 m., Addr. Box 33, La Voz de la Victor. 7-9 am., 10.30 am.-1 pm., 5-11 pm.

(Continued on page 761)

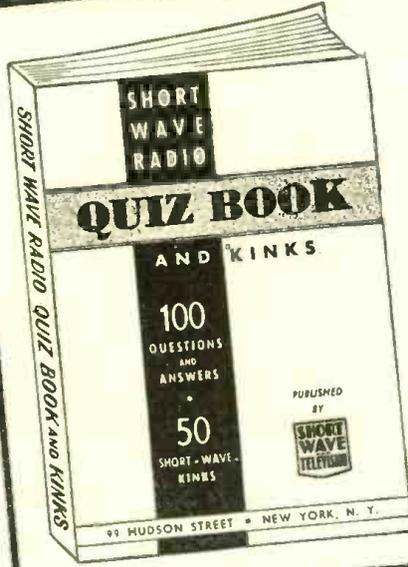

Get Any ONE or ALL FREE!

of These Books Absolutely

HERE is a brand new book—with an unusually interesting content. The text prepared by the Editorial Staff of RADIO AND TELEVISION, contains a variety of material which only experts could select and incorporate in such an excellent volume.

“SHORT WAVE RADIO QUIZ BOOK AND KINKS” cannot be bought—it is sent to you absolutely FREE with your subscription to RADIO AND TELEVISION at the Special Rate of Seven Months for One Dollar. (Old subscribers may get this book by extending their subscription.)

The book contains 64 pages with a heavy flexible colored cover. It measures 5½ x 8½ inches, and includes hundreds of photographs and diagrams. The contents are outlined below.

Contents of the “QUIZ BOOK”


- Questions and Answers Covering S-W transmitters.
- Questions and Answers Covering S-W Receivers.
- Ultra-Short-Wave Transmitters and Receivers.
- S-W “Kinks”—Short-cuts and Practical Wrinkles. Coil Winding Data.
- How to Add an Audio Amplifier to a Small S-W Receiver.

HOW TO “HOOK UP”

- How to Connect an R.F. Stage Ahead of Your Present Receiver.
- Dozens of Novel New Hook-Ups for the S-W Experimenter.
- Clear diagrams showing how to connect the latest type tubes in place of your old tubes, so as to obtain greater DX.

RADIO AND TELEVISION • 99 HUDSON STREET • NEW YORK, N. Y.

TWO OTHER FREE BOOKS FOR YOU!

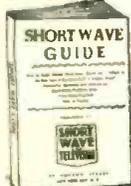

SHORT WAVE GUIDE

Covers hundreds of Short-Wave questions and answers; illustrates popular Short-Wave kinks; gives instructions for building simple Short-Wave receivers; instruction on the best type of antenna to use; diagram and construction details for building a simple “ham” transmitter; practical hints on Short-Wave tuning.



ABC OF TELEVISION

Contains latest material on Television developments. It covers theory of scanning; simple television receiver, how the eye sees; the photo-electric cell; neon lamps; need for broad channel width in transmission of high-fidelity television signals; cathode ray tube and television receivers; Farnsworth system of television transmission, and other features.

RADIO AND TELEVISION, 99 Hudson Street, New York, N. Y. R&T-4-39

Gentlemen: Enclosed you will find my remittance of \$..... for which enter my subscription to RADIO AND TELEVISION as checked below; also send me, postpaid, the book or books which I have marked at the right.

S-W RADIO QUIZ BOOK AND KINKS

ABC OF TELEVISION

SHORT WAVE GUIDE

7 months—\$1.00—choice of any one of three (3) books. (Canadian and foreign—\$1.30)

14 months—\$2.00—choice of any two (2) of the three (3) books. (Canadian and foreign—\$2.60)

21 months—\$3.00—all three books. (Canadian and foreign—\$3.90)

I am a subscriber now, we will extend your present subscription. Old subscriber

New subscriber

Name..... Address.....

City..... State.....

Send your remittance by check or money order. If you send cash or unused U.S. postage stamps, please be sure to register your letter for your own protection.

Let's Listen In with Joe Miller

(Continued from page 727)

(I.D.A.) XGAP verifies promptly. Reports on XPSA, 7.01 mc., Kweiyang, are desired. Don Williams, W6, reports XPSA.

JAPAN

JLG, 7.285 mc., Tokio, is broadcasting daily to Europe from 2:30-4 p.m., but very difficult to hear on East Coast, being in the 40 meter amateur band, and too early for such a frequency to be well heard, even if in the clear.

New "Jap" phones to be added recently are: JVV, 7.26; JVV2, 9.673; JVV3, 11.725; JVV4, 17.823 mc. (I.D.A.)

JIA, on approximately 15.80 mc., in Formosa, recently QSL'd by Jap phone QRA, along with JVL, another phone. JIA was heard at 3:30 a.m., but may also be heard much later, being frequently logged at 6-7:30 a.m.

Murray Buttekan reports JFZC, 17.64 mc., the Chichibu Maru, at 7:45 a.m., JVT, 6.75 mc., at 3:50 a.m., and JVA, 18.91 mc., at 7:30 a.m. FB OMI Ralph Gozen, also W2, got a JVJ veri. JVE, 15.66 mc., heard here at 8:10 a.m.

Anyone reporting Jap phones now will receive a very prompt and certain reply, if report correct, with their new attractive card, recently illustrated, so now is the time to clean up on J's!

U.S.S.R.

RV15, 4.275 mc., at Khabarovsk, Siberia, will positively not verify, according to letter received from Radio Centre, Moscow, recently received by Harold B. Clein, W6. We had wondered why our report of RV15 was not answered, but this clears things up, although a big disappointment.

Gail T. Beyer, W9, reports similar failure to elicit a QSL for ROU, Omsk, from Moscow, so it seems the only stations in the U.S.S.R. that may be verified are S-W Broadcasters in Moscow, RKI, 15.083 mc., and RAN, 9.60 mc., reported on Sunday at 10 p.m., with RKI very strong, by Daryl Sebastian.

ANGOLA

CR6AA, 7.614 mc., at Lobito, was recently "logged," but with a weak signal, at 4:30 p.m. on a Saturday. CR6AA operates Weds. and Sat., 2:45-4:45 p.m., and supposed to be also on Monds., but has never been heard or reported on this day. This makes 3 freqs. heard on this "FB" catch, the 9.6 and 7.177 mc. sigs being verified.

DX REVIEW

TAHITI—FO8AA, 7.10 mc., Papeete, is not QSL'ing reports, according to numerous complaints from readers. We don't know what can be done, except that registered reports may help. FO8AA always has had a bad "rep" for QSL's, but though answering after long delays, usually has come through. We will send a copy of this issue of our column to FO8AA, when published, hoping notice will be taken of this item by the Station Director, and the situation remedied.

FRENCH MOROCCO—CNK, 12.83 mc., Rabat, heard using the usual side-band secrecy transmission at 3:30 a.m., when frequently logged.

NORWAY—LKC, 9.53 mc., Oslo, has been verified by Ray A. Bernhardt, W6, a nice catch for West Coast. LKQ, 11.72 mc., is also reported on same schedule, 4:30-9 a.m., daily, Sun., from 2:30 a.m. Another transmitter on 15.166 mc. is reported on after 10:30 a.m., but may be only on Sundays. (I.D.A.)

TURKEY—TAP, 9.465 mc., Ankara, continues

to pound in afternoons till 5 p.m., or so during week-ends. TAQ, 15.195 mc., is reported on daily 5:30-7 a.m. W. G. Layton, W3, states that the reason why no QSL's of the Turkish stations have been received, at least as yet, is due to the very poor mail service there. Mr. Layton relates he once was in Turkey, and after mailing some 50 letters to the U. S. from there, found that not one ever reached its destination! He adds that evidently the P.O. employees collect stamps, hi! Turkish Ambassador, please note. This mention is made in the light of universal plams regarding lack of answers from TAP—TAQ reports. Ian Jamieson, England, reports TAP at 3 p.m. on.

JOTTINGS

Bert Wolfe, W6, reports the first VU card veri. from VUD2. Also reported by Bert is a very handsome QSL from ZHP, Singapore, FB! Bert says Bangkok, Siam, and CSW will not QSL to him.

G. C. Gallagher, W6, reports a "FB" QSL in ZHO, 6.185 mc., Singapore. A nice catch, OM! Jack Wells recently got a FB YCP, Dutch Borneo veri, and gives our 'ol column all the credit. Thanks, Jack! He also was sent a clipping of a New Zealand paper in which his excellent report of VK9MI, S.S. *Kambla*, was commented upon, this by Miss Eileen Foley, who answers the reports on 9MI. Whatta thrill!

Hal Clein, W6, states ZNB, which FB catch in Buchanaland, recently QSL'd to him, is the friendliest station on the air, judging from his very courteous, personal letter from the operator, Chips Britz. ZNB sends a gorgeous QSL, recently shown here.

HAM STARDUST

20 meters has been rather dead during the past month, mid-Jan. to mid-Feb., but the advent of the A.R.R.L. DX contest, and the fine DX conditions soon to be experienced as spring evidences itself, will doubtless bring much interest back to this usually reliable amateur band.

As this issue will be published just before the Contest begins, we hope a couple of tips will be of assistance to you.

Last year, European "hams" were heard between 1-4 a.m. on East Coast, and many rare calls were "logged," so watch 20 at this time, from the time you read this.

Then, too, some Asiatic DX may be heard between 2-4 a.m. as the J hams are licensed to operate at certain periods daily, and one of them is 2-4 a.m., when a number of J's were well heard last year. J's are also licensed to operate 6-8 a.m. This period is the best time, of course, for East Coast reception of Asiatics.

Africans can be heard during afternoons, and North Africans at same time as Europeans, which will roar in during afternoons, and occasionally, around 10-10:30 p.m. Europeans will often hold up during afternoons till 7 p.m.

Now to reports:

ASIA

VU2FU, 14375, India, announcing as "France, United," reported by Hal Clein, W6, who also reports a "beaut" of a QSL from VU2JN. "FB" DX, Hal!

VU2CO, 14120, and VU2BG, 14145, also reported by Gail Beyer, W9.

(Continued on following page)

NEW Pocket SIZE A.C.-D.C. Volt-Ohm- Milliammeter



Model
666-H
Net Price
\$14.50

5000 VOLTS SELF-CONTAINED

No External Multipliers Necessary

Ranges: AC-DC Voltage at 1000 ohms per volt 0-10-50-250-1000-5000; D.C. Milliamperes 0-10-100-500; Resistance 0-300 shunt (type 10 ohm reading at center scale); 0-250,000 series (type, 3700 ohms at center scale).

Complete in Bakelite case—size 3 1/16" x 5 7/8" x 2 3/4" with exclusive Triplett Low Loss Selector Switch.

Net Price\$14.50

Model 666—same case as above. Reads to 1000 volts AC and DC without external multipliers.

Net Price\$14.00


See Your Jobber—Write for Catalog!

Section 284 Harmon Ave.

TRIPLETT ELECTRICAL INSTRUMENT CO.

Bluffton, Ohio

PYRO PANTAGRAPH

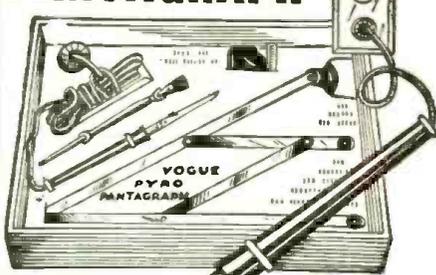

Size of Box:
12 1/2 x 8 1/2
inches

\$2.75

VOGUE

Shipping weight, 3 lbs.

THIS electrical outfit is especially designed for burning designs permanently on materials such as Leather, Wood, Cork, Bakelite, etc. Plug the Pyro-electric pencil in any 110 volt AC or DC outlet and it is ready to be used. Plug and cord furnished.

By the use of the Pantagraph included in the outfit, any design may be reproduced either in original, reduced or enlarged form.


Outfit consists of: one Pyro-electric Pencil; one Pantagraph; three hardwood plaques; one bottle of Varnish; one Brush; one tracing tip and four-page instruction sheet.

Size of box: 12 1/2 x 8 1/2 inches.

Outfit will be forwarded by Express Collect if not sufficient postage included with your order.

WELLWORTH TRADING CO.

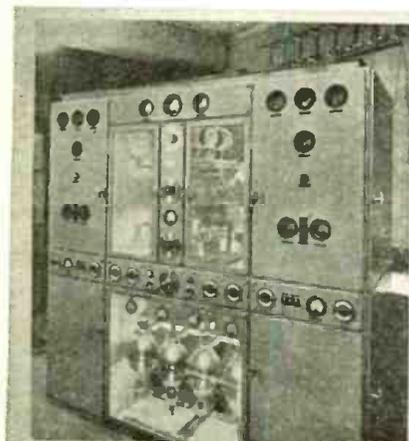558 W. Washington Blvd. Dept. RT-439 Chicago, Ill.



The 1 kW transmitter You have heard. The two crystal controlled oscillators corresponding to two wave-lengths are on both sides of the high level modulated power amplifier.

The Finnish Short Wave Broadcasting Transmitter at Lahti, Suomi (Finland)

Georg. loc. 25° 39' E, 60° 59' N

Mr. Joseph H. Miller

We acknowledge with thanks Your report on our short wave transmissions. It checks well with our own log and we would be pleased to receive further reports from You of the audibility of our other wave-lengths. They are:

M.	Kc.	GMT.
QFD - 31.58	9500	07.11-22.00
OPE - 25.47	11780	06.00-17.05
OIE - 19.75	15190	06.05-09; 14-22
OIH - 16.85	17800	09-14.
OII - 13.92	21550	

Our short wave transmitter is daily on the air and usually relays the regular Finnish Broadcasting Programmes.

8.12.38. Oy. Suomen Vleisradio Ab.


Lahti Vleisradioasema

Lahti, Suomi (Finland)


An Attractive "Veri" Card—one to be proud of.

8 GREAT 10 CENT RADIO BOOKS

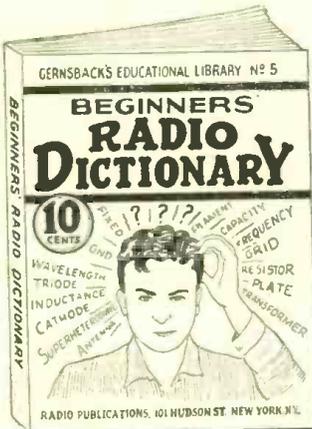RADIO FANS EVERYWHERE—these fine ten cent text books give you an excellent foundation for the study of radio. They are clearly written, profusely illustrated and contain over 15,000 words in each book. You'll be amazed at the wealth of information these books have. Handy for review or reference. **Your money back if you are not pleased!**



FAMOUS GERNSBACK EDUCATIONAL LIBRARY
ADDS FOUR NEW BOOKS!

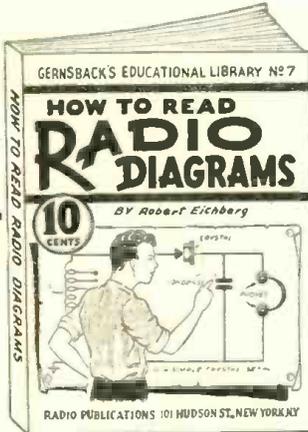


NO. 5—BEGINNERS' RADIO DICTIONARY

Are you puzzled by radio language? Can you define frequency? Kilocycle? Tetrode? Screen grid? Baffle? If you cannot define these very common radio words and dozens of other, more technical, terms used in all radio magazines and instruction books, you need this book in your library. It's as modern as tomorrow—right up to the minute. It tells you in simple language just what the words that puzzle you really mean. You cannot fully understand the articles you read unless you know what radio terms mean. This is the book that explains the meanings to you. Can you afford to be without it, even one day longer?

NO. 7—HOW TO READ RADIO DIAGRAMS

All of the symbols commonly used in radio diagrams are presented in this book, together with pictures of the apparatus they represent and explanations giving an easy method to memorize them. This book, by Robert Eichberg, the well-known radio writer and member of the editorial staff of RADIO-CRAFT magazine, also contains two dozen picture wiring diagrams and two dozen schematic diagrams of simple radio sets that you can build. Every diagram is completely explained in language which is easily understood by the radio beginner. More advanced radio men will be interested in learning the derivation of diagrams, and the many other interesting facts which this book contains.

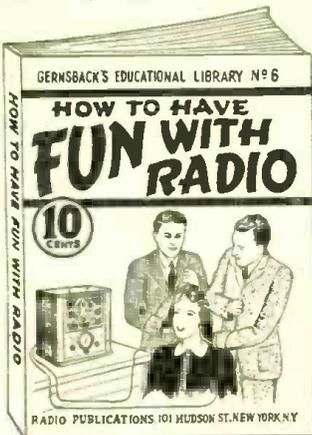

NO. 6—HOW TO HAVE FUN WITH RADIO

Stunts for parties, practical jokes, scientific experiments and other amusements which can be done with your radio set are explained in this fascinating volume. It tells how to make a newspaper talk—how to produce silent music for dances—how to make visible music—how to make a "silent radio" unit, usable by the deafened—how to make toys which dance to radio music—sixteen clever and amusing stunts in all. Any of these can be done by the novice, and most of them require no more equipment than can be found in the average home. Endless hours of added entertainment will be yours if you follow instructions given in this well illustrated book.

4 Other Titles in This Series!

- Four other volumes in this ten-cent radio book series—each on a popular subject—are available. The titles are:
- No. 1—HOW TO BUILD 4 DOERLE SHORT-WAVE SETS
 - No. 2—HOW TO MAKE THE MOST POPULAR ALL-WAVE 1- AND 2-TUBE RECEIVERS
 - No. 3—ALTERNATING CURRENT FOR BEGINNERS
 - No. 4—ALL ABOUT AERIALS

BOOKS ARE ALL UNIFORM

Every book in the GERNSBACK EDUCATIONAL LIBRARY has 32 pages—with illustrations varying from 30 to 66 in number. Each title volume contains over 15,000 words. Positively radio's greatest book buys! If you do not think these books worth the price asked, return them in 24 hours and your money will be instantly refunded.


RADIO PUBLICATIONS
 101 HUDSON STREET NEW YORK, N. Y.

WIN \$10

by suggesting a title for a new Gernsback book! Each of these books gives full details.

PRIZE WINNERS

- ALFRED CETTIE
Seattle, Wash.
Title: ALL ABOUT AERIALS, Book 4
- RUDY RUZICKA
St. Louis, Mo.
Title: BEGINNERS' RADIO DICTIONARY, Book 5
- KENNETH WARNER
Burbank, Ohio
Title: HOW TO READ RADIO DIAGRAMS, Book 7
- CLYDE SORRELL
Rockyford, Colo.
Title: RADIO FOR BEGINNERS, Book 8

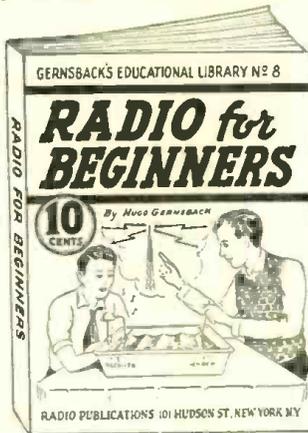

NO. 8—RADIO FOR BEGINNERS

Hugo Gernsback, the internationally famous radio pioneer, author and editor, whose magazines, RADIO & TELEVISION and RADIO-CRAFT are read by millions, scores another triumph with this great book. Any beginner who reads it will get a thorough ground work in radio theory, clearly explained in simple language, and through the use of many illustrations. Analogies are used to make the mysteries of radio as clear as "2+2 is 4". It also contains diagrams and instructions for building simple radio sets, suitable for the novice. Book tells you how transmitters and receivers work, how radio waves traverse space, and dozens of other interesting facts about this most modern means of communication.

MAIL COUPON TODAY!!

RADIO PUBLICATIONS, Dept. R&T-4-39
 101 HUDSON STREET, NEW YORK, N. Y.

Gentlemen: Please send immediately, POSTPAID, the book numbers circled below. I am enclosing...cents—each book being 10c.

1 2 3 4 5 6 7 8

Send FREE list of 48 special 10c publications.

Name

Address

City

State

Remit by check or money order—register letter if you send cash or unused U. S. postage stamps.

Let's Listen In with Joe Miller

(Continued from preceding page)

PK1JR, 14300; PK4KS, 14320; PK4JD, 14020, Java, reported by Mike Soplop, W8. PK4's are in Sumatra. PK4KS also reported by Ralph Gozen, W2. PK1RI, 14350, and PK4JD, 14090, reported by Ian Jamieson, England. PK1VM, 14100, and PK4KS reported by Gail Beyer. PK1GL, 14080, heard here at unusual time of 4:45 a.m.
 XZ2DY, 14350, logged at 7:45 a.m. by Mike Soplop, W8, a FB catch!
 KA1ME, 14260; KA1CS, 14145; KA7EF, Philippines, reported by Mr. Soplop, also. KA1ME also by Mr. Beyer.
 ZC6EC, 14316 (announced) Palestine, heard at 8 a.m. by Ralph Gozen, W2. A real ace!
 F18AC, 14080, French Indo-China, reported by Ian Jamieson, England. XU8ET, 14050, 9 a.m., by Mario Cassina, W2.

AFRICA

"ZS" stations too numerous to mention, and data on them will be of little use now, So. Africa having more or less faded out for the season.
 SU2JR, 14070, Egypt, by Ian Jamieson.
 VQ4ECJ, 14010, Kenya, logged here at 3 p.m., good sig.; also by Ralph Gozen.
 VQ2HC, 14070 and 14320, Northern Rhodesia, reported by Ian Jamieson. Also VQ2FJ, 14130, nice DX!

FB8AD, 14310, Madagascar, also by Ian. FB8AH, 14340, reported by Tom Jordan, W8. FB8AH also by Norm Kriebel, W8.

We skipped over VQ2PL, whose FB card is illustrated this month. VQ2PL reported on 14415 by Mr. Soplop and Mr. Kriebel. Peter Lowth, who is VQ2PL, tells us in the interesting letter: we received with his QSL that his ambition is to some time relay the roar of the famous Victoria Falls in Northern Rhodesia to the fellows here. It would be interesting, indeed! Peter is located but 5 miles from the Falls. Ralph Gozen also reports VQ2PL.

CN8AW, 14110; CN8BA, 14070; CN8AL, 14070 and 14110; CN8MT, 14100; CN8AN, 14040; CN8AY, 14130; CN8MB, 14068; CN8AI, 14070, all reported by Messrs. Kriebel, Gozen, Beyer and Y.T., besides Ted Bottema, so French Morocco is well represented this month! Also CN8MV, 14055, by Y.T.

Also from Egypt is reported SU1MW, 14130, and SU1AX, by Norm Kriebel, 1AX being reported on 14050 by Norm, and on 14028 by Gail Beyer.

ZE1JX, 14030, by Norm and Gail, and ZE1JR, 14074, by Ted Bottema, these in Southern Rhodesia.

CT3AB, 14050, 3:30 p.m., is a "FB" catch in Madeira, for Gail Beyer.

40 METERS

CT3AN, 7090, Madeira, heard regularly around 8:30 p.m., E.S.T., by Ian Jamieson, England.

CN8AJ, 7050, French Morocco, was logged by Norm Kriebel, along with other Africans and Europeans, from 1:30-4 a.m. CN8MT, 7050, by Ralph Gozen.

FA8AW, 7070, FA8CF, 7180, Algeria, also by Norm. FA3WW, 7260, and FA8CF by Ralph Gozen.

Best reception on this band was in early December.

OTHER DX

ZL2BE, 14210, and ZL2JO, 14260, heard after 7:30 a.m. by Norm Kriebel. These in New Zealand. ZL2BE, 14170, also by Ted Bottema.
 ZA1CC, 14130, Albania, reported by Ian Jamieson, at 2:15 p.m. Sun.

SV1CA, 14055, Greece, by Y. T. SP1MR, 14025, Poland, by Y. T. OH2OI, 14160, Finland, Y. T. and Mr. Gozen.

10 METERS

Some fine DX has been reported and heard on this band of late, and we do hope good conditions will continue on this exciting stretch of kilocycles.

From Africa, numbers of ZS stations are heard from 10 a.m.-2 p.m., peaking around noon.

Other Africans on 10 are: SU1MW, 28400, Y. T. and Norm Kriebel, this one from Egypt. ZE1JZ, 28400, So. Rhodesia, by Y. T.

CN8BA, 28150, CN8AV, 28150, in French Morocco, Y. T.

From Oceania are heard ZL2BE, 28500, and ZL2BT, 28400, by Norm Kriebel.

Also from New Zealand, Y. T. hears ZL3IF, 28600, ZL2FY, 28120, ZL2BT and ZL2BE, the latter usually very fine, along with 2FY.

From Greece, we have SV1CA, 28200.

From Latvia, on the recent I.D.A. special broadcast arranged by Roger Legge, an old reporter, and now editor of I.D.A.'s Ama-touring, we had the good fortune to hear a FB catch in YL2CD, 28080. YL2CD was heard R-7 solid, very good.

Some late tips from Hal Clein, W6: YN3DG, 14256, 7128, will gladly QSL, but only if a U.S. 10c piece is sent him. Also, XAR2LA, 14370, aboard a Norwegian freighter, giving his name as Gunnar, and is a ham in Oslo, when home.

We wish to thank all you OM's for the swell bouquets you've thrown at us, and do hope we can continue rating your praise. We sure appreciate it!


World S-W Stations

(Continued from page 758)

Mc.	Call	Station
6.005	CFCX	MONTREAL, CAN., 49.96 m., Can. Marconi Co. Relays CFCF 6.45 am.-12 m.; Sun. 8 am.-10.15 pm.
6.006	VE9DN	DRUMMONDVILLE, QUE., CAN., 49.96 m., Addr. Canadian Marconi Co.
6.002	CXA2	MONTEVIDEO, URUGUAY, 49.98 m. Addr. Rio Negro 1631. Relays LS2, Radio Prieto, Buenos Aires. 7.30-10.30 pm.
6.000	ZBA	SALISBURY, RHODESIA, S. AFRICA, 50 m. (See 6.147 mc., ZEB.) Also Sun. 3.30-5 am.
6.000	XEBT	MEXICO CITY, MEX., 50 m., Addr. P. O. Box 79.44. 8 am.-1 am.

End of Broadcast Band

5.977	CS2WD	LISBON, PORTUGAL, 50.15 m., Addr. Rua Capelo 5. 3.30-6 pm.
5.975	OAX4P	HUANCAYO, PERU, 50.16 m. La Voz del Centro del Peru. 8 pm. on.
5.970	YV5RC	CARACAS, VEN., 50.26 m., Addr. Radio Caracas. Sun. 7 am.-10 pm. Daily 7-8 am., 1-1.45 pm., 4-9.30 or 10 pm.
5.968	HVJ	VATICAN CITY, 50.27 m. Off the air at present.
6.950	HH2S	PORT-AU-PRINCE, HAITI, 50.37 m., Addr. P. O. Box A103. 7-9.45 pm.
5.936	YVIRL	MARACAIBO, VEN., 50.52 m., Addr. Radio Popular, Jose A. Higuera M. P. O. Box 247. Daily 11.43 am.-1.43 pm., 5.13-10.13 pm.; Sun. 9.13 am.-3.13 pm.
5.920	YV4RH	VALENCIA, VEN., 50.68 m. 5-9.30 pm.
5.900	ZNB	MAFEKING, BRI. BECHUANALAND S. AFRICA, 50.84 m. Addr. The Govt. Engineer, P. O. Box 106. 6-7 am. 1-2.30 pm. Ex. Suns.
5.900	TILS	SAN JOSE, COSTA RICA, 50.85 m. 6-10 pm.
5.898	YV3RA	BARQUISIMETO, VEN., 50.86 m., Addr. La Voz de Lara, 12 n.-1 pm., 6-10 pm.
5.885	HI9B	SANTIAGO, D. R., 50.95 m. Irregular 6-11 pm.
5.875	HRN	TEGUCIGALPA, HONDURAS, 51.06 m. 1.15-2.16, 8.30-10 pm.; Sun. 3.30-5.30, 8.30-9.30 pm.
5.855	HIJ	SAN PEDRO DE MACORIS, D. R., 51.25 m., Addr. Box 204. 12 n.-2 pm., 6.30-9 pm.
5.845	YVIR8	MARACAIBO, VEN., 51.3 m., Addr. Apartado 214. 8.45-9.45 am., 11.15 am.-12.15 pm., 4.45-9.45 pm.; Sun. 11.45 am.-12.45 pm.
5.825	TIGPH	SAN JOSE, COSTA RICA, 51.5 m., Addr. Alma Tica, Apartado 800. 11 am.-1 pm., 6-10 pm. Relays TIX 9-10 pm.
5.813	TIGPH2	SAN JOSE, COSTA RICA, 51.59 m., Addr. Senor Gonzalo Pinto, H.
5.790	TGS	GUATEMALA CITY, GUAT., 51.75 m. Casa Presidencial, Senor J. M. Caballero. Irregular.
5.758	YNOP	MANAGUA, NICARAGUA, 52.11 m. 8-9.30 pm.
5.740	YV2RA	SAN CRISTOBAL, VENEZUELA, 52.23 m., Addr. La Voz de Tachira. 11.30 am.-12 n., 5.30-9 pm., Sun. till 10 pm.
5.735	HCIPM	QUITO, ECUADOR, 52.28 m. Irregular 10 pm.-12 m.
5.145	OKIMPT	PRAGUE, CZECHOSLOVAKIA, 58.31 m., Addr. (See OLR, 11.84 mc.) Fri. 4.45-5.10 pm.; Sat. 5.15-5.40 pm.
5.145	PMY	BANDOENG, JAVA, 58.31 m. 5.30-11 am.
4.995	VUD2	DELHI, INDIA, 60.06 m., Addr. All India Radio. 7.30 am.-12.30 pm.
4.950	VUM2	MADRAS, INDIA, 60.61 m. Addr. All India Radio. 7 am.-12 n.
4.905	VUB2	BOMBAY, INDIA, 61.16 m. Addr. All India Radio. 7 am.-12.30 pm.
4.900	HJ3ABH	BOGOTA, COL., 61.19 m., Addr. Apartado 565. 12 n.-2 pm., 6-11 pm.; Sun. 12 n.-2 pm., 4-11 pm.

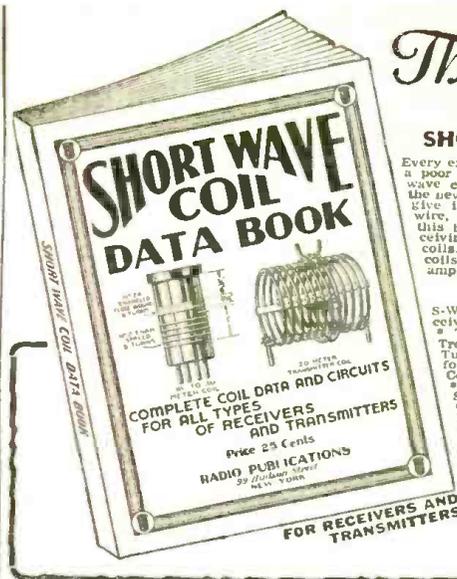

The 1 and ONLY

SHORT WAVE COIL DATA BOOK

Every experimenter knows that the difference between a good and a poor radio set is usually found in the construction of short-wave coils. Coil winding information is vitally important and in this book you will find all "dope" appears. There's illustrations which give instructions on how to wind coils, dimensions, sizes of wire, curves and how to plot them. Every experimenter needs receiving coils, together with many suitable circuits using these coils. Also complete data on various types of transmitting coils with many transmitting circuits such as exciters and amplifiers using the various coils described.

Contents Briefly Outlined

S-W Tuning Inductance Charts • Coil Data for T. R. F. Receivers • One Tube Oscillodyne • Two Tube Bandsreader • The Mono-Coil • 2-Tube Old Reliable • 2-Tube Globe Trotter • 2 Winding Coils—19,500 Meters • Dopic 3-Tube "Signal Gripper" Electrified • 3-Tube Bandsreader for the Ham • General Coverage Coils on Rinsed Forms • Coil Data for Superhet or S-W Converter • Ultra S-W Coils • Switch Coils for S-W Superhets • Experimental Coils • S-W Antenna Tuner • Most Popular S-W Tuning Circuits • Self-Supporting Transmitting Circuits Employing Coils Described • All Band Antenna Tuner for Transmitting • Plug-in Coils for Exciters • Frequency-Wavelength Conversion Chart.

PRICE 25c PREPAID

For a copy of this handy book, send 25c in U.S. Coin or stamps to

RADIO PUBLICATIONS
97 HUDSON STREET NEW YORK, N. Y.



HEY FELLOWS! 6 BACK NUMBERS OF SHORT WAVE AND TELEVISION SENT ANYWHERE IN U.S. FOR 70¢

For a limited time only, and as long as they last, we will send you six back numbers of **SHORT WAVE & TELEVISION** assorted, your choice, for 70 cents.

The usual price for six copies would be \$1.50, and most publishers charge a higher price for back numbers over one year old.

We can supply only the following back numbers: Dec., 1930; Feb., April, June, Sept., Oct., 1931; July, Oct., 1932; Jan., April, Oct., Nov., 1933; Jan., Feb., Mar., May, June, July, Aug., Sept., 1934; 1935—All issues except January, February and March; 1936, 1937, 1938—all issues; 1939—all issues to date.

If you do not specify copies, we will send assorted numbers to fill your order. Note, we cannot exchange the copies for ones that have been sent to you.

Every copy of **SHORT WAVE & TELEVISION**

contains information which you should have. Here is a chance to get those copies.


As only a small supply of back numbers on hand, this offer will be withdrawn as soon as they have been sold.

We accept U. S. stamps, U. S. coin, or money order. Rush your order today.

RADIO & TELEVISION	4-39
99-101 Hudson Street, New York, N. Y.	
Gentlemen: I enclose herewith 70c. for which you are to send me six back number copies of SHORT WAVE & TELEVISION as follows:.....	
Name	
Address	
City	State

Mc.	Call	Station
4.880	VUC2	CALCUTTA, INDIA, 61.48 m. Addr. All India Radio. 6.36 am.-12.06 pm.
4.880	HJ4ABP	MEDELLIN, COL., 61.44 m. 8-11 pm.
4.876	ZRD	DURBAN, SOUTH AFRICA, 61.5 m., Addr. (See ZRK, 9.606 mc.) Daily 12 m.-3.45 pm., Sat. till 4 pm., Sun. till 3.20 pm.
4.842	HJ3ABD	BOGOTA, COL., 61.95 m., Addr. La Nueva Granada, Box 509. 12 n.-2 pm., 7-11 pm., Sun. 5-9 pm.
4.800	HJ1ABE	CARTAGENA, COL., 62.46 m., La Voz de los Laboratorios Fuentes. Addr. Box 31. Daily 8.30 am.-11 pm., Sun. 10 am.-9 pm.
4.780	HJ1ABB	BARRANQUILLA, COL., 62.72 m. La Voz de Barranquilla, Addr. P. O. Box 715. 11.30 am.-1 pm., 4.30-10 pm.
4.772	HJ1ABJ	SANTA MARTA, COL., 62.85 m. 11.30 am.-2 pm., 5.30-10.30 pm. except Wed.
4.740	HJ6ABC	IBAGUE, COL., 63.25 m. 7 pm.-12 m.

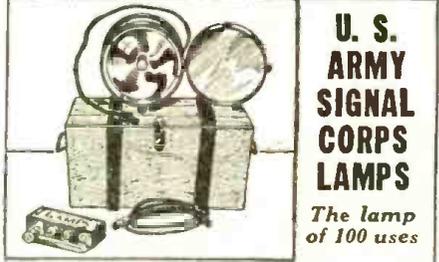Don't Miss—
Latest TELEVISION and FAC-SIMILE News
IN THE MAY NUMBER



U. S. ARMY SIGNAL CORPS LAMPS

The lamp of 100 uses

- Scout Signalling
- Night Bowling Alleys
- Trailer Lamp
- Night Motor Boat Races
- Auto, Truck and Trailer Camps
- Tractor Light
- Camp Light
- Barnyard Lighting
- Night Fishing
- Radio Shacks
- Bungalows
- Picnics, etc.



Large size—12 1/4" wide, 5 3/4" deep, 15" high including socket, fitted with 10" silver plated reflector (no glass, nothing to break). Packed in portable wooden carrying case, with hinged cover, hump and handles. Every case contains weatherproof extension cord and plug, 2 extra bulbs, telegraph signaling key and 16 page U. S. Army Instruction Manual. Shipping weight 18 lbs., Price \$25.00 (Cost the Government about \$25.00)

\$2.50

Send for catalog containing full descriptions of this and many other interesting items.

GOLD SHIELD PRODUCTS
Dept. RT-4-9 350 Greenwich St. New York

COMMERCIAL NOTICES 10¢ A WORD

Under this heading only advertisements of a commercial nature are accepted. Remittance of 10¢ per word should accompany all orders. Copy should reach us not later than the 10th of the month for the second following month's issue.

AGENTS WANTED

300% PROFIT SELLING GOLD Leaf Letters for Store Windows; Free samples. Metallic Co., 446 North Clark Chicago.

CORRESPONDENCE COURSES

CORRESPONDENCE COURSES and educational books, slightly used. Sold, Rented, Exchanged. All subjects. Satisfaction guaranteed. Cash paid for used courses. Complete details and bargain catalog free. Send name, Nelson Company, 3491 Manhattan Building, Chicago.

INSTRUCTION

RADIO ENGINEERING, BROADCASTING, aviation and police radio, servicing, marine and Morse telegraphy taught thoroughly. All expenses low. Catalog free. Dodge's Institute, Coll St., Valparaiso, Ind.

MISCELLANEOUS

7 MILLIAMMETER, HEAVY RUBBER insulation, high voltage lacquered cable, suitable for transmitter. 2¢ per

foot. Gold Shield Products, 350 Greenwich St., New York City.

PATENT ATTORNEYS

INVENTORS—PROTECT YOUR rights before disclosing your invention to anyone. Form "Evidence of Conception"; "Schedule of Government and Attorneys' Fees" and instructions sent free. Lancaster, Allwine & Rommel, 436 Bowen Building, Washington, D. C.

QSL—CARDS—SWL

100 NEAT SWL CARDS PRINTED with your name and address sent post-paid for \$1. Bunch of samples and RST Chart for five cents in stamps. WJBEF, 16 Stockbridge Ave., Lowell, Mass.

QSL SWL CARDS, SAMPLES Free. The Royal Press, Meriden, Conn.

RADIO

STOP—BEFORE YOU BUY A short wave receiver, send dime for our 24-page catalog containing circuit diagrams and information on over 25 Doerle short wave receivers and transmitters. See Dec. 1938 issue for page ad describing a few of our models.

Oscar B. Kusterman, 297 DeKalb Ave., Brooklyn, N.Y.C.

PLANS 18 RECORD-BREAKING Crystal sets, SW record 4250 miles, with "Radiobuilder"—year, 23c. Laboratories, 7700-A East 14th, Oakland, California.

ANY RADIO CIRCUIT DIAGRAM 25c. Order mentioning manufacturer's name, model, Catalog Free. Supreme Publications, 3727 West 13th, Chicago.

CRYSTAL SELECTIVE CRYSTAL set Plans 15c. Trent, Box 291, New Brunswick, N. J.

SHORT WAVE RECEIVERS

WE STILL HAVE A FEW USED Doerle receivers Models D-38, B85 and 7C, reconditioned by factory, at 40% off. See Dec. 1938 Radio and Television for description. Oscar B. Kusterman, 297 DeKalb Ave., Brooklyn, N.Y.C.

SONG POEMS WANTED

WANTED ORIGINAL POEMS, songs for immediate consideration. Send poems to Columbian Music Publishers, Ltd., Dept. K49, Toronto, Can.

FOR SALE (NON COMMERCIAL) 3¢ A WORD

Under this heading we accept advertisements only when goods are offered for sale without profit. Remittance of 3¢ per word should accompany all orders. Copy should reach us not later than the 10th of the month for the second following month's issue.

BRAND NEW RADIO BUG \$4.25 (money back guarantee). 160-80 meter crystals (ground) \$1.15; blanks; 160-80 meter \$1.85; 40-20 meter \$1.00, radio tubes (most popular types) only 20¢ each. Richard Dawson, 1308F, The Dalles, Oregon.

GHIRARDI'S "RADIO PHYSICS Course," second edition \$3.00. Hider's two books Servicing Superheterodynes, Servicing Sets by Instantaneous Measurement \$1.50. Frederick Aldridge, 1228 Shepard St., Petersburg, Virginia.

INTERNATIONAL CORRESPONDENCE School Radio Servicing Course, 1938 edition, complete \$10.00. Mostacello, 2714 Balnbridge Ave., New York City.

HAVE SW-3s, SKY BUDDIES, and other apparatus for sale. Send for List, John Womack, Dimmitt, Texas.

PRACTICALLY NEW INSTRUC- tion graph, seven tapes \$8.98. WILRV, 16 Sanger St., Medford, Mass.

SKY CHAMPION 8 TUBE RE- ceiver, perfect electrical mechanical condition \$35.00. Alvin Abrams, 20 Laurel Hill Terrace, N.Y.C.

SKY BUDDY \$15.00. SW3 \$12.50. FB7 \$19.00. RME-69 \$89.00. W9ARA, Butler, Missouri.

FOR SALE, SEVERAL NEW IN case \$10 3" PM speakers for 38 or 39 Buick \$10 or \$12 list. \$2.75. A. Jonas, 1019 Wood, Flint, Mich.

BARTER AND EXCHANGE — FREE!

NO ADVERTISEMENT TO EXCEED 35 WORDS, INCLUDING NAME AND ADDRESS

Space in this department is not sold. It is intended solely for the benefit of our readers, who wish to buy or exchange radios, parts, phonographs, cameras, bicycles, sporting goods, books, magazines, etc. As we receive no money for these announcements, we cannot accept responsibility for any statements made by the readers. Use these columns freely. Only one advertisement can be accepted from any reader in any one issue. All dealings must be above board. Remember you are using the U. S. mail in all these transactions and therefore you are bound by the U. S. Postal Laws. Describe anything you offer accurately and without exaggeration. Treat your fellow men the way you wish to be treated. We welcome suggestions that will help to make this department interesting and helpful to our readers. Copy should reach us not later than the 10th of the month for the second following month's issue.

accepted from any reader in any one issue. All dealings must be above board. Remember you are using the U. S. mail in all these transactions and therefore you are bound by the U. S. Postal Laws. Describe anything you offer accurately and without exaggeration. Treat your fellow men the way you wish to be treated. We welcome suggestions that will help to make this department interesting and helpful to our readers. Copy should reach us not later than the 10th of the month for the second following month's issue.

HAVE OVER 2,000 BOOKS TO trade for anything I can use. Your list for mine. M. Epstein, 2533 Ruckle, Indianapolis, Ind.

SWAP ANSLEY PORTABLE radio and phono, combination, AC-DC, Philco 20 and 90. Bradley's snowchows, Crosley model 51, two tube portable battery set, silver key wound watch, for Joseph Kubik, 37 Pine Street, Gt. Barrington, Mass.

HAVE FIFTEEN FIVE VOLUMES Science Wonder Stories Magazine complete, first class condition. Amazing Stories dating from August, 1928. Others. Send for list. Trade for communications receiver, radio equipment. J. H. Hood, 37 Club Drive, Greenville, S. C.

WANTED FOR COIN COLLEC- tion 1929 Liberty head nickel, also want Indian head pennies. Will swap 200 U. S. stamps for nickel or for four (4) Indian head pennies. Dawson, 1308F, The Dalles, Oregon.

TRADE AUTOMOBILE AND motorcycle license plates with collectors in other states and countries. Will buy if cheap. Swap shortwave set and big Western hat for old car. Or? Anthony Shiplenus, Newport, N. J.

WANT SAMPLE OF FLINT AND other rocks, minerals (ore), foreign coins, samples of wool (graded) and samples from five different breeds of sheep. Have all kinds of things. C. Raymond, Maple Street, South Hadley Falls, Mass.

WILL GIVE 50 FOREIGN STAMPS for 15 U. S. commens, except NRA, Chicago, and Anthony, 25 postmarks, 10 tax tokens, 1 newspaper for 10 U. S. commens, Orville Arnold, Box 311, Henryetta, Oklahoma.

HAVE CHARLES ATLAS PHYSI- cal Development course, Western Electric pickup, heavy-duty phonomotor, turntable. Want S-W 3 or other short wave receiver. Paul O'Donnell, 83 Saksamore Avenue, Atlantic, Massachusetts.

WILL SWAP 16MM PROJECTOR, radio parts, stamps, 5 meter transceiver, radio books for low power transmitter. All letters ans. Anthony C. Conlin, 83 Westfield Rd., Holyoke, Mass.

HAVE RADIO PARTS, POWER packs, condensers, tubes, one and two tube battery and electric sets. Want rifles, cameras, field glasses or what have you. John Haynes, Doe Run, Mo.

EXCHANGE MAGAZINE SUB- scriptions for transmitting equipment. Will give subscriptions to any magazine for good crystals, transformers and other transmitting apparatus. Like to hear from V.H.F. fans. 100% QSL. R. H. Alexander, Richmond Hill, Ont., Canada.

HAVE BROWN BOBBY DOUGH- nut machine, Jowett dumbbell course complete, McFadden five volume encyclopedia of physical culture. Want Von Schrader rug washer, barbell set, correspondence courses, or what have you? Harold P. Sheehan, Caledonia, Minn.

HAVE STEVENS .22 repeating rifle, headphones, Atwater Kent 5 tube battery radio, reversible sewing machine motor, other parts; want auto radio, double button mike, Riders manuals, ? Harold Hitchen, WGR11, R2, Newberg, Oregon.

SWAP GOOD FOREIGN STAMPS for Lincoln pennies, Indian head pennies, Columbian half dollars or other good U. S. coins. Karlecheks, 905 5th Ave., Moline, Ill.

WANTED—ALL 8 MM AND 16MM films, also camera and projector. Offer books, greeting cards and view cards and some cash. Write to Joseph Narky, Jr., 9610 Kennedy Ave., Cleveland, Ohio.

WANTED — SKY-BUDDY RE- ceiver. Will trade 1,000 different, unused postcard views, Sterling's radio manual, Supreme 333 analyzer, etc. Joseph McGuire, 5922 So. 38th St., Omaha, Nebr.

TRADE 588 PRINTING PRESS, complete modern rack, all accessories, for used FB7X National receiver with coils, good working condition. Trade motion picture camera, projector (Keystone) both perfect working condition for SW3 National, D. M. Sheehan, WILMS, 96 Franklin St., Stonelham, Mass.

EXCHANGE BOOKS, STAMPS, preannals, Buro prints for all radio books, 16 mm films, taxidermy supplies, natural history magazines. Send your swap list with want lists. Joseph Bourette, Box 66, So. Station, Fall River, Mass.

WANTED—265 MMFD. PER SEC- tion split stator condenser, 7.5v. fil. transformer, T40 or T45. Will swap 1961 KC crystal for WFOXP, Edw. T. Blackmon, 2955 Memorial Dr., Decatur, Ga.

WILL TRADE 5-TUBE T.R.F. RE- ceiver, meters, RCA 832's, Cardwell condensers, Thord, 1200V, C.T. at 300 MA for what have you? Write E. Kammerlink, 616 N. Central, Chicago.

HAVE PHILCO OUTPUT METER, Ghirardi's Radio Physics Course, 2nd edit., radio parts. Want 0-1 D.C.M.A., D.P.D.T. Federal antiaircraft switch. All letters answered. Steve Nancy, Main St., Box 273, Twin Rocks, Pa.

SWAP 1 RCA ELECTRIC SET, needs servicing. 1 \$5 microscope, variable condensers, stamps, radio parts and speaker for auto radio, working order, or? Raymond Hower, Rural 3, Bloomsburg, Pa.

HAVE 47 SCIENCE FICTION magazines, Wonder, Amazing, Astounding, etc. 1931 to 1936. Will trade each for 15¢ face in mint U. S. comm. stamps before 1928. Fred W. Wayman, 286 Pike St., Carbondale, Pa.

WILL TRADE NEW 6-TUBE BA- ttery set, Silver-tone radio for typewriter, musical instruments or what have you? Value \$40 in trade. Edward Owens, Wellington, Alabama.

(Continued on opposite page)

The Martian Flash

(Continued from page 720)

images exactly as if one were viewing them from the outside. It took a long time for Martians to become adept in this form of reception, as there are a minimum of ten different wave forms necessary, all being transmitted simultaneously to accomplish this purpose.

Let us suppose, however, that a Martian does not wish to receive the television images being transmitted. That again is very simple. As the Martian antennae is made in such a fashion by nature that it can be straightened out or curled at the tip, (as similarly accomplished by insects.) it is only in the straightened condition that the interception of the oscillating waves is possible. At the same time and using the same means, the sounds are also received and thus the Martian can hear and see what is going on in the distant television transmitter, without any special apparatus of any kind. If he does not wish to receive the television program, he merely relaxes his antennae, which then curls at the end and the reception is blotted out, due to the changed wave length of the head antenna. If anything of special national importance arises, special impulses are transmitted which are received by the curled antennae and the Martian will instantly know that something of unusual significance has occurred. He will automatically straighten out his antennae and will be ready for reception in the flash of a second.

There are all sorts of refinements, but I will only mention one: Suppose a Martian is busy with his own work and can not find the time to have his television-sound program at the time. That makes little difference because he can enjoy it later on if he wishes to. In his own home or in his abode where he performs his work there is a certain recording apparatus which for a whole Martian day, stores not only the television and sound programs but many other programs too. These programs can then be reeled off as it were, from any time of the day simply by pressing or manipulating a few buttons. If, for instance, at what would correspond to noon on Earth one would wish to get the noon program at midnight, manipulation of a few buttons will bring that program instantly. At the end of the day the programs are automatically obliterated.

One can, if he so desires, go to the Central Office and get a program no matter how old it is. Thus, the other day, just for the fun of it, I went to the Central recording office and enjoyed a very fine television and musical presentation which had been recorded 1,250,000 years ago! And I am here to tell you that it was a good program too. It showed, among other things, special ultra-telescopic views of the planet Earth during the midst of one of its periodical ice ages and when Man as yet had not made his initial appearance. Close-ups showed the wild animals still in full reign on the planet and as far as Man was concerned, all I saw was ape-like beings. It made me shiver to think how far the Martians were ahead of us even BEFORE we existed.

This is the third issue of *The Martian Flash*. The publishers would like to know if you like it. Vote and mail coupon.

THE MARTIAN FLASH

STOP IT
 KEEP IT
 Name

Address

Rotating Beam Loop

(Continued from page 722)

Twenty-four inches of 1/2 in. by 1/8 in. iron (an old coal scuttle handle) was fitted with one bolt as a bracket near the top, and a 12-inch piece of dowelling was clipped in this for the rope to run over.

A 6-inch wheel was fixed to a 30-inch length of iron rod (from a car bonnet hinge), and this rod is passed through a hole in a hard wood block near the bottom of the mast, and through the side of the French window-frame. A car window winder makes a neat job on the inside and one complete rotation moves the loop 360°. A compass card under the handle gives the bearing.

The Aerial

The aerial itself was made possible by the discovery that steel cored copper wire is now available cheaply, and two 8 foot lengths of 12 S.W.G. made two very stiff loops. The open ends are 1 inch apart and cemented into two small pieces of bakelite that happened to be available, but celluloid or glass tube would do as well. (Fig. 2)

Eight stand-off insulators were screwed to the ends of the wooden cross, and small brass clips (springs from lamp batteries) hold the two loops firmly in place under the terminals.

At present a waterproof cable, twin rubbered flex, covered with Empire cloth (or oil cloth), as used for car lighting, is being tried. This has worked well up to 14 Mc.; spaced feeders are heavy and clumsy to mount. A matching stub is not being used, as this cable draws into 100 ohms. Up to 14 Mc. power loss is reasonable, and climatic conditions do not bring changes, as with flex or even some open lines; and this cable is also comparatively light.

In case references are not available for a Reinartz loop, the following information is given:—56 Mc., 8 ft. 1/2 in. of wire, 30 inches diameter, loops spaced 3 in.; 28 Mc., 16 ft. 1 in. wire, 60 inches diameter, loops spaced 3 in. Loop ends approximately 1 in. apart.

A narrow beam, in a direction away from the open end of the loop for transmitting, is given.

Results

A month's test with a constant input of 7 watts has obtained an average report of S4 at 20 miles, with a back coverage of S1 using a frequency of 57.488 kc. Short range tests have given reports of S6.

BOOK REVIEW

VAN NOSTRAND'S SCIENTIFIC ENCYCLOPEDIA. 1234 pages, illustrated, cloth covers, size 8" x 11" x 2 1/2". Published by D. Van Nostrand Co., New York City.

Among the many subjects covered by leading authorities, we find Aeronautics, Astronomy, Botany, Geology, Mathematics, Medicine, Navigation, etc. Twenty-one leading scientific authorities wrote it.

All of the subjects are arranged alphabetically and can be located quickly. Under "A," for example, we find such timely and important subjects as airplane engines, airships, alcohols and aviation. Under "B" appears, ably treated and illustrated—balloons, bees, bending moment, binomial formula, blast furnace, blind landing, blood (with color charts), oil burners, etc. Under "C" important topics covered include—cancer, catalysis, chemical compounds, coal, coke and colloids. Under "D" appears—definite integral, derricks, digitalis, dyes, etc. In the "E" section we find eclipses, Einstein theory, electrical topics (such as dynamos, motors and controlling systems), electro-magnets, esters, eugenics and evolution.

The variety of topics included is beyond the scope of this review column, but we might mention a few more subjects just to give the reader some idea of the vast scope of this remarkable volume. Among others we note—fish, flies, fungi, harmonic analysis, helium, hydraulic turbine, interferometers, invertebrate paleontology, Lenz's law, leukemia, ultra short wave, uremia, vectors, X-rays, telephony, television, tonsillitis, etc., etc.

BARTER and EXCHANGE FREE ADS (continued)

- WANTED BEST TYPEWRITER.** Will give ten dollars cash or will exchange fifteen dollars worth Indian stone pipes, pots, bowls, copies of prehistoric for it. Mrs. Nutman, Route 1, Box 125, San Luis Obispo, California.
- HAVE CAMERAS, WATCHES, 55 Stanley plane, Stanley brace, inter machines, studio lights, Masonic books.** Want small plate cameras, kodaks, small radio, radio books and courses and parts. A. S. Sizemore, Box 483, Jackson, Ky.
- HAVE MANY POP. MECH. & Science, other mech. magazines.** 1 tube portable battery receiver, uses 30 tube. Want radio parts, multi-capacity switch, or tube-testing transformer. Robert Dick, 708 W. John St., Martinsburg, W. Va.
- WANTED - UNIVERSAL S.B. label mike.** 10 lbs. Atal. 523 tube. 0-100 MA meter for what do you want in exchange of what have you got besides. John H. Walker, 97-34 Astor Ave., Corona, L. I., N. Y.
- WANT MODERN SHIP RECEIVER.** Navy or R.A. Swap Candler course, Instructor and tapes. Speed-X bug even money. Give particulars. Best ever commercial bands 600 meters up. John A. Patterson, 3239 N. Philip St., Phila., Pa.
- WILL TRADE 22,000 VOLT INDUCTION coil giving 1 1/2 inch spark, for radio parts such as variable condensers, carbon mikes, etc.** James Marshall, 1738 Pacific Ave., Atlantic City, N. J.
- I HAVE MOST ANYTHING. POST-CARDS, souvenirs, etc.** to swap for transportation tokens of street cars, buses, etc. from anywhere, answer all. B. Meltoie, 1030 Big Falls Ave., Akron, Ohio.
- WANTED 40M CRYSTALS, TRADE** for 15 Popular Educators (new) or complete set of QST mags June '37 to '38 and three other late editions of radio 1930 to February, 1931. Stanley Gordon, WYFFN-A.M.S., 15 Summit St., Lord Springs, Ark.
- HAVE COMPLETE N.R.I. COURSE (1928).** Servicing and Transmitting, with code instructor, with 5 tapes. Want S.W. receiver. Make trade offer. Clarence H. Moore, 1322 Gilman St., Philadelphia, Pa.
- SWAP AN EILEN 70-AR RECEIVER** 110 volts with 20-40-80-60 coils. All condition for small tube transmitter, or small 160 mtrs. xtr or what? Maurice Dubreuil, Lavaltrie, Quebec, Canada.
- WANT SCIENCE FICTION. TELEVISION magazines, old and new.** Want old television stuff, test equipment. Have radio magazine, 1923 Popular Mechanics, 1927 television magazine, valued at \$5.00, diagrams, popboy songs, odds. Bill Elstak, Norwell, Kans.
- HAVE SET OF LIONEL STANDARD gauge trains** valued at approximately \$75.00 which I would like to trade for some radio equipment or testing apparatus. Jack Hedlund, 133-16 32 Ave., Flushing, N. Y.
- INTERESTED IN SECURING A Master Teleplex with tape.** Gustave Monrushi, 9918 Lander Ave., Detroit, Mich.
- TRADE: 32 VOLT TO 250 V. power supply.** Silver-tone 7-tube battery set, late model, complete 32 volt Atwater Kent radio 7 tube, crystal mike, carbon mike, for C. J. Gates, 239 Main St., Jonesboro, Ark.
- TRADE: 250 EXCELLENT AIRPLANE pictures.** Army, Navy and foreign planes. What have you in radio you don't want? QTH Raymond Ruben, 24 Hawley St., Lawrence, Mass.
- NEEDED VERY RARELY. MODULATOR of speech amp., xtrals, any kind of xtr, with anything, anything, anything or recording needed.** Swap QSL, SWL cards, QSL 100%. Send details. Ray E. Murphy, 7311 Georgetown Rd., Bethesda, Maryland.
- BATTERY CHARGER 1-20. HOYT meter battery tester 34 h.p. Large hunting knife, sheath, No. 1 pocket Kodak, tripod, Popular Mech., Popular Science, National Geographic mags.** Want good SW receiver, elec. M. Gohr, box 64, Willow Springs, Ill.
- RC-A VICTOR 9-40 RADIO chassis.** tuner, power pack, dynamic speaker and loan. Ideal for experimenters or loud speaker system. Instrument cost \$100.00. Exchange for standard make movie outfit, rifles. P.O. Box 124, Sonnet, Ky.
- WANTED-NATIONAL PW2 TUNING unit.** 160 mmfd. per section, complete with gear box and dial. Aladdin 1FA types S-2242A, S-2242B only. Have instructor card with tapes, oscillator like new. Andrew Balint, 3318 W. 31st St., Cleveland, Ohio.
- WANTED: COILS FOR PILOT Super Wasp battery type s.w. recy.** also Riders manuals. R. Ellimonters and code tapes. Write, Archibald Bursey, Burlington, Newfoundland.
- SWAP ARGUS CANDID CAMERA.** or G.E. 1/4 h.d. electric motor, heavy duty induction type, for model airplane motor or repeating rifle. Ray Cerd, Winters Lane, Cold Springs, Kentucky.
- A 1936 FULTONE S AND L WAVE receiver complete.** in perfect condition, value \$14.00 AC-DC. Trade for bicycle of like value in Arizona only. Send stamp, William Siekle, ltr. 4, Box 652, Tucson, Arizona.
- WANTED 465 KC XTAL. VAR. tube with crystal mike.** (Have typewriter Oliver.) Green Flyer Phonomotor and xtal pickup, multimeter and oscillator, Triplett, SWLs answered, "Let's Swap," Eldon Wooster, Peesburg, Ohio.
- HAVE S-X-11 SUPER SKYRIDER with Hallifasters 1 1/2" speaker.** 8 mm camera, 2 sets SWLs, coils, numerous parts and tubes. Want late model 22 hp outboard, or C. Brown, 333 Hazel St., Lancaster, Pa.
- 3 TUBE TRUFONE SHIRT-wave and broadcast AC mantle receiver and 8-tube AC Silver-tone cabinet broadcast receiver.** 22 pump rifle. Speakers. Need radio books, parts, meters, etc. Al Stanley, 3517 Hennepin Ave., Minneapolis, Minn.
- HAVE \$39.50 ELGIN NATURAL gold watch, pair photo cells, magnetic pick-ups, elec. razor, pair crystal phones.** 2-tube A.C. set. Want Sky Buddy or receiver capable of operating speaker. Al Warren Morris, Williamstown, Pa.
- TRADE. COLLECTION OF APPROXIMATELY 4,000 postal card views.** 12 ca. repeating shotgun, Crosley "flavor" radio, electric shaver. Want outboard motor, stamp collection or what have you? Answer all inquiries. E. Pence, Box 22, Griggsville, Ill.
- TRADE COMPLETE LA SALLE accounting course.** cost \$130.00, for superior radio, 30 watt amplifier, smart ice equip., or G. H. Heldenbrand, Staplehurst, Nebr.
- WANTED-AC-SW3 WITH COILS.** tubes and power supply or Sky Champion or Howard or other suitable SW receiver. Trade \$55 wood bp clarinet. All letters answered. Huddleston, 918 South 25th Street, Temple, Texas.
- ONE PROJECTOR WHITE 3 1/2" lens.** or showing solid object like postcards, snapshots, onto screen, up to six ft. in diameter. Exchange for six volt generator in excellent condition. F. McAnabb, Green City, Missouri.
- WANTED RIDERS MANUALS 1 to 3 volumes.** Will pay cash. Carl M. Johnson, 211 East 20th St., Bronx, N. Y.
- WANTED-CASH OR TRADE-** old radio tubes for hobby collection. Need not be in working condition if eye perfect. Send list. Have duplicates for trade. M. Snively, 1014 Cedar St., Elkhart, Ind.
- CANADIANS-WILL TRADE SWC es Radio & Television mags es radio parts for washing machine gas engine or 250 volt 3/4 mill motor generator.** J. O. S. Hunter, Kensington, U. E. Island.
- WANTED RCA 955 ACORN TUBE,** have new Cardwell variable cond. 15 mmfd., 3 Hammarlund 5-prong Isolating sockets, 2 R.F. chokes 2.1 MH. John Ewarsky, 17 Robert St., So. Paterson, N. J.
- WANTED VARIABLE BEAT FREQUENCY audio oscillator.** Will pay cash. Give make, model, condition and price in first letter. Gardner Radio Service, 2689 L St., San Diego, California.
- TRADE: EILEN RX-14-AR 6-tube T.R.F. receiver.** Cost \$24.40 new. Coils for 20-40-80-160-BC bands. Built in speaker. What have you? All letters answered. 2901 N. Kilbourne Ave., Chicago, Illinois.
- WANTED: U. S. STAMPS, HIGH values, commemoratives, precancelled or sloxan meters.** Will trade magazines including Radio-Craft, old issues of Electrical Experimenter, Esquire, etc. Send for free list. Charles Chosenovitch, 1218 S. Blanchard St., Findlay, Ohio.
- SWAP-TOOLS, CAMERA, CROWN crimping machine, mounted out, 1/2" saw, stereotypy ester, novelties, small printing press, etc.** Want-microscope typewriter, postal scales, 22 cal. rifle, rotary tool. Will exchange lists. Albert O. Rimer, Rimer, Penna.
- 16 H.P. LOCKWOOD OUTBOARD motor.** Will swap for motorcycle, short wave receiver or what have you? W. C. Cotter, 31 Pearl St., Springfield, Mass.
- HAVE NEW \$150 PORTABLE POP-corn machine** for new or nearly new Hallifaster or National receiver, or what have you? Gerald H. Worth, 803 Randolph, Waterloo, Iowa.
- HAVE OVER \$200 WORTH OF high grade s.w. receiver parts and kits to exchange for stamps or receiver such as Sky Champion or Howard 450.** J. Kasperk, 34 Albem Ave., Ocean Side, N. Y.
- SWAP 300 INDIAN HEAD PENNIES, half cents, two- and three-cent pieces, old nickels, half dimes.** Riley xtal, D.B. mike for portable battery receiver or phonograph turntable. W2GPF, 139 So. Day St., Orange, N. J.
- OFFER - BATTERY CHARGER, movie projector and films, violin, phonograph, oscillator, mike, test equipment, aligning tools, radio books and magazines, movie camera, films, or Harry Parker, Sylva, N. C.**
- SWAP F.B. PRINTING FOR S.W. receiver or transmitter.** Part of it will pay spot cash for a small beginner's C.W. transmitter if reasonably priced. Must be complete. Lawrence Pleasant, P.O. Box 58, Mattoon, Illinois.
- WANTED: 5-METER RECEIVER.** Will trade \$3.00 chemical set. ORA J. Krehel, 3381 E. 104 St., Cleveland, Ohio, U.S.A.
- WILL TRADE RADIOS, AMPLIFIERS, and watches.** Want good typewriter. Eugene Cox, Harrisonville, Mo.
- HAVE BLAND NEW AUDITORIUM amplifier** guitar complete with case. Want: good velocity or crystal microphone. Have N.R.I. Radio and Television course complete. What have you? Walter Burling, Waynesville, O.
- HAVE CODE PRACTICE OSCILLATOR, one tube audio amplifier, two magazines, want microphone, 0-100 ma milliammeter, 0-500 volt voltmeter, 6 volt vibrator transformer and vibrators.** William Blecha, Pawnee City, Nebr.
- SWAP FOR TRANSMITTER parts.** Garage battery charger, Prestolite tank, auto radio, 4 yrs. Radio-Craft, Maytag engine, 2-tube Kadette, large telescope, cost over \$200. E. C. Warren, Cape, Mich.
- HAVE BRUNSWICK, JR. POOL table, 48" by 31" (folding legs)** with set of acute balls, triangle, two 400 unfinished wood cues, very good condition. Want testing equipment, or Vercoo Jones, 61 Carlton Ave., Trenton, N. J.
- HAVE ARGUS CANDID CAMERA.** Like new. Want U. S. stamps or short wave equipment or set or what have you? James E. Wilkinn, Box 693, Elkins, W. Va.
- HAVE ONE SUPERIOR ALL-wave signal generator** with audio frequencies. Want a 5 meter transmitter or a receiver or anything that you have to swap. Write what you have. Will answer. Albert Sebesta, Snook, Texas.
- WANTED - POSTCARD SIZE Kodak, F8.3 lens.** Will trade a pair of 800 xmitting tubes, 0-25 MA Weston, 0-100 MA, Triplet, % W2GWP, 7 Avenue B, New York City.
- SWAP-WESTINGHOUSE 110 V. A.C. 200 watt generator, 4 replacement carbon brushes and blueprint, for speed key, Mac. osc., Barbells, etc.** A. Bellan, R.F.D. No. 3, New Brunswick, N. J.
- WANT CODE MACHINE WITH tapes.** Have Dayrad tube checker, Ranser signal generator and Triplet meters. Donald H. Marcotte, Garvin, Minnesota.
- WANTED - STAMPS, POSTAL cards and book matches** from all foreign countries. I will swap to exchange from this end. Will also exchange Colorado tokens for other tokens. Ellis L. Parr, 405 Ash Street, Trinidad, Colorado, U. S. A.
- HAVE 2 I.P.O. TUBBARD MOTOR, 3 B. and L. microscopes, 300 to 2,000 diam., 1 pr. binoculars, 8 pwr., 1 Schick dry shaver, 1 dry swap, Peter Lambert, 27 Vernon Street, Worcester, Mass.**
- WILL SWAP: "HOW TO PLAY Blues on a Harmonica," Brandes "Superior" headphones, type 30 tube.** Will swap for electric shaver or wrist-watch. M. Kocou, 48 Edwards St., Patchogue, N. Y.
- WANTED RADIO PARTS, PREFF-erably headphones or ear condensers.** Have 209 U. S. and foreign stamps. Over half are commemoratives. Two are over fifty years old. Carl O. Hicks, Route 2, Laveine, Okla.
- WANTED: NATIONAL PB7 WITH coils and power supply, or other good communication receiver.** Will pay cash or trade. Have several interesting items to trade. H. S. Lair, Vineyard Haven, Mass.
- HAVE 7 WATT AMP. 4 TUBE, trade for good lathe, good phono pickup motor and turntable, or small gasoline engine.** Trade tubes, R.F.C. coils and aut. coils. Elthie Thompson, Box 481, Kosciusko, Miss.
- HAVE FB D.B. MIKE, SW4 WITH all coils to 18 meters, handset, 0-5 Weston 30 volt-meter, also 3 P1-4 tubes, a real antique.** No wa? s? WILDO, Hoxbury (19), Mass.
- WANTED AN ULTRA STRATOSPHERE "10" complete** with all coils, must be in perfect shape, also want short wave sets and transmitters. Steve Novota, Jr., Moweaqua, Ill.
- CANADIANS-HAVE 2,000 RARE British Colonies, Dominions, stamps mounted, including Coronations.** Collection costing \$110. 80 Stamps Magazine, Rapkin Favorite album, for good transmitter, 50 watts, or Parts, Herbert Wagnan, 14 Lander, Toronto.
- TRADE FOLLOWING PHOTO-graphic articles-8x10 plate Kodak with several old lenses; Foth Derby F:2.5 new, with case; enlarging lens F:3.5; Unirex movie lens F:3.5; radio parts.** For Gerard Lacombe, Box 513, Madawaska, Maine.

(Continued on page 764)

BARTER and EXCHANGE FREE ADS (continued)

S-W League

On the "Ham" Bands

Edited by Elmer R. Fuller

● **CONDITIONS** during the past month have not been any too good, although some very fine business DX has been heard at times. The Europeans have been coming in very well, and about two hundred were reported by our observers in January. Conditions on the ten-meter band have been much better than ever before this season, and about half of the stations were reported on this band. Twenty meters has improved somewhat from the previous month, and is now staying open until a much later hour at night. At present it is open until around 2:00 a.m.

We have learned that ZT6P has changed his call to ZS6CK; his QRA is: E. P. Abdo, 314 Normand Court, 109 Kerk Street, Johannesburg, South Africa.

From February 11 to about March 14, W21WT will be en route to the island of Sumatra on an expedition. During the time he is gone, he will maintain communication with W4DLH of Goulds, Florida. He will also be in communication with PK4KS, PK4CT, and PK4HW.

To get down to business, we have reports from the following sections of the world:

Alabama	Wells, Jack
Arizona	Fuller, Lester
Arkansas	Henderson, Bill
Canada	Clarke, Stanley
Colorado	Wallen, Dan T.
Connecticut	Kemp, Howard
France	Le Rasle, Charles
Georgia	Patterson, C. R. ("Pat")
Illinois	Carling, Len M.
Kansas	Hegler, Burns E.
Louisiana	Wynne, Maurice
Maine	Barker, Elwyn
Nebraska	Noyes, William Dean
New Jersey	Fitzpatrick, John
New York	Herzog, W. F.
	Fuller, Charles H.
	Yours truly
North Carolina	Oglesby, William W., Jr.
Ohio	Gallagher, L. F.
Oregon	Trueman, Elwood C.
Pennsylvania	Hartzell, Clarence
South Carolina	Hildner, Ray
South Africa	Vestland, John F.
	Westman, Oscar
Utah	Parker, Robert
Washington	Lang, Ernest W.

Beginning with this issue, another new plan for listing stations reported heard by our observers is being inaugurated. By use of this new method, it is thought that it will be much more useful to our readers. It is believed that readers are interested more in *where a station is being heard* than in who is hearing it. Therefore, instead of placing the name of the observer after the station reported, the name of the section of the world which that observer represents will be printed.

From Asia, the following stations have been reported. This is the largest number of Asiatics to be reported this season.

Call	Freq.	R	S	Where Heard
XZ2JB	14.3	5	6	Canada
XZ2DY	14.067	4-5	5-8	Penna., South Africa, Ohio
XZ2EX	14.	5	9	South Africa
NURAM	14.06	3	5	Ohio
X18ET	14.13	5	6	France
V12DY	14.3	3	5	Ohio
VU2LY	14.265	5	6	France
VU2FU	14.19	5	9	France, South Africa
VU2CQ	14.12	5	9	France, Ala., Penna.
VU2BU	14.	-	-	France
ZC6AA	14.415	5	6	France
ZC6AE	14.1	5	5	France
ZC6EC	14.36	5	8	France
V12BA	14.0	5	7	France
V12A1	14.08	-	-	France
V52AS	14.	5	8	South Africa
V52AS	14.13	5	9	France
V52RA	14.28	5	6	France
V52RF	14.1	4	5	Ohio
V52GJ	14.04	5	9	France
J2AK	14.	5	9	South Africa
U81B	14.445	5	6	France

Africans have fallen off some since last month, but several are being heard in the eastern United States, and are very consistent in France.

ZS1BL	14.03	5	8	France
ZS1T	14.09	5	7	France
ZS1AX	14.102	5	8	Penna.
ZS1B	14.08	3	4	Ohio
ZS2AZ	14.01	5	8	Canada
ZS2AZ	14.04	5	8	Canada, France
ZS2AF	14.110	5	7	France
	28.215	3	5	Ill.
ZS2N	14.1	4-5	7-8	France, Penna.
ZS3F	14.07	5	9	Penna.
ZS3H	14.06	5	7-8	Canada, Penna.
ZS5AW	28.1	5	7	Canada

HAVE NEW RIDERS VOLS. 2, 4, 5, 6. Philco signal gen. All wave mod. 088. Jewell analyzer. mod. 911. Dayrad tube testers, short wave parts for what? Jos. Bakutis, 794 Quinlan Ave., New Haven, Conn.

HAVE 200W-16 MM MOVIE projector (AC/DC) with 1,000 ft. movie films value \$50.00. Want 8 mm movie equipment, or what have you? J. Winkler, 62 Berken Ave., Clifton, N. J.

SWAP JANUARY ROTARY CONVERTER, 32 V Dc to 110 AC for Sky Buddy or typewriter. In good condition. Cost \$15. Also have 12" dynamic spkr. for crystal parts. Jack Spencer, 313 W. La. Ave., Ruston, La.

HAVE 1/6 H.P. A.C. MOTOR, 2 Maple Eye tubes. Will exchange or buy old coils dated before 1900. Please send exchange list or price in first letter. QRA: Stanley, Box 183, Winchendon, Mass.

WANT MICROSCOPE, TELESCOPE, chemistry outfit, electrical engineering course, large dictionary or encyclopedia, ser. Have audio amplifier, speakers, power packs, 4 radios and bundles of tubes and radio parts. Claude Carpenter, Sweet Springs, Missouri.

INSTRUMENTOGRAPH OR OTHER code machine wanted or set tester. Trade 180V generator, model A100. Utah dynamic speaker with power supply or other radio parts. John Malder, Blanchard, Idaho.

HAVE \$200.00 BUSINESS CORRESPONDENCE course, ten tube battery radio and many radio parts. Swap for test equipment, manuals. Riders manuals, National SW2 or generator. E. S. Barnett, South Boston, Va.

TRADE 2 LIONEL STANDARD trains and equipment worth over \$100, for good .22 repeating rifle and shotgun or late Skyrider or Howard receiver, etc. Also have stamps. Ray Flowers, 671 E. 92 St., Cleveland, Ohio.

WANTED: CHEAP ELECTRIC MOTOR with turntable, suitable for use with pick-up. Tell R.P.M., age, make and price. I will QSL 100%. Don Pettibon, 2117 East Mifflin St., Madison, Wisconsin.

IRELAND CALLING. WILL EXCHANGE stamps, cigarette cards, or post cards for stamps only. British colonials and all mails preferred. Mervyn La. Colhoun, 18 Grove Place, London-derry, Northern Ireland.

WANTED: SWITCH BAND SHORT and long wave receiver. I have books or will pay cash. Not over 6 tubes. Prefer metal ones. Chas. D. Miller, Box 4145, Pinewood, Rural Sta., Miami, Fla.

HAVE 6-TUBE 2-VOLT BATTERY broadcast receiver. Want bathie, electric drill or drill press, ½ h.p. motor, A.C. short wave set or what have you? Carroll P. Clark, Gossville, New Hampshire.

HAVE VICTOR 16 MM MOVIE projector, silent, cost approx. \$100.00. Will trade for a Hallator or Sky Champion. Must be in good condition. L. A. Dore, Co 544, C.C.C., Yellowstone Park, Wyo.

TRADE KELSEY 3x8 PRESS, medal operated, 8 cases of type, new rollers, 2 new type 10 National Union heavy duty tubes. Want low power ten meter upward or outward m.p. H. Cary WOTOF, Eagle Lake, Minn.

YOUR DUCK HUNTING STAMP is worth ten unused purple postage stamps to me, if in good condition. Stamps, covers, postals, seals, radio parts, to swap for same. Drop a postal today. Mervyn Reynolds, Jefferson, Maine.

WILL SWAP CABINETED Majestic speaker, 2 dynamic 5 in. speakers, 2 tube Philmore all wave receiver. Send list for mine. A. S. Brazanskos, 105 Elizabeth St., Athol, Mass.

WANTED: ARGUS ENLARGER or? Have rifle, radio tubes and parts, stamp catalog, back issues of S.W. & T. also many other assorted books and magazines. Robert E. Lloyd, Box 94, Portsmouth, Ohio.

REGULAR LINOTYPE KEYBOARD. Good for learning to operate. Will exchange for receiver or what have you? George Mraz, 615 7th Ave., Williamsport, Pa.

SWAP COMPLETE SET TEACHERS and Pupils Encyclopedias, like new value \$28, for good battery operated amateur receiver. Ernest Verity, Box 20, Goodwater, Sask., Can.

HAVE GE 12,000 VOLT CT 22 milliamper transformer. Buescher B flat soprano saxophone, large stamp collection, mint U. S. commemorative tests. Want transmitting equipment, test instruments, manufactured receiver, crystal microphones. WFER, 1405 East Washington, Boise, Idaho.

HAVE EMERSON DYNAMOTOR, 6 volts input and 180 volts output. Zenith wind charger, Maytag gasoline motor, 32 volt lite plant, Sonora amplifier and speaker. Wanted Riders or Gernsback manuals. Gotfried Streckert, Clifton, Wis.

HAVE B SUPPLY AND NUMEROUS other radio parts to swap for photographic equipment. All letters answered quickly and cheerfully. Billy Griswell, 57 Minard Street, Lockport, New York.

HAVE MOVIE AND CANDID cameras, filters, mint U. S. comm. stamp precancel, electric shaver, etc. Want good reflex camera, enlarger, photographic items, or? Michael Giarrucio, 604 Union Ave., Prov., R. I.

SWAPPERS! I SWAP EVERYTHING under the sun. Mostly hobby goods such as stamps, coins, etc., for what have you? Stamp brings list. Virgil Clemenson, Roswell, South Dakota, U. S. A.

WILL EXCHANGE R.C.A. MAGNETIC speaker, trickle charger, Tungar battery charger, old typewriter; for testing equipment. Prefer good tube tester. Write: J. Marsh, 111 Van Liew Ave., Milltown, N. J.

HAVE NO. 4 ERECTOR, LINO, carving tools, lab. equip., books, speaker, etc. collection, tent, axe, knife, etc. George Fried, 1764 Weeks Ave., Bx., N. Y.

SWAP-FOR USED DO-ALL Deluxe or similar set:—A G.E. Tungar charger. Charges up to 16 batteries. (Swells for serviceman!) Has extra bulb. All A-1 condition! List free. Don Yocum, Bettaville, Ohio.

SWAP: TWO 12 GA. DOUBLE hammer style, Stevens 410 ga. double hammerless shot guns, Eastman 4x5 autographic kodak, registered A.K.C. cocker spaniel pups. Started, trained beagles. Wanted: Kodaks, rifles, Gust Spink, Route 50, Muskegon, Mich.

WANTED: SPRAYBEERY'S LAST regular radio course. Has to trade automatic code machine and code course all-wave amateur set, xmitting parts, milk s. meters, etc. For list write to: S. J. Niewiec, 79 Church St., Broad Brook, Conn.

WANTED: TEST EQUIPMENT, auto radio. Have 57-56-2A5-80 amplifier with 9" Utah spkr., 7148 KC crystal, 4 300M DeVry camera, C. Ford, 4 Clinton St., Potsdam, N. Y.

WANTED RIDER'S MANUALS, 2 G.E. tube, double extension plate camera. Have 1" C.R. tube, excellent barometer, F4.5 ½ VPK camera, 3 yrs. Pop. Sel., 4 yrs. Journal Amer. Chem. Soc. Leo J. Jennings, 75 Hume Ave., Medford.

AM A BEGINNER IN RADIO. Would like to swap parts and correspond with other beginners. Francis Berkshire, Bx. 63, Masontown, Pa.

WANTED: USED 100 MMF 10,000 volt transmitting condenser. Will QSL with YL's in foreign countries only. K. B. Hume, WIKKK, 51 Atlantic Ave., Boothbay Harbor, Maine.

TRADE EASTMAN BABY Brownie camera \$1.00, Unifax model A camera \$0.25. Want camera that takes camera exposures, snapshots. Will add books if your camera costs a little more. Alexander Podstobny, 217 Pine St., Phila., Penna.

WANTED A GOOD SHORT WAVE receiver. Have three months' old Remington portable with case. Also cash if necessary. I. Minichon, 128 Franklin Street, Hightstown, N. J.

WANTED: HAULICRAFTER REELECTRICE. Have 110 aviation and 20 Popular Science magazines. Dick Sauer, 308 Volusia Avenue, Daytona, Ohio. Van Nuys, Calif.

HAVE 133 MAGS., AERO DIGEST, Popular Aviation, Air Trails, Flinck Aces and Popular Mech., 68 Blaispice, all parts from Majestic 70. Want s.w. A.C. receiver or? Joseph Lukas, 87 Bernlee St., Johnson City, N. Y.

SWAP: STAMPS, PRINTING equipment, printing, fiction magazines, and radio parts for communications receiver, radio parts, mechanic magazines or what have you? Earle Hammond, Albion, Maine.

SWAP: 1 ½ H.P. FAIRBANKS-Morse gas engine like new, battery charger A1 shape, ¼ H.P. "B line" 110V electric motor, radio magazines, good A eliminator for radio parts, especially xmitting. Walter Blumer, 82 Jefferson, Wis.

TRADE-NEW KODAK BANTAM, \$27.50 value with anastigmat f4.5 lens, 1/200 S.P. lens and camera in perf. cond. Will trade for SW receiver of similar value. Raymond Mueller, 33 Seventh St., Fond du Lac, Wisconsin.

WANTED TO SWAP PORTER Underwood typewriter for ½ to ¾ HP gasoline engine or good battery radio. Typewriter complete with new ribbon and carrying case. Thomas H. Brook, Haleyville, Alabama.

WANT ENLARGER, DEVELOPING tank, printer, exposure meter, and other photographic equip. Will trade printing of stationery, etc., new ear-phones, phono-pickup, 10 watt amplifier, power supply, QSL's printed or cash. Bill Pearce, P.O. Box 671, Klamath Falls, Ore.

WILL SWAP ONE ELGIN 3 TUBE S.W. receiver and coils complete for xmitter parts, meters or good mike. All mail answered. Pauline White, Pittsfield, Maryland.

WILL EXCHANGE 32 VOLT ONE H.P. generator, D.C. Packard electric razor, 6 volt motor, Hammond typewriter. For 16 mm films. Clare E. Ernst, 1107 Root St., Flint, Mich.

WANTED A 616B MODUL AND speech amp, 616 tubes also. Condenser and mike. Pay cash or swap. Ray Rozek, 712 So. Farragut St., Bay City, Mich.

WANT ELECTRIC DRILL. HAVE numerous transmitting and receiving parts, also many back issues QST to swap for drill. Describe drill and what you need. Herman Yellin, 331 New Lots Ave., Brooklyn, N. Y.

WANT 456 KC AIR TUNED I.F. transformers, 456 KC I.F. crystal, Meissner slide rule, dial, coils, and tuning condensers. Have radio parts. Harry Dinakus, 800 Sixth St., Reading, Pa.

HAVE FISHING TACKLE, RIFLES, radio mags., short wave radio parts, BC parts, power pack and new tubes. Want Stronberg-Carlson No. 69 SW converter or fishing tackle. H. D. Stansel, Lovell, N.

HAVE NATIONAL 45 RECEIVER, 30 pr. coils, feet meter, Mals. transformer, diodes, tubes, misc. Everything for ham xmitter. Want stamps or camera. All letters answered. Jack Cisek, 4 Gibson St., Natrona, Pa.

I HAVE 10" UTAH SPEAKER, 5" RCA speaker with output transformers. I want Halston code records or what have you. O.S.T. (C. B. Dole, 10 Clinton Ave., Rutland, Vermont.

WILL TRADE NEATLY CONSTRUCTED 50 watt CW transmitter, 6L6G xtal and 10 final, for medium power transmitting parts such as power supply, tubes, or what have you? W9HXW, 2119-12 Street, Moline, Illinois.

BEST TRADE OFFER TAKES 25 cycle power transformer, 6 volt speaker, QST class B output transformer, 33, 2A3, 81 tubes, 110 volt, 700 watt, 60 cycle generator, band switch coil assembly, condenser. D. Buck, 43 Hagen Ave., N. Tonawanda, N. Y.

HAVE OLD 9-TUBE PHILCO B.C. receiver, good tone sensitivity, needs minor repairs, trade for typewriter. Ivan Rice, Meredosia, Ill.

WANTED: 5 METER C.W. TRANS-ceiver. Trade home chemical laboratory consisting of approximately 300 different chemicals in vials, jars. Also includes glassware, several books on chemical analysis. Outfit cost \$20. Rudolph Thomas, 1720 Putnam Ave., Brooklyn, N.

HAVE THIRTEEN SIGNAL GENERATOR, Model 1230. Good cond., but less batteries. Will trade for "bug". G. H. Bruns, CCC 4607 DG-98, Dubois, Idaho.

SWAP-ABSOLUTELY ALL NE-cessary parts for six tube super-Meissner I.F.s. Hammarlund's, tubes, power supply, speaker for Gellenda, Gold, enlarger, or Kayak. More by letter if interested. Hubert Sinda, 3703 Belmont, Chicago, Ill. No'n.

WILL EXCHANGE 96-LESSON Spanish guitar course for SW receiver or what have you. Charles A. Nuss, 812 Locust St., Williamsport, Pa.

TRADE FOR GOOD BATTERY all wave radio 4-6 tubes, Mac Practice set, 20 tubes, camera, 2 headsets, 30 Trimm, 39 ARRL Handbook, 2 crystal sets, world globe. Hoyer, Box W, Lemon Grove, California.

SWAP-125 WATT RIG WITH 25-60 cycle supplies for good 5 meter transmitter and receiver, 25 watt P.A. system or Jack Cook (W2ZAMP), Box 419, Simco, Ontario, Canada.

SWAP: THREE POSTMARKS FOR each Plinters peanut bag sent me, one hunting permit stamp brings one hundred, send return postage, all hunting stamps must be on original paper. Stanley Wright, Howard, S. Dak.

WILL SWAP AGFA D6 CAMERA, 6 fewel wrist watch, 50 foreign coins, foreign stamps and currency, of paint, soap, magazines for radio parts and equipment. S. Bederman, 1295 Sheridan Ave., Bronx, N. Y.

2 GOOD HICKOCK HIGH FREQUENCY milliammeters, 0-1000, 0-4000, mounted; Shure 29N microphone (poor condition); Noiseless portable typewriter like new (with case). Want camera or photographic supplies. Robert Elhebrg, 782 West End Avenue, New York City.

WANTED: SKY CHAMPION, SIGNAL generator, beat frequency oscillator, oscilloscope. Trade and cash balance. Must be in excellent condition. Write directly for arrangement. H. S. Loh, 9 Meilen Street, Cambridge, Mass.

SWAP PAIR T-20'S, 50 watt class B transformers, double button mike and stand, pair 600 volt 200 mill UTC with 4 filament windings for 3000 volt condenser or transmitter parts. W.G.U.Y. Rio Hondo, Texas.

(Continued on opposite page)

Call	Freq.	R	S	Where Heard
ZS5T	14.1	5	8	Md.
	28.0	5	8	Neb.
ZS5CL	14.085	3	7	Penna.
ZS6A	14.015	3-4	6	Conn., Ariz.
ZS6BR	14.047	4	6	Conn.
ZS6B	14.120	5	8	Penna., N. C.
ZS6X	14.005	3	6	Penna.
ZS6AJ	14.085	4	8	Penna.
ZS6DW	14.03	4-5	6-8	Md., Ala., N. J., Ohio
ZS6AJ	28.03	4	7	Penna.
ZS6W	14.04	5	7	Md.
ZS6DK	28.26	5	6	Neb.
ZD2H	14.065	5	6	France
ZE1JG	14.3	5	5	France
ZE1JE	14.045	5	8	France
ZE1JX	14.38	5	6	Ohio
CN8AW	14.04	4	6	Conn.
CN8AY	14.095	4	6	Conn.
CN8MV	14.09	4	7	N. J.
ZT6LN	14.08	5	6	Ohio
CN1AF	14.10	5	6-9	Ala., Penna.
CN8BA	14.08	4	6	Ala.
OQ5AJ	28.11	4-5	6-7	Neb., Penna.
SU1MW	14.06	4	6	France
FA3FB	28.52	5	8	Penna.
VQ2HC	14.160	4	5	Ohio
VQ2HL	14.260	5	7	France
VQ3LJP	14.05	4	6	France
VQ4KTB	14.13	5	7-8	France, South Africa
VQ5ELD	14.0	5	5	France

For the benefit of the amateurs in our own country, the following have been heard in foreign countries, mostly across the big ponds. These are all in North America.

TC9BA	14.285	5	8	Canada
TC9AA	14.060	5	8	Canada
K4FAC	28.55	5	8	Canada
K5AF	14.13	5	6-8	Canada, Ore.
K7FBE	14.25	3	6	France
K7FST	14.25	3	6	France
CO2EG	14.2	5	8	France
CO2WM	14.07	5	8	France
CO2L	14.1	5	8	Canada
CO6OM	28.4	5	6	Canada
CO7CX	28.3	5	7	Canada
VP1BA	14.	5	7	South Africa
VP6YB	14.08	5	8	Canada
VP7NS	14.1	5	8	Canada
VP1Q	14.37	5	9	France
H16G	14.160	5	8	France
H17C	14.	5	8	France
NY2AE	28.24	5	8	Canada
T12AV	14.2	5	9	France
VO1V	14.17	5	9	France
VE2AK	28.15	4	6	France
VE4RF	28.3	3	5	France
VE4SS	28.5	3	7	France
W1AFJ	28.7	5	8	France
W1ANA	28.0	5	9	France
W1BXC	28.15	5	8	France
W1CMD	29.25	4	7	France
W1D1K	28.84	5	8-9	France
W1FVO	28.55	5	9	France
W1GUS	28.265	5	8	France
W1HJK	29.4	5	8	France
W1HGD	29.12	5	8	France
W1NVE	28.65	5	9	France
W1KUD	28.54	5	9	France
W1KRW	29.45	5	9	France
W1LMB	28.68	5	8-9	France
W1LNE	28.94	5	9	France
W1WV	29.3	5	8	France
W1BLU	5	6-7	8	South Africa
W1AXA	5	8	8	South Africa
W1AJZ	14.2	5	8	France
W1BUZ	14.175	4	6	France
W1IDQ	14.185	5	7	France
W2BQI	14.24	5	7	France
W21XY	14.225	5	8	France
W2JKQ	14.17	5	7	France, South Africa
W2JP	5	8	8	South Africa
W2ALK	28.725	5	8	France
W2FGB	28.5	5	8	France
W2HJU	28.7	5	8	France
W2JMC	29.3	5	9	France
W21XZ	28.9	4	6-7	France
W2KHR	29.11	5	9	France
W2CLK	29.15	5	8	France
W3B8O	14.4	5	8	France
W3DKY	14.24	5	6	France
W3FN	5	7	7	South Africa
W3CHE	5	7	7	South Africa
W3FOU	28.6	5	9	France
W3HOV	29.115	5	8	France
W3UX	29.0	5	8-9	France
W4BC	14.2	5	8	France
W4DU	14.23	5	8	France
W4BIV	5	7	7	South Africa
W4BMR	5	9	9	South Africa
W4DLH	5	9	9	South Africa
W4AAU	5	7	7	South Africa
W4AE1	29.1	5	8	France
W4DCQ	28.935	5	8	France
W4DWX	29.0	4	7	France
W4EDD	28.7	5	9	France
W4MV	29.445	5	8	France
W5ELW	14.205	4	6	France
W5GDU	5	7	7	South Africa
W5DNY	28.6	5	8	France

(Continued on page 767)

BARTER and EXCHANGE FREE ADS (continued)

WILL TRADE INSTRUCTIONS how to make artificial marble, etch on glass, resilver mirrors and 97 other quality formulas. Also two tube receiver (13-345 meters). What have you? M. E. Schleicher, 930 Hamilton, Peoria, Ill.

HAVE \$25 WORTH OF MODERN radio parts, tubes, books, etc., too numerous to mention to swap for photographic equipment or microscope. Sleser, 56 Willett St., New York, N. Y.

I HAVE AN SW AC-DC RE-ceiver with 3 tubes and coils, runs speaker. Swap for SW3 with coils and tubes. N. Dale, 25 Wall St., Arlington, Mass.

TRADE FOR SKY BUDDY OR Super Clipper. Stevens heavy barrel target rifle. Barrel drilled for scope blocks. Also interested in buying or trading for A.C. Ultra Air Rover 2, transceiver, Bobbie Hoyer, Box 111, Jamul, Calif.

TRADE SW3, 160, 80, 20 BAND-spread coils, power supply, eleven tube, dual band, Kallette radio, dynamic and magnetic speaker, tubes, parts, camera. Want Sky Champion, Sargent 39, NC4, Hue Diamond, Perkinson School, Pennsylvania.

HUNDRED GOOD FORMULAS, radio reading course, "Business Letters," "Tricks and Knacks of Fishing," "Tricks with Coins," guitar and violin instruction books. What have you? W. R. Schroeder, 803 Wisconsin, Peoria, Ill.

WANTED GOOD TYPEWRITER. Have 8 tube super communications receiver 530-24,000 K.C. A.V.C. manual switch, standby switch B.F.O. injection, pitch control, bandwidth, volume control and off switch, R meter. Alvin Neal, Fontana, Calif.

I HAVE FIVE DOLLARS TO spend on radio parts. What will you give me? Eugene Gutman, Co. 4606, C.C.C., Rupert, Idaho.

HAVE A 7-TUBE, 7-BAND RACD Super Clipper. Desire to trade in on a good superhet, will pay difference. A. H. McColloch, R.F.D. No. 4, Monroe City, Missouri.

EXCHANGE AN ALL WAVE T.R.F. five-tube receiver, complete. Has received all continents. Let's hear your trade offers. R. Willey, 1705 E. Burnside St., Portland, Oregon.

WANTED—FOUR OR FIVE TUBE short wave receiver. Have telescopic 10X, stamps worth \$75.00 and one small motor, also science magazines. What have you in exchange. Gavin Lardier, 825 Sibley St., Hammond, Indiana.

SWAP: MOTOROLA CAR RADIO 7 tubes, Weston 0-7 voltmeter, 0-1.5 milliammeter, ham key, other radio parts for double-barreled shotgun or 30-30 or so rifle, or else, Nicholas Denogo, 8148 102nd Ave., Ozone Park, N. Y.

BAND UKR GUITAR ERECTOR motor, auto safety lighter, sharp tuner dial, 2 tube DC radio with amplifier, Postmarks, approval stamps, block folders with plate number, want duplicator. R. Lewis, Griffithville, Ark.

HAVE 2- 5 AND 10 METER RE-ceivers using 6F5-6C5-25L1-25Z5, also 6C6-76-43-25Z5 15-550 meter receiver. Want 5 tube Howard. Exchange printing for test equipment. Shelton Radio Club, 202 So. 2nd St., Brooklyn, N. Y.

SWAP BROWNING 35H AMATEUR receiver chassis, beat note oscillator, phone jack-stand by switch, perfect condition, just overhauled, new tubes, 12" dynamic speaker. Want 1935 Super skydrifter, Patterson PR12-1935, E. Marks, 109-19 96th St., Ozone Park, L. I., N. Y.

SWAP: TRAIN EQUIPMENT, stamps, telescopes, microscopes, army binoculars; also have radio magazines. Wanted—any type of short wave receiver. Send for list. Sid Mickelson, 3817 14th St., N.W., Washington, D. C.

WANT ADVANCED CANDLE code course and associated candle code typing course. Must be complete and in good condition. Have some radio parts or will pay cash if price is right. Harry Greulich, Republic, Ohio.

TRADE HIGH QUALITY 5 METER, 10 watt transceiver, 5 meter transceiver, pressure gauges. For quality test equipment or H.M.S. Pinafore records or album. S. Andrews, 11 Horatio St., Newark, N. J.

WILL SWAP TWO 350 MMF. condensers with diads, one 12A, four 01A tubes in perfect condition for one 1F4, two '30 tubes, three-circuit tuner to match a 350 mmf. condenser. Norman Minks, Terrebonne, Oregon.

WANTED—RECORDING OF "Stardust" 456 K.C. I.F. xtms and to John U. S. and foreign short-wave clubs. I QSL 100%. Paul Bahr, Marlon, Indiana, U. S. A.

WILL BUY ELECTRICAL PORTA-ble and switchboard meters or instruments. Edward L. Boardman, 428 E. 13th St., New York City.

WANT TO TRADE OR BUY transmitting parts. Need: x-tal mlke; power supply components; audio x-formers; tank coils, condensers, etc. \$100 watt transmitter. Have: 843, 801 (fused 10 hours); .410 shotgun; cash. Dean Cooper, So. 17th, Fort Dodge, Iowa.

WANTED: ALL TYPES RADIO testing equipment, also Riders manuals in A-1 condition, also a short course in radio for beginners. Cash. Fred Habson, 501 E. Lowe St., Fairfield, Iowa.

HAVE ELECTRICAL LIBRARY. QST Magazines, other magazines, radios, radio parts, meters, other things. Send swap list for swap list. All letters answered. Want test oscillator and crystal pickup. Bert Agnew, 360 North Rockhill, Alliance, Ohio.

STAMPS TO TRADE! 1300 IN EX-ensive album. Would like to get some value in running order or what have you in this line? Roger Almar, Jr., Concord Rd., Westford, Mass.

WHAT AM I OFFERED IN TRADE for: Radio parts, Robotrol, auto fan roller skates, sheet metal punch, telescope, Jissaw, 2 books? More information on request. Best trade offer takes them. Arthur Hiller, Manito, Ill.

SWAP GENEMOTOR 6 VOLT IN-put, 135 volt 30 ma. output for 6L6 crystal oscillator or preselector or what have you? Write: Lester Fuller, Jr., Selkman, Ariz.

SWL EXCHANGE

SWLS FROM ARIZONA, ARKAN-sas, Delaware, Georgia, Idaho, Kentucky, Nevada, New Mexico, North Carolina, North Dakota, Rhode Island, South Dakota, Tennessee, Vermont, Wisconsin, Wyoming—send your card. 100% QSL. QRA: Jack Hartley, 88 Diamond Bridge Ave., Hawthorne, New Jersey.

IF FELLAS AND YLS, LET'S swap cards. I QSL 100%. You want mine—need yours. QRA: Robert J. Ellis, 3539 17th St., San Francisco, Calif.

WOULD LIKE TO EXCHANGE card with SWL's or A.A.'s anywhere. I QSL 100%. F.N.U. Francis Leslie Leach, 28 Wellington Street, Gloucester, England.

ATTENTION SWLS IN U. S. A. and foreign countries. I QSL and exchange shack photos and postcards of the N. Y. fair 100% and answer promptly. QRA: C. Paterni, 104-44 108th St., Richmond Hill, L. I., N. Y.

SWLS EXCHANGE CARDS WITH all countries. Have attractive VK card. I definitely QSL. Also welcome correspondence on QSL for same. C. Jarlett, 26 Edith Street, Hurstville, N.S.W., Australia.

I WILL GLADLY EXCHANGE SWL cards with anyone anywhere. Carl Prince, Clifton, South Carolina, U. S. A.

SWLS OF THE WORLD U. S. A. and overseas. want to swap SWL cards with all of you. QRA: Bob Anderson, Metropolis, Ill.

SWLS AND HAMS ANYWHERE in the world. I wish to correspond with you. Your SWL or QSL appreciated. I will send you my SWL. QRA: Ed Hoffman, 1744 Wilmet Ave., Chicago, Ill., U. S. A.

WOULD LIKE TO SWAP SWL cards with anyone anywhere. I QSL 100%. QRA: Harlan C. Pruett, 514 Lindeberg Street, Shelby, North Carolina.

SWL FROM IDAHO, NEVADA, Wyoming, Delaware, North Dakota, Louis Kuecera, P.O. Box 102, Apache, Okla.

I EXCHANGE SWL CARDS WITH the entire world. Send me your card and get mine in return. I correspond also. Let's hear from all of you. Ed Ziny, 7217 S. California, Chicago, Illinois, U. S. A.

ATTENTION SWLS IN U. S. AND foreign countries. Let's swap cards. I QSL 100%. The QRA is Armand Lebeau, R.F.D. No. 1, Lee, N.H.

ATTENTION ALL SWLS WILL exchange correspondence and postcard views with anybody in any country. QRA: John Plitzer, 62 Bell St., City Island, New York, U. S. A.

TO ALL SWLS IN THE U.S.A. and foreign countries, would like to exchange my SWL card for one of yours, also swap "shack" photos. I QSL 100%. Howard Perkins, 14814 Pepper Avenue, Cleveland, Ohio, U. S. A.

ATTENTION SWLS IN CANADA, U. S. A. and all foreign countries. I would like to exchange SWL cards with you. Will positively answer all cards received with mine. James W. Newman, 45 Sixth St., New Toronto, Ontario, Canada.

I WOULD LIKE TO EXCHANGE cards with SWL's and Hams all over the world. I promise to QSL as soon as I get ur card. Larry Kozarozyski, 511 West Pine St., Mahanoy City, Pa., U. S. A.

SWLS OF THE WORLD. LET'S swap cards. 100% QSL anywhere by return post. QRA: Wilfred Tarrington, 28 Curzon Rd., Bradford Moor, Bradford, Yorks, England.

SWLS, LET'S SWAP CARDS. Will exchange cards with anyone in the world. Will QSL 100%. QRA: James Nelson, 1838 Erie Street, Toledo, Ohio, U. S. A.

SWL EXCHANGE WOULD LIKE to exchange SWL card in U. S. and foreign countries. I will send you my SWL card. Jose A. Garcia, S. Trinidad alta 23, Santlago de Cuba.

COME ON ALL U SWLS, XYL'S, YL's and OM. Send me ur crds and I will send u mine. QRA: Arnold Shafer, 14816 Pepper Ave., Cleveland, Ohio, U. S. A. 73's. I QSL 100%.

COME SWAPLERS AND GET YOUR-self an Idaho card. I QSL 100%. Will answer all cards. QRA: Herbst. General Delivery, Blackfoot, Idaho.

ATTENTION SWLS, ESPECIALLY you YL's, don't be shy. Let's hear from you. I QSL 100% with anyone, anywhere. My QRA is Stephen Mecerri, 34th St., John Pl., Stamford, Conn., U. S. A.

SWL ANYWHERE. WE WANT TO swap SWL cards. We QSL 100%. QRA: Marvin and Nathan Greenberg, 444 East 32nd St., Paterson, N. J.

SWLS! YOUR ATTENTION PSE. I will exchange SWL cards with any SWL in U. S. A. or foreign countries. All crds received will be promptly answered. What swap, gank? QRA: Bob Greenough, 48 Chapel St., Shirley, Mass.

ATTENTION SWLS ALL OVER the world. I will swap SWL cards 100% with anyone. You send yours, I'll send mine. QRA: Miles H. Mott, 61 Grace Street, Cranston, Rhode Island, U. S. A.

SWLS WILL EXCHANGE SWLS with anyone, anywhere. I QSL 100%. Harry C. Meier, 7 Roosevelt Ave., Cranford, N. J.

WOULD LIKE TO EXCHANGE SWL cards with any SWL or Ham in U. S. or foreign countries. I will QSL 100%. Leonard Meadows, 3855 Stanton Ave., New Boston, Ohio.

ATTENTION SWLS ALL OVER the world. I will swap SWL cards 100% with everyone. My QRA is Paul Ankerman, 404 Lima St., Wapakoneta, Ohio, U. S. A.

ATTENTION ALL SWLERS. I have a new card and wud like to exchange with you. I QSL 100%. QRA: Norman E. Whitton, 76 Green St., Greenwood, Mass., U. S. A.

ATTENTION ALL SWLS IN U. S. A. and foreign countries. Would like to exchange SWL cards with anyone. All cards received answered 100%. William Thistle, 7 Flint St., Greenwood, Miss.

I WOULD LIKE TO HEAR FROM Hams and SWL's anywhere. Will swap cards, photos or view cards 100% with anyone. Stan Brus, 1441 Bell Avenue, North Braddock, Penna.

HI, U HAMS ES SWLS, OM'S or YL's. Send me ur QSL or SWL. I QSL 100% anywhere with my SWL. QRA: M. Coutu, 31, Wingsfield Street, Portsmouth, England.

ATTENTION SWLS ALL OVER the world. I will swap SWL cards 100% with everyone. My QRA is Oscar Corwin, 753 S. Columbia St., Frankfort, Ind.

SWL CARDS SWAPPED WITH anyone. Come on in your hours. Mail me your card, mine in return, m.v. QRA: M. P. Wynne, 210 Hector Ave., Metairie Branch, New Orleans, La.

OVERSEAS SWLS SEND ME UR card. I will QSL 100%. Will also include Brighton view to any SWL sending link of his town to this QRA. R. T. Parsons, 14, Carlyle Avenue, Brighton, 7, Sussex, England.

ATTENTION HAMS — SWLS. Will swap QSL's, shack photos, with any OM's, YL's, XYL's or SWL's. Also pleased to try skebs, 20M, 40M, 80M, C.W. only. Hows about it? VETCW, Summerside, P.E. Island, Canada.

SWLS IN THE UNITED STATES and foreign countries. I exchange SWL cards 100%. Also radio parts to trade. QRA: Donald D. Warnock, Courser, Indiana, U. S. A.

ATTENTION DXERS — WOULD like to exchange notes on reception, receiving equipment, etc. I answer 100%. Also exchange SWL cards. Mario Carline, 2143 Central Ave., Ashland, Ky., U. S. A.

WILL BE GLAD TO EXCHANGE SWL cards and letters with all SWL and DXers all over the world. Albert Pickering, Jr., West Medway, Mass., U. S. A.

WILL EXCHANGE SWL CARDS with any SWL or Ham in U. S. and foreign countries. Also swap stamps 100%. All cards will be answered with my card. Robert Heulton, 1222 W. Thompson St., Phila., Pa., U. S. A.

FREE-FIFTEEN 10¢ PUBLICATIONS

featuring construction of the most popular short-wave receivers and transmitters

with a One-Year's Subscription to Radio & Television

THESE publications are large printed sheets which average in size about 11"x17", the majority of them printed on both sides. All have photographic reproductions of the complete project, as well as detail illustrations. In addition, there are complete wiring diagrams and various technical details to assist the experimenter and builder in constructing the set. Full parts lists are always given, and the printed text runs anywhere from 500 to 3,000 words, depending on the complexity of the radio receiver. ALL RECEIVERS AND TRANSMITTERS ARE STRICTLY UP-TO-DATE; THERE ARE NO ANTIQUES OR OUT-OF-DATE PUBLICATIONS IN THIS

LIST. These projects are particularly valuable to the experimenter and constructor who build "his own". Indeed, the 50 publications shown on this page represent the cream of recent radio construction by the master radio builders of America. Designs of this kind usually are sold for 25¢ to \$1.00 apiece, and frequently you do not get half the technical information we give you. When mailing us your subscription, use the special coupon on this page. Select your 15 projects by their serial numbers. We accept money orders, cash, checks or new U.S. stamps (no foreign stamps or currency accepted). If you send cash or stamps register your letter against possible loss.

THESE 15 PROJECTS, IF BOUGHT SINGLY, WOULD HAVE COST YOU \$1.50. YOU CAN NOW GET THEM ABSOLUTELY FREE!

HOW TO BUILD THE SWITCH BAND-2 RECEIVER. A low-cost receiver for 6-volt battery or A.C. operation which enables the short-wave fan to hear stations in all parts of the world. No. 1

HOW TO MAKE A 2-TUBE RECEIVER FOR THE BEGINNER. This receiver consists of detector and two audio stages. A double purpose tube is used to secure the 2 audio stages. Tubes are for 1½ volt battery operation. No. 2

HOW TO MAKE THE PORTABLE SUPERHET 4. An ace all-wave superhet for battery operation. This receiver features band-spread and has a built-in beat oscillator. No. 3

HOW TO BUILD A 4-BAND 3-TUBE SUPERHET. A 3-tube receiver giving 4-tube results. Rack and panel type construction is employed. It has a regenerative second detector. No. 4

HOW TO MAKE A FIXED-BAND 8-TUBE SUPERHET. This short-wave "fan" receiver tunes over a wide band of frequencies without coil switching or changing. It's a real performer. It operates directly from 110 V. A.C. and has band-spread. No. 5

HOW TO BUILD A 5-TUBE SUPERHET FOR FAN AND HAM. A sure-fire receiver for all short-wave enthusiasts. It uses plug-in coils and iron core I.F. transformers which assure plenty of gain. No. 6

HOW TO MAKE A TWIN-PENTODE RECEIVER. This receiver, especially designed for the beginner, employs but one dual purpose tube which gives results equivalent to a 2-tube receiver. It is for 2-volt battery operation with headphones. No. 7

HOW TO BUILD AN EFFECTIVE SHORT WAVE PRESELECTOR. A signal-booster that will greatly improve reception on any short-wave super. It employs two 6K7 tubes in parallel in a highly efficient circuit in which both input and output are tuned. No. 8

HOW TO BUILD A REGENERATIVE 2-TUBE. This unusual receiver has the tickler coil in the screen grid circuit of the detector. The receiver tunes from 9-270 meters; band-spread is included; metal or glass tubes may be employed. No. 9

HOW TO MAKE THE S.W.&T. COMMUNICATIONS RECEIVER. An unusually fine receiver for the critical Ham and Fan, incorporating many exceptional features. Regeneration is employed in the first detector stage which makes use of an acorn tube. The receiver also incorporates a noise-control circuit, variable selectivity control and a tuning meter. No. 10

HOW TO MAKE A BAND-SWITCHING 2-VOLT RECEIVER. This fine receiver for battery operation employs a band-switching arrangement, enabling the builder to tune from 18-550 meters by flipping a switch. No. 11

HOW TO BUILD THE MULTI-BAND 2 RECEIVER. A receiver for the short-wave beginner. It has a remarkable tuning range of 2-270 meters with band-spread on all bands. Plug-in coils are used and complete data for an A.C. power supply is given. No. 12

HOW TO MAKE THE VS-5 METAL TUBE SUPERHET. This complete all-wave receiver boasts, among other things, variable selectivity, metal tubes, AVC and band-spread. The tuning range is from 17-550 meters. No. 13

HOW TO BUILD THE BEGINNERS 2-TUBE SUPER. A simplified superhet using 2 volt battery tubes which is just the thing for the beginner. It employs plug-in coils which cover a tuning range from 15-200 meters. No. 14

HOW TO MAKE A T.R.F.-3 FAN RECEIVER. This is an all-around receiver employing 2 volt tubes. A T.R.F. stage ahead of the regenerative detector insures good selectivity and sensitivity. Band-spread is provided by a two-speed dial. No. 15

HOW TO BUILD THE FORTY-NINER—A RECEIVER FOR LEAN PURSES. This novel receiver features a space-charge detector and requires only 12 volts of B battery. It uses 2-49 tubes which may be operated from any 2 volt A battery. No. 16

HOW TO MAKE A REAL 5-METER SUPERHET. This carefully designed receiver for ultra-short wave reception employs a straightforward circuit. Careful placement and high quality parts insure fine results. No. 17

HOW TO BUILD THE 2-VOLT SUPER DX-4. This superhet, though small in size is big in performance. Using battery type tubes, it features continuous band-spread, and automatic volume control, which may be cut in or out as desired. No. 18

HOW TO MAKE THE ULTRA-HIGH FREQUENCY WIZARD-6. This is a first-class 5-meter super-regenerative receiver, using acorn tubes in the R.F. and detector stages. The other tubes are of the metal type. The use of the acorn tubes insures exceptionally fine results. No. 19

HOW TO BUILD A HIGH-GAIN METAL-TUBE RECEIVER. This little receiver is a real performer. Tuning from 10-200 meters. Continuous band-spread is provided. No. 20

HOW TO BUILD THE WORLD-WIDE 10-METER CONVERTER. Many enthusiastic reports have been received from the builders of this unit, which may be added to your present receiver for picking up 10 meter signals from all parts of the world. Only 2-tubes are used. No. 21

HOW TO BUILD A DE LUXE 3-TUBER. This is the receiver for the Ham or Fan who wants a really high class receiver of simple design. It employs an unusual band-spreading dial. The circuit, employing metal tubes, has a stage of T.R.F. followed by a regenerative detector and a stage of audio. No. 22

HOW TO BUILD THE OCTODE METAL TUBE-3. This receiver is capable of excellent performance on the short waves. It requires only one plug-in coil for each band as a stage of untuned R.F. precedes the detector. It also has an A.F. stage for boosting the volume to comfortable headphone level. No. 23

HOW TO MAKE THE 3-IN-1 REFLEX SET. A 2-tuber giving 4-tube performance is this receiver which does its work with a minimum of tubes. A 6F7 is used as a combined R.F. amplifier, detector and first audio stage; a 6C5 is used as second audio stage. No. 24

HOW TO BUILD THE 100 WATT QRM DODGER—A COMPACT 5-METER TRANSMITTER. This M.O.F.A. rig puts out a hefty signal and by use of a calibrated vernier oscillator control will overcome the QRM problem on 5 meters. No. 25

HOW TO BUILD A DE LUXE 5-METER MOBILE STATION. A really fine M.O.F.A. mobile transmitter which will work real DX on portable location. It employs five metal tubes. No. 26

HOW TO BUILD THE H-G-M MEDIUM POWER TRANSMITTER. A crystal control set with an output of 80 watts. Band-switching is employed for operation on the 80, 40, 20 and 10 meter Ham bands. It gave excellent results under test. No. 27

HOW TO MAKE THE 806 ALL-BAND TRANSMITTER. An unusual transmitter delivering 400 watts output from an 806 final amplifier. A crystal pen-tet oscillator is used, followed by a driver stage. Real DX has been worked on 10, 20, 40 and 80 meters with this smooth working job. No. 28

HOW TO BUILD A 125-WATT MODULATOR USING 35T's. This is an ideal unit for the amateur and will modulate any transmitter with a power input up to about 400 watts. A total of 10 tubes are used including the power supply unit. No. 29

HOW TO BUILD THE C-O-M 150 WATT TRANSMITTER. An unusual crystal oscillator, multiplier with but one tuned circuit. It uses a pair of RK37's in parallel with a RK39 driver. The crystal oscillator circuit uses a 6L6. No. 30

A LONG-LINES TRANSMITTER FOR 1-METER TRANSMISSION, AND A COMPANION RECEIVER. A really special job for the seriously minded experimenter. This outfit permits short distance contacts in this interesting band. No. 31

HOW TO BUILD A 200 WATT XMITTER WITH PEN-TET EXCITER. This transmitter will really go to town. The use of the Pen-Tet crystal oscillator and frequency multiplier circuit eliminates many headaches from cracked crystals. No. 32

HOW TO BUILD A 10 AND 20 METER TRANSMITTER. A 200 watt transmitter which worked world-wide DX on test. Although compact, it is highly efficient in the 10 and 20 meter bands. Five tubes are used. No. 33

HOW TO MAKE THE WIZARD 1-TUBE 50-WATT TRANSMITTER. An amateur, crystal-controlled c.w. transmitter using the RK20 screen grid pentode. In tests, it compares with 250-watters. No. 34

HOW TO MAKE THE "OSCILLODYNE" 1 TUBE WONDER SET. One of the most sensitive short-wave sets designed, employing a really new circuit for the first time. Battery operated. No. 35

HOW TO MAKE THE "19" TWINPLEX (ONE TUBE PERFORMS AS TWO) RECEIVER. One of the most sensitive 1-tube sets ever designed and very popular. No. 36

HOW TO MAKE THE IMPROVED 3-TUBE DOORLE SET FOR BATTERY OPERATION. One of the finest of the Doorle series, by the famous short-wave inventor. No. 37

HOW TO MAKE THE "GO-GET-EM 2" RECEIVER FOR THE BEGINNER. This unusual 2-tube circuit gives 3-tube results. Battery operated. Excellent for beginners. No. 38

HOW TO MAKE THE 1-TUBE ALL-ELECTRIC OSCILLODYNE. This is the famous electrified short-wave receiver. Easy to build for little money. Operates on A.C. and D.C. No. 39

HOW TO MAKE THE 2 TO 5 METER TWO-TUBE LOUDSPEAKER SET. This receiver may be used with batteries or with an A.C. power pack. Packs a big wallop. No. 40

HOW TO MAKE THE 3-TUBE BATTERY SHORT-WAVE RECEIVER. This receiver was a prize winner in SHORT WAVE CRAFT. An unusual short-wave receiver, easy to build. No. 41

THE BRIEF-CASE SHORT-WAVE RECEIVER AND HOW TO BUILD IT. So small that the entire set, batteries, head set, aerial and everything, goes into a brief case. Stations from Europe are often received. By Hugo Gernsback and Clifford E. Denton. No. 42

HOW TO BUILD THE POCKET SHORT-WAVE RECEIVER. One of the smallest, pocket-size, battery receivers ever designed by Hugo Gernsback and Clifford E. Denton. A marvelous set that brings in European stations. No. 43

HOW TO BUILD THE CIGAR-BOX 1-TUBE "CATCH ALL" RECEIVER. An effective short-wave battery set which fits into a small cigar box, insuring high portability yet great efficiency. No. 44

HOW TO BUILD THE "DUAL-WAVE" SHORT-WAVE BATTERY RECEIVER. With this set, you can hear both ends of radiophone talk, on one set of phones. In other words, you can listen to a ship at sea and the land station communicating with it, simultaneously, by means of this double receiver. No. 45

HOW TO BUILD THE 1-TUBE "53" TWINPLEX RECEIVER. The twinplex, although it has only one tube, works as if it had two. Marvellous in efficiency. Uses either batteries or A.C. power pack for "B" supply. No. 46

HOW TO BUILD THE PORTABLE MINIDYNE SHORT-WAVE BATTERY SET. Uses no aerial, no ground. The total weight is 3½ lbs. and measures 5x5x6 inches. Self-contained batteries, tube, condensers, and loop. Highly sensitive circuit. No. 47

HOW TO BUILD THE HAM-BAND "PEE-WEE" 2-TUBE. A dandy receiver with high efficiency and band-spread tuning. Works a loudspeaker, yet the entire receiver is no larger than your hand. Works with either batteries or an A.C. power pack. No. 48

HOW TO BUILD THE DUO-AMPLIDYNE. The ideal 1-tube set for the beginner. One of the finest 1-tube sets; it really gives 2-tube performance. Made for battery operation. With only ten-foot antenna brings in the good European stations. No. 49

HOW TO BUILD THE "MONO-COIL 2". No more "plug in" coils. This set eliminates bothersome coils and is made to cover short-wave bands. Works with either batteries or A.C. power pack. No. 50

RADIO & TELEVISION, 99 Hudson Street, New York, N. Y.

Gentlemen: Enclosed you will find my remittance of \$2.50 for which enter my subscription to RADIO AND TELEVISION for One Year (12 issues). Send me promptly, absolutely FREE and POSTPAID, the 15 publications I have checked at the right (CANADIAN AND FOREIGN \$3.15.)

NEW SUBSCRIBER EXTEND PRESENT SUBSCRIPTION

Name

Address

City

State

Send remittance by check or money order. Register letter if you send cash or unused U. S. Postage Stamps.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35
36	37	38	39	40
41	42	43	44	45
46	47	48	49	50

RADIO & TELEVISION
99 HUDSON STREET
NEW YORK, N. Y.

On the "Ham" Bands

(Continued from page 765)

Call	Freq.	R	S	Where Heard
W5DW	28.8	3	6	France
W5EB	29.4	5	6	France
W6ITH	14.23	5	9	South Africa
W6BYL	28.85	5	5	France
W6NBU	29.015	5	6	France
W6PDB	29.0	5	8	France
W6EJC	14.16	4	6	France
W7AFS	14.228	5	3-6	France
W7AYO	29.0	5	7	France
W8BJJ	28.85	5	7	France
W8CRR	28.635	5	8	France
W8DST	28.75	5	9	France
W8ETJ	29.4	4	7	France
W8FAR	28.6	5	7	France
W8FGU	29.0	3	7	France
W8HJZ	29.425	5	8	France
W8JLW	29.5	-	-	France
W8NKA	28.915	5	9	France
W8EBS	14.24	5	8	France
W8KQ	14.155	5	7	France
W8OLJ	14.215	-	-	France
W8RSK	14.	-	-	France
W8KWN	14.195	5	8	France
W8NYD	28.6	5	9	France
W8OXY	29.1	5	8-9	France
W8PES	29.46	4	6	France
W8PPR	29.04	5	8	France
W8PYO	28.645	-	-	France
W8RKR	29.1	5	9	France
W8RLT	29.11	3	7	France
W8SRP	28.7	5	8	France
W9ULJ	14.225	5	7	France
W9ZAL	14.	-	-	France
W9UHA		5	7	South Africa
W9WBW		5	8	South Africa
W9CBJ	28.5	5	8	France
W9DRO	28.5	5	8	France
W9EAB	29.11	4	7	France
W9PBY	29.1	5	9	France
W9QHS	28.98	5	9	France
W9ROO	28.515	5	8-9	France
W9TZW	28.91	3	8	France
W9UDW	29.375	5	8	France
W9USU	29.0	5	9	France
W9UWY	28.68	5	8	France
W9WUC	29.315	5	9	France
W9ZNA	29.11	-	-	France

Reception of the South American amateurs is falling off fast. A few months ago, there were too many to publish, but this month it is quite a different story. We have a few reported, but not nearly as many as have been in the past.

VP3AA	14.195	5	9	Ark., Ill., Colo., Me., Ariz., Conn.
LUI DA	14.075	5	6-8	Ark., Wash., Ill., Ariz., N. Y.
LU2AC	28.05	5	8	Canada
LU4BC	14.030	4	6	Wash.
LU4DJ	14.19	5	9	Ark.
LU4PB	14.075	5	6	Ark., Md.
LU4CZ	14.1	4	6	Ill.
LU5CZ	14.04	5	8	Colo.
LU5CK	14.085	4-5	5-9	Ark., Wash., Ill., Ariz., N. Y.
LU7AG	14.02	5	7	Md.
LU7BK	14.095	4	5	Wash.
LU8AB	14.	5	9	South Africa
LU8EC	14.100	5	9	France
LU8BL	14.01	4	7	Ill.
LU9DM	14.	5	9	South Africa
PY1MH	14.01	5	8	France
PY2PV	14.080	4	7	Ark.
PY2MJ	14.155	5	5	N. Y.
PY2JC	14.272	5	5	N. Y.
PY2AC	14.	5	9	South Africa
PY2DA	14.105	4	6	Wash.
PY2CA	14.075	5	4-5	Ark., N. Y.
PY2CT	14.090	5	7	Ark.
PY5AQ	14.03	3-5	5-9	France, South Africa
PY7AI	14.	4	5	Colorado
PY8CF	14.3	5	6-7	Canada, N. Y.
CX1AA	14.090	5	8	France
CX1AH	14.290	5	6	France, Ill.
CX2CO	14.06	3	5	Ill.
CX3AL	14.055	4	5	Ill.
HC1FG	14.02	3	5	Wash.
HC1PZ	14.1	5	8	France, Ill.
HC2CC	14.3	4	6	Md.
HC2HP	14.16	4	6	Ill.
HC2BU	14.265	5	7-8	Canada, N. C., Ohio
ON4DM	14.01	5	5	France
ON4ZK	28.3	5	7	Canada
ON4FE	28.2	5	7	Canada
HK1AG	28.0	5	6	Canada
HK1AZ	14.035	4	6	Connecticut
HK2AA	14.05	4	6	Connecticut
HK3TO	14.25	5	6	N. Y.
HK3CG	14.2	5	8	N. Y.
HK3K	14.28	5	6	Me.
HK3CW	14.01	5	7	Ill.
HK4DF	14.27	5	7	Canada, Colo.
HK5EE	14.07	5	5	Colo.
HK5AR	14.272	3-4	5-7	Ill., N. Y.
HK5DB	14.087	4	6	Ill.
CE1BC	14.253	5	7	N. Y.
CE1AH	14.070	4	6	Wash.
CE2BX	14.	5	9	South Africa
CE2BR	14.14	5	8	Ill., Colo., Ariz.
CE3BK	14.059	5	8	Ill.
	14.10	4	5	N. Y.

(Continued on following page)

FREE CATALOGS and INFORMATION

By carefully reading the advertising columns, you will find many offers to furnish literature containing valuable technical information that will help you in your work. Use this list freely.

Firm	Business	Offer	No.	Cost	Adv. Page
Aerovox Corporation	Parts Mfr.	Catalog		Free	751
Allied Engineering Inst.	Kit Mfr.	Circulars		Free	746
Allied Radio Corp.	Mail Order	Spring Radio Catalog		Free	739
		Radio Builders Handbook		10c	
American Radio Institute	Radio School	Booklet		Free	748
Bliley Electric Co.	Parts Mfr.	Engineering Bulletin	E-6	10c	753
		Circular	A-6	Free	
Brush Development Co.	Parts Mfr.	Catalog		Free	739
Bud Radio, Inc.	Parts Mfr.	Catalog	RT49	Free	752
		Station Log & Data Bk.		10c	
Burstein-Applebee Co.	Mail Order	Catalog		Free	753
Cameradio Co.	Mail Order	1939 Catalog		Free	755
Candler System Co.	Code Course	Book of Facts		Free	748
Cannon, C. F., Co.	Parts Mfr.	Folder	T-4	Free	757
Capitol Radio Engineering Institute	Radio School	Booklet		Free	748
Cornell-Dubilier Elec. Corp.	Parts Mfr.	Catalog	166-A	Free	755
Coyne Electrical School	Trade School	Electrical Catalog		Free	707
		Radio Catalog		Free	
Dodge's Institute	Radio School	Catalog		Free	748
Gold Shield Products	Mail Order	Catalog		Free	750,761
Guthman, Edwin I., & Co.	Set & Parts Mfr.	Information		Free	747
Hammarlund Mfg. Co.	Set & Parts Mfr.	1939 Catalog		Free	737
		Booklet		Free	
Harrison Radio Co.	Mail Order	Information		Free	753
Henry, Bob	Mail Order	Information		Free	750
Howard Radio Company	Set Mfr.	Booklet	430	Free	744
Instructograph Company	Code Machine	Information		Free	748
International Resistance Co.	Parts Mfr.	Literature		Free	743
Korrol Radio Products Co.	Parts Mfr.	Catalog		Free	757
Lafayette Radio Corp.	Set Mfr.	Radio Catalog	76	Free	741
Levine, M. M.	Coil Winding Machines	Information		Free	753
Martin Research & Mfg. Corp.	Radio Keys	Catalog		Free	737
Mass. Radio School	Radio School	52-page Catalog		Free	748
Midwest Radio Corp.	Set Mfr.	1939 Catalog		Free	750
National Company, Inc.	Set & Parts Mfr.	Catalog		Free	I.B.C.
National Plans Institute	Publisher	Book Catalog		Free	750
National Radio Institute	Radio School	64-page Book		Free	705
National Schools	Radio School	Radio & Television Bklt.		Free	748
Radio & Technical Publ. Co.	Radio Textbooks	Circulars on each Book		Free	749
Radio Train. Assn. of Amer.	Radio School	Book		Free	748
RCA Institutes, Inc.	Radio School	Catalog		Free	748
Remington Rand, Inc.	Typewriter Mfr.	Catalog		Free	768
Sargent, E. M., Co.	Set Mfr.	Information		Free	753
Solar Mfg. Corp.	Parts Mfr.	General Parts Catalog	9S	Free	739
		Transmitting Catalog	2X	Free	
		Condenser Testers Cat.	CBCC-1	Free	
Sprague Products Co.	Parts Mfr.	Condenser Catalog		Free	757
Sprayberry Acad. of Radio	Radio School	52-page Book		Free	745
Supreme Publications	Publisher	Information		Free	751
Telex Co.	Code Machine	Booklet	S-4	Free	748
Thordarson Electric Mfg. Co.	Parts Mfr.	Transmitter Guide	344	15c	747
		Sound Amplifier Guide	346	15c	
		Radio Service Guide	342	15c	
		Transformer Manual	340	50c	
Triplett Electrical Inst.Co.	Parts Mfr.	Catalog		Free	759
Tri-State College	Radio School	Catalog		Free	748
Turner Co., The	Parts Mfr.	Bulletin	41-A	Free	755
Wholesale Radio Service Co.	Mail Order	Radio Catalog	76	Free	741
X. L. Radio Laboratories	Parts Mfr.	Information		Free	750
Zenith Radio Corporation	Set Mfr.	Information		Free	B.C.

GREATEST BARGAIN

in 10 years



as little as

Remington NOISELESS Portable
NOW AS LITTLE AS 10c a day

10c A DAY

Imagine a typewriter that speaks in a whisper! You can write in a library, a sick room, a Pullman berth, without disturbing others. And superb performance that literally makes words flow from the machine. The Remington Noiseless Portable is equipped with all attachments that make for complete writing equipment—it manifolds and cuts stencils perfectly. Furnished in black with chromium fittings.

SPECIFICATIONS

Standard keyboard. Takes paper 9.5 inches wide. Standard size, 12 yard ribbon. Makes up to 7 legible carbons. Back spacer. Paper fingers. Roller type. Black key cards with white letters. Double shift key and shift lock. Right and left carriage release. Right and left cylinder knobs. Large cushion rubber feet. Single or double space adjustment. A brand new NOISELESS typewriter, right off the assembly line.

10-DAY FREE TRIAL

For the first time in history you can own a genuine Remington Noiseless Portable for as little as 10c a day or \$3.00 a month. Think of it! The finest Remington Portable ever built at the lowest terms we have ever offered.

And you don't risk a penny! We will send this brand new Remington Noiseless Portable for a **TEN DAYS' FREE TRIAL!** If you are not satisfied, send it back. We pay all shipping charges.

FREE TYPING COURSE

With your Remington Noiseless Portable—absolutely free—a 19-page course in typing teaching you the Touch System, always used by experts. With the help of this course you will find typing the most enjoyable way you ever wrote.



SPECIAL CARRYING CASE

Carrying Case, handsomely covered in DuPont fabric is included with your purchase. The case makes it easy to take your machine anywhere. You can use it on trains, or on your knees at home. Don't delay. Mail the coupon.



MAIL NOW
Remington Rand Inc. Dept. 300-4
465 Washington St., Buffalo, N. Y.

Tell me, without obligation, how to get a Free Trial of a new Remington Noiseless Portable, including Carrying Case and Free Typing Course for as little as 10c a day Send Catalog.

Name.....
Address.....
City.....State.....

On the "Ham" Bands

(Continued from preceding page)

Call	Freq.	R	S	Where Heard
CE3DU	14.05	5	6	France
YV1AQ	14.005	5	6	Wash.
YV1AP	14.2	5	7	Ohio
YV4E	14.2	5	8	Me.
YV4APB	14.16	4	7	Me.
YV4ABG	14.089	4-5	4-8	Ill., Me., N. Y.
YV4AE	14.065	5	7	Wash., Ill., N. J., Colo., Ariz.
YV5AK	14.030	5	8	France, Conn.
YV5ADY	14.11	5	5	N. Y.
YV5ABY	14.1	5	9	Ohio, N. Y.
YV5AY	14.1	5	4	N. Y.
YV5AE	14.165	4	7	N. J.
YV5ABF	14.06	4	6	Colo.
YV6AM	14.087	4	7	Ill.
VP4TK	14.1	5	6	France

Due to the large number of Europeans heard and reported by our observers during January, it is impossible for us to print the usual list. This continent seemed to be very well heard last month, and about two hundred stations were reported. Therefore, we will skip Europe for this issue, but continue to send in your reports on this continent as it will probably be used in the next issue.

From Australia we have only a very few stations reported. They were rarely heard during January.

VK2XU	14.1	5	8	France
VK2ABU	14.05	5	8	Penna.
VK2RY	14.234	4	7	Penna.
VK2JO	14.135	4	6	Ariz.
VK2GN	14.	4	6	South Africa
VK2TL	14.4	5	6	Ohio
VK2AFQ	14.1	5	6	Ohio
VK3KX	14.25	5	9	France
VK3XG	14.337	4	6	Penna.
VK4JP	14.	4	6	South Africa
VK5MF	14.3	5	8	France
VK7CL	14.09	4-5	6	Penna., Ohio
VK9VG	14.31	5	6-8	France

Oceanic stations increased in number during January, particularly those located in the Hawaiian Islands and the Netherland Indies.

K6OFW	14.225	4-5	7-8	Kan., Colo., France, South Africa, Ala.
K6ILW	14.12	5	6-8	Ark., Ore., Colo.
K6IQN	14.085	4	7	Ark., Ill., Colo.
K6CMC	14.1	5	6	Ark., Wash.
K6OQ	14.2	5	6	Ark.
K6RG	28.575	4	8	Ark.
K6GAS	14.235	5	8	Canada
K6PLG	28.4	5	7	Ore.
K6TPV	28.5	5	7	Ore.
K6QQM	28.9	5	8	Ore.
K6LKN	28.5	5	8	Ore.
K6BNR	14.18	5	9	Wash., Ill., Colo., Ariz., Utah
K6PLZ	14.185	5	8	Wash., Ill., Colo.
K6OQE	14.190	5	8	Wash., Ill., Colo., Ariz.
K6OJI	28.375	5	9	Penna.
K6OJI	14.2	5	9	Wash., Ill., Colo., Ariz.
K6KGA	14.18	4-5	3-7	Wash., Ill., Colo., Ariz., Utah
K6MZQ	14.185	4	7	Wash., Colo.
K6OTH	14.175	5	8-9	Wash., South Africa
K6BIR	29.01	4	5	Ill.
K6NVV	28.75	5	6	Ill.
K6QAF	14.21	5	5	Colo.
K6DTT	14.250	5	9	South Africa
VR6AY	14.342	4-5	5-6	Kan., Ohio, Ill., France, Colo., Ala., South Africa

KA1ME	14.145	4-5	6-8	Kan., South Africa
KA1CS	14.310	5	9	South Africa
KA1HS	14.282	5	8	South Africa
KA1BH	14.11	5	9	South Africa
KA1JM	14.	5	8	South Africa
KA2OV	14.228	4	5	Utah
KA7EF	14.14	5	6	Utah, Wash., South Africa
VR2FF	14.2	5	5	France
PK1MF	14.26	5	8	France
PK1MX	14.08	5	9	France
PK1VY	14.285	5	9	France
PK1ZZ	14.3	5	9	France
PK1GR	14.	5	8	South Africa
PK2KT	14.	5	8	South Africa
PK2AY	14.295	5	9	France
PK2FS	14.14	5	9	France
PK3WI	14.225	4-5	6-9	France, South Africa
PK4CB	14.34	5	6	France
PK4KH	14.3	5	7	France
PK4KS	14.31	4	6-7	Kan., Ariz., N. Y.
PK6XX	14.050	5	8	France
ZL3GU	14.3	-	-	France
ZL3IF	28.25	5	6	Ore.
ZL4CB	14.115	4	4	France
ZL6AZ	28.1	5	7	Ore.

Well, that finishes it for another month. It is hoped that you will like our new arrangement, and your letter of comment will be greatly appreciated. If you have any ideas for bettering this department, send them in to us. Your criticisms are always welcome.

Index to Advertisers

Aerovox Corporation	751
Allied Engineering Institute	746
Allied Radio Corporation	739
American Radio Institute	748
B	
Barter & Exchange Free Ads	762-765
Bliley Electric Co.	753
Brush Development Co., The	739
Bud Radio, Inc.	752
Burstein-Applebee Co.	753
C	
Cameradio Co.	755
Candler System Co.	748
Cannon, C. F., Company	757
Capitol Radio Engineering Institute	748
Commercial Notices	762
Cornell-Dubilier Electric Corp.	755
Coyne Electrical School	707
D	
Dataprint Company	752
Dodge's Institute	748
F	
For Sale Ads	762
G	
Gold Shield Products	750, 761
Guthman, Edwin I., & Co., Inc.	747
H	
Hammarlund Manufacturing Co., Inc.	737
Harrison Radio Co.	753
Henry, Rob.	750
Howard Radio Company	744
Hudson Specialties Company	754
I	
Instructograph Company	748
International Resistance Co.	743
K	
Korrol Radio Products Co.	757
L	
Lafayette Radio Corp.	741
Levine, M. M.	753
M	
Martin Research & Manufacturing Corp.	737
Mass. Radio School	748
Midwest Radio Corporation	750
N	
National Company, Inc.	Inside Back Cover
National Plans Institute	750
National Radio Institute	705
National Schools	748
R	
Radio Amateur Course	Inside Front Cover
Radio & Technical Publ. Co.	749
Radio Publications	756, 760, 761
Radio Training Assn. of America	748
RCA Institutes, Inc.	748
Remington Rand, Inc.	768
S	
Sargent, E. M., Co.	753
Solar Mfg. Corp.	739
Sprague Products Co.	757
Sprayberry Academy of Radio	745
Supreme Publications	751
T	
Technifax	756
Telex Co.	748
Thordarson Electric Mfg. Co.	747
Triplet Electrical Instrument Co.	759
Tri-State College	748
Turner Co., The	755
W	
Wellworth Trading Company	756, 759
Wholesale Radio Service, Co., Inc.	741
X	
X. L. Radio Laboratories	750
Z	
Zenith Radio Corporation	Back Cover

(While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.)



NC-44

If you judge receivers on the basis of performance per dollar of cost, you will find the National NC-44 an outstanding value. This seven-tube superhet covers from 550 KC to 30 MC in four ranges. The full-vision dial is carefully calibrated in frequency. A straight-line-frequency main condenser is used in conjunction with a separate band spread condenser, and both have inertia-type tuning. A CW oscillator is provided. The performance of the NC-44 is remarkably fine, even at ten meters where so many receivers are unsatisfactory. The Net Price is only \$49.50, including tubes, speaker and built-in power supply.



NATIONAL COMPANY, INC., MALDEN, MASS.

AMATEURS - YOUR THOUGHTS MAY BE WORTH MONEY

ZENITH RADIO CORPORATION

6001 DICKENS AVENUE

CHICAGO

February 15, 1939

OFFICE OF
E. F. McDONALD, JR.
PRESIDENT

To Radio Amateurs:

This is an invitation to every "ham" in the world.

Most advertisers in magazines, newspapers, etc., tell you how to spend your money. This is not that type of message.

I have always contended that the credit for most of the major developments we have in radio have been due to the American amateur. The radio industry's enormous laboratories have done little but refine that which the amateur discovered. The Zenith Radio Corporation is always ready to reward amateurs who send us suggestions that we have not before had, if we adopt them.

We haven't an engineer in our laboratory over forty years old - they're all ex-"hams," progressive and very much open-minded. To them nothing is impossible. We have found that it is not always the fellow who knows all the rules of why things won't work that produces real results. As a matter of fact, the contrary is usually true.

If you want to see an example of development, drop into a Zenith dealer's store and examine the Wavemagnet model of radio, just put on the market, using no antenna, ground or battery. This is not a set built for "hams." This job was suggested by an amateur and the improved shielded loop was refined by our laboratory. If you know how to build this loop better, tell us and, if your suggestion is novel and we adopt it, we will reward you.

So, you see this was not an ad telling you how to spend your money. It is just an invitation for more of you to correspond with us on further developments.

Cordially yours,

E. F. McDonald, Jr.

HC