

RADIO'S *Complete* MAGAZINE

# RADIO & TELEVISION


**RADIO CONSTRUCTION**

*Department*



**ELECTRICAL EXPERIMENTS**

*Department*

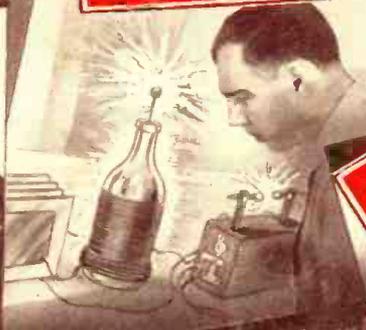


**MARCH OF RADIO**

*Department*



**RADIO HOOK-UPS**

*Depa*

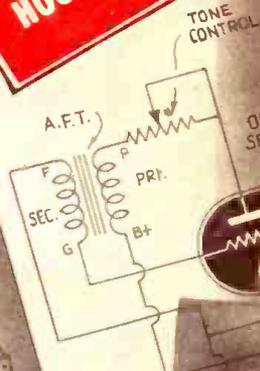


**EASY SET BUILDING**

*Department*



**RADIO KINKS**

*Department*

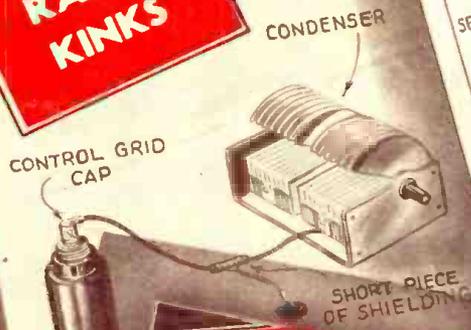


**TELEVISION NEWS**

*Department*




**AMATEUR RADIO**

*Department*

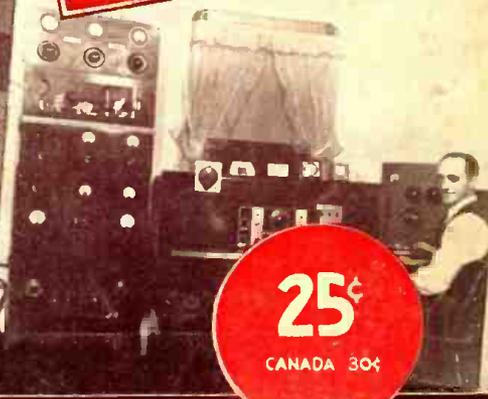

**RADIO PATENTS**

*Department*

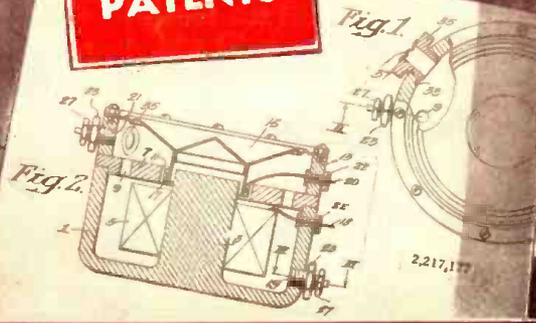

**25¢**

CANADA 30¢

**HUGO GERNSBACK**  
EDITOR

**AMATEUR & EXPERIMENTAL RADIO**

**FEB.**


**CONSTRUCTIVE RADIO ARTICLES**

**1941**


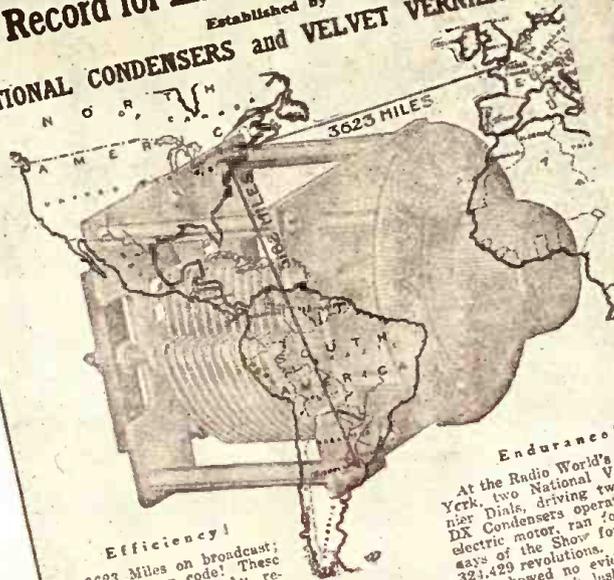
# Achievement!

A Record for Efficiency and Endurance  
Established by  
NATIONAL CONDENSERS and VELVET VERNIER DIALS



### Efficiency!

3623 Miles on broadcast; 5182 miles on code! These records were made by receiving sets of which National DX Condensers and Velvet Vernier Dials were parts. Nationals made the achievement possible. To get distance clearly buy Nationals. They give supreme satisfaction.

Sizes:	.001	.0005	.00035	.00025
Prices:	7.00	6.00	5.75	5.50

Complete with Velvet Vernier Dials. Write for Bulletin No. 104 Q  
Made by NATIONAL COMPANY, INC.  
Engineers and Manufacturers  
110 BROOKLINE ST., CAMBRIDGE, MASS. Estab. 1914

### Endurance!

At the Radio World's Fair, New York, two National Velvet Vernier Dials, driving two National DX Condensers operated by an electric motor, ran for the seven days of the Show for a total of 321,429 revolutions. At the finish they showed no evidence of lost motion or back lash. And they still possessed that velvety smoothness that makes Nationals so desirable.

## BACK IN 1924

### This advertisement appeared in QST Magazine

Back in the radio magazines of sixteen years ago, you will find the names of many almost-forgotten manufacturers. But you will also find a few names that have survived through the excellence of their products. In this select group, National has a special distinction, for with National even the products themselves have survived.

The Velvet Vernier Dial has survived the greatest endurance test of all, and is still the most popular of all dials for amateur work. The DX Condenser has passed the toughest of all efficiency tests; it is still manufactured for commercial and industrial use.

The design features that made these products outstanding 16 years ago have become standard practice. But building to stand the test of time is still, we think, National's most exclusive feature.

NATIONAL COMPANY, INC.  
MALDEN, MASS., U.S.A.

**Men NOW in Radio  
who Don't Think  
they know it All  
Read This**

You don't want to see younger, better-trained men push ahead of you, I know. You don't want Radio's new technical developments to baffle you either. I am sure. You want to get ready to "cash in" on Television, Frequency Modulation, too. I have helped many already in Radio to win promotions, to make more money. Read my message below.

J. E. SMITH, President  
NATIONAL RADIO INSTITUTE  
Established 25 years

He has directed the training of more men for Radio than anyone else—has helped men already in Radio to get ahead, and men not in Radio to get into Radio and win success.



**If You're NOT  
Working in Radio Now  
Read This**

Do you want to make more money? Do you want to cash in on your present interest in Radio, Television, Frequency Modulation? Do you want a full-time job with good pay in one of Radio's many fascinating branches? Or do you want to make extra money in your spare time to boost your present income? If you want to do either of these things—you owe it to yourself to find out how I have trained hundreds of men for jobs in Radio. MAIL THE COUPON BELOW—TODAY.

# Make Me Prove I Can Train You at Home for RADIO and TELEVISION

Clip the coupon and mail it. I'm certain I can train you at home in your spare time to be a Radio Technician. I want to send you a sample lesson free; to examine, read. See how clear and easy it is to understand. See how my Course is planned to help you get a good job in Radio, a young, growing field with a future. You don't have to give up your present job, or spend a lot of money to become a Radio Technicinn. I train you at home nights in your spare time.

**Many Radio Technicians Make  
\$30, \$40, \$50 a week**

Radio broadcasting stations employ operators, technicians, and pay well for trained men. Radio manufacturers employ testers, inspectors, servicemen in good-pay jobs with opportunities for advancement. Radio jobbers and dealers employ installation and servicemen. Many Radio Technicians open their own Radio sales and repair businesses and make \$30, \$40, \$50 a week. Others hold their regular jobs and make \$5 to \$10 a week fixing Radios in spare time. Automobile, police, aviation, commercial Radio; loudspeaker systems, electronic devices, are newer fields offering opportunities to qualified men. My Course includes

Television and Frequency Modulation which promise to open good jobs soon.

Charles F. Helmuth, 419 N. Mass. Ave., Atlantic City, N. J., writes: "I started Radio in the Marines. Later I took the N. R. I. Course. Now I am my own boss, and get jobs over others who were sure they had them. I owe plenty to N. R. I. Training." James E. Ryan, 119 Pebble St., Fall River, Mass., writes: "I was working in a garage when I enrolled with N. R. I. I am now Radio service manager for the M— Furniture Co. for their four stores."

**Many Make \$5 to \$10 a Week Extra  
in Spare Time While Learning**

The day you enroll, in addition to my regular Course, I start sending you Extra Money Job Sheets—start showing you how to do actual Radio repair jobs. Throughout your Course I send plans and directions which have helped many make \$5 to \$10 a week extra in spare time while learning. I send special Radio equipment; show you how to conduct experiments, build circuits. My 50-50 training method makes learning at home interesting, fascinating, practical. I devote more than 10 Lesson Texts exclusively to Television, and in addition Television fundamentals are covered by my regular Course.

**You Get This Professional Servicing Instrument**



This instrument makes practically any test you will be called upon to make in Radio service work on both spare time and full time jobs. It can be used on the test bench, or carried along when out on calls. It measures A.C. and D.C. voltages and currents; tests resistances; has a multi-band oscillator for aligning any set, old or new. You get this instrument to keep as part of your N. R. I. course.

**Get Sample Lesson and 64-Page Book  
Free — Mail Coupon**

Act today. Mail coupon now for Sample Lesson and 64-page Book. They're FREE. They point out Radio's spare-time and full-time opportunities and those coming in Television; tell about my Course in Radio and Television; show more than 100 letters from men I trained, telling what they are doing and earning. Read my money back agreement. Find out what Radio offers you. Mail the coupon in envelope or paste on penny postcard—NOW!

J. E. SMITH, President  
Dept. 1883, National Radio Institute  
Washington, D. C.

**SAMPLE LESSON FREE**

I want to prove that my Course gives practical, money-making information; is easy to understand—is what you need to master Radio. My sample lesson text, "Radio Receiver Troubles—Their Cause and Remedy," covers a long list of Radio receiver troubles in A.C., D.C., battery, universal, auto, T.R.F., super-heterodyne, all-wave, and other types of sets. And a cross reference system gives you the probable cause and a quick way to locate and remedy these set troubles. A special section is devoted to receiver checkup, alignment, balancing, neutralizing and testing. Get this lesson FREE. No obligation. Just mail coupon

**GOOD FOR BOTH 64 PAGE BOOK FREE  
SAMPLE LESSON FREE**

J. E. SMITH, President, Dept. 1883  
National Radio Institute  
Washington, D. C.

Dear Mr. Smith: Mail me FREE, without obligation, your Sample Lesson and 64-page book, "Rich Rewards in Radio," which tells about Radio's spare-time and full-time opportunities and explains your 50-50 method of training men at home to be Radio Technicians. (No salesman will call. Write plainly.)


(Please Check)

I AM doing Radio work.  I am NOT doing Radio work.

Name ..... Age .....

Address .....

City ..... State ..... 14X1

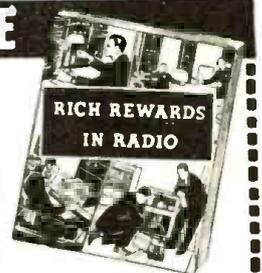

# RADIO & TELEVISION

*The Popular Radio Magazine*

February — 1941  
Vol. XI No. 10

HUGO GERNSBACK, Editor  
H. WINFIELD SECOR, Manag. Editor  
ROBERT EICHBERG, Television and Digest Editor

## In March Issue

An F-M Receiver for the Home Constructor—L. M. Dezettel  
5-Tube Compact Receiver—R. W. Baetz  
Principles of Frequency Modulation—Part II—F. L. Sprayberry  
A Compact High Fidelity 20-Watt Amplifier—H. D. Hooton, W8KPX  
A New F-M System for Amateurs—With Details of Transmitter and Receiver Construction — Ricardo Muniz, E.E., Donald Oestreicher, Warren Oestreicher  
More on the Compact Kilowatt Transmitter—Larry LeKashman  
Bamboo "Beam" Antenna Construction

## In This Issue

### GENERAL FEATURES

Editorial—

YOU Are the Editor—

Hugo Gernsback ..... 581

### MARCH OF RADIO

Color Television on Standard Receivers ..... 582

New F-M Station Has Unique Christening ..... 583

Fluorescent Flag Glows at Night ..... 584

Centimeter Wave Signal Generator for 3000-4000 MC. .... 585

International Radio Review

Connecting Head Phones to Receiving Sets ..... 586

3-Tube A.C. Set ..... 586

Experimental Wheatstone Bridge ..... 586

High-Fidelity All-Wave Tuner, Herman Yellin, W2AJL ..... 589

14-Tube Communications Receiver, Charles R. Leutz ..... 592

A Brand New F-M System for Amateurs, Ricardo Muniz, E.E., Donald Oestreicher, Warren Oestreicher ..... 598

### RADIO CONSTRUCTION

"Power-Plant" for the Workbench ..... 588

High Fidelity All-Wave Tuner, Herman Yellin, W2AJL ..... 589

14-Tube Communications Receiver, Charles R. Leutz ..... 592

A Code Practice Oscillator, Wm. D. Hayes, W6MNU ..... 595

A "Pull-Swing" F-M System for the Amateur, Ricardo Muniz, E.E., Donald Oestreicher, Warren Oestreicher ..... 598

Directional Radio Beam Indicator, Leon F. Leffingwell ..... 602

Photo Cell Relay, L. M. Dezettel, W9SFW ..... 620

4-Tube Regenerative de Luxe Receiver, W. Ward ..... 628

Building a Small Oudin Coil, H. W. Secor ..... 630

### AMATEUR RADIO

14-Tube Communications Receiver, Charles R. Leutz ..... 592

Code Practice Oscillator ..... 595

A New F-M System for Amateurs ..... 598

Directional Beam Indicator ..... 602

Plaque Winner for Best Station Photo ..... 604

A Precision Frequency Monitor .. 606

Compressed Dipole Aerials ..... 608

"CQ", Larry LeKashman, W210P 612

### NEW FEATURES

Applied Radio—Principles of Frequency Modulation, F. L. Sprayberry ..... 616

Experimental Radio—Photo Cell Relay ..... 620

Radio Hookups ..... 622

Easy Set Building—4-Tube Receiver ..... 628

Electrical Experiments—Oudin Coil 630

Radio Patents ..... 632

### ELECTRICAL EXPERIMENTS

Photo Cell Relay ..... 620

Small Oudin Coil ..... 630

### TELEVISION NEWS

Color Television ..... 582

Election Returns Televised ..... 582

Compressed Dipole Aerials ..... 608

Television Patents ..... 632

### MISCELLANEOUS

What Do YOU Think? ..... 579

How to Learn the Code ..... 595

This Month's Ham Plaque Winner 604

Practical Antenna Hints, Larry LeKashman, W210P ..... 614

Frequency Modulation for the Beginner, F. L. Sprayberry ..... 616

Radio Hookups ..... 622

Question Box ..... 625

Radio Kinks ..... 626

4-Tube Regenerative Receiver ... 628

Electrical Experiments ..... 630

Radio Patents ..... 632

New Radio Apparatus ..... 634

An UHF Receiver for F-M and A-M, S. Gordon Taylor ..... 634

Book Review ..... 601

### Certified Circuits



When you see this seal on a set it is a guarantee that it has been tested and certified in our laboratories, as well as privately in different parts of the country. Only constructional—experimental sets are certified.

You need not hesitate to spend money on parts because the set and circuit are bona fide.

This is the only magazine that renders such a service.

Cover Composition by Hugo Gernsback and Thomas D. Pentz

RADIO & TELEVISION—Published monthly on the tenth of the month. Entered as second-class matter Feb. 15, 1938, at the post office at Springfield, Mass., under the act of March 3, 1879. Trademarks and copyrights by permission of H. Gernsback. Text and illustrations are copyright and may not be reproduced without permission. Subscription price \$2.50 a year in the United States (in foreign countries, 75c additional per year to cover postage; Canada 50c additional). Make all subscription checks payable to Popular Book Corporation.

Published by Popular Book Corporation. Publication Office—29 Worthington St., Springfield, Mass. Editorial and Executive Offices—20 Vesey St., New York, N. Y. HUGO GERNSBACK, President; EMIL GROSSMAN, Director of Advertising. European Agents: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, Fleet St., London, England; Brentano's—London and Paris. Australian Agents: McGill's Agency, 179 Elizabeth St., Melbourne.

Copyright 1941 by H. Gernsback

READ AND SEND **CODE**

Learn Easily at Home  
This Quicker Way



No experience needed. Beginners read code quickly, copy accurately. If already an op, speed up your wpm with this approved amazing all Electric Master Telex Code Teacher. Only instrument which records your sending in visible dots and dashes on specially prepared paper tape—then sends back your own key work at any speed you wish. Fascinating, foolproof—gets results because you learn by HEARING as well as SEEING. That is why thousands agree this method is surest and quickest. While not designated standard equipment, Telex is used at many U. S. Army Posts, Naval Training Stations. We furnish Complete Course, lend you the New All Electric Master Telex, and personal instruction with a MONEY-BACK GUARANTEE. Low cost, easy terms. Write today for folder S2, no obligation.

TELEPLEX CO., 67-69 Park Place, New York City  
In Canada write:  
CANADIAN ELECTRONIC INST., TORONTO, ONT.

**AMATEUR RADIO LICENSES**

Study for your licenses the "rhythm" way, the A.R.I. way. Acquire code proficiency in from 3 1/2 to 8 weeks. Theory taught in understandable, non technical language. Classroom courses in New York, home study courses for outside students. Write for list of calls of hundreds of licensed students now on the air.

AMERICAN RADIO INSTITUTE  
1123 BROADWAY, NEW YORK, N. Y.

**EXPERT PHOTOGRAPHY MADE EASY**

Successful photography as a career, for sparetime earnings or as a hobby—made easy through N.Y.I. Training! Personal teaching by leading photographers. Fascinating field, splendid opportunities. Commercial, News, Portrait, Motion Picture, Advertising and Color Photography. Personal Attendance and Home Study Courses. Booklet FREE! N. Y. INSTITUTE OF PHOTOGRAPHY, Dept. 11, 10 West 33 St., New York, N. Y. (30th Year)

**RADIO COURSES**

Mid-Term Classes Now Starting  
RADIO OPERATING—BROADCASTING  
RADIO SERVICING—practical course  
RADIO AMATEUR CODE & TELEVISION  
ELECTRONICS—1 yr. day course 2 yrs. eve. day and evening classes. Booklet Upon Request.

New York Y.M.C.A. Schools  
6 W. 64th Street New York City

**RADIO-TELEVISION**

Oldest, largest Radio-Television school in West trains you for good pay job. Complete instruction including Radio Construction and Service, Broadcast Operating, Sound, Talking Pictures, Television, Public Address, etc. Flexible plan to meet specific needs of those with or without jobs. Transportation allowed to L.A. Farm room and board while learning. Request Free Catalog.

NATIONAL SCHOOLS Dept. RT-2 Los Angeles

**RADIO TECHNOLOGY**

RCA Institutes offer an intensive course of high standard embracing all phases of Radio and Television. Practical training with modern equipment at New York and Chicago schools. Also specialized courses in Aviation Communications, Radio Servicing and Commercial Operating. Catalog Dept. RT-41.

RCA INSTITUTES, INC.  
A Radio Corporation of America Service  
75 Varick St New York, 1154 Merchandise Mart, Chicago

What Do YOU Think?

WHAT ONE READER THINKS OF R. & T.

Editor,

Just a scribble to let you know how much I'm enjoying your magazine.

I note in the "What Do You Think" column, that one reader wants more "1 and 2 tube hook-ups." I have several copies from 1932 to 1935, 36 of them. Perhaps I should mail them to him. If your readers have been buying the magazine very long from newsstands, they should have, by now, all the 1 & 2 tube hook-ups they will want to play with for a lifetime. Maybe he's a new-new beginner. He should ask some of the local boys for some help on set construction. I suppose I'm a little too hard on beginners, not remembering "once upon a time" I was a beginner, too.

I'm in radio for fun—it's a hobby with me. The XYL gets a "bang" out of it, too. She says it keeps me at home where she can watch me. Maybe that's the bang she gets! What!

M. E. VAN NATTAN,  
6151 Walnut Ave.  
Long Beach, Calif.

(There are new hook-ups now and then, you know.—Editor)

A YUGOSLAVIAN SHORT WAVE LISTENER

Editor,

I am a Yugoslav for the first time in the U.S.A. and am a wireless operator on a Yugoslav ship. I am also a Radio Amateur and SWL Fan.

I have at home in Split, Yugoslavia, a Hallcraft Super-Skyrider receiver but my wish is to have one transmitter and to work with the fellows throughout the world. At present we cannot have a transmitter in Yugoslavia for private use.

For years I have received very good phone signals from all continents, and I am sorry that I cannot show you proof of the success of my constant labors.

My greatest wish is to join the Short Wave League and to have a membership in the V.A.C. Club.

All fellows and SWL's who wish to know something about radio in Yugoslavia, and who will write me or send their cards, addresses, etc., may do so. I am enclosing my address and will be very glad when they write; I will answer all.

With best wishes to R. & T. magazine, I remain,

JOSEF A. MLADINA,  
Solinska cesta 40,  
Split, Yugoslavia,  
Europe.

IMPATIENT FOR EACH NEW COPY

Editor,

The tenth of each month finds me at the newsstand anxiously waiting for my copy of RADIO & TELEVISION. I truthfully believe that your magazine is the most complete and understandable radio magazine. I am typical of hundreds of other Short Wave Fans who are just starting to explore the

(Continued on page 640)



36 Volumes in 1 Big Book!

1. Broadcasting System
2. Sound, Speech, Music
3. Electric Theory; Electric Current
4. Elec. Units; Ohm's Law
5. Elec. Circuits; Batteries
6. Magnetism
7. Electromagnetism
8. Electromagnetic Induction
9. Inductance
10. Capacitance; Condensers
11. A.C. Circuits
12. Filters
13. Measuring Instruments
14. Radio Waves
15. Broadcasting
16. Receiving
17. Vacuum Tube Principles
18. V. T. Characteristics
19. Vacuum Tube Construction
20. V. T. Detector and Amplifier Action
21. Radio Frequency Amplification
22. Superhets
23. R.F. Amplifiers; Tuning Coils
24. Audio Amplifiers
25. Loudspeakers
26. Battery Receivers
27. Power-Supply Units
28. Elec. Receivers
29. Auto and Aircraft Radio
30. Phone Pickups; Sound Systems
31. Short-Wave Cells; Cathode-Ray
32. Phototelephony
33. Television
34. Antennas and Grounds
35. Test Sets; Servicing
36. Sound Pictures

**Ghirardi's COMPLETE Course will train you QUICKLY**

Here's your BIG CHANCE to get a thorough training in basic RADIO FUNDAMENTALS—quickly, easily, without previous experience or study. Today there are BIG OPPORTUNITIES and lots more jobs for men with radio training—in radio factories, in radio service shops—and in all branches of the Army and Navy.

**RADIO, SOUND, TELEVISION —MADE EASY AS A, B, C.**

Ghirardi's famous RADIO PHYSICS COURSE is the quickest short-cut radio training you can find. The most complete and most economical too. His clear explanations, graphic illustrations, and 856 self-testing Review Questions make it as easy as understand as a primer. Thousands of successful radio men got their start with this book, and it's used by more radio schools and students than any other radio text in the world! Get this whole 972-page course today for only \$4—and get started on your own radio career!

**Use It 5 Days —OUR RISK!**

Your money back if not fully satisfied. Don't delay—get started—mail this coupon at once!

972 Page 508 illus.

**\$4**  
Only

**RUSH COUPON TODAY!**

Radio & Tech. Publ. Co.,  
R&T-21, 45 Astor Pl., N. Y.  
 Enclosed find \$4. (\$4.50 foreign) for my copy of "RADIO PHYSICS COURSE," with your 5-day Money-Back Guarantee.

Name .....  
Address .....  
City ..... State .....  
 Send me free literature.

**RADIO OPERATOR'S LICENSE GUIDE**

By WAYNE MILLER

Here's a new Guide Book that contains over 1250 questions and answers which will help you pass the new six element examinations for a commercial radio operator's license. It correctly answers all questions contained in the study guide that was recently released by the Federal Communications Commission for the use of those proposing to take its examination. It will not only see you through your examination, but will also serve as a valuable future reference book. \$3.00 postpaid. Refunded if not satisfactory.

R. A. COWELL  
PUBLISHERS' REPRESENTATIVE  
411 7TH STREET, BELLE PLAINE, IOWA

**LEARN RADIO TELEVISION**

500 LICENSED graduates placed in past 7 years in shipping, broadcasting, aviation, police, etc.; we also teach radio servicing and repairing; new beginners' class now forming; 60-page catalog free; oldest, largest and best equipped.

MASS. RADIO SCHOOL  
18 BOYLSTON ST., BOSTON, Mass., Est. 1899

**RADIO ENGINEERING,**

broadcasting, aviation and police radio, servicing, marine radio telegraphy and telephony, Morse telegraphy and railway accounting taught thoroughly. 48 weeks' Engineering course equivalent to 3 years of college radio work. All expenses low. Catalog free. School established 1874. Dodge's Institute, Turner St., Valparaiso, Ind.

# THE FINEST RADIO BOOK FREE

WE EVER OFFERED :-  
the 1940-41 Radio-Television Reference Annual  
With \$1.00 subscription to  
RADIO & TELEVISION


WITH our compliments, we want to send a copy of the 1940 RADIO-TELEVISION REFERENCE ANNUAL to you FREE, if you will simply take advantage of RADIO & TELEVISION magazine's special subscription offer NOW. This offer is being made for a limited time only.

The 1940 RADIO-TELEVISION REFERENCE ANNUAL has 68 pages, large size 8½ x 11½, with over 170 illustrations. The contents of this book has never appeared before in handy book form, its pages cover practically every branch of radio sound, public address, servicing, television, construction articles for advanced radio men and technicians, time and money-saving kinks, wrinkles, useful circuit information, "ham" transmitters and receivers, and a host of other data.

The Annuals have always been regarded as a standard reference work for every practical branch of radio operation and service. This 1940 edition ably sustains this reputation. Every radio man wants a copy of this valuable book. Just as this book will be of unquestionable value to you, so, too, will every monthly issue of RADIO & TELEVISION. This magazine brings you big value every month. It keeps you intelligently informed about new developments in radio and television. You want the news, want it fully but concisely, want it first—that is why you should read RADIO & TELEVISION regularly.

This very special offer is made for just one purpose—we want you as a regular subscriber. The Annual, whose contents appears at the right, is not sold, but a copy is FREE to you if you subscribe now.

**SAME SIZE AS  
RADIO & TELEVISION**

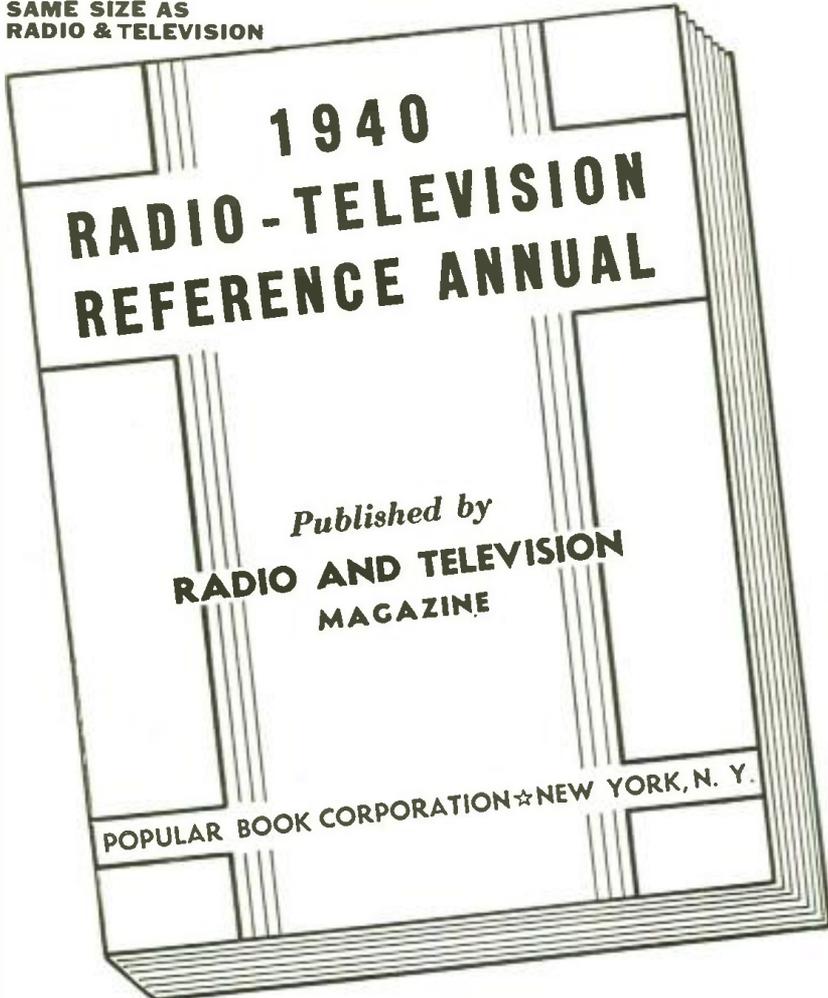

**THIS COUPON BRINGS YOU THE ANNUAL**

**RADIO & TELEVISION • 20 VESEY STREET • NEW YORK, N. Y.**

Gentlemen: Enclosed you will find One Dollar for which enter my subscription to RADIO & TELEVISION Magazine for Eight Months. Send me ABSOLUTELY FREE and POSTPAID, my copy of 1940 RADIO-TELEVISION REFERENCE ANNUAL.

This is a new order  Extend My Present Subscription

NAME ..... ADDRESS .....

CITY ..... STATE .....

**DON'T DELAY — MAIL TODAY!** RT-2-41

**Read the summary of contents  
in this FREE BOOK!**

THE 1940 RADIO-TELEVISION REFERENCE ANNUAL contains a collection of the best and most important articles. Covering as they do nearly every branch of radio, they form a handy reference works. In addition, many time and labor-saving kinks, circuits and wrinkles, tried and tested by practicing Servicemen, experimenters and radio fans have been included. This book cannot be bought anywhere at any price. Yet it is yours by merely subscribing. Use the convenient coupon below.

**BEGINNER'S SIMPLE INEXPENSIVE  
CONSTRUCTION ARTICLES**

Beginner's Breadboard Special - a 1-Tube High-Gain All-Wave Receiver—Wiring Pointers for Radio Beginners—A Watch Charm Size 1-Tube Set—Beginner's Simple Volt-Milliammeter—Making a 1-Tube Broadcast Loop Receiver—A.C.-D.C. Power Supply for Battery Portables—A 1-Tube Short-Waver with Band Coil Switching.

**MORE ADVANCED SET CONSTRUCTION**

The "High-Seas 4" Broadcast Lamp Radio—How to Build a 6-Tube 1.4-Volt Short-Wave Superhet for the "Ham" or Short-Wave Fan—Build the "Lunch Box 3" Super Set - a Broadcast Battery Portable—How to Build a Plug-Together 8 Tube Broadcast Set—The "5-in-4" All-Wave Radio for A.C. Operation—An Easily-Built 3-Tube Midget Broadcast Superheterodyne Receiver.

**THE SERVICEMEN'S SECTION**

Bass Tone Control—Simplified Variable Selectivity—Practical Servicing Pointers—Servicing Universal A.C.-D.C. Receivers—Killing the "Intermittent" Bug—A Service Shop A.C. to D.C. Power Supply—Sideline Money for Servicemen—Adding A.V.C. to any Screen-Grid T.R.F. Receiver—Iron Particles in Speaker Air Gap.

**TEST INSTRUMENTS**

A Useful Neon Lamp Tester—An Inexpensive Output Meter—Making Milliammeter Multipliers—Home-Made Frequency Modulator—The Busy Servicemen's V.T. Volt-Meter.

**PUBLIC ADDRESS AND AMPLIFIERS**

Build this Combination A.C.-D.C. Radio and Inter-Communicator—Speaker Placement in P.A. Work—The Design and Construction of an Inexpensive All-Push-Pull 10-Watt Amplifier—Obscure Sources of Hum in High-Gain Amplifiers—How to Build a High-Fidelity 5-Watt Versatile Amplifier.

**"HAM" SECTION**

Ultra-High Frequency Antennas—The Beginner's Low-Cost Xmitter—Modulator Meter—Phone Monitor—The Beginner's "Ham" Receiver—2½ Meter Acorn Transceiver.

**TELEVISION**

How to Build a 441 Line T.R.F. Television Receiver—Useful Notes on Television Antennas.

**MISCELLANEOUS**

Simple Photo-Cell Relay Set Up—Making a Burglar Alarm—How to Build A.C.-D.C. Capacity Relays—How to Make a Modern Radio Treasure Locator

**USEFUL KINKS, CIRCUITS AND WRINKLES**

Making a Flexible Coupler—Two-Timing Chime—A Simple Portable Aerial—An Improvised Non-Slip Screw-Driver.  
NOTE: The book contains numerous other useful Kinks, Circuits and Wrinkles, not listed here.

(approximately)

**45 ARTICLES**

(approximately)

**170 ILLUSTRATIONS**

**68 BIG PAGES**

**RADIO & TELEVISION  
20 VESEY STREET  
NEW YORK, N. Y.**

# RADIO & TELEVISION

Editorial

## YOU Are the Editor

By HUGO GERNSBACK, Editor

**B**ELIEVE it or not, *you*—the readers—are the real editor and it makes little difference what magazine or newspaper you read. It just means that it is always the reader who influences the editorial contents of any publication. Obvious as this is, it is seldom realized by the average reader who often has the erroneous idea that an editor is a sort of super-human creature who knows more about every subject than any one else. Nothing could be further from the truth. The editor only *interprets*; he may have set ideas of his own about certain subjects, but if he is a good editor he will keep these ideas in the background. After all, it is the reader who buys the publication, and unless he is satisfied with the ideas expressed in it, the publication won't last long. The great trouble with most readers, however, is that they take a magazine too much for granted, and the minute they do not agree with its policy, they drop it like the proverbial hot potato. Others when they do not agree with the editorial policy, immediately begin writing letters to the editor in no uncertain terms—and that is precisely what the editor wants them to do. No publication is worth its salt if it is not criticized, if suggestions are not given day in and day out by readers who either disagree or who think differently on certain subjects.

Here in RADIO & TELEVISION we are fully aware of these problems and we have always been alert not only to new trends, but to criticisms, particularly when such criticism is of a constructive variety.

The editor does not pretend to know it all—far from it—it is his business to present radio progress and other radio material in such form as he believes, that you, the reader, would like to have it. The editors have no preconceived notions as to what should go into the magazine and that is why they must use the guiding heads of its readers.

With all this in mind and feeling that it is possible to get every really worthwhile new and constructive idea from you, the readers, the editor would like to turn this page over to the readers in order to get the best radio thoughts in America.

RADIO & TELEVISION does not want this service for nothing. As announced on this page, the best editorial, or editorial suggestion, which is sent in during the month will be printed here, and the writer of the best letter will be awarded every month, until further notice, a valuable radio receiving set.

Remember that what is wanted are new or novel ideas or suggestions—how radio or television can be used to better advantage; how radio instrumentalities can be used more efficiently; what radio can do to help defense. Or any other worthwhile suggestion that may further the advance of radio in some way.

Other short reader editorials might be on the subject of your viewpoint on radio matters that will arouse discussion with other readers. What we do not wish to print on this page are laudatory letters regarding the magazine itself, or pet peeves on subjects that are not important to radio in general.

It is not necessary that your letters be long. Indeed, they can be quite short. Anywhere from 50 words up, but not more than 500 words, is desirable.

All that you and we want is "meat" and the shorter and the more concise each of your editorials, the better the readers and the editors will like them.

We are giving a few samples of readers' editorials which came in the mail, so you will understand what is wanted.

### THE CODE BUGABOO

If it's all boiled down to the bare facts, I think that learning the code has proved a bugaboo that has enlarged in so many minds that it scares many an embryo ham completely out. I know, it had me scared out too. Then one night I said to myself, "For man, you're just plain lazy, learn that code or forget Ham Radio." I had a lot of wild ideas about how I'd build a transmitter and all that goes with it, I guess everyone does, but there's that ticket looming up in the way. Well, I worked for an hour and a half memorizing the code and by that time I could spell out the name of anything in the room. I'm picking up speed little by little and eventually I'll have it up to where I want it, but the hardest part, as I see it, is over with.

Bob Forman, Monmouth, Ill.

### RADIO TREASURE HUNTING

If anyone tells you that Treasure Hunting with modern radio equipment, including an unromantic head, cannot be made a profitable business—dismiss the thought, for several are paying considerable income tax on account of discoveries of man hidden valuables. They do not use one type of equipment and carry something in their heads as well as hands. Their finds go unheralded for they know it is possible to pay a large premium for talking too much and in the wrong company. Opportunities beckon to those who are willing to make the investment in knowledge before expecting the dividend to come their way. Success in treasure hunting is based on knowledge and the ability to play "dumb" if occasion demands. Those who do not believe in the efficiency of modern equipment may be made into an invaluable aid if proper methods are used.

Thomas E. New,  
Santa Monica, Calif.

### "ENGLAND CAN TAKE IT"

*Editor's Note:* (As one half of the world never knows how the other half lives, the writer of the following letter deserves commendation for the fact that he takes the time to tell Americans regarding present-day English conditions.)

I have taken the trouble of sending you all these notes, etc., because I think you may find them interesting, particularly as there are now no amateur transmitters operating in this country. So I guess you will be interested to know what is going on here. (COPY OF MAIN DETAILS FROM LETTER FROM ENGINEER-IN-CHIEF'S OFFICE [RADIO BRANCH], HARROGATE, ENGLAND, IN ANSWER TO QUESTIONS ASKED BY THE NORTH MANCHESTER RADIO & TELEVISION SOCIETY REGARDING AMATEUR RADIO TRANSMITTING, ETC.)

1. Relative to the confiscation of amateur radio transmitting apparatus, I have to inform you that it is the intention to return such apparatus to the owners after the war and applications for restoration should be addressed to this department on the cessation of hostilities.

2. You can be assured that every reasonable precaution will be taken to ensure the safe custody of apparatus whilst held by the Post Office.

3. The call signs previously held by licensees are cancelled simultaneously with the relative licenses, and no claim to the use of a particular call in any future license could be allowed.

(Continued on page 637)

### FREE RADIO SET

A VALUABLE RADIO SET TO BE AWARDED MONTHLY

Every month, until further notice, RADIO & TELEVISION will award to one of its readers who submits the best short editorial, to be printed on this page, a valuable radio set. Other letters published on the editorial page will receive a free subscription to RADIO & TELEVISION magazine.

All letters for the next month's contest must be received by the editors by the 10th of the month.

For other details of this editorial contest, read further on this page.

## Colored Television on Standard Receiver with New Disc

A standard television receiver was made to pick up colored television images in a demonstration by Dr. E. F. W. Alexanderson to members of the National Television Systems Committee and George H. Payne, member of the F.C.C. The picture shows Dr. Alexanderson and Mr. Payne looking at the receiver.

The demonstration was staged at Dr. Alexanderson's home, where he had in-

stalled a two-color 24-inch revolving disk about a foot in front of the picture end of the cathode ray tube of his standard type receiver. As this whirled at 1,800 revolutions per minute, its transparent field of orange-red and greenish-blue reproduced the studio program in realistic colors. To do this, Dr. Alexanderson explained, a similar colored disk revolved before the iconoscope pick-up tube of the transmitter. Other

than the two disks, everything was the same as with black-and-white television at both studio and receiver.

"In our early experiments we tried both two- and three-color disks," Dr. Alexanderson said. "With two colors and a speed of 1,800 r.p.m. of the disk, the same color succeeded itself 30 times per second. With three colors, they succeeded each other 20 times per second, producing a color flicker. So that is why we decided upon the two colors for the present. We found it did not detract much from the three-color picture. This gives very good results without flicker, and we feel it is most practical with standard commercial receivers."

The demonstration is still of a developmental nature, and General Electric has no plans for introducing color to its television programs for the present.

Prominent among members of the committee which attended the demonstration was Dr. P. C. Goldmark, in charge of television engineering for the Columbia Broadcasting System, which is also interested in adding color to its programs. While in Schenectady the members of the NTSC visited General Electric's television and new FM stations in the Helderbergs and, after the demonstration at Dr. Alexanderson's home, met with G-E scientists for a conference in the company's research laboratory.



Dr. E. F. W. Alexanderson and George H. Payne, F.C.C. member, inspect the new two-color filter which converts black and white receiver to reproduce colored television images.

## Don Lee Television Station Has Novel Features

With excavation completed on the swimming pool atop Mount Lee, workmen recently reached the halfway mark on television station W6XAO, the new \$100,000 building to be the first structure erected exclusively for the electronics art.

A novel feature of the building is that it is entirely shielded with one-ounce copper sheeting on all four sides and the roof. The copper armored pure electro sheets came in sixty-inch wide 120-foot linear rolls and had to be applied with great precision. Especial care had to be taken in soldering the seams between sheets. More than 22,600 square feet of copper were used. The metal was applied to eliminate outside and intra-building interferences

with the delicate cathode tube cameras, according to Thomas Lee, president of the Don Lee Television System.

Purpose of the swimming pool will be to provide a compact stage of operation for "telecasts" of aquatic events. The pool measures 20' x 50'.

The two-story building will have one television stage 60' x 100' and another 25' x 40' with monitor rooms in addition to complete office facilities, transmitter room, experimental laboratory, scene storage rooms, makeup room, lounge viewing room, performers' lounge and other theatrical facilities. Since December 23, 1931, the Don Lee organization has spent more than \$350,000 in television.

With W6XAO located on top of the 1700-foot mountain the television range will be about sixty miles and will bring images to homes in San Fernando Valley, points beyond Malibu, Huntington Beach and Pomona, as well as all sections of Los Angeles and Beverly Hills, said Harry R. Lubcke, Director of Television.

### MOBILE UNITS ACTIVE

Since broadcasting election returns, NBC's television station, W2XBS, has been making mostly remote pickups. The trucks have brought viewers wrestling, hockey, boxing, football, and basketball this autumn and winter.

## Du Mont Discloses Election Return Methods

Somewhat tardily Du Mont engineers have released information as to how they covered election returns over W2XWV. It was done by means of a ticker tape projected on a screen and scanned by use of the usual pick-up tube. This was an experimental broadcast over a 50-watt transmitter and few persons in the metro-

politan area knew that it was on the air. It did not compare in coverage to the NBC telecast on election night, which was described in last month's issue of R. & T.

The accompanying pictures show first the arrangement of the teletype printer feeding directly into the ticker tape projector, which flashed the images onto a translucent screen.

The second picture shows how the screen was set up to be scanned. In the third picture an operator is seen checking the patterns on an oscillograph. A hood is provided over the cathode-ray tube, so that it may be seen clearly in an illuminated room. This permits accurate monitoring of the program.



## Alexanderson's Daughter Christens New FM Station

While her father and mother, Dr. and Mrs. E. F. W. Alexanderson, and her friend, Miss Ellen Wellman watched, Mrs. James H. Burnham crashed a high vacuum tube against the base of the General Electric's new FM antenna for station W2XOY in the Helderbergs near Schenectady. (Company engineers endeavored to create the best possible vacuum for use in this tube, but when it was broken it released no less than 370 quadrillion molecules of various gases, including some 5,000,000 molecules of Xenon, a gas so rare that only a few cubic centimeters of the pure gas are in existence.)

This official christening is seen in one of the accompanying pictures. Another shows a complete view of the new station.

The initial broadcast was put on in Proctor's Theatre at Schenectady, where Phil Spitalny's All-Girl orchestra played before a capacity crowd of 3500. Other features were short talks by FCC member George H. Payne, Charles E. Wilson, President of General Electric, Dr. W. R. G. Baker, manager of the company's radio and television department and chairman of the National Television Systems Committee, and

Dr. R. S. Peare, the company's manager of broadcasting.

In his talk, Mr. Wilson cited frequency modulation as "a new and great achievement." He said: "Unlike the conventional method of broadcasting, which just grew, the development of FM has been carefully

planned and controlled. During several years of experiment in competition with established methods, for many purposes, it has proved itself a superior means of sending radio programs into your home, as well as for many kinds of regular and emergency communication."

Mrs. James H. Burnham, daughter of Dr. and Mrs. Alexanderson, christens new FM station with "bottle of nothing", as parents and friend watch.



A view of the new FM station, christening of which is shown in the photograph above.



The program of music and talks was also broadcast from amplitude-modulated station WGY, and short-wave stations WGEA and WGEQ.

A standard General Electric FM transmitter is used for the new FM station, which covers an area within a radius of about 50 miles from the Helderberg antenna and including Schenectady, Albany and Troy, N. Y. As FM has the characteristics of television, in that the present-type wire lines will not carry the programs, a short-wave transmitter sends the signals from W2XOY's studio in Schenectady to the transmitting station in the Helderbergs.

A G-E three-bay turnstile antenna of new arrangement is being used for W2XOY. Providing a considerable signal gain over previously available similar designs, this antenna has been built to withstand one inch of ice and a hundred-mile-per-hour wind.

### RADIO GIVES CODE & SPANISH LESSONS

Radio code classes for all students wishing to learn or brush up on code are being conducted each Monday evening at 9:00 p.m., E.S.T., over world-wide short-wave Station WRUL on the frequencies 6.04 mc. (49.6 meters) and 11.73 mc. (25.6 meters).

The lessons are for beginners, to give them a firm foundation for the study of code as a hobby or profession. Later a period of instruction for those more advanced in code practice will be inaugurated by WRUL under the direction of W. W. Chamberlain.

Students of this class of the air, from Canada to Florida and Puerto Rico, may submit their lessons after each broadcast for correcting and suggestion for study. Papers are graded and returned to students.

Spanish lessons for radio listeners are also being conducted over world-wide short-wave Station WRUL in Boston on Friday evenings at 9:30 p.m., E.S.T., on the frequencies 6.04 mc. (49.6 meters) and 11.73 mc. (25.6 meters). The classes are repeated on Friday afternoons at 5:30 p.m., E.S.T., on the frequencies 11.79 mc. (25.4 meters) and 15.25 mc. (19.6 meters), to better reach audiences of students, teachers, parents, and those interested in languages as a hobby.

The course begins with simple grammar as a basal text for students who desire to read, speak and write Spanish with the least possible delay. The Inter-America Division will examine and correct all exercises submitted by listeners, and each month there will be a review period.

### FM SPEEDS USE OF RADIO IN ADULT EDUCATION

Cleveland's pioneer high-frequency educational radio broadcast station, WBOE, operated by the Cleveland Board of Education, has been authorized by the F.C.C. to change its type of transmission from amplitude to frequency modulation.

First station to operate in the ultra-short wave band set aside for educational stations in 1938, WBOE has been broadcasting from its own studios to receivers in each of Cleveland's 151 schools since November, 1938.

Now, as commercial FM broadcasting gets under way and high-frequency FM sets become available to the public, WBOE's programs may find listeners in homes as well as in classrooms.

Due to the British blockade, few items are received from continental Europe as mails from Nazi occupied areas seldom come through.

## Fluorescent Flag Glows at Night in "Black Light"

The American flag, glowing with all the intensity of democracy's spirit, shines in a darkened room when treated with certain chemicals. In daylight these flags, made by Dr. J. W. Marden, Assistant Director of Research, Westinghouse Lamp Laboratories, and Dr. N. C. Besse, assistant, appear to be plain white cloth; each, however, has been given a coating of fluorescent materials in the pattern of the flag. Two such flags have been made and a pair of ultra-violet lights is used to illuminate them. Different compounds have been used on each of the flags; one responds to one of the ultra-violet projectors and the other to the second projector, but each is unaffected save by its own projector.

Ultra-violet has many wavelengths from

short to long, like the familiar color spectrum. Organic and inorganic fluorescent materials, of which there are literally hundreds in the world, are activated by many different wavelengths according to their own peculiar characteristics. One "note" of the ultra-violet scale may cause a certain phosphor to fluoresce but fail completely to affect another. The object of research has been to discover the proper wavelengths for activating a great number of different fluorescent compounds.

One flag is a "short-wave" banner which takes on its proper colors only when within reach of short-wave ultra-violet radiations. The staff is coated with zinc silicate and the knob on top with zinc beryllium silicate. The staff becomes green and the knob yellow

white when fluorescing. The red stripes are cadmium borate; the blue field, calcium tungstate; the white stars and bars, magnesium tungstate. The second flag is of a "long-wave" variety and composed of entirely different fluorescent compounds.


The ultra-violet source is a specially designed water-cooled lamp, called a "hydrogen-discharge" lamp. This lamp is necessary because it gives a nearly continuous spectrum in the portion of ultra-violet investigated.

To make photographic records of this phenomenon, fluorescent powders are spread on a clear gelatin film mounted in front of an ordinary panchromatic plate. A yellow, photographic K2 filter is then inserted between the powders and the photographic plate to halt all but visible light.

When the lamp is turned on, ultra-violet radiations cause the fluorescent powders to become alive with light at the point where the ultra-violet would normally hit the photo negative, thereby recording in black and white, their response to the various wavelengths of ultra-violet. Thus the negative is darkened by only the visible fluorescence of the compounds and permanent records made.
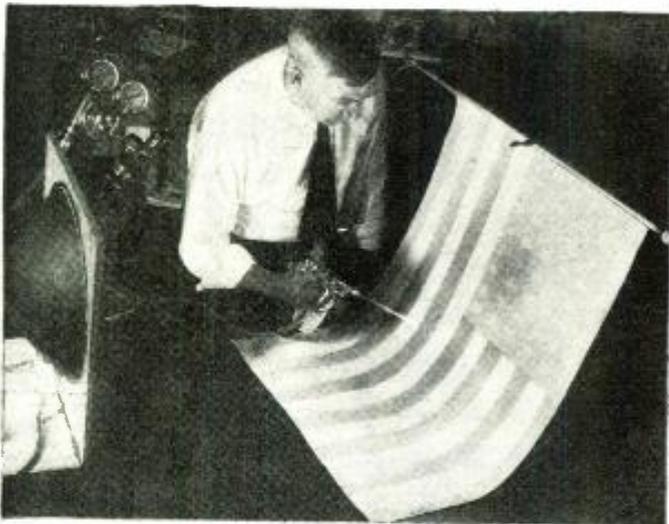
### NAVY "NET" NEEDS MEN

In an exclusive story the *New York Times* reports that the office of Naval Communications in the Navy Department is seeking the co-operation of Hams throughout the U. S. to fill a shortage of about 5,000 men in the personnel of the Navy Communications Reserve. The readers of this magazine are urged to co-operate.



Technician sprays cloth with fluorescent dyes to make it glow with flag's colors in "black light".

### BOAKE BACK

Boake Carter, famous newscaster whose voice has been missing from the ether waves for two years, is now heard thrice



weekly over the WOR-Mutual Network. There was considerable talk in which it was alleged that Carter was "suppressed" when he left the air in 1938. His return should terminate such ugly rumors. One of the most popular commentators, Carter's return proved welcome to listeners.

### SCHOOLS GET U.H.F. BAND FOR EDUCATION

When the Federal Communications Commission approved FM in May, 1940, and recommended it for all ultra-short wave broadcasting, because of its qualities of more faithful sound reproduction and absence of static and interference from other stations, it cleared a range in the high frequencies from 43 to 50 megacycles for commercial broadcasting.

At the suggestion of U. S. Commissioner of Education John W. Studebaker, representing more than 300 universities and colleges and hundreds of school systems and other educational organizations, the F.C.C. moved the educational band to an adjoining position at 42-43 megacycles.

In explaining educational radio's request for a position tangent to the commercial band, Commissioner Studebaker pointed out that FM commercial broadcasting would lead to large scale retail distribution of FM receivers capable of tuning in programs from educational studios.

Cleveland's school board is one of several preparing to enter this new phase of education by radio. San Francisco's Board of Education has received a construction permit for its proposed FM station, KALW, San Mateo (Calif.) Junior College and school systems of Chicago and New York have indicated they will file applications soon. New York's school system, like Cleveland, has been operating a high-frequency

AM station, WNYE, which it expects to change to FM.

Another New York educational institution, the College of the City of New York, has expressed an interest in an educational station. The University of Kentucky operates WBKY, an AM high-frequency station which broadcasts educational programs to schools and community listening centers in rural Kentucky areas, Oklahoma A. and M. is considering establishing a similar service.

Rensselaer Polytechnic Institute is reported to be building an FM station, the Universities of Illinois and Wyoming, and New River State College, Montgomery, W. Va., are collecting equipment, and an alumnus has offered the University of Michigan equipment for an FM station. Nearly a score more educational institutions and school systems are developing plans for stations in the educational band.

WBOE's new frequency allocation is 42.5 megacycles and its power has been doubled to 1000 watts.

### THEATRE TELEVISION COMING

According to apparently well founded rumors, the National Broadcasting Co. is equipping a midtown New York theatre to receive large screen television images. Reports are that the images will be about 12 x 16 feet.

### PHOTO-ELECTRIC PHONOGRAPH RECORDS FOLK SONGS

A newly invented phonograph pick-up, created by Philco Corporation engineers and designed along the same basic engineering principles as applied in its recently announced photo-electric radio phonograph, promises to open a new field in music research.

Students of folk music have made collecting trips into backwood regions. The inadequacies of noting down by ear and hand the melodies which they heard were so obvious that at the first advent of the Edison phonograph they adapted it to their purposes. As years passed and improvements were made in recording, the inadequacies of the early records in turn became obvious. The cylinders, which had been recorded on machines somewhat resembling a modern Dictaphone, became more brittle and fragile with age, and since the precious material they contained could only be brought to life again by pressing a hard diamond or heavy steel point into their grooves, they had to be guarded with great care and only played infrequently for special problems of research.

Since these cylinders contained the only authentic record of the folk music of the last generations, it became of paramount importance to find some means of transcribing it onto newer and more durable discs.

The photo-electric phonograph pick-up recently announced by the Philco Corporation seemed to offer the most promise and therefore the engineers of the Library of Congress Phono-duplication Laboratory brought their problems to the attention of David Grimes, Chief Engineer of Philco Corporation, who offered to attempt to design a new light-weight reproducer suitable for work with the old cylinders. After about two months of intensive research, E. O. Thompson, Philco Corporation engineer, working with Jerome B. Wiesner, Chief Engineer of phono-duplication for the Library, produced a machine which gives every promise of being satisfactory. Now installed in the Library of Congress, it has successfully performed every test assigned it thus far.

This will mean that the American public

shortly will be able to hear thousands of old American folk songs, Indian songs and voices of personalities long deceased. In addition, it is expected that composers and lyricists will edit many of the old musical renditions and create new American music which will be based upon long forgotten melodies.

By use of a slightly different application of the principle of the pick-up arm of the new photo-electric phonograph, these old cylinders are being transferred onto flat disk records, so that they may be played without fear of damage to the sound grooves.

Thousands of these records, which for years have remained in dusty cases because of the danger of scratching away the valuable words and music, can now be made available to research students.

Basic reason for the better results of this experiment is the very slight 5 gram downward pressure of the sapphire stylus in comparison to the approximate 25 gram pressure on the original reproducer stylus.

The sapphire stylus need only float gently in the grooves to produce the necessary motion; as a result the delicate impressions in the wax cylinder are not gouged out and destroyed.


The photo-electric pick-up has been placed on a standard cylinder machine replacing the original pick-up. The photo-electric pick-up is connected in turn by wires to the recording unit. The sound from the wax cylinder is transcribed from the cylinder through the recorder onto a flat disc type record from which any number of additional impressions can be made.

Recently, the first extensive job of transcription was started. Percy Grainger, the renowned pianist and composer, arrived at the Library with over two hundred cylinders, recorded in all parts of the world. The Division of Music in the Library of Congress anticipates that this will be followed by the transcription, not only of the records already in the Archives, but also of other important private collections, and that the wealth of material thus obtained can eventually be made available in useful and durable form to every interested scholar.
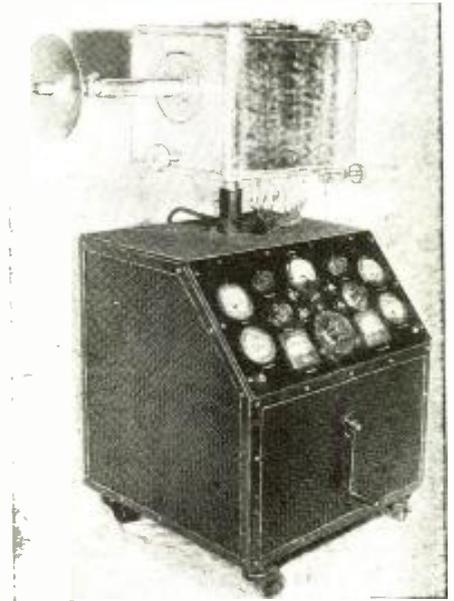
### CENTIMETER WAVE SIGNAL GENERATOR FOR 3000-4000 MC.

A signal generator designed for laboratory research involving the study and development of new radio equipment to operate in the 3000 to 4000 mc. portion of the radio spectrum generates test signals of adjustable intensity and frequency. As it operates at unusually high frequencies, its design is somewhat unconventional.

The oscillator is an end-plate magnetron tube, having a maximum output of about 1 watt in the frequency region of 3000 mc.



(9 cms. wavelength; 1 cm. = 0.4 inch). However, in the signal generator, outputs of 0.01 watt are ample for most tests. The oscillator feeds an antenna from which the generated signal is radiated. Control over the signal strength is obtained by means of an attenuator, and a specially designed thermocouple is used to indicate the output.

At these very high frequencies, which are in the quasi-optical range, difficult problems are encountered in shielding, lead filtering, and also in modulation. The signal generator incorporates new methods of overcoming these difficulties. (Photo courtesy of RC.I)

### 13TH ANNUAL SCIENCE AND ENGINEERING FAIR

Open to all junior and senior high school students who have outstanding experiments or demonstrations to exhibit, the 13th Annual Science and Engineering Fair is an ideal place to show what has been accomplished in the construction phase of club and classroom work in science. All exhibits at the Fair must be the actual creation of student participants. Cash prizes amounting to \$3,000 will be awarded for the best displays. Although the Fair, which is a continuation of the American Institute's annual industrial fairs which began in 1828,

is held in New York City, schools from every part of the United States are represented. Last year over 27,000 people visited the Fair to view 326 exhibits representing working models, experiments, live animals and plants, and technical and mechanical projects. Entries are due March 15, 1941.

All interested students are invited to write to the American Institute Science and Engineering Clubs, 60 East 42nd Street, New York City, for complete information regarding these activities and the general club program.

### FM FOR NASHVILLE POLICE

After operating an amplitude modulated emergency communications system for five years, the city of Nashville, Tenn., has ordered a complete FM system from the General Electric Company.

The system for Nashville will include 1 250-watt and 24 25-watt transmitters, and

30 receivers. A 200-foot tower, to be constructed, will support a half-wave antenna of new design that provides complete lightning protection.

Nashville is the first Southern city to adopt frequency modulation for police communication.

### BROADCASTS TO AMERICA

Philip Noel Baker, M.P., is seen below giving one of the "Britain Speaks" talks which he broadcasts in the BBC's North American service.

A very large number of letters from



overseas listeners arrive daily and each one receives an individual reply. Letters from listeners are welcomed by the BBC, for careful analysis.



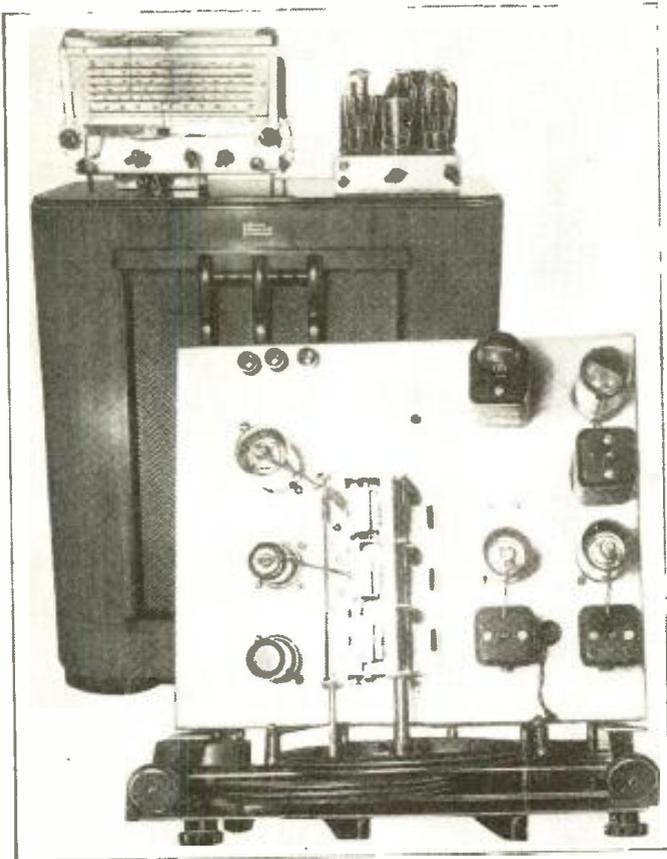
# High-Fidelity All-Wave Tuner



Herman Yellin, W2AJL

As the author points out—those who have listened to F-M broadcasts have suddenly become "fidelity-conscious" listeners. To provide a better equipped tuner for the ordinary broadcast, so that high quality reproduction could be obtained (in connection with the F-M audio amplifier previously described), the author built the tuner here described. A ready-built 5-band coil-switching unit was employed, which simplifies the construction immensely.



The picture above shows the all-wave tuner on top of the Jensen high-fidelity loudspeaker, and the small inset picture shows a top view of the all-wave tuner.

● THE rapidly increasing number of F-M broadcasting stations has increased the number of *fidelity-conscious* listeners. After spending some time at an F-M receiver, the average listener becomes increasingly critical of ordinary A-M broadcasts, resulting in a desire for a broadcast receiver that would reproduce the program with as great a fidelity as possible. While the TRF (tuned radio frequency) type of receiver has often been used for high-fidelity reception, it has a serious drawback in its unsuitability as an effective *all-wave* receiver. With proper design, however, a superhet can deliver a good signal and faithfully reproduce the output of the occasional high-fidelity broadcaster.

It was for these reasons that the writer built an all-wave high-fidelity tuner, capable of being used with the same audio amplifier-speaker system used with his F-M tuner, and able to deliver signals not too inferior in quality when compared with the F-M signals.

#### Ready-Made Coil-Switching Unit Used

In order to simplify construction, a ready-made 5-band coil-switching unit was obtained. This unit tunes from 530 kc. to 32.4 mc. with a special 280 mmf. tuning condenser. Especially made for amateur receivers, which demand the ultimate in tuning ease in the highly crowded Ham bands, the 3-gang condenser has a small rotary trimmer section in parallel with each large condenser section. This really gives us two tuning condensers in one, one for ordinary tuning and the other smaller section, for *band-spread* tuning. This *band-spread* feature is highly effective and a necessity not

only on the Ham bands, but on the foreign *broadcast* bands, where it provides that ease of tuning so sadly missing on the average "all-wave" radio. If the band-spread feature is not desired, an ordinary 3-gang, 280 mmf. condenser can be used, in which case the special band-spread dial with two knobs will not be necessary. Also, if desired, the coil unit can be procured with a different tuning range—42 mc. to 132 kc.—which includes many *long wave* services. A 3-gang 410 mmf. condenser will be needed with this latter coil unit. Either combination of coil switching unit and condenser gang can be used in this tuner, but be sure to get the correct dial since they have directly calibrated scales.

#### Tube Line-Up

Now to the tube line-up. The R.F. stage uses an 1853—well suited for operation on the higher frequency bands, while the detector-mixer employs a 6K8, used only for *mixing*, since a separate tube—a 6J7GT—is used as the high frequency oscillator. In the I.F. stages we have a pair of 6K7GT tubes, followed by a 6SQ7GT performing two functions. The two diodes are paralleled for use as the second detector, while the triode section is used as a beat-frequency oscillator. Note the use of the bantam type glass tubes: these have a metal base connected to the number one pin and a sleeve type of shield can be slipped over the glass envelope, affording effective shielding. The bantam tubes are in some respects superior to the metal type and bid fair to eventually supersede the metal type.

The output of the second detector is fed through a volume control into the output

jack on the back of the chassis, and thence to the external amplifier. No power-supply was built onto this tuner chassis, since the writer's amplifier furnishes sufficient power for this purpose. As the power-supply contained a regulated 105 volt supply, it is used not only for the high frequency oscillator but for the beat frequency oscillator, as well as the 6K8 screen. If a power-supply not having this regulated voltage is used, a 25 watt slider type voltage divider (15,000 ohms) can be connected across the 250 volt supply and adjusted to about 100 volts.

#### Fidelity on the "Broadcast" Band

Returning for the moment to the subject of *fidelity*, it must first of all be remembered that *broadcast* stations are assigned frequencies ten kilocycles apart, and since they have two side-bands, are limited to an audio band width of 5000 cycles. An exception is the case of broadcast stations just above 1500 kc. which are licensed for a greater band width. Although the former stations are not supposed to transmit audio frequencies higher than 5000 cycles, they do so, but the beat note between the higher frequencies of two adjacent channel stations is not heard because of the narrow band width of the ordinary tuner, which may cut off at much less than 5000 cycles. Increasing the band width to make these higher frequencies audible is desirable in those instances where the desired station is not flanked by adjacent channel stations within range of the receiver.

A happy solution to this problem of band width is the use of *variable* band width I.F. transformers. Using I.F. transformers having 3 degrees of band width, it is possible to

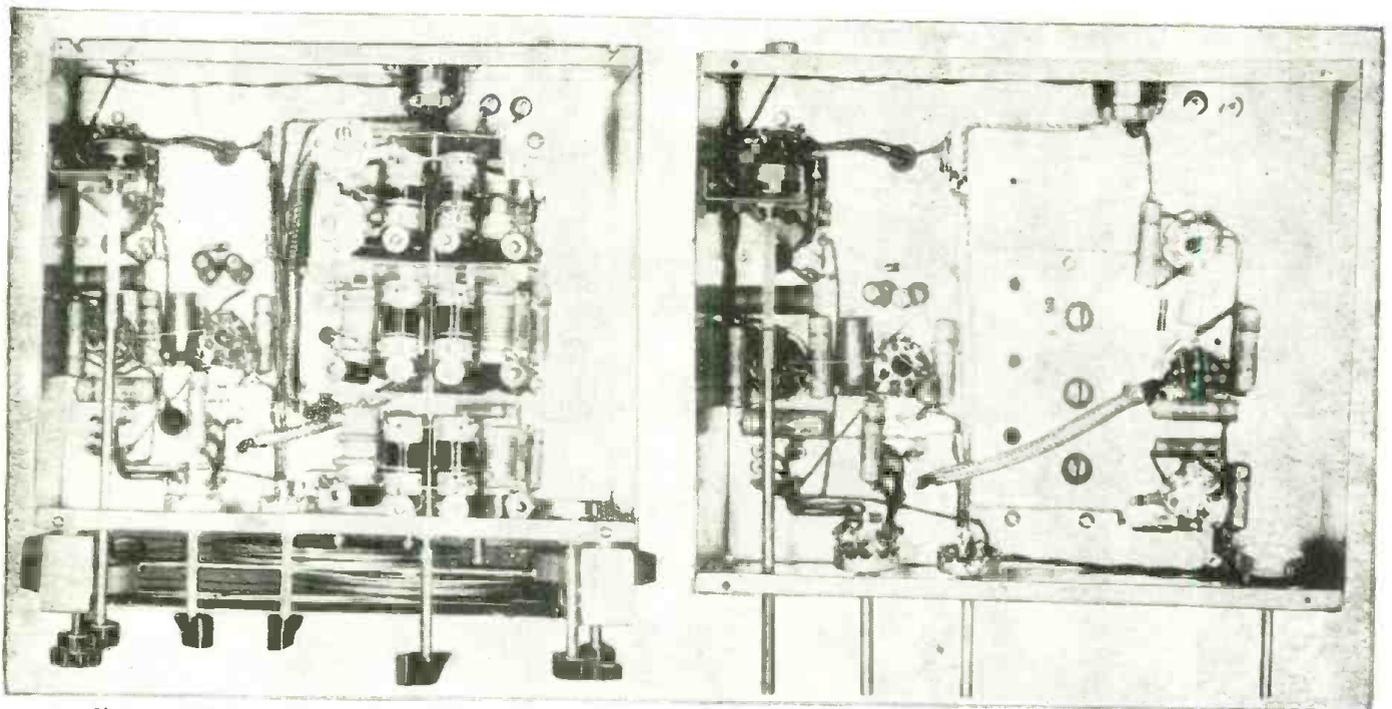


Photo at left shows all-wave tuner with switch coil unit in place. Photo at right—view of tuner before coil unit was installed.

vary the band width from the quite sharp position, desirable for tuning in the Ham bands or the crowded foreign broadcast bands, to the medium position suitable for ordinary work. The third position gives increased band width for listening to the high-fidelity stations, or some of the broadcast stations. It will be found that the high fidelity position of the I.F. band width switch cannot be used on many of the stations, especially on the high frequency end of the broadcast band because a high-pitched whistle will be heard caused by the hetero-

dying between that station and the station in the adjoining channel.


Beat-Frequency Oscillator

The beat-frequency oscillator was incorporated, since it didn't involve the use of an additional tube and more important, it is extremely helpful in locating those weak, distant short-wave stations. For receiving code (C.W.) signals, for which this tuner is eminently qualified, the BFO becomes a necessity. Coupling between the BFO and second detector diode plates is accomplished

by a 3-30 mmf. trimmer—adjusted on a weak signal for loudest beat note. A convenient knob atop the BFO transformer allows the beat note to be adjusted to the most pleasant tone.

The coil assembly requires the use of a chassis 4 inches deep, but as this was unobtainable except in a prohibitively large chassis, a chassis 3 inches deep and 12 x 10 inches wide was used. This resulted in the coil assembly protruding beneath the chassis, but four one inch brass spacers raise the chassis high enough so that the coils do

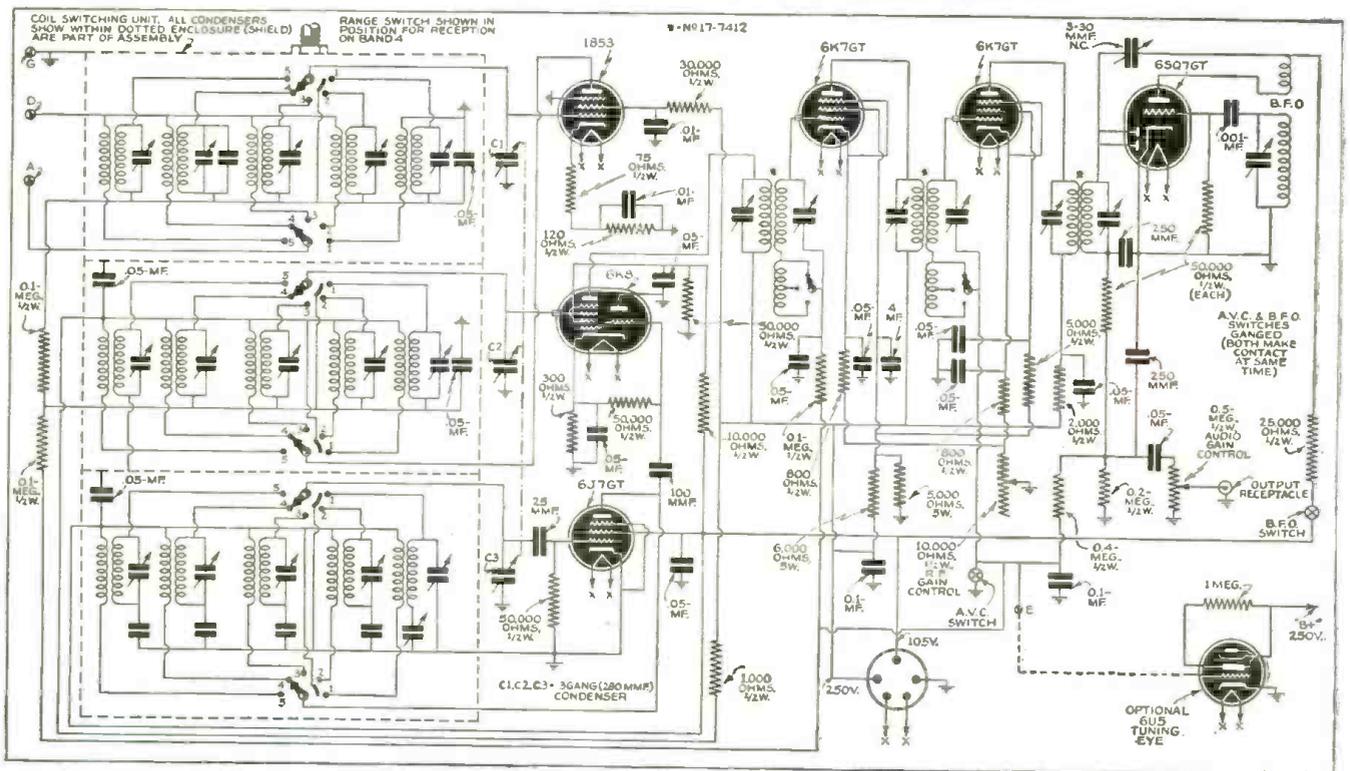Wiring diagram for the high-fidelity all-wave tuner unit here described by Mr. Yellin.



not touch the cabinet shelf. No ill effects were observed as a result of this abbreviated chassis and the unconventional appearance is not apparent when the chassis is mounted inside a cabinet.

## Assembly and Wiring

In mounting and wiring the components, the tuning condenser should be mounted directly above the coil assembly, with the "front end" tubes mounted close to the condenser gang, in the positions shown in the photos. This placement will result in the shortest R.F. leads, and also will place the coil assembly right over the three steatite sockets, necessitating the wiring of these sockets, before the coil assembly is mounted inside the chassis. As a matter of fact, it would be well to wire everything on the chassis and leave the coil assembly for the last, obviating the possibility of damaging any of the coils. If the band-spread dial is used, it will be necessary to support it by bolting it to the chassis.

The lead from the 6K8 plate to the first I.F. transformer is a little long, so it was shielded—not with ordinary shielding, but with the low-capacity type. The plate lead is covered with a piece of half-inch diameter spaghetti or sleeving, and over this is pushed some large shielding braid which is grounded to the chassis. The large diameter of the spaghetti keeps the shielding far enough away from the wire to keep the capacitance between wire and braid quite low. The same method of shielding is used over the antenna leads coming out of the antenna section of the band-switch assembly, which go to the antenna binding posts at the rear of the chassis.

The remainder of the wiring is quite straightforward, and should offer no difficulty since there is really very little of it. The audio volume control is mounted on a small bracket near the rear of the chassis with a brass shaft extension to the chassis front. The 2-pole, 3-position rotary switch used for selecting the I.F. band width is mounted next to the audio gain control and next to this is the AVC-BFO switch which turns off the A.V.C. when the BFO is turned on. At the extreme left of the chassis is the R.F. gain control.

## Alignment Procedure

Alignment should preferably be done with an all-wave signal generator. The I.F. transformers should first be peaked to 450 kc. with the band expansion switch in the sharp position. Either a magic-eye tube or an output meter may be used as an indicator for I.F. as well as R.F. alignment. The all-wave coil assembly is aligned at the factory, so that, if the coils and trimmers are not touched, signals will be heard even without aligning the front end. However, for best results, it is advisable to go over the trimmers. Start off with the lowest frequency band. The tuning condenser should be set at about ten per cent of its maximum capacity, and a signal fed into the receiver—corresponding to the frequency marked on the dial at that point—and the oscillator trimmer adjusted for maximum output as indicated on the indicator. Then adjust the antenna and R.F. (detector) trimmers for maximum output. The tuning condenser is then turned to about 80 per cent of its maximum capacity and a signal fed into the

receiver corresponding to the frequency shown on the dial, and the oscillator padder adjusted for maximum response. The condenser should then be turned back to the first alignment frequency and the antenna and R.F. trimmers rechecked for maximum response at that frequency. Don't retune the oscillator padder. This procedure is followed on each of the other bands. On the two highest frequency bands, however, there is no adjustable oscillator padder, as the coils have been adjusted at the factory for proper "tracking."

A good all-wave type of antenna, with twisted-pair feeders should be used for most effective results.

## Parts List

### BUD RADIO

1—3" x 12" x 10" chassis; No. 1195

### I.R.C.—(Resistors)

- 1—75 ohm ½ watt; type BT½
- 1—120 ohm
- 1—300 ohm
- 2—800 ohm
- 1—1000 ohm
- 1—2000 ohm
- 1—5000 ohm
- 1—10,000 ohm
- 1—25,000 ohm
- 1—50,000 ohm
- 4—50,000 ohm
- 2—100,000 ohm
- 1—200,000 ohm
- 1—400,000 ohm
- 1—5000 ohm 10 watts; type AB
- 1—6000 ohm 10 watts; type AB
- 1—500,000 ohms potentiometer; type 13-133
- 1—10,000 ohm pot. wire-wound; No. W-10,000

### NATIONAL UNION—(Tubes)

- 1—1853
- 1—6K8
- 1—617GT
- 2—6K7GT
- 1—6SQ7GT
- 1—6U5

### AMERICAN PHENOLIC—(Miscell.)

- 1—5-prong plug in flush motor shell (for power supply); No. 61-CP5
- 1—5-prong female plug; No. PF5-11
- 1—Chassis output connector; No. PC1M
- 1—Output plug; No. MC1F
- 1—6-prong plug (female); [for magic-eye tube]; No. PF6

### MEISSNER MFG. CO.—(Coils, I.F. Trans. & Sockets)

- 1—All-wave coil-switching assembly. (530 kc.-32.4 mc.); No. 13-7617
- 1—280 mmf. band-spread tuning condenser; No. 21-5143B
- 1—Electrical band-spread dial; No. 23-8211
- 2—456-ke. band expanding I.F. transformers; No. 17-7412
- 1—456 ke. I.F. transformer; No. 16-5711
- 3—Octal steatite sockets; No. 25-8437
- 3—Octal bakelite socket; No. 25-8209
- 1—3-30 mmf. trimmer; No. 22-5255

### CORNELL-DUBILIER—(Condensers)

- 2—.01 mf. 400 volt condensers; No. DT-4S1
- 4—.05 mf. 400 volt condensers; No. DT-4S5
- 2—.1 mf. 400 volt condensers; No. DT-4P1
- 2—.0001 mf. mica condensers; No. 5WL-5T1
- 2—.00025 mf. mica condensers; No. 5WL-5T25
- 1—.000025 mf. mica condenser; No. 5WL-5Q25
- 1—4 mf. 450 volt electrolytic; No. BR-445

## We Will Pay

regular space rates for good construction articles giving novel and original ideas for building such simple radio apparatus as short wave converters, receiving sets, television and frequency modulation receivers, recording equipment, power supplies, simple set and tube testers, facsimile recorders, etc.



DEALERS SERVICEMEN  
BUILDERS AMATEURS

All Agree!

"Here's the Big Book of  
**RADIO VALUES**"

**FREE**

GET IT NOW!  
212 PAGES!

EVERYTHING IN RADIO!



85 NEW  
Knight  
RADIOS

See them all—1941's Radio Hits! Models for every purpose—at every price. Plastic and wood mantel models; world-wide sets; "Personal" and 3-way Portables; Recorders and Phono-Radio Combinations; Auto Sets; Farm Radios; Amateur Receivers—all at new low prices! See them in this greatest of Radio Catalogs.



Save money on  
EVERYTHING IN RADIO

24 NEW SOUND SYSTEMS, complete P.A. systems; all new Amateur receivers and complete Ham gear selections; parts, tools, test equipment; parts, more than 17,000 quality radio items—you'll find Everything in Radio at Lowest Prices in 1941! ALLIED Catalog



RADIO BUILDERS!

BUILD YOUR OWN! Count on ALLIED for the latest low-cost kits and for help in building any type of radio circuit. ALLIED is headquarters for Radio Builders.

The "Radio Builders Handbook" — valuable beginners' book — easy to understand. Only 10c

New! "Radio Dictionary" compiled by experts, under ALLIED supervision. Gives meanings of all 40,000 commonly used radio terms and words. Only 10c

DON'T MISS THE BARGAIN SECTION!

**ALLIED RADIO**

833 W. Jackson Blvd., Dept. 3-B-1  
Chicago, Illinois


- Send me your FREE 1941 Radio Catalog.
- I enclose 10c for New Radio Dictionary.
- I enclose 10c for Radio Builders' Handbook.

Name .....

Address .....

City ..... State .....

FREE CATALOG

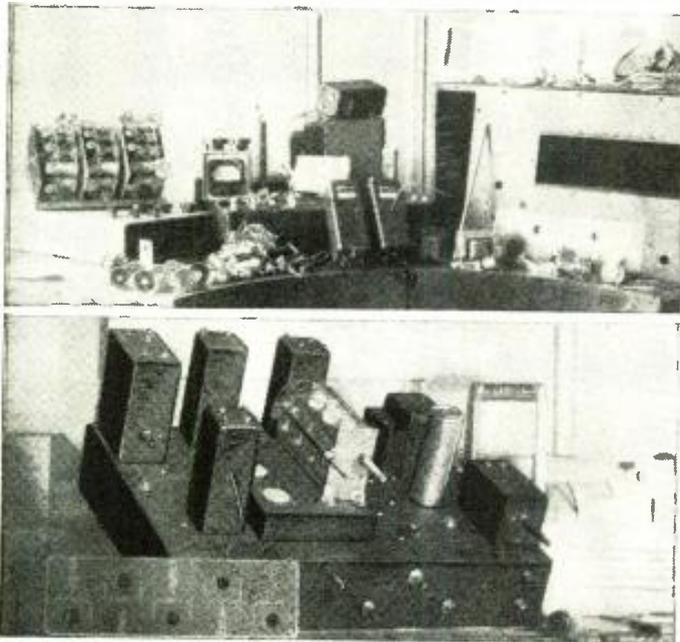

The three photos show respectively—completely finished Communications receiver (above); complete kit of parts (top left), and below—at left—the receiver partly assembled.

## A Low Cost, Highly Efficient Communications Receiver

Charles R. Leutz

The accompanying article describes a 14-tube de Luxe Communications receiver. The average set-builder and Ham will be interested in this set, because all of the delicate tuned sections are factory-wired and pre-aligned, thus insuring perfect results as soon as the set is assembled and wired. The set features tuned R.F. stage, noise silencer, crystal filter, variable pitch BFO, and a direct-reading "R" meter.

● EVERY amateur needs a first-class communications receiver, but with manufactured sets costing several hundred dollars each, a good many "hams" are financially stymied. Attempts to construct a good composite receiver are complicated and usually unsuccessful due to the lack of test apparatus for the final lining-up operations.

A solution for the above problem is the Meissner 14-tube "Traffic Master" Communications Receiver which is available in kit form. The kit includes a complete tuning unit which is factory wired and pre-aligned, which simplifies matters considerably. The intermediate R-F transformers are also factory peaked. The entire kit, tubes and a good speaker can be purchased for a surprisingly nominal amount.

Fig. 1 shows the complete kit parts laid out ready for assembly. Not including the miscellaneous hardware, there are 166 different parts including the 14 tubes and speaker. Fig. 2 shows the assembly of the kit parts up to the point of chassis completion. The completed receiver, ready for operation, is shown in Fig. 3. The complete schematic wiring diagram is given in Fig. 4 and Fig. 5 shows the wiring of the factory pre-aligned five band tuning unit. Detailed information on this tuning unit appeared in the July 1940 issue of RADIO & TELEVISION in an article by the author, entitled "How to Extend the Tuning Range of Your Receiver."

### Design Features of the Set

This communications receiver has the following essential design features:

1. A direct tuned R-F stage to insure favorable image ratio, using a modern tube especially efficient on the higher frequencies, in this case the 1853 "television" tube.

2. "Iron core" Ferrocart Intermediate R-F transformers with air dielectric trimmers.

3. An efficient "Lamb" noise silencer circuit to reduce ignition and similar abrupt electrical disturbances.

4. A Crystal-Filter and crystal-phasing condenser to regulate the obtainable degree of selectivity.

5. A variable-pitch Beat-Frequency Oscillator, free from frequency drift.

6. Stable operation insured by using a Voltage Regulator tube to feed the plate and screen-grid circuits of the oscillator tube, and the plate circuit of the beat frequency oscillator tube.

7. A direct reading "R" Meter.

8. Full frequency coverage from 530 kilocycles to 31 megacycles in five bands, with a liberal over-lap between bands.

9. A band-spread tuning condenser.

10. A separate oscillator tube, efficient over the entire frequency coverage, used in connection with a good mixer tube, in this combination—a 6J7 oscillator and 6K8 mixer.

While this kit is ordinarily used com-

plete, any individual parts or combination of parts may be secured separately. The builder therefore has considerable latitude and can utilize good parts which may be on hand. Or, individual parts such as the Crystal-Filter Assembly, Beat-Frequency Oscillator Assembly or Noise Limiter Circuit parts may be secured and added to existing receivers. This 14-tube receiver design represents the result of considerable qualified development and research work and variations are not suggested unless for some good technical reason.

The tube array is as follows:

1. Pre-aligned tuning unit, 1853 R-F amplifier, 6K8 mixer and 6J7G oscillator
2. Intermediate R-F amplifier, 6L7 first IRF, 6K7 second IRF and 6H6 full-wave detector.
3. Lamb circuit, 6J7 and 6H6.
4. Audio, 6C8G inverter and two 6V6 or 6V6G's in push-pull, class AB.
5. Power-supply, 5V4G full-wave rectifier and VR-150-30 voltage regulator.

### Construction Procedure

Construction of this multiple tube receiver is relatively simple. The kit is accompanied by a large pictorial wiring diagram showing all the various component parts, their location and their connections. A corresponding schematic wiring diagram is available for a check-up. The chassis and front

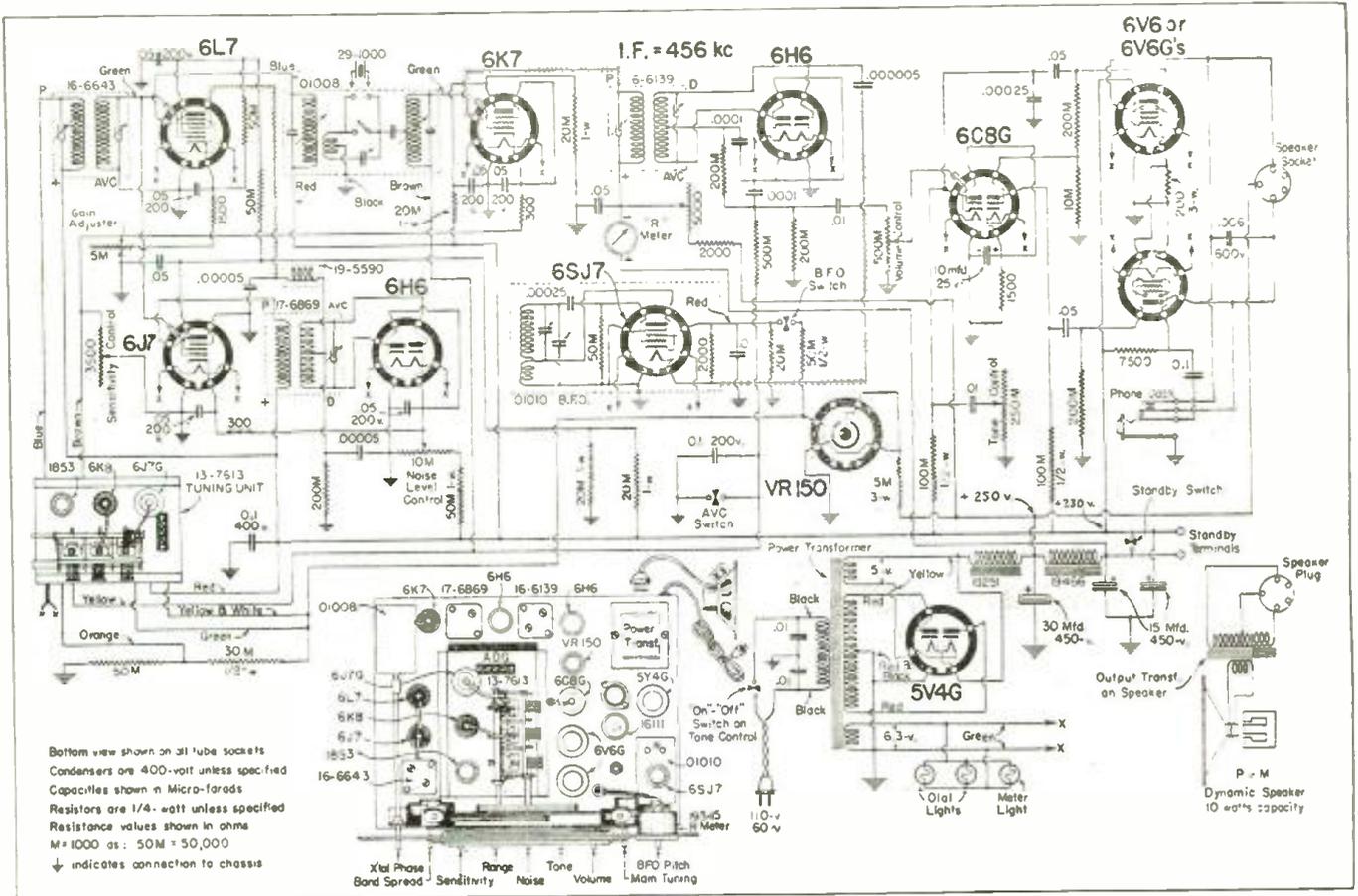


Fig. 3. Schematic wiring diagram for the 14-tube Communications receiver.

panel are drilled and all parts are ready for assembly. The assembled and wired tuning unit is the last item added to the chassis.

The construction is started by mounting the sockets into their chassis position, making sure the "key" points in the proper direction in each case. The heavy parts can then be fastened into place, including the Power Transformer, Filter Condensers, IRF Transformers, Crystal-Filter Unit and the Beat-Frequency Oscillator assembly. After wiring the 5V4G socket, and connecting all the Power Transformer leads, the two power-supply filter-chokes can be mounted and connected.

After completing the filament wiring, the smaller components can be inserted and connected, including the speaker socket, R-F choke, tie lugs, fixed resistors, fixed condensers, variable resistors and the two adjustable resistors.

The toggle switches and phone jack are assembled after adding the front panel, the latter being held to the chassis with spacers and holding screws.

It is not necessary to follow any rigid procedure during wiring; however, it simplifies matters by first connecting the various leads which extend from component parts, for example the leads from the Power Transformer, IRF Transformers, Crystal-Filter, Beat Oscillator, etc. The necessary other long leads can then be connected, including the filament wiring. Then only the connections for the various resistors and condensers remain and these can be made in a very neat manner.

As each connection is made, it should be checked off on the pictorial wiring diagram,

using a colored pencil. Following that procedure carefully, it is almost impossible to make a mistake or omit any of the connections. During wiring care should be taken to make sure no bare leads are accidentally grounded, also that no small bits of solder or wire fall into positions which will cause grounds or short-circuits.

After completing the chassis wiring, the tuning unit assembly can be inserted. There are nine connections from the tuning unit which are now connected to the chassis. These leads are coded and readily identified.


The variable condensers in the tuning unit are set to the fully meshed position and then the dials can be lined up. The main tuning dial pointer is fastened at the extreme low frequency end of the calibration. The band-spread dial is set at zero and fastened.

Mounting the front panel, "R" meter and dial lights completes the assembly.

### Check with Pictorial Diagram

The pictorial wiring diagram, which has been marked off in colored pencil, to indi-

Fig. 5. Coil and switch assembly diagram.

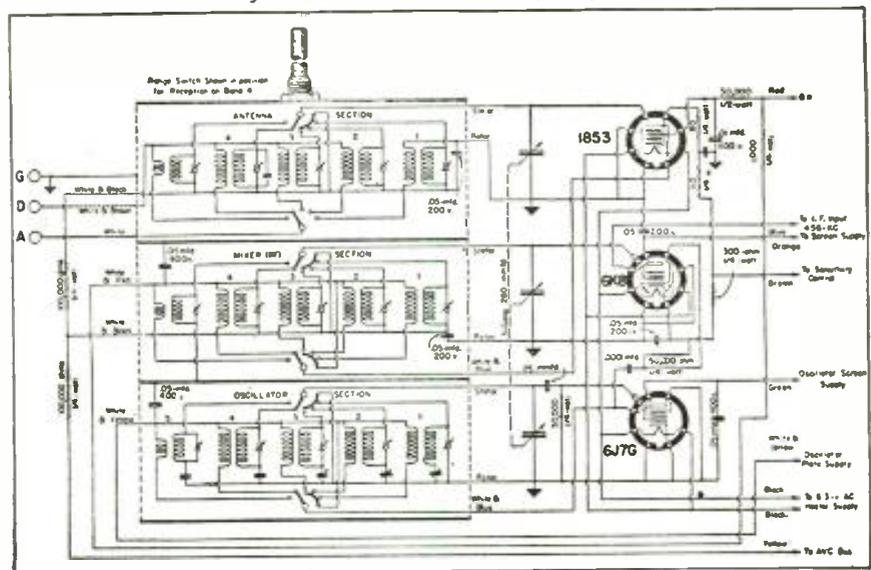

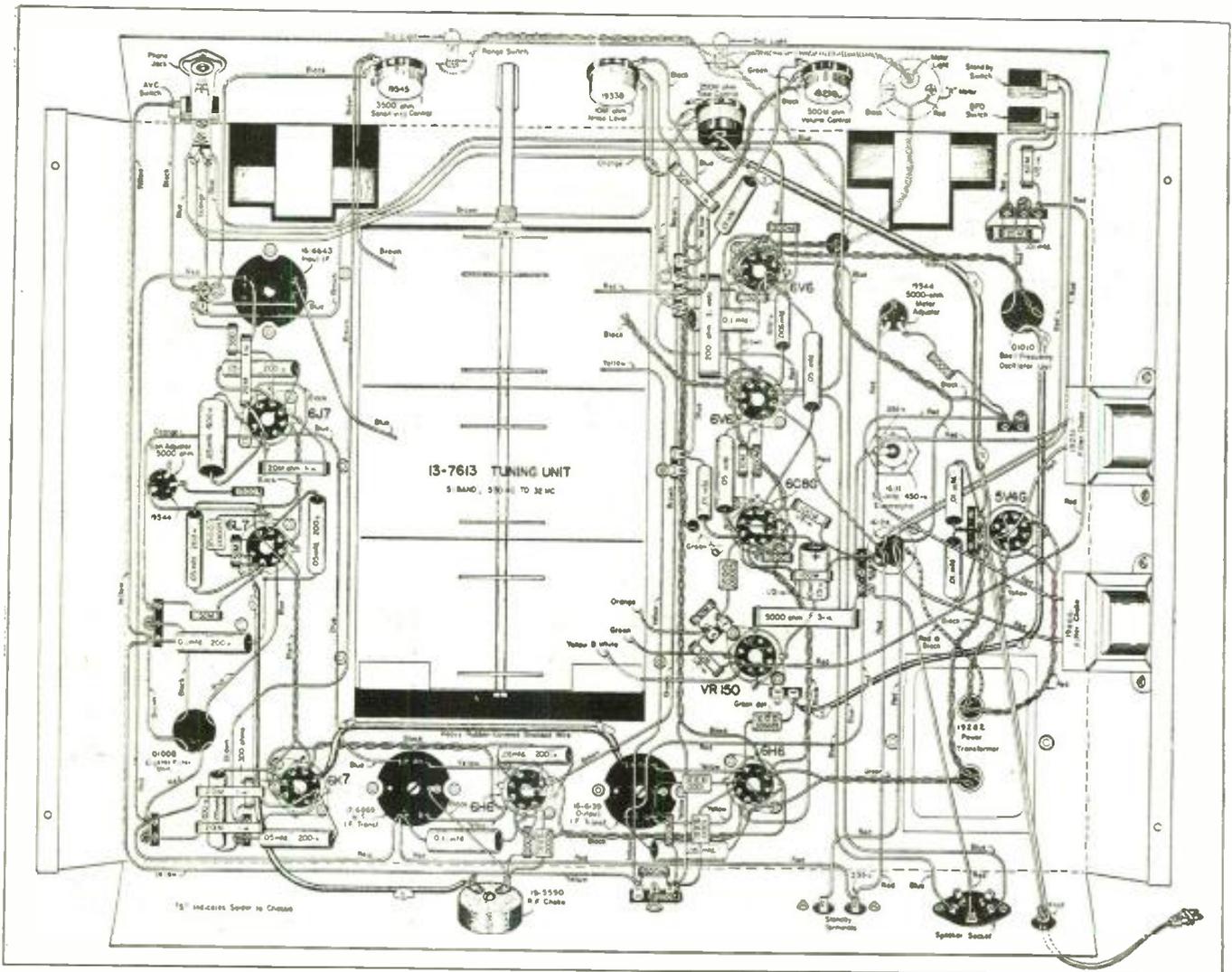


Fig. 6. Pictorial wiring diagram for the 14-tube Communications receiver.

cate wiring progress, should now be examined to determine if any wires have been omitted.

A preliminary voltage test should be made at all sockets, after inserting the tubes and connecting the speaker to the chassis. At the output of the first filter choke a voltage of approximately 250 should be obtained. At the output of the second filter choke the voltage should be about 250. Each tube plate and screen grid can be checked for proper normal voltage, taking into consideration some of the circuits are transformer-coupled and some resistance-coupled.

After checking voltages, the receiver can be given an "air" test. Provided instructions have been followed carefully and none of the factory adjustments altered, satisfactory performance can be expected without further alignment. However, if satisfactory results are lacking, the alignment should be checked in accordance with the instruction book.

For a reasonable fee, a qualified radio technician with a good service oscillator can be called in to check over the entire receiver, in which case top-notch performance can be expected.

Excluding miscellaneous hardware, the complete list of parts making up the receiver are as follows:

\*All parts, unless marked otherwise, supplied by Meissner.

### List of Parts—Communications Receiver\*

- 1—Tuning unit, wired and pre-aligned, No. 137613
- 1—Calibrated dial and escutcheon, No. 23-8229
- 1—Punched chassis, No. 11-8223-A
- 1—"R" meter and light assembly, No. 9119
- 1—Complete crystal filter unit, No. 01008
- 1—Complete beat frequency oscillator unit, No. 01010
- 1—Input I.F. transformer, No. 16-6643
- 1—Output I.F. transformer, No. 16-6139
- 1—Noise-silencer I.F. transformer, No. 17-6869
- 1—Power transformer, No. 1928E
- 1—Filter choke, No. 19251
- 1—Filter choke, No. 19466
- 1—30 mf., 450 v. electrolytic condenser, No. 16111
- 1—15-15 mf., 450 v. electrolytic condenser, No. 16124

- 1—R.F. choke, No. 19-5590
- 10—Moulded octal sockets
- 1—5-prong wafer speaker socket
- 1—250,000 ohm tone control, with switch, No. 19287
- 1—500,000 ohm volume control, No. 19258
- 1—10,000 ohm noise-level control, No. 19338
- 1—3,500 ohm sensitivity control, No. 19545
- 2—5,000 ohm midget adjusters, No. 19544
- 3—Toggle switches, S.P.S.T., No. 19354
- 1—Phone jack, circuit-closing, No. 19360
- 1—10 mf., 25 v. electrolytic condenser
- 2—.1 mf., 400 volt and 1—.1 mf., 200 volt paper condensers
- 4—.05 mf., 400 volt, and 6—.05 mf., 200 volt paper condensers
- 5—.01 400 volt paper condensers
- 1—.006 mf., 600 volt paper condenser
- 1—.00025, 2—.0001, 2—.00005 and 1—.000005 mi. mica condensers
- 1—200 ohm, 3 watt fixed resistor
- 1—5000 ohm, 3 watt fixed resistor
- 1—50,000 and 4—20,000 ohm, 1 watt fixed resistors
- 2—300 ohm, 2—1500 ohm, 1—2000 ohm, 1—7500 ohm, 1—10,000 ohm, 1—20,000 ohm, 3—50,000 ohm, 5—200,000 ohm and 1—500,000 ohm 1/4 watt resistors
- 1—30,000 ohm, 1—50,000 ohm and 2—100,000 ohm, 1/2 watt resistors
- 7—Single insulating tie lugs, 5 double and 1 triple insulating tie lugs
- 1—A.C. cord plug
- 1—Steel cabinet, No. 11-8224, and panel, No. 11-8219
- 1—Set of miscellaneous hardware

### RCA (Tubes)

- 1—1853
- 1—6K8
- 1—6J7G
- 1—6L7
- 1—6J7
- 1—6K7
- 2—6H6
- 1—6SJ7
- 1—6C8G
- 1—VR150
- 1—5V4G
- 2—6V6 or 6V6G

### UTAH (Speaker)




- 1—10" P-M dynamic speaker, 8 watt or more with output transformer for push pull 6V6's in class AB (primary impedance 10,000 ohms)

## HAMS!!

**Don't miss the new series of articles starting in this issue on**

## PULL-SWING "F-M"

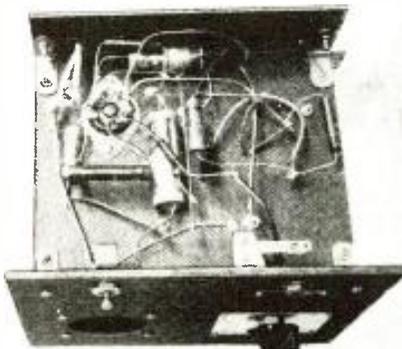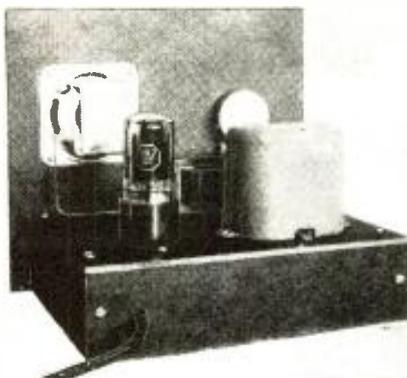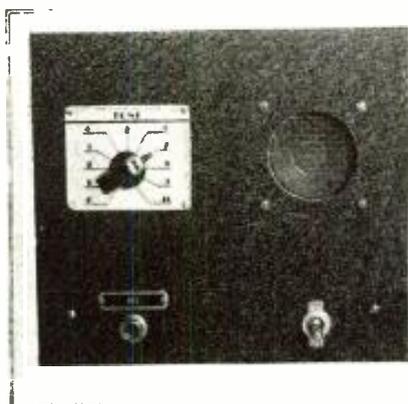**Data on simple Ham Transmitter and Receiver construction will follow.**



The photos in the accompanying group show the code oscillator from various angles; picture above shows front view; upper right photo shows rear view, and lower right photo—bottom view of the oscillator.

## A Code-Practice Oscillator

William D. Hayes, W6MNU

● WITH the increasing emphasis that is being placed on national defense and the need for capable code operators, there is a certain simple piece of equipment which should increase in popularity. The instrument referred to is the *code practice oscillator*. Many old timers may feel that such an instrument is beneath their dignity and that it is intended only for beginners who are struggling with the job of distinguishing "Y" from "Q." However, such is not the case. While it is true that an audio oscillator is valuable to the beginner, there is no reason to believe that it would be any less beneficial to the *self-styled* "speed-demon" who submerges his letters, and especially his numerals, in a sea of dots! As a matter of fact a certain "W5" was received at this station recently who was using *eight dots* on every "5"!

This is probably something of a record, but the operator who puts six dots on a "5" and five dots on a "6" is by no means rare! If these dot dispensers would spend a few minutes each day in keying an audio oscillator and listening critically to their own sending, there might be some improvements made. As it is now, the operator who is trying to receive one of these "dotty" stations feels like Old Mother Hubbard and her children who lived in a shoe—he has so many dots he doesn't know what to do.

Of course there are many other faults besides excessive dottiness such as *running letters together; improper proportioning of the length of the dot with the length of the*

*dash, etc.* However, we all know what the pitfalls are; the difficulty comes in determining which ones we are falling into. And that's where the code practice oscillator comes in!

The output of the oscillator described in this article is sufficient to permit the sending of practice material to a group of a dozen or so persons if desired, and the pitch of the note is *continuously variable* from zero up to about 1500 cycles per second.

### Circuit

Since there is no need for high voltage in a unit of this kind, and since, as always, it is desirable to keep costs down, a half-wave rectifier circuit was chosen for the power supply. This eliminates the necessity for a power transformer, and also permits the oscillator to be operated on either A.C. or D.C. lines.

Only one tube is used, a type 70L7GT, which does *double duty* by serving as half-wave rectifier and oscillator tube combined. Since this tube requires a heater current of only 150 ma., the power drawn from the line when the unit is operating is only about 18 watts. Another advantage of the low heater current is that a small 10-watt resistor is adequate for furnishing the necessary voltage drop in the heater circuit. In wiring the heater circuit of the 70L7GT, the No. 2 pin should be connected to "B" negative, and the No. 7 pin to the 300 ohm dropping resistor. Needless to say, "B" negative should not be grounded.

## Use Meissner



**PRECISION-BUILT PRODUCTS FOR PERFECT PERFORMANCE**  
*Progressively Engineered*  
**FOR THE EXPERIMENTER**

Complete Receiver Kits  
"Essential" Kits for Receivers  
F-M Parts and Receivers  
Television Receiver Kits  
All-Wave Tuning Assemblies  
Antenna, R-F and Oscillator Coils  
Wireless Phono Oscillator Unit  
I-F Transformers of all kinds  
Tuning Condensers, Dials, Switches

### FOR THE SERVICEMAN

New ANALYST  
Wave Traps  
Audio Filter  
Replacement Antenna, R-F and Oscillator Coils  
Replacement I-F Transformers  
Exact Duplicate Replacement Coils  
I-F Transformer Replacement Guide  
Coil Repair and Rewinding Service

### FOR THE AMATEUR

SIGNAL SHIFTER  
SIGNAL SPOTTER  
TRAFFIC-MASTER  
TRAFFIC SCOUT  
MC 28-56 Converter  
R-F Relays

SIGNAL CALIBRATOR  
Line Filter  
Primary Windings  
Replacement Antenna, R-F and Oscillator Coils  
UNI-SIGNAL SELECTOR  
Antenna Relay  
Insulators

### FOR THE SOUND ENGINEER


High-Fidelity P-A Tuner  
"Utility" TRF P-A Tuner  
Dual-Band Super P-A Tuner  
Specially Designed Assemblies  
Custom Engineered Equipment  
Portable Phono-Recorder Unit

### WRITE FOR FREE CATALOG NOW!

Brand new Meissner General Catalog for 1941—now being mailed. A postal card will bring you this valuable guide to dependable Precision-Built parts and equipment. You can't afford to be without it so mail your request TODAY!

Dept. RT-2



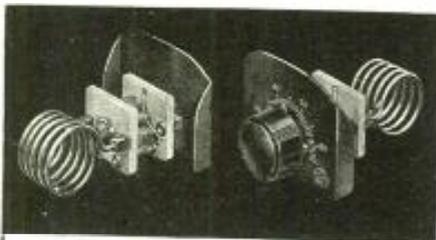

## MIDGET FREQUENCY METERS

Many amateurs and experimenters do not realize that one of the most useful "tools" of the commercial transmitter designer is a series of very small absorption type frequency meters. These handy instruments can be poked into small shield compartments, coil cans, corners of chassis, etc., to check harmonics; parasitics; oscillator-doubler, etc., tank tuning; and a host of other such applications. Quickly enables the design engineer to find out what is really "going on" in a circuit. Sold in sets of 4 in handy protective case or individually.

90605	Range 2.8 to 9.7 mc.	\$1.65
90606	Range 9.0 to 28 mc.	1.65
90607	Range 26 to 65 mc.	1.65
90608	Range 50 to 140 mc.	1.65
90600	Complete set of four, in case	6.50

**JAMES MILLEN MFG. CO. INC.**  
150 EXCHANGE ST. MALDEN, MASS.

## Get the Complete Antenna Story



Steel, Aluminum, Monel Antennas, Marine Antennas, Police Antennas—they're all shown with mountings in the NEW PREMAX CATALOG NO. R-49. Send for it today.

### Premax Products

Div. Chisholm-Ryder Co., Inc.  
4149 Highland Av., NIAGARA FALLS, N. Y.

## CODE PRACTICE OSCILLATORS



Ideal for Class-room or individual practice

New BUD Code Practice Oscillators operate up to 20 pairs of earphones. Any number of keys may be used.

Write for descriptive literature giving complete details.



**BUD RADIO, INC.**  
CLEVELAND, OHIO

A resistance-capacity filter is used for smoothing out the ripple instead of the more common inductance-capacity combination. The only advantage of a choke over a resistor as a filter component is that the choke introduces a much smaller D.C. voltage drop for a given impedance, thereby consuming less power. However, in this particular application the direct current voltage drop and the small amount of power consumed are of no consequence, so that a resistor is the logical choice. The effectiveness of the filter is evidenced by the excellent character of the note.

In order to stabilize the output voltage and to prevent any tendency for the oscillator to chirp when keyed, a 25,000 ohm bleeder is connected across the output filter condenser. This resistor loads the power supply very lightly, but results in a note that does not vary in pitch with keying.

To form the oscillator proper, the tetrode section of the 70L7GT is triode connected, i.e., the screen and plate are tied together, and the output transformer is connected in series with the positive lead. The 50,000 ohm variable resistor in series with the cathode controls the pitch of the oscillator, the more the resistance in the circuit, the higher the pitch. This feature of *continuously variable pitch* not only allows the operator to choose a note to suit his own tastes, but also lessens listening fatigue by making possible a slight shift in the pitch at any time.

If components other than those specified in the parts list are used in the construction of the unit, it may be necessary to change the value of R1 in order to secure correct operation. Values between 10,000 ohms and 50,000 ohms should be tried.

The speaker employed is an Oxford "Little General" which has a two-inch cone and is ideally suited for the purpose. Although the impedance match is not at all critical, an output transformer which is intended to match 7000 ohms to a four-ohm voice coil was found to be very satisfactory, and is therefore recommended. The audio transformer used is of the usual 1:3 step-up variety.

### Construction

Those who dislike struggling with a steel chassis will be pleased to hear that the

oscillator is built up on Masonite. Because the Masonite is so extremely easy to work with, the time needed for construction is reduced over what it would be if steel or aluminum were used. Actually there are many pieces of equipment for which steel offers no particular advantage over Masonite, unless, of course, you enjoy the additional exercise.

The panel is 3/16 of an inch thick and is black crackle finished. It measures 7 inches high by 8 inches long and is cut down from a standard 7x10 panel (ICA No. 810). A small hole about two inches in diameter accommodates the speaker, and a piece of galvanized screening protects the cone from stray screw-drivers and hungry goats. The mounting screws for the speaker can be forced through the mesh of the screening, thereby holding it in place. Natural finished Masonite 1/4 of an inch thick is used for the chassis which is 7 inches long, by 6 inches deep, by 2 inches high. The three pieces of Masonite are fastened together with one-inch brass angle brackets.


### Precautions

Since the key is connected to the 110-volt line, the operator should *avoid connecting himself between key and ground*, and it is advisable to connect the base and level of the key to the cathode circuit of the oscillator rather than to "B" negative.
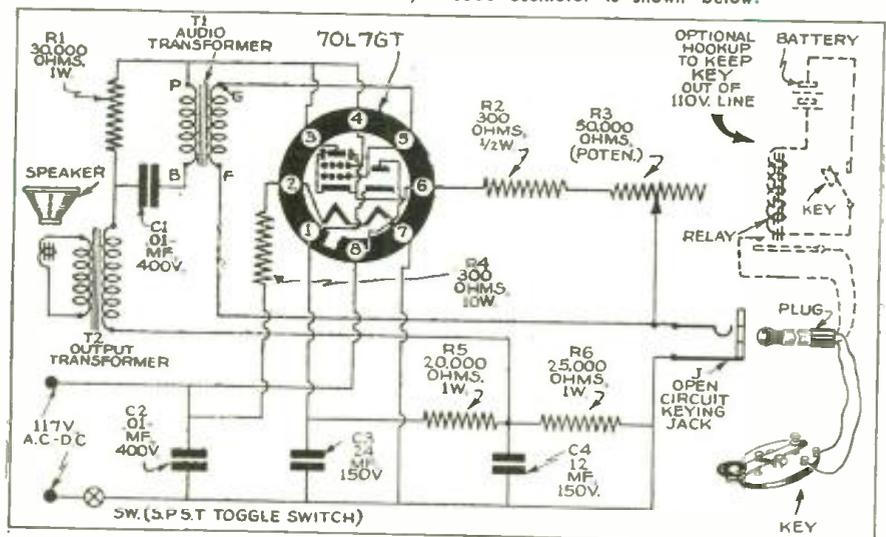
### Other Uses

This little oscillator can serve also as a *keying monitor* by connecting it across a section of the relay that keys the transmitter, or across a pair of auxiliary contacts on the key itself. By tapping across the primary of the output transformer, the tone can be used to modulate an ultra-high frequency rig or for testing a phone transmitter on the lower frequencies. In all of these applications, the characteristic of continuously variable pitch is of advantage, and still other uses will probably suggest themselves to the constructor. A glance at the circuit diagram will show that the unit is exceedingly simple, a squint at the parts list will show that it is inexpensive, and a little experience with it will convince even

Wiring diagram for the Hayes code oscillator is shown below.



the "man from Missouri" that it is a very useful gadget to have around.

Parts List

- R1—30,000 ohms, 1 watt (IRC)
- R2—300 ohms, 1/2 watt (IRC)
- R3—50,000 ohms pot. (Centralab 72-103)
- R4—300 ohms, 10 watts (Ohmite)
- R5—20,000 ohms, 1 watt (IRC)
- R6—25,000 ohms, 1 watt (IRC)
- C1—.01 mf., 400 volt paper (Aerovox)
- C2—.01 mf., 400 volt paper (Aerovox)
- C3—24 mf., 150 volt electro. (Aerovox "Dandee")
- C4—12 mf., 150 volt electro. (Aerovox "Dandee")
- T1—1:3 1/2 audio transformer (UTC S-1)
- T2—7000 ohm plate to 4 ohm voice coil (Thoradon T-13S37)
- Speaker—2-inch permanent magnet (Oxford 2 ZMP)
- J—Open-circuit keying jack (Yaxley)
- S—S.P.S.T. toggle switch (Arrow)
- Tube—RCA 70L7GT
- Nameplate—Crowe

- ALPHABET -

A	●●●	N	●●●●
B	●●●●●	O	●●●●●●
C	●●●●●●	P	●●●●●●●
D	●●●●●●●	Q	●●●●●●●●
E	●●●●●●●●	R	●●●●●●●●
F	●●●●●●●●●	S	●●●●●●●●●
G	●●●●●●●●●●	T	●●●●●●●●●●
H	●●●●●●●●●●●	U	●●●●●●●●●●●
I	●●●●●●●●●●●●	V	●●●●●●●●●●●●
J	●●●●●●●●●●●●●	W	●●●●●●●●●●●●●
K	●●●●●●●●●●●●●●	X	●●●●●●●●●●●●●●
L	●●●●●●●●●●●●●●●	Y	●●●●●●●●●●●●●●●
M	●●●●●●●●●●●●●●●●	Z	●●●●●●●●●●●●●●●●

- NUMERALS -

1	●●●●●●●●	6	●●●●●●●●●●
2	●●●●●●●●●	7	●●●●●●●●●●●
3	●●●●●●●●●●	8	●●●●●●●●●●●●
4	●●●●●●●●●●●	9	●●●●●●●●●●●●●
5	●●●●●●●●●●●●	0	●●●●●●●●●●●●●●

NOTE

A DASH (—) IS EQUAL TO 3 DOTS (●●●)

THE SPACE BETWEEN PARTS OF THE SAME LETTER IS EQUAL TO ONE DOT (●●●)

THE SPACE BETWEEN TWO LETTERS IS EQUAL TO 3 DOTS (●●●X●●●)

THE SPACE BETWEEN TWO WORDS IS EQUAL TO FIVE DOTS (●●●X●●●X●●●X●●●X●●●)

I T I S

**BRITONS CONFISCATE ALIEN APPARATUS**

GERMANS, Austrians and Italians, who are engaged in the practice of medical shortwave diathermy, are out of luck if they live in Great Britain. There, the authorities have confiscated their equipment because such apparatus may easily be converted into radio transmitting stations. Such equipment is virtually a radio transmitter and might easily be connected to an antenna and ground, whereupon its signals could be heard in enemy territory.

**HOLLEY MEDAL AWARDED TO ARMSTRONG**

THE Holley Medal of the American Society of Mechanical Engineers was given to Edwin H. Armstrong, Professor of Electrical Engineering at Columbia University and inventor of the superheterodyne and other useful apparatus for radio. The award was made at the society's annual dinner at the Hotel Astor. Engineers and executives from all over the country attended this important event.

*Get Your* **HOWARD**  
COMMUNICATION RECEIVERS  
*FROM* **ALLIED RADIO**

**Largest Stock  
Amateur Equipment**

You can depend on ALLIED—the world's largest exclusive Radio House for all of your requirements. ALLIED'S complete radio stocks assure prompt shipment on all HOWARD Communication Receivers and associated apparatus. Every HOWARD Receiver is an outstanding performer and an exceptional value. Buy your new HOWARD Receiver from ALLIED—NOW!

**100% RADIO**

ALLIED'S big 212 page 100% complete index to "everything in radio". Listing thousands of up-to-the-minute radio parts, supplies and equipment, it includes specifications, photos and prices on the complete line of HOWARD Communication Receivers and equipment. Send the coupon for your FREE copy. Also send for ALLIED'S new "Dictionary of Radio Terms"—containing the latest word definitions of radio, electronic and television terms—only .10c

**EASY TERMS**

Save time and money with ALLIED'S popular time payment plan. You don't have to pay all cash at ALLIED. You send just a small down payment and the balance is spread out over 6, 8 or 12 months. ALLIED'S small carrying charge is only 60¢ per month. Order today from the New ALLIED Super Catalog!



MODEL 490

HOWARD Model 490 has sensitivity that never knows "crowding" and selectivity that may be varied at will from the hairline sharp position required for CW to the wide band requirements of high fidelity reproduction. Contains 14 tubes. Tunes from 540 KC to 43.5 MC in 5 bands. Incorporates 2 RF stages, calibrated band spread, air tuned IF's, temperature compensated oscillator, split stator tuning condenser, 9 position variable IF selectivity, variable audio fidelity, automatic noise limiter and dozens of other spectacular features. Comes complete with 10" matching speaker and crystal filter.

**AMATEUR NET ..... \$149.50**  
Terms: \$14.95 down, \$11.88 monthly for 12 mos.

HOWARD Model 435, a 6 tube receiver of advanced design, tunes from 540 KC to 43 MC in 4 bands. Bandspread dial electrically spreads out any desired portion of tuning range. Incorporates iron core IF's, BFO, AVC, audio gain control, headphone jack, send-receive switch and built-in dynamic speaker. Has provision for 6 volt power pack. May be converted to Model 436 or 437 at small cost on the Progressive Series Plan.

**AMATEUR NET ..... \$29.95**  
Time payments: \$4.50 down, \$4.50 monthly for 6 months.



MODEL 435

HOWARD Model 436—7 tubes with noise limiter and inertia tuning controls. **AMATEUR NET \$39.95**  
Terms: \$5.95 down, \$6.00 monthly for 6 months.

HOWARD Model 437—9 tubes with RF amplifier and two IF stages. **AMATEUR NET ..... \$54.50**  
Terms: \$5.45 down, \$6.49 monthly for 8 months.



**NEW RADIO DICTIONARY**

Just out—compiled by leading authorities under ALLIED supervision. Gives concise, easy-to-understand definitions of all commonly used radio words and terms. For everyone in Radio. **Send Coupon Today!**

**ONLY 10c**



**FREE**  
212 PAGES  
1941's Irrefutable  
ALLIED RADIO

**SEND COUPON**

**ALLIED RADIO CORP.**  
833 W. Jackson Blvd.  
Dept. 3-BB-1, Chicago, Ill.

- Send your FREE 1941 Radio Catalog.
- I enclose 10c for New Radio Dictionary.

NAME .....

ADDRESS .....

CITY .....

STATE .....

**ALLIED Radio**  
CHICAGO, ILLINOIS

**SETTING A NEW RECORD**


*for Performance and Efficiency*

Hytron U-H-F tubes are the amateur's first choice for both receiving and transmitting.

**WORLD'S RECORD ON 1 1/4 METERS**  
held by W6IOJ, and W6LFN using HY615 tubes in transceivers proves superiority of Hytron design.

*For low power For real power*

**HY114 \$2.00 net    HY615 \$2.00 net    6J5GTX \$0.95 net    HY75 \$3.75 net (illustrated)**  
**HYTRON LABS., 78 Lafayette St., Salem, Mass.**

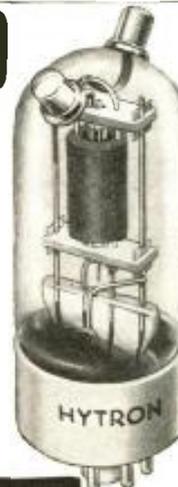

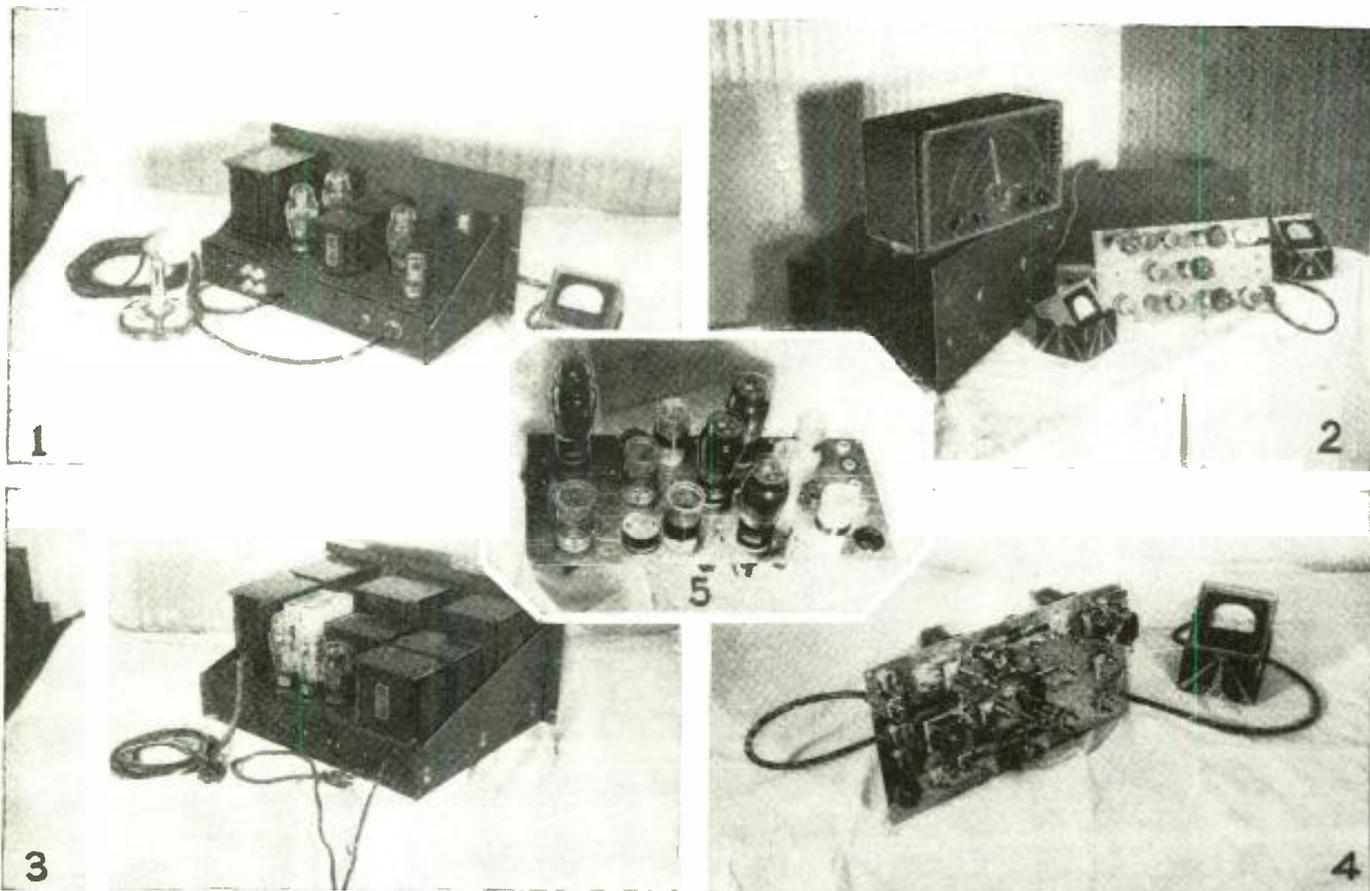


Fig. 1—Experimental audio amplifier. Fig. 2—Complete test set-up for preliminary "pull-swing" F.M. investigations. Fig. 3—Power supply for F.M. Fig. 4—Experimental F.M. modulator. Fig. 5—Top view of F.M. oscillator.

# A "Pull-Swing" Frequency Modulation System for the Amateur



Ricardo Muniz\*, Donald Oestreicher\*\*, Warren Oestreicher\*\*\*

Radio amateurs everywhere will be interested in this brand new system of "wide swing" frequency modulation transmission and reception here described by Mr. Muniz and his associates. A vast amount of laboratory research work has been done on this new system by the authors—all for the purpose of providing a more suitable and greatly simplified method of constructing F.M. transmitters and receivers for the Ham. RADIO & TELEVISION is glad to present this new and original F.M. system to the Ham Fraternity. This is the first of a series of articles on this subject.

proven. (It is felt that the mathematical proof, or explanation of this system is outside the scope of this article.) It is upon this fact (i.e., oscillator control) that the system here described is based.

A pair of crystal-controlled oscillators, which have output frequencies forty kilocycles apart, are modulated in amplitude and out of phase 180 degrees. The outputs are coupled to the grid circuit of an electron-coupled oscillator tuned to a frequency midway between the crystal oscillators' output frequencies. (See Fig. 1.) The frequency of the electron-coupled oscillator is pulled toward the stronger of the two signals when the coupling is correct. Since the control oscillators are varying in strength with the modulating signal, the master oscillator's frequency is swung back and forth in accordance with this signal. (See Fig. 2.)

**Theory.** The intelligence-carrying part of any modulated radio wave is its sidebands. For distortionless transmission, the amplitude of a given sideband should be directly proportional to the signal amplitude and independent of the signal frequency. If a conventional audio system is used with a

● THE R. & T. reader is undoubtedly familiar with the systems of F.M. (Frequency Modulation) transmission in use today (i.e., Armstrong's system of *Phase Modulation*, and the system known as *Reaction Modulation*). These systems present definite and easily recognized disadvantages to the average experimenter. Complexity of equipment and circuit and, therefore, expense is perhaps the greatest reason why amateurs have not wholeheartedly engaged in F.M. experimentation.

The authors have developed a new F.M.

system based on an original idea by W. J. Oestreicher. It is simple, straightforward, easily constructed, adjusted and controlled. Quality satisfactory for *amateur communication* is easily obtainable, while careful design will result in a *high-fidelity* transmitter.

**Basic Principle.** The experimenter has probably come across the phenomenon of oscillator "pulling," especially in superheterodyne receivers. The fact that a stable oscillator will control a less stable oscillator's frequency when they have the proper relative amplitude and frequency difference can be experimentally and mathematically

\*Radio Instructor, Brooklyn Tech. H. S., Eng. WNYE.  
 \*\*Student, Electrical Eng., Brooklyn Polytech., W2LOE.  
 \*\*\*Student, Electrical Eng., Cooper Union, N.Y.C.

frequency modulator, the amplitude of the intelligence-carrying sidebands is *inversely* proportional to the modulation frequency. That is, if the signal amplitude is held constant while the frequency is varied, the amplitude of the sidebands at 10,000 cycles modulation will be one-tenth the amplitude at 1,000 cycles. It is necessary therefore to correct this condition by designing the audio system so that the amplification is proportional to the frequency. We then have the sideband amplitude proportional only to the signal *amplitude*, and thus fulfill the conditions for intelligent transmission.


The output of the *master oscillator* is a complex wave containing components of *twice the frequency* of the wave in its grid circuit, where the modulation actually takes place. These components, or sidebands, are a maximum of 10 kilocycles different from the *deviation* limits of the control frequency. Since in this communications model we have limited the audio range to speech frequencies, a band-pass filter has been included at the output of the master oscillator, designed to pass a band of about 50 to 58 kilocycles. It will therefore exclude the control oscillators' frequencies and modulation components. The band-pass filter is usually a critical circuit to design. However, the *limiter* stage is especially designed to remove amplitude variation as do the following class "C" stages, therefore a flat-top band-pass is not absolutely essential. The "M" type curve which results from any coupling and "Q" in the neighborhood of those required for ideal flat-top band-pass circuits is perfectly usable. (See Fig. 3.)

Since the second harmonic output of the limiter, in the five meter band, has amplitude variation caused by the "M" curve peaks, the conventional resonance curve is used to raise the center frequency response. (See Fig. 4.)


The output of the limiter is represented by curve 1 (Fig. 4). The resultant of all the resonance curves of following stages is represented by curve 2. These curves are *broadened* by damping resistors until they are of approximately a shape to give a resultant curve 3, when combined with curve 1. Any minor amplitude variation left will be unimportant as limiting action at the receiver will remove it.

A series of experiments were performed in order to determine the linearity of modulation. The graph, Fig. 5, shows the results of the first experiment. It will be noticed that in this first set-up the deviation is not proportional to the signal voltage (horizontal axis). After biasing the control oscillators 100 volts positive, the almost linear curve of Fig. 6 resulted. Now the control oscillators, biased 100 volts positive, are modulated 180 degrees *out of phase*. Since it is necessary to keep on the linear portion of the deviation curve the minimum control oscillator voltage had to be 85 and the maximum 115, corresponding to 30% modulation. Because of the effect of the action of one control oscillator on the master oscillator, while considering a positive peak on the other, the percentage of modulation has to be twice this, or 60%.

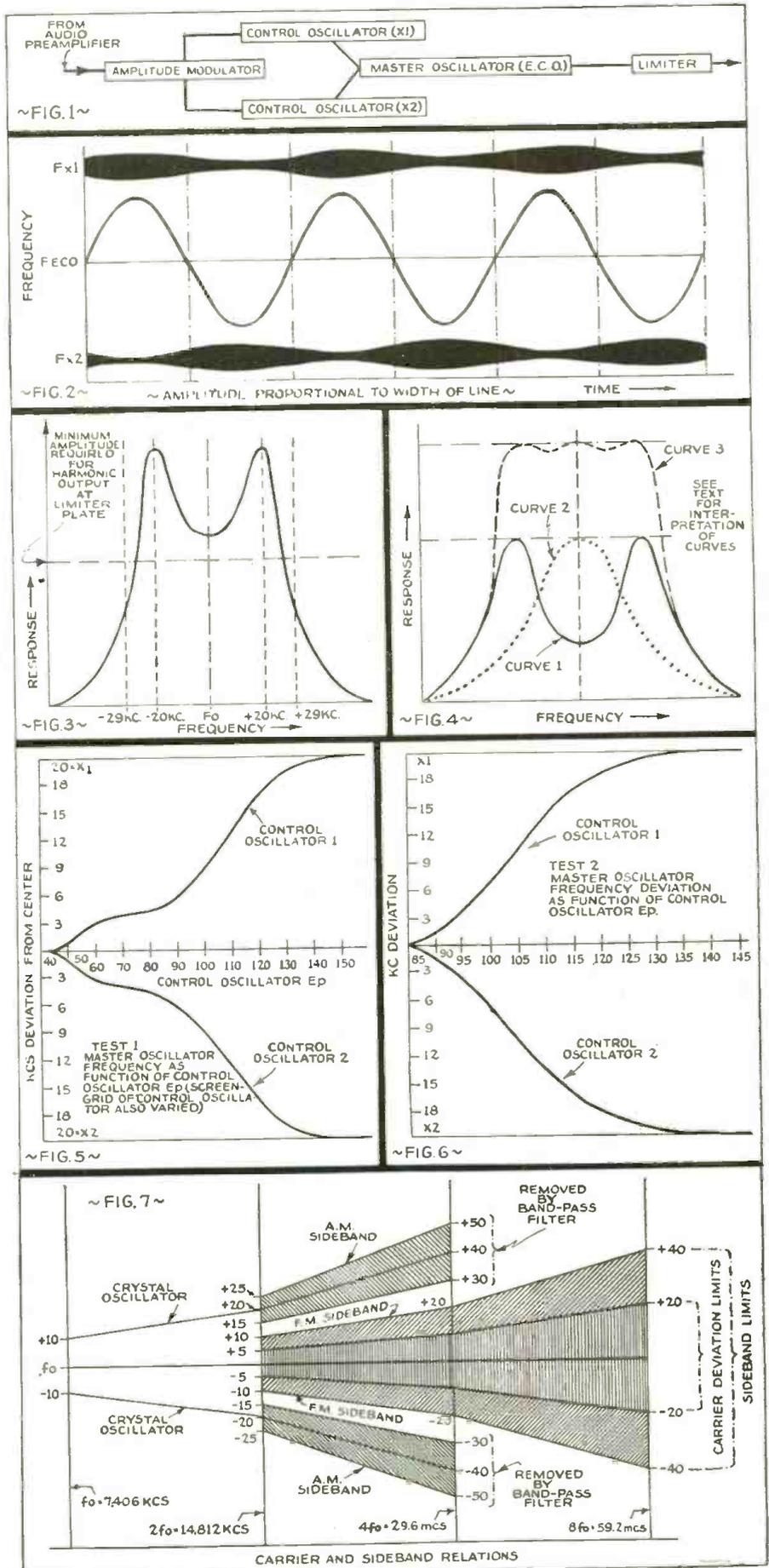**Design.** The crystal oscillators are conventional tri-tet circuits in every respect. The outputs are capacitively coupled to the master, or electron-coupled oscillator grid circuit by means of a balancing condenser.



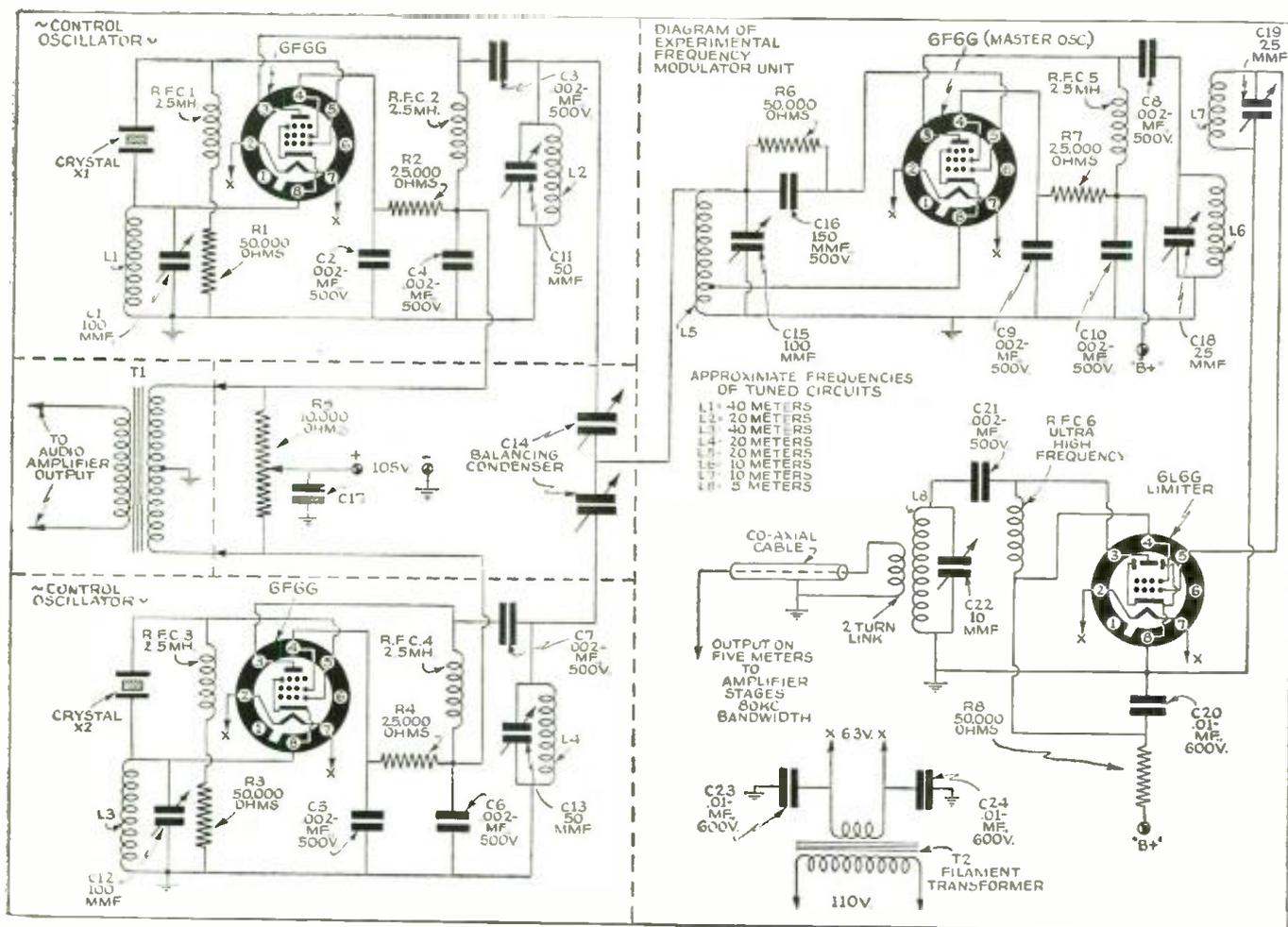Diagrams showing various actions taking place in the F.M. circuits here described.



This diagram shows the new arrangement worked out by Mr. Muniz and his associates, utilizing two control oscillators, which in turn control a master oscillator. In subsequent articles the authors will describe a practical F.M. transmitter, including audio system, complete with power supply and R.F. amplifier circuits, especially designed for Amateur use.

The outputs of the crystal oscillators are on their second harmonics and the grid circuit of the ECO operates midway between these two output frequencies. The crystals, Bliley type BC-3, are ground to 7396 kc. and 7416 kc., making the control oscillators' outputs 14,792 kc. and 14,832, respectively. The master oscillator is tuned to the center of these or 14,812 kc. and its output is at 29,624 kc. plus and minus 20 kc. Since part of the control oscillators' output comes through the master oscillator, the band pass filter, used to keep the response within the band uniform, must also be designed for very low response at the frequencies of the inmost modulation components of the control oscillators. As the sideband caused by the 5 kc. modulation of the control oscillator is 10 kc. from the edge of the F.M. band, the edge of the band-pass curve must change from minimum to maximum in 10 kc., and the "M" type curve, with its sharp rise offers a distinct advantage. Side-band and carrier relations are shown in Fig. 7.

Amplitude limiting occurs when a tube is greatly over-excited, so that the plate is driven to saturation on positive peaks and the grid is driven far past cutoff on negative peaks. This is also an ideal condition for frequency multiplication and the limiter is therefore an efficient doubler. Limiting action is best accomplished by operating the stage at low plate and screen grid voltages (about 100 volts), with no

grid bias, and insuring that the exciting voltage is sufficient to swing the grid from well past cutoff to well above the saturation region.

In the test model, little attention was given to drift in the master oscillator (due to temperature changes). However, the stability encountered was quite satisfactory. In the finished transmitter it is planned to include temperature compensation, if necessary, so that the drift will be held to an absolute minimum.

In order to test the preliminary model a versatile audio system was built. The system had to be of adequate power and frequency range, since it was impossible to accurately predict required power for modulation. The amplifier shown in the photos was designed and built, and while the power required for the final model was not nearly the maximum output, it was satisfactory in every respect. Since the amplifier is subject to redesign, it is considered advisable not to describe its construction now.

The power supply and audio system used in tests were designed about Kenyon "T-Line" components. A detailed description of the power supply will appear in a future article.

In a series of subsequent articles the authors will describe a practical F.M. transmitter, including audio system, complete with power supply and R.F. amplifier circuits. The transmitter is especially planned for amateur use: simplicity of design and

construction combined with ease of adjustment and control were prime considerations.

The authors wish to extend thanks to R.C.A. for the generous loan of instruments, and to the many other companies whose cooperation made these experiments possible.

### Parts List

- BLILEY ELECTRIC CO.**  
 X-2 7416 kc. BC-3 type crystal  
 X-1 7396 kc., BC-3 type crystal
- I.R.C. (Resistors)**  
 4—50,000 ohm. RT-1; R1, R3, R6, R8  
 3—25,000 ohm. BT-1; R2, R4, R7  
 1—50,000 ohm. type E, wire-wound, 9 watt; R5
- KENYON TRANSFORMER CO., INC.**  
 1—T-378 6.3 volt fil. transformer; T2  
 1—T-494 multimatch mod. transformer, on audio amp.; T1
- NATIONAL UNION**  
 3—6F6G tubes  
 1—6L6G tube
- TRIPLETT ELECTRICAL INSTRUMENT CO.**  
 2—0-100 ma. sq. meters, M-327  
 1—0-150 ma. sq. meter, M-327
- A. D. CARDWELL MANUFACTURING CORP.**  
 3—100 mmf. var. cond., ZU-100-AS; C1, C12, C15  
 2—50 mmf. var. cond., ZU-50-AS; C11, C13  
 1—Balancing cond., EU-100-AB; C14 cap. 100 mmf.  
 2—25 mmf. var. cond., ZR-25-AS; C18, C19  
 1—10 mmf. var. cond., ZR-10-AS; C22
- AMERICAN PHENOLIC CORP.**  
 9—5-prong statite sockets, SS5  
 1—6-prong statite socket, SS6  
 4—Super-nip octal sockets, 54-8  
 8—5-prong 912-B coil forms, 24-5P  
 1—6-foot length of No. 72 flexible co-axial cable
- CORNELL-DUBILIER ELECTRIC CORP.**  
 10—.002 mf., IR-5DZ, 500 volt w/kg; C2, C3, C4, C5, C6, C7, C8, C9, C10  
 2—.0015 mf., IR-5T15, 500 volt w/kg; C16  
 2—.002 mf., 9M-22020; C21, C17

**BUD RADIO, INC.**

5—2.5 mh R.F. chokes, C11-920; RFC 1, 2, 3, 4, 5  
1—U.I.F. R.F. choke, C11-925; RFC 6

**P. R. MALLORY & CO.**

1—Jack plugs, No. 75  
1—Midget closed circuit jacks, No. A-2  
1—.01 mf, 600 volt cond., TP-410; C20, C23, C24  
1—1½ inch bar knobs, No. 366  
2—2.5 volt pilot bulbs, No. 170

**INSULINE CORP. OF AMERICA**

4—Flex. shaft couplings, No. 2143  
8—6-inch extension shafts, No. 1249  
1—7" x 12" aluminum sheet, No. 1195

**Coil Specifications**

All wound on 1½ inch Amphenol 912-B forms  
1.1, L3—No. 16 B. & S. enam., 10 turns, close wound  
1.2, L4—No. 16 B. & S. enam., 8 turns, close wound  
1.5, 5 turns, No. 20 enam., spaced in 1 inch tapped, 1½ turns from bottom  
1.8, No. 16 B. & S. enam., 3 turns spaced in 1½ inches  
1.6, 1.7 on one form; 4 turns No. 20 enam. (1.7 var. coupled to L6)

A Meissner 401 Model F.M. receiver Type 9-1023 was used in some of the tests. A slight modification of the oscillator frequency was found sufficient to make it bring in 5-meter band F.M. signals.

**BOOK REVIEW**

**THE RADIO HANDBOOK—Seventh Edition.** Size 7 x 10 inches, stiff cloth covers, 608 pages, profusely illustrated. Published by Editors and Engineers, Ltd., Santa Barbara, Calif.

A most valuable book for every radio student and experimenter. Every Ham needs a copy of this book and no student should be without it. The opening chapters deal with learning the code, fundamental radio and electrical theory, different types of vacuum tubes and how they work, various types of circuits such as the regenerative, super-regenerative, mixer-oscillator, IF and crystal filters, etc. Complete tables covering all the different receiving types of tubes is given, also bottom view of all the tubes, sockets for wiring references, etc. Following chapters deal with details, coil data, etc., on radio receiver construction, including super-heterodynes, pre-selector and converters. Next the book takes up transmitter theory and does a fine job on various types of modulation, speech amplifiers, and includes a chapter on "frequency modulation." Transmitter tubes are thoroughly covered, with complete tables of all the different types; also excitors and data on low-power transmitters. Data on building 600 watt speech and modulator unit is given, and then follows chapters on power supplies, transmitter design, a 200 watt R.F. amplifier, a 400 watt phone transmitter, etc. Other chapters deal with cathode-ray oscilloscopes (with diagrams and construction data), signal generators, various types of UHF antennas, rotary arrays, directive antennas, matching stubs, including a section on "micro-wave" transmitters.

**ELEMENTS OF ACOUSTICAL ENGINEERING**, by Harry F. Olson, E.E., Ph.D. Stiff cloth covers, size 6¼ x 9½ inches, 344 pages, illustrated. Published by D. Van Nostrand Co., New York, N. Y.

The serious student of acoustic engineering will find this new work invaluable, coming as it does from an out-standing authority in the field. (Dr. Olson is Acoustic Research Director of the RCA Manufacturing Co., and whatever he has to say is sure to be of the highest caliber.)

Some of the interesting and vital subjects discussed by Dr. Olson in the opening chapters are—plane and spherical waves, exponential horns, vibrating strings, open and closed pipes, wave filters, corrective networks, etc. The design engineer will find this work extremely valuable, as a vast number of technical formulas are given, having to do with the design of horn and other acoustic chambers. Electro-magnetic and other types of driving systems are discussed, and a number of useful formulas provided. Later chapters deal with such subjects as multiple loud-speaker designs, double-cone and double-cone speakers, loud-speaker baffles, cabinet reproducers, acoustic phase inverters, feedback as applied to a loud-speaker, etc.

A valuable chapter on microphones and their action is included, including velocity and uni-directional microphones. A new treatment is given on the important subject of telephone receivers, with typical receiver curves for different types of receivers. Phonographs are discussed from the acoustic engineering point of view, including "pick-up action." Closing chapters deal with measurement and calibration of microphones, testing of loudspeakers, measurement of acoustic impedance, etc. Other important topics covered are dispersion and collection of sound, acoustical problems in auditoriums, complete reproducing systems, frequency reception of the human ear, loudness of sound, etc., etc. A most valuable and timely treatise.

**"HAVING A SWELL TIME," WRITES ABNER BUGLE, "WISH YOU WERE HERE"**

Abner Bugle is the man who used to write the advertisements for Sprague Condensers.

Nobody could juggle adjectives more gracefully than Abner and, when it came to slapping on the superlatives, even Abner admitted he was just about tops in his profession. But Abner ran into a snag one day, and here is how it happened:

"Look, boss," he wailed to the president of the advertising agency for which he worked, "I'm in a helluva fix. There's nothing more to say about Sprague Atom midget dry electrolytic condensers."

"What!" roared the president, gnashing his teeth so hard he bit the stem off his Meerschaum. "Don't be a fool, Bugle! Why, Atoms build up quicker. They stand higher surges. Their low leakage avoids overheating. They're smaller, and they've got more guts than—"

"I know all that," mourned Abner. "But every cheap condenser makes just about the same claims—whether they can live up to 'em or not. They may not be as good as Atoms in a radio set, but they look just as good in an ad. I don't know what to do."

"Jeepers Creepers, man!" the president's bellow shook the oil painting of the 50th million Sprague TC Tubular hanging on the wall. "And you say you're an advertising expert! Of course Atoms are better. They're unconditionally guaranteed.



There isn't a firecracker in a carload—not in a trainload—two trainloads—three trainloads—"

"I know that, boss," wailed Abner. "But you can't PROVE those things in print. No matter if he fills 'em with mush and wraps 'em in tissue paper, another manufacturer might CLAIM that his condensers are as good as Atoms."

The president did not reply. Grasping pad and pencil, he suddenly began to write. For two hours, Abner stood by, pale and wan and there was no other sound save the feverish scraping of the boss' gold pencil.

"Eureka!" shouted the president finally. "I've got it. Here's what we'll say in our next ad. Listen to this:

"We're glad most condensers are bought on the basis of hard-boiled engineering tests rather than mere advertising claims. When quality is allowed to speak for itself, there can be no mistaking what it says. That's why Spragues are today specified by leading users throughout the world."

"Splendid copy, boss—and it's all true," said Abner, breathing a deep sigh of relief.

"Splendid nothing!" snorted the president. "It's perfect. What's more, you're fired, Bugle. In the future, I'll write the Sprague ads myself."

**SPRAGUE PRODUCTS COMPANY**  
North Adams, Mass.

P.S.—When last heard from, Abner Bugle had become a beachcomber in Tahiti. "Having a swell time—wish you were here," is what he wrote on a post card and added: "It's a great life. Beats advertising to a frazzle."

**BE PREPARED FOR THE NAVY, ARMY or COMMERCIAL FIELD**



WALTER H. CANDLER

For over a quarter of a century the Candler System has trained men at home with their simple, practical system. You, too, can learn code the Candler way, easily and quickly. Let Candler give you that "Co-ordinative Knack" necessary to speed, skill and copying behind. The Communications Reserve of the U. S. Navy is enlisting 5400 expert radio operators. You can qualify in half the usual time for your amateur or commercial license and a good rating by taking Candler Training NOW!

Write today for the New Book of Facts. It's FREE! It tells you how Candler trained world-famous speed champions. Get Candler's inside tips—drop a postcard now to



**CANDLER SYSTEM CO.**


Dept. S-2 ASHEVILLE, N. C., U. S. A.



"Often Copied—But Still the Best"  
**VERNIER DIAL 75c** LESS 10%  
Smooth, Non-Slip Friction Drive; Roto-Buffed, Etched Nickel Silver 284" 0-100 Disc.  
**FREE** Dials, Discs, Knobs, Coil Forms, Switches, Cabinet Kits, Panels, Prism Lac, Polystyrene, and Coil Design Instructions.  
SAMPLE 1½" d. Nickel Silver "Gain" Disc—30c Coin  
**DISTRIBUTORS—Get New Agency Plan. RADIOCRAFTERS**  
1156 Commonwealth Ave., Boston, Mass.

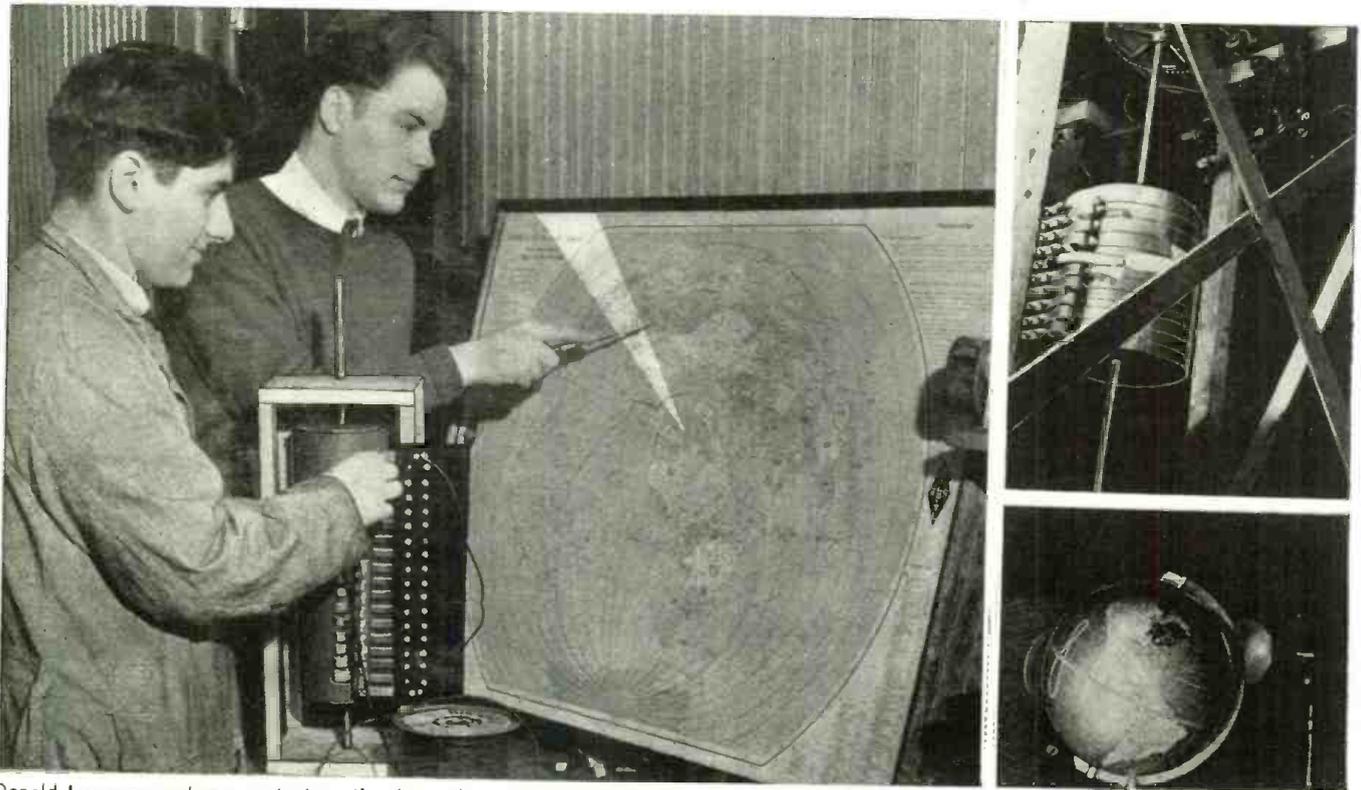**PRECISION CRYSTAL CONTROL FOR ALL AMATEUR BANDS**

**BLILEY CRYSTALS** Now \$3.35 UP  
**BLILEY ELECTRIC CO., ERIE, PA.**



Donald Levenson makes a contact on the drum, the map lights on a 22½ degree angle, while Gilbert Devey points to the lighted section. Two photos at right show globe and selector switch, also the rotary selector switch as mounted on the beam.

# Directional Radio Beam Indicator

Leon M. Leffingwell

● TWO radio amateurs transmitting and receiving over station W8NKI from the fifth floor of Engineering Hall, Carnegie Institute of Technology campus, Pittsburgh, have invented a simple, fool-proof directional SW radio beam indicator for determining the direction their beam antenna is transmitting.

Over a 4½-month period this direction finder has resulted in a 75% increase in the percentage of completed contacts.

Needing the direction finder because they had found it impossible to tell with better than 45-degree accuracy the direction they were transmitting, operators Donald Levenson and Gilbert Devey, sophomores in the School of Electrical Engineering, built the direction finder in one month of spare time.

Before thinking of their new direction finder, operators Levenson and Devey set a convex mirror on the roof of a wing of the building 15 feet out from the transmitting-room window, and set a 200-watt electric light on a flat platform underneath the antenna to illuminate the antenna at night. The mirror reflected the position of the beam.

With the new direction finder installed correctly, says Mr. Levenson, we can transmit accurately within 22½ degrees of the desired location. The indicator consists of an azimuthal map, mounted on a 30-by 40-inch framework with sheet-metal pie-sections in back, dividing the 360-degree map into sixteen sections of 22½ degrees.

## Material Costs About \$30

Working under the direction of Professor Charles Williamson, Assistant in the Physics Department, the operators bought an ARRL map, and 1500 feet of rubber-covered No. 18 twin-stranded lead-in wire for \$10. Then from ½-inch stock yellow pine they made a map case, 30 x 40 x 6 inches. From No. 20-gauge galvanized sheet steel they cut 16 pie-sections, each 22½-inches wide.

Three 60-watt clear-glass candelabra lamps illuminate each pie-section, and strips of one-eighth by one-quarter inch black felt glued between the pie sections, keeps light from passing from one pie section to another. Underneath the ARRL map a piece of ground glass evenly diffuses the light so that the separate lamps will not dazzle the eyes. On top of the map a double thickness of clear, ground glass keeps the map clean. With the \$20 forty-pound map case complete, the operators attached two brass plates to the back and hung it on the wall.

## Rotary Switch Selector Operates Unit

The heart of the system consists of a rotary selector switch with a bakelite drum 4 inches in diameter and 11 inches long. Sixteen metallic wedges, staggered along the surface of the drum, make contact with the contact fingers, lighting each pie-section separately. A hard-rubber contact strip with 16 brass contact fingers (use as many fin-

gers as you desire) has Elkonium contact points between the contact fingers, and a brass plate connects the return leads to the separate contact fingers. Next, brass tubing placed on the drum makes contact between the contact fingers and the brass circuit-return strip. The operators then mounted the contact strip on the framework of the beam tower and mounted the drum on the beam's axle. (See Fig. 2.)

A 17-wire cable runs between the rotary selector and the ARRL map. The station operates via a beam antenna which has three parallel arms, manipulated by a worm-drive "remote control" device. The beam antenna, mounted on the roof of the building directly over the broadcasting room, regiments radio waves in one desired direction. (Fig. 3.)

Another method of operating, similar to the wall map, requires the mounting of a selector switch on a globe of the world and connecting it to the rotary selector switch on the beam.

If it costs too much to run a multiple wire cable from the transmitting room to the antenna, substitute a rotary selector switch, says Mr. Levenson, who operates this set-up on his home transmitter, W8TIN. He mounted a black plastic selector switch on the globe. Then he adjusted the telephone dial by reversing its mechanism, so that the contact springs within the dial touched each other when a direction

**RULES WAIVED FOR RADIO OPERATORS**

● AS a particular convenience to licensees drafted or otherwise called into military service, the Federal Communications Commission has suspended until January 1, 1942, that part of its rules and regulations requiring proof of satisfactory service in connection with renewal of *commercial* and *amateur* radio operators (Section 13.28 governing commercial operators, and Sections 12.26 and 12.06 affecting amateurs). This blanket exemption pertains to nearly 100,000 operators of both classes.

General waiver of these provisions was considered at a conference of Commission officials with representatives of interested labor organizations, including the International Brotherhood of Electrical Workers, Commercial Telegraphers Union of North America, American Communications Association, Maritime Committee of the C.I.O., National Federation of Telephone Workers, Federation of Long Lines Telephone Workers, and the Association of Technical Employees of N.B.C.

The controlling factor in the formulation of this broad and simple procedure was the mutual desire to relieve those called into service of routine details. The Commission is aware of the importance of maintaining the present high standards of proficiency of licensed operators, and also of guarding against a shortage of such skilled workers. It will, accordingly, continue to give these problems careful attention, and should experience indicate the need for change the Commission will act accordingly.

**FROM THE F.C.C. MAIL BAG**

A fake "SOS" marine distress call has been traced by Federal Communications Commission field inspectors to a New England *amateur* radio operator. Investigation developed that the signal which caused useless concern and wasted valuable time was part of a dramatic program reproduced by the amateur in question to give his fellow hams "code practice." The Commission warns the amateur that transmission of this danger signal is inappropriate for code practice, or in any other situation when an actual emergency does not exist.

On the other hand, the Commission has taken cognizance of the valuable contribution by amateurs in providing emergency communication during the recent Texas

flood, when regular wire facilities were temporarily disrupted.

A New Yorker is advised that the holder of a radio operator's license from the Commission who applies for another class of license is required to pass only the added examination elements for the new classification.

A Michigan inquirer is informed that the Commission issues lists of radio stations in various services, but none of ship stations. However, the Bureau of the International Communication Union, Berne, Switzerland, publishes lists of radio stations of the world, among which is a "List of Coast Stations

and Ship Stations."

Nor is the Commission in a position to comply with frequent requests for names and addresses of radio operators in various States. Since the Commission daily handles more than 100 such applications for new licenses, renewals or changes, the compiling of special lists is out of the question.

The call letters KIIASB have been assigned the radio station in the private plane (non-scheduled aircraft) of Robert Taylor, the movie star, operating from Culver City, Calif. The last three letters—ASB—are the initials of the real Taylor's real name, Arlington Spangler Brough.

*Proved*

**DOLLAR VALUE!**



GET AN "HQ" NOW AND YOUR RECEIVER WORRIES WILL BE OVER!



**"HQ-120-X"**

HOW does it perform? How will it stand up? And, how soon will it be obsolete? These are all important questions in determining the actual value of any product. The "HQ-120-X" has established a record which answers all of these questions and assures the amateur of the finest dollar for dollar value. Many owners write that the "HQ" outperforms anything they have ever owned. Its ability to "stand up" is proved by the exceptionally few used "HQ" receivers on the market, despite the thousands which have been sold since the "HQ-120-X" was first introduced. As a matter of fact, we know of hams who bought other makes last year in preference

to the "HQ" but, who this year, traded them in on the "HQ-120-X"—no obsolescence in that! So, if you intend buying a new receiver, by all means see and hear the "HQ-120-X". Its up to the minute performance and sound dollar value have been proved by thousands of users.

**MAIL COUPON TODAY!**

The HAMMARLUND MFG. CO., Inc. RT-2  
424-438 W. 33 St., N. Y. City

Please send "HQ" booklet

Name .....

Address .....

City ..... State .....



Canadian Office: 41 West Ave. No.,  
Hamilton, Ont.


**HAMMARLUND**

EXPORT ADDRESS: 100 VARICK ST., N. Y. City — Cable ARLAB

# A Precision Frequency Monitor

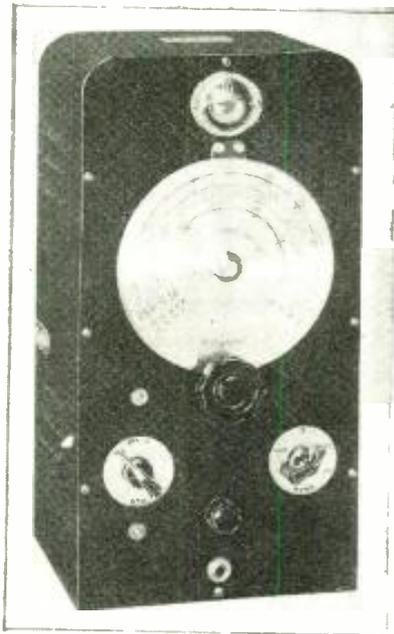F. J. Gaffney\*

This instrument employs the heterodyne method of checking frequency; a method of calibrating the meter is explained.



• THERE are in general two methods which may be employed for determining frequencies of amateur transmitters. The first of these is by means of an absorption meter and the second by the utilization of the heterodyne principle. The former method of measurement consists in bringing a tuned circuit close to the transmitter whose frequency is to be measured and adjusting the frequency of this tuned circuit until a dip is noticed in the reading of the oscillator plate meter or until an indicator such as a flash-light bulb connected in series with the tuned circuit indicates resonance. This method is perhaps the only reliable one for determining the fundamental frequency of the device being measured. It will not serve as an accurate frequency measuring device, however, since numerous factors such as the closeness with which it is coupled to the circuit being

measured and the sharpness of the indicating device affect its reading.

In using the heterodyne method of frequency checking, the radio frequency voltage of the circuit being measured is mixed with the voltage from an accurately calibrated oscillator whose frequency may be adjusted to obtain zero beat with the transmitter frequency. The frequency of the transmitter is then read from a dial on the shaft of the variable condenser of the calibrated oscillator. The calibrated oscillator need not of necessity cover the same range of fundamental frequencies as does the transmitter whose frequency it is desired to check, since harmonics of the calibrated oscillator may be beat with the fundamental of the transmitter whose frequency is being measured. From this it may be seen that a variable oscillator covering any range of frequencies of 2 to 1 can be used to check any frequencies in the spectrum. If it is attempted to make the variable oscillator cover a range of frequencies of 2 to 1, however, it will be found that the accuracy with which the dial may be read is rather poor as compared to that obtainable with smaller frequency ranges. It will be remembered that the amateur bands are rather narrow bands having a harmonic

relationship to each other. This fact makes possible the design of a frequency meter to cover these bands alone which is capable of a high degree of accuracy. It is the purpose of this article to describe a few of the design points of such an instrument.


The characteristics which a heterodyne frequency meter should have are listed below:

1. A circuit arrangement such that the variable oscillators of the frequency meter may be accurately checked against WWV or a standard broadcasting station.
2. Band-spread of the variable oscillators such that the amateur bands cover substantially the entire dial.
3. A stability sufficiently good to enable accurate checks to be made over short periods of time without having to re-set the variable oscillators on calibration.
4. Circuit and controls so arranged that accurate checks may be made rapidly.

To accomplish requirement 1 above, the circuit shown in Fig. 1 was devised. In addition to the variable oscillators which are accurately calibrated, this circuit employs a built-in mixing tube and audio amplifier so that no apparatus other than the frequency meter itself is required for a frequency check. The circuit also incorporates a stable 100 and 1000 kc. oscillator (either frequency may be selected by means of a switch). This allows checking the variable oscillator at many points throughout the range of each band. Three bands are employed on the variable oscillator to give complete band spread on all of the amateur bands as will be explained presently. The 100 and 1000 kc. oscillators are extremely stable and may accurately be set on calibration by beating their frequency in a radio receiver against WWV or a standard broadcasting station. The accuracy of station WWV is within one part in 5,000,000 while that of a standard broadcasting station is within 20 cycles (this corresponds to one part in 27,500 at the low frequency end of the broadcast band). Either of these accuracies far exceeds that required for amateur use.

The operation of the device is briefly as follows: The variable oscillators are turned off and the 100 kc. oscillator turned on. Station WWV or any broadcasting station on a multiple of 100 kc. is tuned in on a radio receiver. A short wire con-

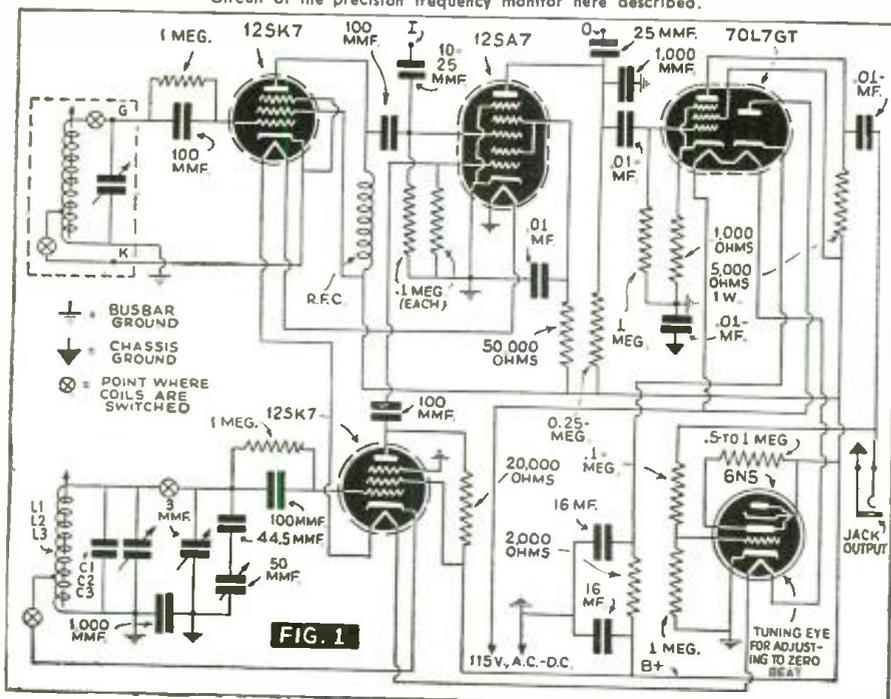Circuit of the precision frequency monitor here described.



\*Chief Engineer, Browning Laboratories.

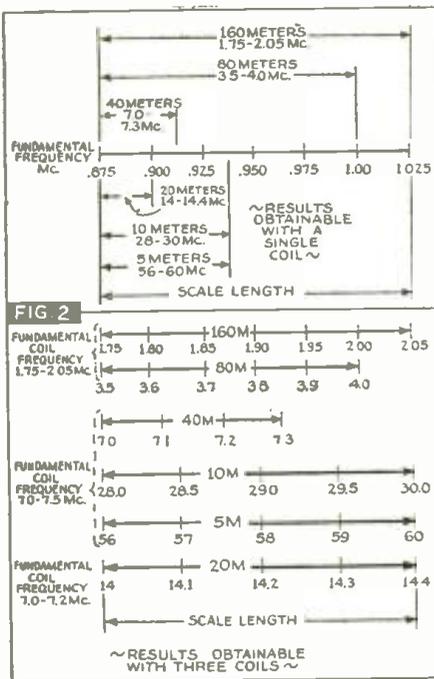


Fig. 2 above shows comparison between the results obtained with three oscillators, and those obtained with a single oscillator.

nected to the plate of the mixer tube through a small condenser is brought close to the antenna input of the receiver. If the 100 kc. oscillator is slightly off calibration, a low-pitched beating tone will be heard in the loud speaker of the receiver. A threaded brass plunger inserted in the coil of the 100 kc. oscillator and rigidly held in position by means of a spring washer is advanced or retarded slightly to change the inductance of the coil so that the 100 kc. oscillator is brought to exactly 100 kc. as indicated by zero beat in the loud speaker. The variable oscillator which it is desired to use is then switched on and the dial adjusted to any point which is a multiple of 100 kc. and which is close to the point on the dial at which it is desired to check a transmitter frequency. Frequencies which may be checked against harmonics of the 100 kc. oscillator are clearly indicated on the dial. Phones inserted in the output of the audio amplifier incorporated in the frequency meter indicate whether or not the variable oscillator is accurately on calibration. Should the variable oscillator be slightly off calibration, a tone will be heard in the phones. The variable oscillator is then adjusted by means of a small trimmer until exact zero beat is obtained in the phones. The 100 kc. oscillator is then switched off and the short lead connected to one of the mixer grids is very loosely coupled to the transmitter. The dial of the variable oscillator is then rotated until zero beat is obtained as indicated in the phones. The transmitter frequency is then read directly from the dial of the frequency meter.

To facilitate accurately setting to zero beat, a tuning eye is incorporated. As zero beat is closely approached, the iris of the tuning eye will flutter, finally opening wide at exact zero beat. This enables much more accurate setting than would be possible with the phones alone.

All of the above procedure takes much


longer to explain than it does to actually perform in practice. The checking of a transmitter frequency including a check of the 100 and 1000 kc. oscillator does not require more than a minute's time. Once the 100 kc. oscillator has been accurately set, frequency adjustments of the transmitter may be made and each frequency check will require less than 30 seconds.

The accuracy of heterodyne meters such as the one described above depends primarily upon the accuracy with which the dial may be read. It is thus desirable to spread the amateur bands over substantially the complete dial to obtain the greatest accuracy. Inasmuch as the amateur bands are all in harmonic relationship, it might be thought that this would be possible with a single variable oscillator. This is not the case, however, inasmuch as the widths of the amateur bands are not proportional to their base frequencies. For instance, the 40-meter band covers a range of from 7 to 7.3 mc., whereas the 20-meter band covers a range of from 14 to 14.4 mc. Thus if a range of frequencies of 7 to 7.3 is spread over the complete dial, the second harmonic of this range will cover a band of frequencies of from 14 to 14.6 resulting in incomplete spread for the 20-meter band. It has been found that to give substantially complete band spread on all of the amateur bands from 160 meters to 5 meters, three variable oscillators are required. This is illustrated in Fig. 2 where the results obtained with three oscillators are compared with those that could be obtained with a single oscillator. Using three variable oscillators and a 5 1/2" dial mounted directly on the shaft of a 270° straight line frequency condenser, it is possible to obtain readings on the 160-meter band to within one kc. of the correct frequency and on the 5-meter band to within 10 kc. of the correct frequency.

Several design features affect the stability of a heterodyne type frequency meter. In general the factors affecting stability may be grouped into two classifications, (a) Those affecting variation in frequency with line voltage; and (b) Those affecting variation in frequency with temperature. Much can be done to satisfy the voltage stability requirement by appropriately placing the cathode tap on the oscillator coils and by running the oscillator tubes at low voltage. Stability with temperature variation is best obtained by locating the coils in such a position that they will change temperature the least amount during warm-up of the apparatus. The coils in the instrument being described are located under the chassis (the chassis is about 7 inches from the bottom of the cabinet), so that all of the heat from the tubes, resistors, etc., which tends to rise in the cabinet will be carried away from the coils. An A.C.-D.C. circuit is employed, thus eliminating the need for a power transformer which is one source of heat. A tube complement is chosen which makes a dropping resistor for the tube filament unnecessary.

To afford a rapid frequency check, the dial of the instrument is directly calibrated in frequency. This prevents the necessity for the use of time-consuming calibration charts. In order to align the variable oscillators so that they accurately track the dial, it is necessary to have control of both the

# New EFFICIENCY

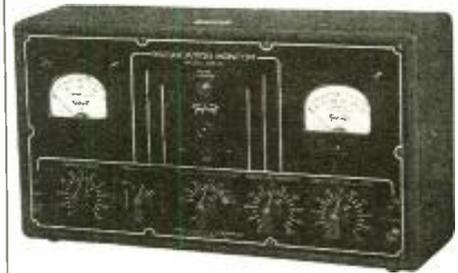

## TRIPLET MODEL 1696-A

You've solved your problem of getting maximum efficiency from your transmitter when you invest in a Model 1696-A Modulation Monitor . . . A new monitor with improved shielding—just the unit for 10-meter bands. Plug it into your AC line—make simple coupling to the transmitter output and the monitor shows:

- Carrier Reference Level ● Per Cent of Modulation ● Instantaneous Neon Flasher (no inertia) indicates when per cent of modulation has exceeded your predetermined set limit. Setting can be from 40 to 120 per cent.
- Helps comply with FCC regulations. Has two RED DOT Lifetime Guaranteed Triplet instruments. Modernist metal case, 1 1/2"x7 1/2"x1 1/2", with black suede electro enamel finish. . . . Black and white panel.

Model 1696-A . . . Amateur Net Price . . . \$34.84

Also available as a rack panel mounting unit.

FOR MORE INFORMATION  
WRITE SECTION 282 HARMON AVENUE

TRIPLET ELECTRICAL INSTRUMENT CO.  
Bluffton, Ohio

## The Famous Johnson "Q"

an original Johnson development, is available in kit form from better jobbers everywhere.

The Johnson Antenna Handbook is now ready at your Jobbers—only 25c, or will be mailed direct on receipt of stamps or coin.

Catalog 966W FREE on Request



inductance and capacitance of the variable oscillators. The inductance of the variable oscillators is controlled by means of a brass plunger similar to that described in connection with the 100 kc. oscillator. The capacitance is controlled by means of small trimmers across each variable oscillator coil. A 3 mmf. variable condenser brought to a front panel control is common to all of the oscillators and is used for accurately setting the oscillator it is desired to use on calibration at any point in its range which is a multiple of 100 kc.

It is believed that the apparatus described above meets all the requirements for accurately checking amateur frequencies on any of the bands between 160 and 5 meters. In fact, although a calibration is not given on the dial, the instrument may also be used for checking 2 1/2 meter transmitters by simply multiplying the frequencies on the 5-meter range by two.

# Compressed Dipole Aerials

E. L. Gardiner, B. Sc.

● IN a recent article\* were described a few simple measurements of field strength illustrating the advantages of directional aerial systems in the reception of short-wave signals. Even the addition of a reflector to the usual dipole was shown to yield a very useful improvement in signal-to-noise ratio. Unfortunately, however, the simplest directional array occupies considerably more space than a plain dipole, and when it is designed for use at wavelengths between 10 and 50 meters, cannot always be accommodated in the space available. The additional wires and spreaders will often be regarded as unsightly, whilst their weight demands the provision of well designed and strongly constructed masts. For example, a dipole and reflector resonating in the 20-meter band will involve two parallel wires each some 32 feet long, and about 17 feet apart. It is not easy to design a self-supporting arrangement of this size, whilst a wooden framework to support conductors of that length is by no means unobtrusive. These difficulties are accentuated when it is desired to erect the whole structure in a rotatable form.

For shorter wavelengths in the neighborhood of five to seven meters it fortunately becomes practicable to construct the dipole and reflector of metal tubing, which can be strong enough to support its own weight in a high wind. Even at these short wavelengths, however, there will be occasions when a reduction in bulk would be very acceptable. Experiments in direction finding may be quoted as an example. Just before the war the writer constructed a dipole and reflector supported by a light wooden framework which could easily be transported by car. This was employed in the field to locate a hidden five-meter transmitter. The latter radiated vertically polarized waves, and the procedure was to rotate the receiving aerial system until signals were at a minimum, when the reflector will be in the direction of the incoming waves.

In this way it was found possible to determine direction with an accuracy of about five degrees, provided of course that the direction of arrival of the waves had not been modified by intervening objects. The aerial structure was 8 feet high and 4 feet wide, and could be fairly easily handled when mounted upon a stout camera tripod fitted with a rotating head. It could hardly be termed convenient, however, and too much time was needed in setting it up, so that the need for a more compact arrangement giving, if possible, more pronounced directional effects was very evident.




Consideration of the possibilities of such an improvement naturally directed attention to the compressed dipole. This form of aerial has been known for many years, and

is used by certain commercial organizations as a television receiving aerial in locations where space is very limited. It is barely mentioned, however, in most handbooks, and very little information seems to be available concerning its general use in short-wave reception. Thus there seemed good reason for carrying out practical tests on similar lines to those described in the previous article already mentioned, and in which the field strength measuring equipment could be pressed into service.
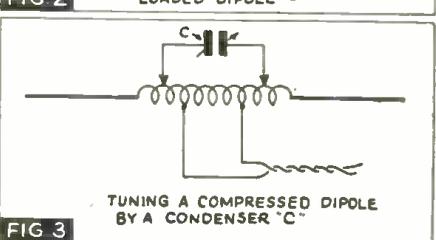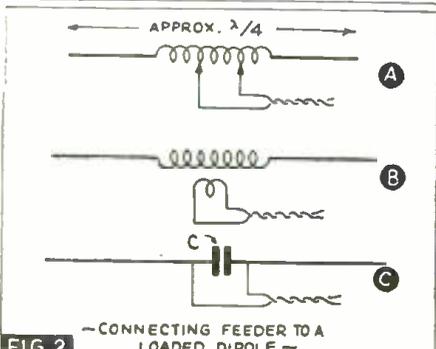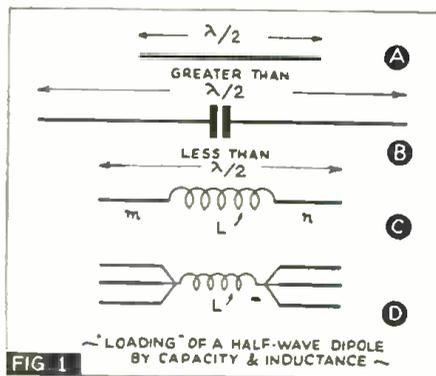
### Half-wave Aerial Characteristics

The ordinary dipole, or more correctly the Hertzian half-wave aerial, resonates to a certain wavelength by virtue of the distributed inductance and capacity of the conductor. In open space the resonant wavelength is slightly more than twice the length of the dipole, which is therefore slightly

Various methods of shortening dipole aerials are shown herewith; this technique is very important, especially where there is little space to erect dipole antennas to cover the longer waves.



less than a half-wavelength long. The proximity of buildings or of other conductors increases the electrical capacity of the wire, and thus reduces the length necessary to resonate at any particular wavelength.

An interesting example of the effect was noticed by the writer when adjusting the length of a 20-meter aerial, one end of which was only a few feet above roof level, whilst the other was 20 feet higher. It was found that the lower end could be reduced in length by some two feet to restore resonance, thus making the two halves of the aerial unequal by that amount with respect to its electrical center. Similarly, the resonant length of a dipole can be increased if the distributed capacity of the wire be reduced. This can be done in practice by the introduction of a condenser into the center of the aerial, and shown at C, in Fig. 1 (b). Since the capacity of two condensers in series is always less than that of either alone, and the added condenser acts in series with the distributed capacity of the aerial wire, the effective value of tuning capacity is reduced. The aerial thus resonates to a shorter wavelength, or must be increased in overall length to resonate at the wavelength to which it responded before the condenser was inserted. It is possible to tune the aerial over a limited range by varying the capacity of the added condenser.

### Reducing Aerial Length

As a rule, however, there is no advantage in increasing the length of a dipole, and it will be more useful to decrease it. By analogy with a tuned circuit employing a coil and condenser, the wavelength will be increased, or the aerial shortened for a fixed wavelength, if either its distributed capacity or inductance be increased. It is inconvenient to increase the capacity to any material extent. To do this by adding a condenser would imply connecting this between the two free ends of the dipole, and would only be possible by the addition of long leads which would modify the action of the whole system profoundly, or by bending the aerial round until the free ends are in close proximity. In either case the aerial becomes a closed loop, and whilst it will in fact resonate to a considerably longer wavelength than before, it is no longer a dipole, and is not within the scope of this discussion.

It is, however, quite convenient to increase the inductance of a dipole by the addition of a coil, which can be inserted at the electrical center as shown at L in Fig. 1 (c). This coil acts in series with the inductance of the wire, increasing the effective value, and thus increasing the resonant wavelength. The distributed capacity is little changed, and the overall length of the dipole must be reduced to bring it back into resonance with the original wavelength.

\*"Aerial Reflectors," The Wireless World, October, 1940.

Being shorter, the aerial is termed a compressed or loaded dipole.

As the value of added inductance is increased the overall length must be reduced to maintain resonance at a particular wavelength, and this shortening process can be continued until finally the dipole itself vanishes, leaving only the loading coil which now resonates by virtue of its own self-capacity. In such an extreme case there would clearly be little radiation from or reception by the "aerial," which has become a closed circuit consisting of a small coil of wire. Some intermediate case must be investigated, and for the purpose of these tests it was decided to choose a value of loading coil which would reduce the overall length to one-half of its original value, or to about a quarter wavelength. The accompanying table gives an idea of the lengths and sizes of loading coil found suitable for wavelengths of from 5 to 20 meters. No. 16 SWG enamelled copper wire was used throughout in constructing the aerials, and the loading coils were wound on a Trolital former 1 1/4 in. in diameter, the turns being spaced by approximately the diameter of the wire. It must be appreciated, however, that whilst the figures given will form a satisfactory starting point from which to work when trying out compressed dipoles, they cannot be regarded as exact. The resonance of these aerials is noticeably sharper than that of a half-wave aerial, and for best results the length should be trimmed experimentally, since it will be determined to some extent by the exact materials used, and particularly by wire diameter and turn spacing.

Approximate design data for compressed dipoles having a length of one-quarter wavelength

Wave-length meters	Approx. length of comp. dipole ft. in.	Turns in loading coil	80 ohm feeder tapped across turns
5	4 0	12	2
7.0	5 6	16	3
10	8 0	22	4
20	16 0	40	6

In order to keep the conditions as simple as possible, the remainder of the dipoles were composed of straight single wires. It is possible to employ as the portions *m* and *n* of Fig. 1 (c) either conductors of larger diameter, such as copper tubes, or several spaced parallel wires joined together at the terminals of the loading coil, as sketched in Fig. 1 (d). By so doing the distributed capacity of these portions is further increased, and either the overall length or the inductance of the loading coil can be decreased somewhat. Clearly the possibilities are extensive, and for the present no attempt has been made to examine the properties of aerials which are compressed to less than a quarter wavelength, or in which multiple wires are used. Probably the chief advantage of increasing the diameter of the arms *m* and *n* lies in the established fact that by so doing the "Q" of the aerial is reduced, and it resonates more broadly over a wider band of wavelengths. This may be important in the particular case of television reception, where some slight loss in image detail may result from the excessive selectivity of a compressed dipole in which a single wire composes the arms, and for which three wires in parallel spaced by about 2 inches can be recommended. A second case which might justify this procedure

would be where a fairly uniform performance over the whole of a wave-band was desired, rather than the best possible performance at any one frequency.

### Feeder Connections

Before experimental tests can be made with a compressed dipole it must be connected by a non-radiating feeder to the transmitter or receiver. Whilst any of the recognized types of feeder could be used, the aerial is symmetrical about its electrical center, and therefore lends itself to a balanced twin-wire transmission line, rather than to the concentric type. Since it is particularly necessary that only the aerial shall radiate, a low-impedance line was preferred to one of a higher impedance, in which the two conductors would be spaced by several inches, because the latter is more likely to become unbalanced during the course of adjustments. A proprietary cable of 80 ohms nominal impedance was selected, having the useful property that the radiation from it was too slight to be measured by the equipment used, even when the cable was not exactly matched to the aerial impedance.


The simplest and most widely used method of coupling is to break the dipole at its electrical center, and, on the assumption that its impedance at this point has the theoretical value of 72 ohms, to insert a cable of about that impedance directly. This system works well in practice, but suffers from the disadvantage that if any steps are taken which change the impedance at the center of the dipole, a mismatch to the feeder must occur. The presence of a reflector near to the dipole will have the effect of lowering this impedance, and thus tends to destroy the desired correct matching between feeder and aerial.

### Matching Impedances

In the case of loaded dipoles a better method of coupling is fortunately available, since it would not be advisable to break the continuity of the loading coil. The feeder may be tapped across a few turns equally placed on each side of the center of the coil, as shown in Fig. 2 (a). Whatever the exact impedance of the feeder or of the aerial, it is now possible to get an exact match, for the impedance across a portion of the loading coil will vary from zero when the two feeder wires are attached at a common central point, up to a comparatively high value when they are separated by the whole coil. At an intermediate point, therefore, an impedance equal to that of the feeder will always exist, and can be found by trial.

An alternative method exists in the form of inductive coupling between the loading coil and a coil of a few turns connected across the ends of the feeder cable, as shown in Fig. 2 (b). For the sake of completeness a method of coupling to the extended dipole of Fig. 1 (b) may be mentioned. Here the feeder is joined directly across the series condenser, as shown in Fig. 2 (c), and the capacity of the latter is selected so that its reactance matches the impedance of the feeder. In this way an exact match to cable of any impedance is possible at one particular wavelength only, but unlike most other arrangements the system will not operate satisfactorily at harmonics of this, since the reactance of the condenser will then be different.

## WIRELESS TRANSCASTER

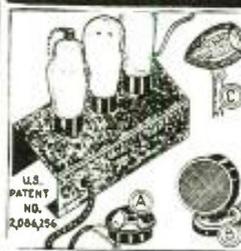

### HUNDREDS

of practical applications. Will broadcast voice or music from any room or floor in home, office or store same building WITHOUT CONNECTING WIRES! Operate from any lighting socket. Transmit your favorite recordings thru any radio without connections between radio and phonograph. Your radio becomes a public address or inter-communication system with a Transcaster.

Home broadcasting without wires. Great fun for parties, auditions. Use as a detective device to listen to secret conversations. A few other uses include wireless nursemaid, pipe law tracer, mind reader, trick ventriloquist, bimbo announcer, talking dog, etc. Impossible to enumerate other uses in this limited space.

**TRANSCASTERS** are available in **FIVE** models, tested and ready to use. All fully guaranteed as to materials and workmanship and also against damage in transit.

**STANDARD MODEL** Excellent beginner's outfit. Includes magnetic speaker as microphone, or any high impedance crystal pickup, record player, **POWERFUL** not to be confused with other tube type outfits. Price amazingly low. Works from a.c. or d.c. Price, complete with 3 tubes, ready to use (less mike) ..... **\$2.95**  
Earphone Mike (Fig. A) ..... 95c additional

**SENIOR MODEL** All electric. Can be used with all types of power mikes. Extra amplification of 50 db. provided. Adjustable frequency range between 1500 and 1750 kc. or if preferred between 500 and 800 kc. Price, (less tubes and mike) ..... **\$3.50**  
Set of 4 matched Tubes for Senior Model ..... **\$1.45**

**DELUXE MODEL TRANSCASTER-TRANSMITTER** Powerful, high-gain device engineered so that it will transmit high-fidelity music without connection wires to remote radio set. No sacrifice of quality or power. Operates from a.c. or d.c. Same frequency range as senior model but greater db. amplification. **\$4.95**  
Price (less tubes and mike) .....  
Set of 4 Matched Tubes for Deluxe Model ..... **\$1.95**

**SPECIAL 5-TUBE TRANSCASTER** This ultra-efficient device has been engineered especially for advanced experimental and professional uses. Employs two extremely high-gain pre-amplifier stages ahead of the audio modulated oscillator. When used with crystal microphone it will pick up and transmit a whisper, with the concealed anyplace in room. Suitable for special police work, for use with recorders, etc. Price, complete with 3 tubes, ready to plug into any a.c. or d.c. outlet (less mike) ..... **\$15.00**

**SPECIAL 3-TUBE BATT. OPERATED TRANSCASTER** Uses newest miniature type **Cameta** size vacuum tubes. Many professional uses. (tubes and batteries less mike) ..... **\$20.00**

**TRANSCASTER ACCESSORIES** Dynamic Microphone, Fig. B \$1.95; \$25 List Wide Range Response Crystal Mike, Fig. C \$7.95; High Impedance Crystal Pickup \$3.45



### RADIO'S MOST AMAZING ACCESSORY

Picks up telephone conversations without tapping wires. Merely plug a device near telephone instrument or wire and listen to both sides of any telephone conversation through the loud speaker of your radio. Works from any a.c. or d.c. outlet. Complete with tubes, ready to use ..... **\$7.90**

### CONSTRUCTIONAL KITS FOR BOYS FROM 9 TO 14

- 30-pc. Radio Exper. Kit includes R.C.A. Tube \$1.00
- 1-Tube B'cast Kit (bat. op.) with tube ..... 1.00
- 1-Tube Short Wave Kit (bat. op.) with tube ..... 1.50
- 2-Tube Elec. Transmitter Kit with tubes ..... 1.50
- 3-Tube Bat. S.W. Kit with 4 coils and tubes ..... 3.45
- 3-Tube Elec. S.W. Kit with 4 coils and tubes ..... 4.25

### PROFESSIONAL COMMUNICATION SETS

- 5-Tube Senior Space Explorer Set. Beam Power. All-Electric, metal tubes, dyn. sprk. 6 coils, wired, tested and ready to use ..... **\$15.35**
- 6-Tube 7-Band Communications Set with tubes and all accessories, Model 7B, wired, tested and ready to use ..... **\$17.45**


**H. G. CISIN, Chief Engineer**

**ALLIED ENGINEERING INSTITUTE**

Dept. S-72

85 Warren St., New York, N. Y.

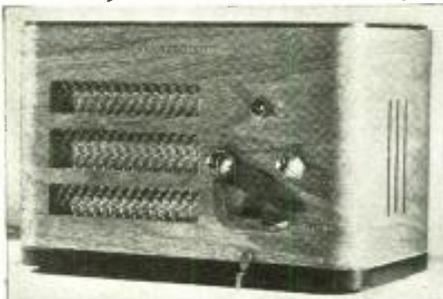**LAST CHANCE**  
that you will have to buy



**Crosley CHATTABOX**  
INTERCOMMUNICATION SYS-**\$1495**  
TEM OF TWO UNITS FOR  
LIST PRICE—\$59.50 A PAIR

Complete two-way wireless loud speaking system. Perfect performance. Plug into any 110 volt house socket A.C. or D.C. Equipped with Call-Listen-Talk switch and volume control.

No installation charges. Modulated carrier signal travels over the electric light lines.

**IDEAL FOR OFFICES, STORES, FACTORIES, SCHOOLS, LIBRARIES, HOMES AND WHEREVER INTERCOMMUNICATION IS DESIRED. EXCELLENT SPEECH CHARACTERISTICS.**

Each unit is housed in beautiful 2 tone veneered cabinet with grilled speaker front.

This Coupon is worth \$1.00 if mailed to us **BEFORE MARCH 15th**

Name .....

Address .....

City .....

**GOLD SHIELD PRODUCTS**  
350 GREENWICH ST. (DEPT. RT-241)  
NEW YORK CITY

★ **PERSONAL SERVICE**  
By *Bill Harrison*

**RECEIVERS**  
**AMATEUR EQUIPMENT**

Fastest service—lowest prices—most liberal trade-in allowances—easiest time payment terms—in the country!


It will pay you to write to me about any Radio Apparatus you need. I guarantee you complete satisfaction and my personal attention.

73 Bill Harrison, W2AVA

\*Send stamp for my latest list of **NEW AND RECONDITIONED RECEIVERS**

**HARRISON RADIO CO.**  
12 WEST BROADWAY - NEW YORK CITY

**SHORT WAVE CONVERTERS for CAR RADIOS**

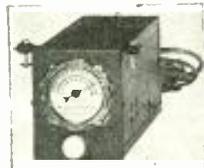

Models 600-A & 500-A shown.

Can be attached to any car radio.

**MODEL 600-A** covers 40-31-25-20-19 and 15 meter bands. Designed for American and Foreign short wave broadcast. Distance range 5,000 to 10,000 miles. List Price ..... \$24.95

**MODEL 700** long wave covers 135 to 410 KC. Receives gov. weather reports, etc. List Price ..... \$24.95

**POLICE UNITS**  
**MODEL 100** 100-A with fixed condensers, covers 1600 to 2600 kilocycles. \$12.50

List Price  
**MODEL 800** Super Sensitive police converter with fixed condenser. Covers 1500 to 2600 kc. Two metal tubes, exceptional distance range. List Price ..... \$15.95  
**MODEL 200** with variable condenser, covers 1550 to 6000 kilocycles. List Price ..... \$17.95  
**MODEL 500-A** with variable condenser and illuminated dial covers 1600 to 6000 kc. Very sensitive, has two metal tubes. Exceptional distance range. List Price \$21.95  
Jobbers and Dealers Wanted

**ABC RADIO LABORATORIES** 3334 N. New Jersey St., Dept. RT-2, Indianapolis, Ind., U.S.A.

It will be remembered that the performance of various arrangements was measured in the present case by connecting the aerial under test to a transmitter adjusted to deliver as far as possible constant power and observing the readings of a field strength meter placed at some two wavelengths from the aerial. It can be safely assumed that the behavior of the aerial under receiving conditions will be complementary to that when tested as a radiator, since the same physical factors are involved in the two cases, and provided that the incoming waves can be assumed to arrive from the direction in which measurements are made.

It was decided first to determine how the radiated field from a compressed dipole of the dimensions given in the table compared with that from a plain dipole. The latter was first set up, under the conditions of the preceding article, and the field strength at a point broadside to the aerial was noted. In this case the feeder was tapped directly into the center of the dipole. A compressed dipole was then erected in the same position, and the same feeder connected across a few turns of the loading coil, as in Fig. 2 (a). This tapping was varied until the radiation from the aerial was at maximum, no change being made to the coupling of the other end of the feeder to the transmitter, or to the adjustments of the latter, which was, of course, crystal controlled. It was noted with great surprise that the field strength from the two aeriels was almost identical, whilst in the second case the feeder current and estimated current in the aerial had increased. The experiment was repeated several times, and on a number of wavelengths, with similar results. It was found that the reduction in overall length of the compressed dipole to one-half of the original was not accompanied, as had been anticipated, by a reduction in the radiated field to 50 per cent or less of its former value, but that if the feeder current was maintained the same in the two cases, the field strength was reduced to between 70 per cent and 80 per cent only, whilst if the feeder tapping point on the loading coil was adjusted to optimum performance as first described, there was practically no reduction observed. Secondly, it was noticed that, whilst no accurate method for measuring the oscillatory current within the dipoles was available, it was clear, from the usual tests of coupling a neon tube or small lamp to the aerial wire, that both the current near the center of the compressed dipole and the

voltage at its free ends was greater.

**Unexpectedly Good Results**

It is generally assumed that the most effective portion of a dipole in radiation or reception is that near the center, in which maximum current flows. It would therefore be expected that, if this portion be coiled up and rendered ineffective as a radiator, the radiation from the whole aerial would suffer considerably. From the evidence it seemed that this was not altogether true.

Whilst calculation of the current distribution within a loaded dipole would not be simple, it seemed likely that the following two effects were mainly responsible for the relatively good performance. First, the "Q" of the compressed dipole had been increased, as was evident from its sharper tuning, and a given amount of power induced in it would thus be expected to set up a larger oscillatory current. The radiation resistance of the aerial was almost certainly lower than that of a plain dipole, and so there would be less damping through radiation. Secondly, it was possible to reach a very effective impedance match into the feeder by the tapping adjustment, and this would still be possible when the aerial formed part of an array, and its impedance was upset by the presence of other elements. The transfer of energy into the aerial was therefore somewhat better, and in conjunction with the former point, these two factors seemed approximately to compensate for the reduced size of the aerial.

As a receiver the compressed dipole may not show up quite so well, since the improved impedance matching will not hold over any wide band of wavelengths. Attempts to confirm this by reception tests over a period indicated that in general signals were noticeably but not seriously weaker than from a full-length dipole, but that when it was possible to tune the aerial exactly to the wanted signals, this difference largely disappeared. A simple and apparently effective method for tuning the aerial was evolved, and is of particular assistance in tuning loaded reflectors. It consisted in joining a small variable condenser across a few turns near the center of the loading inductance. In the case of the five-meter band, the feeder cable was tapped across two turns of the coil, and a 15 nmf. condenser across four turns; Fig. 3. This enabled the aerial to be tuned over some two megacycles, and was fine for reception.—*Courtesy Wireless World, London.*

**RADIO AMATEURS ON DEFENSE BOARD**


● **RESPONDING** to the request of James Lawrence Fly, Chairman of the Defense Communications Board, that it appoint a representative and six regional advisors to the *Amateur Radio Committee* of the Board, the *American Radio Relay League* has announced the following appointments:

As representative: George W. Bailey, of Weston, Mass., president of the League. As alternate and expert advisor: Kenneth B. Warner, West Hartford, Conn., secretary of the League.

As regional advisors, the following: H. L. Caveness, Raleigh, North Carolina; William A. Green, Abilene, Texas; Kenneth T. Hill, Douglaston, Long Island, N. Y.; J. L. McCargar, Oakland, California;

Fred H. Schnell, Chicago; and Dr. Burton T. Simpson, Buffalo, N. Y.

Other members of the *Amateur Radio Committee* include representatives of the Federal Communications Commission, Army, Navy, and the National Youth Administration. The purposes of the committee include the study of all phases of amateur radio facilities. Based on national defense requirements, the committee is expected to consider all questions relating to amateur radio and its place in the defense structure. It will recommend "precautions and restrictions with respect to amateur operations under various emergency conditions, and the allocation of such amateur facilities required by the Army or Navy."

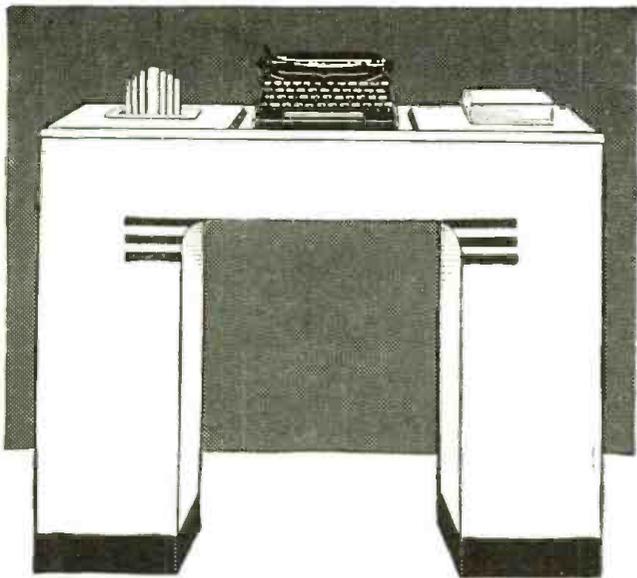

**THIS  
BEAUTIFUL DESK  
for only \$1.00 EXTRA**

WITH ANY  
**REMINGTON**  
PORTABLE TYPEWRITER

*The*  
**COMBINATION**  
FOR AS LITTLE AS  
**10¢ A DAY**

How easy it is to pay for this combination of desk and Remington Deluxe Noiseless Portable Typewriter! Just imagine, a small good will deposit with terms as low as 10c a day to get this combination at once! You will never miss 10c a day. Yet this small sum can actually make you immediately the possessor of this amazing office at home combination. You assume no obligations by sending the coupon.

**THESE TWO EXTRA FOR YOU**

**LEARN TYPING FREE**

To help you even further, you get free with this special offer a 32-page booklet, prepared by experts, to teach you quickly how to typewrite by the touch method. When you buy a Noiseless you get this free Remington Rand gift that increases the pleasure of using your Remington Noiseless Deluxe Portable. Remember, the touch typing book is sent free while this offer holds.

**SPECIAL CARRYING CASE**

The Remington Deluxe Noiseless Portable is light in weight, easily carried about. With this offer Remington supplies a sturdy, beautiful carrying case which rivals in beauty and utility the most attractive higgage you can buy.

**SPECIFICATIONS**

ALL ESSENTIAL FEATURES of large standard office machines appear in the Noiseless Portable—standard 1-row keyboard; back spacer; margin stops and margin release; double shift key and shift lock; two color ribbon and automatic ribbon reverse; variable line spacer; paper fingers; makes as many as seven carbons; takes paper 9.5" wide; writes lines 8.2" wide. There are also extra features like the card writing attachment, black key cards and white letters, touch regulator, rubber cushioned feet. These make typing on a Remington Deluxe Noiseless Portable a distinct pleasure. Thousands of families now using the Remington Deluxe Noiseless Portable know from experience how wonderful it is!



**MAIL COUPON NOW!**

Remington Rand Inc., Dept. 300-2  
465 Washington St., Buffalo, N. Y.


Tell me, without obligation, how to get a Free Trial of a new Remington Deluxe Noiseless Portable, including Carrying Case and Free 32-page Typing Instruction Booklet on terms as low as 10c a day. Send Catalogue.

Name.....  
Address.....  
City..... State.....

"CQ"

Larry LeKashman, W2IOP

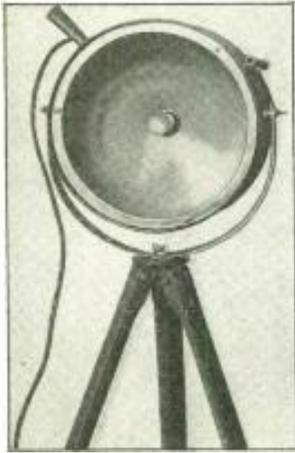**A Spot or Floodlamp  
you will  
be proud to own**



In beautiful black crackle finish with UNIVERSAL BRACKET that may be moved and locked in any position desired. Complete as illustrated, ready to plug into A.C. or D.C. house current. Includes tripod, bulb and rubber cord. Total weight 12 lbs. \$5.50  
When ordering specify whether spot or floodlamp is desired.

- Separate Units**  
Spotlamp, black crackle finish, fitted with Westinghouse frosted bulb, 6 ft. rubber cord with plug for A.C.-D.C. house current. Wt. 7 lbs. \$3.00  
Floodlamp, black crackle finish, fitted with No. 1 G.E. Floodlamp, 6 ft. rubber cord with plug for A.C.-D.C. house current. Wt. 7 lbs. \$3.00  
Tripod, 4½ ft. high with bronze fittings. Weight 6 lbs. \$1.65  
Adjustable Tripod, made of selected straight grained hardwood fitted with sturdy clamps, large thumb nuts and solid metal prongs. Adjustable from 44" to 84". Standard head screw to fit any camera. Weight 6 lbs. \$3.00

All prices quoted FOB, New York.

**GOLD SHIELD PRODUCTS**

Dept. RT-241  
350 Greenwich St. New York

**FLIGHT**

**THE PICTORIAL  
FLYING REVIEW**

Brings you all the phases of world aviation and aeronautics in a non-technical yet educational manner—exciting articles which catch your breath, yet give you the fundamentals of flying and ALL related subjects. FLIGHT keeps you abreast of all the major developments as fast as they appear anywhere.

Now when planes and flying are of vital importance to all, you just can't do without this highly absorbing yet instructive publication. You must be "in the know."

Attractive three-color cover, numerous illustrations. **15¢** copy

Subscription price \$1.50 a year, Canada and foreign \$2.00.

Partial Contents of the February issue: Inside a Bomber on the Attack, Aerial Troop Trailers, Air Battle "Sky Writing," Dive, Altitude and Attack Bombing, Anti-Aircraft Defense, Searchlights—the Curse of the Night Bomber, How R.A.F. Fighting Planes Attack German Bombers, England's Air Raid Precautions, How German Bombers Dive Through Smoke Rings, Barrage Balloons.  
**FLIGHT MAGAZINE**  
20-T Vesey St., New York, N.Y.

● AMATEUR activity is reaching the peak of the winter season. The snow and cold weather keeps the boys busy indoors. The surest sign of increased activity is the fact that 40 meter CW signals actually cover up the South American phones. Good signs bring to mind a letter in the current issue of QST. W9LEM suggests, since there already are "weeks" for everything, we have a National QSL Week. It sounds like a fine idea and there is no reason why everyone interested in cards shouldn't participate. The purpose would be to get everyone to swap cards for all their QSO's of the particular week designated as National QSL Week. It would be an opportunity to fill in cards from states that haven't QSL'd, if the entire gang got into the spirit of the thing. More than that though, it would probably revive a great deal of interest in QSL'ing, which would make for continued swapping of cards in the future.

Letters are continually arriving with various comments on "CQ". While they are all appreciated, unfortunately they do not add to the material for the column. Information is still needed and clubs and individuals are invited to contribute.


W2MCO is sorely beset with BCL trou-

ble. Already threatened with lynching by irate neighbors, Fred is really in a quandary. Most perplexing angle is the fact that W2MCO hasn't been on the air at any time the neighbors complained. Spooks! W2IOP has been testing some new equipment, including an RCA AR77; a 7 watt CW rig; and a 900 watt CW rig. W2VY is busy working at the new WEA station, located at Port Washington. Next time you complain about an antenna falling down think of WJR's 700 footer which collapsed during a freak windstorm in Detroit. W2IJU is on 80 CW now. W2LYR is still a 10 meter phone bug.

W6QMI/2 is also becoming a 28 MC. convert after the results he has been getting with an indoor antenna. With a new receiver practically purchased, W2HP will soon be back on the air. Incidentally W2IOP is now working at Sun Radio in New York City. W2LNY is getting prouder and prouder of his new rig. You would too, if you had just knocked off KC4USB.

The DC Century Club files have been closed for the "duration of the war," or until world conditions justify its continuation. W2GT, Ed Hopper of Bergenfield, New Jersey, with 152 confirmed countries,

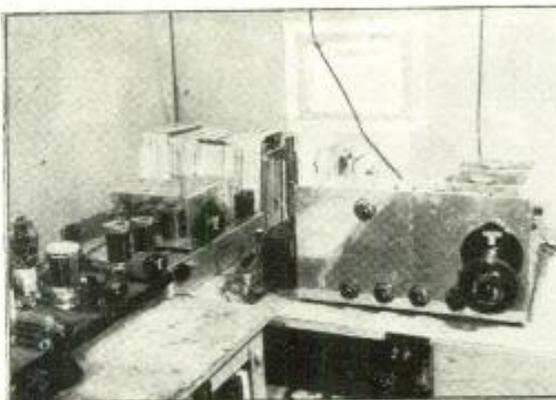A QSL card received "before the war" from GM6WD, Scotland; lower left—Transmitter, Receiver and E.C.O. of station W9YXO; lower right—A Japanese Ham—J5CC.



is top man. Those 152 confirmations will probably keep Ed there for a long time! Those who believe in the real amateur spirit might well take W2GT as their shining example. With all credit to Ed's modesty, and if he knew we were writing this it would never get in print, he is one of ham radio's great characters. Using low power in so far as DX men are concerned, a single 35T, and an HRO receiver, with no rhombics, V beams, or trick gadgets W2GT set up this amazing record. On good authority we have been told of times when W2GT would sit back for hours at a time and actually pass up XU's; J's, and the like, in the hopes of hearing something new. Just let's not forget Mrs. W2GT, without whose cooperation 152 countries would just be a myth.

W2BO, W8OE, and W2LNY waste half their lives in 3 ways. W2MVJ is increasing his power. Oscar Corwin, a super SWL from Frankfort, Indiana, received a fine write up in the local steel publication. From Vic Politi of Fairfield, Conn., we received some information on a few of the locals. WIIBH is off the air because of overtime on his job and lack of DX to keep him hunting. W1MFT received his ARRL code proficiency certificate for 25 WPM. KC4USA, K6IQN, and lots of Cubans are rolling in on 20 meter phone.

While not an amateur station a new Japanese station, JLG-4, is on the 19 meter band and is heard with R9 signals during the morning. W2KHR's brother is now W2MID. W9RFA is sporting W2NET, now that he lives in New York. W2KIK may be found operating army ham station W2MAP.



Shortwave listening shack of Oscar Carwin of Frankfort, Ind.

**O.M. Have You a Harmonic?**

Editor,

Here I sit. Beside me is a rack and panel outfit containing limiting amplifier and monitoring amplifier, in front of me a broadcast transmitter, and on the other side, a 14 tube communications receiver, and in

front of that, a copy of RADIO & TELEVISION, open at the "What Do You Think?" page. Now, I too have a pet grievance to air.

First, I want to say that I am everybody's friend, and being a Ham myself have not the slightest intention of reporting any

amateur for any reason, but did you ever try to watch the meters on a broadcast transmitter, watch your audio levels, and at the same time copy press at between 35 and 40 w.p.m.?

The other day I was sitting here, "cans on" and fingers tricklin' over this keyboard to the tune of W C X, press station on 7850 kc. Suddenly I hear a bang, a hiss, and a half dozen other audio frequencies besides the one I was copying, or by that time, "tryin' to copy," and behind that conglomeration, some son-of-a-so-and-so tryin' to make his young sister say hello into a mic (yes, I could hear him through the beat oscillator and he was about 400 miles away). Now, did you ever hold a match under a thermometer and watch the mercury go up? Well, if you haven't, try it some time when there's a thermometer in the shack you don't want, and, when the mercury gets to the top, watch, with your eyes well away, and you'll see what happened to my temper. To heck with the news. I turned off the beat oscillator and inside of 5 minutes had logged a half a dozen 75 meter phone stations on and near 7850 kc.

Now I don't have to tell you that a transmitter is not working at peak efficiency with a harmonic like that! All that power that is being radiated at twice your frequency isn't doing you any good, but sure can cause someone else a lot of grief, and when it falls outside the Ham bands it's inexcusable! So how about you 75 meter boys giving your "rigs" the once over?

MAX FISHER (B.C. Station CJIC),  
83 Summit Ave., Sault Ste. Marie,  
Ontario, Canada.

**COMPLETE RADIO COURSE \$1.95**  
POSTPAID

**"I am well pleased with the Radio Course. I am at present doing part time radio service work for a radio store."**  
S. T. Alexander, Elroy, Wis.

**PLACED ME IN MY JOB**  
"The R.T.I. Course reprint is a complete education in radio servicing. It put me in my present job at a well known radio shop." James P. McIntyre, Houston, Tex.

**VERY MUCH SATISFIED**  
"I am very well pleased with the Radio Course purchased from you a few weeks ago." M. F. Anderson, Denver, Colo.

**HELPS ANY SERVICEMAN**  
"The R.T.I. Course is worthy of space on any radioman's shelf. He can get the value of the cost in an hour's reading." Wm. C. Mitchell of Parchman, Miss., goes on in his letter to compare this course to resident training costing over \$300.00.

"I am so satisfied with your Radio Technical Institute Course, that I have to congratulate you. This course is worth its price by several times." J. M. Ocasio, New York, N. Y.

**AMAZING REDUCED PRICE**  
Exact reprint of the regular \$39.00 Radio Technical Institute course is offered for only \$1.95, the full price. This is the latest radio course complete in every way and exactly the same as the much higher priced original lessons. Become a radio expert almost for nothing. Act today while the offer lasts.



You quickly learn radio with this simplified training. You really get three courses in one: (1) Elements of Radio and Electricity, (2) Practical Radio Servicing, and (3) Advanced Training.

**LIMITED OFFER**  
No-risk free-trial given. Write to us today while this offer is in effect. Limited quantity of courses printed to sell at the reduced price.

**FOR HOME-STUDY**  
Get ahead in Radio with this practical training. The lessons are clear, interesting, easy to understand and use. Final exam and diploma available after course is finished. Look the course over without any risk.

**10 DAYS FREE EXAMINATION**

SUPREME PUBLICATIONS, Room 536, 3727 W. 13th St., Chicago, Ill.  
Ship the complete course on approval without any obligation to buy. I may keep the course for 10 days. If, for any reason, I am not pleased, you guarantee to refund my money.  
 I will pay \$1.95 and 15¢ postage to the mailman.  
 I am sending \$1.95, the full price, ship postpaid.

Name: .....  
Address: .....

# SPEED Up Your Work!

Learn to Type  
without  
A Typewriter



Master the Touch System—Quickly—  
Accurately Get the "Feel" of Typing  
Before Investing Your Money


Now, you don't have to own a typewriter to learn how to type. The ingenious, patented "Touch-Rite" board gives you all the practice you need for speedy, accurate typing. It teaches you the touch system—the real, professional way universally used in business. You may have been a "hunt-and-peck" typist for the longest time or you may never have used a typewriter before—it doesn't matter, because the "Touch-Rite" teacher will soon permit you to master it. "Touch-Rite" is a scientific substitute for a typewriter. It is a life-size counterpart of a standard keyboard, which is real as to size, position, and "feel". Each key has a depression in the  $\frac{1}{8}$ " thick board, in which the black plastic buttons slide. Printed under each key is a number which indicates the finger of each hand which strikes it—simple as A B C.

"Touch-Rite" is highly recommended by the Principal of Horace Mann School; Director, Bureau of College Res. arch, Columbia College; American Foundation for the Blind; Professor of Experimental Education, New York University; Director of Scarborough School, Scarborough-on-Hudson.

An 8-page illustrated book of instructions will show you how best to use the "Touch-Rite" teacher. **\$2.00**  
Weight 3 lbs. Add postage .....
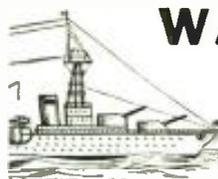
## GOLD SHIELD PRODUCTS

350 Greenwich Street Dept. RT-241 New York, N. Y.



# WARSHIP MODEL PRINTS

\$6-10,000 ton U.S. Navy  
37" Cruiser, Model Blueprints \$3.15  
(Complete Kit, all fittings \$28.00; Hull Kit \$7.75)

- S4—U.S. Destroyer; 30" exact model; blueprints \$1.60 (Hull constr. Kit \$3.60; complete Kit \$33.50)
- S3—"Constitution" (Old Ironsides 25" Model, Blueprints) \$3.20 (Complete Kit \$35.00; Hull Kit \$6.50)
- S7—"Robt. E. Lee"—Mississippi River Steamboat; 28" long; blueprints \$2.60 (Complete Kit \$22.00; Hull Kit \$8.50)
- S2—"Clermont"—first steamboat (blueprints) \$1.10 (Complete Kit for 18" Model—\$7.00 prepaid)

## DATAPRINT CO.

Box 322, Ramsey, New Jersey

### WEIGHT SCALE FOR RECORDERS

For Recording Engineers, Servicemen, etc. Size of ordinary fountain pen. Attractively finished in black, white or color combinations of bakelite. Chrome pickup hook. Instantly determines weight on playback needle or cutting stylus. Indispensable because various recorder mfgs. recommend their own weight limitations on pickups and cutting heads. Proper wt. vital. Eliminates guesswork. Controls depth of cut. Prevents too shallow or too deep grooves.

**UNIVERSAL MICROPHONE CO., LTD.**  
INGLEWOOD, CALIF., U.S.A.

## GOLDENTONE... 50% OFF

DEAL DIRECT FACTORY PRICES — Over 60 models to choose from—4 to 12 tubes. Portables \$8.98 up. Farm sets \$8.98 up. Car sets \$8.98 up. Foreign hand sets \$8.98 up. Samples 30% off. Quantity discounts. Free 1941 Brown train catalog gives details of 10-day FREE trial agent's proposition and discounts. Mail postcard. GOLDENTONE RADIO CO., DEPT. RT, DEARBORN, MICH.

Free Catalog R.C.A.

NO DRY TRIAL! 495 UP TO 1000

REAR GUARANTEE

# Practical Antenna Hints

## Matching Stubs and Rotary Beams

Larry LeKashman, W2IOP

● IF all the material written about antennas was laid end to end, there probably wouldn't be enough bare space on the face of the earth to erect even a vertical.

We shall not attempt to go into the theory of the antenna. Instead, leaving that phase to more complete texts, let us see if we can extract sufficient material from acknowledged designs to really put our antenna to work. Keeping in mind that every antenna installation presents its own problems, no attempt will be made herein to discuss mobile design.

The beginner is often troubled with the *tuned vs. untuned* feeder arguments. The feeder system serves no other function than to transmit energy from a transmitter to the antenna itself; or conversely to transmit energy from an antenna to amplifying stages of a receiver. Thus a tuned antenna simply implies you are tuning the feeder to effect the maximum transfer of energy by achieving an impedance match. An *untuned* line, when operating correctly, is superior to the tuned line since it requires less apparatus to set up and operate. For example, it is possible to load up a transmitter using tuned feeders, without the flat-top radiating any energy—the load being entirely absorbed by the feeders. Such a condition, while it is not uncommon, is much less likely to occur in an untuned line. Generally speaking, if an untuned antenna draws normal current it is working satisfactorily.

The simplest type antenna, other than a mere piece of wire, is of course the *untuned half-wave*. At this point let us consider the most glaring drawback of any untuned antenna. This fault is their limit to *one-band operation, which means a separate antenna for each band*. The antenna data chart accompanying this article shows 16 of the most fundamental antennas. Incidentally, it is from the 1941 edition of the Stancor Hamannual which is available from any amateur dealer. The *concentric line* antenna types are only practical for the *ultra-high* frequencies, because the concentric line is in itself quite expensive. However, its wonderful transmission efficiency makes it well worth consideration, wherever possible. Needless to say that in calculating dimensions, several unknown factors must enter into your figures, but principally height above ground and capacity of surrounding objects. When erecting your antenna in most cases, you must use the "cut and try" method to determine these unknowns—cutting the antenna until it "loads" correctly. Next month we will show several methods of determining length with meters and neon bulbs.

To "straddle the fence" for a moment, let us go on record as a believer in *tuning units* in the station. For general experimental work an antenna tuner is invaluable. Two variable condensers and a coil, sufficiently large to tune to the lowest frequency band worked, is all that is needed. A clip or else a plug system makes it possible to switch

condensers from series to parallel, and *short* turns on the coil if necessary. There are countless methods of mounting these units; our particular "brand" will be shown next month.







It is possible to match a tuned antenna without tuning the feeder, by the use of a *matching stub*. The stub is extremely difficult for the beginner to handle. At present we will leave that phase of antenna construction to any of the radio handbooks. However, there is on the market an excellent kit, the Johnson "Q," which makes use of a *stub*. See Fig. 4. The remainder of this article will be devoted to a simple rotary beam, using the Johnson "Q."

The antenna, because it has untuned feeders which are matched to the flat-top, is very efficient. The antenna is a half-wave, which radiates from the front and back, and has little gain off the ends. Since it is extremely bi-directional, 180° rotation will give 360° coverage. This eliminates costly rotary mechanism and makes possible several novel installations.

Figure 3 shows the arrangement used at W2IOP to rotate a Johnson 20 meter and 10 meter "Q." Fig. 2 shows details of the Q mounting. Premax elements were substituted for wire and adjusted to length on the ground. While elements of this sort are highly recommended, there are two substitutes that are somewhat less expensive. One is  $\frac{1}{2}$ " thin-wall electrical conduit, which is available from any electric supply house. The other substitute is *bamboo*. In this case the poles are put under pressure and wire fastened as shown in Fig. 5. Copper-weld wire, which will not stretch, should be used and is supplied in the Johnson "Q" kits. The basic idea of hinging the "Q" to a central support, or as a matter of fact hinging any bi-directional antenna, is applicable to numerous installations. Those illustrated are merely one particular application of a flexible system.


The *rotary beam* need not be elaborate, even after leaving the efficient and remarkably effective rotary half-wave. The first problem to be approached is of course 360° rotation. In the next article we shall treat in detail one more 180° rotary beam—the "8JK." From that point on, to get complete coverage with our antenna, we must have *complete rotation*. Fig. 1 illustrates a simple and inexpensive method of obtaining complete rotation. The Premax *rotomount* will easily support the weight of a 4-element beam. The diagram shows the rotomount as a hand-driven unit. This system is only practical where a direct line may be run to your operating position, otherwise a motor should be used. Motor drive, as well as further antenna facts, will be taken up next month. Ponder over these for a while and you'll begin to see why Hams get gray.

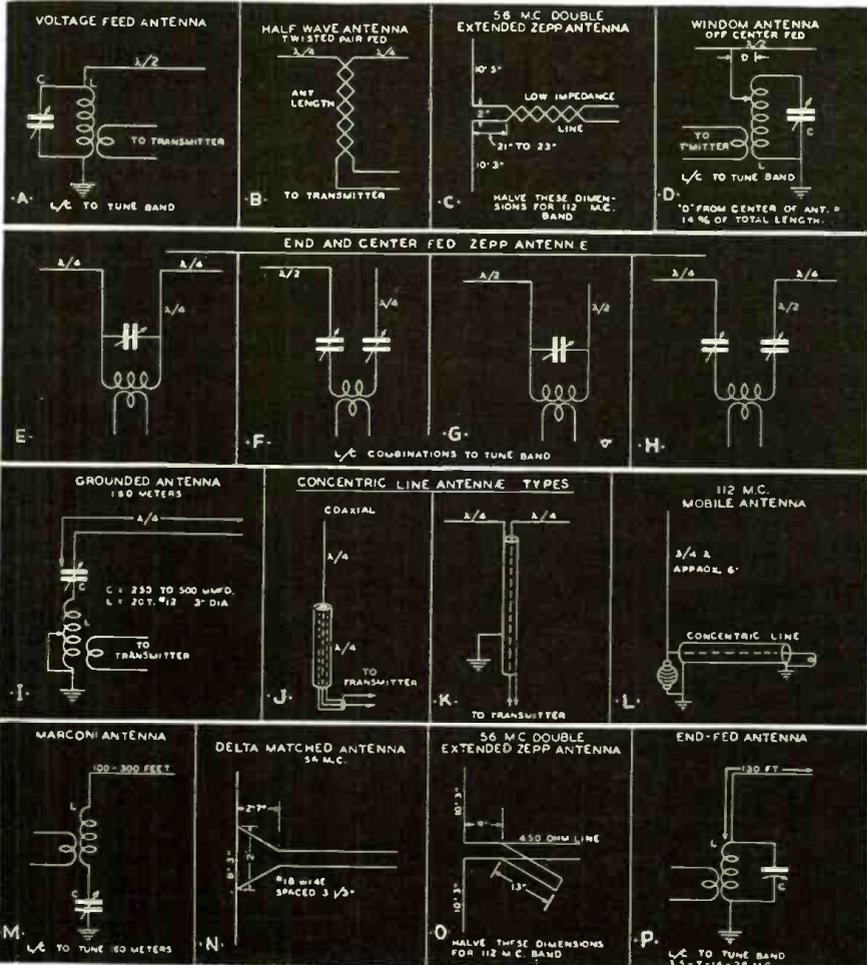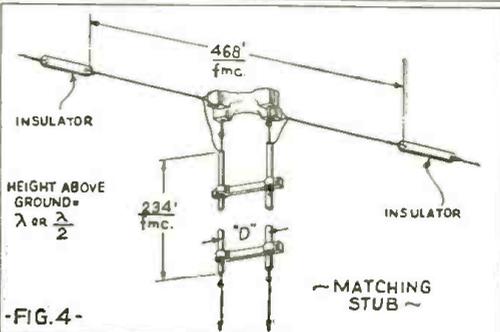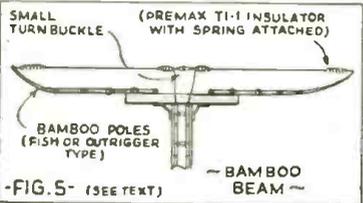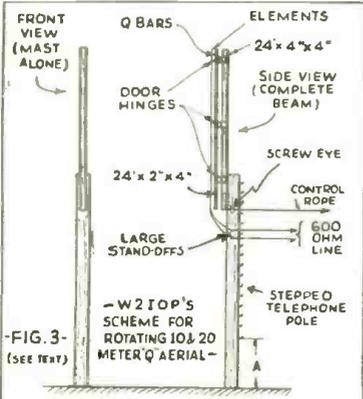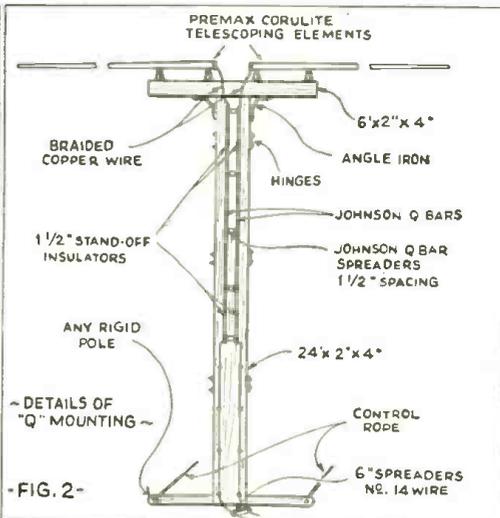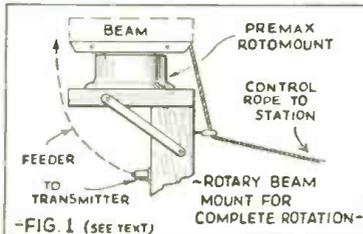(This is the first of a series of antenna articles designed to offer helpful suggestions on your antenna problem, and if possible give you some ideas that will make your antennas work better.)



The illustrations above show various ways of mounting rotary beam antennas as suggested in Mr. LeKashman's article. A very light beam frame may be made of bamboo, as indicated in one of the pictures. A "matching stub" forms an easy method of turning these beams.

## Home Recorder FREE!

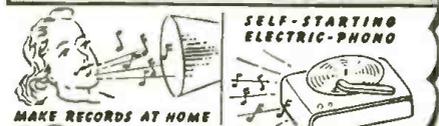

Put this Radio-Phono Chassis In Your Present Cabinet...  
**FACTORY-TO-YOU SAVES UP TO 50%**

Thrilling World-Wide Foreign News DIRECT!

UP \$25 TRADE-IN (On many models up to 18 tubes)

ENJOY listening to fine recordings on electric phonograph—delight in amazing ocean-spanning radio. Make records on Home Recorder (sent FREE for a limited time). Big FREE catalog pictures beautiful 1941 Factory-To-You radio chassis and console values—from 6 to 18 tubes—up to 5 Bands—including Automatic Record-Changing Radio-Phonographs, Home Recorder, etc. Liberal Trade-In! Write today.

**MIDWEST RADIO CORPORATION**  
DEPT. 14-HH CINCINNATI, OHIO

## EVERYTHING IN RADIO

**BURSTEIN-APPLEBEE COMPANY**  
1012-14 MCGEE STREET, KANSAS CITY, MISSOURI

## EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. It affords the quickest and most practical method yet developed. Available tapes from beginning's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.

**MACHINES FOR RENT OR SALE**

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands have used and endorse the Instructograph System. Write today for full particulars and convenient payment and rental plans.

## INSTRUCTOGRAPH COMPANY

Dept. RT, 4701 Sheridan Rd., Chicago, Ill.  
Representatives for Canada  
Radio College of Canada, 54 Bloor St. West, Toronto.

ONE YEAR SERVICE GUARANTEE!  
Sent complete ready to listen with instructions & tiny phone for use in homes, offices, hotels, in boat, etc. SIMPLE TO OPERATE—NO ELECTRICITY NEEDED!  
**SEND NO MONEY!** Pay postman only \$2.99 plus postage charges on arrival or send \$2.99 (Check, M.O., Cash) and yours will be sent postpaid. A MOST UNUSUAL VALUE! ORDER NOW! FREE PLUG IN "MAGICTENNA"—ELIMINATES OUTSIDE WIRES!  
MIDGET RADIO CO., Dept. RT-2, Kearney, Nebr.

Principles of

# Frequency Modulation

F. L. Sprayberry\*

● THE basic theory of frequency modulation is by no means new. It was put in use to a limited extent before the widespread use of the vacuum tube. In fact, it was the outstanding alternative in modulating systems before the vacuum tube made it possible to amplify audio frequencies. Certain applications of frequency modulation appeared in technical literature as early as 1911, and one form of frequency modulation adopted a few years later, remains in use to the present day. It is used in the "compensated wave" transmitter at present.

Although the uses to which frequency modulation has been put have not been extensive, the results of even this meager effort have been so revolutionary that the subject is most worthy of serious study and investigation.

We can best approach the subject of frequency modulation (FM) by a simple comparison of it with amplitude modulation. Amplitude modulation as you know from your previous studies, consists of changing the amplitude of the carrier energy in accordance with a given signal. Frequency modulation on the other hand consists of changing the frequency of the carrier in accordance with the changes of the modulating signal. Great care in amplitude modulation is taken so as not to change the carrier frequency; conversely in frequency modulation great care is taken not to change the carrier amplitude.

Comparing the two modulating methods graphically as in Fig. 1, we have at A, a regular amplitude modulated envelope with which you are familiar. At B, we have a frequency modulated wave modulated by the same audio sine wave or signal as the wave at A. These graphs are of the same type—that is, amplitude of the carrier voltage is plotted vertically while the horizontal distances represent time. The audio wave form is perfectly obvious at A, as it determines the shape of the envelope. At B, however, for FM, the exact audio wave form is less obvious. Since the audio wave form is not clearly indicated in Graph B, we sometimes represent the frequency modulated wave in another way as at C. This curve (C of Fig. 1) is simply a graph of the frequency changes during modulation. Note in Fig. 1C that, as modulation progresses, the carrier actually changes in frequency, increasing to a maximum at  $f_2$  and decreasing to a minimum at  $f_1$ . The dotted base line  $f_0$  shows where the carrier would remain if there were no modulation. The frequency  $f_0$  is the "base" or assigned "mid-carrier" frequency—the frequency at which the transmitter is radiating energy when it is not modulated. Frequency  $f_1$  is a lower frequency and  $f_2$  is a higher frequency than the unmodulated value.

The sine wave or curve shown at C of Fig. 1 represents the manner in which the carrier frequency changes when modulated. Note that, as modulation progresses, the carrier frequency at first increases from  $f_0$  to  $f_2$  and then returns to  $f_0$  and continues reducing to  $f_1$  finally returning to  $f_0$  at time  $T_3$ , which is the end of one audio cycle. The values of  $f_1$  and  $f_2$  will be discussed later but for the time being suffice it to say that  $f_2$  is greater than  $f_0$  and  $f_1$  is less than  $f_0$  by the same amount. Although this graph shows carrier frequency (vertical) plotted against time (horizontal) the exact nature of the carrier frequency changes are obvious and this curve represents equally well the wave form of the modulating signal—a sine wave in this case.

The graph of Fig. 2 is of the same type as that of Fig. 1C but is intended to show the effect of various modulation amplitudes and modulation frequencies on the ultimate carrier. The vertical dimensions of this graph represent kilocycles deviation above (+) and below (-) the assigned or unmodulated carrier  $f_0$ . The horizontal distances are graduated in very short units of time; namely, milliseconds or thousandths of a second. Waves A, B and C all complete one cycle in 1 millisecond and hence are, therefore, 1000 cycle waves but are of three different amplitudes. If they complete 1 cycle in 1/1000 of a second, naturally they would complete 1000 cycles in 1 second. A of Fig. 2 is an audio wave of small amplitude,

B is of medium amplitude and C of larger amplitude. Notice carefully that amplitude or height of each wave in this case is not measured in voltage or current but in frequency deviation. Wave D completes 1/2 cycle in 2 milliseconds which would mean 1 cycle in twice this time or 4 milliseconds. Its frequency is, therefore, 1000/0.004 or 250 cycles. Its amplitude being 1/2 that of C causes just half of the frequency deviation of wave C, while the frequency deviation occurs just 1/4 as fast.

From this information, we see that the amplitude of modulation or degree of modulation expresses itself in frequency deviation—the larger the audio amplitude (amount of audio voltage) the greater the frequency deviation of the carrier and a strict proportionality is preserved with regard to amplitude and frequency of deviation—

that is, the ratio  $\frac{\text{cycles deviation}}{\text{audio volts}}$  is

always the same value or constant regardless of the value of the modulation frequency.

The modulation frequency expresses itself (in the frequency modulated system) simply as the number of times per second that the frequency changes. None of the alternations in any way affects the carrier voltage or ultimate power. When modulation ceases the carrier returns to its fixed frequency value and continues radiating at the same power. Fig. 1B clearly shows that the carrier voltage has a fixed maximum ampli-

Fig. 1 shows at A—amplitude modulated wave; at B—frequency modulated wave. C shows FM audio wave form. Fig. 2 shows effect of modulation amplitudes and frequencies on the carrier.

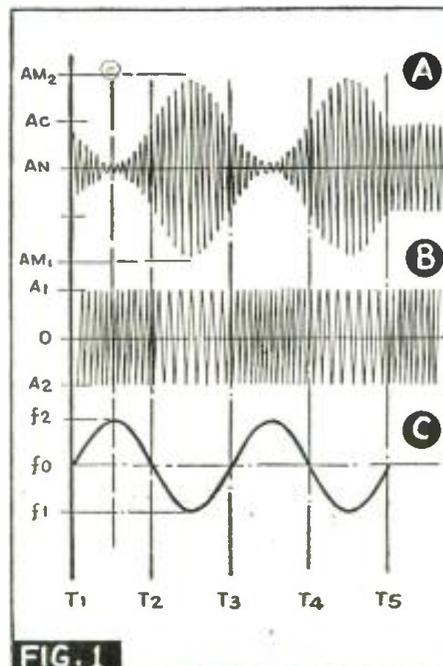


FIG. 1

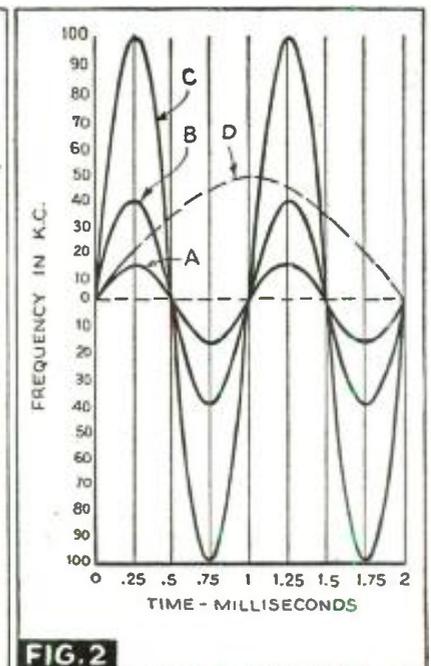


FIG. 2

\*President, Sprayberry Academy of Radio.

tude for each high frequency cycle at all times whether modulated (time T1 to T5) or unmodulated (time beyond T5).

Reactance Tube Method of Frequency Modulation

So far there have been two practical methods of FM used in transmitting circuits. These are: (1) varying the frequency of the master oscillator circuit and amplifying and multiplying this frequency until the desired carrier frequency deviation and power output has been achieved and (2) using a fixed frequency oscillator and varying the frequency by a special means in some following circuit and likewise amplifying and multiplying as above.

The first method mentioned makes use of a so-called "reactance tube" which we will consider in the following. Fig. 3 shows a practical circuit by which we may follow the action.

From our former studies, we know that the frequency of oscillation of the 6SJ7 oscillator is determined primarily by the values of the tank circuit units, L2-C4-C5. We recognize this fact from the familiar basic relationship of L, C and F in the formula:

$$F = \frac{1}{2\pi \sqrt{LC}}$$

Now for frequency modulation we must actually change the frequency of this tank circuit both slowly and quite rapidly—in fact from 30 or 40 times per second up to high audio frequencies—10,000 cycles or more per second. For periodic changes according to a fixed wave form this might conceivably be done mechanically with a motor-driven condenser or a motor-driven coupler associated with the coil, as we find this done in FM signal generators. To make these changes in frequency corresponding with amplitude changes in a voice wave, an entirely automatic and non-mechanical method must be employed. While it is true that we might place a condenser microphone across the tank circuit and let voice waves vary the capacity and thus the frequency, there are many practical limitations to this method.

The first practical method of making proper frequency changes in a circuit like that of Fig. 3 made use of a well known principle of the vacuum tube as will now be explained.

One of the main things which characterize an inductance is the fact that the voltage across it leads the current through it by a phase angle of nearly 90°. Any other electrical device regardless of its nature or construction which can exhibit these properties will act like an inductance to this extent at any rate. It may not fulfill all of the properties of inductance such as lower power factor, energy storage, etc., but it may be used in place of an inductance in circuits which require only the above mentioned properties.

There is no known way mechanically to vary the inductance value of a coil quickly. Therefore, we have to resort to a substitute inductance and the vacuum tube best fulfills this requirement.

Although no vacuum tube has these properties at any two terminals in ordinary use, we can force it to display these properties

to a satisfactory degree. Let us first examine the phase relations of a normally operated tube and then see how we can convert its operation so that its plate signal voltage will lead its plate signal current by nearly 90°. These phase relations are to be found in Fig. 4. As we have learned, the plate current (Ip) is in phase with the grid voltage (Eg) as clearly shown here. By "in phase" we simply mean that the grid voltage and plate current are maximum (most positive) at the same instant, and both are at minimum at the same instant. This is perfectly obvious at A in Fig. 4, and is an operating characteristic of circuits such as are shown at B and C of this figure. Now as the plate current of any amplifying tube increases, it means that the load current, in increasing, produces a higher voltage drop (across the load) in direct proportion to the plate current, and hence the voltage at the plate (Ep) is in opposite phase to the plate current. At the highest value of plate voltage the plate current is lowest.

This is true in amplifiers such as in circuits B and C, Fig. 4, because the plate load resistance in the first case has no effect on the plate voltage-plate current phase, while in the second case (C, Fig. 4) it is just as true at resonance because the impedance formed by C and L forms a pure resistance equivalent. Obviously, any external reactance would cause some phase change in the voltage-load current phase and these conditions as previously described would not be fulfilled.

It is quite obvious in Fig. 4 that the plate signal voltage is simply the amplified grid signal voltage—180° displaced—that is, the plate signal voltage is in reverse phase to the input grid signal voltage Eg.

To carry the thought of making a tube act like an inductance further suppose we simply disregard the plate voltage wave (Ep) at A in Fig. 4 and supply a different plate voltage signal directly to the 6L7 plate from an oscillator source as in Fig. 3. Note that the oscillator has no relation to the input grid of the 6L7 at all. The oscillator is also independent of the plate current of the 6L7 tube. The new plate signal voltage which we shall supply from the oscillator may be of any phase that we choose (with respect to the input grid of the 6L7 tube) and as we have seen, we want this voltage to lead the plate signal current (Ip) wave by 90° in order for the tube to exhibit inductive characteristics. By way of information we indicate a leading phase on a graph always by moving the wave to the left, and for 90°, it will be moved 1/4 cycle

360

to the left (because — = 90).

4

Of course, by now we have completely given up the idea that the 6L7 tube is intended to amplify. In this application we supply a signal to both the grid and plate and wish to make use of the reactance (inductive) properties of the tube rather than its amplifying qualities.

Refer to Fig. 3 again and note that the R.F. signal at the grid end of L2 is fed directly to the plate of the 6L7 modulator, but a blocking condenser C2 is used to prevent the D.C. applied to the 6L7 plate from being shorted to ground through I.2. The value of the blocking condenser C2 is 250 mmf, and it was chosen to have a very

For the nominal amount of 35c we will send you the following value:

1. One duo-tone imperishably etched Bronze Name Plate, size 3x1 1/2 inches with your Social Security number and name permanently stamped upon it.
2. One Genuine Leather Billfold, size 8 1/2 x 3 inches in natural brown color, with four compartments, as per illustration above.

This Pocketbook is our free present to you. Absolutely no strings of any kind. We make you this gift because we expect you to do us a favor by showing your name plate to your friends, to interest them in ordering one for themselves. That's all. Help us and you will profit yourself.

**ACT NOW!** Mail the coupon below and enclose 35c in coins. The bronze name plate and the Leather Billfold will be forwarded to you at once.

PREMIUM DISTRIBUTING SERVICE  
Wrigley Bldg., Chicago, Dept. RT-241  
Enclosed find 35c for which mail to the address below, my Social Security Bronze Plate and the Genuine Leather Billfold without extra cost, as per your offer.

My Social Security Number is .....

NAME .....

ADDRESS .....

CITY ..... STATE .....

**Do YOU want to be a Government radio operator?**  
Additional operators are needed NOW.

Why not learn to be an operator quickly and easily with the Ayres Automatic Code Machine all electric, 50,000 words, practice tapes available, low monthly rental.

TAPES FOR MAC AUTOS, RECORDING SLIPS AND RECORDING INKS

Write AYRES AUTOMATIC CODE MACHINES  
711 Boylston St., Boston, Mass.

small reactance as compared to the A.C. plate resistance of the 6L7 tube to prevent serious phase shift from the oscillator inductance L2 to the 6L7 plate. For example, the A.C. plate resistance of the 6L7 is given as greater than 1 megohm while the reactance of the 250 mmf. condenser at say 2000 KC. is approximately 350 ohms. The phase angle of a resistance and reactance in series is always "arctan (arc tangent or angle whose tangent is) X/R" expressed in the simplest terms. The numerical value of X/R by substitution, considering R to be 1 megohm, is 350/1,000,000 or .00035 which is the arctan of an angle very considerably less than 1/10th of 1 degree, a phase angle which can be entirely neglected. These values may be found in a regular trigonometric table of "natural tangents."

This simply means that the A.C. changes in the plate current of the 6L7 due to this plate signal are substantially in phase with the high frequency voltages applied to the plate from L2.

By means of R4 and the attendant network C3 and R5, the inner control grid of the 6L7 is also supplied with the high frequency voltage from the same point; namely, the top of coil L2. Analyzing this circuit, we find the inner-control-grid input capacitance of 7.5 mmf., to be in parallel with C3 which we will say is adjusted to 7.5 mmf. In parallel, these will total 15 mmf. These two capacities are in turn shunted by a .5 meg. resistor R5, and the group is in series with a 50,000 ohm resistor (R4).

First, we must note that the reactance of a 7.5 mmf. condenser at 2000 KC. is approximately 10,600 ohms.

In all of the work to follow, the accuracy is not intended to be better than 1/10th of 1% as only three significant figures are retained.

$$(1) \quad X_c = \frac{1}{2\pi FC}$$

$$X_c = \frac{1}{6.28 \times 2 \times 10^6 \times 7.5 \times 10^{-12}} = 10,600 \text{ ohms approx.}$$

Where:  $X_c$  is in ohms  
 $\pi = 3.14$  ( $2\pi = 6.28$ )  
 $F = 2,000,000$  cycles ( $2 \times 10^6$ )  
 $C = 7.5 \times 10^{-12}$  fd.

Now two condensers of equal capacity would have just half of this total reactance or  $10,600/2 = 5,300$  ohms. The impedance of these capacities with the 50,000 ohm resistor across them would be as expressed by the following formula:

$$Z = \frac{RX_c}{\sqrt{R^2 + X_c^2}}$$

which by substitutions equals—

$$Z = \frac{500,000 \times 5300}{(500,000)^2 + (5300)^2} = 5,299.7 \text{ ohms}$$

We must resort to mathematics to find the phase angle between the voltage across and current through this entire combination. However, the student familiar with such work can see at a glance that the phase angle is very nearly  $-90^\circ$ —that is, voltage lagging current. We will show the

method of arriving at the value without depending on estimation entirely.

From the geometry of the vectors forming these values we may obtain—

$$\tan \theta = \frac{R}{X}$$

Substituting values in the inverted expression—

$$\theta = \tan^{-1} \frac{R}{X} = \tan^{-1} \frac{500,000}{5,300}$$

$$\theta = \tan^{-1} \frac{500,000}{5,300} \quad \theta = \arctan \frac{R}{X} \text{ and read: Theta equals arc tangent minus R over X.}$$

$$\theta = \tan^{-1} 94.3 \quad \theta = \arctan 94.3$$

$\theta = 89^\circ 25'$  approximately (from table of natural tangents)

You could substitute the proper values in either the "sin" or "cos" functions, and by referring to complete tables of trigonometric functions, find the same angle; namely, nearly  $-89\frac{1}{2}$  degrees and hence very nearly  $-90^\circ$ .

From the above calculations, we find that there is no longer any reason to consider the 500,000 ohm resistor because it has an insignificant effect on the phase angle of the circuit. In other words, it changes the phase from  $-90^\circ$  (for a perfect condenser) to  $-89\frac{1}{2}$  degrees, an amount of phase shift which could not ordinarily be measured. From the A.C. viewpoint, we could, therefore, ignore the 500,000 ohm resistance R5 and simply consider the reactance. However, we are actually more interested in the

method than the answer, and so we shall continue the exact analysis.

Since the condenser-resistance combination which we have just studied is in series with another resistance, we may express their sum as—

$$(2) \quad Z_t = Z_1 + Z_2$$





Where:  $Z_t$  is the total impedance from the top of L2, Fig. 3 to ground,  $Z_1$  is 50,000 ohms and  $Z_2$  is 5,299.7 ohms.

The numerical addition of these two impedances is a complicated procedure but is relatively easy to follow even if you are not familiar with the mathematical principles.  $Z_1$  is a pure resistance, and of course, has no phase angle. On the other hand,  $Z_2$  has a resistance element R5 and a reactance element X (of C3) and that part of it which is a pure reactance has a phase angle of  $-90^\circ$  or is at right angles electrically to the resistance part which, of course, has an angle of  $0^\circ$ . In other words, we may consider the condenser-resistance combination to be made up of two series elements as well as these parallel elements. These must be expressed as though they were in series in order to add the two impedances. The facts that we have at hand are the impedance value (5,299.7) and the phase angle ( $-89^\circ 25'$ ). These two completely describe the impedance when written as—

5,299.7  $\angle -89^\circ 25'$  and read 5,299.7 phase minus 89 degrees 25 minutes.

The equivalent series circuit which would be identified exactly as above would have a resistance and condenser in series. The resistance element is found by multiplying

Fig. 3—"reactance tube" FM modulator. Fig. 4—diagrams used to explain FM action. Fig. 5—curve showing voltage lagging the current.

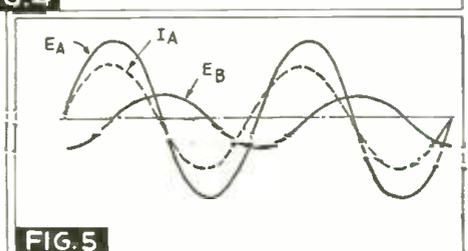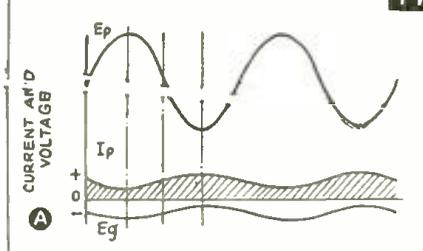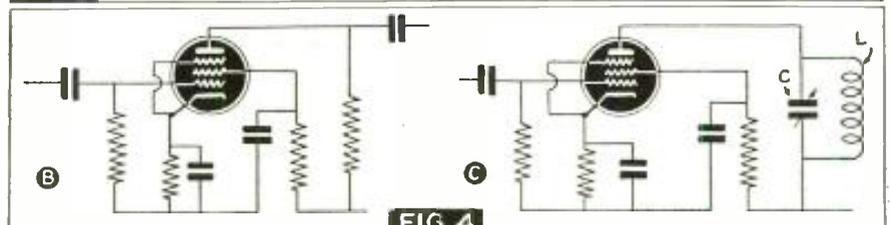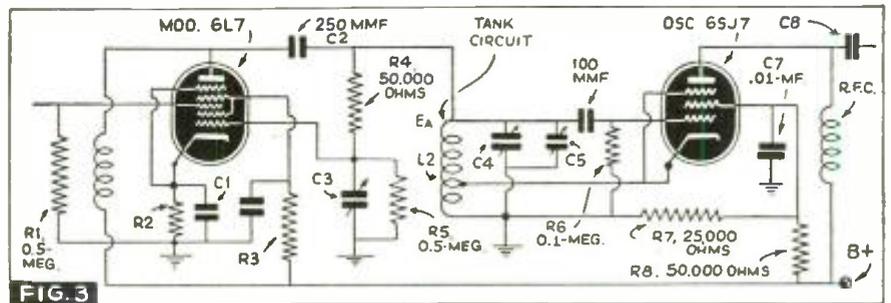

The theory behind the operation of this unit is not at all difficult to understand. You will notice that the grid return is  $22\frac{1}{2}$  volts minus, with respect to the filaments of the tube. If the photo-cell were pulled out, this negative voltage on the grid of the tube would be sufficient to cause plate current cut-off. However, with the photo-cell tube in its socket, we find that there is a grid return path, through the photo-cell tube to plus "B" also. Photo-cells have a characteristic similar to a resistor and when light falls on the cathode surface the resistance effect changes, depending upon the amount of light that reaches it. This means that more or less plus voltage gets onto the grid of the tube, as the light is varied, and the plus voltage bucks the negative voltage already there. Therefore the net negative voltage on the grid is lowered, causing plate current to flow and pull down on the relay armature. The 3 megohm potentiometer is varied until the proper action is obtained with the amount of light you are using.

Many circuits have appeared for A.C.-D.C. operation in the past. This unit will find application where portability is required. It isn't necessary to use as large an "A" and "B" battery as is shown in the photograph, as long as the "B" battery used has a  $22\frac{1}{2}$  volt tap.

There isn't much to putting this little unit together, as you can see. The chassis is only 4" x 2" x 2" but you can make it any size you prefer. A chassis like the one used in this model can be purchased already formed and punched. If a chassis as small as this is used it will be necessary to mount all parts except the relay and finish the wiring up to the relay, leaving leads just long enough to mount and wire the relay afterwards.

The sensitivity control has a screw-driver slot on the shaft. A three-crew terminal strip is mounted on the back of the chassis. The center terminal is wired to the armature of the relay and the two outside terminals are each connected to one of the contacts. In this way you have a choice of a "normally open" or "normally closed" relay control circuit.

Since the greatest change in light gives the surest action, it is important that no extraneous light be permitted to fall on the photo-cell. It is a good idea to build a light tight box to fit over the entire photo-cell relay unit. Cut a hole about  $1\frac{1}{2}$ " in diameter on the side just in front of the photo-cell. If a lens whose focal length is equal to the distance between the opening and the photo-cell is mounted over the opening, still better action will result.

The light used should, if possible, be in the form of a concentrated beam which may be secured by means of reflectors or lenses. A 32 candle-power automobile headlight bulb makes a good light source. It can be operated from a storage battery or 6 volt step-down transformer. However, even a good flashlight will work.

List of Parts

- 1—Adjustment control, 3 megohms
- 1—Knight S.P.D.T. relay, 5000 ohms
- 2—4-prong sockets
- 1—G.M. photo cell
- 1—Knight type 31 tube
- 1—3 megohm,  $\frac{1}{2}$  watt resistor
- 3—feet 4-wire cable
- 1—3-lug terminal strip
- 1—Drilled chassis base
- 1—"A" battery,  $1\frac{1}{2}$  volts
- 2—"B" batteries, 45 volts
- 2—"B" battery plugs
- Miscellaneous hardware

# 10 BEST RADIO BOOKS 10¢ ea.

RADIO FANS EVERYWHERE—these fine ten cent text books give you an excellent foundation for the study of RADIO. They are clearly written, profusely illustrated and contain over 15,000 words in each book. You'll be

amazed at the wealth of information contained in these handy books. Excellent for reference—ideal for every technical library. YOUR MONEY BACK if you are not satisfied. PROMPT SHIPMENTS



**No. 1**  
**HOW TO BUILD FOUR DOERLE SHORT WAVE SETS**  
Thousands of radio fans have built the famous DOERLE Short Wave Radio Receivers. So insistent has been the demand for these receivers, as well as construction details, that this book has been specially published. Contains EVERYTHING that has ever been printed on these famous receivers.



**No. 2**  
**HOW TO MAKE THE MOST POPULAR ALL-WAVE 1- and 2-TUBE RECEIVERS**  
This book contains a number of excellent sets, some of which have appeared in past issues of RADIO-CRAFT. These sets have been carefully engineered. They are not experiments. Not only are these sets described in this book, but it contains all of the illustrations, hookups, etc.



**No. 3**  
**ALTERNATING CURRENT FOR BEGINNERS**  
This book gives the beginner a foothold in electricity and Radio. Electric circuits are explained. Ohm's Law, one of the fundamental laws of radio, is explained; the generation of alternating current; sine waves; the units—volts, amperes, and watts are explained. Condensers, transformers, A.C. instruments, motors and generators.




**No. 4**  
**ALL ABOUT AERIALS**  
This book explains the theory underlying the various types of the inverted "L," the Doublet, the Double Doublet, etc. It explains noise-free reception, how low-impedance transmission lines work; why transposed lead-ins are used. It gives in detail the construction of aerials suitable for long-wave broadcast receivers, for short-wave receivers and for all-wave receivers.



**No. 5**  
**BEGINNERS' RADIO DICTIONARY**  
Are you puzzled by radio language? Can you define Frequency? Kilocycle? Tetrode? Screen grid? Baffle? Anode? Triode? Pole? Ionization? Doude's Law? Harmonic? Gravity Cell? If you cannot define these very common radio words, and dozens of other, more technical, terms used in all radio magazines and instruction books, you need this book in your library.



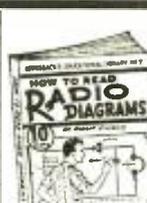**No. 6**  
**HOW TO HAVE FUN WITH RADIO**  
Stunts for parties, practical jokes, scientific experiments and other amusements which can be done with your radio set are explained in this fascinating volume. It tells how to make a newspaper talk—how to produce silent music for dances—how to make visible music—how to make a "silent radio" unit—how to make toys which dance to radio music, etc., etc.



**No. 7**  
**HOW TO READ RADIO DIAGRAMS**  
All of the symbols commonly used in radio diagrams are presented in this book, together with pictures of the apparatus they represent and explanations giving an easy method to memorize them. This book by Robert Eichberg, the well-known radio writer and member of the editorial staff of RADIO-CRAFT Magazine, also contains two dozen picture-writing diagrams of simple radio sets that you can build.



**No. 8**  
**RADIO FOR BEGINNERS**  
Hugo Gernsback, the internationally famous radio pioneer, author and editor, whose famous magazines, RADIO AND TELEVISION and RADIO-CRAFT are read by millions, scores another triumph with this new book. Any beginner who reads it will get a thorough ground work in radio theory, clearly explained in simple language, and through the use of many illustrations. Analogies are used to make the mysteries of radio clear.



**No. 9**  
**SIMPLE ELECTRICAL EXPERIMENTS**  
Over 100 interesting and practical electrical experiments are described in this book, covering every branch of electricity—from simple experiments with magnets to high frequency "stunts." All of the experiments described can be carried out with simple apparatus, most of which can be found about the home.



**No. 10**  
**TELEVISION**  
Every one is asking the question: How does television work? This book explains all of the different systems of television from the simplest to the most complex. It describes in A-B-C style just how the image is scanned, how the scene is picked up by the television camera and broadcast to your home, etc. Various types of television systems are described.

BOOKS ARE ALL UNIFORM

Every book in the GERNSBACK EDUCATIONAL LIBRARY has 32 pages—with illustrations varying from 30 to 60 in number. Each title volume contains over 15,000 words. Positively radio's greatest book buys! If you do not think these books worth the price asked, return them in 24 hours and your money will be instantly refunded.

RADIO PUBLICATIONS • 20 VESEY STREET • NEW YORK, N. Y.

RADIO PUBLICATIONS, Dept. RT-241  
20 VESEY STREET, NEW YORK, N. Y.  
Gentlemen: Please send immediately, POSTPAID, the book numbers circled below, I am enclosing ..... cents—each book being 10c.

1    2    3    4    5    6    7    8    9    10  
NEW    NEW

Send FREE listing of 48 new 10c publications.

Name ..... Address .....

City ..... State .....

Remit by check or money order—register letter if you send cash or unused U. S. postage stamps.

**MAIL COUPON TODAY!**



# ELEMENTARY MATHEMATICS

EASY — SIMPLIFIED — PRACTICAL

**H**ERE is a book for the business man, the technician and craftsman explaining and answering every operation and meaning with interpreting illustrations and examples. It is the key to a simple understanding of many perplexing problems in daily life. In clear, positive and definite language, the author popularizes and clarifies every subject and helps the reader to overcome any apparent difficulty in the study of mathematics. A real home study-course in mathematics for the student or the man who wants to achieve proficiency or desires to brush-up on his knowledge.

Entire Chapter on Special Mathematics for the Radio Technician

### CONTENTS OF BOOK

- CHAPTER I. Arithmetic—Addition—Subtraction—Multiplication—Division.
- CHAPTER II. Factoring and Cancellation—Fractions—Decimals—Percentage—Ratio—and Proportion.
- CHAPTER III. The Metric System.
- CHAPTER IV. How to Measure Surfaces and Capacity (Geometry).
- CHAPTER V. Powers and Involution—Roots and Evolution.
- CHAPTER VI. Mathematics for the Manual and Technical Craftsman—Thermometers—Conversions—Graphs or Curve Plotting—Logarithms—Use of the Slide Rule.
- CHAPTER VII. Special Mathematics for the Radio Technician.
- CHAPTER VIII. Commercial Calculations—Interest—Discounts—Short Cut Arithmetic.
- CHAPTER IX. Weights and Measures—Useful Tables.

ONLY 50c POSTPAID

"Elementary Mathematics" can be carried readily in your pocket. Send Stamps, Cash or Money Order.

## TECHNIFAX

1917 S. State St. RT-241 Chicago, Ill.

FREE

300 Ways to Make Money



68 PAGES

BRAND NEW BOOK 40,000 WORDS in TEXT! In "CASH IN" you get ALL the real money-makers—dozens of profitable tested mail order plans, confidential business secrets, dozens of practical tested formulas, successful tested schemes—actual experiences of men who have started on a shoestring—with less than \$10 capital.

### Buyers of This Book Tell Us—

"Biggest value I've yet to see. Book is worth at least a dollar." S. Budo, B'klyn, N. Y.  
 "Your book is as good if not better than others selling at \$1.00." George Brunet, Montreal, Can.  
 "CASH IN is the best value I have yet to see in the mail order field." Lawrence Fox, Brooklyn, N. Y.  
 "CASH IN" contains only tested ideas covering every type of full- or spare-time enterprise—it's a "master-piece" in business ventures.


BOOK CONTAINS NO ADVERTISING GIVEN FREE TO YOU AS A SAMPLE TO INDUCE YOU TO SELL THIS BOOK AT A PROFIT Send 3c U. S. stamp to pay for mailing charges

NATIONAL PLANS INSTITUTE  
 248-T Fifth Ave., N.Y.C.

### TRANSFER YOUR 1940 MAGAZINES INTO A

"JIFFY"

### Magazine Binder

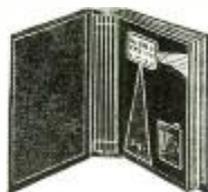

Sturdily built and covered with black fabricoid. Has two stamped metal ends with 12 spring wire separators. Magazines can be inserted and removed in a jiffy. No fuss—no lost time—no labor.

- No. 1. 12" x 9 1/2", with 2-inch back for Radio-Craft, R.&T., Radio News, etc. \$1.50
- No. 2. 10 1/2" x 7 1/2", with 3-inch back for QST, Radio, Popular Mechanics, etc. \$1.25
- No. 3. 8 1/2" x 6 1/2", with 3-inch back for Reader's Digest, etc. \$1.00


P.P. Prepaid in U.S. and Canada

GOLD SHIELD PRODUCTS  
 Dept. RT-241, 350 Greenwich Street, New York City
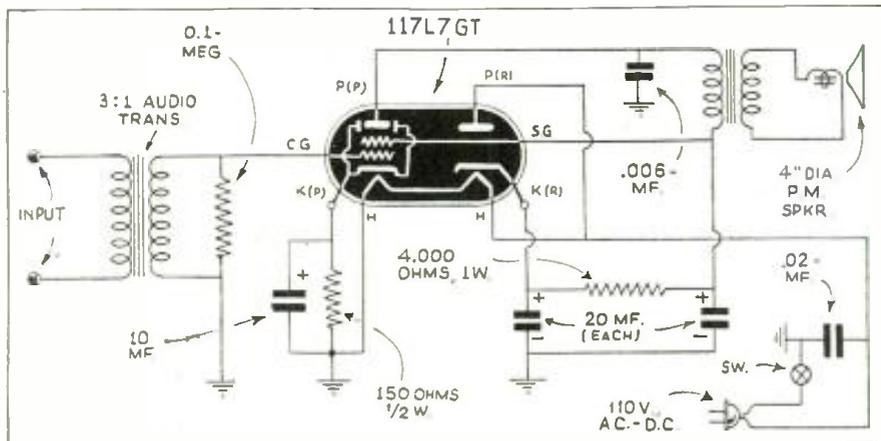
# Diagrams of Interest


This is a new department. If you have a new Hook-Up, send it along; a pencil diagram will do. Be sure to include a brief description.

All diagrams and descriptions accepted and published will be paid for at regular space rates. Diagrams may be for receivers, adapters, amplifiers, etc. Send them to Hook-Up Editor, RADIO & TELEVISION, 20 Vesey St., New York City.




**ONE TUBE AMPLIFIER:** This one-tube audio amplifier submitted by Homer L. Davidson, Fort Dodge, Iowa, can be used with one and two tube receivers as well as crystal sets. This circuit will appeal to many radio beginners as it operates directly from the lighting circuit. The small PM speaker can be picked up cheaply and the cost of the other parts is very nominal.

### Cover Feature

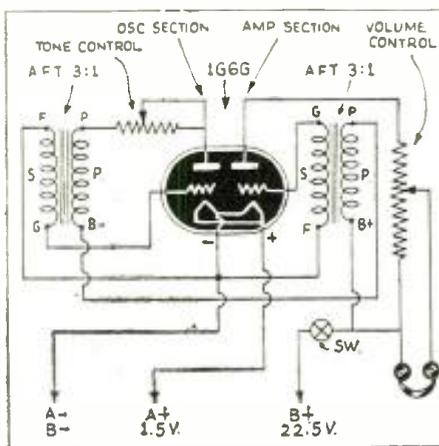


**CODE PRACTICE OSCILLATOR:** As many radio-minded fellows are now feverishly studying the radio code signals, they will be interested in this simple and flexible code oscillator, contributed by Robert Jacobson, Washington, D. C.

### PHONO OSCILLATOR

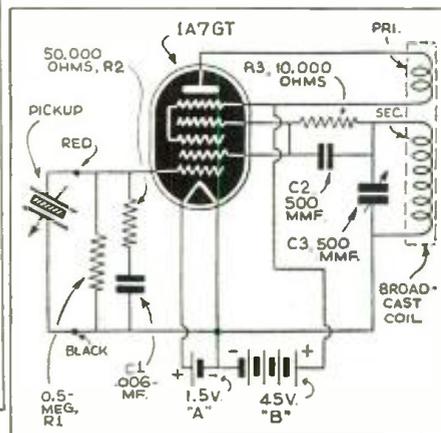

This phono oscillator, which may be used with portable phonographs, may be battery-operated as shown. It was contributed by Daniel Teitler, Bronx, N. Y.


## WHAT'S WRONG WITH THIS DIAGRAM?

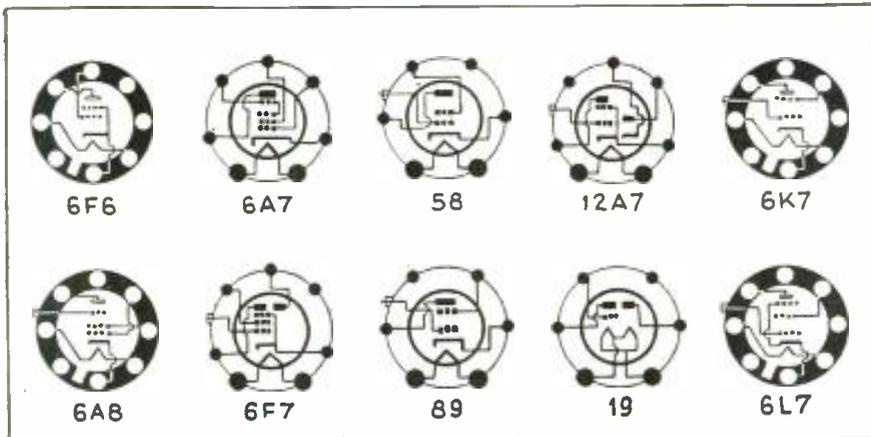

Be honest with yourself and study the diagrams above for at least 3 minutes before turning to the answers on page 640.

# to the Radio Experimenter


## 6-TUBE, 2-BAND RECEIVER FOR A.C.-D.C.

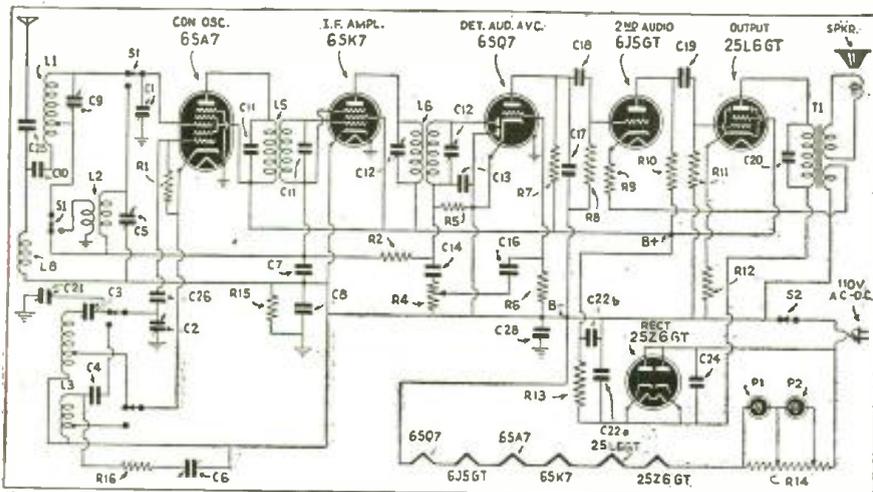

The diagram shown above is for a G.E. Co. 110 volt A.C.-D.C. superhet for shortwave and broadcast band operation. The values of the various condensers and resistors are given below. The I.F. is 455 kc. and the speaker is a 6 1/2-inch PM type.

Symbol	Description	Symbol	Description	Symbol	Description
C-1	Antenna section tuning condenser	C-16	.02 mfd. paper capacitor	L-8	1 1/2 in. antenna choke
C-2	Oscillator section tuning condenser	C-17	220 mmf. mica capacitor	P-1	1141 lamp, Mazda No. 44
C-3	"B" band ladder	C-18	.005 mfd. paper capacitor	P-2	1141 lamp, Mazda No. 44
C-4	5900 mmf. mica capacitor ±5%	C-19	.005 mfd. paper capacitor	R-1	33,000 ohms carbon resistor
C-5	2-20 mmf. "D" band antenna trimmer	C-20	.01 mfd. paper capacitor	R-2	2.2 megohms carbon resistor
C-6	2-20 mmf. "D" band oscillator trimmer	C-21	2-15 mmf. "B" band oscillator trimmer	R-3	2.2 megohms volume control
C-7	.05 mfd. paper capacitor	C-22a	50 mfd. 150 V. dry electrolytic	R-4	470,000 ohms carbon resistor
C-8	0.1 mfd. paper capacitor	C-22b	30 mfd. 150 V. dry electrolytic	R-5	15 megohms carbon resistor
C-9	2-15 mmf. "B" band antenna trimmer	C-23	.05 mfd. paper capacitor	R-6	470,000 ohms carbon resistor
C-10	.01 mfd. paper capacitor	C-24	.01 mfd. paper capacitor	R-7	470,000 ohms carbon resistor
C-13	470 mmf. mica capacitor	C-25	37 mmf. mica capacitor	R-8	1.9 megohm carbon resistor
C-14	.002 mfd. paper capacitor	C-26	0.1 mfd. paper capacitor	R-9	3300 ohms carbon resistor
		L-1	Beam-a-Scope	R-10	39,000 ohms carbon resistor
		L-2	"D" band antenna coil	R-11	470,000 ohms carbon resistor
		L-3	Oscillator coil	R-12	150 ohms carbon resistor
		L-5	1st I.F. transformer	R-13	100 ohms carbon resistor
		L-6	2nd I.F. transformer	R-14	HL-42-D ballast resistor
				R-15	170,000 ohms carbon resistor
				R-16	100 ohms carbon resistor
				T-1	Output transformer

## COMBINATION R.F. AND A.F. AMPLIFIER

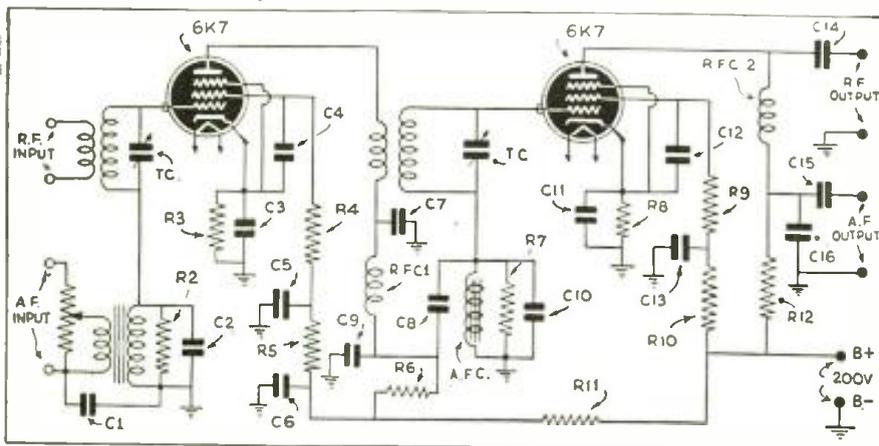

Frank H. Tooker of East Orange, N. J., sent us this diagram. The values of the various condensers and resistors are as follows:

C1=0.1 mf.	C11=0.1 mf.	R5=50,000 ohms	R9=10,000 ohms
C2=.0001 mf.	C12=.01 mf.	R6=20,000 ohms	R10=50,000 ohms
C3=.01 mf.	C13=.01 mf.	R7=100,000 ohms	R11=20,000 ohms
C4=.01 mf.	C14=.00025 mf.	R8=2000 ohms	R12=20,000 ohms
C5=0.1 mf.	C15=.01 mf.		
C6=1.0 mf.	C16=.001 mf.	AFT=audio frequency transformer, ratio 3:1	
C7=.0001 mf.	R1=100,000 ohms	AFC=audio frequency choke, 700 henries	
C8=.01 mf.	R2=100,000 ohms	RFC-1 and RFC-2=R.F. chokes, 25 m.h.	
C9=.001 mf.	R3=2000 ohms	T.C.=tuning condensers, ganged	
C10=.0001 mf.	R4=10,000 ohms		

# RADIO AMATEUR COURSE

By **G.W. Shuart W2AMN**

RADIO AMATEUR COURSE

**SHORT WAVE TELEVISION**

PRICE 50¢

PUBLISHED BY SHORT WAVE and TELEVISION MAGAZINE, NEW YORK.

### Your Money Back—

If the RADIO AMATEUR COURSE does not represent the greatest book value ever offered to the radio "fans" **50c** for .....

To convince you that there isn't a better book buy today, the publishers of the RADIO AMATEUR COURSE make the sensational offer of a money-back guarantee on such a low-priced book. Stop in at any of the many dealers handling this book and examine it. See for yourself if the RADIO AMATEUR COURSE isn't just the book you've always wanted.

Printed on the finest coated paper—well illustrated attractive 4-color cover—complete with radio information you must have. It contains a step-by-step program for obtaining a short-wave radio education.

Written by **GEORGE W. SHUART, W2AMN**, foremost short-wave authority

**148 PAGES**  
6 1/4 x 9 1/2 INCHES  
OVER 150 RADIO DIAGRAMS  
and TECHNICAL PHOTOGRAPHS

**RADIO AND TELEVISION**  
20 Vesey Street New York, N. Y.

See Page 624 for list of our dealers.

**RADIO AND TELEVISION**  
20 Vesey Street, New York, N. Y.

Gentlemen: I enclose herewith my remittance of Fifty Cents (50c) for which please send me POSTPAID, my copy of the RADIO AMATEUR COURSE. (Remit by check or money order; register letter if you send cash or unused U. S. Postage stamps.)

Name .....

Address .....

City ..... State ..... R&T-2-41

# ... THESE OUTSTANDING SHORT WAVE BOOKS ARE Now Available AT YOUR DEALER!

YOU buy parts, tubes, kits, accessories from your local radio dealer—that's what countless thousands of short-wave fans do. Now through a nation-wide distribution service our numerous books are available at your favorite radio dealer—right where you buy other radio equipment. It's more convenient, saves time and you can inspect the books before you buy. Ask your dealer to show you all the books advertised on this page—they're always in stock.



### HOW TO BUILD AND OPERATE SHORT WAVE RECEIVERS

This is the best and most up-to-date book on the subject. It is edited and prepared by the editors of RADIO & TELEVISION and contains a wealth of material on the building and operation, not only of typical short wave receivers, but short wave converters as well.  
150 Illustrations  
78 Pages

### 101 SHORT WAVE HOOK-UPS


Compiled by the Editors of  
RADIO & TELEVISION

Here is a worthwhile book that every short wave listener, every short wave fan, and every short wave amateur has wanted for a long time. It gives you the 101 best short wave hook-ups which have appeared heretofore.  
100 Illustrations  
72 Pages

50c



50c

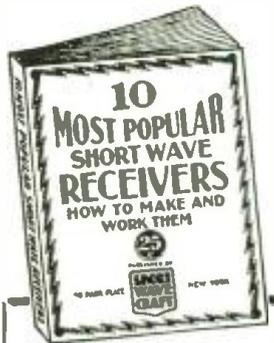

### TEN MOST POPULAR SHORT WAVE RECEIVERS

HOW TO MAKE AND WORK THEM  
The editors of RADIO & TELEVISION have selected ten outstanding short wave receivers and these are described in the new volume. Each receiver is fully illustrated with a complete layout, pictorial representation, photograph of the set complete, hook-up and all worthwhile specifications.  
75 Illustrations  
40 Pages


25c



### HOW TO GET BEST SHORT WAVE RECEPTION

M. HARVEY GERNSBACK tells you everything you have ever wanted to know about short wave reception. The author, a professional radio listener and radio fan for many years, gives you his long experience in radio reception and all that goes with it.  
40 Illustrations  
72 Pages

50c

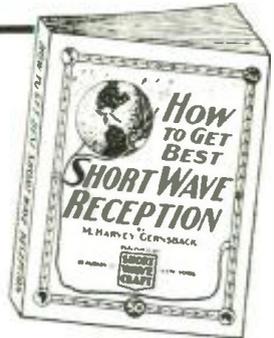

### HOW TO BECOME AN AMATEUR RADIO OPERATOR

By Lieut. Myron F. Eddy, whose experience in the amateur field has made him pre-eminent in this line.

If you intend to become a licensed code operator, if you wish to take up phone work eventually—this is the book you must set.

150 Illustrations  
72 Pages


50c



### THE SHORT WAVE BEGINNER'S BOOK

Here is a book that solves your short wave problems—leading you in easy stages from the simplest fundamentals to the present state of the art as it is known today. It is the only low-priced reference book on short waves for the beginner.  
75 Illustrations  
40 Pages

25c

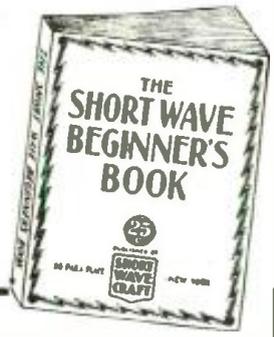

### LOOK FOR YOUR NEAREST DEALER

For convenience the publishers list below dealers in all parts of the world where our books are available. On your next shopping trip be certain to examine these volumes. You're sure to want them for your technical library.

- ALABAMA**  
Walther Bros., Montgomery
- ARIZONA**  
Sem's Cigar Store, Phoenix
- CALIFORNIA**  
Electric Supply Co., Oakland  
Radio Supply Company, Los Angeles  
Radio Television Supply Co., Los Angeles  
Pacific Radio Exchange, Inc., Los Angeles  
Western Auto Supply, Los Angeles  
Scott Wholesale Radio Co., Long Beach  
Vroman's Book Store, Pasadena  
Western Radio & Elec. Co., San Diego  
Scott Wholesale Radio Co., Long Beach  
Grenbach Electric Co., San Francisco  
Technical Book Co., San Francisco  
Zack Radio Supply Co., San Francisco  
Radio Specialties Co., San Jose
- COLORADO**  
Interstate Radio Supply, Denver
- CONNECTICUT**  
The Edward P. Judd Co., New Haven
- DELAWARE**  
Wilmington Elec. Spec. Co., Inc., Wilmington
- FLORIDA**  
Radio Accessories Co., Orlando
- GEORGIA**  
Radio Wire Television, Inc., Atlanta
- ILLINOIS**  
Allied Radio Corporation, Chicago  
Walter C. Braun, Inc., Chicago  
Chicago Radio Apparatus Co., Chicago  
A. C. McClurg & Co., Chicago  
Midwest Radio Mart, Chicago  
Newark Electric Co., Chicago  
Sears, Roebuck & Co., Chicago  
Max Stein & Co., Chicago  
Montgomery Ward & Co., Chicago  
Radio Wire Television, Inc., Chicago
- INDIANA**  
Van Sickle Radio, Indianapolis
- MASSACHUSETTS**  
DeWolfe & Fiske Co., Boston

- The Personal Book Shop, Boston  
Radio Wire Television, Inc., Boston  
Library Book House, Springfield  
Tremont Elec. Supply Co., Boston
- MICHIGAN**  
Risat Brothers, Detroit
- MINNESOTA**  
St. Paul Book & Stat. Co., St. Paul
- MISSOURI**  
Burstein-Applebee Co., Kansas City  
Radio Labs., Kansas City  
Walter Ashe Radio Co., St. Louis  
Van Sickle Radio Co., St. Louis
- NEBRASKA**  
Radio Accessories Company, Omaha
- NEW JERSEY**  
Radio Apparatus Co., Newark  
United Radio Co., Newark  
Radio Wire Television, Inc., Newark
- NEW YORK**  
Fort Orange Radio Dist. Co., Albany  
Radio Wire Television, Inc., Bronx  
Radio Wire Television, Inc., Jamaica, L. I.  
Harrison Radio Co., New York City  
Baker & Taylor Co., New York City  
Blair, the Radio Man, New York City  
David Botten & Co., New York City  
Eagle Radio Co., New York City  
Federated Purchaser, Inc., New York City  
Radio Circular Co., New York City  
G. E. Stechert & Co., New York City  
The Steiger Co., New York City  
Sun Radio Co., New York City  
Terminal Radio Corp., New York City  
Thor Radio Corp., New York City  
Try-Mo Radio Co., New York City  
Van Renssdyck Book Stores, New York City  
Radio Wire Television, Inc., New York City  
R. W. Wilson Co., New York City  
United Radio, Inc., Rochester  
M. Schwartz & Son, Schenectady
- OHIO**  
News Exchange, Akron  
United Radio, Inc., Cincinnati  
College Book Exchange, Toledo

- OREGON**  
J. K. Gill Co., Portland
- PENNSYLVANIA**  
The 437 Store, Philadelphia  
M & H Sporting Goods Co., Philadelphia  
Radio Electric Service Co., Philadelphia  
Cameradio Co., Pittsburgh
- UTAH**  
Radio Supply, Inc., Salt Lake City
- WASHINGTON**  
Seattle Radio Supply Co., Seattle  
Wedel Co., Inc., Seattle
- ARGENTINA**  
Radio Revista, Buenos Aires
- AUSTRALIA**  
McGill's Authorized Agency, Melbourne
- BELGIUM**  
Emil Arens, Brussels
- CANADA**  
T. Eaton & Co., Winnipeg, Man.  
Electrical Supplies, Ltd., Winnipeg, Man.  
Wholesale Radio Supply, Winnipeg, Man.  
Canadian Electrical Supply Co., Ltd., Toronto, Ont.  
Radio Trade Supply Co., Ltd., Toronto, Ont.  
Wholesale Radio Co., Ltd., 1133-35 Bay St., Toronto, Ont.  
Canadian Electrical Supply Co., Ltd., Montreal, P. Q.
- BRAZIL**  
Agencia Soave, Sao Paulo
- CHINA**  
China News Co., Shanghai  
International Booksellers, Ltd., Shanghai
- ENGLAND**  
Gorringer's Amer. News Agency, London
- FRANCE**  
Toute La Radio, Paris
- GERMANY**  
Fehr G.M.B.H. SW15, Berlin NW No. 7
- HOLLAND**  
Radio Peeters, Amsterdam, Z.

- INDIA**  
Empire Book Mart, Bombay
- MEXICO**  
American Book Store, Mexico, D. F.  
Central De Publicaciones, S. A., Mexico, D. F.  
Jaques Salvo, Mexico, D. F.
- NEW ZEALAND**  
Johns, Ltd., Auckland  
James Johnston, Ltd., Dunedin  
Te Aro Book Dept., Ltd., Wellington
- SOUTH AFRICA**  
Technical Book Co., Cape Town  
Central News Agency, Johannesburg  
International House, Johannesburg  
South African Radio Publications, Johannesburg

IF YOUR DEALER DOES NOT CARRY THESE BOOKS, ORDER DIRECT FROM US. FILL OUT COUPON BELOW. SHIPMENT WILL BE MADE IMMEDIATELY.

**POPULAR BOOK CORP.** R&T-2-41  
20 Vesey Street, New York City.

Gentlemen: I enclose herewith my remittance for \_\_\_\_\_ for which please send me the following books:

.....

Name .....

Address .....

City .....

State .....

(Send remittance in form of check or money order. If letter contains cash or unused U. S. postage stamps, register it.)

Edited by Herman Yellin, W2AJL

Short-Wave Receiver

Please publish a diagram of a short-wave receiver, using a 6K7, 6C5 and a 6F6 tube.—S. Kalista, Coaldale, Pa.

A. Shown here is a 4 tube T.R.F. receiver answering your specifications. Either 6K7 or 6SK7 tubes may be used in the R.F. and detector circuits. Condensers C-1 and C-3 are 35 mmf. tuning condensers, while C-2 and C-4 are 100 mmf. band-setting condensers. The coils can be any two-winding, all-wave plug-in

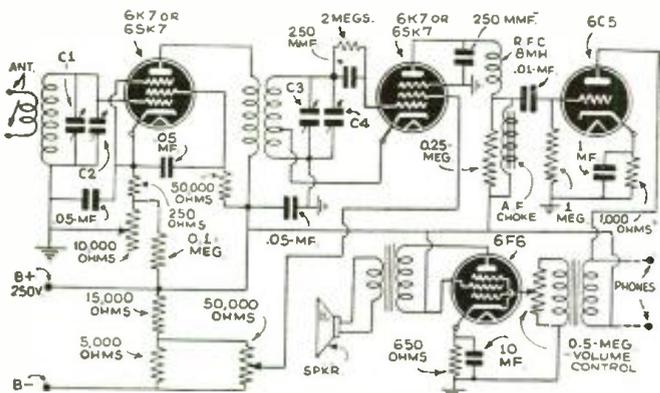


Diagram for 4-tube T.R.F. receiver of the regenerative type. No. 1246.

coils. The detector grid coil is tapped about 20 percent of its length above ground. If it is desired to use phones, they may be connected across the primary of the interstage audio transformer. Use an output transformer having a primary impedance of about 4000 ohms. The audio choke in the plate circuit of the detector is one of the 500 henry low-current types of chokes.

Eliminating Ignition Noises

How can I eliminate ignition noises picked up by the antenna lead-in on my auto radio?—L. Morosic, McCook, Nebraska.

A. The antenna lead-in—that is the connection from the antenna proper to the receiver, can and should be shielded by using low capacity cable. This is similar to ordinary shielded wire except for the much greater thickness of the cable caused by the increased space separating the inner conductor and the outer shield braid. This outer braid should be well grounded at the receiver end, while the inner wire is connected to the antenna terminal post of the receiver.

Regeneration Receiver Trouble

I recently completed the receiver described on page 22, volume 2, of the Gernsback Educational Library. I am using a type 36 tube instead of the one diagrammed and incorporating an A.C. power-supply. However, the set appears to be insensitive and no oscillation can be obtained.—H. S. Emigh, Jackson, Miss.

A. The most common cause of lack of regeneration and non-oscillation in regenerative receivers is a reversed tickler winding. Always try reversing the two leads to the tickler or plate winding. We would also suggest, if you have not already done so, to use a 15,000 or 25,000 ohm control in series with the cathode for controlling volume, instead of the filament control shown in the original set. Either ground one side of the filament or ground the center tap of the filament winding.

Space Charge

What is meant by the space charge of a vacuum tube and what effect has it on the operation of the tube?

A. Not all the electrons emitted by the cathode or filament of a vacuum tube are attracted to the plate. Some of them, having low velocities, remain bunched up around the cathode and act as a screen, lowering the plate current; that is, causing a plate current lower than would result if there were no space charge. These electrons around the cathode keep falling back on the cathode, giving way to other low velocity electrons which also remain near the cathode, only, in turn to be drawn back to the cathode. Increasing the plate voltage, will, of course, reduce the space charge effect for a given filament temperature.

Time Signals

Is there any meaning or code to the signals preceding the sending out of the time signal or dash at the exact hour?

A. The time signal, as transmitted by American Naval stations, begins at five minutes before the hour. It consists of the transmission of a dot for every second, omitting the dot at the following seconds:—

- 29, 51, 56, 57, 58, 59 during the first minute
- 29, 52, 56, 57, 58, 59 during the second minute.
- 29, 53, 56, 57, 58, 59 during the third minute.
- 29, 54, 56, 57, 58, 59 during the fourth minute.
- 29, 51, 52, 53, 54, 55, 56, 57, 58, 59 during the fifth minute.


At the end of the 60th second of the fifth minute, a one second dash is sent, the beginning of which is the time signal.

NAA at Arlington, Virginia, sends time signals almost every hour on a number of frequencies. Their schedule follows. Time is GMT, using the 24 hour clock.

- 113 kc. at 1, 2, 3, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 17, 18, 19, 20, 21, 22, 23 and 24 o'clock.
- 4390 kc. at 2, 3, 8, 9, and 10 o'clock.
- 9425 kc. at 2, 3, 4, 5, 6, 7, 8, 9, 10, 13, 14, 15, 16, 17, 19, 20, 21 and 22 o'clock.
- 12,630 kc. at 2, 3, 8, 9, 10, 14, 15, 20, 21, 22 o'clock.
- 17,370 kc. at 14, 15, 20, 22, and 21 o'clock.

Short-Wave Converter

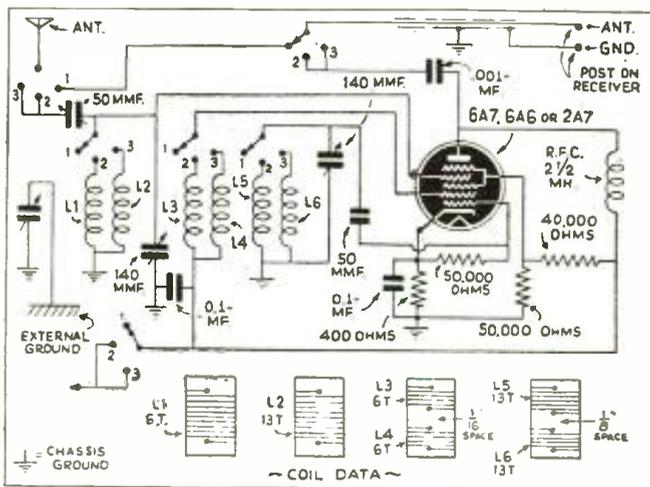Can you send me more detailed information on the converter shown on page 648 of the March issue?—E. S. Iwasko, Lansing, Mich.




Hook-up of short-wave converter, together with coil data. The different coils covering the various short wave-bands are switched into circuit by a ganged switch, in the manner made clear in the diagram. The wire shown connected to points 2 and 3 of the switch, in the lower left-hand corner, goes to B plus. No. 1247.

A. We are reprinting the diagram of this efficient short-wave converter. All parts values as well as coil information are shown. The coils can be wound with No. 20 wire on 1 1/4" diameter forms, 3 1/4" long, space wound to fit the available space. Covering the 13 to 30 meter and 30 to 60 meter bands, it has a novel switching arrangement built around the 6-pole, 3-position switch. On two of its positions, the converter is connected to the receiver as a converter on one of the two short wave bands, while on the third position or position No. 1 in the diagram, the converter is disconnected from the antenna and the antenna is connected to the receiver. The switch can be of the 3-deck rotary type, with two poles per deck.

Queries to be answered by mail (not on this page) should be accompanied by fee of 25c (stamps, coin or money order). Where schematic diagram is necessary, our fee is 50c up to 5 tubes; for 5 to 8 tubes fee is 75c; over 8 tubes, fee is \$1.00. No picture diagrams can be supplied.

**The Cover Kink**  
**First Prize Winner**  
**IMPROVED FIXED**  
**CONDENSER**


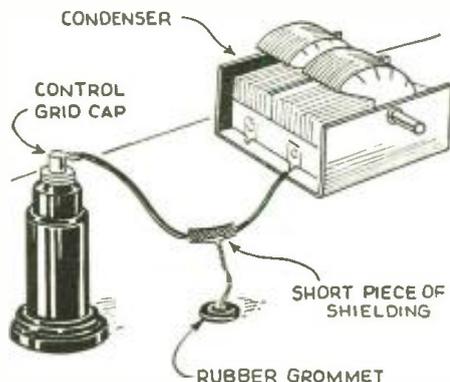
When I need a very small fixed condenser I use the following kink. I substitute one of the wires in the circuit, to which the capacity connection must be made, by a shielded wire from which the shield has been removed for a short space. To this shield a wire is soldered and the condenser is ready.—*Oleg Mechnikoff.*



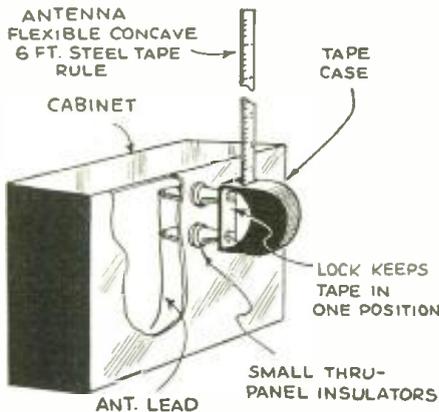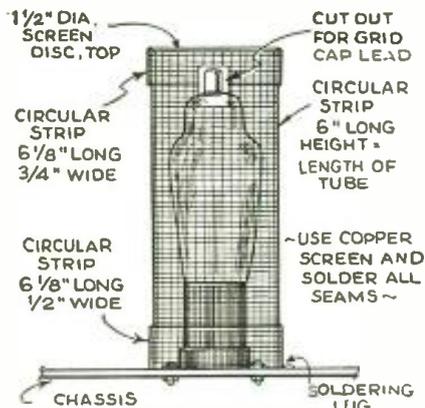**TUBE SHIELD**

This tube shield is made of copper screen, used for window screening. First cut a piece the height of the tube and about 6" long. Cut a notch about  $\frac{1}{4}$ " x  $1\frac{1}{2}$ " in the center of the 6" edge to pass the grid cap lead. Bend this piece into a  $1\frac{1}{2}$ " circle and solder. It is advisable to use acid core solder. Next cut a piece 6" x  $\frac{1}{2}$ " and bend it into a slightly larger circle and solder it to serve as the base. Two soldering lugs are soldered at the bottom in positions where the socket bolts can go through them, to hold down the base and ground it. Then cut another piece 6" x  $\frac{3}{4}$ " for the top circle and form a circle slightly over  $1\frac{1}{2}$ " and solder. A  $\frac{3}{4}$ " x  $\frac{1}{2}$ " notch is cut in this piece also. Last of all a piece about  $1\frac{1}{2}$ " in diameter is cut for the top and soldered to the top circle.—*Bruce H. Stribling.*

*(Copper or other metallic screen makes a very good shielding material, whenever sheet metal is too expensive or is not available for shielding purposes. Due to the overlapping fields set up between the wires forming the screen, the effect is the same as if solid sheet metal was used. A ground connection*




**"STEEL RULE" ANTENNA**

A steel rule of the collapsible concave type makes an excellent antenna for portable radio sets. It is especially convenient for transmitters, since the radiating portion can be adjusted quickly to the exact desired length. Depending on the construction of the cabinet of the portable outfit, the case of the rule can be mounted inside or outside. Two "midget" size feed-through insulators make an excellent support.—*Kurt Rutter.*

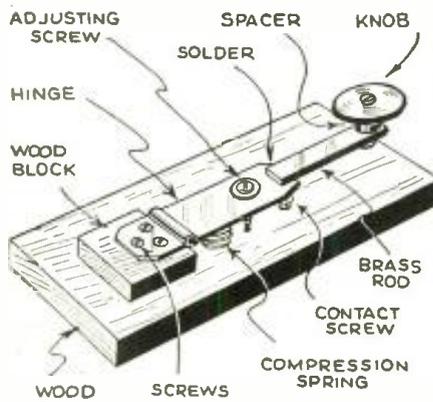**HOME-MADE TELEGRAPH KEY**

Here is a home-made telegraph key that really works. All materials needed, including the lock hasp, are indicated in the diagrams. Mount the hinge section of the hasp on a wood block on a wood base. Set the compression spring in a hole bored in the base and put in the contact screw. The adjusting screw (with a washer to keep it



from slipping through the hole in the hasp) is next put in place. With the knob attached to the brass rod, it is soldered onto the end of the hasp. The contact space and spring tension is adjusted by using the adjusting screw and the contact screw. The key is then ready for operation. In place of the lock hasp any small hinge could easily be substituted.—*Robert V adney.*


*can be easily soldered to such wire screen, and for many purposes a "screen" shield like this will fill the bill very nicely.)*

**RADIO KINKS**

use to you, besides indicating what is wanted. Send a typewritten or ink description with sketch of favorite to the Kink Editor

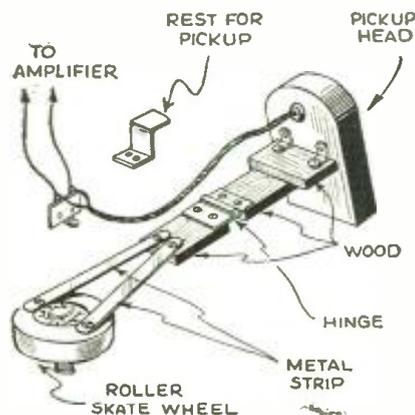**MAKESHIFT PICK-UP ARM**


Here's an emergency arm for the phono pickup. Although it is not streamlined it works just as well. The bearing for the arm is an old roller skate wheel, onto which are soldered two nuts to hold the arm. The two metal strips which fasten to these nuts in turn hold a small wooden strip which is cut in half and held together by an easy action hinge. The other end of the wood can then be fastened to the pickup head with small angles. The wire from the pickup is allowed to ride free in the air and is an-




chored to a binding strip to one side. Two small angles are also used to provide a rest for the pickup. The roller skate wheel and the hinge provide easy action in all directions, and there is not any excessive weight on the record.—*Butler Roberts.*

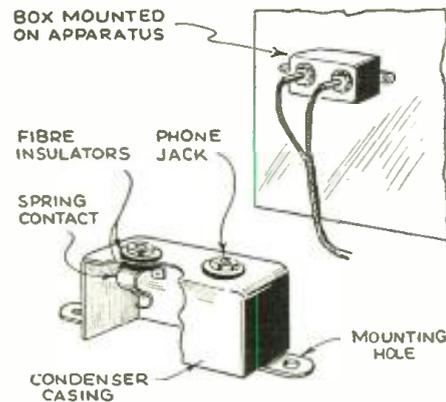**TERMINAL POST**

The construction as you see is very simple. The only thing you need, which can be obtained easily enough from an old radio set, is the can-type by-pass condenser. It can be used for many things. The materials you need are two phone jacks and four washers; the holes are already drilled. It makes a nice appearance on sets that are exposed. It is also useful for the workbench, where meters have to be quickly connected and disconnected.—*James Barrett.*



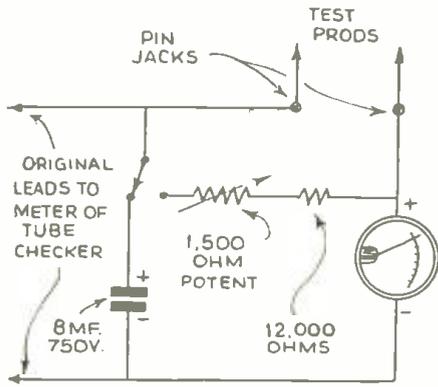published on these pages will win their senders 8 months' subscription to RADIO & TELEVISION. The best kink published each month will win a 2 years' subscription. Read these kinks; they will be of real use to you, besides indicating what is wanted. Send a typewritten or ink description with sketch of favorite to the Kink Editor




**READING HI OHMS ON TUBE CHECKER**

The high voltage obtained from the 8<sup>1</sup>/<sub>2</sub> tube and electrolytic condenser removes the necessity for usual copper oxide rectifier or B battery. Even though the meter has a low sensitivity (of say 125 ohms per volt) and reads 0-5 or 8 ma. instead of the usual 0-1, it is possible to use it as an ohmmeter without impairing its original function. Simply disconnect one lead and follow the diagram. Potentiometer, SPDT switch and two pin-jacks are mounted on the panel. The fixed resistance is determined by the internal resistance of the meter used. The 0-8 meter I use requires 12,000 in series with a 1500 ohm potentiometer, in order to adjust the indicator for zero reading at full scale, when test prods are connected. If not sure of the resistance necessary, try high

ones first and then substitute lower ones until the full scale reading is obtained. Then using several known values across the prods, a scale can be calibrated easily. The limit of good measurability with my set-up—using 0-8 meter, plus an 8 mf. electrolytic condenser, is about 2 megohms. —Don Chamberlin.

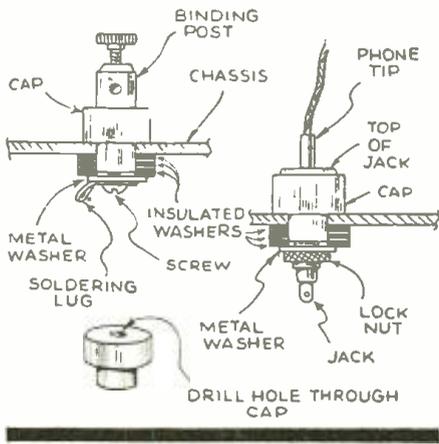**TOOTH-PASTE TUBE CAPS AS INSULATORS**


Here is a use for the composition cap of tooth-paste and shaving cream tubes. By drilling a small hole through it, each cap makes an excellent extruded insulated washer for mounting binding posts on metal chassis. By using the larger sizes and drilling a larger hole, they can also be used to insulate phone tip jacks from metal chassis. In either case, flat insulated washers of



suitable thickness and diameter are slipped over the end of the cap, to take up the slack when cap extension does not come flush with the inside of the panel. These caps are usually of different colors, which makes for quick and easy identification in various applications. A great variety of sizes is also available. —G. A. Soderlund.

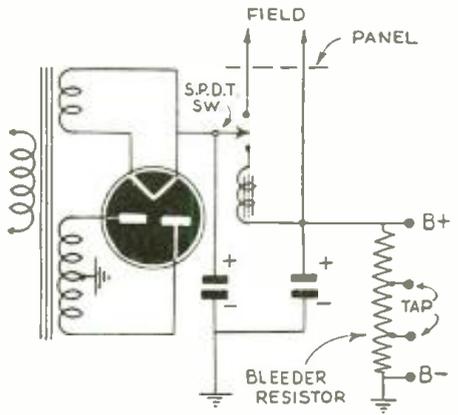**FILTER WRINKLE**

Here is a filter kink I used on a recently constructed power supply. I wanted to hitch up a dynamic speaker on a small set with



low plate drain. At the same time I didn't want to use the field winding as a filter choke permanently in the supply. I solved the problem with a S.P.D.T. switch, two binding posts, and a little re-wiring. —William Whitehead.

**FREE - THIS BEAUTIFUL AND USEFUL 2-WAY LAMP**

**A**LTHOUGH we have offered many fine premiums in the past, we have never before found one that can be as universally useful to everyone as this highly decorative two-way lamp, which we now offer free to our readers. Two-way lamp? Yes, because it can be used as either a vanity or occasional lamp in its normal position, then, with a mere turn of the swivel it becomes a bracket lamp, which can be attached to the wall or woodwork of any room. A useful lamp of this type is highly welcome in any home—including your own. Just think what a handsome gift you can make of it to some friend or relative. Here is the way to receive this beautiful prize. Fill in the coupon in the left-hand corner—clip it out and mail it to us together with your remittance of \$2.50. You will receive a full year's subscription (12 issues) to **RADIO & TELEVISION**—the world's most popular radio magazine. In addition, we will send you absolutely **FREE** one of these wonderful two-way lamps. Old subscribers may renew their subscription now for another year following expiration of their present one and still receive this fine gift. There are only a limited number of lamps available, therefore take advantage of this offer without delay, in order to insure receiving yours.

**RADIO & TELEVISION, 20 Vesey Street, New York, N. Y.**

Gentlemen: Enclosed you will find my remittance of \$2.50 (plus cents shipping charges) for which enter my subscription to **RADIO & TELEVISION** for one year (12 issues). This amount entitles me to a Two-Way Lamp **FREE**, with  fluted shade;  round shade. (See paragraph next to coupon for shipping charges on lamp.)  
 I am a new subscriber.  Extend my present subscription.

Name ..... Address .....

City ..... State ..... 3RT-241

**MAIL THIS COUPON TODAY!**



Above. Used as a wall-lamp, by the simple twist of the swivel. Round shade with colorful ribbon design.


This beautiful little lamp is an asset to any room. The shades are gayly decorated and are made of strong lasting materials. The base is a combination of pressed glass, polished wood and plated metals. Height of lamp, 12 1/2"; shade 8".

At Left. Lamp in normal position for use on vanity or any other piece of furniture. Fluted shade with attractive flower design.

**HOW TO ORDER YOUR LAMP—**

Simply fill in the coupon at the left and mail together with check or money order. Register letter if cash or unused U. S. postage stamps are sent. To cover shipping charges on the lamp, add to your remittance the amount indicated: If you are located east of the Mississippi, add 15c; west of the Mississippi, add 25c; foreign countries, add 40c.

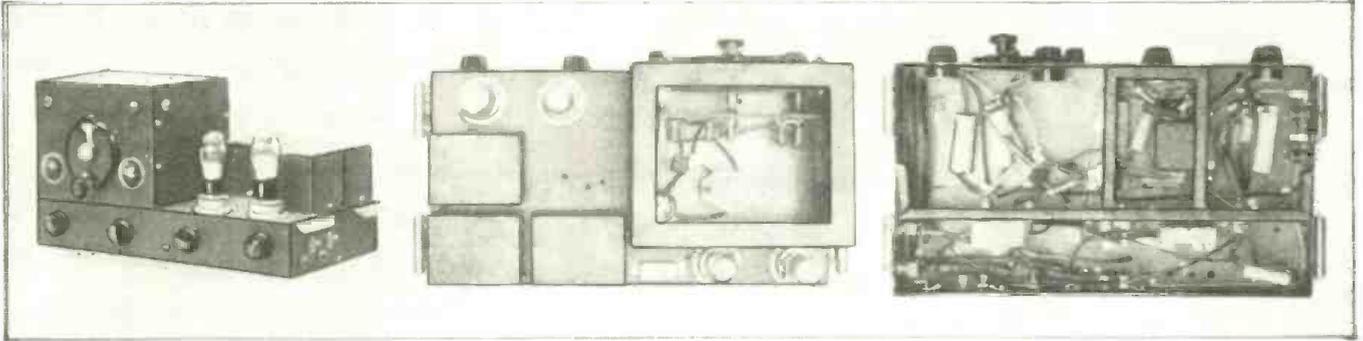**RADIO & TELEVISION, 20 Vesey St., N.Y.C.**



Several views of the 4-tube regenerative receiver here described are shown in the accompanying photos.

# 4-Tube Regen. De Luxe Receiver

W. Ward

● THIS four-tube regenerative receiver has given such excellent satisfaction that the writer feels sure other readers, especially beginners in radio set construction, will want to know the details. By means of *plug-in* coils all the short-wave bands are covered and the *broadcast band* stations as well. Extra smooth regeneration control is provided by means of a dual potentiometer scheme which the writer has worked out. Even with a short antenna, in a crowded city apartment, surprising results have been obtained with this set.

Main Points of Interest: Each point has its own advantage, but taken collectively

For those who hate to tackle the building of a superhet receiver, this super-refined "regenerative" receiver, which has given such remarkable results for Mr. Ward, will find a ready welcome. Remarkable "foreign" station reception has been accomplished with this set using only a short aerial, in a congested city section.

they really do things to, or rather for, the old reliable regenerative circuit.

Vernier Antenna Trimmer—2 condensers used.

Vernier Tuning Condenser—2 condensers used.

Vernier Regeneration—2 potentiometers instead of one.

Twin Filter System—using 2 chokes.


Dual Light Switch for *on* and *off*.

Dual 110 V. Pilots—Illuminate interior, check on power.

1 Amp. Fuse.

Dual electrical outlets on rear of chassis.

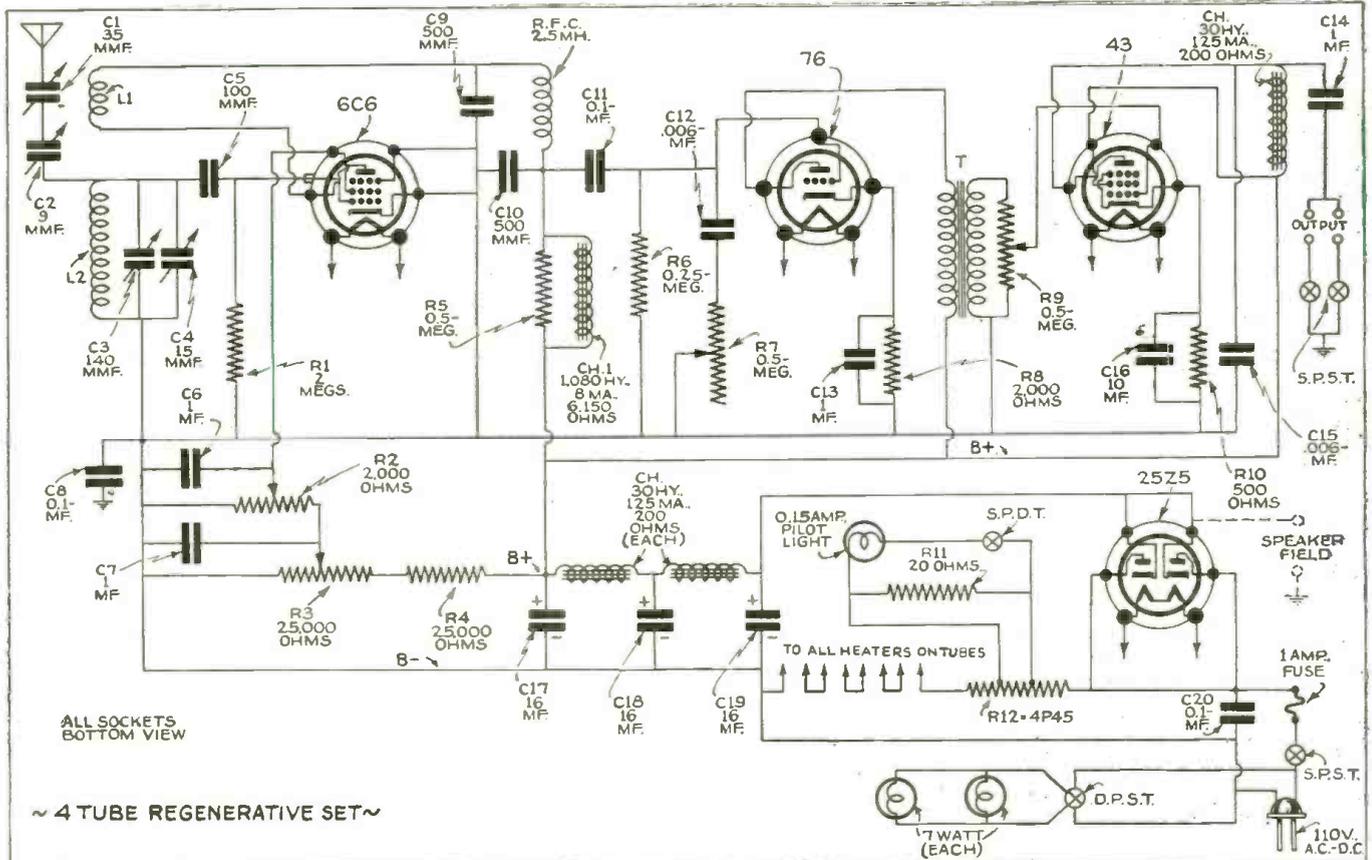The wiring diagram is simple to follow, even for beginners and no aligning of I.F. stages has to be followed.



1 Power Cord plug-in (to table or desk lamp, or transmitter).

Dual jacks in output—separate switch for each.

- 1 Speaker—magnetic or P.M. dynamic.
- 2 Phones or extra speaker.

Tone Control and noise eliminator for C.W. (code) reception.

Audio volume control permits operation of regeneration control at its peak, or *most sensitive* position.

Tubes exposed on chassis for better cooling, plus visual indication of set being turned on.

Partition shielding of each stage is one of the main reasons for this receiver's high stability and selectivity.

Ground connections are made to a separate network mounted on small standoff insulators, thereby removing the hazard of a grounded chassis. The only connection between chassis and ground is through a 0.1 mf. condenser.

### Details of Set

The antenna control condensers are of two different types:

C1—is a National 35 mmf. dual spaced experimenters' type variable, which connects to the antenna and a Bud 1-9 mmf. 6L6 neutralizing semi-variable condenser between the National Condenser and the Hammarlund coil. The National is set at 50 on the dial and the Bud is then set to give smooth regeneration on the band in use. The Bud must be set with a fibre screwdriver or 10" dowel-stick. The 2000 ohms regenerative control No. 1 is set at center position; the 25,000 ohm control No. 2 is then advanced until regeneration occurs, and left in this position. Regeneration is now controlled by the No. 1 2000 ohm control. The 15 mmf. condenser is set around 10 on the National "B" dial, then the 140 mmf. is set at the bottom of the band and left there, all tuning being done with the 15 mmf. condenser. If two stations interfere, tune the one you want to its loudest point and adjust the antenna condenser slightly and the "offender" will disappear. There is a minimum amount of static disturbance on this receiver, but when used on C.W. (code) even this may be removed by setting the tone control properly. The advantage of the audio volume control is immediately apparent to the veteran, but even the novice will soon recognize its value. With this control almost *off*, the European stations roll in at *room volume*; with it on, they chase you out of the house! Amateur phone at Puerto Rico and California are clearly heard and held during three to four contacts. One West Coast Ham was held for one hour and fifteen minutes.

I can hear you say that a Broadcast Station antenna system must have been used to get these results. I will try to explain my location as best I can.

A brownstone house in the heart of New York City; receiver located in rear basement, right near the window—a thirty-five foot antenna with double insulators spaced one foot apart, running from fence to house—the outside insulators spaced about four feet from both ends. The lead-in is only eight feet long, which I believe is the main reason for my success. Once again, keep your lead-in as *short* as possible!

I used the same length antenna elevated up in the air ten floors, with its correspond-

ing long lead-in, and the noise was *terrific*, with no gain in signal strength! I might add that this house is surrounded by all steel buildings and for a period of one year this set has performed the same way, even during the hottest summer days! The author has incorporated in this receiver all the refinements and advantages which he believes to be essential for good results. After all, that is the one thing that counts in any receiver—*RESULTS!*

The fourth can in the parts list, not shown in the picture, sets in the space behind the first audio tube No. 76, and covers the Thordarson choke No. 1. The Bud 1-9 mmf. antenna condenser fits into the space to the left of the 6C6 detector tube.

It is of prime importance that the builder try to use the same parts as here described, in order to obtain the same results—use parts with the exact values specified.

### Parts List

#### HAMMARLUND

- L1 and L2 One SWK4-17-270 meter kit and one SWK4-250-560 meter kit (B.C. coil)
- 1—4-prong isolantite socket
- 1—2.5 mh. R.F. choke

#### BUD

- C2—One 1-9 mmf. 6L6 neutralizing condenser

#### NATIONAL

- C1—35 mmf. dual-spaced midjet condenser
- C3—140 mmf. single-spaced midjet condenser
- C4—15 mmf. dual-spaced midjet condenser
- Type "B" Vermer dial and illuminator

#### CENTRALAB

- R2—2000 ohm regeneration control
- R3—25,000 ohm regeneration control
- R7-R9— $\frac{1}{2}$  meg. tone and volume control

#### SPRAGUE (Condensers)

- C5—100 mmf. mica, 600 v.
- C6, C7—1.0 mf., 400 v. condenser; paper
- C8, C14—1.0 mf., 400 v. condenser; paper
- C8, C11, C20—0.1 mf., 600 v. condenser; paper
- C12, C15—0.06 mf., 600 v. condenser; paper
- C17, C18, C19—16. mf., 250 v. condenser; electrolytic
- C16—10 mf., 50 v. condenser; paper
- C9, C10—500 mmf. mica, 600 v.

#### I.R.C. (Resistors)

- R1—2 megohm,  $\frac{1}{2}$  w. resistor
- R4—25,000 ohm, 1 w. resistor
- R5— $\frac{1}{2}$  megohm,  $\frac{1}{2}$  w. resistor
- R6— $\frac{1}{2}$  megohm,  $\frac{1}{2}$  w. resistor
- R8—2000 ohm, 1 w. resistor
- R10—500 ohm, 2 w. resistor
- R11—20 ohm, 1 w. resistor

#### AMPERITE

- R12—4P 45 ballast tube

#### THORDARSON (Trf. and Chokes)

- T—3 to 1 audio transformer
- CH—3 chokes, 30 henry, 125 ma., 200 ohms
- CH—1 choke, 1080 henry, 8 ma., 6150 ohms

#### LITTELFUSE

- 1—Metal covered fuse mount
- 1—Fuse, 1 amp., 250 v.

#### AMPHENOL

- 2—6-prong sockets, above chassis type, 1 standard type
- 1—5-prong socket, above chassis type
- 1—4-prong socket, above chassis type

#### E. F. JOHNSON

- 14—Standoff insulators,  $\frac{5}{8}$ " high, 6/32 hardware

#### MISCELLANEOUS

- 2—Etched metal dial plates, 0-100,  $1\frac{1}{4}$ " diameter
- 2—Bar knobs for above
- 4—Round bakelite knobs with arrow
- 2—Jewelled pilot brackets with candelabra bases for 7 w., 110 v. bulbs, 1 red, 1 green,  $\frac{1}{2}$ " diameter
- 2—Jewels; 1 red, 1 green,  $\frac{1}{2}$ " diameter for sides
- 2—7 w., 110 v. pilot lamps
- 1—D.P.S.T. switch
- 3—S.P.S.T. switches
- 1—No. 40 brown bead, 0.150 ma. dial light
- 1—Chassis base,  $18" \times 10" \times 3"$
- 1—Detector can,  $9" \times 7\frac{1}{2}" \times 7"$  H
- 4—Choke cans,  $4" \times 3" \times 3\frac{1}{2}"$  H
- 4—Hawdles
- 2— $\frac{1}{2}" \times 1"$  brass spacers
- 3— $\frac{1}{2}" \times \frac{1}{2}"$  shaft couplings
- 1— $\frac{1}{2}"$  fibre shaft
- 1—Piece of bakelite  $\frac{1}{4}" \times 9" \times 6"$  for mounting tuning, hand-spread and antenna condensers
- 2—Panel bearings
- 5—On-off switch plates
- Machine screws, nuts, washers, rubber grommets, paghetti, fibre washers

## GEOPHYSICAL PROSPECTING OUTFITS



### BLUE PRINTS and INSTRUCTIONS

For Building the Following Treasure Finders and Prospecting Outfits

- Folder No. 1. The "Radioflector Pilot"—consists of a 2-tube transmitter and 3-tube receiver. Principle: radiated Wave from transmitter loop is reflected back to receiver loop. Emits visual and aural signals. Tubes used: two 1A5G—two 1N5G—one 1H5G.
- Folder No. 2. The "Harmonic Frequency Locator"—Transmitter radiates low frequency wave to receiver, tuned to one of Harmonics of transmitter. Using regenerative circuit. Emits aural signals. Tubes used: one 1G6G—one 1N5G.
- Folder No. 3. The "Beat-Note Indicator"—Two oscillators so adjusted as to produce beat-note. Emits visual and aural signals. Tubes used: Three type '30.
- Folder No. 4. The "Radio-Balance Surveyor"—a modulated transmitter and very sensitive loop receiver. Principle: Balanced loop. Emits visual and aural signals. By triangulation depth of objects in ground can be established. Tubes used: Seven type '30.
- Folder No. 5. The "Variable Inductance Monitor"—a single tube oscillator generating fixed modulated signals and receiver employing two stages R.F. amplification. Works on the inductance principle. Emits aural signals. Tubes used: six type '30.
- Folder No. 6. The "Hughes Inductance-Balance Explorer"—a single tube Hartley oscillator transmitter and sensitive 3-tube receiver. Principle: Wheatstone bridge. Emits aural signals. Tubes used: two type '30—one type '32—one type '33.
- Folder No. 7. The "Radiodyne Prospector"—a completely shielded instrument. Principle: Balanced loop. Transmitter, receiver and batteries enclosed in steel box. Very large field of radiation and depth of penetration. Emits aural signals. Tubes used: two 1N5G—one 1G4G—one 1H5G—one 1Q5—one 1G4.

With any one of the modern geophysical methods described in the Blue-Print patterns. Radio outfits and instruments can be constructed to locate metal and ore deposits (prospecting); finding lost or buried treasures; metal war relics; sea and land mines and "duds"; mineral deposits; subterranean water veins; oil deposits (under certain circumstances); buried gas and water pipes; tools or other metallic objects sunken in water, etc., etc.

Each set of blueprints and instructions enclosed in heavy envelope ( $9\frac{1}{2}" \times 12\frac{1}{2}"$ ). Blueprints  $22" \times 34"$ ; eight-page illustrated  $8\frac{1}{2}" \times 11"$  fold. **50¢** or of instructions and construction data... Add 5¢ for postage

The complete set of seven folders..... **\$3.00**  
Shipping weight 2 lbs. (add 25¢ for shipping anywhere in U.S.A.)

## TECHNIFAX

RT-241  
1917 S. STATE ST. CHICAGO, ILL.

TECHNIFAX 1917 So. State, Chicago, Ill.

Enclosed herewith \$....., for which mail to address below:

Treasure Finder No. 1, 2, 3, 4, 5, 6, 7.  
Complete set of seven folders,

NAME .....





ADDRESS .....

CITY ..... STATE .....

RT-241

How to Build

# A Small OUDIN Coil

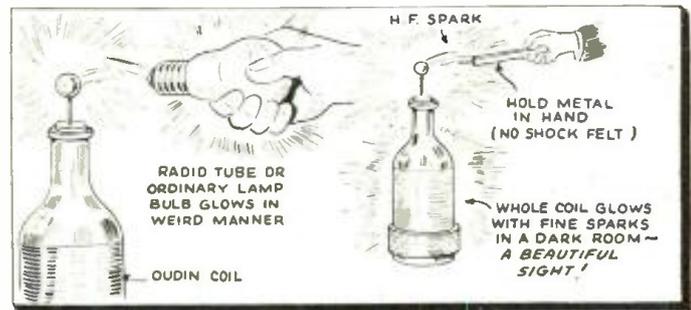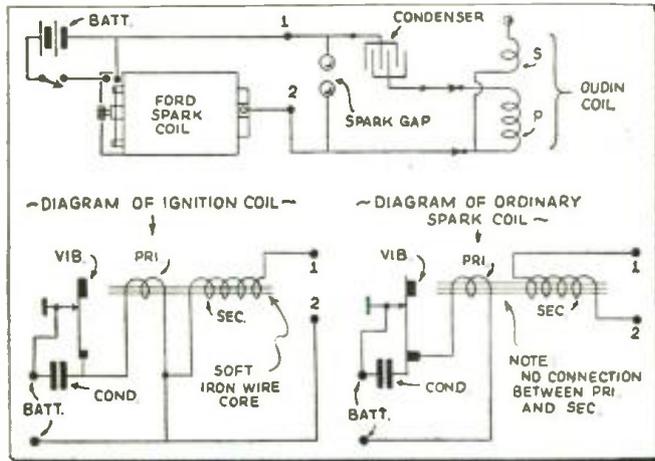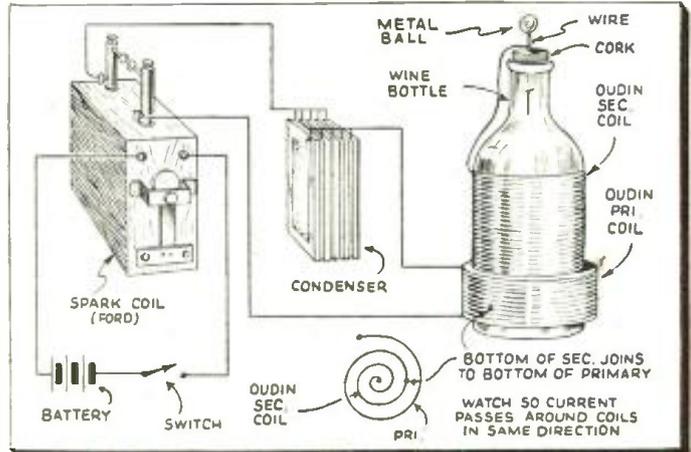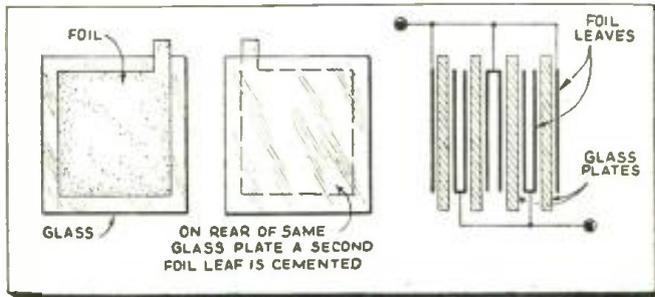

The small "bottle-type" Oudin coil here illustrated can be built at insignificant cost, and it will provide many weird and interesting effects. The Oudin coil consists of a single layer of fine copper wire wound on an old wine bottle, together with a primary of a few turns of heavy wire wound around the base of the coil. The exciter is simply an ordinary spark coil of the ignition type; the condenser is made from a few glass plates, such as old photo negatives, coated with tin-foil.

● THE electrical experimenter can have a lot of fun with a small Oudin coil wound on an old wine bottle, as shown in the accompanying picture. This small, yet powerful, high frequency coil can be excited from a spark coil of the ½ inch variety, more frequently known to the experimenter as an ignition coil. Some people know them more affectionately by the term of Ford spark coil.

The cost of making this apparatus is practically nil, provided you can pick up a second-hand Ford coil from your local garage; or possibly you already have a similar spark coil on hand.

The other parts necessary are a fixed spark gap, comprising a couple of small balls, a glass plate condenser constructed as hereafter described, and the Oudin coil itself, which only requires a small amount of wire wound evenly on a glass bottle (or even a cardboard tube about the size of a one-quart wine bottle).

The glass plate condenser may comprise half a dozen old photo negatives, or else pieces of thin window glass, measuring about 5 x 7 inches each. Each side of the window glass is coated with a piece of tin or other metal foil, cementing the foil to the glass by means of thin shellac or banana oil. The foil leaves are cut ½ inch smaller all around than the size of the glass plate, to avoid sparking over the edges from one plate to the other. Every other metal foil plate is connected to a common terminal, as indicated in the diagram.

The Oudin coil has a primary and secondary winding as the diagram shows. The secondary winding comprises a single layer of about No. 28 insulated or bare copper wire, the turns being spaced a slight distance apart. This can be done easily in a lathe, or if wound by hand—this spacing can be done by winding on a small string or thread along with the wire, the thread being removed afterward (or left in place for that matter).

At the lower end of the Oudin coil a primary winding is arranged, and this may consist of from 6 to 8 turns of No. 12 or 14 rubber covered wire, wound in a single layer about one inch greater in diameter than the diameter of the bottle. One easy way to wind this primary coil is to wind a strip of cardboard (such as used for packing purposes) around the bottom of the Oudin secondary, so that the cardboard is about ½ inch thick. The primary winding may then be wound over this cardboard. In the event that bare wire of No. 12 or 11 gauge is to be used, the turns should be spaced about ¼ inch. The advantage of the bare wire is that spring clips may be used to make connections to the condenser, and these permit varying the number of turns in use.

The upper end of the Oudin secondary coil is connected to a brass or copper rod, supporting a small metal ball at the top. In order to obtain the maximum discharge of high frequency sparks from the metal ball on top of the Oudin coil, the following

adjustments should be made. The vibrator of the spark coil may be adjusted for best results; next the number of glass plates and tin-foil leaves in circuit in the high voltage condenser may be varied; and thirdly, the number of Oudin primary turns in use may be varied by means of the clips as aforementioned.

For those who have the time to do a little experimenting different types of windings may be tried on the Oudin coil; also different types and diameters of primary coils may be tried. As long as no spark takes place between the primary and secondary windings on the Oudin, the smaller the diameter of the primary, the more intense the sparks produced at the free end of the Oudin secondary. Next, the greater the number of turns of fine wire used in the Oudin secondary, the higher the voltage and the longer the sparks produced; but there is a happy medium here, as with too fine a wire, the sparks are too thin and stringy to be spectacular. No. 28 or 30 has been found very effective for this size high frequency coil. Like all other electrical apparatus, the more electrical energy we pump into the Oudin coil, the more spectacular the high frequency spark discharges produced. This size coil may have a considerably greater amount of energy supplied to it than that available from a small half-inch ignition coil, and if you happen to have a larger size spark coil of the vibrator type, you can try it on the Oudin.

When excited by a ½ to ¾ inch ignition

# SUPER SPECIALS

coil, such as the Ford type, high frequency sparks 2 to 3 inches or more in length will be liberated from the ball terminal atop the Oudin.


A number of interesting experiments for home lectures, radio clubs, etc., can be performed with a small Oudin, such as the one here described. Evacuated tubes, including old radio tubes and incandescent lamps, may be lighted by holding them in the hand and approaching the metal base toward the ball terminal of the Oudin. A spark will jump between the ball and the base of the lamp, and it will be illuminated with a weird bluish glow. Lamps may be lighted in this way without any shock, if one keeps his fingers away from the metal lamp base.

To draw sparks into the body from the ball terminal on the Oudin, hold a piece of metal such as a screw-driver or pair of pliers in the hand. The high frequency sparks will jump to the piece of metal and no unpleasant shock will be felt. A slightly disagreeable shock is felt if the bare finger is approached toward the Oudin high voltage terminal. Many other experiments will suggest themselves to those who build the Oudin coil, such as "electric duels," the production of an illuminated cone between two rings of wire, one much smaller than the other and one ring grounded, etc.

While Oudin coils have been excited from vacuum tube oscillators, such as used for radio transmitters, the size and power of the transmitting tube required to produce equivalent results is prohibitive to the average experimenter with a limited pocket-book, compared to the method here described. Of course with larger Oudin or Tesla coils, giving sparks from one to five feet in length, the exciting circuit utilizes a high voltage transformer, a rotary spark gap being used in the condenser circuit feeding the Oudin primary, and of course no vibrator is used with the transformer.
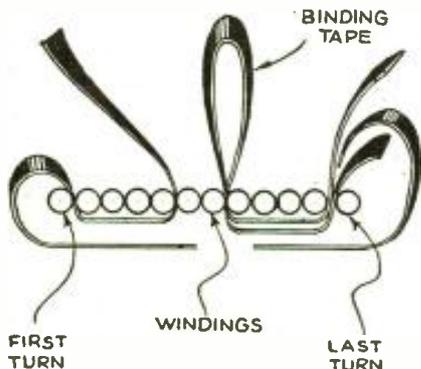
## LOCKING IN "END-TURNS"

For the first turn, lay a piece of tape under and come to the second turn; bring the free end over the first turn, under the second turn and wind on two or three more turns, then pull the free end tight and cut it off. For the last turn, six or seven turns from the last, lay on a piece of tape and wind on one or two turns; then lay on loop, allowing a couple of inches in the loop, then wind on three or four turns and lay the free ends back over the winding and wind on the last turn. Hold it, slip the free end of the single strip between the free ends of the loop, and pull the loop through and out, then take up the slack in the remaining free end and cut it off.—H. L. Kidwell.



All of the attractive items listed here are brand new. ALL are in PERFECT WORKING ORDER. In many cases, the parts alone total more than the price we are asking. 100% satisfaction guaranteed or your money refunded.  
**ORDER FROM THIS PAGE.** Use the convenient coupon below. Include sufficient extra remittance for parcel post charges, also order shipped express, collect. Any excess will be refunded. C.O.D. shipments require 20% deposit. If full remittance accompanies order, deduct 2% discount. Send money order, certified check, new U. S. stamps. No C.O.D. to foreign countries.

**ORDER TODAY LIMITED QUANTITIES PROMPT SHIPMENTS ASSURED**

### 2-SPEED PHONOGRAPH TURNTABLE



Adapts any phonograph for both 33-1/3 and 78 R.P.M. This ingenious device, by simply replacing your present turntable, automatically modernizes your machine to play 33-1/3 R.P.M. high-fidelity transcription records as well as the standard 78 R.P.M. records. Quickly installed by anyone. Complete instructions furnished. Felt-covered turntable measures 12" in diameter and fits all standard phonographs. Packed in original box. Original price \$3. Shp. Wt. 3 lbs.  
**ITEM NO. 89 YOUR PRICE \$5.95**

### 2-WAY LAMP


Ornamental dual purpose lamp. Can be used as a table or vanity lamp in one position. By turning swivel base it becomes a bracket lamp which may be mounted on wall.



Hanger in base is provided for this. Handsome design. Base made of pressed glass, polished wood and plated metal stand. Comes with round shade colorfully decorated with ribbon design, or more elaborate fluted shade with flower design. Height of lamp 12 1/2"; shade 8". Complete with cord. Shipping wt. 2 lbs.  
**ITEM (Plain Shade) NO. 120 98c**  
**ITEM (Fluted Shade) No. 121, YOUR PRICE \$1.05**
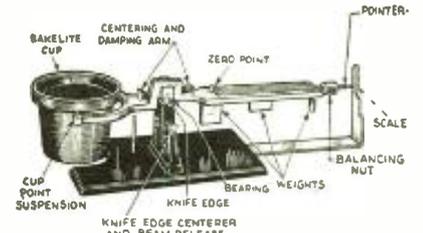
### BENNETT LABORATORY BALANCE

A compact laboratory balance made of finest quality tested materials. Extreme sensitivity (to 2-100ths gram or 2-ths grain). Weighs to one decimal pt. further.



than usual low priced counter scale. Will handle up to 100 grams (about 4 oz.). Bakelite pan; tool steel knife edge; agate bearing for long life and accuracy. Ideal for photographic work and lab use. Handsome streamline design. Graduated either in metric or apothecary system. Shipping wt. 2 lbs.  
**ITEM NO. 122 YOUR PRICE \$7.20**

### 100 POWER TELESCOPE LENS KIT

Make your own high powered 6 ft. telescope! Now you can thrill to a close-up view of the worlds out in space. See the rings around Saturn, the mountains of the moon! Kit contains 3" diam., 75" focal length, ground and polished objective lens and 2 astronomical eye-pieces, magnification 50x and 100x. Complete kit with full instructions.  
**ITEM NO. 123 YOUR PRICE \$1.95**

## New Catalog

**JUST OUT**  
**A POSTAL CARD BRINGS IT TO YOU**  
**SEND FOR IT TODAY**

**HUDSON SPECIALTIES CO., 40 West Broadway, N. Y. C.**

IT'S EASY TO ORDER—CLIP COUPON—MAIL NOW ORDER FROM THIS PAGE.

HUDSON SPECIALTIES CO., 40 West Broadway, Dept. RT-241, New York, N. Y.  
 I have circled below the numbers of the items I'm ordering. My full remittance of \$..... (include shipping charges) is enclosed.  
 OR my deposit of \$..... is enclosed (20% required), ship order C.O.D. for balance. No C.O.D. order for less than \$2.00. (New U. S. stamps, check or money order accepted.)  
 Circle item No. wanted: 86, 87, 89, 97, 120, 121, 122, 123, 124, 125

Name ..... Address .....  
 City ..... State .....

Send remittance by check, stamps or money order; register letter if you send cash or stamps.

### AMAZING BLACK LIGHT!

Powerful 300-Watt Ultra-Violet Bulb



The best and most practical source of ultra-violet light for general experimental and entertainment use. Makes all fluorescent substances brilliantly luminescent. No transformers of any kind needed. Fits any standard lamp socket. Made with special filter glass permitting only ultra-violet rays to come through. Brings out beautiful opalescent hues in various types of materials. Swell for amateur parties, plays, etc., to obtain unique lighting effects. Bulb only. Size of bulb. Shp. Wt. 1 lb.

**ITEM NO. 87 YOUR PRICE \$2.00**

### ULTRA MAGNET

LIFTS MORE THAN 20 TIMES ITS OWN WEIGHT



**LITTLE GIANT MAGNET.** Lifts 5 lbs. easily. Weighs 4 oz. Made of AL-NICO new high-magnetic steel. Complete with keeper. World's most powerful magnet ever made. The experimenter and hobbyist will find hundreds of excellent uses for this high quality permanent magnet. Measures 1 1/2" x 1 1/2". Shp. Wt. 3/4 lbs.

**ITEM NO. 86 YOUR PRICE \$1.00**

### ELECTRIC TURNTABLE




A sturdy electric turntable, ideal for eye-catching window displays. A MUST for alert retailers. Frame made of 16 gauge steel, 16 in. steel turntable makes three revolutions per minute. Turntable supports load of 200 lbs. Ballbearing construction. Rich black enamel finish. Operates on 110 v. A.C. Current cost only 1/4c a day. Size: 5 1/2" high, base 8" square. Shipping wt. 14 lbs.

**ITEM NO. 124 YOUR PRICE \$8.95**
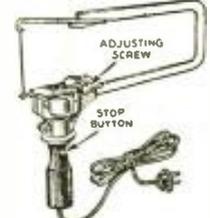
### NEW ELECTRIC MOTOR-SAW

Now you can have all the fun of fine, fast jigsaw work without any of its difficulty. Simply steer the lightning-fast blade and see it seemingly melt its magic way through wood, plastics and building board. 720 STROKES per MINUTE! Average cutting speed 1 foot per minute through 3/4" medium hard wood. Works 3 times faster than any free-hand saw. Operates on 50-60 cycle 110 v. Alternating Current. Screw adjusts blade stroke from 1/4" to 5/16". Off-On Switch built in handle. Complete with 6 ft. power cord and 3 saw blades.



**ITEM NO. 97 YOUR PRICE \$4.85**

### ELECTRIC HUMIDIFIER FOUNTAIN



Add healthful moisture to the air in winter. Evaporates as much as a pint of water in 24 hours. Fountain is 14" in diam. Sprays 8 streams of water 3" above fountain head. Made of spun aluminum. Comes in five colors: Bronze, chrome, copper, red, green. No watery connections required. Just plug into 110 volt, 60 cycle A.C. outlet. Current consumption few cents a month. Complete with base switch and 8 ft. power cord. Shipping wt. 9 lbs. List price \$14.95. Only a limited supply on hand.

**ITEM NO. 125 YOUR PRICE \$4.95**

# Digest of Recent Radio Patents

## Inventions Wanted Patented or Unpatented

We have been successfully selling inventions, patented and unpatented, since 1924. Write us, if you have a practical, useful idea for sale.

**CHARTERED INSTITUTE OF AMERICAN INVENTORS**

Dept. 109 Barrister Building, Washington, D.C.

### GREATEST SLIDE RULE VALUES EVER OFFERED



10 inch enameled slide rule, made of kiln dried seasoned hardwood, has auxiliary removable magnifier with glass to fit (ferrous) runner. This rule has inch, millimeter, sine, log and tangent scales. Packed in individual carrying case. This rule is equal in performance to a \$10.00 rule. Our special price, P.P. prepaid anywhere **\$1.00**

- LAWRENCE 10-inch white enameled slide rule with clear glass magnifier in Black Case. Price includes 36-page instruction book, prepaid... **60c**
- 8" Slide Rule ..... **25c**
- 36 Page Illustrated Book of Instructions .... **10c**
- 36 Page Book Stanley's Slide Rule Practice, 300 Fascinating Examples and Answers .... **10c**
- Secret Code slide rule, with 16-page book... **30c**

Postage Prepaid

### GOLD SHIELD PRODUCTS


Dept. RT-241 350 Greenwich St. New York

**LAST CALL at this LOW PRICE. Short-Wave fans need this WORLD-TIME CLOCK The Only Clock for Universal Use Throughout the Entire World!**

**A REGULAR CLOCK**  
with A.M. and P.M. divided dial

**A WORLD-TIME CLOCK**  
instantly indicating time in all 24 zones

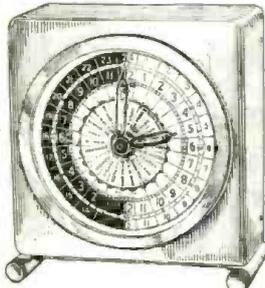**INTERNATIONAL CLOCK**  
with A.M. and P.M. 24 hour dial



Indispensable for Short Wave Fans.

- Electric (for A.C. 110-120 volts, 60 cycles) **\$5.95**
- Spring Model ..... **\$4.95**


P.P. prepaid in U.S.A.  
Remit by check or money order; register letter if you send cash or unused U. S. postage stamps.

### GOLD SHIELD PRODUCTS

350 Greenwich Street, Dept. RT-241, New York City
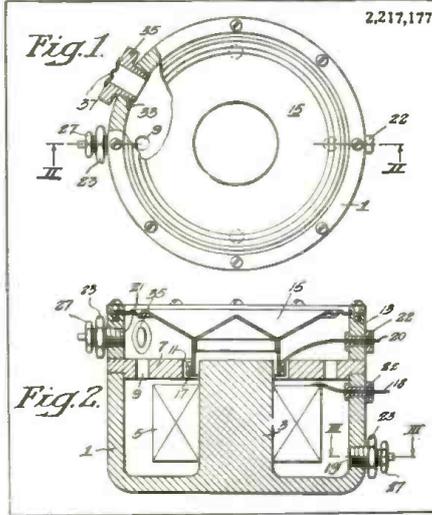
## GAS-FILLED LOUDSPEAKER

● **FRANK MASSA**, assignor to RCA, recently received this patent No. 2,217,177 on a gas-filled loudspeaker. As the drawing shows the container for the speaker mechanism is constructed in a gas-tight manner so that gas may be pumped into the chamber and improve the operating efficiency of the receiver. By filling the housing, for



example, with a gas having high thermal conductivity, the heat generated in the loudspeaker coils will be conducted more easily to the radiating surface of the housing, thus making it possible to increase the power rating of the loudspeaker. Also the temperature rise of the voice coil of the

## PATENTS—TRADE MARKS


Booklet concerning Inventions & Patents Form "Evidence of Conception" with instructions for use and "Schedule of Government and Attorneys Fees"—Free  
**LANCASTER, ALLWINE & ROMMEL**  
Registered Patent Attorneys.  
436 Bowen Bldg. Washington, D. C.

loudspeaker will be greatly reduced, if a highly thermal conductive gas is used as the conducting medium in the magnetic gap in which the voice coil operates.
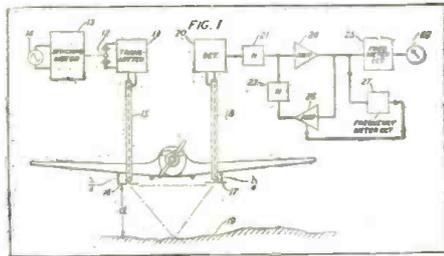
## ALTITUDE INDICATOR

● **RICHARD F. LANE** and **Russell C. Newhouse** of Orange, N. J., assignors to the Bell Telephone Laboratories of New York, have recently received U. S. patent No. 2,206,903 on a Radiant Energy Distance Measuring System. One of the applications of this distance measuring device, is that of determining the height of an airplane above the ground. The distance is measured by radiating waves from one point to another, and receiving these waves reflected back at the first point.

The time interval between radiation and reception is a measure of the distance, and is determined by cyclically varying the frequency of the transmitted waves, at a known rate and over a known range. The frequency difference between the wave being transmitted and the received reflected wave, is therefore, a measure of the distance to the reflecting surface. The measurements are




obtained by beating together the transmitted wave and the echo wave, and measuring the frequency of the resultant difference frequency beat wave.
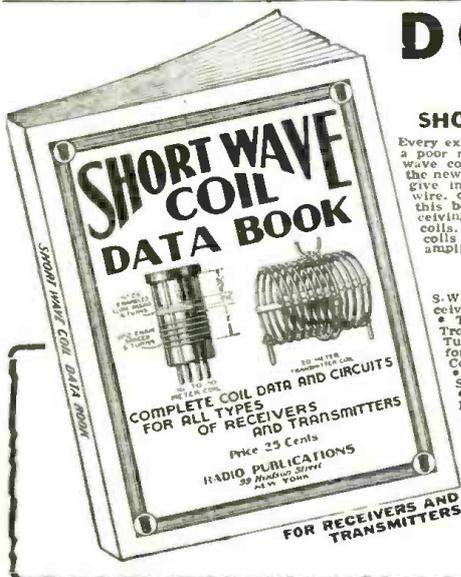
## RECEIVER VOLUME CONTROL

● **ROBERT B. FOSTER** of Los Angeles, Calif., was awarded patent No. 2,219,302 for an improved volume control for use on radio receivers. The claims in this patent can best be visualized by a study of the eleventh claim in this patent which reads as follows:

In a radio control apparatus, the combination with a cabinet, a radio receiver therein, the receiver having a variable tuning means adjustable to different broadcast station positions, means for shifting the same, and a loud-speaker. Further, means are provided of varying the volume of the loud-speaker, an adjustable cam for each broadcast station of the variable tuning means, means for operatively connecting the volume, varying means with all of the cams of the variable tuning means, but with one particular cam at a time, the latter cam corresponding to and depending upon the specifically shifted station-tuning position of the tuning device, and separate means at the outside of the cabinet for each of the cams for separately adjusting each of the cams, said adjusting means being spaced and located in positions corresponding to the station positions of the tuning means.



# DON'T FAIL TO GET THIS

## SHORT WAVE COIL DATA BOOK

Every experimenter knows that the difference between a good and a poor radio set is usually found in the construction of short-wave coils. Coil winding information is vitally important and in the new coil book all "dope" appears. There are illustrations which give instructions on how to wind coils, dimensions, sizes of wire, curves and how to plot them. Every experimenter needs this book—it also contains complete data on all types of receiving coils, together with many suitable circuits using these coils. Also complete data on various types of transmitting coils with many transmitting circuits such as exciters and amplifiers using the various coils described.

### Contents Briefly Outlined

- S-W Tuning Inductance Charts • Coil Data for T. R. F. Receivers • One Tube Oscillodyne • Two Tube Bandspreeder • The Mono-Coil • 2-Tube Old Reliable • 2-Tube Globe Trotter • 2-Winding Coils—10-500 Meters • Dierle 3-Tube "Signal Gripper" Electrified • 3-Tube Bandspreeder for the Home • General Coverage Coils on Ribbed Forms • Coil Data for Superhet or S-W Converter • Ultra S-W Coils • Switch Coils for S-W Superhets • Experimental Coils • S-W Antenna Tuner • Most Popular S-W Tuning Circuits • Self-Supporting Transmitting Circuits Employing Coils Described • All Band Antenna Tuner for Transmitting • Plug-In Coils for Exciters • Frequency-Wavelength Conversion Chart.

### PRICE 25c PREPAID


For a copy of this handy book send 25c in U.S. Coin or stamps to

## RADIO PUBLICATIONS

20 VESEY STREET NEW YORK, N. Y.

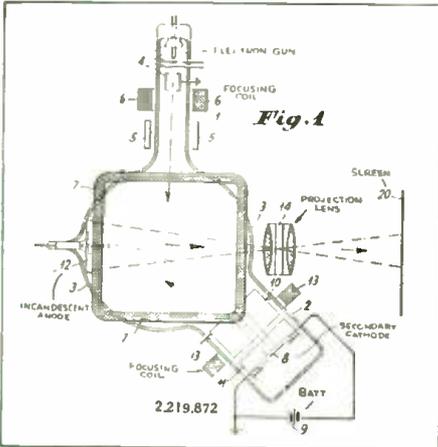**TELEVISION IMAGE PROJECTOR**

● LEONARD MORRIS MYERS of Middlebrough, England, assignor to RCA, recently received this patent No. 2,219,872 on a very interesting and unusual method of producing television images in the form of modulated heat patterns, suitable for projection on a large screen. This invention reproduces television pictures or images, not by fluorescent effect in a fluorescent



screen, but by heating a picture reproducing electrode to incandescence and thus obtaining pictures by light, due to heat. The diagram shows how a secondary cathode is heated by a battery or other source of current. The images projected on to it by the usual cathode-ray gun are, in turn, reflected on to an incandescent anode. From this point the images are radiated through the projection lens on to a screen.

**DIRECTIONAL ANTENNA**

● PHILIP S. CARTER of Port Jefferson, N. Y., recently received a re-issued patent No. 21,609, covering a clever system of directional antenna which does not use a reflector.

The present invention obviates the necessity for reflectors and provides an antenna which is nearly aperiodic over a wide range of frequencies. Use is made of the phenomena of attenuation along radiating wires in order to obtain unidirectionalism without the use of reflectors.

Generally speaking, the invention comprises a pair of approximately equal length antenna radiating sections which are relatively long with respect to the length of the communication wave and angularly disposed with respect to each other, each section, in turn, being composed of a plurality of radiating elements connected together by means of phasing members. In practicing the invention, it is essential that the radiating elements comprising each section be substantially coaxial with respect to one another so that they extend in the same direction and that the phasing elements connecting the radiating elements together shift the phase of the energy an amount just enough to make the ears of the radiation patterns of the different elements in each section add. It will thus be appreciated that the phasing elements which serve to provide maximum radiation from the system and thus maximum attenuation due to radiation should not reverse the phase of the currents between adjacent radiating elements.

*Lowest Priced Publications for Experimenters*

**10 FOR 50c**

Here is a large number of radio, short-wave, and mechanical "how-to-make-it" designs. Each is a special publication originated by masters in their respective fields. For the low price of 50 CENTS, you buy TEN complete Pamphlets with photographic reproductions, complete mechanical layout, and full description to make it possible for anyone to build the project in question.

PLEASE ORDER EACH PROJECT BY ITS PUBLICATION NUMBER, and use the special coupon below. We accept money-orders, cash, checks or new U. S. stamps. (No foreign stamps.) If you send cash or stamps, register your letter. Money refunded if you are not satisfied. ANY TWENTY-FOUR PUBLICATIONS FOR ONE DOLLAR.

**SHORT-WAVE RECEIVER PUBLICATIONS**

- HOW TO MAKE THE "OSCILLODYNE" 1-TUBE WONDER SET.....No. 101
- HOW TO MAKE THE "19" TWINPLEX (ONE TUBE PERFORMS AS TWO) RECEIVER.....No. 102
- HOW TO MAKE THE WIZARD 1-TUBE 50-WATT TRANSMITTER.....No. 103
- HOW TO MAKE THE IMPROVED 3-TUBE DOUBLE SET FOR BATTERY OPERATION.....No. 104
- HOW TO MAKE THE "GO-GET-EM 2" RECEIVER FOR THE BEGINNER.....No. 105
- HOW TO MAKE THE 1-TUBE-ALL-ELECTRIC OSCILLODYNE.....No. 106
- HOW TO MAKE THE 2 TO 5 METER TWO-TUBE LOUDSPEAKER SET.....No. 107
- HOW TO MAKE THE 3-TUBE BATTERY SHORT-WAVE RECEIVER.....No. 108
- THE BRIEF-CASE SHORT-WAVE RECEIVER AND HOW TO BUILD IT.....No. 109
- HOW TO BUILD THE "POCKET SHORT-WAVE RECEIVER".....No. 110
- HOW TO BUILD THE CIGAR-BOX 1-TUBE "CATCH ALL" RECEIVER.....No. 111
- HOW TO BUILD THE "DUAL-WAVE" SHORT-WAVE BATTERY RECEIVER.....No. 112
- HOW TO BUILD THE 1-TUBE "53" TWINPLEX RECEIVER.....No. 113
- HOW TO BUILD THE PORTABLE MINDYNE SHORT-WAVE BATTERY SET.....No. 114
- HOW TO BUILD THE HAM-BAND "PEE-WEE" 2-TUBE.....No. 115
- HOW TO BUILD THE DUO-AMPLIDYNE.....No. 116
- HOW TO BUILD THE "MONO-COIL 2".....No. 117

**RADIO BROADCAST RECEIVER AND SPECIAL RADIO PUBLICATIONS**

- HOW TO MAKE THE A.C.-D.C. "CASH BOX" RECEIVER.....No. 118
- HOW TO MAKE BEGINNER'S 2-TUBE ALL-WAVE SET.....No. 119
- HOW TO BUILD THE "RADIO-LAMP" 4-TUBE TABLE RECEIVER.....No. 120
- HOW TO BUILD A SUPER-SENSITIVE ALL-WAVE CRYSTAL SET.....No. 121
- HOW TO BUILD THE 2-TUBE "PENTODE PORTABLE" BROADCAST SET.....No. 122
- HOW TO BUILD THE RADIO "TREASURE" FINDER.....No. 123
- HOW TO BUILD THE GERMS-BACK ONE-TUBE PENTODE LOUDSPEAKER SET.....No. 124
- HOW TO BUILD THE WORLD'S SMALLEST ONE TUBE BATTERY RADIO.....No. 125
- HOW TO BUILD A 6-TUBE BATTERY ALL-WAVE "FARM PORTABLE" SET.....No. 126
- HOW TO MAKE AN A.C.-D.C. ONE-TUBE "DEAF AID".....No. 127
- HOW TO BUILD A PIANOTRON.....No. 128
- HOW TO BUILD THE ONE-DOLLAR RADIO.....No. 129
- HOW TO MAKE A VARIABLE-TONE CODE PRACTICE SET.....No. 130

**MECHANICAL PROJECTS PUBLICATIONS**

- HOW TO MAKE A SOUTH SEA OUTRIGGER CANOE.....No. 131
- HOW TO BUILD A PEE-WEE AUTOMOBILE.....No. 132
- HOW TO BUILD A DUAL-CONTROL GLIDER.....No. 133
- HOW TO BUILD A HOUSEBOAT ON PONTOONS.....No. 134
- HOW TO MAKE A BAND SAW FROM OLD AUTO PARTS.....No. 135
- HOW TO BUILD A REAL LATHE FOR \$5.00.....No. 136
- HOW TO BUILD A SAIL CATBOAT.....No. 137
- HOW TO BUILD A SIMPLE PORTABLE REFRIGERATOR.....No. 138
- HOW TO BUILD A XYLOPHONE.....No. 139
- HOW TO BUILD THE ROWM-BILE.....No. 140
- HOW TO BUILD LARGE TESLA AND OUDIN COILS GIVING 18-INCH SPARKS.....No. 141
- HOW TO MAKE AN ARC WELDER.....No. 142
- HOW TO USE AN A.C. ARC WELDER.....No. 143
- HOW TO MAKE YOUR OWN MICROSCOPE.....No. 144
- HOW TO MAKE A WIMSHURST ELECTROSTATIC MACHINE.....No. 145
- HOW TO MAKE A POWER DRILL PRESS FROM SCRAP PARTS.....No. 146
- HOW TO BUILD A GOOD LATHE FOR \$1.00.....No. 147
- HOW TO MAKE AND EXPERIMENT WITH AN ELECTROPHOROUS.....No. 148
- HOW TO MAKE AN ELECTRIC ARC WELDER FROM AN AUTOMOBILE GENERATOR.....No. 149

**RADIO PUBLICATIONS • 20 Vesey Street • New York, N.Y**

**RADIO PUBLICATIONS, 20 Vesey Street, New York, N.Y.**

**R&T-2-41**

I enclose \$..... for the publications listed by number at right, at the rate of 50c FOR ANY TEN PUBLICATIONS. NO ORDER FOR LESS THAN 50c ACCEPTED. \$1.00 for 24 publications. These publications are to be sent me postpaid. I have placed a circle around each number which I want.

Name ..... Address .....  
City ..... State .....

101	102	103	104	105	106
107	108	109	110	111	112
113	114	115	116	117	118
119	120	121	122	123	124
125	126	127	128	129	130
131	132	133	134	135	136
137	138	139	140	141	142
143	144	145	146	147	148
					149

**RADIO & TELEVISION OFFERS YOU 6 COPIES R&T FOR 50c**

For a limited time only, and as long as they last, we will send you six back numbers of RADIO & TELEVISION assorted, your choice, for 50 cents.

The usual price for six copies would be \$1.50, and most publishers charge a higher price for back numbers over one year old.

We can supply only the following back numbers: Sept., 1931; Sept., 1934; Aug., Oct., 1935; 1936—all issues except Apr., May and Oct.; 1937—all issues except Feb. and Aug.; 1938—all issues except March and Nov.; 1939—all issues except Jan., March and April; 1940—all issues except Jan. and April; 1941—all issues to date.

If you do not specify copies, we will send assorted numbers to fill your order. Note, we cannot exchange the copies for ones that have been sent to you.

Every copy of RADIO & TELEVISION contains information which you should have. Here is a chance to get those copies. As only a small supply of back numbers on

hand, this offer will be withdrawn as soon as they have been sold.

We accept U. S. stamps, U. S. coin, or money order. Rush your order today.

**RADIO & TELEVISION** 2-41  
20 Vesey Street, New York, N. Y.

Gentlemen: I enclose herewith 50c (Foreign add 25c for postage), for which you are to send me six back numbers of RADIO & TELEVISION as follows:

Name .....  
Address .....  
City ..... State .....

# An U.H.F. Receiver For "FM" and "AM"

S. Gordon Taylor

● THE public is showing definite signs of active interest in the new FM broadcasting. Already *broadcast* listeners are buying receivers capable of tuning in both the regular and FM programs. But what is the radio enthusiast whose interest extends beyond *broadcast* programs going to do about it. Is he going to be satisfied to have equipment which tunes only a single limited range of the ultra-high frequency spectrum—the range of 40 to 50 megacycles where FM is to hold forth, for instance? Or will he want to "go the whole hog" and equip himself to tune over the entire presently useful portion of the U.H.F. range of any from 30 to 100 mc. or higher? And isn't he going to want to listen in on services other than FM in this range?

Many hams and experimenters of the type that pioneered the now ordinary shortwaves have been pondering these questions—and many have come to the conclusion that they want to "shoot the works" by building or otherwise procuring equipment which will tune in not only the FM broadcasts, but the other FM and AM regular and experimental stations, the 5-meter and 2½-meter "ham" bands, the television *audio* broadcasts, etc. There is however, considerable doubt as to just what provisions all this calls for in a receiver. It is hoped that the following brief description of a receiver

made available to the public in recent months for these very purposes will help to clear up these doubts, or at least prove suggestive, both to those who plan to design and build their own equipment and those who plan to buy.

The Hallicrafters Model S-27 is a strictly *ultra-high* frequency receiver designed to provide complete reception facilities for the various types of services now operating (or planned) in these frequency ranges, with the exception of the video portions of television and the actual transcription of facsimile broadcasts.

It covers the continuous range of 27 to 145 megacycles in three bands of 27-45, 45-82 and 81-145 mc. and switches from one band to another in the same manner on the conventional shortwave receiver—and this, incidentally, is something which many have believed impossible without serious losses. But with demonstrated sensitivity of better than one microvolt throughout the 27-46 mc. band, two microvolts for the 45-82 mc. band, and 4 microvolts in the least sensitive spot of the 81-145 mc. range, this receiver definitely disproves the supposition that band-switching prevents attainment of high sensitivity.

The S-27 is a "communications" type receiver, with a relatively large number of controls to provide the needed flexibility for all-service operation. Its primary difference from the communications receivers so popular for tuning the lower frequencies lies in its provision for FM reception, including a much wider range of adjustable selectivity, and an audio system capable of super fidelity.

Its flexibility in operation is indicated by the following summary of the controls provided on the front panel. These include: Tuning "wheel" with illuminated main and *bandspread* dials, A.V.C. off-on switch, manual R.F. and audio gain controls, antenna trimmer condenser to insure accurate R.F. tracking despite loading variations of different antennas, broad-sharp I.F. expansion switch, automatic noise-limiter off-on switch, AM-FM changeover switch, beat-frequency oscillator off-on, B.F.O. pitch control, send-receiver switch, 4-position audio-filter tone control switch, band switch, headphone jack, and meter balance adjustment. The main dial is fully calibrated in megacycles and the *band-spread* dial carries the conventional 0-100 calibration. The meter, which is an "S" meter for AM operation, is automatically switched to serve as a carrier-center indicator for accurate FM tuning.

Diagram of the new Hallicrafters Model S-27 "FM" & "AM" Receiver.


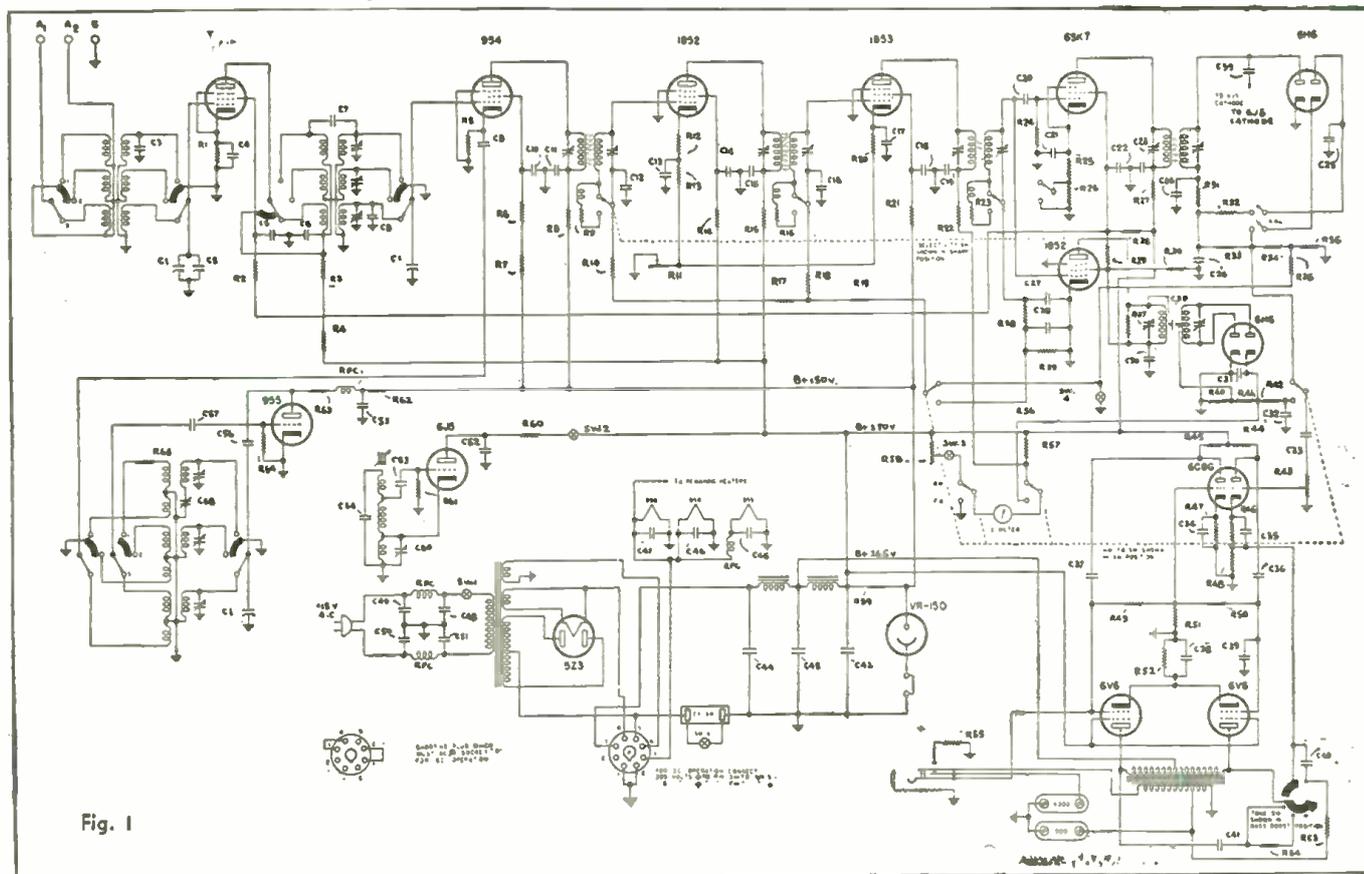


Fig. 1

# New Radio Apparatus

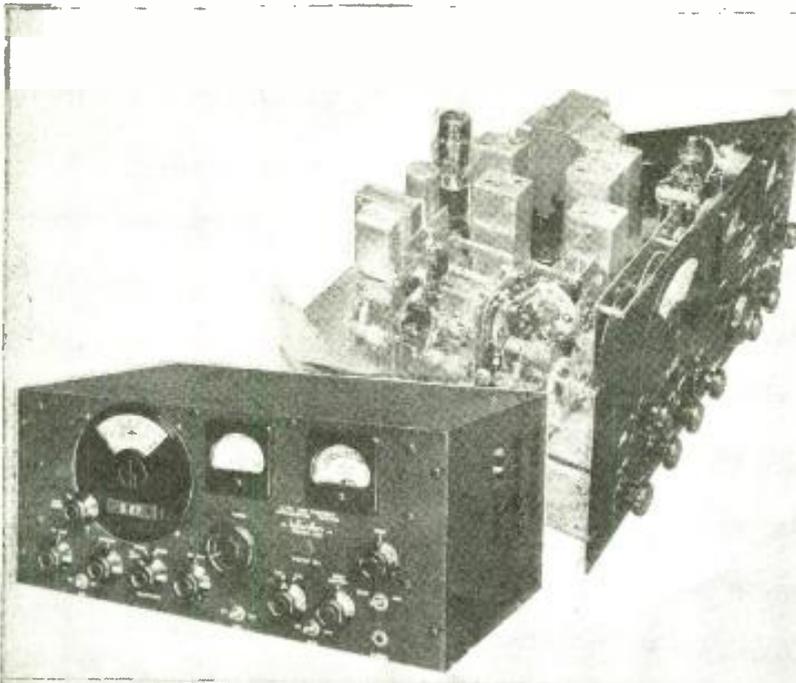

Front View—Combining the wide flexibility of a Communications receiver, with the tone quality of a fine broadcast receiver, this new model provides reception of both "FM" and "AM" stations, throughout the range of 27 to 145 megacycles.

Chassis View—Here the receiver is shown with one panel bracket and R.F. shield removed to disclose the assembly of the R.F. section. Acorn tubes are utilized in the R.F., oscillator and mixer stages for maximum sensitivity.

The complete circuit diagram with capacitor and resistor values appears in Figure 1. Of the total of 15 tubes, 11 are used for both FM and AM reception. These include the R.F. stage, mixer, oscillator, 2 I.F. stages, audio amplifier and phase-inverter stage, push-pull output stage, B.F.O., voltage-regulator tube, and rectifier. When the AM-FM switch is set for AM reception an additional, sharply tuned I.F. stage is inserted in the circuit, plus a diode which serves both as detector and automatic noise-limiter. In the FM position a *limiter* tube and the *discriminator-detector* are substituted for these two. The movement of this switch also automatically makes all other necessary circuit changes, including switching of the meter and of the A.V.C. systems.

At the ultra-high frequencies the R.F. circuits become especially critical as the tubes employed, circuit design and parts layout. The S-27 is one of the first standard receivers to employ acorn tubes. Not only are these capable of higher gain, but their low internal capacity is much more favorable for such circuits, where absolute minimum capacities are essential to efficient operation and wide-range coverage. Tubes of this type are employed for the R.F. stage, oscillator, and mixer. They are mounted projecting through the interstage shield partitions in such position that their grid and plate leads (which are at opposite ends of the tubes are right at the circuits with which they are associated. Other leads are kept to minimum length also. This is accomplished by the carefully planned R.F. layout (shown with its shield cover removed in one of the accompanying photos) in which the coils are mounted directly on the gang-switch terminals, the tuning gang is immediately adjacent to the switch assembly, etc.

The entire R.F. assembly is not only separately shielded but is on a separate sub-chassis, point-supported on the main chassis to eliminate microphonic vibration trouble.

To insure normal life for these acorn tubes, their plates have only 150 volts applied. This supply voltage for both oscillator and mixer is held constant by a VR-150 voltage regulator tube. This offsets line-voltage variations, stabilizes oscillator tuning and permits more uniform mixer operation.

One valuable point worth mentioning in particular is the oscillator coupling system in which a small pick-up coil, closely coupled to the oscillator grid coil, transfers the output to the mixer cathode circuit through a 300-mmf. condenser. This arrangement was adopted after all the conventional coupling and injection schemes failed to produce satisfactory results.

It may be well to point out that the intermediate frequency employed is 5.25 mc. This frequency avoids the peaked, side-band cutting characteristic that would obtain with the conventional low I.F. which, when expanded to maximum would not provide satisfactory band-width for FM reception. Also, this high I.F. results in far better image selectivity.

## Parts List

RESISTORS		
No.	OHMS	WATTS
1	250	1/3
2	1,000	1/3
3	1,000	1/3
4	10,000	1/2
5	2,000	1/3
6	1,000	1/3
7	100,000	1/3
8	1,000	1/3
9	8	1/3
10	00,000	1/3
11	00,000	R. F. Gain Control
12	35	1/3

No.	OHMS	WATTS
13	120	1/3
14	40,000	1/3
15	300	1/3
16	8	1/3
17	100,000	1/3
18	100,000	1/3
19	00,300	1/3
20	200	1/3
21	1,000	1/3
22	300	1/3
23	8	1/3
24	500,000	1/3
25	300	1/3
26	5,000	1/3
27	1,000	1/3
28	7,500	1/3
29	2,000	1/3
30	25,000	1/2
31	50,000	1/3
32	1,000,000	1/3
33	100,000	1/3
34	250,000	1/3
35	500,000	1/3
36	250,000	1/3
37	15,000	1/3
38	50,000	1/3
39	250,000	1/3
40	100,000	1/3
41	100,000	1/3
42	200,000	1/3
43	500,000	Audio Gain Control
44	250,000	1/3
45	250,000	1/3
46	5,000	1/3
47	5,000	1/3
48	120	1/3
49	250,000	1/3
50	250,000	1/3
51	100,000	1/3
52	250	1/3
53	0,000	1/3
54	4,000	1/2
55	5,000	1/3
56	600,000	1/3
57	35	1/3 Wire Wound S. meter Zero Adjust
58	1,500	0 Wire Wound
59	3,200	1/2
60	25,000	1/3
61	50,000	1/3
62	300	1/3
63	5,000	1/3
64	20,000	1/3
65	35	1/3

## CONDENSERS

NO.	CAPACITY	VOLTS	TYPE
1	60 mrf	Per Section	Air
2	15 mmf	Ant. Transformer	3 Ceramics
3	5 mmf		Mica
4	.002 mfd		Mica
5	300 mmf		Mica
6	002 mfd		Mica
7	10. mmf		Ceramic
8	10. mmf		Ceramic
9	300 mmf		Mica
10	300 mmf		Mica
11	.01 mfd	600	Paper
12	.001 mfd		Mica
13	.02 mfd	400	Paper
14	.02 mfd	400	Paper
15	.01 mfd	600	Paper
16	.001 mfd		Mica
17	.02 mfd	400	Paper
18	.02 mfd	400	Paper
19	.01 mfd	600	Paper
20	50 mmf		Mica
21	.02 mfd	400	Paper
22	.02 mfd	400	Paper
23	.01 mfd	600	Paper
24	50 mmf		Mica
25	.05 mfd	400	Paper
26	50 mmf		Mica
27	100 mmf		Mica
28	500 mmf		Mica
29	25 mmf		Mica
30	.002 mfd		Mica
31	50 mmf		Mica
32	500 mmf		Mica
33	.05 mfd	∞	Paper
34	30 mfd	25	Electrolytic
35	30 mfd	25	Electrolytic
36	.05 mfd	400	Paper
37	35 mfd	400	Paper
38	20 mfd		Electrolytic
39	.002 mfd		Mica
40	.05 mfd	400	Paper
41	05 mfd	400	Paper
42	.1 mfd	350	Electrolytic
43	30 mfd	350	Electrolytic
44	10 mfd	400	Electrolytic
45	300 mmf		Mica
46	300 mmf		Mica
47	300 mmf		Mica
48	.01 mfd	600	Paper
49	.01 mfd	600	Paper
50	.01 mfd	600	Paper
51	.01 mfd	600	Paper
52	002 mfd		Mica
53	100 mmf		Mica
54	200 mmf		Ceramic
55	300 mmf		Mica
56	50 mmf		Ceramic
57	.001 mfd		Mica
58	450 mmf		Pad
59	2 mmf		Twisted Pair
60	25 mmf		B. O. Pitch Control Air

# Latest Radio Apparatus News

## New Interference Locator

● THE Interference Locator is an entirely new device, designed in cooperation with outstanding public utility engineers and radio interference specialists to provide an inexpensive, highly sensitive and rugged portable device for the location and isolation of radio interference elimination. It is equally useful in the hands of the radio serviceman who is interested only in "noise" complaints arising from electrical devices attached to power lines, or to the public utility engineer, whose job



An interference locator of improved type and fitted with a directional loop antenna.

it is to eliminate radio noise sources from the power or distribution line itself. In addition, the Sprague IL-2 Locator is ideally adapted for locating underground pipes.

The Locator operates either from self-contained batteries for portable operation, or directly from 115 volt A.C. or D.C. lines. It is equipped with directional loop antenna; an extensible pole antenna is also provided.

Tuning ranges selected by a switch are 500 to 1700 KC; 1.7 to 5 MC; and 15 to 32 MC. Sensitivity is such that an input signal of less than two microvolts will produce a deflection of 10% on the output meter scale. In addition to a loud-speaker unit, the Locator is equipped with a two-range calibrated output meter, thus providing a visual as well as audible measure of interference intensity. Headphones may be attached in locations where high extraneous noise levels exist. A calibrated volume control may be used with the output meter to measure interference suppression devices. Loop antenna can be switched to audio input as a search coil for audio frequency interference pick up or for use as a buried pipe finder. A special coaxial cable, complete with connectors is also available at extra cost, for remote use of pole antenna as a probe.

## New RCA Tubes

● THE Radiotron Division of RCA Mfg. Co. has announced the following new tubes: 3S4 Power Amplifier Pentode (miniature type); 815 Transmitting Push-Pull Beam Power Amplifier; 826 Transmitting Triode (for ultra-high frequency use); 866-A/866 Half-Wave Mercury-Vapor Rectifier; 1625 Transmitting Beam Power Amplifier (with 12.6-volt heater); 1626 Transmitting Triode (with 12.6-volt heater).


The 3S4 is intended for use in the output stage of light-weight A.C.-D.C. battery-operated portable equipment. This new tube has essentially the same characteristics as the miniature type 1S4, but is designed with a filament having a center-tap to permit of either a series-filament or a parallel-filament operating arrangement. The series arrangement requiring only 50 milliamperes has been provided especially for equipment utilizing a source of rectified power for the filament supply.

The 815 is a new push-pull beam power amplifier designed for radio amateur use at ultra-high frequencies. Its high efficiency and high power sensitivity permit full power input with very low driving power. A single 815 operated in push-pull class C telegraph service is capable of handling a power input of 75 watts with less than 1/4 watt of driving power at frequencies as high as 150 megacycles. The total maximum plate dissipation of the 815 is 25 watts. The 815 is also useful as a modulator and as a multiplier. A single 815 can modulate another 815 as power amplifier. In multiplier service, the 815 can be used as a doubler or tripler and at the same time drive an 815 as power amplifier. Mechanical features of the 815 include its balanced and compact structure of beam units, close electrode spacing, short internal leads to minimize lead inductance and resistance, and a "Micanol" wafer octal base. The heaters of the 815 are arranged for either 12.6- or 6.3-volt operation.

The 826 transmitting triode has been designed especially for use at ultra-high frequencies. It may be used as an oscillator, R.F. power amplifier, and frequency multiplier at maximum ratings at frequencies as high as 250 megacycles and at reduced ratings at frequencies as high as 300 megacycles. Maximum plate dissipation of the 826 is 60 watts in class C telegraph service. The 826 features a double-helical filament center-tapped within the tube so that effects of filament inductance can be minimized. In addition, two short, heavy leads are brought out from the grid and from the plate to individual terminals in order to reduce the inductance of these internal connections. All terminals are placed at one end of the bulb so that short leads can be used in neutralizing circuits.

The 866-A 866 is a new half-wave mercury-vapor rectifier to supersede the well-known RCA types 866-A and 866. This new tube combines the ability of the 866-A to withstand high peak inverse voltage and the ability of the 866 to conduct at relatively low applied voltage. The 866-A/866 employs a ceramic cap insulator and is constructed in a dome-top bulb. This construction minimizes danger of bulb cracks caused by corona discharge. An edgewise wound ribbon filament made of a new alloy material provides a large emission reserve and improved life. Two 866-A/866's operating in a full-wave rectifier are capable of delivering to the input of a choke-input filter a rectified voltage of 3180 volts at 0.5 ampere with good regulation.

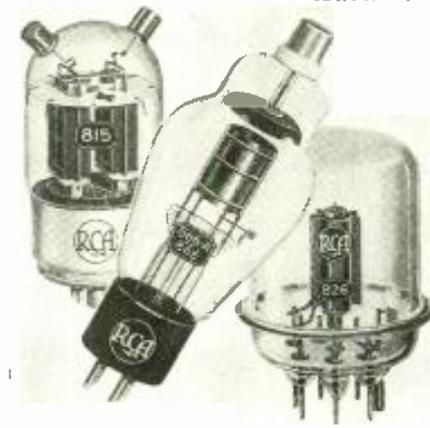The 1625 transmitting beam power amplifier is similar to RCA-807 but it has a 12.6-volt heater



Three new types of RCA tubes recently introduced—the 815 is a transmitting amplifier; the 826 a transmitting triode for UHF; the 866-A/866 a half-wave mercury vapor rectifier.

## In the February, 1941 Number of RADIO-CRAFT

- Opportunities in Military Radio
- Radio Blackout on the High Seas
- Radio Service Data Sheets
- Using a Radio Set to Test Radio Sets
- Visual Dynamic Servicing—Part II
- Modern Microphone Technique (Part I—The Microphone)
- Smallest Radio Tubes!
- "Electric Eye" Burglar Alarm
- F.M. 24-Watt Audio Amplifier—Part III

and a 7-pin base. Because of these features, the 1625 is particularly suitable for use in aircraft radio transmitters. The high power sensitivity of the 1625 makes it especially useful in frequency-multiplier service where high harmonic output is essential. It may also be used as a crystal-oscillator and buffer amplifier in medium-power transmitters with an input up to a half-kilowatt. The 1625 can be operated at maximum ratings at frequencies as high as 60 megacycles and at reduced ratings at frequencies as high as 125 megacycles. Its maximum plate dissipation rating is 30 watts (ICAS).

The 1626, a transmitting triode of the indirectly heated type with 12.6-volt heater, is designed especially for R.F. oscillator service in applications requiring unusual stability of characteristics. The maximum plate dissipation is 5 watts. The 1626 may be operated at maximum ratings at frequencies as high as 30 megacycles, and at reduced ratings at frequencies as high as 90 megacycles. Because of its 12.6-volt heater rating, the 1626 is particularly suitable for use in aircraft radio transmitters.

## 10-Channel Marine Radiophone

● TO its line of marine radiophones Hallicrafters, Inc., has added the "Seagoing" Model HT-12, a 50-watt unit which combines wide operating range with the utmost in operating simplicity. Receiving and transmitting channels, ten of each, are crystal-controlled to eliminate manual tuning, and manual switching is avoided through inclusion of a voice-controlled automatic relay system.

A corrosion proofed metal case, 20 inches square by 12 inches deep, houses both the transmitter and receiver sections. On its front panel are arranged the few simple controls, the telephone handset, a built-in loud-speaker and a meter which provides a visual check on transmitter operation. The power supply is a separate unit and is available in two types, one for direct operation from a 12-volt ship's battery, the other from a 110-volt A.C. source. This latter type also serves where the supply is either 32 or 110 volts D.C., a rotary converter being utilized to adapt it to these supplies.

With the receiver channel selector switch set for the channel of the nearest shore telephone station (or for the ship-to-ship channel) the owner can keep in constant touch with what is going on and will hear calls intended for him. In addition, provision is made for connection of an automatic bell ringer which will ring only when his boat is called.

The receiver is a sensitive and selective 7-tube superheterodyne with one stage of pre-selection, built-in I.F. wavetrap and highly effective A.V.C. and Q.A.V.C. systems.



A 10-Channel Marine Radiophone.

## New Bulletin by Amphenol

The new Amphenol blue book catalog No. 62 for 1941 has arrived. Every imaginable type of socket, plug, connector, etc., is illustrated and described therein. Also insulating materials and accessories of all kinds for radio, aircraft and electrical purposes. Insulating materials, coil forms, etc., of Amphenol 912-A and polystyrene insulated co-axial cables and fittings for HF and UHF applications are included. The catalog contains illustrations in detail of the newest co-axial cables for amateur use, as well as commercial applications. Steatite sockets and plugs are shown, loktal MIP sockets, a special 20-contact socket and plug for special cable connections, adapters of all kinds, test instrument accessories, miniature sockets and connectors, all types of microphone connectors, circuit-breaking power plugs, etc. Laboratory punch and dies for making holes in chassis are illustrated and described, and a goodly assortment of radio hardware. Plugs and sockets are now available in different colors, which is often desirable for special radio apparatus, especially "test" instruments.

# New Radio Apparatus

## Multi-Section Plug-in Filter



● **RECOGNIZING** the inefficiency of ordinary plug-in filters, engineers of the Sprague Products Company have designed LF-2, a special multiple section and inductance and capacity filter for use on very troublesome sources of radio interference. Designed for installation at the power outlet to which the interfering device is connected, the LF-2 unit takes much of the guesswork out of selecting the proper filter for any electrical device drawing up to ½ ampere. It has proved effective for interference-producing electrical shavers, hair dryers, erasing machines and similar electrical equipment.

These new types may be briefly described as follows:  
Type 6SD7GT is a semi-remote cutoff relatively high trans-conductance pentode, for use as an R.F. and I.F. amplifier.  
Type 6U6GT is a beam-power amplifier designed for reasonably high output, at lower supply voltage than normally required.  
Type 7L7 is a "lock-in" base sharp cut-off, relatively high trans-conductance pentode, for use where the higher trans-conductance types are not required.  
Type 7N7 is a "lock-in" base twin triode having separate cathode leads, with consequently increased circuit versatility.

## New Raytheon Tubes

● **FOUR** interesting new tubes have been introduced by the Raytheon Production Corporation. These recently developed tubes are the types 6SD7GT, 6U6GT, 7L7 and 7N7. The 6SD7GT and 6U6GT fall into the bantam category, while the 7L7 and 7N7 are of the "lock-in" type.

These new types may be briefly described as follows:

Type 6SD7GT is a semi-remote cutoff relatively high trans-conductance pentode, for use as an R.F. and I.F. amplifier.

Type 6U6GT is a beam-power amplifier designed for reasonably high output, at lower supply voltage than normally required.

Type 7L7 is a "lock-in" base sharp cut-off, relatively high trans-conductance pentode, for use where the higher trans-conductance types are not required.

Type 7N7 is a "lock-in" base twin triode having separate cathode leads, with consequently increased circuit versatility.

The 6SD7GT pentode, a semi-remote cutoff amplifier of the heater type, may be mounted in any position. It has a small wafer octal 8-pin base with metal shell. The heater voltage is 6.3 volts and the current .3 amp. Maximum plate voltage is 300. Maximum screen voltage 125; plate dissipation 4 watts.

The 6U6GT beam power amplifier is a heater type tube, can be mounted in any position and its base is an intermediate shell octal 7-pin. The tube has 6.3 volt heater and draws .75 amp. Maximum plate voltage is 200, screen voltage 135, plate dissipation 11 watts. The power output of this tube in class A1 is 5.5 watts with 200 volts on the plate.

The 7N7 twin triode amplifier of the heater type has a locking-in 8-pin base. This is a twin triode amplifier tube, designed for use as a voltage amplifier or phase inverter in radio receivers. Heater voltage is 7 and heater current is .64 amp. Maximum plate voltage is 300 and maximum plate dissipation per plate is 2.5 watts. The tube has an amplification factor of 20.

The 7L7 pentode is a sharp cutoff amplifier and has a locking-in 8-pin base. The tube has 7 volt heater and draws .32 amp. Maximum plate voltage 250 volts and maximum screen voltage 125. Plate dissipation 1.5 watts. This tube was designed for use as a high frequency or audio amplifier in radio receivers.

# COMMERCIAL NOTICES 10¢ A WORD

Under this heading only advertisements of a commercial nature are accepted. Remittance of 10¢ per word should accompany all orders. Copy should reach us not later than the 10th of the month for the second following month's issue.

**A.C. GENERATORS**  
110 VOLT A.C. AUTOMOBILE GENERATORS. Easily installed. Perfect performance. Operates amplifiers, movies, etc. LeJay Manufacturing, 150 LeJay Building, Minneapolis, Minn.

**BUSINESS OPPORTUNITIES**  
FOR SALE IN NORTHERN W. VA. town of 25,000, radio repair and sound equipment business. Owner in ill health; no reasonable offer refused. Write—Joseph R. Silverman, Phipps Clinic, Johns Hopkins Hosp., Baltimore, Md.

**DIATHERMY MACHINES**  
FOR SALE—DIATHERMY Machine, custom-built by radio engineer. Machine substantially built with high patient safety factor. 200-300 watts output. Neat professional appearance. Automatic safety time switches. All necessary pads and electrodes. 16 meters. Cost \$350.00. Will sacrifice for \$150.00

**MOTORS**  
RECONDITIONED MOTORS, 1/50 HP, AC-DC, Nickel \$1.50; 1/30 HP, Black \$2.50. Fully guaranteed. F.O.R.

Less than 1 year old. Will demonstrate. Write for appointment, L. Feldman, 566 W. 191st Street, Apt. 15, New York City.

**INSTRUCTION**  
LET A GRADUATE ELECTRICAL engineer help you solve your radio or electrical problems, large or small. Satisfaction guaranteed. Write details for price quotation. William Hayes, Box 1433-T, Oakland, California.

**\$15.00 S.T.E.A.M. ENGINEERING**  
(course—8 vols. \$4.50; Radio and Electrical text-book bargains—see list. Life of Napoleon, 3 de luxe volumes \$3.00. \$10.00 New Encyclopedia of Science, 1300 pp. \$4.50; Hopkins' "Experimental Science," 2 vols. \$3.50. Harry Ackerson, Box 322, Ramsey, N. J.

**CONDENSERS** 10 PIP, TUBES 10. Free lists. Butler, 1311-T McGee, Kansas City, Mo.

New York. Wonderful value limited quantity. Act Promptly! Gold Shield Products, Dept. 241, 350 Greenwich St., New York City.

**PATENT ATTORNEYS**  
INVENTORS — PROTECT YOUR rights before disclosing your invention to anyone. Form "Evidence of Conception," "Schedule of Government and Attorneys' Fees" and instructions sent free. Lancaster, Allwine & Rommel, 436 Bowen Building, Washington, D. C.

**QSL—CARDS—SWL**  
QSLs, SWLs. COLORFUL — Educational, W9KXL, 819 Wyandotte, Kansas City, Mo.

**RADIO PARTS**  
CONDENSERS 10 PIP, TUBES 10. Free lists. Butler, 1311-T McGee, Kansas City, Mo.

# FOR SALE (NON COMMERCIAL) 3¢ A WORD

Under this heading we accept advertisements only when goods are offered for sale without profit. Remittance of 3¢ per word should accompany all orders. Copy should reach us not later than the 10th of the month for the second following month's issue.

**RIDER'S MANUALS, VOLUMES I-VI**, complete and in brand new condition. \$25.00. E. Sontos, 33 Hinchman Ave., Dover, N. J.

**RECONDITIONED GUARANTEED** communications receivers cheap. Free trial. Terms. Hallcrafters, Nationals, Hammarlunds, RMEs, RCAs, Howards.

**and all other makes and models at low prices.** Write for free list. W9ARA, Butler, Missouri.

**DON'T BUY A RECEIVER UNTIL** you get my free list of reconditioned, guaranteed receivers! Practically all models at money saving prices. Trade-ins. Time Payments. Send for list.

W2AVA, 12 West Broadway, New York.

**NATIONAL SW3 A.C. FOR SALE**, good shape bandspread coils for the 20, 40, 80 meter bands minus power supply—\$10.00. W9CIP, H. Fulmer, 319 N. 69th St., Wauwatosa, Wis.

**WANTED REMOTE CONTROL** Motor tuners used on C-10nial 33-34 A.C. RCA 82-86 or Kolster Radios; Arvin tuner advertised in Wholesale Radio Catalog. Have 4 dozen prisms—cash. C. Vorlicek, 5105 Fleet Ave., Cleveland, Ohio.

**WILL SWAP S.W.-2, POWER SUPPLY**, practice oscillator, tubes. Want good S.W.—7-6 receiver, good condition. Anthony Conlin, 83 Westfield Rd., Holyoke, Mass.

**TRADE: RADIO TELEVISION TUBE** tester, Model T.V., very late model; Kato Converter, 32 volts, 110 volts. A.C., 150 watts; Rider's Manual No. one, for Sky Buddy, Gernsback's Manuals, Gottfried Strickert, Chilton, Wis.

**FAIR IRON CORE AIRTUNED 1800** Kc. I.F. transformers, metal cabinet, phones, 2 speed 5" dial, other parts. Want Brush phones, crystal pickup. J. McTigue, 30 Bennett Ave., Binghamton, N. Y.

**WILL TRADE 5 TO 8 TUBE** chassis, fine for practical experimental purposes; also old radio magazines and parts. Want photographic apparatus, stamps, tools, books, magazines or what have you? Highland, 315 N. Garfield, Arlington, Virginia.

**HAVE INSTRUMENTS FROM DIS-**mantled test bench, books, courses and short wave receiver, which will trade for what? Write for list and send me yours. T. G. Watt, Chanute, Kans.

**WANTED: A USED CANDLER** Junior Code Course. Please give conditions and lowest price. Helmut Jorzig, 1224 Bush St., Red Wing, Minn.

**SWAP: 5x8 PRINTING OUTFIT**, radio items, fluorescent lighting equipment, photographic items, etc. Want: Misc. printing equipment, photographic items. Model R.I. equipment, etc. Your list for mine. Hansen, Box 41, Albert Lea, Minn.

**WILL TRADE RADIO EQUIPMENT**, including tube super climber receiver, 410 Radio City Multitester, Telex Code Sender which is spring wound, and other equipment. Write to Harvie Williamson, Quitaque, Texas.

**SWAP RADIO MAGAZINES—7 QST**, 13 Itadio News, 2 Radio, 7 Radio-Craft, 1939 and 1940 issues; 24 Radio & Television, 1939-1940. All 53 magazines for a Mystery Record Player or write to T. Marks, 109-19 96th St., Ozone Park, L. I., N. Y.

**TRADE A NUMBER OF OLD AND** new style tubes, all used. A-1 condition, also odds and ends of radio equipment, for meters, test equipment. Radio text books preferred. Please send letter giving full details. All letters answered, lists exchanged. Joseph Erdell, 75 W. 85th St., New York City.

Wanted: USED AMATEUR RECEIVER, also small transmitter. Walter Blumer, Stoughton, Wis.

**HAVE: AUTOMATIC RIFLE, PIANO** accordion, radios, books, code machines. Want: Communication receiver, books—Modern Radio Series, (Artistic Modulation, Oscillators at Work and all Rider books, James Smith, Box 612, Spindale, N. C.

**WANTED: BROADCAST RECEIVERS** and parts for public address, pickups, mikes, etc. Answer all letters. K. Dussil, 1906 5th Ave., Belleplaine, Iowa.

**WHAT TRADE AM I OFFERED** for new Candler Code course, Hicok Tube Test, U.H.F. Paris, Television Equipment and Photo Cell-Helay complete. Steve Novota, Jr., 406 S. Plum St., Mowasqua, Ill.

**WANTED: USED AMATEUR RE-**ceiver, also small transmitter. Walter Blumer, Stoughton, Wis.

**HAVE: AUTOMATIC RIFLE, PIANO** accordion, radios, books, code machines. Want: Communication receiver, books—Modern Radio Series, (Artistic Modulation, Oscillators at Work and all Rider books, James Smith, Box 612, Spindale, N. C.

**WANTED: BROADCAST RECEIVERS** and parts for public address, pickups, mikes, etc. Answer all letters. K. Dussil, 1906 5th Ave., Belleplaine, Iowa.

**WHAT TRADE AM I OFFERED** for new Candler Code course, Hicok Tube Test, U.H.F. Paris, Television Equipment and Photo Cell-Helay complete. Steve Novota, Jr., 406 S. Plum St., Mowasqua, Ill.

**WANTED: USED AMATEUR RE-**ceiver, also small transmitter. Walter Blumer, Stoughton, Wis.

**HAVE: AUTOMATIC RIFLE, PIANO** accordion, radios, books, code machines. Want: Communication receiver, books—Modern Radio Series, (Artistic Modulation, Oscillators at Work and all Rider books, James Smith, Box 612, Spindale, N. C.

**WANTED: BROADCAST RECEIVERS** and parts for public address, pickups, mikes, etc. Answer all letters. K. Dussil, 1906 5th Ave., Belleplaine, Iowa.

**WHAT TRADE AM I OFFERED** for new Candler Code course, Hicok Tube Test, U.H.F. Paris, Television Equipment and Photo Cell-Helay complete. Steve Novota, Jr., 406 S. Plum St., Mowasqua, Ill.

**WANTED: USED AMATEUR RE-**ceiver, also small transmitter. Walter Blumer, Stoughton, Wis.

**HAVE: AUTOMATIC RIFLE, PIANO** accordion, radios, books, code machines. Want: Communication receiver, books—Modern Radio Series, (Artistic Modulation, Oscillators at Work and all Rider books, James Smith, Box 612, Spindale, N. C.

**WANTED: BROADCAST RECEIVERS** and parts for public address, pickups, mikes, etc. Answer all letters. K. Dussil, 1906 5th Ave., Belleplaine, Iowa.

**WHAT TRADE AM I OFFERED** for new Candler Code course, Hicok Tube Test, U.H.F. Paris, Television Equipment and Photo Cell-Helay complete. Steve Novota, Jr., 406 S. Plum St., Mowasqua, Ill.

**WANTED: USED AMATEUR RE-**ceiver, also small transmitter. Walter Blumer, Stoughton, Wis.

**HAVE: AUTOMATIC RIFLE, PIANO** accordion, radios, books, code machines. Want: Communication receiver, books—Modern Radio Series, (Artistic Modulation, Oscillators at Work and all Rider books, James Smith, Box 612, Spindale, N. C.

**WANTED: BROADCAST RECEIVERS** and parts for public address, pickups, mikes, etc. Answer all letters. K. Dussil, 1906 5th Ave., Belleplaine, Iowa.

**WHAT TRADE AM I OFFERED** for new Candler Code course, Hicok Tube Test, U.H.F. Paris, Television Equipment and Photo Cell-Helay complete. Steve Novota, Jr., 406 S. Plum St., Mowasqua, Ill.

**WANTED: USED AMATEUR RE-**ceiver, also small transmitter. Walter Blumer, Stoughton, Wis.

# BARTER AND EXCHANGE — 1¢ A WORD

NO ADVERTISEMENT TO EXCEED 35 WORDS, INCLUDING NAME AND ADDRESS

Space in this department is intended solely for the benefit of our readers, who wish to BUY or EXCHANGE anything in the Radio, Television and Photographic fields for Radio, Photographic and other merchandise; therefore we charge only 1¢ a word. Each word in a name and address is counted. Remittance should accompany order.

Only one advertisement can be accepted from any reader in any one issue.

Copy should reach us not later than the 10th of the month for the second following month's issue.

We cannot accept responsibility for any statements made by the readers.

All dealings MUST be above board. Remember you are using the U. S. mail in all these transactions and therefore you are bound by the U. S. Postal Laws. Describe anything you offer accurately and without exaggeration. Treat your fellow men the way you wish to be treated.

We welcome suggestions that will help to make this department interesting and helpful to our readers.

**SWAP: HIGH POWERED RIFLE**, 14 watt amplifier with 12" speaker, 15" Jensen Electro dynamic Speaker, Electronics Magazine, 37-40, Hammarlund dual 35 condensers, 1 1/2" hole saw, for anything in radio. Need receiver. Stanley Garner, 29 W. Chestnut St., Norristown, Pa.

**INTERESTED IN A GOOD 4x5** speed graphic or movie and still photographic equipment. Also want experimental radio parts in good condition. Send me your list and state your needs. George Pitherny, 54 East 100 St., New York City.

**TRADE IN ON A GOOD COMMUN-**ications receiver such as RME, National or Hammarlund; Astatic T-40 crystal microphone, also 1940 Sks Selector with built-in Pre-selector and noise silencer. Both perfect condition. W. L. States, 9205 Whitney Ave., Elmhurst, L. I., N. Y.

**HAVE: NATIONAL FB-7 COM-**plete, radio parts, magazines. Want: Universal Clipper or similar receiver. James Gruhschak, 93 Westbury Park, Watertown, Conn.

**TRADE: BROADCAST RECEIVERS** and parts for public address, pickups, mikes, etc. Answer all letters. K. Dussil, 1906 5th Ave., Belleplaine, Iowa.

**WHAT TRADE AM I OFFERED** for new Candler Code course, Hicok Tube Test, U.H.F. Paris, Television Equipment and Photo Cell-Helay complete. Steve Novota, Jr., 406 S. Plum St., Mowasqua, Ill.

**WANTED: USED AMATEUR RE-**ceiver, also small transmitter. Walter Blumer, Stoughton, Wis.

**HAVE: AUTOMATIC RIFLE, PIANO** accordion, radios, books, code machines. Want: Communication receiver, books—Modern Radio Series, (Artistic Modulation, Oscillators at Work and all Rider books, James Smith, Box 612, Spindale, N. C.

**WANTED: BROADCAST RECEIVERS** and parts for public address, pickups, mikes, etc. Answer all letters. K. Dussil, 1906 5th Ave., Belleplaine, Iowa.

**WHAT TRADE AM I OFFERED** for new Candler Code course, Hicok Tube Test, U.H.F. Paris, Television Equipment and Photo Cell-Helay complete. Steve Novota, Jr., 406 S. Plum St., Mowasqua, Ill.

**WANTED: USED AMATEUR RE-**ceiver, also small transmitter. Walter Blumer, Stoughton, Wis.

**HAVE: AUTOMATIC RIFLE, PIANO** accordion, radios, books, code machines. Want: Communication receiver, books—Modern Radio Series, (Artistic Modulation, Oscillators at Work and all Rider books, James Smith, Box 612, Spindale, N. C.

**WANTED: BROADCAST RECEIVERS** and parts for public address, pickups, mikes, etc. Answer all letters. K. Dussil, 1906 5th Ave., Belleplaine, Iowa.

**WHAT TRADE AM I OFFERED** for new Candler Code course, Hicok Tube Test, U.H.F. Paris, Television Equipment and Photo Cell-Helay complete. Steve Novota, Jr., 406 S. Plum St., Mowasqua, Ill.

**WANTED: USED AMATEUR RE-**ceiver, also small transmitter. Walter Blumer, Stoughton, Wis.

**HAVE: AUTOMATIC RIFLE, PIANO** accordion, radios, books, code machines. Want: Communication receiver, books—Modern Radio Series, (Artistic Modulation, Oscillators at Work and all Rider books, James Smith, Box 612, Spindale, N. C.

**WANTED GOOD 8MM CAMERA** and projector. Will pay cash or trade. C. Ostron, 8247 4th Ave., N.E., Seattle, Wash.

**WILL TRADE 5 TO 8 TUBE** chassis, fine for practical experimental purposes; also old radio magazines and parts. Want photographic apparatus, stamps, tools, books, magazines or what have you? Highland, 315 N. Garfield, Arlington, Virginia.

**HAVE INSTRUMENTS FROM DIS-**mantled test bench, books, courses and short wave receiver, which will trade for what? Write for list and send me yours. T. G. Watt, Chanute, Kans.

**WANTED: A USED CANDLER** Junior Code Course. Please give conditions and lowest price. Helmut Jorzig, 1224 Bush St., Red Wing, Minn.

**SWAP: 5x8 PRINTING OUTFIT**, radio items, fluorescent lighting equipment, photographic items, etc. Want: Misc. printing equipment, photographic items. Model R.I. equipment, etc. Your list for mine. Hansen, Box 41, Albert Lea, Minn.

**WILL TRADE RADIO EQUIPMENT**, including tube super climber receiver, 410 Radio City Multitester, Telex Code Sender which is spring wound, and other equipment. Write to Harvie Williamson, Quitaque, Texas.

**SWAP RADIO MAGAZINES—7 QST**, 13 Itadio News, 2 Radio, 7 Radio-Craft, 1939 and 1940 issues; 24 Radio & Television, 1939-1940. All 53 magazines for a Mystery Record Player or write to T. Marks, 109-19 96th St., Ozone Park, L. I., N. Y.

**TRADE A NUMBER OF OLD AND** new style tubes, all used. A-1 condition, also odds and ends of radio equipment, for meters, test equipment. Radio text books preferred. Please send letter giving full details. All letters answered, lists exchanged. Joseph Erdell, 75 W. 85th St., New York City.

**WANTED REMOTE CONTROL** Motor tuners used on C-10nial 33-34 A.C. RCA 82-86 or Kolster Radios; Arvin tuner advertised in Wholesale Radio Catalog. Have 4 dozen prisms—cash. C. Vorlicek, 5105 Fleet Ave., Cleveland, Ohio.

**WILL SWAP S.W.-2, POWER SUPPLY**, practice oscillator, tubes. Want good S.W.—7-6 receiver, good condition. Anthony Conlin, 83 Westfield Rd., Holyoke, Mass.

**TRADE: RADIO TELEVISION TUBE** tester, Model T.V., very late model; Kato Converter, 32 volts, 110 volts. A.C., 150 watts; Rider's Manual No. one, for Sky Buddy, Gernsback's Manuals, Gottfried Strickert, Chilton, Wis.

**FAIR IRON CORE AIRTUNED 1800** Kc. I.F. transformers, metal cabinet, phones, 2 speed 5" dial, other parts. Want Brush phones, crystal pickup. J. McTigue, 30 Bennett Ave., Binghamton, N. Y.

**WANTED: USED AMATEUR RE-**ceiver, also small transmitter. Walter Blumer, Stoughton, Wis.

**HAVE: AUTOMATIC RIFLE, PIANO** accordion, radios, books, code machines. Want: Communication receiver, books—Modern Radio Series, (Artistic Modulation, Oscillators at Work and all Rider books, James Smith, Box 612, Spindale, N. C.

**WANTED: BROADCAST RECEIVERS** and parts for public address, pickups, mikes, etc. Answer all letters. K. Dussil, 1906 5th Ave., Belleplaine, Iowa.

**WHAT TRADE AM I OFFERED** for new Candler Code course, Hicok Tube Test, U.H.F. Paris, Television Equipment and Photo Cell-Helay complete. Steve Novota, Jr., 406 S. Plum St., Mowasqua, Ill.

**WANTED: USED AMATEUR RE-**ceiver, also small transmitter. Walter Blumer, Stoughton, Wis.

## SWL EXCHANGE

This department is for the benefit of all short wave listeners who wish to exchange SWL cards. Remittance of 1¢ a word for each word in the name and address should accompany order.

**UNITED STATES**  
PAUL ANKERMAN, 401 Lima Street, Wapakoneta, Ohio.

O. BARNESON, 6332 Metropolitan Station, Los Angeles.

JAMES BRUNSELL, 5105 N. Winchester, Chicago, Ill.

JOHN BURROWS, 17 Avon Lane, Westbury, N. Y.

CLYDE MOSS, JR., 586 Inn Street, Chillicothe, Ohio.

BILL WHITE, 1910 Hughtt Ave., Superior, Wisconsin.

## YOU Are the Editor

(Continued from page 581)

4. If, and when experimental wireless facilities are restored, the question of an adjustment of fees and of the grant of fresh licenses will be given consideration. (This was in answer to the following question,—“Will new licenses for transmitting have to be taken out after the war, or will

those holding them at the time of confiscation be able to carry on with the old license until the number of months, etc., for which it is still available are ended?”

R. LAWTON, Secretary, North Manchester Radio & Television Society, Manchester, England.

Address—Readers' Editorials, RADIO & TELEVISION, 20 Vesey Street, New York, N. Y.

## FREE CATALOGS and INFORMATION

By carefully reading the advertising columns, you will find many offers to furnish literature containing valuable technical information that will help you in your work. Use this list freely.

Firm	Business	Offer	No.	Cost	Adv. Page
ABC Radio Laboratories Allied Engineering Institute Allied Radio Corp.	Set Mfr.	Information		Free	610
	Kit Mfr.	Circulars		Free	609
	Mail Order	1941 Radio Catalog New Radio Dictionary Radio Builder's Handbook		Free 10c 10c	591.97
American Radio Institute Amperite Co. Ayers, Automatic Code Machines Bliley Electric Co.	Radio School	Booklet		Free	579
	Parts Mfr.	Replacement Chart	"S"	Free	604
	Code Machines	Information		Free	617
	Parts Mfr.	Circular	D-2	Free	601
		Engineering Bulletin	E-6	10c	
		Bulletin	E-7	Free	
		Circular	A-7	Free	
Bridge, Harry P. Bud Radio, Inc. Burststein-Applebee Co. Candler System Co. Cannon, C. F., Co. Chartered Institute of American Inventors Cowell, R. A. Dodge's Institute Goldentone Radio Co. Gold Shield Products	Stamps	Information		Free	620
	Parts Mfr.	Literature		Free	596
	Mail Order	1941 Catalog	57	Free	615
	Code Course	Book of Facts		Free	601
	Parts Mfr.	Folder	T-20	Free	604
	Inventors Organization	Booklet		Free	632
	Publisher's Rep.	Information		Free	579
	Radio School	Catalog		Free	579
	Set Mfr.	1941 Bargain Catalog		Free	614
	Mail Order	Catalog		Free	610, 12, 14, 22, 32
Hallicrafters, Inc. Hammarlund Mfg. Co. Harrison Radio Co. Harvey Radio Company Henry Radio Shop Hudson Specialties Co. Hytron Laboratories Instructograph Company Johnson, E. F., Co.	Set Mfr.	Literature		Free	B.C.
	Set & Parts Mfr.	"HQ" Booklet		Free	605
	Mail Order	Information—List		Free	610
	Mail Order	Information		Free	603
	Mail Order	Information		Free	604
	Mail Order	Catalog		Free	631
	Tube Mfr.	Information		Free	597
	Code Machine	Information		Free	615
	Parts Mfr.	Catalog	966W	Free	607
		Antenna Handbook		25c	
		Booklet		Free	632
	Lancaster, Allwine & Rommel Mass. Radio School Meissner Mfg. Co. Midget Radio Co. Midwest Radio Corp. Miles Reproducer Co. Millen, J., Mfg. Co., Inc. National Company, Inc. National Radio Institute National Schools Nelson Co. N. Y. Institute of Photography New York Y.M.C.A. Schools Premax Products Radio & Technical Publ. Co. Radiocrafters RCA Institutes, Inc. Remington Rand Sprague Products Company Sprayberry Acad. of Radio Supreme Publications Teleplex Co. Triplet Electrical Inst. Co. Universal Microphone Co., Ltd.	Patent Attorneys	Booklet		Free
Radio School		60-Page Catalog		Free	579
Kit & Parts Mfr.		1941 Catalog		Free	595
Set Mfr.		Information		Free	615
Set Mfr.		1941 Catalog		Free	615
Sound Recording		Bulletins		Free	617
Parts Mfr.		Catalog		Free	596
Set & Parts Mfr.		Literature		Free	I.F.C.
Radio School		64-Page Book		Free	577
Radio School		Catalog		Free	579
Used Courses		72-Page Catalog		Free	604
Photography School		Booklet		Free	579
Trade School		Booklet		Free	579
Parts Mfr.		Catalog	R-49	Free	596
Radio Textbooks		Circulars on each book		Free	579
Parts Mfr.		Information		Free	601
Radio School		Catalog		Free	579
Typewriter Mfr.		Catalog		Free	611
Parts Mfr.	Catalog		Free	601	
Radio School	52-Page Book		Free	I.B.C.	
Publisher	Information		Free	613	
Code Machines	Folder	S-2	Free	579	
Parts Mfr.	Catalog		Free	607	
Parts Mfr.	Information		Free	614	

### New "Hamannual"

● THE fifth edition of the "Hamannual" has just been announced by the Standard Transformer Corporation. This is a 48 page, two color catalog which describes completely twelve different transmitters and six amplifiers. A complete circuit is given on each unit in blueprint form. All the component parts lists are shown, together with the original manufacturers' part numbers.

This year for the first time a complete array of power-supply kits is offered.

Many other new features are incorporated in the book. The Hamannual is available either from the Stancor distributor or direct from the factory at 15 cents net.

### Bulletin Analyzes Radio Interference Faults

● SERVICEMEN who have made it a point to study radio interference elimination as a means to increased profits in this rapidly growing phase of the business, will find much of general interest in an entirely new 8-page bulletin, "Radio Interference Elimination for Public Utilities," just issued by Sprague Products Company.



This includes a complete description of the causes and cures of radio interference on power transmission and distribution lines as developed by Sprague engineers in more than three years of field and laboratory work. Although it is written primarily from the angle of the public utility company and deals with problems relating directly to public utility power lines, the booklet should prove helpful to servicemen who specialize in interference elimination work. It will serve as a guide in helping them diagnose radio noise complaints.

A copy will be sent free upon request to bona fide radio servicemen.

### New Meissner Catalog

● THE new 1941 general catalog showing the various products of the Meissner Manufacturing Company has come to the reviewer's desk. This is an unusually interesting catalog, as it contains description and illustration of "frequency modulation" chassis and parts for building such a receiver. Also we note complete FM console and table models in cabinets. Television receiver "kits" are also listed and we find a liberal assortment of receiving set kits, including a 12-tube all-wave "home" receiver. Other receiving set kits include 7, 8, and 9 tube jobs; student midget set; A.C.-D.C. portable superhet; and 4, 5, and 6 tube receiving set kits. Another section of the catalog covers P.A. tuners and kits, the new Meissner Analyst (a test instrument for servicemen), a signal calibrator, all-wave tuning units, phono oscillators, I.F. transformers of both the air and iron-core type, etc. Other apparatus covered in the catalog are—filters, R.F. chokes, variable condensers, and several interesting dials—including those with "hand-spread."

### Sun Sound Systems Catalog

● SUN RADIO CO. of New York City has just released an illustrated 24-page public address booklet that should prove of interest to all in the sound field. Among the equipment described and illustrated are amplifiers and sound systems of every type and classification, including portable systems, mobile systems and complete indoor and outdoor installations suitable for the smallest auditorium or the largest arena or stadium. In addition, a number of pages are devoted to such P.A. accessories as microphones, speakers, pickups, phono motors, tuners, recorders, etc. A copy of the catalog will be gladly sent to interested persons upon request.




# FREE TO YOU!
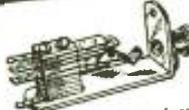
## RADIO PARTS AND ACCESSORIES

HERE is some real BIG NEWS for you! Through a fortunate arrangement which we have been able to make, we can now offer you FREE premiums of such extraordinary value that they overshadow anything we have ever offered in the past with subscriptions to RADIO & TELEVISION Magazine.

NEVER BEFORE, in the 11 years' history of the magazine, have we offered such worthwhile premiums. All of these radio parts and accessories can be used to good advantage by the "ham" or constructor in his daily experiments.



**TELEPHONE JACK**  
Substantial long frame phone jack, 2-circuit filament control type. Opens 2 circuits, closes 3rd when plug is inserted. variety of control purposes in radio and telephone work. 2 3/4" long, 1" high. Ship. weight 4 oz.  
**Premium No. 1 (3 Pts.) Val. 35c.**



**PUNCHED CHASSIS**  
Heavy plated steel chassis with holes punched for 11 tubes, power transformer, speaker, plug and tuning dial. Great for large experimental sets, transmitters, etc. Reinforced construction. 13"x7 1/2"x2 1/4". Ship weight 3 lbs.  
**Premium No. 2 (5 Pts.) Val. 25c.**




**TWO GANG POTENTIOMETER**  
Well-made Yaxley 2 gang wire wound potentiometer. 2 units are insulated from each other. One is 5000, the other is dual action volume control (antenna and bias in broadcast receiver). Also useful in experimental circuits. Ship. weight 1 lb.  
**Premium No. 3 (5 Pts.) Val. 25c.**



**ALLOY CHASSIS**  
Medium weight alloy metal chassis punched for power transformer and 8 tubes as well as numerous mounting holes. Easily drilled metal. Open ends. Well made 10 3/4"x6 1/2"x2 1/2". Ship. weight 2 lbs.  
**Premium No. 4 (5 Pts.) Val. 25c.**

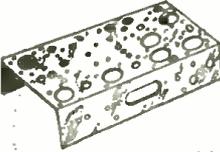These parts are given to you IN ADDITION to the cut-rate subscription prices we list below:  
7 mos. for \$1 (saving you 75c over the single-copy price)  
16 mos. for \$2 (saving you \$2 over the single-copy price)  
24 mos. for \$3 (saving you \$3 over the single-copy price)



**7 TUBE CHASSIS**  
Alloy metal chassis punched for 7 tubes, condensers, etc. Ideal for building small sets or simple apparatus. Metal is easy to drill. Size 10 1/2"x5 3/4"x2". Ship. wgt. 2 lbs.  
**Premium No. 5 (5 Pts.) Val. 25c.**



**CONNECTING CABLE & TERMINAL**  
Unusually well made Philco 8 foot, 5 wire cable with spade terminals at one end and terminal block with 8 positions at other end. Wires color coded. Well insulated. May be used for remote control or battery connections, etc. Terminal block 3"x3"x3/4". Ship. weight 1 lb.  
**Premium No. 6 (6 Pts.) Val. 35c.**

And, of course, the longer your subscription runs, the more merchandise you obtain FREE. As we expect a tremendous response to this offer, we would suggest that you send your remittance without delay, as our supply of parts is limited and we won't be able to duplicate this offer again.



**LOUDSPEAKER UNIT**  
Kellox magnetic loudspeaker unit for use with horn speaker. Has adjustable diaphragm. May be used as pillow speaker or attached to acoustic phonograph. Also useful as sensitive microphone for voice reproduction. Threaded (7/8" diam.) throat. Size 2 1/2" diam., 1 1/2" deep. Ship. wgt., 2 lbs.  
**Premium No. 7 (10 Pts.) Val. 75c.**

**IF YOU ARE A RADIO EXPERIMENTER, AMATEUR OR SERVICEMAN, TAKE ADVANTAGE OF THIS MARVELOUS OPPORTUNITY NOW!**

A SHORT while ago we were informed that one of the largest surplus houses in the East was ready to sacrifice a huge quantity of radio parts and accessories which cost the original manufacturers thousands of dollars. We entered into an agreement with this house whereby we suggested to them to allow us to offer these parts to our readers in connection with subscription offers. The surplus house enthusiastically endorsed our plan. We—the publishers—pay the surplus house cash for each of these parts, and you—the reaper of this fortunate arrangement—will get these valuable radio parts and accessories ABSOLUTELY FREE. This is positively the first time that we have been enabled to make such an unprecedented offer which in many ways sounds too good to be true. Nevertheless, we vouch for it in every way and we know you will not be disappointed. This special arrangement enables us to offer you this valuable merchandise FREE with your subscription to RADIO & TELEVISION magazine, at a price which is already a tremendous saving over the newsstand cost. This is how the plan works:— Next to the premium number of each item, we show its point value.

- For each 7 months' subscription (\$1.00) you receive 15 points' worth of merchandise free.
- For each 16 months' subscription (\$2.00) you receive 30 points' worth of merchandise free.
- For each 24 months' subscription (\$3.00) you receive 45 points' worth of merchandise free.

For instance, if you send us a seven months' subscription at \$1.00, you are entitled to 15 points' worth of free merchandise. You may order one No. 4 (5 points) and one No. 7 (10 points). Or if you wish, one each of numbers 2, 3 and 4 (each 5 points), or any other combination which totals 15 points.

Similarly, if you send us a 16 months' subscription (\$2.00) you may order any combination of merchandise which totals 30 points. On a 24 months' subscription (\$3.00), any combination totalling 45 points. Due to the high cost of the merchandise, we cannot ship the articles

prepaid, therefore we show the weight of each piece, packed. If you wish your free parts sent by parcel post, please add to your remittance a sufficient amount to cover postage. Or, if you would rather have us send the parcel express charges collect, we will be glad to do so.

Please remember that we do not sell these articles. You cannot buy them from us at any price. In order to make sure that you receive your parts promptly, ORDER TODAY. Fill out the coupon, clip and mail to us together with the proper remittance.

**ALL RADIO PARTS ARE NEW AND UNUSED**  
Many are in their Original Packing

**IMPORTANT TO PRESENT SUBSCRIBERS**  
If you are already a subscriber or have recently subscribed to the magazine, this offer still holds good for you, too. We merely will lengthen your subscription for either 7 months, 16 months or 24 months, as the case may be. There is a place on the coupon which provides for this.

**RADIO & TELEVISION, 20 Vesey Street, New York, N. Y. RT-241**

Please enter my subscription to RADIO & TELEVISION for

- 7 months—\$1.00. Plus 15 points' worth of FREE radio parts.
- 16 months—\$2.00. Plus 30 points' worth of FREE radio parts.
- 24 months—\$3.00. Plus 45 points' worth of FREE radio parts.
- I enclose my remittance for \$..... which includes parcel post charges on the FREE parts I am ordering.
- Please send the merchandise to me express charges collect.
- I am a subscriber now. Lengthen my subscription for ..... months:

I am circling the numbers of the parts I wish to have you send me Free.  
Nos. 1 2 3 4 5 6 7

Name ..... Address .....

City ..... State .....

(Send remittance in form of check or money order. If you send cash or unused U. S. postage stamps, be sure to register your letter.)

**DON'T MISS THIS OPPORTUNITY! WE ASSURE YOU THAT YOU WON'T BE DISAPPOINTED. ORDER TODAY! SIMPLY FILL OUT THE COUPON. PROMPT SHIPMENT ASSURED!**

**RADIO & TELEVISION**  
20 VESEY STREET  
NEW YORK, N. Y.

Index to Advertisers

<b>A</b>	
ABC Radio Laboratories	610
Allied Engineering Institute	609
Allied Radio Corporation	591, 597
American Radio Institute	579
Amperite Co.	604
Ayers Automatic Code Machines	617
<b>B</b>	
Barter & Exchange Ads.	637
Biley Electric Co.	601
Bridge, Harry P.	620
Bud Radio, Inc.	596
Burstein-Applebee Co.	615
<b>C</b>	
Candler System Co.	601
Cannon, C. F., Co.	604
Chartered Institute of American Inventors	632
Commercial Notices	637
Cowell, R. A.	579
<b>D</b>	
Dataprint Company	614, 619
Dodge's Institute	579
<b>F</b>	
Flight Magazine	612
For Sale Ads	637
<b>G</b>	
Goldentone Radio Co.	614
Gold Shield Products	610, 612, 614, 622, 632
<b>H</b>	
Hallicrafters, Inc.	Back Cover
Hammarlund Manufacturing Co., Inc.	605
Harrison Radio Co.	610
Harvey Radio Company	603
Henry Radio Shop	604
Hudson Specialties Company	631
Hytron Laboratories	597
<b>I</b>	
Instructograph Company	615
<b>J</b>	
Johnson, J. F., Co.	607
<b>L</b>	
Lancaster, Allwine & Rommel	632
<b>M</b>	
Mass. Radio School	579
Meissner Mfg. Co.	595
Midget Radio Co.	615
Midwest Radio Corporation	615
Miles Reproducer Co.	617
Millen, James, Mfg. Co., Inc.	596
<b>N</b>	
National Company, Inc.	Inside Front Cover
National Plans Institute	622
National Radio Institute	577
National School	579
Nelson Co.	604
N. Y. Institute of Photography	579
New York Y. M. C. A. Schools	579
<b>P</b>	
Premax Products	596
Premium Distributing Service	617
<b>R</b>	
Radio Amateur Course	623
Radio & Technical Publ. Co.	579
Radiocrafters	601
Radio Publications	619, 621, 632, 633
Radio-Television Reference Annual	580
RCA Institutes, Inc.	579
Remington-Rand, Inc.	611
<b>S</b>	
Sprague Products Company	601
Sprayberry Academy of Radio	Inside Back Cover
Supreme Publications	613
<b>T</b>	
Technifax	622, 629
Teleplex Co.	579
Triplett Electrical Instrument Co.	607
<b>W</b>	
Universal Microphone Co., Ltd.	614

(While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.)

What Do YOU Think?

(Continued from page 579)

short wave fields, and like the others I rely upon your FB magazine to furnish me with understandable and complete data.

I recently built my first receiver from a circuit appearing in your magazine, and it works very well. I am also planning to build my transmitter from circuits in your magazine, as soon as I am a little more advanced; I can easily follow your diagrams, although I am a beginner. I am a SWL and will swap cards 100% promptly with anyone who desires such.

In closing, I believe that your editorials should be praised, as they put the short wave experimenter in a high position and prove the importance of radio in war and peace, which is especially important in these troubled times.

DICK VESTY,

Box 305,

Alexandria Bay, New York

A SUGGESTION

Editor,

The equipment in my S-W shack consists of three standard receivers. The one to the left is used for my home-made public address system.

I have been reading R. & T. for some time and I do sincerely believe R. & T. is the most complete magazine for all om's & yl's interested in radio. The departments that interest me are: What Do You Think, the Want Ads, and Circuits. It would be very FB if you awarded some kind of trophy or certificate to SWL photos. Your magazine is "tops" with me.

WILLIAM A. WHITE, JR.,

2109 E. 3rd St.,

Superior, Wis.

1933 and '34, especially the "Doerle" sets. This would greatly increase R. & T.'s popularity among us fellows of 14 or 15, who have to work for our money, as these sets cost less to build.

Another suggestion is that you return the Barter & Exchange column to its former "free" status.

PHIL ADAMS,AK,

4650 Forman Ave.,

North Hollywood,

Calif.

(We constantly endeavor to present several simple articles in each issue, which will appeal to the beginner. We think you will agree that some excellent beginner's articles have appeared in recent numbers of RADIO & TELEVISION.—Editor)

HE'LL EXCHANGE CARDS

Editor,

The receivers here are a 5-tube Emerson and a 7-tube Zenith. Most of my DXing is done on the 20 meter band. I have logged 32 countries, verified 28 of them. The antenna is a 110 foot Marconi, and a 35 ft. doublet. I have been reading R. & T. for about a year now, and just renewed my subscription. Well, I'll have to be wishing your FB magazine 73 (best regards) now. If any of you SWL's want my card, send me yours, and you'll get mine by return mail.


Yours DXingly,

THORNTON LYFORD,

260 Woodlawn Ave.

Hubbard Woods, Ill.

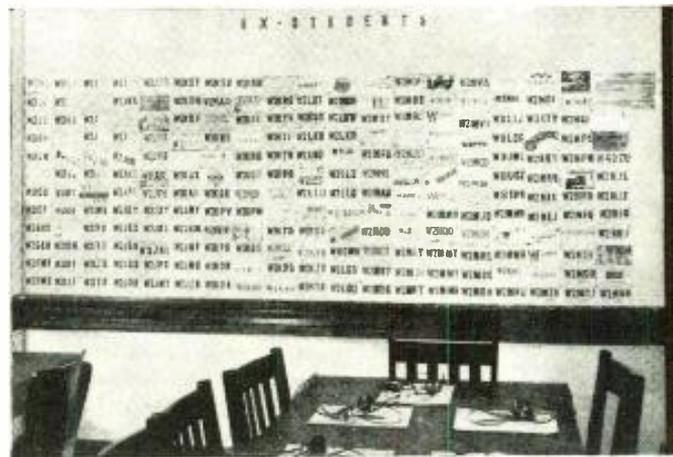Here is a "different" QSL card collection—but stations put on the air! Photo above shows approximately 600 amateurs put on the air by the American Radio Institute.



A "BRICKBAT"

Editor,

I am just a beginner in the radio game, but I feel entitled to make a criticism of your magazine. It is excellent for hoary-haired hams and their like, but what about us beginners? I first bought your magazine because of a couple of beginner's articles in it. The next few months it was OK, and I got into the habit of buying R. & T. as it came on the stands. I was getting my money's worth then, but for the past few months it seems too complicated. I suggest that you reprint some of your articles of

ANSWERS TO PUZZLE DIAGRAM ON PAGE 622

- 6F6, control grid missing pin #5
  - 6A7, control grid missing, Cap 58, suppressor grid missing, pin #4
  - 12A7, screen grid missing, pin #3
  - 6K7, screen grid missing, pin #4
  - 6AB, screen grid missing, pin #4
  - 6F7, grid missing, triode section, pin #5
  - 89, screen grid missing, pin #3
  - 19, grid missing, output section, pin #4
  - 6L7, screen grid missing, pin #4
- Symbols show bottom view of socket.

# FULL EQUIPMENT

## Included WITH

# SPRAYBERRY RADIO TRAINING!

*Experience Easily Acquired at Home!*



**HOW TO MAKE MONEY IN RADIO**  
 SPRAYBERRY ACADEMY OF RADIO

## OVER 100 EXPERIMENTS

plus Many Other Special Features

ALL DESIGNED TO HELP YOU MAKE FAST PROGRESS!

SPRAYBERRY Training starts right at the beginning of Radio . . . unfolds each subject in a simplified, logical, understandable style. You easily learn Television, Frequency Modulation, Signal Tracing, Mobile Radio (Auto-Tank), Aviation Radio, Electronics, Facsimile Radio, Radio Set Repair and Installation Work. You learn quickly in your spare hours . . . AT HOME OR AT CAMP.

Training Prepares You for a Business of Your Own . . .  
 Or Good Radio Jobs at Excellent Pay!

The great, fascinating and progressive field of Radio and Television offers many opportunities to the man who wants to get ahead. There is good money to be made. My Training is designed to give you quick access to these opportunities. SPRAYBERRY Methods are thorough and practical. Your Training will not interfere with your present work.

You Get Professional Test Equipment  
 plus Experimental Outfits!

. . . Includes 146 RADIO PARTS for building a complete Receiver, RADIO TOOLS and a modern TESTER-ANALYZER. You also receive 8 BIG SHIPMENTS OF RADIO EQUIPMENT for conducting actual experiments with your own hands. I show you how to create Radio defects . . . how to correct them. This practical "beforehand" experience will come in handy again and again when you are called on to do actual Radio repair work later on.

### READ WHAT THESE FELLOWS SAY ABOUT THE NEW PRACTICAL SPRAYBERRY TRAINING

EARNED \$250 SINCE STARTING

"I have only completed one-third of the Sprayberry Course and I find it very interesting, which makes it easy to learn. By devoting several hours of my spare time daily to studying and servicing, I have made about \$250 gross since starting the Course." Earl W. Hostetter, R. No. 4, Lebanon, Pa.

"SO MUCH FOR SO LITTLE"

"Now just a few words about your Course—the more I get from it, the more I wonder how you can give so much for so little.

"I believe it to be the finest of its kind obtainable, and I would urge anyone wishing to study Radio seriously to take your Course." George W. Elliott, 521 Elwyn St., Neilson, B. C., Canada.

"MADE OVER \$300 NET IN SIX MONTHS"

"While I have not hung out my 'shingle' yet, I have made over \$300 net in the past six months, doing some full and some part time Radio servicing. I am completely satisfied in every way with your Course, and I am mighty glad I signed on the 'dotted line,' making me a student of the Sprayberry Academy of Radio." Wendell M. Caldwell, 93 Hickory St., Rochester, N. Y.

### Cash In on Radio's Rich Opportunities

No matter if you desire to BE YOUR OWN BOSS in your own business or hold down a good job in Radio, my Training will give you the useful information and knowledge to win success. Days of delay mean precious time wasted. Start training for a money-making Radio career—right now.

**REMEMBER —THE SPRAYBERRY COURSE IS SOLD UNDER A MONEY-BACK AGREEMENT**

146 RADIO PARTS

RADIO TOOLS

TESTER-ANALYZER



No Previous Experience Needed

It makes no difference what your education has been. I can fit you quickly for a good-paying Radio job. I make it easy for you to grasp Radio principles and remember them. Your success is my full responsibility.

### EARN WHILE YOU LEARN

My BUSINESS BUILDERS show you how to put your equipment to actual use in handling money-making Radio Service Jobs shortly after you begin training.

Learn More About the SPRAYBERRY Method And How Easy It Is to Start

The complete details of my fundamental Course and Advanced Training Course . . . all features are fully described in my new, valuable 32-page FREE Book. Send for your copy. No obligation.

All Equipment Becomes Your Personal Property

**DON'T DELAY! ACT NOW!**

SPRAYBERRY ACADEMY OF RADIO

F. L. Sprayberry, Pres.  
 445-B University Place, N. W.  
 Washington, D. C.

Please send my FREE copy of "HOW TO MAKE MONEY IN RADIO."

Name . . . . . Age . . . . .

Address . . . . .

City . . . . . State . . . . .

Tear off this coupon, mail in envelope or paste on penny postcard.

**RUSH THIS COUPON for BIG FREE BOOK**  
 GIVING COMPLETE FACTS

www.americanradiohistory.com

*New High Fidelity*

# FM-AM TUNER

## MODEL S-31

*High Fidelity Tuner  
for Frequency Mod-  
ulation and Ampli-  
tude Modulated  
Reception.*



**N**OW you can have FM-AM reception by a turn of the bandswitch with the Model S-31 Hallicrafters commercial FM-AM Tuner. Covering the broadcast (AM) band and the 40-51 mc. high frequency (FM) band. The Tuner combines the FM and AM circuits in one chassis with either instantly available at the turn of the bandswitch.

**SPECIFICATIONS**—9 tubes—Frequency range, band one; 550 to 1600 kc., band two; 40 to 51 mc.—Power output 130 milliwatts undistorted—Output impedances 500 and 5000 ohms—Power consumption 120 watts—Controls: bandswitch, radiophone switch, main tuning, audio gain, tone control, "S" meter adjustment, phone jack. Operating from 115-125 volts, 60 cycles AC. Panel dimensions 19" x 8 $\frac{3}{4}$ ". Dust cover dimensions 17" x 8 $\frac{3}{4}$ " x 11 $\frac{1}{2}$ ". Write for prices.



## AMPLIFIER FOR MODEL S-31 TUNER

The Model S-31, a Hallicrafters amplifier, delivers 25 watts of high fidelity audio power to either speaker or 500 ohm load. Designed for rack mounting and for use as a companion unit to the FM-AM Model S-31 Tuner, it will provide reproduction of sparkling depth and brilliance.

**SPECIFICATIONS**—6 tubes—Fidelity 2 DB from 50 to 15,000 cycles gain—Channel No. 1, microphone (high impedance) 96 DB—Channel No. 2, phone (low impedance) 60 DB—Power output 25 watts—Power consumption 100 watts—Output impedance No. 1, 500 ohms; No. 2, 8 ohms; No. 3, 4 ohms. Dimensions: panel 19" x 8 $\frac{3}{4}$ ". Dust cover 18" x 8 $\frac{3}{4}$ " x 10". Write for prices.

the hallicrafters inc.

CHICAGO, U. S. A.

USED BY 33 GOVERNMENTS • • • SOLD IN 89 COUNTRIES