

Basic Radio Course

JOHN T. FRYE

Basic Radio Course

(COMPLETELY REVISED EDITION)

JOHN T. FRYE

GERNSBACK LIBRARY, INC., NEW YORK, N.Y.



Revised Edition

© 1961 Gernsback Library, Inc.

First Edition © 1951 Hugo Gernsback

*All rights reserved under Universal
International, and Pan-American
Copyright Conventions.*

Library of Congress Catalog Card No. 61-16513

CONTENTS

Chapter	THE ELECTRON THEORY	9
1	The nucleus. Electron attraction. Positive and negative ions. Conductors. Insulators. Electromotive force. Electron charge. Direct and alternating currents. Cycles and frequency. Coulomb. Amperes and milliamperes. Resistance. Ohms and megohms. Voltage.	
2	OHM'S LAW AND THE RESISTOR	16
	Current flow. Ohm's law. Using Ohm's law. Fixed and variable resistors. Carbon and wirewound resistors. Rheostats and potentiometers. The volume control. Why resistance is important. Voltage division. Heat and power. Wattage.	
3	WHAT IS INDUCTION?	24
	Electron motion. Magnetic field. Left-hand rule. The inductor. Magnetic lines of force. Magnetism induces current. Self-induction. Bucking voltage. Inductance. The henry. Inductors and chokes.	
4	CAPACITANCE	32
	Capacitors. Stray capacitance. Charge. Dielectric. Charge storage. Farad. Dielectric constant. Leakage. Power factor. Capacitor construction.	
5	HOW CAPACITORS ARE MADE	39
	Interleaved plates. Variable air capacitor. Mica capacitors. The silvered mica. Paper capacitors. Oil-filled types. Electrolytics. Oxide film. The dry electrolytic. Etched foil. Fabricated-plate electrolytics. Polarization. Ceramic capacitors. Temperature coefficient.	
6	REACTANCE, IMPEDANCE AND PHASE	46
	The tuned circuit. Phase: leading and lagging. In phase. Phase shift. Rate of change of current. Induced e.m.f. Capacitive reactance. Inductive reactance. Equivalent resistance. Impedance.	
7	RESONANT CIRCUITS	55
	Series- and parallel-tuned circuits. Resonant frequency. Figure of merit or "Q". Parallel circuits. Tuned-circuit loading. Wavetraps. Tuning resonant circuits. Inductive and capacitive tuning.	
8	TRANSFORMERS—HOW THEY WORK	64
	High voltage or high current. Primary coil. Secondary coil. Cores. Air core. Transformation ratios. Turns ratio. Magnetic flux. Lenz's law. Magnetizing current. Hysteresis and eddy-current losses. Magnetic inertia. Laminated cores. Transformer applications and troubles.	
9	THE DIODE VACUUM TUBE	72
	Experimental setup. Plate (anode). Filament. A- and B-batteries. Kinetic energy. Electron emission. Indirectly heated cathode. Plate current. Saturation current. Diodes. Gassy tubes. Weak, noisy and microphonic tubes.	
10	TRIODE AND TETRODE TUBES	79
	Coated filaments. Thorium. Filament temperature. Space charge. Mercury vapor. Enter the triode. Control grid. Bias. Electrode arrangement. Amplification factor. Plate-load resistor. Coupling capacitor. The screen grid. The tetrode. Circuit of a tetrode amplifier.	
11	THE PENTODE VACUUM TUBE	87
	Secondary emission. Tetrode curve. The suppressor grid. Suppressor alters curve. The beam tube. Tube types. Hybrid tubes. Compactrons.	
12	VACUUM-TUBE CHARACTERISTICS	94
	The graph. Plotting curves. Test circuit. Plate-family curves. Transfer characteristic. Amplification factor. Plate resistance. Transconductance. Mutual conductance. Mho and micromho. Dynamic characteristics. Load line. Voltage gain.	
13	THE POWER SUPPLY	101
	B-supply rectifiers. Half- and full-wave rectifiers. Smoothing filters. Choke-input filter. Capacitor-input filter. Power supply troubles.	

CONTENTS

Chapter	POWER SUPPLY TYPES	109
14	A.c.-d.c. supply. Ballast resistor. Transformerless heater string. Line-cord resistor. Typical a.c.-d.c. supply. Three-way supply. Voltage-doubler supply. Auto-radio supplies. Nonsynchronous vibrator power supply. Synchronous vibrator power supply. Transistor d.c.-to-d.c. converter.	
	SOUND AND SPEAKERS	118
15	Brief review of sound. Compression and rarefaction of sound. Frequency. Pitch. Loudness. The dynamic speaker. Field coil. Pole piece. Voice coil. Spider. Frame. Permanent magnets. Sound and the ear. Low-note difficulties. Sound-pressure curve. Repair problems.	
	THE POWER OUTPUT STAGE	126
16	Voice-coil impedance. The output stage. Plate resistance. Conditions for maximum transfer of power. Output transformer. Turns ratio. Universal output transformer.	
	THE VOLTAGE AMPLIFIER	135
17	Audio voltage amplifier. Distortion. Power. Voltage amplification versus load resistance. Phase inversion. Triode dynamic characteristics. Push-pull amplifier. Harmonics. Fundamental wave. Harmonic distortion.	
	DEMODULATING THE R.F.	145
18	Modulation. Detector or demodulator. R.f. carrier envelope. Demodulating the signal. Rectify the r.f. Simple crystal set. Crystal detector. Vacuum-tube diode detector. Grid-leak detector. Power detector. R.f. choke.	
	RECEIVER SELECTIVITY	155
19	Getting better selectivity. Basic tuned-radio frequency (t.r.f) circuit. Cascaded r.f. stages. Tuned-circuit frequency response. I.f. transformers. The superheterodyne. A converter tube. The intermediate frequency. Trimmer-tuned and slug-tuned transformers. Coupling. Critical coupling. How much bandwidth. Defects in the i.f. stage.	
	THE CONVERTER STAGE	164
20	Mixers. Beat frequencies. How a mixer works. Why detection? Triode mixer. The mixer tube. Image rejection. More sophisticated circuits. Pentagrid converter. Triode-hexode mixer circuit.	
	SOME OSCILLATOR CIRCUITS	173
21	Damped oscillation. Driven oscillator. Vacuum-tube oscillator. Tickler coil. Circuit variations. Armstrong, Meissner, Hartley and Colpitts oscillators. Oscillator tracking. Padder capacitor.	
	HOW TO TRAP A SIGNAL	181
22	Snaring the signal. High-impedance loop antenna. Loopstick. Directional properties. Improved loop antennas.	
	SIGNALS IN SPACE	188
23	Ground waves. Sky waves. The ionosphere layer. Fading. Automatic volume control. The detector circuit. Remote-cutoff tubes. Delayed a.v.c.	
	TRANSISTOR RADIOS	196
24	How transistors are made. Electrons and holes as current carriers. N- and P-type material. Leakage. Breakdown or avalanche voltage. Semiconductor rectification. Inside the transistor. Where transistors get their gain. More about transistors. Transistors compared to vacuum tubes. Transistor receiver circuits. Printed circuits and service techniques.	
	INSTRUMENTS AND TOOLS	208
25	A versatile instrument. V.o.m. Basic circuitry. V.t.v.m. Signal generator. Tube tester. Signal tracer. Other tools you need.	
	SERVICING TECHNIQUES	214
26	Troubleshooting methods. Voltage measurement. Leaky capacitors. Open transformers. Service manuals. Resistance measurements. Circuit disturbance testing. Signal-injection system. Signal-tracing method.	
	INDEX	221

PREFACE TO THE REVISED EDITION

THE fine reception given *Basic Radio Course* in past years has been most gratifying. Many letters from individuals and schools regarding the readability and helpfulness of the book have pleased me immensely, and, being human, I have been even more pleased by the continuing high level of sales year after year. Competition in the technical electronic book field has increased sharply in the past decade, and the fact the original BRC has held its own indicates it must be benefiting from the most significant of all advertising, the word-of-mouth kind.

But the electronic field is a vital growing thing, and even a "basic" book on the subject needs to be reviewed and brought up to date after a while. In the preparation of the revision, every sentence of the original edition was read and pondered in the light of these four questions: (1) Is this still true? (2) Is it still important? (3) Is there more that should be said on the subject? (4) Can this be said more clearly?

Few pages subjected to such an inquisition escaped some revision. In most cases words, sentences, paragraphs or whole pages were added to embrace new developments or to improve the clarity. In a few instances, obsolescent material was deleted. An example is the material on tuning indicators and pushbutton tuning. Ten years ago a high percentage of radios featured these; now practically none do. Cutting out material that presently is only of historic interest provided room for new and useful information, such as a whole new chapter on transistors, diodes and printed circuits.

But the revision extends to more than just the rewriting of the text. New illustrations have been used throughout the book; chapters and chapter headings have been rearranged; review questions have been added at the end of each chapter; and the book has been set in new easy-to-read type. In short, every effort has been made to preserve everything good and time-tested in the original version while new material has been blended in to bring the book up to the minute and to make it more attractive and useful.

I am more convinced than ever that a light touch and a little humor in the writing style makes the acquisition of serious knowledge easier and more pleasant for the reader. Finally, though I know it is shameless of me to admit it, I had fun writing this book originally; I enjoyed re-reading it; and I am proud of this revision. I hope you like it, too!

JOHN T. FRYE

PREFACE

WHEN radio servicing started there was a wide knowledge-gap between the men who designed and built radios and the men who serviced them. Those early technicians were well-named “radio mechanics,” for most of them were recruited directly from garages, battery shops, and electrical stores. The tools they carried with them were those that could be found on any auto repair bench, and the troubles they sought were mostly easily-detected mechanical failures, such as open filaments, broken connections, dead batteries, and short-circuits. The radio mechanic taught himself to locate and repair these defects without bothering to learn much about the *why* of radio reception, and what technical knowledge he did have was usually held in the form of hazy, ill-fitting mechanical analogies.

Then into this radio paradise entered trouble in the form of increasing receiver complexity. The new-fangled superheterodyne was prey to a whole host of maladies, none of which could be identified with the unaided sense of sight, hearing, touch or smell. New “tools” in the form of electronic instruments as complicated as the receivers themselves began to appear on the market to aid in diagnosing and correcting these troubles; but before these instruments could tell the technician whether or not a particular portion of the circuit was operating normally, he had to know what was *supposed* to be going on in that circuit, and he had to be able to interpret and understand what the instruments were trying to tell him. In short, the would-be technician is forced—often quite against his will—to narrow the gap between what the radio engineer *must* know and what the radio technician *should* know: he had to become *less* of a mechanic and *more* of a technician.

Unfortunately, the need for technical knowledge today is a lot more evident than the means of satisfying it. Men who write books

seem to consider radio theory strictly the province of the radio engineer, and most of their books are written in engineering jargon that may be crystal-clear to the man who has spent several college years learning technical doubletalk but is something less than transparent to the fellow who has ducked into radio through the side door of experience. When an occasional technical subject is "written down" for the radio technician, it is over-simplified to such an extent that both the theory discussed and the reader's patience suffer.

This book is intended to lie between these two extremes. It is written directly at the man whose primary interest in radio is of a practical nature, but it assumes that man wants to know *why* and *how* the apparatus with which he is dealing does its work.

While every effort is made to present basic radio theory in a clear, interesting, and graphic form, this theory is not reduced and distorted into electronic baby-talk. Instead, an attempt is made to raise the understanding of the reader through a step-by-step procedure and through the lavish use of analogies to the point where he can swallow the theory in its undiluted form. At the same time, through the casual introduction but careful explanation of technical terms, the technical vocabulary of the reader is gradually built up until, at the end of the book, he will be prepared to tackle and understand articles that would have been so much gibberish to him before.

Finally, the book has been deliberately written in an informal style that may seem startling to those who are accustomed to seeing technical writing always wearing formal dress. The writer not only believes that all learning should be fun, but he is firmly convinced that a little joking now and then is the best of bicarbonates to aid in the easy digestion of a complicated subject.

JOHN T. FRYE

1

THE ELECTRON THEORY

.....

THERE seems to be a growing idea in some quarters that radio servicing is being lifted out of the reach of the ordinary man. There are those who strongly hint that, unless you have a college degree in electrical engineering and have done post-graduate work on the neutron bomb, you have no business taking the back off an a.c.-d.c. receiver to replace a dial lamp.

"Modern receivers are so complicated," they tell us, "what with transistors and printed circuits and everything, it is almost hopeless for the ordinary fellow to try to learn radio servicing."

To all of this the author says simply but emphatically, "Baloney!"

Anyone who can read and understand what he reads, who can reason from observed effect back to a logical cause, and who can handle a soldering iron, can learn to repair radio receivers *and do a good job of it*. Like everything else, radio servicing looks a lot more complicated and difficult to the uninitiated than it does to someone who works with it every day.

"I don't see how they can make head or tail of all that mess of wires," a customer will often exclaim when he sees his receiver chassis turned upside down on the service bench. What he does not grasp is that there is a great deal of repetition in both parts and circuits. The simplest and the most complicated receivers are each just an assembly of tubes, capacitors, resistors, coils, trans-

formers, wire, and hardware. It is true that each of these basic components can have various forms, but the form has nothing to do with obedience to the laws of electricity. A tuned circuit consisting of a coil and a capacitor looks the same to an electron whether it encounters the circuit in a home-made crystal set or the most modern and expensive television receiver. If you understand exactly what takes place in the single tuned circuit of the crystal receiver, you need not be concerned because the TV set has dozens of similar turned circuits. Tuned circuits are not like girl friends; an increase in the number does not necessarily increase the complications.

The would-be serviceman must understand the nature and behavior of electrical currents. Then he must take up the various pieces of radio apparatus one at a time and consider them both from the point of view of their action in various electrical circuits and from the practical angle of physical construction, common defects, causes of failure, etc. Then he will be in a position to know exactly *why* a capacitor is used in any circuit and the effect its inclusion will have on the circuit action; he will be able to recognize the many different forms that capacitors take; he will be prepared to diagnose correctly the symptoms of a defective capacitor; and he will be able to do the same thing with any other piece of radio equipment.

Once thoroughly familiar with both the theory and practice of every item that is used in the design of a radio receiver or other electronic device, he will understand readily the functioning of any new circuit he encounters, for the "new" part of the circuit will be simply one of arrangement. To him it will represent just another grouping of his thoroughly understood circuit elements.

This book is a down-to-earth, "horse-sense" radio course, but do not get the idea that radio theory is to be neglected. You cannot become a good radio serviceman without a clear understanding of radio theory, but you can learn your theory in practical, usable form, stripped of all the double talk that makes it seem so much more complicated and difficult than it really is. Let us look at an example:

If we pass an alternating current through a capacitor and vary the frequency, we find that, as the frequency increases, more current passes through the capacitor. The engineers would have us remember: "The reactance of a capacitor is an inverse function of frequency."

If you want to remember it that way, go right ahead; but if

you prefer simply to recall that, as the frequency of an alternating current goes up, the resistance of a capacitor to the passage of that current goes down, and *vice versa*, you will be just as correct. Really to know a thing and to be able to use it, you must know it in your own words.

But enough of telling what we are going to do! Let's start doing it!

The electron theory

Accepting the electron theory is a good bit like ordering hash in a restaurant: you must have faith. It is universally agreed that all matter is made up of atoms; yet no one, not even with the aid of the most powerful microscope, has ever seen an atom. But it is only by dissecting the atom — and it takes millions of them to make up a speck of dust — that we are able to find an electron.

The ordinary garden variety of atom is made up of assorted particles of electricity. In the center is a particle of *positive* electricity called the *nucleus*, and around this circulate one or more particles of *negative* electricity called *electrons*, in about the same manner as the planets in our solar system revolve about the sun.

The thing to keep in mind about these various particles is that there are strong forces of attraction and repulsion connected with them. For example, a positive nucleus has more attraction for a negative electron than a throbbing crooner has for bobby-soxers, but two negative electrons or two positive nuclei simply can't stand the sight of each other any more than can two women wearing identical dresses.

Ordinarily, the positive charge of the nucleus and the negative charge of an atom are in exact balance, but sometimes an atom loses one of its electrons and so becomes slightly positive, in which case it is called a *positive ion*. If, on the other hand, it becomes slightly negative by picking up an extra electron, it is called a *negative ion*. In either case, the atom is said to be *ionized*.

An atom that has lost one of its electrons and becomes positive has no morals at all, for it will steal any loose electron it can from a neighboring atom. This state of affairs makes it possible for an electron with an itching foot to swing along from one atom to another; and when we have enough of these electrons all traveling in the same direction for an appreciable length of time, we have an electric current.

Some materials give up electrons easily and allow them to move about when attracted electrically. Called *good conductors*, such

materials include most metals. On the other hand, there are substances which stubbornly hang on to their electrons and refuse to give up any appreciable amount of them, even under strong electrical pressure. Materials of this kind, such as air, glass, and rubber, are called *insulators*.

The method by which electrons are persuaded to move through a conductor is the application of an *electromotive force* (e.m.f.) across the ends of the conductor. This electromotive force is produced in various ways, each of which produces a crowd of electrons at one end of a conductor and a scarcity of them at the other. One of the most common is by the chemical action in a battery. The chemical action is such that one terminal of the battery becomes positive and has a very strong attraction for negative electrons, and the other terminal becomes negative and is able to give up electrons very readily because it has a surplus of them.

When this battery is connected across a conductor, say a piece of wire, the electrons start slipping from the atoms near the positive terminal to that terminal. These atoms, in turn, grab some electrons from their neighbors on the other side. The neighbors do the same thing, and the process continues until the atoms at the negative end of the wire replenish their losses from the negative terminal of the battery. This whole bucket-brigade movement of electrical charge takes place at the terrific speed of nearly 186,000 miles a second.

Understand that a single electron does not zip from one end of the conductor to the other at this dizzy pace. The movement is similar to that which takes place when the last one of a whole row of dominoes, standing on end right next to each other, is pushed over — the toppling movement flashes to the end of the row in a split second; yet each domino has moved but a short distance.

Each electron does drift slowly from one end of the conductor to the other, but its speed is much less and its path is much more erratic than that of the electrical charge itself. If we could paint an individual electron a bright red and were able to follow its progress through the conductor, we would find it following as erratic a path as a pin-ball-machine marble and moving along at an average speed of about 1 foot in 11 seconds.¹ This is its linear speed through the conductor. It whirls around the nucleus at 100 miles per second.

¹Mueller, *Introduction to Electrical Engineering*, McGraw-Hill.

When the electrons move in a single direction through a conductor, we have *direct current* (d.c.). All batteries and some generators produce an e.m.f. resulting in d.c. Other devices, especially certain kinds of generators, produce an e.m.f. that periodically reverses its direction; the current that results from this type of voltage is called *alternating current* (a.c.). Each terminal of such

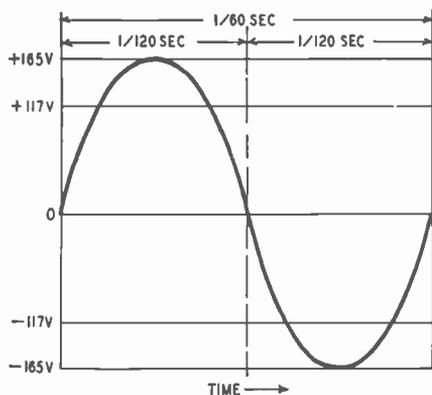


Fig. 101. Graph above shows a 60-cycle, 117-volt wave.

a generator keeps changing from positive to negative and back again, and the other terminal keeps changing its charge so as always to remain opposite to that of the first terminal.

The speed with which this voltage reverses may be from a few times a second to millions of times a second. The portion of its action during which an a.c. voltage starts at zero, builds up to a peak in one direction, falls to zero, builds up to a peak in the opposite direction, and again falls to zero is called a *cycle*. The number of cycles that occur in a second is the *frequency* of the alternating current. Most a.c. voltages furnished to residences are of the 60-cycle variety, and the diagram in Fig. 101 shows how a complete cycle takes place in $1/60$ of a second.

To use electricity, we must be able to control it; and to secure control, we must have methods of measuring it. The early physicists decided to establish a connection between the newly discovered electricity and the old established standards of weight; so they said that the amount of electricity required to deposit .001118 gram of silver from a standard solution of silver nitrate in water should be known as the *coulomb*. If a coulomb of elec-

tricity — about 6.28×10^{18} (6,280,000,000,000,000) electrons — flows past a given point in a second, a current of one *ampere* is said to be flowing. A thousandth of an ampere is termed a *milliampere*.

The unit used to measure the *resistance* of a conductor to the flow of current is the ohm. It was defined as the resistance offered to an unvarying electrical current by a column of mercury, 14.4521 grams in weight, at the temperature of melting ice, with a constant cross-sectional area, and 106.3 centimeters long. The *megohm*, often used in radio work, is 1,000,000 ohms.

Once the ampere and the ohm have been determined, the *volt*, the unit of e.m.f. is easily defined. It is simply the amount of e.m.f. that will cause a current of 1 ampere to flow through a resistance of 1 ohm.

And so we come to the end of the first chapter, and I still have not told you how to fix a radio; but do not be impatient. If you have understood all the foregoing, you have established for yourself a solid foundation upon which a complete mastery of the theory and practice of radio can be built.

QUESTIONS

1. Describe the arrangement of electrical charges in an atom.
2. How is an atom ionized?
3. What is the basic difference between a good conductor and an insulator?
4. How fast does an electrical charge travel?
5. What is the average speed of an electron through a conductor? What is its rotational speed around its nucleus?
6. What is the difference between *direct current* and *alternating current*?
7. Name two possible sources of direct current.
8. What is the machine called that produces alternating current?
9. Why is the electrical power furnished homes usually called "60-cycle a.c."?
10. Define *coulomb*, *ampere*, *milliampere*.
11. What is an *ohm*? a *megohm*?
12. What is a *volt*?

2

OHM'S LAW AND THE RESISTOR

.....

IN the first chapter we learned that an electric current is made up of a movement of minute negative particles called *electrons*; that these electrons are always attracted by a positive charge, so that an electric current always flows *from negative to positive*; and that we measure current in *amperes*, electromotive force in *volts*, and resistance to the passage of current in *ohms*. Now let's take it from there.

The man who gave his name to the unit of resistance had the bright idea of tying the units of current, voltage, and resistance together, in a simple formula so that, if you know any two of them, you could always find the third. This formula, which is known as Ohm's law, gets more of a workout than a drugstore telephone on a Saturday night, for you simply cannot do anything electrical without using it. You cannot even turn on your flashlight without Ohm's law getting into the act!

The importance of the formula is equaled only by its simplicity and ease of application. Ohm's law states that the current, measured in amperes, flowing in any portion of an electrical circuit is equal to the applied electromotive force in volts divided by the resistance in ohms. That is

$$\text{Amperes} = \frac{\text{Ohms}}{\text{Volts}}$$

Since the current is referred to as the "intensity," the voltage as the "electromotive force," and the resistance to the passage of

current simply as the “resistance,” the formula is usually written with the first letters of these three terms

$$I = \frac{E}{R} \quad (1)$$

If we multiply both sides of equation 1 by R , we have


$$RI = E \text{ or } E = IR \quad (2)$$

Dividing both sides of equation 2 by I gives us

$$R = \frac{E}{I} \quad (3)$$

These various forms of Ohm’s law enable us to determine quickly an unknown voltage, current, or resistance if we know the other two. Let us take the circuit of Fig. 201 as an example. Here we have three resistors, of 1, 2, and 3 ohms, respectively, hooked in series across a 12-volt battery. When resistors are connected in series, the total resistance is equal to the sum of their individual resistances; so we know that the resistance from A to D is equal to 6 ohms. We also know that the battery voltage that appears across these points is 12 volts; so we simply substitute

Fig. 201. The circuit at the right shows how resistors in series can be used in a voltage-dividing network. The voltage drop across each resistor can be calculated by using Ohm’s law. The sum of the voltage drops must be exactly equal to the battery voltage. A device requiring 2 volts for its proper operation could be placed across A and B . Similarly a part needing 4 volts could be shunted across B and C .

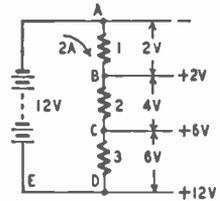

these values in equation 1, and we find that 2 amperes of current will be flowing from point A to point D .

Using Ohm’s law

Ohm’s law applies to any portion of a circuit. Let’s consider just that portion between points A and B . We know that 2 amperes of current are flowing through this, as well as every other part of the circuit, and we know that the resistance between these two points is 1 ohm. Substituting these two values in equation 2, we find that the voltage drop from point A to point B is 2 volts. In the same way we learn that the voltage from B to C is 4 volts, and that from C to D is 6 volts. When these three voltages are

added together, they total the same 12 volts with which we started; we have that pleasant and slightly surprised feeling we get when our check stubs and the bank's report on our balance come out exactly together.

This pleasant discovery is expressed by Kirchhoff's law, another of the rules by which radio and electricity work. Kirchhoff's law is a very simple one and it is valuable because it provides a way of checking the accuracy of calculations. The voltage drops in all parts of a circuit, it says, should, when added together, equal the voltage of the source. If, for instance, we had in addition to the 2-, 4-, and 6-volt drops of Fig. 201, an extra 2-volt drop, the total would be 14 volts. The battery (source) supplies only 12 volts so we would know something had gone wrong with our arithmetic and we should try it again.

Just to prove how well we can handle Mr. Ohm's handy little gadget, suppose we wanted to reduce the current flowing in our circuit from 2 amperes to 1 ampere. How would we go about it? Well, we have our battery voltage of 12, and we know that we want 1 ampere of current to flow; so suppose we substitute these two values in equation 3. We come up with 12 ohms as the required resistance. But there are already 6 ohms in the circuit; so we simply put another 6-ohm resistor in series with those we already have — say between points D and E — and our current is reduced to the required 1 ampere. For practice, why don't you figure out the difference that this will make in the voltages appearing at points B, C, and D?

In dealing with Ohm's law, there is one thing to keep clearly in mind: it works only when the quantities are expressed in volts, ohms, and amperes. Ten milliamperes should be written: .010 ampere: Two megohms would be expressed as 2,000,000 ohms.

Fixed and variable resistors

Resistance is packaged in units called *resistors*. Some idea of their wide variety of sizes, shapes, and materials can be seen in Fig. 202. The most common type in radio work is the so-called carbon resistor, made by combining powdered carbon or graphite with a synthetic resin and an inert material such as talc, molding this into short sticks, and attaching flexible wire leads to the ends. By regulating the amount of carbon or graphite, the resistors can be made to have values from a fraction of an ohm to several million ohms. Cheap and small, they are not capable of handling much current without being damaged by the heating effect of

that current; furthermore, they are quite likely to change value with age and temperature.

Wire-wound resistors are made by winding a wire made of a high-resistance metal such as Nichrome on an insulating form. Capable of handling much more current than composition resistors, they are also more stable. At the same time, they are more costly and bulky, and occasionally the wire fractures, resulting in their changing without warning from their normal value to an almost infinite resistance. Wire-wound resistors seldom exceed 100,000 ohms in value.

It is often desirable to be able to vary the value of a resistor. A slider can be arranged to move along the resistor and to make contact with the resistance element, varying the amount of resistance that appears between the slider and either end. If the resistor is made in the form of a circle, the slider can be attached to a shaft passing through the center of the circular resistance element, and then the variation in resistance can be accomplished by rotating this shaft with a knob. Such a knob-adjusting resistor is variously known as a rheostat, potentiometer, or volume control. The resistance element may be either wire-wound or composition. In volume controls, where the current requirements are ordinarily very small, it is usually composition.

Why resistance is important

At first glance, you might think that resistance was a kind of villain of the piece. Here we have gone to a lot of trouble trying to cause an electric current to flow, either by building a battery or constructing a generator, and now Old Man Resistance is in there doing his level best to gum up the works by throttling the flow of current!

Actually, the ohm is as important as the volt, for, although the volt may be considered the generating force, the ohm is the controlling unit; and if we are to use an electric current, we must be able to control it. Being able to vary the amount of resistance in a circuit gives us a "valve-action" control of the current flowing through the circuit. At the same time, reference to Fig. 201 will reveal another use for resistance, that of "voltage dividing." As can be seen, the 12 battery volts can be sliced up like a length of bologna into any number of smaller voltages by the use of resistors.

Still another use for resistance is to enable us to convert a change in current into a change in voltage. Take a look at

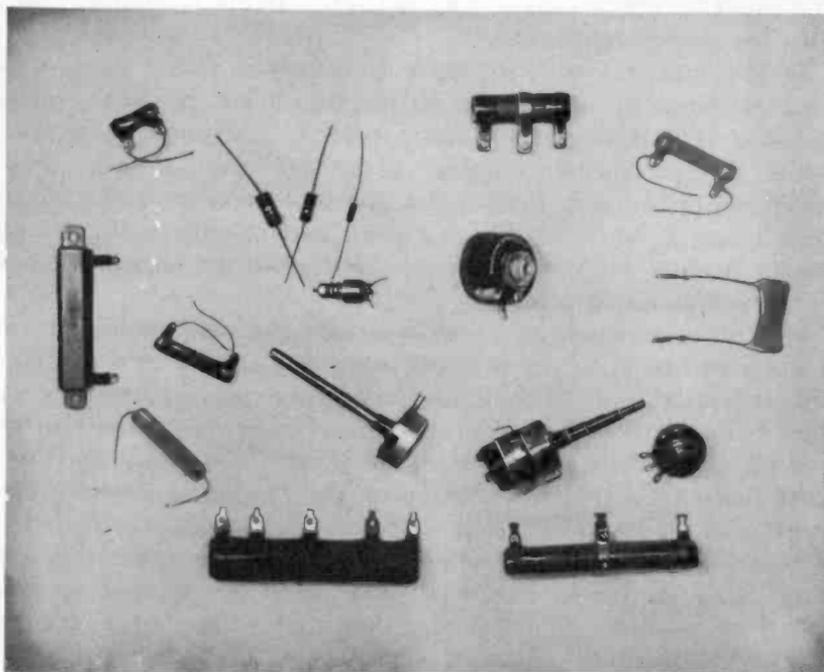


Fig. 202. Various types of fixed and variable resistors are shown here.

Fig. 203. Here we have a variable resistor R_1 and a fixed resistor R_2 hooked in series across a battery. The amount of current flowing through this circuit will depend upon the voltage of the battery and the resistance of R_2 plus that portion of R_1 through which the current passes. Any change in the amount of R_1 's resistance used in the circuit results in a change in the amount of current flowing. We know that the voltage appearing across R_2 depends upon the current flowing through it — for didn't Mr. Ohm decree that $E = IR$? So the change in current caused by

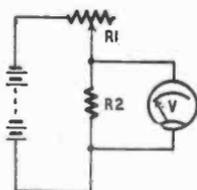


Fig. 203. The current flowing in the circuit shown at the left is determined by the setting of the variable arm of R_1 . The meter indicates the voltage across R_2 . The voltage across R_2 increases as R_1 decreases. Note that the meter does not read the battery voltage but simply the voltage across R_2 . The voltage drop across R_2 can never be greater than the battery voltage.

varying R_1 is faithfully reflected as a change in the voltage across R_2 . When we start studying vacuum-tube circuits, you will see how important this use of resistors is.

Heat and power

In Chapter 1 we defined a good conductor as any material that gave up electrons easily and so permitted a current to flow through it readily. The materials of which resistors are made are no such pushover for an electromotive force, because they do not give up their electrons without a heated struggle. I use the word "heated" advisedly, for actual heat is generated by the passage of current through a conductor. This heat arises from the energy used in prying loose the electrons from the atoms of the resistance material. Since the electrical force that performs this prying is measured in volts, and since it takes more energy to move several electrons than it does only one, it is not surprising to find that the amount of heat produced is related both to the voltage and the current.

The amount of electrical energy or *power* expended — or dissipated as heat, in the case of a resistor — is measured in *watts*. The power in watts consumed in any circuit is equal to the product of the volts and the amperes; or, expressed in formula form

$$P = EI. \quad (4)$$

Equation 2 told us that $E = IR$; and when we substituted this value of E in equation 4, we have

$$P = I^2R. \quad (5)$$

Because electrical energy that is transformed into heat is considered lost, we often hear the heat losses of a resistor or conductor called the "I²R losses." Resistors are rated in wattage as well as resistance, and the wattage ratings vary all the way from a fraction of a watt carbon resistors to wire-wound resistors of 100 or more watts.

Suppose we need a 1,000-ohm resistor that must pass 50 milliamperes of current. According to equation 5 the wattage requirements will be equal to $.050^2 \times 1,000$, or 2.5 watts. It is a good practice to allow for a 100% overload; so we select a 5-watt resistor.

You have heard about the boast of the packing houses that they use every part of the hog except his squeal. Well, the electrical engineers are just as good, for they even put these I²R losses to work. In a vacuum tube, for example, it is necessary to raise the temperature of one of the elements in order to persuade it to give

up electrons more easily. This heating is accomplished by passing an electrical current through a resistance wire (the filament) inside the tube. When you look at the incandescent filament of a dial lamp, you are staring some I^2R losses right in the face.

And so we arrive at the end of another chapter. By this time you should be on good terms with amperes, volts, and ohms. In fact, if anyone hands you any two of these measuring units, you should be able to rub them together and, with the aid of Ohm's law, produce the third right out of thin air. By the same token you should feel right at home with resistors. You should know what they are made of, what they are used for, why they get all hot and bothered when an electrical current is passed through them. And finally, you should know what's watt!

QUESTIONS

1. Does an electric current flow from positive to negative or *vice versa*?
2. State Ohm's law in words and give the formula.
3. Why is this law so useful in working with electricity?
4. State Kirchhoff's law and explain how it aids in checking calculations.
5. What do we call a packaged form of resistance?
6. Name two kinds of resistors.
7. Give two important uses of resistance in a circuit.
8. Why does the flow of electricity through a conductor generate heat?
9. What unit measures the power expended or dissipated as heat in a resistor or electrical circuit?
10. What is the formula for calculating wattage?
11. What are I^2R losses?
12. Explain how these "losses" are put to use in a vacuum tube.

3

WHAT IS INDUCTION?



HAVE you sat in a hotel lobby where all was quiet until a cute blonde got up from where she had been sitting unnoticed behind a potted palm and glided across the floor? If you have, you may have noticed — if you were not too busy watching the blonde — that there was something about the girl *in motion* that seemed to exert a magnetic effect on every masculine head in the lobby.

Well, what this blonde has, our friend the little electron has, too; for as soon as an electron starts to move, it is surrounded by a magnetic field. Let me repeat this, for it is one of the most important facts in radio: *an electron in motion is surrounded by a magnetic field.*

The magnetic field surrounding a single hustling electron is too small to be easily measured with crude instruments; but when a few million of them cavort along through a wire, it is easy to observe the total magnetic field generated. Fig. 301 shows a vertical wire carrying a current, with four compasses grouped around the wire. Since a magnetic field is the only force that affects a compass needle, and since lines of magnetic force enter the S pole of the compass needle and leave by the N pole, we can see that the magnetic field about the wire consists of circulating concentric lines of force. Reversing the direction of the current causes the needles to reverse their positions, indicating the truth of the left-hand rule for wires:

Grasp the wire with the left hand so that the thumb points in

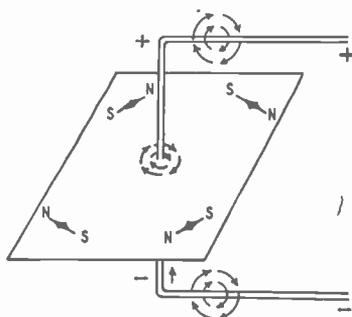


Fig. 301. *The field around an electric current.*

the direction the current is flowing; then the fingers will be pointing in the direction in which the magnetic lines of force encircle the wire.

(Radiomen used to go along with Ben Franklin's original mistake and pretend the current flows from positive to negative — although we know that just the opposite is true. They, of course, had to use the right hand.)

Increasing and decreasing the current while moving the compass needles to different distances from the wire will show that the strength of the magnetic field is related to the amount of current flowing. It is easy to see why. More current means that more electrons are moving, and the total magnetic field about the wire is simply the sum of the magnetic fields of the individual electrons that are passing through the wire.

The inductor

Suppose we wind our length of wire into a coil. What happens to the magnetic field about the wire? Fig. 302, showing two adja-

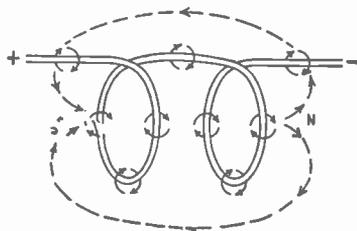


Fig. 302. *The fields help or hinder each other.*

cent turns of such a coil with an exaggerated separation between the turns, gives the answer. For one thing, we see that as the magnetic lines of force continue their dog-chasing-his-tail routine about the wire of each loop, all of these lines pass through the center of the loop, and as they do so, they are all traveling in the same direction. This is true for all the turns of the coil: when the lines of force are at the "most inside" point of the coil, they are all traveling in the same direction. A half-turn later, when each circling line of force is at its greatest distance from the center of the coil, it is traveling in exactly the opposite direction; and that means that *all* of the lines of force of two side-by-side turns are traveling in opposite directions.

When we reflect that these magnetic lines of force are true *forces* and can be added when they are working together, we come to the following conclusions about a coil of wire carrying a direct current:

1. The circulating lines of force about the wire add together inside and outside the coil to produce new and stronger lines of force that issue from one end of the coil, return outside to the opposite end, and then pass through the center of the coil.

2. Between the adjacent turns, the opposite-going lines of force oppose each other and so cancel.

3. The new magnetic field is most intense inside the coil where all of the lines of force are crowded together.

4. The coil has a N and a S pole as does a bar magnet, and reversing the direction of current through the coil causes these poles to exchange places.

5. Since the individual fields of all the turns of wire are added together to produce the field of the coil, it follows that the more turns of wire there are, the stronger will be the magnetic field of the coil. Also, since the strength of the field of each individual turn depends upon the amount of current flowing through it, so does the strength of the field of the coil as a whole depend on the current.

If a bar of iron is thrust through the center of our coil, the magnetic field is greatly increased. The reason is that a magnetic line of force feels about iron the way a cat feels about catnip. It just loves to wriggle through that soft iron, and it will endure a great deal of crowding to be permitted to do so. In fact, a coil with an iron core will accommodate several hundred times as many lines of force as will the same coil carrying the same cur-

rent with only air in its center. The more lines of force there are, the stronger is the magnetic field.

Magnetism creates current

One of the nicest things about the study of electricity is that it is such a *vice versa* business: There are so many statements in this subject to which you can add, "And so is the opposite true." An example is our statement about the moving electron creating a magnetic field. *If a conductor is cut by the lines of force of a magnetic field, an e.m.f. is set up in the conductor which causes electrons to move, or current to flow.*

When we speak of the conductor being "cut by lines of force," we mean that either the conductor or the lines of force must be moving. A wire moved between the poles of a horseshoe magnet, a bar magnet thrust into a coil, or a wire placed so as to intercept the expanding and contracting lines of force that surround another wire through which a current of varying intensity is flowing all fulfill this requirement. Remember, though, that either the field or the conductor has to hold still while the other moves through it—or else one has to be zigging when the other is zagging.

The intensity of the e.m.f. "induced" by this action depends upon how many lines of force are cut in how short a time. This means that a strong magnetic field with many lines of force and a very rapid movement of either those lines of force or the conductor will produce a high voltage.

Self-induction

And now we are ready to meet *self-induction*, which is just about as bull-headed and conservative a quality as you will find anywhere, inside electricity or out! It simply cannot bear a change. Take the case of Fig. 303. Here we have a battery connected across an iron-core coil of many turns. A lamp that barely lights on the battery voltage is across the coil, and a switch and an ammeter are in series with it and the battery.

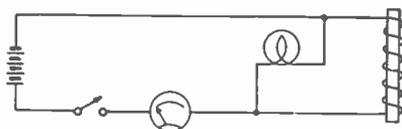


Fig. 303. Setup to demonstrate self-induction.

When we close the switch, the light glows dimly; but the hand of the current-indicating meter rises quite slowly to a maximum reading. Why so slowly? We know that electrons move with the speed of light. Why are the little cusses apparently dragging their feet just because there is a coil in the circuit? Well, when the current started to flow through the coil, a magnetic field started to build up around that coil. As the lines of force of this expanding field cut the turns of the coil, an e.m.f. was induced in those windings that had a polarity opposite to the voltage applied by the battery. This "bucking" voltage was very nearly equal to the battery voltage.

However, as the induced bucking voltage or back-e.m.f. approached the battery voltage, it slowed down the increasing current from the battery. This in turn slowed down the expansion of the magnetic field that was producing the bucking voltage.

As you can see, this gives the battery voltage the whip-hand: if the induced e.m.f. could rise to the value of the battery voltage, it would stop the current flow; and this would spell its own doom. The net result is that the battery steadily wins the tug of war, but it takes time. Eventually the current rises to the maximum amount the battery can push through the resistance of the coil wire, and then the magnetic field ceases to expand. It just hovers out there in the vicinity of the coil without either increasing or decreasing. Since the lines of force are no longer moving and cutting the turns of the coil, there is no more back-e.m.f.

Now let us quickly open the switch. Instantly the ammeter falls to zero, and at the same instant the lamp flashes very brightly and then goes out. Where did this lamp-flashing voltage — obviously higher than our battery voltage — come from? How could current continue to flow through the lamp *after* the battery had been cut off? Gremlins?

No, the answer lies in what happened to that hovering magnetic field when we opened the switch. Since this cut off the sustaining current, we simply knocked the props from under that field, and it did the only thing it could do: collapsed. As the field contracted, the lines of force whizzed through the coil turns faster than a small boy going through his yard gate at curfew time; and the speed with which these lines of force intercepted the wires accounts for the fact that a high e.m.f. — higher than the battery voltage — was set up in the coil.

You remember that the e.m.f. generated by the expanding magnetic field was of such polarity as to resist the voltage of the

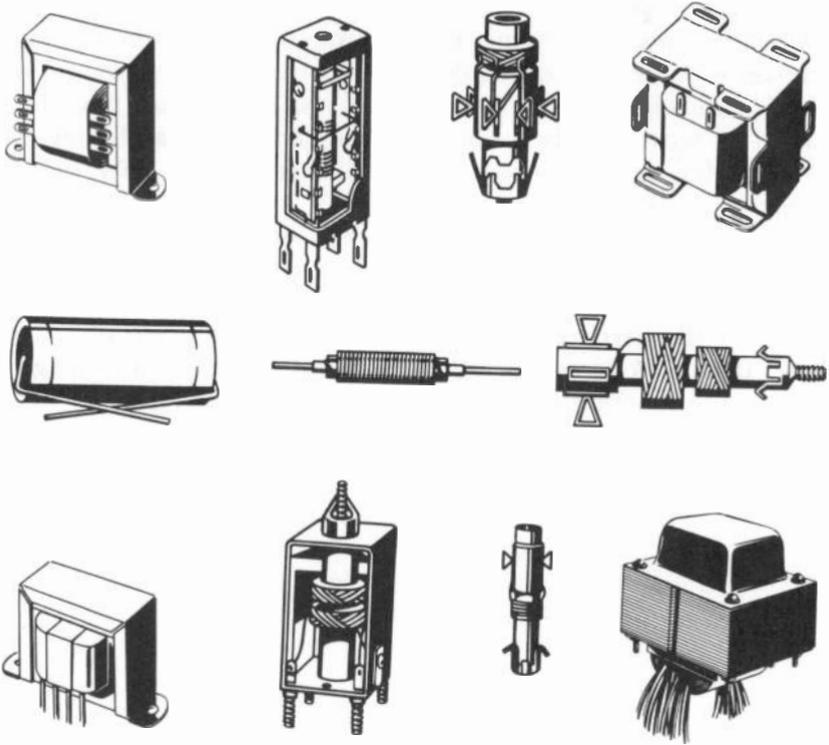


Fig. 304. This group of inductors includes many types of transformers and chokes. (Stancor Electronics, Inc.)

battery. As might be suspected, the voltage induced by the collapsing field is of opposite polarity and tries to keep the current flowing after the battery has been cut off. After doing all it could to prevent the current from starting to flow in the first place, now the self-inductance does all it can to prevent that current from stopping!

This property of a coil or wire that tends to *prevent any change* in the current passing through it — that always tries to preserve the *status quo* — is called *inductance*. The unit of measurement of how much of this property a circuit element has is the *henry*. When a current change of 1 ampere per second in a circuit produces an induced e.m.f. of 1 volt, the circuit is said to have an inductance of 1 henry. If 2 volts are produced, the inductance is 2 henrys, etc. Smaller units are the *millihenry* (one thousandth of a henry) and the *microhenry* (one millionth of a henry).

Inductors are often used in radio work, but they are usually called by some other name. For example, we have filter and audio chokes which consist of many turns of wire on iron cores and may have inductances from 1 to 100 henrys. R.f. chokes have fewer turns of wire usually with a nonmagnetic core, and they vary from a few microhenrys to 100 millihenrys. Fig. 304 shows a typical group of coils (inductors).

Inductance is chiefly concerned with coils, and anything having to do with coils is of major importance in radio. This business of magnetic induction is the key to understanding what goes on in many of the parts you find in any radio receiver. Do not, therefore, dismiss it as not being of practical value. A knowledge of magnetic induction is as practical in understanding radio as the knowledge of the alphabet is in learning to read.

QUESTIONS

1. What surrounds an electron *in motion*?
2. Give the left-hand rule for determining the direction of the magnetic field around a conductor.
3. What effect does increasing the current through a conductor have on the magnetic field around that conductor?
4. Name two factors that determine the strength of the magnetic field around an air-core coil.
5. How can this magnetic field be strengthened without increasing the current or the number of turns in the coil?
6. What happens when a conductor is cut by the lines of force of a magnetic field?
7. What determines the intensity of the voltage produced in this manner?
8. Describe a simple apparatus to demonstrate self-induction.
9. Does a self-induced voltage aid or oppose the current producing it?
10. Why is self-induction called a "conservative" quality?
11. Define *henry*, *millihenry* and *microhenry*.
12. By what other names are inductors known?

4

CAPACITANCE

.....

EVERY electrical circuit, whether it be a 1-inch length of wire or a cross-country telegraph line, has three "built-in" electrical properties: resistance, inductance, and capacitance. The first two of these we have already encountered in previous chapters; now we are ready to grapple with the third.

Capacitance is like discarded chewing gum; you may find it almost anywhere. *Any time you have two electrical conductors separated by a nonconducting medium, you have a capacitor;* and a capacitor is to capacitance what a doghouse is to a dog; it is where you normally expect to find it. By the light of this definition, you can see that your pocket watch and the furnace in the basement below form a capacitor; so does a wire and the antenna stretched above it; so does a moisture-bearing cloud and the earth beneath.

In this free or "stray" state, capacitance is of little or no value; in fact it is often a nuisance. But when it is controlled and "lumped" in definite units, it is every bit as important to electricity as are resistance and inductance.

In its "cultured" state, capacitance comes in the packaged form of *condensers*, the former name for *capacitors*. There is a wide variety in the form and material used in such capacitors; but before we start studying these practical units, let us see how a simple basic capacitor operates. Once we grasp how it works, we shall know how all capacitance units function.

Take a good look at Fig. 401. Here we have a capacitor C, con-

sisting of two parallel flat metal plates with an air space between them. Switch S2 connects across these plates. The double-pole switch S1 permits us to connect the battery directly to the plates. An ammeter, an instrument for indicating both the intensity and direction of any electrical current passing through it, is inserted in the lead going to the top plate of the capacitor.

To begin, let us say that S1 is open and that we have momentarily closed S2 and then reopened it.

Now, suppose we close switch S1. As we do so, the ammeter pointer flips over and then drops back to zero, indicating that a momentary current passed through it. Next, let us open S1 so as to disconnect the battery. What happens? Nothing; the ammeter pointer does not budge. But, suppose we now close S2. As we do so, the ammeter needle flicks again, but in the opposite direction, indicating a reverse flow of current.

Paradox or sense?

Several questions should be pulsing through your head at this point: Why did current flow in this circuit when we connected the battery? There was no complete circuit, for the plates of the capacitor were separated by insulating air. After the current

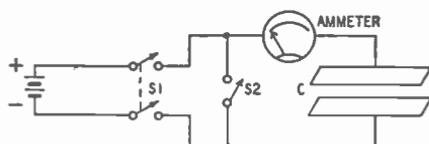


Fig. 401. Test setup shows capacitance effects.

started flowing, why did it stop? Where did the current come from that caused the meter to flick when we closed S2? It could not come from the battery, for that had already been disconnected.

The explanations, as usual, go back to electron theory. The momentary closing of switch S2 before we connected the battery allowed any excess of electrons on either capacitor plate to flow through the switch and balance the electron distribution. At the instant the battery was connected, however, the positive terminal put a strong "come hither" on the negative electrons of the top plate, and they surged through the wire and the ammeter to that terminal, causing the ammeter to register their passage as they did so. At the same instant, the pent-up excess of electrons on the

negative terminal of the battery rushed out on to the bottom plate of the capacitor like school kids spilling out on the playground at recess. The result of this simultaneous "push-pull" action was to leave the top plate with a deficiency of electrons, giving it a strong positive charge, while the lower plate was strictly "Standing Room Only" with electrons and so had a negative charge.

As more and more electrons left the top plate and crowded on the lower plate, the charges on the two plates increased in *opposite directions* until the difference between them was exactly equal to the difference in potential between the two terminals of the battery. At this point, the electrons stopped flowing, because the pushing and pulling force of the charged plates exactly balanced the equal and opposing forces of the battery terminals.

Nothing happened when we opened S1, for there was no path by which the excess of electrons on the lower plate could reach the electron-hungry upper plate. Since this state of unbalance still existed, a voltage equal to that of the battery still was present between the plates, even though the battery itself had been disconnected.

The instant we closed S2 we provided the needed connecting path, and the displaced electrons rushed through it and through the ammeter to the upper plate. Since this time the electrons were flowing *to* the upper plate instead of *away* from it — as they were when the battery was first connected—the ammeter pointer moved in the opposite direction. As soon as the electrons were once more evenly divided between the two plates, they ceased to flow; and we were right back to the point we were before we started charging and discharging the capacitor.

We might have made one other experiment: When we had the battery connected to the capacitor (S1 closed), if we had slid a sheet of glass between the plates, we should have noticed that the ammeter pointer flicked again, indicating that more charge was moving into the capacitor. When we removed the glass, the pointer would have moved in the opposite direction, showing that this new additional charge had moved back out of the capacitor. An explanation of why the material used as the insulating medium of a capacitor (it is called the capacitor dielectric) affects the charge the capacitor will take will be given a little later.

It is apparent that a capacitor is a device for storing an electrical charge. The measure of its ability to do this storing is its *capacitance*. The amount of the charge stored depends upon how many electrons we can force to leave the top plate and congregate on

the bottom plate. We know that the more voltage we have in our charging battery, the more power we have to do this forcing; so it should not come as a surprise that the unit used to measure the capacitance depends both on the number of electrons stored and the voltage necessary to do the storing. This unit is called the *farad*. One farad is the capacitance of a capacitor *in which a coulomb* (6.28×10^{18} electrons) of electricity is stored when an e.m.f. of 1 volt is applied. This unit is too large for practical use; so the *microfarad* (μf), a millionth part of a farad, and the *micro-microfarad* ($\mu\mu\text{f}$), a millionth part of a microfarad, are always used in radio.

The "why" of capacitance

We have explained *what* happens when a capacitor is charged, but we have not explained *why*. Truth to tell, the pundits of electronics tend to take refuge in such phrases as "it is believed," "the theory is held," and "we may assume" when they go to talking about this subject; but here is what is generally thought:

A charged capacitor looks like Fig. 402 in which the ellipses between the plates represent, in a greatly exaggerated form, the out-of-round orbits of the electrons of the dielectric atoms in their paths about their respective positive nuclei. The orbits are out-of-round because of the attraction of the positively charged upper plate and the repulsion of the negatively charged lower plate. Were the electrons of the dielectric free to move, they would go straight to the positive plate; but since they are tightly bound, the best they can do is deviate slightly from their normal circular path.

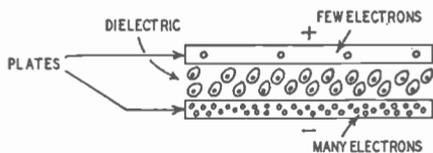


Fig. 402. Capacitor plates after being charged.

When these orbits are comparatively easy to push out-of-round, their counter-repelling action on the electrons trying to muscle their way on to the negative plate will be comparatively weak, just as a weak spring puts up a feeble resistance to being compressed; consequently a large number of electrons can force their

way into the plate. The capacitance of the capacitor will be larger than it would be with a dielectric material in which the electron orbits were harder to distort. In the latter case, since the dielectric electrons would stubbornly refuse to budge from their orbits, the electrons trying to wedge their way on to the negative plate by distorting these orbits would be rebuffed, and the storage ability would be lessened.

We could increase the capacitance by using a thinner slice of dielectric material, allowing the plates to come closer together. This would reduce the total number of the repelling dielectric electrons and so permit more electrons to collect on the negative plate of the capacitor.

It is evident, then, that we can increase capacitance in three different ways:

(1) We can increase the size of the active portion of the plates. The active portions of the plates are the portions that are directly opposite each other and with the dielectric material squarely between them. Increasing the size of these portions means that we have more electrons to draw from the positive plate and more room on the negative plate to store them. When you remember that the resistance of the electrons of the dielectric material is "softened up" by the *double* action of the lower and upper plates, working as a combined pushing and pulling team, you can see why only the portions of the plates considered active have much effect on the capacitance.

(2) We can reduce the thickness of the dielectric material as discussed above.

(3) We can use a dielectric material whose electron orbits are more easily distorted.

The effect that the dielectric has on the capacitance is called the *dielectric constant* of the material and is expressed by the symbol *K*. Air is assigned a *K* of 1, and all other materials are compared with this. For example, replacing the air dielectric of a given capacitor with mica will multiply its capacitance about 5 to 7 times; so we say that mica has a *K* or dielectric constant, of 5-7. In the same way glass has a *K* of 4.5-7, and some rutile ceramics have a *K* of several hundred. No wonder the little cusses can pack so much capacitance in so small a space!

An ideal capacitor would be one with insulation so perfect that absolutely no current could leak across from one plate to the other; but ideal capacitors are like ideal picnics — they are never quite realized. We have *no* perfect insulators, and there is always

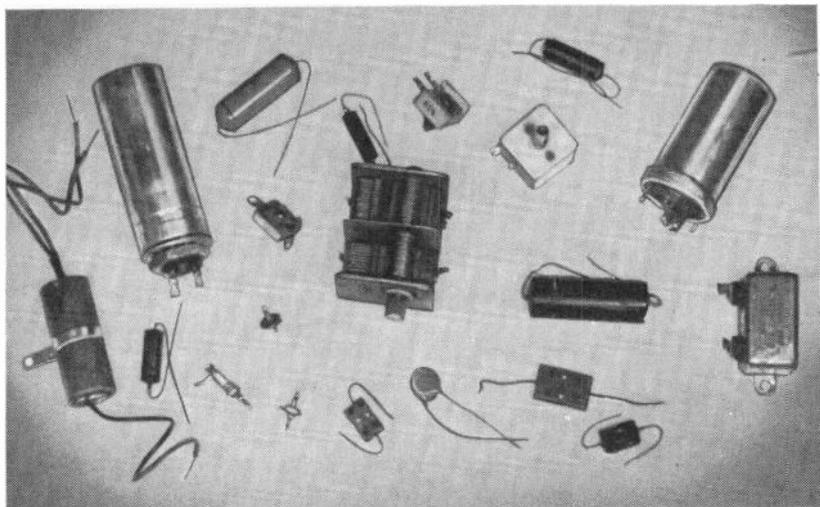


Fig. 403. These capacitors illustrate some of the many types the technician will encounter in servicing.

some leakage. A capacitor with high leakage current is said to have a *high power factor*; just remember that in capacitors power factors are like living costs — the lower, the better.

If we keep increasing the voltage across the plates of a capacitor, we eventually reach a point where the current will break through the dielectric and destroy it (unless, of course, it is air). Increasing the thickness of the dielectric will make this breakdown voltage higher, but it will also reduce the capacitance. Most capacitors used in radio work carry, in addition to their capacitance value, a marking indicating the maximum voltage with which they are to be used. These voltage ratings may vary all the way from a few volts to several thousand for various applications.

The picture (Fig. 403) shows the wide variety of capacitors used in radio work. In the next chapter we will take up the actual construction of capacitors, the good and bad points of each type. We will also find out why it is necessary to have so many different forms of capacitors when they all operate on the same basic principle.

If you are impatient to get to this discussion of the practical aspects of capacitor construction, just remember that unless you have a good, firm grasp of the theory of operation, you will have a hard time understanding *any* type of construction, whether it be an internal combustion engine or a baby's three-cornered pants!

QUESTIONS

1. What are the basic elements of a capacitor?
2. Describe a simple practical capacitor.
3. What happens when a capacitor is connected to a battery? Why does the current cease after the capacitor is fully charged?
4. Why does a voltage remain across the capacitor terminals after the battery has been disconnected?
5. Define the unit used to measure capacitance.
6. What is a *microfarad*? a *micromicrofarad*?
7. Describe in detail how the nature of the dielectric affects the storage capacity of a capacitor.
8. Give three ways in which capacitance can be increased.
9. What is the dielectric constant and what is its symbol?
10. Give the K of air, of mica, of glass and of rutile ceramics.
11. Does a good capacitor have a high or low power factor? Explain.
12. What does the "maximum voltage rating" of a capacitor mean?

5

HOW CAPACITORS ARE MADE



A CAPACITOR, we learned in the last chapter, is a device for storing an electrical charge; and the amount of charge stored depends upon the voltage applied and the capacitance of the capacitor. We found that capacitance was related to the active area of the capacitor plates, the spacing between those plates, and the K of the dielectric employed. Two desirable features in a capacitor are low leakage current and high breakdown voltage. Now let us see how all these factors enter into the construction of actual capacitors used in radio work.

There are more ways of designating capacitors than there are of describing pretty girls, but one of the most common methods is to refer to the dielectric material; so let us begin with *air* capacitors—those with only air between their plates.

The simple capacitor discussed in the previous chapter used only two plates, but most air capacitors use several. The plates are divided into two sets, with all the plates of each set connected together, and with the plates of one set interleaved with the plates of the other, as shown in Fig. 501. This is to economize on space. You will recall that in a charged capacitor the electrons are crowded onto that portion of the negative plate facing the positive plate. That means that in a simple capacitor only one surface of the plate is used for electron storage.

However, as can be seen in Fig. 501, when the plates are interleaved, each surface of each negative plate is charged with elec-

trons when it is between two positive plates, and the result is the same as doubling the size of the plates in a two-plate capacitor. It is just like buttering your bread on both sides!

By arranging our capacitor so that we can control the degree of interleaving of the plates, we can produce a variable capacitor similar to most air-spaced units used in radio work. Very stable as to capacitance, they have almost zero leakage current. They are bulky, though, and it is difficult to build very much capacitance into a reasonable space. You seldom see air capacitors of more than 500 μf . The main trouble that develops in these capacitors is warping or bending of the plates so that they touch and short out. Occasionally sufficient dust gets between the plates to form a low-resistance path. In a variable capacitor, one set of plates (the rotor) must move, and a sliding wiper contact is used to make an electrical connection to this set. Sometimes dirt or corrosion causes this contact to become erratic.

A capacitor of considerably greater capacitance can be built in the same space by using thin sheets of mica as the dielectric and by employing much thinner metal plates. These *mica* capacitors, as they are called, are enclosed in a case of bakelite or similar material for mechanical protection and to keep out moisture.

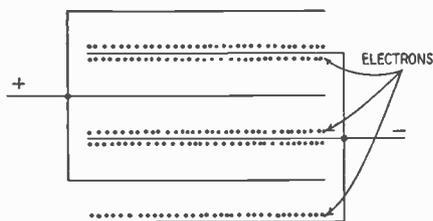


Fig. 501. Interleaved plates of a basic air-dielectric capacitor.

Since mica has a higher K than air, mica capacitors are more compact than air capacitors. Their leakage is nearly as low; and, by using thicker sheets of mica, the breakdown voltage can be made very high. You will find them in ranges from about 100 to several thousand volts, and from 100 μf to about 0.1 μf . However, they are comparatively expensive; and, as breakdown voltage and capacitance increase, they become quite bulky. A very stable type of mica capacitor, the *silver mica*, is made by silver plating directly onto the mica sheets instead of metal plates.

Mica capacitors do not give much trouble, but they do give some. In fact, like an "angel child," micas develop faults just often enough to waste a lot of your time checking everything else before your suspicion finally falls on them. Occasionally they break down and short out, or the wire lead connecting to a set of plates makes a poor contact and causes an "open" capacitor. More rarely, moisture may get in and cause a high leakage current.

Paper capacitors are the workhorses of radio; they really carry the load. Even an a.c.-d.c. midget has a dozen or so of them. They usually consist of two long, thin strips of aluminum foil, insulated by paper and rolled up in a tight little cylinder, with wire leads from each strip of foil being brought out of opposite ends. They are covered, treated with oil, and sealed with wax against moisture.

Paper capacitors are ordinarily found in values from about .001 to several microfarads, and from 100 to 1,600 volts. They are more compact than micas and cheaper, but they have somewhat higher leakage currents and deteriorate with age because of the gradual penetration of moisture into the paper.

Immersing a paper capacitor in certain types of oil increases its breakdown voltage and also increases its life because the oil prevents the entrance of moisture. That is why military equipment and equipment that *must* be dependable, uses *oil-filled* capacitors instead of the ordinary paper kind. The smaller ones are sometimes called "bathtubs."

Thin plastic films are also used, in place of the paper, as a dielectric, and some of these plastic-film capacitors have electrical qualities superior even to mica units.

Paper capacitors have the same shorting and open troubles to which micas are occasionally prey, but they have them much more often. They are more likely to become leaky, too; and if they become too hot, the wax runs out of them and allows moisture to enter easily. Still they are by far the most often-used capacitors in radio because of low cost.

For securing the most capacitance in the least space for the smallest amount of money, *electrolytic* capacitors are the answer. These come in two kinds, wet and dry. Fig. 502 is a sketch of a wet electrolytic. It consists of an aluminum plate, called the anode, immersed in an electrolyte, such as a boric acid solution. The anode has on its surface a very thin oxide film that has been formed electrochemically prior to assembling the capacitor and putting it into its case.

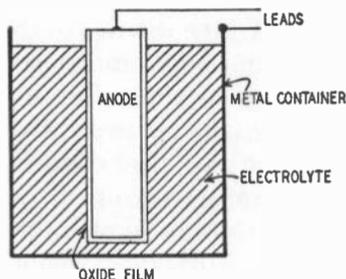


Fig. 502. All modern electrolytic capacitors were developed from this basic wet electrolytic structure.

Following the previous explanations, you might jump to the conclusion that the electrolyte is the dielectric, but that is not true. The dielectric is the thin oxide film—which incidentally has a K of about 10. The aluminum anode forms one plate of the capacitor, and the electrolyte forms the other; the metal container simply serves as a means of making contact with the electrolyte.

Dry electrolytic, like *dry cell*, is somewhat of a misnomer. *Damp electrolytic* would be better, for in such a capacitor the liquid electrolyte is replaced with a paste. What is more, the anode is replaced with an oxide-coated strip of aluminum foil, and the container is replaced with an uncoated strip of foil called the cathode foil. These two strips of foil, with the electrolytic paste and a suitable mechanical separator between them, are rolled into a bundle in exactly the same way as are paper capacitors. The result is a convenient cylinder.

The capacitance depends on the surface area of the anode and on the nature and thickness of the film. To increase the surface area, the anode foil is frequently etched with acid, and the increased area of the “hills and valleys” thus produced on the foil surface increases the capacitance of an *etched-foil* capacitor over that of a plain-foil unit by two to seven times. Another way of doing the same thing is to spray molten aluminum on a strip of cotton gauze to produce a gridlike anode that will give a capacitance 10 times that of a plain anode strip. These are called *fabricated-plate* electrolytic capacitors.

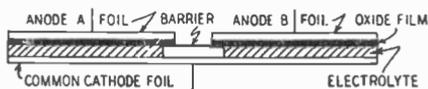


Fig. 503. Basic structure of a dual dry electrolytic capacitor.

The thickness and nature of the oxide film are determined by the forming process. While a thinner film increases the capacitance, it also lowers the breakdown voltage. Electrolytics used in electronics are found in capacitances of a couple to several thousand microfarads and in a voltage range up to 600. By using more than one anode strip or more than one cathode strip, and by having barrier strips separating these units, it is possible to have more than one capacitor in a single container. Fig. 503 shows one such dual-unit arrangement.

Electrolytics are unlike other capacitors in that they ordinarily are *polarized*. This means that they must be used only with d.c. voltages and that the anode must always be connected to the positive point. If these rules are not followed, the oxide film will disintegrate and the capacitor will be destroyed.

An electrolytic capacitor is only as good as its oxide film, and various factors can injure this coating. A temporary surge of high voltage may puncture it; but if the voltage is quickly reduced, the film will usually heal itself. A reverse current through the capacitor, impurities in the materials used, long subjection to too high a voltage, and too many months spent lying unused on the shelf will usually result in permanent damage. Electrolytics are usually designed to operate between 32 and 140 degrees F, and they should not be subjected to temperatures far beyond these extremes for any great length of time.

If the film is broken down, the capacitor usually appears as a partial or complete short, and the leakage current is excessive. If the electrolyte dries out or if one of the connecting leads becomes separated from its foil, the capacitor shows an open circuit. Sometimes, before complete evaporation of the electrolyte, the capacitor shows a marked loss of capacitance.

Ceramic capacitors enjoy a deserved popularity. They consist of tubes or disks of rutile ceramic with opposite surfaces plated with silver. The two silver coatings are the capacitor plates, and the ceramic material is the dielectric—with a K up into the hundreds!

Ceramics, like some women, seem to have everything—small size, high capacitance, high voltage rating, and low power factor. What is more, by regulating the mixture of the ceramic material, the capacitor can be made to have a positive, zero, or negative temperature coefficient, which is another way of saying that the capacitance can be made to increase, stay the same, or decrease with a rise in temperature. This feature compensates for heat

changes in other components of an electrical circuit. When the capacitance of these components "zigs" with an increase in temperature, you can employ a ceramic capacitor that "zags" an equal amount, and *vice-versa*, and thus maintain the over-all capacitance constant.

The manufacturers did not develop all these different types just to show what they could do. Each type fills a particular need. The choice for a particular job depends upon which will do the work best for the least cost. In some spots the most important thing is lots of capacitance; so an electrolytic is used. At another point the capacitor must not change its value; so a silver-mica unit is employed. If the leakage must be extremely low, an ordinary mica serves nicely; and for run-of-the-mill applications, paper capacitors do the job. Where space is at a premium or leads must be kept short, as in high-frequency applications, disc ceramics are the ticket. Air-spaced units are used for variable and semivariable duty because of obvious mechanical advantages.

Now that we have become thoroughly familiar with the strengths and weaknesses of the coil and the capacitor, it is high time that our hero and heroine meet; and that they will do in the next chapter. Don't miss this thrilling event, folks, "When Coil Meets Capacitor," for that is how radio began!

QUESTIONS

1. What are the advantages and disadvantages of air-dielectric capacitors?
2. How is a mica capacitor made? a silver mica capacitor?
3. Describe the construction of a paper capacitor. What are its advantages and disadvantages?
4. What capacitor provides the most capacitance in the least space for the smallest cost?
5. What constitutes the dielectric of an electrolytic capacitor?
6. Is a dry electrolytic really dry? Explain.
7. What do we mean when we say an electrolytic capacitor is "polarized?"
8. What happens if such a capacitor is connected into a circuit so that it is exposed to a reversed polarity voltage?
9. How are ceramic capacitors made?
10. List several good points of these units.
11. What do we mean when we say a capacitor has a positive, zero or negative temperature coefficient?
12. Explain why so many types of capacitors are used.

6

REACTANCE, IMPEDANCE AND PHASE

.....

WE are now nearly ready to splice inductance and capacitance together into that blissful state known as "the tuned circuit." But before the actual wedding takes place, we ought to make sure that the union can withstand any and all strains that may be placed upon it. It is true that we have observed how both an inductance and a capacitance behave under the influence of a direct current, but do we know what they will do when an a.c. voltage starts pushing and tugging at them? Perhaps it would be well to investigate this angle before we bestow our blessing on the marriage.

You cannot penetrate very far into the a.c. woods without having a clear understanding of *phase*; so we may as well get that straight right now. Phase simply means *comparative time of occurrence* as applied to actions, changes, or events. If two things happen together, we say they are *in phase*. If one happens first, we say that it has a *leading phase*. The thing that happens second is said to have a *lagging phase* with respect to the first.

Consider the case of you and your one-and-only doing a dance step. If the feet of both are in phase, her foot moves back at the same instant your foot moves forward. If your foot has a leading phase, it will move forward before hers is out of the way, and you will probably step on her toes and be told you are a poor dancer. If your foot has a lagging phase, she is doing the leading, and you are going to be a henpecked man!

As applied to electricity, phase usually means a comparison between similar changes in two or more different voltages or between a single voltage and its accompanying current. For example, Fig. 601 shows what happens when an a.c. voltage is applied across a pure resistance. Don't be surprised if you don't see it; Fig. 601 has probably balled up more students than any other diagram in the science of radio! It's supposed to show the life history of a cycle of alternating current. In our figure, having chosen the standard 60-cycle current, our base line is laid off in fractions of a 1/60 second. This makes it a time chart, just like the rolls that record the temperature for a day, with a thermometer-controlled pen making a continuous track. Any point on the voltage curve on the chart will tell you just what the voltage is at that instant—the curve is simply a combination of all those instantaneous voltages.

No, alternating current really does not wiggle as the chart might lead you to believe. What happens is that current from the alternator starts to flow through the resistor, starting with very low (zero, to be exact) voltage and current. Both current and voltage rise until, at the end of 1/240 second, we have maximums of 170 volts (dashed line) and 2½ amperes (solid line).

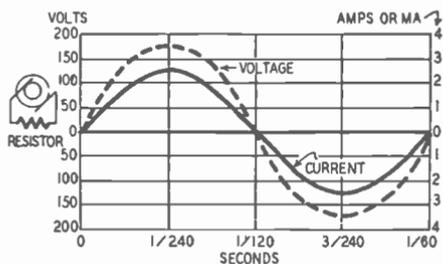


Fig. 601. *E and I in a resistance are in phase.*

The exact quantities are unimportant; in many radio circuits we have alternating currents of some hundreds of volts at only a few milliamperes, and in some welding circuits there may be hundreds of amperes with only a few volts. In most a.c. diagrams, voltage and current curves are arbitrarily drawn the same height—see Figs. 602 and 603. The only reason we didn't do it here is that the two curves would then be on top of each other, and you couldn't tell them apart. Neither is the frequency important; we have used 60 cycles because it's common, but the story would be equally true at radio frequencies.

But now—because of the way an alternator is built—our voltage and current start to drop, and at the end of $1/120$ second there is no voltage across the resistor and no current flowing through it. Then the current starts to flow through the resistor *in the opposite direction*. Our clever mathematicians represent these volts and amps in the reverse direction by just drawing the voltage and amperage curves in the opposite direction to the first ones. Neat, eh?

Following the chart, we find that voltage and current in this direction again rise to a maximum in $1/240$ second from the time they started, and in another $1/240$ second are also back to zero. Total time $1/60$ second, and we are back at the end of the circle (or cycle — it's the Greek word for circle) and ready to start all over again.

This is all to tell you what you probably don't need to be convinced of — that the voltage across the resistor and the current through it are exactly in phase, and that when the voltage is maximum or minimum, so is the current; and both reverse precisely in step. But when the resistor is replaced by either an inductor or capacitor, this harmonious state of affairs no longer prevails. A *phase shift* takes place, and the current reaches a maximum value at a different time from that at which the voltage is highest. Let us see why.

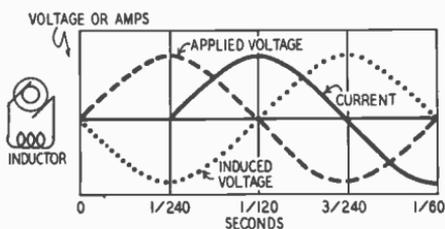


Fig. 602. Phase relations in inductive circuit.

Fig. 602 shows what happens when an inductance is placed across the output of an a.c. generator. The dashed line shows the voltage applied to the coil. You will recall from our discussion of self-induction (read it again if you don't) that the changing current through the coil produces a counter-e.m.f. (voltage) very nearly equal to the applied voltage but directly opposed to it. This induced voltage is shown by the dotted line. Notice that when the applied voltage is positive (or for a.c. it might be better

to say "in one direction") this induced voltage is negative ("in the other direction") and *vice versa*.

Remember that this induced e.m.f. is produced by the expanding or contracting lines of force cutting the turns of the inductor. Further recall (or re-read) that these lines of force are in motion *only when the current is changing value*. Still further, the induced

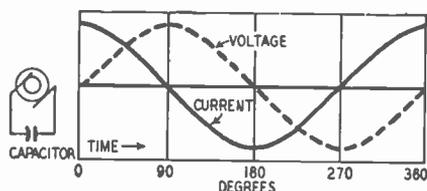


Fig. 603. Current leads in capacitive circuit.

voltage is highest when the movement of the lines of force — and consequently the *rate of change* of current — is fastest. Keeping all of this in mind (yes, I know it's a neat trick), where would you say the rate of change of current on Fig. 602 is the greatest? the least?

The solid line represents the current flow. The rate of change is highest when this line is most nearest vertical; least, when it is horizontal. As you suspected all along — but can now see on the diagram — the rate of current change is least when the current itself is maximum. It is at these maximum-current points that the induced voltage — sustained *only* by a *changing* current — is zero. On the other hand, the *rate of change* is greatest at the point where the current is just starting to reverse its direction or cross the zero line; and this is the point of maximum induced voltage.

In experimenting with an induction coil, we found that the current reached a steady value a split second *after* the voltage was applied. We can see from our diagram that the current peaks are separated from both the induced and the applied voltage peaks by a quarter of a cycle. Since we know that we must apply the voltage first, we can see that in a pure inductance the current lags the applied voltage by a quarter of a cycle.

The armature of an a.c. generator has to make one complete revolution or turn through 360 degrees to produce one complete cycle of voltage. The angle through which this armature has turned from the starting point is indicated in degrees along the time axis. This is all there is to "degrees," as applied to phase

lead or lag or other a.c. terms. It is convenient to divide the cycle (remember, it's a circle) into 360 degrees and refer to fractions of a cycle in degrees instead of saying — as we did, clumsily — $1/240$ second, etc. Every quarter of a cycle is seen to occupy 90 degrees. Do you see why we say that, *in a pure inductance, changes in current lag changes in applied voltage by 90 electrical degrees?*

Fig. 603 shows what happens when an a.c. generator is connected across a capacitor. The dashed line again represents the value and polarity of the applied e.m.f. with respect to time. As the voltage first starts to rise in the "positive" direction, electrons are easily pushed onto one of the plates of the capacitor and rush on at their maximum rate, for they encounter little resistance. But as this plate acquires more charge, its voltage rises (note dashed line) and begins to repel the electrons the generator is trying to force upon it. The movement of electrons, which makes up the current in wire circuits, slows down and finally stops when the applied e.m.f. and the electron charge have reached their maximum values (at 90° , or one-quarter of a cycle). Then, as the applied voltage starts to decrease, *the packed electrons begin to flow back into the wire*, against the applied voltage, through the generator, and on to the other plate. They keep right on flowing in increasing number while the applied voltage falls to zero and starts to build up in the opposite direction; but the current again begins to droop as the other plate nears its maximum charge. Thus we see that the current through the circuit is maximum when the applied voltage is minimum and is at its minimum when applied voltage is highest. Since the electrons have to flow onto the plate of the capacitor *before* its voltage can rise, it is easy to see why *the current through a pure capacitance leads the applied e.m.f. by 90 electrical degrees.*

You have noticed that a capacitor, which says a firm "No!" to the passage of d.c. after it has once become charged, seems to murmur a coy "Maybe" or even "Yes" to the knocking of a.c.? While the electrons do not actually pass through the dielectric material, their rushing back and forth through the connecting circuit from one plate to another creates an alternating current in that circuit just as if the capacitor were replaced by a resistor.

We say "resistor" instead of "short circuit," for the capacitor does offer some opposition, depending on its capacitance and the frequency of the applied a.c., to the passage of current. As the capacitance is increased, more electrons must be moved to charge it each time; therefore, the current that is composed of the move-

ment of these electrons is increased just as if the equivalent resistance represented by the capacitor were lowered. If the frequency of the applied voltage is increased, the electrons have to make more trips back and forth between the plates in a given length of time, and more electron trips mean more total current just as if the equivalent resistance were lowered again.

This "equivalent resistance" offered by a capacitor to the passage of a.c. is called *capacitive reactance*, has the symbol X_c , is measured in ohms just like resistance, and for any given capacitor can be found by the formula:

$$X_c = \frac{1}{2\pi f C},$$

in which f is the frequency in cycles per second, C is the capacitance in *farads*, and 6.28 is 2π (π is your old friend of grammar-school days, 3.1416). If you want to know the reactance of a 1- μ f capacitor at 60-cycles, you simply substitute in the formula, not forgetting to change microfarads to farads. Or if you want to work with microfarads, simply multiply the numerator by a million, thus:

$$X_c = \frac{1,000,000}{(6.28) (60) (1)},$$

and you find that the answer is approximately 2,654 ohms.

When you recall that an inductance is stubbornly opposed to any change in the amount of current flowing through it, and also remember that the current in an a.c. circuit is changing almost continuously, it should be easy to see that an inductance, too, is going to offer more than a little opposition to the flow of a.c.

The amount of this opposition increases when either the inductance or the frequency of the applied voltage is increased. Since the induced or opposing voltage increases with the amount of inductance encountered, it is not hard to understand why a greater inductance will offer more opposition to the flow of current. The induced voltage also depends on the speed with which the expanding and contracting lines of force cut the wire; and since an increase in frequency means that the lines have to speed up in order to go through their expanding-contracting routine more often in the same space of time, no great brain is required to grasp why an increase in frequency stirs up more opposition to current flow.

This resistance which an inductance presents to the flow of a.c.

is called *inductive reactance*. It has the symbol X_L , is measured in ohms, and is found by the formula:

$$X_L = 2\pi f L,$$

in which f is again the frequency in cycles per second, L is the inductance in henrys, and the 2π is 6.28, the same ancient mathematical pastry we had served up in capacitive reactance. If we want to know the reactance of a 10-henry choke to a 60-cycle voltage, simply substitute in the formula:

$$X_L = (2) \times (3.1416) \times (60) \times (10).$$

and we find the answer: just under 3,770 ohms.

To review a little while we catch our breath: *Resistance* is the opposition offered to the flow of a steady direct current; *Reactance* is a specialized form of opposition that a.c. runs into. Reactance comes in two flavors: *capacitive or inductive*, according to whether the current leads or lags the voltage. While all three impede the flow of current, they are not at all alike. Resistance uses up power and dissipates it in the form of heat. Reactance transforms electric current into a magnetic field in an inductance or an electrostatic field in a capacitor for a portion of a cycle and then returns this stored energy as an electric current during the remainder of the cycle. With pure reactance in the circuit — never actually found in practice — the energy is just swapped back and forth from one form to another without any loss of power. In a purely reactive circuit, there is a 90-degree phase shift in one direction or the other from the in-phase condition of a purely resistive circuit. The more resistance we have in comparison to the reactance, the fewer are the degrees of phase shift (the closer together are current and voltage maximums or minimums).

Capacitive and inductive reactances have exactly the opposite effect on phase, and can be combined just like positive and negative numbers. In a circuit containing both, the effective reactance is found simply by subtracting the smaller reactance from the larger and giving it the name of the larger. For example, in a circuit containing 15 ohms of capacitive reactance and 10 ohms of inductive reactance, we just take 10 from 15 and say that the circuit has 5 ohms of capacitive reactance.

In addition to reactance, all actual circuits have some resistance; and we have a special word to describe this total opposition

to a.c. That word is *impedance*, represented by the symbol Z , and it means "reactance and resistance." The two are somewhat like fractions and decimals in that you cannot add them directly. You have to extract the square root of the sum of their squares, which gives us the formula for finding impedance:

$$Z = \sqrt{R^2 + (X_c - X_L)^2}$$

Suppose, for example, we have a circuit containing 4 ohms of resistance, 10 ohms of capacitive reactance, and 7 ohms of inductive reactance (total reactance $10 - 7$, or 3 ohms capacitive). Substituting these values in the formula:

$$Z = \sqrt{4^2 + (10 - 7)^2} = \sqrt{16 + 9} = \sqrt{25} = 5 \text{ ohms.}$$

A typical inductor, capacitor, and resistor are shown in Fig. 604.



Fig. 604. Chief actors—inductor, capacitor, resistor.
(Stancor Electronics, Inc.)

But here is the end of the chapter, and the union of capacitance and inductance into a tuned circuit — like the marriage of a woman and a reluctant man — has been repeatedly postponed. These nuptials will take place in the very next chapter!

QUESTIONS

1. What is the general meaning of *phase*? What does it mean in electricity?
2. What is the phase relationship of voltage and current through a resistor?
3. What is the phase relationship in a pure inductance? Why?
4. What is the phase relationship in a pure capacitance? Why?
5. What is another way of saying current lags voltage by a quarter-cycle?
6. What do we call the "equivalent resistance" offered by a capacitor to the passage of a.c.?
7. Give the formula for capacitive reactance.
8. Define *inductive reactance* and give the formula for it.
9. What is the chief difference between resistance and reactance with regard to power consumption?
10. What is the value and nature of the reactance of a circuit with 15 ohms of capacitive reactance and 25 ohms of inductive reactance?
11. Define *impedance* and give the formula for obtaining it.
12. What is the impedance of a circuit containing 8 ohms of resistance, 10 ohms of capacitive reactance and 4 ohms of inductive reactance?


7

RESONANT CIRCUITS

.....

TUNED circuits do for the radio engineer what good looks do for a girl: they allow him to select what he wants and reject what he does not want — from the available alternating current spectrum. This ability to put out the welcome mat for a particular frequency and to cold-shoulder others is of utmost importance. It permits the engineer to “tune” his radio circuits, and without tuning there would be no radio as we know it.

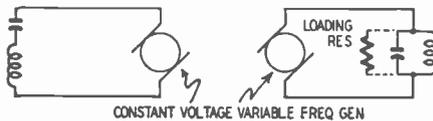Since all tuned circuits consist, essentially, of combinations of a capacitor and an inductance, their variety is not infinite. In fact, they come in just two models: the *series* and the *parallel*, of which Figs. 701 and 702 are illustrations. Note carefully that the



Figs. 701 and 702. *The series and parallel tuned circuits.*

two types are determined by whether or not the *applied voltage* is inserted in series with the capacitor and inductance or whether both of these circuit elements are arranged in parallel with this applied e.m.f. A parallel tuned circuit is *not* so named because the capacitor and coil are in parallel with each other, but because both of these are connected in parallel with — or directly across — *the applied voltage*. In a series circuit, the applied current must

go through *both* coil and capacitor; in a parallel circuit it has its choice.

Suppose the series circuit of Fig. 701 is connected across a generator of constant voltage but variable frequency. Then suppose we change from a very low to a very high frequency. Recalling that the reactance (resistance to the passage of a.c.) of a capacitor goes down with an increase in frequency whereas the reactance of a coil goes up, we can see that at a low frequency the excessive capacitive reactance prevents much current from flowing through our series circuit. At the high frequency, on the other hand, our capacitive reactance decreases, but the inductive reactance rises sharply and still prevents a great deal of current from passing. However, at some one frequency, called the *resonant frequency*, the reactance of the coil and that of the capacitor will be exactly equal, and the current will rise to a maximum value.

The reason for this rise in current is clear when we remember that capacitive reactance and inductive reactance are *opposite* in sign and must be combined like positive and negative numbers in algebra. Remember that a capacitor causes the current to rush *ahead* of the voltage, but an inductor holds it lagging *back* after the voltage; therefore, when the two are in series, the one undoes what the other does. This means that at resonance our total reactance is equal to the sum of two numbers equal in value but

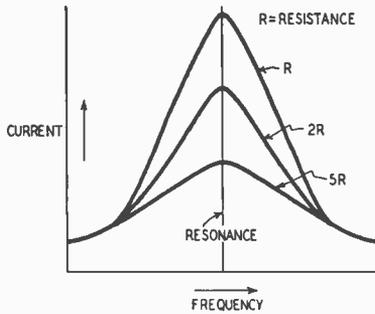


Fig. 703. Resistance effect on series circuit.

opposite in sign — or zero. Since the reactances cancel, the only thing impeding the flow of current through the series circuit is the ohmic resistance.

The lower this resistance is, the higher the current at resonance, as is shown in Fig. 703. When resistance is increased, it flattens

out the current peak; but since the resistance enters the picture seriously only in the immediate vicinity of resonance, the curves tend to coincide at points removed from resonance and at which the capacitive or inductive reactance is much greater than the resistance.

At the resonant frequency, the sizes of the coil and the capacitor are such that the time necessary for charging and discharging the capacitor is equal to the time needed for building up the current through the inductor and letting it die down. The discharging capacitor sends a heavy pulse of current through the coil; and when this current dies down, the collapsing magnetic field returns this charge to the capacitor. Look at Fig. 704. Suppose we had a coil and capacitor hooked up as in Fig. 702 and were able suddenly to put a big negative charge on one of the capacitor plates, as in 704-a. Electrons would immediately attempt to flow around to the other plate to neutralize the charge and get everything back to normal again. But in doing so, they have to flow through the inductor. This sets up a magnetic field which tries to oppose their passage. At 704-b we see a big magnetic field and no excess of electrons on either plate. The current is ready to stop flowing. But now the magnetic field starts to collapse, forcing electrons around (still in the same direction) onto the bottom plate of the capacitor. By the time the field has collapsed entirely, the situation is as in 704-c, and the electrons, now crowded onto the bottom plate, start to flow around to the top again, producing the condition of 704-d, which is identical with 704-b, except that current is flowing in the opposite direction.

At resonance, this swapping of energy is precisely timed, and heavy current is moved through the circuit. At frequencies other

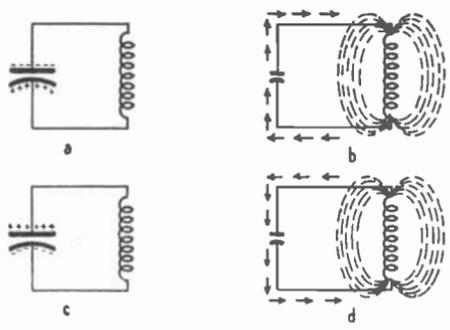


Fig. 704. The electron flow in a tuned circuit.

than resonance, things are more or less out of step, and the consequent confusion reduces the amount of current that can be handled.

A check with a voltmeter across the capacitor and the inductance of a *series-tuned circuit* reveals that a *considerably higher a.c. voltage is found across each than across the combination of the two*. To understand how one plus one can equal considerably less than two, remember that, although the current through a purely resistive resonant circuit is in phase with the applied voltage, this same current is leading the voltage across the capacitor by nearly 90 degrees and lagging the voltage across the inductance by approximately the same angle — just another way of saying that the voltages across the capacitor and the inductance are nearly 180 degrees out of phase with each other. Voltages 180 degrees out of phase are “bucking” voltages, working directly opposite to and cancelling the effects of each other. That is why the total voltage across the combination of capacitor and inductor can be less than the voltage measured across either one of them.

Let us consider an example: Suppose, as is shown in Fig. 705, a 1-henry coil and a 7.03- μf capacitor are connected in series across a generator that put out 100 volts at 60 cycles. Suppose, too, that the total ohmic resistance of choke and capacitor is 100 ohms.

Using the formulas $X_L = 2\pi fL$ and $X_C = \frac{1}{2\pi fC}$ to find the reactances of the coil and capacitor, respectively, we discover (by no coincidence!) that each has, at 60 cycles, a reactance of about 377 ohms. Since these two reactances cancel each other, only the 100 ohms resistance impedes the flow of current through the circuit.

Fig. 705. The values chosen for the coil and capacitor in the circuit shown at the right are for resonance at 60 cycles.



Whipping out and applying our trusty Ohm's Law ($I = E/R = 100/100$) we learn that our 100-volt generator will send 1 ampere of current surging back and forth through the circuit. But the voltage drop across a capacitor or coil is equal to its reactance in ohms multiplied by the amperes of current flowing through it: thus we discover that we would have about 377 volts across our capacitor and *another 377 volts* across our inductance. Believe it

or not, but you can try it with any 100-volt a.c. source and a 1,000-ohm-per-volt (or more) meter!

Assuming that what we want to do with our series tuned circuit is to obtain a maximum flow of current through it, our best circuit is the one with the least resistance. Since the major portion of this resistance below 30 megacycles is contained in the coil, it follows that a high-inductance, low-resistance coil is ideal. The symbol Q , used to indicate this measure of merit of a coil, is defined as the ratio between the coil's reactance and its resistance. If we were to assume that our coil had a resistance of 100 ohms then the Q of the coil used in our illustration would be equal to $377/100$ or about 3.75. Coils used in radio work may have Q 's exceeding 100.

Parallel circuits

When our variable-frequency generator is hooked across the parallel tuned circuit of Fig. 702, we find that at a low frequency the inductive reactance of the coil forms a low-impedance path across the terminals. At a high frequency, the capacitive reactance of the capacitor does the same thing. However, there is one frequency, again the resonant frequency, at which the two reactances are equal; at this frequency there is a high impedance to the flow of current from the line through the parallel tuned circuit.

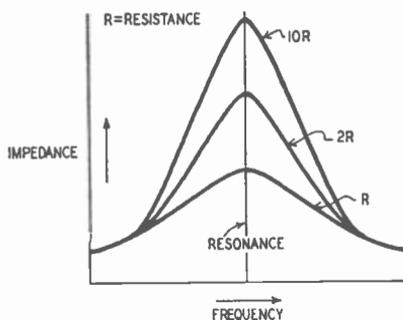


Fig. 706. Resistance lowers Q of parallel circuit.

Fig. 706 shows the impedance of a parallel tuned circuit. Note that it is almost an exact replica of the current-curve of the series tuned circuit.

The *why* of this sharp increase in impedance at resonance is

wrapped up in the fact that the currents through the inductive and capacitive branches of our parallel tuned circuit are 180 degrees out of phase with each other. While the current is flowing from top to bottom through the coil, it is flowing from bottom to top through the capacitor, and *vice versa*. Actually the current is oscillating back and forth through the tuned circuit like the balance wheel of a watch, and this current and the voltages it produces *are so timed* that very little current from the line is able to flow through the circuit.

Assume that the generator has built up a negative peak voltage on the top plate of the capacitor in Fig. 702. As this voltage begins to subside, the capacitor charge starts to force current through the coil and develops an expanding magnetic field about that coil. During the next quarter cycle, when the line voltage begins to build toward a negative peak voltage on the bottom plate of the capacitor, the collapsing magnetic field of the coil forces a counter e.m.f. of its own onto this plate to buck out the voltage from the line. When the line voltage reverses itself and rushes around to the top plate again to see if it cannot get its foot in the door there, this counter e.m.f. is right back there to slam the door in its face; and as long as the circuit is tuned to resonance, this exasperating voltage produced by the oscillating current within the tuned circuit is never caught napping.

The whole thing is similar to, and about as frustrating, as, patting a mirror. No matter how nimbly you move, that other guy behind the glass always meets your outstretched palm with the flat of his own hand!

There are just two ways to cross up this bar-the-door-they're-coming-in-the-window routine: One is to detune the circuit and thus throw off the timing of the oscillating current so that the line voltage can sneak some current through. The other is to weaken the voltage produced by the oscillating current by placing a resistor across the circuit. The current that flows through the resistor is dissipated in the form of heat and so is "lost," and the remainder of the circulating current is not sufficient to produce a voltage great enough to buck out the line voltage. This effectively reduces the resonant impedance peak of the circuit as is shown in Fig. 706. Sometimes we deliberately "load" a parallel tuned circuit with a resistor to make it present a more uniform (but lower) impedance to an extended range of frequencies.

While an unloaded parallel tuned circuit draws very little current from the line, the circulating currents inside the circuit

itself are usually high, being many times the line current.

To review: in a series tuned circuit at resonance, the current and the applied e.m.f. are in phase; the current is maximum; the impedance is minimum, equal to the ohmic resistance, and resistive; the voltage across the inductor is equal and opposite in sign to that across the capacitor; and both of the latter voltages are greater than the applied e.m.f.

In a parallel tuned circuit at resonance, the impedance is maximum and resistive; the current from the line is minimum; the circulating currents between the capacitor and coil are high.

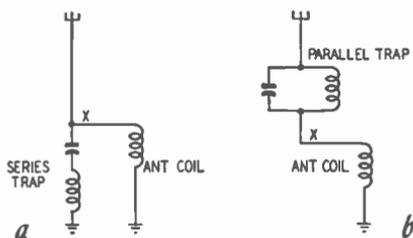


Fig. 707. Tuned circuits employed as wavetraps.

Perhaps their use as wave traps best illustrates the fundamental differences between the actions of the two circuits. Fig. 707 is an example. At 707-a, the series trap forms a very low impedance path between the antenna lead and the ground at its resonant frequency, while it presents a higher impedance to all other frequencies and forces them to pass through the antenna coil to reach ground. At 707-b the parallel tuned circuit in series with the antenna lead says "thou shalt not pass" to its resonant frequency, but it presents little or no obstacle to the passage of all other frequencies. The kind of guy who wears both belt and suspenders and never wants to be half safe could use both of these circuits to get rid of a single unwanted signal. (Not a joke — sometimes it's necessary!) The parallel circuit would keep most of it from reaching point X, and the series circuit would bypass the rest to ground.

To align our tuned circuits (or vary its resonant frequency), we must change either the inductance or the capacitance. We can use a variable capacitor with a fixed inductance, or a fixed capacitance with a variable inductance. Mechanically, it is usually

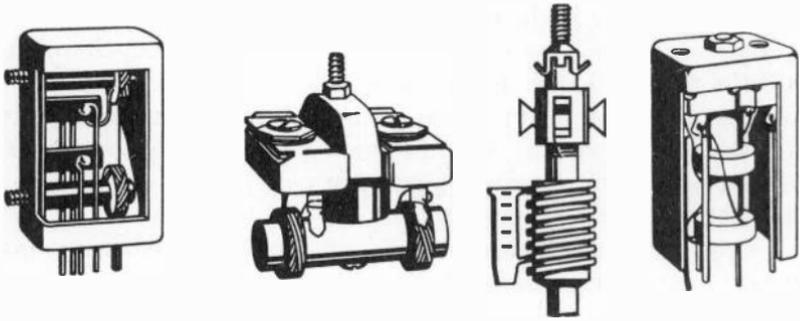


Fig. 708. *Typical tuned circuits are either trimmer- or slug-tuned.* (Stancor Electronics, Inc.)

easier to vary the capacitance with circuits requiring large amounts of inductance and variable inductances in high-frequency circuits where the inductance is comparatively small. Varying the inductance is easily accomplished by moving the core, or slug, in and out along the axis of the coil winding. A ferrous (or ferrite) core, a magnetic material, will increase the inductance and the reactance as it enters the coil; a non-ferrous core (brass, etc.) will reduce the inductance. A coil tuned with a movable slug is shown second from right in Fig. 708. The same illustration shows a number of tuned circuits.

The thing to keep clearly in mind is that tuned circuits permit you to single out a particular frequency and lead it down an irresistible path or to throw an insurmountable barrier across its way. You are the boss!

QUESTIONS

1. What determines if a coil-and-capacitor combination is a series-tuned or parallel-tuned circuit?
2. Under what condition does maximum current flow through a series-tuned circuit?
3. What limits this current at resonance?
4. Explain how in a resonant series-tuned circuit the voltage measured across either the coil or capacitor may be greater than the applied voltage.
5. Define the Q of a coil.
6. How does a high- Q coil encourage a maximum flow of current in a series-tuned circuit?
7. As a parallel-tuned circuit is varied through resonance, how does the impedance vary? Why?
8. Name two ways of reducing the impedance of a resonant parallel-tuned circuit.
9. Compare the current drawn from the line with the circulating currents in a parallel-tuned circuit.
10. Compare parallel- and series-tuned circuits at resonance.
11. Describe the operation of series and parallel wave-traps.
12. What is the main function of tuned circuits?

8

TRANSFORMERS—HOW THEY WORK




VERY few drivers do not understand why there is a gearshift in a car. You know it provides a choice between speed *or* power. Where the highway is smooth and level, high gear hustles the car along at a good gait without the application of much torque to the rear wheels and without racing the motor; but when climbing a hill or plowing through sand, low gear sacrifices speed to provide the driving wheels with increased rotating power.

What the gearshift transmission does for the automobile designer, the *transformer* does for the electrical engineer: it enables him to *transform* a given a.c. voltage to a higher voltage at a lower current, or to a lower voltage at higher current. Notice that voltage and current act like two kids on a seesaw: when one goes up, the other goes down.

This handy device for stepping voltage up or down is really very simple in construction. It consists of two coils so arranged physically that the magnetic field produced by passing an alternating current or a pulsating direct current through one of the coils (called the *primary*) also surrounds the turns of the other coil (called the *secondary*). The medium through which the magnetic field passes in *coupling* the two coils together is called the *core* of the transformer.

Fig. 801 is a diagram of a simple air-core transformer. When we apply an a.c. voltage across the primary, the variations of current produce an expanding and contracting magnetic field

Fig. 801. The dashed lines represent the magnetic lines of force. Not all these flux lines reach from the primary to the secondary as shown in this drawing.

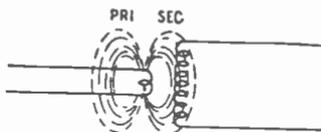

about the coil. The lines of force of this field will be constantly swishing back and forth through the turns of the secondary coil. We know that when moving lines of force are intercepted by a conductor, a current is generated in that conductor. The frequency of the current generated in the secondary is the same as that applied to the primary, but the voltage and amount of current available depend upon other factors.

Note in Fig. 801 that only some of the primary lines of force are intercepted by the secondary. Not much can be done to correct this without introducing other more serious losses in transformers which operate at radio frequencies. But, at audio and power frequencies, winding two coils upon a common iron core means that practically all the magnetic field produced by the current though the primary acts upon the turns of the secondary.

This is true because a magnetic line of force feels very much "that way" about soft iron, and it never passes through air if a soft-iron path is available. Consequently, as is shown by the dashed-line path of Fig. 802, practically all the magnetic field produced by the primary is confined to the iron core, which it threads through to act upon the secondary. What is more, the intensity of the magnetic field produced by the current flowing through the primary is greatly increased by the iron core, as we learned when studying inductance.

Transformation ratios

When a dog scratches fleas, he scratches himself as well as the fleas. The magnetic field produced by the primary of a transformer does about the same thing. Not only does it act upon the turns of the secondary, but it acts upon the turns of the primary as well and produces a back e.m.f. (voltage) that is nearly equal to the applied voltage producing the field. In fact, if there were no losses, it *would* equal the applied voltage, and no current would flow.

Watch closely now, we are going to do a little tricky but true reasoning. If we applied 10 volts across a 2-turn primary, and if the magnetic field produced developed a counter-e.m.f. of nearly 10 volts, would it not be safe to say that every primary turn cut

by this magnetic field produced very nearly 5 volts of back-electromotive force? Suppose, then we have a 6-turn secondary. Since the same magnetic field that produces the counter-e.m.f. in the primary is also working on the secondary, is not not logical to expect to find close to 5 volts per turn, or 30 volts across a 6-turn secondary? Well, that is exactly what we do find; and all of this leads up, after a little reflection, to a general statement: *the ratio of primary to secondary voltage of a transformer is practically equal to the ratio of the number of turns of wire in the two windings.*

For example, if we have 100 volts across a 100-turn primary, we will find 10 volts across a 10-turn secondary and 300 volts if the secondary has 300 turns.

Without the resistor in place across the secondary of Fig. 802, we should find our ammeter in series with the primary showing very little current, for the counter-e.m.f. would keep much current from flowing. But if we insert a low resistance across the secondary so that considerable current flows through it, we find our primary current greatly increased. Why is this? With no actual conducting path between the two windings, why does the current in the primary rise in sympathy with the increase in secondary current?

The answer lies in what happens to the magnetic flux passing through the core. When no current is being drawn from the secondary, this flux produces a bucking e.m.f. (electromotive force or voltage) that holds the primary current down to a very low level.

Don't hurry past this bucking e.m.f. — it's the important part of the story! The magnetic field which produces an e.m.f. of nearly 5 volts per turn in each turn of the secondary also produces a voltage of almost 5 volts per turn *in the primary itself.* But a field set up around any winding by a changing voltage

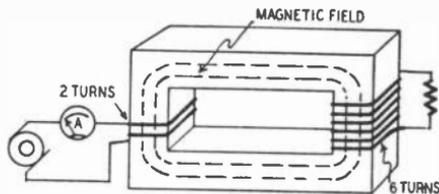


Fig. 802. Step-up transformer with iron core.

across it (current through it) produces in the same winding a voltage which opposes the original voltage which set up the field (Lenz's law). If there were no losses in the transformer, that counter-e.m.f. — or voltage if you prefer — would be exactly as strong as the line voltage and no current would flow. But all wire has resistance, and there are losses (which we will discuss later) in the best designed core. So we do have a small flow, called the *magnetizing current*.

However, when current flows through the secondary winding, that current produces a magnetic field of its own that *opposes* and partially cancels the magnetic field of the primary. Since the counter-e.m.f. of the primary depends upon the strength of its own field, a reduction in this field means a lowered back-e.m.f. and a consequent increase in primary current.

It is a cardinal principle of physics that "power out equals power in — less losses." Power in electricity is measured in watts, the product of volts and amperes. Mull this over a bit and you will see why, for a given power input to the primary, the current in the secondary goes down as the voltage goes up. Suppose we put in 50 watts to the primary of our transformer and ignore losses. That means that we have 50 watts available in the secondary. We can take our 50 watts in any combination of volts and amperes whose product is equal to 50. For example, we can have 10 volts at 5 amperes, 50 volts at 1 ampere, 100 volts at 0.5 ampere, and so on.

Evidently, any increase in the power taken from the secondary results in an increase in the current flowing through the primary. The actual d.c. resistance of the primary is seldom great enough to hold the current down to the current-carrying capacity of the wire, and the counter-e.m.f. or self-inductance of the primary is depended upon to prevent the current from rising too high. If such a heavy load is placed upon the secondary that this counter-e.m.f. is lowered too much, the wire of the primary will overheat and the transformer be destroyed, in spite of the fact that the secondary winding is heavy enough to carry its current safely.

Transformer losses

We have been ignoring transformer losses about as long as we can, so we may as well take them up here and now. Outside of the small loss due to the resistance of the windings, transformer losses usually take two forms: *hysteresis* losses and *eddy-current* losses.

When an a.c. voltage is impressed across the primary of a trans-

former, it produces in the iron core a magnetic field which reverses direction at twice the line frequency. Under the compulsion of this field, the atoms of the core have to keep shifting their position through 180 degrees to have their individual fields lined up with the reversing polarity of the primary field.

Now magnetic substances possess a quality that might be termed *magnetic inertia*, for they tend to retain any magnetism they have once acquired, and it takes energy to get rid of it. The magnetism in such a substance — because of this inertia — always lags behind the magnetic force trying to change it. This resistance to magnetic change is called *hysteresis*, and the energy expended in overcoming it is called *hysteresis loss*. This loss appears in the form of heat developed in the core material.

In some materials the molecules permit themselves to be flipped around with comparatively little resistance, while others are harder to change than bad habits. Hard steel has a high hysteresis loss, while annealed silicon steel has a comparatively low one. This explains why silicon steel is the favorite transformer core material.

Eddy currents

If we used a solid steel core like that of Fig. 802 for our transformer, the closed core would act as a single-turn secondary and have a low voltage induced in it by the varying magnetic field passing through it. This would produce circular currents — which would flow at right angles to the main magnetic field — in the core, as shown in the cross section of Fig. 803. These currents would be very large because of the low resistance of the large cross section of the core material. They would heat the core and waste energy. Such core currents, because of their circular direction, are called *eddy currents*.

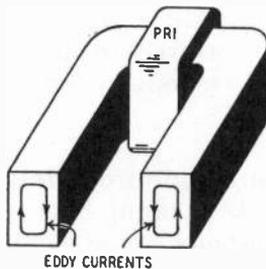


Fig. 803. The path followed by eddy currents.

To reduce eddy currents, the core is built up of thin sheets of metal insulated from one another, as shown in Fig. 804. Eddy currents still exist in each separate lamination, but because the cross section of the lamination is small and the silicon present adds to the resistance to current flow, the eddy currents in the individual laminations remain comparatively puny — so puny, in fact, that the sum of all the little eddy currents does not add up to anything like the big papa eddy current we had with the solid core.

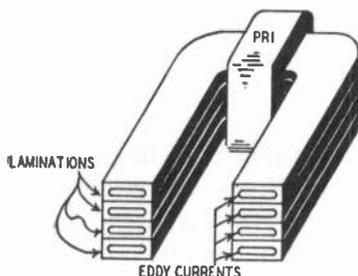


Fig. 804. Laminations reduce the flow of eddy currents.

As the frequency is increased, eddy-current and hysteresis losses go up; that is why we find air-core transformers being used at radio frequencies. In some cases a special form of powdered-iron core — made up of very minute particles of iron insulated from each other and glued together — is used as the core for radio-frequency transformers. If the core is adjustable, it can be slid in and out to vary the inductance of the coil and tune the circuit.

The radio engineer can do almost as many things with a transformer as a woman can with a bobby pin. He uses it to step voltages up and down, to transfer an a.c. voltage from one circuit to another without disturbing the d.c. components in the two circuits, to provide a low-loss coupling between two different impedances. Isolation transformers are popular for providing the radio technician with a 117-volt line current that does not have one side grounded, as is shown in Fig. 805. This is very useful in working on a.c.-d.c. receivers that employ one side of the line for B—, since it reduces the chance of shock.

A common requirement in a radio receiver is to have two separate low voltages for heating the filaments of the tubes and a high voltage for use in supplying the B-voltage. Instead of using three

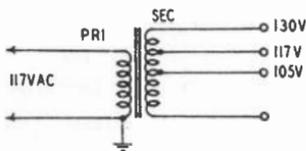


Fig. 805. The isolation transformer frees circuits from the electric light system ground. An isolation transformer is a sensible safety measure.

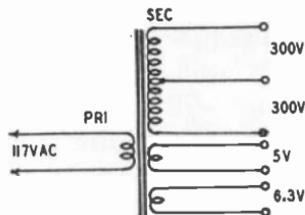


Fig. 806. Several windings may be combined on a core, as in this power transformer.

transformers, we can use a single transformer with three separate secondaries, as diagrammed in Fig. 806.

Transformer troubles

The main troubles encountered in transformers are open windings, shorts between windings, shorts between turns of the same winding, and shorts between a winding and the core. If a single turn is shorted, very heavy current flows through it and quickly develops a great deal of heat, damaging the insulation of neighboring turns and producing more shorted turns. However, if a well-built transformer is not subjected to overload; if voltage surges, such as are produced by lightning, are not allowed to enter the primary; and if insulation-destroying moisture is kept out, a transformer is a highly efficient, trouble-proof electrical device.

While we have touched on several different phases of transformer action, the subject is by no means exhausted. We will return to it later when studying such special cases as i.f. transformers, in which both the primary and secondary windings are tuned to the a.c. frequency being passed.

In the next chapter, though, we are going to see what happens to this electron we have been hounding through coils, capacitors, and resistors when it enters the vacuum tube. Do not miss this special attraction!

QUESTIONS

1. What is the basic function of a transformer?
2. What are the three essential components of a transformer?
3. What purpose is served by the transformer core?
4. What determines the ratio of primary to secondary voltage in a transformer?
5. Explain why increasing the load across the secondary of a transformer increases the current through the primary.
6. What are the two major sources of transformer losses?
7. What is *hysteresis*?
8. What are *eddy currents*?
9. Why is a low-frequency transformer core built up of thin insulated sheets of annealed silicon steel?
10. Give several uses for transformers in radio circuits.
11. How can a transformer be used to produce several separate voltages of different values from a single source voltage?
12. List several causes of transformer failure.

9

THE DIODE VACUUM TUBE

.....

HAVING spied on the busy electron while it skipped through conductors, resistors, coils, capacitors, and transformers, you may feel that you are an authority on the behavior of the little cuss; but until you have observed one doing its stuff inside a vacuum

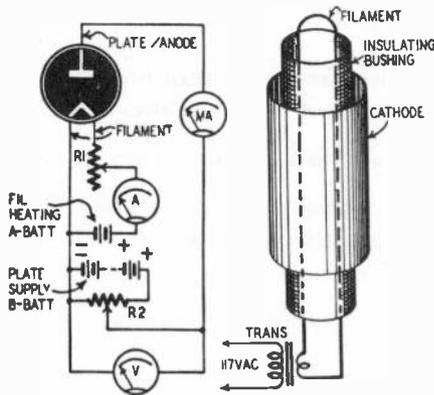


Fig. 901 (Left). Test setup illustrates diode action. Fig. 902 (Right). Cathode is cylinder surrounding the filament.

tube, you really have little idea of the power and versatility packed into one of these tiny charges of negative electricity.

Take a look at the experimental setup diagrammed in Fig. 901. The circle represents a hollow glass sphere in which are con-

tained a couple of loops of resistance wire and a small metal plate mounted near to, but not touching, this wire. Leads are brought out from the plate (sometimes termed the anode), and from both ends of the "filament" wire, and all the air possible has been pumped from the glass bulb before sealing it.

A low-voltage battery (called an "A" battery), an ammeter, variable resistor R1, and the filament are connected in series. Another, higher-voltage battery (called a "B" battery), with its negative terminal connected to the negative terminal of the filament battery, has variable resistor R2 bridged across it so that any positive voltage from zero (at the extreme left-hand position) to the full battery voltage (at the extreme right-hand position) may be selected by the moving slider. A voltmeter is arranged to read this voltage. The slider connects through a milliammeter to the plate of our "vacuum tube."

With the slider of R2 set at zero positive voltage (extreme left), let us slowly decrease the resistance of R1, permitting more and more current to flow from the "A" battery through the filament. The passage of this current produces heat in the filament wire; and when enough current flows, the wire becomes red hot. Our ammeter reveals how much current is flowing through the filament, but our milliammeter still stays near zero. However, if we move the slider of R2 to the positive end of the battery, the milliammeter indicates that current is now passing through it!

Where does this current come from? It must be flowing from the high-voltage battery, but where is the complete circuit? Surely the current cannot pass through the space between the filament and the plate inside the glass sphere, for we have always thought of a vacuum as being a perfect insulator; yet, there is no other logical explanation of what that milliammeter pointer is saying. The current *must* be bridging the gap inside the bulb, but how?

Remember that back in Chapter 1 we found there are always a number of free electrons wandering aimlessly around through any conducting material? By applying voltage, we can control the direction and speed of this movement of electrons to a certain degree; but even with no e.m.f. applied, the restless little jiggers are constantly hopping around from one atom to another.

When they come to the surface of the conductor, however, they bump into a force, somewhat resembling the surface tension of water, that keeps them from passing through. While they possess some *kinetic energy* (kinetic energy is power acquired through motion; it is the reason a soft hand can slap so hard), they do not

have enough to shoot through this surface barrier. They must have help if they are to escape into "the wild blue yonder."

Providing heat is the easiest way to supply this help. When the temperature of a body is raised, free electrons begin to feel freer and friskier by the second. They start to accelerate and to shoot madly about like a bunch of water bugs playing tag, and sooner or later one of them takes a long running jump and pops right through the surface of the body into the air or vacuum surrounding it. As the temperature goes still higher, more and more of these heat-propelled electrons make the grade until finally the heated object is surrounded by a veritable cloud of fugitive particles that it has *emitted*.

Please note that it makes no difference *how* the emitting body is heated. It could be done with a blowtorch, a gas flame, the focused rays of the sun, etc., but inasmuch as the emitting material must be heated inside a vacuum in our radio tubes, the heating effect of an electric current has proved to be the most practical.

Sometimes the filament itself is the emitting body (or cathode), as is the case in Fig. 901; but in other instances the emission is from an *indirectly heated cathode*, as is shown in Fig. 902. Here the filament is heated by current from an alternating-current transformer, and this heat passes through a bushing made of electrically insulating but heat-conducting material and raises the temperature of the sleeve-like cathode to the proper temperature for emission. Tubes are therefore loosely divided into "filament" and (indirectly heated) "cathode" types.

When an electron is emitted, its negative charge is subtracted from the total charge of the emitting body; therefore the body becomes unbalanced in a positive direction, tending to attract the negative electron back into itself if some other stronger force is not exerted on that negative particle. That is where the plate in our vacuum tube enters the picture. If the plate is positively charged with respect to the emitting filament, it tends to attract to itself the electrons that have escaped into the vacuum; and when there is a constant parade of electrons from the filament or cathode of a vacuum tube to the plate, we have a *plate current*.

These electrons pass from the plate to the positive terminal of the battery through the milliammeter, causing it to deflect. Incidentally, when only 10 ma is flowing, 6.28×10^{16} electrons are being emitted by the filament and attracted to the plate every second. However, the electrons flow from the negative terminal of the battery into the filament at the same rate at which

they return to the positive terminal *via* the plate; so no electrons are really lost or gained.

Now that the mystery of how current can flow through a vacuum has been cleared up, let us do a little more experimenting with the apparatus shown in Fig. 901. Suppose R1 is adjusted until our filament just begins to glow a dull red and that R2 is then manipulated so that the voltage applied to the plate starts at zero and advances in 10-volt steps. At each step, let us carefully note the values of the plate voltage and the plate current.

Next, let us increase the current through the filament until the filament is a bright cherry red, and then let us repeat our step-by-step increasing of the plate voltage, again carefully noting the changes in the readings of the voltmeter and the milliammeter. Finally, let us combine the results of these two observations in one graph, Fig. 903.

From this graph we can see that as the plate voltage increases, the plate current for the low-filament-current condition also increases, rapidly at first and then leveling off until a further increase in plate voltage produces practically no increase in plate current. The same thing is true after we have increased the filament current, but now the leveling-off point occurs at a higher value of plate current. For low plate voltages, the plate current is practically the same for high or low values of filament current.

The total number of electrons emitted from the filament depends upon its temperature, which in turn depends upon the current passing through it. The total number of electrons attracted to the plate depends upon, first, how many are emitted by the filament and, second, what percentage of these the attraction of the plate voltage can win over from the attraction of the filament itself. The higher the plate voltage, the higher is this percentage.

When our filament glowed a dull red, a limited amount of electrons were released. When the plate voltage was low, only a small number of these could be attracted to the plate instead of returning to the filament; but as the voltage, and consequently the attraction, of the plate went up, more and more of the available electrons succumbed to its siren call until finally it was getting *all* of them. Beyond this point, an increase in plate voltage obviously could not increase the plate current.

When we increased the filament current and raised the temperature of the filament, we increased the number of electrons

emitted. Under these conditions, it was necessary to raise the plate voltage still higher before it was attracting the total increased output of the filament. It is apparent that for every value of filament current there is a certain value of plate voltage which will attract *all* the emitted electrons and beyond which no further increase will result in more plate current. This maximum current is called the *saturation current* of the tube, and it is important that the tube be so designed that this saturation condition is never reached with the normal values of filament current and plate voltage that are applied.

Why the vacuum?

Perhaps you are wondering why there is a "vacuum" in vacuum tubes. Emission *will* take place in the open air, but there are two good reasons for placing our tube elements inside a vacuum. In the first place, if the filament were heated red-hot in the open air, it would oxidize quickly and be destroyed. In the second place, if the space between the filament and the plate were not emptied, the poor little electron would have a tough time trying to shoulder its way through the bulky atoms of air and gas which have a mass some 1,800 times that of its own.

The two-element tube that we have been studying is a fundamental type, as we shall note in the next chapter; yet this *diode*, as it is called, is used in some form or other in nearly every radio and television set on the market today. Diodes, like people, come in all sizes and shapes. Some of them are glass, ceramic or metal type tube diodes, while others are semiconductor selenium, germanium, or silicon diodes.

Diode tubes are subject to practically all the ills suffered by their more complicated brethren. If the filament breaks, we have no way of raising the temperature to the emitting point; and "open" filaments are one of the most common causes of tube failure. It is equally obvious that if any two elements, such as the filament and plate, actually touch each other, the tube cannot function normally. This "shorted element" route is one by which many tubes reach the junk pile.

As was pointed out before, the operation of the tube depends upon the elements being housed in a good vacuum, and anything that impairs this vacuum will ruin the operation of the tube. Occasionally minute amounts of gas remain in the tube or escape from some of the elements after sealing; then the tube becomes "gassy." Gassy tubes cause many headaches in the radio repair

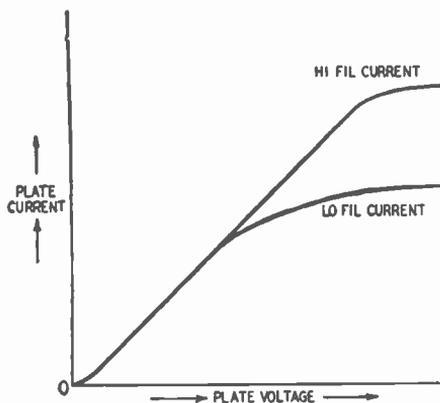


Fig. 903. *Hotter filament emits more.*

business, for they are not always as easy to detect as other defective types.

Even under normal conditions, the electron emission of a filament or cathode will fall off after a while, and this deterioration will be speeded up if the tube is subjected to overloads. Such reduced emission results in the "weak" tubes indicated by a tube tester.

Poor connections between the leads and the tube elements can result in "noisy" tubes that make a rasping, static-like sound in the speaker; and if the various elements are not held rigidly in place, the tube will often make a ringing sound come from the speaker when the tube is touched or bumped. Such tubes, because they behave like a microphone, are called "microphonic."

QUESTIONS

1. What is the name used for the battery that heats the filament of a tube? that supplies the plate potential?
2. Describe how current manages to pass from filament to plate through the vacuum inside a tube.
3. How are electrons encouraged to leave the filament?
4. Define *filament emission, indirectly-heated cathode, plate current.*
5. What two factors affect plate current in a diode?
6. What is *saturation current*?
7. Why is the vacuum necessary inside a vacuum tube?
8. List several types of diodes.
9. What are some causes of diode tube failure?
10. What is meant by a "gassy" tube?
11. Why do tubes eventually become "weak"?
12. What causes a tube to become noisy? microphonic?

10

TRIODE AND TETRODE TUBES



As pointed out in Chapter 9, the Father Adam of all electronic tubes is the two-element diode. One of the elements, the plate or anode, is simply a piece of metal without any special fussiness in its makeup. But the other, the cathode (or filament), is the key element in almost every electron tube—no matter how complicated it may be—because the electrons boiled out of it make up the emitted current that goes through the tube. In tube design the cathode material is extremely important; so let us dig a little deeper into the subject of cathodes.

In most tubes, the only way to make a cathode emit is to heat it. As with incandescent lamps, tungsten is the only wire that can stay hot enough to emit any practical quantities of electrons without melting. Pure tungsten filaments used in many large transmitting tubes are heated to a dazzling white—to 2,000 degrees C. (3,600 degrees F.).

Tungsten, while it stands up under heat, is not the best emitting material, and therefore many medium-sized transmitting tubes have tungsten filaments coated with thorium. These *thoriated* filaments liberate plenty of electrons when they are heated to a bright yellow—about 1,700 degrees C. (3,000 degrees F.).

But the filaments or cathodes of most radio and TV receiving tubes are coated with a mixture of barium and strontium oxides on a nickel-alloy base. They need be heated to only approximately 700 to 750 degrees C. (1,300 degrees F. to 1,400 degrees F.) to make enough electrons to boil out.

There always has to be a villain in the piece though, and the mustache-twirler of electron-tube current flow is the *space charge*. Picture the stage set for plate-current flow: the filament is heated and a positive charge from the B-battery or power supply is connected to the plate. Some of the electrons emitted from the cathode are pulled across to the plate by its positive charge. But other emitted electrons are not reaching the plate because the B-voltage simply isn't high enough; and they are just standing around between the filament (or cathode) and the plate doing nothing. This little cloud of not-so-innocent bystanders is called the space charge; being composed of electrons, it is charged negatively.

Now, as the heat of the cathode boils out more electrons from its surface, the space charge tries to push these electrons back onto the cathode—the negative space charge repels the negative emitted electrons. The positive plate is shouting, “Come on over!” to the electrons; but the space charge is commanding, “Get back on that cathode!” The space charge is nearer the cathode than is the plate; so the newly emitted electrons feel the effects of the space charge much more than those of the plate. Result: few electrons get to the plate and plate current is low.

One way to cut down the bad effect of the space charge is simply to cut down the distance between cathode and plate. In some rectifiers the cathode and plate are only .02 inch apart. Another way is to put a little mercury in the tube. When the filament heats, the mercury vaporizes and becomes a gas. When an electron on its way to the plate hits a mercury-vapor atom, it knocks loose one of the mercury atom's electrons. This electron promptly beats it over to the plate like a little boy at the end of a school day. The mercury atom now is missing one electron. Looking around, it discovers the space charge and snatches an electron from it. The mercury atom is whole again—and electrically neutral—but by gobbling up that electron from the space charge, it has reduced the space charge and aided the hard-working plate to attract a larger current.

Enter the triode

The early radio engineers, viewing this steady flow of electrons from cathode to plate, began to feel like small boys watching the stream coming out of a garden hose: they wanted to stick something into the current and see what would happen.

The something they inserted was a *grid*, and that is how the *triode* tube was born.

The grid is a mesh of fine wire wound around supports so that it surrounds the cathode. The drawing of a broken-open triode in Fig. 1001 shows the grid wire plainly. The drawing also shows the element structure of a typical triode vacuum tube.

The *control grid*, as its full name goes, is usually *biased* negative with respect to the cathode; that is, a negative d.c. charge is permanently placed on it. Sometimes a small battery is used; at other times the negative terminal of a power supply operated from the a.c. power line supplies the bias; and in still other cases other methods are brought into play. But the net result is that the grid is more negative than the cathode.

If the grid were positive, it would act somewhat like another plate—it would attract electrons, and there would be a grid current just as there is a plate current. Although the grid *is* positive in a few rare circuits, it is negative in most applications and does not attract any of the emitted electrons to itself.

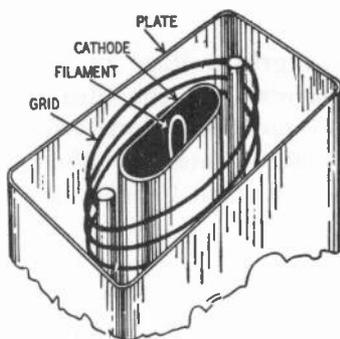


Fig. 1001. Arrangement of cathode and filament, grid, and plate in triode tube.

Like a water-logged life preserver, a negative grid not only is no help, it is a hindrance—it not only does not pull electrons away from the cathode but pushes them back!

So here we have the plate pulling electrons from the cathode and the grid pushing them back on. The question is: who has the most to say in this war of purposes? Answer: the grid. Reason: because it is so much closer to the cathode than is the plate.

When the grid goes negative, it is like a traffic policeman putting up his hand—traffic slows down or stops, as desired. When

it goes more positive (or less negative), you can imagine the policeman vigorously motioning all the cars to move on. When the *plate* voltage changes, however, it's as though a policeman 10 blocks away were directing the traffic. There is some effect on the electron traffic around the cathode but not much.

When the grid does become less negative and lets the plate pull electrons away from the cathode, the electrons pass right through the spaces in the grid mesh, just as the cars in traffic go by the policeman.

With all this in mind it is easy to see why the grid voltage has much more effect on the plate current than the plate voltage has. To state it another way, a small change in grid voltage produces a change in plate current which could only be duplicated by a much larger change in plate voltage.

You can prove this yourself with equipment no more complicated than that shown in Fig. 1002. A triode is wired so that both grid and plate voltages can be varied and plate current read on the milliammeter.

Suppose we start with -8 volts on the grid and $+250$ volts on the plate. Because of the construction of the tube, the plate current is 9 ma.

Now we change the grid voltage to -10 . The milliammeter reads 5 ma, which agrees with the idea that making the grid more negative pushes more electrons back on the cathode so they can't reach the plate. Remember, then, that to decrease the plate current by 4 ma, we had to make a 2-volt change in grid potential.

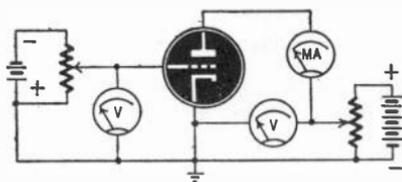


Fig. 1002. Test setup shows μ of a triode.

Now reset the grid voltage to -8 (so that 9 ma is flowing again). This time the object is to see how much the *plate* voltage must be changed to get plate current down to 5 ma. So we vary the plate-voltage control until the current is 5 ma. A look at the plate voltmeter shows 210 volts. Note that a 40-volt *plate-*

potential change was necessary to get the same effect on the plate current as was obtained with only a 2-volt grid change! The ratio of the two, $40/2$ or 20 , is the *amplification factor* (μ or μ) of the tube.

To make practical use of the tube as an amplifier, however, we must have some way of taking the amplified voltage changes and feeding them to other points in the equipment. The plate load resistor in Fig. 1003 is the part that solves the problem. As the plate current changes because of grid-voltage changes, the current rising and falling through the resistor creates a changing voltage drop across it. If the tube is operated correctly, the voltage changes across the load duplicate exactly the voltage changes at the grid, except that they are much larger.

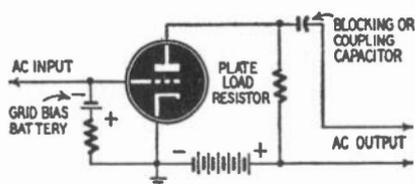


Fig. 1003. A plate load resistor is added.

They are *not* 20 times as large, though — there's a fly in the ointment. Every time the plate current rises, the drop across the resistor rises too . . . it must to furnish output. But the voltage on the plate is now less because much less than the full battery voltage reaches the plate. Of course, the lessened plate voltage does not entirely nullify the effect of the more positive grid voltage, because, as you remember, plate voltage is not anywhere near as effective in controlling the tube as is grid voltage. It does cut down the amplification somewhat, however, and, depending on the values of resistance and voltage used, the output voltage is only about 14 times the input.

There is one point to get straight: the tube does not take the input voltage and stretch it in some mysterious way to get a bigger output. The tube really does not amplify at all! It is a *control device*. It works similarly to the filling station hoist that sends your car up in the air so the garageman can work underneath it. The attendant works a little valve — and presto! your 3,000-pound automobile rises before your eyes. It isn't the attendant's hand that does the work, of course. It's the compressed air stored in a tank, released in the desired quantity by the little hand valve.

A vacuum tube is just like the little valve and the plate or B-battery like the stored compressed air. The incoming signal on the grid simply releases and dams up the stored electrical energy in accordance with its desires. There is no grid current, so no power is taken by the grid either from the batteries or from the controlling input signal. The output voltage — every bit of it — is energy from the B-battery. If there were no grid signal, there would just be a steady d.c. voltage across the load resistor. There would be no output because the capacitor prevents d.c. from passing. But when the grid signal starts alternately repelling and passing electrons, the d.c. across the resistor rises and falls with the plate-current changes. That gives it an a.c. character, and it passes through the capacitor.

The screen grid

Remember that, while the amplification factor of the triode is 20, we could get a real amplification of only 14 times in the practical circuit of Fig. 1003 because plate-voltage changes gummed up the works. The cure is to add another grid to the tube. Called the *screen grid* (or simply screen), it is located between the control grid and the plate, as in Fig. 1004.

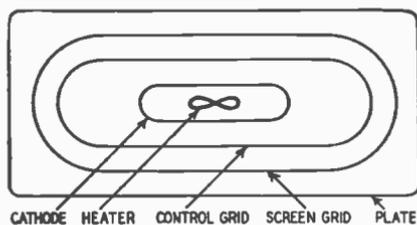


Fig. 1004. Screen between grid and plate.

The screen operates at all times with a positive voltage on it, a voltage about half that of the plate (more or less). The hookup appears in Fig. 1005. The screen voltage is fixed and does not vary with the plate current. Because it is positive, it helps the plate attract electrons from the cathode; most of the electrons, however, pass through the screen wires and go to the plate — screen current is very small.

Now the tube works just as before, with this exception: while the plate voltage changes periodically (just as it did before), the screen voltage does not. And because the screen is closer to the electron source (the cathode) than the plate, its pulling power is

greater. As a result, the plate voltage changes don't have anything approaching the effectiveness they had before in cutting down amplification. Even when the plate voltage is low, there is almost as much positive force pulling electrons through the tube as when the plate voltage is high. The amplification of a *tetrode*, as this tube is called, is many times higher than that of a simple triode.

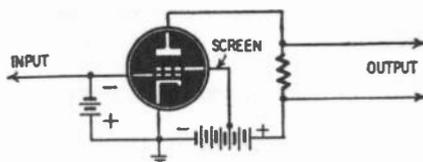


Fig. 1005. Circuit of a tetrode amplifier.

Another advantage of the screen is its reduction of grid-to-plate capacitance. Those two elements form the plates of a small capacitor through which some of the tube's output can feed back to the input, especially at higher frequencies. *Feedback* can produce all kinds of hair-raising effects, as we will find later on, but the screen grid, placed right in the middle of the grid-plate capacitance, breaks it up by acting like a shield or screen (hence its name) and reduces the capacitance (which may be several micro-microfarads in a triode) to something less than $.01 \mu\text{f}$ in the tetrode.

In the next chapter we will take a quick glance at a couple of more tube types and then wade into tube characteristics. Knowing the characteristics of a tube is just like having a trusted friend give you the lowdown on a coming blind date: it tells you exactly what kind of a performance you can expect!

QUESTIONS

1. What filament material will withstand the highest temperature?
2. Why are thoriated tungsten filaments used?
3. Of what are the filaments and cathodes of most radio tubes made?
4. How does a *space charge* reduce plate current?
5. Describe two ways of reducing space charge in a diode.
6. What new element converts a *diode* to a *triode*?
7. Where is it placed?
8. What do we mean by *grid bias*?
9. Describe how varying the grid voltage controls the plate current.
10. Is our name "amplifying tube" or the British name "valve" the more accurate name for a vacuum tube? Explain.
11. Define the *amplification factor* of a tube.
12. What new tube element reduces the effect of plate-voltage variations upon plate current? Describe its action.

11

THE PENTODE VACUUM TUBE

.....

MORE than 20,000 miles a second! That's the speed at which an electron hits the plate of the tetrode described in Chapter 10. No wonder that the terrific impact of the speeding electron knocks other electrons loose from the plate. It's like throwing an apple at an apple tree; if you throw hard enough, a whole shower of fruit falls to the ground.

Secondary emission

Up to now the only emission we have run into was that from the cathode, caused by heat, but now we have electrons emitted from the plate — and without any heat at all! This kind of knock-'em-loose emission is called *secondary emission* because it can't take place until a "primary" electron from the cathode comes along to do the knocking.

Secondary emission in a triode bothers no one. The plate is usually the only positive electrode in the tube and its irresistible fascination for the negative secondary electrons pulls them right back where they came from. The negative grid helps to shoo them on their way.

But the tetrode is a different story, for the screen is also positive, and some of the secondary electrons are attracted to it. The plate actually loses electrons to the screen. This wrong-way traffic is just about as upsetting inside our tube as it would be on a one-way street. Collisions occur between the "in reverse" electrons and

those emitted from the cathode; furthermore, electrons arriving from the cathode are repelled by the cloud of secondary electrons surrounding the plate.

The graph of Fig. 1101 shows these upsetting effects. The curves show how plate and screen currents vary when the plate voltage is changed. During the experiment, the screen is held at 80 volts. The test circuit appears in Fig. 1102. Beginning with zero plate

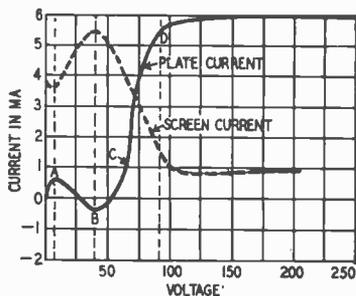


Fig. 1101. Curves show tetrode behavior.

voltage (potentiometer arm at ground end), plate current is zero. There is screen current, because the screen is 80 volts positive and acts like a plate.

Now we run up a little plate voltage, say about 10 volts. There is a little rise in plate current and a little drop in screen current because some of the electrons from the cathode are reaching the positive plate instead of going to the screen. The attraction of

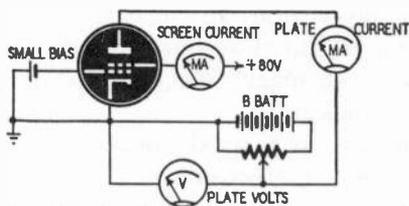


Fig. 1102. Circuit for obtaining tetrode curves.

the plate is not great enough to make them travel really fast, so they dislodge no secondary electrons from the plate.

As the plate voltage rises above the 10-volt level, however, the electrons speed up and a few secondary electrons are knocked off

the plate. Remember that the total plate current is made up of the electrons that reach it from the cathode *minus the secondary electrons grabbed by the screen*. As the plate voltage rises, the speed gets higher and higher, knocking off more and more secondary electrons for the screen to steal. As the graph plainly shows, the net plate current between voltages A and B actually gets *less* as the plate voltage rises, and the screen current increases! After a while, in fact, the impact of primary electrons is so great that each one of them knocks loose *several* secondary electrons from the plate. This is clearly a losing proposition — the plate is giving up more electrons than it is getting. So, as the solid curve shows, not only does the net plate current go down to zero, but it actually flows in the wrong direction. We indicate this topsy-turvy state of affairs by showing “negative” (wrong-direction) plate current.

As the voltage is increased beyond point B, the growing attraction of the plate begins to enable it to hold its own against the siren call of the screen. A higher percentage of the secondary electrons commence to fall back onto the plate instead of going to the screen grid, and the plate current starts to increase again. At point D the plate has become positive enough to put an end to the screen’s theft of its electrons, and it reclaims *all* of its emitted particles. From this point on, the plate current is little affected by the plate voltage. The screen and control grid voltages, determine the plate current, as we learned in Chapter 10.

If the plate voltage always stayed in the region beyond point D, secondary emission would cause no trouble; but when a tube is working in a circuit, the plate current is constantly changing. By the same token, so is the plate voltage, because of the varying drop across the plate load resistance. (See Chapter 10.) In fact, when the grid is driven strongly positive, the plate voltage may dip *below* the screen voltage.

When this happens, we have lost a good bit of our ability to control the plate current solely with the grid signal; for, as we have just seen, a change in the plate voltage in this lower-voltage region has a very decided effect on the plate current on its own hook. If we are to avoid the bad effects of this double control, we must either keep signal voltages very small so that the plate voltage will not swing down near the screen voltage, and thus sacrifice a large portion of the tube’s ability to amplify; or we must use a very high plate voltage to ensure the same thing even with increased amplification. What is really needed is some device

that will put a stop to this dominance secondary emission gives to plate voltage over plate current.

The suppressor grid

Just such a device is the *suppressor grid*, which looks much like the control and screen grids, although the spacing between turns is usually greater. It is found between the plate and the screen and is connected — often inside the tube — to the cathode. This is the fifth element added to our tube, so the family name of *pentode* (*pente* is Greek for five) is given to tubes with suppressor grids.

Since the suppressor grid is negative with respect to the plate, it sends secondary electrons right back to the plate instead of letting them pass through its turns to the screen. Control of the plate current is restored to the control grid, even under conditions where the instantaneous plate voltage dips below the screen voltage. In power output tubes, this means higher power output with lower grid-driving voltage; in tubes used to amplify radio frequencies, signal voltages can be amplified tremendously without employing high plate voltages. Fig. 1103 shows how adding a suppressor grid takes the dip out of the plate-voltage-vs.-plate current curve of the tetrode. Remember that the effect of the suppressor grid on secondary emission is the same as that of a

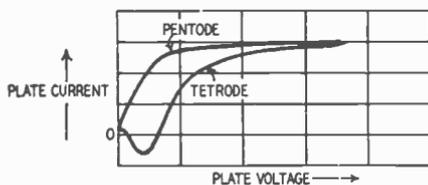


Fig. 1103. Adding suppressor alters curve.

good kissproof lipstick; the act isn't prevented from taking place, but it is kept from causing any trouble!

The beam tube

One special kind of tube contains no suppressor but arrives at the same result as the pentode. Fig. 1104 is a cutaway drawing of a *beam* type tube. The beam-forming plates are connected to the cathode. The negative beam plates repel electrons so that they are all concentrated in a stream directed at the curved parts of the plate. The plates also prevent any secondary electrons from sneak-

ing over to the screen by the side doors — outside the beam.

As the electron stream goes through the negatively-charged wires of the control grid, the repulsion of these wires molds the beam of electrons into a stack of flat sheets of electrons — sheets that pass between the wires of the screen, too, because the screen wires are carefully placed so as to be in the “shadow” produced by the negative grid wires.

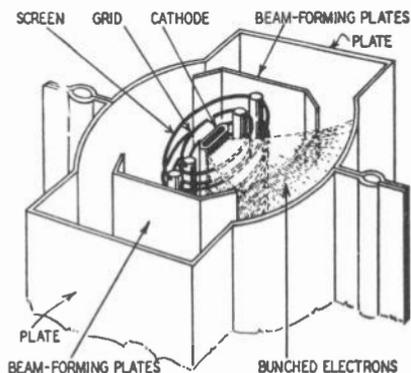


Fig. 1104. *Beam tube needs no suppressor.*

The sheets of electrons pass between the wires of the screen, which are aligned with the grid wires. Since the electrons do not hit the screen wires directly, the screen takes very few of them and almost all go to the plate where they can do the most good.

The steady voltage on the screen may often be higher than the instantaneous plate voltage, while it is varying rapidly to amplify a signal; therefore, the screen is more attractive to the electrons than is the plate. After the electrons have passed through the screen, this greater attraction slows them up — they are not as anxious to get to the plate as they thought they were! Because of the “braking” action, the slowed-up electrons bunch up between screen and plate, as the heavier dashed lines in Fig. 1104 show. The concentration of electrons results in a negative space charge, a “wall” between plate and grid, which prevents secondary electrons knocked out of the plate from getting to the screen. This electron “wall” works just as effectively as a suppressor would.

Tube types

We have by no means pumped the well dry on the subject of different types of electron tubes. There are literally hundreds of

varieties on the shelves of any well stocked radio store. Many of the differences, though, are produced by mechanical variations in the filament structure, the basing arrangement, or the housing of a single basic type. For example, beam tubes have been manufactured with filaments that operate at 1.4, 6.3, 12.6, 25, 35, 50, 70, and 117 volts. Beam tubes come in small, medium, and large envelopes; and the envelope may be made of either metal or glass. If we look at the bases, we find beam tubes with miniature bases, with octal and loktal bases.

Another flock of types is produced by a kind of electronic grafting, in which two or more basic types of tubes are housed in the same envelope and are built around a common cathode. This method produces some fearsome sounding names, such as "duo-diode-hi-mu-triode"; but that name really describes nothing more awful than a hybrid tube in which two diodes and a high-amplification triode are all clustered around the same cathode inside one envelope. And the 12-pin "compactrons" house the equivalents of three separate tubes, a rectifier, a pentode power amplifier and a triode and detector diode all inside a single envelope.

QUESTIONS

1. What is *secondary emission*?
2. How does it interfere with the ability of the grid to control plate current in a screen-grid tube?
3. Explain the conditions under which plate current can actually flow in the wrong direction — away from the plate.
4. What can we do about signal voltages or plate voltage to prevent this?
5. What is a *suppressor grid*?
6. What is the name of a tube that contains such a grid?
7. How does a suppressor grid correct the evils of secondary emission?
8. How does its use improve a power output tube?
9. How does it improve a voltage amplifying tube?
10. Tell how a beam tube achieves the same effect without the extra grid.
11. Describe mechanical variations that result in different tube types.
12. What is a *duo-diode-hi-mu-triode*? a *compactron*?

12

VACUUM-TUBE CHARACTERISTICS

.....

THE story of a vacuum tube can be told only very superficially in words. We can say how many pins it has, what kind of an envelope, the filament voltage, the number of elements, and the inter-electrode capacitances. But that doesn't give much of an idea of what to expect from the tube when we use it in a circuit. The real questions are:

1. How much amplification (or in some cases, how much power output) can you get under a certain set of conditions?
2. How much voltage (a.c. and d.c.) should be applied to each element?
3. What impedances should be connected to the elements?

These three points are important because they alone determine how the tube will perform electrically, whether it will do a specific job, and how the circuit elements must be chosen for best results in a particular case. They are not easily summed up in a single statement, for they are interdependent; change any one of them and the others change, too.

The best way to show interdependent and variable quantities is in a graph. That is how most tube data is given in manuals.

The usual tube book gives a set of curves like those in Fig. 1201 for each tube. Plate current is plotted here against plate voltage with a separate curve for each value of grid voltage. All voltages are d.c. The test circuit used in plotting the curves appears in

Fig. 1202. Filament and grid voltages are held constant while the plate voltage is varied. At each plate voltage value the plate current is read. Then the grid voltage is changed and the plate-voltage changes are gone through again and plotted.

To obtain the curves of Fig. 1201, for instance, the grid voltage was set at zero (grid grounded) with the potentiometer, the plate voltage set at various values and the plate current measured at each voltage. Dots were made at these points and the curve drawn. Then the grid voltage was raised to -2 and the same procedure followed with the new grid voltage. Several of these curves form a *plate family*. The same thing is done with tetrodes and pentodes, with fixed screen voltages. Often screen current is plotted on the same graph, using dashed lines to distinguish it from plate current.

The same information can be given in a slightly different way. Plate current plotted against grid volts, with a separate curve for each value of plate voltage, forms a *transfer characteristic* graph, which gives essentially the same information as a plate family.

Amplification factor

We learned in Chapter 10 that the *amplification factor*, or " μ ," of a tube is simply a number telling how many times more effective grid voltage is than a plate voltage change in producing a change in plate current. For example, look at the -4 -volt curve of Fig. 1201. At one convenient point the plate voltage is 105 and plate current 2 ma. Now look at the -6 -volt curve. At 105 volts the current is only about 0.2 ma. To get the 2-ma plate current again (keeping grid voltage -6) we have to go to approximately 145 plate volts. A 40-volt change in plate voltage is necessary to restore to its original value a current that was varied by a 2-volt grid change in the opposite direction. Hence the μ is $40/2$, or 20.

Plate resistance

The plate resistance of a tube is found by dividing a small change in plate voltage by the change in plate current it causes. For example, if we check a number of the curves on Fig. 1201, selecting parts where they are straightest, we find that changing the plate voltage by 10 or a little less, with grid voltage unchanged, produces a change of 1 ma in plate current. The plate resistance is then $10/.001$ (ampere) or 10,000 ohms. A bigger graph could be read more accurately.

Transconductance

Control-grid-plate transconductance or simply transconductance or mutual conductance (it's called more names than a baseball umpire) is abbreviated g_m and is probably the best value by which to judge how good a tube is as an amplifier. It is defined

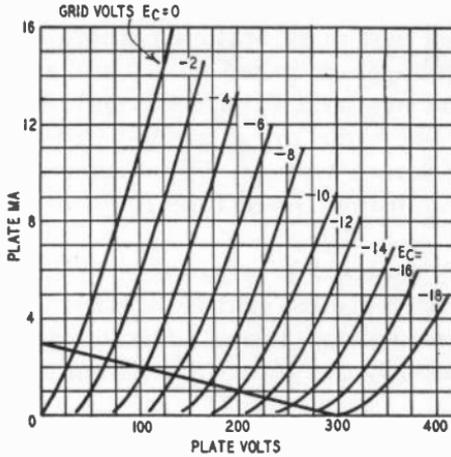


Fig. 1201. Family of plate curves shows performance of the tube graphically.

as “the small change in plate current divided by the small change in grid voltage required to produce it.” All other voltages are supposed to remain the same. Since our smallest divisions of grid voltage are a full 2 volts, we cannot readily make this measure-

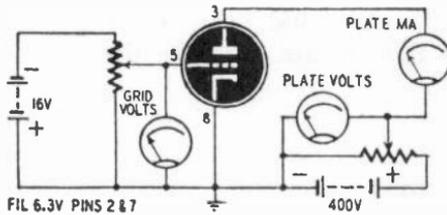


Fig. 1202. Test circuit for making chart.

ment on the chart, though it could be done easily on the actual test setup.

As an example, if a grid shift of 1 volt produces a change of 2.5 ma in the plate current, the transconductance is equal to

.0025/1, or .0025 "mhos." The *mho* (ohm spelled backward) is the basic unit of conductance — which is the reciprocal or opposite of resistance.

A handier, pocket-size unit is the *micromho* or millionth of a mho. The transconductance of a triode under typical operating conditions may run between 2,500 and 3,000 micromhos. See how close you can come to it using the graph.

Dynamic characteristics

The measurements and curves you have seen so far are *static* characteristics, made under standing-still conditions. You get about as much useful information from them as you would out of watching a new driver maneuvering a car in a large deserted lot. By watching him in the lot, you can tell whether he knows what the pedals are for and if he has the strength to turn the steering wheel (and in the right direction!). But none of that information and ability is useful until he gets out on the road and reacts to different — and *changing* — conditions that he will encounter there.

The same is true of the tube. Used in an amplifier circuit, it will encounter impedances not present in the tests; it will deal with a.c. voltages and currents; it will have to adapt itself to changing conditions. A little simple calculation, using ruler, pencil, and paper, will tell us what the tube will do under *dynamic* — moving — conditions, when it is in useful operation as an amplifier.

Suppose we are to use the triode in a simple voltage-amplifier circuit (Fig. 1203). We choose the value of R_1 to be 100,000 ohms. C_1 is merely a blocking capacitor preventing d.c. from passing into the following stage. A grid resistor in series with the bias battery permits us to place a negative (d.c.) voltage on the grid without any likelihood of shorting out incoming signals.

What will happen in our circuit with the values for R_1 and the bias and B-voltages we have chosen? What values are needed to obtain the amplification we want? If we know the answer to the first of this pair of questions, the second question answers itself.

If the bias does not cut off the tube, the plate current causes a d.c. voltage drop in R_1 ; therefore, the plate has *less* than 300 volts on it. The static curves in Fig. 1201 no longer tell the whole story, for, if we choose a certain grid voltage, the chart shows that the plate current depends on the plate voltage — but with R_1 in the circuit we don't know what the plate voltage is.

Load line

The solution is to draw a *load line* on the graph to show just what the plate voltage is for each value of grid voltage, with R1 in circuit.

It's a simple matter of reasoning. If the voltage at the plate is really 300 volts in the circuit of Fig. 1203, there is no drop across R1, which means that plate current must be zero. On the graph, we place a dot at the intersection of 300 plate volts and zero current.

If the plate voltage is zero, the tube must be effectively a dead short between cathode and plate, and *all* the B-voltage is across R1. This never happens in practice (unless the tube has shorted elements, in which case, watch things burn!), but it is useful as a piece of brainwork. If all the B-voltage is across the resistor, we can easily figure the current: $I = E/R = 300/100,000 = .003$ ampere or 3 ma. That means that if the plate voltage approaches zero, plate current approaches 3 ma; and we can dot the appropriate intersection on the graph. Joining the two dots with a line will show the true dynamic characteristic of the tube when it is placed in its circuit.

Note that the value of R1 and the B-voltage determined the placement of the *load line*. Other values would give other lines. The static plate family, on the other hand, is a set of curves that remain the same no matter how the tube is used. We can define dynamic characteristics, therefore, as the characteristics of the tube *in the actual circuit and under the actual conditions in which it is used*.

The load line tells us what the plate voltage, plate current, and grid voltage really are at any time while the tube is working. We need only one to find the other two. If we have a grid voltage of -10, for example, the plate current is 1 ma and the plate voltage is 200.

These values are dynamic — they apply just as much to a.c. as to d.c. Suppose we connect an audio generator to the input terminals. Assume for the moment that the bias battery is shorted. The audio signal has a peak amplitude of 10 volts. At its 10-volt negative peak, the tube's plate voltage is 200; when the audio is at zero, plate voltage is 35. The tube's plate voltage has changed during the half-cycle by 200 - 35 or 165 volts. Since the change is at an audio rate, it goes through C1 and appears at the output terminals as an enlarged replica (more or less perfect) of the input

signal. The enlargement is easy to figure: the input signal was 10 volts peak; the output was 165 volts peak. The magnification, *amplification*, or *voltage gain*, was 165/10 or 16.5 times. Note that the voltage gain, like other dynamic characteristics, depends on the circuit used.

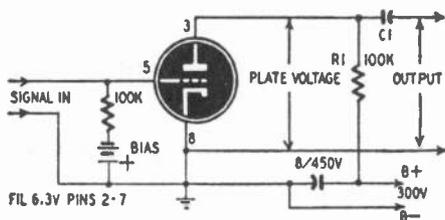


Fig. 1203. A typical triode voltage amplifier.

The dynamic characteristics are too important to be brushed over thus lightly here; we will discuss them more thoroughly later in relationship to amplifiers.

Meanwhile, note that the three main tube characteristics are related to each other, as would be expected. Multiply the transconductance (mhos) by the plate resistance to get the amplification factor, or:

$$g_m = \frac{\mu}{r_p}, \text{ to recast the equation.}$$

Thus, if we know two of these characteristics, we can always find the third one.

Each major tube manufacturer publishes a tube manual in which all of the above characteristics, as well as many other items of useful information, are given for the tubes he produces. Such a book is as important and necessary to the radio technician as a cookbook to a career-girl bride. You will realize why when future chapters refer to and *use* tube characteristics over and over again.

QUESTIONS

1. What three things do we need to know about a tube to use it intelligently?
2. Describe how a plate family of tube characteristics are obtained.
3. How can the amplification factor of a tube be determined from these curves?
4. How can we determine the *plate resistance* from the curves?
5. Define *mutual conductance*. Why is it important?
6. What is a *mho*? a *micromho*? How are they used?
7. What is the difference between "static" and "dynamic" characteristics?
8. Define *dynamic characteristics* as applied to a tube.
9. Describe how to draw a *load line*.
10. Show how the dynamic characteristics can be used to determine the voltage amplification of a tube in a particular circuit.
11. What is the relationship between the *transconductance*, *plate resistance* and *amplification factor* of a tube?
12. Where are tube-characteristic graphs found?

13

THE POWER SUPPLY



THE crystal set and its modern lineal descendant, the transistor receiver, are not dependent on the usual power supply required by AM, FM and TV sets and most electronic devices that utilize vacuum tubes.

By itself, though, a vacuum tube is a cold and lifeless thing, about as full of magic as an empty pop bottle. Not until a filament current has warmed the cathode and given its electrons a stimulating hotfoot do they start swarming from the cathode surface; and only when the proper voltages have been applied to the tube's electrodes can these darting electrons be pushed and pulled into precise behavior patterns that are able to delight our eyes with the sight of distant events and our ears with the sound of faraway music.

It follows, then, that all ordinary radio receivers must have some source of power that will heat the filaments of the tubes and also provide proper voltages for the electrodes. Batteries, the first answer to this need, are still used in portable receivers. A low-voltage, high-current A-battery is used to heat the filaments, connected either in series or in parallel. A higher-voltage, lower-current B-battery furnishes the electrode potentials. Quite often both of these batteries come in a single battery pack.

Battery power, while practical for sets used only intermittently, is expensive if called upon to supply a powerful, multitube console that is tuned in on a wake-up program the first thing in the morning, kept blasting with news and music all day long, and not

turned off until after the last newscast at night. Radio engineers looking around for a cheaper source of power focused on the house-current socket. If they could make the electricity that came out of that socket do the job that the electricity from their batteries had been doing, they would be sitting pretty. The only catch was that batteries furnished d.c. whereas a.c. came from the light sockets.

That did not daunt our heroes. First they set out to solve the problem of how to use a.c. to heat the filaments. They could not use this pulsing, reversing current to heat the slender filaments of their radio tubes because the filaments in those old-style tubes heated and cooled too quickly — so quickly, in fact, that the temperature, and consequently the emission, of these tubes rose and fell right in step with the reversing 60-cycle current. The result was a bad hum.

Two separate solutions were quickly found. First, increasing the bulk and current-carrying capacity of the filament allowed it to store sufficient heat so it could stay hot and continue to emit during the brief periods when the a.c. was falling to zero and reversing its direction. Second, heating the emitting cathode *indirectly* from a separate filament made the emission independent of rapid filament-current variations.

B-supply rectifiers

That took care of the A-supply, but getting rid of the B-battery was not so easy. The voltages applied to the plates and screens of the tubes had to be steady direct current. The manner in which the neat trick of converting a.c. into smooth-flowing d.c. is performed is really a two-part drama. Act One is called *Rectification*, and Act Two is titled *Filtering*.

Half-wave rectifier

Fig. 1301 shows one way of rectifying an alternating current. The transformer's primary is connected to the house current. The

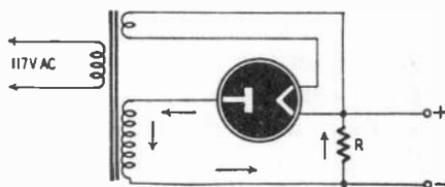


Fig. 1301. *The basic half-wave rectifier.*

smaller of the two secondary windings develops the correct voltage for heating the heavy filament of the diode tube. The larger secondary develops an a.c. voltage slightly higher than the d.c. voltage required.

From our study of a.c. we know that, during one half of every cycle of voltage, the top end of the high-voltage secondary will be positive, and during the next half negative, with respect to the bottom end, which is connected through R to the filament. When the top end of the high-voltage secondary is positive, the plate of the rectifier is positive with respect to the filament. Under these conditions, electrons from the filament are attracted to the plate and flow down through the transformer winding and up through resistor R back to the filament, as shown by the arrows. When the top end of the high-voltage secondary is negative, however, no current flows, the electrons being repelled by the negative charge on the plate.

The result of this check-valve action exerted by the rectifier tube is shown in Fig. 1302. Notice that the current flowing through resistor R of Fig. 1301 is in the form of pulses resembling half of a sine wave. Note, too, that these pulses are separated by the time interval required for the supply voltage to go through the negative half of its cycle. Since the system uses only half of the 60-cycle wave, it is a *half-wave rectifier*.

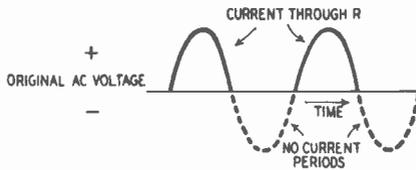


Fig. 1302. Half of the a.c. wave is used.

Efficiency-loving engineers, though, couldn't bear to see their rectifying system just sit there and twiddle its thumbs during half of every a.c. cycle; furthermore, smoothing out that pulse, wait-a-while, pulse, wait-a-while kind of d.c. took quite a bit of doing. Pressed by these annoyances, they worked out the *full-wave rectifier* shown in Fig. 1303.

Full-wave rectifier

Again we have a transformer with a secondary winding to heat the filament of our rectifier tube, but now our rectifier has *two*

plates marked A and B. What is more, the high-voltage secondary has its ends connected to these two plates, while a wire brought out from the center of the winding now goes to R. Now the a.c. voltage across the ends of the transformer winding is slightly more than twice the d.c. voltage required.

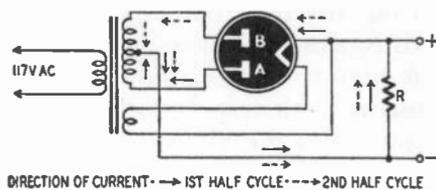


Fig. 1303. Duo-diode full-wave rectifier.

Let us say that the voltage appearing across the entire high-voltage winding is 600 volts. Then, when the top end is 600 volts positive with respect to the bottom end, it is only 300 volts positive with respect to the lead brought out from halfway down the winding. And when the bottom end is 600 volts positive with respect to the top end, that bottom end is 300 volts positive with respect to the centertap. That centertap is just like a man sitting in the middle of a see-saw: first one end of the board rises above him and then the other; there is always a downgrade to him from one of the two ends of the plank.

Recalling that the ends of the windings are connected to the plates of the tube and the centertap is connected through R to the filament, you can see that except for the tiny flicks of time when the a.c. voltage is passing through zero one plate or the other of the tube is always positive with respect to the filament. We know that under these conditions electrons move from the heated filament to whichever of the plates happens to be positive at the time, will flow down through one half of the winding to the centertap, and then will return through R to the filament. During the time a plate is negative, of course, it catches no electrons; thus each plate works only half of the time. But between the two of them, they keep current pulsing through R almost continuously. Fig. 1304 shows this clearly.

Smoothing filters

The output of the full-wave rectifier is a decided improvement over that of the half-wave job, but it still looks too much like the

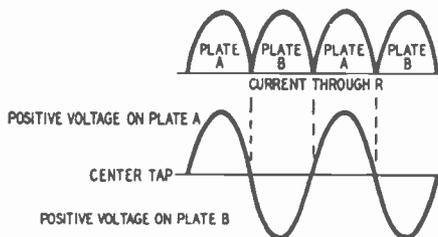


Fig. 1304. Tube plates conduct alternately.

bouncing gait of a frog for use on the plates of our tubes. We have to smooth out those peaks and valleys, and that is where our *filter* comes in.

Fig. 1305 shows a *choke-input filter* connected directly across the output of our rectifier. C is a capacitor of several microfarads and L is an iron-core filter choke of 10 to 30 henries. When the

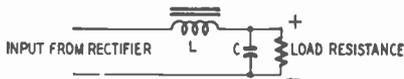


Fig. 1305. A choke-input smoothing filter.

rectifier tries to send its pulsing direct current through L, it runs head on into the choke's strong dislike for any *change* in the amount of current passing through it. We learned in our study of inductance that self-inductance bucks any increase in current through a choke, while the collapsing field of the inductance will provide extra current in an attempt to prevent any faltering or reduction in the steady value. These efforts on the part of the choke to keep the current on an even keel result in lowering the peaks and filling in the valleys of the pulsing current delivered to the input of the filter from the rectifier.

Capacitor C stores up current during the small voltage peaks delivered to it from the choke and then returns this stored charge to the load when a dip in voltage starts to occur. This action still further smooths out the voltage across the load resistance. If additional filtering is wanted, another choke and capacitor can be added.

Fig. 1306 is the diagram of a *capacitor-input filter*. The only difference is the addition of another capacitor C1, which charges to the peak voltage available from the rectifier. Between peaks this charge is partially lost by current flowing through the choke



Fig. 1306. This filter has capacitor input.

and the load resistance, but each peak restores the charge, as is shown by Fig. 1307.

The only time current flows from the rectifier is during the intervals when the rectifier output voltage is higher than the charge on C1. This means that current is taken from the rectifier during only a small portion of each cycle in the capacitor-input filter instead of flowing continuously as in the choke-input type. For a given amount of current drawn from the outputs of the filters, this means that the rectifier will have to deliver considerably heavier pulses of current to the filter of Fig. 1306 than it will to that of Fig. 1305, since the same amount of current has to be delivered in considerably less total time. That is why it is much easier to overload the rectifier tube with a capacitor-input filter than with a choke input.

Another difference between the two is in the d.c. voltage output. The output voltage of the choke-input filter is usually the *average* voltage of the rectifier output, while the output of the capacitor-input filter, especially with light loads, approximates the *peak* voltage of this output (minus the drop across the choke resistance). However, the output of the choke-input system falls off much more slowly under an increasing current load than will that of the capacitor-input filter. In general, though, the higher voltage available from a transformer with a capacitor-input filter makes this type by far the most popular with radio manufacturers and also with hobbyists.

Power supply troubles

Power-supply troubles put lots of money into the pockets of radio technicians, and most of these troubles are quite easy to locate. For example, a rectifier tube that does not light because the filament is broken can usually be spotted at a glance; yet a radio containing such a tube will be as dead as a burnt match.

The eyes, too, are useful in deciding if there are any shorted filter capacitors. When a veteran technician first turns on a radio set, he watches the rectifier plates closely. If these plates show no color, he feels safe in leaving the set turned on while he makes

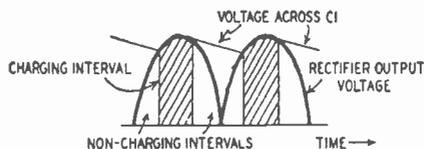


Fig. 1307. Rectifier delivers heavy pulses.

other tests; but if the plates start to turn red, he quickly snaps off the receiver before damage is done to the rectifier tube or the transformer. In the latter case, he can feel fairly sure that one of the filter capacitors has shorted and provided a low-resistance return path for the electrons, allowing millions of them to bombard the plates and make them red hot from the impact very quickly.

On the other hand, if one of the capacitors opens up, the ears can easily detect the hum that appears in the speaker because of loss of the filtering action of the defective unit. The trained ear can even tell *which* of the two capacitors has opened because of the subtle difference in the type of hum produced.

Even the nose has its place in analyzing power supply troubles, for it can quickly detect the odor that clings to a transformer that has been overheated. This foul, pungent odor, beside which that of a skunk is pleasant by comparison, is impossible to describe adequately, but once smelled is impossible to forget or mistake for anything else.

However, I am not trying to say that you should depend entirely on your senses to locate power supply troubles. The point is that they are not hard to find, and those that cannot be seen, heard, felt, tasted, or smelled can be readily ferreted out with a volt-ohmmeter.

We are not through with the subject of power supplies. What we have studied this far are the fundamental types. Now we are ready to go ahead and investigate the a.c.-d.c. power supply, the auto radio type, the transistor dc-to-dc converter, the voltage-doubling rectifier, and so on. These and other interesting and practical variations will be taken up in the next chapter.

QUESTIONS

1. What are the two power needs of a vacuum-tube radio?
2. Why cannot ac be used to light battery-type tube filaments?
3. What changes in the electron-emitting element makes such use possible?
4. Describe the operation of a half-wave and a full-wave rectifier.
5. Which is the more efficient?
6. Why is the output of a full-wave rectifier easier to filter than that of a half-wave rectifier?
7. Compare the choke-input filter with the capacitor-input filter.
8. Why can more current be drawn from the choke-input type?
9. Which has the better regulation?
10. Which type is the most common in household radios? Why?
11. Name some power supply troubles.
12. Explain how the senses can be used to locate many of these.

14

POWER SUPPLY TYPES

.....

THE last chapter discussed the common garden variety of power supply diagrammed in Fig. 1401. While this supply does an excellent job, there are at least three things wrong with it from the point of view of the radio manufacturer: it is heavy, it is bulky, and — most important of all — it costs too much.

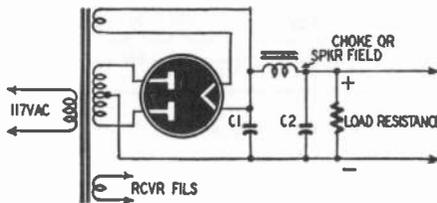


Fig. 1401. A basic full-wave power supply.

All three of these complaints point accusing fingers at the bulky, heavy, expensive transformer and iron-core choke. To get rid of these two items — especially the transformer — was a *must* for compact, lightweight, cheap receivers.

A.C.-D.C. supply

Disposing of the choke was easy. As we shall learn in the next chapter, speakers may have *field coils* that consist of thousands of turns of wire wound on an iron core. Direct current must pass through this coil to make the speaker perform as it should. If we

replace our filter choke with this field coil, such a current *will* pass through its turns; furthermore, the ready-to-hand inductance of the iron-core coil will perform exactly the same filtering job that the choke has been doing. Thus, by making the field coil do double duty, we can discard the filter choke.

Getting rid of the transformer, however, is like trying to put on *Uncle Tom's Cabin* without Simon Legree. It may be a villain, but it plays important parts in both the A- and the B-supplies. Radical changes must be made in both of these before the transformer can be torn out by the roots and discarded.

Fig. 1402 shows the first step in accomplishing this. The filaments of all the tubes and a *ballast resistor* are connected directly across the 117-volt a.c. line. As can be seen, the voltage needed across the string of tube filaments is the sum of the individual tube requirements. The difference between this voltage and the line voltage is accounted for by the voltage drop across the ballast resistor.

In Fig. 1402, for example, are two tubes with 25-volt filaments and three using 6 volts on the filaments. That means that 68 volts is needed across the filament string. The ballast resistor, then, must be designed so there will be a 49-volt drop across it when the tubes are drawing their rated filament current.

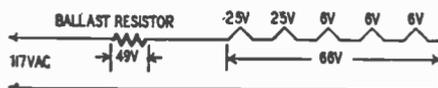


Fig. 1402. Early transformerless heater string.

These tubes, used in the early a.c.-d.c. sets, had filaments that drew 0.3 ampere. When this current is multiplied by the 49-volt drop across the resistor, the resistor dissipates 14.7 watts in doing its voltage-dropping chore.

This amount of heat being constantly released within the close confines of a small cabinet did the capacitors and other parts no noticeable good; so the ballast resistor was fabricated as a separate, asbestos-sheathed resistance wire right into the line cord. This took the heat out of the cabinet, all right; but unfortunately the resistance wire did not take too kindly to the twisting, bending, tying-into-knots that most line cords suffer.

Then the tube manufacturers came dashing to the rescue. They brought out sets of tubes whose total filament voltages were exactly equal to the line voltage; and, to keep the wattage of the

tubes the same, they reduced the current requirements to 0.15 ampere. This got rid of the ballast resistor as well as the filament-heating portion of the transformer; and these tubes, with their various octal, loktal, or miniature bases, are the ones used in most a.c.-d.c. sets.

There is only one flaw in the setup — it is hard on tubes. Any service technician knows that he will put three tubes into a transformerless receiver for every one he replaces in a set using a transformer. The fault is that the cold filament resistance is much less than the hot filament resistance. As a result, when the set is first turned on, a heavy surge of current passes through the filament wires. The strong magnetic fields that surround adjacent loops of the filament wire inside a cathode act upon each other, making the filament “wriggle” violently under the influence of this heavy current; and often the movement either fractures the filament or causes it to short out to the cathode sleeve.

The only reason the transformer is easier on tubes is that the regulation of the voltage delivered by the transformer secondary to the filaments is much poorer than is that of the line. When there is a demand for heavy current, the transformer secondary voltage sags and so cannot deliver it; but the 117-volt line can, and does put it out—much to the detriment of the tube filaments.

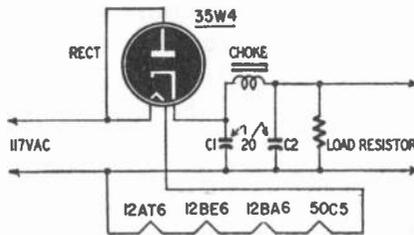


Fig. 1403. A typical a.c.-d.c. supply.

Radio engineering progresses in spirals, and some series-string-filament sets are again employing a special type ballast resistor with a cold resistance several times its hot resistance. With such a resistor in series with the tube filaments, the initial current is quite low and rises slowly to rated value as the filaments and the ballast warm up. Another protective arrangement employs a bi-metal thermal switch that shorts out a series resistor after the tubes are warm.

But now let us look at Fig. 1403, which is the essential power supply circuit of an a.c.-d.c. receiver, and see how the B-voltage is secured. All of the tube filaments are hooked in series directly across the line. The plate of the half-wave rectifier tube is connected to the top side of the line. The cathode of this tube is connected through the filter choke and the load resistance to the other side of the 117-volt a.c. main. Outside of the fact that our rectifier has a cathode, this rectifier circuit is very similar to the half-wave transformer circuit described in Chapter 13. In that circuit, however, the electrons that flowed to the plate from the cathode (during the portion of the cycle when the former was positive) returned to the cathode by flowing around through the transformer secondary and the load resistance. In this circuit, there is no such apparent low-resistance return path from the plate to the "B-Minus" lead.

There is a return path, nevertheless, even though you do not see it. This path is through the windings of the generator producing the 117-volt a.c. The fact that this generator may be several miles away from the point where the receiver is operating means nothing to an electron.

The filter circuit operates just as did those described in the previous chapter. The working voltage of the filter capacitors does not need to be so high, because the rectifier puts out only slightly more than 100 volts of filtered d.c. Capacitors of 150 working volts are normally used. Quite often the filter choke is replaced by a 1,000-2,000-ohm resistor. While such a resistor is cheaper, it is not as good at filtering as is the choke; thus it is necessary to increase the size of the capacitors to around 50 μf each.

If this a.c.-d.c. radio were plugged into a 117-volt d.c. main with the positive side of the line connected to the plate, current would flow through the rectifier continuously instead of in pulses as it does on a.c. The d.c. would heat the filaments just as well as a.c. and our set would operate quite satisfactorily. A transformer set could not operate on such current, for the d.c. would quickly burn out the transformer primary.

That is why manufacturers call these transformerless sets "a.c.-d.c." Of course, the possibility that the ordinary buyer will use the set on d.c. (except in a few large cities) is about equal to that of his winning the Irish sweepstakes, but it is much better sales psychology to talk about even the most useless "extra" your product may have than it is to mention what has been left out!

Three-way supply

The *three-way portable* design does still more. It will work on 117 volts of either a.c. or d.c., or on self-contained batteries. Fig. 1404 shows the basic power supply of such a receiver. When the 3-gang switch is thrown to the battery position, the 7.5-volt A-battery heats the four filaments hooked in series, and the 90-volt B-battery supplies the plate and screen voltages.

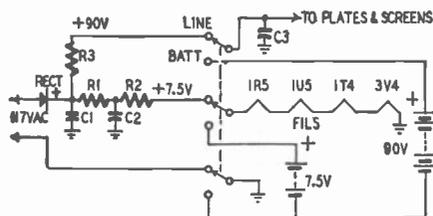


Fig. 1404. Supply for three-way portable.

When the switch is thrown the other way, the *semiconductor rectifier* permits the 117-volts a.c. across it to pass in only one direction. The crystalline structure of this compact little diode does the job of a vacuum-tube without drawing filament current. Note how few parts are used in the a.c.-d.c. supply (top Fig. 1405) com-

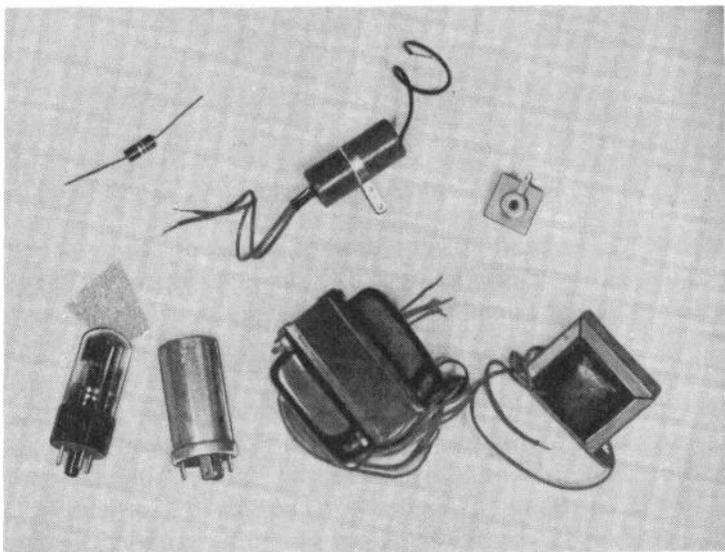


Fig. 1405. Parts for transformer-type B-supply are replaced by the a.c.-d.c. parts above.

pared with the transformer-type supply. The three-way portable power supply, like so many other radio circuits, is not too widely used. But don't be too surprised to find it put to work once again, as is, or modified, in some radio or television receiver.

Voltage-doubler supply

The transformerless power supplies so far discussed have outputs roughly equal to the line voltage, but it is possible to secure an output voltage twice the line voltage without using a step-up transformer. This is done by a gadget called a *voltage doubler*, one form of which is shown in Fig. 1406.

When the side of the line connected to the plate of the upper diode is positive, electrons attracted from the cathode leave C1 with a charge nearly equal to the line voltage. When this same side of the line swings negative, current flow ceases in the upper diode; but as the cathode of the lower diode becomes more and more negative, electrons flow from it to the plate, and charge C2 to the line voltage. C1 and C2 are connected so their charges are in series and add together; therefore, twice the line voltage appears across the load resistance.

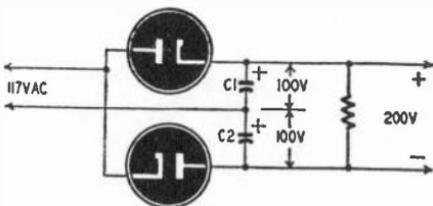


Fig. 1406. A full-wave voltage doubler.

The output voltage is very dependent upon the the capacitance and condition of C1 and C2. Too, the output voltage falls off rapidly when the load current is increased.

Auto-radio supplies

The typical American cannot long enjoy doing anything unless he can do it in his car; so he began to demand an automobile radio. The first ones used the car battery to heat the filaments of the tubes and B-batteries to supply the other electrode voltages. But radio engineers began scheming to add the burden of the B-supply to the already long-suffering car battery. What was needed was some way to step up the battery's 6 or 12 volts of

direct current in the same way a transformer steps up alternating voltage.

Then they remembered that pulsating d.c. in the primary of a transformer results in an expanding and contracting magnetic field that reacts upon the secondary winding in very nearly the same manner as does a.c. across the primary. They devised the circuit shown in Fig. 1407.

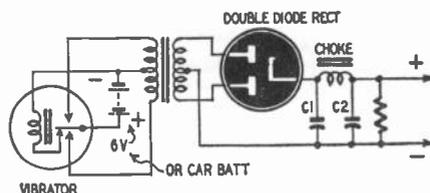


Fig. 1407. *Nonsynchronous vibrator power supply.*

The *vibrator* is simply a buzzer mechanism that keeps the reed vibrating back and forth so that it touches first one contact then the other. When the top is touched, current flows from the battery through the contact points then *down* through the top half of the transformer primary. When the lower one is touched, current flows through it then on *up* through the bottom half of the primary. The effect of these two regular, opposite-going pulses of current is practically equal to an a.c. voltage across the primary. Consequently, the voltage is stepped up, rectified, and filtered just as it would be if the transformer were operating on a.c. The steady d.c. from the battery has been changed to pulsating d.c., then converted and elevated to a much higher a.c. voltage, next rectified and so changed back to a pulsating d.c., and finally smoothed out by the filter so that it once more is pure d.c.!

Fig. 1408 shows how a *synchronous vibrator* can be used to do away with even the rectifier. Two sets of contacts are employed to ground one end of the primary and one end of the secondary simultaneously. The grounding is done in such a sequence that the d.c. pulse in the primary produces a voltage in the secondary that makes the ungrounded end of this winding positive by a certain value. This means that the centertap of the secondary is positive by half of this value with respect to ground.

Then when the reed swings the other way and grounds the other ends of the primary and secondary, the end of the secondary that had been grounded becomes positive; but this change still

leaves the centertap positive with respect to ground. The result is that every complete cycle of the reed causes two pulses of d.c. voltage to appear at the centertap with respect to ground. All that is required is to filter out this pulsating voltage and apply it

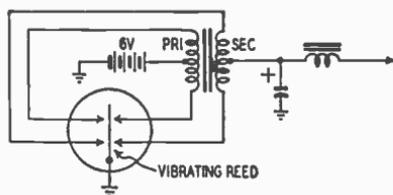


Fig. 1408. Synchronous vibrator power supply.

to our plates and screens. No rectifier is necessary with this circuit. Most vibrators operate at 115 cycles so filtering is simpler.

Nothing is irreplaceable in electronics. In some power supplies two heavy-duty transistors replace even the vibrator. These are connected in an oscillating multivibrator circuit so that each transistor draws current through its half of the primary for half a cycle while the other is cut off. The transistors simply do electronically what the vibrator does mechanically. Units have been designed to plug in, in place of a vibrator, at higher cost.

A bonus of the 12-volt system was the opportunity to get rid of the B-supply for the car radio. Tubes with different internal structure were developed that operate with a B-plus no higher than the 12 volts applied to their filaments. A receiver using these tubes needs only a filter to remove electrical system noises from the battery or generator voltage applied. The usual decoupling filters are still used with all auto radios, whether they are the 12-volt tube variety, the transistor type or a "hybrid" that employs both transistors and tubes.

While some of the described circuits are not popular at the moment in household radios, their principles are used in other applications. The power supply rectifier principle is the same as that of the detector. Voltage multiplier circuits are used in TV and industrial equipment. The crystal detector of years past is the semiconductor and diode detector of today—with greater efficiency and more convenience in a smaller package. Vibrators (called *choppers*) are used in sensitive industrial d.c. voltage measuring equipment.

So, you see, basic principles are never completely discarded.

QUESTIONS

1. From the manufacturer's point of view, what three things are wrong with a transformer type power supply?
2. In older radios what was substituted for the filter choke?
3. How were tube filaments heated from the line voltage in early sets?
4. How was heat released by the ballast resistor moved outside the receiver cabinet? What new troubles then developed?
5. What was done to get rid of the ballast resistor altogether?
6. Why are the 0.15-ampere ac-dc tubes subject to frequent filament failure?
7. Describe modern ballast-resistor arrangements.
8. Where is the return path for B-voltage supply electrons in a typical ac-dc receiver?
9. What are the three ways in which a "three-way portable" will work?
10. Draw the diagram and describe the action of a voltage-doubler circuit.
11. Describe how a vibrator power supply can raise the low dc car battery voltage to a high dc plate voltage.
12. Show how a synchronous vibrator or *transistors* can be used to improve on the basic vibrator power supply design.

15

SOUND AND SPEAKERS



"The music goes 'round and 'round
And it comes out here!"

NEVER do I hear the words of that song of years ago without grinning and thinking they might well be a beautifully brief description of the whole complicated business of radio.

Certainly the music *does* go 'round and 'round from the moment it enters the microphone of the broadcast studio and is transformed into a weak audio-frequency current.

By the time the signal reaches the receiving antenna, it is so enfeebled by its journey that once more it must be nursed back to health before it is ready for the operation of being separated from the carrier. Nurses R.F. Amplification, Conversion, and I.F. Amplification have charge of this building-up process; and Doctor Detection performs the operation. After that, the audio signal must still be passed through the audio amplifier of the receiver before it "comes out here."

The "here" that actually releases the captive sound from the magic spell of electricity is the *speaker*. It might be called a microphone in reverse, for, just as a microphone is a device for changing sound waves into electrical currents, a speaker is a device for changing electrical currents back into sound waves. The speaker is at the very end of the whole process of radio reception, in which it has the very last word. So it stands to reason that it is a most important piece of apparatus. Unless it does its job well, the good work of all the other units goes for nothing.

Brief review of sound

Since a speaker is a sound device, let's review briefly some of the properties of sound before examining speaker operation:

Sound is "the sensation produced by a stimulation of the auditory nerves by vibrational energy." Suppose we strike the tuning fork of Fig. 1501 and start it vibrating. As a prong of the fork moves back and forth, it alternately causes the molecules of air next to it to be pushed together and to be spread apart. These *compressions* and *rarefactions* travel through the molecules of air. To understand *how*, imagine that we have several croquet balls lined up in a shallow trough and separated by equal lengths of a large-diameter coil spring. If we strike a ball at one end of the trough, it will compress the spring between it and the next ball. That ball will pass this shove along to the next, while the first ball is being thrust backward by the first compressed spring. In this manner the motion originally given to the first ball will travel through the whole string, causing each ball first to move closer to its neighbor and then to spring away from it.

In exactly the same way, the thrusts that the tuning fork gives to the surrounding air is transmitted to the ear, and these tiny variations in pressure cause the eardrum to move back and forth in step with the tuning fork. In that instant, vibration becomes sound.

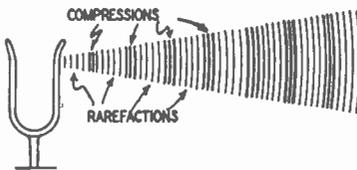


Fig. 1501. *Vibrating fork sets up waves.*

A compression and an accompanying rarefaction make up a *sound wave*. If we could see these waves moving from the fork to the ear, we would notice that, when the fork vibrates slowly, only a few waves pass in front of us in a given space of time; so we might say that the *frequency* or *pitch* of the sound is low. Moreover, we would notice that the distance between two adjacent compressions is quite great, or that the sound wave is *long*.

On the other hand, when the fork vibrates rapidly, the number of waves passing before us is greatly increased. We say that

the sound now has a higher frequency or pitch. At the same time, the wavelength would be noticeably shorter.

When the fork vibrates violently, it gives much stronger shoves to the air molecules than it does when moving through a small arc. The varying amount of energy thus imparted to and contained in the sound waves is referred to as the *intensity* or *amplitude* of the sound. The ear recognizes this difference in intensity as a variation in the *loudness*.

The current that is delivered to the speaker is an *electrical* reproduction of the *physical* sound that fathers it. This current is alternating in nature, but the frequency is not monotonously fixed as it is in the 60-cycle light mains. Instead, it is free to vary from instant to instant so that the electrical cycles per second are exactly equal to the number of sound waves per second striking the microphone. At the same time the power of the alternating current goes up and down in accordance with the intensity of the sound waves. A weak 1,000-cycle tone will produce a weak 1,000-cycle alternating current at the output of our receiver; but a loud 5,000-cycle sound will produce a powerful 5,000-cycle current at the same place.

The dynamic speaker

Now we are ready to see how a speaker changes this alternating current back into sound. Take a look at Fig. 1502, a drawing which illustrates the elements of a speaker mechanism.

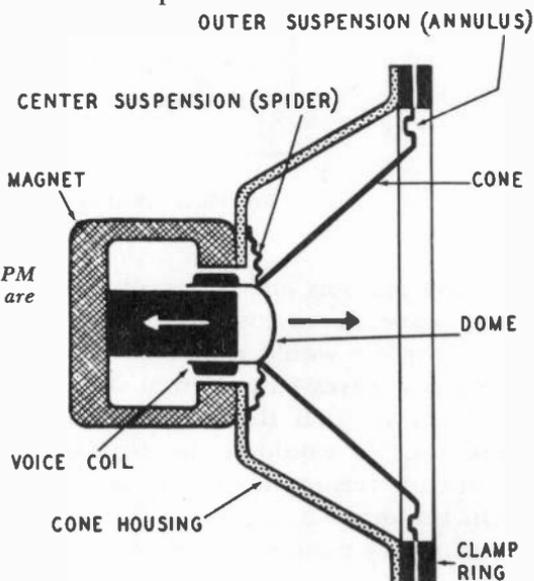


Fig. 1502. Cross-section of PM and electrodynamic speakers are quite similar.

The *field coil* consists of thousands of turns of wire wound in many layers in a doughnut form that fits snugly around the cylindrical soft-iron *pole piece*. This pole piece is firmly fastened to the rear of the heavy, soft-iron *frame* and projects through the exact center of a hole in the front of this frame, leaving a small space between the pole piece and sides of the hole. A tube of paper with a coil of wire wound in two or four layers around it is slipped over the pole piece and rests in this space. This is the *voice coil*. It must not touch either the pole piece or the frame; therefore, a flexible brace, called the *spider*, holds the voice coil centered in the narrow space, allowing it to move freely backward and forward on the pole piece. A paper *cone* is cemented to the voice coil, and the outer edge of this cone is also flexibly supported so that it may move back and forth with the voice coil.

Suppose we pass a direct current through the field coil. From our study of magnetism we know that this will magnetize the pole piece. The lines of force of its field will flow out the front end of the pole piece cross the gap between it and the frame and then return to the rear of the pole piece through the soft-iron frame. There will be a very concentrated steady magnetic field in the small air gap in which the voice coil rests. This coil is needed only to create a strong magnetic field in the space in which the voice coil works. (However, radio engineers make a virtue of a necessity and still may use the field coil for a filter choke.) We learned how to make powerful, compact, permanent magnets many times stronger. When a permanent magnet is used to replace a section of the pole piece, the speaker works just as it did with the field coil; but a great saving has been made in cost and weight, and we no longer need a source of field-coil current. Such speakers are called "permanent-magnet dynamic speakers" or, less formally, "PM speakers."

We pass another current through the turns of the voice coil. This current will produce a magnetic field of its own, and we shall have two different sets of magnetic lines of force. The interaction between these two magnetic fields will cause the voice coil to move back or forth on the pole piece. The direction of movement will depend upon the direction of current flow through the voice coil, and the amount of movement will depend upon the strength of the current.

Stopping right here, can't you guess what will happen when we connect the output of our radio receiver to the voice coil? Remember this output is an alternating current whose fre-

quency varies with the pitch of the sound producing it and whose power reflects the loudness of the original sound. Since the direction of movement of the voice coil depends upon the direction of current through it, an alternating current will cause it to move back and forth, exactly in step with the frequency of the varying current through the coil. Here we have a *vibrating* object that can produce sound! A stronger current will cause the coil to have a greater movement than a weak current; thus a *violent* swing of the tuning fork will produce a *loud* sound that will result in a *strong* current that will cause a *violent* movement of the voice coil and cone and produce a *loud* sound.

The whole thing sounds rather like a dog chasing his tail, but it establishes the point that the sound from the speaker is almost exactly the same as that in the broadcast studio — and that is our goal.

The human ear cannot hear vibrations of all frequencies. Any frequency between 15 and 20,000 cycles is called an audio frequency, but the range of hearing of most people is probably between 30 and 16,000 cycles per second. What is more, the response of the ear is similar to the spelling of Ohio: “round on the ends and high in the middle,” as is shown in Fig. 1503. Sounds of equal actual intensity seem much louder in the range between 500 and 3,000 cycles than when pitched either above or below this range.

Low-note difficulties

If the ear is to hear low-pitched tones at all, the speaker must move a considerable mass of air to produce the necessary changes in pressure with the comparatively slow-motion movement of the voice coil. That is why the cone is attached to the coil. It acts like a piston and allows the voice coil to set a large quantity of air into motion.

Even this advantage is largely lost at low frequencies without the use of a baffle. As the cone moves forward, it compresses the air in front of it and lessens the pressure behind it. At low frequencies, this cone movement is comparatively slow, and the pressure being built up in front simply slides over the edge of the cone and reduces the partial vacuum we are trying to create behind. It is like trying to use a 3-inch piston in a 4-inch cylinder: most of the pressure simply escapes past the sides of the piston, and the net result is very little change in pressure front or back.

The remedy is to lengthen the path the pressure or sound wave must travel in going from in front of the cone to the back so that by the time it gets there all ready to do its dirty work, the cone has started back and the arriving pressure wave actually contributes to the pressure the backward-moving cone is starting to build up behind the speaker. The name *baffle* is given to the means used to lengthen this path.

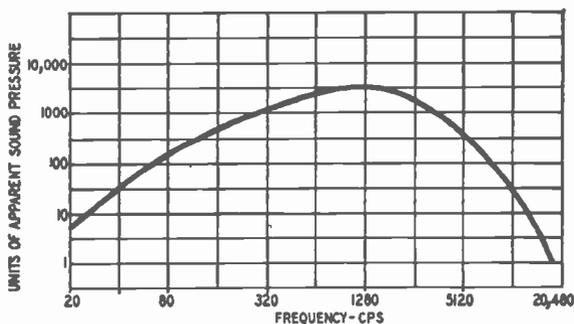


Fig. 1503. *Apparent sound pressure curve.*

While a large cone and voice coil help reproduce the low frequencies, the increased mass of these items seriously interferes with the reproduction of high frequencies. If you have trouble in understanding *why*, just reflect on how much easier it is to flutter a handkerchief than a bed quilt! By making the cone out of flexible material we can help the situation, for then the whole cone will move back and forth at the low frequencies while just the inner portion will follow the rapid vibrations necessary for high-frequency reproduction.

The best solution is the use of more speakers. A small “tweeter” is especially designed for the highs, and a large “woofer” is intended to reproduce the low frequencies. Both of these speakers can be contained in a single unit. A device known as a cross-over network separates the frequencies below the crossover frequency—usually somewhere between 400 and 2,000 cycles—from those above it and feeds each set of frequencies to the speaker which is best able to reproduce them.

Repair problems

Most of the troubles which appear to originate in the speaker of a receiver are actually in the output transformer usually at-

tached to the speaker. A burned-out primary is responsible in nine out of ten cases, and can easily be detected by checking with an ohmmeter. A red-hot screen in the output tube is another indication of an open plate lead and points unerringly to the burned-out transformer primary.

Real speaker troubles consist of shorted or open voice and field coils, of voice coils that are not properly centered and so rub on the pole piece or frame, of breaks in the flexible leads that connect the output transformer to the voice coil, and of cracked, worn, and warped speaker cones. Some speakers may have provisions for recentering the voice coil by shifting the spider. The best repairs for most faults mentioned is simply to replace the defective parts. Small faults in the cone can be repaired with speaker cement; but extensive use of this expedient will result in a cone that is not uniformly flexible and cannot perform as intended. In the case of small, inexpensive speakers that are defective, often a complete new speaker is the most practical solution; special or very expensive speakers warrant repairing.

All in all, speakers that have not been excessively abused give very little trouble and in no way deserve the suspicion that radio owners always direct at them when their sets go dead.

QUESTIONS

1. Basically, what kind of a device is a *speaker*?
2. Define *sound wave*, *frequency* or *pitch*, *intensity* or *amplitude*.
3. Describe the parts of a field-coil dynamic speaker.
4. What is the purpose of the *spider*?
5. What is a *PM speaker*?
6. What are *audio frequencies*?
7. Which of these frequencies sound the loudest to the human ear?
8. What must be added to a speaker to enable it to reproduce low frequencies? Explain.
9. What is a *tweeter*? a *woofer*?
10. What does a red-hot screen grid in an output tube usually indicate?
11. What can be done about a voice coil that is rubbing on the pole piece?
12. What can be done about small cracks in the speaker cone?

16

THE POWER OUTPUT STAGE

• • • • •

THAT hallowed phrase from the world of baseball . . . Tinker to Evers to Chance . . . is a classic description of split-second, three-way cooperation. In a radio receiver, though, we have another example of one-two-three team play that might well be paraphrased: "output stage to transformer to speaker." Let us examine this trio, starting with that familiar member, the speaker.

Voice-coil impedance

In the last chapter we learned that to make a speaker "work," we must have a varying current flowing through the voice coil. This voice coil cannot contain many turns of wire for two good reasons: first, there simply is not room for a large coil in the restricted space in which the voice coil moves, and this space cannot be increased without weakening the strong magnetic field needed in the air gap.

Second, more turns of wire would increase the inductance, and inductance is something we do *not* need in a voice coil. The reason is that inductive reactance — unlike pure resistance — plays favorites with frequencies, and it has low-down tastes. It will allow a low frequency to pass with comparatively little hindrance, but its opposition grows stronger and stronger as the frequency becomes higher and higher. Such partiality would mean that a speaker with a highly inductive voice coil would unduly accent some audio frequencies and play down others. The sounds com-

ing from such a speaker would not be a true reproduction of the sound originally heard in the broadcasting studio.

Voice-coil inductances are like whiskers: we cannot get rid of them entirely, but we can keep them whittled down. The way to keep inductance small is simply to keep the number of turns low. Unfortunately this solution, like the solution of nearly every other problem in this wacky radio business, gives birth to a new problem. The strength of the magnetic field produced by currents in the voice coil depends on two things — the number of turns in the coil and the strength of the current. If we are going to have few turns, we are going to have to have lots of current. Heavy current means large wire. Large wire means low resistance — and that is what our voice coil has. You will soon see why this low resistance complicates coupling a speaker to the radio receiver.

Usually the d.c. resistance of a dynamic speaker voice coil lies somewhere between 1 and 20 ohms. The impedance of the coil — resistance plus inductive reactance — is roughly 25% higher than the pure resistance. For example, a voice coil that has 4 ohms of resistance will present approximately a 5-ohm impedance to a frequency of 400 cycles per second, this being the frequency at which many voice coil impedances are measured. This is good, for the impedance of our coil consists chiefly of resistance and will present a fairly uniform impedance to all audio frequencies. High-fidelity speakers may be measured at 1 kc.

The output stage

Now let us go to the other end of this triple-play combination and consider the *output stage* of the receiver. By “stage” we mean a tube or combination of tubes, together with proper input and output circuits, that performs a single operation on the signal passing through the receiver. The output stage is the one that handles the signal just before it is delivered to the speaker. The essential parts of an output stage, are shown in Fig. 1601. For the purpose of our study, we shall assume that our output stage consists of a single triode tube connected as shown in Fig. 1602.

An alternating, audio-frequency voltage is delivered through capacitor C from the preceding stage to the grid of our output tube and appears across resistor R. This means that the alternating voltage is really in series with the fixed negative voltage that the bias battery delivers to the grid. Voltages in series can be added like positive and negative numbers in algebra. That means that when the audio voltage is on the negative half of the cycle,

its value is added to the bias voltage and makes the grid more negative. During the positive half of the cycle, its value is subtracted from the negative bias voltage and the grid becomes less negative.

Fig. 1603 shows what happens to the plate current while the grid voltage is waltzing around in this dizzy fashion. As might be predicted from our study of triode action, the plate current rises and falls right in step as the voltage on the grid becomes less and more negative. As is evident from Fig. 1603, the pattern of the plate current is a reproduction of the audio voltage applied to the grid.

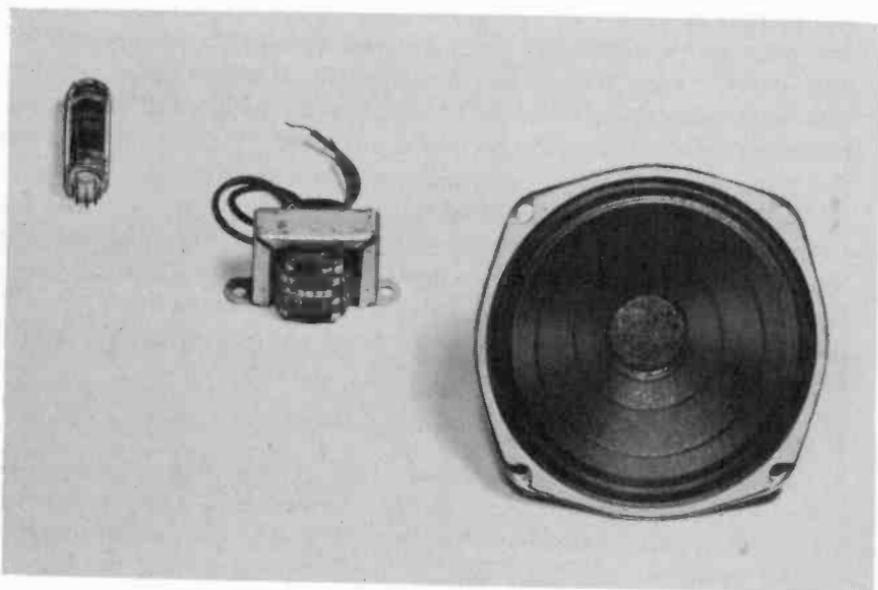


Fig. 1601. *Three essentials of the output stage are tube, transformer and loudspeaker.* (Allied Radio Corp.)

“Eureka!” you are probably shouting in your best Greek accent. “Here we have exactly what we need to make our speaker do its stuff: a varying current that follows curves better than a bikini bathing suit! All we have to do now is to place our voice coil in the plate lead of the output tube and sit back and listen to the program rolling in loud and clear.”

Not so fast, my friend! You are forgetting something — or several somethings. Remember we said few turns on the voice coil meant heavier currents — or rather excursions of current, for it is

variation in current that makes our voice coil move back and forth. Well, the plate current swings of our triode are not likely to exceed 100 milliamperes, and that is far too small a current to get much action out of our speaker.

And there is another point. You will recall that when we talked about characteristics of vacuum tubes we found that every tube has a *plate resistance*. If we consider our output tube a generator of power — and it really is — this plate resistance represents the internal resistance of our generator. It is an easily demonstrated fact that a maximum transfer of energy takes place between a generator of power and the thing receiving the power when the impedance of the “giver” exactly matches that of the “givee.” (I’m haunted by the feeling that there is some sort of analogy in there to a playboy trying to give a mink coat to a chorus girl, but I can’t quite pin it down.)

To demonstrate this “easily demonstrated fact,” suppose we consider Fig. 1604. Here we have a 100-volt generator with an internal resistance R_i of 10 ohms and a variable external resistance R_e that is used as the load. Table 16-1 shows what happens to the current, the voltage drop across R_e , and the power dissipated by R_e as its resistance is set at various values. You don’t need 20-20 vision to see that the *maximum power* is delivered to the load when its resistance is 10 ohms, the same as the internal resistance of the generator. Either increasing or decreasing this load resistance results in a loss of power. You might also note, for future reference, that the *maximum voltage* across the load resistance does *not* appear at this point but goes up as the load resistance increases.

Table 16-1 — Conditions for Maximum Transfer of Power

I	II	III	IV
R_e (Ohms)	Current (Amperes)	Voltage across R_e	Power in Watts $II \times III$
1	9.09	9.09	82.6
5	6.66	33.3	222.0
10	5	50.0	250.0
40	2	80.0	160.0
100	0.909	90.9	82.6

This is easy to see if you will consider that when R_e is made small, the output voltage gets smaller, until R_e gets to zero and there is no output voltage. With no output voltage there can’t

be any power because the power is equal to voltage \times current.

Going the other way, if R_p is made larger, the current keeps getting smaller until there isn't enough current to have any output power.

If our triode power tube has 250 volts on the plate, a plate resistance of 800 ohms; it will deliver the most power to a load in its plate circuit if the impedance of this load is also 800 ohms. But, when a tube is thus putting out its maximum amount of power, the plate current variations do not exactly follow the grid voltage current changes, and we have some *distortion of the signal*. (More about this distortion subject in the next chapter.)

This distortion can be reduced by increasing the load resistance to something more than twice the plate resistance. This means a reduction from the maximum power output of our tube, but the loss is so small the ear cannot detect it. For obtaining maximum "undistorted power output" from our load resistance should be 2,500 ohms.

And now we see why the low resistance of our voice coil presents a problem. There is a lot of difference between the 2,500 ohms needed in series with our output tube's plate lead and the 5 ohms or so of impedance in our voice coil. If we placed the voice coil in the plate lead, practically no power would be delivered to the speaker. What we need is some dingus that will allow us to "match" the high plate resistance of the output tube to the low voice-coil impedance of the speaker in the same way that a plumber uses a reducing coupling when he wants to connect a large pipe and a small one together.

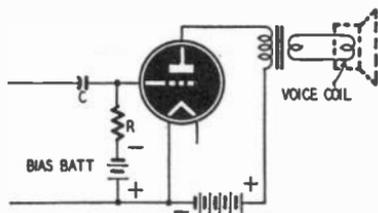


Fig. 1602. A single triode output stage.

Output transformer

In discussing the transformer we said it provided a method of changing high voltage at low current into low voltage at high current. Suppose we place a transformer between the output tube

and the speaker as is shown in Fig. 1602. Let the primary winding placed in series with the plate lead consist of many turns of fine wire, while the secondary connecting across the voice coil is made up of a few turns of heavy wire.

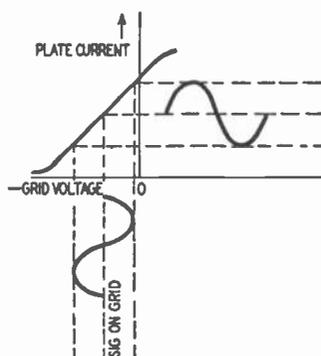


Fig. 1603. *Output varies with grid signal.*

A review of the transformer action story will help us understand exactly what takes place when an audio signal appears on the grid of the output tube. First, this causes the plate current to rise and fall. The surging of this varying current through the primary of the transformer sets up an expanding and contracting magnetic field that, in turn, produces an alternating current in the secondary winding. The flow of this current through the voice coil makes the cone move back and forth and produce sound from the speaker.

Because of the high inductance of the primary, a considerable voltage appears across this winding. Since our transformer is of the "step down" type, much less voltage appears across the secondary, but the current in the secondary is accordingly much heavier than the primary.

As explained before, when a low resistance is placed across the secondary of a transformer, the heavy current that this causes to flow in that winding produces a magnetic field that weakens the back-electromotive-force or impedance of the primary. If we increase the value of this load resistance and so reduce the current in the secondary, more "bucking voltage" is available to the primary and its impedance to the flow of a variable current rises. It follows then that we make the primary impedance anything we wish simply by varying the load across the secondary. The

whole thing works like a pair of long-bladed scissors in which a ¼-inch opening of the handles results in a couple of inches of separation of the points.

Just as the amount of control that the handles have over the blades of the shears depends upon the ratio of the lengths of these two elements, so does the effect of secondary load upon the primary impedance of our output transformer depend upon the ratio between the number of turns of wire on each of these two windings. This relationship has been neatly expressed in one of those formulas so dear to the heart of the engineer:

$$N = \sqrt{\frac{Z_s}{Z_p}}$$

In this formula N is the turns ratio, secondary to primary; Z_s is the impedance of the load connected to the secondary; and Z_p is the impedance presented by the primary. Let's see if we can use this simple-looking critter to figure out the turns ratio needed:

Z_s is 5 ohms; Z_p is 2,500 ohms; so N must equal

$$\sqrt{\frac{5}{2,500}} \text{ or } \sqrt{\frac{1}{500}} = \frac{1}{22}$$

That means that our turns ratio will be just about 1/22. If our primary contains 220 turns, our secondary should have 10 turns.

The universal output transformer

In practical radio servicing it would be most inconvenient to have to obtain an exact duplicate unit for each output transformer replacement job, and it isn't necessary. "Universal" output transformers, of the type diagrammed in Fig. 1605 are provided for this purpose. A tapped secondary allows you to have any turns ratio needed. Either the primary or the secondary *could* be tapped to secure the proper turns ratios needed for matching various output tubes to a wide variety of voice coils, but it is easier to tap the secondary.

You do not have to use your adding machine, slide rule, or abacus to figure out just which taps to use for matching a certain tube to a certain voice coil. A chart furnished with the transformer tells exactly what taps are needed to do any job you may encounter. For example, one such chart shows that if a particular tube is connected across the primary, a 1-ohm voice coil should

be connected across taps 5-6 of the secondary; a 6-ohm coil across taps 1-5; a 12-ohm coil across taps 1-6, etc.

If the proper match is not made, the quality of reproduction will suffer, although the average ear may not notice the distortion until the mismatch is quite serious. In general, the distortion will be worse if the tube is forced to work into a load that is below its plate resistance than if it works into a load that is higher than the recommended value. Usually the low frequencies are accented if the output tube is made to work into a too-high impedance, while the high frequencies are pushed up when the output impedance is too low.

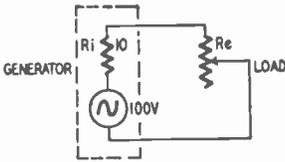


Fig. 1604. Output varies as the load is changed.

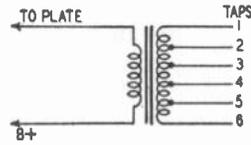


Fig. 1605. Taps allow variety of matching.

Many output stages consist of two tubes working in a *push-pull* circuit, but this will be taken up in the next chapter in which we really delve into the *Care, Feeding, and Love-Life of the Audio Amplifier*.

QUESTIONS

1. Why is inductive reactance a villain in voice-coil impedance?
2. What are usual values of dynamic-speaker voice-coil impedance?
3. Roughly, how much greater is the voice-coil impedance than its dc resistance?
4. What is meant by a *stage* in a radio receiver?
5. Why can't the voice coil of the speaker simply be connected in the plate circuit of the output tube?
6. Under what impedance conditions does a maximum transfer of power take place between a generator and a load?
7. Why, then, is an output tube made to work into a load higher than its plate resistance?
8. What device matches the high impedance of the tube plate circuit to the low impedance of the voice coil?
9. What formula gives the relationship between the impedances of the primary and secondary of a transformer and their turns ratio?
10. Describe a *universal* output transformer.
11. What is the effect on reproduction if a tube is forced to work into too low an impedance?
12. What is the effect if the impedance is too high?

17

THE VOLTAGE AMPLIFIER

.....

IN our crablike method of progressing backward through a radio receiver, we always assume that each stage will receive just the right kind of a signal from the stage before it. When we discussed power amplifiers we found that we needed an audio-frequency signal on the grid of that amplifier to make it work.

This audio voltage must be pretty husky if the output tube is to be worked at full power. A little reflection shows why this is so: a power output tube must have a relatively heavy plate current to develop much power (power is always the product of *voltage and current*) in its plate circuit. This means that the plate resistance of the tube must be low. The way to lower the plate resistance of a triode is to move the plate closer to the cathode, thus reducing the amplification factor of the triode. A low amplification factor makes it necessary to have large swings of grid voltage to produce large swings of plate current.

In a triode power amplifier, the peak-to-peak voltage required on the grid for full power output may be as high as 70 to 80. Screen grid and beam tubes can deliver high power outputs with much lower grid voltage swings, but even they require high audio voltages (from 2 to 20 volts approximately) on their grids.

But the audio voltage that results when the audio portion is peeled off the carrier by the detector is often only a small fraction of a volt. Before this puny voltage can swing the grid of our power amplifier back and forth as it should be swung, it must be

given a shot of spinach juice or something that will make it many times more powerful.

The "builder-upper" that does this trick is called an *audio-frequency amplifier* or simply an *audio amplifier*. Its job is to take the little audio voltage delivered to it by the detector and consisting of frequencies from 50 to 15,000 cycles per second and amplify this voltage many times, being careful to play no favorites and to boost all of the frequencies exactly in proportion to the amplitude they had before the boosting operation started. If all of the frequencies are not uniformly boosted, we have what is called *distortion*. The voice or music that comes out of the amplifier no longer sounds like what went into it. The result is about the same aurally as the visual experience of peering into one of those magnifying shaving mirrors: there is plenty of enlargement, but the perceived result does not bear much resemblance to the original! If necessary, two or more stages of audio amplification can be used between the detector and the power amplifier; but this is usually not necessary, at least in small receivers; a single pentode can amplify a signal 150 times or more.

Audio voltage amplifier

Fig. 1701 shows the basic circuit of an audio amplifier stage. A triode is used for simplicity. This should look familiar to you for

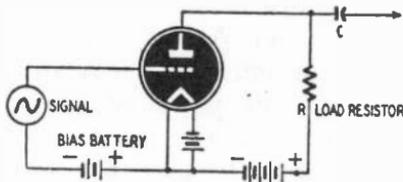


Fig. 1701. Basic audio voltage amplifier circuit.

it is nearly the same circuit as that of the power amplifier studied in the last chapter. The only difference is that we have a resistor in the plate lead instead of an output transformer primary.

A power amplifier and a voltage amplifier are really first cousins. The big difference lies in what we want them to deliver. In Chapter 16 we wanted *power* (volts \times amperes) to drive our speakers; so we selected a tube with a husky plate current and adjusted our plate load impedance for very nearly maximum power output. You will recall that this load was raised from the one that would give the most power output (equal to the plate

resistance) to more than twice this figure in order to reduce distortion.

No power is used in the grid circuit of the power amplifier because no current flows in this circuit. Only voltage is needed; therefore, all our audio amplifier stage need do is amplify voltage. With that in mind, we select a tube with a high amplification factor, such as a pentode or a high-mu triode, and we use a plate-loading resistor with a value several times the plate resistance of the tube. Fig. 1702 shows how the actual amplification of the tube approaches its amplification factor as the plate resistance is increased.

Remember the discussion of the dynamic characteristics of vacuum tubes? These dynamic characteristics revealed exactly how the plate current varied in accordance with the grid voltage when various values of plate resistance were used. Fig. 1703 shows a whole family of dynamic-characteristic curves for a triode. Each curve represents a different value of plate load resistance.

Fig. 1704 is a close-up study of what happens when we select one of these curves, the one with the 50,000-ohm plate resistor, and apply an audio voltage that swings 2 volts either side of zero center to the grid. This audio voltage is applied in series with -5 volts of bias on the grid.

Notice that if you read along the left side of the graph, the vertical divisions represent plate current in milliamperes; while if you read along the right side, they stand for the actual voltage on the plate after the voltage drop across R has been subtracted from the 300-volt plate supply.

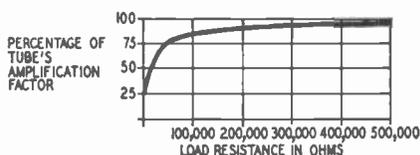


Fig. 1702. *Voltage amplification versus load resistance.*

Before the audio signal is applied to the grid, our -5 volts of bias causes the tube to draw 2 milliamperes of plate current. The drop through R ($.002 \times 50,000$) is 100 volts, leaving 200 volts on the plate. When the audio grid swings to its maximum negative value of 2 volts, the total grid voltage is $-5 + -2$, or -7 volts. At this point our plate current falls to about $1\frac{1}{3}$ milliamperes,

the drop across R ($.0013 \times 50,000$) is only about 65 volts, and the voltage on the plate rises to 235 volts.

On the other hand, when the audio voltage swings to its most positive value, the total grid voltage becomes $-5 + +2$, or -3 volts; and the plate current rises to the vicinity of $2\text{-}2/3$ milliamperes. This makes the voltage drop across R ($.00266 \times 50,000$) approximately 135, and the plate voltage falls to 165.

Phase inversion

Keep in mind that for *every* value of grid voltage lying between these extremes there is a corresponding different plate current value and consequently a different plate voltage value. Any movement of the grid voltage in a positive direction immediately produces a proportionate *increase* in the voltage drop across R and an accompanying *decrease* in actual voltage on the plate of the tube. By the same token an increase of the grid voltage in the negative direction produces an increase in the positive plate voltage on the plate for the reasons just mentioned. Since a negative-going grid voltage results in a positive-going plate voltage, we say the grid and plate voltages are 180 degrees out of phase.

If we concern ourselves only with the voltage actually appearing across R — and we can separate this varying voltage from the d.c. voltage by leading it off with a capacitor C — we find that

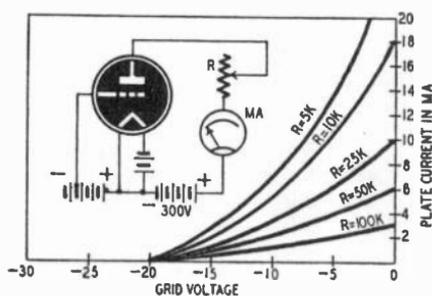


Fig. 1703. Triode dynamic characteristics.

we have a king-size replica of the voltage on the grid of our audio amplifier. In the example we have been studying we know that our actual plate voltage varied from 165 to 235, or a total range of 70. Since this was produced by a peak-to-peak grid voltage of 4, we can see that our amplifier has amplified the grid voltage about $17\frac{1}{2}$ times.

Yes, a technician has to be as familiar with curves as a beauty contest judge. Not only must he know which curve to select but he must also know what portion of that curve to use. Fig. 1705 shows what happens if the fixed bias is set so that the curved portion of the "curve" is used. No longer is the plate current pattern a faithful reproduction of the audio

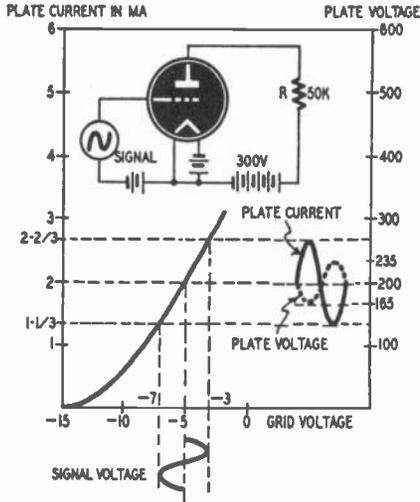


Fig. 1704. The grid signal varies both plate current and voltage.

voltage presented to the grid. It is non-symmetrical or lopsided. Under such conditions the audio signals being amplified by the tube are certain to be distorted and will not sound true to the ear.

In the same way too large a signal on the grid of the tube will

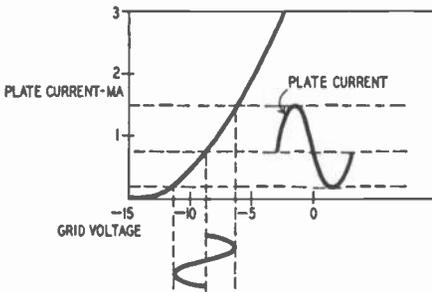


Fig. 1705. Incorrect biasing causes distorted output.

result in distortion as shown by Fig. 1706. If the audio signal is too great, the extremes of its swing cannot be kept on the straight portion of the curve, even though the bias is correctly set for the middle of this straight part. In this case the tips of the sine wave are flattened by this "overloading" of the audio amplifier.

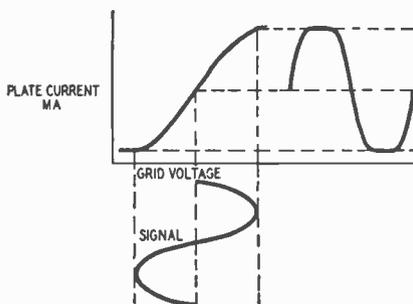


Fig. 1706. Too large a signal on the grid distorts the output signal.

Push-pull amplifier

By using two tubes in a push-pull circuit such as the one shown in Fig. 1707, we can have an exciting voltage for our amplifier that is twice that of a single tube. In this circuit the audio voltage is delivered to the grids by means of the input transformer. When one end of the secondary of T1 is positive, the opposite end is negative; so only half of this total audio grid voltage can appear between the negative terminal of the bias battery and either grid. In the same way, while the plate current of one tube is rising that of the other tube is falling. Because of the way they pass through the two halves of the primary of T2, these opposite-going

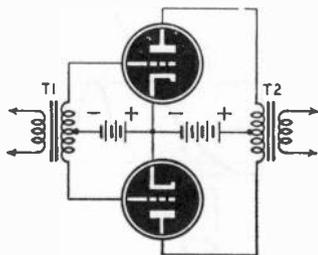


Fig. 1707. Basic push-pull amplifier circuit.

currents produce voltages in the transformer that are in the *same* direction and so add together. This means that a push-pull stage has twice the power output of a single stage. As a matter of fact,

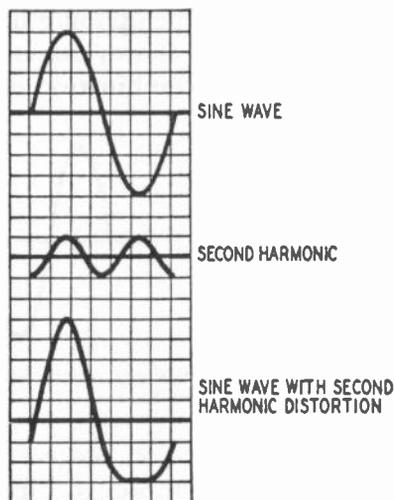


Fig. 1708. *Second-harmonic distortion.*

it has more than twice the power output because a push-pull amplifier has less distortion and so can be made to put out increased power with less distortion.

Harmonic distortion

To understand *why* a push-pull stage has less distortion, you must realize that an audio signal is like a pretty girl; it is seldom seen alone. Accompanying it are other lesser audio voltages called *harmonics*. A harmonic is an audio voltage that is some multiple of the fundamental audio frequency. For example, if our fundamental frequency is 400 cycles, the second harmonic is 800 cycles; the third, 1,200; the fourth, 1,600, etc. Unfortunately the voltages of these harmonics combine with the voltage of the fundamental and produce changes in the waveshape of that fundamental that spell distortion. Fig. 1708 shows how the presence of a second-harmonic voltage wave can foul up a nicely shaped fundamental wave.

In a push-pull amplifier, the even-numbered harmonics are made to cancel their distorting effects on a signal passing through a single tube by combining the output of both tubes in the trans-

former in the plate circuit. Fig. 1709 shows exactly how this takes place. At A, the solid line shows the harmonic-distorted wave produced by tube No. 1 of the push-pull stage. The dotted line portrays the similarly distorted output of tube No. 2, but notice that here the higher peaks appear on the opposite side of the line than they did for tube No. 1. At B is shown the amplified distortion-free wave that results from the combination of these two waves.

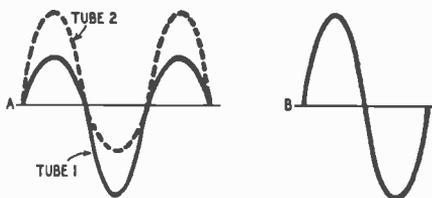


Fig. 1709. *Push-pull amplifier cancels even harmonics.*

Incidentally, this same cancellation process also takes out any power supply hum that may be impressed directly on the plates of the push-pull output tubes; it does not, however, remove any hum that may be introduced into the amplifier from preceding stages. Neither does a push-pull amplifier reduce the distortion produced by odd-numbered harmonics, such as the third, fifth, seventh, etc.; but since the amplitude of the harmonic usually diminishes as its frequency departs farther from that of the fundamental, getting rid of the second harmonic is very much worth while.

Let us summarize what we have said about audio voltage amplifiers in this chapter. The job of this part of the radio receiver is to build up the small signal that is put out by the detector so it will be big enough to drive the power output stage. The audio amplifier looks like the power amplifier except that it has a resistor in its plate lead instead of a transformer primary.

It must boost all the frequencies in the same proportion, otherwise we get amplitude distortion. Sometimes a receiver needs two or more stages of audio frequency amplification. An audio amplifier is shown in Fig. 1710.

Related to the voltage amplifier is the push-pull amplifier, which is a power amplifier using two tubes to put out twice as much power as one tube will. Push-pull improves the output stage by canceling even harmonics which are introduced by the tubes.

Push-pull stages are found more often in the power output portion of a receiver than they are in the voltage amplifier section. As you will discover, push-pull action can be had without using an input transformer, but that is a refinement that will be taken up

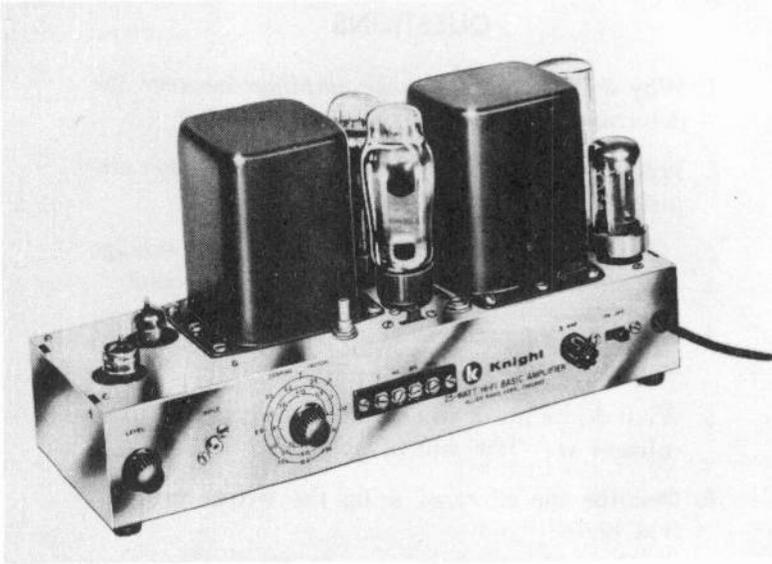


Fig. 1710. A 25-watt hi-fi amplifier that has the power supply on same chassis.

later. Right now, Watson, slip your service revolver into the pocket of your great-coat and bring me my fore-and-aft cap and my magnifying glass, for we are about to start studying *detection!*

QUESTIONS

1. Why do we need a *voltage amplifier* between the detector stage and the power output tube?
2. Precisely what is the job of this audio voltage amplifier?
3. What is the chief difference between the voltage amplifier circuit and the output stage circuit?
4. How can we predict the operation of a voltage amplifier stage?
5. What do we mean when we say the grid and plate voltages are "180° out of phase"?
6. Describe the effect of using the wrong value of grid bias?
7. What happens if too large a signal is presented to the grid?
8. Why can two tubes in push-pull deliver more than twice the output of a single tube before the same distortion level is reached?
9. What is a harmonic?
10. What effect does the presence of harmonics have on an audio voltage?
11. What benefits, in addition to increased power, are obtained from a push-pull stage?
12. Which harmonic would you expect to be the stronger, the second or the fifth?

18

DEMODULATING THE R. F.



IT would be nice if we could simply attach our audio amplifier to a receiving antenna and sit back and listen to a radio program rolling in loud and clear. Unfortunately, it is not that simple. Before our radio signal can be handled by an audio amplifier, it must go through a process called “detection” or, more accurately, “demodulation.”

You cannot explain the word “divorce” to a man who does not know the meaning of “marriage”; and, by the same token, before *demodulation* can be understood, one must know a little something about *modulation*.

Modulation

Modulation is the process by which the audio-frequency currents produced by a microphone are joined to the radio-frequency carrier currents generated by the transmitter. This truly is a marriage of convenience. The audio-frequency electromagnetic waves cannot travel through air for more than a few feet at most. Radio-frequency waves, on the other hand, can hop through space with the greatest of ease, but the ear will not respond to their rapid vibrations of hundreds of thousands of cycles per second. The obvious solution to the problem of transporting audio-frequency waves through space is simply to arrange some method by which they can ride piggy-back on earth-girdling radio-frequency waves from the transmitter to the receiver. Once they have arrived at their destination, the two can be separated and the audio-fre-

quency currents used to drive our speaker. The gadget that does the separating is called a *detector* or *demodulator*.

The audio voltage modulates the radio-frequency carrier in much the same way that you can "modulate" the stream of water issuing from the nozzle of a garden hose by applying varying pressure to a kink in that hose. The audio voltage exerts a kind of "valving" action on the carrier that causes the amplitude of that carrier to vary exactly in step with the audio voltage.

Fig. 1801 shows graphically how the modulating audio voltage influences the carrier. The graph represents the way the voltage changes with time. At 1801-a we have an unmodulated carrier showing the cycles of radio-frequency voltage. For a station in the middle of the broadcast band, these would be about 1,000,000 per second. Fig. 1801-b shows a complex audio-frequency wave consisting of various audio frequencies of different intensities. At 1801-c we show the carrier wave "envelope" that results when the audio wave modulates that carrier. Note that when the audio signal is zero, our carrier is of normal amplitude. As the audio signal increases in a positive direction, the carrier amplitude

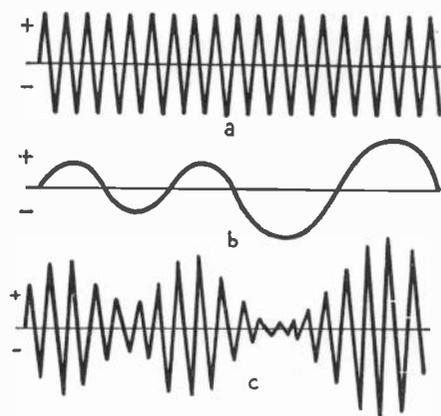


Fig. 1801. The r.f. carrier (a) is modulated by a.f. signal (b) to form the amplitude-modulated signal (c).

increases just as does the amount of water issuing from the hose when you relax your pressure on the kink. As the modulating voltage increases in a negative direction, the amplitude of the carrier is greatly reduced, just as the water flow is reduced to a trickle when you clamp down on the hose.

This modulated carrier is the signal our radio set receives. You

will notice that the frequency of the actual carrier remains unchanged. Only its amplitude changes. Under modulation the carrier develops a series of bulges and notches like the neck of an ostrich swallowing different-sized oranges. If the modulating voltage swings are strong, the bulges and accompanying dips are large; if this voltage is weak, the variations are barely perceptible. Also, if the modulating frequency is high, many of these bulges in amplitude appear in a short space of time; if low, only a few appear.

There is one marked difference between the audio voltage and the modulated carrier envelope produced by this voltage: the audio voltage appears first on one side of the zero and then on the other so that its force is exerted first in one direction and then in the opposite; but our modulated carrier expands and contracts simultaneously and similarly both above and below the center line (because a half-cycle of a.f. modulates many cycles of r.f.). That means that the equal and opposite voltages tend to cancel each other. The effect is about the same as if you held a strip of rubber in the center while someone pulled on the two ends with equal pressure. As far as you could tell by the feel at the point you were holding, nothing would be happening.

Demodulating the signal

If we are to recover our audio voltage from this modulated carrier, we must find a way of changing this "two-way stretch" back into a one-way stretch. The method of doing this is simple: split the carrier in two right down the center and use half of it. Since the top and bottom halves are identical, either will contain all of the information needed about the original modulating voltage.

This "splitting" is not hard if we remember that a top-and-bottom graph is just an engineer's way of saying that the current in the circuit flows one way half the time and the other way the other half. So what must be done is to *rectify* the r.f. current. That leaves us with a pulsating direct current; actually one with two sets of pulsations — those of the r.f. and those of the a.f.

We filter this pulsating current just enough to smooth out the r.f. peaks but not enough to bother the a.f. changes caused by the modulating voltage. Since the lowest radio frequency used in broadcasting is over 500,000 cycles per second and the highest audio frequency that can be heard somewhere around 15,000 cycles, that is easy.

Then we are left with a current whose pulsations reproduce those of the current which originally modulated the r.f. signal.

Fig. 1802 is a diagram of one of the earliest practical methods of detection. The crystal detector (indicated by XTAL) consists of a piece of galena (a common ore of lead) contacted by the sharp point of a phosphor-bronze wire called a *catwhisker*. It is

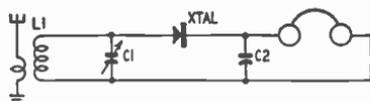


Fig. 1802. Circuit of a simple crystal set.

a peculiarity of this tiny contact that it will allow current to flow easily from the catwhisker to the galena but presents a very high resistance to the flow of current from the galena to the catwhisker.

In our diagram the radio signal is picked up by the antenna and inductively transferred to the tuned circuit L1-C1. The alternating radio-frequency voltage across this circuit is applied to the headphones *through* the crystal detector. Remembering that the crystal will allow current to flow in only one direction, we can easily see how half of our radio signal will be cut off as shown in Fig. 1803.

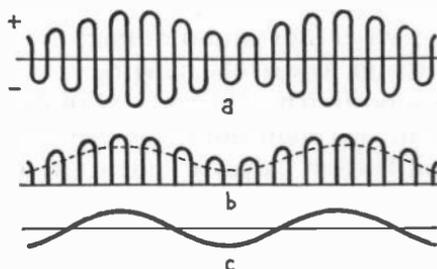


Fig. 1803. In detection, the modulated carrier (a) is cut in half (b) and the high frequency is filtered, giving us the original audio signal (c).

At Fig. 1803-a is the modulated carrier. This envelope is altered as shown in Fig. 1803-b by the crystal's refusal to pass pulses of current going in two directions. Only the pulses going *up* from the zero line are allowed to pass through. These pulses of current work together to charge capacitor C2 with a varying voltage as indicated by the dotted line of Fig. 1803-b. This capacitor discharges this varying voltage through the earphones.

Since the charge of C2 is made up of the average of the voltage pulses contributed by the expanding and contracting carrier, the voltage on this capacitor looks like Fig. 1803-c. This voltage wave is a faithful reproduction of the original audio voltage that modulated the carrier. C2 and the coils in the headphone make up our r.f. filter.

Catwhisker crystal detectors are seldom used these days. They are too hard to adjust and to keep in adjustment. The efficiency of the detector action is critically dependent upon the pressure of the catwhisker on the crystal and also varies greatly from one spot on the crystal surface to another. Furthermore, the crystal detector did not handle either extremely weak or extremely strong signals very well. It was superseded by the vacuum-tube diode detector diagrammed in Fig. 1804.

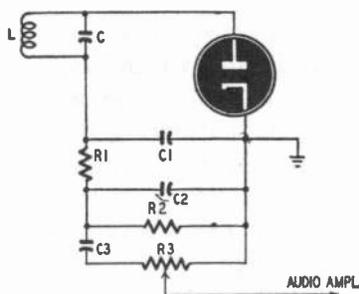


Fig. 1804. *The vacuum-tube diode detector.*

The diode detector

Although this circuit looks much more complicated, it functions just as did the crystal detector. The signal voltage appears across the tuned circuit L-C just as before, and the alternating r.f. voltage appears between the plate and cathode of the vacuum tube. While the plate is positive, as it is every half-cycle of r.f. voltage, electrons flow from the cathode to the plate. The more positive the plate swings, the more electrons it attracts. This means that when the carrier is expanding and the positive pulses of r.f. energy are increasing in amplitude, an increasing number of electrons go to the plate. When the carrier is decreasing and each pulse of voltage is weaker than the one just before it, the total electron flow decreases. The electrons actually flow in spurts as dictated by the evenly spaced positive pulses of r.f. voltage, but these spurts are blended together by the filter C1-R1-C2 to

produce a continuous flow that follows faithfully the variations in the amplitude of the modulated carrier.

Electrons attracted to the plate from the cathode return to the cathode through L and resistors R1 and R2. Resistor R1, together with capacitors C1 and C2, act as a filter to smooth out the

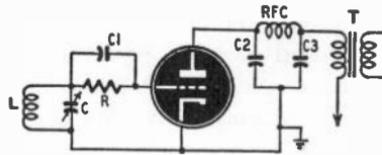


Fig. 1805. The grid leak detector is very sensitive.

“spurty” nature of the current delivered from the diode plate. The capacitors are large enough to offer a very low resistance bypassing action to the high-frequency variations resulting from the rectification of the individual r.f. pulses, but not large enough to have any material effect on the comparatively low-frequency variations resulting from demodulating the carrier envelope.

When this current, varying in accordance with the original audio voltage, flows through R2, it causes a voltage to appear across the resistor that is an exact reproduction of the original audio signal. Passing through capacitor C3, this voltage also appears across R3, the volume control. The slider on this control permits any fraction of the total audio voltage to be selected and passed along to the audio amplifier.

The grid leak detector

While the diode detector is much like the crystal detector in its “check-valve” action, it was not the immediate successor of the crystal detector. The grid leak detector actually supplanted the galena and catwhisker combination. Fig. 1805 is a diagram of a triode grid leak detector.

If you think of the grid as taking the place of the diode plate, you can see that the input portion of this circuit is really quite

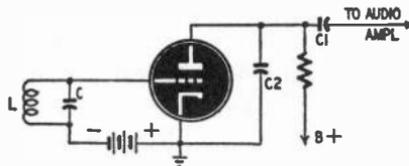


Fig. 1806. The power detector is biased to cutoff.

similar to that of our diode detector. The resistor across which the audio voltage develops has been moved to the grid leg of the input coil, and a capacitor is placed across this resistor so that the

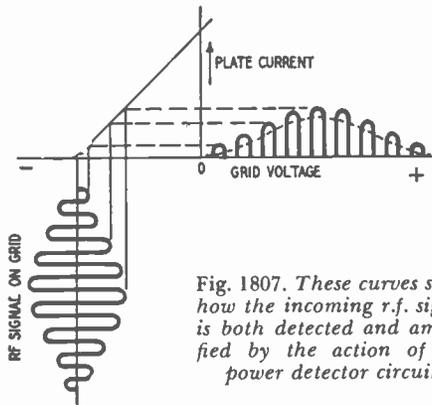


Fig. 1807. These curves show how the incoming r.f. signal is both detected and amplified by the action of the power detector circuit.

r.f. voltage can still be applied between the grid and the cathode; but we still have a condition in which the electrons will flow to the grid, just as they did to the diode plate, when that element is made positive by the half-cycle swings of r.f. voltage. The electron current to the grid, and consequently the voltage across resistor R — which is called the “grid leak” — varies in accordance with the amplitude of the modulated carrier.

The resistance value of the grid leak is sufficiently high (usually 2 to 10 megohms) so that the electrons attracted to the grid during the positive half-cycles of the r.f. carrier do not have time to leak off during the negative half-cycles; but it is at the same time small enough so that the negative voltage on the grid can go up and down in unison with the changes in amplitude of the modulated carrier. This leaves only the audio signal on the grid.

Now stop thinking of our grid as a diode plate and look upon the tube as an ordinary amplifier. On the grid we have a varying voltage that exactly reproduces the audio voltage originally impressed on the carrier. The triode amplifies this audio voltage in the normal manner, and we have an amplified audio voltage across the primary of transformer T that leads into the audio amplifier. C2 and C3, together with the radio-frequency choke RFC, remove any trace of the radio-frequency ripple that might get through to the plate of the triode.

The grid leak detector is very sensitive because it combines the functions of detection and amplification. A pentode can be used in place of the triode to obtain still greater sensitivity. One big

drawback of the grid leak detector is that, if it is made very sensitive to weak signals by the proper selection of values for the grid leak and the grid capacitor, it will distort strong signals badly.

The power detector

The "power detector" of Fig. 1806 will handle very strong signals without distortion. It looks like and is an ordinary amplifier circuit except that the bias is set so the tube is working very near the plate current cutoff portion of the curve, as is shown in Fig. 1807. Bias batteries are generally not used in practical circuits.

Since the plate current is practically zero with no signal on the grid, the negative swings of the r.f. voltage impressed on the grid have no effect on the plate current (it can't go below zero) but the positive half-cycles cause pulses of r.f. current to flow in the plate circuit as shown. These positive pulses of current increase or decrease in step with the amplitude of the voltage pulses on the grid. The charging and discharging action of capacitor C2 blends these separate pulses together into a varying current that rises and falls in step with the outline of the modulated carrier, as is shown by the dotted line. What we really have here is a combination of rectification (only the positive half-cycles of voltage affect the plate current) plus amplification. Since the grid bias is very negative, extremely large signals can be handled without overloading the detector.

This completes the types of detectors that have been used to receive amplitude-modulated radio signals. Each rightfully has enjoyed its day in the sun. The crystal detector has one decided advantage: it was entirely self-sufficient. No filament or plate batteries are needed to help it do its job.

The grid leak detector was much more sensitive—in fact, it is still the most sensitive of all detectors—but it could reproduce faithfully the audio portion of weak signals only. When the signal grew strong, the sensitive grid leak detector was over-loaded and caused distortion in the signal.

The power detector can handle much larger signals without introducing distortion, and it is between the diode and the grid leak detector as far as sensitivity is concerned. What is more, since it causes no rectified current to flow through the tuned input circuit, it does not "load" this circuit and so reduce its sharpness of tuning. All other detectors mentioned do have this defect.

With the introduction of the pentode amplifier tube sensitivity in a detector became of little importance. R.f. amplifiers could easily build up a weak signal to almost any value before it was presented to the detector. That is why the diode, in spite of its low sensitivity, became the most popular detector. It is unbeatable in its ability to handle any strength of signal without introducing distortion. What is more, it can do its job of detecting and, at the same time, produce other useful by-products, such as automatic volume control voltage which will be discussed in a later chapter.

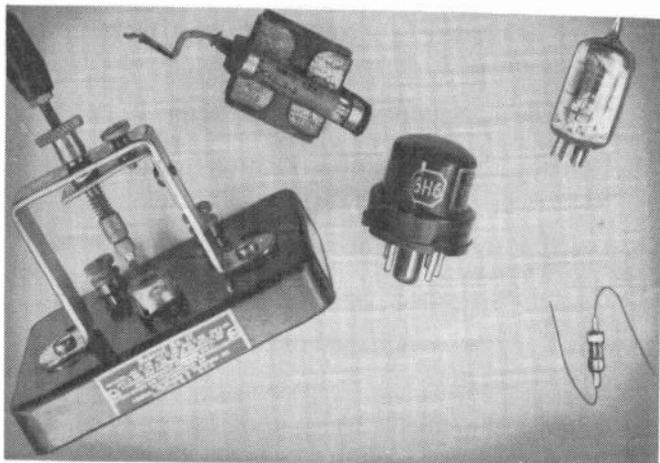


Fig. 1808. *Detector history—crystal to crystal. (Left to right): An old catwhisker detector; a grid capacitor with grid leak; 6H6 and 6AL5 diode detector tubes; germanium crystal diode in lower right corner.*

In the last few years a new form of crystal detector has become popular. This is the tiny germanium crystal diode seen in the photograph, Fig. 1808. The catwhisker in this unit is sealed in permanent optimum adjustment, and it will handle much more current than would the old galena job. That frees it of the two main drawbacks of its ancestor.

Thus, once more we see demonstrated that amazing and oft-repeated cycle wherein one generation of radio engineers banishes a particular gadget to the electronic attic, and then the next generation hauls the item out of the garret, dusts it off, makes a few changes, and puts it back into use until something better comes along!

QUESTIONS

1. Why do we need a *carrier* in a radio signal?
2. Describe how the carrier is modulated by the audio signal at the transmitter.
3. What is needed to recover the audio signal from the modulated carrier?
4. Describe the action of a crystal detector.
5. Describe the action of a vacuum-tube diode detector.
6. Describe the action of a grid-leak detector.
7. How does a power detector operate?
8. What are the advantages and disadvantages of the crystal detector?
9. What is the chief advantage of the grid leak detector?
10. What is its limitation?
11. What are the chief advantages of the power detector?
12. Why has the diode, in spite of its low sensitivity, become the most popular detector?

19

RECEIVER SELECTIVITY



A VERY young bird takes a lot of feeding and will swallow practically anything dropped into its gaping mouth. The detector stage described in Chapter 18 is much like this little bird: it requires a lot of signal to keep it going, and it will handle, without discrimination, almost anything fed into it.

But by the time a signal from a broadcast station reaches the receiving antenna it is usually about as strong as high-school prom punch; furthermore, two or three dozen broadcast signals may be on the antenna at the same time. If all of these signals were dumped into a detector, and if they were strong enough to be detected, a wild mixture of voice, music, and other sounds would come out of the speaker simultaneously.

To avoid such a bedlam, we need a special sort of selective amplifier between the antenna and the detector. Not only must this amplifier be able to build up the strength of received radio-frequency (r.f.) signals as an audio amplifier increases the amplitude of audio signals, but our radio-frequency amplifier must be able to select a particular broadcast signal from all those present on the antenna and amplify this one signal exclusively, while actually barring the passage of any other than the selected signal from the antenna to the detector.

Fig. 1901 reveals a simple way of doing this. It is a skeleton diagram of the basic elements of a tuned radio-frequency amplifier (t.r.f.). The antenna circuit is inductively coupled to the grid circuit of the first tube by the air-core radio-frequency trans-

former T1. The secondary of this transformer is tuned by the variable capacitor C1. The current inductively coupled from the primary of T1 is actually introduced *in series* with the secondary and the capacitor C1.

A series-tuned circuit presents a very low impedance to its resonant frequency and a higher impedance to all other frequencies. This means that the current in the circuit is much higher at resonance, as is the voltage drop across both the coil and the capacitor. In fact, the drop across either one of these elements is higher than the applied voltage; but at any other frequency than resonance, the voltage appearing across, say the capacitor, is greatly diminished, as shown by the resonance curve of Fig. 1902.

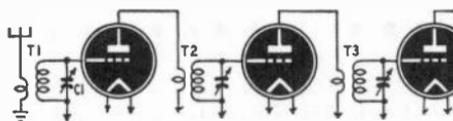


Fig. 1901. Basic tuned-radio frequency (t.r.f.) circuit.

This means that the signal voltage applied to the grid of the first tube and the one amplified by that tube will be high *only* for the frequency to which the tuned circuit is resonant. All other signal voltages in the primary will either be eliminated from the secondary or be greatly reduced. By varying the capacitance of C1 we can change the frequency to which our circuit is tuned and so select first one and then another broadcast signal to amplify.

Getting better selectivity

Unfortunately, a single tuned-radio-frequency stage seldom provides either the amplification or the selectivity necessary to receive a weak distant station without interference from a strong local one, especially if the two stations are near each other in frequency. The problem is solved by following the advice Grandma used to give on the subject of keeping warm with petticoats: if one doesn't do the job, use more of 'em! Two or three r.f. amplifier stages are arranged one after the other as shown in Fig. 1901. Thus, each amplifier tube takes up the job of boosting the signal right where the preceding stage left off.

This explains why "cascaded" r.f. stages can be used to get the required amplification, and Fig. 1903 shows why the increased

number of tuned circuits results in an improvement in selectivity. A band of frequencies of uniform strength is presented to the input of the first r.f. stage. Because of the selective amplification of this stage, the output shows the frequencies 5 kilocycles (kc) each side of resonance are only one-half the amplitude of

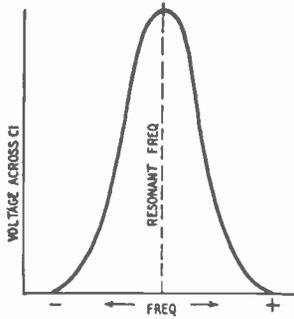


Fig. 1902. Frequency response of a single tuned circuit.

the resonant frequency F . Then, when this amplified signal gets to the next stage these 5-kilocycles-off-resonance frequencies are again amplified only half as much as the resonant frequency. Thus, since they were only half as strong to begin with, they are reduced to a strength only one-fourth that of the resonant frequency.

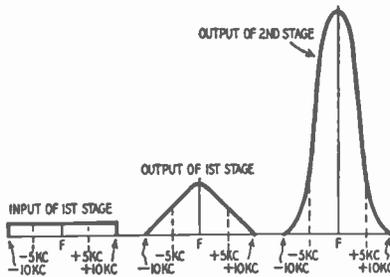


Fig. 1903. Cascaded r.f. stages will increase selectivity.

All the cascaded r.f. stages must be tuned to exactly the same frequency for most effective action. At first, each variable capacitor was adjusted by a separate dial. This made tuning the receiver too slow and complicated; so the tuning capacitors were "ganged," either by a system of pulleys and belts or by attaching the rotors of the capacitors all to the same shaft.

While this made it possible to keep the various tuned circuits "tracking" fairly close together as the tuning dial was rotated, there were always some discrepancies because it is practically impossible to manufacture identical capacitors and coils in mass

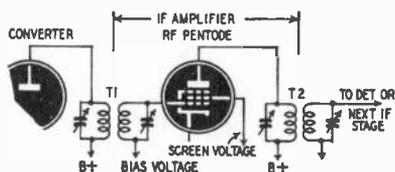


Fig. 1904. Circuit of a typical i.f. amplifier.

production. Even if it were possible, other metal objects near these units would change their characteristics when mounted in a receiver.

There are other faults in a tuned radio-frequency amplifier. For one thing, the efficiency of such an amplifier falls off as the

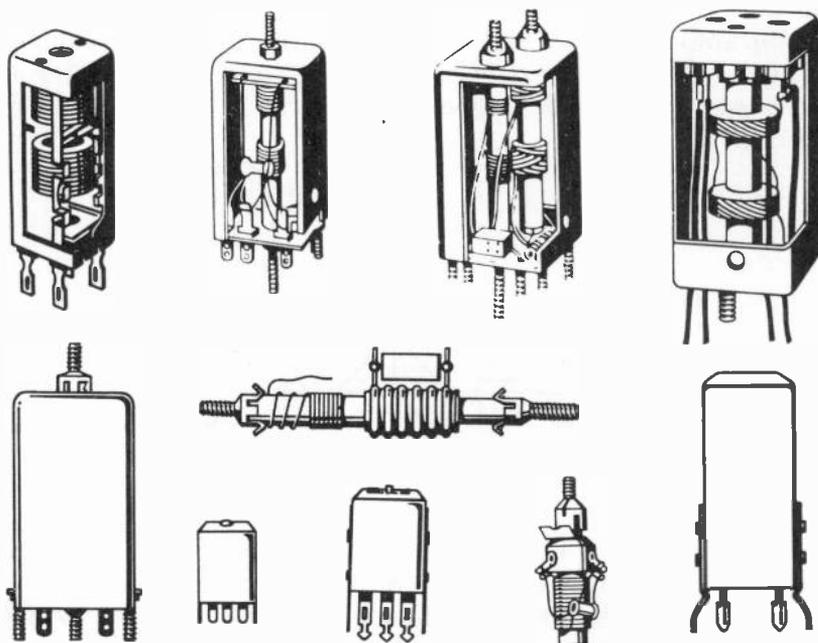


Fig. 1905. This drawing shows many types of i.f. transformers. At right is a trimmer-tuned type; the rest are slug-tuned types. (Stancor Electronics, Inc.)

frequency goes up and the losses that always accompany a rise in frequency increase. What is more, the selectivity also is variable. At 540 kc an interfering station 10 kc away from the frequency of the desired station has a separation of about 2% of the frequency; but at 1,600 kc, the other end of the broadcast band, this same 10 kc represents little more than one-half of 1%. That means that a tuned radio-frequency amplifier does not do nearly so good a job of separating stations at the high end of the broadcast band as it does at the low. Moreover, a large number of separate variable tuned circuits make a receiver both expensive and bulky.

The superheterodyne

A solution to almost all of these problems is to convert any frequency wanted to a single specified low frequency and then use a special one-frequency amplifier to do all the amplifying in this one channel. This funneling of all broadcast frequencies into a single amplifier frequency has many advantages. For one thing, the single frequency can be lower than the lowest broadcast channel, and this low frequency improves both the amplifying efficiency and the selectivity. Since the amplifying is all done at the same frequency, irrespective of the frequency of the broadcast signal being received, this means more uniform selectivity and sensitivity. Bulky and expensive variable tuning capacitors can be replaced with inexpensive and compact trimmer types, and shielding these smaller units is much less of a problem.

The superheterodyne receiver does all this. A single variable-tuned circuit is usually used to lead the desired signal from the antenna into a *converter* tube. Here the signal is converted to the *intermediate frequency* (i.f.) usually in the neighborhood of 455 kilocycles — and then fed into the intermediate-frequency amplifier, which is diagrammed in Fig. 1904. At this point, let's not bother about "how" this frequency-converting trick is accomplished. That will be explained to your complete satisfaction — let us hope — in a subsequent chapter.

You will note that the i.f. amplifier bears some resemblance to the r.f. amplifier; but the difference as the French deputy said about the differences between the sexes, is important. For one thing, both primary and secondary of the i.f. transformers are tuned. This gives four tuned circuits for only a single stage of intermediate-frequency amplification. Since we know that tuned circuits are what give an amplifier stage its selectivity, we are not

surprised to learn that in most ordinary broadcast receivers a single stage of i.f. provides all the selectivity needed. It provides all the amplification needed, too. The low frequency used, the high efficiency of the transformer, and the high gain of modern radio-frequency pentodes all combine to give us i.f. amplifier stages with gains of 100 and better.

The drawing, Fig. 1905, shows how various types of i.f. transformers are constructed. Such transformers may consist of two coils, usually mounted some distance apart and provided with screwdriver-adjustment trimmer capacitors for tuning each coil. Ordinarily a metal shield can completely enclose the transformer. Sometimes the coils are tuned by moving pieces of special metal in and out of their fields. In the transformer shown at the upper left of the picture, metal cups of this nature are screwed down over the coils to tune them. In other transformers of this *slug-tuned* type, slugs of this special metal are moved in and out of the center of the coils to change their resonant frequencies.

Coupling

The coupling between the primary and the secondary coils — determined by the position and separation of the coils — is of the utmost importance. Fig. 1906 shows why. Curve A represents very loose coupling with low current induced in the secondary, a current that peaks sharply at the resonant frequency. As the coupling is tightened, the current increases and the response curve keeps widening out until finally the curve of B is reached. At this *critical coupling* point, maximum current flows in the secondary at the resonant frequency. Moving the coils still closer

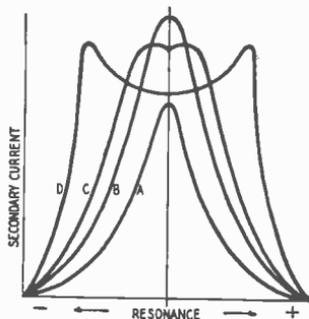


Fig. 1906. I.f. transformer bandwidth increases as coupling is increased.

together reduces the current at resonance and increases current at frequencies on either side of the resonant frequency. Curves C and D, respectively, show the progressive double-humping effect of further tightening of the coupling.

This peculiar condition results as the coils are moved closer together because the secondary reflects more and more impedance into the primary and this reflected impedance combines with the primary's own impedance to displace the current peaks of the

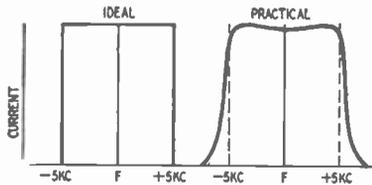


Fig. 1907. Illustration at the left shows ideal response curve while that at the right shows practical curve.

primary to each side of resonance. And because the voltage induced in the secondary is directly related to the current flowing in the primary, similar twin peaks also show up in the secondary response curve.

Obviously if the coupling is too loose, very little signal is transferred from the primary to the secondary. On the other hand, if the coupling is too tight, the selectivity goes to pot. Critical coupling is ordinarily the best all-around arrangement; however there are cases in which it is necessary to sacrifice maximum signal transfer for increased selectivity or deliberately to exceed critical coupling to widen the response curve.

How much bandwidth?

To understand why the sharpest response curve is not always the most desirable, we must absorb a new fact about the process of modulation: when a radio-frequency r.f. carrier is modulated by an audio-frequency (a.f.) two new frequencies called "sidebands," are produced, one on either side of the carrier. The frequencies of the sidebands are equal to the carrier frequency *plus* the modulating frequency and the carrier frequency *minus* the modulating frequency. For example, if we have a 1,000-kc carrier modulated with 1,000 cycles (1-kc), the sidebands are at 999 and 1,001 kc. 5,000-cycles (5-kc) produces sidebands at 995 and 1,005 kc.

These sidebands must be received without serious distortion or reduction if the modulating information they contain is to come clearly from the speaker. That means that the i.f. amplifying channel must be wide enough to pass them. If only 1,000 cycles are used to modulate the carrier, an i.f. amplifier that is 2 kilocycles wide would be sufficient; but when music with high notes up to 5,000 cycles is received, the amplifier must pass a band of frequencies 10 kc wide to avoid distortion.

Various methods are used to widen the response curve of high-fidelity receivers to approach the *ideal* curve of Fig. 1907. The practical curve can be achieved by overcoupling, by loading the tuned circuits with resistors, by deliberately resonating the tuned circuits to slightly different frequencies — called “flat-topping” — or by a combination of these methods.

Defects in the i.f. stage

I.f. amplifier troubles, outside of simple misalignment, fall into three broad classes: the stage oscillates; the response cannot be made sharp enough; gain is insufficient. Oscillation usually results from open bypass capacitors in the circuit, from poor shielding between the plate and grid circuits of the tube, or from a defective tube. Broad response results from defects in the windings of the i.f. transformer, such as shorted turns or high resistance, or from the coils having moved too close to each other. Defective windings may also produce low gain, as will windings that have slid too far apart or tuning capacitors that are shorted or defective so that they cannot resonate the associated winding to the proper frequency.

QUESTIONS

1. Why don't we connect the detector stage of a receiver directly to the antenna?
2. Describe the operation of a tuned radio-frequency circuit.
3. How can the selectivity offered by a single tuned stage be improved?
4. What do we mean by *tracking* tuned stages?
5. Name some faults of the tuned radio-frequency type receiver.
6. Show how the superheterodyne circuit corrects these.
7. Describe the basic operation of the superheterodyne circuit.
8. How is an intermediate-frequency transformer made?
9. What is *critical coupling*?
10. Why is other than critical coupling sometimes used?
11. Why must the if system of a high-fidelity receiver pass a band of frequencies greater than 10 kc wide?
12. List defects that occur in an i.f. stage.

20

THE CONVERTER STAGE

.....

Did you ever see sausage being made? A lot of different ingredients are tossed into the hopper of the meat grinder, but when they come out the other end of the machine, they are all sausage.

The superheterodyne receiver is a lot like this sausage grinder. The receiver can accept r.f. signals of widely different frequencies and convert them into a single "intermediate frequency" which will then pass through the i.f. amplifier. The grinder that reduces all the radio signals to a common denominator goes by the name of "converter" or "mixer" tube, and this chapter concerns itself with what kind of business goes on inside that tube. Two kinds of mixers are shown in Fig. 2001.

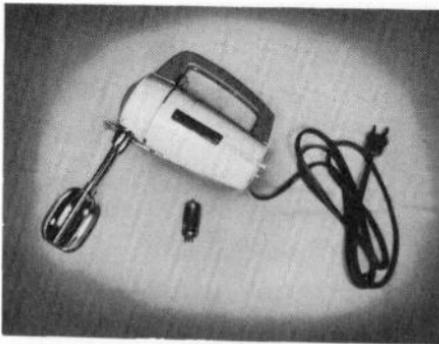


Fig. 2001. Mixers may vary widely in appearance.

The names applied to the tube give excellent clues to how it performs its presto-change-o miracle: it “converts” the incoming signals of various frequencies into a single intermediate frequency, and it does this by “mixing” each of those incoming signals with another signal that is generated in the receiver.

Beat frequencies

To understand why we can take a broadcast signal that is operating on, say 1,000 kc, mix it with another signal brewed in the receiver, and end with a signal exactly on the 455-kc intermediate frequency, we must explore the phenomena known as “beat frequencies.”

The authorities tell us: “If two or more alternating currents of different frequencies are present in an element having unilateral current flow properties, not only will the two original frequencies be present in the output but also currents having frequencies equal to the sum, and difference, of the original frequencies. These two new frequencies are known as *beat frequencies*.”

How a mixer works

Now that is just dandy, but we want to know *why*; so let us take a look at Figs. 2002 and 2003.

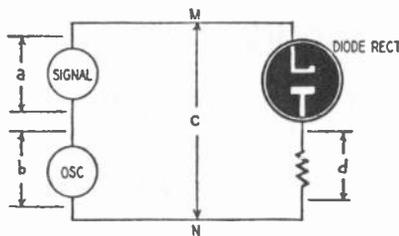


Fig. 2002. Diagram showing the elements needed in a converter.

Fig. 2002 shows two alternating-current generators, a diode rectifier tube, and a resistor, all connected in series. One of the generators is labeled *SIGNAL* and is operating at 12 cycles per second. The other, labeled *OSCILLATOR*, operates at 10 cycles per second. The reason for this name-calling will be given later.

Fig. 2003 portrays what takes place in various sections of the circuit of Fig. 2002. Fig. 2003-a shows the voltage output of the signal generator for a period of 1 second. At Fig. 2003-b we have

the output of the oscillator generator *during the same second*.

Since the generators are connected in series, the voltage-across points M-N (c) will be affected by voltages a and b from both generators. When the outputs of the two are in the same direction — that is, when corresponding terminals of the generators have the same polarity — the two voltages aid each other and the total voltage appearing across M-N is equal to the sum of the separate voltages. On the other hand, when one generator output voltage is positive while the other negative, the two voltages buck each other, and we have to subtract the negative voltage from the positive voltage.

Fig. 2003-c shows this interaction of the two generator voltages. The two voltages start out exactly in step, both rising from zero line; but since the signal voltage has to make 12 complete cycles during the time that the oscillator voltage is making only 10, they obviously cannot stay in step or “in phase.” By the time voltage-b starts rising on the first quarter of its second cycle, voltage-a is at the end of the first quarter of its fourth cycle, voltage-c is ending the third quarter of its third cycle. (See point O). The combined voltages are at minimum because voltage-a and voltage-b are bucking. However, by the time the oscillator voltage is rising on the first quarter of its sixth cycle, the signal voltage is also rising on the first quarter of its seventh cycle. The dashed lines,

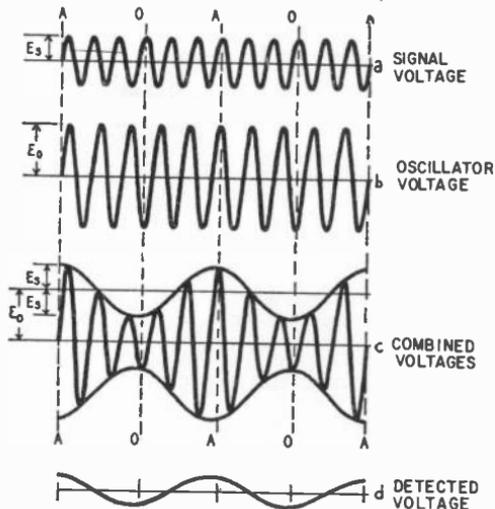


Fig. 2003. When the 12-cycle curve (a) is added to the 10-cycle curve (b) the result is a curve (c) modulated at the difference frequency of 2 cycles. Curve (d) is the detected voltage.

labeled A for aiding and O for opposing show that the output of the two generators aid and oppose each other at a rhythmic, regular rate; and this alternate helping-hindering action causes the amplitude of the combination voltage envelope shown at Fig. 2003-c to vary.

To see the matter from another angle, suppose we consider the analogy of two clocks, one of which goes tick-tock 40 times a minute and another which makes this sound thirty times a minute. At the beginning of the minute, both say "tick" so nearly at the same time that the result is a very loud sound. Then the ticks start drawing apart until finally one clock is saying "tick" at the same time the other is saying "tock." From that point on, the ticks start drawing closer together again until finally, at the end of 6 seconds, both clocks say "tick" simultaneously again, and we have another exceptionally loud sound.

This cycle repeats with a reinforced "tick" every 6 seconds. If we counted all of the ticks and tocks and then divided by 2, we should find that we had 70 tick-tock combinations per minute. The exceptionally loud ticks happen every 6 seconds; so we should have 10 of those per minute.

In other words, combining the 40-cycle-per-minute sound with the 30-cycle-per-minute sound, gives two new sounds: one is the sum of the two sound-frequencies, or 70 cycles per minute; and the other is the reinforced sound at 10 cycles per minute.

The positive and negative voltage peaks of our two generators combine in precisely the same way, and they also produce two new frequencies: one is equal to the sum of all the positive peaks plus all the negative peaks (of both generators) divided by 2 — or simply the sum of the two frequencies; and the other, that results from the periodic reinforcing action of coinciding "in phase" peaks, is equal to the difference between the two frequencies.

Why detection?

In Fig. 2003-c we see that the voltage envelope goes through a contraction-expansion cycle two times a second; and this frequency is the difference between the signal frequency of 12 cycles and the oscillator of 10 cycles.

But we must do something else to get our hands on this difference frequency. True, the two frequencies have been mixed and so the result is a voltage envelope that is modulated at the desired difference frequencies; but we must first extract that modulating frequency from the envelope.

That is where the “element having unilateral current-flow properties” come in. In Chapter 18 we learned that the way to recover modulation from a modulated envelope is to pass it through a “detector.” We also learned that a detector is a device that either passes current in only one direction or reacts much more enthusiastically to a voltage in one direction than it does to one in the opposite direction.

The diode tube of Fig. 2002 is such a device, for we know that current can pass through it only from the cathode to the plate. This means that only half of the envelope of Fig. 2003-c can pass through the tube and the resistor. As a result, the voltage across the resistor (d) will rise and fall right along with the outline of the top or bottom edge of 2003-c. Fig. 2003-d shows the alternating-current voltage that appears after the combined voltages pass through a detector.

Now that we know the *modus operandi* of mixing two frequencies to get a third, let's try our hand on a practical circuit. Look at Fig. 2004. A triode tube is connected as an ordinary grid-leak detector with a couple of important differences: between the bottom of L1 and the cathode is a coil that is inductively coupled to an “oscillator,” and the primary of an i.f. transformer appears in the plate circuit. In the next chapter we shall take up in great detail the subject of oscillators, but for the present it is enough to know that an oscillator is a generator of alternating current and can be made to operate on practically any desired frequency.

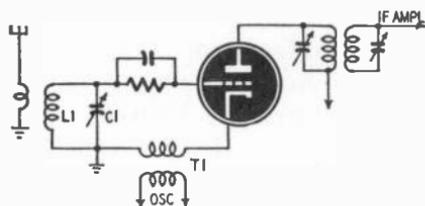


Fig. 2004. Circuit of a triode mixer. It looks almost like a grid leak detector.

Now, suppose a radio signal of 1,000 kc strikes our antenna and appears across the tuned circuit L1-C1 resonated to that frequency. At the same time, suppose our oscillator is operating on a frequency of 1,455 kc and that this frequency is delivered through T1 so that it appears between the bottom of L1 and the

cathode. In other words, the 1,000-kc and the 1,455-kc frequencies are in series so that their combined voltages are presented to the grid circuit of the tube.

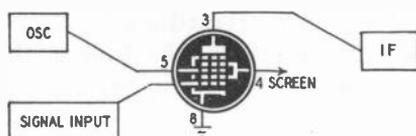


Fig. 2005. Circuit for frequency conversion with a mixer tube. This type of circuit needs a separate oscillator.

Our study of the similar circuit of Fig. 2002 tells us that this mixture of frequencies will result in a voltage envelope that is modulated at a frequency equal to the difference between the other two — in this case $1,455 - 1,000$ or 455 kc. We further know that when this envelope is passed through the detector tube, the modulating frequency will appear in the plate circuit. The tuned circuit of the i.f. transformer selects this “difference frequency” from the others that also appear in the plate circuit and starts it on its way through the i.f. amplifier.

If we want to receive a signal on 1,400 kc, we adjust our oscillator to a frequency of 455 kc higher (to 1,855 kc), and once more the difference frequency is the required intermediate frequency. By the same token, a 600-kc signal can be converted to the i.f. frequency by mixing it with a 1,055-kc frequency from the oscillator.

Image rejection

You are wondering why we bother with a tuned circuit connected to the antenna when we can change any signal to the intermediate frequency simply by parking the oscillator 455 kc away from that signal. You are forgetting one thing: *two* signals can be 455 kc from the oscillator frequency, one above it and one below it. For example, when we set our oscillator to 1,055 kc to receive a station on 600 kc, another station on 1,510 kc could also beat with our oscillator and produce a difference frequency of 455 kc. This would be accepted by our i.f. amplifier just as readily as one produced by beating with the 600-kc signal, and both signals would be heard at once. A tuned circuit that selects one of these signals and rejects the other is the solution.

In a practical receiver the tuning of the oscillator and of the

signal input circuit are mechanically coupled together and so arranged that there is always a difference between them equal to the i.f. of the receiver. Usually, in a broadcast receiver, the oscillator operates on the high-frequency side of the signal being received; so, if we have an intermediate frequency of 455 kc, the oscillator frequency is always 455 kc higher than the resonant frequency of the input circuit. Any station operating on the "image frequency" 455 kc higher than the oscillator frequency will be rejected by the input circuit that is always tuned 455 kc lower than the oscillator.

More sophisticated circuits

Many tubes have been built specifically for the job of frequency conversion. One such tube is shown in Fig. 2005. In addition to the usual plate, screen, cathode, and suppressor elements, this tube has *two* input grids, both of which can control the plate current. That means that when the signal voltage is connected to one grid and the oscillator to the other, these combined influences determine the plate current, just as they did when both appeared together on the grid of our triode. The only difference is that the mixing now takes place in the electron stream instead of the grid circuit.

The tube operates over a nonlinear portion of its curve and so gives "power detection" action to the mixed frequencies. In Chapter 18 we learned detectors of this type are not sensitive to weak-signal carriers. A substantial portion of the bending part of the tube's curve must be brought into play to get unequal amplification of positive and negative peaks required for detection. A very small portion of the curve, such as used by a weak carrier, does not have enough bend to accomplish this.

The local oscillator always furnishes a strong "carrier" — usually better than 20 volts peak-to-peak — and the strength of the signal itself merely determines the depth of the i.f. modulation impressed on this supplied "carrier." A close study of Fig. 2003-c will reveal this is true. Thus we see that the oscillator voltage is not only necessary for mixing with the signal voltage, but also improves the efficiency of the detector part of our converter.

Pentagrid converter

The mixer tube, however, requires a separate oscillator, therefore the "pentagrid converter," combining mixer and oscillator in one tube is popular. Fig. 2006 illustrates a pentagrid converter

in a typical circuit. Grid Nos. 1 and 2 (pin connections 5 and 6) form the control grid and anode, respectively, of a triode oscillator, with pulses of current flowing to grid No. 2 at the oscillator frequency. Not all of the electrons that reach grid No. 2 stop there, however. Some of these spurts of electrons continue on toward the plate and are further modified by the signal voltage

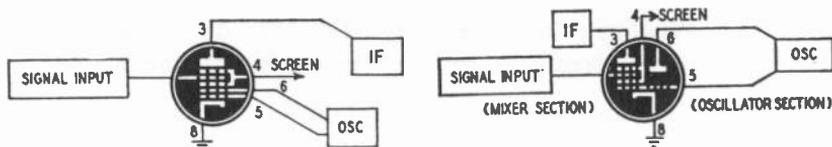


Fig. 2006. Pentagrid converter circuit. Fig. 2007. Triode-hexode mixer circuit.

impressed on grid No. 4 (signal input grid). Thus the electron stream that finally reaches the plate has been shaped first by the oscillator frequency and then by the signal frequency. The detector action of this five-grid tube is like the mixer tube.

Still another type of mixer is the triode-hexode illustrated in Fig. 2007. In the envelope of this tube we have a triode oscillator and a hexode mixer. The grid of the oscillator section is connected internally to one of the two input grids of the mixer section and so causes the oscillator voltage to appear on that grid. The signal input frequency is connected to the other input grid, and the mixing and detection action from this point forward is quite like that of the mixer.

You will meet various modifications of these basic mixer circuits from time to time, but you can unscramble them all if you keep the following in mind. When two a.c. frequencies appear together, they produce a voltage envelope that is modulated at a frequency equal to the difference between them. This difference frequency can be separated from the other two by passing the mixture through any nonlinear "detector" device.

QUESTIONS

1. What two names are given to the stage that changes the received broadcast station frequency to the i.f.?
2. Give the physical law covering the generation of beat frequencies.
3. What is meant by "an element having unilateral current-flow properties"?
4. If two frequencies, A and B, are mixed together, what new frequencies are generated?
5. Is making both frequencies appear across the same resistor enough to produce beat frequencies? What else is needed?
6. Where is the frequency used to beat with the received signal obtained?
7. Does a superheterodyne use the sum or difference frequency to produce the i.f.?
8. What is an *image frequency*? How is it rejected in the receiver?
9. How is the tuning of the r.f. stage and the oscillator stage kept in step?
10. Describe the operation of a special mixer tube.
11. How does a pentagrid converter work?
12. Describe the operation of a triode-hexode mixer.

21

SOME OSCILLATOR CIRCUITS



EVERY radio signal, from tiny coded “beeps” of a satellite transmitter to the output of a broadcast station is born from an oscillator. After a radio signal has grown husky enough to leave the transmitting antenna, it soon meets a receiver. If this receiver is a superheterodyne — and the odds are better than a 1,000 to 1 that it is — the radio signal meets another little oscillator in the receiver. Our radio signal is no laggard in love, and marriage takes place in a fraction of a microsecond. Out of this union is born a little intermediate-frequency signal that is the “spittin’ image” of its father; except that it has a different frequency.

The word “oscillator” comes from a Latin word that means to swing back and forth. The rocking chair and the clock pendulum are mechanical oscillators. If an empty rocking chair is given a push, it will continue to rock back and forth through decreasingly smaller arcs until it stops. A subsiding oscillation like this is called a “damped” oscillation.

If enough aiding power is delivered to a swinging object to overcome losses due to friction, air resistance, etc., the oscillation does not die out but continues as long as power is fed to it. Such a continuing oscillator (clock pendulum, for example) is called a “driven” oscillator.

When we think about an electrical counterpart of the mechanical oscillator, our mind naturally turns to a coil-across-capacitor combination. When a coil is placed across a charged capacitor, electrons rush from the negative plate through the coil. This current builds up a strong magnetic field about the coil. The

collapse of this field continues to drive the electrons toward the plate that was positive, giving that plate a negative charge. Then the whole process is reversed. The electrons keep surging through the coil from one capacitor plate to the other until circuit losses finally succeed in damping the oscillation. The frequency of these oscillating current surges is near the resonant frequency of the tuned circuit.

If we can put more energy into this oscillating circuit — extra power that will *work with* the oscillating current—we can replace the energy lost and so keep the circuit oscillating indefinitely, just as the tiny pushes given to the clock pendulum keep it oscillating. Since we can control the frequency of electrical oscillation by changing the resonant frequency of the tuned circuit, such an oscillator is an a.c. generator (a generator with no moving parts!) that will operate on any frequency we choose, up to many millions of cycles per second.

The trick is to inject those little extra pushes of current with precisely the right timing so that they will aid rather than oppose the oscillating current in the tuned circuit; and when you consider that the current may be swinging back and forth a hundred million times a second, that might appear about as easy as trying to hurl an egg, intact, between the whirring blades of an electric fan. The feat is accomplished by connecting our oscillating tuned circuit to a vacuum tube so that the oscillations themselves trigger and direct the insertion of this “booster” energy.

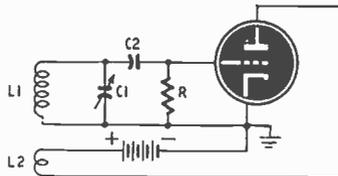


Fig. 2101. Simple feedback oscillator.

Vacuum-tube oscillators

Fig. 2101 illustrates one way of doing this. L1-C1 is the variable tuned circuit. C2 applies the voltage appearing at the top of this circuit directly to the triode grid. The grid leak R furnishes bias for the tube in a manner to be described later. Current flows from the cathode to the plate of the tube and then returns to the cathode through L2, inductively coupled to L1.

Suppose that a tiny disturbance in the grid circuit causes the grid to go slightly positive. This causes an increase in plate current. The magnetic field about L2 expands as this current increases and the lines of force cut the turns of L1 and induce a voltage in it. This voltage is of the proper polarity to add to the positive charge of the grid. A further increase in plate current results along with still more inductive coupling, or feedback, from the plate to the grid circuit.

This current-building-up process continues until the voltage drop across the reactance of L2 calls a halt. At this point the instantaneous voltage on the plate is so low that there is no further increase in plate current even though the grid does go more positive. The magnetic field about L2 stops expanding and starts to collapse. This induces a reverse voltage in L1 so that the charge on the grid starts to move in a negative direction. This negative-going grid voltage aids the falling off of plate current, and the decreasing plate current, through the magnetic coupling, keeps driving the grid more and more negative.

Finally the plate current is zero and making the grid voltage more negative can produce no further change. Then the voltage ceases to be induced in L1 by L2, and the grid voltage starts to go positive again. The actual frequency of these reversing surges of current is determined by the resonant frequency of L1-C1. The energy fed back from the plate simply helps the charge on the grid to move in whichever direction it is going. To be sure these oscillations will be sustained, enough of this energy must be fed back to compensate for the losses in the grid circuit. The actual amount of feedback depends upon the amount of coupling between the circuit and the *tickler* coil L2.

The grid leak develops bias for the oscillator tube. While the grid is positive, it attracts more electrons than can leak off to ground during the part of the cycle in which the grid is negative. The electrons thus trapped on the grid give it a negative bias.

When the tube is not oscillating it has zero bias. The amplification is then maximum and the circuit is so unstable that the least disturbance will set into motion this chain of events that leads to sustained oscillation. Under the more stable conditions of fixed bias, the tube would be harder to start oscillating. Grid-leak bias automatically adjusts itself to the best value for sustaining oscillation when the load on the oscillator changes. If power is taken from the tank circuit and the amplitude of the voltage swings is reduced, the grid attracts fewer electrons, the bias is lowered, and

the plate current increases. The heavier plate current surges help replace the energy lost from the tank circuit to the load.

Some circuit variations

While these basic principles are true for all oscillator circuits, there are many ways to apply them. Fig. 2102 shows some popular ones. We see in Fig. 2102-a (Armstrong oscillator), that the frequency-determining tuned circuit can be in the plate circuit instead of the grid circuit; or, as shown in Fig. 2102-b (Meissner oscillator), it can be in altogether a separate circuit that is inductively coupled to both the plate and grid circuits.

Fig. 2102-c (Hartley oscillator), reveals that two separate coils are not needed. Here the plate current flows through part of the tank coil. Inductive coupling between this part of the coil and the whole coil gives us transformer action just as if two separate windings were used. Fig. 2102-d is similar to the circuit of Fig.

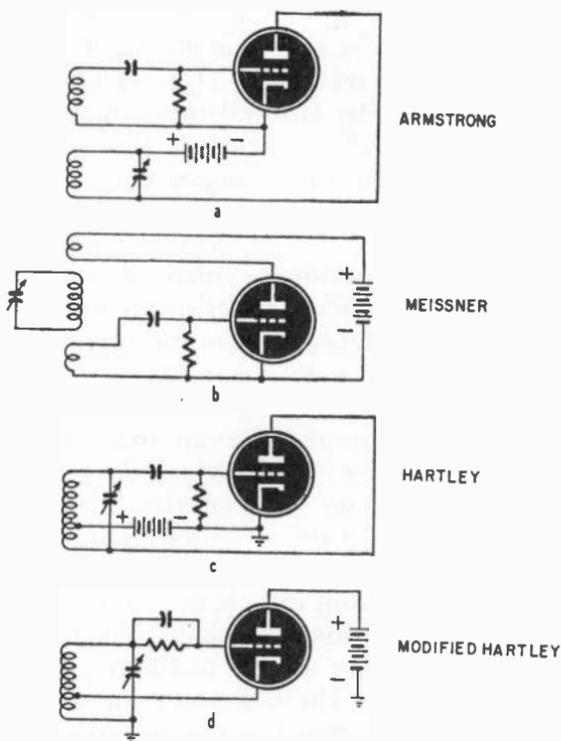


Fig. 2102. Some commonly used oscillator circuits.

2102-c. If you have trouble, at first, in seeing how 2102-d provides coupling between the plate and grid circuits, just remember that the plate current also flows through the cathode circuit. The pulses of plate current appear between the tap on the coil and ground.

Fig. 2103 is known as the Colpitts. Here the cathode goes to a tap on a capacitive voltage divider instead of an inductive voltage divider, as it did in the Hartley. The amount of feedback depends upon the ratio of the capacitive reactances of C1 and C2. The Colpitts circuit is sometimes used in slug-tuned push-button oscillator circuits or for receivers working on the long-wave "weather" bands.

Incidentally, as the capacitance of the tuned circuit is increased, heavier currents circulate in the circuit and the losses go up. For this reason, an oscillator usually oscillates more vigorously on the high-frequency end. You must always provide enough feedback to make sure that the amplitude of oscillation is satisfactory at the low end.

However, you can get too much of a good thing; and feedback is no exception. If you have too much feedback, the oscillator is likely to develop a second, unwanted or parasitic mode of oscillation that will put birdies to twittering on the signals as they are tuned in, especially on the high-frequency end of the band.

Oscillator tracking

Tracking refers to the fact that the two tuned circuits shown in Fig. 2104 must follow certain tuning paths if our superheterodyne receiver is to work as it should.

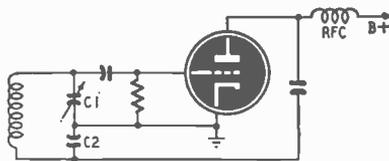


Fig. 2103. This Colpitts oscillator has a capacitive voltage divider.

You will recall that the oscillator frequency must always be spaced from the signal frequency you wish to receive by the intermediate frequency. Usually the oscillator operates on the high-frequency side of the signal. That means that if we wish to tune a band of 540 to 1620 kc, and if our i.f. is 455 kc, the oscillator must tune through a range of 995 to 2075 kc.

In each case the total span of frequencies being 1,080 kc you might think that identical tuning capacitors on a single shaft, used with two different values of inductance, would accomplish our purpose of keeping the oscillator circuit always 455 kc higher than the signal input circuit. But you would be wrong. The spans of frequency are the same, but a ratio of 540 to 1620 kc is exactly 1 to 3, while from 995 to 2075 kc the ratio is slightly less than 1 to 2. If identical capacitor sections are used to resonate the two coils to frequencies 455 kc apart at the high end of the band, the gap between the two tuned circuits steadily narrows as the tuning capacitor is tuned toward the low-frequency end of the band.

One way to keep the tuned circuits 455 kc apart is to use a tuning capacitor with two sections having different shapes and sizes of plates. One section of this capacitor varies from 8.7 to 170.7 μf , while the larger section goes from 11 to 431 μf . When such a capacitor is used with proper coils, the oscillator will always be tuned 455 kc higher than the signal input circuit for any setting of the capacitor shaft.

The padder capacitor

This method, unfortunately, can only be used on a single band — unless you want to use more than one tuning capacitor! However, a padder capacitor together with a capacitor section that has uncut plates can make that section seem as though the plates were tailored to the oscillator circuit needs; furthermore, different padders can be used on different bands so that the same tuning capacitor section can be used to track the oscillator correctly on each of these bands.

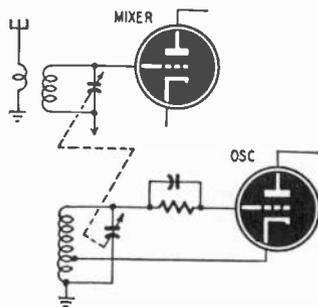


Fig. 2104. In the superhet, the oscillator and mixer tuning capacitors are on one shaft as indicated by the dashed line.

Fig. 2105 helps understand how this is done. The tuning capacitor C_t and the padding capacitor C_p are in series across the coil. When two capacitors are in series, their total capacitance is equal to their product divided by their sum. Let us assume that the maximum capacitance C_t is $431\ \mu\text{f}$, just as is the section tuning the signal input circuit. C_p is a semivariable capacitor adjustable by a screwdriver. If we adjust this capacitor to about $280\ \mu\text{f}$, we find that the series combination of C_t and C_p is very close to the $170.7\ \mu\text{f}$ maximum capacitance furnished by the cut-plate section of the other tuning capacitor.

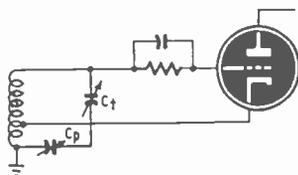


Fig. 2105. For correct tracking, a padder capacitor is used in series with the tuning capacitor.

As the frequency of the oscillator is tuned higher, the fixed capacitance of C_p has less and less reactance. At the same time the reactance of C_t steadily increases. By the time the high-frequency end of the band is reached, the reactance of C_t is so much greater than that of C_p that the tuning capacitor is almost entirely responsible for the tuning of the oscillator circuit. As the circuit is tuned toward the low-frequency end of the band, however, the padder capacitor reactance has more of a "hobbling" action on the tuning capacitor and makes the effective maximum capacitance much less than it would be without the padder. By using the proper value of inductance and the proper padder, an oscillator circuit may be made to track exactly at three different points in the tuning range. Deviation from the exact frequency at other points is negligible.

Oscillator troubles

Oscillator failures are usually due to defective coils, bad grid-coupling capacitors, or defective grid-leak resistors. The best way to check an oscillator is to measure the negative voltage on the grid with a vacuum-tube voltmeter. No voltage indicates an oscillator that is not functioning, and the amplitude of the voltage at different settings of the tuning capacitor reveals whether there are any weak spots in the oscillator's output.

QUESTIONS

1. Are oscillators important in radio? Explain.
2. What is necessary for sustained oscillation?
3. Describe the operation of a vacuum-tube oscillator.
4. What advantage comes from using a grid-leak to bias the oscillator?
5. Sketch the circuits of the Armstrong, Meissner, Hartley and Colpitts oscillators.
6. What is the effect of too much feedback? too little?
7. Why can't identical capacitors be used to track the r.f. and oscillator circuits?
8. Describe a mechanical method of tracking these circuits.
9. How can a padder capacitor be used to accomplish the same thing?
10. What is the best way to check the operation of an oscillator?
11. Should the output be uniform from one end of the band to the other?
12. What causes most oscillator failures?

22

HOW TO TRAP A SIGNAL



BEFORE we set out to trap a signal we should have some idea of the characteristics of the game we are after. The "game" in this instance is a transmitted signal; and, while its characteristics are more complicated than the rules for playing postoffice, they are by no means beyond comprehension.

We know that when 60-cycle a.c. flows through a wire, the conductor is surrounded by a changing magnetic field. Part of the electrical energy is alternately stored in this field and then returned to the wire. If the frequency is increased to 10,000 cycles a second and beyond, some of the energy delivered to the field

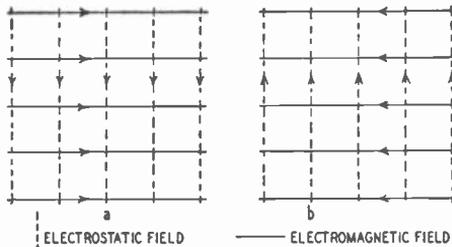


Fig. 2201. Patterns showing the electromagnetic and electrostatic fields of force of a radiated signal.

about the wire does not return to the conductor but sails off into space as radiated energy. When a transmitting antenna is substituted for our conducting wire encouragement is given to the a.c. energy to leave home and keep going.

Fig. 2201-a gives us a head-on view of this free-wheeling radio wave as it zips through space directly toward us at a speed of 186,000 miles a second. Notice that there are really two fields, which share the energy of the wave equally between them: an *electrostatic* or “voltage” field, and an *electromagnetic* or “current-inducing” field. These two fields are inseparable and always act at right angles to each other. Both operate at right angles to the direction of travel.

Broadcast-band waves ordinarily have their electrostatic fields producing lines of force in a vertical direction with regard to the earth and are said to be “vertically polarized.” Television stations in the United States send out waves whose electrostatic stress is exerted parallel to the earth and are called “horizontally polarized” waves.

At the instant pictured in Fig. 2201-a, the electrostatic stress is from top to bottom, and the electromagnetic stress is from left to right. Fig. 2201-b pictures the same wave passing the same place at a time interval equal to one-half wavelength later. Note that by now the electrostatic stress is from bottom to top and the electromagnetic stress is from right to left.

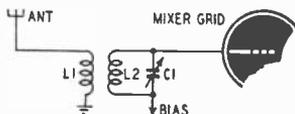


Fig. 2202. Antenna circuit inductively coupled to mixer grid.

The thing to keep clearly in mind is that these two fields are *moving* and that as they move past a stationary portion of space they produce stresses in that space. For example, as the electrostatic portion of the wave encounters two points in space, one directly above the other, first the top point will be positive with respect to the bottom point and then vice versa. If the two points are connected by a length of wire, an alternating current will flow in this wire as the radio wave zips past it.

Snaring the signal

Fig. 2202 shows how we take advantage of this fact to trap a signal for our receiver. A vertical wire is connected through coil L1 to earth. The top of this antenna and the earth constitute the two “points in space” mentioned previously. The current flowing

in L1 is inductively coupled to tuned circuit L2-C1. By resonating this tuned circuit to the signal we want to receive, we can reject all other signals flowing in the antenna circuit and allow only the wanted one to appear on the grid of our mixer tube.

This "outside" antenna provides a good method of intercepting a radio signal, but it has disadvantages. First, since its effectiveness depends to a large degree on its height, it is difficult to install; second, special precautions must be taken to prevent this elevated antenna from extending the welcome-mat to a bolt of lightning; third, few antennas of this kind do anything for the appearance of a home; and fourth, a radio needing such an antenna is rooted to one spot near where the lead-in is brought into the house. Fortunately the necessity for outside antennas for broadcast-band receivers has been almost eliminated.

As can be seen from Fig. 2203, the *high-impedance loop antenna* is really an expanded antenna transformer. Instead of occupying only a couple of inches of space, the secondary of the transformer is wound in the form of a spiral or large diameter

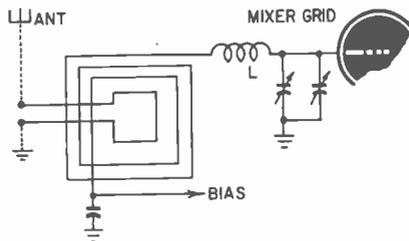


Fig. 2203. *High-impedance helix-type loop antenna.*

helix so that it has an area of many square inches. In this enlarged form, it can intercept a sizeable portion of the field of a radio wave and so provide sufficient signal for the receiver without an outside antenna.

Where space is at a premium, as in portable transistor receivers, the "loop" is wound in the form of a long coil on a circular rod or flat strip of ferrite material. These "loopstick" antennas provide high inductance, high Q and good signal-capturing ability in a very small space.

Directional properties

Such a loop antenna is directional; it will receive a signal much better when the loop is arranged so that its plane is

paralleled to the line of transmission of the radio signal than it will when this plane is at right angles to the line of transmission. If you will look at the simplified one-turn loop shown in Fig. 2204, you can see why. At 2204-a the incoming signal strikes both sides of the loop simultaneously. The currents induced in the two sides of the loop by the passing magnetic field — the loop depends upon the electromagnetic field of the radio wave for its

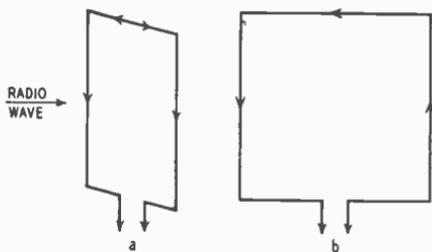


Fig. 2204. This diagram shows the directional properties of the loop antenna.

action — are equal and opposite in phase; so they simply buck each other and the signal is received very weakly if at all.

At 2204-b, however, the wave strikes one side before the other. If you keep in mind that, as the wave moves through space, its fields are constantly shifting back and forth, you can see that the direction and intensity of the current induced in the first leg of the loop cannot be identical with the direction and intensity of the current induced in the second leg, because the wave has traveled through space between these two encounters and the electromagnetic field that produces the current has changed somewhat during that short trip. Since the two currents are not identical, they cannot balance each other out, and we shall have an alternating current flowing in our loop. Do not think that the two currents are *in phase* when the loop is parallel to the line of transmission — the loop would have to have its two sides a half-wavelength apart for that — but they are not 180 degrees out of phase as they are when the plane of the loop is at right angles to this line. This slight shift away from the 180-degrees-out-of-phase condition is all that is needed to let a signal be received.

The voltage pickup is proportional to the loop area. The farther the loop is located from the chassis or any other large metal object, the lower is its distributed capacitance, the higher is its

Q , the sharper it tunes, and the more directional it is. Unfortunately, the usual small receiver permits the loop to be placed only an inch or so from the chassis. One way of overcoming some of these disadvantages is to have the loop detachable from the receiver and arranged so that it can be held in the best position by suction cups.

Improved loop antennas

An approach that is more electronic and less mechanical is diagrammed in Fig. 2205. Here a loading coil L is used in series with the loop. This loading coil has a high Q and a low distributed capacitance. Since the distributed capacitance of the loop circuit is thus reduced, the tuning range of the loop is extended

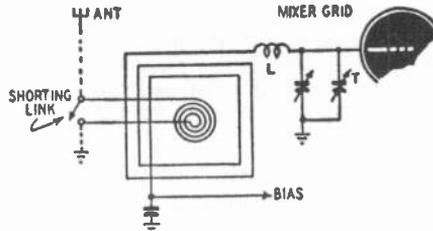


Fig. 2205. Adding a loading coil L to the loop antenna gives it better response.

for use with a given capacitor. Raising the Q of the tuned circuit gives sharper tuning and better signal response. In many receivers, this loading coil is slug-tuned for best tracking over the tuning range.

Provisions are usually made for connecting an outside antenna to these loops for receiving distant or weak stations. A low-cost way of doing this is to place a single turn of wire around the loop at the low-potential side as is shown in Fig. 2203. Such an arrangement favors the high-frequency end of the band, but that can be overcome by inserting a resistor of 500 or 1,000 ohms in series with the single turn. If too much coupling is provided, the signals tend to be hum-modulated and the selectivity suffers.

A high-impedance primary, shown in Fig. 2205, gives more uniform coupling than does the single-turn job of Fig. 2203, but is guilty of the cardinal sin of manufacturing: it costs more! When such a high-impedance primary is used, it is usually provided with a shorting link to be used when an external antenna is not connected. This is to prevent the absorption of energy by the primary coil at its resonant points that fall in the broadcast band.

One manufacturer has still another system for getting around the disadvantages of the high-impedance loop. He uses a low-impedance loop, as shown in Fig. 2206, which consists of two to four turns of large-diameter wire. This is inductively coupled to the grid of the mixer tube through a very high-Q autotransformer. The low-impedance loop is relatively insensitive to ca-

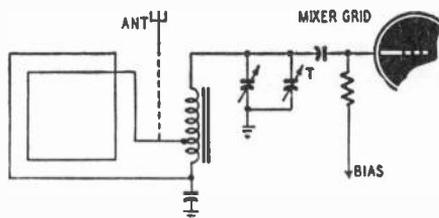


Fig. 2206. By using only a few turns on the loop but coupling it to the mixer through a high Q autotransformer, the antenna response can also be improved.

pacitance effects and to calibration changes due to changing its position. Both the Q and the response are practically uniform throughout the broadcast band. An external antenna, when used, is connected directly to the high-potential side of the loop.

Many of the better receivers place loop antennas inside electrostatic shields. This serves the double purpose of cutting down on much man-made interference and of insuring uniformly distributed capacitance effects for the loop.

The directional properties of a loop antenna are fine for cutting down on interference, either from an unwanted radio station or from a noise source that occupies a single point in space.

QUESTIONS

1. Of what two components is a radio wave composed?
2. How are broadcast waves polarized? television station waves?
3. Describe how passing radio waves induce currents in a vertical antenna.
4. List four disadvantages of an outside antenna.
5. What, basically, is a *high-impedance loop antenna*?
6. What are the advantages of a *loopstick* antenna coil?
7. Explain why a loop antenna is directional.
8. In what directions does a loop antenna receive best? worst?
9. What factors affect the amount of signal delivered by a loop?
10. Name some ways to achieve a high-Q and low distributed capacitance in a loop antenna.
11. What advantages accrue from placing the loop inside an electrostatic shield?
12. In what way can the directional properties of a loop antenna be put to use?

23

SIGNALS IN SPACE



IN the last chapter we implied that waves traveled a straight path from transmitting antenna to receiving antennas. That is not the case!

Ground waves

Fig. 2301 shows what happens. Some of the waves from the transmitter at A follow the surface of the earth like the one designated G. These "ground waves" induce currents in the earth,

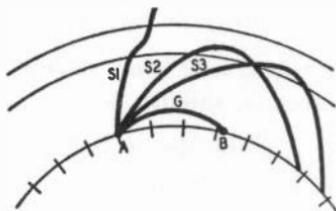


Fig. 2301. *How radio waves act in space.*

and the resistance of the earth causes them to die out rapidly, particularly at higher frequencies. On the broadcast band these waves account for daytime reception. They are good for about 50 miles at the high-frequency end of the band and up to 200 miles at the low-frequency end.

Sky waves

Then there are "sky waves" that travel upward from the transmitter at angles, as shown at S1, S2, and S3. Some of these, like S1, keep traveling, never to be heard from again. Others, like S2 and S3, meet "something" up there that persuades them to turn back to earth.

The "something" that turns them back is a series of ionized layers above the earth's surface at distances from 30 to 250 miles. Gases in the upper atmosphere, bombarded by ultra-violet and cosmic ray radiation, become ionized. Since these gases hover at various heights according to their weight, and since the bombardment is more effective as the atmosphere becomes rarer, the ionization is in layers, each layer being more ionized than the one below it.

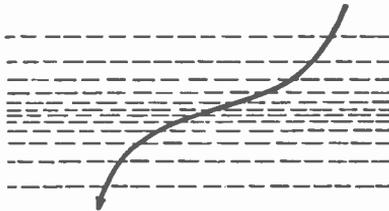


Fig. 2302. *Wave path in an ionized layer.*

Radio waves are bent when they pass through an intensely ionized layer. The wave behaves as though it hates ions and wants to avoid them. This is shown in Fig. 2302. As the radio wave enters the ionized layer, it moves away from the deeply ionized portion of the layer; but once it is forced to pass through this center portion, it reverses its direction of curvature so as to escape from the layer quickly.

The amount of bending depends upon the angle with which the radio wave strikes the layer, the wave frequency, and the intensity of ionization of the layer. If the wave strikes the layer nearly at right angles, as shown at A in Fig. 2303, there is little bending. As this angle decreases, the bending becomes more pronounced, as illustrated at C and D. A low-frequency wave bends or "refracts" more than one of higher frequency. If a wave strikes the layer at an angle that just permits it to be bent back to earth, a higher frequency wave will pass through. Often a wave will

penetrate a lower layer only to be turned back by the increased ionization of the layer above it, as pictured at B.

The subject of what happens to a radio wave in the ionosphere is complicated. All we need know is that sky waves can be bent back to earth; that most broadcast-frequency sky waves are absorbed during day time but are not absorbed at night; and that the spot to which a wave returns depends upon several variable factors.

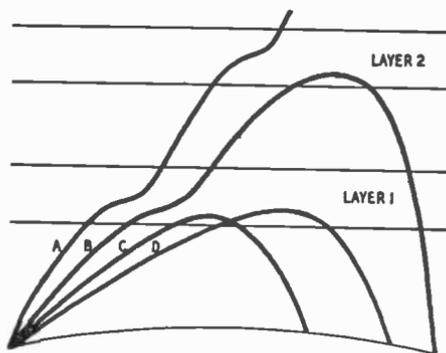


Fig. 2303. *The amount of bending depends on the angle at which the wave strikes.*

Fading

And now we are ready to take up *fading*. As the curtain rises on this drama, we see the transmitting antenna. The ground wave is saying to the sky wave, "You take the high road and I'll take the low road, and I'll get there before you." It is this choice of paths from the transmitter to the receiving location that causes trouble.

If the receiver is near the transmitter, reception is dominated by the ground wave and is not affected by sky waves from the ionosphere. As the distance from the transmitter increases, the ground wave grows weaker until it cannot be heard. At this point and beyond, the station cannot be received in the daytime. At night the waves "reflected" from the ionized layers permits reception.

Where the sky wave and ground wave are received equally well, we have an area of bad fading. Since the two portions of the same signal cover different distances, they may arrive with a difference in "phasing" that will cause them to add or to buck one another. In the first case, the resulting signal will become stronger; in the latter the two portions may so cancel that nothing

can be heard. Since the path the sky wave travels changes with shifts in the height and ionization of the refracting layer, the signal may vary between these two extremes.

You might think that once the receiving station was beyond the reach of the ground wave, fading would end, but such is not always the case. The wave-bending ionosphere is unstable and the path of a wave through this ionosphere is constantly changing. At one time the receiver may be getting the full intensity of the refracted wave, while a few minutes later this center of intensity may have shifted miles away.

What is worse, the sideband frequencies of the wave may travel different paths in the ionosphere and when they arrive at the receiver the phase of these intelligence-carrying sidebands may be different from what they were at the transmitter. Music or voice may be garbled by the interaction of these out-of-phase sidebands. This brand of fading accompanied by distortion is called "selective fading."

Automatic volume control

The cure for fading, once found, was simple. *Automatic volume control* was the poor name selected for it—"poor" because any attempt to hold the volume at a constant level, making the whisper of the flute as loud as the bellow of the tuba, would result in amplitude distortion. What was done was to make the r.f. sensitivity of the receiver inversely proportional to the intensity of the signal. As the signal intensity goes up, the receiver sensitivity goes down, and *vice versa*. The result is that the signal delivered to the detector is practically independent of variations in the strength of the received signal. A. v. c. will not cure the "selective" type of fading, however.

Control is secured by varying the bias voltage applied to the r.f., mixer, and i.f. stages. As the negative bias on the grids of these tubes is increased, their ability to amplify is decreased, and the sensitivity of the receiver is reduced. Since we want this bias voltage to rise and fall with the strength of the received signal, the best place to get such a control voltage is from the signal itself.

Fig. 2304 shows how this is done. The diagram inside the dotted lines is the diode detector. Rectifying action of the diode causes three simultaneous events to happen in this circuit: (1) pulses of rectified r.f. carrier current come down through L1 and are filtered by R1, C1 and C2. (2) audio fluctuations of the

demodulated carrier appear across R2 and are transferred to the volume control by the coupling capacitor; and (3) the rectified current going to ground through R2 produces a voltage drop across the resistor. This last voltage is the one we are interested in.

The d.c. voltage drop across R2 is produced by rectifying the carrier envelope; so it is directly proportional to the amplitude of the carrier. If this amplitude increases, point A becomes more negative with respect to ground; if it decreases — another way of saying the signal intensity goes down — point A becomes less negative.

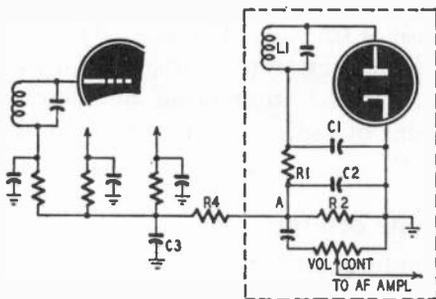


Fig. 2304. A detector circuit with *avc*.

Before this controlling voltage can be used, we must comb out the a.f. variations still present at point A. This is done by means of filter R4-C3.

The values of this resistor and capacitor are carefully chosen and should not be changed. When a capacitor charges and discharges through a resistor, the time required for the voltage to build up and fall depends upon the values of the two components. What we want is a combination that will be too slow to follow the voltage variations caused by the lowest audio frequency but fast enough to let the system have time to “recover” when we tune our set. Otherwise, when tuning from a strong station past a weak one, the sensitivity of the receiver might not have time to adjust itself after leaving the strong station, and the weak station would not be heard. The usual time constant is 0.1 second.

This negative voltage is fed to the grids of the controlled tubes through resistors that prevent coupling between the grid circuits. Tubes controlled by a.v.c. are the “remote-cutoff” type. These tubes are provided with a certain amount of minimum fixed bias

— such as cathode bias — so that the plate current does not become excessive when no a.v.c. voltage is being produced.

Delayed A.V.C.

In ordinary a.v.c., controlling action starts on the weakest signal and reduces the gain of the receiver when increased sensitivity would really help. "Delayed a.v.c.," as diagrammed in Fig. 2305, shows the circuit for overcoming this problem. Diode D1 is used for detection. The i.f. signal is also applied, through C1, to D2. The cathode of D2 is positive with respect to ground, which

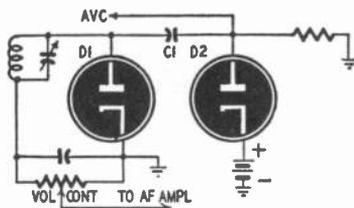


Fig. 2305. A basic delayed *avc* circuit.

makes the plate negative with respect to the cathode. As long as the peak amplitude of the i.f. signal applied to D2 is less than this bias voltage, there will be no rectification, and no a.v.c. voltage. As soon as the peak i.f. voltage rises above this bias voltage, rectification begins and the a.v.c. voltage is developed.

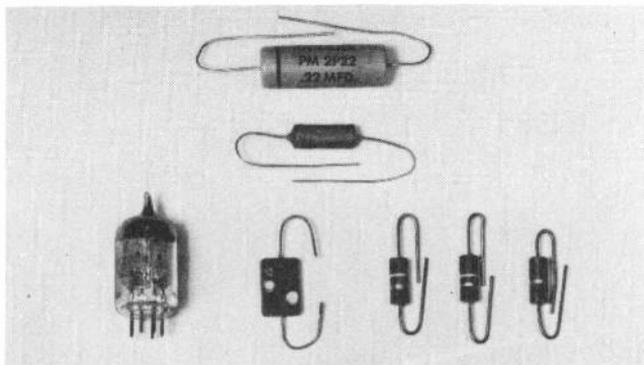


Fig. 2306. Only a few components are necessary for a complete *a.v.c.* system. (Allied Radio Corp.)

A. V. C. troubles

A.v.c. troubles are usually due to failures of capacitors, resistors, or diodes in the a.v.c. circuit. Since the voltages are fed to the grids

of the tubes through high-ohmage resistors, even a slightly leaky capacitor, will short-circuit the a.v.c. voltage.

A worse trouble is an intermittently leaky capacitor, which will produce its own type of fading. Where the complaint is "fading" or "intermittent," it is a good idea to replace all capacitors in the a.v.c. circuit and to make sure the resistors are not changing their value.

As shown in the photo, Fig. 2306, a few simple parts are required to form an a.v.c. system. A few resistors, a few capacitors, and a diode, are all that are necessary.

QUESTIONS

1. On the broadcast band, how far is ground-wave reception had?
2. What accounts for nighttime reception beyond this distance?
3. What returns sky waves to earth?
4. What happens to most broadcast-band sky waves during the daytime?
5. Why is fading particularly bad in the area reached by the ground wave?
6. What is *selective fading*?
7. Describe briefly how an *automatic volume-control* system works.
8. What kind of tubes should be used in stages controlled by a.v.c.?
9. What is *delayed a.v.c.*?
10. Why is delayed a.v.c. used?
11. Describe a delayed a.v.c. circuit.
12. What causes most a.v.c. troubles?

24

TRANSISTOR RADIOS

.....

TRANSISTOR radios have become increasingly popular during the past several years. At first glance, such a set as shown in Fig. 2401 may look radically different from the tube receivers we have been studying, but careful examination reduces the major differences to three: (1) transistors instead of tubes are used as amplifiers, frequency converters, oscillators and detectors; (2) transistor sets almost invariably employ printed circuit wiring, and (3) transistor receiver components are ordinarily much smaller and have ratings different than tube-receiver counterparts.

But in a transistor radio a capacitor is still a capacitor, a resistor is still a resistor, and a transformer is still a transformer. An electron continues to tread its habitual path through these parts arranged in the familiar superheterodyne circuit, just as it does in a tube set. It would seem, then, the only *new* information we need is a working knowledge of how a solid-state transistor manages to perform the same functions as a vacuum tube and a grasp of important mechanical differences in circuitry and parts.

This is close to the truth, but I would not mislead you into thinking a *complete* understanding of transistor theory, made up of half atomic physics and half electronics, is easily acquired. It is not. However, if we butter the new subject with what we already know, if we take it in small bites and if we chew each bite thoroughly, we shall manage to digest all the information

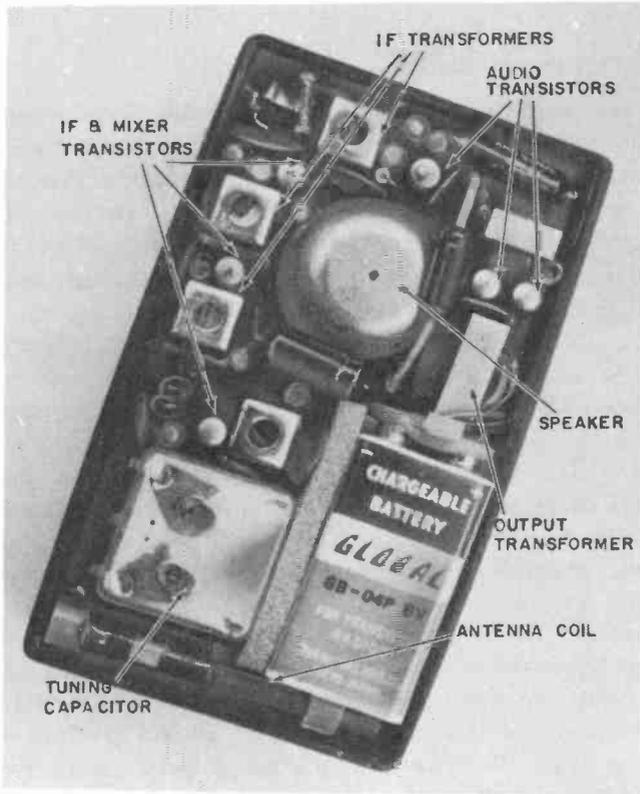


Fig. 2401. Typical arrangement of parts inside of a pocket transistor radio. The front view is at the left.

we need to understand how these receivers operate. Will you join me?

How transistors are made

Transistors, made of semiconductor materials such as germanium and silicon, are somewhere between the metals and insulators in their ability to conduct electricity. In its pure state, germanium presents a very high resistance to the passage of current. Each germanium crystal atom has four valence electrons in its outer shell. Each of these sort of "holds hands" with another valence electron belonging to one of four adjacent atoms. This hand-holding is called a *co-valent bond*, and the result is a nice, stable, tidy arrangement like a "couples only" party at which there are no stag electrons rattling around loose to carry a current.

Adding a little impurity lowers the resistance of the germanium. (I feel there is a moral in there somewhere.) Sometimes the impurity is arsenic, an atom that has five valence electrons. Four of these promptly form co-valent bonds with electrons in four adjacent germanium atoms, but the fifth electron is like the fellow caught in the center of a game of musical chairs: he has no place to sit down. So he wanders off, leaving his parent atom with a positive charge but locked in position, and his card reads: "Have negative charge, will travel." Travel he does when a potential is applied. Since arsenic-treated germanium has an excess of negatively charged electrons provided by the *donor* arsenic atoms, it is called *n-type*.

When the impurity is indium, we have an atom that has three valence electrons. Each of these forms a co-valent bond with an electron in an adjacent atom, and the electron needed to form the fourth co-valent bond is borrowed from another germanium atom. This leaves the lender with a *hole* in its atomic structure that gives it a positive charge. This hole can actually move through the doped germanium, creating a current. Since the current is made up of a movement of positively charged holes, this semiconductor material is called *p-type*.

Electrons and holes as current carriers

The idea of a *nothing*, like a hole, carrying a *something*, like an electric current, sort of gets you, doesn't it? Actually the concept is not quite so fantastic as it sounds. Picture a group of five

germanium atoms lined up in a row as shown in Fig. 2402. Nos. 1 through 4 each has a normal complement of four valence electrons, but No. 5 has been robbed of an electron by an *acceptor* indium atom that needed it to make a fourth at co-valent bond-

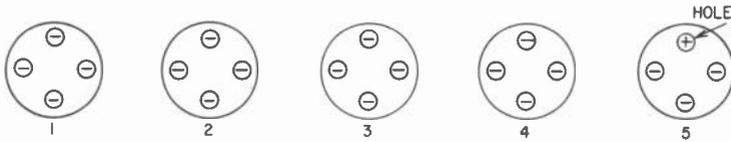


Fig. 2402. How a "hole" moves through a semiconductor.

ing. Keep in mind that an atom with all its electrons has a neutral charge, but losing an electron leaves it with a positive charge.

Now suppose No. 5 steals an electron from No. 4. The "hole" and its accompanying positive charge moves from No. 5 to No. 4. In the same way, the hole can move through No. 3 and No. 2 and reach No. 1. No electron moved more than the distance of one atom, yet our positively charged hole moved from the right end of the line clear to the left. Just as a movement of free negative electrons can carry a current through n-type material, so can a movement of free positive holes carry a current through p-type material. When a hole and a free electron collide, they unite in a process termed *recombination*, and both cease to exist as free charge carriers.

Now we are ready to see what happens when we combine these two types of material in the same crystal structure called a germanium diode. As shown in Fig. 2403, the p-type terminal is called the anode and the n-type terminal the cathode. Fig. 2403-a shows the diode with a battery applying *reverse* bias to its terminals. The holes in the p-region are attracted from the junction to the negative terminal, and the free electrons in the n-region are attracted to the positive terminal. The result is few carriers reach and cross the junction; so little reverse or *leakage* current flows through the rectifier even when the applied voltage is comparatively large. However, if we keep pushing this voltage up, we eventually reach a *breakdown* or *avalanche* voltage that gives the leakage electrons crossing the junction enough energy to create new electron-hole pairs by collision. This process mush-

rooms, and the current, fattening upon the multiplying current carriers, will destroy the rectifier if not limited by external circuitry.

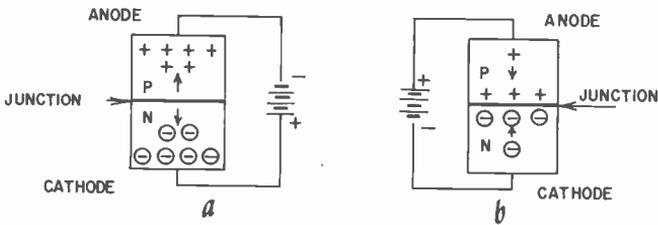


Fig. 2403. Electron arrangement in a diode with reverse-bias (a) and forward bias (b).

At Fig. 2403-b we see the same rectifier connected in the *forward* bias or conducting manner. Now the positive holes are repelled by the positive anode, and the free electrons are repelled by the negative cathode. Both move across the junction and recombine with their opposites. Electrons are siphoned off by the positive anode and move around through the battery. Holes thus created move down to replace those crossing the junction. Negative electrons feed in from the cathode to replace those crossing the junction. Thus a considerable current flows through the diode even with a very small applied voltage. Keeping the action of both bias states in mind, we see that, if an a.c. voltage is applied to the diode, current will flow through it in d.c. pulses during alternate half-cycles, just as happens when this voltage is applied to a tube diode.

Inside the transistor

Finally we are ready to tackle the junction-transistor “sandwiches” shown in Fig. 2404. Fig. 2404-a shows a thin layer of p-type material between two n-type layers. This is called an n-p-n transistor. The position of the layers is reversed in Fig. 2404-b to form a p-n-p transistor. In either case, one of the outside layers is called the *emitter*, the other is called the *collector*, and the center layer is termed the *base*. Potentials are applied so the emitter-base junction is forward-biased and the collector-

base junction is reverse-biased. Let's see what happens in Fig. 2404-a under these conditions.

Electrons are injected from the emitter into the base region. A few of these recombine with holes in the base material to constitute a small base current, but most of them continue right on through the very thin base layer into the collector region


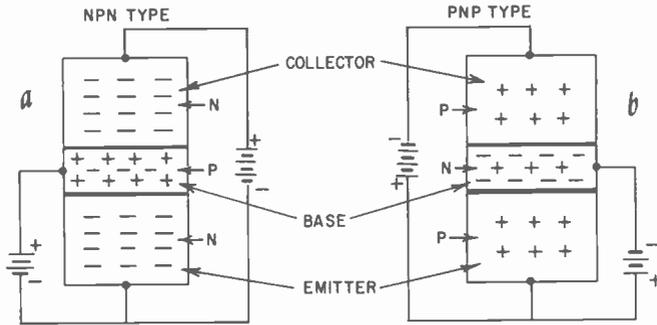


Fig. 2404. *N-p-n* transistor (a) and *p-n-p* transistor (b).

where they are attracted by the high positive collector voltage and flow back through the collector battery to the emitter. If all the electrons injected by the emitter into the base managed to reach the collector, the transistor's *alpha* (ratio of a change in collector current to the change in emitter current producing it) would be 1; but since some of the electrons recombine with holes in the base region, this ideal is not reached. Practical values of *alpha*, which is similar to the *mu* of a tube, range from 0.80 to 0.999 in commercial junction transistors. The p-n-p transistor of Fig. 2404-b acts in the same manner except that the injected current carriers from the emitter are holes that pass through the n-type base to the negatively charged collector terminal.

Keep in mind a very small change in emitter-base potential produces a large change in the number of carriers emitted into the base region, and collector current depends directly upon the availability of these carriers there. In other words, emitter current, corresponding to base-emitter voltage, exerts a "valving" action on collector current in the same way grid potential affects the plate current of a tube.

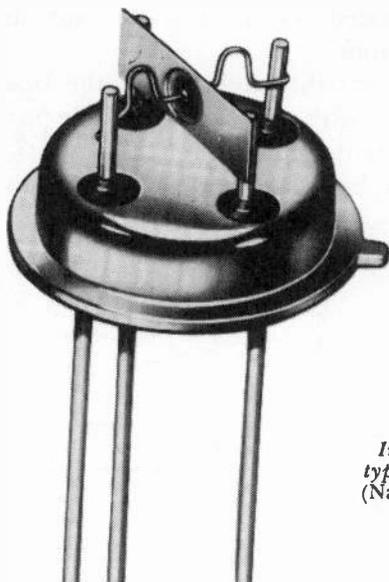

Internal view of one of many types of transistor construction. (National Semiconductor Corp.)

A transistor is a three-terminal affair, and input and output circuits can be arranged in a variety of ways to obtain totally different sets of characteristics. An emitter arrow pointing toward the base indicates a p-n-p transistor; an emitter arrow pointing away from the base designates an n-p-n type. (Fig. 2405).


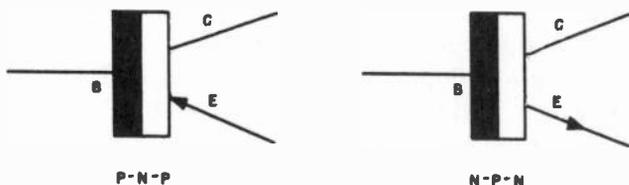


Fig. 2405. Electronic symbols for p-n-p and n-p-n transistors.

Where transistors get their gain

When you look at the grounded emitter circuit of Fig. 2406-a, you may wonder how it can achieve voltage and power amplification when the emitter current modulated by the signal is actu-


CIRCUIT CONFIGURATION

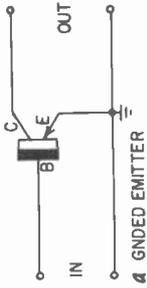



Moderate input impedance
 Moderate output impedance
 High current gain
 High voltage gain
 Highest power gain

GENERAL CHARACTERISTICS

CIRCUIT CONFIGURATION

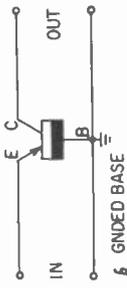

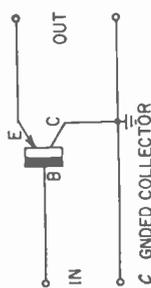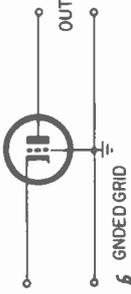Lowest input impedance
 Highest output impedance
 Low current gain
 High voltage gain
 Moderate power gain



Highest input impedance
 Lowest output impedance
 High current gain
 Unity voltage gain
 Lowest power gain

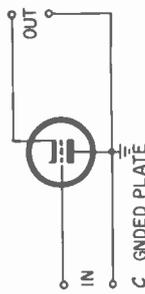


Fig. 2406. Transistor amplifier configurations with equivalent tube circuits. Can be used with either p-n-p or n-p-n types.

ally greater than the output collector current. The answer lies in the difference between input and output impedances. The signal is introduced between emitter and base. This junction is forward biased, draws comparatively more current with a low bias voltage, and so has a low resistance and low impedance. The collector junction is reverse-biased, draws less current with much higher voltage, and so has a high resistive impedance requiring a high value of load resistance to match it.


In a typical arrangement, an input signal of .02 volt rms across 400 ohms impedance will cause collector-current fluctuations that will develop 1.6 volts rms across a 10,000-ohm collector load resistor. That is a voltage amplification of 80. Using the power formula $W = E^2/R$ on both input and output circuits, we find the input power is 0.000,001 watt and the output power is 0.000,256 watt for a power gain of 256. A mouthful of air can blow out a candle with a single gentle puff, but forcing that same mouthful of air into a tight balloon takes a lot of effort. That is the difference between an equal amount of "current" flowing in a low-impedance and in a high-impedance circuit.

This is by no means the whole transistor story. Entire books have been written on the construction and performance of various types of transistors, such as the mesa, drift, surface barrier, tetrode and Unijunction, not to mention their near relatives, the silicon-controlled rectifier and the tunnel diode. But we have mastered the basic principles of transistors. We know they can amplify — and therefore oscillate. We know the nonlinear nature of their junctions can provide rectification, detection and mixing action. Let's see how they do their stuff in a practical radio.

Transistor receiver circuits

Fig. 2407 is the circuit of a typical transistor receiver. It has an n-p-n autodyne converter that acts as a combination local oscillator and mixer, two n-p-n transistor i.f. stages, a diode detector, a p-n-p audio driver, and two p-n-p transistors in a push-pull output stage. Note how low-impedance untuned secondaries are used on the antenna and i.f. transformers to match the low input impedances of the transistors. Observe, also, that C10, an audio coupling capacitor, is a 6 μ f 6-volt electrolytic instead of the .01 paper capacitor found here with a high-input-impedance tube.

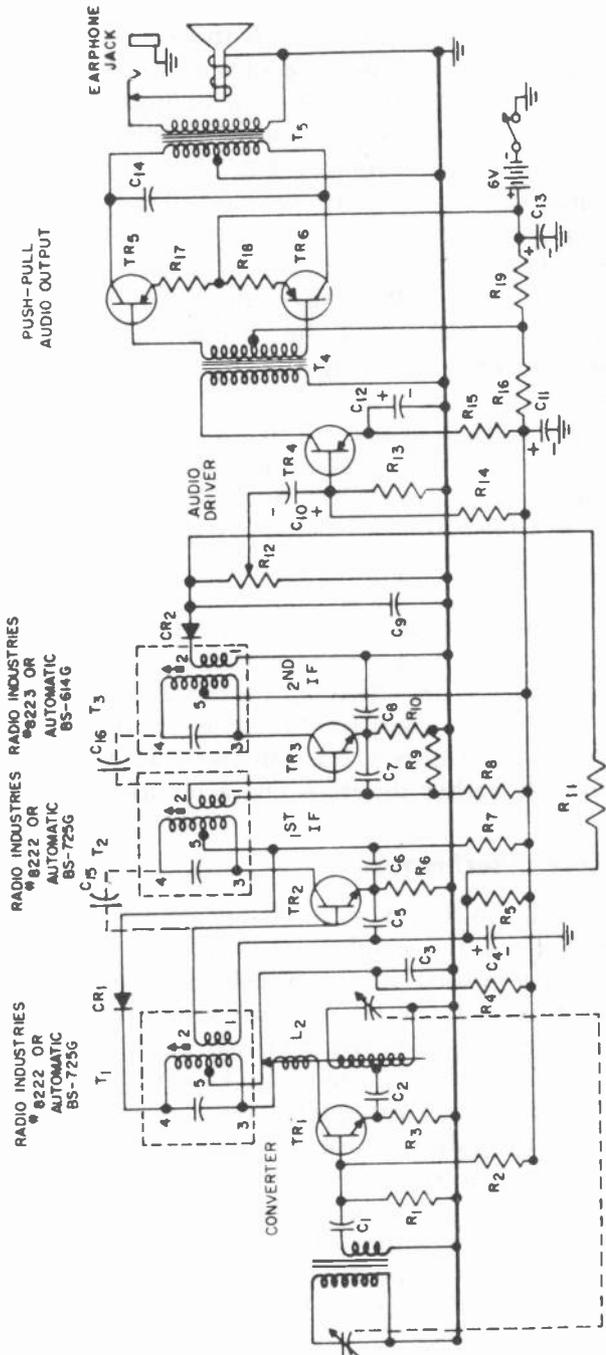Signal current rectified by CR2 and flowing to ground through



RADIO INDUSTRIES
8222 OR
AUTOMATIC
BS-725G

RADIO INDUSTRIES
8223 OR
AUTOMATIC
BS-614G

PUSH-PULL
AUDIO OUTPUT

- | | | | |
|-----------------|-----------------------------|-----------------|---------------------|
| R1, R8, _____ | 10,000 ohms | CR1, CR2, _____ | IN64G or equiv. |
| R2, _____ | 15,000 ohms | TR1, _____ | G-E 2N1087 |
| R3, _____ | 500 ohms | TR2, _____ | G-E 2N293 |
| R4, _____ | 270 ohms | TR3, _____ | G-E 2N169 or 2N1121 |
| R5, _____ | 47,000 ohms | TR4, _____ | G-E 2N192 or 2N324 |
| R6, _____ | 27,000 ohms | TR5, TR6, _____ | G-E 2N188A or 2N320 |
| R7, R9, _____ | 2,200 ohms | T4 = _____ | 3600Ω/2000Ω CT |
| R10, _____ | 1,000 ohms | T5 = _____ | 3600Ω CT/VC |
| R11, R14, _____ | 4,700 ohms | T1, T2, _____ | Interstage II |
| R12, _____ | 10,000 ohm 1/2w audio taper | T3, _____ | Output II |
| | | C15, C16, _____ | Neut Cap (See Text) |

- | | |
|-------------------------------|------------|
| R13, _____ | 68,000 ohm |
| R15, _____ | 470 ohm |
| R16, _____ | 100 ohm |
| R17, R18, _____ | 8.2 ohm |
| R19, _____ | 33 ohm |
| C1, _____ | .02μf |
| C2, C3, C5, C6, C7, C8, _____ | .01μf |
| C4, C10, _____ | 6μf-6v |
| C7, _____ | .05μf |
| C9, _____ | 50μf-12v |
| C11, C12, C13, _____ | .2μf |
| C14, _____ | .2μf |

Fig. 2407. Representative circuit of a six-transistor broadcast receiver. (General Electric Co.)

the volume control develops a positive voltage proportional to the strength of the received signal. This positive voltage fed to the base of the first i.f. transistor reduces both the emitter current and the gain of that transistor. Because of leakage current, a transistor cannot be cut completely off by this method; so the diode CR1 is used to bolster the a.v.c. action. This diode connects voltage-wise between the collectors of TR1 and TR2 and signal-wise across the major portion of the primary of T1. With weak signals, the voltages across R4 and R7 reverse-bias the diode so it exerts no influence. However, when strong-signal a.v.c. action reduces the collector current of TR2, the voltages shift so the diode conducts and acts as an increasingly heavy shunt across the i.f. transformer primary, greatly reducing the signal fed to the second i.f. transistor.

Rate-grown n-p-n transistors shown here provide a stable, non-oscillating i.f. amplifier without neutralization, but this is not the case with p-n-p alloy transistors. They must be neutralized by adding C15 and C16, shown in dotted lines. Actual values of these capacitors will depend on the collector capacitances of the transistors.

Capacitors used in transistor radios are usually larger in capacity, lower in voltage rating and much smaller in size than tube-radio capacitors. Resistors are often $\frac{1}{4}$ watt. Speakers and tuning capacitors are much more compact. Coils, i.f. transformers and audio transformers are not only a fraction the size of tube-receiver types but have altogether different characteristics.

Printed circuits and service techniques

Printed-circuit wiring is produced in a variety of ways, but essentially it consists of metal-foil conductors bonded to an insulating board. Parts are mounted on the board and connected to appropriate points of the foil-conductor maze. Circuit-tracing a crowded transistor printed-circuit board is virtually impossible, and a "wiring diagram" that lists important check points on the printed circuit is a near necessity. Fortunately, these are available from set manufacturers and publishers of service data.

Resistance-checking of transistor radios is misleading at best and can be damaging. It is misleading because transistors and electrolytic capacitors connected across various portions of the circuit are *polarized* devices that display radically different resistances with different polarity of the ohmmeter probes. Even if the

transistors are removed from their sockets, the ohmmeter voltage may damage low-voltage electrolytic capacitors with reverse-polarity current. If accurate voltage data are at hand, careful voltage checks with a low-range v.t.v.m. will often localize trouble. Signal injection and signal-tracing are excellent techniques for pinpointing defects in transistor radios.

You have been told to suspect tubes the very first thing, but a bad transistor is the *last* thing you look for. Transistors are as tough as Job and as long-lived as Methuselah — unless they are abused. Weak batteries, leaky capacitors, tiny cracks in printed-circuit leads, poor connections, open or changed-value resistors, and printed circuits that are corroded and partially shorted by acid leaking from spent batteries — these are the most common causes of trouble in transistor receivers.

Be careful in replacing parts on a printed circuit. Too much heat will loosen the bond between foil and board. A pencil-type soldering iron helps prevent this and also is excellent for working in the tight corners of these small receivers.

QUESTIONS

1. List three major differences between transistor and tube radios.
2. What is a *semiconductor* material?
3. What is *n-type germanium*?
4. What is *p-type germanium*?
5. Explain how a movement of *holes* can constitute an electric current.
6. Define *avalanche voltage*.
7. Describe the makeup and operation of a junction transistor.
8. Define *emitter, collector, base, alpha*.
9. What is the difference between an n-p-n and a p-n-p transistor?
10. How, in a transistor in which input current is greater than output current, is it possible to achieve voltage and power amplification?

25

INSTRUMENTS AND TOOLS

• • • • •

RADIO servicing equipment falls into two classifications: trouble-locating tools and trouble-repairing tools. First consider those used to find the causes of receiver failure. These trouble-detecting devices are essentially "electronic"; that is, they are actuated by or produce voltages and currents that are, in turn, manifestations of electron behavior.

A versatile instrument

The old standby of the technician is the volt-ohm-milliammeter abbreviated v.o.m. This instrument is a low-current meter that can be switched into suitable circuits for measuring alternating or direct voltages, direct current, or resistance. Various ranges are ordinarily provided. For example, a typical v.o.m. has the following ranges for indicating d.c. milliamperes, d.c. volts, or a.c. volts: 0 to 5, 25, 125, 250, 500, 1,250. The ohms scale run: 0 to 2,000, 20,000, 200,000, 2,000,000 and 20,000,000.

A choice of several ranges is an aid to accuracy. Service instruments are usually rated at an accuracy of 2% of the full-scale reading. That means the permissible error on the 1,250-volt scale is 25 volts; but on the 125-volt scale is only 2.5 volts. To insure accuracy, the value being read should be at least 50% of the full-scale reading of the meter. This can be arranged with a wide variety of values to be measured, by having several meter ranges available.

Fig. 2501 shows the basic circuits of a d.c. milliammeter, a d.c. voltmeter, an a.c. voltmeter, and a d.c. ohmmeter, respectively.

The meter itself (M in the diagrams) is a d.c. meter with a sensitivity such that 1 ma of current will make it read full-scale.

In Fig. 2501-a, all the current passing through the probes must also pass through the meter. The maximum current that can be measured is that of the meter rating. It is possible, as indicated, to switch *shunt* resistors across the meter so that the probe current can divide, part going through the shunt resistor and part through the meter. By proportioning the resistance of the shunt to that of the meter, we can allow any desired fraction of the total current to flow through the meter.

For example, if our meter has a resistance of 45 ohms and the shunt has a resistance of 5 ohms, 9/10 of the probe current will go through the shunt and 1/10 through the milliammeter. Every reading on our shunted meter scale now indicates exactly 10 times the amount of current flowing in the probes. We can arrange a new scale to show this amount. With shunts of decreasing resistance, the meter will indicate increasing ranges of current.

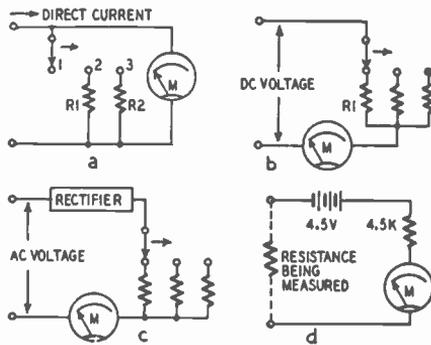


Fig. 2501. The four basic v.o.m. circuits.

In the voltmeter circuit of 2501-b, suppose R1 is 5,000 ohms. Neglecting the small resistance of the meter, 5 volts across the probes will send 1 ma of current through the meter, 2.5 volts will send 0.5 ma, etc. The current through the meter varies directly with the voltage across the probes. If we increase the value of the series resistance to 50,000 ohms, 50 volts will be needed to make a new scale in which meter current is translated into volts-across-the-probes, and we have a *voltmeter*. Increasing the range of the voltmeter is simply a matter of increasing the value of series resistance.

Measuring a.c. looks as though it might present a problem (since our meter will react only to d.c.), but it really isn't. We

put in a rectifier; it jerks the zig-zag out of the a.c. and makes it over into d.c. that our meter can handle. By employing proper values of resistance in Fig. 2501-c, our current-reading meter can be made to indicate the r.m.s. value of an a.c. voltage across the test prods.

Fig. 2501-d is a simplified ohmmeter. It consists of a battery, a fixed resistance, our meter, and a pair of test prods all in series. Suppose our battery is 4.5 volts and the resistor is 4,500 ohms. When our prods are shorted together the battery sends 1 ma of current through the meter, making the pointer swing over to the full-scale mark, which we label "0 ohms." Now, if we place a resistor between the probes, the current will be reduced and our pointer will not swing so far. The meter scale can be marked so that the pointer will indicate the exact value of resistance between the probes. Ohmmeters actually used in v.o.m. circuits are not this simple, but follow the same principle.

A v.o.m. used as a voltmeter has one serious objection: it draws appreciable current from the circuit being tested. Consider the typical screen-supply circuit of Fig. 2502. The screen draws 1.5 ma and is fed through a resistor of 100,000 ohms from a 250-volt source. If we try to measure the screen voltage with our voltmeter, the current used by the meter will have to be added to that already flowing through the dropping resistor. Even if this current is only 0.5 ma, its value added to the 1.5 ma drawn by the screen will reduce the normal screen voltage of 100 to an *indicated voltage* of 50. Therefore multimeters with 10 to 50 μ a movements are popular.

Other trouble finders

The vacuum-tube voltmeter, abbreviated v.t.v.m., goes even further to correct this. Basically, it employs the amplifying properties of a vacuum tube so that the voltage being measured is applied to the grid of a tube with the current-reading meter in the plate circuit. Since no current flows in the grid circuit, no power is absorbed from the circuit being tested, and a more accurate indication of voltage is had. The v.t.v.m. can measure resistance values up to one billion ohms, and it is practically impossible to injure the meter by employing too low a range for measuring a voltage — an easily made mistake that has sent many a v.o.m. to its last windup!

The v.t.v.m. has two main disadvantages: most v.t.v.m.'s will not measure current, and all of them must have their vacuum

tubes supplied with power from the power line or from batteries.

The signal generator is another important service instrument. Essentially it is a tiny transmitter that will produce an r.f. signal of the desired frequency. This signal can be used in its pure r.f. form or with 400-cycle tone modulation, and its strength can be varied from zero to a value stronger than would be put into a receiver by a powerful transmitter. The signal generator can produce the proper signal for exciting any stage of a receiver. It is absolutely necessary for the proper alignment of the i.f. stages of a superheterodyne receiver! A good signal generator is one whose dial readings of frequency are accurate and stable, whose output can be thoroughly controlled, and whose construction is such that it will retain these virtues year after year.

Some technicians insist that a tube tester is not a service instrument—it is just to sell tubes! They mean that a good technician can quickly spot an under-par tube by its effect on the receiver itself. While that is partly true, a tube checker often permits the discovery of a bad tube without removing the chassis from the cabinet; furthermore, the public has a childlike faith in tube testers and is suspicious of a service technician without one.

These instruments vary in price and in simplicity of operation. None will do a 100% job of revealing tube shortcomings; but even a low-priced tester will reveal 95% of the bad tubes. Thanks to the stream of tubes hatched up by tube engineers, a tube checker becomes out of date faster than a risqué story at a salesman's convention. That is why many technicians are slow to buy expensive types of testers, preferring to use tube substitution to reveal the few defective tubes that a low-priced tester will not catch.

Another electronic bloodhound is the signal tracer. This instrument consists of a high-gain audio amplifier preceded by a probe that provides either an isolating resistor or a detecting device at its business end. This detector may be a vacuum tube or a germanium crystal, but its purpose is to strip the modulation from any r.f. signal it encounters. The modulation can then be handled by the amplifier and heard in the tracer speaker. With such an instrument a strong modulated signal can be followed

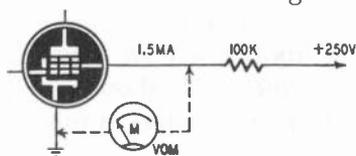


Fig. 2502. The v.o.m. type voltmeter cannot be used in high-resistance circuits.

stage by stage through the receiver from antenna to speaker. The stage where trouble starts is thus revealed, and then the v.o.m. or v.t.v.m. can take it from there.

Other tools you need

The radio technician can never have too many screwdrivers. He needs them in all sizes from the tiny, long-bladed job used to loosen stubborn deep-set screws to the stubby, broad-bitted driver for tightening large chassis bolts. A good mechanic always selects the proper-sized screwdriver for use on a particular screw-head, and he *must* have the proper driver for use on Phillip's screws. He should have a driver with a screw-holding feature for placing screws and bolts in the cramped quarters found in radio work; and he must have several special-insulation aligning screwdrivers for adjusting i.f. and r.f. trimmers.

A good set of hex-nut drivers is another required tool. The walls of the sockets should be thin so that the wrench may be slipped over a nut in a tight spot, and the stems should be hollow so that the wrenches can be used to tighten nuts on the extra-long machine screws and control shafts that are often used. A set of small open end wrenches are fine for working in places that will not allow a hex-nut driver to be used. A small adjustable wrench should be available for handling non standard nuts that are encountered in radio work. A 1-inch vice-grip wrench is excellent for this purpose, for it can also serve as a small vise to hold parts together while being soldered.

Every service bench should have a pair of lineman's pliers, needlenose pliers, flat-nose pliers, ignition pliers, and eyebrow tweezers. Jobs will be found in service work that only one of these tools can do.

What electric clippers are to the barber the electric soldering iron is to the service technician, and he should have good ones. Service technicians today use a solder gun for their work. These irons have many desirable features. They are quick heating, always ready for action. Every service shop also needs a heavy-duty iron of 200 watts for chassis soldering and for other jobs requiring lots of heat. A pencil type iron is excellent for working on transistor radios and other printed or miniature circuits.

There are many miscellaneous tools used in service work: speaker shims for centering speaker voice coils about pole pieces; wire-strippers for removing insulation from wires; a metal (hack) saw for cutting volume-control shafts; a pair of good sharp,

diagonal cutters that will bite a wire cleanly in two; an electric drill to drill out rivets and make holes in the chassis; chemicals for cleaning volume controls, switch contacts, etc.; cement for repairing speaker cones and for fastening coil turns; and thinners for softening these cements when necessary.



Fig. 2503. *Basic equipment needed to begin a radio repair business.*

If you are going to do auto-radio servicing you will need a way of powering these sets on the bench; either a battery-and-charger combination or a battery substitute powered from the light line. There are such things as capacitor checkers, audio generators, cathode-ray oscilloscopes, etc., that are fine to have and which can be useful after you have acquired enough money to buy them, but you do not need them to start in business. Put the rest of your capital in a good set of service manuals. The manuals will give you more help than a room full of "advanced" servicing instruments when you are starting in business — and for some time thereafter, too.

Fig. 2503 illustrates some of the tools and test instruments used by the service technician. The tool in the center foreground is a wire stripper. With the screwdrivers, diagonal cutters, long-nose pliers, hex-nut drivers and open-end wrenches form a *basic* collection of hand tools. In the upper right is a versatile signal generator that can also be used for an inductance and capacitance checker, among other things. The v.t.v.m. will check resistance, hence, all three basic components for all radio servicing can be tested.

26

SERVICING TECHNIQUES

.....

“**S**ERVICE technique” is the hoity-toity phrase used to describe something that is as essential to a service technician as a skimpy bathing suit is to a beauty contestant. The service technician may be the best brain in the business, and he may have the most completely equipped shop in these United States; but unless he can actually put those brains and that equipment to work servicing radios speedily and well, he is not going to offer much competition to the other boys in the game. In the words of the song: “It’s what you do with what you got that counts”; and what-you-do-with-what-you-got is just another name for your service technique. It is the *way* you go about locating and repairing receiver faults.

Strictly speaking, the important part of the technique is the procedure employed in trouble-shooting, for locating the trouble is by far the most important work that the technician performs. It is the part of his job that requires the most time, training, and equipment, the part for which the major portion of the service charge is really made. Actual repairing is usually simply a matter of snipping out a defective part and soldering in a new one; but even the best of technicians will occasionally sweat blood determining just which of the vast number of parts in a large receiver needs this replacement treatment.

Trouble-shooting methods

Down through the years several different systems of trouble-shooting have enjoyed popular favor. Each of these systems is

important enough so that every technician should thoroughly understand and be able to practice all of them.

Voltage measurement

“Voltage measurement” is probably the long-time favorite system with most radiomen. It is based on the assumption that most troubles that afflict a radio — such as open resistors or coils and shorted capacitors — cause changes to occur in the voltages applied to the various tube elements. If the voltages present at the tube sockets are carefully checked against the voltages that *should* be there, any discrepancy will point the finger of guilt directly at the defective part.

Take the example of the single-tube output stage diagrammed in Fig. 2601. All voltages are measured with respect to ground. A positive voltage on the grid would indicate that C1 was partially shorted or leaky. No voltage on the plate would mean that C2 was shorted or the primary of T1 was open. No voltage on either the plate or screen would mean that C4 was shorted or that there was some trouble in the B-plus supply. If the cathode voltage is exceptionally high, R3 must be open; if too low, C3 is probably leaky, etc.

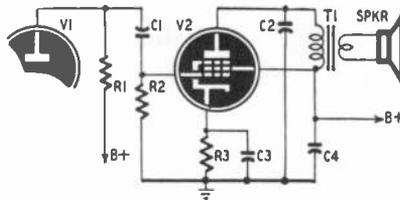


Fig. 2601. A single-tube output circuit.

One trouble with this system is that the user must know what voltages should be present on each tube element. A general idea may be obtained from the recommended voltages given in a tube manual; but a much better source of this information is a voltage chart prepared either by the manufacturer or by the publisher of service manuals. Of course, after years of experience, the technician learns to know what voltages may be reasonably expected at the tube sockets of simple receivers; but even the experienced technician prefers to work from a service manual in performing his voltage measurements. The voltage measurement system at work is illustrated in Fig. 2602.

Another objection to the voltage measuring system is that the set must be turned on while the checks are made. That means if there is a serious short in the receiver, some component may be overheating during this time.

Resistance measurement

“Resistance measurement” overcomes this last objection, for it can be carried on while the set is unplugged from the line. It assumes that most radio troubles upset the resistance values normally present between each socket lug and the ground or from one socket lug to another. For example, referring again to Fig. 2601, if C1 is shorted, an ohmmeter will quickly reveal it when a check is made from the plate of V1 to the grid of V2. A very low resistance from plate to ground means that C2 is shorted; and a zero resistance from screen to ground indicates that C4 is ditto. Infinite resistance between plate and screen points to the primary of T1 being open. A resistance check from cathode to ground will instantly show if R3 is open or if R3 is shorted.

Service manuals indicate the normal resistance from each tube pin to ground in the same way that they give the proper voltage at each socket connection. The service manual is even more important in resistance measurement than it is in voltage measurement, because the tube manual cannot help here. Both of these methods fall down completely when it comes to showing up such defects as “open” capacitors that produce no change in resistance or voltage.

Circuit disturbance testing

One of the oldest methods of trouble-shooting is now dignified by the name of “circuit disturbance testing.” We used to call it simply “touching the grid caps or pulling the tubes.” In this system the grids of the tubes were touched with a metallic object, such as a screw-driver blade, or a tube was pulled from its socket while the radio was turned on. If the portion of the receiver between that particular tube and the speaker was functioning normally, a loud “click” would be heard whenever the plate circuit was broken by removing the tube; or, if the tube was amplifying normally, by the surge sent through the tube by disturbing the grid circuit. By starting at the output stage and proceeding toward the antenna end of the set and noting at just which stage no click could be heard, a fairly good idea was obtained as to where the trouble was. The voltage measurement

or the resistance measurement system could be brought into play to pin-point the defect.

While this method is fast and simple and requires no extra equipment, it has a number of disadvantages. For one thing, most modern tubes are of the single-ended type with the grids beneath the chassis; and it is much more difficult to reach them there than it was when they were at the top of the tube. Then, too, the system is not very practical with a.c.-d.c. sets that have all of the tube filaments connected in series. Removing any tube in such a set will usually cause a click in the speaker, since removing a tube is equivalent to turning off the set. Another disadvantage is that this method gives only a very rough idea of where the trouble is. You still have to use another method to run down the defective part.

Signal injection system

An improvement on the rather crude circuit disturbance method is the "signal injection" system. In this procedure, a signal of the proper nature is placed upon each grid, starting at the output stage and moving toward the front of the receiver. For example, a 400-cycle note from a signal generator is used on the grids of the audio stages, the i.f. frequency is used on the intermediate stages, and the frequency to which the receiver is tuned is presented to the r.f. and mixer grids.

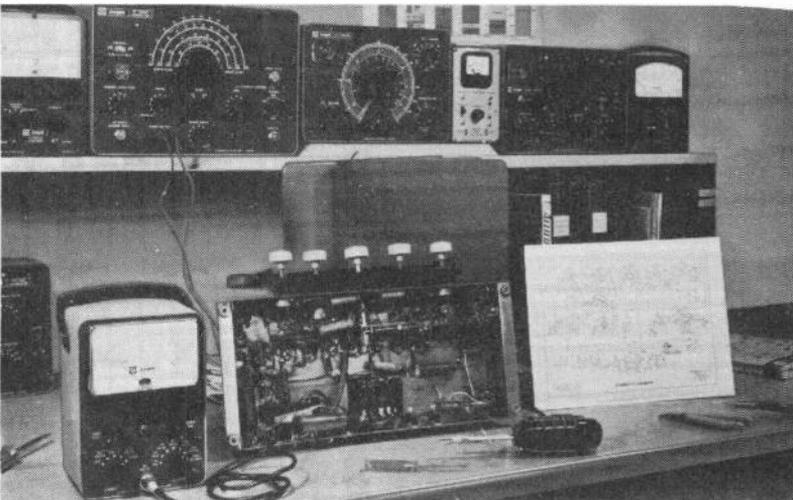


Fig. 2602. The voltage measurement system at work. Readings obtained on the v.t.v.m. are compared with the normal values given in the service manual.

By noting just where the signal ceases to pass through the set or where it becomes distorted, the operator can determine rather closely where the trouble is lurking. Again, though, the final finger-pointing has to be performed by the voltmeter or ohmmeter. However, this system would have revealed if C1 of Fig. 2601 was open. In that case, when the signal generator was placed on the grid side of the capacitor, the signal would have gone on through to the speaker; but when it was placed on the plate side, no signal would have been heard.

Signal tracing method

Another method with considerable favor is the "signal tracing" system. This method uses some form of detector—vacuum tube or crystal—mounted in the end of a probe which is connected to a high-gain audio amplifier. When this probe is touched to a point at which there is even a small amount of modulated r.f. energy, the modulation is detected and can be heard in the speaker of the signal-tracer amplifier. Provision is made so that plain audio frequencies can also be picked up by the probe.

The usual procedure in using the signal tracer is to feed a fairly strong modulated signal into the antenna of a receiver, either from a signal generator or from a strong local broadcast station, and then to trace the passage of this signal, step by step, down through the receiver until it suddenly disappears. By touching the probe first to the grid and then to the plate of a particular stage, not only will the presence or absence of the signal be noted, but also the actual amplification of the tube is revealed, both by the increase in signal as heard in the speaker and by the indication on a signal-strength meter that is built into many of the signal tracers. Furthermore, any noise or distortion originating in that particular stage instantly shows up.

While this system requires a specialized instrument, the writer strongly favors its use, especially by the beginning service technician. After you are experienced, you will be able, nine times out of ten, to make a very shrewd guess as to what is wrong with a receiver simply by listening to it; and then you can quickly double-check your suspicions by making only a few voltage or resistance checks. Until you get this experience, though, about all you can do with either of the first two methods discussed is to go doggedly through the set, measuring every socket connection until you find something wrong. That is a discouraging and

time-consuming business. It is much better to use a signal tracer to point out the particular stage in which the trouble starts and then use your voltmeter or ohmmeter to close in on the actual culprit. Even after you become a hot-shot technician, you will still find your signal tracer indispensable for running down noise, clearing up distortion, etc.

Use all methods

The good technician should regard trouble-shooting systems in the same way a gay bachelor feels about his feminine friends: he is familiar with all, but married to none. Any one of the systems, if followed persistently and exclusively, in the end will usually turn up a receiver fault; but the same thing can be done much more quickly and easily by using first one system and then another as convenience and the information at hand would seem to indicate.

Let us take a single example: Suppose you are using signal tracing and have followed the signal right up to the grid of the output tube of Fig. 2601 but do not hear any signal at the plate. Next you check the plate voltage and find there is none. This could be caused by either a shorted C2 or an open primary of T1; so next you check the resistance from plate to ground. If C2 is at fault, this resistance will be zero. If the primary is bad, the resistance shown will be infinite. In the latter event, a final "clincher" check can be made from plate to screen.

Had you stuck to voltage or resistance measurement exclusively, you might have checked every other socket connection in the set before finally stumbling on the plate of the output tube; but by using the signal tracer you were able to narrow your search down to this one stage in a few seconds. Then, by resorting to the other two trouble-shooting methods, you were able to decide, by making only two or three measurements, exactly what part needed replacing.

That is good servicing, for every measurement was made with a definite purpose in mind and was the direct outgrowth of a previous test. A good technician does little haphazard measuring. He realizes that the real trouble-shooting is actually done in the mind, and he uses his instruments merely to feed information and clues to his intellect. Instead of dabbing his test prods here and there without rhyme or reason, he spends a lot of time studying the circuit diagram, trying to match the symptoms exhibited by the receiver to possible component failures; and then he uses his

instruments to prove or disprove his studied guesses as to likely causes of the difficulty.

Screwdriver mechanics

Every now and then you will run across a radio technician whose boast is of the number of tools and test equipment he does *not* have. He will confidently tell you of the hundreds of sets he has fixed with a wet fingertip or an old screwdriver. He will conveniently forget to tell you about all the receivers he cannot fix, or the total number of call backs by irate customers.

On the other hand you will find the service technician who is instrument happy. His bench is so cluttered with every variety of service instrument that he has no room for repair work.

These two types are extremes. The first one tries to do all his servicing in his head to the complete exclusion of all test instruments. He does not realize that test equipment can either confirm a mental diagnosis, or reveal the trouble where mental gymnastics are just not enough. The second type of service technician believes that his test instruments can do his thinking for him—and that if he gets enough pieces of test equipment he will not have to do any thinking at all.

Fortunately, most successful service technicians steer a middle course. They realize that test instruments are essential—but so is a modest amount of thinking.

I confess it seems a dirty trick that *now* I tell you that you have to think to fix radios; but I was afraid that if I admitted this discouraging fact right in the beginning, before you learned how painless thinking can be when it is mixed with a little fun, you would quit me cold. However, now that you have waded through everything from Ohm's law to the theory of pentagrid converters, I have not the slightest hesitation in divulging that you will need more brains than solder in service work.

It is my hope that the chief aim of this book has been realized: to explain the basic principles of radio in the down-to-earth language that we ordinary fellows use and understand. While I have done my best to keep the promise that you were to become thoroughly acquainted with the appearance, function, and weaknesses of every component normally found in a radio receiver, the presentation of this material has been deliberately casual and not too serious in tone. The writer has always held with Lin Yutang that, "Seriousness, after all, is only a sign of effort, and effort is a sign of imperfect mastery."

INDEX

A

A-Battery	73, 101
A.C.	13
AC-DC Battery Supply	113
AC-DC Power Supply	109
Acceptor	199
Air Capacitor	39
Alpha	201
Alternating Current	13
Alternator	116
Ampere	14
Amplification	83
Amplification Factor	83, 95
Amplifier:	
Audio	136
Push-Pull	140
T.R.F.	155
Voltage	135
Anode	73
Antenna:	
Directional	183
Loop	183
Loopstick	183
Outside	183
Armstrong Oscillator	176
Audio:	
Amplifier	136
Choke	30
Distortion	139
Auto Radio, Hybrid	116
Auto-Radio Supply	115
Automatic Volume Control	191
Automatic Volume Control, Delayed	193
Avalanche Voltage	199
A.V.C.	191
A.V.C., Delayed	193
Average Voltage	106

B

B-Battery	73
B-Supply Rectifier	102
Baffle	123
Ballast Resistor	110
Bandwidth	161
Base	201
Bath tub Capacitor	41
Battery, A-	73, 101
Battery, B-	73, 101
Beam Vacuum Tube	90
Beat Frequency	165
Bias, Forward	200
Bias, Reverse	199
Bond, Co-valent	198
Breakdown	199
Buckling-Voltage	28

C

Capacitance	32
Capacitive Reactance	51
Capacitor:	
Air	39
Bath tub	41
Ceramic	43
Construction	37
Coupling	84
Dielectric	34

Capacitor: (Cont.)

Dry Electrolytic	42
Electrolytic	41
Etched-Foil	42
Fabricated Plate	42
Ganged	157
Input Filter	105
Leakage	37
Mica	40
Oil-Filled	41
Oxide Film	41
Padder	178
Paper	41
Polarized	43
Power Factor	37
Silver Mica	40
Tracking	158
Variable	40, 157
Capacitors	32, 39
Carbon	18
Carbon, Resistor	18
Carrier Envelope	146
Cathode	74, 79
Catwhisker	148
Ceramic Capacitor	43
Characteristic:	
Curve	95
Dynamic	97
Static	97
Charge, Space	80
Chart, Transistor Circuit Characteristics ..	204
Choke:	
Audio	30
Field Coil	109
Filter	30
Input Filter	105
R.F.	30
Chopper	116
Coil:	
Field	121
Loading of	60
Tickler	175
Coils	25
Collector	201
Colpitts Oscillator	177
Compactron	92
Composition Resistor	18
Compression by Sound	119
Condenser (see Capacitor)	
Conductor	11
Cone, Speaker	121
Constant, Dielectric	36
Control Grid	81
Converter	164
Converter Tube	159
Core:	
Adjustable	69
Ferrous	62
Iron	27
Laminated	69
Non-Ferrous	62
Coulomb	13, 35
Counter-E.M.F.	49
Coupling	160
Coupling Capacitor	84
Co-valent Bond	198
Critical Coupling	160
Crossover	123
Crystal Detector	148

Current:	
Alternating	13
Carriers	198
Direct	13
Eddy	67
Flow	16
Leakage	41
Magnetizing	67
Plate	74
Saturation	76
Surge, Filament	111
Curve:	
Characteristic	95
Plate Family	95
R.F. Response	157
R.F. Transformer Bandwidth	160
Tetrode	88
Cycle	13

D

Damped Oscillation	173
D.C.	13
Decoupling Filter	116
Delayed A.V.C.	193
Demodulation	145
Detection	145
Detector:	
Crystal	148
Diode	149
Grid-Leak	150
History	153
Power	152
Vacuum-Tube	149
With A.V.C.	192
Detectors	146, 167
Dielectric	34
Dielectric Constant	36
Diode	76
Diode Detector	149
Diode, Vacuum Tube	72
Direct Current	13
Distortion, Audio	139
Distortion, Harmonic	141
Donor	198
Dry Electrolytic Capacitor	42
Dynamic Characteristics	97
Dynamic Speaker	120

E

Eddy-Current Losses	67
Electricity, Negative	11
Electricity, Positive	11
Electron	11, 16
Electron Distribution	33
Electron Speed	12
Electrolyte, Capacitor	41
Electrolytic Capacitor	41
Electrolytic Capacitor, Dry	42
Electromotive Force	12, 16
E.M.F.	12
E.M.F., Counter	49
Emission	74
Emission, Secondary	87
Emitter	201
Energy, Kinetic	73
Etched-Foil Capacitor	42

F

Fabricated-Plate Capacitor	42
Fading	190
Farad	35
Field:	
Coil	121
Coil Choke	109
Magnetic	24
Figure of Merit	59

Filament:	
Current Surge	111
Temperature of	79
Thoriated	79
Filaments	73
Filter:	
Capacitor-Input	105
Choke	30
Choke-Input	105
Decoupling	116
Smoothing	104
Flow, Current	16
Force, Electromotive	12, 16
Force, Lines of	26
Formula:	
Capacitive Reactance	51, 58
Figure of Merit	59
Inductive Reactance	52, 58
Q	59
Turns Ratio	132
Forward Bias	200
Frame, Speaker	121
Frequency:	
Beat	165
Image	169
Intermediate	159
Resonant	56
Full-Wave Rectifier	103

G

Gain, Voltage	99
Galena	148
Gassy Vacuum Tube	76
Germanium	198
Graphite	18
Grid:	
Bias	81
Control	81
Leak Detector	150
Screen	84
Suppressor	90
Ground Waves	188

H

Half-Wave Rectifier	102
Harmonic Distortion	141
Hartley Oscillator	176
Heat	21
Heater	73
Henry	29
Hole	198
Horizontal Polarization	182
Hybrid Auto-Radio	116
Hysteresis Losses	67

I

I.F. Transformer	158
Image Rejection	169
Impedance	46, 53
Impedance, Measuring Voice-Coil	127
Impedance, Voice-Coil	126
Induced E.M.F.	49
Inductance, Variable	61
Induction	24
Induction, Self-	27
Inductive Reactance	52
Inductor	25
Intermediate Frequency	159
Inverter, Phase	138
Ion, Negative	11
Ion, Positive	11
Ionosphere	190
Iron-Core	27
Iron, Soft-	26
Insulator	12
Intensity	16

J

Junction Transistor	201
---------------------------	-----

K

Kinetic Energy	73
Kirchhoff's Law	18

L

Lagging Phase	46
Law, Kirchhoff's	18
Law, Ohm's	16
Leading Phase	46
Leakage	37
Leakage Current	41
Left-Hand Rule	24
Line Cord Resistor	110
Lines of Force	26
Load Line	98
Loading of Coil	60
Loading of Tuned Circuit	60
Loop Antenna	183
Loopstick Antenna	183
Loss, I ² R	21
Losses, Eddy-Current	67
Losses, Hysteresis	67
Loudness	120
Loudspeaker	118

M

Magnetic:	
Field	24
Inertia	68
Pole	24
Magnetizing Current	67
Measurement, Resistance	216
Measurement, Voltage	215
Megohm	14
Meissner Oscillator	176
Mercury Vapor	80
Meter, Multi-	210
Meter Shunt	209
Mho	97
Mica Capacitor	40
Microfarad	35
Microhenry	29
Micromho	97
Micromicrofarad	35
Microphonic Vacuum Tube	77
Milliampere	14
Millihenry	29
Modulation	145
Mu	83, 95
Multimeters	210
Mutual Conductance	96

-N

Negative Electricity	11
Network, Crossover	123
Nichrome	19
Noisy Vacuum Tube	77
Nonsynchronous Vibrator	115
N-Type	198
Nucleus	11

O

Ohm	14, 16
Ohm's Law	16
Oil-Filled Capacitor	41
Oscillator:	
Armstrong	176
Colpitts	177
Hartley	176
Meissner	176
Tracking	177
Overloading	139
Oxide Film Capacitor	41

P

Padder Capacitor	178
Paper Capacitor	41
Peak Voltage	106
Pentode	90
Permanent Magnet	121
Phase	46
Phase Inversion	138
Phase Shift	48
Pitch	119
Plate:	
Current	74
Beam-Forming	90
Load	83
Resistance	95, 129
PM Speaker	121
Polarized Capacitors	43
Pole, Magnetic	24
Pole Piece	121
Positive Electricity	11
Positive Ion	11
Potentiometer	19
Power:	
Detector	152
Factor, Capacitor	37
Maximum Transfer of	129
Transformer	104
Power Supply:	
A.C.-D.C.	109
Auto-Radio	115
Nonsynchronous Vibrator	115
Synchronous Vibrator	115
Three-Way	113
Transformerless	110
Voltage-Doubler	114
Primary, Transformer	64
Printed-Circuits	207
Probe, R.F.	211
Push-Pull Amplifier	140

Q

Q of Coil	59
-----------------	----

R

Rarefactions, Sound	119
Reactance	46, 52
Reactance, Capacitive	51
Reactance, Inductive	52
Recombination	199
Rectifier:	
B-Supply	102
Full-Wave	103
Half-Wave	102
Semiconductor	113
Rectifiers	80
Resistance	14
Resistance Measurement	216
Resistance, Plate	95, 129
Resistor:	
Ballast	110
Carbon	18
Line Cord	110
Plate Load	83
Variable	19
Wirewound	19
Resistors	18
Resonance	56
Resonant Frequency	56
Reverse Bias	199
R.F.:	
Choke	30
Envelope	146
Probe	211
Response Curve	157
Signal	155
Rheostat	19
Right-hand Rule	24

Rule, Left Hand	24	Tube:	
Rule, Right-Hand	25	Converter	159, 164
S		Mixer	164
Saturation Current	76	Pentagrid Converter	170
Screen Grid	84	Remote-Cutoff	192
Secondary Emission	87	Tester	211
Secondary, Transformer	64	Triode-Hexode	171
Selectivity	155	Tuned Circuit:	
Selectivity, Better	156	Loading	60
Self-Induction	27	Parallel	55
Semiconductor Rectifier	113	Series	55, 156
Series-Tuned Circuit	156	Tracking	158
Shunt, Meter	209	Tuned Circuits	46
Signal:		Tuned Coil, Slug	62
Injection	217	Turns Ratio Formula	132
R.F.	155	Tweeter	123
Tracer	211	V	
Tracing	218	Vacuum Tube:	
Silicon	198	Beam	90
Silver Mica Capacitor	40	Characteristics of	94
Sky Wave	189	Compactron	92
Slug-Tuned Transformer	160	Defects	77
Smoothing Filter	104	Diode	72, 76
Soft-Iron	26	Gassy	76
Sound	118	Hybrid	92
Sound Wave	119	Microphonic	77
Space Charge	80	Noisy	77
Speaker	118	Plate Resistance	95
Speaker, Dynamic	120	Tester	211
Spider	121	Voltmeter	210
Superheterodyne	159	Weak	77
Suppressor Grid	90	Valve	83
Surge, Filament Current	111	Valve Action	146
Symbol, Transistor	203	Variable:	
Synchronous Vibrator	115	Capacitor	40
		Inductance	61
		Resistor	19
		Vertical Polarization	182
T		Vibrator:	
Table, Transfer of Power	129	Frequency	116
Talc	18	Nonsynchronous	115
Tetrode	79, 85	Synchronous	115
Tetrode Curve	88	Voice-Coil Impedance	126
Thoriated Filament	79	Volt	14
Thorium	79	Voltage:	
Tickler Coil	175	Amplifier	135
Tracer, Signal	211	Avalanche	199
Transconductance	96	Average	106
Transformer:		Bucking	28
Adjustable Core	69	Doubler-Supply	114
Air-Core	64	Gain	99
I.F.	158	Measurement	215
Laminated Core	69	Peak	106
Losses	67	Volume Control	19
Output	130	Volume Control, Automatic	191
Power	104	V.O.M.	208
Primary	64	V.T.V.M.	210
Secondary	64	W	
Slug-Tuned	160	Watts	21
Troubles	70	Wave:	
Universal Output	132	Ground	188
Transformerless Power Supply	110	Sky	189
Transistor:		Sound	119
Characteristics	204	Trap	61
Junction	201	Weak Vacuum Tube	77
Symbols	203	Wirewound Resistor	19
T.R.F. Amplifier	155	Woofer	123
Triode	79, 80		